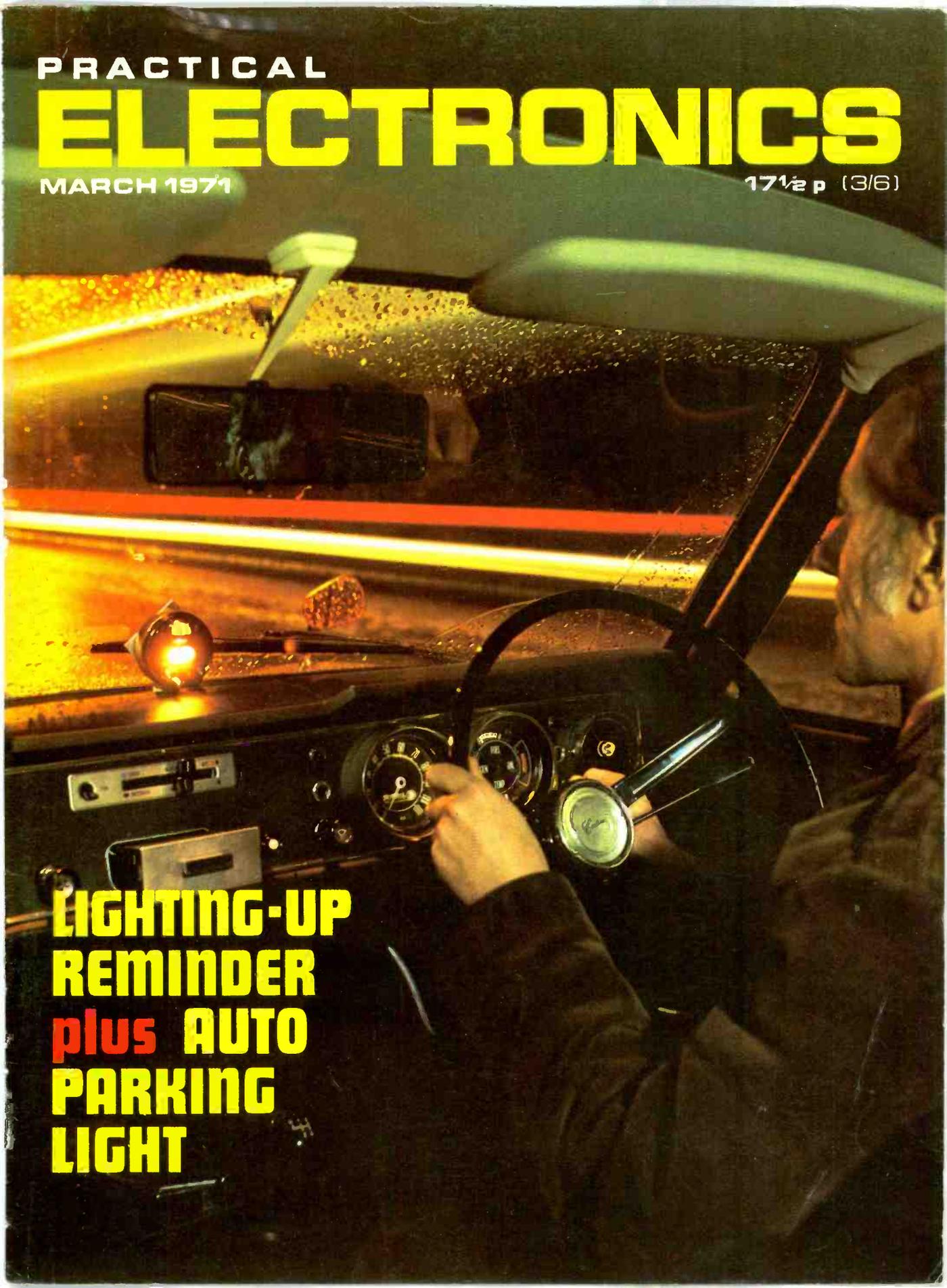


PRACTICAL

ELECTRONICS

MARCH 1971

17½ p (3/6)



**LIGHTING-UP
REMINDER
plus AUTO
PARKING
LIGHT**

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 1/4" — 3.2 mm CHISEL FACE

B 14 3/16" — 2.4 mm CHISEL FACE

B 24 1/8" — 4.75 mm SCREWDRIIVER FACE

B 12 1/8" — 4.75 mm EYELET BIT

B 58 1/4" — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL 1/4" — 4.75 mm CHISEL FACE

B 38 LL 1/4" — 3.2 mm CHISEL FACE

B 14 LL 3/16" — 2.4 mm CHISEL FACE

B 44 LL 1/4" — 4.75 mm SCREWDRIIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

* Write for price list and catalogue



ADCOLA PRODUCTS LTD.
(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21857

EX RENTAL TV's

17"
SLIMLINE
405 ONLY
£19-95

2 YEARS' GUARANTEE
FREE ILLUSTRATED
LIST OF TELEVISIONS
17"—19"—21"—23"

19"
SLIMLINE
405/625
BBC 2
£29-95



WIDE RANGE OF MODELS
DEMONSTRATIONS DAILY



CARR. INS.
£1-50

STEREO RECORD PLAYER CABINET

£5-97 1/2



Cloth covered. Two tone Blue/Black.
Size 14 1/2" x 24" x 8 1/2". P. & P. 53p.

TV TUBES REBUILT GUARANTEED 2 YEARS



14"—£3-95, 17" & 19"—£5-95, 21" & 23"—£6-45.
Exchanged Bowls. Carr. 53p.

PRESS BUTTON SWITCHING UNITS. 4 Banks 17p. 6 Banks 27p. P. & P. 5p.

TRANSISTORS 15p EACH. OC44, OC45, OC71, OC81, OC81D, AF114, AF117, AC128.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3

Stamp for Free List

PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

EXPERIMENTER'S PRINTED CIRCUIT KIT 50p


Postage & Pack. 10p (UK)

Commonwealth:

SURFACE MAIL 15p

AIR MAIL 50p

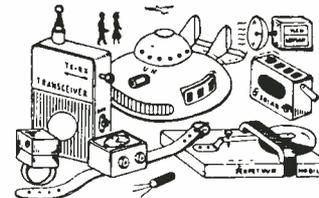Australia, New Zealand,
South Africa, Canada



(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Transmitter. "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

YORK ELECTRICS, Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

DISCOSOUND



DISCOSOUND 40 PRE-AMP

The Discosound 40 offers the same specification as the D.J. Disco Amp without the power output stage. Size 16in x 7in x 7in. Self powered and ideal for use with the Discosound 100 Power Amplifier below and one of the outstanding features is that it is capable of running ten of these Power Amplifiers (Total 1,000W).

PRICE £40.10.0 inc. P. & P.


DISCOSOUND 100 POWER AMPLIFIER



A 100W RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000Hz ±2dB. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound 40, or can be used with any other high quality pre-amp control unit. Completely built and tested on steel Chassis.

PRICE £49.10.0 inc. P. & P.

DJ70S INTEGRATED MIXER-AMPLIFIER

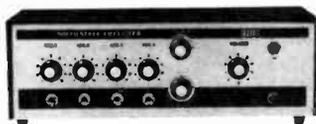

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70W R.M.S.) a frequency response (30-20,000Hz ±3dB) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs, etc., or anywhere that high quality high output is required. Size: 15½in x 5in x 6in.

PRICE £63.0.0 inc. P. & P.

Also available DJ105S 30W P.A. Amplifier. Similar specification to above.

PRICE £41.0.0 inc. P. & P.

For full details of these and all Discosound Products write direct to:

DISCOSOUND

122 BALLS POND ROAD, LONDON, N.1. Tel. 01-254 5779

Full money back guarantee if returned within 10 days


All Discosound Products are guaranteed for 12 months

Demonstrations given at any time



B.D.1. TURNTABLE KIT

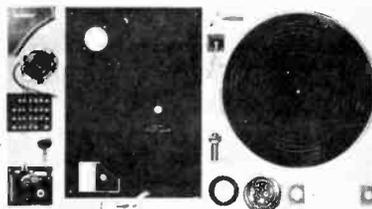The famous B.D.1. turntable which operates at 33½ or 45 r.p.m. incorporates a flexible belt drive system, virtually eliminating vibration and transmission noise — AND IS NOW AVAILABLE IN KIT FORM! So simple to construct — such a beautiful performance, and now it's so easy to own the best!



Rec. Retail Price **£13.28**


Price list and illustrated literature on request to

A. R. SUGDEN & CO. (Engineers) LTD.

Market Street, Brighouse HD6 1DX, Yorkshire.

Tel. 2142

BE AS DIM AS YOU LIKE!

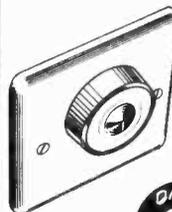

The 'TRIMLITE' Dimmer Switch puts the right amount of light on the subject.

- A fully insulated light control.
- Provides maximum safety and reliability.
- TV/Radio interference suppressed.
- Enhances television viewing.
- A must for children's rooms, entertaining.
- Save money and extend lamp life.
- Controls up to 300 watts of lighting.
- Replaces old switches using same two wires.

ONLY **69p**

inc. p. & p. in the U.K.

BREMAR ENGINEERING
QUEEN MARY'S AVENUE
WATFORD, HERTS. WD1 7JR


Be well-equipped

You need not worry about the painful and lingering minor burns that occur from time to time in leisure pursuits if you keep BURNZE close to hand. This unique new scientific aerosol cools and anaesthetizes. BURNZE takes the heat out of a burn in just 8 seconds, then controls the blistering and pain that steal skill from nimble fingers. Be well-equipped - buy BURNZE, from chemists.

Potter & Clarke Ltd Croydon
CR9 3LP



★ TRANSISTORISED FM TUNER ★

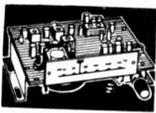

6 TRANSISTOR
HIGH QUALITY
TUNER, SIZE
ONLY 6 4/2in.
3 I.F. stages.
Double tuned filter-
eliminator. Ample
output to feed most
amplifiers. Operates
on 9V battery. Coverage 88-108 MHz. Ready
built ready for use. Fantastic value for
money. £8.97. P. & P. 121p.
Stereo multiplex adaptors £4.97.

AVO CT471A MULTIMETER

Battery operated fully transistorised.
Sensitivity 100mΩ/V. Measures AC/DC
Voltage 12mV to 1,200V. AC/DC Current
12uA to 1.2 Amp. Resistance 12 ohm to
120 mΩ HF, VHF, UHF. Voltage with
multiplier 4v to 400v up to 50 Mc/s, 40mV to
4V up to 1,000 Mc/s. Offered in perfect
condition. £55 each. Carr. 50p.

CRYSTAL CALIBRATORS No. 10

Small portable crystal
controlled wavemeter.
Size 7 1/2" x 4". Frequency
range 500 Kc/s to
10 Mc/s (up to 30 Mc/s
on harmonics). Calibrated
dial. Power requirements 300 V.D.C.
15mA and 12 V.D.C.
0.3A. Excellent condition.
£24.47. Carr. 371p.

TAPE CASSETTES

Top quality in plastic library boxes.
C60 60 min 421p 3 for £1.22.
C90 90 min 421p 3 for £1.80.
C120 120 min 751p 3 for £2.17.
Cassette Head Cleaner 56p. All Post extra.

AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality
precision instrument for
the industry by Airtec.
Frequency coverage
20-200 Mc/s. AM
C.W./P.M. Incorporates
precision dial, level meter, precision
attenuator 1/4V-100mV. Operation from
12V d.c. or 0/110/200/250V a.c. Size
12 8 1/2 in. Supplied in brand new
condition complete with all connectors
fully tested. £45. Carr. £1.

AVO CT.38 ELECTRONIC MULTIMETERS

High quality 97 range instrument which
measures a.c. and d.c. Voltages. Current,
Resistance and Power Output Ranges d.c.
volts 250mV-10,000V (10 meg Ω-110 meg Ω
input). D.c. current 10μA-25A. Ohms.
0-1,000 meg Ω a.c. volt 100mV-250V (with
R.F. measuring head up to 250MHz) a.c.
current 10μA-25A. Power output 500
watts-8 watts. Operation 0/110/200/250V a.c.
Supplied in perfect condition complete with
circuit lead and R.F. probe. £25. Carr. 75p.

ADMIRALTY 62B RECEIVERS

High quality 10 valve
receiver manufactured by
Murphy. Coverage in 5
bands 150-300 Kc/s; 560
Kc/s-1.5 Mc/s; 3.9-30.5
Kc/s. I.F. 500/KHz. In-
corporates 2 R.F. and 3 I.F.
stages, bandpass filter,
noise limiter, crystal con-
trolled B.F.O. calibrator
I.F. output, etc. Built-in speaker, output for
phones. Operation 150/230V a.c. Size
19 1/2 x 16in. Weight 114lb. Offered
in good working condition. £22.50. Carr.
£1-50. With circuit diagrams. Also available
B41 L.F. version of above. 15KHz-700Hz.
£17.50. Carr. £1-50.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low
cost economy oscillo-
scope for everyday use.
Y amp. Bandwidth
2 CPS-1 MHz. Input
imp. 2 meg Ω 25 P.F.
Illuminated scale. 2in.
tube. 115
230mm. Weight 8lb.
220/240 V a.c. Supplied
brand new with hand-
book. £22.50. Carr. 50p.

TO-3 PORTABLE OSCILLOSCOPE

3in tube. Y amp. Sensitivity
0.1V p-p/cm. Band-
width 1.5 cps-1.5MHz.
Input imp. 2 meg Ω 25P.F.
X amp. sensitivity 0.9V
p-p/cm. Bandwidth 1.5cps
-800KHz. Input imp. 2
meg Ω 20P.F. Time base
5 ranges 10 cps-300KHz.
Synchronization. Internal
external. Illuminated scale 140 x 215 x 390
mm. Weight 15 1/2lb 220/240V. A.C. Supplied
brand new with handbook. £37.50. Carr. 50p.

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT
DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN
STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!
CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100 100 x 80 mm		TYPE S-80 80 mm square fronts	
500μA	£3-12	50μA	£3-12
1mA	£2-97	50-0-50μA	£2-97
20V d.c.	£2-97	100μA	£2-97
50V d.c.	£2-97	100-0-100μA	£2-97
300V d.c.	£2-97	500μA	£2-62
1A d.c.	£2-97	1mA	£2-47
50-0-50μA	£3-37	20V d.c.	£2-47
100μA	£3-37	300V a.c.	£2-62
100-0-100μA	£2-25	50V d.c.	£2-47
		300V d.c.	£2-47
		VU Meter	£3-37

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in 4 1/2in fronts.		Type MR.38P. 1 21/32in square fronts.	
50μA	£2-60	150mA	£1-37
50-0-50μA	£2-10	200mA	£1-37
100μA	£2-10	300mA	£1-37
100-0-100μA	£2-10	500mA	£1-37
200μA	£2-75	750mA	£1-37
500μA	£2-75	1A	£1-37
500-0-500μA	£2-60	2A	£1-37
1mA	£2-60	5A	£1-37
1-0-1mA	£2-60	10A	£1-37
5mA	£2-60	30V d.c.	£2-10
10mA	£2-60	150V d.c.	£2-10
		300V d.c.	£2-10
		500V d.c.	£2-10
		150V a.c.	£2-10
		300V a.c.	£2-10
		500V a.c.	£2-10
		1A	£2-10
		10mA	£2-10
		20mA	£2-10
		50mA	£2-10
		100mA	£2-10
		500μA	£2-10
		50-0-50μA	£2-10
		100μA	£2-10
		100-0-100μA	£2-10
		200μA	£2-10
		500μA	£2-10
		500-0-500μA	£2-10
		1mA	£2-10
		10mA	£2-10
		20mA	£2-10
		50mA	£2-10
		100mA	£2-10
		500μA	£2-10
		50-0-50μA	£2-10
		100μA	£2-10
		100-0-100μA	£2-10
		200μA	£2-10
		500μA	£2-10
		500-0-500μA	£2-10
		1mA	£2-10
		10mA	£2-10
		20mA	£2-10
		50mA	£2-10
		100mA	£2-10
		500μA	£2-10
		50-0-50μA	£2-10
		100μA	£2-10
		100-0-100μA	£2-10
		200μA	£2-10
		500μA	£2-10
		500-0-500μA	£2-10
		1mA	£2-10
		10mA	£2-10
		20mA	£2-10
		50mA	£2-10
		100mA	£2-10
		500μA	£2-10
		50-0-50μA	£2-10
		100μA	£2-10
		100-0-100μA	£2-10
		200μA	£2-10
		500μA	£2-10
		500-0-500μA	£2-10
		1mA	£2-10
		10mA	£2-10
		20mA	£2-10
		50mA	£2-10
		100mA	£2-10
		500μA	£2-10
		50-0-50μA	£2-10
		100μA	£2-10
		100-0-100μA	£2-10
		200μA	£2-10
		500μA	£2-10

SEMI-CONDUCTORS/VALVES

BRAND NEW & FULLY GUARANTEED

TRANSISTORS

IN914	71p	AC125	25p	BBY38	20p
IN4001	71p	AC154	15p	BBY39	22p
IN4002	71p	AC176	25p	BBY61	32p
IN4003	10p	AC187	30p	BBY66	90p
IN4004	10p	AC188	30p	BBY95A	10p
IN4005	15p	AC177	30p	BY100	17p
IN4006	15p	AC178	25p	BY124	15p
IN4007	20p	ACY19	25p	BY126	15p
IN4148	71p	ACY20	22p	BY127	20p
IN5054	22p	ACY21	22p	BY210	40p
2G301	20p	ACY22	17p	BYZ11	35p
2G302	22p	ACY28	17p	BYZ12	30p
2G303	25p	ACY40	16p	BYZ43	25p
2G306	37p	AD140	50p	BY480	97p
2G308	37p	AD149	50p	MJ481	21p
2G309	30p	AD161	37p	MFF102	42p
2G371	32p	AD162	37p	MFF103	42p
2G374	37p	AF114	32p	MFF104	37p
2G381	25p	AF115	30p	MFF105	40p
2N696	17p	AF116	32p	NKT213	25p
2N697	17p	AF117	25p	NKT214	15p
2N698	42p	AF118	62p	NKT215	22p
2N706	15p	AF119	25p	NKT216	22p
2N708	15p	AF126	17p	NKT241	27p
2N914	22p	AF127	17p	NKT261	20p
2N916	22p	AF139	30p	NKT271	25p
2N918	37p	AF178	47p	NKT272	25p
2N929	37p	AF180	52p	NKT275	25p
2N930	37p	AF181	42p	NKT278	25p
2N1181	20p	AF185	40p	NKT281	27p
2N1182	30p	AF239	42p	NKT403	75p
2N1302	20p	ASy26	25p	NKT404	62p
2N1303	22p	ASy27	32p	NKT405	75p
2N1304	25p	ASy28	25p	NKT773	29p
2N1305	25p	ASy27	42p	NKT10439	37p
2N1306	25p	AYU10	97p	OA5	15p
2N1307	25p	BAy31	71p	OA10	25p
2N1308	25p	BC107	12p	OA47	10p
2N1309	25p	BC108	12p	OA70	10p
2N1313	25p	BC113	25p	OA79	10p
2N1888	32p	BC116	40p	OA81	10p
2N1893	32p	BC125	55p	OA85	12p
2N2147	75p	BC126	55p	OA90	10p
2N2160	62p	BC147	17p	OA91	71p
2N2193	47p	BC148	18p	OA95	71p
2N2217	27p	BC149	20p	OA200	71p
2N2218	30p	BC167	15p	OA202	10p
2N2219	30p	BC172	17p	OA210	17p
2N2368	17p	BC173	37p	OC19	37p
2N2369	20p	BC177	37p	OC20	97p
2N2369A	20p	BC186	37p	OC22	47p
2N2484	20p	BC182L	20p	OC23	50p
2N2613	35p	BC122L	22p	OC24	50p
2N2646	52p	BCY30	30p	OC25	50p
2N2647	52p	BCY31	30p	OC26	25p
2N2923	17p	BCY32	30p	OC28	62p
2N2924	17p	BCY33	30p	OC29	62p
2N2925	17p	BCY34	25p	OC35	50p
2N2926G	12p	BCY35	30p	OC36	62p
2N2926Y	12p	BCY42	15p	OC41	25p
2N2926L	12p	BCY43	20p	OC42	30p
2N3053	25p	BCY71	30p	OC44	17p
2N3054	50p	BCY72	17p	OC45	15p
2N3055	75p	BCZ11	37p	OC46	27p
2N3391A	30p	BD121	65p	OC70	12p
2N3416	37p	BD122	82p	OC71	25p
2N3670	17p	BD124	20p	OC72	25p
2N3702	87p	BF115	25p	OC73	30p
2N3703	15p	BF117	47p	OC74	30p
2N3704	17p	BF167	25p	OC75	25p
2N3705	15p	BF173	30p	OC76	25p
2N3706	25p	BF180	37p	OC77	40p
2N3707	15p	BF181	37p	OC81	25p
2N3709	17p	BF182	32p	OC81D	20p
2N3710	15p	BF184	25p	OC82	25p
2N3711	12p	BF185	25p	OC83	25p
2N3819	35p	BF194	17p	OC84	25p
2N3803	35p	BF195	15p	OC189	25p
2N3804	35p	BF200	37p	OC189	20p
2N3805	37p	BF224	30p	OC170	25p
2N3806	37p	BF225	30p	OC171	30p
2N4058	17p	BFX12	22p	OC200	37p
2N4059	25p	BFX13	22p	OC201	47p
2N4061	15p	BFX29	30p	OC202	37p
2N4062	22p	BFX30	32p	OC203	37p
2N4286	15p	BFX44	37p	OC204	40p
2N4287	17p	BFX45	37p	OC205	62p
2N4288	15p	BFX86	32p	OC207	75p
2N4289	17p	BFX87	32p	OC271	97p
2N4290	15p	BFX88	25p	OPF12	60p
2N4291	15p	BFY18	25p	ORP60	40p
2N4292	15p	BFY20	25p	F346A	25p
2N5354	27p	BFY30	22p	FL4091	15p
2N5355	27p	BFY31	22p	FL4092	15p
28102	25p	BFY52	22p	FL4002	15p
28103	37p	BFY90	67p	FL4004	17p
28104	37p	BSX19	17p	FL4005	10p
40250	50p	BSX20	17p	FL4006	20p
40361	50p	BSX21	17p	FL4007	20p
40362	50p	BSX76	15p	FL1843	40p
AC107	87p	BSY26	15p	FL1844	12p
AC126	25p	BSY27	80p	FL1845	17p
AC127	25p	BSY28	17p	FL1846	17p

THYRISTORS

PIV	50	100	200	300	350	400
1A	25p	27p	40p	45p	—	47p
3A	30p	37p	40p	45p	—	50p
5A	—	55p	65p	—	—	75p
7A	—	55p	65p	70p	—	87p
100A	—	—	—	—	22-50	22-75

VALVES

32p	2Z34	30p	EL95	35p	
32p	2Z5Z	42p	EM80	40p	
32p	2Z6Z	57p	EM81	42p	
1R4	30C15	75p	EM84	37p	
1R5	30C17	75p	EM85	55p	
1R6	30C18	75p	EM87	55p	
1R7	30F35	55p	EY31	40p	
1R4	30P11	77p	EY86	40p	
1R5	30FL12	92p	EY87	42p	
32p	30FL14	77p	EZ40	37p	
30Q4	30L15	85p	EZ41	45p	
35A	30L17	85p	EZ80	27p	
3V4	40P12	80p	EZ81	27p	
5R4	55P19	75p	EZ82	47p	
5U4	30P11	77p	EZ84	55p	
5Y4	40P13L	90p	KT86	11-37p	
5Y3	30P11A	85p	KT88	11-67p	
3Z4G	37p	3Z5L6	47p	MU14	40p
6/30L2	75p	6/3W4	25p	PCB80	40p
6AC7	20P324	25p	PC86	57p	
6AG7	37p	3Z3Z5	25p	PC88	65p
6AK5	50P5B5	35p	PC88	65p	
6AK6	57p	50C5	35p	PC97	42p
6AL5	16p	80	45p	PC900	47p
6AM6	22p	80A2	37p	PC84	35p
6AS6	30P12	47p	PC85	40p	
6AS6	30P125	80p	PC88	40p	
6AT6	25p	5783	65p	PC89	52p
6AU6	25p	6146	11-50	PCC189	55p
6AV6	32p	AZ31	35p	PCF80	32p
6BA6	22p	CY31	35p	PCF82	34p
6BE6	25p	DAF91	27p	PCF84	45p
6BF6	42p	DF96	30p	PCF85	55p
6BJ6	42p	DF91	32p	PCF800	75p
6BQ7A	37p	DF96	30p	PCF801	50p
6BR7	85p	DK91	35p	PCF802	50p
6BR8	65p	DK92	45p	PCF805	75p
6BW6	60p	DK96	45p	PCF806	65p
6BZ6	67p	DL92	35p	PCF807	77p
6C2	32p	DL94	40p	PCL82	35p
6C4	30p	DL96	37p	PCL83	60p
6C6	11-15	DM70	32p	PCL84	44p
6CL6	50p	DY86	32p	PCL85	47p
6CW4	62p	DY87	35p	PCL86	47p
6F1	62p	EB8C	62p	PL200	55p
6F8G	58p	EA42	75p	PL36	55p
6F13	35p	EABC80	32p	PL81	47p
6F14	60p	EA42	60p	PL82	45p
6F15	55p	EB91	16p	PL83	40p
6F18	40p	EB41	52p	PL84	30p
6F23	77p	EB8C1	32p	PL89	75p
6F26	47p	EB8C2	40p	PL90A	30p
6F34	47p	EBF83	42p	PY32	55p
6F35	20p	EBF89	32p	PY33	62p
6G5	60p	EBL21	60p	PY80	32p
6J6	17p	EC86	60p	PY81	30p
6K7	42p	EC88	60p	PY92	30p
6K8G	30p	ECX40	55p	PY93	30p
6L6GT	45p	ECX84	60p	PY88	40p
6LD20	32p	ECX85	27p	PY800	50p
6M7	37p	ECC88	40p	PY801	50p
6O4	60p	ECF80	35p	U25	75p
6O7	30p	ECF82	35p	U26	75p
6P8T	35p	ECF86	62p	U50	30p
6R7	40p	ECF91	57p	U52	30p
6R8L	30p	ECH35	60p	U191	70p
6R8T	27p	ECH42	65p	U281	40p
6S4	40p	ECH81	27p	U282	40p
6S4T	42p	ECH83	42p	U301	57p
6V6	25p	ECL80	45p	U801	41p
6X4	60p	ECL82	32p	UABC80	30p
6X5G	27p	ECL83	62p	UAF42	52p
6X5GT	27p	EF36A	42p	UBC41	47p
6X5GT	27p	EF37A	47p	UBC81	40p
6Y7	25p	EF39	40p	UBF80	35p
10C1	90p	EF40	60p	UBF89	35p
10P13	55p	EF41	62p	UC84	30p
10P14	42p	EF42	70p	UC85	30p
12A76	25p	EF80	25p	UCF80	52p
12A77	20p	EF85	35p	UCH21	55p
12A78	25p	EF86	32p	UCH42	65p
12A79	30p	EF89	27p	UCH81	32p
12AV6	30p	EF91	22p	UCL82	35p
12B46	32p	EF92	37p	UCL83	60p
12B68	32p	EF183	32p	UF40	50p
12B77	32p	EF184	35p	UF80	37p
19AQ5	32p	EH90	40p	UF85	40p
20D1	45p	EL34	52p	UF89	35p
20F2	75p	EL33	41p	UL41	80p
20L1	55p	EL41	55p	UL94	32p
20P1	50p	EL42	57p	UL95	30p
20P3	60p	EL81	50p	UY85	30p
20P4	11-EL84	25p	VR105/30	27p	
20P5	21-EL85	41p	—	—	
25L6	37p	EL91	25p	VR150/30	25p

ZENER DIODES

400W (3-3 to 33V)	15p
1-5W (2-4 to 200V)	20p
10W (3-8 to 100V)	25p

INTEGRATED CIRCUITS

L800	40p	L914	49p
LM32	62p	LM102	42p
LM103	42p	MC1303	30p
MC1302	42p	MC1304	42-75p
PA246	42-62p	CA3005	—
CA1271	CA3011	82p	—
CA3052	41-82p	FCH131	50p
FCH132	50p	FCH141	50p
FJH121	50p	FJH181	50p
FJH221	50p	FJH231	50p
FJH241	50p	FJH251	50p
FJJ121	87p	FJJ131	87p
FJJ211	FJJ211	11-2	

RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2µsec to 100µsec/cm. Supplied complete with all accessories and instructions. £87. Carr. paid.




MARCONI CT44/TF956 AF ABSORPTION WATTMETER

1 µwatt to 6 watts. £80. Carr. £1.


TE111 DECADE RESISTANCE ATTENUATOR

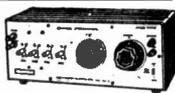Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600Ω range (0.1dB × 10) + (1dB × 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (1-3dB). Accuracy: ±0.5dB. ±indication dB: 0-0.1. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new £27.50. P. & P. 25p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

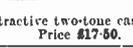Sine 18-200,000Hz; Square 18-20,000Hz. Output max +10dB (10kΩ). Operation internal batteries. Attractive two-tone case 7 1/4" x 5 1/2" x 2 1/2". Price £17.50. Carr. 17p.



Attractive two-tone case 7 1/4" x 5 1/2" x 2 1/2". Price £17.50. Carr. 17p.



TE-16A Transistorised Signal Generator. 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 51-51.31. Complete with instructions and leads. £7.97. P. & P. 20p.

BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max. +10dB (10kΩ). Operation 220/240V a.c. Size 215mm x 150mm x 120mm. Price £27.50. Carr. 25p.



T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: -0.1 / 0.03 / 0.1 / 0.3 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. ±0.5%. Complete with instructions. Supplied brand new complete with leads and instructions. Operation 230V a.c. £17.50. Carr. 25p.



TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.c. volts 1.5-1,500V. A.c. volts 1.5-1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional Probes available: R.F. £2.12; H.V. £2.50.



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

150W. £2.37. P. & P. 17p.
300W. £2.25. P. & P. 22p.
500W. £2.97. P. & P. 32p.
1,000W. £7.22. P. & P. 37p.
1,500W. £8.97. P. & P. 42p.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 220/240V a.c. Output continuously variable from 20V to 230V. Model MR2305 5A 6A x 46 x 43mm, £8.37. Model MR2310 10A 90 x 88 x 60mm, £11.97. Postage 12p.



MULTIMETERS for EVERY purpose!

TECH PT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA. d.c. 0/100K. £1.97. P. & P. 12p.

MODEL TE-500. 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50µA/250mA. 0/60K/6 meg. -20 to +62dB. £3.75. P. & P. 15p.

MODEL TE-70. 30,000 O.P.V. with overload protection, mirror scale 0/5/25/100/250/500/1,000V a.c. 0/10/50/250/500/1,000V d.c. 0/10/50/250/500µA/500mA. 12 amp. d.c. 0/60K/6 Meg./60 Meg. £3.71. Post paid.

MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/3/30/300mA. 0/16K/160K/1.6M/16 meg. £5.50. P. & P. 15p.

TMK MODEL TW-50K. 48 ranges, mirror scale. 50K/Volt d.c. 5K/Volt a.c. D.c. volts: 0-125, 0-25, 1-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2-5, 5, 25, 50, 250, 500mA. 5, 10A. Resistance: 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +81-dB. £8.87. P. & P. 17p.

TE-900 20,000 Ω/VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6in full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V a.c. 0/25/125/500/2500/10,000V d.c. 0/50µA/110/100/500mA/10A d.c. 0/2K/200K/20 meg. ohm. £15. P. & P. 25p.

MODEL 5025. 57 ranges, giant 5 1/2in meter, polarity reverse switch. Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.c. Volts: 0-125, 0-25, 1-25, 6, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2-5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 1K, 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +85dB. £12.50. P. & P. 17p.

MODEL TE12. 20,000 O.P.V. 0/0.6/30/120/600/1,200/3,000/6,000V d.c. 1/6/30/120/600/1,200V a.c. 0/60µA/6/60/600mA. 0/60K/600K/6meg/60. Megohm 50PF. 2 MF. £5.97. P. & P. 17p.

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and ICO, μ in or μ pp. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £6.97. P. & P. 15p.



"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality Low price Immediate delivery

MODEL S-260 General Purpose Bench Mounting

1A	£5.50
2.5A	£6.75
5A	£9.75
8A	£14.50
10A	£16.50
12A	£21.00
20A	£37.00

MODEL S-260 B Panel Mounting

1A	£5.50
2.5A	£6.62

Please add postage

ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS
Special discounts for quantity

HONOR TE.10A. 20kΩ/Volt 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 0/50µA/2-5mA 250mA d.c. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100 mfd. 0-100-0-1 mfd. £3.47. P. & P. 15p.

MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0/0.6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. -20 to +63dB. £5.97. P. & P. 15p.

MODEL TE 80. 20,000 O.P.V. 0/10/50/100/500/1,000V. a.c. 0/5/25/50/250/500/1,000V d.c. 0-5µA. 5/50/500mA./0/6K/60K/600K/6 Meg. £4.87. P. & P. 15p.

MODEL TE-90. 50,000 O.P.V. Mirror scale, overload protection. 003/13/60/300/600/1,200V d.c. 0/6/30/120/300/1,200V a.c. 0-0.3/0.6/600mA. d.c. 16K/160K/1.6/16 meg. -20 to +63dB. £7.50. P. & P. 15p.

TMK MODEL TW-200C. Features Resettable Overload Button. Sensitivity: 20KΩ/Volt d.c. 5KΩ/Volt a.c. D.c. volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 0-2.5, 10, 50, 250, 1,000V. D.c. currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K, 5 meg. Decibels: -20 to +82dB. £11.50. P. & P. 17p.

MODEL AB-100D. 100KΩ/Volt. 5in, mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10µA/6/60/300mA/12A. 0/2K/200K/2M/200M. -20 to +17dB. £12.50. P. & P. 17p.

TMK LAB TESTER. 100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 O.P.V. d.c. 5V/Volt a.c. D.c. volts: 0-5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 600, 1,000V. D.c. current: 10, 100µA, 10, 100, 600mA, 2-5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle. Size 7 1/4" x 6 1/2" x 3 1/2". £18.90. P. & P. 25p.

SKYWOOD SW-500

50 KΩ/Volt. Mirror scale DC Volts 0.6/3/12/30/300/600. AC Volts 3/30/300/600. DC Current 20µA/6/60/600mA. Resistance 10K/100 K/1Meg/10 Meg. Decibels -20 to +57dB £7.50. P. & P. 15p.

270° WIDE ANGLE 1mA METERS
MW1-6 60mm square £3.75. MW1-8 80mm square £4.97. P. & P. extra.



UNR-30 RECEIVER
4 Bands covering 560KHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £16.75. Carr. 37p.

W862 TRANSCEIVERS

Large quantity available for EXPORT! Excellent condition. Enquiries invited.



UR-1A SOLID STATE COMMUNICATION RECEIVER
4 Bands covering 55KHz-30MHz. FET, 8 Meter. Variable BFO for SSB. Built in Speaker, Bandspread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in 4 1/2in 7in. Brand new with instructions. £25. Carr. 37p.



LAFAYETTE HA-600 RECEIVER
General coverage 150-400KHz, 550KHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Bandspread, RF Gain. 15in 9 1/2in 8 1/2in 18in. 220/240V a.c. or 12V d.c. Brand new with instructions. £45. Carr. 50p.



LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER
3-3.4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54MHz. Dual conversion, 2 mech. filters, product detector, variable BFO, 8 Meter, 100KHz calibrator. 220/240V a.c. or 12V d.c. 15in x 9 1/2in x 8 1/2in. 18in. Brand new with instructions. £57.50. Carr. paid (100KHz Crystal £1.97 extra).

CLASS D WAVEMETERS

A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. £5.97. Carr. 37p. or brand new. £7.97. Carr. 37p.

FULL RANGE OF TRIO EQUIPMENT

VOLTAGE STABILISER TRANSFORMERS
180-260V input. Output 230V. Available 150W or 225W. £12.50. Carr. 25p.

EDDYSTONE VHF RECEIVERS MODEL 770R. 19-165 Mc/s. Excellent condition. £150.

INTERCOM/BABY SITTER

Transistorised Incams, ideal for home, office/workshop, etc. 2-way buzzer call system. For desk or wall mounting. Supplied complete with connecting wire, battery or brand new. £7.97. P. & P. 25p.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.97. P. & P. 17p.

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 Lisle Street, London, W.C.2 Tel: 01-437 8204
34 Lisle Street, London, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -
147, Church Street,
London, W.2
Tel: 01-262 6562
(Trade supplied)

COME AND JOIN US . . .

Why not join our team of enthusiastic staff? We need managerial and sales staff with a genuine interest in electronic components to help us run South East London's leading component stores.

We offer interesting work in a pleasant atmosphere with good opportunities of promotion in a rapidly expanding company.

Contact Mr. Hyde for further details.



OPEN DAILY
9.15 a.m. - 6 p.m.
(Closed all day
Thursday)


Garland Bros. Ltd.

TELEPHONE
01-692 4412

DEPTFORD BROADWAY (Corner of Brookmill Road)
LONDON, S.E.8

NEW! HANDY! TIDY! multi-drawer I-N-T-E-R-L-O-C-K-I-N-G storage units

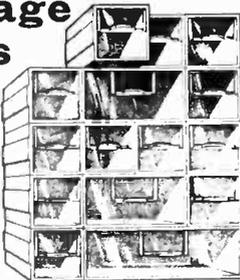A PLACE
FOR
EVERYTHING
EVERYTHING
IN ITS
PLACE!



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (5ins 2 1/2ins 2 1/2ins)
Usually 2 1/1 each, OUR PRICE: 37/- DOZEN
DOUBLE UNITS (5ins 4 1/2ins 2 1/2ins)
Usually 4 1/1 each, OUR PRICE: 45/- DOZEN

PLUS QUANTITY DISCOUNTS!

Order £5 and over DEDUCT 1/- in the £
Orders £10 and over DEDUCT 1/6 in the £
Orders £20 and over DEDUCT 2/- in the £

PACKING POSTAGE CARRIAGE: Add 6/- to all orders under £5. Orders £5 and over, packing postage carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID

IVORYET
LIMITED

(Dept. PE3) 31 ALBERT RD.
HENDON, LONDON, NW4

NEW BOOKS

101 EASY HAM RADIO PROJECTS

by Robert M. Brown and Tom Kneitel (Feb.) £1.50

ABC'S OF PETS

by Rufus P. Turner (Feb.) £1.25

NOVEL EXPERIMENTS WITH ELECTRICITY

by John Potter Shields (Feb.) £1.25

SHORT WAVE LISTENER'S GUIDE

by H. Charles Woodruff (Feb.) £1.30

CLOSED-CIRCUIT T.V. PRODUCTION TECHNIQUES

by Larry Goodwin and Thomas Koehring (Mar.) £2.00

RADIO RECEIVER SERVICING GUIDE

by Robert G. Middleton (Mar.) £1.90

ABC'S OF INFRARED

by Burton Bernard (Mar.) £1.40

COLLECTED BASIC CIRCUITS

by D. I. P. Stretton and A. W. Hartley (Mar.) £2.00

**FOULSHAM-SAMS
TECHNICAL BOOKS**
(W. FOULSHAM & CO. LTD.)
YEovil RD., SLOUGH, BUCKS, ENGLAND

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 45 - ; 11 element, 52 6; 14 element, 60 - ; 18 element, 70 - ; Wall Mounting with Cranked Arm, 7 element, 65 - ; 11 element, 75 - ; 14 element, 82 6; 18 element, 90 - ; Chimney Mounting Arrays Complete, 7 element, 80 - ; 11 element, 87 6; 14 element, 95 - ; 18 element, 105 - Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 18 yd. King Teleboosters - Labgear U.H.F. Boosters from 75 - ; Belling Lee "Concord" all Band V.H.F. U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8 - . Accessories 3 - . C.W.O. or C.O.D.

BBC · ITV · FM AERIALS



B.B.C. (Band D), Loft, 35 - ; Wall S.D. 32 6, "H" array, 60 - ; I.T.V. (Band 3), 5 element loft array, 45 - ; 7 element, 55 - ; Wall mounting 5 element, 65 - ; Combined BBC ITV loft 1 + 5, 55 - ; 1 + 7, 67 6; Wall mounting 1 + 5, 77 6; Chimney mounting 1 + 5, 90 - ; Pre-amps from 75 - ;

Combined BBC1 ITV BBC2 Aerials, 1 + 5 + 9, 80 - ; 1 + 5 + 14, 90 - ; 1 + 7 + 14, 100 - ; Available loft only.

F.M. Radio Loft S.D. 19 6, "H" 38 6, 3 element array, 57 6; Standard co-axial cable 1 - yd. Coax plugs, 1 8; Outlet boxes, 6 - ; Diplexer crossover boxes, 17 6; p.p. Aerials, 8 - ; accessories, 3 - ; C.W.O. or C.O.D. (min. C.O.D. charge 3 6) 1 - for fully illustrated Lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)
40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

LOW COST ELECTRONIC & SCIENTIFIC EQUIPMENT & COMPONENTS

MOTORS

HYSTERESIS REVERSIBLE MOTOR

Incorporating two coils. Each coil when energized will produce opposite rotation of output shaft. 120V 60Hz 1/10 r.p.m. When run on 50Hz it will give a speed of 1/12 r.p.m. Price £1.25. P. & P. free.

LOW TORQUE HYSTERESIS MOTOR MA23

Extremely quiet running motor with high starting torque. Has many uses such as chart drives, discotoneque colour wheels, etc. 1/20 r.p.m., 1/12 r.p.m., 1/10 r.p.m., 1/20V 50Hz, 1/12, 1/18, 1/24, 1/240 r.p.m. 1/20, 1/60, 1/16, 1/15, 1 r.p.m., 20 r.p.m. £1.50 post free.



HYSTERESIS CLUTCH MOTOR

With integral clutch allowing the motor to drop out of engagement with the gear train, thereby facilitating easy resetting when used in timers or in conjunction with a light spring. 6 oz torque at 240V 50Hz, 1/12 r.p.m., 1/10 r.p.m., 1/20 r.p.m., 1/12 r.p.m., 1/18 r.p.m., 1/24 r.p.m., 1/240 r.p.m., 1/20, 1/60, 1/16, 1/15, 1 r.p.m., 20 r.p.m. 24V 50Hz, 1/20 r.p.m., 1/12 r.p.m. £1.25 each. P. & P. 25p.

D.C. MOTORS

Similar to above type MD 83. 28V 1/20 r.p.m., 1/60 r.p.m., 1 r.p.m. 12V 1/20 r.p.m. 24V 1/15 r.p.m. 30V 1/12 r.p.m. £1.50. P. & P. 25p.

SYNCHRONOUS MOTORS

200/250V 50Hz. New condition, ex-equipment. 8.7 r.p.m. and 1 r.p.m. Self starting, complete with gearing shaft 1/2 in dia., 1/2 in long. £1.50.

ELECTRIC CLOCK MOTOR

NEW 200-250V, 50Hz, 2W. Synchronous induction motor. 3 revs. per hour. O/P shaft, 1/2 in dia., 1/2 in long. Clockwise rotation. Three-holed mounting at 120° on 2 in PCD. Price £1 post free.

SINGLE SPEED TAPE DECK



1/2 in tape, takes 7 in spools, 1 1/2 in per sec. 3 motors, facility for remote control operation. Record/replay heads with separate erase head plus fast erase facility. Ex-equipment. Less spools. Price £5.98. P. & P. 75p.

SOLENOIDS

High quality solidly constructed solenoids. Actuated by 24V 45Ω coil. Overall length 3 in x 1 in square with 1/2 in travel of the 1/2 in dia. shaft 43p. P. & P. 15p. 24V. 70 ohm. Armature 1/2 in movement. Lug type fitting. L. 1 1/2 in x 7/8 in x 1/2 in. Price 25p. P. & P. 15p.

MINIATURE UNISELECTORS

3 bank, 12 way, 250 or 1400 ohm, 24V models available. Type 2500A. Supplied complete with plug-in base. Size 3 in x 1 in x 2 in. A very neat precision component. Price £5.25. P. & P. 25p. 6 bank 25 way 50V 75 ohm. Make before break. Half Cycle type. 2 sets of wiper arms at 180°. Price £3.13 post free.



GOOD QUALITY INSTRUMENTS TAKEN IN PART EXCHANGE OR PURCHASED FOR CASH!

PORTABLE WHEATSTONE BRIDGE

Specification. Type: Moving Coil Galvanometer. Ranges: 1. 0.05 to 5 ohms. 2. 0.5 to 50 ohms. 3. 5 to 500 ohms. 4. 50 to 5,000 ohms. 5. 500 to 50,000 ohms. Scales: Switched. Slidewire: 0.5 to 50. Galvanometer Scale: 10-10-10. Case: Moulded plastic. Internal Source: 4V Dry battery. Dimensions: 200 x 110 x 65mm. Weight: 0.9kg. List price £25. Our price £9.99p.

AVOMETERS

These well-known portable test instruments have been overhauled and are offered complete with leads, crocodile clips and probes.



Model 10	£14
Model 40, 47A, 48A	£16
Model 7	£17
Model 7X	£19.50
Model 8	£28
Model 8X	£33
Model HR	£20

Model 48A complete with voltage multiplier for 480V and 3600V. Current shunts for 120A and 480A. A.C. Current transformer for 20A and 60A. In special wooden box. 47A and 48A are Admiralty patterns of the model 40. £16.75. P. & P. 75p.

RESET TIMERS — ACRO TIMER BY MAYDON


Synchronous motor driven timer providing manual adjusted delay. Delay time is set on graduated dial. Press button closes contact and drives motor which drives an arm until it actuates the load switch. The arm then returns to initial position for repeat action. Various ranges available. 230V 50Hz Load contacts 15A 230V. £5.

HIGH SPEED IMPULSE COUNTERS

by Davis, Wynn & Andrews. 4 in dial and pointer registers up to 100 and 4-digit counter both manually resettable. The drive to the counter is by an inverse escapement so that there is no loading of the pointer mechanism when digits are changed and adjustable pawls are unnecessary. Coil resistance 100 ohms for nominal volt operation, but the device works reliably from 20V at rates up to 10 impulses/sec. In circuit with a thyatron, or neontron, counting rates up to 100 impulses/sec are possible provided pulse width is restricted to keep mean current to 100mA. New, £6.88.



RIGHT ANGLED GEAR BOXES

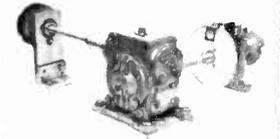

Gear boxes give a drive ratio of 2.5:1 at right angles to the input. Driveable through the 1/2 shaft only. Dimensions 4 in wide x 3 1/2 in deep x 4 1/2 in high. Robust construction in cast iron. Price £3.20. With pulley and ball race shaft mountings. Price £4.97. Carriage 75p.

WIDE RANGE OF PRECISION MULTI-TURN POTENTIOMETERS IN STOCK

TACHOMETERS

Portable and precision instruments by Smiths. Incorporating 4 mechanically selected ranges of 500, 1,000, 5,000 and 50,000 r.p.m. Within 2% accuracy, supplied with accessories and carrying case. A neat and compact instrument. Bargain at £19.50. P. & P. 25p.



AYO TRANSISTOR ANALYSER CT 446

A portable direct-reading instrument capable of giving accurate transistor measurements in the grounded emitter configuration. Battery power unit 1.5V to 10.5V in 5 steps. Base current 0-1mA, 1-40mA. Collector current 250 mA. Size: 15 1/2 x 9 1/2 x 5 in. Weight with batteries: 15 lb. Price £42.50. Carriage extra.

6 DIGIT ELECTRICAL IMPULSE COUNTER

New Type EM 101 24V Resettable £5
New P.O. Type 5 digit 330 Ohms £3.50
110V D.C. 4400 Ohms coil Ex-equip. £2.98
Packing and postage free.

VEEDER ROOT 6 DIGIT COUNTER

Suitable for counting all kinds of production runs, business machine operation. Mechanically driven. Reset type KA 1337, manual knob. Ex-equip. but new condition. Special price £1.25 plus 25p, P. & P.

3 DIGIT RESETTABLE COUNTER

Totalising 48V d.c. at 48mA: 10 impulses/sec. Length 4 in x 7 in x 1 in. Price £4 post free.

6 DIGIT RESETTABLE COUNTER

Totalising 240V 50Hz. Viewing window 2 in x 3 in. Ex-equipment. Price £2.76. P. & P. 25p.

6 DIGIT TOTALISING NON-RESETTABLE COUNTER

Mechanical operation. Chromium finish. Length 1 1/2 in x 3 in x 1 in with viewing window 3/4 in x 1 in. Ex-equipment. Price 48p. P. & P. 13p.

BERKELEY DECIMAL COUNTING UNIT 0-9

Direct reading octal base plug in unit electronic counter. The number counts received is indicated by one of ten neon lamps behind acetate panel. The unit counts from 0-9 the tenth pulse resetting to zero and simultaneously generating an o/p signal. Circuits can be connected in cascade. Power supply 6.3V d.c. Cut on/Cut off 15V. Price £3.50 p. & p. free.



MINIATURE DIGITAL DISPLAY

Operates on a rear projection 6.3V pilot lamp. Character size 2 in high, 0-9 digits with degree symbol, i.e. (4°). Dimensions 1 in wide, 3 in deep, 1 1/2 in high. List price 6 gns. Our price £2.73.



1 in characters £3.
4 in characters £9. Post free.

EAC DIGIVISOR Mk. II DIGITAL READ-OUT DISPLAY

Uses a sensitive moving coil movement to project digits 0-9 on to a viewing screen via an optical lens system. Image height 1/2 in. Lamp 6.3V. Sensitivity 250 micro-amp. Dimensions L. 4 1/2 in. W. 2 1/2 in. H. 1 1/2 in. Price £3.50. P. & P. 25p.



NEW SERIES M3 BY KGM DIGITAL INDICATORS

Provides selective viewing up to 10 character. Ideal where space is limited. Price £3.



BRAND NEW 4 Digit Counter with electrical reset

High quality counter operating from 12V D.C. 120mA at 10 impulses/sec. W. 1 1/2 in H. 2 1/2 in L. 4 in. Price £5.25. P. & P. free.

MINIATURE MOVING COIL RELAY 5115


By Sangamo Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance 310 micro amps. 315Ω. List price £4.50. Our price £1.15.

NUMICATORS

Fig. size 16mm. Coiled cathode gas filled in line 0-9 digital display tubes. Long life expectancy. Minimum striking voltage 180V. Side reading Type XX 7, XX 23 and XX 3 amber. Price £1.15. End reading GR 10 M/U clear £1.40 post free.

MEMORY CORE STORES

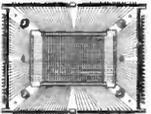42 x 52 2K bit ferrite core store complete with 84 OA10 load diodes. Ideal for building computer store or holding information in binary form. Price £2.75. P. & P. 38p.



MEMORY PLANES

Ferrite core memory planes with wired Ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Ideal for building computer store or holding information in binary form. Price £2.75. P. & P. 38p.

LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW

High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c./d.c. commutator motors fitted to portable electric hand drills. Fits standard 2 in conduit box. 240V, 50Hz, 400W. Price £2.99. P. & P. 13p.



RAPID HEAT SOURCE



from brand new Infra Red Tubular Quartz Lamps. Ideally suited as heat source for Drying Ovens, Egg Hatching, Incubators, etc., 240V, 1,440W, 20,000 Angstroms. Length 12 in x 3/4 in dia. Price 75p. P. & P. 25p.

STOCK CLEARANCE

All items are offered in "As is condition"
Oscilloscope Airtec 249 £10
Oscilloscope Airtec 723 £10
L.P. Osc. Dawes 400C £15
Crystal Calibrator Marconi TF 723A £15
Safety Ohmmeter Evershed and Vignoles £5
Bridge Oscillator Airtec 703 £5
L.F. Oscillator Furzehill G 420 £7.50
Valve Voltmeter Furzehill 378 B/2 1mV-100V. 5 ranges. £3.50 post free.
Creed Morse Receivers Model 7B. £15. Carr. £3.
New Highgrade Moving Coil AC/DC Voltmeters. 2 ranges 0-150 and 0-300V. 200 Ohms/V. 3/4 meter mirror scale in teak case. £10.50 post free.

ELECTRONIC BROKERS LTD.
(Dept. PE), 49-53 PANCRAS RD · LONDON NW1
01-837 7781 TELEX 267307
Open Mon.—Fri. 9—6 p.m.

STEPHENS

ELECTRONICS
P.O. BOX 26
AYLESBURY
BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded

The Diamond Tip is .007in radius, thus making it compatible to play stereo records on mono equipment without damage to the record; and of course full stereo.
BRITISH MADE
EXPORT ENQUIRIES WELCOME

CARTRIDGES

	Inc. P.T. each		Inc. P.T. each
ACOS GP79	63p	8X5M 8/8	£1-81
GP91-18c	£1-05	8X5H 8/8	£1-81
2-11	89p	8X5M D/8	£2
12-49	77p	8X5H D/8	£2
50-500	87p	X4N D/8	£1-36
GP91-28c	As above	GOLDRING	
GP91-35c	As above	850	£5-25
Suitable to replace TC8 etc.		8800	£7-35
GP92	£1-32	(8800E)	£15
GP93-1	£1-24	(8800 Super E)	£19-50
GP94-1	£1-55	RONETTE	
GP94-5	£1-80	105	8/8 99p
GP95	£1-24	106	8/8 99p
GP96	£1-57	DC400	8/8 70p
Acos 104 1-10	£2-09	DC4008C	8/8 70p
1-25	£1-99	105	D/8 £1-12
20-50	£1-91	106	D/8 £1-12
51-499	£1-77	DC400	D/8 84p
		DC4008C	D/8 84p
B.S.R.		SONOTONE	
X3M 8/8	£1-39	8TA	D/8 £1-25
X3H 8/8	£1-39	9TA	D/8 £1-79
X5M 8/8	£1-39	9TANC	D/8 £1-79
X5H 8/8	£1-39		

DE BANKS MAGNETIC RECORDING TAPES

POLYESTER				POLYESTER			
Length	Spool Size in.	Price		Length	Spool Size in.	Price	
Standard Play				Double Play			
600ft	5	50p	1200ft	5	85p		
850ft	5 1/2	63p	1800ft	7	£1		
1200ft	7	70p					
Long Play							
210ft	3	27p	1800ft	5	87p		
450ft	4	43p	2400ft	7	£1-30		

EMPTY TAPE REELS

3in	7p
5in	11p
5 1/2in	13p
7in	18p

CASSETTES

Boxed in Plastic Library Packs
C90 53p
C90 65p
C120 87p

P. & P. 7p on all orders.

STYLLI

ACOS	Sapphire	Diamond	ELAC	KST9	Sapphire	Diamond
GP59	13p	37p	(FE1B)	33p	47p	
GP65	13p	37p	ER5MB	33p	47p	
GP67	13p	37p	ER5MX	33p	47p	
GP73-1	33p	47p	ER5B	33p	47p	
GP73-2	33p	47p	ER60 Stereo	33p	47p	
GP79	13p	37p				
GP81-1	13p	37p	DECCA			
GP91-1	33p	47p	Deram diamond only	£1-39		
GP91-2	33p	47p	GARRARD			
GP91-3	33p	47p	EV25 Stereo	13p	37p	
GP91-18c	33p	47p	G82	13p	37p	
GP91-38c	33p	47p	G8	13p	37p	
GP94-1	33p	47p	GCE12	13p	37p	
GP95-1	33p	47p	GCS10/1	13p	37p	
GP96	33p	47p	GCS10/2	13p	37p	
HGP37	13p	37p	S1-2-3	33p	47p	
104	13p	37p	T81	33p	47p	
			T82	33p	47p	
			T83	33p	47p	
B.S.R.			GOLDRING			
BSR C1 (ST3)	33p	47p	CM50	13p	37p	
BSR TC8H	13p	37p	CM60	13p	37p	
BSR TC8M	13p	37p	MX1	13p	37p	
BSR ST5	33p	47p	MX2	13p	37p	
BSR ST9	33p	47p	Stereo C880	13p	37p	
BSR ST10	33p	47p				
BSR X1M	33p	47p	PERPETUUM EBNER			
BSR X1H	33p	47p	FE188	33p	47p	
BSR X3M	33p	47p	PHILIPS			
BSR X3H	33p	47p	AG3016	13p	37p	
BSR X5H	33p	47p	AG3063	13p	37p	
BSR X4H	33p	47p	AG3306	33p	47p	
			AG3100/3306	33p	47p	
			AG3400	13p	37p	
COLLARO			RONETTE BINOFLUID			
Collaro Studio			B40	13p	37p	
Collaro-Ronett			DC284	13p	37p	
TX88	13p	37p	SONOTONE			
Colliel SK1	13p	37p	2T	33p	47p	
Dual CDR2/CD83	33p	47p	3T	33p	47p	
(DN2)	33p	47p	8TA4	33p	47p	
Dual CDR3/390	33p	47p	9TA	33p	47p	
(D3)	33p	47p	9TA/11C	33p	47p	
ELAC KST9	33p	47p	19T	33p	47p	
(PE10)	33p	47p	20T	13p	37p	

SEMICONDUCTORS · BRAND NEW · MANUFACTURERS' MARKINGS · NO REMARKED DEVICES

2N3684	62p	2N2613	35p	2N3708	17p	2N5287	£2-62	AC128	80p	BC115	32p	BD132	97p	BFY41	50p	GET113	20p	NKT249	20p	OC20	75p
2N404	22p	2N2614	30p	2N3709	17p	2N5305	37p	AC154	22p	BC116	32p	BDY11	£1-37	BFY50	62p	GET118	20p	NKT243	62p	OC22	50p
2N696	20p	2N2646	57p	2N3710	20p	2N5306	40p	AC176	85p	BC116A	37p	BDY17	£1-87	BFY51	22p	GET119	20p	NKT244	17p	OC23	50p
2N697	20p	2N2696	32p	2N3711	20p	2N5307	37p	AC187	62p	BC117	39p	BDY18	£2-47	BFY52	22p	GET120	52p	NKT261	20p	OC25	57p
2N698	20p	2N2711	30p	2N3713	£1-50	2N5308	37p	AC188	37p	BC118	38p	BDY19	£3-12	BFY53	22p	GET873	12p	NKT264	30p	OC26	32p
2N699	62p	2N2712	30p	2N3714	£1-75	2N5309	62p	ACV17	27p	BC121	20p	BDY20	£1-52	BFY56A	57p	GET880	30p	NKT271	20p	OC28	62p
2N706	12p	2N2713	30p	2N3819	35p	2N5310	42p	ACV18	25p	BC125	55p	BDY38	97p	BFY73	30p	GET887	20p	NKT272	20p	OC29	75p
2N708	15p	2N2714	30p	2N3823	£1-12	2N5354	27p	ACV19	25p	BC126	65p	BDY60	£1-80	BFY76	42p	GET889	22p	NKT274	20p	OC33	40p
2N708	15p	2N2865	62p	2N3826	30p	2N5355	27p	ACV20	25p	BC134	57p	BDY61	£1-80	BFY77	57p	GET890	22p	NKT275	20p	OC36	62p
2N719	62p	2N2904	35p	2N3854	27p	2N5356	32p	ACV21	25p	BC134	57p	BDY62	£1-37	BFY90	67p	GET896	22p	NKT281	20p	OC41	25p
2N718	25p	2N2904A	40p	2N3854	27p	2N5356	32p	ACV22	20p	BC140	37p	BFY15	25p	BFY98	27p	GET897	22p	NKT401	87p	OC42	25p
2N718A	30p	2N2906	40p	2N3855	27p	2N5356	32p	ACV28	20p	BC147	17p	BFY17	47p	BFY99	25p	GET898	22p	NKT402	80p	OC44	20p
2N728	30p	2N2906A	45p	2N3855A	30p	2N5357	37p	ACV40	20p	BC148	15p	BFY17	47p	BFW59	25p	MAT100	30p	NKT403	75p	OC45	12p
2N727	30p	2N2906	40p	2N3856	30p	2N5357	37p	ACV41	25p	BC149	15p	BFY18	25p	BFX23	£1-35	MAT101	30p	NKT404	62p	OC46	15p
2N914	17p	2N2906A	32p	2N3856A	35p	2N5357	37p	ACV42	40p	BC157	50p	BFY19	32p	BFX29	£1-80	MAT120	30p	NKT405	62p	OC70	15p
2N916	17p	2N2907	40p	2N3858	25p	2N5358	37p	AD140	40p	BC158	17p	BFY20	£1-80	BFY20	£1-80	MAT121	30p	NKT406	62p	OC71	15p
2N918	30p	2N2923	40p	2N3858A	25p	2N5358	37p	AD149	57p	BC158	17p	BFY21	£1-80	BFY21	£1-80	MAT122	30p	NKT407	62p	OC72	12p
2N929	22p	2N2924	17p	2N3859	27p	2N5359	37p	AD150	62p	BC159	20p	BFY22	£1-80	BFY22	£1-80	MAT123	30p	NKT408	62p	OC73	12p
2N930	27p	2N2925	17p	2N3859A	27p	2N5359	37p	AD161	37p	BC160	62p	BFY23	£1-80	BFY23	£1-80	MAT124	30p	NKT409	62p	OC74	32p
2N987	52p	2N2926	17p	2N3860	30p	2N5359	37p	AD162	37p	BC161	62p	BFY24	£1-80	BFY24	£1-80	MAT125	30p	NKT410	62p	OC75	22p
2N1131	27p	Green	14p	2N3861	30p	2N5360	37p	AD163	37p	BC162	17p	BFY25	£1-80	BFY25	£1-80	MAT126	30p	NKT411	62p	OC76	22p
2N1132	27p	Yellow	12p	2N3862	£1-50	2N5361	37p	AD164	25p	BC163	14p	BFY26	£1-80	BFY26	£1-80	MAT127	30p	NKT412	62p	OC77	22p
2N1302	17p	Orange	12p	2N3863	£1-50	2N5362	37p	AD165	25p	BC164	14p	BFY27	£1-80	BFY27	£1-80	MAT128	30p	NKT413	62p	OC78	25p
2N1303	17p	Green	12p	2N3864	30p	2N5363	37p	AD166	25p	BC165	14p	BFY28	£1-80	BFY28	£1-80	MAT129	30p	NKT414	62p	OC79	25p
2N1303	17p	Orange	12p	2N3865	30p	2N5364	37p	AD167	25p	BC166	14p	BFY29	£1-80	BFY29	£1-80	MAT130	30p	NKT415	62p	OC80	25p
2N1303	17p	Orange	12p	2N3866	30p	2N5365	37p	AD168	25p	BC167	14p	BFY30	£1-80	BFY30	£1-80	MAT131	30p	NKT416	62p	OC81	25p
2N1303	17p	Orange	12p	2N3867	30p	2N5366	37p	AD169	25p	BC168	14p	BFY31	£1-80	BFY31	£1-80	MAT132	30p	NKT417	62p	OC82	25p
2N1303	17p	Orange	12p	2N3868	30p	2N5367	37p	AD170	25p	BC169	14p	BFY32	£1-80	BFY32	£1-80	MAT133	30p	NKT418	62p	OC83	25p
2N1303	17p	Orange	12p	2N3869	30p	2N5368	37p	AD171	25p	BC170	14p	BFY33	£1-80	BFY33	£1-80	MAT134	30p	NKT419	62p	OC84	25p
2N1303	17p	Orange	12p	2N3870	30p	2N5369	37p	AD172	25p												

Take your Wellerchoice* in Soldering




Low Initial Cost *

Low initial cost Marksman irons, to cover most soldering needs. Screw-in tips on 15W and 25W make it easier to change the tips, which are nickel-plated and factory pre-tinned for longer life. The shanks are stainless steel to concentrate heat at the tips.

Instant Heat for Rapid Soldering *

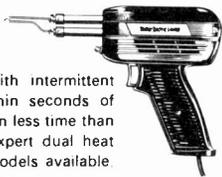Instant heat soldering guns to deal with intermittent soldering. Working heat is reached within seconds of pressing the trigger, so the job is finished in less time than it takes for a normal iron to heat up. Expert dual heat (100/140W) and Heavy Duty (275W) models available. Alternative tips available for plastics working.



Weller Electric Limited

Redkirk Way, Horsham, Sussex Tel: 0403 61747

NOW AVAILABLE LASKY'S AUDIO TRONICS CATALOGUE 1971

THERE'S MORE &
MORE & MORE
FOR EVERYONE!

The great new 1971 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiasts, Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio accessories, and introduces LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.
LASKY'S RADIO LTD. (Dept. PE)
3-15 Cavell Street, London E1 2BN



Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "OPPORTUNITIES IN TELECOMMUNICATIONS/TV AND RADIO". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.

FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 371B, ALDERMASTON COURT, READING RG7 4PF



POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. 371B, Aldermaston Court, Reading RG7 4PF
Please send books and full information — free and without obligation.



NAME..... AGE.....

ADDRESS.....

OCCUPATION.....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Litesold

SOLDERING INSTRUMENTS



- SIX SIZES—10 WATTS TO 60 WATTS
- EXCELLENT THERMAL STABILITY
- STRONG, LIGHTWEIGHT, COMFORTABLY ELEGANT DESIGN
- UNEQUALLED PERFORMANCE
- PUSH-IN BITS, COPPER OR LONG-LIFE
- INDICATOR LAMPS OPTIONAL ON ALL MODELS
- ALL VOLTAGES
- EASY MAINTENANCE

PLEASE ASK FOR NEW LEAFLETS 37/1001/3

LIGHT SOLDERING DEVELOPMENTS LTD

28 Sydenham Road, Croydon CR9 2LL
Telephone 01-688 8589 & 4559



Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)

Transistors, etc. AC126 18p; AF110 15p, AF116 15p, AF117 20p, OA5 71p, OA81 71p, OA85 71p, OC23 22p, OC25 30p, OC28 27p, OC28 42p, OC33 42p, OC44 14p, OC45 15p, OC71 12p, OC72 12p, OC75 12p, OC81 12p, OC81D 12p, OC82D 12p, OC170 20p, OC171 12p. Many more in list. **Diodes, etc.** BY100 800piv 14p, 4 Amp series 2123 300piv 20p, BY212 600piv 25p, BY211 900piv 30p, BY210 1200piv 25p. (Charges 61p up to 11, paid for 12 and over.) **Sub-Min. Transformers:** OUTPUT 3Ω for OC72, etc. 14p, (1p to 6 1/2p). **MULTIMETER.** Our famous 20000 Ω per V 44-621 (15p). Details and other in list. **SOLDERING IRON.** Slim, modern, British high-speed 81", all parts replaceable, highest quality, full guarantee: 41-071 (10p). **DIAMOND STYLII** Replacements for IBS TC40LP, TC58, TC81P/STEREO; COLLARO 01; RONETTE HP40LP; GARRARD GC2LP and GC2LP; ACOS 8, ACOS 8 GP85/87, all at 40p. **AC/DC:** BSR 8T4 (8T3, 8T5), 8T8 (8T9); SONOTONE 8TA, 8TA, 8TAHC; PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304); Garrard GK825 all at 75p (6p). All are of the very highest quality. **Double Diamond:** 8T4 (8T3, 8T5); 8T10 (8T9, 8T8); 9TA, 9TAHC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP918C for all GP91-8C cartridges: All at £1.50 (6p). **PICK-UP CARTRIDGES** All standard fittings and stylus. MONO (GP672 75p STEREO-COMPATIBLE (MONO) (GP918C £1.00). STEREO GP93 41-271. STEREO CERAMIC GP94 41-921. MONOTONE STEREO 8TAHC (DIA.) 42-271. **GOLDRING** GR50 44-871. GR60 42-50. GR80E 413-50. GR80 SUPER E 419-50 (61p all types or Reg. Post 22p). **STYLII FOR ALL ABOVE TYPES**, including GOLDRING available. **RECORDING TAPE.** Still the finest quality Mylar available: Standard 5" 600 ft. 26p 5" 900 ft. 50p 7" 1200 ft. 66p. **LONG PLAY** 5" 900 ft. 50p 5" 1200 ft. 56p 7" 1800 ft. 90p (71p on 5" and 3 1/2" 9p on 7"). **MICROPHONES** Crystal Mic 91, hand/desk 81p, MC45 Curved metal handgrip 41, CM21 Grey hand/desk 62p, Btick 60" 41-021; CM70 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands 41-47; (All 6p LAPEL (or hand) with clip 32p (6p). All are fitted with base and slide-out Cream hand/table MINY 77p (9p) MS10, 50K Ω for desk, tapered with base and slide-out adaptor 41-971; MS11, Similar, but fixed on swivel swan neck to switch-fitted base 22-22; (Either 16p). Type 209 Cardioid ball, 50K/800 Ω, omni-dir., built-in vol. control, on/off switch, special lead, handle (as good as money can buy) 22-30, DM160, Non-Dir. Ball, 50K Ω, switch, cable, adaptor 22-871 (27p) either). **MICROPHONE INSERTS.** Dia. 1/8" x 3", 8 or 15 Ω (state which) 22-121 (25p) with single flared para. tweeter cone 8 or 15 Ω (state which) 22-75 (25p); with two tweeters and crossover network 8 or 15 Ω (state which) 22-75 (25p). **VIBRATORS.** Genuine Plessey 12V 4-pin non-synch. 121HD4, 2 1/2" ex. pins 27p. Am. 12V 4-pin, non-synch. 7/16th, longer, 22p 12V 7-pin Synch. (128R7) 62p (all types 61p per vibrator). **CONNECTING WIRE.** Packs of 5 coils asept. coils. ea. coil 5yds. Solid core 14p (6p). Flexible 16p (71p). Super thin for transistor wiring 16p (6p). **PICK-UP WIRE.** Super thin twin flex. screened and sheathed 6p yd. (6p up to 6yds. over, free). **RETRACTABLE Flex. Leads.** (Curlies) 6ft. phono plug ea. end 22p. 12ft. 35p. 6ft. phono plug/phono socket other end 25p. 42p (6p per lead, all types). **SEND S.A.E.** for full free lists—Teleton and small 3W and 7W trans. amplifiers, Electrolytics, Vol. Controls, all types of radio switches, car and portable expanding aeriads, Meters, Test prods, all types of Brit. & Cont. standard and min. plugs and sockets, SDR's, Thyristors, croc. clips (various), terminals, etc. etc. and many "Special Offer" lines at lowest possible prices.

FELSTEAD ELECTRONICS (PES02)
LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE
Cash with order only. No C.O.D. or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p unacceptable, excluding postage. S.A.E. please for enquiries or cannot be replied to. Changes apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

Send 5p for New Comprehensive I.C. and Semiconductor price list (24 pages)

INTEGRATED CIRCUITS

NEW LOW PRICES • FULLY GUARANTEED

BCA	5p	MOTOROLA	1-9	10+	25+	MULLARD	5p	
CA3000	1.40	MC708G	0.91	—	0.95	L16EAR	1.62	
3005	1.80	MC724P	0.66	—	0.55	TA1241	4.95	
7	2.65	MC788P	0.82	—	0.69	243	1.50	
11	0.75	MC789P	0.66	—	0.55	263	0.77	
12	1.05	MC790P	1.24	—	1.03	293	0.97	
13	1.25	MC792P	0.66	—	0.55	300	1.75	
18	0.85	MC799P	0.66	—	0.55	310	1.25	
18A	1.10	MC1303L	2.70	—	2.28	320	0.72	
19	0.85	MC1304P	3.60	—	3.00	330	1.75	
20	1.30	MC838P	5.49	—	4.67	435	1.47	
20A	1.60	MC1552G	4.61	—	3.84	321	1.83	
21	1.60	MC1435L	3.45	—	2.87	322	3.60	
22	1.30	MC1709QC	0.95	—	0.82	330	4.95	
23	1.10	Data sheets	0.12	extra	—	811	4.45	
26	1.00					TAB101	0.97	
28A	0.75	FAIRCHILD				TAD100	1.97	
28B	1.05	1-5	6-11	12+	50+	TAD110	1.97	
29	0.90	5p	5p	5p	5p	MULLARD DTL	5p	
29A	1.65	L900	0.42	0.40	0.37	FCH101	0.77	
30	1.40	L914	0.42	0.40	0.37	FCH121	1.05	
33	1.25	L923	0.62	0.50	0.55	FCH201	1.32	
36	0.75	702C	1.12	1.06	0.97	FCH231	1.50	
39	0.85	709C	0.75	0.67	0.65	FCJ101	1.62	
41	1.10	710C	0.75	0.67	0.65	FCJ111	1.50	
42	1.10	713C	0.75	0.67	0.65	FCJ201	1.62	
43	1.40	716C	2.90	2.50	—	FCJ211	2.75	
44	1.20	741C	0.97	0.92	0.85	0.75	FCJ101	4.87
45	1.25	N.B. 709C and 741C TO-5 or DIL. package				FCY101	1.05	
46	0.75	TEXAS TTL				MULLARD TTL	5p	
47	1.40	5p				FJH101	0.87	
48	2.05	SN7400N	0.50	FJH121	0.87	FJH121	0.87	
49	1.60	SN7401N	0.50	FJH141	0.87	FJH141	0.87	
50	1.85	SN7402N	0.50	FJH161	0.87	FJH161	0.87	
51	1.25	SN7403N	0.50	FJH171	0.91	FJH171	0.91	
52	1.65	SN7404N	0.50	FJH221	0.87	FJH221	0.87	
53	0.50	SN7405N	0.50	FJH101	1.87	FJH101	1.87	
54	1.10	SN7410N	0.50	FJH121	1.87	FJH121	1.87	
55	2.40	SN7413N	0.50	FJH141	3.12	FJH141	3.12	
59	1.65	SN7420N	0.50	FJH191	1.87	FJH191	1.87	
64	1.20	SN7441N	2.02	FJH211	1.87	FJH211	1.87	
		SN7480N	1.97	FJH211	3.12	FJH211	3.12	
		SN72709N	0.87	FJY101	0.80	FJY101	0.80	

Post & Packing 10p per order.
TELEPHONE 01-452 0161 A. MARSHALL & SONS LTD. TELEX 21422
28 CRICKWOOD BROADWAY, LONDON, N.W.2
CALLERS WELCOME 9-5.30 SATURDAY 9-5
SEE OUR MAIN ADVERTISEMENT ON PAGE 258 FOR SEMICONDUCTORS

Send for your copy of the **HEATHKIT** 1971 CATALOGUEit's **FREE** on request




MARINE




SPEAKERS


HI-FI & AUDIO

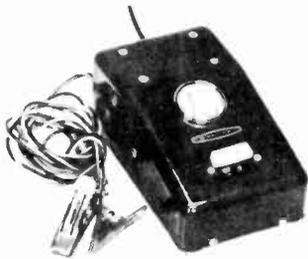

CONSUMER

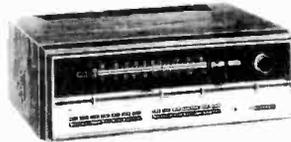

SHORTWAVE

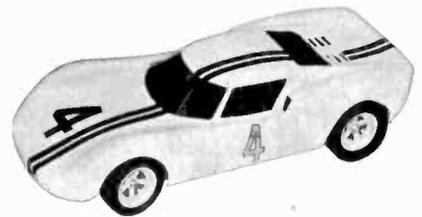

R/C MODELS

Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.
- ★ Save up to 50% over factory built equipment.
- ★ Money saving direct from factory prices.



A Schlumberger Company

HEATH (Gloucester) LTD., GLOUCESTER GL2 6EE

Many other models in wide range

(BLOCK CAPITALS PLEASE)

**FILL IN THE COUPON
FOR YOUR FREE
CATALOGUE TODAY**

Name

Address

Post Code

25/3A/71

Lasky's

Astrad ORION

THE WORLD'S SMALLEST TWO WAVEBAND, 6 TRANSISTOR RADIO

Music, news, sport, wherever you are. 7-day money back guarantee if you are not absolutely delighted with the results. Make no mistake, this is a real radio, not a toy or crystal set! Fully built and tested, ready for immediate use. NO EXTRAS. This minute radio will play anywhere—any time, beach, garden, park, home, office, school, etc. The super sensitive 6 transistor circuit is fully tunable over both long and medium wavebands, with built-in ferrite rod aerial to provide excellent selection.



The Orion operates from one tiny battery, either mercury or nickel cadmium, for long life and economical running cost. The output is via a crystal-type personal earphone, giving extreme clarity, which prevents disturbing other people when used in public parks, open spaces, etc. The small size of the Orion allows it to be carried easily in the pocket or handbag, and it is also supplied with an attractive presentation case. Complete with earpiece, battery and carrying case.

Specification. Waveband coverage: Medium 525kc/s to 1,605kc/s; Long 150kc/s to 308kc/s. Sensitivity: 35mV/m max. Selectivity (at -30kc/s detuning) -10dB. Power consumption: 4mA max. Power source: 1 1.4V Mercury battery. Mallory type RM625 or equivalent. Mallory battery is not rechargeable.

COMPLETE WITH EARPIECE ONLY RECHARGEABLE BATTERY POST POCKET CARRYING CASE £1.48 18p

*Spare rechargeable battery 18p extra—post FREE with radio.

BARGAIN PACKAGE COMPRISING—1 ORION RADIO 1 RECHARGEABLE BATTERY AND BATTERY CHARGER £2 20p

BATTERY CHARGER

THE BATTERY WE SUPPLY WITH THE ORION IS A RECHARGEABLE TYPE. BATTERY CHARGERS ARE AVAILABLE TO RECHARGE THE BATTERY AGAIN AND AGAIN. OPERATES ON HOME MAINS 200/240 VOLTS A.C.

Battery life is approx. 10 hours. Charging time: 10 hours. A spare battery will enable you to keep your Orion constantly in use.

LASKY'S PRICE 85p Post Free with Radio

EXCLUSIVE TMI & TM5

MODEL TM-1 MINI-TESTER

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to $\pm 3\%$ of full scale. Click stop, range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green figuring. Ohms zero.

- DC/V: 0-10-50-250-1,000 at 1K/OPV.
- AC/V: 0-10-50-250-1,000 at 1K/OPV.
- DC CURRENT: 0-1mA, 100mA.
- Resistance: 0-150k Ω .
- Decibels: -10dB to +22dB.
- Complete with test leads, battery and instructions.




Size Only 3 1/2in. x 2 1/2in. x 1 1/2in.

LASKY'S PRICE £1.95 POST 13p MODEL TM-5 EX OHMS/V POCKET MULTIMETER

Another new look pocket multimeter from Lasky's providing top quality and value. The "slimline" impact resistant case—size 4 1/2in x 2 1/2in x 1 1/2in, fitted with extra large 3 1/2in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

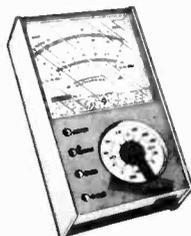- DC/V: 3-15-150-300-1,200 at 5K/OPV.
- AC/V: 6-30-300-600 at 2.5K/OPV.
- DC Current: 0-330 μ A, 0-300mA.
- Resistance: 0-10k Ω , 0-1M Ω .
- Decibels: -10dB to +16dB.
- Complete with test leads, battery and instructions.



LASKY'S PRICE £2.95 POST 13p

MP.60

High-precision low-mass fully counter-balanced pick-up arm, heavy balanced turntable, simply operated controls, viscous cueing device, slide in cartridge carrier, four pole motor.

McDONALD

McDONALD PROFESSIONAL SERIES FOUR SPEED SINGLE PLAY UNIT



POST 35p

LASKY'S PRICE £11.50

complete with plinth and cover **£15.00 POST 40p**

610 AUTOMATIC TURNTABLE

Same specifications as the MP.60 but with synchronous four pole motor and full automatic change facilities.

LASKY'S PRICE £13.95 POST 35p WITH PLINTH AND COVER £17.75 POST 40p

510 AUTOMATIC TURNTABLE

Counter balanced pick-up arm, pressed steel turntable, bias compensator, viscous cueing and synchronous four pole motor.

LASKY'S PRICE £11.75 POST 35p WITH PLINTH AND COVER £15.50 POST 40p

310 AUTOMATIC TURNTABLE

Low mass square section pick-up arm, cue and pause lever, visual stylus pressure indicator, slide in cartridge carrier, four pole motor.

LASKY'S PRICE £9.95 POST 35p WITH PLINTH AND COVER £13.75 POST 40p

BSR McDONALD PACKAGES

PACKAGE No. 1

BSR McDONALD 510 4 Speed Autochange	£16.03
AUDIO DEVELOPMENT AD76K Magnetic Cartridge	£ 4.50
BSR Afromosia Plinth with black mounting board	£ 4.44
BSR Smoked Perspex Dust Cover	£ 3.17
Recommended retail price	£28.14

LASKY'S PRICE £23.25 POST 40p

ADD £5.50 if M2100/E is preferred
ADD £6.50 if Shure M44/5 is preferred

PACKAGE No. 2

BSR McDONALD 310 4 Speed Autochanger	£12.95
AD76K Magnetic Cartridge	£ 4.50
BSR Afromosia Plinth with black mounting board	£ 4.44
BSR Smoked Perspex Dust Cover	£ 3.17
Recommended retail price	£25.06

LASKY'S PRICE £21.50

ADD 50p if BSR Ceramic Cartridge is preferred

NOW AVAILABLE LASKY'S EXCLUSIVE

LASKY-McDONALD plinth and cover available separately at

£4.75 POST 25p

WAFER TYPE ELECTRO DYNAMIC

This revolutionary idea in sound reproduction functions in a similar manner to the cone loudspeaker system. In place of the conventional paper cone is a flat, rigid plastic panel only a fraction of the depth of the equivalent cone structure. With a flat rectangular panel a larger piston area is also available thereby reducing the size compared with an equivalent cone loudspeaker. Power capacity: 20 watts (peak). Freq. range, 40Hz-20,000 Hz. Input imp.: 8 ohms. Size: 1 1/2in x 1 1/4in x 1 1/4in. Weight: 9oz.



Only 1 1/4" THICK!!

LASKY'S PRICE £5.75 each £11 for two.


Post 20p each

SONY TFM 8030L

BARGAIN SCOOP

HIGH PERFORMANCE 11 TRANSISTOR THREE WAVEBAND PORTABLE BATTERY MAINS RADIO

This is a really top performance, top quality solid state receiver packed with SONY know-how and backed by the outstanding reliability for which SONY are renowned. Now this outstanding set is available from Lasky's at over 27% below the manufacturer's list price making it without a doubt the No. ONE SCOOP of 1971! Just look at these outstanding features. Covers MW, LW and FM (VHF). 11 transistor circuit for high sensitivity and stability. Powerful output to 5in PM Dynamic speaker with rich clear tone quality. AFC for drift free VHF reception. Pushbutton wavechange selectors and tone control. Choice of three power sources—9V battery, household mains or car battery with suitable adaptors. Dial light for use in the dark. External jacks for earphone, tape recording, external power input and car aerial. Ultra modern styling and superb finish with padded leatherette covered cabinet for superior sound damping with chrome trim, strong carrying handle. The SONY TFM 8030L will entertain your leisure hours anywhere, anytime with exciting sound, news, sport music, etc. Technical specification: Freq. range. FM 87-108 MHz, LW150-285kHz, MW530-1,605 kHz. Circuit: 11 transistors, 7 diodes and 2 thermistors. Aerial System: Directional telescopic for FM, internal ferrite bar for LW/MW Power Output: 1.85W max. Speaker PM Dynamic-4Ωimp. Power Source: 9V power pack battery (Ever Ready PP9 or equiv.), AC mains with adaptor, Car battery with adaptor. Size: 9½(W)×8½(H)×3½(D). Complete with earphone and battery.

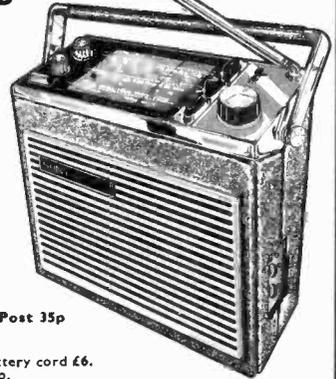

Post 35p


MANUFACTURER'S LIST PRICE **£29.75**

LASKY'S SPECIAL OFFER LIST PRICE **£21.50**

Optional Extras. SONY AC-90e AC adapter £4. DCC-126 stabilised car battery cord £6. Both post FREE if purchased with radio.

EXCLUSIVE Sinclair Project 60

DIGITAL CLOCK SCOOP!

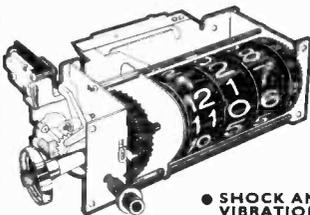

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10-minute division "click" set alarm (up to 12-hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life.

The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min, and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4½W × 1½H × 3½D (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS

LASKY'S PRICE **£6.95** Post 18p


SPECIAL QUOTATIONS FOR QUANTITIES

TTC C-1051 METER

A completely new design 20,000 U.P.V. pocket multimeter with mirror scale and built-in thermal protection. Exceptionally large easy to read meter with D'Arsnonval movement. Colour coded scales. Single positive click-in, recessed selection switch for all ranges. Ohms zero adjustment. Range spec. a.c. volts: 0-6-30-300-1,200V at 10K/ohms/V. DC volts: 0-3-15-150-300-1,2KV at 20K/ohms/V. Resistance: 0-60K-6mega. DC current: 0-60A-300 mA. Decibels: -20dB to +17 dB. Extremely high standard of accuracy on all ranges. Uses one 1½V penlight battery. Strong impact resistant plastic cabinet—size only 4½ × 3¼ × 1½in. Two colour buff/green finish. Complete with test leads and battery.



LASKY'S PRICE **£4.25** Post 13p

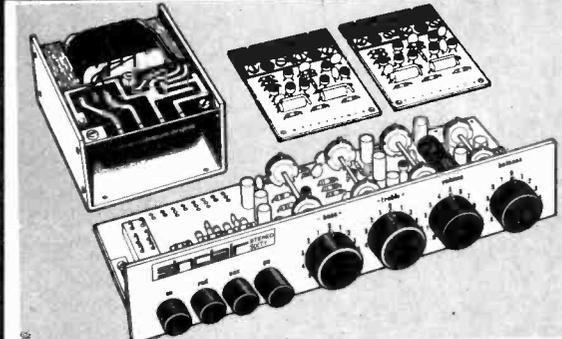

Project 60 is a range of modules which connect together to form a complete stereo amplifier. The modules are: 1. Z-30 high gain power amp. 2. Stereo-60 pre-amp control unit. 3. The PZ-5 unbalanced and PZ-6 stabilised power supplies. A complete system comprises two Z-30's, one Stereo-60 and a PZ-5 or PZ-6.

STEREO 60 SPECIFICATION

Input sensitivities: Radio up to 3mV, Magnetic Pick-up 3mV; correct to R.I.A.A. curve ±1dB: 20 to 25,000Hz. Ceramic Pick-up up to 3mV; Auxiliary up to 3mV ● Output: **£9.97** ½
IV ● Signal to noise: better than 70dB ● Front panel: brushed aluminium with black knobs and controls ● Size: 5¼ × 1½ × 4in. Post 17½p

Z-30 SPECIFICATION

● Power output: 15W R.M.S. into 5ohms using a 35V supply ● Frequency response: 30 to 300,000Hz ±1dB ● Distortion: 0.02% ● Signal to noise: better than 70dB ● Input sensitivity: 250mV into 100K ohms ● Loudspeaker imp: 3 to 15 ohms ● Power requirements: from 8 to 35V DC (The Z-30 will operate from batteries if required) ● Size: 3¼ × 2¼ × 4in. **£4.47** ½ Post 17½p

PZ5

30V unbalanced—sufficient to drive two Z-30's and a Stereo 60 for domestic applications. **£4.97** ½ Post 12½p

PZ6

35V stabilised—ideal for driving two Z-30's and a Stereo 60 for low efficiency speakers. **£7.97** ½ Post 12½p

PACKAGE PRICE For Stereo 60 two Z-30's and one PZ-5. **£20** Post 50p

OUT NOW LASKY'S NEW 1971 AUDIO-TRONICS CATALOGUE

Send your name and address and 13p for post and inclusion on our regular mailing list.

Lasky's Radio Ltd

207 EOGWARE ROAD, LONDON, W.2. Tel: 01-723 3271

33 TOTTENHAM CT. RD, LONDON, W1P 9RB. Tel: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRE

42.45 TOTTENHAM CT. RD, LONDON, W1P 9RO. Tel: 01-580 2753

Open all day, 9 a.m.—6 p.m. Monday to Saturday



ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

We make computers. We also train computer engineers. Could we train you?

We're the Education Division of one of the world's largest Computer manufacturers (and who's better qualified to teach Computer Engineering than a Computer manufacturer?)

Already, we've set up 39 Centres throughout the world to train Computer personnel. Now, the 40th has opened in London, with complete courses for Computer Engineers.

The curriculum includes Basic Electronics, Computer Circuitry, Development in Computer Design with the emphasis on practical work on the world's most advanced computers.

The first courses start in September and last approximately 6 months. We are now interviewing possible students

for these courses.

If you are interested in the challenge of being responsible for the maintenance of a computer installation or if you feel you'd like a move into today's fastest growing space-age industry we'd like to hear from you. We'll give you all the details, assess your abilities and give you an honest answer about future prospects.

CONTROL DATA

LIMITED

CONTROL DATA INSTITUTE

The Education Division of one of the world's largest computer manufacturers

If there's a phone handy, ring us now at

01-637 2171

between 9 am and 9 pm (Mon-Fri) and ask for Mr. Parkes

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77-79 Wells Street, London W1. Please give me further information

Name (Block Capitals) _____

Address _____

Age _____

Phone _____

4C1



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

... carefully written ...

... I am very satisfied with these carefully written and well expressed manuals ... A.W., Shanklin.

... valuable assistance ...

... Your valuable assistance has enabled me to find a good position as a Radio and TV Engineer ... D.S., Bristol.

... they are invaluable ...

... I find that as a base for a course in Electronics they are invaluable and I have yet to find anything even to approach the same standard ... H.N., Rotherham.

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER !!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50. Cash Price on Down Payment of £1 followed by 4 fortnightly payments of £1 each (Total £5). BASIC ELECTRONICS £5.40. Cash Price or Down Payment of £1 followed by 5 fortnightly payments of £1 each (Total £6). This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY

BASIC ELECTRONICS

Prices include Postage and Packing.

Signature _____

(If under 18 signature required of parent or guardian)

NAME _____
BLOCK LETTERS

FULL POSTAL ADDRESS _____



2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £8.75. Post and ins. 38p.

12 volt Car Battery Trickle Charger. Made in Japan, this is very small and neat. Regular use will keep your car battery in good trim throughout the winter. Silly price £1.25 plus 23p postage and insurance.

QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available £1.



PLINTH AND COVER

Suitable for most auto changers, teak base with tinted perspex cover, £4.25 plus 33p postage. Special set for Balfour autochanger £4.25 plus 33p postage.



THRYSOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 w. from full brilliance to out. Assembled and wired ready to install. £3.



AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.95 plus 25p post and ins.



COMPUTER TAPE

2,400 ft of the best magnetic tape money can buy. Made by E.M.I., 1in. wide almost unbreakable and on a 10in. metal computer spool. Users have claimed successful results with video as well as sound recordings £1 plus 33p post. Cassette to hold spool 20p extra.




HORSTMANN "TIME & SET" SWITCH (A 30 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50. Post and ins. 23p.

1 HOUR MINUTE TIMER Made by famous Smiths company, these have a large clear dial, size 4 1/2in. x 3 1/2in., which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch, £1.15.



THE FULL-FI STEREO SIX

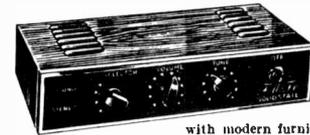

with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. Price is £9 plus 33p post and insurance.

The amplifier sensation of the year

You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet, elegantly styled and teak finished to blend

STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 1in spindle 2in long—with locking washer and nut.

No. of Poles 2 way 3 way 4 way 5 way 6 way 8 way 9 way 10 way 12 way

1 pole	38p	33p	38p	33p	38p	33p	38p	33p	38p
2 poles	38p	38p	38p	38p	38p	38p	38p	38p	38p
3 poles	38p	38p	38p	38p	55p	55p	55p	55p	55p
4 poles	38p	38p	38p	38p	55p	55p	55p	55p	55p
5 poles	38p	38p	55p	55p	75p	75p	75p	75p	75p
6 poles	38p	55p	55p	55p	75p	75p	75p	75p	75p
7 poles	55p	55p	55p	75p	95p	95p	95p	95p	95p
8 poles	55p	55p	55p	75p	95p	95p	95p	95p	95p
9 poles	55p	55p	75p	75p	£1.15	£1.15	£1.15	£1.15	£1.15
10 poles	55p	55p	75p	95p	£1.15	£1.15	£1.15	£1.15	£1.15
11 poles	55p	75p	75p	95p	£1.35	£1.35	£1.35	£1.35	£1.35
12 poles	55p	75p	75p	95p	£1.35	£1.35	£1.35	£1.35	£1.35

Where postage is not stated then orders over £5 are post free. Below £5 add 14p. S.A.E. with enquiries please.

SPARTAN Portable RADIO

Long and medium wave, 7 transistors, size 6in. x 4in. x 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, carplug and case. £3.75 plus 25p post and ins.



MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available. 500, 850, and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2in. diameter 5in. long. Price 90p plus 23p post and ins.



MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. £1 each.



DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 50p each, plus 18p post and insurance, 6 or more post free.



0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits. 18p each, £1.20 doz.



ELECTRONICS (CROYDON) LTD
Dept. PE, 266 London Road, Croydon CR0 2TH
Also 102/3 Tamworth Road, Croydon

4-STATION INTERCOM



£6.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 40p.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.95. P. & P. 45p extra.

INTERCOM/BABY ALARM



£3.15

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 12p. P. & P. 25p.

Transistor TELEPHONE AMPLIFIER



£2.98

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 12p extra. P. & P. 18p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/12)
169 KENSINGTON HIGH STREET, LONDON. W.8

FREE

in Practical Woodworking, out now
Large-Scale Blueprint for the Wood Nymph dayboat

... a handsome 16ft. by 6ft. 6in. beam day-cruiser which can be built at home by any enthusiastic woodworker. Step-by-step instructions start in the March issue.


Other interesting projects: DINING ROOM TABLE AND CHAIRS, PERIOD-STYLE DRESSING TABLE, KITCHEN CUPBOARDS.

Free-Entry Competition to win a tool kit.

PRACTICAL WOODWORKING

March issue OUT NOW 17p.

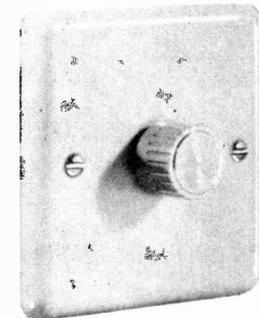Vary the strength of your lighting with a **DIMMASWITCH**



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V, 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3. 4. 0d plus 1/6d post and packing Kit Form: £2. 14. 0d plus 1/6d post and packing Please send C.W.O. to:-

DEXTER & COMPANY
1 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH. Tel: 0244-25883.
As supplied to H.M. Government Departments, Hospitals, Local Authorities, etc.

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smiths, these units are fitted to make top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on the recorder. Offered at only a fraction of the regular price—new and unused only £2. less than the value of the clock alone—post and insurance 14p.



20 AMP ELECTRICAL PROGRAMMER

Learn in your sleep: Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 x 2 1/2 in. deep. Metal encased, glass fronted with chrome surround. Offered at £2.40 plus postage and insurance 23p.



MAINS CONNECTOR

A quick way to connect equipment to the mains safely and firmly; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7,029 cables. 65p each.



FLOUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for lab tanks and indoor plants. Chokes are super-efficient, metal resin filled. Kit A—15-20W, £1. Kit B—30-40W, £1. Kit C—80W, £1.20. Kit E—65W, £1.20. Kit F for 8ft 125W tube £1.75. Kit MFL is for 8in, 9in and 12in miniature tubes, £1. Kit MF2 for 21in 13W miniature tube, £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit MFL 18p on first kit then 18p on each two kits ordered.

BLANKET SWITCH

Double pole with neon lead into side so luminous in dark. Ideal for dark room light or for use with waterproof element—new plastic case 30p each. 3 heat model 40p.



BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1A. Listed at £1.40 each we offer these while our stocks last at only 65p each.

40 WATT 12in. HI-FI SPEAKER

Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and public address. Handling 40 watts R.M.S.—Cone moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms. Chassis diam. 12in.—12 1/2 in. over mounting lugs. Overall height 5 1/2 in. A £10 speaker offered this month for £27 plus 38p post and ins.



CONTROL DRILL SPEEDS

DRILL CONTROLLER
Electrically changes speed. From approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts case, everything and full instructions and full insurance.



£1.50, plus 13p post and insurance.

PROTECT VALUABLE DEVICES FROM THERMAL RUN-AWAY OR OVERHEATING

Thyristors, rectifiers, transistors, etc. which use heat-sinks can easily be protected. Simply make the contact thermostats part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removed range setting is between 80 to 800deg.F. Price 50p.




INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 3 ICs all new and perfect, first-grade devices, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only £1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.

THIS MONTH'S SNIP

ELECTRIC TIME SWITCH

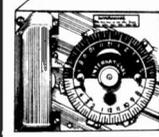Made by Smiths these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. £2.50, post and ins. 23p. Additional time contacts 50p pair.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2 less plug; £2.25 with fitted 13 amp plug; £2.40 with fitted 15 amp plug, plus 23p P. & I.



BARGAIN OF THE YEAR

MICROSONIC KEYCHAIN RADIO
7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 in.—complete with soft leather zippered bag. Specification:—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1,600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 455 Kc/s or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only £1.25 plus 13p post and insurance, less batteries, 6 for £7, post free. Rechargeable batteries 43p pair. Charger 43p.



REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types. **Miniature.** 1in long x approximately 1/4 in diameter. Will make and break up to 1A up to 300 volts. Price 18p each, £1.20 dozen. **Standard.** 2in long x 1/4 in diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 10p each, 80p per dozen. **Flat.** Flat type, 2in long, 1/4 in thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 30p each, £3 per dozen. Small ceramic magnets to operate these reed switches 8p each, 80p dozen.

HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment. 100 mfd. 25V, 8p each 60p doz. 200 mfd. 25V, 8p each 75p doz. 250 mfd. 50V, 16p each £1.65 doz. 400 mfd. 40V, 22p each £2.80 doz. 500 mfd. 12V, 10p each £1.05 doz. 500 mfd. 20V, 18p each £1.80 doz. 500 mfd. 50V, 22p each £2.40 doz. 500 mfd. 350V, 43p each £4.50 doz. 1000 mfd. 12V, 15p each £1.50 doz. 1000 mfd. 18V, 17p each £1.70 doz. 1000 mfd. 64V, 37p each £4 doz. 2000 mfd. 25V, 34p each £3.95 doz. 2000 mfd. 12V, 10p each £1.05 doz. 10,000 mfd. 6V, 29p each £3 doz. 10,000 mfd. 15V, 43p each £4.50 doz. 15,000 mfd. 10V, 53p each £5 doz. 60,000 mfd. 8V, £1.10 each £11 doz. 70,000 mfd. 13V, £2 each £20 doz.

3 AMP 18V BATTERY CHARGER KIT—comprising 230/40 mains transformer with 3 amp secondary and 3 amp rectifier £1.15 + 23p post.

SONOTONE STEREO CARTRIDGE. Turnover type, ref. No. 19 T1. This fits most British pick-ups and is a really excellent reproducer. Limited quantity, £1.

6 AMP 3 PIN SOCKETS. These are always good stock, you never know when you will need some. Famous make, brown bakelite, standard size, 12 for 65p plus 23p post.

DITTO WITH SWITCH. 12 for £1 plus 23p post. **18 AMP SOCKETS, FLUSH MOUNTING.** Bakelite, cream, less switch, 5 for £1.

2 AMP 3 PIN SWITCHED SOCKETS for surface mounting, brown bakelite, 40 doz. Made by famous maker, 13p each or £1.20 dozen.

100 ASSORTED SILICON RECTIFIERS G.P. AND SWITCHING DIODES. Small and very small sizes. A real snip for experimenters, 65p per 100.

MAINS SUPPRESSION ADAPTOR for preventing mains interference caused by vacuum cleaners, razors, sewing machines, etc. rated at 4 amps, simply plug this into your 5 amp 3 pin socket, 30p each.

A NEW SERVICE TO READERS
A bulletin of special snips and "too few to advertise" lines posted to subscribers each month. It will be called "Advance Advert News" and the Subscription is 50p per year, including our completed 1971 catalogue when this is published.


19-PIECE SOCKET SET

Complete with wall or bench rack. An ideal gift for the motorist. 80p + 23p; post and insurance. Most useful sizes from 1/4 in to 1 1/2 in.



HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 13 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 3 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from Makers probably over £10 each. Special snip price £5.75 plus 23p post and insurance. Don't miss this terrific bargain.

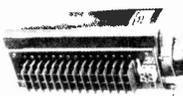

ERGOTROL UNITS

These units made by the Mullard Group are for operating and controlling d.c. Motors and equipment from A.C. mains.

Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods.

These units are contained in wall mounting cabinets with front control panel on which are fuse—push buttons for on/off and the variable thyristor firing control.

4 models are available—all are brand new in makers cases:
Model 2410 for up to 5 amps £17-80
Model 2411 for up to 10 amps £27-80



Where postage is not stated then orders over £5 are post free. Below £5 add 14p. Semiconductor add 5p post. Over £1 post free. S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CR0 2TH
Also 102/3 Tamworth Road, Croydon

WATERPROOF HEATING ELEMENTS

26 yards length 70W. Self-regulating temperature control. 50p post free.



MICRO SWITCH

5 amp, changeover contacts, 8p each, 90p doz. 15 amp Model 10p each or £1.05 doz.



BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES**. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24	25-99	100 up
BP00 7400N	Quad 2-input NAND gate	0-83	0-27	0-28
BP01 7401N	Quad 2-input NAND gate—open collector	0-83	0-27	0-28
BP04 7404N	HEX inverter	0-83	0-27	0-28
BP10 7410N	Triple 3-input NAND gate	0-83	0-27	0-28
BP20 7420N	Dual 4-input NAND gate	0-83	0-27	0-28
BP30 7430N	Single 8-input NAND gate	0-83	0-27	0-28
BP40 7440N	Dual 4-input buffer gate	0-83	0-27	0-28
BP41 7441N	BCD to decimal decoder and NIT driver	1-18	1-00	0-87
BP42 7442N	BCD to decimal decoder (TTL O/P)	1-18	1-00	0-87
BP50 7450N	Dual 2-input and/or not gate—expandable	0-83	0-27	0-28
BP53 7453N	Single 8-input and/or not gate—expandable	0-83	0-27	0-28
BP60 7460N	Dual 4-input—expandable	0-83	0-27	0-28
BP70 7470N	Single JK flip-flop—edge triggered	0-45	0-40	0-35
BP72 7472N	Single master slave JK flip-flop	0-45	0-40	0-35
BP73 7473N	Dual master slave JK flip-flop	0-50	0-45	0-43
BP74 7474N	Dual D flip-flop	0-50	0-45	0-43
BP75 7475N	Quad bistable latch	0-55	0-50	0-47
BP76 7476N	Dual master slave flip-flop with preset and clear	0-55	0-50	0-47
BP83 7483N	Four bit binary adder	1-30	1-18	1-00
BP89 7490N	BCD decade counter	1-18	1-00	0-87
BP92 7492N	Divide by 12 4-bit binary counter	1-18	1-00	0-87
BP93 7493N	Divide by 16 4-bit binary counter	1-18	1-00	0-87
BP94 7494N	Dual entry 4-bit shift register	1-18	1-00	0-87
BP95 7495N	4-Bit up-down shift register	1-18	1-00	0-87
BP96 7496N	5-Bit shift register	1-20	1-06	0-93

Data is available for the above Series of Integrated Circuits in booklet form, price 13p

LINEAR I.C.'s

Type No.	Case	Leads	Description	Price		
				1-24	25-99	100 up
BP 201C—8L201C	TO-5	8	G.P. Amp	65p	55p	45p
BP 701C—8L701C	TO-5	8	OP Amp	65p	55p	45p
BP 702C—8L702C	TO-5	8	OP Amp Direct OP	65p	55p	45p
BP 702 —72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p	45p	40p
BP 709 —72709	D.I.L.	14	High OP Amp	53p	45p	40p
BP 709P—8LA709C	TO-5	8	High Gain OP Amp	53p	45p	40p
BP 741 —72741	D.I.L.	14	High Gain OP Amp (Protected)	75p	60p	50p
8A 703C—8LA703C	TO-5	6	R.F.—I.F. Amp	48p	35p	27p
TAA 263—	TO-72	4	A.F. Amp	70p	60p	55p
TAA 293—	TO-74	10	G.P. Amp	90p	75p	70p

TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	8p	PAK No.	8p
UIC00	7400N 0-50	UIC73	7473N 0-50
UIC01	7401N 0-50	UIC74	7474N 0-50
UIC02	7402N 0-50	UIC75	7475N 0-50
UIC03	7403N 0-50	UIC76	7476N 0-50
UIC04	7404N 0-50	UIC80	7480N 0-50
UIC05	7405N 0-50	UIC82	7482N 0-50
UIC10	7410N 0-50	UIC83	7483N 0-50
UIC20	7420N 0-50	UIC86	7486N 0-50
UIC40	7440N 0-50	UIC90	7490N 0-50
UIC41	7441N 0-50	UIC92	7492N 0-50
UIC42	7442N 0-50	UIC93	7493N 0-50
UIC60	7460N 0-50	UIC94	7494N 0-50
UIC51	7451N 0-50	UIC95	7495N 0-50
UIC60	7460N 0-50	UIC96	7496N 0-50
UIC70	7470N 0-50	UICX1	ASST'D 74's 1-50
UIC72	7472N 0-50		

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

DUAL IN-LINE LOW PROFILE SOCKETS

14 and 16 lead sockets for use with dual-in-line Integrated Circuits.

Order No.	Price each
T8014 14 pin type	1-24 35p 25-99 25p 100 up 20p
T8016 16 pin type	1-24 45p 25-99 35p 100 up 30p

RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty. prices each
Epoxy case To-5 temp. range 15°C to 55°C	1-11 12-24 25-99 100 +
μL 900 Buffer	40p 35p 30p 27p
μL 914 Dual two-input gate	40p 35p 30p 27p
μL 923 J-K flip-flop	53p 50p 47p 45p

Full data and circuits for I.C.'s in Booklet form, price 7p.

DTL DIGITAL I.C.'s

DTL dual-in-line package	Price each
Type MC844P expandable dual 4-input NAND Power-Gate	60p each
Type MC846P clocked flip-flop	75p each

FULL DATA SUPPLIED WITH UNITS

All prices quoted in New Pence. Please send all orders direct to our warehouse and despatch department.

BI-PAK SEMICONDUCTORS

P.O. BOX 6, WARE, HERTS.

Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. Giro No. 388-7006.

YATES ELECTRONICS

(FLITWICK) LTD.

(FLITWICK) LTD.

RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction. 1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W Erie wire wound.

Power	Tolerance	Range	Valves available	Price
watts				1-99 100+
1/4	5%	4.7Ω-2.2MΩ	E24	1-0p 0-7p
1/4	10%	3.3MΩ-10MΩ	E12	1-0p 0-7p
1/4	10%	1Ω-3.9Ω	E12	1-0p 0-7p
1/4	5%	4.7Ω-1MΩ	E12	1-0p 0-7p
4	10%	1Ω-10Ω	E12	7 1/2p 7 1/2p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ. E12 pack 325 resistors £2.20. E24 pack 650 resistors £4.20.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7 1/2p. 0.33μF, 11p. 0.47μF, 13p. 160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 0.15μF, 0.22μF, 4p. 0.33μF, 6p. 0.47μF, 7 1/2p. 0.68μF, 11p. 1.0μF, 12 1/2p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3 1/2p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6 1/2p. 0.47μF, 8 1/2p. 0.68μF, 11p. 1.0μF, 13p.

MYLAR FILM CAPACITORS

100V: 0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2 1/2p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1.0μF, £2.90.

ELECTROLYTIC CAPACITORS—One Price—5p Each

Mullard C426 series (μF/V): 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 16/10, 32/10, 64/10, 125/10, 200/10, 10/16, 20/16, 40/16, 80/16, 125/16, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 4/40, 8/40, 16/40, 32/40, 50/40, 2.5/64, 5/64, 10/64, 32/64.

Miniature P.C. mounting (μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

POTENTIOMETERS

Carbon track 5kΩ to 1MΩ, log or linear (log 1/4W, lin 1/4W). Single, 12 1/2p. Dual gang (stereo), 40p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix). Sub-miniature 0-1 watt, 4p each. Miniature 0.25 watt, 5p each.

SEMICONDUCTORS

AC126 15p	BFY52 22 1/2p	OC81 15p	2N3055 72p
AC127 15p	BSY56 30p	OC82 15p	2N3702 15p
AC128 15p	B5X21 25p	ORP12 47 1/2p	2N3703 14p
AD140 40p	BY124 7 1/2p	IN4001 7 1/2p	2N3704 17 1/2p
AF115 17 1/2p	BYZ10 30p	IN4002 10p	2N3705 15p
AF117 17 1/2p	BYZ13 20p	IN4003 11p	2N3706 12p
BC107 14p	OA85 7 1/2p	IN4004 12 1/2p	2N3707 18 1/2p
BC108 10p	OA91 7 1/2p	IN4005 14p	2N3708 10p
BC109 14p	OA202 7 1/2p	IN4006 15p	2N3709 11p
BFY50 22p	OC71 15p	IN4007 16p	2N3710 12p
BFY51 19p	OC72 15p	2N2926 11p	2N3711 14p

ZENER DIODES

400mW 5% 3.3V to 30V, 17 1/2p.

VEROBOARD

0-1	0-15	0-15	0-1
2 1/2 x 3 1/2	22p 16p	17 x 3 1/2 (plain)	52 1/2p
2 1/2 x 5	24p 24p	17 x 2 1/2 (plain)	37 1/2p
3 1/2 x 3 1/2	24p 24p	2 1/2 x 5 (plain)	17 1/2p
3 1/2 x 5	27p 27p	2 1/2 x 3 1/2 (plain)	15p
17 x 2 1/2	75p 57 1/2p	Pin insertion tool	47 1/2p
17 x 3 1/2	100p 75p	Spot face cutter	37 1/2p
17 x 5 (plain)	75p	Pkt. 36 pins	15p 15p

ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W, 4P3W, 22 1/2p.

PLUGS AND SOCKETS

Standard 1/4 in screened	17 1/2p	2.5mm insulated	7 1/2p
Standard 1/4 in insulated	14p	3.5mm insulated	7 1/2p
Stereo 1/4 in screened	35p	3.5mm screened	12 1/2p
Standard 1/4 in socket	15p	2.5mm socket	7 1/2p
Stereo 1/4 in socket	17 1/2p	3.5mm socket	7 1/2p

BRUSHED ALUMINIUM PANELS

12" x 6" — 25p; 12" x 2 1/2" — 15p; 6" x 1 1/2" — 10p.

C.W.O. please. Post and packing, please add 7 1/2p to orders under £2. Data sheets are available for most of the components listed, and will be sent free on request.

8E39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

COMPLETE STEREO SYSTEM

FOR ONLY **£40.95**
CARRIAGE £1.75



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends; Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.95. Carr. 40p). Now Available **MATCHING F.M. TUNER £22.05.**

PREMIER STEREO SYSTEM "TWO"

As system "ONE" above but with Garrard SP25.


PREMIER PRICE £47 Carr. £1.75

MIDLAND AM/FM STEREO TUNER AMPLIFIERS

Two new all solid state receivers from Midland at economical prices. Beautifully styled in slimline cabinets.




MODEL 19-520

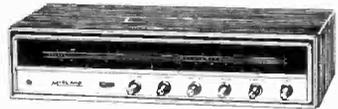

MODEL 19-542

Specifications	Model 19-520	Model 19-542
Semi	19 transistors, 12 diodes, conductors 2 varistors	22 transistors, 12 diodes
Tuning range	FM 88-108 MHz FM Stereo Multiplex AM 530-1635 kHz	FM 88-108 MHz FM Stereo Multiplex AM 535-1695 kHz
Aerial	Internal AM and external FM	Internal AM and external FM
Frequency Response	50-17,000 Hz	35-20,000 Hz
Power Output	2 1/2 watts rms per channel (8 watts music power)	4 watts rms per channel (18 watts music power)
Inputs	Ceramic phono	Magnetic/Ceramic phono and aux.
Speaker impedance	4-8 ohm	8 ohm
Controls	Power on/off, Volume, tone, balance, tuning, AFC, Stereo indicator	On/off, Volume, bass, treble, balance, tuning, AFC, Stereo indicator
Function	AM, FM, FM Stereo, Phono (Stereo indicator light)	AM, FM, FM Stereo, Ceramic, Magnetic, Aux.
Size	15" x 8 1/2" x 3 1/2"	16 1/2" x 9 1/2" x 3 1/2"
PRICE	£30.45 Carr. & Ins. 50p	£44 Carr. & Ins. 50p

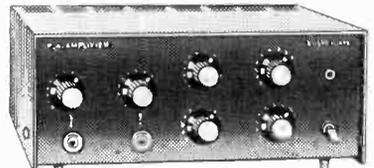50 WATT PUBLIC ADDRESS AMPLIFIER MODEL PA-5000



A top quality amplifier giving 50 watts rms power output (80W peak). Incorporates 8 transistors and 4 silicon diodes (silicon output transistors). Inputs for 2 microphones each with individual volume controls, plus phono/aux input. Master volume control and Bass and Treble Controls. Well presented front panel for ease of operation, on/off power flick switch and pilot light. Output impedance 4/8/16 ohms Mike 1 and 2 sensitivity 2mV (50k Ohm) Phono/Aux 300mV (100k Ohm). Frequency response 50-20,000Hz. Fused output and thermal overload protection. A.C. Mains 220-250V, 50/60Hz. Size 13 1/2 in x 9 in x 5 in.

PREMIER PRICE £39 P. & P. 50p

E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2 1/2 in tweeters and crossover network. Available with 8 or 15 ohm impedance. Handling capacity 10W. Brand new.



£3.47 P. & P. 40p

HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2 in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.



£2.47 P. & P. 25p

STEREO STETHOSCOPE SET Low imp. £1.25. P. & P. 10p
MONO STETHOSCOPE SET Low imp. 52p. P. & P. 10p

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 1/2 x 3 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phonoplugs output. Attractive teak wood grain finish case.



Mono Model £3 Stereo Model £3.47 P. & P. 12p


POCKET SIZE MULTI-TESTER

With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0.5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50µA-2.5mA-250mA D.C. 0-6000 ohms-6 megohms, 10µµf-0.001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions.



£4.90 P. & P. 17p

SPECIAL OFFER!

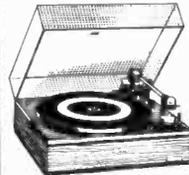

Garrard SP25 Mk. II Single Record Player. Fitted Goldring G850 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Parapex Cover. Total list Price over £24.
PREMIER PRICE £18.90
P. & P. 50p



TAPE CASSETTES

C60 (60 min.) 37p 3 for £1.05
C90 (90 min.) 62p 3 for £1.80
C120 (120 min.) 87p 3 for £2.55
P. & P. 3p

All cassettes can be supplied with library cases at 3p extra each.



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3' 250' P.V.C.	28p	LP6 5 1/2' 1200' P.V.C.	62p
TT3 3' 450' POLYESTER	37p	DT6 5 1/2' 1800' POLYESTER	£1.12
DT3 3 1/2' 600' POLYESTER	57p	TT6 5 1/2' 2400' POLYESTER	£1.87
SP5 5' 800' P.V.C.	42p	SP7 7' 1200' P.V.C.	62p
LP5 5' 900' P.V.C.	50p	DT7 7' 1800' P.V.C.	75p
DT5 5' 1200' POLYESTER	75p	DT7 7' 2400' POLYESTER	£1.25
		TT7 7' 3600' POLYESTER	£2.50

TAPE SPOOLS 3" 5p, 5 1/2" 7" 9p.
Post and Packing 3" 5p, 5 1/2" 8p, 7" 10p. (3 reels and over Post Free.)


PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM C.T.R. TEL: 01-636 3451



ROC ELECTRONICS

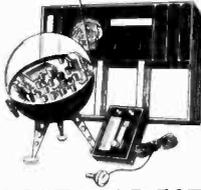20 PROJECT SOLAR ELECTRONIC KIT Mod. R.128



This ultra modern Project Kit is shaped for the space age. Carried inside a transparent domed 4 1/2" capsule the R.128 comes complete with a self-contained solar cell to power any one of 20 projects ranging from a one transistor radio to a Morse set complete with key and Morse training code. Supplied complete with easy to follow instructions and even the cement to assemble this unique electronic space capsule.

PRICE £4-50



2 OCTAVE ELECTRONIC ORGAN KIT Mod. R.129

Complete with a music book containing 10 easy to play songs the R.129 solid state organ kit covers 2 full octaves. Slotting into a fitted hardwood case the top panel carries the key assemblies and all the components including the loudspeaker. Like all Roc Electronic Kits every item is included down to the last nut and bolt so that the constructor can start assembly within minutes of opening the package.

PRICE £4-50

10 PROJECT INTEGRATED CIRCUIT KIT Model R.127

Using a robust Solid State Integrated circuit the R.127 kits will build any one of these projects: (1) Germanium Radio. (2) Test Oscillator. (3) Morse Telegraph Training Set. (4) I.C.T. Transistor Radio. (5) Germanium 1 Transistor Radio. (6) Record Player Amp. (7) Continuity Tester. (8) AF Signal Tracer. (9) Radio Transmitter. (10) Water Purity Tester.

PRICE £3-50

2 TRANSISTOR SOLAR RADIO KIT Model R.126

Like all Roc Electronic Kits the R.126 uses reliable no-solder connections to produce a complete 2 transistor radio in under 2 hours. As well as battery operation the kit is supplied complete with a solar cell to provide power from the Sun or any strong light source.

PRICE £2-50



CRYSTAL RADIO KIT Model R.125

This easy to build Radio is based on the same circuit developed by Marconi for the very first radio transmission but uses a modern ferrite aerial for maximum efficiency. A perfect introduction to Radio Theory.

PRICE £1-50



16 WATT STEREO AMPLIFIER Model R.138



As well as separate bass and treble controls the R.138 features switched main and remote speaker outputs so that the same stereo installation can be used to drive independent stereo speaker systems.

Fitted in a well finished walnut cabinet the brushed aluminium front panel and sensible control knobs set this amplifier in the professional class.

SPECIFICATION: Output: 16 Watts Total, 8 Watts per Channel. Frequency range: 30-20,000Hz. Inputs: Phono & Tuner. Outputs: Speakers Main, Speakers Remote, Tape Out, and Headphones. Controls: Bass, Treble, Volume, Balance (all ganged) Mode, Speakers Stereo/Mono and Power on/off.

PRICE £16-50



5 WATT 8 TRACK CARTRIDGE STEREO AMPLIFIER Model R.133

Just slot in one of the many 8 track cartridge tapes available for a continuous programme of your favourite music. A manual programme override switch enables you to switch from one track to the next at the push of a button at the same time a numbered indicator lights up to show which track is playing. Beautifully finished in an oiled walnut cabinet the R.133 is mechanically engineered to provide long and reliable service. **SPECIFICATION:** Tape speed: 9.5 cm/sec (3 1/4 i.p.s.). Wow & flutter: better than 0.3%. Frequency range: 40-12,000Hz. Cross talk: better than 45dB at 1,000Hz. Output: 5W total. 2.5W per channel. Amplifier outputs: 200mV.



PRICE £36-00



STEREO HEADPHONES Model R.328

Built up to a standard not down to a price, the R.328 stereo headphones represent a breakthrough in value for money.

A valuable addition to any stereo installation they will provide many hours of listening pleasure.

SPECIFICATION: Matching impedance: 8-16 ohms. Frequency range: 30-15,000Hz.

PRICE £2-40


PROFESSIONAL SOLID STATE FOUR BAND COMMUNICATION RECEIVER Model R.135

This is the communication receiver that you have long been waiting for. Fully transistorised and continuous coverage from 555kHz to 30MHz in four bands including illuminated electronic bandspread for 160-10 metres. Also incorporated is an internal speaker, automatic noise limiter, SSB/AM/CW Switch, AVC Switch, S Meter, Receive and Standby Switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. The R.135 will run off of 240V a.c. dry batteries or any 12V d.c. negative ground source.

PRICE £45-00



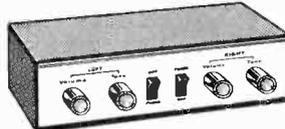10 WATT TRANSISTOR STEREO AMPLIFIER Model R.137



With separate tone and volume controls on each channel and inputs for both phono and tuner, this 10 transistor amplifier is the ideal start to an excellent budget system. Frequency response 70-20 KHz. Output impedance 8-16 ohm. Attractively styled with brushed aluminium front panel.

PRICE £9-50



10 WATT BUDGET STEREO ALL TRANSISTOR AMPLIFIER Model R.136



Ideal as a second stereo system or for the newcomer to Hi-Fi who wishes to upgrade existing equipment the R.136 sounds every bit as good as it looks. As well as inputs for crystal or ceramic cartridge the R.136 has a Stereo Tuner input which accepts the matching R.134 Stereo AM/FM Tuner.

The Satin Finish front panel carries a stereo headphone socket as well as volume, balance, tone (all ganged) speaker, mode and selector controls. Supplied complete with oiled walnut enclosure.

SPECIFICATION: Output: 10 watts total. 5 watts per channel. Frequency Range: 35-18,000Hz. Inputs: Phono and Tuner.

PRICE £13-00



AM/FM/MPX STEREO TUNER Model R.134



Perfect Matching Unit to the R.136 Amplifier. The R.134 Stereo Tuner is designed to give years of reliable performance. The Tuning Band covers AM & FM with a separate stereo beacon to indicate when stereo broadcasts are being received.

SPECIFICATION: FM frequency range: 88-108MHz. Usable sensitivity: 18µV. Stereo separation: 26dB at 1kHz. Image rejection: 65dB. AM frequency range: 535-1,605kHz. Usable sensitivity: 280µV.

PRICE £21-00



STEREO FM/AM/MPX TUNER AMPLIFIER Model R.124

Another Roc Exclusive offering top value for money performance the R.124 is a Stereo Tuner/Amp with facilities only usually found in much more expensive units. Features like separate bass and treble controls, automatic frequency control switch and stereo headphone socket give the R.124 a price to specification ratio second to none.

Housed in a handsome walnut cabinet the classical low line styling of the R.124 will grace any home. **SPECIFICATION:** FM: Frequency range: 88-108MHz. Usable sensitivity: 20µV. Stereo separation: 26dB at 1kHz, 20dB minimum. Image Rejection: 55dB. AM: Frequency Range: 535-1605kHz. Usable sensitivity: 300µV. Audio Section: Total Output Power: 4W. Phono Input: 200mV at 1MΩ. Tape Input: 100mV at 100KΩ.

PRICE £29-95



H.P. Terms available for personal callers on purchases over £30.

RETURN OF POST MAIL ORDER SERVICE Dept. PE

Orders under £10 please add 25p post and packing. Orders over £10 sent post free.

ROC ELECTRONICS LIMITED

193 EDGWARE ROAD LONDON W2 1ET

TELEPHONE: 01-723 6211

Shop open 9-6 Monday-Saturday (Thurs. 1 p.m.)

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES
Advertisement Manager D. W. B. TILLEARD

BUT, SERIOUSLY

DO SOME of us on occasion take this business a trifle too seriously? We feel this could be true, for now and again someone is heard to imply that so and so design is a flippant use of electronics.

Getting straight down to grass roots, let us consider any classic circuit arrangement; in fact suppose we take a well known building block such as the multivibrator, as a general illustration. This circuit has a habit of cropping up in the most unlikely guises, as we all know. It may appear in an item of test gear such as a c.r.o. trace doubler or a voltage to frequency converter, in a car lamp flasher, in the tone generator section of an organ, in a digital calculator, or in a "toss the coin" game, to name but a few. This ubiquity helps to demonstrate the point that an electronic circuit *as such* has no innate purpose apart from the purely electronic function it has been expressly designed to perform; and this alone is not enough. Outside purely academic circles, the circuit requires some gainful employment to justify its existence. Providing it is within the circuit's capabilities, the precise nature of the task it may be given is, in an electronic sense, irrelevant. It may be useful or it may be frivolous. There is no list of prescribed duties that circuits must restrict themselves to! They work for us as we decree.

Electronics is a very "human" technology, simply because it is easily adaptable to most of our whims and needs. And it plays, quite rightly, a major part in our amusement and entertainment, no less that in the "serious" activities of life.

To be fair we must not forget that to some individuals the study of electronic circuitry can be an end in itself. Academic minds so inclined can derive plenty of intellectual pleasure from the analysis of circuit behaviour without too much worrying about specific applications. But to most of us electronics surely means more than conducting a minute anatomical examination of a pretty trace on the c.r.t., or indulging in a prolonged immersion in mathematics, however good all this may be for the mind. When it comes to the crunch, electronics is a tool and the most proper and sensible thing is to apply it however and wherever we can, to serve us at both work and play.

If there are theoreticians who still shudder at some frivolous application of the technology, there is a homely example for them to ponder. Let them consider the television receiver—that embodiment of many elegant electronic techniques, a mass produced complex of circuitry that has been designed principally for our entertainment. Just dare suggest that this cathode ray companion and comforter for millions be redesignated something like a "communications monitor" and provide nothing but news and elevating cultural programmes, and the whole nation would go on strike! F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

AUTOCHECKLIGHT	198
MULTI-FUNCTION LOGIC CIRCUIT	202
"P.E. GEMINI" DUAL PURPOSE STEREO AMPLIFIER	206
P.E. DIGITAL CLOCK	216

SPECIAL SERIES

MAKING THE MOST OF LOGIC IC's—9	228
------------------------------------	-----

GENERAL FEATURES

INGENUITY UNLIMITED	226
POWER CONTROL WITH TRIACS	237

BEGINNERS


SIMPLE REFLEX RECEIVER	222
------------------------	-----

NEWS AND COMMENT

EDITORIAL	197
SPACEWATCH	201
MARKET PLACE	205
ELECTRONORAMA	224
ON THE FRINGE	245
BOAT SHOW	246
READOUT	249

Our April issue will be published on
Friday, March 19

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.25 (£2 5s. 0d).
Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

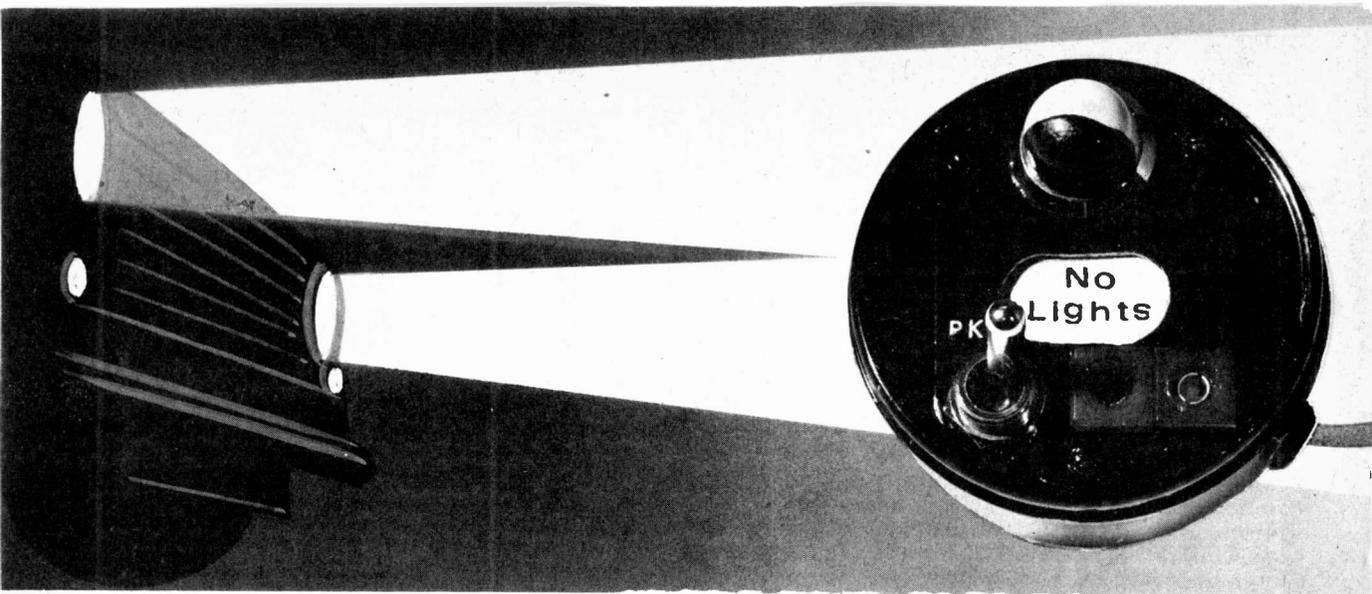

MANY drivers are not regular users of parking lamps and tend to use side lights when parking in a strange situation. Because they would not use an automatic parking light very often, they do not consider it a worthwhile investment. The added facility of a lighting up reminder that this circuit offers will thus make the parking lamp worthwhile. The circuit is very simple and provides the following facilities:

- (a) An automatic parking lamp that turns itself on and off at dusk and dawn.
- (b) A warning system when the car is used with no lights in poor light or after lighting up time.
- (c) A warning indication, while driving, as lighting up time approaches.
- (d) Automatic cancellation of either system when the sidelights are switched on.
- (e) No additional control switching when on route.

The complete unit can be attached to the car dash panel or to the windscreen where it is in view of the driver. Only three wires need to be connected to the car wiring which is not altered in any way. Both positive and negative earth 12 volt circuits are given, and for cars already fitted with an automatic parking light, only part of the circuit need be built. The unit utilises a standard parking lamp so if such a lamp is already used it can now be automated.

CIRCUIT

The fundamental circuit adapted for both positive and negative earth systems is shown in Figs. 1a and 1b; this illustrates the operation of the system using normal ignition and side light switching. With switch S1 in the "normal" position the circuit is operative when the ignition is on and the sidelights off. The circuit is then in the lighting up reminder state and LP2 will signal the approach of lighting up time when *en route*, or when about to move off without lights when they are required.

With S1 in the "park" position, the sidelights switched off and a parking lamp (LP1) plugged into SK1 and SK2, the circuit will function as an automatic parking light, the ignition switch and LP2 being out of circuit.

LIGHT DEPENDENT RESISTOR

As daylight decreases, the l.d.r. (light dependent resistor—X1) resistance increases and since this forms a potential divider with R1 at the base of TR1, when

the determined light level is reached, a switching function is triggered between transistors TR1 and TR2 so that TR2 conducts and consequently illuminates LP2 to show up the expression "no lights". The switching function is preferred to an emitter follower because there is no heat build-up across transistor TR2 while the input signal is developing. The life of the transistor is therefore prolonged. Resistor R3 is made up of two 22 ohm resistors in parallel.

The same circuit operation is carried out for both the parking lamp and internal warning system and the ignition/battery supplies are selected in conjunction with the appropriate lamp by the operation of the double pole changeover switch S1.

SYSTEM CANCELLATION

Both systems are cancelled when the normal sidelight switching operation is carried out following the internal warning, or where sidelights are required when parked. The circuit is completed via the filaments of the sidelights, rear light and number plate light; with the sidelight switch off, the small current required for the system flows through the paralleled filaments of the sidelights and associated lamps. When, however, these lamps are switched on, the circuit is shorted out and the no lights warning or the parking lamp, cease to operate.

If the car is garaged or parked within the law, the switch remains in the normal position and both systems are isolated. A check is readily available for both systems when light is shielded from X1. It is to be noted that LP2 will hunt if the l.d.r. picks up reflected light from the hand or any other adjacent surface capable of reflecting light on to the sensor.

OPERATIONAL LIGHT RANGE

The operational range of the system is good and operational levels of light may be selected by the insertion of light filters under the cover of the l.d.r. These may be in the form of ordinary thin paper and are far more economical than the inclusion of a variable resistance in the circuit.

With the engine running when *en route*, the internal lamp may flicker as the critical light period approaches. This is due to voltage variation of the car's supply (the charging system) but since the flicker is an added attraction factor, the necessity for voltage stabilisation is considered unnecessary and not in the interests of economy.

CONSTRUCTION

The prototype unit was housed in a small tobacco tin, the lid of which was reinforced with aluminium. Holes can be cut in the lid and aluminium plate for X1 mounting, SK1 and SK2, S1 and the "no lights" indication. The legend "no lights" may be printed on tracing paper and inserted, between two protective celluloid layers, under the aluminium panel which is attached to the lid by three 6B.A. screws.

The mounting for X1 and LP2 holder were obtained from a single indication lamp dismantled for the purpose. SK1 and SK2 can be banana sockets or any

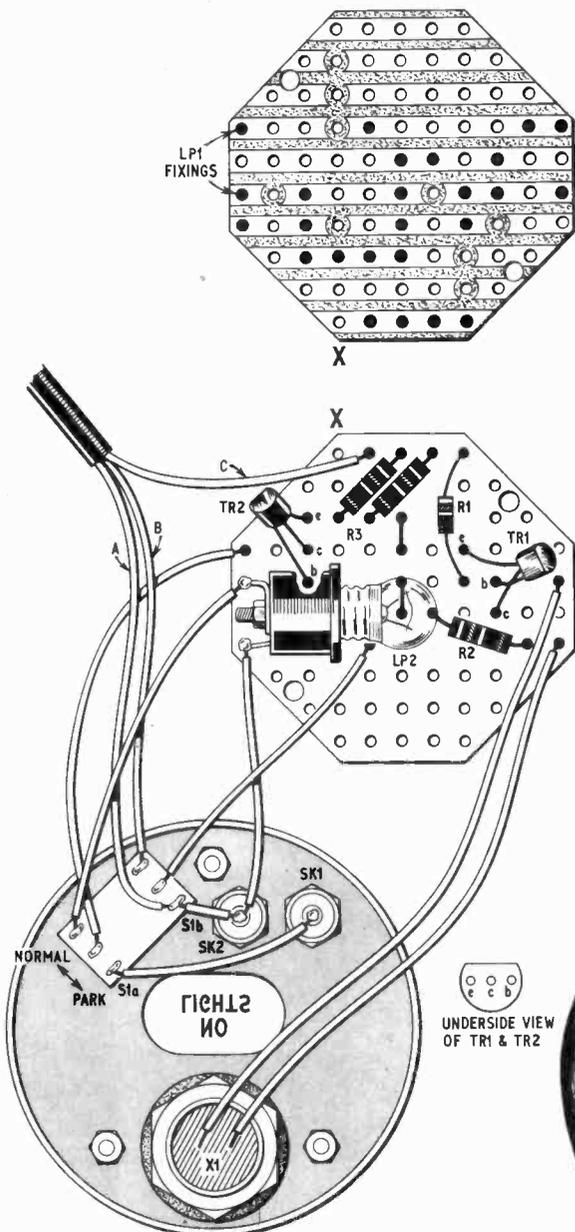


Fig. 2. Layout and wiring diagram of the prototype unit housed in a tobacco tin case. This is the negative earth system; for positive earth version the wire connected to S1b wiper is removed and reconnected to SK2, link between SK2 and S1b is removed. Wire "C" is taken to S1b wiper and a new wire—which now becomes "C"—is connected to SK2

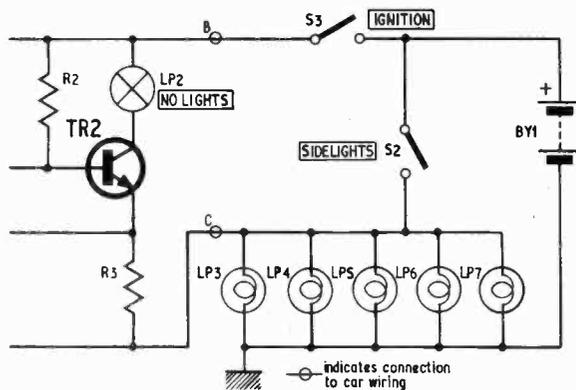


Fig. 3. Circuit diagram of the negative earth system for lighting up reminder only. Connections "B" and "C" are reversed for a positive earth system


special socket to suit the parking light. The three core lead that connects the circuit to the car wiring can be taken out through a grommet hole in the side of the case.


Components in the prototype were mounted on a piece of 0.2 inch matrix Veroboard, fixed inside the tin by two 6B.A. screws and spacers (see Fig. 2). The inside of the tin should be protected by insulation tape so that no connection is made between the circuit and earth on the car. It is, of course, possible to use any form of construction, since the layout of components is not critical—the unit could be built into the dashboard of many cars and LP2 could be housed in a warning light mounting chosen to correspond with the other panel warning lamps.

REMINDER ONLY

If it is required to provide a lighting up reminder only—without the facility of an automatic parking light—then S1, SK1 and SK2, and the connection to S2 (sidelights switch) on the car battery side may be omitted (see Fig. 3).

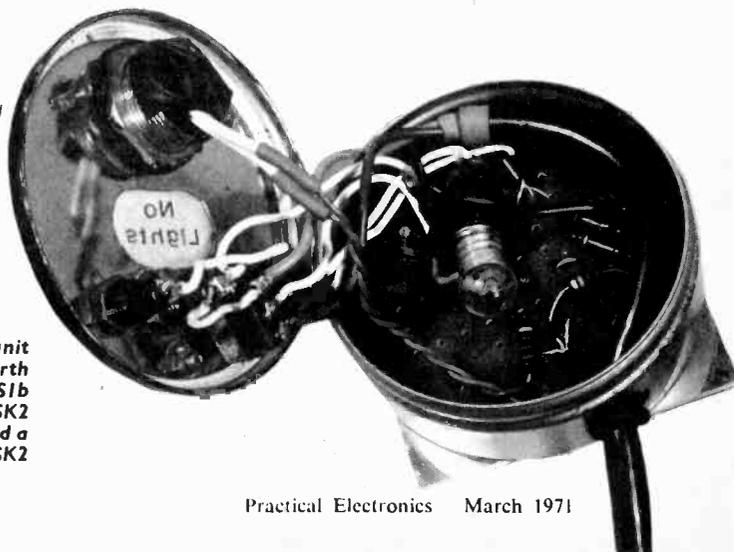When the complete system is operated in the lighting up reminder mode, LP1 can be unplugged from SK1 and SK2 and hence the no lights warning may be cancelled by operation of S1 (change to "park" position) as well as by switching on the sidelights. ★



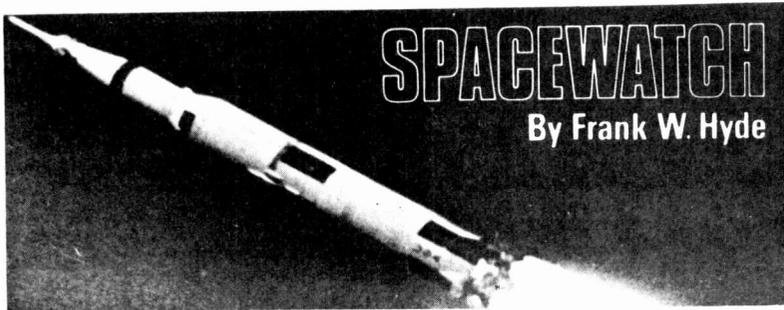

SOVIET ACHIEVEMENTS IN SPACE

After a period of apparent inactivity, the Soviet Union has in the past two years or so made some significant advances that have been spread over the whole area of space activities. The Russians have for a long time favoured the use of space platforms and automatic probes. They have covered the human element involved by longer periods under space conditions, and experimented with the transfer of astronauts from one vehicle to another.

The local earth-moon activities have formed a part of their programme but they have paid a good deal of attention to the special techniques required to explore the other planets. Already they have had two attempts to land robot craft on Venus and now a third attempt has been made.

The unfortunate loss of *Lunik 15* at the time of the *Apollo 11* mission was a particular disappointment, but served to indicate the difficulties that attend attempts to maintain communication, with vehicles that are at a low level in areas where there are mountains involved.

COLLECTING MOON SAMPLES

However the loss of control of *Lunik 15* was more than compensated by the successful mission of *Lunik 16*. This vehicle departed from the earth for the moon with the main task of collecting, automatically, samples of lunar soil, putting them into containers, and returning them to earth. The vehicle consisted of a descent platform carrying the return vehicle, which carried the drilling mechanism and control. Altogether something in excess of 100 grammes of lunar material was recovered.

The point of operation was in the Sea of Fertility, 56° 18' W and 0° 41' S, which is some 900km from the site of the *Apollo 11* landing. The material was friable surface substance of fine grain, for the first 15cm of the sample. The next section from 15cm to 33cm was of variable granular material with some larger inclusions of the order of 3mm in diameter. The last section from 33cm to 35cm was of large grain with some fragments of bedrock.

In appearance the material is a very dark grey almost black powdery

substance. The mean specific gravity of the material was of the order of 1.2 and the variation in particle size ranged from 70 μ m at the surface to 120 μ m at the lowest depth. The composition appears to be basaltic with some feldspar and some metallic iron and vitreous particles. Some isotopes of short life were found and altogether about 70 chemical elements were present.

A comparison with the specimens brought back by *Apollo 12* shows very close agreement in the percentage of the various elements.

SOYUS 9

Andrian Nikolayev, who captained *Soyus 9*, has made some interesting comments on the 18-day flight. Month long flights are feasible but anything longer would require different techniques. There would be need for more efficient and extensive conditioning and also new medical procedures.

The post flight effects of this mission were very much more marked than those encountered with the shorter flights. Walking was found to be difficult over a period of days and there was frequent stumbling. They found it difficult to climb stairs, sometimes hard to stand upright.

A notable feature was the wasting of the lower limbs by as much as 4cm round the hips and 2cm round the shins. This appears to result from the loss of muscle tissue in the legs which are normally used to support the body at 1g. There was a loss of body weight of 5kg for the new astronaut Sevastianov and a little less for Nikolayev. However, they both recovered their normal weight in three weeks.

LUNOKHOD

The mobile moon vehicle *Lunokhod* was an exciting event and represented a new era in space technology. Although an instrument unit, previously landed by the United States, had been made to hop, *Lunokhod 1* is the first vehicle to be landed on the moon and become mobile under guidance from the earth direct. When the difficulties are properly realised, a task of this kind becomes a major point in history.

Because it is the first time that such a successful operation has been

mounted, a whole new vista in the exploration of the moon becomes available. Provided that communications between the base station and the unit can be maintained, many new areas of the moon can be explored in detail.

At the moment this is feasible only in open areas because in hilly or mountainous regions loss of communication could be disastrous. This points to the likelihood that control from a space platform would be the ultimate aim. A very great advantage is that a mobile system remotely controlled would enable special regions to be explored which might be impossible for manned units.

MANNED FLIGHTS

It is significant that the Soviet space scientists do not regard the robot as the principal method. This is borne out by the fact that the internal environment of *Lunokhod 1* is similar to a life support system having a temperature between 16 and 18 degrees centigrade and a pressure of between 730 and 780mm Hg.


The present instrumentation could be built into a manned cabin without modification. From this it could well be surmised that a manned landing is still part of Soviet plans. Also there is a distinct suggestion that the Russians are looking further afield to Mars for automated surface units.

LUNAR EXPERIMENTS

Although not much appeared in the initial stages about the type of experiments being undertaken, the following were included in the mission.

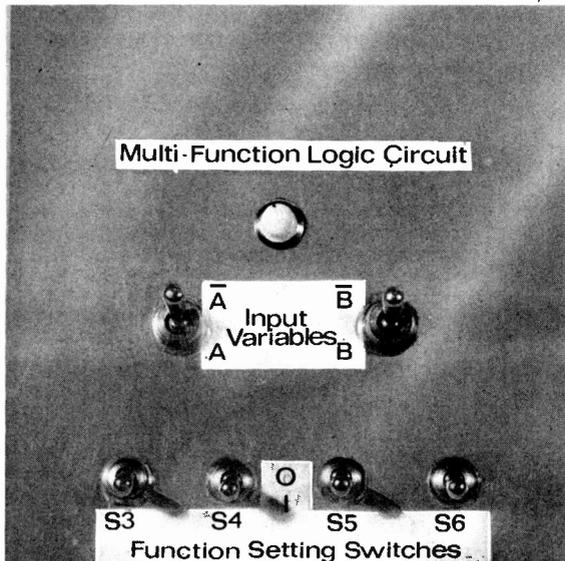- (a) Determination of the composition of the surface of the moon using x-ray photometry.
- (b) Measurement of extra-galactic x-radiation using an x-ray telescope to make long exposure studies of weak sources. These cannot be done effectively (where distant sources are concerned) with rockets and satellites.
- (c) Assessing the mechanical properties of the lunar soil by impressing a special stamp.
- (d) The study of cosmic radiation from the sun.
- (e) Experiments which involve the radiation from the moon itself.
- (f) The very important co-operative effort of France and the Soviet Union in a laser experiment to determine accurately the earth-moon distance.

A special system of telemetric sensors is in use to measure the stresses acting on the chassis of the vehicle and a great deal of television recording is being made of the tracks that are made on the lunar surface.



For demonstration purposes, it is convenient to be able to produce any of these 16 functions without having to construct separate gates. The multi-function logic circuit makes it possible to establish any required function simply by selecting the appropriate combination with four switches.

FUNCTIONS OF BINARY VARIABLES

In the logic diagram of Fig. 1, each of the four switches S3, S4, S5, and S6 puts a 0 or 1 condition on its respective gate input, according to Table 1. This lists the function logic output corresponding to each of the 16 functions.

The switch settings are, in fact, those that would appear in a truth table of the desired function.

The A,B inputs are connected to decode each of the four possible input conditions and so select the appropriate gate as follows:

Input state	$\bar{A}\bar{B}$	$A\bar{B}$	$\bar{A}B$	AB
Gate selected	G1	G2	G3	G4

The G5 gate output will therefore assume a 0 or 1 condition depending both on the position of the

MULTI-FUNCTION LOGIC CIRCUIT

By P. A. Davis, A.M.Inst.E.

A LOGIC function expresses the relationship between the input and output logic states of a circuit. The basic logic functions AND, OR and NOT are part of a series of functions.

With two input variables, A and B, four different input conditions can occur:

$$\bar{A}\bar{B} \quad A\bar{B} \quad \bar{A}B \quad AB$$

These four conditions could produce a 0 or 1 at the output, depending on the circuit logic, hence a total of 2⁴ or 16 functions are possible.


function setting switches and on the particular combination of the A, B inputs.

A 1 condition will light the lamp via the lamp driver but a 0 condition will not.

CIRCUIT

The multi-function logic circuit makes use of two integrated circuits. These i.c.s are three and four input NAND gates; the SN7410N and SN7420N respectively.

Fig. 1. Logic diagram of multi-function unit. Here two i.c.s incorporating 3- and 4-input NAND gates are used. Gate input numbers refer to the device pin connections as seen in Fig. 2

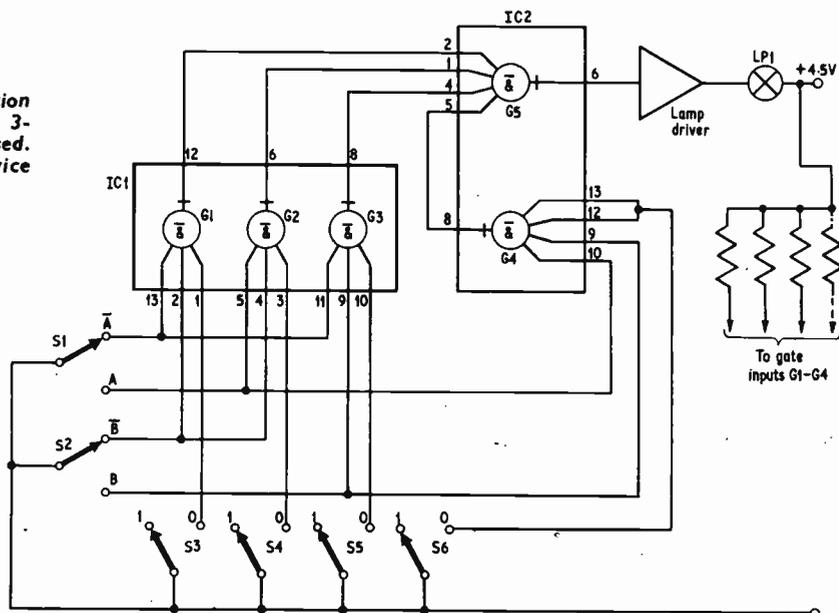

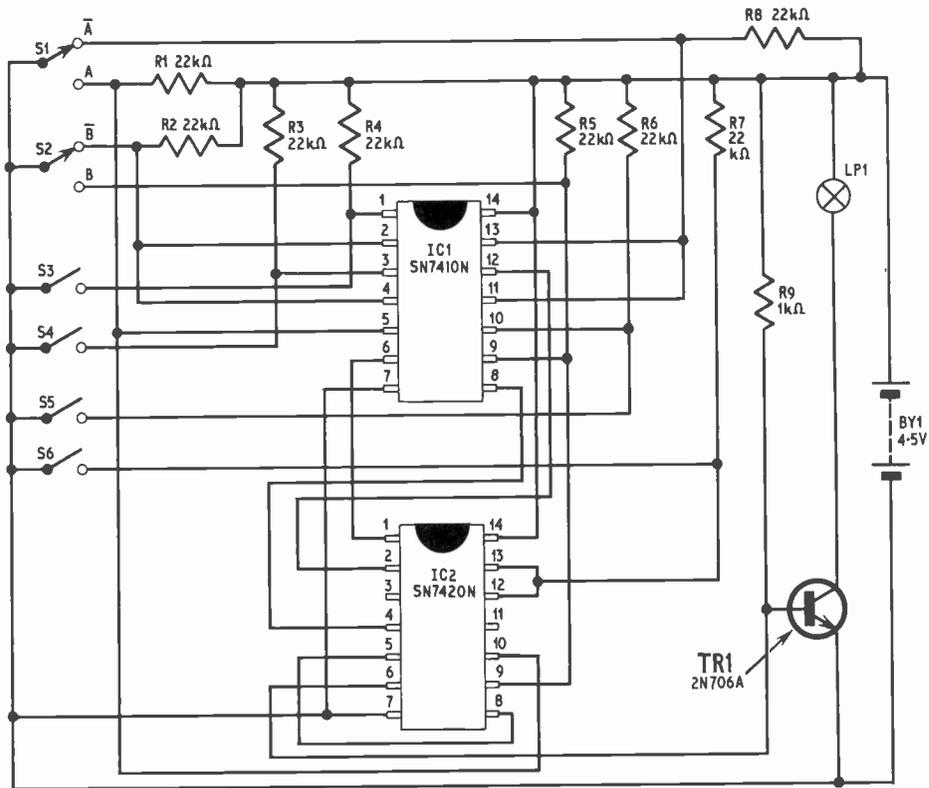


Fig. 2. Circuit diagram of unit. Note that all gate inputs have a positive bias

In the circuit diagram (Fig. 2), all the switched gate inputs are taken to the positive rail by way of resistors. This ensures that each input is held at logic 1 when its switch is opened.

The unused input at gate G4 is connected to a used input rather than left floating.

Fig. 3 shows the i.c. gate configuration used.

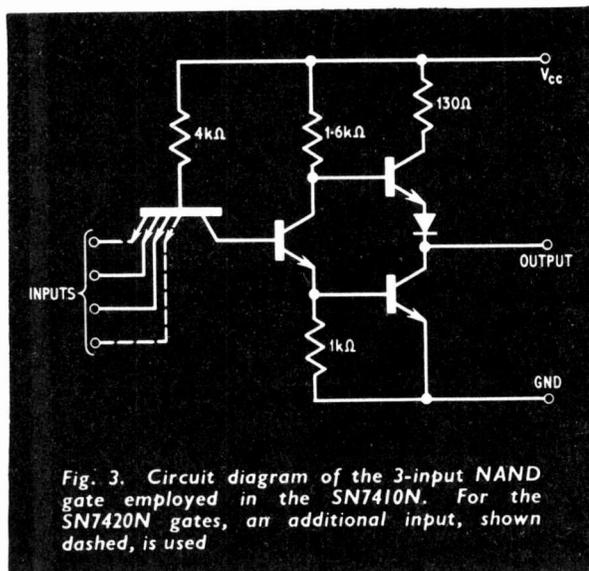


Fig. 3. Circuit diagram of the 3-input NAND gate employed in the SN7410N. For the SN7420N gates, an additional input, shown dashed, is used

Table 1. FUNCTIONS OF TWO BINARY VARIABLES

Function number	Function setting switches S3 S4 S5 S6	Logic function produced	Function name
1	0 0 0 1	$A \cdot B$	AND
2	0 0 1 0	$\bar{A} \cdot B$	
3	0 0 1 1	B	B
4	0 1 0 0	$A \cdot \bar{B}$	
5	0 1 0 1	A	A
6	0 1 1 0	$\bar{A} \cdot B + A \cdot \bar{B}$	Exclusive OR
7	0 1 1 1	$A + B$	OR
8	1 0 0 0	$\bar{A} \cdot \bar{B} = \overline{A + B}$	NOR
9	1 0 0 1	$A \cdot B + \bar{A} \cdot \bar{B}$	Logical Equivalence
10	1 0 1 0	\bar{A}	NOT A
11	1 0 1 1	$\bar{A} + B$	
12	1 1 0 0	\bar{B}	NOT B
13	1 1 0 1	$A + \bar{B}$	
14	1 1 1 0	$\bar{A} + \bar{B} = \overline{A \cdot B}$	NAND
15	1 1 1 1	1	1
16	0 0 0 0	0	0

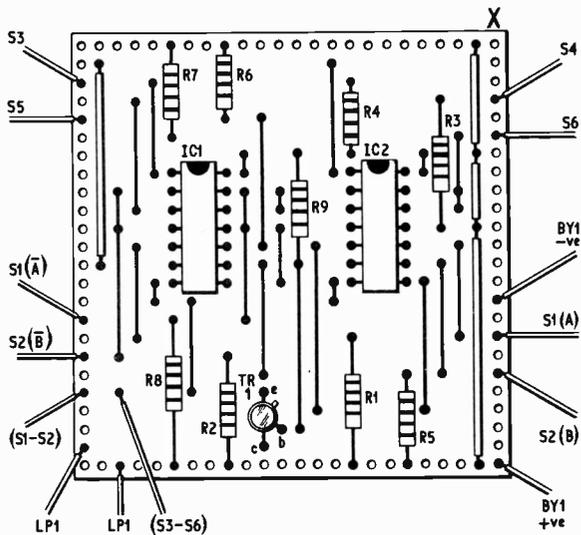


Fig. 4. Component layout and wiring for topside and underside of Veroboard

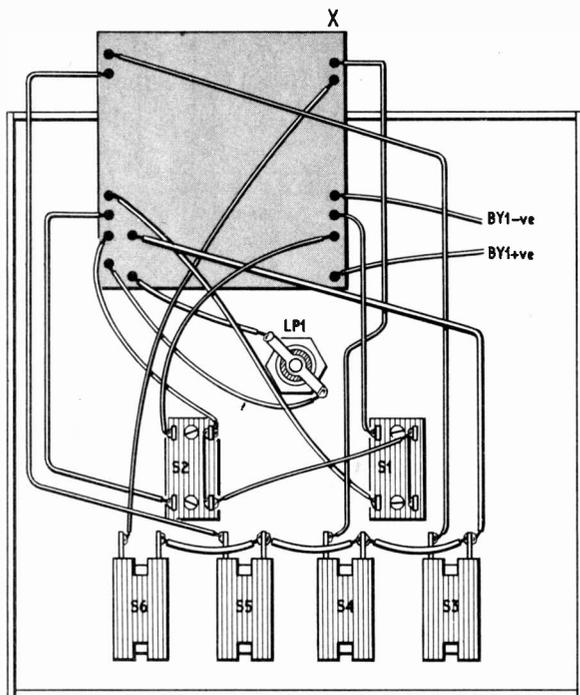
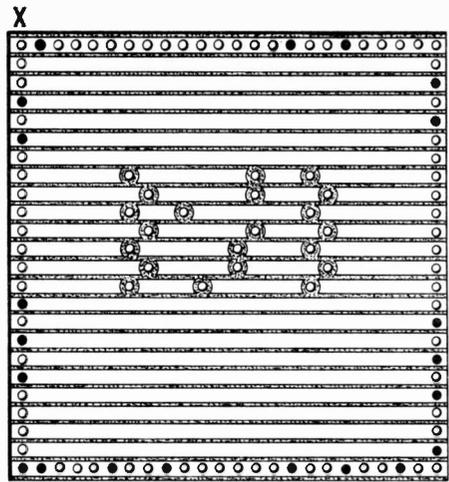


Fig. 5. Veroboard and control panel interwiring on an aluminium chassis plate

CONSTRUCTION

Apart from the chassis mounted switches and lamp, all of the components are mounted on a single piece of Veroboard as given in Fig. 4. To accommodate the dual-in-line i.c. packages, Veroboard of 0.1in matrix is used.

Wiring of the switches to the board is shown in Fig. 5. Positioning of these will depend very much on the preference of the user; whether a large or small display is required.

COMPONENTS . . .

Resistors

R1-R8 22k Ω (8 off)
R9 1k Ω
All 10%, 1/4 watt carbon

Transistor

TR1 2N706A

Integrated Circuits

IC1 SN7410N
IC2 SN7420N

Switches

S1-S2 Single pole changeover (2 off)
S3-S6 Single pole on/off (4 off)

Lamp

LPI Miniature indicator 6V 0.06A (Electroniques)

Miscellaneous

0.1in matrix Veroboard 2 1/2in x 2 1/2in, Vero pins (14 off), Aluminium chassis 8in x 6in x 1 1/4in

OPERATION

To operate the completed unit, first select the required function from Table 1. This function is then set using the switches S3, S4, S5, and S6.

Each input combination of A,B is then operated on by this function, and the result, a 1 or 0, will appear at the output of gate G5. If the output is 1 the lamp will light.

Say, for example, the OR function is required. Table 1 gives the function switch setting as 0111 (Function 7).

With these switches set accordingly, the switches S1 and S2 are set to A,B. It will be found that the lamp lights, hence, we can conclude that provided that A or B (or both) is present at the input, the lamp lights.

Apart from the convenience of the unit for demonstrating logic functions, it can be useful as part of a training programme — particularly if the function governing the input-output relationship has to be deduced from the unit's behaviour. ★

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

WIPER DELAY

There are many windscreen wiper control units on the market and, as our readers will have noted, the problem with many circuits is that they are unable to accommodate the various wiring configurations and wiper motor types in use on all modern cars.

Wiperdwell, a unit manufactured by Automents Ltd., is one unit that can be used with all types of self-parking wiper motors and can easily be fitted by the average motorist in a very short time. The unit allows the selection, by a single control, of the most suitable wiping frequency for slight rain, fog and snow—a principle that works extremely well.

The unit can be fitted using a drill and screwdriver, comprehensive connection instructions are supplied and physical connection is made by way of "piggy back" connectors thus avoiding altering existing wiring and obviating soldering.

The Wiperdwell unit will not affect the normal operation of the wipers, can give up to 20 seconds between sweep delay, costs £4.75 and is supplied with a six month guarantee.

MINIATURE SWITCHES

Sub-miniature toggle-switches with a rating of 6A at 125V or 3A at 250V a.c. suitable for most of our constructional projects are now being marketed by WEL Components Ltd.

The switches have a breakdown voltage of 1,000V a.c. with insulation resistance of more than 100 megohms at 500V d.c. The switch contact resistance is typically less than 5 milli-ohms at 1A 2.4V d.c.

The switches are moulded in phenolic melamine with solder tag connections and are available in two types—Type TS106D is a single-pole double throw and costs approximately 37½p (7s 6d) each. Type TS206N is a double-pole double throw and costs approximately 47½p (9s 6d).

Addresses of nearest stockists can be obtained from WEL Components Ltd., 5 Loverock Road, Reading, Berkshire.

Another range of sub-miniature toggle and pushbutton switches suitable for many P.E. projects are those manufactured by Birch Stolec Ltd.

The switches include toggle, lever lock, rocker and momentary push-button types with one, two, three or four poles.

Contact ratings are: coin silver contacts, 5A resistive load at 115V a.c., or 2A at 250V a.c.; brass contacts with gold over nickel plate, 0.4V/A maximum at 20V maximum (a.c. or d.c.); coin silver contacts with gold over nickel plate, 5A resistive load at 115V a.c. or 28V d.c., or 2A at 250V a.c., and 0.4V/A maximum (a.c. or d.c.).

Available with short or long toggles with nine different colour caps, the switches can also be supplied for printed circuit board or angled mounting.

Full details of these switches and addresses of nearest stockists can be obtained from Birch-Stolec Ltd., Ponswood Industrial Estate, Windmill Road, Hastings, Sussex.


Also, we have been informed that Gothic Electronic Components, Beacon House, Hampton Street, Birmingham 19, have been appointed stockists and distributors of the complete range of standard and miniature thumbwheel switches from Birch-Stolec.

REED RELAY

Two new miniature encapsulated reed relays supplied with either one normally open reed switch or one changeover contact are the most recent products from Osmor Ltd.

Ideal for printed circuit board mounting, the type ERA has maximum d.c. contact ratings of 10W 200V 0.5 d.c. and type ERC is rated at 4W 28V 0.1A d.c.

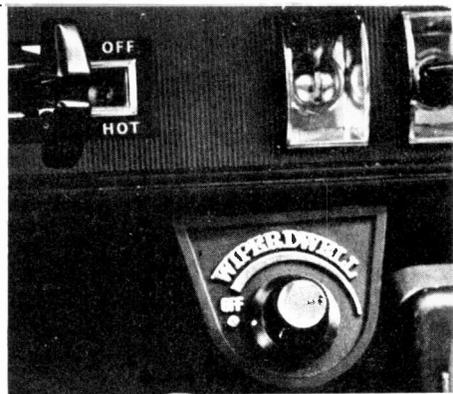The relays are available for 6V, 12V and 24V operation, and are colour coded for easy identification. The



Wiperdwell windscreen wiper control from Automents

coil is wound on a glass-filled nylon bobbin, and a magnetic screen is fitted as standard.

The complete relay is encapsulated in glass-filled nylon and measures only 22mm (¾in) × 10.5mm (¾in) diameter.

Price of the relays vary according to type and quantity; full details can be obtained from Osmor Ltd., 540 Purley Way, Croydon, Surrey, CR9 4DY, or at 53 London Road, Leicester, LE2 0PD.

TAPE HEAD CLEANING

Suitable for all compact cassette tape recorders and car player units, Multicore Solders have recently introduced a new tape head cleaning cassette tape.

It comprises a cassette tape container in which high quality cleaning tape is incorporated to clean tape heads, capstan and pinch wheel. Used in the same manner as a tape cassette by placing in the machine and operating in the play-back position, the whole operation takes approximately one minute.


Supplied in a plastics container the Bib Size 31 cassette tape head cleaner retails at 53p (10s. 7d.) and is available from most hi fi shops.

Osmor miniature reed relay

Bib cassette tape head cleaner from Multicore Solders

Miniature toggle switches marketed by WEL Components

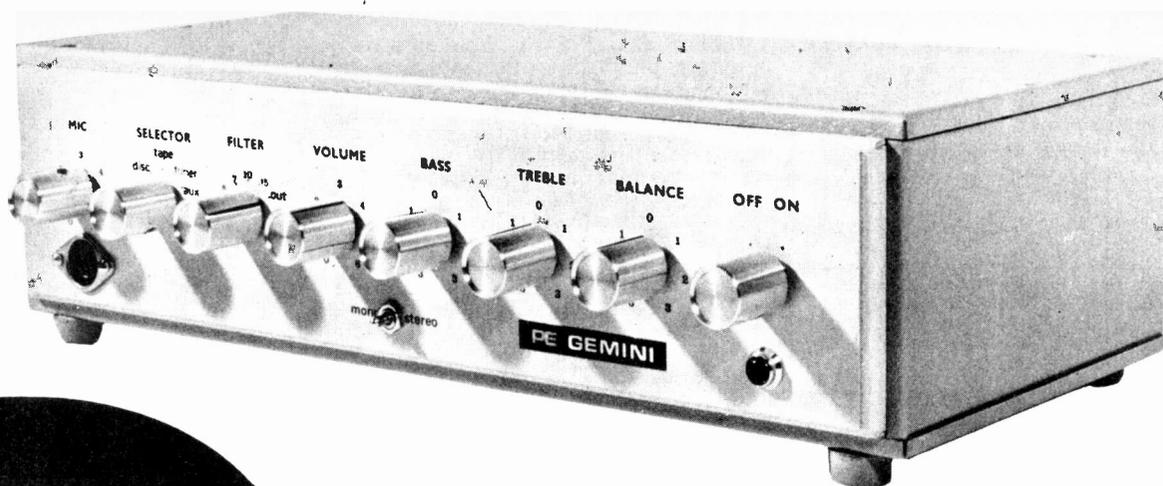Birch-Stolec miniature toggle and pushbutton switches



**PE
GEMINI**

DUAL PURPOSE STEREO AMPLIFIER

PART FIVE

By D. S. GIBBS and I. M. SHAW (FERRANTI LTD)

IN this, the final part of the P.E. Gemini dual purpose stereo amplifier, we give final construction details of the pre-amplifier, a fault finding chart and hints on using the completed amplifier.

DRILLING

The pre-amplifier is housed in a Contil Mod-2 case size G and the dummy front panel (aluminium $12\frac{1}{2}$ in \times $2\frac{1}{4}$ in \times 18 s.w.g.) was actually cut from the unused main amplifier chassis. Full drilling dimensions for the box and panels are given in Figs. 36, 37, and 38.

Miniature toggle switches were used in the prototype for S1, S2, and S5 and the holes for these and the pilot light LP1 must be drilled to suit whatever components the constructor has available. The best arrangement is to drill the front panel and the dummy front panel whilst they are clamped together to ensure that any slight errors do not prevent the components from fitting through the holes. All the holes must be de-burred with a file or a large drill.

FRONT PANEL

To obtain a presentable finished article the dummy front panel can be rubbed with wire wool, using household soap and water, in one direction along the length of the panel. This process should be continued until all the scratches have been removed. A very good "brushed aluminium" finish can be obtained in this way; a satin finish can be obtained if the panel is coarse sand blasted by some local workshop or garage. Care must be taken not to introduce any fingerprints or grease before the panel is sprayed with Letracote gloss.

LABELLING


The front and rear panels can now be labelled using the same method as for the main amplifier cabinet, i.e. one light coat of Letracote gloss, apply the letters and then a further two coats of Letracote. As can be seen in the photographs, the prototype controls have numbers of relative magnitude arranged around them. The indication dots for these numbers can be marked first lightly in pencil with the help of the template, Fig. 39. The template is transferred to a thin piece of celluloid by drilling small holes in the required places. The celluloid template can then be placed over the dummy front panel and the dots marked in lightly in pencil. This method ensures that the dots exactly line up with the 30 degree switch positions and that the dots round the other controls are all at the same angles and radii.

ASSEMBLY

The front panel components are now mounted, not forgetting the dummy front panel which is held on by the control spindle nuts. Care must be taken not to mark the dummy front panel whilst tightening the various nuts and screws. The rear panel components, C52 (using a suitable capacitor clamp) and the assembled printed circuit board should be mounted on the appropriate parts of the case.

WIRING

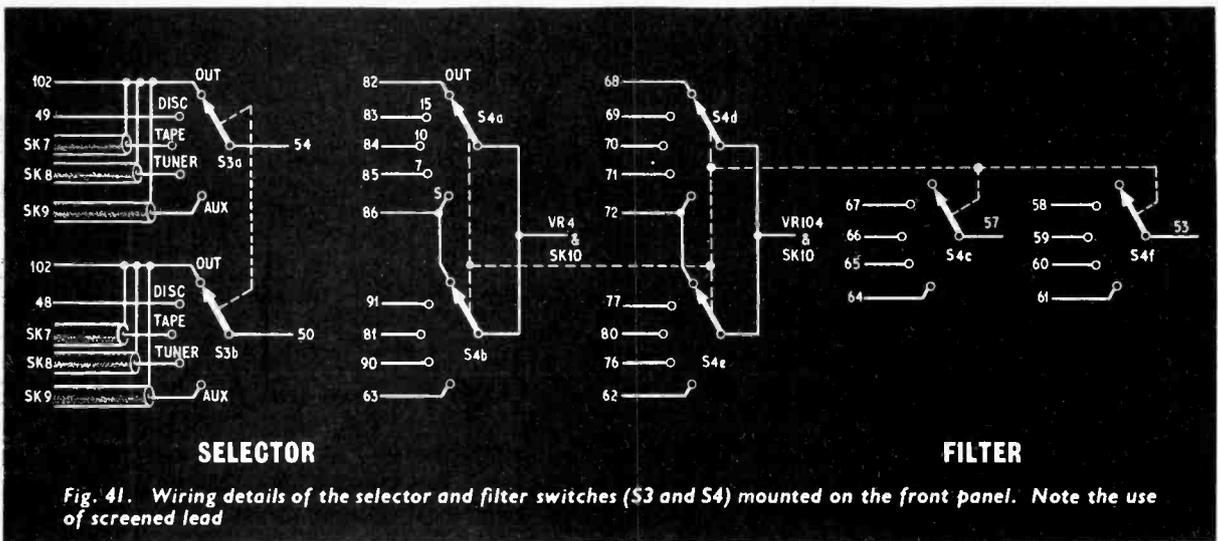The wiring should be executed with the case dismantled, i.e. opened out like an exploded diagram, to make the connections to the front and rear panels easier. Any systematic way of wiring the interconnections can be adopted but it is recommended that many



different colours are used for identification purposes. The components which are wired to the tone controls, C45, C46, C47, C145, C146, C147, must have sleeved wire ends and as short leads as practicable. The same applies to the four resistors in the area around S1, and SK5. The only internal screened cables necessary are the ones from the input sockets to S3, with the actual


screens being connected to a stout tinned copper wire joining the "Out" positions of the selector switch. The sole connection between the case and the negative rail must be at SK5 as indicated, or complications may arise due to an earth loop being formed which could result in an incurable hum. The earth from the mains input cable is connected to a solder tag which is on the same bolt as C52 capacitor clip, but on the other side of the screening plate. This screen is fitted on final assembly in convenient holes between the mains switch and balance control such that it touches neither. As with the main amplifier the paint may have to be removed from around the screw holes to ensure that all the different sections of the box make electrical connection with each other. Finally, the feet can be fitted to the base of the case. Figs. 40, 41 and 42 give the wiring up details.

INTER UNIT CONNECTIONS


The cable which supplies power to the pre-amplifiers and audio to the main amplifier must be made a suitable length to suit the particular installation. Any multi-core (at least three core) screened cable can be used since the output impedance of the pre-amplifier is quite low. We have not given any pin connection numbers for this cable because we have noticed that in some cases the numbers on plugs and sockets do not always correspond with each other. All that is required is that the channels do not inadvertently get reversed and that the earth and supply rails have a continuous path from the main amplifier. This cable must be in place before power is applied to the main amplifier or the charging current taken by C6 and C106, if this plug is inserted after the power has been applied, may damage the driver and output transistors.

FAULT FINDING

This is a complex amplifier and it is possible that the constructor will have some problems to iron out before it works perfectly. Most faults will be due to: wires left unconnected or connected to the wrong place, components inserted at the wrong place on the printed circuit board, transistors or diodes inserted the wrong way round (easily done with the Ferranti devices), or surplus solder bridging the gap between two printed circuit tracks.

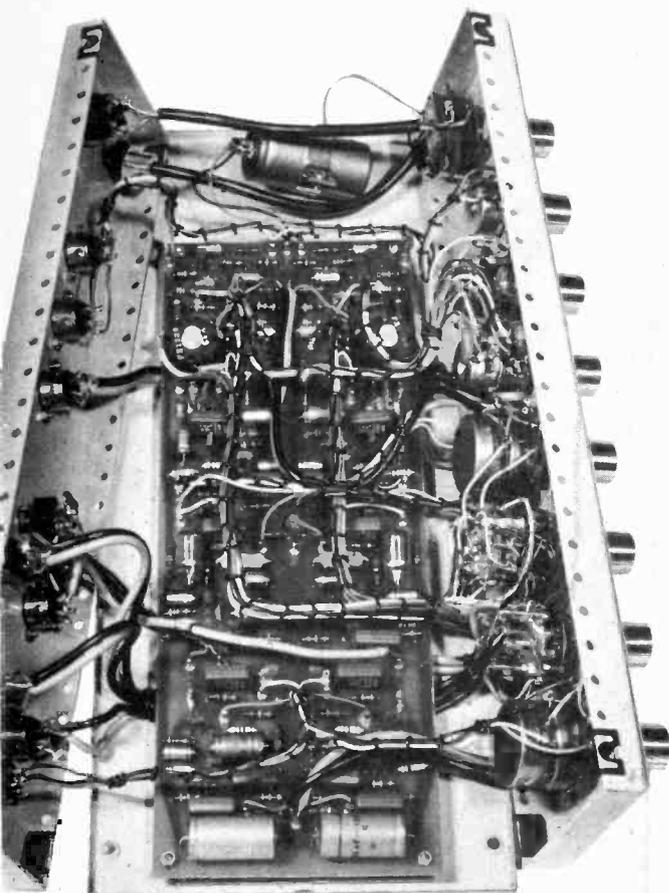

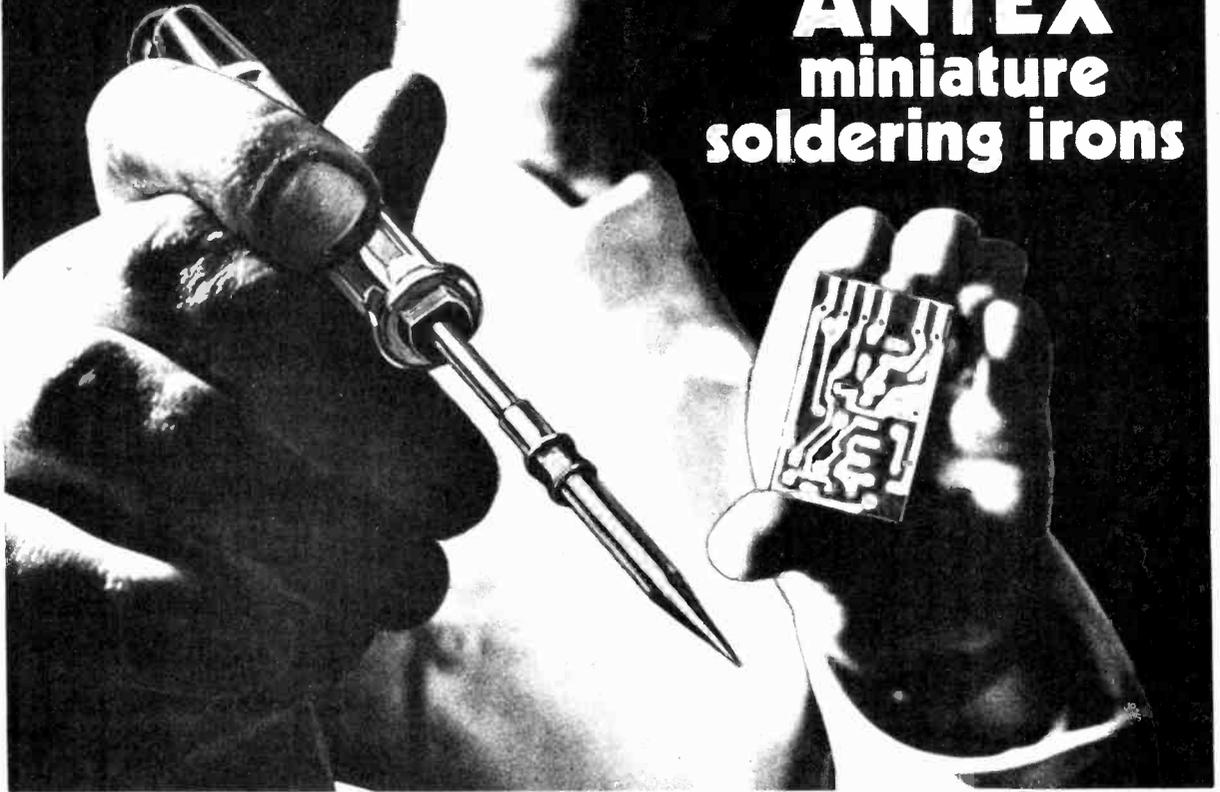take a good look at **ANTEX** miniature soldering irons



G18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. £1.80 (36/-)



E20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From £1.80 (36/-)



ES25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From £1.80 (36/-)



F40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From £2.35 (47/-) Spare bits and elements for all models and voltages immediately available from stock.

Complete precision soldering kit



PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional

This kit—in a rigid plastic "tool-box"—contains

- Model CN 15 watts miniature iron, fitted 3/32" bit
- Interchangeable spare bits 1/8", 3/16"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash **£2.75 (55/-)** to Antex



Model CN 240/2 15 watts - 240 volts **£1.70 (34/-)**

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone Plymouth 67377/8.
Telex 45296. Giro No. 2581000.

Please send me the Antex colour catalogue

Please send me the following irons

Quantity Model Bit Size Volts Price


.....
.....
.....

I enclose cheque/P.O./cash value

NAME

ADDRESS

..... PE3

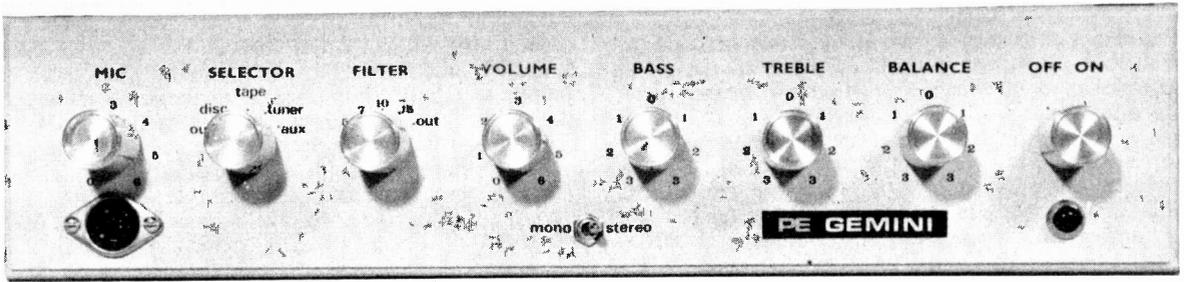

Photograph of the front panel showing control designations

Faulty components are rare, especially if one uses new components of good quality, and if it is found that one of the transistors or diodes is defective after testing the amplifier, make sure that it was not destroyed by a wiring error before replacing it. To avoid expensive accidents great care should be taken to check all the wiring thoroughly before connecting the amplifier to the mains—it will be too late afterwards.

Given time and patience, most faults can be tracked down with a multimeter. An instrument of at least 20,000 ohms per volt is recommended. An oscilloscope

and an audio oscillator can save a lot of time and trouble, particularly with faults such as distortion and oscillation. And if it is required to test the amplifier through its full specification, a wave analyser and a squarewave generator will also be required.

To assist in getting the amplifier to work correctly, a table giving the normal voltages at various points in the circuit, is given on page 212, together with a list of fault symptoms and their most likely causes. This will help to track down most faults with the minimum of trouble, but we can not claim to have thought of everything.

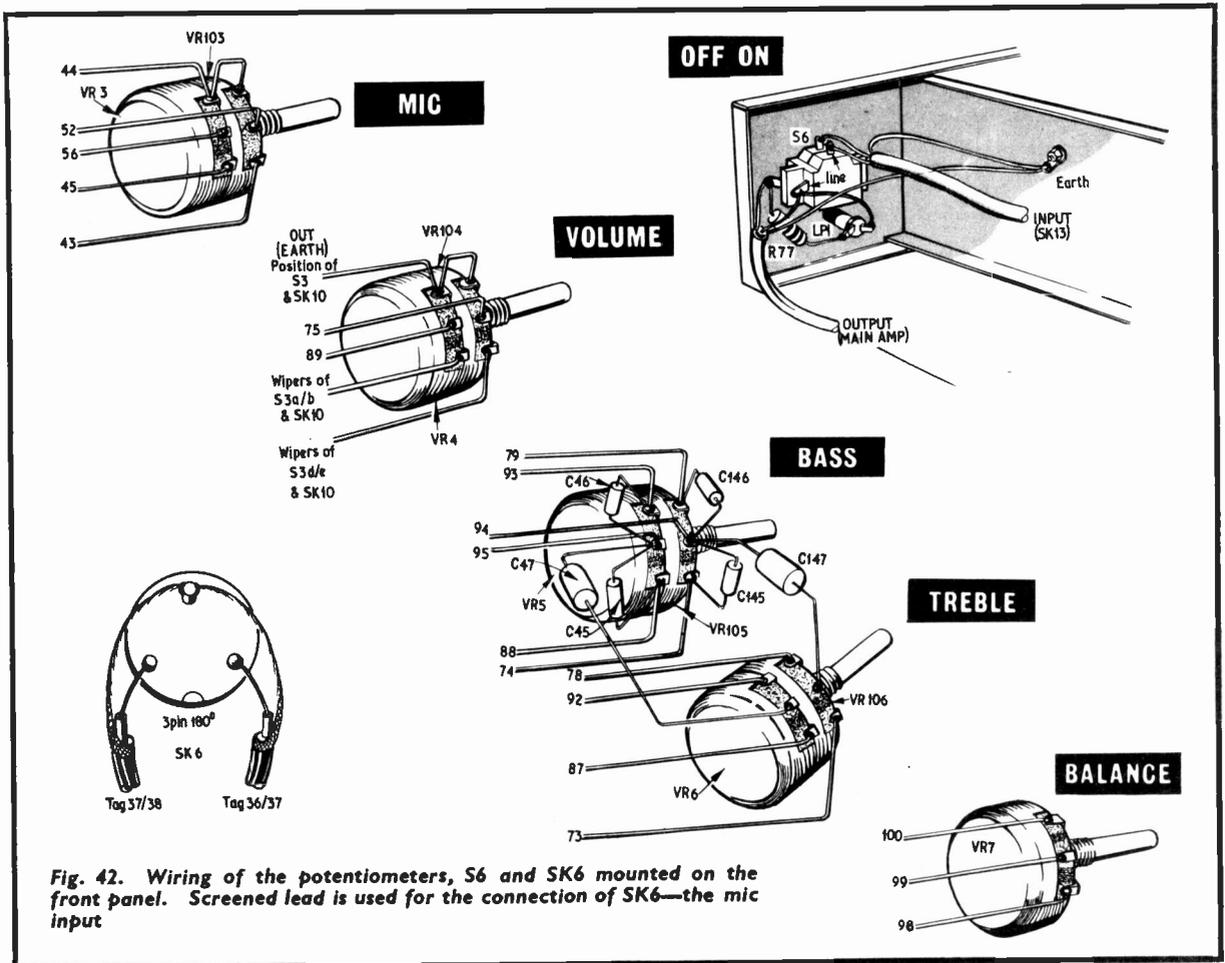


Fig. 42. Wiring of the potentiometers, S6 and SK6 mounted on the front panel. Screened lead is used for the connection of SK6—the mic input

CONNECTING UP

The amplifier is working perfectly, a record deck or f.m. tuner is connected to it; on switching on there is a loud hum on both channels. This happens to nearly every audio enthusiast sooner or later and the usual cause is an earth loop. This arises when both the amplifier and the piece of equipment to which it is connected are earthed separately to the mains. A small a.c. voltage is induced into the earth leads of both units and when they are connected together a 50Hz current flows in the outer braid of the coax cable between them, causing an objectionable hum. The cure is simply to disconnect *one* of the earths, preferably not the amplifier, and so break the loop. The record player deck or f.m. tuner, etc. will then be earthed via the amplifier. Another source of hum arises if the earth connection between the amplifier and the ancillary equipment gets broken whilst still leaving the signal lead (coax inner) connected. This causes a really colossal hum, often accompanied by a chorus of radio stations.

The prototype amplifier did not show any sign of radio breakthrough but if it is to be operated near a

transmitter and breakthrough is experienced, connect a capacitor of 100 to 1,000pF directly between each input and earth, alternatively a ferrite bead may be placed on each of the input leads (directly at the input sockets in both cases). Radio breakthrough can also be a symptom of h.f. oscillation in the circuit.

Supposing the amplifier is working perfectly, but there is only an output from one channel. The first thing to do is to check the wiring of the input plug, especially if using a ready made lead. The P.E. Gemini is wired as Fig. 43a which is the DIN standard for amplifiers but many of the ready made leads, intended for tape recorders, etc. are wired as Fig. 43b.

Low impedance signal sources, such as a tape recorder, f.m. tuner or low impedance dynamic microphone, can be connected up with ordinary twin screened (stereo) cable, but low capacitance screened cable should be used for high impedance sources, particularly magnetic pickups. The popular stereo cable has a capacitance of 100pF or more per foot, and only 4 to 5 feet is required to produce a resonance at 10kHz with a normal 500mH magnetic pickup. Twin lighting flex is quite suitable for connecting up the loudspeakers.

PE GEMINI CHECK CHART

POWER SUPPLY

Normal Voltages (no load)

Across secondary	45-55V (50Hz)
Across C3	65-75V
Across output terminals....	55V
Across D1 and C2	10V
Between 0V rail and TR1 base	9.3V
Across R4	0.7V
Across R5	1.4V

Fault symptoms and possible causes

Output voltage zero

- (1) Fuse blown. Check for cause before replacing.
- (2) Bad contact in mains plug and socket.
- (3) C1 short circuit, or short circuit present across output.
- (4) R6 omitted or open circuit.
- (5) D2, D3, D4, or D5 open circuit.

Output voltage low

- (1) D1 or C2 wrong way round.
- (2) TR1, TR2 or TR3 open circuit or wrongly connected.
- (3) R1 or R2 wrong value.
- (4) Wrong transformer taps connected.

Output voltage high

- (1) D1 omitted or open circuit.
- (2) TR1, TR2 or TR3 short circuit or wrongly connected.
- (3) R1, R2, or R6 wrong value.

IMPORTANT: The power supply should be tested and adjusted to the correct voltage before the ht+ leads to the amplifier are connected.

MAIN AMPLIFIER

Normal Voltages

(Referred to common rail unless otherwise specified.)

H.T. rail	55V d.c.
Output terminal	27.5V
Emitter of TR4	26.7V
Junction of R9 and R10....	26.2V
Base of TR5	0.7V
Collector of TR5	0.5V
Base of TR6	1.3V
Collector of TR6	27V
Across TR7 coll/emitter ...	1-1.5V
Junction of R15 and R16 ..	47V
Across R25 and R26	0.7V

Fault symptoms and possible causes

Voltage at output terminal high

- (1) TR10 or TR12 short circuit or wrongly connected.
- (2) TR4, TR5, TR6, TR11 or TR13 o/c.
- (3) R9, R10 wrong value or R10 o/c.
- (4) C8 s/c or leaky.

Voltage at output terminal low

- (1) TR4, TR5, TR6, TR11 or TR13 s/c or wrongly connected.
- (2) TR10 or TR12 open circuit.
- (3) R9, R10 wrong value or R9 open circuit.
- (4) C6, C7 leaky or short circuit.

Bias current too low

- (1) TR7 short circuit.
- (2) R18 or R19 wrong value.

Bias current too high

- (1) TR7 o/c or wrongly connected.
- (2) R18 or R19 wrong value.

PREAMPLIFIER

Normal Voltages

(Referred to common rail unless otherwise specified)

H.T. rail	40V
Across C16	37.5V
TR14 and TR16 emitters ...	18V
TR15 and TR17 collectors ...	18V
TR15 and TR17 emitters ...	28.5V
TR18 emitter	6.8V
TR19 emitter	24V
TR20 emitter	9V
TR21 emitter	20V

Fault symptoms and possible causes

No output for all inputs

- (1) No h.t., check wiring and C52.
- (2) TR18, 19, 20, or 21 s/c or o/c.
- (3) Wiring error after S3.

Weak distorted output for all inputs

- (1) H.T. voltage excessively low.
- (2) TR18, TR19, TR20, or TR21 inserted wrong way round.
- (3) C33, C48, or C50 leaky or s/c.
- (4) Incorrect resistor value.

No output or weak distorted output on disc

- (1) TR14, TR15 o/c, s/c, or connected wrong way round.
- (2) C17, C18, or C23 leaky.
- (3) Incorrect resistor value.

No output or weak distorted output on Mic

- (1) TR16, TR17 o/c, s/c, or connected wrong way round.
- (2) C25, C27, or C29 leaky.
- (3) Incorrect resistor value.

Add 100 for right-hand channel component numbers o/c = open circuit s/c = short circuit

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC. ● LARGE STOCKS ● NO SURPLUS

BARGAINS IN NEW SEMICONDUCTORS

Many items at new reduced prices. All power types supplied with free insulating sets

2N696	20p	2N2924	80p	40361	55p	BC148	14p	BFX87	29p
2N697	22p	2N2925	80p	40362	55p	BC149	15p	BFX88	29p
2N706	12p	2N2926	11p	AG107	46p	BC153	35p	BFY50	23p
2N930	29p	2N3033	27p	AC126	20p	BC154	38p	BFY51	20p
2N1131	36p	2N3225	54p	AC127	20p	BC157	19p	BFY52	23p
2N1132	40p	2N3702	13p	AC128	20p	BC158	17p	B8X20	16p
2N1302	10p	2N3703	13p	AC153K	25p	BC159	18p	C407	17p
2N1303	18p	2N3704	13p	AC176	27p	BC167	15p	MC140	26p
2N1304	25p	2N3705	13p	ACY20	20p	BC168	11p	MP86531	25p
2N1305	23p	2N3706	13p	ACY22	16p	BC169	13p	MP86534	30p
2N1306	33p	2N3707	13p	AD140	56p	BC177	17p	NKT211	25p
2N1307	33p	2N3708	13p	AD142	71p	BC178	15p	NKT212	25p
2N1308	36p	2N3709	13p	AD149	60p	BC179	17p	NKT214	23p
2N1309	36p	2N3710	13p	AD161	40p	BC182L	13p	NKT274	18p
2N1613	23p	2N3711	13p	AD162	40p	BC185L	11p	NKT403	65p
2N1711	25p	2N3704	15p	AF114	30p	BC184L	15p	NKT405	79p
2N1893	54p	2N3904	15p	AF115	35p	BC212L	25p	OC71	29p
2N2147	95p	2N3906	35p	AF117	28p	BC213L	25p	OC81	29p
2N2218	33p	2N4058	20p	AF124	30p	BC214L	25p	OC81D	17p
2N2218A	43p	2N4059	20p	AF127	28p	BCY70	18p	ZTX300	25p
2N2219	38p	2N4060	20p	AF130	48p	BCY71	33p	ZTX301	17p
2N2219A	53p	2N4061	20p	AF239	49p	BCY72	15p	ZTX302	22p
2N2270	62p	2N4062	20p	ASY26	27p	BF115	38p	ZTX303	22p
2N2369A	19p	2N4124	18p	ASY28	27p	BF167	43p	ZTX304	25p
2N2483	35p	2N4126	27p	BC107	14p	BF173	50p	ZTX500	25p
2N2484	42p	2N4284	15p	BC108	12p	BF194	17p	ZTX501	25p
2N2904	38p	2N4286	15p	BC109	14p	BF195	18p	ZTX502	30p
2N2904A	42p	2N4289	15p	BC125	55p	BFX29	25p	ZTX503	25p
2N2905	44p	2N4291	15p	BC126	55p	BFX84	25p	ZTX504	60p
2N2905A	47p	2N4292	15p	BC147	15p	BFX85	34p		

PEAK SOUND PRODUCTS ENGLEFIELD AMPLIFIER



12 + 12
watts RMS
per channel

Stereo amplifier in modular kit form (including cabinet) 12 watts per channel £38.45. Cabinet kit only £6. These prices net.

BAXANDALL SPEAKER SYSTEM



Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15Ω 50RM109 speaker unit. Kit £13.90 net; built £19.40 net.

MAINLINE AMPLIFIER KITS

RCA/SGS designed main amplifier kits. Input sensitivity 500-700mV for full output into 8Ω.

Power	Kit price	Suitable unreg. power supply kit
12W	£5.40 net	£4.60
25W	£9.50 net	N/A
40W	£10.50 net	£5.75
70W	£12.60 net	£6.94

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220kΩ	E12	7p	6p	6p
C	1W	5%	4.7Ω-330kΩ	E24	1p	0.8p	0.7p
C	1W	10%	4.7Ω-10MΩ	E12	1p	0.8p	0.7p
C	1W	5%	4.7Ω-10MΩ	E24	1.2p	1p	0.9p
C	1W	10%	4.7Ω-10MΩ	E12	2.5p	2.5p	1.9p
MO	1W	±2%	10Ω-1MΩ	E24	4p	3.5p	3p
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7p	7p	6p
WW	3W	5%	12Ω-10kΩ	E12	7p	7p	6p
WW	7W	5%	12Ω-10kΩ	E12	9p	9p	8p

CODES: C = carbon film high stability low noise. MO = metal oxide Electroisol TR5 ultra low noise. WW = wire wound Plessey.

VALUES: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decales. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decales.

Prices are in pence each for same ohmic value and power rating. NOT mixed values. (Ignore fractions of 1p on total resistor order.)

INTEGRATED CIRCUIT AMPLIFIERS

SINGLAI IC10 complete with instruction book giving amplifier circuit details and range of applications. £2.85 net. Components pack for stereo inc. mains transformer, controls, etc., £4.75 net.

PLESSEY 5L40SA. Only £2.75 each net. 3W into 7.5Ω for 18V supply. Application data 10p; free with two or more.

WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W ... 24p each

SLIDER SWITCHES P.D.T.

... 15p each

NEON INDICATOR LAMPS all 200/250V

Square bezel, red only ... 19p
Round chrome bezel, red, amber, clear ... 23p each
Toggle switches, 250V a.c. 1.5A. Chrome dolly and chrome nilled nut S.P.S.T. 19p; S.P.D.T. 22p; D.P.D.T. 28p; S.P.D.T. centre off 26p.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC (70 points) only £1. Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC (208 points) only £2.50. Full range stocked.

MULLARD POLYESTER C280 series

250V 20%, 0.01, 0.022, 0.033, 0.047, 3p ea.; 0.068, 0.1, 0.15, 4p ea.; 0.22, 5p, 10%, 0.33, 7p; 0.47, 8p; 0.68, 11p; 1μF, 13p; 1.5μF, 21p; 2.2μF, 24p.

MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 6p each.
Values (μF/V): 0.61/64, 1/40, 1.6/25, 2.5/16, 2.5/64, 4/10, 4/40, 5/64, 6.4/40, 6.4/25, 8.4, 8/40, 10/25, 10/16, 10/64, 12.5/25, 16/40, 20/16, 20/64, 25/64, 25/25, 32/4, 32/10, 32/40, 32/64, 40/16, 40/25, 50/64, 50/25, 50/40, 64/4, 64/10, 80/25, 80/16, 80/25, 100/64, 125/4, 125/10, 125/16, 160/25, 200/64, 200/10, 250/4, 320/25, 320/64, 400/4, 500/25.

LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 38p; 2000/25 37p; 2000/50 37p; 2500/64 84p; 2500/70 97p; 5000/25 62p; 5000/50 11-10; 5000/100 12-01; 10000/15 85p; 10000/25 11-23.

MEDIUM RANGE ELECTROLYTICS

Axial leads: 30/50 8p; 100/50 12p; 250/25 12p; 330/25 12p; 250/50 19p; 500/25 19p; 500/50 22p; 1000/25 20p; 1000/50 30p; 2000/25 30p.

SMALL ELECTROLYTICS

Axial leads: 4.7/10, 4.7/25, 5/50, 5p ea. 10/10, 10/25, 10/50, 33/10, 50/10, 5p ea. 25/25, 25/50, 47/25, 100/10, 220/10, 6p ea.

ENAMELLED COPPER WIRE even No. SWG

only 2 oz. reels: 16-22 SWG 23p; 24-30 SWG 27p; 32, 34 SWG, 29p; 36, 38 SWG, 34p; 4 oz. reels 16-22 SWG only 41p.

30 WATT BAILEY AMPLIFIER KIT

Sensitivity 1.2V for full output into 8Ω. Transistors and PCB for one channel £7.30. Transistors and PCBs for two channels £14.60. Capacitors and resistors (metal oxide) £2 per channel. Complete unregulated power supply kit £4.78.

ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 19p ea. 1W: 6.8V to 82V 33p ea. 1.5W: 4.7V to 75V 60p ea. Clip to increase 1.5W rating to 3 watts (type 286F) 4p.

CARBON TRACK POTENTIOMETERS, long spindles.

Double wiper ensures minimum noise level.
Single gang linear 220Ω to 2.2MΩ 12p
Single gang log 4.7KΩ to 2.2MΩ 12p
Dual gang linear 4.7KΩ to 2.2MΩ 42p
Dual gang log 4.7MΩ to 2.2MΩ 42p
Log/antilog 10K, 47K, 1MΩ only 42p
Dual antilog 10K only 42p
Any type with 1A D.P. mains switch, extra 12p.
Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting 5p each.

TYGON SPEAKER MATERIAL

Seven designs, 36in x 27in sheets, £1.57. Pattern books, send S.A.E. plus 3p in stamps.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over £2. Please add 10p if under. Overseas orders welcome: carriage charged at cost.

IMPORTANT—Please ensure that cheques dated on and after February 16th are drawn in declinal currency. Otherwise they will not be accepted.

ELECTROVALUE

Dept. PE371, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9—5.30; Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3). Telex 264475

NEW FROM TRS

This money saving **STEREO 8 + 8 AMPLIFIER**
in a new **PRE-ASSEMBLED MODULAR PRESENTATION**

A new conception in modular assembly which makes construction even easier than ever and results even better. Two pre-amp and two power amp modules, factory built, tested and guaranteed by a world famous maker come to you ready mounted with mains power unit on chassis forming part of the attractive TRS cabinet and simply need wiring for immediate use. A generous 8 watt RMS output per channel into 3-5 ohms is assured. Cabinet with aluminium front, charcoal grey top and wood sides measures 12in x 8½in x 2½in.

- Frequency resp.: 50Hz-16kHz ±3dB.
- Input: 110mV per P.U., radio 240mV.
- Output: 8W per channel. RMS into 3-5Ω. Slightly less per 8-15Ω speakers.
- Record and playback facilities (via external tape pre-amp).
- Bass/Treble/Volume/Balance /Input/On-off controls.



Complete kit assembled ready to wire up with mains lead and instructions. Unsurpassed value at only

£17.50

Carriage and packing 38p in U.K.

Descriptive leaflet on request. AVAILABLE SHORTLY—Speaker and Cabinet assembly. Comprising 8in unit and flat-pack cabinet, size 18in x 12in x 10in—Anticipated prices £5.50.

COMPONENTS CORNER

VYNAIR speaker and cabinet covering by ICI. Send 5p for samples—refundable on purchase. 12½p per sq.ft. £1.38 per yd. 48in wide.

BONDACOUST speaker wadding 1in thick, 18in wide, per yard 42½p.

VEROBOARD in all latest sizes and forms. inc. 2½in x 3½in, 16p; 2½in x 5in or 3½in x 3½in, 23p; 3½in x 5in, 21p; 17in x 3½in, 75p.

VOLUME CONTROLS. Long spindles all values 5Kohms to 2meg., log or lin., less switch 17½p; with switch 25p.

Twin gauged stereo, 5K to 2meg. less switch, 48p; with switch 100K to 2meg. 52p.

STEREO BALANCE CONTROLS. Log/ Anti-log 5K, 10K, ½, 1 or 2meg., 52p.

RESISTORS, CAPACITORS, WIRE, etc., etc.

MORE AMPLIFIERS FROM TRS

MULLARD VALVE AMPLIFIERS

- 5-10 basic kit (mono) £10.99. Carr. 28p.
- 2 valve mono pre-amp basic kit for above £7.65. Carr. 28p.
- 10-10 stereo amplifier kit £18.99. Carr. 63p.

TRS 50 WATT VALVE AMPLIFIER

A ruggedly built unit in ventilated steel case with carrying handles: size 12in x 8in x 8in. Two input channels mixable (10mV and 150mV) bass and treble controls. EL 34's output (mono) in push-pull, with fixed bias. Excellent for P.A., musical group work, etc. Brand new and guaranteed £30. Carriage 75p.

FOR YOUR STEREO 8+8 OR OTHER HI-FI SYSTEMS


Plinth and motor assembly comprising modern style teak finished plinth cut to take famous Garrard AT6 auto/single playing unit wired for stereo, with hard smoke grey perspex lid, Plinth and AT6 less cartridge £12.50 (Carr. and packing 53p).

SPECIAL CARTRIDGE OFFER TO PURCHASERS OF ABOVE ONLY

Acos stereo 6P93-1 (sapphire) £1.25.
Sonotone 9TA/HC (diamond) £2.
Shure M.94 (Mag., diamond) £3.50.
Mag. P.U. requires special pre-amp if used with 8+8.

TRS RADIO COMPONENT SPECIALISTS
70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY
Tel. 01-654 2188

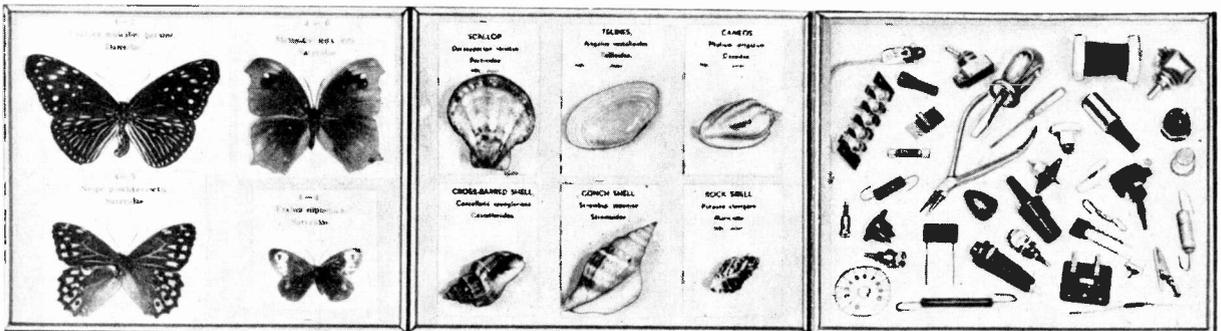Open all day Sats., Weds.—1 p.m. Almost next to Thornton Heath Stn. (S.R.)



SORRY we can't help you with your collection of Coins, Butterflies, shells, etc. . . .

We realise of course that you don't want components for displaying in a case, but for putting to good use in your latest radio or electronic project. You want to be able to get just what you need quickly and easily, preferably from a single supplier. That's where the **Home Radio Components Catalogue** comes to your aid.

In its pages are listed over 8,000 items, more than 1,500 of them illustrated. A cross-referenced index makes it simplicity itself to find just the parts you need, and the Price Supplement puts you in the picture price-wise. On receipt of your written or telephoned order we despatch your components by return post. The catalogue is yours for only 62½p. (42½p plus 20p post and packing). Wonderful value, especially as every copy contains six vouchers, each worth 5p when used as directed.

POST THE COUPON with your cheque or P.O. for 62½p
The price of 62½p applies only to catalogues purchased by U.K. customers.

BUT when it comes to **ELECTRONIC COMPONENTS** we certainly can!


Please write Name and Address in block capitals

Name

Address



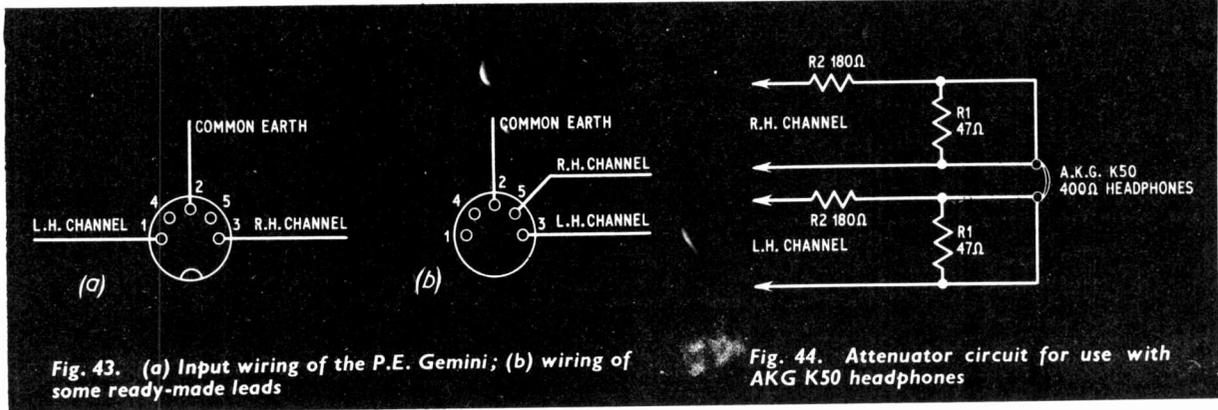HOME RADIO (Components) LTD.
Dept. PE, 234-240 London Road, Mitcham CR4 3HD



TAPE INPUT

The tape input of the P.E. Gemini preamplifier has a flat frequency response and a sensitivity of 100mV at 50 kilohms, suitable for connection to the equalised output of a tape recorder or tape unit. The input is like this to accommodate the wide choice of speeds and equalisation standards (DIN, CCIR, and NAB at 15, 7½, 3¾, 1⅞ i.p.s.) many extra components and some complicated wiring and switching would be needed. If the low level output of your tape recorder is not equalised you will have to construct an "add on" equalisation stage to give an output of 100mV.

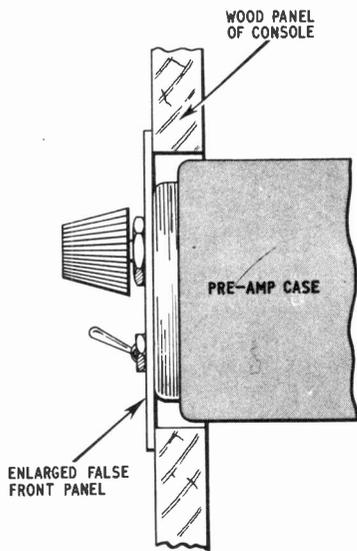


Fig. 45. Method of mounting the pre-amplifier in a console

HEADPHONE OUTPUT

The headphone output from the main amplifier is connected directly to the loudspeaker outputs and in most cases it will be necessary for the constructor to add an attenuator to reduce the volume to a comfortable level. Because of the wide variation in headphone impedances (4 to 600 ohms) and sensitivity between different types, the constructor will have to determine the correct values experimentally; Fig. 44 shows the circuit used, the values given being suitable for AKG K50 headphones of 400 ohms impedance. Resistor R1 should not be greater than the impedance of the earpiece and (R1 + R2) should not be less than 15 ohms, and preferably greater than 100 ohms if the attenuator is permanently wired to the amplifier. Some headphones have a built in attenuator and these can be connected directly to the headphone output socket.


CASES

The Contil Mod 2 cases, used for both units, were chosen because they are relatively cheap, easily obtainable, and have an attractive if somewhat functional appearance. There is no reason why the constructor should not design his own case to match other equipment, provided that the case is well screened and the layout given is closely adhered to.

The preamplifier may be mounted in a console by increasing the size of the front panel so that it covers the hole required, as shown in Fig. 45. The front panel can be secured by screws from the front or clamps behind the panel. ★

ACKNOWLEDGEMENTS

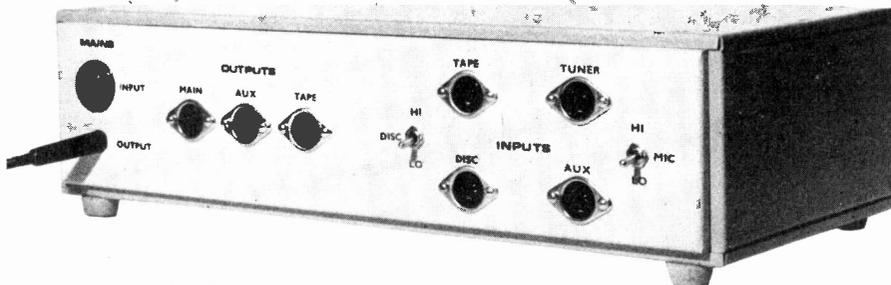The authors wish to thank Ferranti Ltd. for permission to publish this article and also L. Morral, R. J. Grundy and M. A. Rambaut for help given at various stages of the construction of the P.E. Gemini Amplifier.



Note: In Fig. 14 the arrow from tag 24 should go to FS2 not FS1. Main amplifier components list—R12 and R112 should be 1.2kΩ not 1kΩ.

DIGI-CLOCK

By R. W. Coles

Part 4

AS MENTIONED in the first part of this article, "Contil" Mod-2 case type "C" is used to house the Digi-Clock, and this makes construction much simpler than if a "one-off" case design were to be employed.

The front and back panels of these cases are formed from p.v.c. covered aluminium, which makes the necessary hole cutting quite easy. The only tools absolutely necessary are a hand drill and a good file, but a clean and neat finish can be more easily achieved with a nibbling tool such as the "Monodex" sheet metal cutter.

CONSTRUCTION ON CHASSIS

The chassis supplied with the case is also made of aluminium and is used as a base-plate for all the main components, including the three circuit boards which are spaced from it only by three 6BA nuts. The chassis is earthed and acts as a low impedance "ground plane" for the logic circuitry, thus increasing the noise immunity of the system.


The series pass transistor TR2 employed by the 5V regulator uses the chassis as a heat sink; it is vital that this transistor is isolated from the aluminium by an insulating mica washer of the type normally supplied with this type of device.

Drilling dimensions for the chassis and front and back panels are given in the diagrams, and it is important to remember that some of the chassis holes are required to match other holes drilled by the constructor in the circuit boards and the display panel bracket. It is preferable to match these chassis holes to the latter, rather than drill all the holes straight from the diagrams.

The mounting bracket for the "Nixie" tubes is made from $\frac{1}{8}$ in s.r.b.p. sheet, and as can be seen from the diagram, the tubes are inserted directly into holes drilled in this bracket, no bases being employed.

With the dimensions given, the tubes are a tight fit in their mountings, and no extra fixative was used in the prototype. A dab of contact adhesive could be used if necessary, and still allow the tubes to be removed should this ever be desirable. Valve bases type B12A are available for the GN5A although the numeral spacing would have to be altered if these are used, since the tubes would not be so close together.

The decimal point indicator is mounted in a $\frac{3}{8}$ in coil former or some other suitable tube, cut to the dimensions shown, and fastened to the display panel with contact adhesive. When being installed, the neon is simply pushed through from the rear of the bracket, its insulated leads providing all the tension necessary to retain it in the tube.

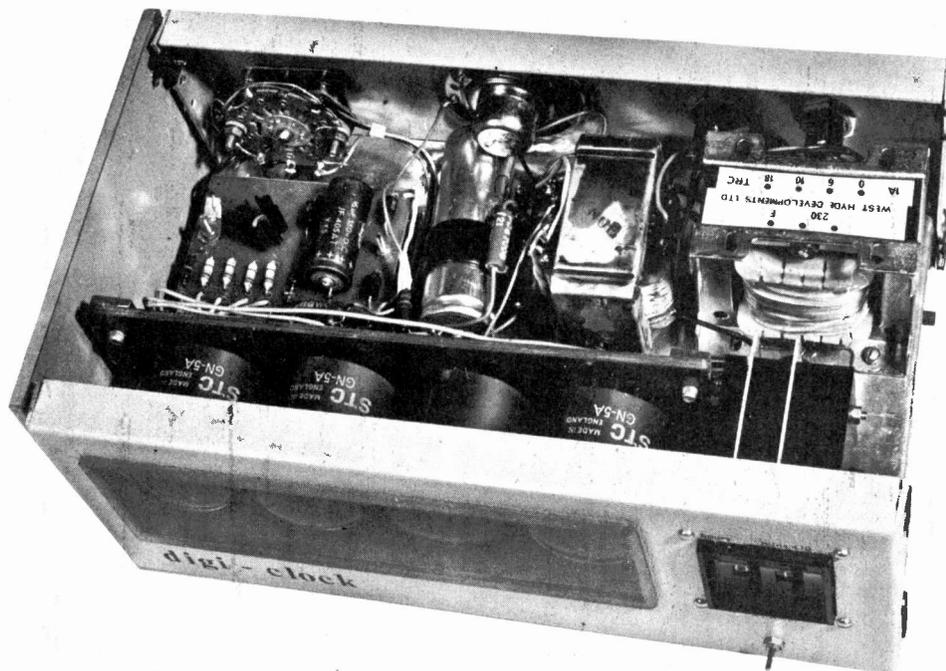

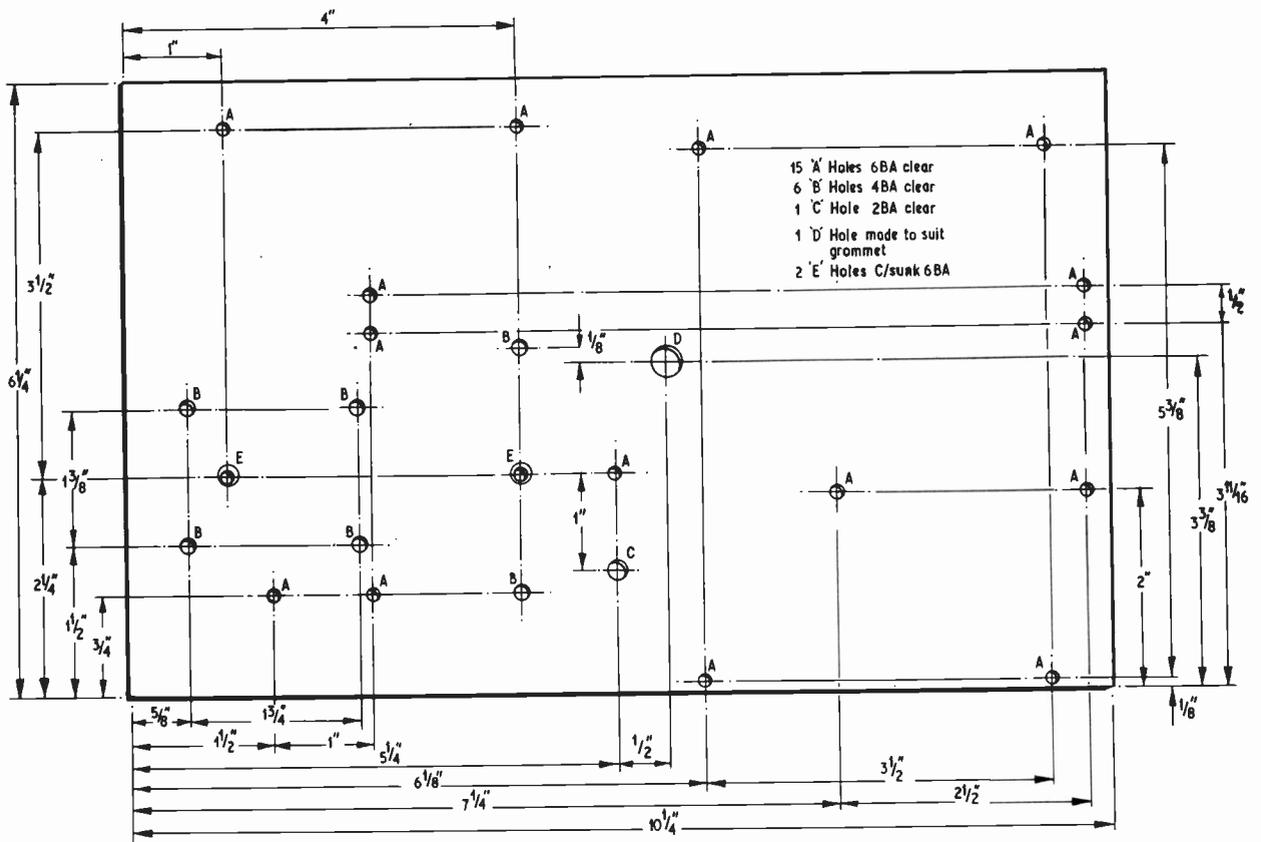


Fig. 17. Chassis drilling details assuming components used are as specified in the components list. Modifications may be necessary for variations of component type. Clearance above chassis $2\frac{3}{4}$ in

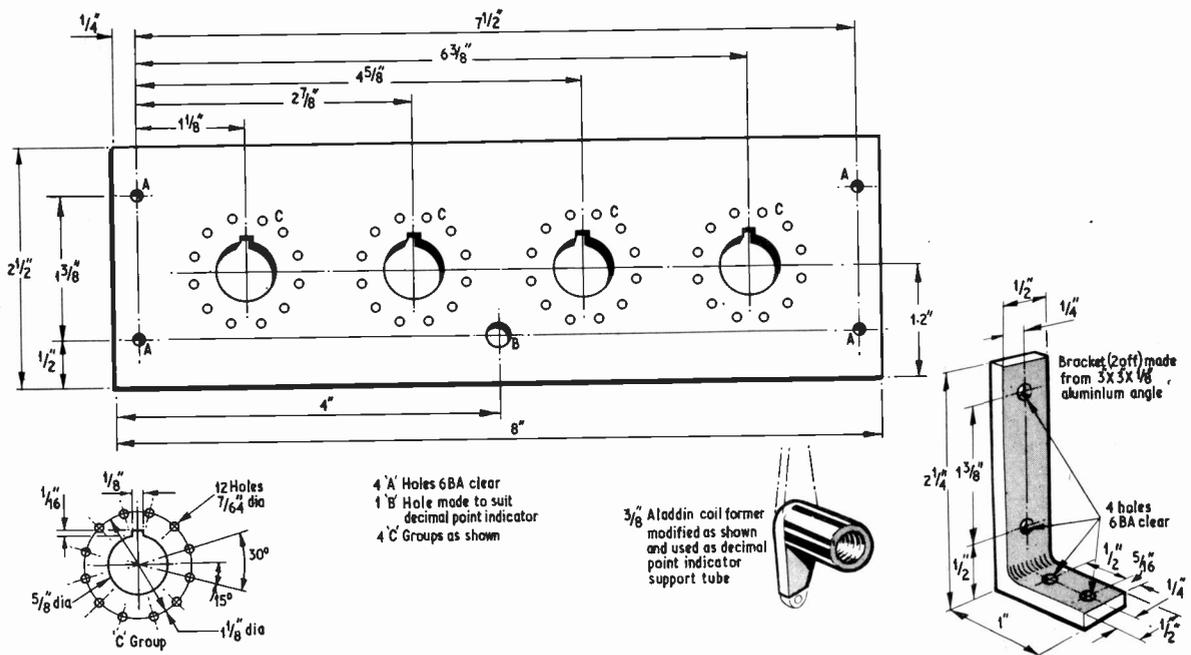


Fig. 18. Display panel drilling for "Nixie" tubes

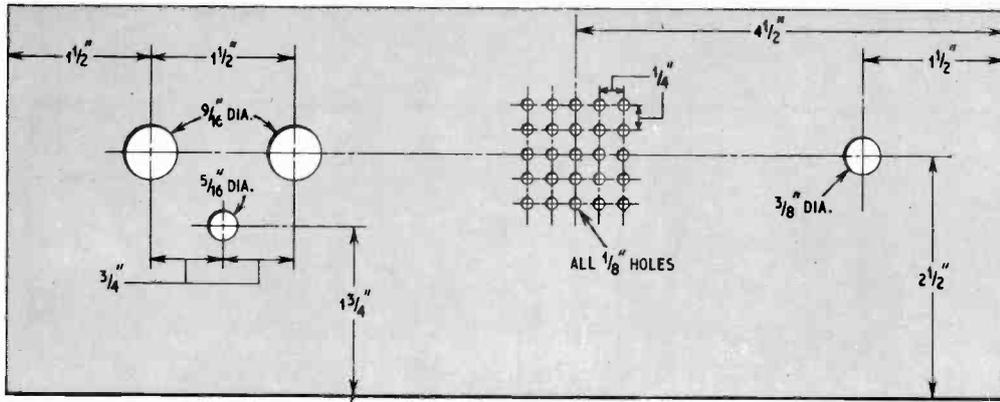


Fig. 19. Back panel drilling details for components specified

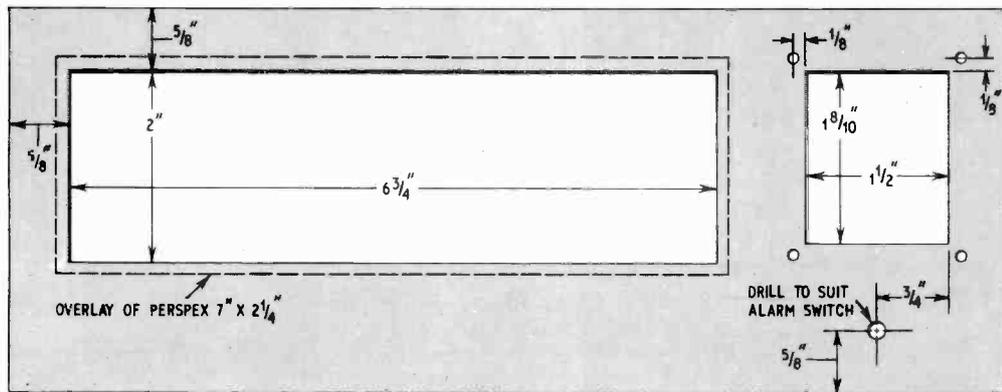


Fig. 20. Front panel drilling details for components specified

Table 1: CONNECTIONS TO MAIN CLOCK BOARD "A"

(a) Plain side terminations

IC Number	Hole Number	Board "A" Outlet	Wire Colour	Destination
—Resistor R1—				
1	6E	1	green	T2, 6.3V
6	2E	2	black	S1a wiper
6	6A	3	red	S1c wiper
13	4F	4	orange	S1b wiper
13	3C	5	red	Board B5
13	3B	6	orange	Board B4
9	2H	7	pink	Board B3
12	3E	8	violet	Board B1
9	2F	9	green	Board B9
ALL	Ground Rail	10	blue	Board B13
ALL	+V _{cc} rail	11	black	chassis
11	7G	12	red	Board B12
13	6H	13	brown	Board B10
13	6G	14	yellow	Board B2
13	3A	15	yellow	(optional hours × 10 zero line to V1 pin 10)
13	6A	16	yellow	V1 pin 1
13	7E	17	grey	V3 pin 10
13	6A	18	pink	V3 pin 1
13	7E	19	white	V3 pin 2
13	6A	20	violet	V3 pin 3
13	7E	21	yellow	V3 pin 4
13	6F	22	green	V3 pin 5

(b) Copper side terminations

IC Number	Hole Number	Board "A" Outlet	Wire Colour	Destination
—	—	23	—	—
—	—	24	—	—
14	6H	25	pink	V4 pin 10
14	6G	26	green	V4 pin 1
14	2A	27	red	V4 pin 2
14	6A	28	brown	V4 pin 3
14	6E	29	black	V4 pin 4
14	6F	30	white	V4 pin 5
14	6C	31	yellow	V4 pin 6
14	6B	32	orange	V4 pin 7
14	2H	33	grey	V4 pin 8
14	2G	34	violet	V4 pin 9
12	6H	34	orange	V2 pin 1
12	7G	36	green	V2 pin 2
12	2A	37	grey	V2 pin 3
12	7A	38	brown	V2 pin 4
12	7E	39	pink	V2 pin 5
12	7F	40	yellow	V2 pin 6
12	7C	41	red	V2 pin 7
12	7B	42	black	V2 pin 8
12	2H	43	white	V2 pin 9
12	2G	44	violet	V2 pin 10

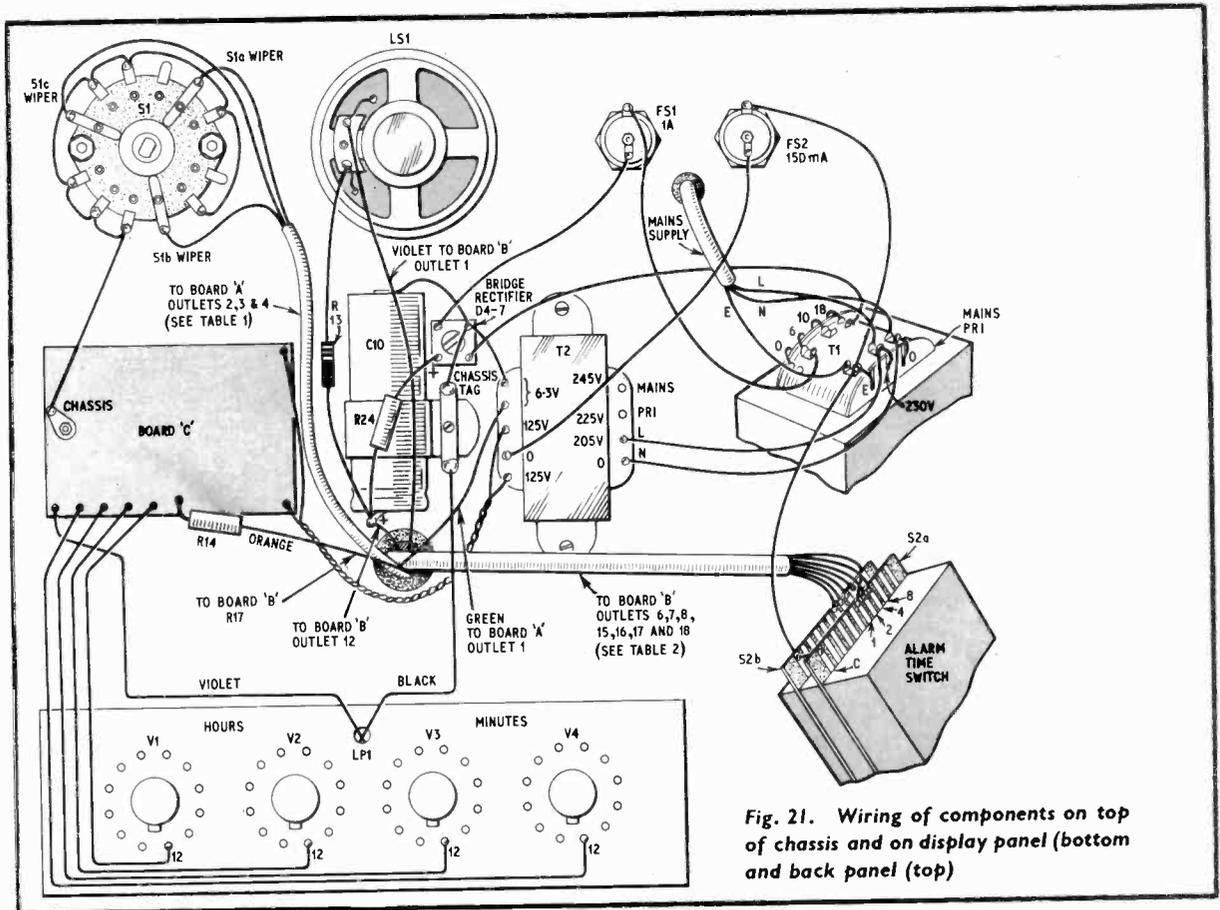


Fig. 21. Wiring of components on top of chassis and on display panel (bottom and back panel (top))

Table 2: CONNECTIONS TO ALARM BOARD "B"
Copper side terminations only

IC Number	Hole Number	Board "B" Outlet	Wire Colour	Destination
19	7D	1	violet	LS1
15	3H	2	yellow	Board A14
15	3F	3	pink	Board A7
15	3A	4	orange	Board A6
15	7B	5	red	Board A5
15	3E	6	black	S2a/4
15	3B	7	violet	S2a/2
15	6C	8	brown	S2a/1
16	2H	9	green	Board A9
16	3F	10	brown	Board A13
ALL	Ground Rail	11	black	chassis
ALL	+V _{cc} rail	12	red	Board A12 (5V)
16	2A	13	blue	Board A10
16	6B	14	violet	Board A8
16	6H	15	orange	S2b/8
16	3E	16	grey	S2b/4
16	3B	17	red	S2b/2
16	6C	18	blue	S2b/1
18	6D	19	orange	S3 (OFF)
(collector of TR1)		20	red	TR2 collector, (10V).
Resistor R21, 22	4B	21	yellow	TR2 emitter
(TR1 emitter)	3F	22	green	TR2 base

PRINTED BOARDS "A" AND "B"

The circuit boards carrying the i.c.s are mounted on the chassis by means of 6BA bolts passing through each corner. Remember that the printed sides of these boards are adjacent to the chassis in the final assembly, and it will be necessary to make breaks in some cases in the printed tracks near the corner holes to prevent shorts to the chassis via the spacer nuts. Any breaks made for this purpose must be reconnected with wire links on the wiring side of the board.


Note that in Fig. 13 last month C8 should be connected to the link wire to C7 and pin 4 of IC19.

Using 1in long bolts at the board corners allows their use as "legs" to support the chassis during wiring up, damage to the delicate boards being avoided. The transformers perform a similar task on the other side of the chassis.

WIRING UP

Once all the major components have been mounted on the chassis and the circuit boards have been tested for accuracy of fit, wiring up of the power supplies can be carried out. There is no need to attach the back panel wiring permanently at this stage, although it should be hooked in temporarily while the power supplies are tested, before proceeding further.

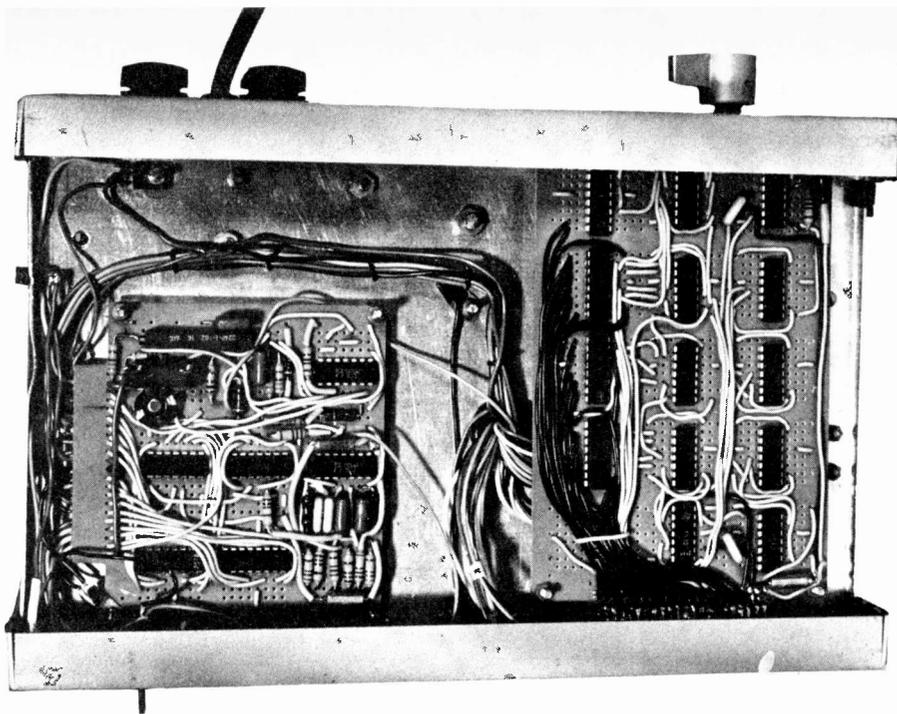When the power supplies are operating satisfactorily, the interboard wiring can be started, remembering that the 5V regulator board has two wires leaving it which do not pass through the edge connector. All connections are given in Tables 1 and 2 for the boards



carrying the i.c.s. It is most important that only very fine p.v.c. covered flexible wire be used for this stage of the wiring, no other type of wire is suitable, as will become obvious as you proceed to wire up the Main Clock Board "A" edge connector with its 42 connections.

On completion of the interboard wiring the front and rear panels and their associated components can be attached to the chassis and the wiring finished off. The alarm speaker should be glued carefully to the rear panel with contact adhesive, making sure that it does not foul the smoothing capacitor or bridge rectifier wiring. The orange tinted Perspex filter is also fixed to the outside of the "Nixie" window front-panel cut-out with contact adhesive, and of course it is important that this operation be carried out with care to ensure a neat appearance.

The front and rear panels are finished off with "Letra-set" dry print transfer lettering. The lettering should be sprayed with clear lacquer fixative to avoid damage during handling.

TESTING

There are no controls on the Digi-Clock which have to be set-up before operation, except the voltage control on the 5V regulator which should be set-up when the regulator wiring is completed, before its connection to the V_{cc} lines to the i.c. boards. This control setting should be rechecked with the clock operating normally, to ensure that the 5V line is as accurate as possible.

If on switching on for the first time, all appears healthy, the set-time switch may be used to set the display to the correct time.

With the switch set to the "fast" position, the minutes counter will be counting 600 times faster than normal, making it a simple job to set the display to within about 15 minutes of the correct time. The slow position is then used to facilitate the final setting, a minute being clocked up every second. As soon as the display is correct the switch is returned to the "normal" position, and the clock continues normally.

If all is still well, the alarm circuit can now be checked. With the alarm "reset" switch in the "off" position, any valid time may be entered on the thumbwheel switches, after which the "alarm reset" switch is returned to the "set" state. When the "hours" and "tens of minutes" display counts to the same time as the alarm setting, the alarm should sound, and may be silenced by returning the "reset" switch to the "off" position. This check can be carried out with the clock running at a fast speed, making it a quick job to test all the alarm settings.

FAULT LOCATION

If problems are encountered during any of these tests, a constructor who has become familiar with the logic of the Digi-Clock should find it a fairly simple matter to trouble-shoot with the aid of a logic probe such as that shown in Fig. 22 or even a multimeter set to the low voltage range.

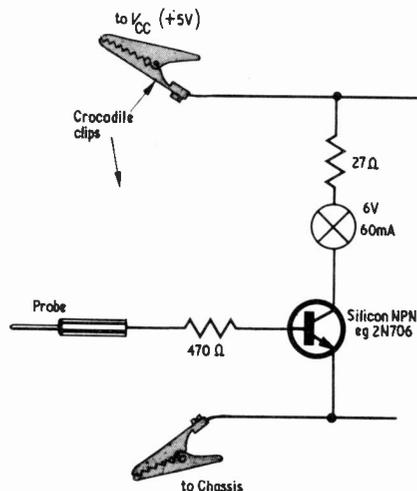


Fig. 22. Simple test circuit or logic probe

The important thing to remember if a fault is present in the logic circuitry, is that ten minutes working out what could be the problem with a pencil and paper, is worth hours of aimless probing and measuring. Logic faults, providing they have symptoms observable through the display, are not hard to find because they always follow some form of sequence, which, when analysed, usually yields the answer, without any testing in the usual sense.

One of the easiest faults to occur is the incorrect sequence of time indication, possibly with more than one digit showing on one tube. In this case, check that there are no short circuits or solder runs between adjacent outlets on the Main Clock Board "A". If erroneous alarm triggering should occur, check for a similar fault on the Alarm Board "B". Also make sure that the copper strips are cut correctly as shown at "X" in the first photograph (last month).

Check for solder runs between adjacent strips of copper; where these should not occur remove the solder. The wiring diagrams in Figs. 5 and 13 show the only places where these may occur intentionally.

The wiring tables and diagrams give colours to the wires as they were in the prototype. There is no reason why these should not be changed, but they are given to help the constructor to follow the wiring through if a fault is apparent.

TENS OF HOURS DISPLAY

Readers may have noticed that in the block diagram given in part one of this project, the tens of hours "Nixie" has two connections to its cathodes, one being a dotted line to the "0" numeral. This connection was shown in this way because it is a matter of personal taste whether the "0" needs to be used at all, a more conventional readout being given by allowing this tube to be completely blank during the hours of one to nine o'clock.

The decoder is, of course, able to accommodate either method, and the wiring diagram given in part one includes an edge connector contact for the "0" at outlet 15 of Board "A" so that it can be wired up if desired. This would be connected to pin 10 of V1.

MODIFICATIONS

Apart from the alarm expansion scheme discussed in Part 2, many other improvements can be incorporated in the Digi-Clock if required. The operation of the clock counters could be altered to conform to the 24 hour system, counting could be extended to include an a.m./p.m. flip-flop, or even a calendar, provided the extra components required could be accommodated.

A slave display, or even several slave displays, could be driven by the basic circuit. In this case the outputs of the clock counters should be buffered by TTL gates or inverters and fed to lines which terminate in further buffers at the slave end.

Fairly long lines could be driven by this method because of the slow speed operation and the relative unimportance of noise at this end of the system. The slave units would consist of a few buffer gates as mentioned and four SN7441AN decoders to drive the "Nixies". A simple power supply would also be needed.

Finally, for anyone who finds the fairly high outlay on the Digi-Clock components unjustifiable, the master-slaves system might tip the balance, because this type of system would become more economic as more slaves were added. ★



SOUND CONTROLLED LIGHT DISPLAY

Following its recent success at the Audio & Music Fair, Practical Electronics now presents the full do-it-yourself details of this fascinating addition to the sound scene. Part one of this series appears in the April issue.

P.E. Aurora is a controlled colour light display system which can be fed from any audio amplifier to provide the appropriate mood setting in the home or discotheque. It will respond to serious music or pop and can be arranged to give random displays from a digital sequencer.


Also:

- ★ BOAT SPEED INDICATOR
- ★ DOOR YODELLER

PRACTICAL
ELECTRONICS

APRIL ISSUE ON SALE
MARCH 19

SIMPLE REFLEX RECEIVER

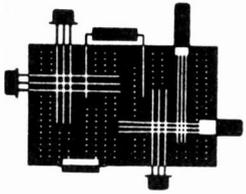

**A SPECIAL
PROJECT FOR
BEGINNERS**

RECEIVER

THE crystal receiver has for a long time been for many their first introduction to table top electronics. It isn't difficult to seek out the reason for its appeal, for this first-time project can be an unending source of entertainment pleasure for a modest outlay.

For the T-Dec form of plug-in construction that has been maintained throughout this series, the choice of receiver circuit was based on the requirements of good stability, that is no "howls" or unwelcome oscillations, and excellent volume with little aerial and no earth in areas of good signal strength.

REFLEX ACTION

Radio signals are characteristically of high frequency. For the medium wave-band which this receiver will tune to, this covers the range from 500 to 1,500kHz (200 to 600 metres).

Since many transmitters are sending out signals in this band, the receiver must be able to select the one required. In the block diagram of the receiver Fig. 1, the tuned circuit enables such selection to be made.

Since the currents generated in the aerial system are extremely weak, it is necessary to amplify them before they reach the diode detector.

The detector has the job of removing the desired audio signal from the high frequency signal which has, in effect, carried it pick-a-back from the transmitter.

The title of the circuit, "reflex", derives from what now follows. Audio output from the detector is reflected back through the r.f. amplifier so that this stage plays a dual role in boosting first the r.f. and then the extracted a.f. signals.

The output is taken through a further amplifying stage and then to the headphones.

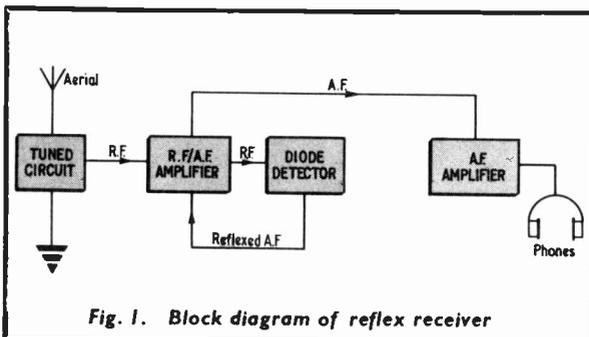


Fig. 1. Block diagram of reflex receiver

RECEIVER CIRCUIT

The complete receiver circuit diagram is given in Fig. 2. Here the tuned circuit consists of T1 primary and TC1. An aerial coupling capacitor C1 is included to improve selectivity; however, it must be borne in mind that with this simple type of single tuned circuit receiver, station separation is not ideal since it follows that the more tuned circuits used, the sharper is the tuning of that receiver.

The coils of the aerial transformer are wound on a ferrite slab which has the capacity to concentrate r.f. energy in its length and so improve signal strength. In areas where signals are very strong, it may be possible to dispense with a wire aerial and earth provided the slab aerial is orientated for maximum signal.

CHOKES

The selected r.f. signal voltage is passed to the base of TR1 by transformer action. Biasing of this amplifier is achieved by R1, R2 and R4.

The low level signal appears amplified at the collector but at this juncture it is faced with two routes to follow. The choke L1 offers a high impedance path to radio frequency signal current whilst C3 does not. Signal voltages developed across L2 are applied to the detector D1, the desired audio programme material is then "unloaded" from the r.f. carrier and passed back to the input of TR1, via C6.

The audio signal is amplified and passed directly to the load resistor R3 since at low frequencies the resistance of the choke L1 is small. The capacitor C5 passes this a.f. signal to a second amplifier stage, TR2, which provides the power for the headset.

SETTING UP

Providing the component layout of Fig. 3 is adhered to, no reception problems should be encountered.

Whilst this receiver will give a good account of itself even with a short length of wire connected to C1, a good aerial will increase the sensitivity enormously in areas of difficult reception.

To demonstrate the effectiveness of a fair sized aerial, try connecting the co-axial outer of the television aerial to C1, after first removing it from the set. Crocodile clips can be used for this. Bedtime listeners will find the bedsprings a convenient aerial, here once again, a crocodile clip will prove a suitable connector.

In general, at medium wavelengths, the receiving aerial takes the form of a vertical wire length, a common variant includes a horizontal top section of a few metres, but this sort of receptor would only be justified with the most elementary of crystal receivers.

SPANNING THE BAND

To cover the medium waveband, it may be necessary to adjust the aerial coils on the ferrite slab. This merely involves moving the coil former until, say, Radios 1 to 4 can be tuned using TC1.



COMPONENTS . . .

Resistors

- R1 20k Ω
- R2 3.9k Ω
- R3 6.8k Ω
- R4 4.7k Ω
- R5 27k Ω
- R6 10k Ω
- R7 3.3k Ω
- All $\pm 10\%$, $\frac{1}{4}$ watt carbon

Capacitors

- C1 100pF
- C2 0.01 μ F
- C3 0.001 μ F
- C4 25 μ F elect. 6V
- C5 10 μ F elect. 15V
- C6 8 μ F elect. 15V
- C7 0.01 μ F
- C8 25 μ F elect. 6V

Transistors

- TR1 OC44
- TR2 AC126

Diodes

- D1 1GPI0
or OA81 (germanium)

Aerial Transformer

- T1 FS3 Ferrite slab aerial
(G. W. Smith & Co. (Radio) Ltd)

Inductors

- L1, L2 1.5mH r.f. chokes (2 off)

Tuning Capacitor

- TC1 208pF variable

Miscellaneous

- X1 High impedance
headphones
or earpiece,
- BY1 9 volt battery
T-Dec, wire links

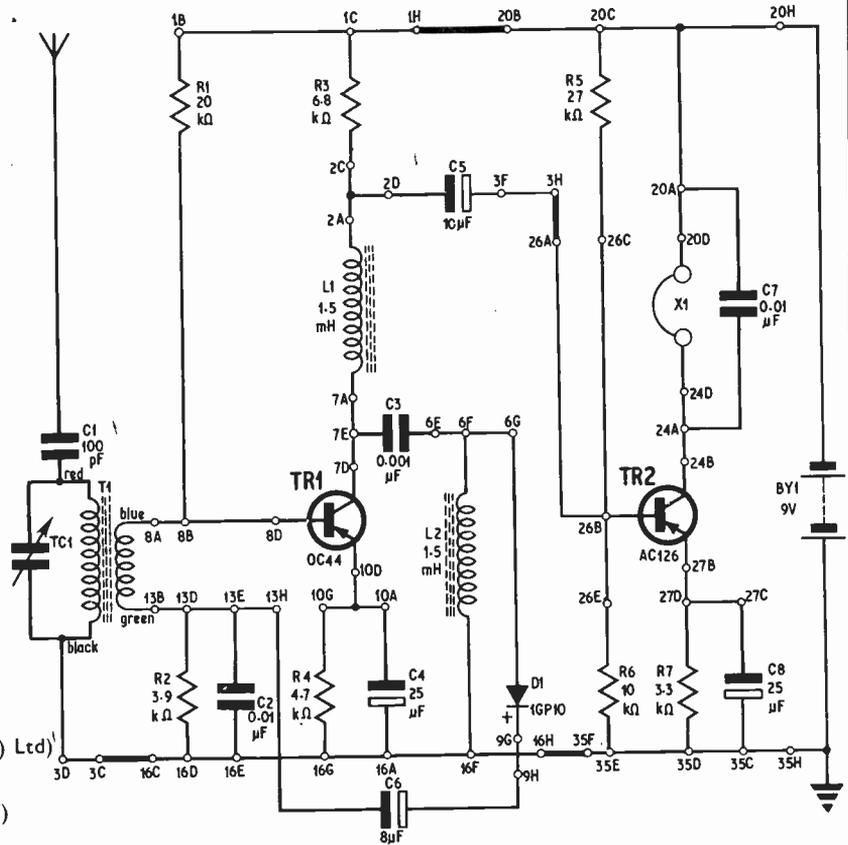


Fig. 2. Circuit diagram showing T-Dec connections. Thick lines indicate wire links

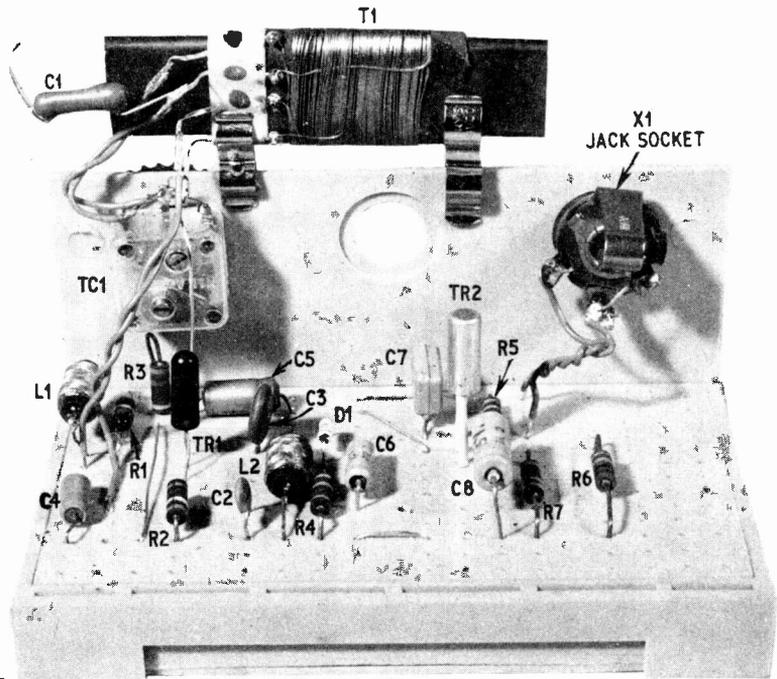


Fig. 3. Component layout on T-Dec. Small Terry clips connected back-to-back are used for aerial retention



Racing Car Data Display

MINIATURE, battery powered transmitters, fitted to the sides of racing cars, are being used for the first time in America, to increase spectator interest. They give instant, continued information on the position of every car on the track.

Underground sensors at the track—Ontario Motor Speedway, California—enable the transmitters accurately to “fix” the car’s position at all stages of a race. The transmitters feed this information direct to a computer which evaluates it, prints out the race order, and relays the race data direct to visual displays on three 60 foot pylons.

The radio transmitters used in this revolutionary scoring system rely upon the power provided by four 1.5V Mallory alkaline batteries (left).

The innovation has proved so popular with spectators that the track organisers now plan to install an additional and even more sophisticated display—a mammoth animated sign which gives times, laps, car numbers and other digital information.

Unfortunately electronics does not always keep everybody happy. Used on the race track it has information and entertainment value and probably upsets or inconveniences nobody, however a slightly different application—still relating to cars—and many motorists get hot under the collar and start writing letters to magazines and the police about unfair and unashamed trickery. The application is of course the radar speed meter and no doubt many readers will be interested to know that an improved version has recently been announced by Shorrock Developments Ltd., part of the Hawker Siddeley Group Ltd. (see below).

Above: A transmitter being fitted to a racing car
Below: One of the 60 foot display pylons

ELECTRONORAM




New Sh(orr)ock for Fast Drivers

The Shorrock microwave radar meter has two advantages over equipment at present used by the police: firstly, it is about two-thirds cheaper; and, secondly, it is much less obtrusive.

The Shorrock equipment is contained in a standard document case, weighing 20lb (9kg) complete. For use, the radar head is left at the roadside and a cable is run to the document case which can be used from a car parked in a side turning or other comfortable site. Power is provided by two 9V dry batteries and calibration can be carried out using the tuning fork provided.

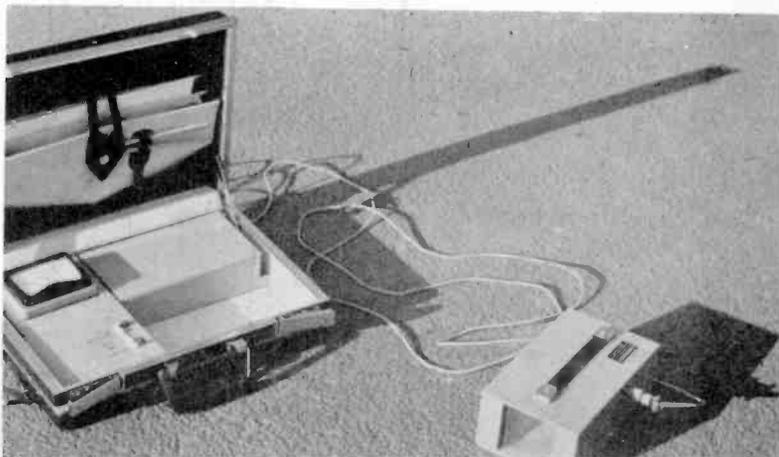More than 40 county authorities are using Shorrock speed indication equipment and police forces are showing interest in it.






Quietened noise on Musicassettes

DECCA 8-track stereo Musicassettes are now in full production at the Company's own factory at Bridgnorth and made exclusively from master tapes utilising the Dolby "A" noise reduction system which produces a significantly improved signal to noise ratio. It is claimed that these Musicassettes offer the best quality of sound now available on this format and that this single factor will be one of the most significant selling points.

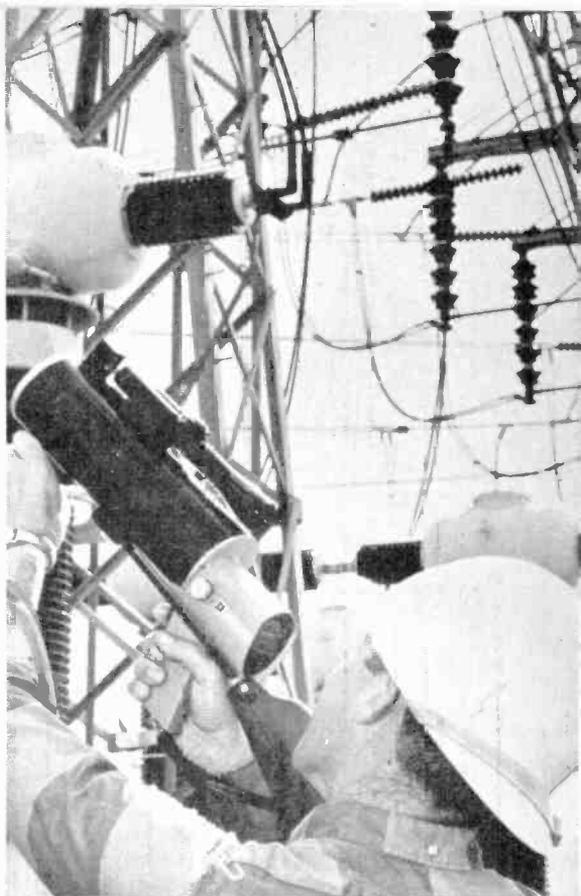The tape duplicating equipment consists of two mother reproducers (also known as "master machines"), two loop bins and 13 slave recorders. One mother reproducer and loop bin is seen in the foreground of the photograph.



Infra-red Thermometer Finds Faults in Wiring

A NEW infra-red thermometer—the LR120 Raynger—has recently been announced by A. Levermore and Co. Ltd. The LR120, shown above, has many industrial uses but the prime applications are in the electricity generating and distribution industry for locating faults in overhead cable connectors, transformers, splices, etc. which show themselves by small temperature rises.


To cope with these difficult operating conditions, the Raynger, which is battery operated and completely portable, has been designed to measure temperatures between 0 and 100 degrees Centigrade above ambient, giving a resolution of better than 2 degrees. The ratio of distance to object size is 120:1, e.g. a 2 inch diameter area can be accurately measured at 20 feet distant.

Computerised Telephone Trouble Shooter


AN aptly-named Argus computer system to watch over the reliability of the telephone service has been ordered by the Post Office from Ferranti Ltd. The Argus 500 configuration is to be installed in Leicester about the end of 1971 for trials that could lead country-wide to the faster detection of faults, further improvements of service for customers, and cost savings.

Acting as a round-the-clock trouble shooter, the £180,000 on-line computer system will monitor performance, draw instant attention to faults and impending breakdowns and alert maintenance engineers, enabling them to start repair work much sooner. Repairs will often be completed without the customers being aware that a fault has ever developed.

The computer will help network development staff to provide additional plant where it is needed by tracing the pattern of calls and identifying the most commonly used routes, and by keeping a constant check on the volume of calls being made. It will also analyse signals from the equipment-testing devices already used to provide engineers with information on fault-prone equipment. The computer's analysis of these tests of individual pieces of exchange will show where overhaul is needed and provide an additional safeguard against breakdown.

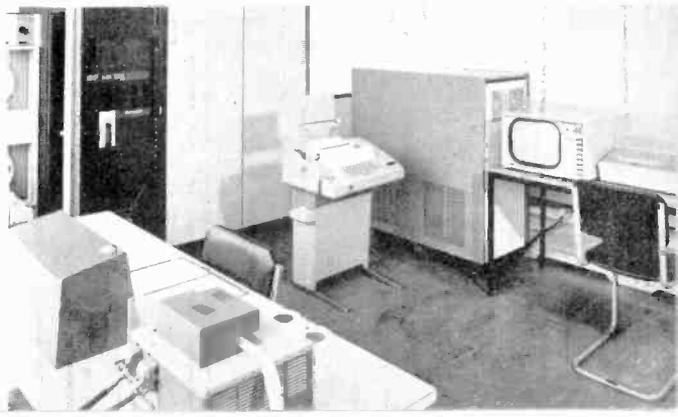

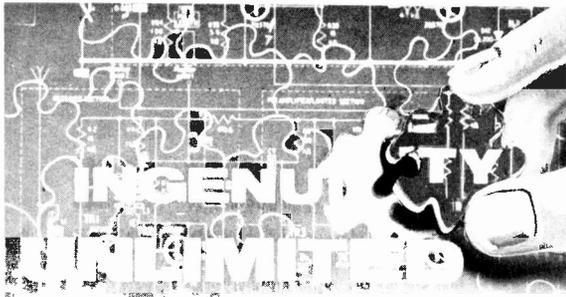Right—a typical Argus 500 configuration, this is a similar system to that to be installed at West Wigston Exchange, Leicester.



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merit.

FUSE FAILURE INDICATOR

A SIMPLE way of giving an indication of when a mains fuse has blown is to connect a neon and its series resistance in parallel with the fuse as in Fig. 1. When the fuse is intact the resistor and neon are shorted, but when the fuse has blown they are effectively connected across the mains via the load resistance and the neon will strike.

A neat way of using a neon to indicate in a positive manner if the fuse is intact or not, is to have the neon lit steadily under normal conditions and for it to flash at a desired rate, should the fuse blow. The circuit evolved is a simple modification to an RC relaxation-oscillator in which a capacitor is charged via a resistor (see Fig. 2a) until it reaches the striking voltage of the neon. At this point the neon strikes, discharging the capacitor to a level at which the neon extinguishes. The capacitor then commences to recharge and the cycle repeats, Fig. 2b.

Referring to Fig. 3, with the fuse intact, on positive half cycles current is fed to the neon and capacitor via D1, D2, R1, and R2, whose resultant resistance is such that good, even illumination of the neon takes place. Should the fuse blow, however, diode D2 is connected via the load to the neutral side of the supply and is therefore reverse biased. Current is then limited by the larger resistance R1 to give a long time constant. The capacitor takes longer to reach the striking voltage of the neon with the result that the neon flashes repeatedly drawing the attention of the operator to it. One advantage of this circuit is that the neon will flash irrespective of the load resistance, whether it is open or short circuit.

The flash rate can be adjusted by altering the value of either C1 or R1, but if R1 is altered then corresponding alterations will have to be made to R2.

One point to notice is that as C1 is charged to the striking voltage of the neon, the diodes should have a peak inverse voltage rating greater than peak mains plus this striking voltage.

S. J. Forrest,
Witney,
Oxford.

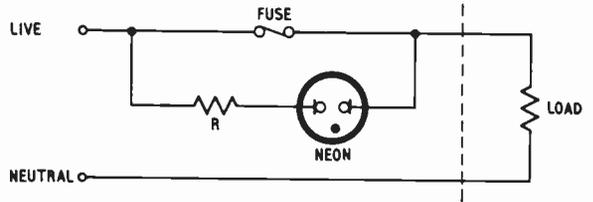


Fig. 1. Simple fuse failure circuit diagram

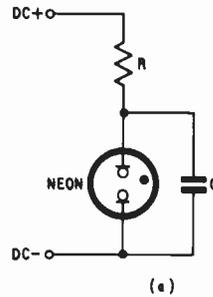


Fig. 2a. Circuit diagram for a flashing neon indicator


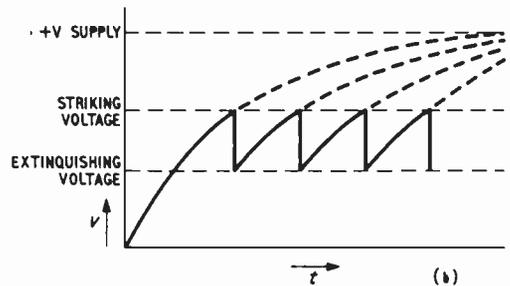


Fig. 2b. Graph showing the effect of the capacitor on the voltage across the neon

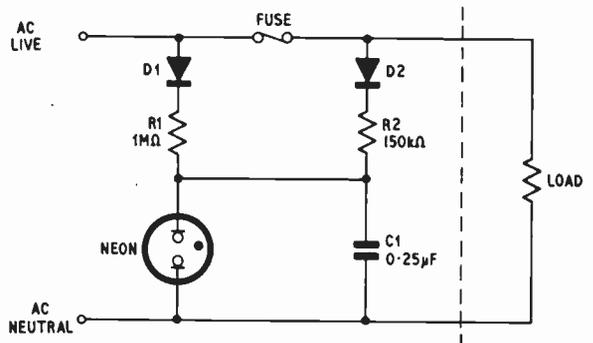

FLASH RATE FOR VALUES GIVEN = APPROX 2 PER SEC

Fig. 3. Final circuit diagram for the flashing neon version of the fuse failure indicator

LINEAR SCALE OHMMETER

ENCLOSE a circuit for a linear scale ohmmeter which may be of interest to your readers.

The circuit diagram Fig. 1a consists of a constant current generator TR1 and TR2, and a high input impedance meter driver TR4. A constant current is sent through the unknown resistor R_x and the voltage across it measured. Transistor TR3 compensates for the V_{be} drop across TR4. The current is set by varying

potentiometer VR1, which can be replaced by several resistors to give switched ranges, Fig. 1b.

On setting up, a one per cent resistor of value equal to the desired f.s.d. is used as R_x and VR1 is adjusted to give full scale deflection. The meter will then read any value resistor in that range as a linear proportion of full-scale.

For very high ranges, the single emitter follower should be replaced by a two-stage circuit as shown in Fig. 2. In theory there is no limit to the range, but in practice, components limit the maximum range.

The advantages of this circuit over conventional linear ohmmeters is that a cheap meter can be used, and the unit is accurate over a wide range of temperatures.

Ian R. Hornby,
Timperley,
Cheshire.

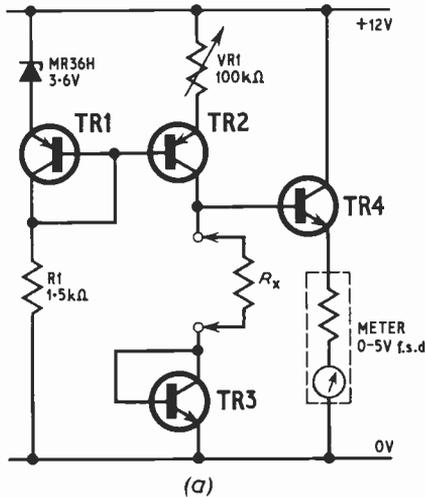


Fig. 1a. Circuit diagram of the linear scale ohmmeter

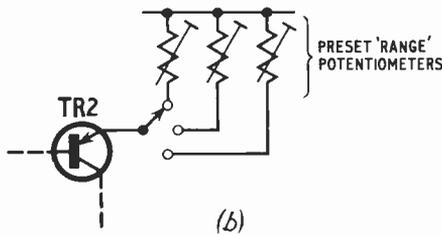


Fig. 1b. Adding a switched range

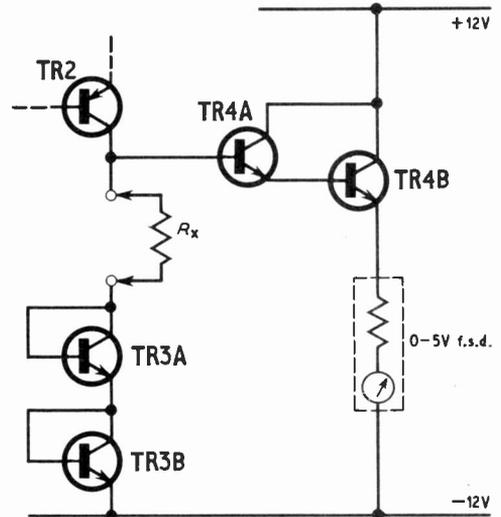



Fig. 2. Two-stage version for very high ranges

Lights!

The "P.E. Aurora Lighting Display" will be included among the exhibits making up the *Electric Theatre*. This is an exhibition of artistic works which make specific use of electrics, electronics and mechanics to create effects with light and sound.

The *Electric Theatre* will be held at the Institute of Contemporary Arts, Nash House, The Mall, London, S.W.1., from March 18 to April 18 inclusive, 11 a.m. to 10.30 p.m. daily. Admission (at the door) 25p, students and members ICA 15p.

MAKING THE MOST OF LOGIC IC's

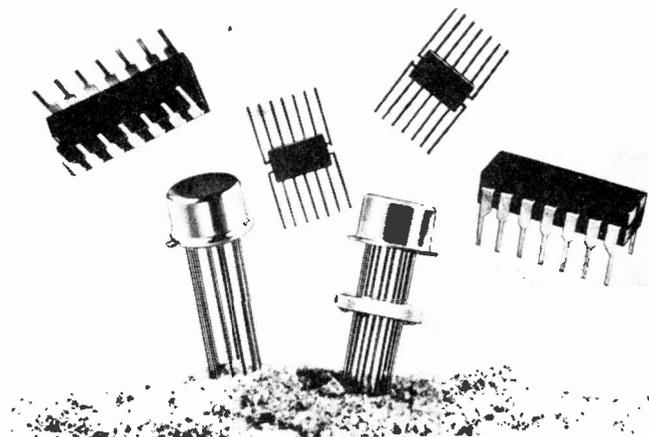

PART NINE—By R. W. COLES MEDIUM SCALE INTEGRATION

ALL monolithic i.c.s start off as discs of silicon, an inch or so in diameter, on which may be built several thousand simple gates. We have already seen that by connecting together gates only, it is possible to build many different types of flip-flop, and by connecting together flip-flops it is possible to build counters and shift registers.

It is only a short step from this line of reasoning, that counters and shift registers could be built at the i.c. processing stage, by joining together a large number of gates to produce the logic required. This is, in fact, how MSI devices are built.

BASIC MSI CONCEPT

A chip of silicon cut from the disc and containing around 30 gates, has a layer of metal deposited as an interconnection pattern, perhaps to form a four stage binary counter. The finished chip is mounted on a lead frame and packaged in the usual way as there are no space problems to worry about.

A dual-in-line pack is vast compared with the silicon chip it contains, whether it forms a flip-flop or a counter. The limitation to this process comes only with the restricted number of lead-outs the standard package can accommodate, not the size of the chip it can contain.

Fortunately the lead-out problem is not as severe as one might imagine, because most of the interconnections required to produce a complex function device are performed internally. Only the essential inputs and outputs are required to see the light of day.

What does this process do to help the designer or experimenter? The most obvious effect is the reduction in cost, a decade counter built using separate gate and flip-flop packages could cost in the region of £3 10s (£3.5), whereas the same function can be obtained from the MSI range for about £2. The number of packages in this example is reduced by a factor of three, another very important saving.

Using MSI, it is possible to think in terms of counters

as building blocks instead of just flip-flops. The design of this larger block has already been carried out by the manufacturer, so a system is much easier to design, or it may be more complex for the same design effort.

All these things add up to an impressive list of advantages, which can be put to good use by the amateur constructor.

BUILDING BLOCKS

TTL complex functions are contained in the usual 14- and 16-pin dual-in-line packages, and their equivalent in the flat-pack range; there is no external difference apart from the way the pins protrude. The inputs and outputs are completely compatible with the rest of the family, and usually employ the same type of circuitry.

However, the gates used inside the package are sometimes different in construction, because internal gates may not need the fan-out capability of others which have to drive external circuits. It is not intended here to go too deeply into the internal workings of MSI devices; earlier articles have already described the individual circuits in the TTL range.

We need only treat them as the useful building blocks that they are.

MSI COUNTERS

Several different counters are available in the 74 series, each of which may be used for many different jobs and connected in several different configurations. Let us have a look at a typical example, the 7490 decade counter, which is shown in Fig. 9.1.

This counter, like the others in the series, is a ripple type, made up of four master/slave flip-flops; three of them are JK types and one a set/reset. It consists of two separate sections, a divide-by-five stage and a divide-by-two stage, which may be externally interconnected to give two different count modes, depending on the application.

The asynchronous flip-flop inputs are connected to two internal NAND gates which, when enabled, allow the counter to be reset either to zero (0000) or nine (1001).

If the count input is connected to the divide-by-two input, and the output of flip-flop A is connected to the divide-by-five input, the counter will count in the binary coded decimal code, as shown in the truth table in Fig. 9.1a. In this mode the counter behaves as a normal four-stage binary counter until it reaches the count of nine; the next clock pulse sets the counter to the all zeros state.

This type of counter is employed when the outputs have to be decoded to drive indicator tubes, for instance in a frequency counter, or integrating digital voltmeter.

The secondary count mode is obtained by connecting the count input to the divide-by-five input, and the output of flip-flop D to the divide-by-two input, in effect causing the output of the divide-by-five counter to be divided by two, the opposite of the first count mode.

The truth table for this type of count is also shown in Fig. 9.1b, and it can be seen that the divide-by-ten output is taken from flip-flop A as a symmetrical waveform, up for five counts and down for five counts. This kind of count code is generally called the 1245 code, and is useful where these counters are used just as frequency dividers, for instance in frequency synthesisers.

These counters may be used to divide by numbers less than ten by using the reset gates to detect the desired final count plus one, and reset the counter to 0000, or even nine, at this time. Any division by less than ten is possible, and an application is shown in Fig. 9.2, where a 7490 is used as a divide-by-six counter.

The other two counters in the series are similar to the 7490, but have a divide-by-six and divide-by-eight section respectively, instead of the divide-by-five of the 7490. They also do not have the facility of nine reset, only the zero reset is included.

MSI DECIMAL DECODERS

Very often, the output of a decade counter is required to be decoded to the "one-of-ten" decimal equivalent of the binary count, in order that it may be displayed on some form of indicator. It is not surprising then, to find that the 74 MSI range contains several circuits which are capable of achieving this.

As an example let us look at the 7441 decoder/driver package. The 7441 takes a four-line binary coded decimal input word, and by means of gates and inverters, decodes this information into its decimal form, giving ten separate outputs. The outputs in this case are not designed to drive other logic gates, but to drive neon number indicating tubes such as "Nixies".

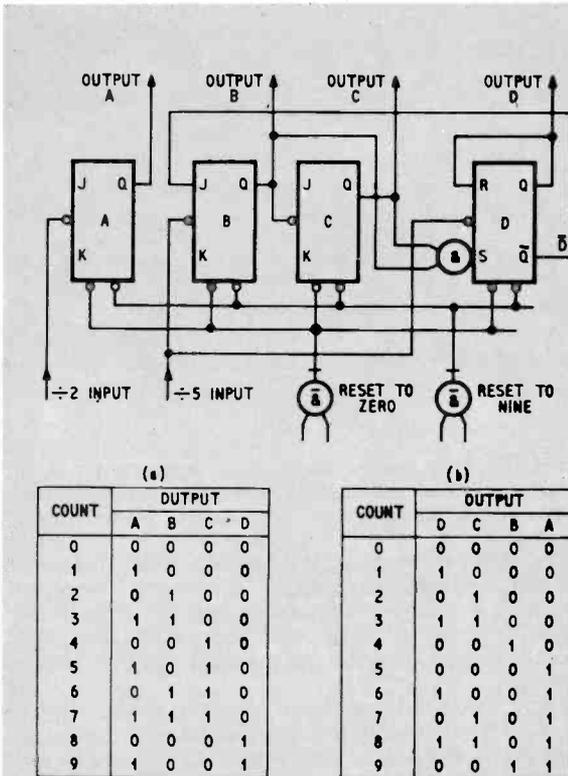


Fig. 9.1. The SN7490 decade counter with truth tables for (a) binary coded decimal (b.c.d.) count mode and (b) symmetrical ÷10 mode

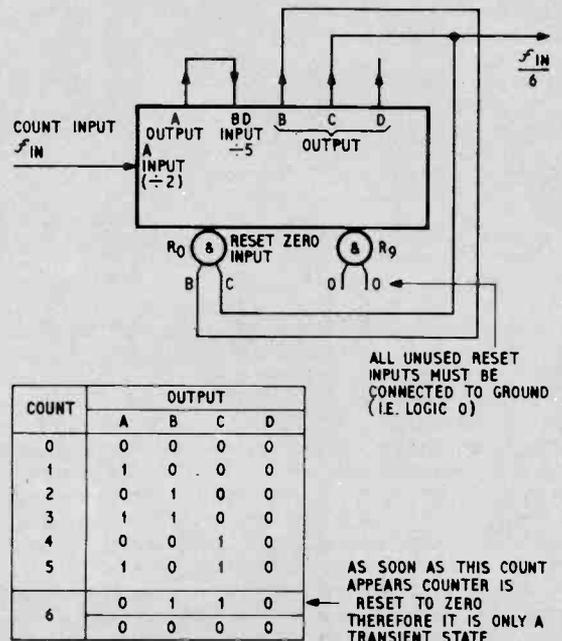


Fig. 9.2. The SN7490 used as a ÷6 counter with truth table

This type of indicating tube uses ten separate cathodes, each in the shape of a decimal character, and a common anode. The anode is connected, through a limiting resistor, to an h.t. supply of the order of 200 volts. When a particular cathode is grounded the number it represents is illuminated by the ionisation of the neon gas surrounding it.

Fortunately, it is not necessary to use transistors which will stand 200 volts on their collectors to drive these tubes, because reducing the voltage across them by only (say) 50 volts is sufficient to extinguish them, as this reduces the total voltage to below the "striking" potential.

In fact, the output transistors of the 7441 will withstand at least 55 volts, and to ensure that this rating

Many other types of decoding may be performed with the large range of circuits available in the 74 series. Some have the standard TTL output stage, others will drive incandescent lamps. Some will even drive seven segment display systems, and in these, more than 35 separate gates are employed.

MSI ADDERS

Adder circuitry, as we have already seen, is fairly complex, and now that computers are growing faster and faster, the use of parallel arithmetic is increasing, bringing with it a demand for large numbers of separate "full-adder" blocks.

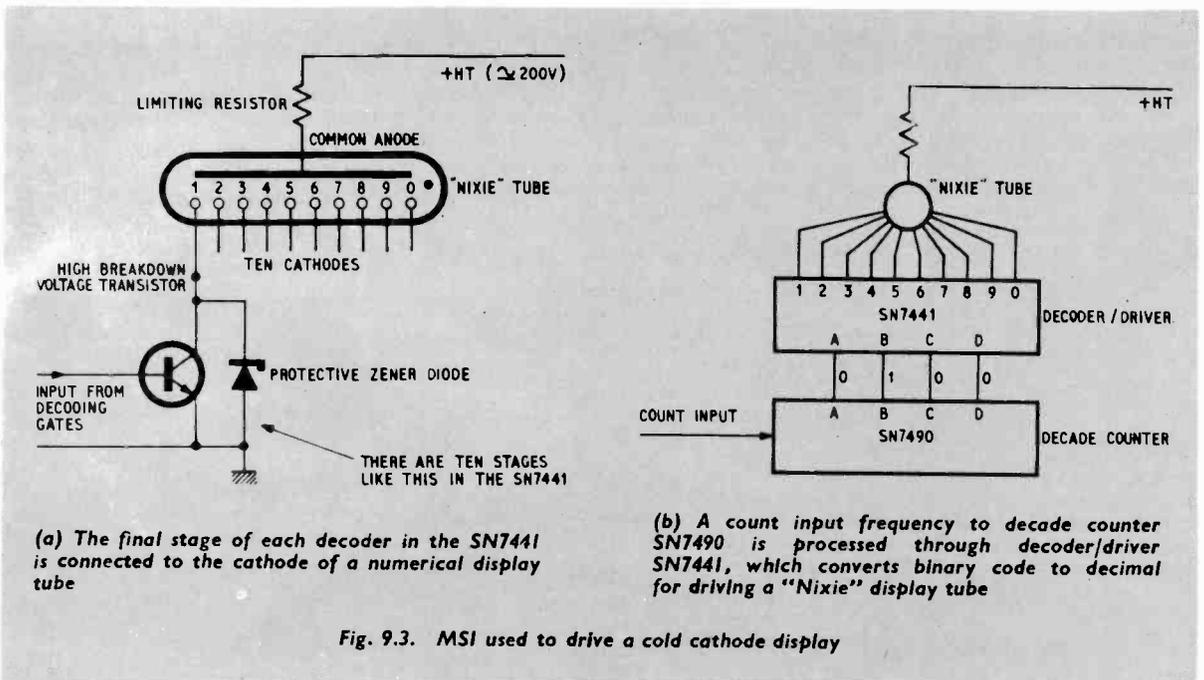


Fig. 9.3. MSI used to drive a cold cathode display

is not exceeded a Zener diode is connected from collector to ground. The basic idea of the output circuits used with these i.c.s is shown in Fig. 9.3.

To drive the ten output stages the four line binary word at the input to the 7441 has to be decoded by appropriate gating, and to carry out this decoding correctly, complementary information is necessary, i.e. A and NOT A, B and NOT B, etc. The generation of the inverted form of the input word is carried out internally, which makes things much easier, as only the true information needs to be supplied.

There is no doubt that this i.c. represents excellent value for money when compared with any of the possible discrete approaches. Even if i.c.s were employed to perform the gating, the price of ten high breakdown transistors would be more than a single 7441, which is a fraction of the size.

Fig. 9.3b shows the 7441 being used to decode the output of a 7490 decade counter, which has reached a count of two. This could represent one stage of a frequency counter.

The 74 MSI range offers three separate types of full-adder. The one which is, perhaps, most interesting is the 7483, so let us have a closer look at this one as an example.

The 7483 has four complete full-adders crammed into one 16-pin dual-in-line package. Because it is intended for use in parallel addition computers, the carry line is internally connected between the four adders, making it possible to add two four-bit numbers together in less than 50ns.

There are A and B inputs to each adder, with a single carry input to the first stage, and a single carry out from the fourth stage; four separate sum outputs are provided.

The logic of the 7483 is shown in Fig. 9.4; it is left to the interested reader to work out the truth table of the entire system, which will be in line with that given with the discrete-gate version in the section on gates.

Readers may think that it is unlikely they will be building a parallel arithmetic computer in the near future, and so this particular i.c. is of little interest, but a

PHILIPS STEREO AUTOCHANGER

£8.15.0 Post 5/-

Precision hi-fi quality at bargain price. Silver and grey deck framed in black finish. 10 in. dia. turntable. 4 speeds, 16, 33, 45 and 78 r.p.m. Plays 7, 10, 12 in. discs which can be mixed. Fitted renowned Philips plug-in Xtal AG3306 with dual sapphire stylus for LP/EP/78. Sensitivity 100mV. Frequency response 30cps-18Kc/s. Lightweight stylus pressure 5-6 grammes. Board space required 14 1/2 in. Above 4 in. Below 2 1/2 in. 12 months guarantee. Also available with GP310 diamond stylus LP Stereo EP and Sapphire 78. 21 extra.

MATCHED TEAK PLINTH with PLASTIC COVER. Only 26 extra or Cut-out plywood base board 10/- extra.

BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13 1/2 in. Above motor board 3 in. Below 2 in. AC 200/250V.

with STEREO/MONO XTAL £7 Post 5/-

BSR Minichanger UASO Stereo/Mono. Plays 12", 10" or 7" records. Size 12" 8 in. AC 200/250V. Post 5/- £8

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II £15. Model 3600 Stereo/Mono Autochanger £13. Post 5/-

Model 3500 Stereo/Mono Autochanger £14. Post 5/-

RECORD PLAYER PORTABLE CABINET. Space for amplifier and autochanger. Post 5/- 75/-

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 2-stage with triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer. Knobs, loudspeaker, valves ECL82, E280. Response 50-12,000 cps. Sensitivity 200mV. Post 5/- £4

RCS 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UY55. Post 5/- £3

R.C.S. TEAKWOOD BASE Ready cut out for mounting (plate player make and model). £65/-

R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable unbreakable plastic, attractive appearance. £65/-

EMI PICK-UP ARM. With mono xtal and stylus 25/-

EMI JUNIOR 4 SPEED RECORD PLAYER. Mains operated motor and pick up. Post 5/- £3

EMI-PI PICK UP CARTRIDGES. Diamond Stereo Mono: ELA 58/-; GP94 55/-; GP93 45/-; Mono GP91 30/-; GC8 25/-; GP67 19/-; ACOS L.P. only 10/-

All standard fixing complete with stylus.

WEYRAD P50 - TRANSISTOR COILS

BAW Ferrite Aerial 13/- Spare Cores 7d

O.F. P50/15C 10/- Driver Trans. LFD7A 10/-

I.F. P50/2CC 470 kc/s 6/7 Printed Circuit, PCA 10/-

3rd I.F. P50/3CC 6/7 J.F. Tuning Gang 11/-

P51 or P51.2 6/7 Weyrad Booklet 2/-

P50/8V 6/7 OPT 11/-

Mullard Ferrite Rod 8 in. 4/- 6 in. 5/-

VOLUME CONTROLS 80ohm Coax 9d. yd.

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 3/-, D.P. 5/-

STEREO L/S 11/-, D.P. 15/-

Edge UK. S.P. Transistor, 5/-

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 to 100 K. 5/-

WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K. 8/-

VEROBOARD 0-15 MATRIX

2 1/2 in. 3/9; 2 1/4 in. 3/2; 3 1/4 in. 3/9; 3 1/2 in. 5/2

EDGE CONNECTORS 16 way 5/-; 24 way 7/7

FINB 36 per packet 3/5; **FACE CUTTERS** 7/7

S.R.S.F. Board 0-15 MATRIX 2 1/2 in. wide 7d. per lin.

1 in. wide 9d. per lin.; 5 in. wide 1/1 per lin. (up to 17 in.).

B.L.P. undrilled 1/4 in. Board 10 8in. 3/-

SLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides, 7 x 4 in., 6/-; 11 x 3 in., 8/-; 11 1/2 in. 10/-; 11 1/2 in. 12/-; 15 x 14 in., 15/-; 9 x 7 1/2 in., 8/6; 11 1/2 in., 14/6

ALUMINIUM PANELS 18 s.w.g. 12 1/2 in. 7/-; 14 1/2 in. 6/-; 12 x 3 in. 5/-; 10 x 7 in. 4/-; 8 x 3 in. 3/-; 6 x 4 in. 2/-

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 5/- each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 5/- each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/-, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-, 6 water 42/-

TOGGLE SWITCHES, sp. 2/9; sp. dt. 3/7; dp. 3/7; dp. dt. 4/7

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive 35/-

LOW RESISTANCE HEADPHONES 8-ohms 40/-

DE LUXE STEREO HEADPHONES 8 ohms 65/-

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 47/- Post 3/-

200/250 v. A.C. Leaflet S.A.E.

Minimum Post and Packing 2/-

RETURN OF POST DESPATCH.

HI-FI STOCKISTS.

CUSTOMERS FREE CAR PARK.

CALLERS WELCOME.

RADIO COMPONENT SPECIALISTS

List 1/-

Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 1-3, 68 pass door. S.R. Stn. Selhurst. Tel. 01-884-1688

GENERAL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE

for Mike, Tape, P.U., Guitar.
Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 1 1/2". Response 25 c.p.s. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. 18/- Post free Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS

2/850V 2/9 100/25V 2/- 16+18/500V 11/-
4/350V 2/9 250/25V 2/9 50+50/350V 7/-
8/450V 2/9 500/25V 4/- 80+100/350V 11/7

16/450V 3/- 8+8/450V 3/7 32+32/250V 3/7
32/450V 4/- 8+16/450V 4/- 32+32/450V 6/7
25/25V 2/- 16+16/450V 5/- 32+32+32/350V 8/7
50/50V 2/- 32+32/350V 5/- 100+50+50/350V 9/7

SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-, 500, 1000mF 4V 8/7, 2500mF 25V 7/-

CERAMIC 1pF to 0.01mF, 9d. Silver Mica 2 to 5000pF, 9d. PAPER 350V-0.1 9d, 0.5 2/6; 1mF 3/-; 2mF 150V 3/-

500V-0.001 to 0.05 9d; 0.1-1/-; 0.25 1/8; 0.47 5/-
1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 0.2, 9d.

SILVER MICA. Close tolerance 1%, 2, 2.5, 500pF 1/7; 500-2,200pF 2/-; 2,700-5,000pF 4/-; 6,300pF-0.1mF 6/- each.

TWIN GANG "0-0" 20pF+176pF, 11/-; Slow motion drive 385pF+385pF with 25pF+25pF, 11/-; 500pF slow motion, standard 9/-; small 3-gang 500pF 22/-

SHORT WAVE SINGLE. 25pF, 50pF, 11/-

CHROME TELESCOPE AERIALS 23in. Swivel base 4/-

TUNING. Solid dielectric, 100pF, 500pF, 7/- each.

TRIMMERS. Compression 3pF, 2, 10pF, 11/-

HIGH STABILITY. 1 w. 2%, 10 ohms to 10 meg., 2/-; Ditto 5%. Preferred values 10 ohms to 10 meg., 9d.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 2/- each; 2 watt, 1 ohm to 8-2 ohms, 2/-

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
1 in. 16/7 1 in. 17/7 1 in. 19/7 1 in. 24/7 2 1/2 in. 44/3
1 in. 16/7 1 in. 19/7 1 in. 20/7 2 in. 29/7 2 in. 57/3
1 in. 16/9 1 in. 19/7 1 in. 21/7 2 in. 39/9 1 in. sq. 36/7

AM - FM/VHF TUNING GANG

Super quality small size 1 1/2 1 1/2 1 1/2 in. plus spindle 1 1/2 in. 365+365 pF with 25+25 pF. British made. Geared slow motion drive 6.1. Plastic dust cover. 6BA tapped front fixing. 10/- POST FREE

MAINS TRANSFORMERS Post 5/- each

250-0-250 50 mA. 6.3 v. 2 amps, centre tapped 22/-

250-0-250 80 mA. 6.3 v. 4 amp. 28/-

250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-

350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-

300-0-300 v. 120 mA. 6.3 v. 2 a. C.T. 6.3 v. 2 a. 50/-

MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2/- 2 in. 15/-

MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 in. 18/-

HEATER TRANS. 6.3 v. 1 v. 2, 3, 4, 5, 6, 8 v. 1 amp. 11/-

Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6, 8 v. 1 amp. 16/-

GENERAL PURPOSE LOW VOLTAGE. Tapped outputs 5, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. 38/-

1 amp. 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 45, 48, 38/-

AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60W. 24/-; 150W. 38/-; 500W. 45; 1000W. 21/-

CHARGER TRANSFORMERS. Input 200/250V for 6 or 12v. 1 1/2 amp., 24/-; 4 amp., 38/-

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs, 1 amp. 8/-; 2 amp. 11/-; 4 amp. 17/-

E.M.I. 13 1/2 x 8 in. LOUDSPEAKERS

With flared tweeter cone and ceramic magnet, 10 watts. Base res. 45-60 cps. Flux 10,000 gauss. 45/-

State 3 or 8 or 15 ohm. Post 3/- each

Also with twin tweeters. With crossover, 10 watt. £4

State 3 or 8 or 15 ohm. Post 3/- each

Recommended Teak Cabinet Size 18 1/2 in. 9 in. Post 5/- £5

10W MINI-MODULE 65/- LOUDSPEAKER KIT Post 5/-

Triple speaker system combining on ready cut baffle in chipboard 15 in. 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the audible spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE. 18 x 10 x 9 in. Modern Scandinavian style. £5 Post 5/-

fluted front design for Mini-Module.

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12 in MAJOR £9

30-14,500 c.p.s., 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.10.0

BAKER "GROUP SOUND" SPEAKERS

'Group 25' 'Group 35' 'Group 50' 'Group 50'

12 inch £7 12 inch £9 15 inch £19

25 watt 35 watt 50 watt

3 or 8 or 15 ohm 3 or 8 or 15 ohm 8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 10 or 12in round Loudspeaker 49 Post 5/-

For 12 x 8in or 8in round Loudspeaker 45 Post 5/-

For 10 x 6in or 6in round Loudspeaker 44 Post 5/-

LOUDSPEAKER CABINET WADDING 18in wide, 3/- ft

THIS ELAC CONE TWEETER IS OF THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 2 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. 38/- Post 2/-

TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2 in. x 4 in. with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm impedance. Post 2/-

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm 30/-

De Luxe Horn Tweeters 2-18 Kc/s, 15W, 8 ohm 60/-

TWO-WAY 3000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 19/-

SPECIAL OFFER! 80 ohm. 2Tn. 2 1/2 in. dia. 35 ohm. 3 in. 25 ohm. 3 in. dia. 6 4 in. 8 5 in. 18/- EACH

18 in. TYPE 8 ohm 8 4 in. 3 ohm, 2 1/2 in. 5 in. 5 in. 3 in. 7 4 in.

LOUDSPEAKERS P.M. 3 OHMS, 6 1/2 in. 22/-; 8 5 in. 25/-; 8 2 in. 18/-; 8 in. 3 1/2 in. 10 8 in. 35

5 in. WOOFER, 8 watt max. 20-10,000 cps. 8 or 15 ohm. 38/-

ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm 50/-

RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8 in. 4 watt or 16 in. 5 watt or 12 in. 6 watt, 3 or 8 or 15 ohm. 38/- each

OUTPUT TRANS. EL84 etc. 5/-

MIKE TRANS. 50-1.5 SPEAKER COVERING MATERIALS. Samples Large S.A.E.

GOODMANS OUTPUT TRANSFORMER 4 watt push pull for valves EL84, etc. 3, 8 and 15 ohms 17/-

100 WATT HIGH POWER P.A. AMPLIFIER

4 inputs speech and music. Response 10-30,000 cps. Matches all loudspeakers (4 ohm for full Post power 100 watts British rating). Details S.A.E. £36 Free

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 5/- Post free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 5/8 in. £10

BARGAIN FM TUNER as above. Chassis only, less cabinet. £7.10

FM STEREO MULTIFLEX ADAPTOR for above or general use. Ready made with 4 transistors, 6 diodes £5

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.10

COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE 3/7

OUTLET BOXES. SURFACE OR FLUSH 5/-

BALANCED TWIN FEEDERS 1 1/2-1/2 in. 80 ohms or 300 ohms.

JACK SOCKET Std. open-circuit 2 1/2 in. closed circuit 4 1/2 in.

Chrome Lead Socket 7/7. **Phono Plugs** 1 1/2 in. **Phono Socket** 1 1/2 in.

JACK PLUGS Std. Chrome 3/-; 3.5mm Chrome 2/9. **DIN SOCKETS** Chassis 3-pin 1 1/2 in. 5-pin 2/-.

DIN SOCKETS Lead 3-pin 3/7; 5-pin 5/-.

DIN PLUGS 3-pin 3/7; 5-pin 5/-.

VALVE HOLDERS, 1 1/2 in.; CERAMIC 1 1/2 in.; CANS 1 1/2 in.

E.M.I. TAPE MOTORS. 120v. or 240v. AC 1,200 r.p.m. 4 pole 135mA Spindle 0.187-0.75 in. Size 3 1/2 in. 25/-

2 1/2 in. (Illustrated). Post 3/-

BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 in. 3/20. Size 1 1/2 in. 17/-

2 1/2 in. 1 1/2 in. Post 3/-

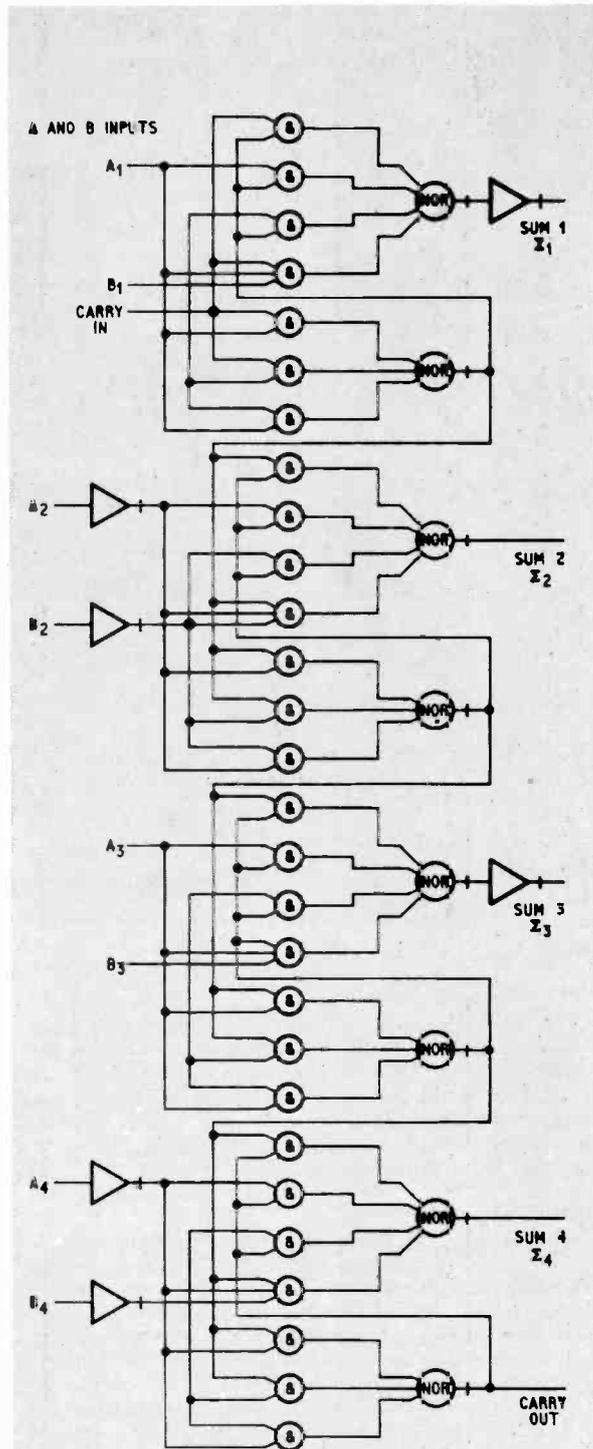


Fig. 9.4. Quad adder type SN7483 logic diagram. A total of 90 transistors, including multi-emitter versions, are incorporated in this one package with 10 diodes and 70 resistors

package such as this could come in handy for all sorts of uses, apart from computer arithmetic.

Counters of a most useful type can be built using this package in conjunction with a shift register. Counting is, after all, just the repeated addition of one to the contents of a store. Counting down requires the subtraction of one; both operations are made simple with these adders.

If the carry input is grounded, and two changing words applied to the A and B inputs, the four sum outputs will only go to a 1 when the two input words are exactly opposite, or complementary. By feeding the sum outputs to a 4-input NAND gate, a four bit non-equivalence gate emerges using only one and a half

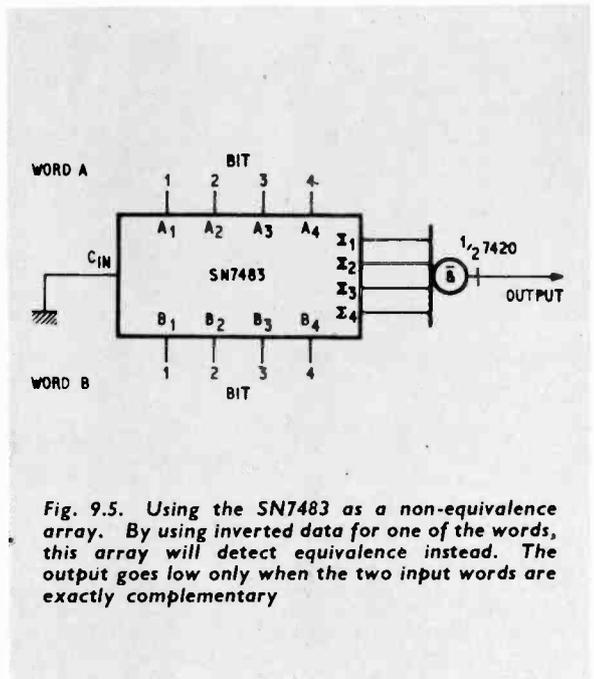


Fig. 9.5. Using the SN7483 as a non-equivalence array. By using inverted data for one of the words, this array will detect equivalence instead. The output goes low only when the two input words are exactly complementary

packages, a useful device indeed which can be better appreciated by looking at Fig. 9.5.


The other adders in the series are the 7480 single-bit and the 7482 double-bit devices, both of which have greater versatility than the 7483 due to the extra pins available on the package.

MSI SHIFT REGISTERS


Several types of shift register are available in this series, and between them they cover almost all the likely applications. All the shift registers use RS master/slave flip-flops, but because the clock input to these devices is buffered, and therefore inverted, they shift data on the positive edge of the input clock.

As all these registers have different applications and we have already gone over basic principles in the TTL flip-flop section last month. It is only necessary here to have a brief look at them all. The block diagrams and package layouts are shown in Fig. 9.6.


(a) 8-BIT SHIFT REGISTER SN7491A

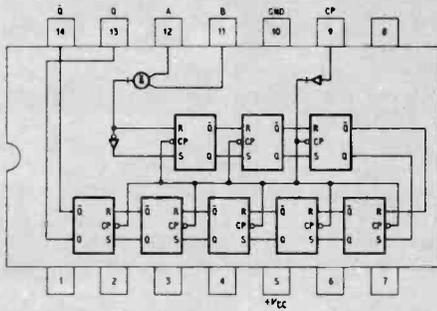

(b) 4-BIT SHIFT REGISTER SN7494A

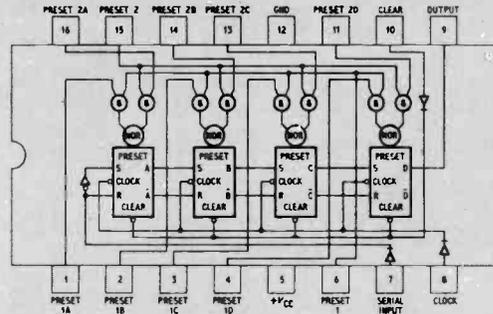

(c) 4-BIT SHIFT REGISTER SN7495A

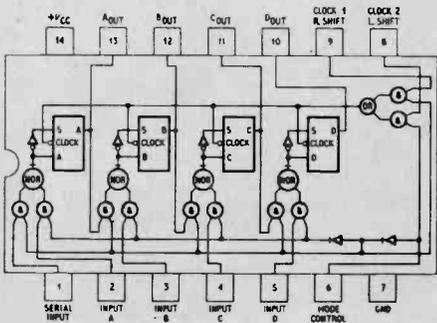

(d) 5-BIT SHIFT REGISTER SN7496A

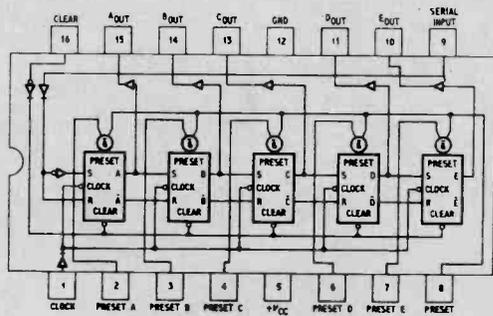


Fig. 9.6. Package diagrams of 74 Series shift registers

7491 Eight-bit Register

The 7491 is an eight-bit serial register, and information must be both inserted and withdrawn serially, as no individual inputs or outputs are available from the separate flip-flops. As with the other registers the clock input is buffered and therefore represents only one load. Data input gating is provided allowing "input enable" logic to be performed.

7494 Four-bit Register

This register is organised as a dual source parallel to serial converter, data being entered by means of the asynchronous inputs. Two preset enable inputs allow the data to be entered from either of the two sources, through four AND-OR-INVERT gates. The common clock and clear lines are buffered, and a serial input is provided.

7495 Four-bit Register

The 7495 is a versatile register which has both parallel inputs and outputs provided. Parallel entry is synchronous, and is entered through AND-OR-INVERT gates which are controlled by the mode control input. When the mode control input is low, the register will shift data serially, from left to right.

Separate clock inputs are available for the two operational modes, and these are again controlled by the mode control input. By using external gates it is possible to make this register shift in both directions, i.e. right to left or left to right.

7496 Five-bit Register

The 7496 is similar to the 7494 except that asynchronous data can be entered from only one source, but parallel outputs from each flip-flop are available. A preset enable input is provided. As all inputs and outputs are available from each stage parallel/serial, parallel/parallel, serial/parallel and serial/serial operation may be employed.

VERSATILITY

As can be seen, these shift registers leave little to be desired in the way of versatility, and of course by cascading several of them it is possible to build a register of any length which may be required. Apart from their use as storage devices it is also possible to build counters of various kinds, including the Unitary and Johnson types.

We have, in this brief introduction, only scratched the surface of the series 74 MSI, but the examples examined should set many an inventive mind buzzing, and there is really no reason why simple computers should not be designed by amateur constructors, using these devices, almost all of which are now available from advertisers in this magazine.


Next month : Metal Oxide Silicon ICs (MOS)

Britain's most popular kits...

Heathkit, the beginner as well as the experienced man's first choice...

Want to know more...? the unique Heathkit one-step-at-a-time construction manual is your guarantee to kit building success. To see for yourself how easy it all is, simply order the manual for the model of your choice (price only 10/- each). If you order a kit at a later date the manual price can be deducted. Your first step is to send for the Free catalogue, yours for only the price of a postage stamp.

STEREO RECORD PLAYER

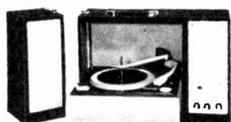

Exciting Sound—Budget Price

Kit K/SRP-1 £32.50
Carr. 80p

SEVERN AM/FM RADIO



Beautiful Looks—Luxury Sound

Kit K/Severn £19.90
Carr. 50p

POWERFUL CAR RADIO



Heathkit Value — Powerful Output

Kit K/CR-1 £13.80
(less speaker) Carr. 30p

30W STEREO AMPLIFIER



Stereo Gram, Radio, Aux. inputs

Kit K/TSA-12 £36.00
(cab. extra) Carr. 50p


ECONOMY SW RECEIVER



World-wide Reception—1 to 30 MHz plus 550-1620 KHz

Kit K/GR-64 £25.00
Carr. 50p

STEREO TUNER/AMPLIFIER

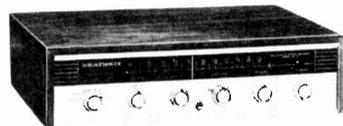

One of today's best values

Kit K/AR-14 £59.00
(cab. extra) Carr. 60p

PORTABLE 'VVM'



For Hobbyists—Householders

Kit K/IM-17 £17.30
Carr. 30p

AMBASSADOR SPEAKER

Remarkable sound quality for its price



Kit K/Ambassador £33.00
Carr. 80p

AUTO TUNE-UP METER



For D.I.Y. Car Mechanics

Kit K/ID-29 £15.80
Carr. 30p



A Schlumberger Company

HEATH (Glos.) LTD.
GLOUCESTER GL2 6EE

Many more wonderful kits to choose from

Please send me FREE catalogue

51/3/71

NAME

ADDRESS

POST CODE

VALUE ALL THE WAY

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A		3A		7A		10A		16A		30A	
	TO-5	TO-66										
50	\$0.23	\$0.25	\$0.47	\$0.50	\$0.53	\$0.58	\$0.68	\$0.75	\$1.15	\$1.40	\$1.60	\$1.80
100	\$0.25	\$0.33	\$0.58	\$0.61	\$0.68	\$0.75	\$1.15	\$1.40	\$1.60	\$1.80	\$2.00	\$2.20
200	\$0.35	\$0.37	\$0.57	\$0.61	\$0.68	\$0.75	\$1.15	\$1.40	\$1.60	\$1.80	\$2.00	\$2.20
400	\$0.48	\$0.47	\$0.67	\$0.75	\$0.83	\$0.93	\$1.25	\$1.50	\$1.75	\$2.00	\$2.25	\$2.50
600	\$0.53	\$0.57	\$0.77	\$0.87	\$0.95	\$1.05	\$1.40	\$1.60	\$1.80	\$2.00	\$2.25	\$2.50
800	\$0.68	\$0.70	\$0.90	\$1.00	\$1.10	\$1.20	\$1.50	\$1.75	\$2.00	\$2.25	\$2.50	\$2.75

SIL. RECTS. TESTED

PIV	300mA		750mA		1A		1.5A		3A		10A		30A	
	\$p													
50	\$0.04	\$0.05	\$0.05	\$0.07	\$0.14	\$0.21	\$0.21	\$0.21	\$0.47	\$0.50	\$0.53	\$0.58	\$0.68	\$0.75
100	\$0.04	\$0.05	\$0.05	\$0.13	\$0.16	\$0.23	\$0.23	\$0.23	\$0.47	\$0.50	\$0.53	\$0.58	\$0.68	\$0.75
200	\$0.05	\$0.09	\$0.06	\$0.14	\$0.20	\$0.24	\$0.24	\$0.24	\$0.50	\$0.53	\$0.58	\$0.68	\$0.75	\$0.80
400	\$0.06	\$0.13	\$0.07	\$0.20	\$0.27	\$0.37	\$0.37	\$0.37	\$0.68	\$0.75	\$0.83	\$1.15	\$1.40	\$1.60
600	\$0.07	\$0.16	\$0.10	\$0.23	\$0.34	\$0.45	\$0.45	\$0.45	\$0.75	\$0.83	\$0.93	\$1.25	\$1.50	\$1.75
800	\$0.10	\$0.17	\$0.13	\$0.25	\$0.37	\$0.55	\$0.55	\$0.55	\$0.83	\$0.93	\$1.05	\$1.40	\$1.60	\$1.80
1000	\$0.11	\$0.25	\$0.15	\$0.30	\$0.46	\$0.63	\$0.63	\$0.63	\$0.93	\$1.05	\$1.20	\$1.50	\$1.75	\$2.00
1200	---	---	---	\$0.33	\$0.57	\$0.75	\$0.75	\$0.75	---	---	---	---	---	---

TRIACS

VBOM	2A		6A		10A	
	TO-1	TO-66	TO-88	TO-1	TO-66	TO-88
100	\$0.50	\$0.63	\$1.00	\$0.50	\$0.63	\$1.00
200	\$0.70	\$0.90	\$1.25	\$0.70	\$0.90	\$1.25
400	\$0.90	\$1.00	\$1.60	\$0.90	\$1.00	\$1.60

SILICON HIGH VOLT-AGE RECTIFIERS
10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 80p each.

DIACS
FOR USE WITH TRIACS
BR100 ... 37p each

2A POTTED BRIDGE RECTIFIERS 200V 50p

UNIJUNCTION

UT46. Eqt. 2N2646, Eqt. T1843, BEN3000 27p each, 25-99 25p 100 UP 20p.

NPN SILICON PLANAR
BC107/8/9, 10p each; 50-99, 8p; 100 up, 8p each; 1,000 off, 7p each. Fully tested and coded TO-18 case.

FREE

One 50p Pack of your own choice free with orders valued \$4 or over.

AF239 VHF GERM. SIEMENS PNP TRANSISTORS. RF MIXER & OSC. UP TO 300 MHz. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE: 1-24 87p each, 25-99 84p each 100 & 80p each.

FET'S

2N 3819 ... 35p
2N 3820 ... 38p
MPF105 ... 40p

CADMIUM CELLS

ORP12 43p
ORP60, ORP61 40p each

PHOTO TRANS.

OCPT1 Type. 43p

EX-EQUIPMENT MULLARD

AF117 transistors. Large can 4 leads type. Leads cut short but still usable, real value at 15 for 50p.

SIL. G.P. DIODES 50

300mA V 30 0.50
40PIV (Min.) 100 1.50
Sub-Min. 500 5.00
Full Tested 1,000 9.00
Ideal for Organ Builders.

D13D1 Silicon Unilateral switch 50p each.

A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

ADI61 NPN ADI62 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.
For mains driven output stage of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 85p PER PAIR

HIGH POWER SILICON PLANAR TRANSISTORS. TO-3.

FERRANTI ZT1487
VCB60 1c 6A FT. 1M/CS
VCE40 Ptot. 75W
VEB8 hFE15-45
PRICE 30p EACH

2N3055 115 WATT SIL. POWER NPN

OUR PRICE 85p EACH

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-35V. 400mV (DO-7 Case) 13p ea. 11W (Top-Hat) 17p ea. 10W (80-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed Pak No. EQVT
T1 8 2G371A OC71
T2 8 2G374 OC75
T3 8 2G374A OC81D
T4 8 2G381A OC81
T5 8 2G382T OC82
T6 8 2G344A OC44
T7 8 2G346A OC45
T8 8 2G378 OC78
T9 8 2G389A 2N1302
T10 2G417 AF117
All 50p each pack

2N2060 NPN SIL. DUAL TRANS. CODE D1699

TEXAS. Our price 25p

120 VOB NIXIE DRIVER TRANSISTOR 81m

BX21 & C407, 2N1893 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18

Eqt. ZTX300 5p each. Any Qty.

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	\$0.50
U2	60 Mixed germanium transistors AF/RF	\$0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	\$0.50
U4	40 Germanium transistors like OC81, AC128	\$0.50
U5	60 200mA sub-min. Sil. diodes	\$0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	\$0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	\$0.50
U8	50 Sil. planar diodes 250mA, OA/200/202	\$0.50
U9	20 Mixed volts 1 watt Zener diodes	\$0.50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	\$0.50
U13	30 PNP-NPN sil. transistors OC200 & 2B104	\$0.50
U14	150 Mixed silicon and germanium diodes	\$0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	\$0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	\$0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	\$0.50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	\$0.50
U19	25 Silicon NPN transistors like BC108	\$0.50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	\$0.50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	\$0.50
U23	30 Madt's like MAT series PNP transistors	\$0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	\$0.50
U25	25 300Mc/s NPN sil. transistors 2N708, BSY27	\$0.50
U26	30 Fast switching silicon diodes like IN914 micro-min	\$0.50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc. 8 assorted pieces	\$0.50
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	\$1.00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	\$0.50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	\$0.50
U33	15 Plastic case 1 amp silicon rectifiers IN4000 series	\$0.50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2B302/4	\$0.50
U35	25 Sil. planar trans. PNP TO-18 2N2906	\$0.50
U36	25 Sil. planar NPN trans. TO-5 BFY50/51/52	\$0.50
U37	30 Sil. alloy trans. 80-2 PNP, OC200 2B322	\$0.50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	\$0.50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	\$0.50
U40	10 Dual trans. 6 lead TO-5 2N2060	\$0.50
U41	25 RF germ. trans. TO-1 OC45 NKT72	\$0.50
U42	10 VHF germ. PNP trans. TO-1 NKT767 AF117	\$0.50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

GENERAL PURPOSE GERM., PNP POWER TRANSISTORS

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR: OC26-28-29 30-35-36, NKT401-403-404-405-406-450-451-452-453, T13027-3028, 2N350A, 2N436A-437A-438A, 2N511-511A & B, 2G220-222, ETC. SPECIFICATION
VCEO 80V VCEO 50V IC 10A PT 30 WATTS HFE 30-170.
PRICE 1-24 25-99 100 up 43p each 40p each 38p each

GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR: 2N3055, BDY20, BDY11. SPECIFICATION
VCEO 100V, VCEO 60V, IC 15AMPS, PT. 115 WATTS. Hfe 20-100. FT MHZ.
PRICE 1-24 25-99 100 + 55p each 50p each 47p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY27/28/95A.

All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20 For 0.50
50 For 1.00
100 For 1.75
500 For 7.50
1000 For 18.00

SURPLUS A.E.I. 40A GERM. JUNCTION RECTIFIERS. For Power Applications

Type GP6C20 400PIV 40p each
GP6C30 600PIV 50p each

ALL PRICES QUOTED IN NEW PENCE.

Giro No. 388-7006.

NEW QUALITY TESTED PAKS

Pack	Description	Price
Q1	20 Red spot trans. PNP	\$0.50
Q2	16 White spot R.F. trans. PNP	\$0.50
Q3	4 OC77 type trans.	\$0.50
Q4	6 Matched trans. OC44/46/81/81D	\$0.50
Q5	4 OC72 transistors	\$0.50
Q6	4 OC73 transistors	\$0.50
Q7	4 AC128 trans. PNP high gain	\$0.50
Q8	4 AC126 trans. PNP	\$0.50
Q9	7 OC81 type trans.	\$0.50
Q10	7 OC71 type trans.	\$0.50
Q11	4 AC127/128 comp. pairs PNP/NPN	\$0.50
Q12	3 AF116 type trans.	\$0.50
Q13	3 AF117 type trans.	\$0.50
Q14	3 OC171 H.F. type trans.	\$0.50
Q15	5 2N2926 sil. epoxy trans.	\$0.50
Q16	2 GET880 low noise germ. trans.	\$0.50
Q17	3 NPN 1 BT141 & 2 ST140	\$0.50
Q18	4 Madt's 2 MAT 100 & 2 MAT 120	\$0.50
Q19	4 Madt's 2 MAT 101 & 1 MAT 121	\$0.50
Q20	4 OC44 germ. trans. A.F.	\$0.50
Q21	3 AC127 NPN germ. trans.	\$0.50
Q22	20 NKT trans. A.F. R.F. coded	\$0.50
Q23	10 OA202 sil. diodes sub-min.	\$0.50
Q24	8 OA81 diodes	\$0.50
Q25	6 IN914 sil. diodes 750V 75mA	\$0.50
Q26	8 OA95 germ. diodes sub-min. IN69	\$0.50
Q27	2 10A 600PIV sil. rect. IB45R	\$0.50
Q28	2 Sil. power rect. BYZ13	\$0.50
Q29	4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	\$0.50
Q30	7 Sil. switch trans. 2N706 NPN	\$0.50
Q31	6 Sil. switch trans. 2N708 NPN	\$0.50
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	\$0.50
Q33	3 Sil. NPN trans. 2N1711	\$0.50
Q34	7 Sil. NPN trans. 2N2369, 300MHZ.	\$0.50
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	\$0.50
Q36	7 2N3646 TO-18 plastic 300MHZ NPN	\$0.50
Q37	3 2N3053 NPN sil. trans.	\$0.50
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702	\$0.50
Q39	7 NPN trans. 4 x 2N3704, 3 x 2N3705	\$0.50
Q40	7 NPN amp. 4 x 2N3707, 2 x 2N3708	\$0.50
Q41	3 Plastic NPN TO-18 2N3904	\$0.50
Q42	6 NPN trans. 2N5172	\$0.50
Q43	7 BC107 NPN trans.	\$0.50
Q44	7 NPN trans. 4 x BC108, 3 x BC109	\$0.50
Q45	3 BC113 NPN TO-18 trans.	\$0.50
Q46	3 BC115 NPN TO-5 trans.	\$0.50
Q47	6 NPN high gain 3 x BC167, 3 x BC168	\$0.50
Q48	4 BCY70 NPN trans. TO-18	\$0.50
Q49	4 NPN trans. 2 x BFY51, 2 x BFY52	\$0.50
Q50	7 BSY28 NPN switch TO-18	\$0.50
Q51	7 BSY95A NPN trans. 300MHZ.	\$0.50
Q52	8 BY100 type sil. rect.	\$1.00
Q53	25 Sil. & germ. trans. mixed all marked new	1.50

PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 50 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards £3. P. & P. 30p.

TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK 75p each.

GERM. POWER TRANS.


Type	Price each
OC20	50p
OC22	30p
OC23	35p
OC25	28p
OC26	28p
OC28	40p
OC29	40p
OC25	35p
OC36	40p
AD140	40p
AD142	40p
AD149	43p

OUR STOCKS of individual devices

are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available EX-Stock at very competitive prices.

BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERT

POWER CONTROL

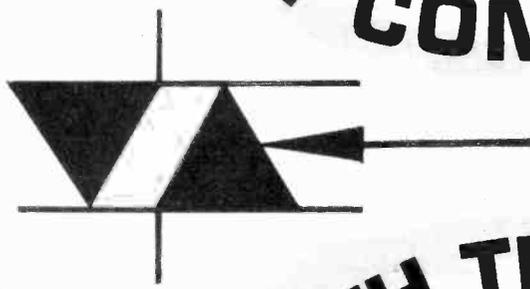

BY W.WILLIAMSON

WITH TRIACS

TRIAC is the name used to identify the triode a.c. semiconductor bidirectional switch. It is basically two reverse blocking triode thyristors or silicon controlled rectifiers connected in inverse parallel, but with a common control electrode (gate). As the triac is a development of the thyristor, it is logical to describe this first and then compare with the triac to show the advantages and disadvantages of both devices.

REVERSE BLOCKING THYRISTOR

The thyristor is a four-layer semiconductor device which has two stable states, one being the conducting state and the other the non-conducting state. The characteristics are shown in Fig. 1.

In the forward blocking region, i.e. when the anode is positive with respect to the cathode, an increase in the voltage across the device has little or no effect on the leakage current until the forward breakover voltage is reached. Increasing the voltage past this point causes the current through the device to increase rapidly, and the voltage across it to fall to about a volt.

The device is now in the conducting state and will remain in this state providing the anode current is above a certain minimum value known as the holding current. If the current through the device falls below the holding current, the device again reverts to the non-conducting state.

If the voltage across the thyristor is increased in the reverse direction, only a small current flows until the voltage reaches the reverse avalanche region where the anode current increases very rapidly and may destroy the device.

Looking again at Fig. 1, we can see that as the gate current I_g is increased, the breakover voltage is reduced. If the gate current is high enough, the device will act like a rectifier.

Normally the thyristor is used in applications where the voltage across the device is well below the forward breakover voltage and is triggered into the conducting region by increasing the gate current. This method requires only small gate currents to switch large anode currents and is therefore the most useful method of turning the device on.

Once the thyristor goes into the conducting state, the gate has no control, and the device continues to conduct, therefore the gate current may be removed as soon as the device is turned on. This typically takes $20\mu s$, and so a fast pulse can be used for triggering.

TRIAC

The characteristics of the triac are shown in Fig. 2.

From the characteristics it can be seen that the triac operates like the thyristor, but can breakover into the conducting state for either polarity of applied voltage. The triac, like the thyristor, can be triggered into the conducting state by a gate signal, but unlike the thyristor it can be triggered by a positive or negative gate signal. Thus the triac has four possible modes of operation within first and third quadrants of current/voltage characteristic:

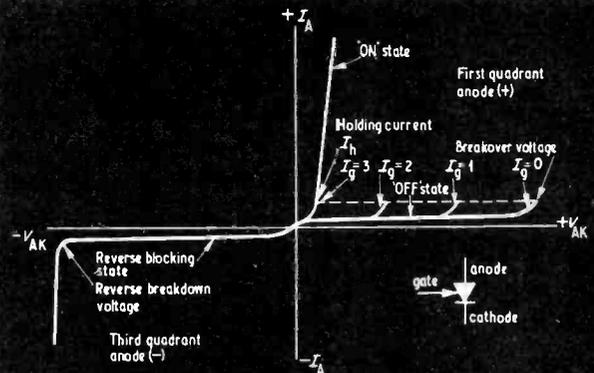


Fig. 1. Voltage current characteristic of a reverse blocking triode thyristor and circuit symbol

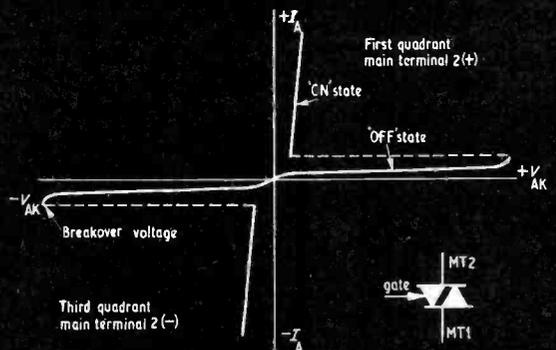


Fig. 2. Voltage current characteristic of a bidirectional triode thyristor or triac and circuit symbol

- I(-) MT2 positive and gate signal negative with respect to MT1
- I(+) MT2 positive and gate signal positive with respect to MT1
- III(-) MT2 negative and gate signal negative with respect to MT1
- III(+) MT2 negative and gate signal positive with respect to MT1

MT1 and MT2 are "main terminals 1 and 2" and used in place of cathode and anode, because the device conducts in either direction.

With no gate signal, the triac blocks in both directions so long as the voltage across it remains below the break-over voltage. If the voltage does exceed the breakover voltage, the triac turns on, and providing the current through it is limited to a safe value, then the device is unharmed, unlike the thyristor which may be damaged by an excessive reverse voltage.

Once in the conducting state, the triac will remain so until the current through the device is reduced to less than the holding current, and only then will the device turn off.

If the voltage applied to a triac is reversed in a very short time, then the triac, instead of turning off as the thyristor would do, merely turns on in the opposite direction. In order to ensure that the triac turns off reliably, it is necessary to reduce the current through it to below the holding current for a period of time before reapplying a voltage. This limits the frequency of operation of the triac to somewhere over the 60Hz

mark, but as the main use for the triac is in 50Hz and 60Hz control circuits, this is not a serious limitation.

TRIGGERING

The triac may be triggered into conduction by either d.c., a.c. or pulsed signals applied to the gate. If d.c. is used, the voltage must exceed about 3V, but the power in the gate circuit must be limited.

An example of d.c. triggering is shown in Fig. 3. This type of circuit is useful for switching large currents using a low current switch.

A.C. triggering is perhaps the most useful method to use for a.c. mains power control, because the gate signal is synchronised from the controlled supply. An example of a.c. triggering is shown in Fig. 4.

TRIGGER DIODE

A.C. triggering may also be achieved by using a bidirectional trigger diode (diac), the characteristics of which are shown in Fig. 5.

From these characteristics it can be seen that the device has similar properties to that of the triac, but because the negative resistance portion of the characteristic extends over the whole operating range the device does not latch into the conducting state. A typical breakover voltage for the trigger diode is $\pm 30V$.

An example of a circuit using a trigger diode and triac is given in Fig. 6. More will be said about this type of circuit later.

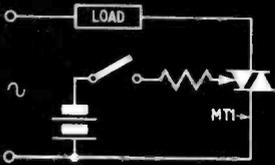


Fig. 3. Simple d.c. triggering for a triac

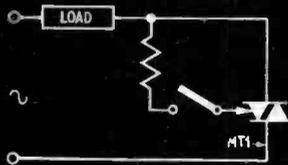


Fig. 4. Synchronous a.c. triggering for a triac

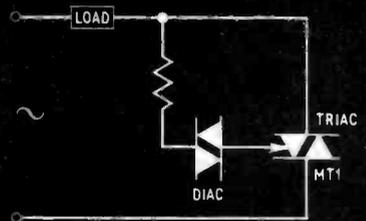


Fig. 6. A diac used for synchronous a.c. triggering of a triac

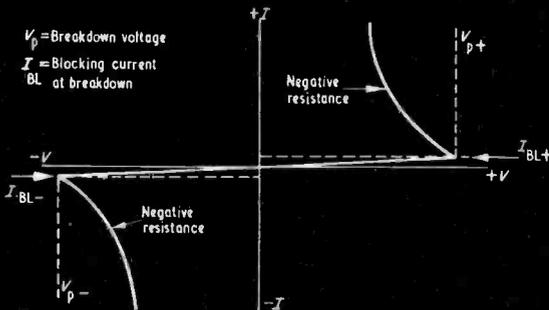


Fig. 5. Voltage current characteristic of a bidirectional trigger diode or diac

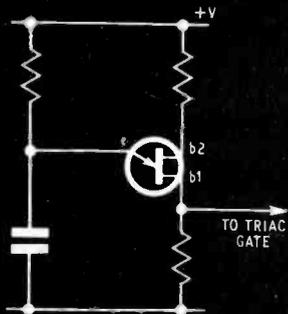


Fig. 7. Relaxation oscillator with a u.j.t. for triggering a thyristor or triac

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response $\pm 3dB$ 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth $\pm 3dB$ 12-15,000Hz. Bass boost approx. to $\pm 12dB$. Treble cut approx. to $-16dB$. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide 8" deep \times 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or sent 18p plus large S.A.E.

PRICES
AMPLIFIER KIT, £10.50 P. & P. 5p.
POWER PACK KIT, £2. P. & P. 25p.
CABINET, £2. P. & P. 25p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.50. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discophone use, etc.

FANTASTIC "POLY PLANAR" WATER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size only 11 1/2" \times 14 1/2" \times 1 1/4" deep. Weight only 19 ozs. Can replace cone speakers in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature $-20^{\circ}F$ to $+175^{\circ}F$. Power handling 10 watts rms (20 watts peak). Impedance 8 ohm only. Response 40 Hz—20 KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Head S.A.E. for full details. Only £5.75 each. P. & P. 25p.

MAGNAVOX DESK TYPE MOVING COIL MICROPHONE. Mono Impedance. Brand New—Special Price £21.00. P. & P. 10p.

SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohm. 85p. P. & P. 8p.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 85p. P. & P. 8p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1.05. P. & P. 8p.

HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. £1.98. P. & P. 13p.

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF \times 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 k Ω I.F. Size approx. 2 \times 1 \times 1 1/2". Only 43p. P. & P. 13p.

HONEYWELL MICROSWITCHES 8/P. C/O. Push-button action. Rating 250V. AC at 15 amps. Size approx. 1 1/2" \times 1/2" \times 1/2". 25p each. P. & P. 5p (6 or more post free).

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to approx. 22 1/2". Maximum diameter 1/2". 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL \times 3 1/2inW \times 3inD. Price £1.75. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.88. P. & P. 18p. Tapped Primary 200-220-240V. Sec. 21.5V at 500mA. 65p. P. & P. 13p.

BATTERY CHARGER TRANSFORMERS. 200/240V. Input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3 \times 2 \times 2 1/2". Brand New. Price £1.05. P. & P. 25p.

HIGH GRADE COPPER LAMINATE BOARDS 8 \times 6 \times 1/4" in. FIVE for 50p. P. & P. 10p.

SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2in high \times 10 1/2in wide \times 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in \times 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Curr. 50p.

Also available in 8 ohm with EMI 13in \times 8in. bass speaker with parasitic tweeter. £6.50. Curr. 50p.

LOUDSPEAKER BARGAINS

3in 4 ohm 50p. P. & P. 13p. 5in 3 ohm 80p. P. & P. 15p. 7 \times 4in 3 ohm £1.05. P. & P. 20p. 10 \times 6in 3 or 15 ohm £1.75. P. & P. 30p. E.M.I. 8 \times 3in 3 ohm with high flux magnet £1.30. P. & P. 20p. E.M.I. 13 1/2 \times 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 13 \times 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" \times 8" twin cone (parasitic tweeter) 8 ohm £2.55. P. & P. 30p.

BRAND NEW. 12in 15W H/D Speakers. 3 or 15 ohm. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly £5.50. P. & P. 38p. Guitar models: 25w £6.50. 35w £8.50.

E.M.I. 3in HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohm 60p each. P. & P. 13p.

12in "EA" TWIN CONE LOUDSPEAKER 10 watts peak handling. 3 or 15 ohm. £1.98. P. & P. 30p. **35 OHM SPEAKERS.** 3in 70p. P. & P. 13p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2.95. P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/2 \times 1 1/2 \times 1/2 in. Brand new—complete with instructions. Price 85p. P. & P. 13p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono to stylus and cartridge for LP/78, ONLY £1. P. & P. 8p.


QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound main transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. \times 3 1/2" \times 6 1/2" high. Ready built and tested. PRICE £3.75. P. & P. 30p. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4.88. P. & P. 35p.

DE LUXE QUALITY PORTABLE R/P CABINET MK II 1 inch motor board size 14 1/2" \times 12in. clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 \times 16 \times 8in. PRICE £3.98. P. & P. 48p.

10/14 WATT HI-FI AMPLIFIER KIT

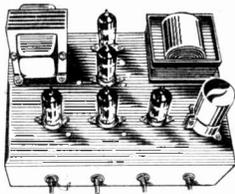A stylishly finished monaural amplifier with an output of 14 watts from 2 EL34s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.




Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line cut 2 EL24s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7.97. P. & P. 43p. Also available ready built and tested complete with std. input sockets, £9.97. P. & P. 43p.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V13/10p, 50p; OCT1 25p; OCT6 30p; AF117 15p; 2G339 (NPN) 15p; Set of Mullard transistors OC44, 2-OC45, AC128D, matched pair AC129 £1.25; ORP12 Cadmium Sulphide Cell 55p. All post free.

VERY POWERFUL COMPACT MOTOR

For 12V. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" \times 1 1/2" \times 1 1/2". Free shaft 3/16" dia. \times 1/4" L. Ideal for Model Makers, etc. ONLY 38p each. P. & P. 5p. 3 or more post free (A few 6V. versions also available).

DE LUXE STEREO AMPLIFIER

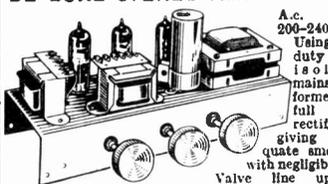

A.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2 \times ECL86 Triode Pentodes. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 16in. \times 6in. \times 3in. Overall height including valves 5in. Ready built and tested to a high standard. Price £3.92. P. & P. 40p.

4-SPEED RECORD PLAYER BARGAINS

Main models. All brand new in maker's packing. LATEST B.S.R. G109/AS1 4-SPEED AUTOCRANGER. With latest mono compatible cartridge £6.97. Carr. 33p.

With stereo cartridge £7.97. Carr. 33p. **SUITABLE PLINETH UNIT FOR ABOVE** with rigid plastic cover. £6.75 complete. P. & P. 43p.

LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60, etc. S.A.E. for Latest Prices!

PLINETH UNITS cut out for Garrard Models 1025, 2025, 2000, 3000, 3500, etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.75 complete. P. & P. 43p.

LATEST ACOS GP91/18C Mono Compatible Cartridge with 1/2 stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

ACOS HI-G Single sided mono cartridge for LP & EP. ONLY 50p. Post Free.

SONOTONE STABCOMP COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p.


Also available fitted with twin Diamond T/O stylus for Stereo LP. ONLY £3. P. & P. 10p.

LATEST ROSETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1.63. P. & P. 10p.


LATEST ROSETTE T/O Mono Compatible Cartridge for EP/EP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type PA. Peak output in excess of 1 1/2 watts. All standard British components. Built on printed circuit panel size 6 \times 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or 81 Mullard AC 128B and matched pair of AC128 C/O). 9 volt operation. Everything supplied, i.e. battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 18p (Free with Kit). All parts sold separately. SPECIAL PRICE £2.48. P. & P. 15p. Also ready built and tested. £2.75. P. & P. 15p.

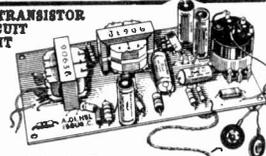

3-VALVE AUDIO AMPLIFIER HA34 MK II Designed for Hi-Fi reproduction of records on a gramophone. Ready built on plated heavy gauge metal chassis, size 7 1/2in. \times 4in. \times 4 1/2in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 30p.

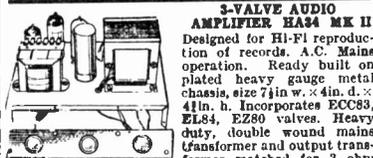

HEL "FOUR" TRANSISTOR KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 30p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3 1/2 watts. Volume and tone controls. Chassis size only 7in. wide \times 3in. deep \times 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.

OUR ROCK BOTTOM BARGAIN PRICE £2.75 P. & P. 30p

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.
170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
 - C. & G. Electronic Servicing
 - R.T.E.B. Radio/T.V. Servicing Certificate
 - Radio Amateurs' Examination
 - Radio Operators' Certs.
 - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics



EST. 1891

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 151, Intertext House, Stewarts Rd., London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME AGE

(Block Capitals Please)

ADDRESS

3/71

INTERNATIONAL CORRESPONDENCE SCHOOLS

VARI-STAT THERMOSTATIC SOLDERING IRON

HIGH PRODUCTION MINIATURE MODEL D. 50 WATT

Weight ... 2 oz.
Heating time ... 50 seconds
Bit Sizes ... 1/16", 3/32", 1/8", 3/16", 1/4"
Nickel or Iron Plated
Voltage ... 250 to 12 volts
Price ... £3.30

HIGH PRODUCTION INSTRUMENT MODEL H. 150 WATT

Weight ... 6 oz.
Heating time ... 1 min. 45 sec.
Bit Sizes ... 3/16", 1/4", 3/8", 7/16"
Nickel or Iron Plated
Voltage ... 250 to 24 volts
Price ... £4.75

OTHER VARI-STAT IRONS:

Miniature Model M 50 watt Push-in Bits 1/32" 1/16", 3/32"
Instrument Model B 70 watt Bit Size 11/64"
Industrial Model I 500 watt Bit Size 5/8"

CARDROSS ENGINEERING CO. LTD.
Woodyard Road, Dumbarton

Phone: Dumbarton 2655

MINIATURE IRON (Half Size)

LEARN HOW COMPUTERS WORK WITH COMPUKIT




CompuKit 1 is a practical do-it-yourself teaching aid designed to remove the mystery from digital computers, logic and Boolean algebra. "Cheap, Quick and Clean . . . and, clear winner on all counts" says the Times Educational Supplement. Accompanied by easy-to-follow instruction book.

Ideal as a gift to amateurs, intelligent teenagers, teachers, etc.
Unassembled kit, complete, Type CK1/U £10.50 (P. & P. 30p).
Assembled, fully tested, ready to use, Type CK1/A £13.50 (P. & P. 30p).
Also available CompuKit 1 Deluxe Model and CompuKit 2 I.C. Patchboard.

Cash with order, or further information, from
LIMROSE ELECTRONICS (PE), Lymm, Cheshire
Tel.: LYMM (092 575) 3019

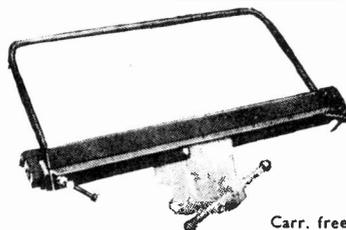PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

Carr. free

No. 1. Capacity 18 gauge mild steel × 36in. wide ... £15.00
No. 2. Capacity 18 gauge mild steel × 24in. wide ... £10.00
No. 3. Capacity 16 gauge mild steel × 18in. wide ... £10.00
Also new bench models. Capacities 48in. × 18 gauge £40. 36in. × 18 gauge £30.00. 24in. × 16 gauge £29.00. Carriage free.
End folding attachments for radio chassis. Tray and Box making for 36in. model, 5/6 per ft. Other models 3/6. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals. One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

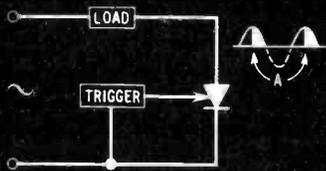


Fig. 8. Phase control triggering of a thyristor

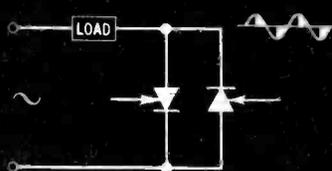


Fig. 9. Phase control triggering of two thyristors back to back in inverse parallel

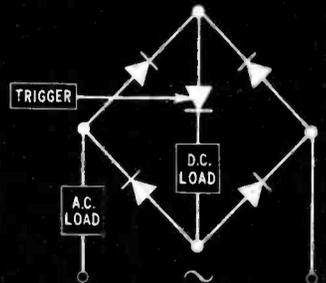


Fig. 10. Full wave phase control with a bridge rectifier arrangement

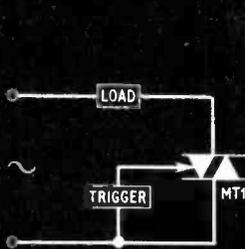


Fig. 11. Simple full wave control of a triac with a trigger circuit

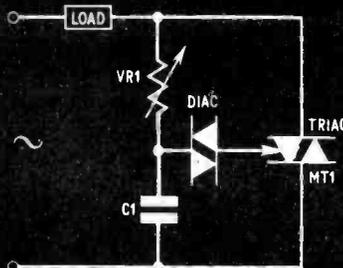


Fig. 12. Simple triac phase control

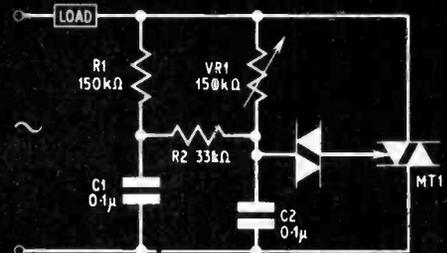


Fig. 13. Obtaining smooth power control of a lamp with two timing circuits

UNIUNCTION TRANSISTOR TRIGGERING

The third type of triggering mentioned is pulse triggering and this is sometimes achieved by using a unijunction transistor. The basic u.j.t. relaxation oscillator used for triggering purposes is shown in Fig. 7.

There are many other methods of triggering thyristors and triacs such as pulse transformers and neon lamps, but the last few examples illustrate the main methods of triggering.

The most common applications for the triac is in motor speed control, heater control, or light dimming.

By using the triac instead of the thyristor, a considerable saving in components may be made.

This coupled with the fact that the triac is less expensive than using two thyristors makes the triac very attractive indeed.

PHASE CONTROL

In the majority of domestic controllers, such as lamp dimmers, phase control is used to vary the brightness. In phase control, current from an a.c. supply is connected to the load for part of each cycle. The length of time during each cycle for which the current is connected to the load, determines the amount of power dissipated in the load. Therefore if the load is a lamp, then the brightness of the lamp may be varied.

Using a thyristor for phase control, as in Fig. 8, we can achieve half-wave control, i.e. only positive half-cycles are controlled, negative ones being blocked by the thyristor. If the thyristor is triggered at point A in Fig. 8, then the white portion of the waveform represents the power supplied to the load. Thus if the triggering point is moved to a point earlier in each half-cycle, then more power will be dissipated in the load, and vice versa.

FULL WAVE CONTROL

If we use two thyristors, as in Fig. 9, then we can achieve full-wave control, one switching the positive half-cycles and the other switching the negative half-cycles. Unfortunately this method requires insulated gate signals for the two thyristors, which is commonly achieved by using pulse transformers in the gate circuits.

Yet another way of achieving full-wave phase control using a thyristor is illustrated in Fig. 10. This circuit has the great advantage that it may be used for controlling a.c. or d.c. loads, but for purely a.c. control it is an expensive method as it requires four diodes with a high p.i.v., and a current rating equal to that of the load.

By far the most simple and reliable method of full-wave a.c. control is the circuit shown in Fig. 11. This circuit uses a triac as the controlling element and requires only a simple trigger circuit to make it function.

The simplest practical triac phase control circuit is shown in Fig. 12. This circuit is extremely economical as it uses only four components, the function of which are as follows. VR1 and C1 form a phase shift network, the amount of phase shift varying with the setting of VR1.

When the voltage on C1 exceeds the breakover voltage of the diac, it conducts and C1 is partially discharged into the triac gate. The triac is triggered into conduction for the remainder of the half-cycle.

Unfortunately this simple circuit has a limited range of control the load current jumping from zero to some intermediate value as the control is advanced and only then may be controlled smoothly up to full power. This effect may be reduced by using a circuit with a double time constant as shown in Fig. 13, giving very smooth power control.

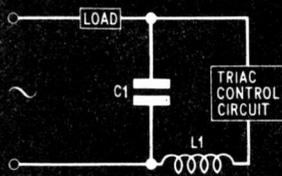


Fig. 14. Simple suppression of r.f. interference

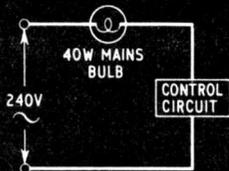


Fig. 15. The dimmer circuit in Fig. 13 is connected in series with the load

INTERFERENCE SUPPRESSION

In thyristor and triac control circuits, the load current rises from zero to maximum in a few micro-seconds. This sharply rising current causes radio frequency interference to be generated, which can cause great annoyance on the a.m. bands. Fig. 14 shows a very simple method of interference suppression.

A small inductor of a few microhenries is used to slow the rate of rise of current, but if used on its own, the interference can still be sufficient to be annoying. The addition of the shunt capacitor C1 further reduces the interference to negligible proportions for domestic applications.

TRIAC LAMP DIMMER

The circuit given in Fig. 13 can form the basis of a triac lamp dimmer which can be fitted behind a wall switch plate, giving continuously variable light control.

It is advisable to incorporate the suppression shown in Fig. 14 to reduce interference, starting with component values of $0.1\mu\text{F}$ for C1, and adjusting for the best results, with an r.f. choke rated at a minimum of 2A. This choke could be made by winding about 40 turns of thin single core p.v.c. connecting wire on a ferrite ring core or rod.

The triac should be rated at a minimum of 400V p.i.v. 3A for domestic lamp dimming. There are several available that would suit the purpose; the author used a General Electric type SC35D in conjunction with diac type ST2. Some readers may prefer to try a quadac which incorporates a triac and diac in one encapsulation.

The triac is mounted on a small "L" shaped bracket which is mounted on to a small component board. No difficulty should be experienced in constructing the unit and providing care is taken, the unit is perfectly safe.

The potentiometer may be wired to give full brightness immediately the switch on the potentiometer goes on, and then dim the light as the control is advanced, or to give minimum brightness rising to maximum as the control is advanced. The triac should be rated to withstand initial surge of current which occurs due to the cold filament, when the lamp is first switched on.

CHECKING AND FITTING

When the circuit has been wired up, the circuit may be tested by wiring it in series with a mains bulb and connecting these across the mains as in Fig. 15. The control should give smooth flicker-free control of the lamp up to full brightness, and the lamp should be extinguished by the switch.

Before fitting the dimmer, it is wise to wrap a piece of heavy polythene around the circuit to ensure that nothing shorts to the metal switch box. It may be found that the switch box is too shallow for the body of the potentiometer. If this is the case then it will be necessary to obtain a deeper box from an electrical shop.

After fitting the unit, the mains should be reconnected and the unit tried out. If everything has been carefully insulated, then no trouble should be encountered.

This dimmer should only be used with incandescent filament lamps rated at 230-250 volts a.c. 50Hz. The lamp power should not exceed 500 watts. Fluorescent lights are not suitable. ★

SOUND '71

This magazine will be exhibiting at Sound '71, sponsored by the Association of Public Address Engineers. The "P.E. Gemini Dual Purpose Amplifier" will be the main feature on our stand. Sound '71 will be held at Camden Town Hall, London, March 16-19, 10 a.m. to 6 p.m. (Final day 5 p.m.) Admission (free) by ticket, obtainable upon request from the Secretary, A.P.A.E., 394 Northolt Road, South Harrow, Middlesex.

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

	£p		£p
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-17	OC201	0-25
AC176	0-25	2G301	0-13
AC177	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
BF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15	Power Transistors	
BFY50	0-20	OC20	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-15	OC35	0-25
BSY95A	0-15	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	AUY10	1-25
OC45	0-13	2S034	0-25
OC71	0-13	2N3055	0-63
OC72	0-13		
OC73	0-17	Diodes	
OC81	0-13	AAY42	0-10
OC81D	0-13	OA95	0-10
OC83	0-20	OA79	0-09
OC139	0-13	OAB1	0-09
OC140	0-17	IN9114	0-07

FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

CLEARANCE LINES

DON'T MISS THIS LAST CHANCE ONLY A FEW LEFT

UHF/VHF T.V. TUNER UNITS
TU.2 CONTAINING 2 AF186's & 2 AF178's
PRICE 50p. P. & P. 13p EACH UNIT
All the units have many other components, e.g. Capacitors, Resistors, Coils and tuning condensers, etc. Although these are manufacturers' rejects they are not beyond repair as has been proven by many of our customers.

ALL TUNER UNITS ARE SUPPLIED WITH CONNECTION DATA

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each
post and packing 23p.

SPECIAL LINE

1 AMP Bridge rectifiers 3in Square
100 PIV. = 25p. 400 PIV. = 33p. 800 PIV. = 40p.

PAK F.3. 13p
Complementary Set. PAIR
NPN/PNP Germ. Trans.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1
Post and packing 23p.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output, Pair	50p
B81	10	Reed Switches, mixed types large and small	50p
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	50p
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	50p
B92	4	NPN, Sil. Trans. AO6 = BSX20, 2N2369 500MHz, 360mW	50p
B93	5	GET113 Trans. equiv. to ACY17-21 PNP Germ.	50p
B99	200	Mixed Capacitors. Postage 13p. Approx. quantity, counted by weight	50p
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p

RETURN OF THE UNBEATABLE P.I PAK. NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.I ONLY 50p
10p P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

FREE CATALOGUE AND LISTS for:-

**ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART**

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS 8 FOR £1
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, metal TO-5 can. 25300 type, direct replacement for the OC200/203 range.
- TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
- TYPE "D" NPN Silicon planar, plastic TO-18 case. Audio preamplifier or 500mW output stage, of the BC113/4/5 range.
- TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1/4 watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

SPECIAL OFFER
GERMANIUM BRIDGE RECTIFIERS
GEX 541 FINNED

SINGLE PHASE | THREE PHASE
12 Amp. 48 Volts | 18 Amp. 74 Volts

Ideal for Battery Chargers or Power Units

Offered at fraction of makers cost **Only 63p Each**
Post & Packing 13p.

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344




LIND-AIR AUDIO

C.1001 MULTI-TESTER



Overload protection 20,000 Ω per volt; a.c. volts 10, 50, 250, 1,000V; d.c. volts 5-25, 125; 500, 2,500V; d.c. current 0-50mA, 0-250mA; Resistance 0-60k Ω 0-6M Ω ; decibels -20 to +22dB. Size of meter 4 1/4" x 3 1/4" x 1 1/4". Complete with case. **£4.50.** P. & P. 3/6.


C.1050 MULTI-TESTER

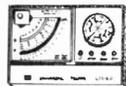

Ranges: D.C. Voltage: 0, 3, 15, 150, 600, 1,200V (10,000 Ω per V). A.C. Voltage: 0, 6, 30, 300, 1,200V (5,000 Ω per Volt).

D.C. Current: 0-120mA, 0-300mA. Resistance: 0-50k Ω . 0-5 M Ω (R x 10) (R x 1K). Decibels: -20 to +17dB. **£8.19.6.** P. & P. 3/6.


C.1052 MULTI-TESTER

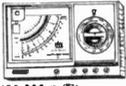

Ranges: A.C. Voltage: 6, 30, 120, 300, 1,200 (15,000 Ω V). D.C. Voltage: 0-6, 3, 15, 60, 300, 1,200 (30,000 Ω V).

D.C. Current: 0, 0-0.3, 3, 30, 300mA. Resistance: 0, 6 Ω , 60 Ω , 600 Ω , 6M Ω . Decibels: -20 to +63dB. **£7.70.** P. & P. 3/6.

E.M.I. LOUDSPEAKERS

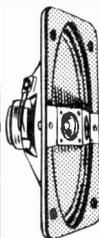

MODEL 460. 13 1/2" x 8 1/2" elliptical with twin tweeters. 8 Ω impedance. 10 watts. Brand new, guaranteed.

Lind-Air Price **£3.19.6.** P. & P. 4/6 each.

MODEL 150. 13 1/2" x 8 1/2" elliptical, 3 and 15 Ω impedance. 10 watts.

Lind-Air Price **£2.19.6.** P. & P. 4/6 each.

SANYO COLORANO AM/FM PORTABLE RADIO



10 transistor circuit, covers long, medium and VHF/FM wavebands, and will receive your local VHF stations. Internal aerial plus telescopic aerial for peak reception. Size 7 1/4" x 4 1/4" x 2 1/4". New in makers' cartons with complete with carphone (Batteries 3/4 extra).

1-year guarantee. Price **£9.19.6.** P. & P. 3/6.

GARRARD HI-FI TURNTABLES




2025 T/C with stereo cartridge **£8.19.6**
3000 with Sonotone 9TAHCD stereo cartridge **£10.19.6**
SP25 Mk. III **£12.19.6**
SL65B **£15.19.6**
Base and cover for above **£2.19.6**
AP76 **£19.10.0**
SL72B **£24.19.6**
SL75B **£28.7.0**
SL95B **£39.9.0**
Base and cover for above **£8.19.6**
401 **£28.10.0**
P. & P. Decks, 12/6; Base and Cover, 10/-; Deck / Base / Cover, 17/6.

THIS MONTH'S SPECIAL OFFERS!

SP25 Mk. III with base **£12.19.6** P. & P. 15/-
SP25 Mk. III with Sonotone 9TAHCD cartridge and base **£15.14.6** P. & P. 15/-

S-DeC BREADBOARD

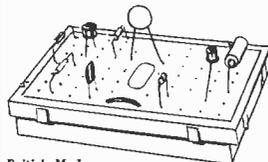

British Made Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. **£1.** P. & P. 3/6.
4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. **£8.18.0.** P. & P. 3/6.
T-DeC KIT **£3.10.0.** P. & P. 3/6.
S-DeC STOR **£2.10.0.** P. & P. 3/6.

WELLER "EXPERT" SOLDERING GUN



Comfortable and easy to use. 240V AC. Instant dual heat 100/140 watt with two position trigger control. **£3.7.6.** P. & P. 5/6.

18/19, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.
Tel: 01-580 2225 / 7679
Open 9-6 Mon-Sat (Thurs until 7)

All Mail Orders and Inquiries to Dept. PE3, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-637 1801.

94-96, UPPER PARLIAMENT STREET, NOTTINGHAM
Tel: Nottingham 40403 (STD 0602)
Open 9-6 Mon-Sat (Weds until 7.30)

OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS

Prim 200/240V a.c. TX1 425-0-425V 250mA, 6-3V 4ACT, 6-3V 4ACT, 0-5-6, 3V 3A, **£6-75**; TX2, 250-0-250V 150mA, 6-3V 4ACT, 0-5-6-3V 3A, **£3-92**; TX3, 300-0-300V 120mA, 6-3V 2ACT, 6-3V 2A, 6-3V 1A, **£3-92**; TX4, 250-0-250V 60mA, 6-3V 1.5A, **£2-10**; MT1 200V 30mA, 6-3V 1A, **£1-20**; MT2 230V 40mA, 6-3V 1.5A, **£1-50**; MT2A 250V 60mA, 6-3V 2A, **£1-87**; NT3 Prim 110/240V Sec 250V 100mA, 6-3V 2A, **£2-25**.

MULTIVOLT TRANSFORMERS

Prim 200/240V a.c. OMT4/1 one tapped sec, 5-20-30-40-60V giving 5-10-15-20-25-30-35-40-55-60, 10-0-10; 20-0-20, 30-0-30V a.c. 1A, **£2-25**; ditto trans, 2A OMT4/2, **£3-37**; OMT5/1 one tapped sec, 40-50-60-80-90-100-110V a.c. 1A, **£3-37**.

LOW VOLTAGE TRANSFORMERS

Prim 200/240V a.c. 6-3V 1.5A, **£8p**; 3A, **£1**; 6A CT, **£1-70**; 12V 1.5A, **£1-05**; 3A CT, **£1-70**; 6A CT, **£2-25**; 18V 1.5A CT, **£3-21**; 24V 1.5A CT, **£1-75**; 3A CT, **£2-90**; 5A, **£3-75**; 8A, **£5-02**; 12A, **£8-75**.

MIDGET RECTIFIER TRANSFORMERS

For FW rectification, size 1 1/2" x 2" x 1 1/4", Prim 200/240V a.c. output, PPT1 9-0-9V 0.3A, PPT2 12-0-12V 0.25A, PPT3 20-0-20V 0.15A, **£1-12**; each; ditto size 2" x 2 1/4" x 1 1/4", MTV1 9-0-9V 1A, MTV2 12-0-12V 1A; MTV3 20-0-20V 0.75A, **£1-12**; each.

O/P TRANSFORMERS

P.P. sec tapped 3-7.5-15 ohms, A-A 6-6K 30W (KT66, etc.), **£3-92**; 30W, 3K (EL34, KT88, etc.), **£6-75**; 100W 5K (EL34, KT88, etc.), **£11-25**.

LOUDSPEAKERS

Ex equipment perfect, 3 ohms only, 3in at 40p each, p.p. 15p min.

LOUDSPEAKERS, HI-FI, P.A., GUITARS, ETC.

New boxed, famous makes, 25W, 25-50, 35W, 25-50; 50W, 10; 60W, 12; 100W, 20; E.M.I. 13" x 8in, 10W, 3, 8 and 15 ohms, **£2-25**; fitted two tweeters crossover network, HI-FI, 3, 8 and 15 ohms, 24. Horn Tweeters 2-16kHz, 8 or 15 ohms, **£1-50**.

MULTI-WAY CONNECTORS (BELLING LEE)

18 way, new, for line, inter chassis, etc., pair, 25p.

12 FLUORESCENT LIGHTING

12V fittings with tube, 8W, 23-75; 13W, 26-25; Inverters 13V, 20W, 27-50; twin 20W or single 40W, 29; twin 30W or single 50W, 21; Extensive range, lists S.A.E.

Carriage extra all orders.

S.A.E. ALL ENQUIRIES PLEASE, MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

WAH-WAH PEDAL KIT

SELECTIVE AMPLIFIER MODULE.

The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design, **£1.75.** (35/-) Assembled and tested module **£2.13.** (42/6)

FOOT VOLUME CONTROL PEDAL.

Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module.

Pedal unit now only **£5.13.** (£5.2.6)

Complete kit for Wah-Wah pedal now only **£6.50.** (£6.10.0)

All post free.

Send 15p (3/-) for our catalogue of components, testmeters, musical electronics and more details of the above items.

Callers welcome.

WILSIC ELECTRONICS LIMITED

6 COPLEY ROAD, DONCASTER YORKSHIRE

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) **£2** each. P. & P. 15p.
9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) **£2.50** each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17

NEW 9TH EDITION RADIO VALVE AND TRANSISTOR DATA

Characteristics of 3,000 Valves and Cathode Ray Tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits

Compiled by A. M. Ball

75p Postage 10p

HI FI YEAR BOOK 1971

£1. Postage 10p.

ELECTRONICS POCKET BOOK

by J. P. Hawker/J. A. Reddihough.

£1.40. Postage 5p.

TAPE RECORDERS by H. W. Hellyer.

£2.25. Postage 8p.

TUNERS & AMPLIFIERS by John Earl.

£2.10. Postage 8p.

BEGINNER'S GUIDE TO RADIO by Gordon J. King.

£1. Postage 5p.

TRANSISTOR AUDIO & RADIO CIRCUITS (Mullard) £1.50.

Postage 5p.

TRANSISTOR MANUAL (G.E.C.)

£1.05 Postage 8p.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADDington 4185

Closed Saturday 1 p.m.

Gerry Brown . . .

ON THE FRINGE



Exsanguinated

There I lay, exchanging platitudes with this bright young nurse, as 450 odd milligrams of my life-blood trickled into some remote bottle. Would it, I wondered, be converted direct to plasma, or perhaps help to save some drunken driver's neck the following week-end. As I, somewhat mechanically, continued with the conversation my mind entered a reverie of ideas about this rather wonderful stuff that we would all find it so hard to do without.

Blood is supposed to contain a fair quantity of iron, I mused. Could it be magnetic? It is difficult to remember ever having sufficient amounts of it to experiment with and, in any case, not being charged with the motive to become a second "Dracula", had never really given such matters another thought!

Nevertheless, it now occurred to me that if, indeed, blood was magnetic (or perhaps, more likely, magnetically susceptible), the possibilities could be quite awe-inspiring. For example, the earth's magnetic field might have some influence on the flow of blood around our systems, and what about the effect of stray fields from transformers and the like? The effect on the capillary action of the smaller blood vessels could be quite dramatic couldn't it? Surely, I told myself, things were getting out of all proportion.

Not to be deterred, I changed tack slightly away from the gory path, and began entertaining thoughts about the chances of inducing currents in the nervous system through similar agencies. "Do you think", I butted into the, now one-sided, conversation, "that it would be a possibility to influence the brain with magnetic fields?". As you may imagine, the nurse knew little more about what I was talking about than I did, and she replied in a hushed whisper, as though to one demented, "You've nearly given your pint, I 'spect you'll feel better after your tea 'n biscuits".

Putting an optimistic face on the situation and dropping back onto my pillow, I lapsed into day dreaming again. Electric currents can be induced in copper wires, so why shouldn't the same apply to the effects of magnetism on liquids.

Subtle influence

If such really is the case this could mean that, quite unbeknown to us, magnetic fields might have some kind of modulating influence upon certain parts of the body and, who knows, perhaps even modify our very thoughts in certain subtle ways!

No, this was too much to accept in one go; the loss of blood must obviously be having its effect I considered, so decided to re-examine the idea later and in the meantime put up with the good-natured ministrations of my N.B.T.S. attendant.

Two months later I was chatting with an old friend of mine, a librarian, about this rather crazy idea of mine and, would you believe . . . he referred me to a paper written only a couple of years or so ago about the effect on reaction-time performance by magnetic fields! The paper concerned was pretty lengthy, so only the main import of its discussion will be given here.

Apparently, three individuals of the medical profession, and all from the Syracuse area of New York, had discovered quite a profound relationship between the difference in the time taken to react to the appearance of a light source with and without the influence of a fairly weak (5 to 11 gauss) magnetic field. Initially, the field, which was generated by a couple of 14.5in diameter Helmholtz coils placed near the head, was non-oscillatory and showed no effect.

Later, instead of a d.c. current being used to drive the coils, a low frequency a.c. signal was employed. Immediately, there appeared to be a perceptible change in the rate of response and, indeed, this was confirmed over some four groups of 50 subsequent trials. Every time the field was present a distinct increase in the reaction time occurred.

It is extremely difficult to know just what to make of their findings. One thing though is sure, never will I go out again in a magnetic storm without first donning my lead-lined crash hat!


By any other name

Only a matter of months ago I was nattering about tomatoes showing electrical reactions to the application of heat to their skins! Well it seems they are not the only ones among the vegetable kingdom to "blow their cool" in this way! The latest addition to the "psychosensitive" list is the "veg" which one would have thought held first place; it's the rose.

This time it is the Russians who have un-earthed the effect. It seems that hundreds of experiments have recently been performed at the Moscow Agricultural Academy which reveal that in addition to the rose reacting to tactile (touch) stimuli, it also displays a form of crude memory. According to *Pravda*, the Communist newspaper, the researches show that

rose bushes exhibit electrical activity similar to nerve discharges observed in man!

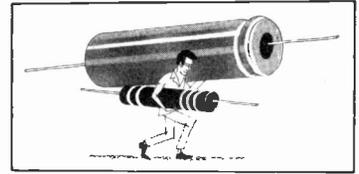All this has yet to be demonstrated to me; perhaps we shall be hearing a lot more of these findings in the not too distant future though.



So long

Wouldn't it be nice if we could gain access to the methods (whatever they may be) employed in man and other animals for generating huge time-constants? I mean if someone says "See you in an hour and a half", the chances are that, provided they said where, you will see them.

Yes, I agree, we would probably be using our watch, or maybe available clocks; who knows, we may even be relying upon the position of the sun in the sky. Assuming though that none of these methods were available, we would still feel fairly confident that the time period could be judged with a reasonable degree of accuracy. How?

Well, "hunger-pains" aside, no one is by any means certain. It could have an oscillatory principle I am told, and someone has even suggested a pulse coincidence basis.

Actually, in electronic practice, this latter idea works well for generating long time-constants; perhaps you would like to try it. Fig. 1 shows the general arrangement. An AND gate receives the outputs from two astable pulse generators, the frequencies of which are both very low and slightly different; the gate thus only returns an output when the input pulses are coincident.

With the frequencies given, only one pulse should appear at the output of the gate approximately every hour! This can be used to set a bistable or whatever application one may have in mind.

Only one problem exists with this kind of timer . . . one has to wait such a long time during the setting-up periods to establish that the correct frequencies exist!

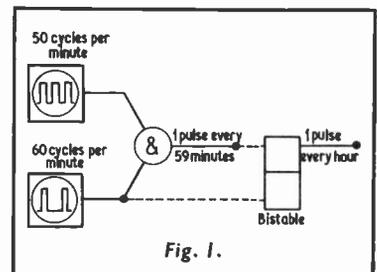


Fig. 1.



Acoustron 2-11
echo ranger and
computer
(above)




Seafarer depth
sounder (right)

BOAT SHOW 1971




Echo sounder
from Space Age
Electronics

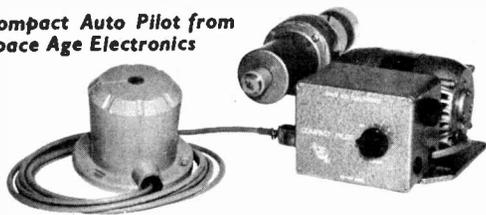Compact Auto Pilot from
Space Age Electronics



Wind direction and
speed indicator

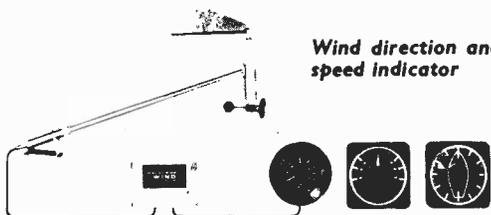

It is always interesting to note the developments in marine electronics during the past year at the London International Boat Show. Last year in our Boat Show report we noted that there were more firms displaying electronic gear and a greater range of instruments available; the same trend is repeated this year.

The advantages of solid state electronics in marine equipment were particularly evident from two new equipments, these are: the Acoustron 2-11, forward looking echo ranger and computer by Apollo Electronics Ltd., and a digital readout echo sounder by Marine Electronics Ltd. These instruments use integrated circuits to provide, compact design with clear, unmistakable readout, low power consumption and greater reliability than more conventional designs.

Acoustron 2-11 will no doubt interest almost every owner of power craft of a reasonable size. This computerised sonar uses two narrow transducer beams to probe under and ahead of the boat. The resultant echoes are used by computer circuitry to predict the possibility of grounding and to give visual and audible warning of impending danger. Warning time and depth warning can be selected as can the memory time to suit various coastlines and conditions.

LOW COST RADAR AND SONAR

Low cost is always an attraction when buying equipment, particularly if it is well constructed and has a good specification. This year has seen the first under £500 radar for small boats from Electronic Laboratories (Marine) Ltd.; the radar, called Seascan, is completely housed in two units—the scanner transceiver and the display unit. It has a working range from 25 yards to 16 nautical miles, which is covered in six switched ranges. If this radar is as popular as the Seafarer depth sounder from the same firm, and we think at the price (£450) it will be, both yachtsmen and Electronic Laboratories should be very pleased.

Space Age Electronics Ltd. are marketing what is claimed to be the world's most powerful small boat echo sounder for £35, using neon readout, and an auto pilot costing £99 that is claimed to be the world's cheapest pilot for small yachts and motor cruisers. This company is one to watch for future developments and they have said that they should be showing some interesting new instruments next year. Marine Electronics are marketing a neon echo sounder for £39 with built-in depth warning; they also sell a meter type sounder and the digital readout unit mentioned earlier.

WIND SPEED INDICATOR

New developments in equipment from Brookes and Gatehouse consist of a simplified, lightweight wind direction and speed indicator—Hengist and Horsa model C—although primarily intended for the cruising yachtsman, these models will no doubt appeal to the racing man since they are lighter in weight, more simple to use and the masthead unit will give slightly less windage.

From chatting to various stand holders, it is apparent that most of the firms are engaged in development of various new equipments and some, such as Baron Instruments and Space Age Electronics, are hinting strongly of exciting new projects next year. The added competition from new firms that have launched marine electronic equipment within the last few years, has brought about a fast moving industry that is quality and price conscious and that will have to be up to date to survive.




LOOK!

PRACTICAL!

VISUAL!


EXCITING!

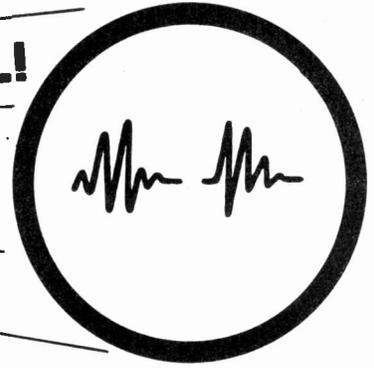

a new 4-way method of mastering
ELECTRONICS
 by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

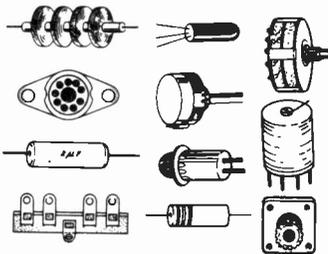complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

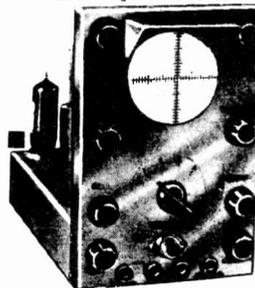a modern and professional **CATHODE RAY OSCILLOSCOPE**



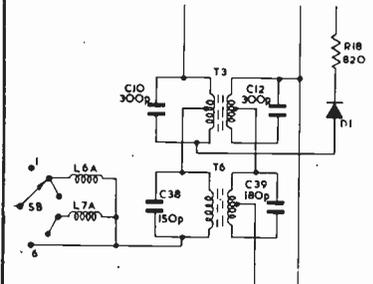3 ▶ READ and DRAW and UNDERSTAND CIRCUIT DIAGRAMS



4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E. 3

**Mail Orders: DRAYTON BASSETT, TAMWORTH, STAFFS
ELECTRONIC COMPONENTS**

G. F. MILWARD

Wholesale/Retail: 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

WIRE-ENDED TYPES **NOTE: IT IS ESSENTIAL THAT REFERENCE NUMBER IS QUOTED WHEN ORDERING THESE CAPACITORS**

REF. No.	Value	REF. No.	Value	REF. No.	Value	REF. No.	Value
G1/11	20/450V	H1/11	8/6V	H4/1	20/4/275V	H7/2A	20/6/4V
G1/13	40/50V	H2/1	32/150V	H4/13	400/50V	H7/3	25/12V
G2/5	10/6V	H2/2	64/2.5V	H4/14	500/4V	H7/4	25/25V
G2/6	8/12V (REV)	H2/6A	24/275V	H5/7	30/6V	H7/4A	25/20V
G3/7	100/25V	H2/8	32/150V	H5/11	400/6.4V	H7/5	40/15V
G3/14	100/180V	H2/9A	2/150V	H5/12	320/10V	H7/6	50/3V
G5/9	8/8/450V	H2/10A	16/32/350V	H5/14	5/6V	H7/6A	26/50V
G6/13A	40/450V	H2/11A	32/275V	H6/6	200/3V	H7/7	50/12V
H1/3	1/6V	H3/7A	500/12V	H6/7	200/16V	H7/7A	50/10V
H1/4	4/4V	H3/8	750/12V	H6/13	500/3V	H7/8	50/15V
H1/5	6/6V	H3/10A	30/10V	H7/1	10/12V	H7/9	60/12V
H1/7	20/6V	H3/12	16/50 (REV)	H7/2	20/15V		

CAN TYPES		CAN TYPES		CAN TYPES		CAN TYPES	
REF. No.	Value	REF. No.	Value	REF. No.	Value	REF. No.	Value
G2/1	6,000/30V	G4/7	40/40/275V	G5/7	100/400/300V	G6/9	60/200/300V
G2/5	125/200V (REV)	G4/7A	40/40/450V	G5/7A	45,000/12V	G6/12A	1,000/12V
G2/10	50/50V	G4/11	2,000/25V	G6/1	12,000/15V	H5/4	325/25V
G3/4	650/300V	G4/12	150/30V	G6/3	2,000/15V	H6/14	400/275V
G3/9	100/200/250V	G4/13	100/200/16/275V	G6/4	2,000/15V	H1/5	2,000/18V
G3/10	40/20/10/350V	G5/1	8,000/70V	G6/5	1,000/1,500/25V	H1/6	125/200V
G3/13A	2,000/30V	G5/3	35,000/15V	G6/5A	1,600/80V	H1/12	200/275V
G4/1	300/700/320V	G5/4	39,000/10V	G6/6	1,000/60V	H2/6	50/275V
G4/5A	60/350V	G5/4A	500/100V	G6/8	200/250V	H2/9	16/16/450V
G4/6	60/200/275V						

TAG ENDS		TAG ENDS		TAG ENDS		TAG ENDS	
REF. No.	Value	REF. No.	Value	REF. No.	Value	REF. No.	Value
G1/4	4/150V	G1/12	40/450V	G4/5	16/300V	G6/4	1,000/50V
G1/5	8/275V	G2/4	40/300V	G4/9	8/8/350V	G6/7	100/275V
G1/5A	32/350V	G2/13	100/50V	G4/10	350/25V	G6/12	1,000/12V
G1/7	16/16/275V	G4/3A	200/25V	G6/1A	3,000/15V		

PRINTED CIRCUIT, CAN TYPE		PRINTED CIRCUIT, CAN TYPE		PRINTED CIRCUIT, CAN TYPE		PRINTED CIRCUIT, CAN TYPE	
REF. No.	Value	REF. No.	Value	REF. No.	Value	REF. No.	Value
G1/6	16/32/450V	G3/11	100/350V	G5/13	40/100/350V	H3/9	100/275V
G1/8A	16/350V	G3/12	100/200/16/16/300V	G5/13A	40/40/40/40/350V	H3/10	100/250V
G1/10	32/275V	G3/13	64/275V	G6/11	40/350V	H3/13A	16/16/275V
G1/14	16/275V	G4/3	250/150V	G6/12	250/25V	H4/4	400/6 (REV)
G2/10	100/100/350V	G4/4	50/50/200V	H1/10A	10/10/350V	H4/6	64/275V
G2/12	100/150V	G4/8	40/40/450V	H1/12	200/275V	H4/7	32/32/350V
G2/14	20/10/10/450V	G5/6	60/100/275V	H1/13	250/150V	H4/8	8/8/8/275V
G3/1	60/100/350V	G5/10	100/100/50/350V	H2/4	50/80/300V	H4/10	10/10/425V
G3/6	100/250V	G5/11	100/200/25V	H2/6	50/275V	H4/13	400/250V
G3/6A	50/50/350V	G5/12	100/20/10/350/20/50V	H2/11	32/32/250V	H5/1	150/200V
G3/8A	100/25V, 100/12V			H2/12	50/50/150V		

PRINTED CIRCUIT TYPE, WIRE LEADS		PRINTED CIRCUIT TYPE, WIRE LEADS		PRINTED CIRCUIT TYPE, WIRE LEADS		PRINTED CIRCUIT TYPE, WIRE LEADS	
REF. No.	Value	REF. No.	Value	REF. No.	Value	REF. No.	Value
G1/9	16/275V	H3/15	350/12V	H6/5	150/25V	H6/14A	5/15V
H2/7	10/25V	H5/1	150/30V	H6/10	300/9V	H7/12	65/15V
H2/12A	350/12V	H5/14A	1,100/10V	H6/11	300/15V	H7/15	100/16
H2/15	12.5/40V						

SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE!!!!

RESISTORS, 1/2 watt		TRANSISTORS	
assorted	100 50p	P.N.P. Untested but mainly	50 50p
Wire-wound 1 to 3 watt	20 50p	O.K.	50 50p
5 to 7 watt	15 50p	N.P.N. Untested but mainly	50 50p
10 watts	10 50p	O.K.	50 50p
Multi-tapped	12 50p	OCF 71 equivalent	5 50p
PAPER CONDENSERS		Light-sensitive Diodes	10 50p
TV types	50 50p	(These produce up to 1ma from light)	
Miniature	100 50p	OC44 Mullard 1st grade	4 50p
ELECTROLYTIC CONDENSERS		OC45 Mullard Boxed	4 50p
Suitable for Mains		2G378 Output, Marked	4 50p
Radio/TV	10 50p	2G371 Driver, Marked	4 50p
Transistor types	20 50p	ASY 22, Marked	5 50p
Mixed (both types)	15 50p	BY 127 Rectifiers	4 50p
POLYSTYRENE CONDENSERS		IN4007 Rectifiers	4 50p
100 50p		IT2000 (peak)	4 50p
MULLARD POLYESTER COND.		Large Selenium	6 50p
50 50p		DIODES (OA 81 & OA 91)	40 50p
SILVER MICA WIRE-WOUND 3-Watt SLIDERS		WIRE	
15 50p		Solid Core. Insulated 100yds.	50p
VOLUME CONTROLS.		Stranded ditto	50yds.
Assorted	5 50p	SOLAR CELLS.	
NUTS AND BOLTS. Mixed length/type		Small	2 50p
8 B.A.	100 50p	(6 cells will power a Micromatic radio)	
6 B.A.	100 50p	CO-AXIAL CABLE.	
4 B.A.	100 50p	Semi Air-spaced	15yds. 50p
2 B.A.	100 50p	CRYSTAL TAPE RECORDER	
METAL SPEAKER GRILLES		MIKES	1 50p
7in. x 3in.	6 50p	CRYSTAL EARPIECES	
EARPIECES, Magnetic		3.5mm Plug	2 50p
No Plug	6 50p	TRANSISTORISED Signal Injector	
No Plug	6 50p		1 50p
2.5mm Plug	4 50p	TRANSISTORISED Signal Tracer	
3.5mm Plug	4 50p		1 50p
500 MICRO-AMP LEVEL METERS		TRANSISTORISED CAR REV. COUNTER KIT (Needs 1ma meter as indicator)	
1 50p			1 50p
VEROBOARD, TRIAL PACK 5 BOARDS + CUTTER			
50p			

SINCLAIR AMPLIFIERS AND SPEAKERS. Complete range in stock. All at 10% discount on list.

VEROBOARD	
Value	Price
2in x 1in x 0.15in 6p	5in x 3in x 0.1in 24p
3in x 2in x 0.15in 16p	17in x 2in x 0.15in 55p
3in x 3in x 0.15in 20p	17in x 3in x 0.15in 74p
5in x 2in x 0.15in 20p	3in x 2in x 0.1in 21p

Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0-1 or 0-15) 36 for 18p. Special Offer Pack consisting of 5 2in x 1in boards and a Spot Face Cutter—50p.

RECORD PLAYER CARTRIDGES. Well below normal prices!
 G90 Magnetic Stereo Cartridges, Diamond Needle, 6mv output, £4. ACOS GP 6/72 (Mono, Crystal) 75p. ACOS GP 9/13 (Compatible, Crystal) £1. ACOS GP 9/11 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 9/31/D (Stereo, Crystal, Diamond) £1.63. ACOS GP 9/41 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 9/41/D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 9/51 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

TRANSISTORISED FLUORESCENT LIGHTS, 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 22in x 2in x 1in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

MULLARD POLYESTER CONDENSERS
 1,000pf, 1,200pf, 1,500pf, 1,800pf, 2,200pf, 15p per dozen (all 400V working). 0.15µf, 0.22µf, 0.27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

RESISTORS
 1/2 and 3 watt. Most values in stock. 50p per 100. 10p per dozen of any one value. **WIRE WOUND MAINS DROPPERS.** Hundreds of values, from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS
 Large range in stock, 75p per 100 of any one value. 15p per dozen.

RECORDING TAPE BARGAIN! The very best British Made low-noise high-quality Tape! 5in Standard 38p. Long-play 45p. 5in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices?

£5 WORTH OF COMPONENTS FREE!!!!
 Thinking of learning another language? If so apply to us for details of LINGUAPHONE courses. We will GIVE you £5 worth of components of your selection quite free of charge when you purchase a course!!!!

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 10p.

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Shipwreck

Sir—I recently finished making your game "Operation Seasearch" and I am writing to point out a defect in the circuit given for this game in your December 1970 edition. I feel that this should be pointed out to other readers who may be considering building the game. This defect will not usually cause difficulty but it may in certain circumstances as explained below.

This difficulty is as follows. With reference to the enclosed diagram, Fig. 1, it can be seen that if the "Raider" is at say, *Aa*, and the "Supply Ship" at *Ba*, current can pass to S5 when it is in position "A" or "B". If S6 is in position "a", current will be passed to S2a and thus to LP1 when S9 is depressed. Thus S5 can be in position "B" and on depressing S9 LP1 will glow showing that the raider has been detected, when in fact it hasn't. This situation can occur in a number of positions.

D. W. Guest,
St. Helens,
Lancs.

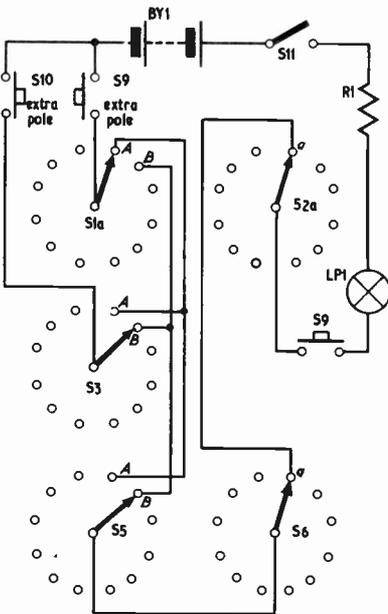


Fig. 1

Mr. Guest is quite right; this is a point that was omitted in the original article. The condition occurs when either searching ship is in line with the "Raider" along one axis and also in line with the "Supply Ship" along the other axis. Overcoming the condition can be done quite simply by inserting a second pole of each push button where indicated. This was not done in the prototype on the grounds of economy, as a second pole was needed in the later "Submarine Game", and three pole push buttons come a bit expensive!

Actually, in the game situation the phenomenon is not so drastic as it might appear. Firstly, the chances of the right conditions arising in any one game move are approximately 70 to 1 against. (Suffice to say that in innumerable games, it has occurred only two or three times.) Secondly, since both players take turns to control the "Raider", the chances against each player are exactly equal.

On the few occasions that the situation has arisen, we have attributed the discovery of the "Raider's" position to an accidental sighting by long-range aircraft, which satisfied our sense of the propriety of things—it gave the searcher another "fix" on the "Raider's" position just as he has in variations 3 and 6, page 989.—D.R.D.

Economic damper

Sir—May I congratulate you on the series of articles currently running on using logic i.c.'s; they are very useful to me. Also, the "Digital Clock" is a very useful design but, as is very often the case, the difficulty in obtaining parts (Nixie tubes in this case) at the right price, tends to put a damper on one's enthusiasm.

After several enquiries and visits to shops I may be able to satisfy my requirements, given several more weeks. Of course, I know it is possible to get anything if you are prepared to pay top prices, but I begrudge doing this when I know that someone must be selling the equivalent article much cheaper.

Referring to Gerry Brown's brake fluid level detector (*On The Fringe*, November 1970 issue), I had the same idea myself a few months ago but on trying it out I found that as soon as the fluid was shaken up a thin film of fluid adhered to the insulated cap,

thus permanently shorting the probe, see Fig. 1 (below).

Did Mr. Brown have this trouble or was it just a theoretical circuit?

John Westmoreland,
Bispham,
Blackpool.

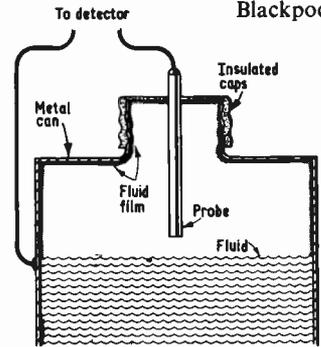


Fig. 1

Fuzz thump

Sir—Reference to the "Fuzz Circuit" included in *Ingenuity Unlimited*, December 1970 issue. Having constructed this circuit, I found as have probably many of your readers, that it needs quite a considerable clout, on even the lowest guitar string (open E) to set off the trigger circuit, once it is stable, and it has zero response to the top E and B strings at standard tuning.

Modifying the circuit by wiring resistor R1 (1M Ω) directly between the base and collector of TR1 and changing the value of C5 to 10 μ F 10V working should cure the above problems.

B. K. Cox,
Wellingtonborough,
Northants.

DECIMAL CURRENCY AND P.E.

Readers throughout the world are probably aware that British currency is being decimalised with effect from February 15, 1971. The following notes are issued for their guidance when writing to Practical Electronics.

1. Cheques and postal orders should show amounts payable in decimal currency. Leaflets are available at all branches of British Banks.

2. Readers' cheques and postal orders written in £ s d will not be accepted by the publishers of *Practical Electronics* after February 15, 1971.

3. Handwritten cheques of more than £1 which include new pence, should use a hyphen in place of the decimal point (e.g. £7-80, £30-06).

4. Postage rates in the U.K. on and after February 15 will be 2½p second class and 3p first class for up to 4 ounces. Old £ s d stamps used on and after this date must be at the new rate of 6d second class, 7d first class for up to 4 ounces. Readers requiring a reply to correspondence are asked to use the correct postage rate on s.a.e.

Sinclair Project 60



the world's most advanced high fidelity modules

Sinclair Project 60 presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.


Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.
Tel. St. Ives (048 06) 4311

sinclair

System	The Units to use	together with	Cost of Units
A Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£9.6 (£4.47½)
B Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.9.0 (£9.45)
C 20+20 W. R.M.S. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	£23.18.0 (£23.90)
D 20+20 W. R.M.S. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.18.0 (£26.90)
E 40+40 W. R.M.S. deluxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr	As for D	£32.17.6 (£32.87½)
F Outdoor P.A. system	Z.50	Mic., up to 4 P.A. speakers controls, etc.	£5.9.6 (£5.47½)
G Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£17.8.6 (£17.42½)
H High pass and low pass filters	A.F.U.	C, D or E	£5.19.6 (£5.97½)
J Radio	Stereo F.M. Tuner	C, D or E	£25.0.0

Sinclair Project 60

Z.30 & Z.50 power amplifiers

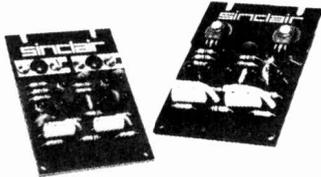

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications). Power Outputs


Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.
Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts
Frequency response: 30 to 300,000 Hz ± 1 dB
Distortion: 0.02% into 8 ohms
Signal to noise ratio: better than 70dB un-weighted.

Input sensitivity: 250mV into 100 Kohms. For speakers from 3 to 15 ohms impedance. Size $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$ in.

Z.30
Built, tested and guaranteed with circuits and instructions manual **89/6 (£4.47 $\frac{1}{2}$)**

Z.50
Built, tested and guaranteed with circuits and instructions manual **109/6 (£5.47 $\frac{1}{2}$)**

Power Supply Units

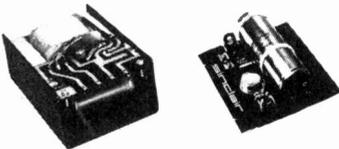

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ-5 30 volts unstabilised £4.19.6 (£4.97 $\frac{1}{2}$)

PZ-6 35 volts stabilised £7.19.6 (£7.97 $\frac{1}{2}$)

PZ-8 45 volts stabilised

(less mains transformer) **£5.19.6 (£5.97 $\frac{1}{2}$)**

PZ-8 mains transformer £5.19.6 (£5.97 $\frac{1}{2}$)

Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost

Stereo 60 pre-amp/control unit



Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS

Input sensitivities: Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve ± 1 dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV.

Output: 250mV.

Signal-to-noise ratio: better than 70dB.

Channel matching: within 1dB.

Tone controls: TREBLE + 15 to -15dB at 10KHz. BASS + 15 to -15dB at 100Hz.


Front panel: brushed aluminium with black knobs and controls.

Size: $8\frac{1}{2} \times 1\frac{1}{2} \times 4$ ins.

Built, tested and guaranteed.

£9.19.6 (£9.97 $\frac{1}{2}$)

Active Filter Unit

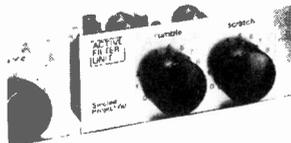

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

£5.19.6 (£5.97 $\frac{1}{2}$)

Stereo FM Tuner



first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS:

Number of transistors: 16 plus 20 in I.C.

Tuning range: 87.5 to 108 MHz.

Capture ratio: 1.5dB

Sensitivity: 2 μ V for 30dB quieting; 7 μ V for full limiting.

Squelch level: 20 μ V.

A.F.C. range: ± 200 KHz

Signal to noise ratio: >65 dB

Audio frequency response: 10Hz—15KHz (± 1 dB)

Total harmonic distortion: 0.15% for 30% modulation

Stereo decoder operating level: 2 μ V

Pilot tone suppression: 30dB

Cross talk: 40dB

I.F. frequency: 10.7 MHz


Output voltage: 2 x 150mV R.M.S

Aerial impedance: 75 Ohms

Indicators: Mains on; Stereo on; tuning indicator

Operating voltage: 25-30 VDC

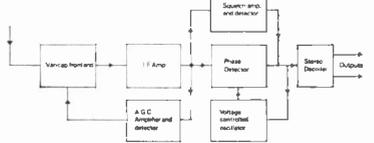Size: 3.6 x 1.6 x 8.15 inches: 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

for which I enclose cash/cheque/money order.

PE371

Sinclair IC10 / Q16 / Micromatic

IC10



The world's most advanced high fidelity amplifier

This is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, having 5 watts RMS output (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, and is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is more rugged and has considerable performance advantages, including complete freedom from thermal runaway and a very low level of distortion. The IC10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. It may also be used in other applications including car radios, electronic organs, servo amplifiers (it is dc coupled throughout) etc.

Circuit Description


The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. There is generous negative feedback round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

Each IC10 is sold with a comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include oscillators, etc. The pre-amp section can be used as an RF or IF amplifier without any additional transistors.

Specifications:

Output: 10 watts peak, 5 watts RMS continuous.
 Frequency response: 5Hz to 100kHz $1 \pm$ dB.
 Total harmonic distortion: Less than 1% at full output.
 Load impedance: 3 to 15 ohms.
 Power gain: 110 dB (100,000,000,000 times) total.
 Supply voltage: 8 to 18 volts. (A Sinclair power unit, PZ.7 is available for mains operation).
 Size: $1 \times 0.4 \times 0.2$ in. plus heat sink and tags.
 Sensitivity: 5 mV.
 Input impedance: Adjustable externally up to 2.5 Mohms.
 Price (with manual) - **59/6** (£2 97½) post free.

Q16

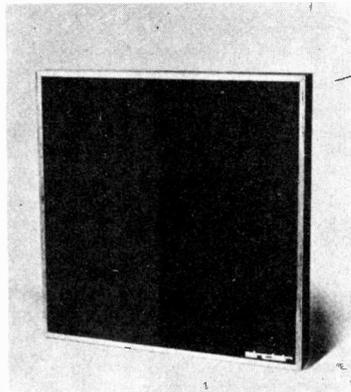

High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

Specifications:

Construction: Special sealed seamless sound or pressure chamber with internal baffle.
 Loading: up to 14 watts TMS.
 Input impedance: 8 ohms.
 Frequency response: From 60 to 16,000 Hz, confirmed by independently plotted B and K curve.
 Driver unit: Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and a special cone suspension for excellent transient response.
 Size and styling: $9\frac{1}{2}$ in square on face x $4\frac{1}{2}$ in. deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
 Price **£8.19.6.** (£8.97½).

Micromatic



Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute and attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

Specifications:

Size: $36 \times 33 \times 13$ mm ($1\frac{4}{5} \times 1\frac{3}{10} \times \frac{1}{2}$ in.)
 Weight: including batteries, 28.4 gm (1 oz.).
 Case: Black plastic with anodised aluminium front panel and spun aluminium dial.
 Tuning: medium wave band with bandspread at higher frequencies, (550 to 1,600 Hz).
 Earpiece: Magnetic type.
 On/off switching: By inserting and withdrawing earpiece plug.
 Kit in pack with earpiece, case, instructions and solder **49/6** (£2.47½).
 Ready built, tested and guaranteed, with earpiece **59/6** (£2.97½).
 Two Mallory Mercury batteries type RM675 required. From radio shops, chemists, etc.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

Name _____

Address _____

for which I enclose cash/cheque/money order.

Sinclair Radionics Ltd., London Road
 St. Ives, Huntingdonshire PE17 4HJ.
 Tel: St. Ives (046 06) 4311

sinclair

SOUND 71

International

Exhibition of equipment for the industrial & entertainment fields

CAMDEN TOWN HALL (opposite St. Pancras Station) LONDON
MARCH 16-19 1971 ● 1000 HRS-1800 HRS DAILY (Final day 1000 hrs-1700 hrs)

Late night opening Wednesday to 20.00 hrs.

Admission free by trade card or by ticket from :
The Association of Public Address Engineers,
394 Northolt Road, South Harrow, Middlesex, HA2 8EY.
Telephone : 01-864 3405/6

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY-
Get these air drying **GREY HAMMER**
NOW! OR **BLACK WRINKLE**
(CRACKLE) finishes

Yukan Aerosol spraykit contains 453g fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue, Modern Eggshell Black Wrinkle (Crackle) all at 85p at our counter or 90p carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (339g self-spray cans only) 75p carriage paid.

SPECIAL OFFER! 1 can plus optional transferable snap-on trigger handle (value 25p) for 96p carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:
DEPT: K2 YUKAN, 307a, EDGWARE ROAD, LONDON, W2 1BN

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations - We can supply you too.


Open all day Saturday. Closed Thursday afternoons.



**The most accurate
pocket size
CALCULATOR
in the world**

The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4.25 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

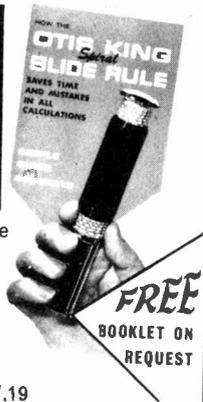CARBIC LTD. (Dept. K2)
54 Dundonald Road, London, S.W.19



**You should read the
Goodmans
High Fidelity Manuals**

Goodmans High Fidelity Manuals are of vital interest to you, and contain constructive and informative articles on all aspects of High Fidelity sound.

One manual contains specifications, descriptions and full colour illustrations of the entire current range of loudspeaker cabinets, systems, amplifiers and F.M. tuners. The construction manual contains the information needed by those enthusiasts who prefer to make their own High Fidelity or musical instrument loudspeaker systems.

These manuals are available free from

Goodmans Loudspeakers Limited
Axiom Works Lancelot Road Wembley Middx. Tel: 01-902 1200

Please send me:
Full colour manual (Tick as required)
Construction manual

Name _____
Address _____

P.E.3

TRANSISTORS
BRAND NEW FULLY GUARANTEED
NEW TYPES—NEW PRICES
SEND FOR FREE COPY TODAY

2N404	22p	BAV38	17p	BY100	15p
2N496	17p	BC107	12p	BY127	20p
2N697	17p	BC108	12p	BY182	85p
2N706	10p	BC109	12p	BY211	40p
2N706A	12p	BC113	25p	BY210	35p
2N930	25p	BC114	35p	BY211	35p
2N1131	30p	BC115	32p	BY212	30p
2N1132	30p	BC116	40p	BY213	25p
2N1302	20p	BC116A	37p	BY214	10p
2N1303	22p	BC119	37p	GET102	30p
2N1304	25p	BC119	50p	GET111	40p
2N1305	25p	BC134	37p	GET880	37p
2N1306	25p	BC135	30p	GET882	25p
2N1307	25p	BC136	35p	MAT100	25p
2N1308	30p	BC137	40p	MAT101	30p
2N1309	25p	BC138	40p	MAT120	25p
2N1613	32p	BC147	17p	MAT121	30p
2N1711	25p	BC148	12p	MJ2801	£1.37
2N2147	75p	BC149	20p	MJ2901	£2.25
2N2160	65p	BC154	37p	MJE370	97p
2N2218	30p	BC157	20p	MJE250	87p
2N2219	32p	BC158	17p	MJE2955	70p
2N2222	32p	BC159	15p	MJE2955	£1.37
2N2262A	37p	BC177	25p	MJE3055	87p
2N2369	20p	BC178	25p	MPF102	42p
2N2484	35p	BC179	27p	MPF103	35p
2N2646	50p	BCY30	25p	MPF104	37p
2N2904	30p	BCY31	30p	MPF105	40p
2N2904A	32p	BCY32	30p	NKT213	23p
2N2905	37p	BCY33	30p	NKT214	25p
2N2906	30p	BCY34	30p	NKT216	37p
2N2906A	32p	BCY38	40p	NKT217	40p
2N2907	37p	BCY39	60p	NKT277	20p
2N2926	12p	BCY40	50p	NKT403	75p
2N3011	25p	BCY41	15p	NKT404	62p
2N3053	25p	BCY42	15p	OA5	10p
2N3054	30p	BCY43	15p	OA9	10p
2N3055	75p	BCY58	25p	OA10	25p
2N3525	£1.10	BCY59	25p	OA7	10p
2N3702	12p	BCY70	20p	OA70	10p
2N3703	12p	BCY71	30p	OA73	10p
2N3704	17p	BCY72	30p	OA79	70p
2N3705	17p	BCY78	30p	OA81	10p
2N3707	15p	BCY79	30p	OA85	12p
2N3709	12p	BCZ10	35p	OA90	10p
2N3710	12p	BCZ11	40p	OA91	7p
2N3819	35p	BD112	50p	OA95	7p
2N3820	60p	BD121	60p	OA97	7p
2N4058	50p	BD123	80p	OA202	10p
2N4061	15p	BD124	62p	OC16	50p
2N4547	35p	BD125	50p	OC20	97p
2N4548	37p	BD131	75p	OC23	60p
2N4549	50p	BD132	85p	OC24	60p
2N5301	50p	BD153	62p	OC24	60p
2N5302	50p	BD155	62p	OC25	60p
2N5303	40p	BDY10	£1.25	OC26	25p
2N5304	75p	BDY11	£1.62	OC28	62p
40250	50p	BDY17	£1.50	OC29	62p
40361	55p	BDY18	£1.75	OC35	50p
40362	60p	BDY19	£1.97	OC36	62p
AAV30	10p	BF061	£1.25	OC41	25p
AAV42	10p	BF062	£1.00	OC42	30p
AAZ13	12p	BF115	25p	OC43	40p
AAZ17	10p	BF152	30p	OC44	17p
AC107	37p	BF154	40p	OC45	15p
AC126	25p	BF158	30p	OC70	12p
AC127	25p	BF159	60p	OC71	15p
AC178	25p	BF171	30p	OC72	25p
AC178	25p	BF170	35p	OC73	30p
AC187	30p	BF173	30p	OC74	30p
AC188	30p	BF177	40p	OC75	25p
ACY17	30p	BF178	25p	OC76	25p
ACY18	25p	BF179	40p	OC77	40p
ACY19	25p	BF180	37p	OC81	25p
ACY20	32p	BF181	37p	OC82	25p
ACY21	22p	BF182	32p	OC83	25p
ACY22	17p	BF184	25p	OC84	25p
ACY30	50p	BF185	25p	OC139	25p
ACY40	15p	BF194	17p	OC140	37p
AD140	50p	BF195	15p	OC141	62p
AD149	50p	BF196	15p	OC170	25p
AF161	37p	BF197	15p	OC171	30p
AF162	37p	BF200	37p	OC200	60p
AF114	25p	BF274	37p	OC201	60p
AF115	25p	BFV87	25p	OC202	75p
AF116	25p	BFV88	25p	OC203	40p
AF117	25p	BFV89	20p	OC204	40p
AF118	62p	BFV90	22p	OC205	75p
AF124	25p	BFV91	20p	OC206	90p
AF125	20p	BFX13	25p	OC207	90p
AF126	17p	BFX29	30p	OC271	97p
AF127	17p	BFX30	32p	ORP12	50p
AF128	17p	BFX31	32p	ORP13	50p
AF129	30p	BFX37	32p	ORP60	40p
AF178	47p	BFX40	37p	ORP61	42p
AF179	47p	BFX45	40p	ZTX107	15p
AF180	52p	BFX86	32p	ZTX300	12p
AF181	42p	BFX87	32p	ZTX500	20p
AF186	40p	BFX88	30p	ZTX503	20p
AF239	42p	BFY18	30p	ZTX531	30p
ASV26	25p	BFY20	30p		
ASV27	32p	BFY51	20p		
ASV28	25p	BFY52	22p		
ASV29	30p	BFY53	17p		
ASV67	47p	BFY64	42p		
AS221	42p	BFY90	65p		
BA115	7p	BSX20	17p		
BA164	17p	BSY51	37p		
BAX13	6p	BSX76	15p		
BAX16	7p	BSY95	15p		
BAX31	7p	BSY95A	15p		

HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW CERAMIC FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS

Part No.	Description	Price 1-49	Price 50-99	Price 100+	Price 500+
7400	Quad 2-Input NAND Gate	25p	20p	18p	15p
7401	Quad 2-Input NAND Gate Open Collector	25p	20p	18p	15p
7402	Quad 2-Input Positive Nor Gate	25p	20p	18p	15p
7404	HEX Inverter	25p	20p	18p	15p
7405	HEX Inverter With Open Collector	25p	20p	18p	15p
7410	Triple 3-Input NAND Gate	25p	20p	18p	15p
7430	Single 8-Input NAND Gate	25p	20p	18p	15p
7440	Dual 4-Input Buffer Gate	25p	20p	18p	15p
7441	BCD To Decimal Decoder and NIX Driver	£1.00	90p	80p	75p
7442	BCD To Decimal Decode (TTL)	£1.00	90p	80p	75p
7443	Dual 2-Input And/Or/Not Gate—Expandable	25p	20p	18p	15p
7453	Single 8-Input And/Or/Not Gate—Expandable	25p	20p	18p	15p
7460	Dual 4-Input—Expandable	25p	20p	18p	15p
7470	Single JK Flip Flop—Edge Triggered	40p	35p	30p	25p
7472	Single Master Slave JK Flip Flop	40p	35p	30p	25p
7473	Dual Master Slave JK Flip Flop	45p	40p	35p	30p
7474	Dual D Flip Flop	45p	40p	35p	30p
7475	Quad Bistable Latch	50p	45p	40p	35p
7476	Dual Master Slave Flip Flop With Preset	50p	45p	40p	35p
7483	Four Bit Binary Counter	£1.00	90p	80p	75p
7490	BCD Decode Binary	£1.00	90p	80p	75p
7492	Divide by 12, 4 Bit Binary Counter	£1.00	90p	80p	75p
7493	Divide by 16, 4 Bit Binary Counter	£1.00	90p	80p	75p
7494	Binary 4 Bit Shift Register	£1.00	90p	80p	75p
7495	4 Bit Up Down Shift Register	£1.00	90p	80p	75p
7496	5 Bit Shift Register	£1.00	90p	80p	75p

Data available for above series in booklet form, price 10p. Larger quantity prices, Extn. 4. Dual In-line 14-pin Sockets 30p each. 16-pin 35p each.

TRIACS GENERAL ELECTRIC

P.I. Cur. Volts	Cur. 1-49	(All stud mounting)	50+	100+	500+
SC35A	100	3A	90p	75p	65p
SC35B	200	3A	95p	80p	70p
SC35D	400	3A	£1.00	85p	75p
SC40A	100	6A	£1.00	85p	75p
SC40B	200	6A	£1.20	£1.00	85p
SC40D	400	6A	£1.25	£1.10	£1.00
SC45A	100	10A	£1.25	£1.10	£1.00
SC45B	200	10A	£1.35	£1.20	£1.10
SC45D	400	10A	£1.50	£1.35	£1.20
SC50A	100	15A	£1.65	£1.50	£1.35
SC50B	200	15A	£1.75	£1.60	£1.45
SC50D	400	15A	£2.00	£1.75	£1.60
SC40E	500	6A	£1.50	£1.25	£1.10
SC45E	500	10A	£1.75	£1.50	£1.35
SC50E	500	15A	£2.25	£2.00	£1.75

DIAC ST2 20p
Larger Quantity Prices on Application, Extn. 4.

R.C.A. INTEGRATED LINEAR TYPES

CA3005	£1.20	CA3035	£1.25
CA3011	75p	CA3036	90p
CA3012	90p	CA3039	85p
CA3013	£1.10	CA3041	£1.10
CA3014	£1.45	CA3042	£1.10
CA3018	£1.10	CA3043	£1.40
CA3020	£1.25	CA3044	£1.25
CA3021	£1.55	CA3045	£1.35
CA3022	£1.30	CA3046	85p
CA3023	£1.25	CA3048	£1.25
CA3026	£1.00	CA3051	£1.35
CA3028A	£1.20	Application notes	10p for each type

INTEGRATED CIRCUITS

PA246	5 Watt	£2.65
TA263	Mullard	75p
TAD100	Mullard	£2.00
TAD110	Mullard	£2.00
MCI303	Motorola	£2.60
UL900	Fairchild	40p
UL914	Fairchild	40p
UL923	Fairchild	60p
LA709C	Fairchild	75p
MCI304	Motorola	£2.75

ZENER DIODES

400M/W 5% MINATURE	1 WATT 5% PLASTIC WIRE ENDS
BZY88 range all voltages 3.3V-33V 15p each	6-8V all voltages 25p each
100 + 10p	25 + 20p
500 + 9p	100 + 18p
1000 + 8p	500 + 16p
any one type	1000 + 15p
	any one type

3 WATT PLASTIC WIRE ENDS
5%
All voltages 6-8-100V 30p each
100 + 25p
500 + 23p
1000 + 21p
any one type

7 WATT STUD MOUNTING
5%
All voltages 5-1V-100V 40p each
25 + 35p
100 + 30p
any one type

POWER RECTIFIERS SILICON RECTIFIERS STUD MOUNTING 6 AMP RANGE

P.I.V.	1-49	50+	100+	500+
BYZ10	800	400	35p	30p
BYZ11	600	35p	30p	25p
BYZ12	400	30p	25p	20p
BYZ13	200	25p	20p	17p

10 AMP RECTIFIERS

SK103	100	45p	40p	37p
SK203	200	50p	45p	42p
SK403	400	55p	50p	45p
SK603	600	60p	55p	50p
SK803	800	75p	70p	65p

15 AMP RECTIFIERS

SL1	100	50p	45p	45p
SL2	200	60p	55p	50p
SL4	400	65p	60p	55p
SL6	600	75p	70p	65p
SL8	800	90p	85p	80p

SEMICONDUCTORS
LOOK AT THESE PRICES FOR QUANTITIES FROM STOCK

AF114	25p	Mullard 25 + 20p 100 + 17p
AF115	25p	Mullard 25 + 20p 100 + 17p
AF116	25p	Mullard 25 + 20p 100 + 17p
AF117	25p	Mullard 25 + 20p 100 + 17p
2N3055	75p	Mullard 115W Silicon Power 25 + 65p 100 + 55p
2N3819	35p	Texas Instruments 100 + 30p 25 + 25p 500 + 23p
BFY90	65p	Motorola 1000MC/S 25 + 60p 100 + 52p 500 + 48p
2N2646	50p	Motorola 100 + 37p 500 + 33p
AF139	30p	Siemens V.H.F. 100 + 22p 500 + 19p
AF186	40p	Mullard V.H.F. 25 + 35p 100 + 30p 500 + 25p
OC170	25p	25 + 21p 100 + 17p 500 + 15p
BYZ13	25p	Mullard 6A 200V 25 + 20p 100 + 17p 500 + 15p
OC171	30p	25 + 27p 100 + 22p
BC107, BC108, BC109	12p	I.T.T. Planars 25 + 11p 100 + 10p 500 + 8p 1000 + 6p
BY127	20p	Mullard I.000V 1 amp Plastic 25 + 17p 100 + 15p
BC113	25p	5GS 25 + 20p 100 + 17p 500 +


TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7" 4in speaker. Air spaced gauged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9" 7" 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 25p (5/-) (FREE with parts).

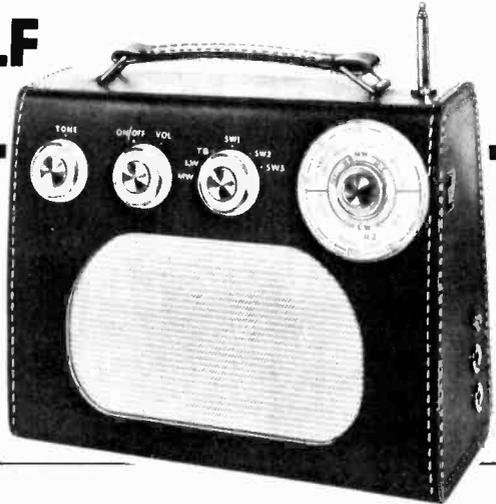Total building costs **£6.98** P. & P. Overseas
38p (7/7) P. & P.
(£6.19.7) 85p (17/-)



roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7" 4in P.M. speaker. Air spaced gauged tuning condenser. Volume on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9" 7" 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (3/-) (FREE with parts).




Total building costs **£5.98** P. & P. Personal Earpiece with switched socket for
38p (7/7) private listening. 25p (5/-) extra.
(£5.19.7)
Overseas P. & P. 85p (17/-)

NEW! transeight

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9" 5 1/2" 2 1/2in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (5/-) (FREE with parts).

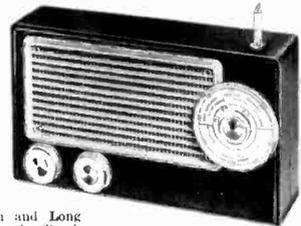


Total building costs **£4.48** P. & P. Earpiece with switched socket for private
28p (5/7) listening 25p (5/-) extra.
(£4.9.7)
Overseas P. & P. 65p (13/-)

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

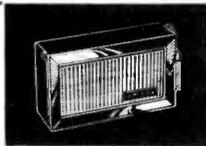Attractive black and gold case. Size 5 1/2" 1 1/2" 3 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (1/7) (FREE with parts).



Total building costs **£2.23** P. & P.
18p (3/7)
(£2.4.7)
Overseas P. & P. 50p (10/-)

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2" 4 1/2" 1 1/2in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (1/7) (FREE with parts).



Total building costs **£2.38** P. & P.
19p (3/9)
(£2.7.7)
Overseas P. & P. 50p (10/-)

IMPROVED MODEL! roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9" 5 1/2" 2 1/2in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—5 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (2/-) (FREE with parts).



Total building costs **£3.98** P. & P.
23p (4/7)
(£3.19.7)
Overseas P. & P. 65p (13/-)

RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £ please send items marked

ROAMER EIGHT ROAMER SEVEN
TRANSEIGHT POCKET FIVE
TRANSONA FIVE ROAMER SIX

Parts price list and plans for

Name

Address

* Callers side entrance Stylo Shoe Shop
* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PE 27


R+TV

RADIO & TV COMPONENTS (Acton) Ltd.

Post to: 21d High St., Acton, London W3 6NG
 Personal shoppers to 323 Edgware Road, London, W.2
ALL ORDERS BY POST TO OUR ACTON BRANCH
 Terms C.W.O. All enquiries S.A.E.

Complete Stereo System £43

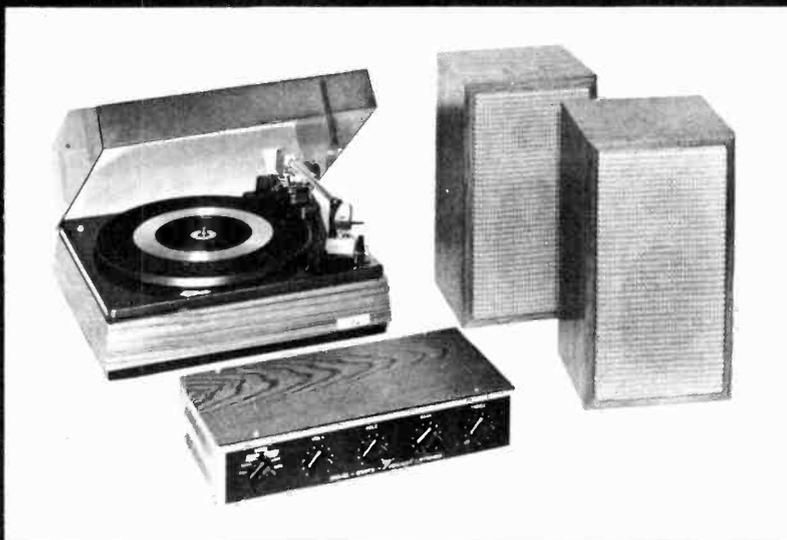WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER




This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½ in. x 10½ in. x 6½ in., the Duo type 2 speakers are teak finished with matching Vynair grills. They incorporate a 3 ohm 13in. x 8in drive unit with parasitic tweeter. Maximum power hardly 10 watts, price:

£13.50 per pair plus £1.50 P. & P.

Complete stereo system £43 plus P. & P. £2.50

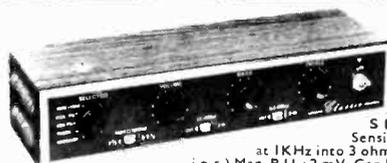With Mk. II Amplifier and Magnetic Cartridge £48 plus P. & P. £2.50



The Classic

Simulated teak case

£9.50

Plus P. & P. 50p

SPECIFICATION:

Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape Head: 3mV (at 3½ i.p.s.) Mag. P.U.: 2 mV. Cer. P.U.: 80mV. Tuner: 100mV. Aux. 100mV. Tape/Rec. Output. Equalisation for each input is correct to within +2dB (R.I.A.A.) from 20Hz to 20KHz. Tone Control Range: Bass: 13dB at 60Hz. Treble: ±14dB at 15KHz. Total Distortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V. Size 12½ in long, 4½ in deep, 2½ in high. Built and tested.



THE RELIANT Mk. II

SOLID STATE GENERAL PURPOSE AMPLIFIER

£7.25 Plus P. & P. 37p

Simulated teak case

SPECIFICATION:

Output: 10 watts into a 3 ohms speaker. Inputs: (1) for mike (10mV). Input (2) for gram. radio (250mV). Transistors: 4 silicon and three germanium. Mains input: 220/250 volts. Size: 10½ x 4½ x 2½ in.



ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. MAINS POWER PACK KIT: 9/6 (47p) extra.

£5.25 Plus P. & P. 37p. Circuit 13p Free with parts.

THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3 in. MAINS POWER PACK KIT: 47p extra. £5.25 Plus P. & P. 37p. Circuit 13p. Free with parts.



The Viscount F.E.T. Mk. I £14.25

Plus 50p P.&P.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

SPECIFICATION

Output per channel—10W rms. into 3 ohms. Frequency bandwidth 20Hz to 20kHz ±1dB @ 1W. Total distortion @ 1kHz @ 9W 0.5%. Input sensitivities—CER. P.U. 100mV into 3 MΩ. Tuner 100mV into 100kΩ. Tape 100mV into 100kΩ. Overload factor—Better than 26dB. Signal to noise ratio—70dB on all inputs (with vol. max).

Controls—6 position selector switch (3 pos. stereo and 3 pos. mono), separate vol. controls for left and right channels. Bass ±14dB @ 60Hz; Treble (with D.P.S. on/off) ±12dB @ 10kHz. Tape recording output sockets on each channel.

Size 12½ in x 6 in x 2½ in simulated teak case. Built and tested.

Mk. II (MAG. P.U.) £15.75 Post & packing 50p extra. Specification same as Mk. I, but with the following inputs: Mag. P.U. CER. P.U. Tuner.

Spec. on Mag. P.U. 3mV @ 1kHz input impedance 47kΩ. Fully equalised to within ±1dB RIAA. Signal to noise ratio—65dB (vol. max.).


LIQUIDATED STOCK

DANSETTE

TOURISTE MK3

CAR RADIO

ALL TRANSISTOR

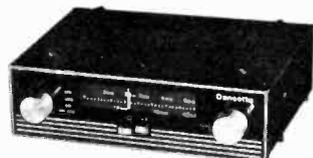

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" x 2" x 4½" deep.

Originally sold completely built for £15.4.6 (£15.23)

SET OF PARTS

Circuit diagram 13p, free with parts Speaker, baffle and fixing kit £1.25 extra plus P. & P. 20p

plus 37p P. & P. £6.30

Speaker postage free when ordered with parts

SOUND 50


SOUND 50 AMPLIFIER AND SPEAKER SYSTEM

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power 45 watts R.M.S. (Sine wave drive). **Frequency response**—3db points 30 Hz at 18 KHz. **Total distortion** less than 2% at rated output. **Signal to noise ratio:** better than 60db. **Speaker Impedance** 3, 8 or 15 ohms. **Bass Control Range** ±13db at 60 Hz. **Treble Control Range** ±12db at 10 KHz. **Inputs** 4 inputs at 5 mV into 470 K. Each pair of inputs controlled by separate volume control. 2 inputs at 200 mV into 470 K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

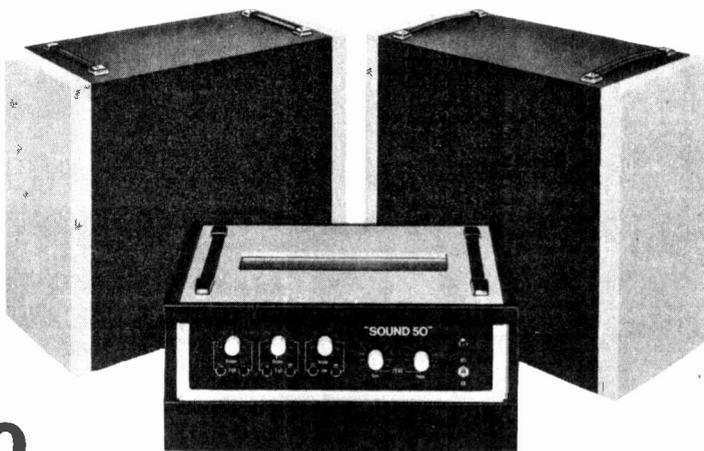SPEAKERS—Size 20" x 20" x 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.



COMPLETE SYSTEM £50

plus £4 P. & P.

Amplifier £28-50 plus £1 P. & P.

Speakers each £12-50 plus £1-50 P. & P.

RADIO & TV COMPONENTS (ACTON) LTD.


21d High Street, Acton, London W3 6NG

Personal shoppers to 323 Edgware Road, London, W.2

Goods not despatched outside U.K.

Terms C.W.O.

All Enquiries S.A.E.

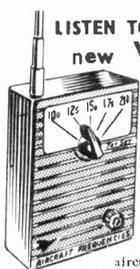

LISTEN TO AIRCRAFT COMMUNICATIONS

new V.H.F. AIRCRAFT BAND CONVERTER

ONLY £2-37½


(47/6)

Listen in to AIRLINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting cross-talk between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tensions on take-downs. Be with them when they have to take nerve-racking decisions in emergencies—tune in to the international distress frequency. Covers aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC.

This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4½in x 3in x 1½in. All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny pocket radios). **NO CONNECTIONS WHATSOEVER NEEDED.** Use indoors or outdoors. **SEND NOW.** ONLY £2-37½ + 22p for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately).

REAL WORKING ELECTRONIC ORGAN ONLY £2-75

(55/-)

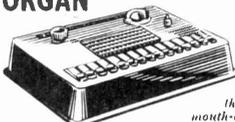

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised, no valves. **Proper self-contained loudspeaker.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", "Silent Night", "Auld Lang Syne", and lots of similar tunes on this real working electronic organ. Size 13½in x 10in x 2½in. Uses standard battery. Have the thrill and excitement of building it together with the pleasure of playing a real electronic organ. **Play it anywhere.** No soldering necessary. Easy as A.B.C. to make following the fully illustrated, step-by-step instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low price. ONLY £2-75 + 22p P. & P. (55/- + 4/6) for all parts, including case, loudspeaker, transistor, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, instructions, etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

FIND BURIED TREASURE! TREASURE LOCATOR—

NOW IT'S HERE AT LAST,



after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location (no phones used—uses only transistor radio which clips inside—no connections needed). **FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAX SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! Can be built with ease in one short evening with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions. Fully transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13½in x 10in x 2½in. **Great demand expected at this remarkably low price—All parts including detector head, case, nuts, screws, wire, simple instructions, etc. Send now £2-37½ + 32p P. & P. (47/6 + 6/6)** (Telescopic handle as illustrated £1-25 (25/-) extra). Parts available separately. Made up looks worth £15.

ONLY £2-37½

(47/6)

MAKE 5 PROJECTS INCLUDING 3 TRANSISTOR LOUDSPEAKER RADIO



LIMITED QUANTITY £1-97½

(39/6)

Amazing Radio Construction set for £1-97½ (39/6). A complete Home Radio Course. No experience needed. Parts including

simple instructions for each design. Illustrated Step-by-Step plans, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation Box size 14in x 10in x 2½in 37½p extra (7/6) if reqd. (parts avail. separately). Send only £1-97½ + 22p P. & P. (39/6 + 4/6).

Examine at home for 7 days. Your money back if not delighted.

CONCORD ELECTRONICS LTD.

SHORTWAVE TRANSISTOR RADIO

ONLY £2-25

(45/-)



CAN BE BUILT IN ONE EVENING At last! After trying countless circuits searching for easy build, work-first-time short waver. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 75 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. **Eavesdrop on unusual broadcasts.** Uses PP3 battery. Transistorised (no valves). Size only 3in. x 4½in. x 1½in. As tremendous demand anticipated price held to only £2-25 + 17½p P. & P. (45/- + 3/6) for all parts incl. Cabinet, screws, instr., etc. Parts available separately.

(P.E.16) 8 WESTBOURNE GROVE LONDON W.2
(Near Bayswater Tube) Callers welcome. 9-6 including Saturdays

BRAND NEW

SEMICONDUCTORS & COMPONENTS

GUARANTEED

TRANSISTORS

2G301	20p	2N3405	45p	40309	32p	BC172	15p	BSW70	27p	NKT238	25p
2G302	20p	2N3414	22p	40310	45p	BC175	22p	BSX19	17p	NKT240	27p
2G303	20p	2N3415	22p	40311	35p	BC182	12p	BSX20	17p	NKT241	27p
2G306	42p	2N3416	37p	40312	47p	BC183	12p	BSX21	37p	NKT242	27p
2G308	30p	2N3417	37p	40314	37p	BC184	15p	BSX26	45p	NKT243	27p
2G309	30p	2N3570	21p	40315	47p	BC211L	12p	BSX27	47p	NKT244	27p
2G371	30p	2N3572	97p	40323	37p	BCY30	27p	BSX28	37p	NKT245	27p
2G374	30p	2N3605	27p	40324	47p	BCY31	27p	BSX60	82p	NKT261	20p
2G381	22p	2N3606	27p	40326	37p	BCY32	37p	BSX61	27p	NKT262	30p
2N404	22p	2N3607	22p	40329	30p	BCY33	20p	BSX76	22p	NKT264	20p
2N686	20p	2N3702	12p	40344	27p	BCY34	22p	BSX77	22p	NKT271	20p
2N697	20p	2N3703	12p	40347	40p	BCY38	22p	BSX78	27p	NKT272	20p
2N698	25p	2N3704	17p	40348	52p	BCY39	52p	BSX78	27p	NKT274	20p
2N706	12p	2N3705	15p	40360	42p	BCY40	37p	BSY10	27p	NKT275	20p
2N706A	12p	2N3706	12p	40361	47p	BCY42	15p	BSY11	27p	NKT281	27p
2N708	15p	2N3707	15p	40362	57p	BCY43	15p	BSY24	15p	NKT401	87p
2N709	62p	2N3708	9p	40370	32p	BCY54	32p	BSY25	15p	NKT402	80p
2N718	25p	2N3709	10p	40406	57p	BCY58	22p	BSY26	17p	NKT403	75p
2N726	30p	2N3710	11p	40407	22p	BCY59	22p	BSY27	17p	NKT404	62p
2N727	30p	2N3711	12p	40408	52p	BCY60	67p	BSY28	17p	NKT405	75p
2N914	17p	2N3715	22-22	40410	62p	BCY70	20p	BSY29	17p	NKT406	62p
2N916	17p	2N3716	22-90	40467A	57p	BCY71	42p	BSY32	25p	NKT451	62p
2N918	30p	2N3791	22-75	40468A	35p	BCY72	17p	BSY39	25p	NKT452	62p
2N920	22p	2N3819	35p	40600	57p	BCZ10	27p	BSY37	25p	NKT453	47p
2N930	27p	2N3823	37p	AC126	15p	BCZ11	42p	BSY38	22p	NKT403F	32p
2N1090	22p	2N3824	37p	AC127	15p	BD116	11-12	BSY39	22p	NKT671F	32p
2N1091	22p	2N3834A	47p	AC107	15p	BD121	65p	BSY40	32p	NKT674F	30p
2N1181	25p	2N3855	27p	AC128	15p	BD123	82p	BSY51	32p	NKT677F	30p
2N1182	25p	2N3855A	30p	AC129	20p	BD124	60p	BSY52	32p	NKT773	30p
2N1302	17p	2N3856	30p	AC154	22p	BD131	97p	BSY53	32p	NKT781	30p
2N1303	17p	2N3856A	35p	AC176	25p	BD132	87p	BSY54	40p	NKT10419	40p
2N1304	22p	2N3856B	35p	AC187	82p	BDY11	11-12	BSY55	90p	NKT10439	37p
2N1305A	22p	2N3857A	30p	AC188	27p	BDY17	11-12	BSY78	47p	NKT10519	32p
2N1306	25p	2N3859	37p	AC177	37p	BDY18	11-12	BSY79	45p	NKT20329	47p
2N1307	25p	2N3859A	32p	AC128	20p	BDY19	11-12	BSY90	57p	NKT80111	77p
2N1308	30p	2N3860	30p	ACY19	25p	BDY20	11-97	BSY95A	12p	NKT80112	77p
2N1309	30p	2N3866	21-50	ACY20	25p	BDY38	87p	BDY60	82p	NKT80211	12-12
2N1507	17p	2N3877	40p	ACY21	25p	BDY61	82p	BDY62	21-25	C111	75p
2N1613	17p	2N3877A	40p	ACY22	20p	BDY62	21-25	BDY62	21-25	C124	40p
2N1631	35p	2N3900	37p	ACY28	20p	BDY61	82p	BDY62	21-25	C125	55p
2N1632	30p	2N3900A	40p	ACY29	20p	BDY62	21-25	BDY62	21-25	C126	40p
2N1637	30p	2N3901	97p	ACY41	25p	BDY61	82p	BDY62	21-25	C128	37p
2N1638	27p	2N3903	35p	ACY44	40p	BF117	47p	BF163	37p	C428	37p
2N1639	97p	2N3904	35p	AD140	52p	BF167	37p	BF167	37p	C744	30p
2N1711	25p	2N3905	25p	AD149	57p	BF173	32p	BF173	32p	D161	37p
2N1880	32p	2N3906	37p	AD150	57p	BF178	32p	BF178	32p	D162	40p
2N1893	37p	2N4058	17p	AD161	37p	BF178	32p	BF178	32p	D163	37p
2N2147	82p	2N4059	10p	AD162	47p	BF178	32p	BF178	32p	D164	40p
2N2148	57p	2N4060	12p	AF106	25p	BF178	32p	BF178	32p	D164	40p
2N2160	57p	2N4061	12p	AF114	25p	BF180	30p	BF180	30p	OC22	50p
2N2163	40p	2N4062	12p	AF115	30p	BF181	32p	BF181	32p	OC23	50p
2N2193A	42p	2N4244	47p	AF116	20p	BF184	42p	BF184	42p	OC24	50p
2N2194A	30p	2N4282	17p	AF116	20p	BF185	42p	BF185	42p	OC26	27p
2N2217	27p	2N4296	17p	AF117	25p	BF194	17p	GET102	30p	OC28	62p
2N2218	32p	2N4287	17p	AF119	20p	BF195	20p	GET113	20p	OC29	62p
2N2219	32p	2N4288	17p	AF124	20p	BF196	42p	GET114	20p	OC35	50p
2N2220	30p	2N4289	17p	AF125	20p	BF197	42p	GET115	20p	OC36	62p
2N2221	25p	2N4290	17p	AF126	20p	BF198	42p	GET116	20p	OC41	22p
2N2222	30p	2N4291	17p	AF126	20p	BF200	52p	GET120	52p	OC42	25p
2N2227	01-07	2N4292	12p	AF127	17p	BF224	20p	GET873	12p	OC44	20p
2N2229	30p	2N4303	47p	AF178	42p	BF225	20p	GET880	30p	OC45	15p
2N2368	17p	2N5027	52p	AF179	72p	BF237	22p	GET887	20p	OC46	15p
2N2369	17p	2N5028	87p	AF180	52p	BF238	22p	GET889	22p	OC47	15p
2N2369A	17p	2N5029	47p	AF181	42p	BF244	32p	GET890	22p	OC71	12p
2N2410	42p	2N5030	42p	AF181	42p	BFW38	27p	GET896	22p	OC72	12p
2N2483	27p	2N5172	12p	AF239	42p	BFW59	25p	GET897	22p	OC74	32p
2N2484	32p	2N5174	52p	AF280	20p	BFW60	25p	GET898	22p	OC75	22p
2N2539	22p	2N5175	52p	AFZ11	32p	BFW61	27p	GET898	22p	OC76	22p
2N2540	22p	2N5176	45p	ASY26	25p	BFX12	22p	OC77	30p	OC77	30p
2N2613	35p	2N5222A	40p	ASY27	37p	BFX28	30p	MJ400	01-07	OC80	25p
2N2614	30p	2N5223	45p	ASY28	27p	BFX30	30p	MJ420	01-12	OC81	25p
2N2646	57p	2N5248	42p	ASY29	27p	BFX30	30p	MJ421	01-12	OC82	25p
2N2696	32p	2N5249	67p	ASY29	27p	BFX43	37p	MJ430	01-02	OC83	25p
2N2711	25p	2N5265	22-25	ASY30	25p	BFX44	37p	MJ440	05p	OC89	32p
2N2712	25p	2N5266	22-75	ASY51	32p	BFX68	37p	MJ480	97p	OC130	32p
2N2713	27p	2N5267	22-62	ASY54	25p	BFX84	25p	MJ481	01-25	OC170	30p
2N2714	30p	2N5303	37p	ASY86	32p	BFX86	32p	MJ490	01-12	OC171	30p
2N2865	40p	2N5306	40p	ASZ20	37p	BFX86	32p	MJ491	01-37	OC200	37p
2N2904	30p	2N5307	37p	ASZ21	37p	BFX87	27p	MJ1800	22-17	OC201	47p
2N2904A	32p	2N5308	37p	AI103	42p	BFX88	25p	MJE340	82p	OC292	62p
2N2905	37p	2N5309	62p	AIY10	21-50	BFX89	62p	MJE520	87p	OC293	42p
2N2905A	40p	2N5310	42p	BFY10	32p	BFX93A	70p	MJE521	87p	OC294	42p
2N2906	25p	2N5354	27p	BFY11	42p	BFY10	32p	MPF102	42p	OC295	62p
2N2906A	27p	2N5355	37p	BFY11	42p	BFY11	42p	MPF103	37p	OC297	75p
2N2907	30p	2N5356	37p	BFY12	42p	BFY17	22p	MPF104	37p	OCP71	42p
2N2923	15p	2N5365	47p	BFY12	42p	BFY18	12p	MPF105	37p	ORP12	62p
2N2924	15p	2N5366	32p	BFY13	12p	BFY19	32p	MP83638	32p	ORP61	62p
2N2925	15p	2N5367	37p	BFY13	12p	BFY20	32p	NKT0013	47p	P340A	22p
2N2926	15p	2N5457	37p	BFY21	17p	BFY21	17p	NKT124	42p	T1P29A	50p
Green	12p	280045	55p	BC118	32p	BFY24	45p	NKT125	27p	T1P30A	50p
Yellow	12p	28020	22p	BC121	20p	BFY25	25p	NKT126	27p	T1P31	50p
Orange	12p	28102	50p	BC122	20p	BFY26	20p	NKT127	27p	T1P32	50p
2N3011	30p	28103	25p	BC125	55p	BFY29	50p	NKT128	27p	T1P33A	50p
2N3014	32p	28104	25p	BC126	55p	BFY30	50p	NKT129	27p	T1P34	50p
2N3033	25p	28105	32p	BC140	37p	BFY43	62p	NKT130	32p	T1P35	50p
2N3054	50p	28502	35p	BC147	42p	BFY48	62p	NKT131	32p	T1P36	50p
2N3055	75p	28503	27p	BC148	12p	BFY50	22p	NKT132	30p	T1P37	50p

ENAMELLED COPPER WIRE

S.W.G.	½lb. Reel	1lb. Reel
18-22	62½p	92½p
23-30	65p	97½p
31-35	67½p	£1 02½
36-40	82½p	£1 32½
41-44	97½p	£1 62½

Orders despatched by return of post.

Please add 12½p per item P. and P.

Supplied by:

BANNER TRANSFORMERS
(Dept. PE), Brooks Street
Higher Hillgate, Stockport, Cheshire

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94,
Set of 4 for £1-02, DAF96, DF96, DK96, DL96, 4 for £1-45

Set	5p	5p	5p	5p	5p	5p	5p				
1A7GT	0-37	25U4GT	0-57	DL92	0-28	EL90	0-26	PCL82	0-36	UCB41	0-52
1H5GT	0-38	30C1	0-32	DL94	0-37	EL500	0-62	PCL83	0-60	UBF80	0-28
1N5GT	0-38	30C15	0-63	DL96	0-36	EM80	0-41	PCL84	0-37	UBF89	0-33
1R5	0-28	30C17	0-80	DY86	0-28	EM81	0-41	PCL85	0-45	UCQ84	0-35
1S5	0-21	30C18	0-47	DY87	0-28	EM84	0-33	PCL86	0-41	UCQ85	0-36
1T4	0-16	30F5	0-76	EAB'80	0-32	EM87	0-37	PCL88	0-72	UCF80	0-36
3S4	0-28	30FL1	0-63	EAF42	0-50	EY51	0-36	PCL800	0-77	UCH42	0-62
3V4	0-37	30FL12	0-72	EB91	0-11	EY86	0-32	PEN44	0-42	UCH81	0-32
5Y3GT	0-30	30FL14	0-72	EBC33	0-40	EZ40	0-43	PEN366	0-70	UCL82	0-35
2Z4G	0-37	30L1	0-32	EBC41	0-52	EZ41	0-43	PFL200	0-58	UCL83	0-55
6/90L2	0-58	30L15	0-85	EBC80	0-22	EZ80	0-23	PL38	0-48	UF41	0-62
6AL5	0-11	30L17	0-73	EBF80	0-33	EZ81	0-24	PL81	0-46	UF80	0-33
6AM6	0-13	30P4	0-65	EBF89	0-31	EZ82	0-43	PL81A	0-51	UL41	0-60
6AQ5	0-26	30P12	0-77	ECC81	0-18	EZ84	0-48	PL82	0-30	UL84	0-35
6AT6	0-22	30P19	0-65	ECC82	0-23	KT41	0-77	PL83	0-35	UM80	0-22
6AU6	0-22	30PL1	0-63	ECC83	0-35	KT61	0-48	PL84	0-32	UM84	0-25
6BA6	0-22	30PL13	0-88	ECC85	0-28	KT66	0-83	PL500	0-65	UY41	0-41
6BE6	0-26	30P14	0-70	ECC84	0-60	LN319	0-63	PL504	0-67	UY85	0-28
6BJ6	0-42	30PL15	0-72	ECCF80	0-30	LN329	0-72	PM84	0-37	VP48	0-77
6BW7	0-60	35L6GT	0-43	ECCF82	0-30	LN339	0-63	PX25	1-17	W119	0-35
6CD6G	1-10	35W4	0-22	ECH35	0-30	N78	0-87	PY32	0-55	Z77	0-22
6F14	0-45	35Z4GT	0-25	ECH42	0-63	PABC80	0-35	PY33	0-55	Transistors	
6F23	0-73	807	0-45	ECH81	0-28	PC86	0-51	PY81	0-28	AC107	0-17
6F25	0-62	6063	0-62	ECH83	0-41	PC88	0-51	PY82	0-26	AC127	0-18
6K7G	0-12	60YP2	0-47	ECL80	0-35	PC97	0-40	PY83	0-28	AD140	0-37
6K8G	0-17	AZ31	0-47	ECL80	0-35	PC97	0-40	PY88	0-34	AF115	0-20
6SL7GT	0-27	B349	0-65	ECL82	0-33	PC900	0-37	PY800	0-37	AF116	0-20
6V6G	0-17	B729	0-62	ECL86	0-40	PC984	0-32	PY801	0-37	AF117	0-20
6V6GT	0-32	CCH35	0-67	EF39	0-23	PC985	0-30	R19	0-32	AF118	0-48
6X4	0-23	CL33	0-92	EF41	0-58	PC988	0-46	R20	0-68	AF125	0-17
6X5GT	0-28	CY31	0-53	EF80	0-23	PC989	0-47	T25	0-68	AF127	0-17
10P18	0-35	DAC92	0-36	EF85	0-31	PCC189	0-45	U47	0-68	OC26	0-25
10P13	0-60	DAF91	0-21	EF85	0-31	PCC189	0-45	U47	0-68	OC44	0-12
12AH8	2-25	DAF96	0-30	EF86	0-31	PCC805	0-65	U49	0-68	OC45	0-12
12AT7	0-18	DF33	0-38	EF89	0-26	PCF80	0-32	U78	0-24	OC71	0-12
12AU6	0-23	DF91	0-16	EF91	0-18	PCF82	0-32	U191	0-62	OC72	0-12
12AU7	0-23	DF96	0-36	EF183	0-28	PCF86	0-47	U193	0-42	OC75	0-12
12AX7	0-23	DI77	0-22	EF184	0-32	PCF800	0-67	U251	0-72	OC81	0-12
198B6G	0-37	DK32	0-37	EF190	0-42	PCF801	0-32	U301	0-55	OC81D	0-12
20P2	0-67	DK91	0-28	EL33	0-48	PCF802	0-45	U329	0-72	OC82D	0-12
20P3	0-85	DK92	0-42	EL34	0-47	PCF805	0-67	U801	0-98	OC82	0-12
20P4	0-92	DK96	0-36	EL41	0-55	PCF806	0-58	UABC80	0-32	OC82D	0-12
25L6GT	0-25	DL35	0-25	EL84	0-24	PCF808	0-72	UAF42	0-51	OC170	0-22

READERS RADIO (P.E.)
85 TORQUAY GARDENS, REDBRIDGE, ILFORD,
ESSEX. Tel. 01-550 7441

Postage on 1 valve 5p extra. On 2 valves or more, postage 3p per valve extra. Any Parcel Insured against Damage in Transit 3p extra.

If you can put a 'Yes' in every box, you might just make a RADIO TECHNICIAN in Air Traffic Control

An all-consuming interest in telecommunications

At least one year's practical experience in telecommunications, preferably with 'ONC' or 'C and G' technical qualifications

A highly developed sense of responsibility

Willingness to undergo a rigorous programme of training

Aged 19 or over

To the right man, the National Air Traffic Control Service offers the prospect of an interesting and steadily developing career as a Radio Technician in air traffic control.

The work involves the installation and maintenance of some of the very latest electronic equipment at civil airports, radar stations and other specialist establishments all over the country. Important today, the job will become increasingly vital as Britain's air traffic continues to grow, and prospects for promotion are excellent. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over). Scale maximum £1590 (higher rates at Heathrow). The annual leave allowance is good, and there is a non-contributory pension for established staff.

If you feel you can meet the demands of this rather special job—and you have a strong determination to succeed—you are invited to complete the coupon below.

Send this coupon for full details and application form
To: A J Edwards, C Eng, MIEE, The Adelphi,
Room 705, John Adam Street, London WC2N 6BQ,
marking your envelope 'Recruitment'.

Name

Address

PET, G4

Not applicable to residents outside the United Kingdom

NATCS

National Air Traffic Control Service

Practical Electronics Classified Advertisements

RATES: 7½p per word (minimum 12 words). Box No. 7½p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

MISCELLANEOUS

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'
DEPT. K2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

NEW! NEW!! NEW!!!

The Sweetest Sound You Ever Heard

An exciting new, all silicon, power amplifier module to a completely NEW design. Minimum cross-over distortion, not dependent on supply voltage, eliminates unpleasant 'transistor sound'. Specially designed to work well from simple, unregulated power supply, 50-58 v. 11 transistors, short circuit proof, unconditionally stable, temperature stabilised. 400 m/v input for 30 watts RMS (8 ohms). Output impedance 8-16 ohms. Completely built on 16 swg heatsink. Neat, space-saving, upright mounting. Fully tested and guaranteed with comprehensive instructions.

£8.75 each. P. & P. 25p. Stereo pair. Post free

ELECTRONIC SUPPLIES

P.O. BOX 148, SHEFFIELD S17 3EX

HOLIDAY FOR BOYS. 14/16 years August 1971, specialising in engineering, electronics, photography. Tuition and practical work including karting. 11 days—£15. Write for free brochure: INTER-SCHOOL CHRISTIAN FELLOWSHIP, 47 Marylebone Lane, London, W1M 6AX.

CIRCUIT BOARD ETCHING KITS, full instructions, £1. C.W.O. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

MUSICAL MIRACLES

WAA-WAA Pedal. Complete kit of all parts, robust cabinet, mechanism and instructions. Huge sales, well proven design. Only £2.45 complete. Or built and tested £4.75 post free.
Rhythm Box. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtrox, etc., costs under £17.
Organ Percussion units £14. Bass pedal and other fascinating effects, fuzz, tremolo, etc.
Send s.a.e. for list: D.E.W. LTD.
254 Ringwood Road, Ferndown, Dorset

FULL SPECIFICATION TRANSISTORS: Texas, S.G.S., etc. BC108B 11p; BC109C 12p; 2N3705 14p; BFY51 17p. 5p Postage S.A.E. List. GREENWELD, 24 Goodhart Way, W. Wickham, Kent.

Whether Buying or Selling a Classified Advertisement in PRACTICAL ELECTRONICS could be the answer to your Problem For details write to:

Classified Advertisement Dept.
PRACTICAL ELECTRONICS
Fleetway House
Farringdon Street
London EC4A 4AD

MISCELLANEOUS (continued)

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p each or

Any 16 transistors for only £1.
ACY22 BSY27 OC201 2N3702
BC108 OC45 OC202 2N3703
BC109 OC71 ZTX300 2N3705
BFY51 OC72 2N706 2N3706
BFY52 OC200 2N2926 2N3708

MONEY BACK GUARANTEE. P. & P. 5p
J. M. KING (B)
17 Buckridge, Portpool Lane, London, E.C.1

BIG BARGAIN PARCEL 75p

POST PAID

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed £3.63 POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding. Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send stamps to value of 10 new pence NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 50p). No callers please, mail-order ONLY.

AUDIOSCAN Dept. P.E.3
4, PRINCES SQUARE
HARROGATE, YORKS.

PSYCHEDELIC LUMINOPHONICS


Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another one of these in YOUR BACKROOM—YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"! DON'T PUT IT OFF! SEND 15p for your list—NOW

BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY
Designs by GERRY BROWN and JOHN SALMON and presented on TV

FASCINATING INTERNATIONAL MAGAZINES, unobtainable elsewhere. Parcel £1. S.A.E. List. PARALAB, Downton, Wilts.

MISCELLANEOUS (continued)

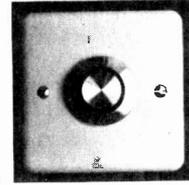

THE
N
I
T
E
T
E

Dimmerswitch

Will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is fitted in a matter of minutes. An MK mounting frame is supplied, for use when more depth is required.

Complete Kit: £2.85 (57p)
PRICE: Built & tested: £3.35 (67p)

Diathane Ltd.

111, Sheffield Road, Wymondham, NORFOLK.
£0.10 postage & packing

BUILD IT in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

SERVICE SHEETS

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Rd., London, W.6 (01-743 8441).

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS
25p EACH, MANUALS FROM 50p
PLEASE ENCLOSE LARGE S.A.E. WITH ALL INQUIRIES AND ORDERS.
OTHERWISE LETTERS NOT ATTENDED TO (Uncrossed P.O.'s please, original returned if service sheets not available.)
FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER

C. CARANNA
71 BEAUFORT PARK, LONDON, N.W.11
MAIL ORDER ONLY

LADDERS

VARNISHED TIMBER from manufacturer; Lowest prices anywhere: 15ft. ext. £5.50; 17ft. ext., £5.75; 20ft. ext., £6.25; 21ft. ext., £7; 24ft. ext., £8.10; 29ft. ext., £9.25; 31ft. ext., £11.15; 36ft., triple ext., £14.50. Carr. 70p; Free Lists. Also aluminium ext. and loft ladders. Callers welcome. Dept. PEE, HOME SALES, Baldwin Road, Stourport, Worcs. Tel. Stourport 2574.

EDUCATIONAL

TELEVISION



This private College provides efficient theoretical and practical training in Radio and TV Servicing. One-year day courses, commencing in April, Sept., and January, are available for beginners, and shortened courses for men who have had previous training. Write for free prospectus to:—

London Electronics College, Dept. LX/3. 20 Penywern Road, Earls Court, London, S.W.5 Tel. 01-373 8721

HUNDREDS OF TOP PAID JOBS in engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful FREE book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write **CHAMBERS COLLEGE** (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

A.M.S.E. (Elec.), City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV., etc. Send for full details and illustrated book — FREE. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

GRADUATE C.E. (CB). Certificate awarded to experienced Radio, TV Electronics Engineers, Testers and Inspectors. Exemption from the examination possible. **REGISTRAR**, College of Electronics (Cambridge), 1A Carlyle Road, Cambridge.

BOOKS AND PUBLICATIONS

SURPLUS HANDBOOKS

19 set Circuit and Notes 7/- P.P. 9d
 1155 set Circuit and Notes 7/- P.P. 9d
 H.R.O. Technical Instructions 6/- P.P. 9d
 38 set Technical Instructions 6/- P.P. 9d
 46 set Working Instructions 6/- P.P. 9d
 88 set Technical Instructions 7/6 P.P. 9d
 BC. 221 Circuit and Notes 6/- P.P. 9d
 Wavemeter Class D Tech. Instr 6/- P.P. 9d
 18 set Circuit and Notes 6/- P.P. 9d
 BC.1000 (31 set) Circuit & Notes 6/- P.P. 9d
 CR.100/B.28 Circuit and Notes 10/6 P.P. 1/-
 R.107 Circuit and Notes 7/6 P.P. 9d
 A.R.88D. Instruction Manual 18/6 P.P. 9d
 62 set Circuit and Notes 7/- P.P. 9d
 52 set Sender & Receiver Circuits 8/- post free
 Circuit Diagrams 5/6 each post free.
 R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26.
 A.1134, T.1154, CR.300, BC.342, BC.312.
 BC.348, J.E.M.P. BC.624, 22, 1475(88), 1392.
 Colour Code Indicator 2/6 P.P. 6d.
 S.A.E. with all enquiries please
 Postage rates apply to U.K. only.
 Mail order only to:
Instructional Handbook Supplies
 Dept. P.E., Talbot House, 28 Talbot Gardens
 Leeds 8

MUSICAL INSTRUMENTS

ELECTRONIC ORGAN DIVIDER CIRCUITS

These i.c. divider circuits contain one master oscillator and six dividers. The output is square wave with a rise time of approximately 20 n secs. and size is only 2 1/2" x 1 1/2" x 1/2".
 Price 75/- (£3.75) each or £42 per dozen, postage paid. Cash with order please, to:
**AUDIONIC, 105 Anson Road
 Great Wyrley, Walsall WS6 6JP**

SITUATIONS VACANT

EAGLE INTERNATIONAL require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact **MR. MORROW** 01-636 0961.

ST. BARTHOLOMEW'S/ST. LEONARD'S HOSPITALS RENAL DIALYSIS UNIT

An

ELECTRONIC TECHNICIAN

is required to work in the Renal Dialysis Unit at St. Leonard's Hospital serving N.E. London and the County of Essex.

This is an interesting and worthwhile career for someone who likes working as a member of a team, and who can drive a Land Rover (or would be willing to learn). Experience in electronics would be an advantage but opportunities exist for training and further study.

The salary will be on the scale for Physics Technicians Grade V (£1,035-£1,335 + £90 London Weighting) plus payments for overtime. Required qualifications are: ONC in Electrical Engineering or Applied Physics, or two "A" levels with appropriate experience.

Further details will be given on application to Hospital Secretary, St. Leonard's Hospital, Nuttall Street, London N1 5LZ.

TAPE RECORDERS

TAPE BARGAINS. Double play AMPEX, 7in, 2,400ft reels, packed in RECOTAPE sealed boxes. Superb quality, fully guaranteed, 2 for **£2-87 1/2**, 6 for **£7-50**. 5 1/2in, 1,800ft reels as above, 2 for **£2-10**, 6 for **£5-37 1/2**. 7in, 1,800ft L.P., 2 for **£2-07 1/2**, 6 for **£6**. 5 1/2in D.P. 1,800ft, 2 for **£2-27 1/2**, 6 for **£6-50**. 5 1/2in L.P. 1,200ft, 2 for **£1-37 1/2**, 6 for **£3-87 1/2**. Money back if not delighted. 12 1/2p. P. & P. on all orders under £5. **MUSIC TAPES MAIL ORDER**, 38 High Street, Salisbury, Wilts.

NOW SAVE ON CASSETTES

AUDEMAG Compact Cassettes, fully guaranteed top quality, in plastic library boxes with giant 6 x 4 label giving double writing space.

	3	6	10
C80	£1.71	£2.71	£3.50
C90	£1.57 1/2	£2.90	£5
C180	£1.92 1/2	£3.67 1/2	£6.50

12 1/2p P. & P. on all orders under £3.

Money back if not satisfied.

MUSIC TAPES MAIL ORDER
 38 High Street, Salisbury, Wilts.

FOR SALE

SEEN MY CAT? 5,000 Items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. **WHISTON**, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

PARVALUX S.D. 9 GEARED MOTORS. 230/250V a.c. 1-phase. 30 r.p.m. 33 lb/in torque. Price 24 each, post free. **U.K. CUNLIFFE WORK TRANSPORTERS LTD.**, Church Road, Rolleston-on-Dove, Nr. Burton-on-Trent, Staffs.



Established 1891

TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the I C S trained man. Let I C S train YOU for a well-paid post in this expanding field.

I C S courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how I C S can help YOU in your career. Full details of I C S courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

INTERNATIONAL CORRESPONDENCE SCHOOLS

A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!

International Correspondence Schools
 (Dept. 152), Intertext House, Stewarts Road,
 London, S.W.8

NAME.....
 Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION..... 3/71.

FOR SALE (continued)

MORSE MADE EASY !!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-680 2896 or send 4p stamp for explanatory booklet to:

GBHC (Box 19), 45 GREEN LANE, PURLEY, SURREY

PSYCHEDELIC COLOURED LIGHT DISPLAY. Sound operated, three channels, £17. S.A.E. for details. A. T. J. BLOCKLEY, 335 Leeds Road, Newton Hill, Wakefield, Yorks.

ELECTRONIC COMPONENTS, tools and books for sale. J. VERNON, 8 Southfields Avenue, Oadby, Leicester.

WANTED

CASH PAID for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London. W.7. 01-567 5400/2971.

WE BUY NEW VALVES. Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

HIGHEST CASH PRICES for tape recorders. 9.30-5. Immediate quotations. 01-472 2185.

RECEIVERS AND COMPONENTS

A CORNUCOPIA OF COMPONENTS! Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

BIG OLD HALF-INCH PHOTOCELLS ARE OBSOLETE!

Latest type high slope broad spectral response, miniature CdS cell, case similar TO-5 but smaller, by famous American manufacturer. Brand new and tested. 62p (12/6).

Precision engineered optical probe body for above, for light or enlarger meter. 75p (15/-).

Professional quality slope-front instrument case 15 x 9 x 6 1/2 in. Well known manufacturers' overstock, duo-grey, det. panel 15 x 8 in. finished and pierced, 2 meters, controls, etc. plus spare blank panel. While stocks last, only £2-75 (55/-) plus 25p (5p) p. & p.

Cadmium-plated chassis and brackets, etc. for above, 75p (15/-) plus 17p (3/6) p. & p.

Sub-min. vert. PC preset resistors 1-2.5-10-25-100-250K, 1M. 5p (1/-).

6-cell 225MA-Hr Ni-Cd rechargeable batts., ex new eqpt. 87p (17/6) plus 12p (2/6) p. & p. Few single cells 17p (3/6) each.

2-p 6-way rotary switch, boxed. 17p (3/6).

Quality CdS transistor enlarger type lightmeter, 3 1/2 in mirror scale meter. Measures 0-01 to 1,000 lux on 3 ranges and overrange. Complete with probe and instructions, less PPS battery £9-50 (£9 10/-) plus 50p (10/-) p. & p.

5p (1/-) p. & p. except where stated.

STERAD INSTRUMENTS LTD.

CHARLTON ROAD, SHEPTON MALLET, SOMERSET

RECEIVERS AND COMPONENTS

(continued)

RADIO CONTROL AT A PRICE YOU CAN AFFORD
RADIO CONTROL PRODUCTS

FOR THE REMOTE CONTROL OF MECHANISMS OF ALL KINDS

TRANSMITTER

- NEW SMALLER UNIT
- CRYSTAL CONTROLLED
- ON 27 MHZ
- 9V OPERATION
- SILICON TRANSISTORS
- TRANSMITTER £6-50



RECEIVER

- NEW TINY RELAYLESS
- SIZE ONLY 3.5 x 2.8 x .2 cms
- WEIGHT 20 gms
- 4.5V WORKING
- WILL OPERATE LIGHTS, MOTORS OR ACTUATORS DIRECT
- RECEIVER £4-50
- RELAY VERSION + £1-25

EXCELLENT RANGE AND PERFORMANCE

Transmitter and matched Superhet Receiver £18-90 Relay + £1-25
Digital proportional equipment available.

ALL UNITS ARE CAREFULLY TESTED BEFORE SALE AND ARE FULLY GUARANTEED

RADIO CONTROL PRODUCTS
123 BEWDLEY HILL
KIDDERMINSTER, WORCS.

PRINTED CIRCUIT BOARDS for P.E. PROJECTS

All boards drilled and roller tinned complete with layout drawing.

EXAMPLES

Marine Tachometer (May 1970) 25p ea. Musical Stave (May 1970) 40p ea.
Vaa-Vaa pedal Vol. 4 No. 7 14p ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 42p ea.

S.A.E. for List. Now available from:- HENRY'S RADIO LTD., Edgware Road, London, W.2
P.H. ELECTRONICS, Industrial Estate, Sandwich, Kent. Tel. 2517

R & R RADIO

51 Burnley Road, Rawtenstall

Rossendale, Lancs

Tel.: Rossendale 3152

TESTED VALVES—3 MONTHS' GUARANTEE

EBF80	15p	PCC84	15p	PY800	17p
EBF89	17p	PCF80	15p	PY801	17p
ECC82	15p	PLC82	20p	U191	22p
ECL80	15p	PL36	25p	30C15	25p
EF80	10p	PY33	25p	PCF86	25p
EF85	15p	PY81	17p	PCL85	25p
EY86	20p	PY82	15p	PCL84	25p

Copper Laminate Board, for etching. 1p per sq.in. Double sided 1 1/2p per sq.in. Any size cut, min. order 50p plus 10% P. & P.

Postage on Valves: one valve 4p, up to 6 2 1/2p, over 6 post paid.

Microcircuits			
709	47p	741	88p
PA234	87p	PA237	£1.57
SL402A	£1-80	MEL11	47p
7410	28p	7420	28p
		7430	28p

Transistors			
ME0402	21p	ME0412	20p
ME4102	12p	ME6101	15p
2N5172	9p	2N4059	15p
		ME4101	11p
		MP8111	35p
		2N3055	65p

Rectifiers			
1N4001	7p	1N4003	9p
1N4002	8p	1N4004	10p
PL4002	10p	PL4003	11p
W005	37p	W02	40p
		PD40	62p

JEF ELECTRONICS (P.E.3)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O. P. & P. 5p per order. Overseas 40p. Money back if not satisfied.

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25V 1-10mfd, 3 1/2p. 20-100 mfd, 4p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02, 2p. 0-04, 0-05, 0-1, 2 1/2p. Mullard miniature Carbon Film Resistors E12 Series 1/4W 1 Q-10 Q, 3 for 5p. Postage 5p. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

HI-STAB RESISTORS mixed bag, 100, 50p; 250, £1. Please send cash with order to ELM-BRIDGE INSTRUMENTS LTD., Island Farm Avenue, West Molesey Trading Estate, Surrey.

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.
SPECIAL BARGAIN PACK. 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 60p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 20p.

LARGE CAPACITY ELECTROLYTICS
10,000MFD 30V } 40p each, P. & P. 6p.
16,000MFD 12V }
or £3-50 per doz. Carr. 50p.

250 MIXED RESISTORS 62p
1/2 & 1 watt.

150 MIXED HI STABS 62p
1/2, 1 & 1 watt 5% & better.

EXTRACTOR/BLOWER FANS (PAPST)
100 CFM 2,800 RPM 4 1/2in x 4 1/2in x 2 1/2in. Ideal for kitchen extraction, instrument cooling, etc. etc. £2-50, P. & P. 25p. 240V a.c. 50 cycles

DIODES EX EQPT. SILICON

1 Amp 1,000 PIV 4 for 50p
20 Amp 150 PIV 4 for £1.
P. & P. 5p.

BARGAIN RELAY OFFER

Single pole change over silver contacts 20V to 50V. 2.5kΩ coil. 8 for 50p. P. & P. 6p.

KEYTRONICS mail order only
52 EARLS COURT ROAD
LONDON, W.8 01-478 8499

TRANSFORMER KITS
Consisting of:- CLAMPS, WINDING BOBBIN AND LAMINATIONS

Max. Rating	Ref. No.	Price	P. & P.
5 VA	74/63	45p	7 1/2p
10 VA	35/75	52 1/2p	12 1/2p
15 VA	147/88	75p	17 1/2p
25 VA	29/1	£1-02 1/2	22 1/2p
50 VA	78/125	£1-77 1/2	27 1/2p
75 VA	78/150	£2-37 1/2	32 1/2p
100 VA	120/125	£2-75	37 1/2p

Transformer designs up to 100VA 50p ea., larger kits and designs available on request.

Supplied by:

WEST DIDSURY TRANSFORMERS
Brooks Street, Higher Hillgate
Stockport, Cheshire SK1 3EU
Tel. 061-480 6479

DUAL-GATE MOSFET MEM554C, for Wireless World Communication Receiver **65p**, U.K. post paid. List 24p. **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

COMPUTER PANELS. 5-BC108 diodes, 15p (3/-), post 5p (1/-), 4-50p (10/-), post 15p (3/-), 8-OC76/OC72/OC42, 8-OC70 diodes, 40p (8/-), post 10p (2/-) per panel, 8-OC170 diodes, 40p (8/-), post 5p (1/-) per panel, 2-OC170, 2-GET87 or 4MD834, 5-100mfd 12V Electrolytics, post core, etc., 30p (6/-), post 8p (1/7) per panel.

PANELS WITH VHF NPN AND/OR PNP SILICON TRANSISTORS, resistors, diodes, capacitors, etc. Panels with 4 transistors 10p (2/-), with 6-8, 15p (3/-), 10-12, 25p (5/-), 14-16, 30p (6/-), 24, 40p (8/-), 30-32, 50p (10/-). Post up to four 15p (3/-), five or over, 25p (5/-).

MIXED TRANSISTORS ON PANELS. 50 for 80p (16/-), 100 for £1.35 (27/-). C.P. panels with resistors, caps, and diodes, 6 for 25p (5/-). Post 3p (3/-) for six.

POLYSTYRENE CAPACITORS. 125V, 18, 22, 120, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 15p (3/-) dozen. Post free with other goods otherwise 10p (2/-).

ASSORTED COMPONENTS. 7lb. £1 (20/-) C.P. **J.W.B. RADIO**
75 Hayfield Road, Salford 6, Lancs.
MAIL ORDER ONLY

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62p per doz.; £3.75 per 100; £27.50 per 1,000; £250 per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

PRINTED CIRCUITS

PE 'Gemini' STEREO AMPLIFIER (Dec. 1970)
Twin Channel Main Amplifier. Stabilised Power Supply.
Total price £1-13. P/P. 8p.

All boards are fibreglass, drilled and tin plated with reverse side screen printed for easy component and connection identification.

SAE for PC board list of other current projects.
SERVITRON ELECTRONICS, 18 Beckedean Ave., Poulton-Le-Fyde, Blackpool, Lancs.
FY6 8BG

CAPACITORS. Dubillier, 0.1µF 500V, 30p doz., £2.10 per 100. Hunts 0.04µF 500V, 15p doz., £1 per 100; 0.001µF and 0.005µF 350V, 15p doz., £1 per 100. Skeleton Presets, 2K Ω, 6p, Co-ax Sockets on isolation panel, 6p, 60p doz. Jack Plugs, Standard, 9p; 3.5mm, 6p; 400-200-50-16µF 300V, 30p, £3 per doz. Recording Tape, 5in LP, 45p, 5½in LP, 60p. Post and packing on all orders 10p. Send S.A.E. for list. **M. DZUBAS, 158 Bradshawgate, Bolton, Lancs.**

UNIQUE 15 WATT CLASS B AUDIO-AMPLIFIER MODULE ONLY 2" x 1" x 5/16" plus tags

Complete with external coupling and decoupling capacitors, etc. **£3.99**

Bendix BHA-0002 is a class B Quasi-complementary audio amplifier using latest thick film construction, ensuring uniform performance and optimum reliability. Power rating, 15W, continuous into a conventional speaker load of 3-2Ω. Complete with external coupling and decoupling capacitors and bias adjust resistor as necessary.

- Sensitivity: 350mV into 18K Ω
- Power required: 30V at 1 amp max.
- Heat sink suggested: 6in x 6in all for max. continuous output

Suitable power supply component pack and circuit diagram **£2.75** mono, £3.50 stereo.

Pre-amplifier component pack including full bass and treble tone controls and inputs for magnetic and ceramic cartridges (using Peak Sound products) **£3-25** mono, **£7-25** stereo. Components for mono including four input and one output socket (D.I.N.) **£11-75**. Components for stereo including four input and two output connectors (D.I.N.), esutechon, knobs, mains and mono/stereo switches **£21-75**.

Spares available. Post free U.K. only. Full data 15p post free.

DALYNE COMPONENTS

Gayton Road • Blisworth • Northants

AUDIO EFFECTS

5 SHAW LANE, HALIFAX, YORKS.
LATEST DESIGN—BUY WITH CONFIDENCE FROM PROVEN DESIGNERS

Radio Control
Single channel T.X. Small compact crystal controlled printed circuit. Easy to build and tune. Push Pull O/P. All silicon transistors. Micro action tone switch. Bottom loaded aerial. Coil on P.C. board. Fantastic O/P. Everything bar case in kit form at £6 post paid. Coils ready wound 10/- (50p) extra. Undrilled alloy case 8/- (40p). Ready built in case **£8.50 (£8-25)** post paid.

Super regen RX
Miniature, lightweight, supersensitive. Uses PP3 or pen cells. Silicon transistors. Front end works straight off. O/P without relay (drives actuator direct) or through 6V 300 ohm relay (not provided). Ideal for model aircraft. In kit form at only **£3.50 (£3-25)** post paid.

Available Shortly
Superhet kit with cascade front end, dual AGC loops. Super selective. Recommended soldering iron Antex 15 watt 32/6 (£1-62).

Ham Band Transistor Superhet Receiver Kit
Uses Denco plug in coils 500kHz to 30kHz in 4 ranges. Normally supplied with kit 1.5MHz to 5MHz extra ranges 12/- (60p) each. Slow motion tuning. Push pull audio output to your 8ohm speaker, black perspex predrilled front panel. In kit form at **£9.12.6 (£9-62)** ready built, calibrated and guaranteed at **£15.5.0 (£15-25)**.

Power Controller
Full wave control using braded tric rated 15 amp 3kW. Single control zero to full power. In strong metal box with 13 amp main socket outlet, ideal for fires, drills, floodlights, motors, etc. Ready built at **£9.15.0 (£9-75)** post paid. In kit form with full instructions **£7.5.0 (£7-25)** post paid.


Vox Switch
Make a noise, it switches, high imp. L/P for XTL mike. Drives your 12 volt relay. Ready built **£3.10.0 (£3-50)** or in kit form **£2.7.6 (£2-37)**.

Reverberation Amplifier
Self contained transistorised. Batt. operated. Entirely different approach to sound reproduction. With this unit proper sound delay through reverberation, tones are created truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug in microphone, guitar, etc., and O/P into your amplifier. Encased in beautiful walnut cabinet 7¼" x 3" x 4¼" at only **£10.15.0 (£10-75)** post paid.


Pocket Metronome
Variable beat. Drives your speaker or earpiece provided, uses PP3. In attractive plastic case at **£1.17.6 (£1-87)** or as a kit at **£1.7.6 (£1-37)** both post paid.

Morse Oscillator
Just attach your key. Drives your speaker or earpiece provided. Works on pen cells. Ready built in case as above **£1.5.0 (£1-25)** as a kit 17/6 (87.) both post paid. Latest Mullard manual on audio amps, etc., 32/6 (£1-62) post paid.

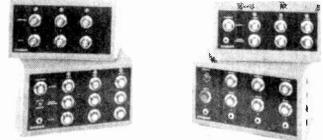Texas Transistors
Driver, NPN and PNP complementary symmetry. Pack of three 7/- (35p) post paid.



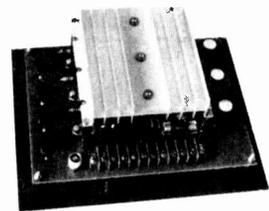Complete range of Kinetic Lighting Effects units and 100W Mixer-Amplifier. Send 5p in stamps for further details.



Still available—our ever-popular Mk.2 Psychodelic Lighting Unit, manufactured on professional fibre-glass printed-circuit board material.

Drive voltage is derived directly from amplifier output or across speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

Uses latest full-wave triac circuitry and incorporates signal input level and minimum ambient light level controls. Will drive up to 1.5kW per channel at 240V a.c. Complete printed-circuit board assembly built and tested. Size 8½in x 6½in x 3½in. plus 50p carriage **£17.50 net**

INSTRUMENTAL AUDIO EFFECTS

CREATE "PHASE" on your tape recordings, records, etc., unique electronic circuitry enables you to create "phase" at the turn of a knob. Just connect between pre-amp. and power-amp.

This is not waa-waa, white-noise or swish but genuine phase-shift created electronically. Input and output impedances match to 10-50kΩ. Operates from 9V battery. Complete printed-circuit assembly, built and tested. Size 4in. 2½in. 1½in. **£3.25** plus 10p carriage.

OR **£2.50** plus 10p carriage in KIT FORM
SUPER "FUZZ" UNIT. Connects between guitar and amplifier. Operates from 9V battery. Complete printed-circuit board assembly, built and tested. Size 3½in. 2½in. ½in. **£3.25** plus 10p carriage.
OR **£2.50** plus 10p carriage in KIT FORM

MAIL ORDER ONLY
S.a.e. for all enquiries

Dabar Electronic Products
98a Lichfield Street, Walsall, Staffs.

Your local component stockist

East Anglia

EAGLE

Electronics

Eagle St.

IPSWICH

58075

TELERADIO ELECTRONICS

JOIN THE FASCINATING HOBBY OF RADIO CONTROL. BUILD A SINGLE CHANNEL SYSTEM FOR ABOUT £12 OR A SOPHISTICATED PROPORTIONAL SYSTEM FOR £80

Details from the specialists: **TELERADIO CO. (P.E.)**
325-7 FORE STREET, EDMONTON, N.9

LOW VOLTAGE AMPLIFIER Few only at plus 12½p P. & P. **£1.75**

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.

With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.



ACOS STETHOSET. 200 ohm d.c. Res. stetho- set complete with 5ft of wire. Ideal for private listening on radio and tape recorder. These stethosets are made to very high standards, they are used but in good condition and are all guaranteed. Well below original Price at 80p plus 7½p P. & P.



CRESCENT RADIO LTD.
11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.
No. 11 MAYES RD. LONDON N22 6TL

EMI LOUDSPEAKER 450
10W 13in x 8in ± two 2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. **£3.25** plus 37½p P. & P. each.



EMI LOUDSPEAKER 150
10 watts. 13x8 base unit. Plus a flared centre cone. Designed to handle the higher frequencies. Please state imp required. 3.8.15 Ω. A bargain at **£2.50** plus 37½p P. & P. each.

PSYCHEDELIC LIGHT CONTROL UNIT
Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18.50** plus 37½p P. & P.



If you require more information please send S.A.E.

SHELF UNIT
Two teak finish shelves on a black frame (overall size: 28in x 25in x 12in). Ideal for hi fi equipment: amplifiers, speaker cabinets, etc. The perfect answer for housing unit audio and equipment. This unit is wall mounting. **£2.50** plus 37½p P. & P.




BATTERY ELIMINATOR
Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. main through this compact eliminator. 2½in x 2in x 3in approx. 4½V **£1.50**, 6V **£1.50**, 9V **£1.50**, 7½V complete with cable and plug for Philips Cassette. **£2** plus 7½p P. & P. each.



CRESCENT CASSETTES
Top quality cassettes at unbeatable prices (complete with standard storage case): C60 37½p, C90 62½p, C120 87½p plus 5p P. & P.



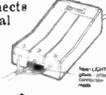MAINS KEYNECTOR
Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage, demonstrations, etc. Multi connections can be made (max. load 13A fused). **ONLY £2.32½** P. & P. Free on this item.



BARGAIN BOARDS
Components galore for the experimenter. Ex computer boards with: Resistors, Capacitors, and useful Transistors—at least 4 transistors per board. BARGAIN PRICE 30p per board 5 BOARDS **£1.20**. P. & P. Free on this item.



HIGH QUALITY IMPORTED HEADPHONES
1,000 Ω per phone **80p** TTC
2,000 Ω per phone **87½p** G1105
Plus 10p P. & P. per pair.



STEREO HEADSET
8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. **£2.50** plus 10p P. & P.



STEREO JUNCTION BOX
For stereo amplifiers without stereo jack socket. **£1.25** plus 7½p P. & P.



CHROME TV STAND
28in x 8½in x 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at: **£1.62½** plus 25p P. & P.



BRIGHTNESS CONTROL
Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price **£2.75** plus 5p P. & P. each.



WE HOLD THE LARGEST STOCK OF RETAIL COMPONENTS IN LONDON — SEND S.A.E. FOR FREE LISTS

LEGS
15½in high, 7½in wide at top, 13in wide at bottom. In modern matt black finish ideal for all types of cabinets, loudspeaker plinth, record player, etc. **75p** per pair plus 15p P. & P.



1 MILLION SILICON PLANAR TRANSISTORS
NPN-PNP PLASTIC AND METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

TYPE STN18
Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77. Price: 500 £9, 1,000 £15

TYPE STP18
Silicon Planar Transistors pnp TO 18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18. Price: 500 £9, 1,000 £15

TYPE STNL
Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mW medium to high gain, available in npn or pnp and types similar to: NPN 2N2926 — 2N2711 — 2N3391 — 2N3707 — 2N3711 — BC167-8-9. Price: 500 £7-50; 1,000 £13

TYPE STPL
As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL. Price: 500 £7-50; 1,000 £13

TYPE STNK
Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, I.C. 200mA, 300mW and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8. Price: 500 £9-50; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.
All prices in pounds and new pence.
All goods Ex-stock sent by return. Cash with order please to:


DIOTRAN SALES
P.O. Box 5, WARE, Herts.
S.A.E. For full list of surplus semiconductors

BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board— obtainable from your local Retailer

Trade enquiries to:
NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

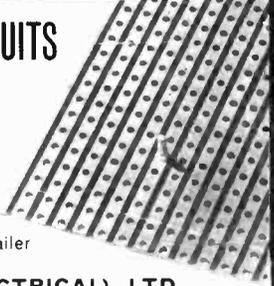Technical enquiries to:
VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants



BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power 35 watts
Bass Resonance 35 c.p.s.
Flux Density 15,000 gauss
Voice coil impedance 8 or 15 ohms models
Useful response 20-14,000 c.p.s.
Nett weight 15 lbs.

£19
POST FREE

GUITAR MODEL "GROUP 50" 50 watt rating 19W
Latest catalogue 1/- with enclosure plans

Baker Reproducers Ltd
Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665



In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Numerical Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.
WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept 316A, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



POST THIS COUPON TODAY

To: B.I.E.T., Dept 316A, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES



HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

TRANSISTOR AMPLIFIERS NEW RANGES NOW IN STOCK

(Leaflets Ref. No. 6 and 8).
Post, etc., 20p (4/-).

4-300 4TR 9V 300mW	£1.75 (35/-)
104 4TR 9V 1W	£2.12 (43/5)
304 4TR 9V 3W	£2.47 (49/5)
555 6TR 12V 3W	£2.75 (55/-)
PA7 6TR 16V 7W	£3.62 (72/5)
608 6TR 24V 10W	£4.12 (82/5)
410 4TR 28V 10W	£4.97 (99/5)
MPA12/3 6TR 18V 12W	£4.50 (90/-)
MPA12/15 6TR 36V 12W	£5.25 (105/-)
Z30 9TR 30V 20W	£3.75 (75/-)
PA25 10TR (Special) 25W	£7.50 (150/-)
Z50 30V 40W	£5.47 (109/5)
PA50 12TR (Special) 50W	£9.50 (190/-)
100 100W with power supply	£19.50 (390/-)
	post 45p (9/-)



OPTIONAL POWER SUPPLIES

P500 Switchable (One or Two) for 104, 304	£2.62 (52/5)
P520 Switchable (One or Two) for PA7	£3.47 (69/5)
MS24/40 Switchable (One or Two) for MPA12/3 or MPA12/15	£4.50 (90/-)
PZ5 for Z30 £3.97 (79/5)	or PZ6 for Z30 £6.97 (139/5)
PZ8 for Z50 £5.97 (119/5).	Transformer £2.25 (45/-)
P11 for 608 £2.87 (57/5).	P15 for 410 £2.62 (52/5)
MU442 for 1 or 2 PA25 or 1 only PA50	£6.50 (130/-)

PROJECT 60 PACKAGE DEALS

2x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £19. Carr. 40p. Or with PZ6 power supply, £21. Carr. 40p. 2x Z50 amplifier, stereo 60 pre-amplifier PZ8 power supply, £21.50, p.p. 40p. Transformer for PZ8 £2.25 extra. Any of the above with Active Filter units add £4.87 or with pair Q16 speakers add £16. Also NEW FM TUNER, £23.

BUILD THIS VHF FM TUNER



5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 and 7. TOTAL £6.97 (129/-), p.p. 20p (4/-). Cabinet £1, Decoder Kit £5.97, Tuning meter £1.75. Mains unit (optional) Model PS900 £2.47 (49/5). Mains unit for Tuner and Decoder PS1200 £2.62 (52/5).

BUILD YOURSELF A QUALITY RADIO



Excellent printed circuit design with full power output. Fully tunable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions. Total cost £6.98 (€6.19.6), p.p. 35p (7/-). All parts sold separately. Ask for Leaflet No. 1.

HI-FI TO SUIT EVERY POCKET



CHOOSE FROM 100 STEREO SYSTEMS

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only). FREE—Stock Lists Nos. 16/17 on request—BEST VALUE IN U.K.

HENRY'S LATEST CATALOGUE



Now 350 pages

WHY NOT SEND AWAY TODAY?

- * COMPONENTS, TEST GEAR
- * EQUIPMENT, MODULES
- * SPECIAL OFFERS, Etc., Etc.

Everything for the constructor. Complete with 50p value discount vouchers for use with purchase. Price 41p, post free.

FREE 8 page Transistor, IC, Diode lists No. 36

FREE 16 page Organs to Build brochure No. 9

FREE Decks and Hi-Fi Stocks Lists No. 16/17


FREE PA, Disco and Lighting List No. 18

FREE Quotations for all Electronics—send list and S.A.E.

TEST EQUIPMENT FOR HOME, SCHOOL & PROFESSIONAL USE




AF105 50k/V multimeter (illus.). Price £8.50 (190/-), p.p. 20p (4/-). Leather case £1.42 (28/5).
200H 20k/V. Price £3.87 (77/5), p.p. 20p (4/-). Case 62p (12/5).
500 30k/V multimeter. Price £8.87 (177/5), p.p. 20p (4/-). Leather case £1.50 (30/-).
THL33 2k/V. Price £4.12 (82/5), p.p. 15p (3/-). Leather case £1.15 (23/-).
TE65 Valve voltmeter (illus.). Price £17.50 (350/-), p.p. 40p (8/-).
SE250B Pocket pencil signal injector £1.75 post paid.

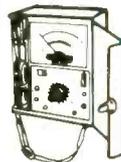

TE20D RF generator. Price £15, p.p. 40p (8/-).
TE22D Matching audio generator. Price £17, p.p. 40p (8/-).
TE15 Grid dip meter. Price £12.50, p.p. 40p.
TO3 Scope 3 in. tube. Price £37.50, p.p. 50p.
TE22 Audio Generator. £17, p.p. 40p.

(Get a copy of our latest catalogue for full specifications and further ranges.)

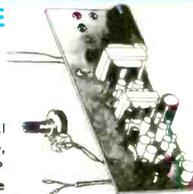NEW MINIATURE LOW COST AMPLIFIER MODEL 4-300



9V operated or mains unit optional transformer (MT98 70p (14/-)), 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fitted volume control and leads. Size 5 1/2in x 1 1/2in x 3 1/2in. Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.

Price £1.75 (35/-), p.p. 15p (3/-). Complete with FREE leaflet No. 8.

STC TIME DELAY MODULE



Ideal for experimenters, educational projects as well as for practical uses. Delay adjustable 3-15 secs. Operates 9-12 volts. Heavy Duty Relay Contacts. Complete with suggested applications sheet. Price £1.75 (35/-) post paid.

GARRARD TAPE DECK



Price £9.97

199/6, p.p. 33p (6/6) (3 1/2in. tape 300ft. and spool 40p (8/-))

9V operated 2-speed tape deck fitted Record/Replay x track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9in x 6 1/2in x 1 1/2in and 2 1/2in below motor board. Takes up to 4in spools. Supplied Brand New.

HENELEC SELF-POWERED TRANSAMPLIFIERS

Designed for use with PA25 and PA50 Amplifiers.



SLIM MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS, FET's and IC's, DIN SOCKETS, ETC., fitted. Self powered PUSH-BUTTON SELECTION, 200dB BASS AND TREBLE BOOST AND CUT. All inputs provided plus TAPE RECORD and REPLAY.

GOLD AND SILVER FINISH. Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.

* FET9/4. Mono with built-in mic. mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12.50 (€12.10), p.p. 20p (4/-).

* FET154 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16.50 (€6.10), p.p. 25p (5/-).


* Also suitable for use with any power amplifier. Suggested types PA25, PA50, MPA12/3, MPA12/15.

SIMPLICITY TO MOUNT

EASY TO USE

All units no soldering—just edge connectors and plugs

25 WATT & 50 WATT SILICON AMPLIFIERS

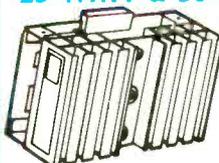

LOOK AT THE SPECIFICATIONS!

- At full power 0.3% distortion.
- At full power—1dB 11 c/s to 40 kc/s.
- Response—1dB 11 c/s to 100 kc/s.
- Rise time 2usec.
- Short circuit proof plus limiting cct. No. 25 on request.

FREE LEAFLET No. 25 on request

PA25 10 transistor all silicon differential input 400mV sensitivity. 25W Rms into 8 ohms. Supplied with edge connector harness size 5in x 3in x 2in.
PA50 12 transistor version 50W Rms into 3 to 4 ohms. Size 5in x 3in x 4in.
MU442. Power supply for one or two PA25 or one PA50.
PA25, £7.50. PA50, £9.50. MU442, £6. P.P. 20p each.

DESIGNED FOR QUALITY, PERFORMANCE AND PRICE

As specified for many "Practical Wireless" 1970 projects

Electronic Components & Test Gear Centre
356 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre
309 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 6963

Mail Order and Industrial Sales Dept.
303 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 1008/9

OPEN 9 a.m. to 6 p.m. MONDAY TO SATURDAY — 9 a.m. to 1 p.m. THURSDAYS — OPEN ALL DAY SATURDAY