

PRACTICAL

ELECTRONICS

MARCH 1972

20p



ALSO INSIDE
GUITAR TREMOLO

EXTRA 8 PAGE
AUDIO SUPPLEMENT
PICK-UPS AND
TURNTABLE UNITS

NEW
SERIES

ALPHA
NUMERIC
DISPLAYS

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · ELECTRONIC COMPONENTS · TEST · PA · DISCOTHEQUE · LIGHTING · MAIL ORDER

10th EDITION CATALOGUE

350

pages fully detailed and illustrated covering every aspect of Electronics — plus data, circuit aids and information

PRICE 55p POST PAID (40p FOR CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—by catalogue by post only. All other mail and callers to "303", see below.

A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

HOME EQUIPMENT



AF105 50kV multimeter (illus.). Price £8.50, p.p. 20p. Leather case £14.2.
200H 20kV. Price £3.87, p.p. 20p. Case 62p.
500 30kV multimeter. Price £8.87, p.p. 20p. Leather case £15.50.
THL33 2kV. Price £4.12, p.p. 15p. Leather case £11.15.
TE65 Valve voltmeter. Price £17.50, p.p. 40p.
SE250B Pocket pencil signal injector. Price £1.75, p.p. 15p.



SE500 Pocket pencil signal tracer. Price £1.50, p.p. 15p.
TE20D RF generator. Price £15, p.p. 40p.
TE22D Matching audio generator. Price £17, p.p. 40p.
TE15 Grid dip meter. Price £12.50, p.p. 40p.
TO3 Scope 3in tube. Price £35.50, p.p. 50p.
TE22 Audio Generator. Price £17, p.p. 40p.
CI-5 Pulse Scope. £39.00, p.p. 50p.
U4341 A.C./D.C. Multitester and transistor tester. A.C. and D.C. current. In steel case. Price £10.50, p.p. 15p.
TMK500 30kV Multitester. Price £8.87, p.p. 13p. Leather case £1.98.

LARGEST RANGE of Panel Meters, Edge Meters and Test Equipment of every sort. Full details in latest catalogue—see above.
Carriage etc., 50p each; 75p per pair for kits

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2" and Ceramic Magnet
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 390 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

SPEAKER KITS

WHARFEDALE 4-8 ohms PEERLESS 8 ohm Systems
Unit 3. 8in 15W £10.20 20-2. 8in 30W £11.25
Unit 4. 12in 25W £13.50 20-3. 8in 40W £16.75
Unit 5. 12in 35W £19.50 30/12. 12in 40W £22.75
GOODMANS DIN 20 KIT 20W, 4 ohm. £10.75
Carriage, etc., 50p each; 75p per pair for kits.

STEREO HEADPHONES

With stereo jack. Post 15p
Dulci SH650D £2.25
Rotel RH600 £4.67
Akai ASE95 £5.50
Eagle SE30 £5.97
Koss K711 £7.97
Pioneer SE30 £9.45
Koss PRO4A £15.50



HI-FI TO SUIT EVERY POCKET



SAVE UP TO 40% ON LIST UP TO 40% OFF PRICES PLUS FREE BIG GROOV-KLEEN Value £1.99.
ROTA 1500 5 + 5 watts. Garrard 2025TC with 9TAHC diamond ceramic. Plinth/Cover. Type 60 Compact Speakers. Size 16" x 9 1/2" x 6 1/2".
SAVE £44.90 Carr. £2

TELETON "206" Garrard SP25 Mk. III. Goldring G800 Series Cart. Plinth/Cover. New 15 watt Quality SDL1 Bookshelf Speaker Systems, all leads, etc.
SAVE £54.95 Carr. £2

TELETON F2000 Med. Wave, Stereo FM Tuner Amplifier. Garrard 2025TC, 9TAHC Diam., Plinth/Cover. Type 60 Speaker Systems as above, all leads, etc.
SAVE £56.95 Carr. £2

or with 2 x SA125 Speakers £49.50 Carr. £2

ROTA 3200 10 + 10 watt. Garrard SP25 III/G800H. Plinth/Cover. New 15 watt SDL2 Twin Speaker Systems, all leads, etc.
SAVE £65.50 Carr. £2

Low prices plus 12 months' guarantee and demonstrations

FREE—Latest Special Price Stock List and Stereo Systems, Ref. 16/17.

FREE BROCHURES

- ★ P.A., DISCO and LIGHTING No. 18
- ★ TRANSISTORS, I.C.'s No. 36

20 WATT I.C. AMPLIFIER

Toshiba 20 watt Power Amplifier, £4.57
Toshiba Pre-Amplifier I.C., £1.50
Data and suggested circuits No. 42, 10p
SL403D 3 watt I.C., with 8 page data and circuits, £1.50
IC12 6 watt I.C., £2.50

TEXAS PRE-AMPLIFIERS AND 1-100W AMPLIFIERS

Circuits, layouts and data £1.25. Post paid.

NIXIE TUBES

(post 15p per order)
XN3 or XN13 0-9 side view with data sheet, 85p each.
GN4 end view 0-9 with socket and data, £1.75
All I.C.'s for Digital Clocks in circuit. HENRY'S CLOCK CIRCUIT No. 29/2, 15p

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300kc/s BAND-WIDTH PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6.97, p.p. 20p. 100p. Decoder Kit £5.97. Tuning meter £1.75. Mains unit (optional) Model PS1900 £2.47. Mains unit for Tuner and Decoder PS1200 £2.62. Cabinet



HIGH QUALITY SILICON AMPLIFIER AND PRE-AMPS

Self-powered Silicon-FET Pre-Amplifier. Push-button selectors, tape record/play, adjustable levels, drive up to 4 x PA25 or 2 x PA50. FET 9/4 Mono or single channel. All facilities plus microphone. Mixing.

SPECIAL OFFER £10.50
SILICON POWER AMPLIFIERS RMS OUTPUT PA25 25 watts into 8 ohms, £7.50. PA50 50 watts into 4 ohms, £9.50. MU442 Power Supply for 1 or 2 PA25's or 1 only PA50. £6. Post 20p. FREE BROCHURE NO. 25 ON REQUEST. NO SOLDERING—ALL UNITS INTERCONNECTING. ON DEMONSTRATION AT "356".

TERRIFIC SAVINGS!

GARRARD - BSR - THORENS GOLDRING - PIONEER CONNOISSEUR



CHASSIS (P) (less cartridge)	ASSEMBLED (P) (less cartridge)	ASSEMBLED (P) (with cart. P and C) 2025TC/9TAHCD
*SP25 Mk. III £11.30	MP60 (TDIP) £17.65	SP25 £14.95
*AP76 £20.50	MP60 (TDIP) £17.65	3-G800H £19.95
*MP60 £11.30	HT70PC £23.50	AP76-G800 £29.95
*MP610 £15.15	PL12AC £36.50	HT70PC/G800 £29.95
*HT70 £16.60	GL72/PC £36.95	
GL72 £22.95	GL75 PC £47.75	
GL75 £28.97	TD150AB/TX1 £45.50	
DUAL 1215 £39.00	BD25AU £33.50	

CHASSIS WITH CARTRIDGE (P) SPECIAL PRICE WITH *2025TC/9TAHCD £9.50 CARTRIDGE—ADD *3000/9TAHCD £9.95
TEAK *P1/T1 Std. £3.25
PLINTH *BNI Deluxe £8.30
WITH *P4/T4 Std. £4.75
COVER *BN4 Deluxe £8.30
(State *B6/T6 Std. £3.25 deck) *BSR Deluxe £6.25

Post, etc.: Chassis 50p, with Plinth/Cover 70p, Plinth/Cover 30p, Carts. 15p.

300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled 4TR Amplifier. Size 5 1/2" x 1 1/2" x 3 1/2", 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost. £17.5 p.p. 15p (or 2 for £3.25 p.p. 15p).



SINCLAIR PROJECT 60 PACKAGE DEALS—SAVE POUNDS

2. x 230 amplifier, stereo 60 pre-amp, P25 power supply, £16.75, Carr. 40p. Or with P26 power supply £18.25. Carr. 40p. x 250 amplifier, stereo 60 pre-amp, P28 power supply £20.25. Carr. 40p. Transformer for P28 £2.45 extra. New! Project "605" stereo system £21.50. Any of the above with Active Filter unit add £4.75 or with pair G16 speakers add £16. Also new FM Tuner £20.25. 2000 Amplifier £23.75, p.p. 50p. 3000 Amplifier £31.50. Also IC12 £2.50.



"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandsread for extra selectivity. Also slow motion geared tuning, 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.

TOTAL COST TO BUILD £7.98, p.p. 32p (Batt. 22p). All parts sold separately—Leaflet No. 2. "771" PORTABLE (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.



MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

Electronic Components, Audio and Test Gear Centre
356 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 5854

P.A., Disco & Lighting Centre
309 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 1008/9

"309", "354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY

*Components in stock for most published designs—send large SAE with list for parts quote for your circuit.

Now! From EMI precision speakers and enclosures in matched money-saving kits

EMI speakers are internationally recognised—used in the highest quality sound reproduction equipment. Because of this world-wide demand, EMI matched speaker kits are available to you at a really keen price.

And now, EMI introduce the commonsense cost-saving approach to high quality speaker enclosures. Available in complete easily assembled kit form—all you need is a screwdriver—they form the ideal

combination of superb sound reproduction and good looks you'll be proud to have in your home.

There are eight kits—from compact book-shelf units to large floor standing enclosures—all finished in selected wood veneer, with matched loudspeaker kits handling from 5-35 Watts.

Realise the full fidelity of your audio system at a fraction of the cost of comparable speaker assemblies. Contact your hi-fi dealer or send to EMI for full details

2 x 280
2 x 154



A member of the
EMI Group of Companies.
International leaders in Electronics,
Records and Entertainment.



Perfection in Sound

EMI Sound Products Ltd., Hayes, Middlesex.
Telephone: 01-573 3888, Ext. 667

SAVE £20.25 NOW!

THIS FANTASTIC OFFER ONLY FROM US!

fabulous BRAND NEW **SOLID STATE** BATTERY/MAINS AC

This equipment's got EVERYTHING!

Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44

OUR PRICE **£23.75** CARR. ETC. 35p

Latest sensation in the world of sound! First-class makers. Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder and Player combined! AND runs off standard batteries or mains (plus in the 220/240V AC line cord). Record, play back anything, anywhere! Even tape direct from Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44. WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Push-button Keyboard Control panel! * New "pop-up" Cassette ejection system! * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic leveller! * Separate ON/OFF, HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in approx.)! * Magnificently made case, size 11 1/2in x 9in x 3 1/2in overall approx., with carry handle (DESIGNS VARY SLIGHTLY). Takes standard 30, 60, 90 or 120-minute Philips Cassette Tapes obtainable everywhere. The amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country—plus BBC, National, VHF. Picks up dozens of foreign stations. Also fabulous in car! You could pay ££££'s more for a Car Radio or Car Cassette player ALONE! **OUR FANTASTIC PRICE £23.75. CARR. 35p.** Simple instructions, remote control microphone with on/off switch and microphone stand. **BONUS—Standard Batteries and Cassette Tape 25p extra if required, refund if not delighted.**

COMMERCIAL TRAVELLERS Please note: Merchandising office at our Holborn Store. (PERSONAL SHOPPERS WELCOME AT BOTH OUR STORES.)

SHOPERTUNITIES LTD. S11

ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!

BRAND NEW RUSSIAN WORLD BEATER!

WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!

6 WAVEBAND 10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

£9.97p BOX POST ETC. 43p

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

THE VERY LATEST MODEL, SUPERSEDING ALL PREVIOUS MODELS—THE FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pinpoint" station selection! Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands, including Standard Long, Medium and Short Wave to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even messages from all over the world! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in length. It's also a fabulous CAR RADIO—any speed requires no additional aerial. **UNIQUE!** Elegant Black, White and Chrome finish case. SIZE 10 1/2in x 8in x 3 1/2in, overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST, ETC., 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

*COMPARE ITS PERFORMANCE WITH **£34 RADIOS!**

Dept. PE/14, 164 UXBRIDGE ROAD, LONDON W12 8AG (facing Shepherds Bush Green) (THURSDAY 1, FRIDAY 7). Also at 37/39 High Holborn, LONDON W.C.1. (THURSDAY 7 p.m.) Both stores open MON-SAT 9 a.m.-6 p.m.

SAFEBLOC

of robust construction

Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.


If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH

Special bulk order wholesale and industrial rates on application

RENDAR®

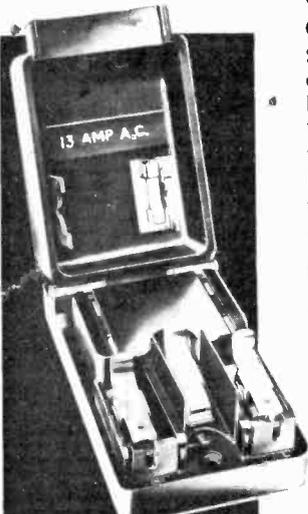Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642



P.E. GEMINI

Pre-amplifier P.C.B.	£1.95
Main Amplifier P.C.B.	£1.45
Power Supply P.C.B.	60p
Pre-amplifier Semiconductors	£1.75
Main Amplifier Semiconductors	£7.25
Power Supply Semiconductors	£2.50
Packing and Postage on all orders	15p

All Semiconductors available separately.
Full range of Ferranti semiconductors available at low prices.
Send S.A.E. for list.

DAVIAN ELECTRONICS
P.O. BOX 38 OLDHAM LANCs

The most accurate pocket size CALCULATOR in the world

The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4.50 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.


CARBIC LTD. (Dept. PE 39)
54 Dundonald Road, London SW19 3PH

FREE BOOKLET ON REQUEST





I.L.P. (Electronics) Ltd

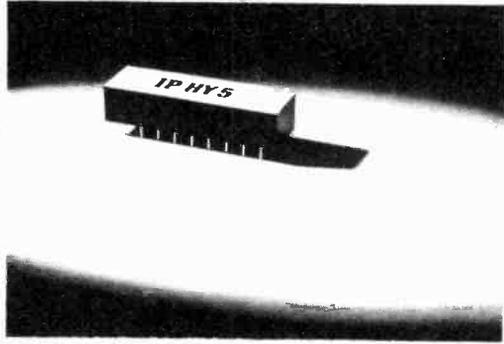

A WORLDS FIRST TO JOIN THE WORLDS BEST

The HY5 is a unique and revolutionary concept in High-Fidelity pre-amplifiers. Thanks to the latest techniques, all feedback and equalization networks are, for the first time, combined into an integrated pre-amplifier circuit.

Simply by adding volume, treble, bass potentiometers and only three stabilizing capacitors, which are supplied, your HY5 is complete and ready for use.

The HY5 provides equalization for almost every conceivable input. This years developments in equalization technique enables precise correction for both output voltage and frequency response for any crystal or ceramic cartridge. Yet another feature of the HY5 is its inbuilt stabilization circuit, allowing it to be run off any unregulated power amplifier supply.

The HY5 contains a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo preamplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY40 and PSU45 forms a completely integrated system.

INPUTS

Magnetic Pick-up (within ± 1 db RIAA curve) 2mV.
Tape Replay (external components to suit head): 4mV.
Microphone (flat) 10mV.
Ceramic Pick-up (equalized and compensatable) 20-2000mV variable.
Tuner (flat) 250mV.
Auxiliary 1 250mV.
Auxiliary 2 2-20mV.

OUTPUTS

Main Pre-amp output 500mV.
Direct tape output 120mV.

ACTIVE TONE CONTROLS

Treble ± 12 db.
Bass ± 12 db.

INTERNAL STABILIZATION

Enables the HY5 to share an unregulated supply with the Power Amplifier.

SUPPLY VOLTAGE

15-25 volt.

SUPPLY CURRENT

5mA approx.

OVERLOAD CAPABILITY

better than 28db on most sensitive input infinite on tuner and auxl.

OUTPUT NOISE VOLTAGE

0.5mV.

PRICE

Mono £3-60 Stereo £7-20

HY40 IS POWER AMP PERFECTION

Lets face it—an immediate success, the HY40 is here to stay.

HY40 means Hybrid Power, power neatly locked away inside an Integrated Circuit. Power the modern way, simply mount only five additional components on a printed circuit board (all of which are supplied with the HY40). Power not only for Hi-Fi, power for Groups, for public address, for industry, power for all.


HY40 is HI-FI POWER ILP are POWER PROUD

In addition to the P.C. board and manual supplied with the HY40 we now include the five remaining components, at minimal cost, needed to complete the assembly of a High Performance Power Amplifier.

By merely combining two HY40s with a Stereo Preamplifier (2 x HY5) and simple Power Supply (PSU45), premium quality stereo may be obtained for a very modest outlay.

The free manual supplied with the HY40 gives clear, easy build instructions for Power Supply; volume, bass, treble and balance controls, together with inputs for Ceramic and Magnetic Pick-ups, Tape, Tuner and Auxiliary functions.

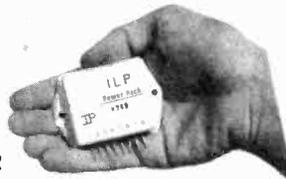Internally the HY40 is based on conventional and proven circuit techniques developed over recent years.



OUTPUT POWER British Rating 40 WATTS PEAK, 20 watts RMS continuous.

LOAD IMPEDANCE 4-16 ohms

INPUT IMPEDANCE 22Kohms at 1Khz.

INPUT SENSITIVITY 300 mV for maximum output.

VOLTAGE GAIN 30db at 1KHz.

FREQUENCY RESPONSE 5Hz-60KHz ± 1 db.

TOTAL DISTORTION less than 1% (typical 0.1%) at all output powers.

SUPPLY VOLTAGE ± 22.5 volts D.C.

SUPPLY CURRENT 0.8 amps maximum.

PRICE: including comprehensive manual, P.C. Board and FIVE EXTRA COMPONENTS:

MONO £4-40 STEREO £8-80 all post free.

POWER SUPPLY PSU45



The PSU45 is specifically designed to supply, simultaneously, your HY40 (in mono or stereo format) and one or two HY5s.

Spec.

PSU45 ± 22.5 volts, 2 amps simultaneously.

PRICE: £4-50 including Postage and Packing

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT
TELEPHONE: CANTERBURY 63218

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
	7-5	TO-66	TO-66		TO-48	TO-48
50	0.23	0.25	0.47	0.50	0.53	1.15
100	0.25	0.28	0.53	0.58	0.62	1.40
200	0.35	0.37	0.67	0.81	0.75	1.60
400	0.43	0.47	0.87	0.75	0.93	1.75
600	0.53	0.57	0.77	0.97	1.25	
800	0.63	0.70	0.80	1.20	1.50	4.00

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.08	0.08	0.07	0.14	0.21	0.47
100	0.06	0.06	0.06	0.13	0.18	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.16	0.10	0.23	0.34	0.45	1.85
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.83	2.50
1200		0.33		0.33	0.57	0.75	

TRIACS

VBO	2A	6A	10A
TO-1	TO-66	TO-88	
50	0.50	0.83	1.00
200	0.70	0.90	1.25
400	1.00	1.00	1.60

LUCAS SILICON RECTIFIERS
35 amp, 400 P.I.V. Stud type. ± 1.10 each.

DIACS WITH TRIACS
BR100 D32 ± 1.00 each

2A POTTED BRIDGE RECTIFIERS 200V 50p

UNIUNION
UT48, Eqvt. 2N2646, Eqvt. T1843, BEN3000
27p each, 25-99 25p
100 UP 20p.

JUMBO COMPONENT PAKS
MIXED ELECTRONIC COMPONENTS
Exceptionally good value

NPN SILICON PLANAR
BC107 8p, 10p each;
50-99 8p, 100-99 10p
8p each, 1.000 off.
7p each. Fully tested and coded TO-18 case.

FREE
One 50p Pak of your own choice free with orders valued \$4 or over.

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P. & F. **\$1.50 only**
Plus our satisfaction or money back guarantee.

AF239 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 900 MHz. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE: 1-24 37p each, 25-99 34p each, 100-99 30p each

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-30V - 400mV (10-7 Case) 13p ea. 11W (Top-Hat) 18p ea. 10W (SO-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

SPECIAL OFFER
2N2926 (Y) (O). 10 for 50p. 25 for \$1. 20,000 TO CLEAR.

CADMIUM CELLS
ORP12 43p
ORP50, ORP61 40p each

PHOTO TRANS.
OCP71 Type. 43p

SIL. G.P. DIODES 5p
300mW 30... 0.50
40P (Min.) 100... 1.50
Sub-Min. 500... 5.00
Full Tested 1,000... 9.00
Ideal for Organ Builders.

D13D1 Silicon Unilateral switch 50p each.
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed Pak No. EQVT

T1	8 2G371B	OC71
T2	8 D1374	OC75
T3	8 D1216	OC81D
T4	8 2G381T	OC81
T5	8 2G382T	OC81
T6	8 2G344B	OC44
T7	8 2G345B	OC45
T8	8 2G378	OC78
T9	8 2G399A	2N1302
T10	8 2G417	AF117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1899 TEXAS. Our price 25p each.

120 VCB NIXIE DRIVER TRANSISTOR. Sim. 38X21 & C407, 2N1893 FULLY TESTED AND CODED N1290 - 1-24 17p each. 70-5 NPN. 25 up 45p each.

Sil. trans. suitable for P.E. Organ Metal TO-18 Eqvt. ZTX300 5p each. Any Qty.

EX-EQUIPMENT MULLARD
AF117 transistors. Large can 4 leads type. Leads cut short but still usable. Real value at 15 for 50p.

KING OF THE PAKS Unequaled Value and Quality SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back. Pak No.

U1	120 Glass sub-min. general purpose germanium diodes	0.50
U2	60 Mixed germanium transistors AF/RF	0.50
U3	75 Germanium gold bonded diodes sim. OA3, OA47	0.50
U4	40 Germanium transistors like OC81, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0.50
U8	50 Sil. planar diodes 250mA, OA200/202	0.50
U9	20 Mixed volts 1 watt Zener diodes	0.50
U10	30 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U11	30 PNP-NPN sil. transistors OC200 & 28104	0.50
U14	150 Mixed silicon and germanium diodes	0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	0.50
U23	30 Malt's like MAT series PNP transistors	0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300Mc/s NPN silicon transistors 2N708, BSY27	0.50
U26	30 Fast switching silicon diodes like IN914 micro-min	0.50
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	1.00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0.50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	0.50
U33	Plastic case 1 amp silicon rectifiers IN4000 series	0.50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	0.50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0.50
U36	25 sil. planar NPN trans. TO-5 BFY30/51/52	0.50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 28322	0.50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0.50
U39	30 RF germ. PNP trans. 2N1308/5 TO-5	0.50
U40	10 Dual trans. 6 lead TO-5 2N2060	0.50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF117.	0.50
U43	25 Sil. trans. plastic TO-18 A.F. BC113/114	0.50
U44	20 Sil. trans. plastic TO-5 BC115/116	0.50
U45	7 3A SCR's TO-66 up to 600 PIV	1.00

Some Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

NEW QUALITY TESTED PAKS

Pak	Description	Price
Q1	20 Red pot trans. PNP AF	0.50
Q2	16 White spot R.F. trans. PNP	0.50
Q3	4 OC77 type trans.	0.50
Q4	6 Matched trans. OC44/46/81/81D	0.50
Q5	4 OC75 transistors	0.50
Q6	4 OC73 transistors	0.50
Q7	4 AC128 trans. PNP high gain	0.50
Q8	4 AC126 trans. PNP	0.50
Q9	7 OC81 type trans.	0.50
Q10	7 OC71 type trans.	0.50
Q11	2 AC127/128 comp. pairs PNP/NPN	0.50
Q12	3 AF116 type trans.	0.50
Q13	4 AC117 type trans.	0.50
Q14	3 OC171 H.F. type trans.	0.50
Q15	5 2N2926 sil. epoxy trans.	0.50
Q16	2 GET880 low noise germ. trans.	0.50
Q17	3 NPN 1 ST141 & 2 ST140	0.50
Q18	4 Malt's 2 MAT 100 & 2 MAT 120	0.50
Q19	3 Malt's 2 MAT 101 & 1 MAT 121	0.50
Q20	4 OC34 germ. trans. A.F.	0.50
Q21	3 AC127 NPN germ. trans.	0.50
Q22	20 NKT trans. A.F. R.F. coded	0.50
Q23	10 OA202 sil. diodes sub-min.	0.50
Q24	8 OA81 diodes	0.50
Q25	6 IN914 sil. diodes 75PIV 75mA	0.50
Q26	8 OA95 germ. diodes sub-min. IN69	0.50
Q27	2 10A 600PIV sil. rect. 1845R	0.50
Q28	2 Sil. power rect. BYZ13	0.50
Q29	4 Sil. trans. 2 x 2N698, 1 x 2N697, 1 x 2N698	0.50
Q30	7 Sil. switch trans. 2N706 NPN	0.50
Q31	6 Sil. switch trans. 2N708 NPN	0.50
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0.50
Q33	3 Sil. NPN trans. 2N1171	0.50
Q34	7 Sil. NPN trans. 2N3699, 500MHZ.	0.50
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0.50
Q36	7 2N3646 TO-18 plastic 300MHZ NPN	0.50
Q37	3 2N3053 NPN sil. trans.	0.50
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702	0.50
Q39	7 NPN trans. 4 x 2N3704, 3 x 2N3705	0.50
Q40	7 NPN amp. 4 x 2N3707, 3 x 2N3708	0.50
Q41	3 Plastic NPN TO-18 2N3904	0.50
Q42	6 NPN trans. 2N5172	0.50
Q43	7 BC107 NPN trans.	0.50
Q44	7 NPN trans. 4 x BC108, 3 x BC109	0.50
Q45	3 BC113 NPN TO-18 trans.	0.50
Q46	3 BC115 NPN TO-5 trans.	0.50
Q47	6 NPN high gain 3 x BC167, 3 x BC168	0.50
Q48	4 BCX70 NPN trans. TO-18	0.50
Q49	4 NPN trans. 2 x BFY51, 2 x BFY52	0.50
Q50	7 BSY28 NPN switch TO-18	0.50
Q51	7 RB95A NPN trans. 300MHZ.	0.50
Q52	8 BY100 type sil. rect.	1.00
Q53	25 Sil. & germ. trans. mixed all marked new	1.50

PRINTED CIRCUITS—EX-COMPUTER
Packed with semiconductors and components, 10 boards give a guarantee of 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & F. 100 Boards \$3. P. & F.

POWER TRANSISTOR BONANZA!

GENERAL PURPOSE GERM. PNP POWER TRANSISTORS
Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE:—OC35-28-29-30-35-36. NKT 401-403-404 405-406-430-451-452-453. T13027-3028, 2N250A, 2N456A-457A-458A, 2N511 A & B, 2G220-222, ETC. SPECIFICATION V_{CE} 80V V_{CE} 50V I_C 10A PT. 30 WATTS H_{ie} 30-170

PRICE	1-24 100 up
	43p each 40p each 36p each

AD161 PNP
AD162 PNP
OF GERM. POWER TRANSISTORS. OUR LOWEST PRICE OF 85p PER PAIR

SILICON 50 WATTS MATCHED NPN-PNP
BIP19 pnp TO-3 plastic.
BIP20 pnp Brand new V_{CE} 10V V_{CE} 50V I_C 10A H_{FE} type 200 H_{FE} 300 H_{FE}

OUR PRICE PER PAIR	1-24 25-99 100
	pra. prs. prs.
	80p 55p 50p

2N3055
15 WATT SIL. POWER NPN
Price 65p each.

NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

FEET'S
2N3819 35p 2N5458 50p
2N3820 30p 2N5459 40p
2N3821 35p BFV10 40p
2N3823 30p MPP105 40p

PHOTO TRANS.
OCP71 Type. 43p

SILICON PHOTO TRANSISTOR. TO-18 Lens and NPN Sim. to BP 25 and P21. BRAND NEW. Full data available. Fully guaranteed.
Qty. 1-24 25-99 100 up
Price each 45p 40p 35p

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY27/28/95K. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	2p	100 For	1.75
	20 For	500 For	7.50
	50 For	1000 For	13.00

OUR STOCKS of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

RTL MICROLOGIC CIRCUITS

	Price each
uL900 Buffer	35p 33p 27p
uL914 Dual 2/p	
gate	35p 33p 27p
uL923 J-K flip-flop	50p 47p 45p

Data and Circuits Booklet for I.C.'s Free 7p.

Dual-In-Line Low Profile Sockets
14 and 16 Lead Sockets for use with Dual-In-Line Integrated Circuits

	Price each
Order No.	1-24 25-99 100 up
T80 14 pin type	30p 27p 25p
T80 16 pin type	30p 32p 30p

-the lowest prices!

74 Series T.T.L. I.C.'s DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.



BI-PAK Order No.	Price and qty. prices			BI-PAK Order No.	Price and qty. prices		
	1-24	25-99	100 up		1-24	25-99	100 up
BP00=8N7400	0-15	0-14	0-12	BP86=8N7486	0-32	0-30	0-28
BP01=8N7401	0-15	0-14	0-12	BP90=8N7490	0-87	0-84	0-88
BP02=8N7402	0-15	0-14	0-12	BP91=8N7491A	0-87	0-84	0-78
BP03=8N7403	0-15	0-14	0-12	BP92=8N7492	0-87	0-84	0-88
BP04=8N7404	0-15	0-14	0-12	BP93=8N7493	0-87	0-84	0-88
BP05=8N7405	0-15	0-14	0-12	BP94=8N7494	0-77	0-74	0-88
BP07=8N7407	0-18	0-17	0-16	BP95=8N7495	0-77	0-74	0-88
BP08=8N7408	0-18	0-17	0-16	BP96=8N7496	0-77	0-74	0-88
BP09=8N7409	0-18	0-17	0-16	BP100=8N74100	1-75	1-65	1-55
BP10=8N7410	0-15	0-14	0-12	BP104=8N74104	0-87	0-84	0-88
BP13=8N7413	0-29	0-28	0-24	BP105=8N74105	0-97	0-94	0-88
BP16=8N7416	0-43	0-40	0-38	BP107=8N74107	0-40	0-38	0-38
BP17=8N7417	0-43	0-40	0-38	BP110=8N74110	0-55	0-53	0-50
BP20=8N7420	0-15	0-14	0-12	BP111=8N74111	1-25	1-15	1-00
BP30=8N7430	0-15	0-14	0-12	BP118=8N74118	1-00	0-95	0-90
BP40=8N7440	0-15	0-14	0-12	BP119=8N74119	1-35	1-25	1-10
BP41=8N7441	0-67	0-64	0-58	BP121=8N74121	0-87	0-84	0-88
BP42=8N7442	0-67	0-64	0-58	BP140=8N74145	1-50	1-40	1-30
BP43=8N7443	1-85	1-85	1-75	BP150=8N74150	1-80	1-70	1-80
BP44=8N7444	1-85	1-85	1-75	BP151=8N74151	1-00	0-95	0-90
BP45=8N7445	1-95	1-85	1-75	BP155=8N74155	1-20	1-10	0-95
BP46=8N7446	0-97	0-94	0-88	BP158=8N74158	1-80	1-70	1-60
BP47=8N7447	0-97	0-94	0-88	BP155=8N74155	1-40	1-30	1-20
BP48=8N7448	0-97	0-94	0-88	BP156=8N74156	1-40	1-30	1-20
BP49=8N7449	0-15	0-14	0-12	BP160=8N74160	1-80	1-70	1-80
BP51=8N7451	0-15	0-14	0-12	BP161=8N74161	1-80	1-70	1-80
BP53=8N7453	0-15	0-14	0-12	BP163=8N74163	2-00	1-80	1-80
BP54=8N7454	0-15	0-14	0-12	BP164=8N74164	2-00	1-80	1-80
BP60=8N7460	0-15	0-14	0-12	BP181=8N74181	2-75	2-60	2-40
BP70=8N7470	0-29	0-28	0-24	BP182=8N74182	0-97	0-94	0-88
BP72=8N7472	0-29	0-28	0-24	BP190=8N74190	3-50	3-25	3-00
BP73=8N7473	0-37	0-35	0-32	BP191=8N74191	3-50	3-25	3-00
BP74=8N7474	0-37	0-35	0-32	BP192=8N74192	2-10	1-95	1-75
BP75=8N7475	0-47	0-45	0-42	BP193=8N74193	2-10	1-95	1-75
BP76=8N7476	0-43	0-40	0-38	BP195=8N74195	1-10	1-05	0-95
BP80=8N7480	0-67	0-64	0-58	BP198=8N74198	1-80	1-70	1-60
BP81=8N7481	0-67	0-64	0-58	BP197=8N74197	1-80	1-70	1-60
BP82=8N7482	0-97	0-94	0-88	BP198=8N74198	5-50	5-00	4-00
BP83=8N7483	1-10	1-05	0-95	BP199=8N74199	5-50	5-00	4-00

PRICE-MIX. Devices may be mixed to qualify for quantity prices.

PRICES for quantities in excess of 500 pieces mixed, on application.

Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442.

NUMERICAL INDICATOR TUBE Type MG-17G

Cold Cathode gas-filled, side-viewing numerals (0-9) and Decimal Point.

COLOUR: Neon Red.

DATA: Anode supply voltage 180 min V d.c.
Cathode current: 0.35 Nom mA d.c.

Ideal for use in constructing Digital Clocks, Desk Calculators, etc., and many products described in this magazine. We recommend use of BP41 or BP141 to drive this tube.



Full data available on request.

PRICE: 1-5, £1.55; 6-25, £1.40 ACTUAL SIZE

BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	Price		
				1-24	25-99	100 up
BP 201C—8L201C	TO-5	8	G.P. Amp	63p	53p	45p
BP 701C—8L701C	TO-5	8	OP Amp	63p	53p	45p
BP 702C—8L702C	TO-5	8	OP Amp Direct OP	63p	53p	45p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p	45p	40p
BP 709—72709	D.I.L.	14	High OP Amp	53p	45p	40p
BP 709P—μA709P	TO-5	8	High Gain OP Amp	53p	45p	40p
BP 710—72710	D.I.L.	14	Differential comparator	53p	45p	40p
BP 711—μA711	TO-5	10	Dual comparator	58p	50p	45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p	60p	50p
μA 703C—μA703C	TO-5	6	R.F.—I.F. Amp	43p	35p	27p
TAA 263—	TO-72	4	A.F. Amp	70p	60p	55p
TAA 292—	TO-74	10	I.F. Amp	90p	75p	70p
TAA 350—	TO-5	8	Wide load limiting amplifier	170p	158p	150p

STOP PRESS! NOW OPEN

BI-PAK'S NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices. Expert technical advice freely given.

18 BALDOCK ST. (A10) WARE, HERTS. Tel. 61593
OPEN 9.15-6 TUES. to SATS. FRIDAYS UNTIL 8 p.m.

ANOTHER BI-PAK FIRST!

THE NEW S.G.S. EA 1000
AUDIO AMPLIFIER
MODULE



***GUARANTEED NOT LESS THAN 3 WATTS RMS**

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA1021 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40mV for 1 watt VOLT-AGE GAIN 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50Hz to 25KHz for -3dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1".
- Typical Total Harmonic distortion at 1 watt less than 1%.
- Supply voltage (V_s)=24V 150hm load. Module Tested and guaranteed.

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

NOTE THESE PRICES!

I.C.'s		DTL 930 SERIES	LOGIC
Type No.	Function	1-24	25-99 100 up
BP930	Expandable dual 4-input NAND	13p	11p 10p
BP932	Expandable dual 4-input NAND buffer	13p	12p 11p
BP933	Dual 4-input expander	13p	12p 11p
BP935	Expandable Hex Inverter	13p	12p 11p
BP936	Hex Inverter	13p	12p 11p
BP944	Dual 4-input NAND expandable buffer without pull-up	13p	12p 11p
BP945	Master-slave JK or RS	25p	24p 22p
BP946	Quad, 2-input NAND	12p	11p 10p
BP948	Master-slave JK or RS	25p	24p 22p
BP951	Monostable	65p	60p 55p
BP952	Triple 3-input NAND	12p	11p 10p
BP9093	Dual Master-slave JK with separate clock	40p	38p 35p
BP9094	Dual Master-slave JK with separate clock	40p	38p 35p
BP9097	Dual Master-slave JK with Common Clock	40p	38p 35p
BP9099	Dual Master-slave JK Common Clock	40p	38p 35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only.)

DTL AND TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	Pak No.	Pak No.	Pak No.
UIC930 = 12 x μA 930	50p	UIC948 = 8 x μA 948	50p
UIC932 = 12 x μA 932	50p	UIC951 = 5 x μA 951	50p
UIC933 = 12 x μA 933	50p	UIC961 = 12 x μA 961	50p
UIC935 = 12 x μA 935	50p	UIC969 = 5 x μA 969	50p
UIC936 = 12 x μA 936	50p	UIC9094 = 5 x μA 9094	50p
UIC944 = 12 x μA 944	50p	UIC9097 = 5 x μA 9097	50p
UIC945 = 8 x μA 945	50p	UIC9099 = 5 x μA 9099	50p
UIC946 = 12 x μA 946	50p	UIC x 925 Assorted 930 Series	£1.50

Paks cannot be split but 25 Assorted Pieces (our mix) is available as PAK UICX9. Data Booklet available for the BP930 Series, PRICE 13p.

UIC00 = 12 x 7400N	50p	UIC46 = 5 x 7446N	50p	UIC81 = 5 x 7481N	50p
UIC01 = 12 x 7401N	50p	UIC47 = 5 x 7447N	50p	UIC82 = 5 x 7482N	50p
UIC02 = 12 x 7402N	50p	UIC48 = 5 x 7448N	50p	UIC83 = 5 x 7483N	50p
UIC03 = 12 x 7403N	50p	UIC50 = 12 x 7450N	50p	UIC86 = 5 x 7486N	50p
UIC04 = 12 x 7404N	50p	UIC51 = 12 x 7451N	50p	UIC90 = 5 x 7490N	50p
UIC05 = 12 x 7405N	50p	UIC53 = 12 x 7453N	50p	UIC91 = 5 x 7491N	50p
UIC10 = 12 x 7410N	50p	UIC54 = 12 x 7454N	50p	UIC92 = 5 x 7492N	50p
UIC13 = 8 x 7413N	50p	UIC60 = 12 x 7460N	50p	UIC93 = 5 x 7493N	50p
UIC20 = 12 x 7420N	50p	UIC70 = 8 x 7470N	50p	UIC94 = 5 x 7494N	50p
UIC40 = 12 x 7440N	50p	UIC72 = 8 x 7472N	50p	UIC95 = 5 x 7495N	50p
UIC41 = 5 x 7441N	50p	UIC73 = 8 x 7473N	50p	UIC96 = 5 x 7496N	50p
UIC42 = 5 x 7442N	50p	UIC74 = 8 x 7474N	50p	UIC97 = 5 x 7497N	50p
UIC43 = 5 x 7443N	50p	UIC75 = 8 x 7475N	50p	UICX1 = 25 x Assort'd	74's £1.50
UIC44 = 5 x 7444N	50p	UIC76 = 8 x 7476N	50p		
UIC45 = 5 x 7445N	50p	UIC80 = 5 x 7480N	50p		

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department


BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

BUILD A PROJECT 'X'

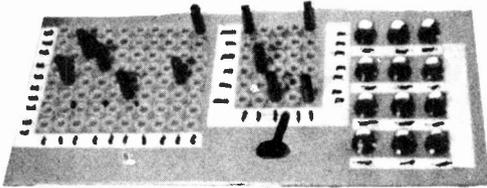

SYNTHESISER

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES

MAN-SIZED ROBUST PATCHBOARD

MAKE A "PATCH" AS IF YOU MEAN IT. "K-L-O-N-K" and it's MADE!

No fiddling with fragile patch pins. No cables. Countless possible combinations giving **FULL RANGE EFFECTS**.

VOLTAGE CONTROL

Voltage-controlled filters, oscillators, amplifiers and . . . *P-H-A-S-E*

Yes, **Dewtron** have perfected **voltage-controlled phase** in module form.

CASH SAVINGS

by buying modules and parts in bulk!
All modules are available separately:

Ring Modulator RM2, £7. Voltage-controlled Oscillator VC01, £9.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £12.50. White noise type WN1, £6. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12.

Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc.

ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! (Joystick control optional.)

With over 7 years' unblemished reputation in these pages, **Dewtron** continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group.

Send s.a.e. for synthesiser details or send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

HANDYMEN SWEAR BY IT

IT'S WHAT THE
TRADE USES

cleans hands

Manufactured by
deb CHEMICAL PROPRIETARIES LIMITED,
BELPER, DERBY, DE5 1JX

Introduction to Field Effect Transistors



by J. Watson Ph.D.,
University of Wales

128 pages about the theory and applications of field effect transistors: • Introduction to the field effect transistor • Characteristics, parameters and tolerances of the field effect transistor • Biasing and audio-frequency amplification • Voltage-controlled resistors, current limiters and d.c. amplifiers • High-frequency amplifiers and mixers • FET switches, choppers and analogue gates. • Integrated circuits • Miscellaneous devices and applications. Price £1.00



SILICONIX LTD.
Sketty, Swansea, SA2 8BA
Tel: Swansea (0792) 21221



Please send _____ copy/copies of "an Introduction to Field Effect Transistors" for which I enclose cheque/P.O. No. _____ to the value of £

Name _____

Company _____

Address _____

price
£1.00
inc. P&P

Siliconix Limited

BI-PRE-PAK



TELEPHONE DIALS
Standard Post Office type.
Guaranteed in working order.

ONLY 50p

8 RELAYS FOR £1
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
BB1	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC7175 uncodded black glass type PNP Germ.	50p
H19	10	OC8181D uncodded white glass type PNP Germ.	50p
H28	20	OC200/11/23 PNP Silicon uncodded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA, Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		4p	
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	OG301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-30
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194	0-15	Power Transistors	
BF274	0-15	OC20	0-50
BFY50	0-20	OC23	0-30
BSY35	0-57	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-37
BSY29	0-13	OC36	0-37
BSY95A	0-15	AD149	0-30
OC41	0-13	AUY10	1-25
OC44	0-13	AS034	0-25
OC45	0-13	IN3055	0-50
OC71	0-13		
OC72	0-13	Diodes	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN914	0-07

F.E.T. PRICE BREAKTHROUGH !!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.
IN4004, 500+ at 5p each; 1,000+ at 5p each.
IN4006, 500+ at 6p each; 1,000+ at 5p each.
IN4007, 500+ at 8p each; 1,000+ at 7p each.

FREE CATALOGUE AND LISTS FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS



CLEARANCE LINES

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested			
Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-00	90p	80p
UL914 Dual 2 I/P Gate	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines: B.P.I Transistor Equivalents and Substitutes;

This includes many thousands of British U.S.A., European and C.V. equivalents. **The Iliffe Radio Valve & Transistor Data Book 9th Edition;** Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications.

40p

75p

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD


DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHCEND (0702) 46344

WHARFEDALE SPEAKER BARGAINS

DENTON 2

SAVE £8.40

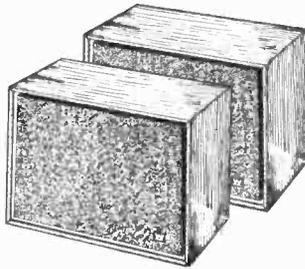Sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8in. bass unit with 3in pressure unit, coupled by a Wharfedale crossover network. Rated input: 18 watts maximum. Frequency response: 65-17,000Hz. Impedance: 4/8 ohms. Cabinet 9½in x 14in x 8½in.



ALL SPEAKERS AVAILABLE IN TEAK OR WALNUT

List Price LASKY'S
£39.90 PRICE

PER PAIR **£31.50** C & P £2

	List Price	Lasky's C & P Price		List Price	Lasky's C & P Price		
LINTON 2	£49.90	£39.95	£2	ROSEDALE	£65.00	£50.00	£1
per pair				each			
TRITON 3	£65.00	£53.50	£2	UNIT 3	£12.50	£9.70	50p
per pair				each			
MELTON 2	£35.00	£25.50	£1	UNIT 4	£18.00	£12.50	50p
per pair				each			
DOVEDALE 3	£45.00	£33.00	£1	UNIT 5	£26.00	£18.50	50p
each				each			

EXCLUSIVE TM-1


1,000 Ohms Volt MINI-TESTER

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to 3in of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case with white and metallic red/green figuring. Ohms zero adjustment.

Size Only

- 3½in x 2½in x 1½in
- DC/V: 0-10-50-250-1,000 at 1k OPV
- AC/V: 0-10-50-250-1,000 at 1k OPV
- DC CURRENT: 0-1mA, 100mA

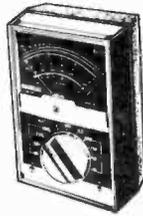- Resistance: 0-150k
- Decibels: -10dB to 22dB
- Complete with test leads, battery and instructions



LASKY'S PRICE **£1.85**

C & P 15p

TM-5 5K ohms/V POCKET MULTIMETER

Another new look pocket multimeter from Lasky's providing top quality and value. The "mini" impact resistant case, size 4½in x 2½in x 1½in, fitted with extra large 2½in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC/V: 3-15-150-300-1,200 at 5k OPV
- AC/V: 6-30-300-600 at 2.5k/OPV
- DC Current 0-300µA, 0-300mA

- Resistance: 0-10k/ohms, 0-1M/ohm
- Decibels: -10dB to +16dB
- Complete with test leads, battery and instructions.

LASKY'S PRICE **£2.75**

C & P 35p

LASKY'S NEW "LOW NOISE" CASSETTES FROM the U.S.A.

Model	Singles	5	10	20
C. 60	32p	£1.52	£2.96	£5.60
C. 90	50p	£2.37	£4.62	£8.75
C. 120	69p	£3.27	£6.38	£10.85

Post Each 7p. 5-25p. 10-40p. 20-65p.

OUT NOW! 1972 AUDIO-TRONICS

The great new 1972 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and don't miss LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

ALSO the fantastic £1,000 plus SON'Y Colour TV Audio-Tronics '72 Competition

TMK MODEL 200 METER KIT

TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement, mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional circuit and operating instructions.

Specification

20,000 P.O.V. Multimeter. Features 24 measurement ranges with mirror scale accuracy. DC/V and current: 2% A.C.V: 3%. Resistance: 3%. Special 0-6V DC range for transistor circuit measurements.




ONLY

LASKY'S PRICE **£4.60**

C & P 15p

DIGITAL CLOCK SCOOP

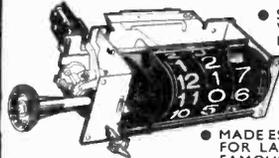

- SHOCK AND VIBRATION PROOF
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION

- BUILT-IN ALARM BUZZER

EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing. The clock measures 4½W x 1½H x 3½D (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions.


HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS

LASKY'S PRICE **£6.50**

C & P 25p

SPECIAL QUOTATIONS FOR QUANTITIES

BARGAIN SCOOP!

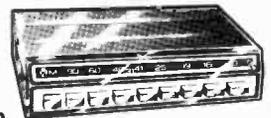

PYE S.W. CAR RADIO CONVERTER MODEL 2649

High quality transistorised and ultra compact Shortwave Converter for use with any suitable MW (AM) Car Radio. Self powered for use on 12V positive or negative earth systems. The model 2649 is simply connected to the radio via the aerial socket and provides shortwave covering in 9 push-button selected band spread ranges (13, 16, 19, 25, 31, 41, 49, 60 and 90 M) combined with the normal radio tuning to give full cover from 3.2MHz-21.75MHz. On/off switch and by-pass switch for normal MW radio use. Complete with mounting bracket fitting and alignment instructions. Black hammer crackle finished case—size: 6(W) x 1¼(H) x 3¼(D) in.

Made to sell approx. £20 LASKY'S PRICE **£8.75**

C & P 20p

Lasky's Radio Limited

Branches:

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271.
33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605
Open all day 9 a.m. - 6 p.m. Monday to Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573
Open all day 9 a.m. - 6 p.m. Monday to Saturday

NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812
Open all day Thursday, early closing 1 p.m. Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST. TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821





"Where can I get exclusive ROC ELECTRONICS!"

ACADEMY STEREO CASSETTE TAPE DECK, MODEL CS-20000

No hi-fi system is complete without one—hook it up to any ROC or other good quality amplifier, and the results are fantastic! The CS-20000 records and plays back. A big feature is its easy-to-use piano-key controls. Easy-to-get-at mic inputs are on top; line inputs and outputs at the rear.

Dual-channel recording level meter. Pop-up cassette ejection. Stereo/Mono button. Tape counter. Pause control. Tape speed 1½ ips (4-75 cms). Frequency response 100-10,000 Hz. Wow and flutter better than 0.3%. Rewind time better than 80 sec with C60 cassette. Engineered throughout to the highest electrical and mechanical standards. Size 16" wide, 4½" high and 8" deep. Walnut cabinet with satin aluminium trims.

ROC PRICE
£54.95

Including two pencil microphones and all connecting leads.
Normal Price £65.00



ROC PRICE
£98.50

Including connecting leads.
Normal Price £115.00

REALISTIC HI-FI 36-WATT STEREO CONCERTMASTER FM-AM RECEIVER SYSTEM, MODEL 12-694

Brightly designed tuner/amplifier with two matching speakers. All three units in beautifully finished walnut cabinets with smart aluminium vertical trims. The tuning dial is fronted by unique Black glass. Figures light up behind it in green when the unit is on. Separate easy-to-operate Left and Right volume controls.

Microswitch for on/off Programme selector. Separate bass and treble controls. Headphones socket on front panel for easy access. Single tuning knob for FM and AM. Built-in aerials, facilities for external FM aerial. Illuminated dial. Stereo broadcast indicator light. Each speaker has 6½" bass and 3" treble units. Output: 9 watts r.m.s. per channel into 8 ohms. Frequency response: 30 to 20,000 Hz. FM: frequency range 80-108 MHz, sensitivity 2.5µV, stereo separation 30dB, image rejection 40dB. AM: frequency range 530-1605 kHz, sensitivity 100µV. Sizes: speakers 8" wide, 12" high and 9½" deep; receiver 6" wide, 12" high and 9½" deep. And their sophisticated appearance matches the excellence of the specification.

ROC PRICE
£76.50

Normal Price £95.00



ROC PRICE
£27.25

Normal Price £39.95 each.

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted — for under £46.00. Saving over £10.00 on the normal retail value.

Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls — magnetic phono (high/low) tuner, aux, mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz + 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono — 50dB; tuner/aux — 65dB. How's that for a specification! Size 14½" wide, 3½" high, 10½" deep.

ROC PRICE
£43.75

Normal Price £55.50




8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST

The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual override. Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed 3½ ips (9.5 cms). Frequency response: playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect in a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut. Including connecting leads.

ROC PRICE
£39.95

Normal Price £49.00

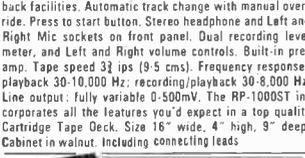


25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-5b

This high quality speaker has its own built-in 3-way sound response switch.

Giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10½" x 7½" x 8½". Exactly right for matching the most modern decor.

ROC PRICE
£33.20

Normal Price £42.00

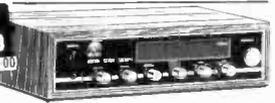

PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16


This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received — that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much — separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz. AM 535-1605 kHz. Frequency response: 50-10,000 Hz + 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4½" high, 8" deep.

ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5½" wide, 1½" high and 6½" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 60mV; signal-to-noise ratio better than 45dB.

ROC PRICE
£5.50

Normal Price £7.75

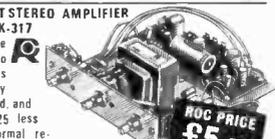

ROC PRICE
£18.25

Normal Price £25.20



OLSON AM-372 16-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price — nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you — reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12½" wide, 3½" high, 7½" deep.

ROC PRICE
£10.50

Normal Price £14.70



OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as it's good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free to supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz; AM: 525-1605 kHz. 60dB. Size: 11½" wide, 4" high, 7½" deep.

ROC PRICE
£39.95

Normal Price £50.00



REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5½" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/headphone enameled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz + 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.

ROC PRICE
£14.50

Normal Price £21.00



REALISTIC TM-100 AM/FM/MPX STEREO TUNER

Here's another unit that gives you fabulous value in miniature! Designed specifically to match the Realistic SA-100B in both appearance, size and performance, the TM-100 is superb value-for-money. It gives you the full FM and AM ranges — FM, 88-108 MHz, AM, 535-1605 kHz. Sensitivities: FM 5µV, AM 250µV. Image rejection 50dB.

ROC PRICE
£23.25

Normal Price £28.60



OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for tapping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3-0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size 11½" wide, 4" high, 7½" deep. The specification reads well — sounds even better!

ROC PRICE
£29.00

Normal Price £39.50



8-TRACK HOME STEREO CARTRIDGE PLAYER MODEL E1

With this unit, you can play any standard 8-track cartridge on the market — at a fraction of the normal retail value! It gives you a total of 5 watts of power, to feed into two 8-ohm speakers. The frequency response is 50 to 10,000 Hz, giving you a fine tonal quality that can't be bettered at anything near this price. The E1 has separate tone, balance and volume controls, giving you complete freedom to select the sound you want to hear. Tape speed is 3½ ips, and wow and flutter are both less than 0.3%. Size 11½" wide, 5" high, 11" deep.

R.446 3-WAY MATCHED SPEAKERS

These will do justice to your amplifier — and to your pocket. At only £16.40 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6½" deep.

OLSON AM-357 4-WATT STEREO AMPLIFIER

Here's marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2½" high, 4½" wide.



ROC PRICE
£16.40

Normal Price £22.50 per pair.



units at lowest prices?..."

Compare our prices with any other unit on the hi-fi market, and you'll find you won't beat ROC unit prices. No matter where you live, London or Land's End!

Take a good look at all these super audio equipment bargains. They're all on demonstration at our Shop from 9 to 6 p.m. Monday to Saturday, late night Thursday until 7 p.m. But don't worry if you can't get there yourself. Our Mail Order service is at your disposal. With the same exclusive ROC equipment - and at the same super value-for-money prices!

When you invest in ROC equipment, you're getting much more than an exclusive product. You're getting value for money that is literally unbeatable. ROC units are bought direct from the manufacturer, and ALL the savings ROC derive from this are passed on to you!

At ROC Electronics, we take extra care to select only the best buys. We check everything before you do - and it's fully guaranteed whether you buy at the shop or by Mail Order.



ROC
exclusive unit

TOP VALUE • TOP QUALITY ACCESSORIES THAT EVERY HI-FI ENTHUSIAST NEEDS TO COMPLETE HIS SYSTEM

Every item shown here is the best of its kind within its price range. Buy them separately or at the same time as the other top-value audio products listed.

THORENS TD150AB/II
Transcription Turntable
Complete with pick-up arm,
plinth and cover. £52.31



R.328 STEREO HEADPHONE
If you're starting in hi-fi, and you discover the need for a pair of really good stereo headphones, the R.328 is ideal, at a price you can afford. They have padded ear cushions, a 6-foot cord and jack plug. Frequency range 30-15,000 Hz. Impedance 8 ohms per channel. **ROC PRICE £2-95**



EAGLE SE-80 STUDIO STEREO HEADPHONE

Here's the ultimate in headphone design! Apart from its fantastic ability to reproduce all the frequencies from 20 to 20,000 Hz, the SE-80 has eliminated the discomfort and strain associated with traditional headphone design. Eagle has designed and produced a pair of headphones which breaks with all previous concepts. You hear all the sound crisp and clear. In fact, the reproduction is so good, that it compares favourably with the most expensive hi-fi speaker systems. Separate slider volume control on each earpiece. Impedance: 8 ohm per channel. **ROC PRICE £14-90**



R.186 STEREO HEADPHONE JUNCTION BOX

If you want easy, fingertip control of headphones and loudspeakers, here's the ideal solution to the problem. All you do is connect it to your speakers and amplifier, plug in your headphones - and you're ready to take over! At the flick of a slide switch, you can have headphones alone, or speakers alone, or both together. Input: suitable for use with amplifiers rated up to 20 watts. Size: 2 1/4" x 3 1/2" x 1 1/2". **ROC PRICE £1-50**



EAGLE SE-30 STEREO HEADPHONE

This model is for the more discriminating listener. For a start the frequency range extends from 30 to 16,000 Hz. And you can adjust the volume of each earpiece independently. There's also a mono/stereo switch. For maximum comfort, the ear cushions are covered in soft leathers. **ROC PRICE £7-05**



TTC HR-007 HEADPHONE RADII

When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW. Normal Price £9.45 **ROC PRICE £7-65**



EAGLE 8-TRACK CAR STEREO PLAYER, CS.8

Drive to the sound of music - with this fabulous 8-Track Car Stereo Player. It gives you superb tone and power to fill the car with stereo sound. Ideal for use with R.151 or R.152 speakers. Complete with all mounting accessories. For negative earth electrical systems only. Output: 2.5 watts per channel. Frequency range: 70-10,000 Hz. Wow and flutter: less than 0.3%. Tape speed: 3.5 cm/sec. Channel selector: automatic with manual over-ride. Mounting dimensions: 5 1/2" x 5 1/2" x 2 1/4". **ROC PRICE £27-20**

"WATTS" RECORD CLEANERS

The original "Dust Bug" Automatic Record Cleaner keeps your records clean as they play. £1-20 Watts Disc Preener. Keeps new records like new - for perfect record reproduction. 35p

R.307 TRANSISTORIZED STEREO PRE-AMPLIFIER

Now your amplifier that could only reproduce ceramic or crystal pick-up cartridges, can accept signals from moving-magnet cartridges! The R.307 steps up signals from between 5-20mV to 200-800 mV. Input: 5-20mV. Equalization: RIAA. Output: 200-800mV flat. Frequency range: 20-22,000 Hz. Dimensions: 3 1/2" x 1 1/2" x 2 1/4". Supply: 240 Vac. **ROC PRICE £4-92**

15-FOOT STEREO HEADPHONE EXTENSION CORD R.362

Fitted with heavy duty 3-circuit stereo plug at one end and a matching stereo socket at the other. **ROC PRICE £1-30**

STEREO HEADPHONE "Y" ADAPTOR R.361

Enables you to use two sets of stereo headphones from a single socket. Fitted with male plug and two female sockets. **ROC PRICE £1-30**

R.151 STEREO CAR SPEAKERS

Smart black, tough, plastic cases, each containing a high flux 110mm diameter speaker unit. Just what you need to go with the CS.8 Cartridge Player or any other car stereo system. Fitted with over three yards of connecting cable. Dimensions: 6 1/2" x 5 1/2" x 3 1/2". Impedance: 8 ohms per speaker. Rating: 5 watts max per speaker. **ROC PRICE £3-72**

R.152 STEREO CAR SPEAKERS

These sloping front speakers match the CS.8 Cartridge Player or any other car stereo system. Fitted with high flux 110mm diameter speaker unit, and over three yards of connecting cable. Dimensions: 6 1/2" x 6 1/2" x 3 1/2". Impedance: 8 ohms per speaker. Rating: 5 watts max. per speaker. **ROC PRICE £4-96**

EAGLE LC.05 STEREO MAGNETIC CARTRIDGE

For fabulous reproduction at a very low price, you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: ±1.5dB. Channel separation: 20dB. Recommended stylus pressure: 2.4 grams. Compliance: 9 x 10⁻⁶ cm/dyne. **ROC PRICE £4-75**

EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE

Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ±1dB. Channel separation: 28dB. Compliance: 12 x 10⁻⁶ cm/dyne. **ROC PRICE £6-37**

R.088 MATCHED STEREO LOUD-SPEAKERS

Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9-50** pair

R.088 MATCHED STEREO LOUD-SPEAKERS


Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9-50** pair

EAGLE DL.67 HIGH COMPLIANCE 3-WAY TEAK SPEAKER SYSTEM

From a rich, deep, 35 Hz bass to above the limit of human hearing - this fantastic response comes from such a small size - only 10" x 6" x 6 1/2"! The DL.67 is the end product of several years' effort into the problems of full frequency response from small cabinets. The DL.67 has a dual cone high compliance bass mid range unit, and a horn tweeter. The speaker has a variable brilliance control to suit individual rooms - a feature normally only found on very expensive speaker systems. Power handling capacity: 10 watts rms, 20 watts peak. Frequency range: 35-20,000 Hz. Flux density: 11,000 gauss. Impedance: 8 ohms. Dimensions: 11 1/2" high x 8" wide x 6 1/2" deep. Finish: oiled teak. **ROC PRICE £18-80** each

HERE'S A RANGE OF AUDIO SYSTEMS BUILT AROUND EXCLUSIVE ROC AMPLIFIERS AND TUNERS

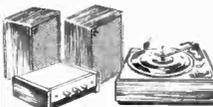Now run your eye over the prices, select the System nearest to your budget - and you've hit on the best value that your money can buy! Supplied with all necessary leads and plugs, ready to use.



OLSON AM-357 SYSTEM
Olson AM-357 Stereo Amplifier, Garrard 2025 T/C Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.088 4 watt Speakers. Normal Price £45-28 **ROC PRICE £36-70**



OLSON AM-372 SYSTEM
Olson AM-372 Stereo Amplifier, Garrard 2025 T/C Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers. Normal Price £68-18 **ROC PRICE £51-53**



REALISTIC SA-100B SYSTEM
Realistic SA-100B Stereo Amplifier, Garrard 2025TC Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers. Matching TM-100 Stereo Tuner £23-25 extra if required. Normal Price £63-98 **ROC PRICE £47-60**



PALACE SYSTEM
Palace SSA-16 Stereo Tuner Amplifier, Garrard 2025 T/C autochanger with stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers. Normal Price £84-98 **ROC PRICE £66-30**



REALISTIC 12-694 SYSTEM
Realistic 12-694 Stereo Tuner Amplifier with matching speakers and Garrard SP25 Mk III with Eagle LC.07 Stereo Magnetic Cartridge and plinth and cover. Normal Price £144-05 **ROC PRICE £124-50**



OLSON AM-395 SYSTEM
Olson AM-395 Stereo Amplifier, Garrard SP25 Mk III Record Player with Eagle LC.07 Stereo Magnetic Cartridge, plinth and cover and a pair of Eagle DL.67 Speakers. Matching RA.310 Stereo Tuner £39-95 extra if required. Normal Price £106-65 **ROC PRICE £92-60**



REALISTIC SA-500 SYSTEM
Realistic SA-500 Stereo Amplifier, Garrard SP25 Mk III Single Record Player with Eagle LC.07 Stereo Magnetic Cartridge, plinth and cover and a pair of Cryster CE.5b Speakers. Normal Price £157-95 **ROC PRICE £124-00**



ROC E1 SYSTEM
ROC E1 8 track Stereo Cartridge Player complete with a pair of ROC R.088 4 watt Speakers. Normal Price £59-10 **ROC PRICE £49-45**

Return-of-post
mail order service.
Over £10 post free
(UK only). Add 25p
for p & p to orders
under £10
HP terms available
for callers

ROC ELECTRONICS LTD

N. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211

CALLERS WELCOME AT THE SHOP
9-6 MON TO SAT,
LATE NIGHT THURSDAY 7 PM





who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

Not as a Programmer but an Operator - No maths and no special education.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new data preparation personnel will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 734 2874 NOW!

Or post the coupon today for full details FREE and without obligation.

London Computer Operators Training Centre,

E2, Oxford House, 9/15 Oxford Street, London, W.1.

Telephone (01) 734 2874.

127/131 The Piazza, Dept. E2. Piccadilly Plaza, Manchester 1.

Telephone (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name _____

Address _____

Tel.: _____

RST VALVE MAIL ORDER CO.
BLACKWOOD HALL
16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free

sp	sp	sp	sp	sp	sp
1N21 0-17	AC126 0-20	BF173 0-25	GJAM 0-28	OC43 0-17	
1N23 0-20	AC127 0-25	BF181 0-25	GJ4M 0-25	OC44 0-17	
1N65 0-25	AC128 0-20	BF184 0-20	GJ7M 0-27	OC44M 0-17	
1N263 0-20	AC187 0-25	BF185 0-20	HG1005 0-40	OC45 0-12	
1N266 0-20	AC188 0-25	BF194 0-17	H8100A 0-20	OC45M 0-12	
1N645 0-25	ACY17 0-20	BF195 0-15	MAT100 0-25	OC46 0-27	
1N725A 0-20	ACY18 0-25	BF196 0-15	MAT101 0-25	OC7 0-20	
1N914 0-07	ACY19 0-25	BF197 0-15	MAT120 0-25	OC58 0-20	
1N4007 0-20	ACY20 0-20	BF861 0-22	MAT121 0-20	OC59 0-25	
18021 0-20	ACY21 0-20	BF898 0-22	MJE520 0-27	OC66 0-20	
18113 0-15	ACY22 0-10	BFX12 0-20	MJE2955 1-27	OC70 0-20	
18130 0-12	ACY27 0-25	BFX13 0-25	MJE3055 0-27	OC71 0-12	
18131 0-15	ACY28 0-17	BFX21 0-25	NKT218 1-12	OC72 0-20	
18202 0-22	ACY39 0-20	BFX30 0-25	NKT129 0-20	OC73 0-20	
2Q240 1-27	ACY40 0-15	BFX35 0-25	NKT211 0-25	OC74 0-20	
2G301 0-20	ACY41 0-15	BFX63 0-20	NKT218 0-25	OC75 0-25	
2G302 0-22	ACY44 0-25	BFX84 0-25	NKT214 0-15	OC76 0-25	
2G306 0-20	AD140 0-20	BFX85 0-20	NKT216 0-27	OC77 0-20	
2G371 0-22	AD149 0-20	BFX86 0-25	NKT217 0-25	OC78 0-20	
2G381 0-25	AD161 0-20	BFX87 0-25	NKT218 0-25	OC79 0-20	
2G414 0-30	AD182 0-27	BFX88 0-20	NKT219 0-25	OC81 0-20	
2G417 0-22	AF106 0-30	BFY10 1-00	NKT222 0-20	OC81D 0-20	
2N214 0-43	AF114 0-25	BFY11 1-25	NKT224 0-22	OC81M 0-20	
2N247 0-25	AF115 0-25	BFY17 0-25	NKT251 0-24	OC81DM 0-18	
2N250 0-50	AF118 0-25	BFY18 0-25	NKT271 0-25	OC81Z 0-40	
2N404 0-20	AF117 0-25	BFY19 0-25	NKT272 0-25	OC82 0-25	
2N297 0-20	AF120 0-25	BFY24 0-25	NKT273 0-25	OC82D 0-20	
2N698 0-20	AF119 0-20	BFY44 1-20	NKT279 0-20	OC83 0-25	
2N708 0-10	AF124 0-25	BFY60 1-20	NKT275 0-25	OC84 0-25	
2N706A 0-12	AF125 0-20	BFY61 0-20	NKT277 0-20	OC114 0-25	
2N708 0-15	AF126 0-17	BFY62 0-20	NKT278 0-25	OC122 0-20	
2N709 0-25	AF127 0-17	BFY63 0-17	NKT301 0-40	OC123 0-25	
2N711 0-27	AF130 0-20	BFY64 0-42	NKT304 0-75	OC139 0-25	
2N687 0-52	AF178 0-55	BFY65 0-65	NKT403 0-25	OC140 0-25	
2N1090 0-30	AF179 0-65	B8X27 0-50	NKT404 0-55	OC141 0-20	
2N1091 0-33	AF180 0-62	B8X60 0-25	NKT678 0-20	OC169 0-20	
2N1131 0-25	AF181 0-42	B8X76 0-15	NKT713 0-25	OC170 0-25	
2N1132 0-25	AF186 0-40	B8Y26 0-18	NKT773 0-25	OC171 0-20	
2N1302 0-18	AFY119 1-13	B8Y27 0-17	NKT777 0-25	OC200 0-40	
2N1303 0-18	AFZ11 0-25	BFV51 0-25	07B5 0-25	OC201 0-70	
2N1304 0-22	AFZ12 1-00	B8Y95A 0-12	0A5 0-20	OC202 0-20	
2N1305 0-22	ASV26 0-25	B8Y95 0-12	0A6 0-12	OC203 0-40	
2N1306 0-25	ASV27 0-22	BT102/500R 0-75	0A7 0-10	OC204 0-40	
2N1307 0-25	ASV28 0-25	BTY42 0-22	0A7 0-25	OC205 0-75	
2N1308 0-25	ASV29 0-20	BTY79/100R 0-45	0A9 0-10	OC206 0-20	
2N1309 0-25	ASV30 0-25	BTY79/100R 0-45	0A74 0-10	OC207 0-20	
2N1420 0-22	ASV50 0-17	BTY79/400R 0-75	0A79 0-10	OC480 0-20	
2N1507 0-22	ASV51 0-40	BY100 1-25	0A85 0-12	OC721 0-20	
2N1526 0-22	ASV53 0-20	BY126 0-15	0A86 0-15	ORP12 0-50	
2N1909 2-25	ASV55 0-20	BY127 0-17	0A90 0-25	ORP60 0-40	
2N2147 0-75	ASV62 0-25	BY182 0-25	0A95 0-25	ORP61 0-42	
2N2148 0-60	ASV86 0-25	BY210 0-25	0A96 0-25	ORP62 0-25	
2N2160 0-40	ASZ21 0-25	BYZ13 0-25	0A200 0-07	SAC40 0-25	
2N2218 0-20	ASZ23 0-75	BYZ15 0-25	0A202 0-10	SFT308 0-25	
2N2219 0-20	AUY10 0-25	BYZ16 0-25	0A202 0-10	ST722 0-25	
2N2287 1-08	AU101 1-00	BYZ17 0-10	0A210 0-25	ST723 0-25	
2N2297 0-20	BC107 0-10	BYZ18 0-10	0A211 0-20	SX68 0-20	
2N2369A 0-15	BC108 0-10	BYZ19 0-10	0A2200 0-55	SX681 0-20	
2N2444 1-22	BC109 0-10	BYZ20 0-25	0A201 0-20	SX685 0-40	
2N2413 0-22	BC113 0-25	BYZ21 0-25	0A2202 0-42	SX640 0-50	
2N2646 0-45	BC115 0-20	BYZ16 0-62	0A2203 0-42	SX641 0-55	
2N2712 0-25	BC116 0-25	BYZ88C3V3 0-20	0A2204 0-20	SX642 0-60	
2N2784 0-50	BC116A 0-20	C111 0-15	0A2205 0-42	SX644 0-75	
2N2846 0-75	BC118 0-25	CR81/05 0-25	0A2207 0-47	V15/30P 0-50	
2N2848 0-42	BC121 0-20	CR81/40 0-47	0A2208 0-32	V30/201P 0-75	
2N2849 0-25	BC125 0-42	CS4B 0-50	0A2209 0-22	V60/201P 0-50	
2N2906 0-20	BC126 0-65	DD000 0-15	0A2210 0-32	XA101 0-10	
2N2907 0-23	BC140 0-55	DD003 0-15	0A2212 0-45	XA102 0-15	
2N2924 0-22	BC147 0-15	DD008 0-25	0A2222 0-45	XA151 0-15	
2N2925 0-15	BC148 0-11	DD008 0-25	0A2224 0-45	XA152 0-15	
2N2926 0-10	BC149 0-11	GD3 0-25	0A2241 0-22	XA161 0-25	
2N3054 0-50	BC157 0-15	GD4 0-05	0A2242 0-22	XA162 0-25	
2N3055 0-75	BC158 0-12	G5 0-25	0A2244 0-22	XB101 0-43	
2N3702 0-10	BC160 0-63	GD8 0-25	0A2290 0-22	XB102 0-10	
2N3705 0-10	BC169 0-13	GD8 0-05	0A2290 0-22	XB103 0-25	
2N3706 0-22	BCY31 0-35	GD12 0-05	OC16T 0-25	XB113 0-12	
2N3707 0-12	BCY32 0-55	GET102 0-20	OC19 0-27	XB121 0-43	
2N3709 0-10	BCY33 0-25	GET103 0-22	OC20 0-25	ZR24 0-25	
2N3711 0-12	BCY34 0-30	GET113 0-15	OC22 0-20	Z8170 0-10	
2N3819 0-25	BCY38 0-40	GET114 0-15	OC23 0-20	Z8271 0-18	
2N3820 0-20	BCY39 1-00	GET115 0-45	OC25 0-27	ZT21 0-25	
2N3823 0-75	BCY40 0-50	GET116 0-50	OC26 0-25	ZT43 0-25	
2N5027 0-52	BCY42 0-25	GET120 0-25	OC28 0-22	ZTX107 0-15	
2N5088 0-25	BCY70 0-15	GET122 0-25	OC29 0-20	ZTX108 0-15	
28005 1-00	BCY71 0-20	GET872 0-30	OC30 0-40	ZTX300 0-12	
28178 0-40	BCZ10 0-35	GET875 0-25	OC35 0-50	ZTX304 0-25	
28901 0-50	BCZ11 0-50	GET880 0-37	OC38 0-20	ZTX500 0-16	
28904 0-75	BD121 0-05	GET881 0-25	OC41 0-25	ZTX503 0-17	
28501 0-27	BD123 0-20	GET882 0-25	OC42 0-20	ZTX531 0-25	
28703 0-22	BD124 0-75	GET885 0-25			
AA129 0-20	BFY11 1-22	GEX44 0-25			
AAZ12 0-20	BF115 0-25	GEX45/1 0-10			
AAZ13 0-12	BF117 0-50	GEX941 0-15			
AC107 0-27	BF167 0-25	GJ3M 0-25			

SEMI-CONDUCTOR SET FOR P. E. GEMINI AMPLIFIER £13.95

SEND S.A.E. FOR LIST OF 8,000 TYPES VALVES, TUBES AND TRANSISTORS

Open daily to callers: Mon.-Sat. 9 a.m.-5 p.m.
 Closed Sat. 1.30 p.m.-2.30 p.m.

Terms C.W.O. only | Tel. 01-769 099/1649

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

TYPE SW. 100 100 x 80 mm		TYPE S-80 80 mm square fronts	
500μA	23-35	50μA	23-20
1mA	23-10	50-0-50μA	23-10
20V d.c.	23-10	100μA	22-75
50V d.c.	23-10	100-0-100μA	23-10
300V d.c.	23-10	500μA	23-00
1A d.c.	23-10	1mA	22-80
5A d.c.	23-10	5A d.c.	22-80
300V a.c.	23-10	50V d.c.	22-80
VI Meter	23-75	300V d.c.	22-80
		VI Meter	23-87

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in. fronts.

50μA	23-60	50-0-50μA	23-10	100μA	23-00	200μA	23-00	500-0-500μA	23-80	1mA	22-80	1-0-1mA	22-80	5mA	22-80	10mA	22-80												
500μA	22-80	1A	22-80	5A	22-80	15A	22-80	30A	22-80	300V d.c.	22-80	50V d.c.	22-80	150V d.c.	22-80	300V d.c.	22-80	8 Meter	22-87	1mA	22-87	5A a.c.*	22-80	10A a.c.*	22-80	20A a.c.*	22-80	30A a.c.*	22-80

Type MR.88P. 1 21/32in. square fronts.

100μA	21-60	300μA	21-60	500μA	21-60	1A	21-60	5A	21-60	15A	21-60	30A	21-60	100μA	21-60	1mA	21-60	5mA	21-60	10mA	21-60	50μA	22-10	50-0-50μA	21-90	100μA	21-90	200μA	21-75	500μA	21-65	1mA	21-60	1-0-1mA	21-70	2mA	21-60	10mA	21-60	20mA	21-60	50mA	21-60	100mA	21-60	50μA	22-25	50-0-50μA	22-10	100μA	21-87	200μA	21-75	500μA	21-70	1mA	21-70	1-0-1mA	21-70	2mA	21-70	10mA	21-70	20mA	21-70	50mA	21-70	100mA	21-70	50μA	22-25	50-0-50μA	22-10	100μA	21-87	200μA	21-75	500μA	21-70	1mA	21-70	1-0-1mA	21-70	2mA	21-70	10mA	21-70	20mA	21-70	50mA	21-70	100mA	21-70
-------	-------	-------	-------	-------	-------	----	-------	----	-------	-----	-------	-----	-------	-------	-------	-----	-------	-----	-------	------	-------	------	-------	-----------	-------	-------	-------	-------	-------	-------	-------	-----	-------	---------	-------	-----	-------	------	-------	------	-------	------	-------	-------	-------	------	-------	-----------	-------	-------	-------	-------	-------	-------	-------	-----	-------	---------	-------	-----	-------	------	-------	------	-------	------	-------	-------	-------	------	-------	-----------	-------	-------	-------	-------	-------	-------	-------	-----	-------	---------	-------	-----	-------	------	-------	------	-------	------	-------	-------	-------

"SEW" BAKELITE PANEL METERS

Type MR.85 3 1/2in. square fronts.

50μA	23-37	50-0-50μA	22-75	100μA	22-75	200μA	22-85	500μA	22-40	1mA	22-20	5A	22-20	10A	22-20	15A	22-20	20A	22-20	30A	22-20	50A	22-20	5V d.c.	22-20	10V d.c.	22-20	20V d.c.	22-20	50V d.c.	22-20	150V d.c.	22-20	300V d.c.	22-20	500μA	22-20	1mA	22-37	5A a.c.*	22-20	100mA a.c.*	22-20	200mA a.c.*	22-20	500mA a.c.*	22-20	1A a.c.*	22-20	5A a.c.*	22-20	10A a.c.*	22-20	20A a.c.*	22-20	30A a.c.*	22-20
------	-------	-----------	-------	-------	-------	-------	-------	-------	-------	-----	-------	----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	---------	-------	----------	-------	----------	-------	----------	-------	-----------	-------	-----------	-------	-------	-------	-----	-------	----------	-------	-------------	-------	-------------	-------	-------------	-------	----------	-------	----------	-------	-----------	-------	-----------	-------	-----------	-------

*** MOVING IRON — ALL OTHERS MOVING COIL**
 Please add postage

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 105mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. The easily accessible coil movement is demonstrate internal in the following ranges:

50μA	25-00	20V d.c.	24-40
100μA	24-65	50V d.c.	24-40
1mA	24-40	300V d.c.	24-40
50-0-50μA	24-65	300V d.c.	24-40
1-0-1mA	24-40	Dual range	
1A d.c.	24-40	500mA/5A d.c.	24-65
5A d.c.	24-40	5V/50V d.c.	24-65
10V d.c.	24-40		

MULTIMETERS for EVERY purpose!

ROUND SCALE TYPE PENCIL TESTER MODEL TS.68

Completely portable, simple to use pocket sized tester. Ranges: 0/3 30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY £1-97 P. & P. 13p.

MODEL TE-90. 50,000 O.P.V. Mirror scale, overload protection.

0.03/0.3/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY £1-97 P. & P. 13p.

SKYWOND SW-500

50 KΩ/Volt. Mirror scale. 100 Volts DC. 0.5/5/12/30/300/600V AC. 50/500/1,200V d.c. 0/60/300/600/1,200V a.c. 1/0.2/0.6/60/600mA. d.c. 0/0.6/1/60K/1-6/16 meg. -20 to +63dB. £7-50. P. & P. 15p.

370 WTR MULTIMETER

Features AC current ranges. 20,000 o.p.v. 0/5/2-5/10/50/250/500/1000V DC. 0/2-5/10/50/250/500/1000V AC. 0/50μA/1/10/100mA/1/10 Amp DC. 0/100mA/1/10 Amp AC. 0/5K/50K/500K/5MEG/50MΩ. -20 +63dB. £15. P. & P. 25p.

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and ICQ, *npn* or *ppn*. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £6-97. P. & P. 15p.

AG76 AUDIO GENERATOR

Portable, mains operated. Sine wave 20 to 200,000 Hz. Square wave 20 to 30,000 Hz. Output voltage Sine 17V P/P. Square 21V P/P. Distortion less than 1%. £17-50. P. & P. 35p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120Kc/s-500Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 37p. Size 140 x 215 x 170 mm.

BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine Hz to 100KHz. Square 20Hz to 20KHz. Output max. +10dB (10KΩ). Operation 220/240V a.c. Size 215mm x 150mm x 120mm. Price £27-50. Carr. 25p.

240° WIDE ANGLE 1mA METERS

MW1-6 60mm square £3-97. MW1-8 80mm square £4-97. P. & P. extra.

TRANSISTORISED L.C.R. AC MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Range: R. 1Ω-11.1 megΩ ±1%. L. 1μH - 1 H. C. 10pF - 100μF. 6 Ranges -2%. C. 10pF - 111.0 mF d.c. 6 Ranges -2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Metric indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2 in. £20. P. & P. 25p.

UM.049 MULTIMETER

20,000 O.P.V. overload protection. 0/3/30/60/300/600/3000 V AC. 0/6/30/300/600V AC. 0/60/600/1200/2400 V AC. 0/60/60/600/6000 MA. DC. 0/0.0K/0.0K/10K. -20 to +63dB. £4-50. P. & P. 15p.

MODEL 1092 Testmeter

5,000 O.P.V. 0/3/15/30/300/1200V d.c. 0/6/30/300/600V AC. 0/300μA/300 MA. 0/10K/1 megΩ. Decibels -10 to +16dB. £2-75 each + 15p P. & P.

TKM MODEL TW-50K 46 ranges, mirror scale, 50K/10V DC.

5K/Volt AT. DC: 0/2.5/5/10/25/50/100/250/500/1000V AC. Volts: 1-5, 3, 5, 10, 25, 50, 100, 250, 500, 1000V. D.C. Current: 25, 50μA, 2.5, 5, 10, 25, 50, 100mA, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEGΩ. Decibels: -20 to +63dB. £3-85. P. & P. 17p.

HT100B4 MULTIMETER

Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection. 0/2-5/10/50/250/500/1000V DC. 0/2-5/10/50/250/1000V AC. 0/10/250μA/2-5/250MA/10 Amp D.C. 10 Amp A.C. 0/20K/20MEG/20MEGΩ. -20 +63dB. £12-50. P. & P. 25p.

RUSSIAN 22 RANGE MULTIMETER

U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V d.c., 2-5/10/50/250/500/1000V a.c. D.c. current 100μA/1/10/100mA/A. Resistance 20/30/300/300K/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £5-97. P. & P. 25p.

TO-3 PORTABLE OSCILLOSCOPE

3in tube. Y amp. Sensitivity 0.1V p-p/CM. Bandwidth 1.5 cps-1.5MHz. Input imp. 2 megΩ 25pF. X amp. sensitivity 0.9V/800KHz. Input imp. 2 megΩ 20pF. Time base, 5 ranges 10cp-300KHz. Synchronisation. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15lb 220/240V a.c. Supplied brand new with handbook. £37-50. Carr. 50p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt d.c. but can be used to measure a wide range of a.c. and d.c. volt, current and ohms with optional plug-in cards. Specification: Accuracy: ±0.2, ±1 digit. Resolution: 1mV. No. of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic Zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V d.c. Input: Fully floating (3 poles). Input power: 110-230V. 50/60 cycles. Overall size: 2 1/2 in. x 2 1/2 in. x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. £49-97 Carr. 50p

G. W. SMITH & CO (RADIO) LTD.
 Also see next two pages

HI-FI EQUIPMENT

SAVE UP TO 33 1/2% OR MORE

SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!

RECORD DECKS

B.S.R. Mini Mono:	£4.97	
G129:	£6.70	
MP60:	£10.75	
810:	£14.65	A176
310:	£11.85	SL72B
810:	£9.65	SL75B
810:	£24.47	SL95B
MP60 TP14:	£17.65	401
MP60 TP12:	£15.85	401
610 T.P.D.I.:	£20.97	ZERO 100A
510 T.P.D.I.:	£18.75	ZERO 100S
210 Package:	£9.85	GOLDRING
H.T. 70:	£15.55	GL69D
H.T. 70 Package:	£22.50	GL72
		GL72D
		GL75
		GL75D
		GL75E
		GL75F
		GL75G
		GL75H
		GL75I
		GL75J
		GL75K
		GL75L
		GL75M
		GL75N
		GL75O
		GL75P
		GL75Q
		GL75R
		GL75S
		GL75T
		GL75U
		GL75V
		GL75W
		GL75X
		GL75Y
		GL75Z
		GL75AA
		GL75AB
		GL75AC
		GL75AD
		GL75AE
		GL75AF
		GL75AG
		GL75AH
		GL75AI
		GL75AJ
		GL75AK
		GL75AL
		GL75AM
		GL75AN
		GL75AO
		GL75AP
		GL75AQ
		GL75AR
		GL75AS
		GL75AT
		GL75AU
		GL75AV
		GL75AW
		GL75AX
		GL75AY
		GL75AZ
		GL75BA
		GL75BB
		GL75BC
		GL75BD
		GL75BE
		GL75BF
		GL75BG
		GL75BH
		GL75BI
		GL75BJ
		GL75BK
		GL75BL
		GL75BM
		GL75BN
		GL75BO
		GL75BP
		GL75BQ
		GL75BR
		GL75BS
		GL75BT
		GL75BU
		GL75BV
		GL75BW
		GL75BX
		GL75BY
		GL75BZ
		GL75CA
		GL75CB
		GL75CC
		GL75CD
		GL75CE
		GL75CF
		GL75CG
		GL75CH
		GL75CI
		GL75CJ
		GL75CK
		GL75CL
		GL75CM
		GL75CN
		GL75CO
		GL75CP
		GL75CQ
		GL75CR
		GL75CS
		GL75CT
		GL75CU
		GL75CV
		GL75CW
		GL75CX
		GL75CY
		GL75CZ
		GL75DA
		GL75DB
		GL75DC
		GL75DD
		GL75DE
		GL75DF
		GL75DG
		GL75DH
		GL75DI
		GL75DJ
		GL75DK
		GL75DL
		GL75DM
		GL75DN
		GL75DO
		GL75DP
		GL75DQ
		GL75DR
		GL75DS
		GL75DT
		GL75DU
		GL75DV
		GL75DW
		GL75DX
		GL75DY
		GL75DZ
		GL75EA
		GL75EB
		GL75EC
		GL75ED
		GL75EE
		GL75EF
		GL75EG
		GL75EH
		GL75EI
		GL75EJ
		GL75EK
		GL75EL
		GL75EM
		GL75EN
		GL75EO
		GL75EP
		GL75EQ
		GL75ER
		GL75ES
		GL75ET
		GL75EU
		GL75EV
		GL75EW
		GL75EX
		GL75EY
		GL75EZ
		GL75FA
		GL75FB
		GL75FC
		GL75FD
		GL75FE
		GL75FF
		GL75FG
		GL75FH
		GL75FI
		GL75FJ
		GL75FK
		GL75FL
		GL75FM
		GL75FN
		GL75FO
		GL75FP
		GL75FQ
		GL75FR
		GL75FS
		GL75FT
		GL75FU
		GL75FV
		GL75FW
		GL75FX
		GL75FY
		GL75FZ
		GL75GA
		GL75GB
		GL75GC
		GL75GD
		GL75GE
		GL75GF
		GL75GG
		GL75GH
		GL75GI
		GL75GJ
		GL75GK
		GL75GL
		GL75GM
		GL75GN
		GL75GO
		GL75GP
		GL75GQ
		GL75GR
		GL75GS
		GL75GT
		GL75GU
		GL75GV
		GL75GW
		GL75GX
		GL75GY
		GL75GZ
		GL75HA
		GL75HB
		GL75HC
		GL75HD
		GL75HE
		GL75HF
		GL75HG
		GL75HH
		GL75HI
		GL75HJ
		GL75HK
		GL75HL
		GL75HM
		GL75HN
		GL75HO
		GL75HP
		GL75HQ
		GL75HR
		GL75HS
		GL75HT
		GL75HU
		GL75HV
		GL75HW
		GL75HX
		GL75HY
		GL75HZ
		GL75IA
		GL75IB
		GL75IC
		GL75ID
		GL75IE
		GL75IF
		GL75IG
		GL75IH
		GL75II
		GL75IJ
		GL75IK
		GL75IL
		GL75IM
		GL75IN
		GL75IO
		GL75IP
		GL75IQ
		GL75IR
		GL75IS
		GL75IT
		GL75IU
		GL75IV
		GL75IW
		GL75IX
		GL75IY
		GL75IZ
		GL75JA
		GL75JB
		GL75JC
		GL75JD
		GL75JE
		GL75JF
		GL75JG
		GL75JH
		GL75JI
		GL75JJ
		GL75JK
		GL75JL
		GL75JM
		GL75JN
		GL75JO
		GL75JP
		GL75JQ
		GL75JR
		GL75JS
		GL75JT
		GL75JU
		GL75JV
		GL75JW
		GL75JX
		GL75JY
		GL75JZ
		GL75KA
		GL75KB
		GL75KC
		GL75KD
		GL75KE
		GL75KF
		GL75KG
		GL75KH
		GL75KI
		GL75KJ
		GL75KK
		GL75KL
		GL75KM
		GL75KN
		GL75KO
		GL75KP
		GL75KQ
		GL75KR
		GL75KS
		GL75KT
		GL75KU
		GL75KV
		GL75KW
		GL75KX
		GL75KY
		GL75KZ
		GL75LA
		GL75LB
		GL75LC
		GL75LD
		GL75LE
		GL75LF
		GL75LG
		GL75LH
		GL75LI
		GL75LJ
		GL75LK
		GL75LL
		GL75LM
		GL75LN
		GL75LO
		GL75LP
		GL75LQ
		GL75LR
		GL75LS
		GL75LT
		GL75LU
		GL75LV
		GL75LW
		GL75LX
		GL75LY
		GL75LZ
		GL75MA
		GL75MB
		GL75MC
		GL75MD
		GL75ME
		GL75MF
		GL75MG
		GL75MH
		GL75MI
		GL75MJ
		GL75MK
		GL75ML
		GL75MN
		GL75MO
		GL75MP
		GL75MQ
		GL75MR
		GL75MS
		GL75MT
		GL75MU
		GL75MV
		GL75MW
		GL75MX
		GL75MY
		GL75MZ
		GL75NA
		GL75NB
		GL75NC
		GL75ND
		GL75NE
		GL75NF
		GL75NG
		GL75NH
		GL75NI
		GL75NJ
		GL75NK
		GL75NL
		GL75NM
		GL75NN
		GL75NO
		GL75NP
		GL75NQ
		GL75NR
		GL75NS
		GL75NT
		GL75NU
		GL75NV
		GL75NW
		GL75NX
		GL75NY
		GL75NZ
		GL75OA
		GL75OB
		GL75OC
		GL75OD
		GL75OE
		GL75OF
		GL75OG
		GL75OH
		GL75OI
		GL75OJ
		GL75OK
		GL75OL
		GL75OM
		GL75ON
		GL75OO
		GL75OP
		GL75OQ
		GL75OR
		GL75OS
		GL75OT
		GL75OU
		GL75OV
		GL75OW
		GL75OX
		GL75OY
		GL75OZ
		GL75PA
		GL75PB
		GL75PC
		GL75PD
		GL75PE
		GL75PF
		GL75PG
		GL75PH
		GL75PI
		GL75PJ
		GL75PK
		GL75PL
		GL75PM
		GL75PN
		GL75PO
		GL75PP
		GL75PQ

SOUND 72

International

BLOOMSBURY CENTRE HOTEL, CORAM STREET, RUSSELL SQUARE, LONDON, W.C.1.
14th-16th MARCH 1972 ● 1000—1800hrs. DAILY (FINAL DAY 1000—1600hrs.)

Sponsored by
The Association of Public Address
Engineers


6 Conduit Street
London W1R 9TG
Telephone 01-493 5256

Tickets available to members (free of
charge) from above address.

Non-members admitted by purchase of
catalogue, price 15p, at door.

PUBLIC ADDRESS AND ALLIED EQUIPMENT

BLACK LIGHT

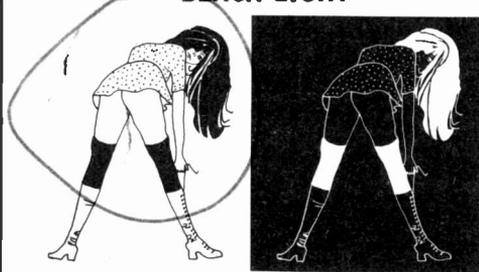

THE OUT OF SIGHT LIGHT



This kit consists of a high-pressure mercury discharge lamp enclosed in a deep blue-violet outer bulb. This absorbs all visible light given by the discharge but transmits the long-wave ultra-violet rays.

The unit performs in a similar fashion to the fluorescent tube type units in use in some discotheques but instead uses a 3-pin B.C. lamp fitted into a high intensity spot-fitting, with fully adjustable swivel bearing. The reflector is also fully adjustable and the unit may be mounted in any position and focused as desired.

White shirts and dresses glow "Whiter than white". Paint scenes on walls, etc., with our special fluorescent paint, focus the black-light from across the room and switch-on. The pictures glow brilliantly as if by magic!

Full kit includes lamp, reflector, control-gear, generous samples of five different colours of fluorescent paint and full instructions. Price £25 carr. paid. S.A.E. with all inquiries.

PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required. Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7½in x 4½in x 2in approx. Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P. S.A.E. with all enquiries.

PSYCHEDELIC LIGHTING UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid. S.A.E. with all inquiries.

DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET, WALSALL, STAFFS WS1 1UZ
WALSALL 34365
MAIL ORDER ONLY

DISCOUNTS UP TO

60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

AKAI · LEAK · SINCLAIR · TELETON · ARMSTRONG · ROTEL
THORENS · PHILIPS · GOLDRING · ROGERS · PIONEER

SPECIAL OFFER £18

Garrard SP25 Mk. III
Goldring G800H
Teak plinth and tinted cover.
Ready wired for immediate use.
Please add £1.25 for post and packing.

TURNTABLES

Please add 50p for P. & P.
*GARRARD 1025T with cartridge £5.97

Garrard 5P25 Mk. III	£10.95
Garrard 2025TC with Sonotone 9TAHC	£9.20
Garrard Zero 100-Auto (New Product)	£41.25
Garrard Zero 100-Single Play (New Product)	£38.25
Garrard SL65B	£13.95
Garrard AP76	£20.25
Garrard 401	£27.95
BSR MP60	£10.00
Pioneer PL12AC	£26.00
Thorens TD125	£62.50
Thorens 150ABII	£42.50
Goldring GL72/2	£21.75
Goldring GL72/P2	£27.20
Goldring GL75	£27.95
Goldring GL75 P	£35.95

AMPLIFIERS

Please add 50p for P. & P.

Alpha Highgate FA400	£33.00
Armstrong 521 (cased)	£44.50
Amstrad 8000 Mk. II	£16.95
Amstrad IC2000	£29.95
Leak 30 Delta Range (New Prod.)	£51.00
Leak 70 Delta Range (New Prod.)	£61.00
Metrosound ST20E	£26.00
Philips R580	£18.00
Pioneer SA600	P/A
Pioneer SA700	£65.00
Pioneer SA900	£92.00
Rogers R/brook Chassis	£35.50
Rogers R/brook Cased	£39.50
Rogers R/bourne Chassis	£44.00
Rogers R/bourne Cased	£48.50
Sansui AU101	£32.00
Tripletone 800 Amp Series 3	£28.50
Europhon 10 + 10	£16.95
Goldring Lenco 15 watts	£32.95

All prices correct at time of going to press

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE7) 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.
MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card)
2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

Rotel RA 301	£32.75
Rotel RA 601	£49.80
Sinclair 2000 Mk. II	£21.50
Sinclair 3000	£29.75
Sinclair PRO 60/2 + Z30 PZ5	£15.75
Sinclair PRO 60/2 + Z30 PZ6	£17.75
Sinclair PRO 60/2 + Z50	£37.95
PZ8/Trans	£22.95
Sinclair AFU	£4.70
Sinclair 605 (New Product)	£20.50
Goodmans Max. Amp.	£37.95
Teleton 5AQ206B (New Prod.)	£17.95
Wharfedale	£42.25
Sinclair IC12 integrated circuit amplifier	£1.85
Eagle TSA149 7w RMS	£24.95
Eagle TSA151 15w RMS	£34.50

CARTRIDGES

Please add 10p for P. & P.

Goldring GB50	£3.65
Goldring GB80	£6.25
Goldring GB800E	£10.50
Goldring GB800SE	£15.50
Sonotone 9TAHC Diamond	£1.45
Shure M3DM	£4.50
Shure M44E	£7.25
Shure M445/7C	£7.00
Shure M55E	£8.75
Shure M75E	£12.45
Shure V15 Type 2	£27.75
Shure M44E	£7.25
Shure M31E	£8.50
Shure M32E	£8.00
*Audio Technica AT35	£6.95
*Audio Technica AT66	£4.95
*GCS 36	95p

PLINTHS & COVERS



(as illustrated)
Plus 35p post and packing. Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25, 2025TC, 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR McDonald MP60 and others.

For AP76; AP75; SL72B; SL75; SL95B; £4.20 plus 55p P. & P. Also finished in walnut to match Japanese equipment—at no extra charge.

*£3.20

TRANSFORMERS

MAINS ISOLATING SERIES
PRIMARY 200/250V. SEC. 240V. C.T. 120V. & EARTH SHIELDED

ALSO AVAILABLE WITH 115/120V. SEC. WINDINGS.

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	£	P & P
07	20	1 11	7 x 6 x 6.5	1.40	70
61	100	5 12	10.2 x 8.9 x 8.3	2.28	52
62	250	12 4	9.5 x 12.7 x 11.4	5.05	67
63	500	27 0	17.1 x 11.4 x 15.9	9.74	**
92	1000	40 0	17.8 x 17.1 x 21.6	17.94	**
128	2000	63 0	24.1 x 21.6 x 15.2	29.66	**
129	3000	84 0	21.6 x 21.6 x 20.3	46.38	**
190	6000	178 0	31.1 x 35.6 x 17.1	76.11	**

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	£	P & P
113	20	1 11	7.3 x 4.3 x 4.4	0-115-210-240	0.74	20
64	75	1 14	7.0 x 6.4 x 6.0	0-115-210-240	1.44	30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	1.74	36
66	300	6 0	10.2 x 10.2 x 9.5	" " "	3.38	52
67	500	12 8	14.0 x 10.2 x 11.4	" " "	5.03	67
84	1000	16 0	14.4 x 14.0 x 14.0	" " "	9.12	82
93	1500	28 9	13.5 x 14.9 x 16.5	" " "	13.22	**
95	2000	40 0	17.8 x 16.5 x 21.6	" " "	17.26	**
73	3000	45 8	17.4 x 18.1 x 21.3	" " "	23.47	**

TOTALLY ENCLOSED 115V AUTO TRANSFORMER
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £6.85, P & P 67p.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 200-500 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	£	P & P
111	0.5 0.25	12	7.6 x 5.7 x 4.4	0-12V at 0.25A x 2	0.74	22
213	1.0 0.5	1 0	8.3 x 5.1 x 5.1	0-12V at 0.5A x 2	0.88	22
71	2 1	0 0	7.0 x 6.4 x 5.7	0-12V at 1A x 2	1.62	22
18	4 2	2 4	7.0 x 7.0 x 7.0	0-12V at 2A x 2	1.62	26
70	6 3	3 12	10.2 x 7.6 x 8.6	0-12V at 3A x 2	1.95	42
72	10 5	6 3	7.9 x 10.8 x 10.2	0-12V at 5A x 2	1.54	52
17	16 8	7 8	12.1 x 9.5 x 10.2	0-12V at 8A x 2	3.95	52
115	20 10	11 13	12.1 x 14.4 x 10.2	0-12V at 10A x 2	5.03	67
187	30 15	16 12	13.3 x 11.1 x 12.1	0-12V at 15A x 2	9.28	82
226	60 30	34 0	17.0 x 14.5 x 12.5	0-12V at 30A x 2	17.05	**

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
112	0.5	1 4	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	0.88	12
79	1.0	2 0	7.0 x 6.4 x 6.0	" " "	1.18	36
3	2.0	3 2	8.9 x 7.0 x 7.6	" " "	1.75	36
20	3.0	4 6	10.2 x 8.9 x 8.6	" " "	2.76	42
21	4.0	6 0	10.2 x 10.0 x 8.6	" " "	2.56	52
51	5.0	6 8	12.1 x 10.0 x 8.6	" " "	3.18	52
117	6.0	7 8	12.1 x 10.0 x 10.2	" " "	3.79	52
89	10.0	12 2	14.0 x 10.2 x 11.4	" " "	6.21	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
102	0.5	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1.16	30
103	1.0	2 10	8.3 x 7.3 x 7.0	" " "	1.62	36
104	2.0	5 0	10.2 x 8.9 x 8.6	" " "	1.95	42
105	3.0	6 0	10.2 x 10.2 x 8.3	" " "	3.18	52
106	4.0	9 4	12.1 x 11.4 x 10.2	" " "	4.20	52
107	6.0	12 4	12.1 x 11.1 x 13.3	" " "	6.21	67
118	8.0	18 9	13.3 x 13.3 x 12.1	" " "	8.10	97
119	10.0	19 12	16.5 x 14.5 x 15.9	" " "	10.13	97

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
124	0.5	2 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1.18	36
126	1.0	3 0	8.9 x 7.6 x 7.6	" " "	1.64	36
127	2.0	5 6	10.2 x 8.9 x 8.6	" " "	2.56	42
125	3.0	8 8	11.9 x 9.5 x 10.0	" " "	3.90	52
123	4.0	10 6	11.4 x 9.5 x 11.4	" " "	5.03	67
120	6.0	16 12	13.3 x 12.1 x 12.1	" " "	7.28	82
122	10.0	23 2	16.5 x 12.7 x 16.5	" " "	12.05	**

*Carriage via B.R.S.

LEAD AC BATTERY CHARGER TYPES
PRIMARY 200-250 VOLT FOR CHARGING 6 OR 12 VOLT BATTERIES

Ref. No.	Amps.	Weight lb oz	Size cm.	£	P & P
45	1.5	1 9	7.0 x 6.0 x 6.0	1.17	10
5	4.0	3 11	10.2 x 7.0 x 8.3	1.77	12
86	6.0	5 12	10.2 x 8.9 x 8.3	2.67	52
146	8.0	6 4	8.9 x 10.2 x 10.2	3.04	52
50	12.5	11 14	13.3 x 10.8 x 12.1	4.52	67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

TRANSISTORS
TO MANUFACTURERS FULL SPECIFICATIONS

BC107/108/109 9p each	2N 3055 68p each with mica and bushes	AD 161/162 60p pair with mica and bushes
100 + 7p	25 + 60p	25 + 55p
500 + 9p	100 + 45p	100 + 50p
Minimum order 10 pieces this range.	500 + 40p	500 + 45p
		1000 + 40p

★ Quantity prices on application
Also stocked: SEMICONDUCTORS · VALVES
MULTIMETERS · MAINS KEYNECTOR
ELECTROSIL METAL OXIDE RESISTORS

BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY
LONDON W2 4AH Tel: 01-229 6681/2
NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS AND AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. Switched earpiece socket complete with earpiece. 10 transistors plus 3 diodes. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser with VHF section. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS

£8.50

P.P. & INS. 50p
(OVERSEAS P. & P. £1)



ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.98** P.P. & INS. 41p (OVERSEAS P. & P. £1)


ROAMER SEVEN Mk. IV



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

TOTAL BUILDING COSTS **£5.98** P.P. & INS. 41p (OVERSEAS P. & P. £1)


ROAMER SIX

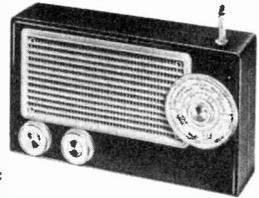

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£3.98** P.P. & INS. 26p (OVERSEAS P. & P. £1)


POCKET FIVE

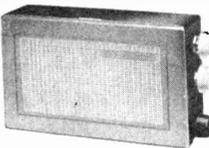

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes. Sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 3 1/2in x 1 1/2in x 3/4in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£2.23** P.P. & INS. 21p (OVERSEAS P. & P. 63p)

TRANSONA FIVE

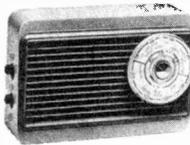


NOW WITH 3in SPEAKER

3 TUNABLE WAVEBANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone 3in moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£2.50** P.P. & INS. 22p (OVERSEAS P. & P. 63p)

TRANS EIGHT

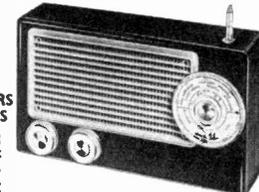

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£4.48** P.P. & INS. 31p (OVERSEAS P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4" x 2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/4in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

ALL PARTS INCLUDING CASE AND PLANS **£5.50** P.P. & INS. 31p (OVERSEAS P. & P. £1)

FULL AFTER SALES SERVICE

★ Callers side entrance Barratts Shoe Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday

RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN ROAMER SEVEN
ROAMER EIGHT TRANS EIGHT
TRANSONA FIVE ROAMER SIX
POCKET FIVE EDU-KIT

Parts price list and plans for **TRANS EIGHT**

Name

Address

P.E. 39

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

CAPACITORS

2.2pF	500V	S/M	71p	0.0027μF	500V	S/M	15p
3.3pF	500V	S/M	71p	0.0033μF	500V	Cer.	5p
5pF	500V	S/M	71p	0.0033μF	500V	P.S.	6p
10pF	125V	P.S.	71p	0.0033μF	1,000V	MDC	6p
15pF	125V	P.S.	5p	0.0036μF	500V	S/M	15p
15pF	500V	Cer.	71p	0.0047μF	125V	P.S.	9p
18pF	500V	S/M	5p	0.0047μF	500V	Poly.	6p
22pF	125V	P.S.	4p	0.0047μF	500V	S/M	20p
22pF	500V	S/M	71p	0.0051μF	1,000V	MDC	6p
25pF	500V	S/M	71p	0.0051μF	100V	Mylar	3p
27pF	500V	Cer.	4p	0.0068μF	500V	Cer.	3p
33pF	125V	P.S.	5p	0.0068μF	500V	S/M	30p
33pF	500V	S/M	71p	0.0068μF	500V	Poly.	6p
39pF	500V	S/M	71p	0.0082μF	125V	P.S.	10p
47pF	125V	P.S.	71p	0.0082μF	500V	Poly.	4p
47pF	500V	Cer.	4p	0.01μF	125V	P.S.	10p
50pF	500V	S/M	71p	0.01μF	160V	Poly.	4p
56pF	500V	S/M	71p	0.01μF	250V	M.F.	3p
68pF	125V	P.S.	5p	0.01μF	400V	Poly.	3p
68pF	500V	S/M	71p	0.01μF	500V	Cer.	5p
39pF	500V	S/M	71p	0.01μF	500V	S/M	30p
39pF	500V	S/M	71p	0.01μF	500V	Paper	6p
100pF	125V	P.S.	5p	0.01μF	1,000V	MDC	9p
100pF	500V	S/M	71p	0.015μF	160V	Poly.	3p
100pF	500V	Cer.	5p	0.015μF	400V	Poly.	3p
120pF	500V	S/M	71p	0.02μF	100V	Mylar	3p
150pF	125V	P.S.	5p	0.022μF	18V	Disc	5p
150pF	500V	S/M	71p	0.022μF	250V	M.F.	3p
150pF	500V	Cer.	71p	0.022μF	400V	Poly.	3p
180pF	500V	S/M	71p	0.022μF	600V	MDC	71p
200pF	500V	S/M	71p	0.022μF	1,000V	MDC	9p
220pF	125V	P.S.	5p	0.033μF	250V	M.F.	4p
220pF	500V	Cer.	5p	0.033μF	400V	Poly.	4p
250pF	500V	S/M	8p	0.047μF	12V	Disc	6p
270pF	500V	Cer.	5p	0.047μF	160V	Poly.	3p
300pF	500V	S/M	8p	0.047μF	250V	M.F.	3p
330pF	125V	P.S.	5p	0.047μF	400V	Poly.	4p
330pF	500V	S/M	8p	0.047μF	500V	Paper	8p
390pF	500V	S/M	8p	0.047μF	1,000V	MDC	10p
470pF	125V	P.S.	5p	0.1μF	30V	Disc	6p
470pF	750V	Disc	5p	0.1μF	250V	M.F.	4p
500pF	500V	S/M	8p	0.1μF	400V	Poly.	5p
560pF	500V	S/M	8p	0.1μF	600V	MDC	10p
680pF	125V	P.S.	6p	0.1μF	1,000V	MDC	13p
680pF	500V	S/M	8p	0.15μF	250V	M.F.	5p
820pF	500V	S/M	8p	0.22μF	160V	Poly.	6p
0.001μF	100V	Mylar	3p	0.22μF	250V	M.F.	10p
0.001μF	125V	P.S.	6p	0.22μF	400V	Foil	10p
0.001μF	400V	Cer.	3p	0.22μF	1,000V	MDC	15p
0.001μF	500V	S/M	10p	0.33μF	250V	M.F.	8p
0.001μF	500V	Cer.	5p	0.47μF	250V	M.F.	8p
0.001μF	1,000V	MDC	6p	0.47μF	400V	Foil	15p
0.0015μF	400V	Poly.	3p	0.47μF	1,000V	MDC	20p
0.0015μF	500V	S/M	10p	1.0μF	250V	M.F.	15p
0.0015μF	500V	Cer.	5p				
0.0018μF	500V	S/M	10p				
0.002μF	100V	Mylar	3p				
0.002μF	500V	Cer.	5p				
0.0022μF	125V	P.S.	6p				
0.0022μF	500V	S/M	10p				
0.0022μF	1,000V	MDC	6p				

Note: S/M = silver mica 1% tol.
P.S. = polystyrene 2% tol.
MDC = a.c. rating = 300V.
M.F. = Mullard min. foil.
Cer. = ceramic.

RESISTORS

All 5%, high-stability, E12 values.
‡ watt—1p; † watt—4p; 2 watt—6p.

LOW Ω RESISTORS

2‡ watt wire-wound, 1 Ω.
1.8 Ω, 2.7 Ω, 3.3 Ω, 3.9 Ω.
4.7 Ω, 5.6 Ω, 6.8 Ω, 8.2 Ω.

10p

CONTROLS, Log. or Lin

Single, less switch, 15p
Single, D.P. switch, 24p
Tandem, less switch, 40p
5k Ω, 10k Ω, 25k Ω, 50k Ω, 100k Ω, 250k Ω,
500k Ω, 1M Ω, 2M Ω.

FUSES

1‡ in glass—2ip
60, 100, 150, 250, 500, 750mA; 1, 1.25, 1.5,
2, 2.5, 3, 5, 7.5, 10, 15 amp.

1‡ in glass—2ip

100, 250, 500mA; 1, 2.5 amp.

Anti-surge 1‡ in—8p

250, 500, 750, 850mA; 1, 4.5, 2, 3 amp.

Anti-surge 20mm—5p

80, 125, 200, 315, 400, 500, 630, 800mA;
1, 2 amp.

ELECTROLYTICS

10μF	64V	8p
25μF	50V	8p
50μF	50V	10p
100μF	25V	10p
100μF	50V	10p
250μF	25V	12p
250μF	50V	17p
500μF	25V	18p
500μF	50V	25p
1,000μF	25V	27p
1,000μF	50V	39p
2,000μF	25V	36p
2,000μF	50V	53p
2,500μF	25V	45p
2,500μF	50V	60p
3,000μF	25V	48p
5,000μF	25V	55p
5,000μF	50V	98p

SILICON BRIDGE RECTIFIERS

40 P.I.V.,
1.5 amp. **50p**

PANEL FUSE-HOLDERS

For 1‡ in fuses 18p
For 20mm fuses 15p


ZENER DIODES

From 2 to 33 volts.
400mW, 15p; 1.5 watt, 22ip

PLUGS

Car aerial
Co-axial
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 4 pin
D.I.N. 5 pin, 180°
D.I.N. 5 pin, 240°
D.I.N. 6 pin
Jack, 2‡mm unscreened
Jack, 2‡mm screened
Jack, 3‡mm unscreened
Jack, 3‡mm screened
Jack, 4‡in unscreened
Jack, 4‡in screened
Jack, stereo, unscreened
Jack, stereo, screened
Phono, plastic top
Phono, plated metal
Wander, red or black
Banana 4mm red or black

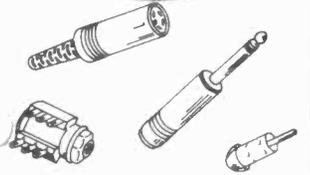14p
8p
7p
13p
14p
13p
15p
13p
9p
10p
8p
12p
12p
20p
20p
35p
5p
3p
12p
6p



SOCKETS

Car aerial
Co-axial, surface
Co-axial, flush
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 5 pin, 180°
D.I.N. 5 pin, 240°
Jack, 2‡mm
Jack, 3‡mm
Jack, 4‡in unscreened
Jack, 4‡in switched
Jack, stereo, switched
Phono, single
Phono, 2 on a strip
Phono, 3 on a strip
Phono, 4 on a strip
Wander, single, red or black
Wander, twin strip
Banana 4mm red or black

8p
8p
8p
10p
9p
9p
10p
10p
15p
24p
5p
7p
9p
10p
3p
7p
6p

LINE SOCKETS

Car aerial
Co-axial
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 5 pin, 180°
D.I.N. 5 pin, 240°
Jack, 3‡mm
Jack, 4‡in screened
Jack, stereo, screened
Phono, plated metal

14p
17p
13p
16p
16p
15p
14p
14p
15p
15p
14p
14p
15p
15p
14p

TRANSISTORS

AC127	17p	BC109	11p	BFX29	38p	ST141	23p
AC128	17p	BC147	12p	BFX84	25p	UT46	35p
AC176	22p	BC148	12p	BFX88	30p	2N696	15p
AC187	22p	BC149	12p	BFY50	21p	2N706A	12p
AC188	27p	BC157	14p	BFY51	21p	2N2926G	14p
AC188	27p	BC158	14p	BFY52	22p	2N2926	13p
AC199	25p	BC159	14p	MAT100	25p	2N2926	12p
AD149	25p	BD131	75p	MAT101	29p	2N3053	21p
AD161/162	72p	BD132	75p	MAT120	25p	2N3054	60p
ADT140	62p	BF115	25p	MAT121	29p	2N3055	72p
AF118	25p	BF178	32p	OC28	58p	2N3702	15p
AF124	22p	BF179	56p	OC35	48p	2N3703	14p
AF125	19p	BF180	30p	OC44	25p	2N3704	15p
AF126	20p	BF181	30p	OC45	12p	2N3705	14p
AF127	19p	BF184	30p	OC71	11p	2N3705	14p
AF178	67p	BF185	32p	OC72	13p	2N3706	14p
AF179	66p	BF194	14p	OC75	20p	2N3711	14p
AF180	66p	BF195	14p	OC200	27p	2N3819	35p
AF239	32p	BF198	28p	OC201	38p	2N4058	17p
BC107	11p	BF197	15p	OCPT1	60p	2N4558	17p
BC108	11p	BFW10	70p	ST140	13p	2N5459	60p

MINIATURE ELECTROLYTICS

1μF	25V	30μF	15V
2.5μF	64V	50μF	15V
4μF	40V	100μF	15V
5μF	64V		
8μF	15V		
8μF	40V		
10μF	15V		
16μF	40V		
25μF	25V		

DIODES

AA119	11p
OA47	71p
OA90	71p
OA91	71p
OA202	10p
BY100	15p
BY127	22ip
BYZ12	22ip

MAIL ORDERS: C.W.O. only. Please include 10p p. & p. (Air mail extra). S.A.E. with all enquiries please. Telephone 01-692 4412

28watts, r.m.s. 40Hz to 40kHz \pm 3dB



Viscount III Audio Suite complete £49

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.



PRICES SYSTEM 1

Viscount III R101 amplifier	£22 + 90p	P.&P.
2 x Duo Type II speakers	£14 + £2	P.&P.
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23 + £1.50	P.&P.
Total	£59	

Available complete for only **£52 + £3.50**
P.&P.

SYSTEM 2

Viscount III R101 amplifier	£22 + 90p	P.&P.
2 x Duo Type III speakers	£32 + £3	P.&P.
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23 + £1.50	P.&P.
Total	£77	

Available complete for **£69 + £4** P.&P.

SYSTEM 3

Viscount III R100 Amplifier	£17 + 90p	P.&P.
2 x Duo Type II speakers	£14 + £2	P.&P.
Garrard SP25 Mk. III with CER. diamond cartridge, plinth and cover	£21 + £1.50	P.&P.
Total	£52	

Available complete for only **£49 + £3.50**
P.&P.

SPEAKERS Duo Type II

Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10W, 3 ohms. Simulated Teak cabinet. **£14 pair + £2 P. & P.**

Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit 13½in x 8½in with H.F. speaker. Max. power 20W at 3 ohms. Frequency range 20Hz to 20kHz. Teak veneer cabinet. **£32 pair + £3 P. & P.**

SPECIFICATION R100/101

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within \pm 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities; headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max.) R101—P.U.1. and radio—65dB. P.U.2—58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 43½ x 9in x 3½in.

R+TV

Radio and TV Components (Acton) Ltd. 21D High Street, Acton, London, W3 6NG
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

Goods not dispatched outside U.K.

FIND BURIED TREASURE!

Transistorised Treasure Locator



This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES, ETC. ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy-to-follow, step-by-step, fully illustrated instructions—uses standard PPS battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2-37 + 25p p & p.** (Sectional handle as illustrated 75p extra.) Parts available separately. Made up looks worth £15!

ONLY £2-37

SHORTWAVE TRANSISTOR RADIO

ONLY £2-25



Anyone from 9 years up can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. **Eavesdrop on unusual broadcasts.** Uses PPS battery. Size only 3in x 4½in x 1½in. **Only £2-25 + 17p p & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately.)

Eavesdrop on the exciting world of Aircraft Communications—

V.H.F. AIRCRAFT BAND CONVERTER ONLY £2-37



Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower, clear for yourself the disciplined voices hiding tensions on talk dozens. Be with them when they have to take nerve ripping decisions in emergencies. Tune into the international distress frequency. Covers the aircraft frequency band including **HEATHROW, GATWICK, LUTON, RINGWAY, PRESTON, WICK, ETC. ETC. CLEAR AS A BELL.** This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PPS battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables) **NO CONNECTIONS WHATSOEVER NEEDED. SEND ONLY £2-37 + 25p p & p for kit including case, nuts, screws, wire, etc. etc.** (Parts available separately.)

SLEEP INDUCER

ONLY £2-75



Do you wake up in the night and can't get off to sleep again? Would you like to be gently soothed and to satisfying sleep every night? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether. The effect it has on people is amazingly very similar to hypnosis. All transistor. No knowledge of electronics or radio needed. Step-by-step instructions. No soldering necessary. Kit includes case, nuts, wire, screws, etc. **SEND £2-75 + 25p p & p (parts available separately.)**

ELECTRONIC ORGAN


ONLY £2-75



Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Fully transistorised. **SELF-CONTAINED LOUD-SPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary, simple as ABC to make. *Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions.* **ONLY £2-75 + 25p p & p for kit, including case, nuts, screws, simple instructions, etc.** Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

READY BUILT AND TESTED TREASURE LOCATOR MODULE

ONLY £4-95

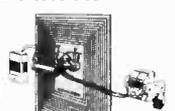

FULLY TRANSLATORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PPS battery and phones and it's working. Put it in a case, screw a handle on and **YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20!** EXTREMELY SENSITIVE—PICKS UPATES EARTH, SAND, ROCK, WATER, ETC. EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. So sensitive it will detect certain objects buried **SEVERAL FEET BELOW GROUND.** GIVES CLEAR SIGNAL ON ONE COIN: **£4-95 + 30p carr.** etc.

BUILD 5 RADIO AND ELECTRONIC PROJECTS

ONLY £1-97



Amazing Radio Construction set! Become a radio expert for £1-97. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation box 37p extra as illus. (if required) (parts available separately) no soldering necessary. **Send £1-97 + 25p p & p.**

SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON



ONLY £2-25

CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! The RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. **IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron.** Once used you will never want to be without it—**TAKE IT ANYWHERE.** Uses standard PPS batteries (current used so small that battery life is almost shelf-life). **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components nuts, Screws, Wire, etc., no soldering. **Send only £2-25 + 25p p & p.** (Parts available separately.)


CONCORD ELECTRONICS LTD. (P.E.27), 8 Westbourne Grove, London, W.2. Callers Welcome 9 a.m.-6 p.m. inc. Saturday

TOURIST

MARK 3 CAR RADIO

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in 2in 4½in deep.

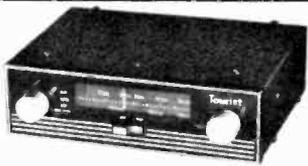

SET OF PARTS

£6-30 Plus P. & P. 50p

Speaker postage free when ordered with parts

Circuit diagram 13p, free with parts Speaker, baffle and fixing kit **£1-25 extra plus P. & P. 25p**

SOUND 50


50 WATT AMPLIFIER & SPEAKER SYSTEM



Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: -3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: ±13dB at 60Hz. Treble Control Range: ±12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power. **SPEAKERS!** Size 20in x 20in x 10in incorporating 12in heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

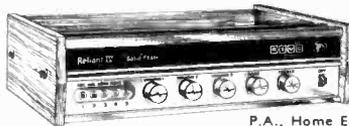COMPLETE SYSTEM £50 Plus £6 p & p. or available separately Amplifier: £28-50 plus £1-50 P. & P. Speaker: £12-50 each plus £2-25 P. & P.



RELIANT MK. IV

The Reliant Mk. IV provides a high standard of sound reproduction, with full mixing facilities. Its versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate bass and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry
- ★ Attractive Styling

1. Crystal Mic. or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 and 5 are suitable for a wide range of medium output equipment (Gram, Turner, etc.) Organ, etc.) All 250mV sensitivity.

CONTROLS: 3 Volume controls. Bass control range ±13dB @ 60 Hz. Treble control range ±12dB @ 15KHz. Separate ON/OFF Switch. Neon Indicator. **POWER OUTPUT:** 12 Watts R.M.S. into 3 to 4 ohms speaker.

SIGNAL/NOISE: Better than -60dB on inputs 3, 4 and 5 and -50dB on 1 and 2. **SUPPLY:** 220 to 250V A.C. Mains. **SIZE:** 12½in x 6in x 3½in.

PRICE


£9-50

Plus P. & P. 60p

CONTINENTAL 4-TRACK, 3-SPEED TAPE DECK

with high impedance heads R.C. 74 tape deck. Three speeds—7½, 1½ and 1½ i.p.s. 4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7in. The R.C. 74 is driven by a powerful 200/250V 50-cycle a.c. motor. A heavy, accurately balanced flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7in. Fast rewind in both directions. Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

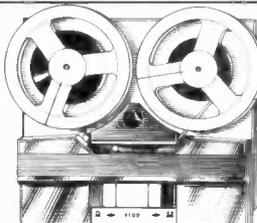The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6in. Even single deck fully tested before dispatch. Spools not supplied. **£15.** Plus 75p P. & P.



R+TV RADIO & TV COMPONENTS (ACTON) LIMITED

See opposite page for addresses



E.240 20 watt 240 volts soldering iron fitted with ¼" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and ¼" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**

CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70**

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and ¼" are obtainable. Price **£1.83**.



your soldering appliance specialists.



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety; fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and ¼" available. Can also be supplied for 220 volts. Price **£1.80**

CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price **£1.95**



SK. 2 SOLDERING KIT


This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40**.



MES. 12

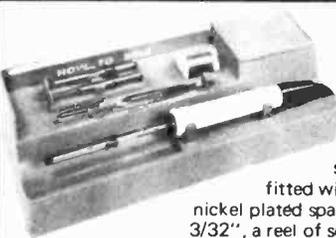A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price **£1.95**.



SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price **£2.75**

sign here to answer all your soldering problems.



from electrical, radio or car accessory shops or from **Antex Ltd., Freepost** (no stamp required) **Plymouth**
PL1 1BR Telephone 0752 67377/8

Please send the Antex colour catalogue.

Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name _____
 Address _____

PE 3

VOL. 8
March

No. 3
1972

PRACTICAL ELECTRONICS

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial D. BARRINGTON G. GODBOLD S. R. LEWIS B.Sc. (Eng.)

Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY R. J. GOODMAN

Advertisement Manager D. W. B. TILLEARD

IN CHARACTER

THE requirement for direct readout of data at high operating speeds from a variety of equipments ranging from large computers to pocket size calculators, and from process counters to digital voltmeters, has provoked intense development work into opto-electronic devices. This month we commence an important new series dealing with alpha and numeric displays intended for such purposes.

The present day range of such devices is particularly interesting in that it includes representative examples based on all three traditional electronic processes: the glow discharge in a gas filled tube, the incandescent filament in a vacuum tube, and now the semiconductor light emitting diode. (An interesting parallel to the course of development of those fundamental active devices, the valve and semiconductor.) As for the future, this holds promise of further advancement in the form of plasma panels and liquid crystals. What has become known as optoelectronics is now perhaps the most important new frontier of advancing electronic technology.

Regarding character representation, it seems there often has to be a compromise between style and technical possibility. This is especially true in the case of the latest kind of display devices designed to operate from low voltage lines and to be driven directly from an i.c. Some ingenious arrangements have been devised in order to provide easily recognisable characters which are sufficiently bright for viewing under normal lighting conditions. But in the process, technical limitations have wrought some havoc with the graceful curved roman characters which have been long in general literary use. The resulting severely angular characters are less pleasing in an aesthetic sense, but as more and more digital instruments come into everyday use their general acceptance seems assured.

Maybe the ousting of the elegant cursive letter is somehow appropriate, in view of the reduced part now played by varying-amplitude sinusoidal waveforms. Sharp bursts of current are the prime movers in today's high speed circuits; and pulses are well typified by those partially dismembered characters built up from discrete spots or bars of light.

Sad but true, cursive copperplate writing, however beautiful to look at, belongs to the leisurely past; austere functional characters are the handwriting of this vigorous (some might say vicious) data acquiring and consuming age. If an artist had been commissioned to evoke the visual significance of digital techniques he could hardly have bettered this character style brought about through technical expedience and necessity. F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

TREMOLO UNIT	206
PHOTOCELL THYRISTOR SWITCH	208
GENERAL PURPOSE AMPLIFIER	214
MODEL SERVO CONTROL	230

SPECIAL SERIES

ALPHA-NUMERIC DISPLAYS — I	200
RADIO ASTRONOMY TECHNIQUES — 10	221

GENERAL FEATURES

INGENUITY UNLIMITED	228
THE UNIUNCTION TRANSISTOR	238

NEWS AND COMMENT

EDITORIAL	199
SPACEWATCH	213
POINTS ARISING	218
ELECTRONORAMA	226
PATENTS REVIEW	229
BOOK REVIEWS	234
ON THE FRINGE	237
INDUSTRY NOTEBOOK	246
READOUT	247

SPECIAL SUPPLEMENT

PICKUPS AND TURNTABLES

Our April issue will be published on Friday, March 10.

© IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65 (£2 13s. 0d). Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202



ALPHA NUMERIC DISPLAYS

By R.W. Coles

Part ① Data display
formats and cold
cathode tubes

THE growth explosion in the electronic handling of numerical data has brought with it a great demand for simple systems to display the processed data in a readily understandable form for human interpretation. Electronic data handling in this context is a loose term which covers a wide variety of equipment from the mighty computer to the humble batch counter or digital clock, all of which have need of a means of interfacing their data with people.

Amateur enthusiasts will have little need of the print-out facilities of the larger computers, some of which can print the results of their deliberations at the rate of several pages per second, but there is an increasing amateur application area for simple "Nixie" type displays for use in counters, measuring instruments, and, of course, clocks and calculators.

Alpha-numeric display devices available, or potentially available, to the amateur market are appearing in bewildering profusion, and now seems a good time to review the operation and application of the most useful types, along with some ideas on how to use them in complete display systems.

- 1** Six figure, seven segment L.E.D. display. Ferranti
- 2** Seven segment, L.E.D. display. Litronix (Guest International Ltd.)
- 3** Seven segment, filament indicator. Minitron, type 3015F (A. Marshall & Son)
- 4** Cold cathode, neon filled numerical indicator Mullard, type ZM1020
- 5** Cold cathode, neon filled character indicator. Mullard, type ZM1263
- 6** Cold cathode, neon filled character indicator. Mullard
- 7** Seven segment, luminescent filament indicator. Atron (West Hyde Developments Ltd.)

(U.K. suppliers are shown in brackets)

DATA FORMATS

There are quite a large number of technologies employed to form the heart of display devices: cold cathode tubes, incandescent filaments, fluorescent phosphors, gallium arsenide light emitting diodes (L.E.D.s), being but a few examples. Before looking into the operation of these various displays it is as well to look at the data formats available, as these are common to all device technologies.

Every type of readout is based on one of three basic data formats, the particular form employed being governed mainly by the variety of data to be displayed, the simpler types handling only the numerals, and generally costing less in consequence.

DISCRETE CHARACTERS

The simplest format available, and the one which potentially gives the most pleasing and easy to interpret display, employs a separate character for each display option. The character set to be displayed is "stored" in the device during manufacture, and may take the form of a set of shaped wire cathodes in a "Nixie" tube, or a set of tiny photographic transparencies to be projected onto a screen by an incandescent lamp in another type of indicator. In either case, a separate character is used for each symbol. The word symbol is used because with this system a device can be produced to display any type of alphabetic, numeric, or symbolic character, in any type of style, limited only by the designer's imagination.

While the flexibility and readability of this format are both excellent, in a practical device vocabulary is rather limited due to the space required to store the separate symbols, and for this reason this format is used only when a comparatively small repertoire is required, 0 to 9, plus and minus or kHz/MHz for example.

DOT MATRIX

By constructing a display device from a matrix of dots, which may be individually illuminated if required, a very versatile indicator is formed which does not have a limited repertoire like the discrete character type.

A dot matrix can be built from separate filament lamps, light emitting diodes, gas discharges, and others, and though the readability is perhaps slightly worse than the discrete types, the wide variety of characters which can be handled by each device more than compensates.

Fig. 1.1 shows 36 characters of the A.S.C.I.I. (American Standard Code for Information Interface) code, which can be displayed on a group of 35 dots arranged as a 7x5 matrix. A single plane readout with such an impressive character capability can be used to handle even the most sophisticated display tasks but the crunch comes with the decoding and driving electronics required to handle the matrix.

Taking the A.S.C.I.I. code as an example, each character is defined by a six bit binary word, and it is necessary to decode this information to a form which is suitable for driving the matrix directly, for example, telling the display to light up all of rows 3 and 5 to form an equals sign. In a nutshell, the decoder has to decode the binary code to its one-of-sixty-four decimal equivalent, which is then used to determine the state of each of 35 dots. In these days of M.O.S. large scale integrated circuits this is not such a difficult or expensive task as it may appear at first sight.

BAR MATRIX

The two formats discussed so far represent opposite extremes of display versatility, and for some applications it is handy to have a system which bridges the gap between the two. This compromise is available in the form of bar matrix displays, which are obtainable with varying degrees of complexity, and hence a wide range of repertoires.

The simplest bar matrix display format is the "seven segment" type, which handles all the numerals, nine letters, and one or two symbols. This type of readout is competitive with the discrete


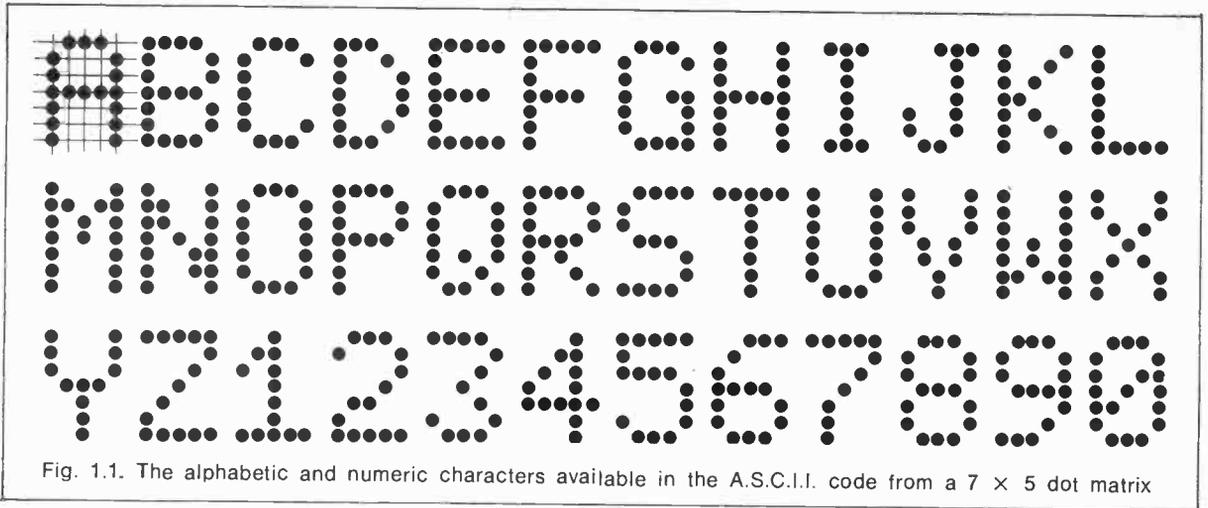


Fig. 1.1. The alphabetic and numeric characters available in the A.S.C.I.I. code from a 7 × 5 dot matrix

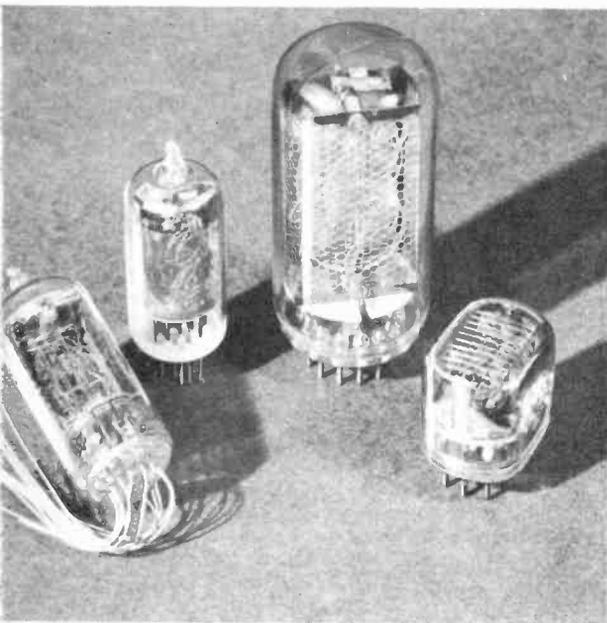

Some of the shapes and sizes of commercially available cold cathode tubes

character type, and is likely to prove more popular in the long run. Already seven segment displays are obtainable in incandescent, fluorescent, and L.E.D. technologies, and decoding/driving i.c.s are becoming very cheap, a definite area to watch for practical requirements of the future.

Fig. 1.2 shows the "seven segment" format, and as can be seen, it is based on a stylised figure of eight made from seven individually illuminated bars. The character set available is quite extensive considering the simplicity of the format, though in general these devices are used only for numeric data, decoders being available for this task. The most obvious drawback of this system is that the characters are highly stylised, and not as we would normally write them, a problem which can be eased to some extent by using zero suppression to enhance readability of multi-digit arrays. We will be looking at the way zero suppression is achieved later on.

To overcome readability problems of the basic seven segment indicator, a version using a different bar format has been developed, and this type is shown in Fig. 1.3. To achieve this some of the versatility of the simple version is lost, and some may consider the numerals a bit "wonky" but in use this version gives a very easy to read display whilst retaining the simplicity of the parallel bar type, decoding being of the same nature.

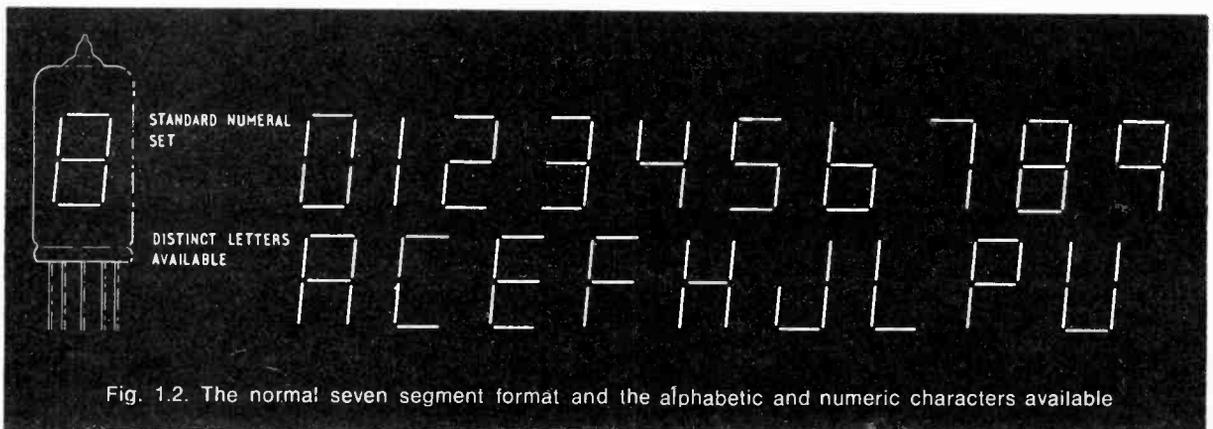


Fig. 1.2. The normal seven segment format and the alphabetic and numeric characters available


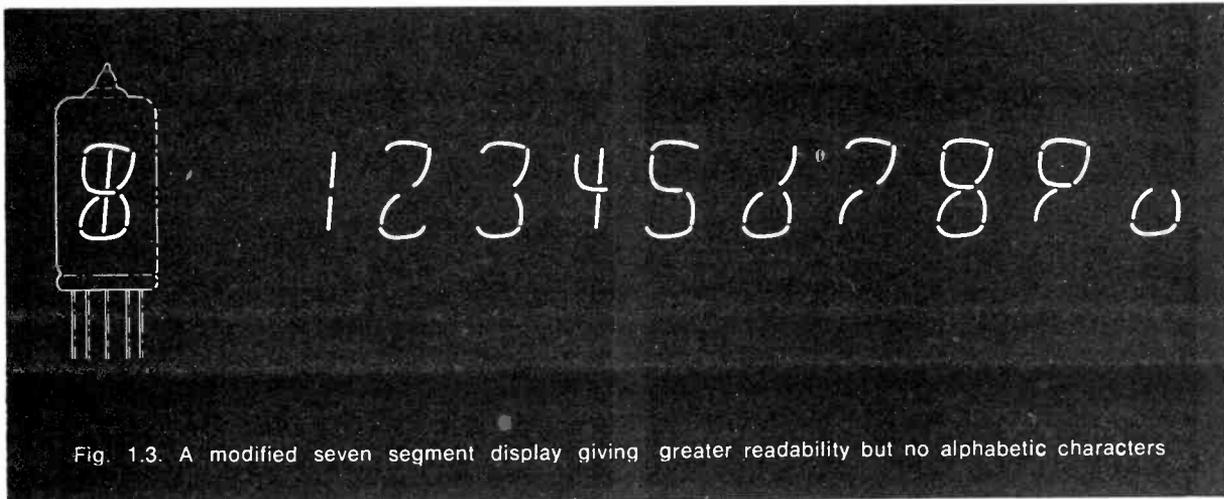


Fig. 1.3. A modified seven segment display giving greater readability but no alphabetic characters

By increasing the number of bars used it is possible to build a device which will handle all the alphabet characters as well as the numerals, and in Fig. 1.4 a possible format using 14 separate bars is shown with its character set (several types of symbol or punctuation mark are also possible). With so many bars as this, the decoding/driving problem again rears its ugly head, resort being made to either M.O.S. arrays or to complex discrete gate decoders.

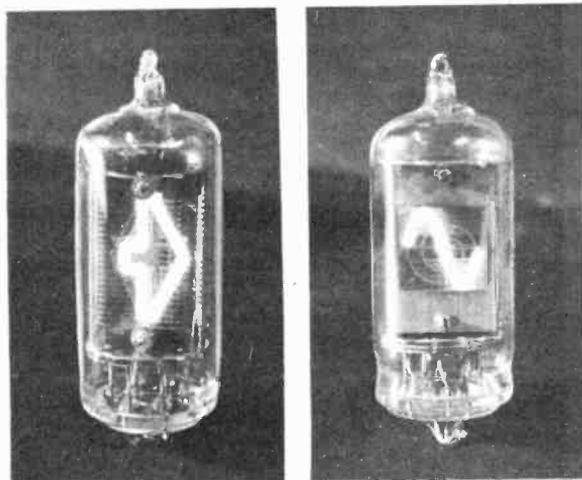As we have seen, formats are available to readout manufacturers to enable them to produce a device at the right price and complexity to suit every application. Most of the technologies used can be incorporated into several of the formats, a situation which leads to the present (and very desirable) state where there are literally hundreds of devices to choose from.



Two cold cathode character indicator tubes

COLD CATHODE DISPLAYS

Perhaps the most well-known type of alpha-numeric display and one which has been featured in

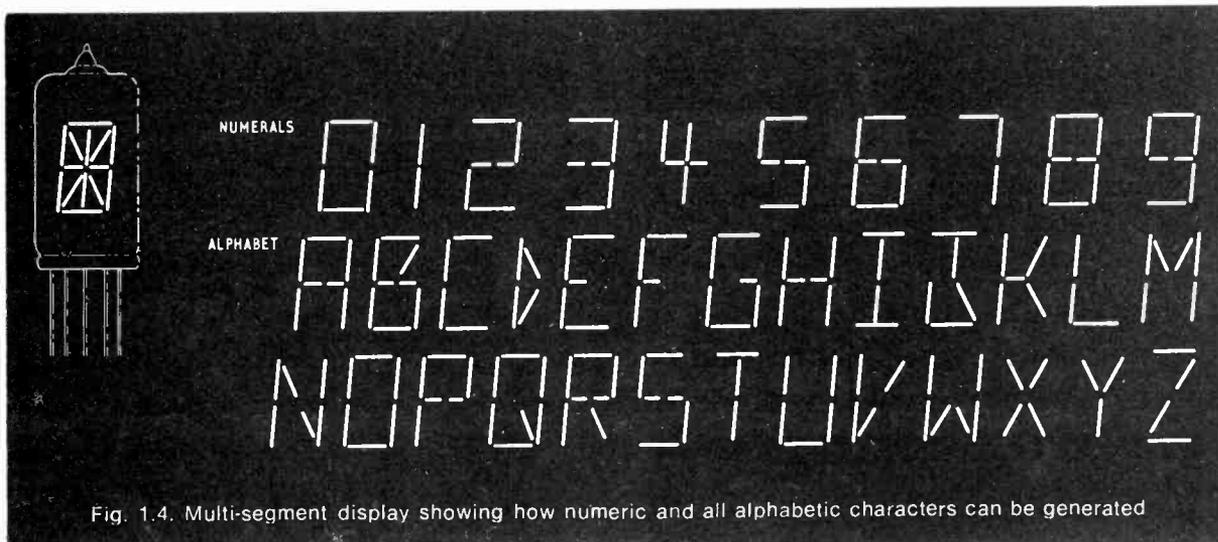


Fig. 1.4. Multi-segment display showing how numeric and all alphabetic characters can be generated


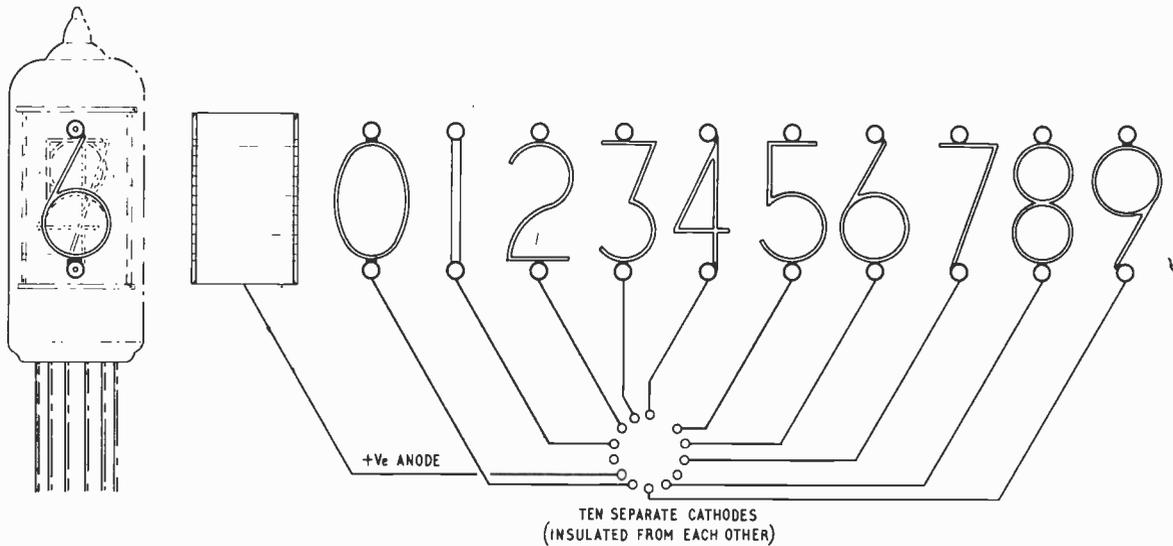


Fig. 1.5. Internal construction of a side-viewing cold-cathode numeric indicator tube

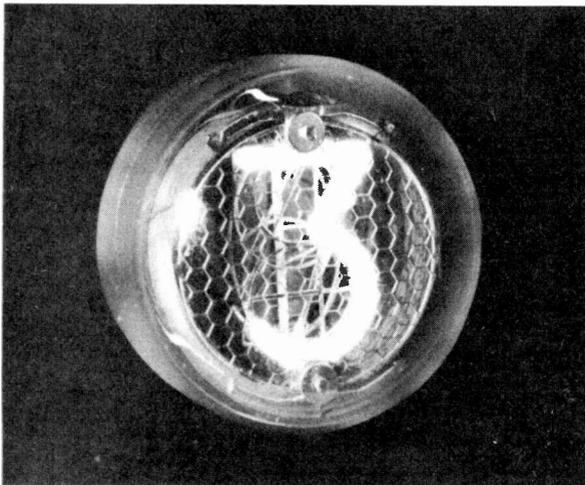

A top-viewing cold cathode tube

several articles in this magazine in the past, is the cold cathode numerical indicator tube called variously "Nixies", "Numicators" and "Numbertrons". These tubes use the same principle of operation as standard neon indicator lamps, that is the ionisation of neon gas by the application of a suitable voltage across them.

The standard type consist of a number of discrete character shaped cathodes, mounted one behind the other, viewed through a metal grid which forms the anode, all contained in a neon filled glass envelope similar to that used for valves. (Fig. 1.5). The cathodes are insulated from one another and spaced as closely as possible to make a compact assembly with a reasonable field of view.

In operation the anode is connected to a high positive voltage through a current limiting resistor, and the required cathode is grounded by the driving circuitry (which may consist of relays, valves, transistors or an i.c.). The voltage developed across the anode-cathode system causes the neon gas to ionise, and with careful physical design a uniform glow is produced round the cathode selected.

The glow colour is a mixture of blue and orange, and if the tube is used without a colour filter reflections from the other cathodes and the anode produce a rather indistinct blurred display. With a red filter positioned in front of the tube, either as an envelope lacquer or a window material common to several digits, background glow can be cut out completely, producing a very pleasing readout. The anode voltage required is not critical, in fact the higher the better, but there is a lower limit set at about 180 to 200V below which some tubes will be very slow to ionise, and more difficult to control.

DRIVING CIRCUITRY

To consider the operation of these tubes in a simple circuit see Fig. 1.6. When the selected cathode is grounded by means of the switch the tube will strike, illuminating the required character. When the neon gas is ionised a current flows through it, limited

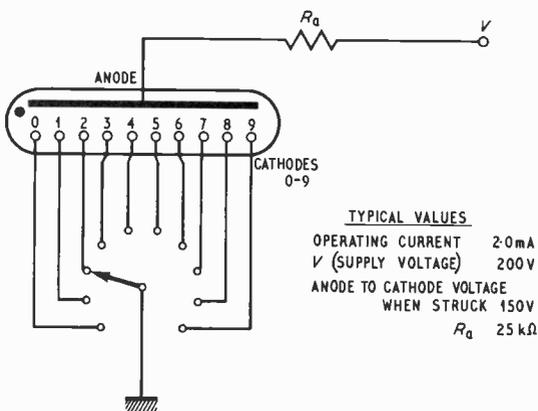


Fig. 1.6. Calculation of the limiting resistor and power supply

by the resistor R_a and the voltage across the tube necessary to maintain conduction. If the anode voltage could fall below the maintaining value then conduction would cease, reducing the voltage drop across R_a and causing the tube to strike again, in a sort of feedback action.

The operating conditions of the tube are thus set by the resistor R_a , and the value required can either be calculated precisely from manufacturers' data sheets, or in the absence of such information a very rough rule of thumb which suffices for the large majority of applications, can be employed. A good average value of operating current for these devices is 2mA, this is the first assumption necessary to use the rule of thumb, and modifications to this figure can be made if desired on the grounds that a big tube will work better with a larger value, and a small one with less.

The next assumption needed concerns the anode to cathode maintaining voltage which will be present across the tube when it is struck, and a useful guess here is 150V. Using these two figures and the known value of the H.T. voltage (V) to be used, the resistor value can be calculated thus:

$$R_a = \frac{\text{H.T. voltage} - \text{maintaining voltage}}{\text{cathode current}}$$

Using the values mentioned above this works out as

$$R_a = \frac{200 - 150}{2} \text{ kilohms,}$$

giving a value of 25 kilohms for R_a , and this is likely to be adequate for most medium sized tubes, and is within a few kilohms of the values worked out from extensive calculations dealing with particular, coded tubes. It should be stressed here that if data is available it is far better to perform the calculations which take into account manufacturing spreads, tube individualities, and the bias on other cathodes, but if data is not available (as so often is the amateur's lot) the rule of thumb will get those tubes burning regardless.

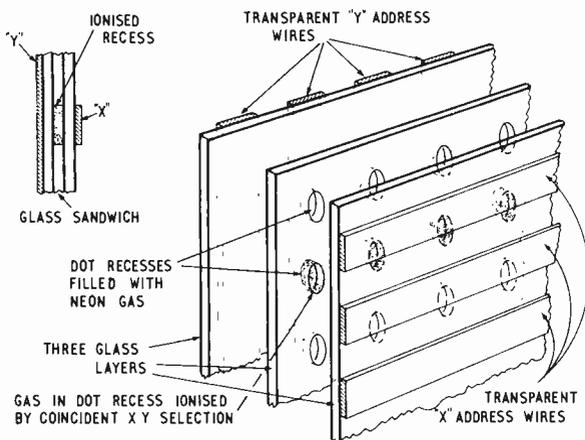


Fig. 1.7. Construction of a dot matrix neon-filled cold cathode tube



A Mullard "Pandicon" fourteen numeral cold cathode tube


OTHER COLD CATHODE FORMATS

The standard Nixie is not the only format used with the cold cathode technology, and both bar and dot matrix versions are available. The bar types have cathodes which form the segments of the format, and operate in a similar fashion to the standard neon tube, identical supply voltages and drivers being required.


The dot type display uses a somewhat different physical construction, each dot in the matrix operates as an individual glow discharge light source, and the required dots are selected by an X/Y addressing array of transparent, thin film, metal lines (Fig. 1.7). Note that the address lines do not come into direct contact with the gas in the recesses, the ionising potential being applied capacitively as a.c. pulses. This type of display is a recent innovation, and promises to be a very useful technique for displaying several lines of data at a time when it will be cheaper than using separate tubes.

Despite these other formats availability, they are not yet an economical choice for the amateur, and in the notes on decoding and driving for cold cathode tubes, we will deal specifically with the discrete character type.

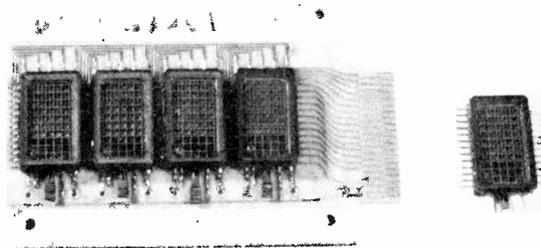Next month: Driving and decoding circuits for cold cathode tubes



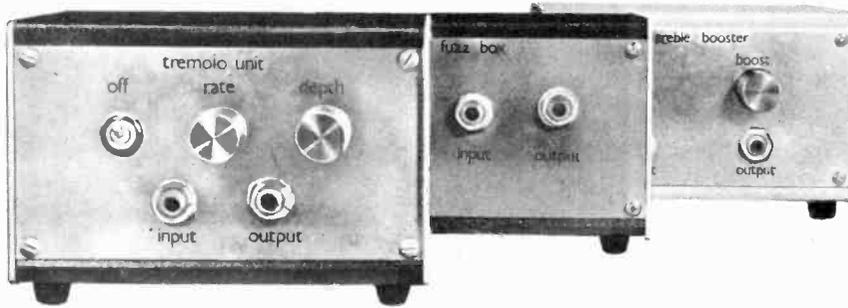A cold cathode dot matrix display. In this type each dot can be individually illuminated (Mullard)



TREMOLO UNIT

The first of three guitar effects units which will add new dimensions to the sounds produced.

By A. Russell

MANY electric guitar players will have noted the high cost of commercially available sound effects units. The tremolo unit described here was designed around cheap, easily available components. It is simple to build and economical with battery power and it will provide a potent tremulant effect for a guitar input with controls available for both tremolo rate and depth of sound produced.

across VR2 and TR3 is suddenly very much reduced when TR3 does conduct. With the transistor switched off the guitar signal passes through the unit unchanged. As TR3 is being switched at a regular rate the output level will vary in depth to produce a tremolo effect.

HOW IT WORKS

In the circuit diagram of Fig. 1, the multivibrator circuit comprising TR1, TR2, switches at a rate made variable by VR1, between 1Hz and 10Hz.

As the collector of TR2 rises and falls between 0V and 8V the capacitor C3 will charge at a rate determined by the CR product of R5 and C3. As the voltage of C3 rises exponentially there comes a point when TR3 switches on. If a guitar is connected to JK1 the output to JK2 which is normally developed

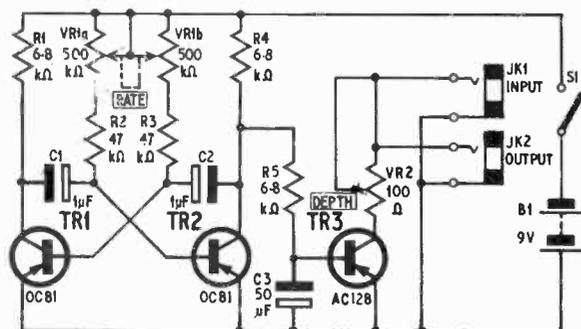


Fig. 1. Circuit diagram of Tremolo Unit

COMPONENTS . . .

Resistors

- R1 6.8kΩ
- R2, R3 47kΩ (2 off)
- R4, R5 6.8kΩ (2 off) - 5p.
- All ½ watt, 10% carbon

Capacitors

- C1, C2 1μF elect. 12V (2 off) 15p.
- C3 50μF elect. 12V

Transistors

- TR1, TR2 OC81 (2 off) 30
- TR3 AC128 22

Potentiometers

- VR1 500kΩ dual gang carbon linear 24p
- VR2 100Ω carbon linear 24p.

Switch

- S1 on/off toggle 50p

Miscellaneous

- SK1, SK2 Standard jack sockets (2 off)
- BY1—PP3 9V
- Battery connectors
- Veroboard 0.15 matrix 2in × 2½in
- Plastic angle (see text)
- Instrument case 6½in × 4in × 4in (G. W. Smith)
- Control knobs (2 off)

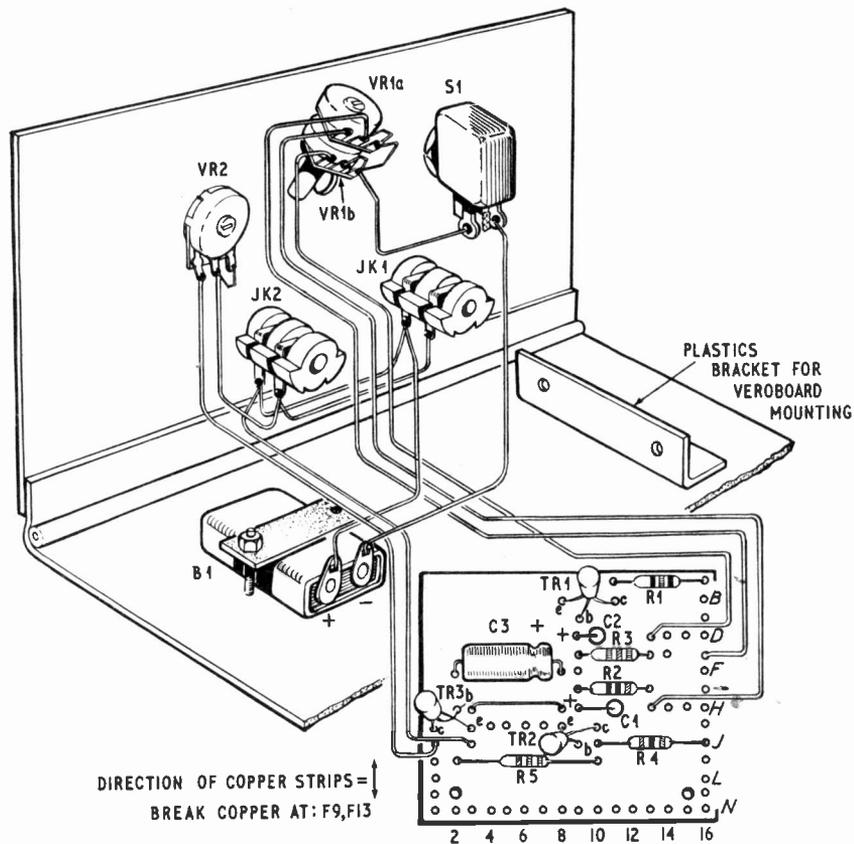


Fig. 2. Component board layout and interwiring details

With VR2 a variable resistor the depth of effect can be altered but there is a point when multivibrator breakthrough is slightly apparent as a ticking noise. While this is not objectionable the unit can be switched off when the guitar is not being played, although if used in a group the ticking would not normally be noticeable above the other instruments.

Increasing the value of C3 may damp this a little, but there will be a maximum above which the tremolo effect will not be satisfactory.

CONSTRUCTION

The majority of components are assembled on a 2in × 2½in piece of Veroboard as in Fig. 2. Also shown are the connections of this to the control panel.


A piece of ½in plastics angle was Araldited to the board and drilled for screw mounting to the case. For ease of operation S1 can be replaced by a foot-switch connected by way of a socket at the front panel.


TESTING

When the unit is completed the wiring should be checked ensuring that the electrolytic capacitors in the multivibrator are the right way round. Should the polarity of these be reversed the multivibrator will probably operate but at the wrong frequency.

Connect the unit to the amplifier and guitar and switch on. Check the operation of the rate and depth controls. If all is satisfactory the case panels can be assembled so completing the construction.

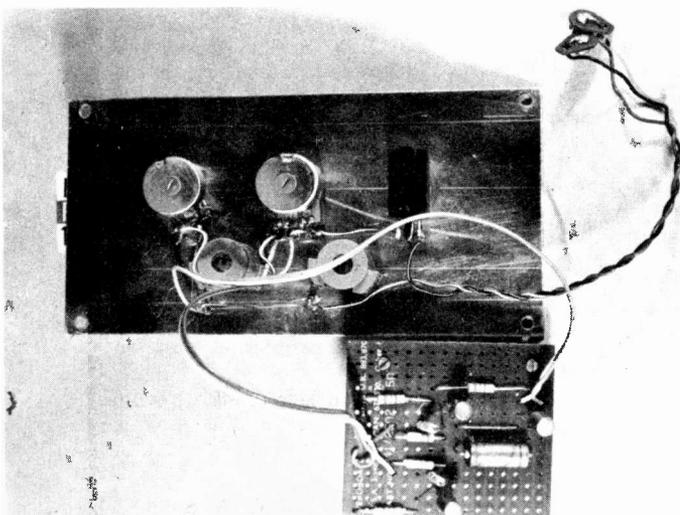Some loss of signal should be expected when the tremolo unit is connected and if the gain of the amplifier is not sufficient to compensate for this a preamplifier may be necessary. If so, it should be connected between the unit and the amplifier. ★



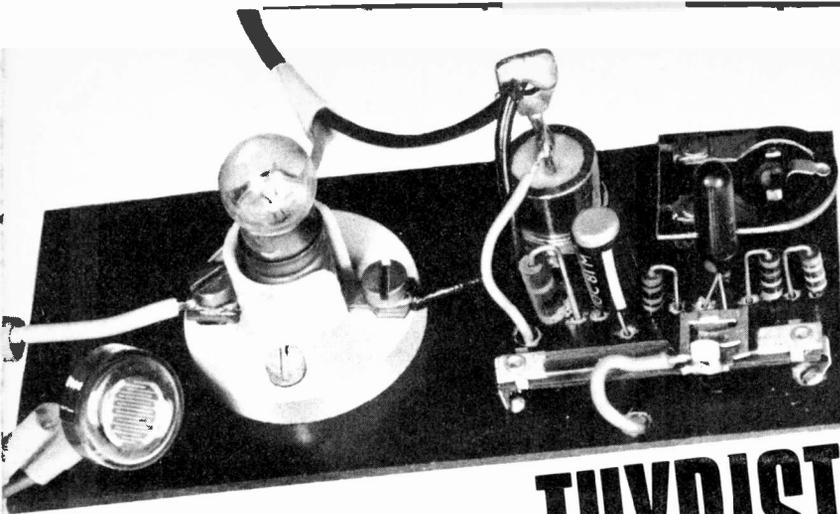

PHOTOCELL THYRISTOR SWITCH

By L.H.Olsen & D.A.Reeves

THE following circuit is for an automatic, light-operated switch which offers reliability and high sensitivity to light variation but low sensitivity to component changes.

The electronic experimentalist constructing a light-operated switch generally must contend with a variety of electronic and mechanical problems. This circuit is an all solid-state design employing a thyristor as the load current switch. Simplicity and economy are apparent with the design. The unit is either self-latching, remaining on after initial activation, or an on-off switch following light variations. The choice depends on whether the power supply is smoothed or simply half-wave rectified a.c., respectively. Load currents approaching 5 or 10 amps are allowed with a relatively inexpensive range of thyristors. In the off state, only a very low leakage current in the order of a few microamps is drawn.

SIGNAL INPUT

The cadmium sulphide photoresistive cell, PCC1, in Fig. 1 acts as a voltage divider in conjunction with the series pair of resistors R1 and VR1. In bright light conditions, the photoresistor has a nominal resistance of approximately 500 ohms.

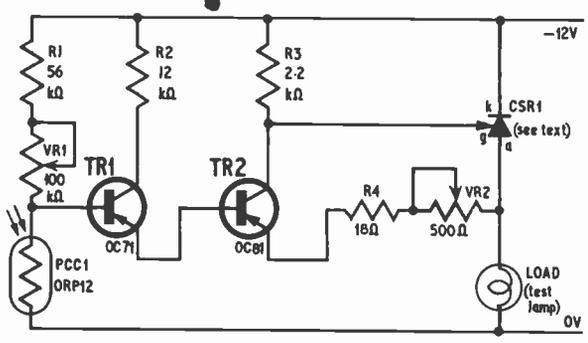


Fig. 1. Circuit diagram of the photocell thyristor switch

This value will hold the base bias on transistor TR1 near zero volts which corresponds to the off or non-conducting state. In low light conditions, the base bias increases (negatively) as PCC1 resistance increases in the voltage divider. TR1 becomes forward biased with emitter current increasing to some maximum value.

TRANSISTOR STAGES

The high gain transistor pair TR1 and TR2 act as both voltage follower and current amplifier with respect to the photocell.

When TR1 is biased off, the relative base-emitter bias of TR2 is zero. Thus negligible current will flow in the emitter-collector circuit of TR2. The direct connection between the emitter of TR1 and base of TR2 gives a high degree of current sensitivity at the collector of TR2 to variations in photocell resistance changes. Current through the voltage divider and in TR1 are in the order of microamps, whatever the state of the circuit.

As TR2 is biased on by conduction through the emitter of TR1, large current flow is possible through the circuit formed by the load, R4 and VR2 in TR2 emitter lead, and the thyristor gate-cathode junction in TR2 collector lead. Switching the thyristor on requires moderate current for approximately 50 microseconds after which the thyristor gate serves no purpose in maintaining anode to cathode conduction.

To prevent possibly destructive power dissipation in TR2, a self-biasing feature links TR2 and the thyristor.

THYRISTOR OPERATION

The device has a *pnpn* construction as shown in Fig. 2a. The *p* and *n* material of the terminal regions are the anode and cathode, respectively. A lead from the internal *p*-type semiconductor material serves as the gate for switching the thyristor from the off state to conduction. The gate requires a current of roughly 25 milliamps to trigger the device on.

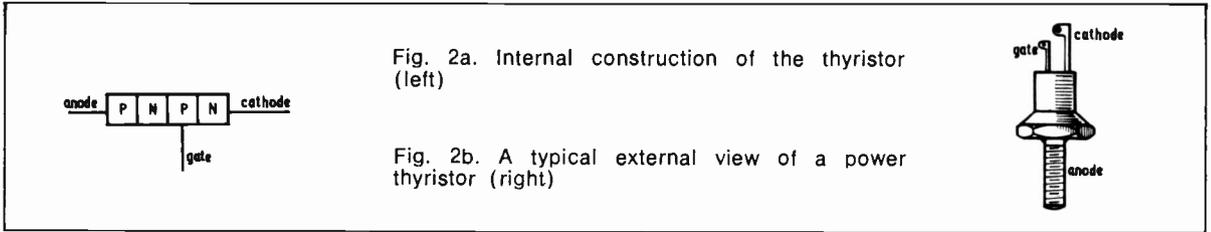


Fig. 2a. Internal construction of the thyristor (left)

Fig. 2b. A typical external view of a power thyristor (right)

It is recommended that the gate-cathode junction never be reverse biased, i.e. the gate should not be allowed to become more negative than the cathode.

Thyristors act as diodes when supplied with an a.c. power supply. Note here that the gate should be protected by a series diode when supplied with a.c. voltage. Thyristors are self-latching to the on state after the gate signal has been applied, but when the supply voltage falls to zero as with an a.c. supply, the thyristor switches off and remains off unless a gate signal occurs during the next cycle.

Physically, high power thyristors are encased for mounting on a heat sink. The threaded stud on one end is the anode (leading to the positive end of a power supply for conduction). The opposite end contains two tags, the larger being the cathode and the smaller being the gate, see Fig. 2b.

SELF-BIASING ACTION

Looking at the transients as the thyristor is switched on reveals an interesting circuit characteristic. As TR2 begins to conduct, current flows through the gate of the thyristor. So long as the current is insufficient to switch the thyristor on, the emitter of TR2 remains near zero volts. When the thyristor switches on, the full supply voltage rapidly appears across the load rather than the thyristor.

In the switching process, the emitter of TR2 swings to full negative potential while TR1 holds the base of TR2 at a positive voltage with respect to the negative rail. Thus TR2 is switched off by this reverse biasing process.

The sensitivity of TR1 and TR2 means that conduction to the thyristor gate occurs rapidly as the

light level crosses a threshold set by VR1. The variable resistor VR2 assists by holding small conduction currents below the gate threshold level. Once conduction begins at the thyristor, the otherwise wasted current in TR2 is limited to a duration of a few microseconds.

CONSTRUCTION

Due to the simplicity of this circuit, wiring details can be arranged to suit the reader's own requirements. A suggested layout is shown in Fig. 3. Obviously miniaturisation can easily be achieved. R1, VR1, R2 and R3 dissipate less than $\frac{1}{4}$ watt of power. Due to the short duration of power dissipation in R4 and VR2, these resistors can be $\frac{1}{4}$ watt.

Throughout the circuit, fixed resistance values are not critical so that any reasonably close resistor should be sufficient. R1 and R4 are included as safety resistors to protect the circuit from accidental zeroing of VR1 or VR2 during the setting up procedure. They should not be omitted during construction.

The selection and mounting of a thyristor should be done with the care usually given to semiconductor components.

SETTING UP

After constructing and checking connections in the circuit, turn VR1 and VR2 to their maximum resistance setting. Set the photocell in the required light conditions for switching on, remembering that in bright light the circuit should be off. With the power on, bring the value of VR2 down until the circuit switches on. Next, adjust VR2 back to a

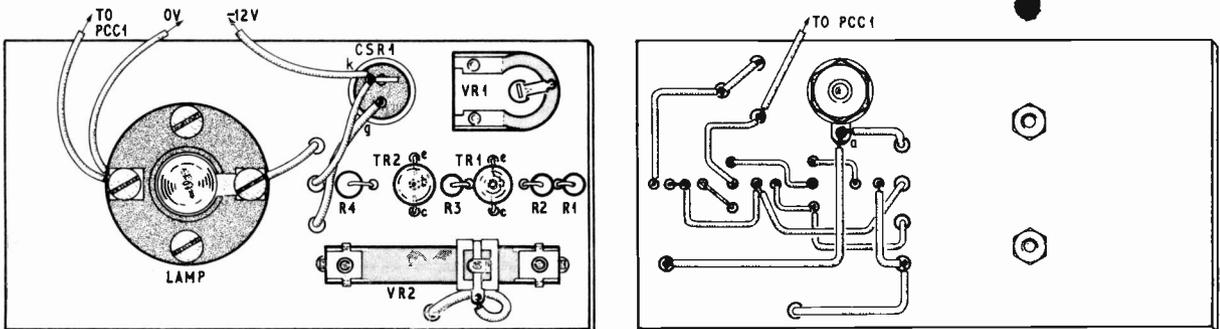


Fig. 3. Wiring details of the prototype

higher resistance so as to hold a test lamp off. The lead to the test lamp must be broken and re-made to switch the thyristor off (or the power supply switched off).

VR2 is a rougher control than VR1 for switching in relative darkness. They reverse their function in this respect when set to switch in brighter lighting.

Resistor R1 may be increased toward 100k Ω or 150k Ω if more sensitivity in dark conditions is needed, i.e. if the circuit is to differentiate between very dim lighting levels. These settings are moderately sensitive to a shift in the supply voltage although the circuit was found to function readily over a $\pm 30\%$ change from the stated 12V supply voltage.

MODIFICATIONS

In its present state the circuit can actuate parking lights or various detection systems. The speed of switching is controlled by the slowest element in the circuit. In this case, the photocell is the slow link for the detection of a rapid variation between lighting shades. The response time is somewhere around 50 milliseconds.

If an external voltage pulse or photodiode is used at the base of TR1, the switching time drops to roughly 50 microseconds. This is better than a relay reaction time. The transistors, even if not those suggested in the circuit diagram, generally switch in a range of fractions of a microsecond to a few microseconds, which is a negligible time.

Other signal sources may be a photo-transistor, a piezoelectric crystal giving a pressure sensing switch, or capacitive or inductive reactance giving a frequency sensitive switch.

SUGGESTED APPLICATIONS

Applications of this simple circuit are closely related to the power rating of the thyristor selected by the constructor. The authors used in the prototype an unmarked thyristor of approximately 30 volts p.i.v. in a 5 amp case, as may be purchased from many electronics shops.

A 5 amp thyristor used with the test lamp at 2 watts was sufficient in the authors' application to switch on automobile lights which draw about 30 watts. This still represents only half the current rating of the thyristor.

The other rating to bear in mind is the peak inverse voltage which may be regarded as being roughly a measure of the forward voltage hold-off rating.

The maximum voltage is restricted to the maximum voltage allowed by the transistors.

With some imagination a voltage dropping resistor and Zener diode may be added to allow increased voltage on the thyristor, whilst the transistors are protected to below their limit values.

Besides finding convenient use of the switch for parking lights, the authors also found the circuit was ample to operate a small mechanical cycle counter, for which the input was generated by a rotating disc with a segment cut out, permitting light to fall onto the photocell. On this application full wave rectified voltage was supplied to the circuit, again referring to the thyristor, the part of each voltage cycle which dropped to zero ensured that the thyristor turned off as opposed to latching on as it is designed to do when constant d.c. voltage is the power source.

COMPONENTS...

Resistors

R1 56k Ω

R2 12k Ω

R3 2.2k Ω

R4 18 Ω $\frac{1}{4}$ watt

All resistors $\pm 10\%$, $\frac{1}{8}$ W unless otherwise stated

Potentiometers

VR1 100k Ω carbon skeleton preset

VR2 500 Ω wirewound linear slider

Transistors

TR1 OC71 or equivalent

TR2 OC81 or equivalent

Thyristor

CSR1 5RC5 (International Rectifier Co.)

5A 50V p.i.v. (Gate triggers at 2 volts, 15mA)

Light Dependent Resistor

PCC1 ORP12

Miscellaneous

Paxolin sheet or Veroboard 3in \times 2in \times $\frac{1}{16}$ in
M.E.S. lamp and holder (see text)

A counter and parking light application have been mentioned. The thyristor load may also be a burglar alarm set off by interrupting a light source.

The idea in each application is to replace the test lamp load with a working load. Then a thyristor is inserted which has the correct rating in terms of a sufficient value for the maximum current and voltage applied. Remember that the transistors are giving a high gain so that there appears to be a fair disparity between the current drawn by the thyristor and by the rest of the circuit; a large thyristor current—say 10 amps—can be expected.

THYRISTOR SELECTION

Either latching or non-latching action is possible and a range of load voltages and currents are possible according to the type power source, whether d.c. or rectified a.c. respectively, and the selected value of the thyristor.

If a constant d.c. power source is used then the device will be latched on without regard to the photocell until the power source is removed.

To find the correct thyristor current rating either

- take the value of current given for your load, or
- divide rated wattage by the applied volts, or
- divide applied voltage by the rated load resistance.

Then select the next largest thyristor so that there is a factor of safety.



Further suggestions for the load which may be developed quickly are a d.c. solenoid coil, a relay coil—the relay poles doing multiple switching or H.T. switching—or a simple resistive load such as a light. If the photoresistor were sensitive to the light from a flame, the switch could be used for flame detection.

Other suggestions are left to the reader. ★

look! electronics really mastered

... practical
... visual
... exciting!

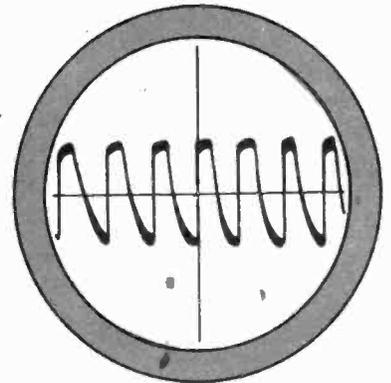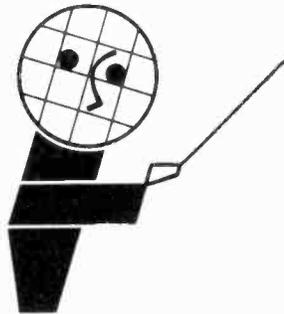no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

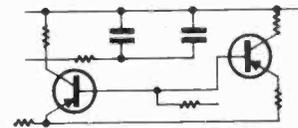2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME

BLOCK CAPS

ADDRESS

PLEASE P.W.6

special free gift also to all our students

HENRY'S FOR **FIRST GRADE BRAND BRANDED** GERMANIUM AND SILICON TRANSISTORS, DIODES, RECTIFIERS, TRIACS, FETS, ZENERS, BRIDGES AND INTEGRATED CIRCUITS
 BY ATES · EMIHUS · FAIRCHILD · FERRANTI · I.T.T. · MULLARD · NEWMARKET · PHILIPS · R.C.A. · TEXAS

TRANSISTORS

A SELECTION FROM OUR LIST

AA4730 10p	BD115 75p	OC18 50p	2N1303 18p
AA4742 15p	BD123 85p	OC20 25p	2N1304 22p
AAZ13 10p	BD124 80p	OC22 50p	2N1305 22p
AAZ15 10p	BD131 75p	OC23 50p	2N1306 25p
AAZ17 10p	BD132 80p	OC24 50p	2N1307 25p
AC107 85p	BDY11	OC26 40p	2N1308 25p
AC126 80p		OC28 40p	2N1309 25p
AC127 50p	BDY17	OC29 60p	2N1613 25p
AC128 20p	BDY38 65p	OC35 50p	2N2147 75p
AC176 20p	BDY60	OC36 50p	2N2160 60p
AC187 35p	\$1.00	OC42 40p	2N2217 35p
AC188 85p		OC43 50p	2N2218 35p
AC197 15p	BF115 35p	OC44 15p	2N2218A
ACY18 25p	BF154 80p	OC45 15p	2N2219 25p
ACY19 25p	BF158 15p	OC70 25p	2N2219A
ACY20 20p	BF159 35p	OC71 15p	
ACY21 20p	BF180 35p	OC72 25p	
ACY22 10p	BF194 15p	OC75 35p	2N2220 25p
ACY29 55p	BF195 15p	OC76 25p	2N2221 20p
ACY40 25p	BF196 15p	OC77 25p	2N2222A
ACY41 15p	BF197 15p	OC81 20p	
ACY44 25p	BFX13 25p	OC81D 20p	2N2222A
AD140 60p	BFX29 25p	OC81Z 40p	2N2222A
AD149 40p	BFX30 25p	OC83 25p	
AD161 65p	BFX84 25p	OC84 25p	2N2369 15p
AD192 35p	BFY52 20p	OC139 20p	2N2369A
AF114 25p	BFY88 25p	OC140 40p	
AF115 25p	BFY87 25p	OC141 40p	2N2646 40p
AF116 25p	BFY88 20p	OC170 25p	2N2904 20p
AF117 20p	BFY18 25p	OC171 20p	2N2904A
AF118 60p	BFY50 20p	OC200 10p	
AF124 25p	BFY51 20p	OC201 75p	2N2905 25p
AF125 20p	BFY52 20p	OC202 25p	2N2905A
AF126 20p	BFY53 15p	OC206 95p	
AF127 20p	BFY60 20p	OC271 97p	2N2906 20p
AF139 30p	BRX20 15p	ORP12 50p	2N2906A
AF180 50p	BRX21 20p	ORP80 25p	
AF181 45p	BRX27 15p	ST140 15p	2N2907 25p
AF185 20p	BRX28 15p	ST141 25p	2N2907A
AF186 40p	BRX95 12p	TIP29A 50p	
AF239 40p	BT105 25p	TIP30A 20p	2N2925 15p
ABY26 25p	BT106 15p	TIP31A 60p	2N2926 10p
ABY27 25p	BT126 12p	TIP32A 70p	2N3011 30p
ABY28 25p	BT124 15p	TIP33A 25p	2N3053 20p
ABY29 30p	BT182 90p	TIP34 40p	2N3054 50p
ABZ21 55p	BYZ10 85p	TIP34A 40p	2N3055 75p
BA100 15p	BYZ11 30p		2N3525
BA102 30p	BYZ12 30p	TI843 40p	
BA110 25p	BYZ13 25p	TI850 10p	2N3614 55p
BA115 7p	BZY7841 00	TI851 10p	2N3702 15p
BA116 5p	BZY7842 00	TI852 10p	2N3703 15p
BAX16 7p	GET103 25p	TI860 18p	2N3704 12p
BAY31 7p	GET111 45p	TI861 20p	2N3705 10p
BAY38 5p	GET113 25p	TI862 20p	2N3707 12p
BC107 10p	GET114 20p	V405A 25p	2N3708 10p
BC108 10p	GET115 50p	V405B 35p	2N3714
BC109 60p	GET116 50p	V406 45p	2N3715 22.00
BC109C 12p	GET880 45p	W06 45p	2N3715
BC110 10p	GEX882 30p	ZTX107 15p	2N3716
BC112 20p	GTN66	ZTX108 12p	2N3716
BC115 20p	\$1.50	ZTX109 10p	2N3716
BC116 20p	GM378A 55p	ZTX300 15p	2N3771
BC116A 25p	MA110 25p	ZTX301 15p	2N3771
BC117 20p	MA121 7p	ZTX302 20p	2N3772
BC118 20p	MC724F 60p	ZTX303 20p	2N3772
BC119 30p	MJ420 80p	ZTX304 25p	2N3773
BC124 20p	MJ421 80p	ZTX500 15p	2N3773
BC125 15p	MJ2801	ZTX501 15p	2N3791
BC136 20p	\$1.10	ZTX502 17p	2N3812 25p
BC137 20p	MJ2901	ZTX503 17p	2N3820 55p
BC138 20p	\$1.50	ZTX504 40p	2N3820 55p
BC147 12p	MJE340 50p	ZTX531 25p	2N3823 95p
BC148 10p	MJE370 80p	IN914 7p	2N3824 95p
BC149 12p	MJE371 80p	IN916 10p	2N3803 20p
BC153 20p	MJE520 75p	IN4148 7p	2N3806 25p
BC154 20p	NET405 75p	1844 7p	2N4088 12p
BC167 10p	MJE2955	18921 7p	2N4061 12p
BC169 15p	\$1.10	18922 8p	2N4062 12p
BC169C 15p	MJE3055	26301 25p	2N4288 12p
BC177 20p	75p	20302 30p	2N4290 12p
BC178 20p	MPSA06 80p	20303 30p	2N4871 35p
BC179 20p	MPSA58 20p	20304 30p	2N4872 35p
BC182L 10p	MPSA70 15p	20305 30p	2N4873 35p
BC183L 10p	MPS106 50p	20306 30p	2N4874 35p
BC184L 12p	MPS156 55p	20307 30p	2N4875 35p
BC212L 12p	NKT214 20p	20706 10p	40360 40p
BC213L 12p	NKT216 35p	20706A 12p	40381 40p
BC214L 12p	NET405 75p	20910 15p	40392 50p
BCY30 40p	NKT404 55p	20930 12p	40430 10.00
BCY31 40p	OAS 25p	20987 40p	40543 65p
BCY32 60p	OAI5 25p	2N1131 25p	40594 10.05
BCY33 30p	OAT7 10p	2N1132 25p	40595 10.05
BCY34 35p	OAT9 10p	2N1302 18p	40636 10.10
BCY39 30p	OAS79 10p		
BCY40 50p	OAS9 10p		
BCY70 15p	OAS5 10p		
BCY71 20p	OAS200 10p		
BCY72 15p	OA202 10p		

Full transistor list available - send for your free copy today!

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL7 SERIES BRANDED FAIRCHILD, I.T.T. AND TEXAS DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICING

No.	Description	1-11	12-24	25-99	100+	250+
7400	Quad 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	14p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7404	Hex inverter	20p	18p	14p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	14p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	14p	14p	12p
7413	Dual 4-input Schmitt triggers	20p	18p	14p	14p	12p
7480	Dual 4-input NAND gates	20p	18p	14p	14p	12p
7483	Single 8-input NAND gates	20p	18p	14p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	14p	14p	12p
7441	BCD-Decimal decoder/Nixie driver	75p	75p	70p	60p	55p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	75p	70p	60p	55p
7443	Excess 3-Decimal decoder/TTL outputs	\$1.80	95p	90p	80p	70p
7447	BCD-Decimal 7 seg. decoder/indicator driver	\$1.75	\$1.80	\$1.45	\$1.30	\$1.15
7448	BCD-Decimal 7 seg. decoder/driver TTL O/P	\$1.75	\$1.80	\$1.45	\$1.30	\$1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7452	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7453	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7454	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7455	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7456	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7457	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7458	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7459	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7460	Dual 4-input expanders	20p	18p	14p	14p	12p
7470	Single J-K flip-flop (gated inputs)	20p	18p	14p	14p	12p
7472	Single J-K flip-flop (gated inputs)	20p	18p	14p	14p	12p
7473	Dual J-K flip-flop	40p	37p	35p	33p	30p
7474	Dual J-K flip-flop	40p	37p	35p	33p	30p
7475	Quad 2-input bistable latch	45p	42p	40p	38p	35p
7476	Dual J-K flip-flops with Preset and Clear	40p	37p	35p	33p	30p
7480	Quad Full Adder	80p	75p	67p	55p	50p
7481	16-bit read/write memory	\$1.25	\$1.15	\$1.10	\$1.00	90p
7482	2-bit binary Full Adder	87p	80p	70p	60p	50p
7483	4-bit binary Full Adder	\$1.00	90p	85p	80p	75p
7484	16-bit RAN with gated write inputs	745p	80p	85p	80p	75p
7485	Quad 2-input Exclusive OR gates	45p	41p	38p	35p	33p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	\$2.00	95p	90p	80p	70p
7492	Divide twelve counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	75p	70p	65p	60p	55p
7494	Dual 2-line 4-bit shift register	85p	80p	75p	70p	65p
7495	4-bit up-down shift register	85p	80p	75p	70p	65p
7496	5-bit parallel/in/out shift register	\$1.00	97p	95p	90p	85p
74100	8-bit bistable latch	\$2.50	\$2.30	\$2.00	\$1.75	\$1.50
74118	Hexapole Set-Reset latches	\$1.00	95p	90p	80p	70p
74121	Monostable multivibrators	60p	55p	50p	48p	41p
74141	BCD-Decimal decoder/Nixie driver	\$1.80	\$1.40	\$1.20	\$1.10	\$1.00
74145	BCD-Decimal decoder (4-10-line) TTL O/P	\$1.80	\$1.40	\$1.20	\$1.10	\$1.00
74150	16-bit data selector/multiplexer	\$3.35	\$3.20	\$2.85	\$2.15	\$2.05
74151	8-bit data selector/multiplexer	\$1.10	95p	90p	80p	70p
74153	Dual 4-line to 1-line data selector/multiplexer	\$1.35	\$1.27	\$1.20	\$1.15	\$1.10
74154	16-bit decoder/demultiplexer	\$2.00	\$1.75	\$1.55	\$1.30	\$1.05
74155	Dual 2-line to 4-line decoder/demultiplexer	\$1.55	\$1.47	\$1.35	\$1.10	\$1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	\$1.55	\$1.47	\$1.35	\$1.10	\$1.05
74190	Sync decade up-down counter, 1-line mode	\$1.85	\$1.85	\$1.75	\$1.60	\$1.50
74191	Sync 4-bit up-down counter, 1-line mode	\$1.85	\$1.85	\$1.75	\$1.60	\$1.50
74192	Sync decade up-down counter, 2-line mode	\$2.00	\$1.90	\$1.80	\$1.65	\$1.55
74193	Sync 4-bit up-down counter, 2-line mode	\$2.00	\$1.90	\$1.80	\$1.60	\$1.40
74196	Asynchronous presettable decade counter	\$1.80	\$1.70	\$1.60	\$1.40	\$1.30
74197	Asynchronous presettable 4-bit binary counter	\$1.80	\$1.70	\$1.60	\$1.40	\$1.30

Complete data on the above in booklet 20 pages, Ref. 29, 5p post paid. Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

INTEGRATED CIRCUITS

MPC4000P	55p
MPC4010P	55p
IC12	22.50
PA246	11.50
TAD100	11.50
TAD110	11.50
MC724P	50p
7902(TOS)	45p
7903(TOS)	45p
7909(D.I.L.)	45p
7230(TOS)	11.00
741C(TOS)	80p
MC1303P	22.00
MC1304P	22.50
IC1403D	11.50
741C(DIL)	75p
914(TOS)	40p
923(TOS)	40p
TO8HIBA	20 watt amp
TO8HIBB	20 watt amp
Pre amp	\$1.50

PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier

Complete with 8-pair sockets, circuits and data. **£1.50** ea.



BY FRANK W. HYDE

HIGH POWER IN THE IONOSPHERE

There are a number of areas where man attempts to modify his environment to suit his needs and the latest of these would appear to have a possible future effect on communication systems.

The new experiments in this direction have been made using a radio telescope, with a 1,000 feet diameter dish, located at Arecibo. The very high powers that have been used with this radio telescope dish have resulted in the heating of the *F*-layer of the ionosphere.

The idea that this might be possible has been talked about for a number of years. The writer was engaged in some of this work when the ITA television system was inaugurated. It was noticed then that when a high powered station was opened the transmissions appeared to become reduced in intensity after about three months.

Although a few people accepted that this was due to ionospheric modification the work was not pursued for lack of support. Now in the intense beam that is obtained with this giant dish, it is possible to follow up early ideas, particularly those put forward in 1970 by a team at Boulder, Colorado, using a very large aerial array.

The Arecibo dish has already established itself as a pioneer instrument. It confirmed beyond doubt the rotation period of Venus and also proved the correct rotation period of Mercury.

Since it is the largest dish in the world there have been many calls on its use by radio astronomers and the ionospheric teams have felt that they have been rather overshadowed by the astronomers. However, the dish may for a time at least revert to its original planned purpose which was the study of the ionosphere.

The author, W. E. Gordon, has made a preliminary report of what has been accomplished with the 100kW transmitter, which operates in the 5 to 10MHz band. The actual frequency of the experiments was 5.62MHz. It is possible to use the radar equipment at the same time as the "heater" transmitter. It is, therefore, possible to observe the effects of the high power on the ionosphere.

When the transmitter is switched on the temperature of the *F*-layer increases and airglow appears together with infra-red activity. The variation in heating is measured at 430MHz and a contour map plotted for changes of temperature. It is clear from these maps that plasma forms like a bubble some 100km in length and 50km across. Aligned with the magnetic field this rather cigar-shaped plasma shows a temperature rise of some 300° C over the normal temperature of the region which is of the order of 1,000° C.

Naturally such an area has a direct effect on communications since the reflecting property is affected. It may become a useful tool in the propagation conditioning of the ionosphere.

MARTIAN MOONS

Much speculation has been made about the inner Martian moonlet Phobos in the past, including a

suggestion that it was hollow or an artificial body, because of the low density that it appeared to have.


Since *Mariner 9* went into orbit around Mars on November 13 a raging dust storm had obscured the surface features of the planet. So scientists directed its television cameras towards one, then the other of the two martian moons. Some scientists regard Phobos and its sister moon Deimos as even more attractive research targets than Mars.


Of all the moons in the solar system, Phobos is the only one moving around its planet faster than the rotation of its parent body and no one has yet suggested a reasonable explanation for this unique behaviour, reminiscent of man-made satellites.

Both the satellites of Mars have now been photographed and the pictures of Phobos show it to be a rather miserable irregular chunk of rock. It is crater marked, with at least one huge crater, and its size is approximately 15 miles by 13 miles. The natural conclusion must follow that it is a captured asteroid.

During the journey towards Mars the probe photographed Deimos from a distance of 5,300 miles. It was described in the preliminary reports as being potato shaped, about 8 miles across and have groove like markings. The irregular shape is compatible with its small size.

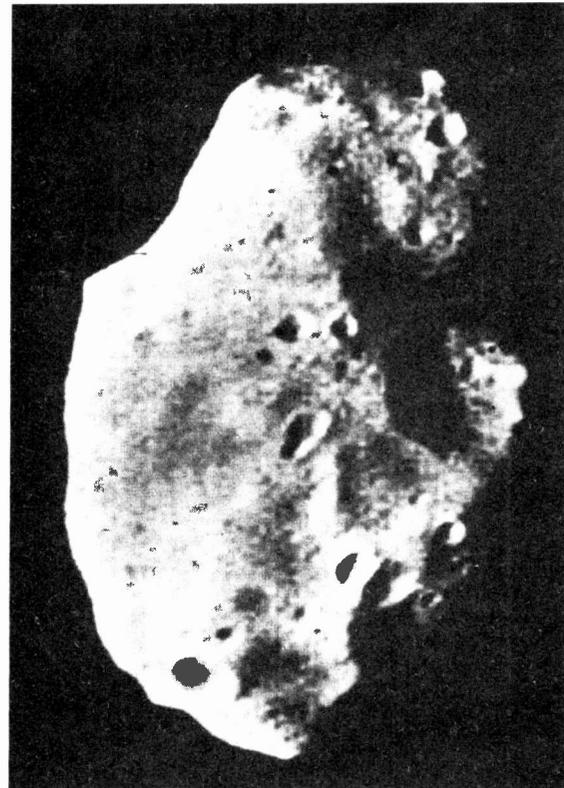Rugged surface features of the irregularly shaped Martian moonlet Phobos are visible in this computer enhanced photo. The photograph was taken by *Mariner 9* during the 34th orbit of Mars.



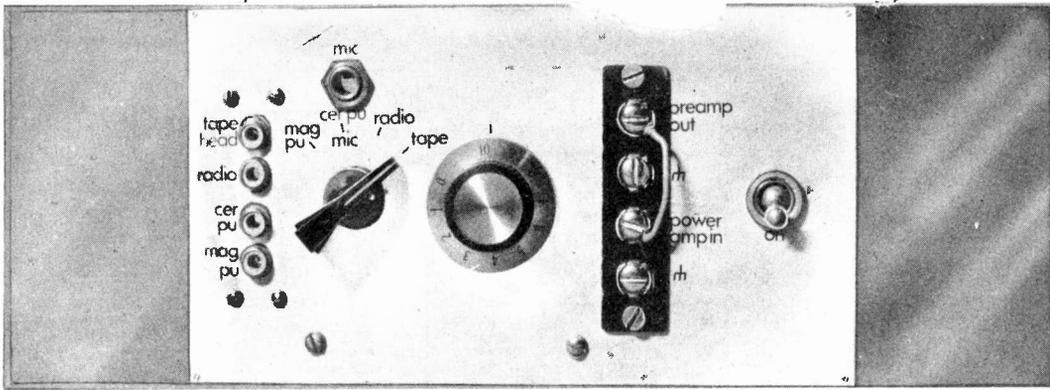

GENERAL PURPOSE AMPLIFIER

An experimenter's amplifier with input sensitivities to suit most bench requirements **By F. C. JUDD**

THE general purpose amplifier described in this article has inputs suitable for a wide variety of audio signal sources including those requiring special frequency-correction such as magnetic pick-up cartridges and tape heads. The amplifier can be split into two sections and operated (a) as a signal pre-amplifier and (b) as a small power amplifier, each being independently usable.

There are five input sockets and these can be used for the following signal sources:

(SK4) For all magnetic pick-up cartridges. Provides RIAA frequency response correction and has a nominal input sensitivity of 6mV at 56 kilohms.

(SK3) For ceramic or crystal pick-up cartridges of high impedance and output signal. The high input impedance provides the necessary equalisation for record replay.

(JK1) Input sensitivity is approximately 2mV. Suitable for microphones from 200 ohms impedance and upward.

(SK2) Suitable for radio tuners and/or tape record/replay units with linear output or any linear signal source of between 100mV and 500mV.

(SK1) Input sensitivity 5mV. Suitable for direct connection from medium impedance tape heads and provides a compromise CCIR/NAB replay characteristic.

The sixth possible input is direct to the output amplifier via the volume control. This will permit connection of linear signal sources in excess of about 500mV which would otherwise overload the pre-amplifier.

The power amplifier will deliver 3 watts r.m.s. power to any small loudspeaker of between 5 and 15 ohms and its input sensitivity via the direct input link to the volume control is 80mV for 3 watts output. The pre-amplifier will deliver 80mV from its link output terminal for the following input ratings:

Magnetic pick-up (SK4) 6mV 56 kilohms

Ceramic pick-up (SK3) 100mV 820 kilohms

Microphone (JK1) 2mV 100 kilohms

Radio (SK2) 100mV 120 kilohms

Tape head (SK1) 5mV 100 kilohms


THE CIRCUIT

The circuit is shown in Fig. 1. The inputs are selected by S1a and where necessary taken through suitable attenuation networks to TR1 which, with TR2, forms a direct coupled pre-amplifier. Negative feedback is used to control gain and/or equalisation and is taken from TR2 collector via the networks, and S1b to the emitter of TR1.

The pre-amplifier output is taken to the link terminal strip and then by VR1 (volume control) to the output amplifier. When the link is uncoupled the pre-amplifier output can be used to drive any other external amplifier. Alternatively, signals may be taken directly to the output amplifier by way of VR1.

The output amplifier itself is a fairly simple driver and complementary pair output arrangement and providing the specified components are used and the heatsinks are to the dimensions given, it requires no special adjustment or protection against thermal runaway.

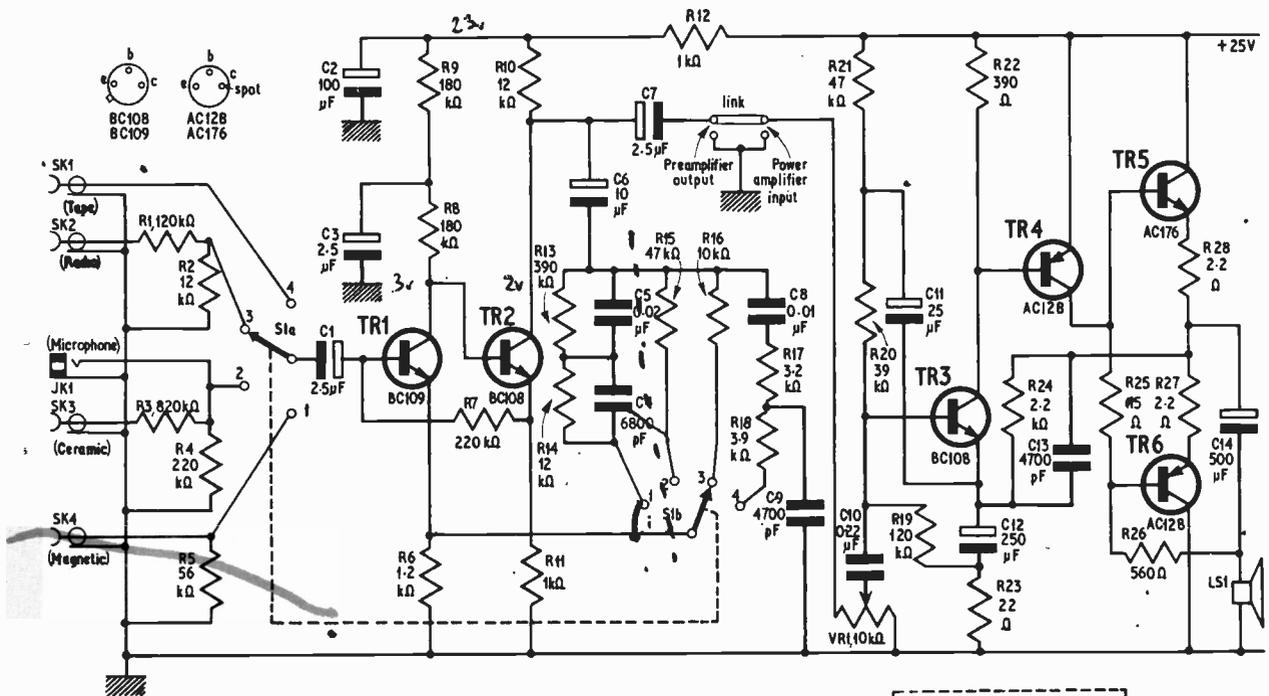The power supply employs a transformer with a centre tapped secondary delivering 13V either side. Note that only 13V are applied to the rectifier, that



COMPONENTS . . .

Resistors

R1 120k Ω	R15 47k Ω
R2 12k Ω	R16 10k Ω
R3 820k Ω	R17 3.2k Ω
R4 220k Ω	R18 3.9k Ω
R5 56k Ω	R19 120k Ω
R6 1.2k Ω	R20 39k Ω
R7 220k Ω	R21 47k Ω
R8 180k Ω	R22 390 Ω
R9 180k Ω	R23 22 Ω
R10 12k Ω	R24 2.2k Ω
R11 1k Ω	R25 15 Ω
R12 1k Ω	R26 560 Ω
R13 390k Ω	R27 2.2 Ω 2.5W
R14 12k Ω	R28 2.2 Ω 2.5W

All $\frac{1}{4}$ W, 10% carbon except where otherwise stated

Capacitors

C1 2.5 μ F elect. 16V	C8 0.01 μ F
C2 100 μ F elect. 40V	C9 4,700pF
C3 2.5 μ F elect. 16V	C10 0.22 μ F
C4 6,800pF	C11 25 μ F elect. 25V
C5 0.02 μ F	C12 250 μ F elect. 25V
C6 10 μ F elect. 25V	C13 4,700pF
C7 2.5 μ F elect. 16V	C14 500 μ F elect. 25V
	C15 2,500 elect. 40V

Transistors

TP1 BC109
TR2 BC108
TR3 BC108
TR4 AC128
TR5 AC176
TR6 AC128

Potentiometers

VR1 10k Ω carbon logarithmic

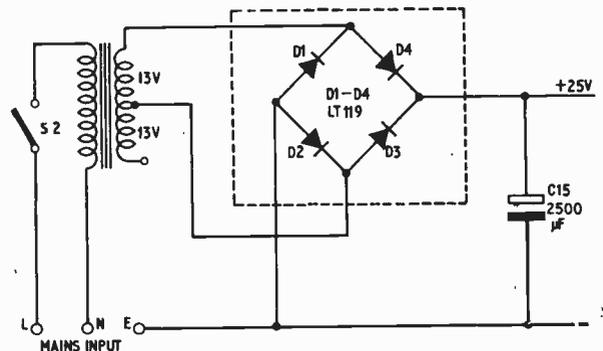


Fig. 1. Circuit diagram of amplifier and power supply

Switches

- S1 Double pole 4-way switch
- S2 Mains on/off toggle switch

Transformer

- T1 Mains transformer, 13-0-13V secondaries type TS2/13 (Henry's Radio)

Sockets


- SK1-SK4 Phono sockets (4 off)
- JK1 Standard jack socket

Rectifier

- D1-D4 Rectifier type LT119 (Henry's Radio)

Miscellaneous

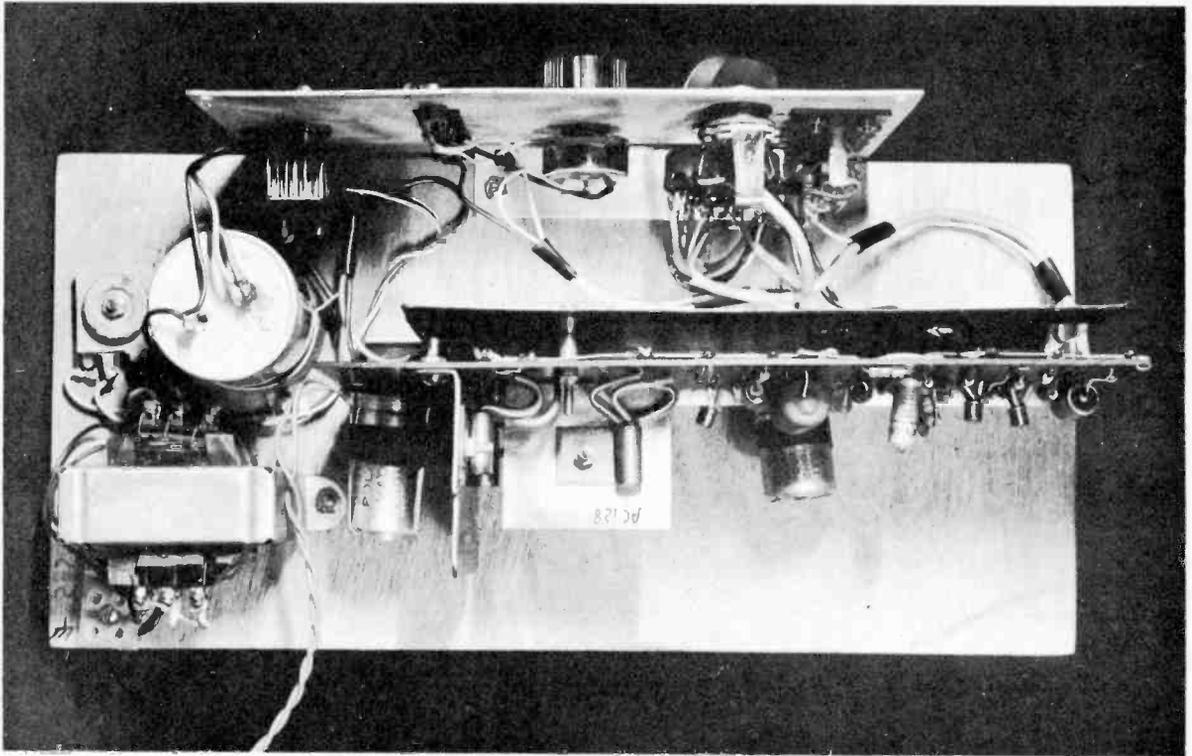Link terminals—4-way strip type TS64 (Henry's Radio), 0.15in matrix plain Veroboard $3\frac{1}{2}$ in \times 8in, heatsinks and copper transistor clips (3 off), 8in \times $\frac{3}{8}$ in aluminium angle. Plywood for base board and cabinet.



Baseboard assembly of amplifier control panel, component board and power supply. Note the use of aluminium heat sinks for mounting the output stage transistors and aluminium screening for the underside of the components board

is, only one half of the winding is used. This provides 25V d.c. to the amplifier which falls to approximately 22V when the power stage is delivering its full output.

CONSTRUCTION

The entire pre-amplifier and output stage can be assembled on a single circuit board as shown in Fig. 3. The input sockets, the selector switch S1, the link terminal strip and volume control, etc. are mounted on the control panel as in Fig. 2.

The transistors TR4, TR5 and TR6 are mounted on aluminium heatsinks with copper transistor clips. Do not cut the transistor leads and place a piece of sleeving over each to prevent short circuits. The circuit board is plain s.r.b.p. (0.15in matrix) which is mounted on an aluminium screen by means of stand-off spacers and 6B.A. bolts. The complete assembly is attached to the base board on a length of aluminium angle. The control panel is also mounted on the baseboard by similar means.

The lead from the common of S1a to C1 must be screened with the screen grounded at the component board.

PERFORMANCE AND TESTING

Before connecting check the output pair and driver transistor circuitry in particular as both *npn* and *pnp* transistors are used and it is quite easy to connect them wrongly with obvious results. It is

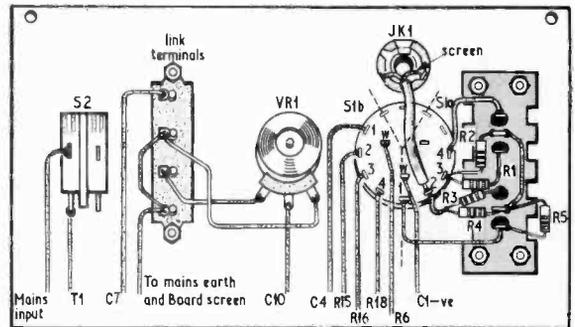


Fig. 2. Component layout and wiring of amplifier control panel. Apart from S2 all flying leads should be routed to the component board

also worth checking the power supply before connecting the positive line to the amplifier and make sure that 25V only are available.

The quiescent current of the amplifier with no signal input should be approximately 22mA. At maximum r.m.s. power output the current will rise to about 200mA and the rail volts will fall to about 22V. The amplifier is quite safe with the speaker disconnected but do not short circuit the speaker terminals whilst power is being developed.

AMPLIFIER CIRCUIT BOARD



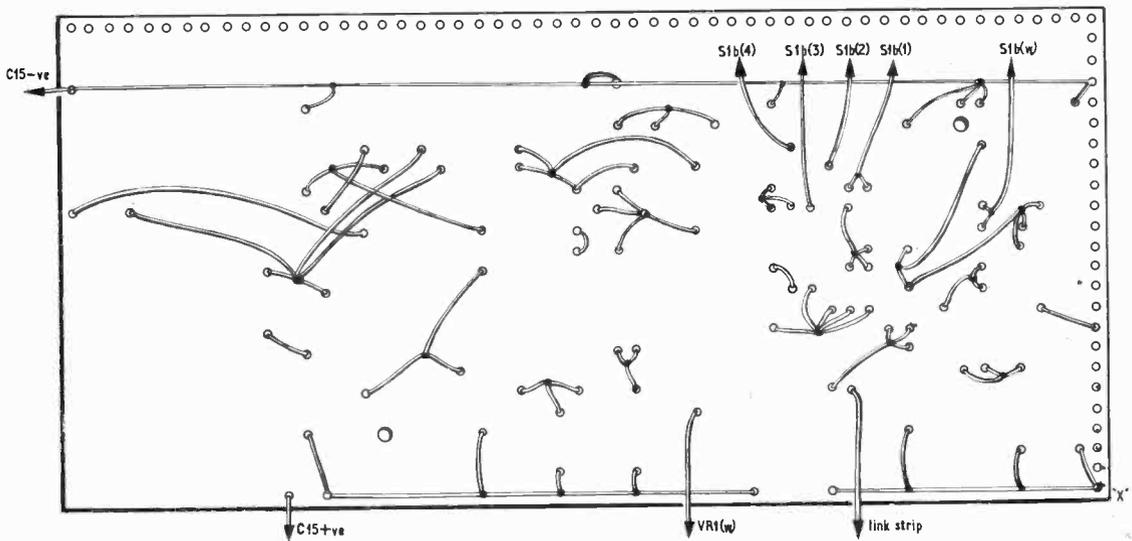


Fig. 3. Board layout and wiring of pre-amplifier and output stage

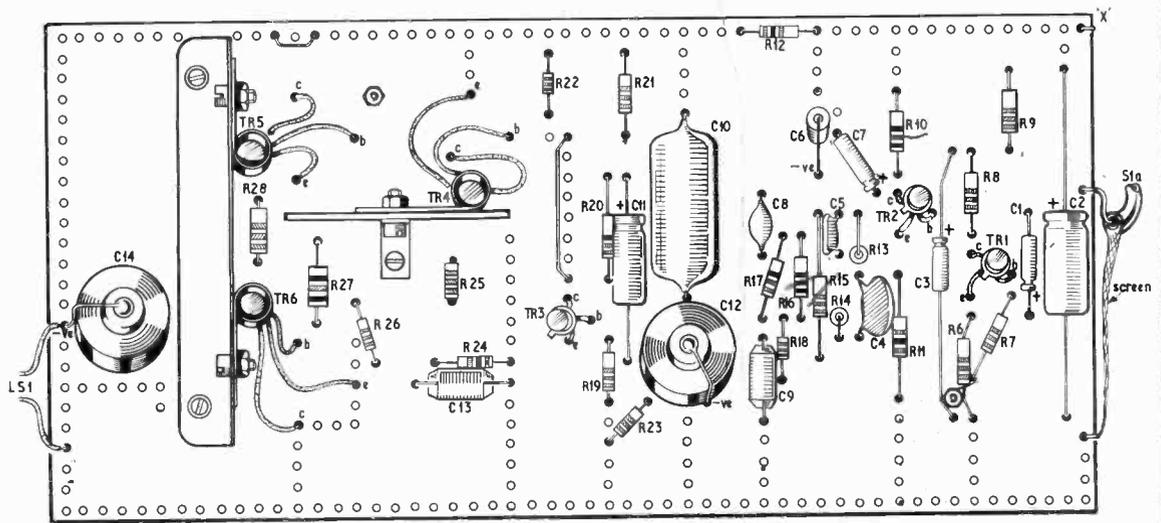

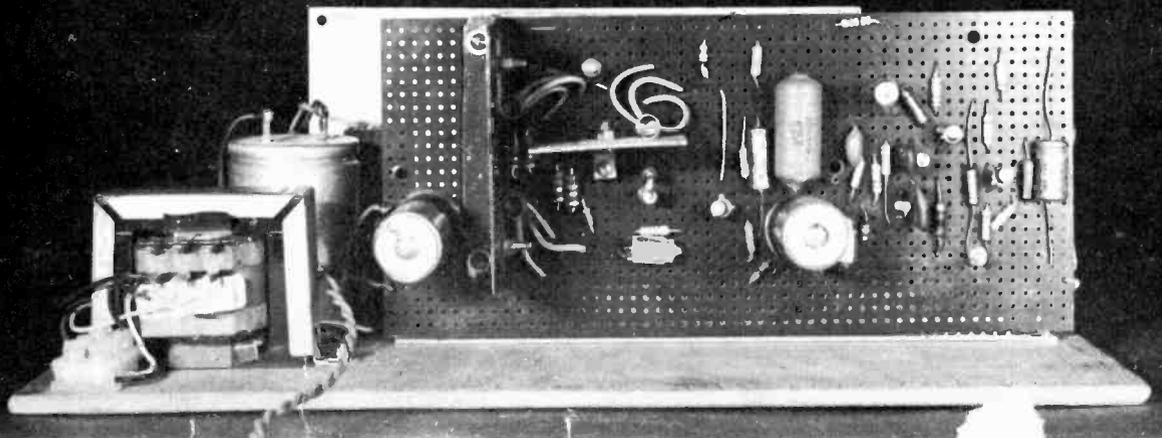

The amplifier being used to check a record deck. One of the many bench applications of the unit

If possible the signal input sensitivities should be checked but providing the circuit has been correctly wired these should comply with the figures given.

The frequency response of the power stage is given in Fig. 4 but can be extended a little at the low frequency end by doubling the value of the output coupling capacitor C14, that is, making this 1,000 μ F. The same graph shows the response from

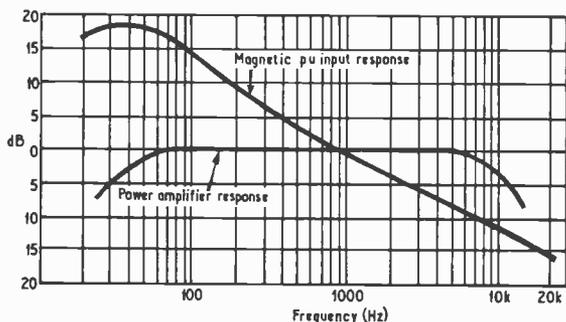


Fig. 4. Graphs of magnetic pick-up and frequency responses

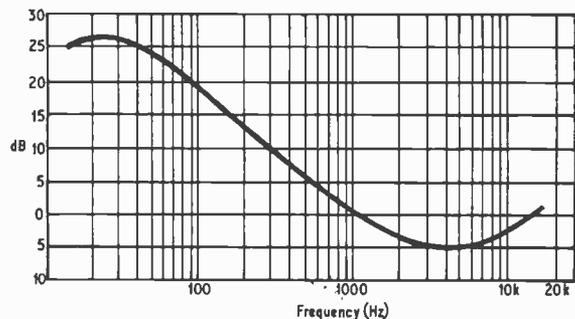


Fig. 5. Tape head input frequency response

the magnetic pick-up input which is to RIAA characteristic. The response from the tape head input (Fig. 5) is between CCIR and NAB characteristics and provides a replay response more in line with that used on modern domestic tape recorders. It is suitable for tape speeds of 7½ and 3¼ inches per second.

The combined response of the pre-amplifier and power amplifier for radio or microphone input is as shown in Fig. 4 although the response of the pre-amplifier by itself is considerably wider and extends down to 20Hz and to well above 25,000Hz. The hum and noise level for the complete amplifier is better than -60dB for all inputs.

A SUITABLE CABINET

The cabinet size or shape is not critical and it need be only large enough to accommodate the amplifier and a loudspeaker which may be any round or elliptical type capable of handling 3 to 4 watts of audio.

APPLICATIONS

The amplifier has many applications as a bench testing instrument for audio signal sources of all kinds and could be duplicated for stereo reproduction with the second channel run from the spare 13V mains transformer secondary with an extra rectifier and smoothing capacitor. The circuit could also be used for a small record player in which case the switching and components for unwanted inputs need not be included. For example, for a mono record player with a ceramic or crystal pick-up the switch S1 is omitted, the collector of TR2 coupled back to the emitter of TR1 via C6 and R15 and the input taken via R3 straight to C1 with R4 connected from R3 to earth as shown. The link terminals would not be necessary so C7 would be connected straight to the top of VR1.

One final point. It may be found worthwhile to place a screen (thin tinplate or aluminium) underneath the baseboard and connect this to common earth to prevent hum pick up particularly from bench mains wiring.



POINTS ARISING

I.C. DIGITAL DICE (December 1971)

There should not be a connection between gate output G6 and common, that is P14 and P15 on the Veroboard layout.

P.E. SCORPIO IGNITION SYSTEM (November, December 1971)

See letter on Readout page 248

PHOTOPRINT PROCESS CONTROL


(January 1972)

Components List page 26. TR5 should be type 2N2926G.

Fig. 2 page 24. R16 is 3.3 ohms or 6.8 ohms as in the Components List.

FS1 could be a 1A anti-surge fuse for better protection.

BUDGET HIGH-FIDELITY STEREO SYSTEMS

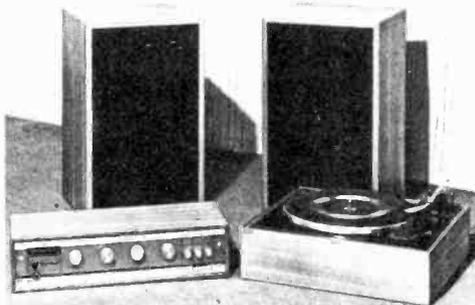

PREMIER STEREO SYSTEM "ONE" consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player and fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch, Headphone socket. Power on/off. Black leatherette cabinet with aluminium front panel. Size 12½in x 6½in x 2½in. (Amplifier available separately if required £18-25. Carr. 40p.)

PREMIER STEREO SYSTEM "TWO", as above but with Garrard SP25 Mk. III and magnetic cartridge. **ONLY £48.** Carr. £1-75.

ONLY £57-75
carr. £1-75

PREMIER STEREO SYSTEM "THREE." This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pick-up, tuner, tape in and out. Stereo earphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of HMP Speakers size 10½in x 10½in x 9in fitted EM1 units complete the matching system. **ONLY £57-75.** Carr. £1-75.

ONLY £40-95
carr. £1-75

FREE
all leads and plugs supplied free with all systems

PREMIER HI-FI OFFERS!

- Philips 580 Stereo Amplifier (List £29-00) **£23-00**
- Rogers Ravensbrook 11 Stereo Amplifier in teak case (List £52-50) **£39-50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £84) **£49-00**
- Metrosound ST20E Stereo Amplifier in teak case (List £39-50) **£28-50**
- Goldring GL75 less cartridge (List £41-61) **£29-00**
- Garrard SP25 111 with Goldring G800 cartridge (List £28-35) **£15-50**
- Garrard AP76 less cartridge **£19-50**

Garrard 401 Transcription Unit (List £40-15) **£29-00**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£12-45**

Carriage and Insurance 50p extra any item.



TAPE CASSETTES

C60 (60 min.)	37p	3 for £1-05
C90 (90 min.)	62p	3 for £1-80
C120 (120 min.)	87p	3 for £2-55

P. & P. 5p

FREE Cassette Head Cleaner with every 10 cassettes purchased
All cassettes can be supplied with library cases at 3p extra each.

SP25 Mk III SPECIAL!



Garrard SP25 Mk. III Single Record Player. Fitted Goldring G800 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Perspex Cover.

Total list Price over £34.

PREMIER PRICE £18-90
P. & P. 50p



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft lead and stereo jack plug. **£2-47** P. & P. 25p


STEREO STETHOSCOPE SET Low imp. **£1-25.** P. & P. 10p
MONO STETHOSCOPE SET Low imp. **52p.** P. & P. 10p

E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2½in tweeters and crossover network. Available with 8 or 15 ohm impedance. Handling capacity 10W. Brand new. **£3-47** P. & P. 40p

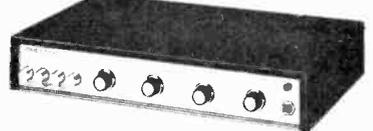NEW LOW COST PREMIER 800 STEREO AMPLIFIER



A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000Hz ± 2db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Mono/Stereo switch. Stereo Headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½in x 6½in x 2½in.

ONLY £16-25 Carr. 40p



"WELLER EXPERT" SOLDER GUN

Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat 100/140 watt. 240 volt A.C. **£4-25** P. & P. 30p

"Weller Marksman" Soldering Iron Lightweight, ½in pencil bit, 25 watt. 240 volt A.C. **£1-50 P. & P. 15p**

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3'	250'	P.V.C.	28p	LP6 5 1/2'	1200'	P.V.C.	75p
TT3 3'	450'	POLYESTER	37p	DT6 5 1/2'	1800'	POLYESTER	£1-12
DT3 3 1/2'	600'	POLYESTER	57p	TT6 5 1/2'	2400'	POLYESTER	£1-37
SP5 5'	600'	P.V.C.	42p	SP7 7'	1800'	P.V.C.	62p
LP5 5'	900'	P.V.C.	57p	LP7 7'	1800'	P.V.C.	75p
DT5 5'	1200'	POLYESTER	75p	DT7 7'	2400'	POLYESTER	£1-25
				TT7 7'	3600'	POLYESTER	£2-50

TAPE SPOOLS 3" 5p, 5 1/2" 51", 7" 9p.
Post and Packing 3" 5p, 5 1/2" 8p, 7" 10p. (3 reels and over Post Free.)



PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



NEW

from Goodmans for constructors


Din 20 Kit

20 watt, high fidelity loudspeaker kit contains all parts necessary to complete the system, except timber and other material for the cabinet itself, with detailed, illustrated instructions.

Specification: 20 Watts DIN, 4 ohms impedance, 8 ins bass unit, dome HF radiator, crossover frequency 4,000 Hz.




Axent 100

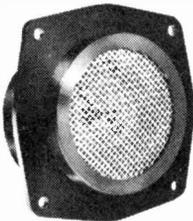

Dome HF Radiator with integral crossover. Capable of high frequency sound reproduction with negligible distortion in systems rated up to 30 Watts DIN, this 'state of the art' drive unit has an integral crossover which cuts frequencies below 3kHz at a rate of 12dB/Octave.

Audiom 100

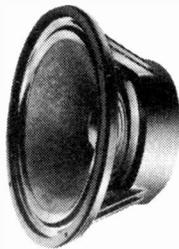12 inch high fidelity bass loudspeaker. For use as a bass unit in two-way systems, the sensitivity and high frequency roll-off of the Audiom 100 has been tailored to match the Axent 100.



Goodmans

Sound reasoning.

THORN A member of the Thorn Group

Please send Free leaflets on Constructors Equipment

Name

Address

PE2

Goodmans Loudspeakers Ltd.,
Downley Road, Havant, Hampshire PO9 2NL

SAVE UP TO £10

on the Boots Audio System now!*



The amplifier is fitted with controls for treble, bass and stereo balance and a special contour control. Power output 4 watts.
The deck made by Philips has autochange and single-play facility, with a manually operated pick-up lift, ceramic cartridge, diamond stylus and transparent dust cover.
The Loudspeakers are 6½" dual cone high flux units.
The Mono Radio Tuner covers VHF, Medium and Long Wavebands. Mono but stereo convertible if required. Mains powered. (can be purchased separately).

This Unit Stereo and Mono Radio Tuner are the components of the popular Boots Audio System. • Now you can buy them both for only £67.90 instead of £77.90. • Or separately – The Unit Stereo normally £52.90 is now £47.90 a saving of £5. • The Radio Tuner, normally £25 is now £20, a saving of £5.

And you can be sure you're getting good value for money. This superb Audio System is normally great value at £77.90.

It has up-to-the-minute styling, using electronically matched components to provide outstanding performance.

Such an excellent bargain can be yours for just £67.90. And once you've come along to a Boots Audio and Record Department you'll find lots of interesting things to delight the music lover. But don't delay because the offer ends on March 11th.

*These special offers are available from Boots Audio and Record Departments, while stocks last from Jan 31st to March 11th.



Connoisseur

S.A.U. 2 Pickup Arm


Recognised as one of today's most advanced pickup arms it features:



- * Auto-bias Compensator
- * Precision Balance
- * Hydraulic Lowering Device
- * New Adjustable Head Shell

S.C.U. 1 Stereo Cartridge

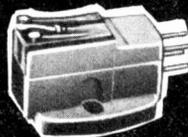
A quality cartridge designed specifically for the person who appreciates his equipment.



Precision Stylus Balance

An inexpensive and useful gift for the hi-fi enthusiast. It's simplicity itself to work out and adjust the weight of the stylus so as to give correct working

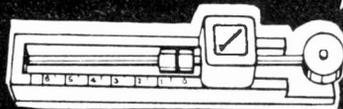conditions and perfect results. Covers a range from 0-6 grams with 1 gram calibrations.



A.R. SUGDEN & CO. (ENGINEERS) LTD.

Market Street, Brighouse HD6 1DX, Yorkshire. Telephone: 2142.

PICK UPS.....

& TURNTABLES

Whether you are a hi fi fanatic with an ultimate desire to reproduce recorded sound at its very best, or just an average person who likes music around the house without being too particular about the techniques or finesse of the result, this supplement has been devised to explain some of the more important points about pickups and turntable units that most users may meet.

That equipment used to rotate a recorded disc and detect the recorded signal is sometimes called (a) a record deck; (b) a transcription unit; (c) an autochanger; (d) turntable and pickup. A record deck is the general term applied without any implications of quality. A transcription unit has by convention implied high quality often with the finest performance currently available. An autochanger is a record deck with extra mechanisms to change the disc at the end of replay and operate the pickup on and off the disc.

Whatever class of equipment interests you, it is fairly certain that manufacturers' literature will offer you some or all of the important technical features that you will wish to know to assess the value-for-money factor of your intended purchase.



Philips GA308 record deck



Transcription turntable Thorens TD124 Series II and SME 3309 Series II pickup arm with rest, side thrust correction weight, counterbalance weight at the rear and tracking weight on the side



Garrard autochanger AT60 Mk II

BEFORE going into characteristics individually let us first consider the equipment as a whole. The sensitive element, which translates information stored in the disc groove is a transducer—frequently called a cartridge. Its function is to generate electrical signals from vibrations of a stylus caused by varying patterns of modulation in the groove wall. The principles are the same for mono (single channel) or stereo (dual channel);

recordings. The significant difference is the direction in which the stylus is vibrated and the relationship between the signals derived as will be explained later.

The cartridge is fitted to the underside of the pickup head, which may or may not be detachable from the pick-up arm. A modern cartridge usually carries two holes or slots in its mounting with a "standard" pitch of 0.5in for securing to the head shell.

The motive power to rotate the disc is provided by a synchronous motor driven turntable operated from an a.c. mains supply.

The translation of the recorded information into an electrical signal is loaded with mechanical and electrical problems, although current engineering practice has enabled the designer to master them. Extremely high quality reproduction from disc is now possible in two and four channels.

HOW THE STEREO PICKUP WORKS

As is well known, sound signals recorded monophonically or from a centre-stage sound source causes the replay stylus to vibrate laterally. See Fig. 1a.

In the case of two-channel stereo records, the two walls of a V-shaped groove are modulated independently (Fig. 1b). The wall nearest the centre of the disc carries the left channel information; the other carries the right channel information.

Depending on the phasing between the left and right signals, the replay stylus vibrates laterally when there is only mono or centre-of-stage stereo information (Fig. 2d), indicating in-phase conditions; and towards the vertical when the stereo information is at a maximum (Fig. 2c), indicating anti-phase conditions. Intermediate phase conditions result in different angles of vibration (Figs. 2a and 2b).

Some of the latest "four channel" or quadraphonic discs carry hall ambience effects in one or two rear channels by the phasing interplay between the front left and right channels, with the rear channels being derived from anti-phase information. The four channels are matrixed into the two channels of the disc, so that when

four-channel replay is required a corresponding decoding matrix is adopted, the disc replaying in normal two-channel stereo.

Another scheme is based on the front two channels being recorded almost normally, with the two rear channels introduced by frequency modulated signals with sidebands extending to some 50kHz. This is called the "discrete" system because the four channels are handled in isolation throughout.

At the time of writing there is no quadrophonic disc standard, but ideas on both methods exist, with variations of the former.

Compatibility is one key note, which refers to the ability of the four channel system to replay in stereo or, indeed, in mono with minimal loss.

Correctly balanced mono replay from stereo discs is achieved by using a mono cartridge or a stereo type with the two channels correctly phased in parallel or series into the single replay channel. However, the stylus assembly must be endowed with adequate vertical compliance to avoid the inertia of the whole pickup from trying to follow the vertical vibrations of the stylus!



Fig. 1a. Stylus tip in a mono recording groove; first half-cycle



Fig. 1b. Stylus tip in a mono recording groove; second half-cycle

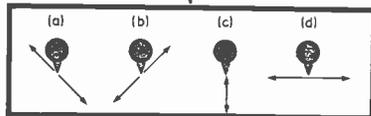


Fig. 2. Modes of stylus vibration. (a) left channel, (b) right channel, (c) equal left and right in anti-phase, (d) equal left and right in-phase

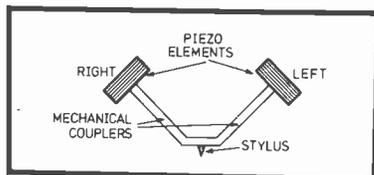


Fig. 3. Elementary features of a piezoelectric stereo cartridge

PIEZOELECTRIC PICKUPS

The pickup transducer is most frequently an electromagnetic or piezoelectric generator, the latter using Rochelle salt or ceramic elements. Fig. 3 shows the essential features.

Rochelle salt crystal has the advantage of providing high output, having a high dielectric constant and hence high capacitance and relatively high compliance. Unfortunately it suffers the disadvantages of distortions due to moisture and temperature sensitivity.

Ceramic, on the other hand, is impervious to atmospheric conditions, is capable of a better frequency response than Rochelle salt, but has a smaller output.


Rochelle salt crystal pickups have now been largely superseded by ceramic types and are employed mostly in the mass market type of equipment. The high output, sometimes 1V or more, can cut amplification costs, and in some low priced equipment the power amplifier stage is driven direct from the crystal pickup.

Typical ceramic pickup output is 50 to 100mV, and was used extensively at one time in budget price systems, but now that the better performance of magnetic pickups can be obtained for little more than the price of some ceramic types, the latter are tending to lose favour.


Since the output of a piezoelectric pickup is roughly proportional to the amplitude of modulation, it can be used when correctly loaded without equalisation, which can reduce the cost of the amplifier.



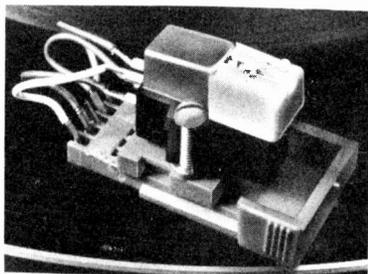Acos Crystal cartridge GP91-1SC for single channel (mono) replay of stereo or mono recordings



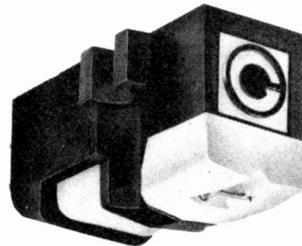Audio-Technica AT-55 cartridge fitted into a headshell. Notice the mounting screw on the near side



The Goldring G800 induced field cartridge. Also uses the variable reluctance principle

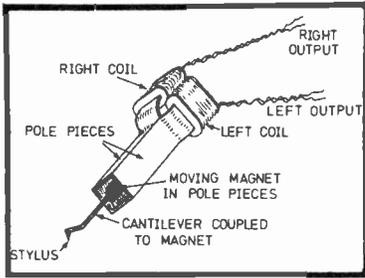


Fig. 4. Moving magnet cartridge showing the stylus coupling

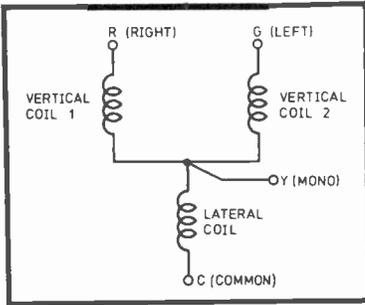


Fig. 5. Coil system of the Decca sum-and-difference pickup

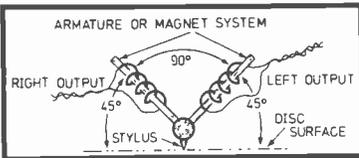


Fig. 6. Showing how the left and right generators are independently operated by the 45/45 stereo cut


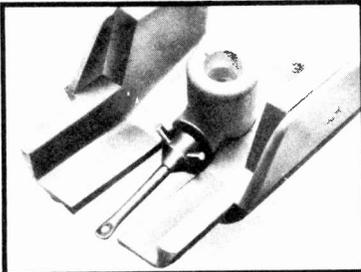


Fig. 7. The V magnet system on the end of the cantilever corresponds to the 45/45 stereo cut. This is from the AT35 Audio-Technica cartridge

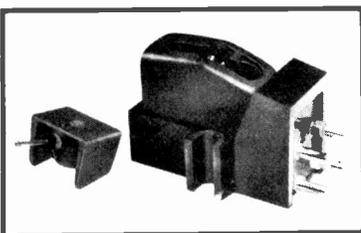

Most magnetic cartridges are designed so that the stylus assembly can be removed from the main body for cleaning or replacement. This is the Audio Technica AT35

MAGNETIC PICKUPS

Magnetic pickups come in a diversity of types, although all of them exploit the basic electromagnetic principle (Fig. 4). Most common types are moving coil, moving magnet and variable reluctance, where a ferrous armature vibrates between "magnet" pole-pieces. Induced current can be excited in either a field coil (moving magnet) or armature coil (moving coil) by stylus vibrations.

When the field is provided by a magnet which is not in contact with the pole-pieces, the term "induced magnet" is sometimes adopted, as

the field is coupled to the micro-mass armature.

Magnetic pickups produce an output proportional to the velocity of the modulation. Since this modulation is recorded on a rising characteristic (i.e. bass cut and treble boost), corresponding approximately to constant amplitude characteristics, equalisation is required at the amplifier. This should be designed to correct the frequency response of the reproduced sound signal. Typical output is a little over 1mV per cm/s velocity.

SUM-AND-DIFFERENCE PICKUP

One type of magnetic pickup is based on the variable reluctance principle, but employs a set of three coils from which the two stereo signals are obtained. The coils of the Decca sum-and-difference pickup are shown in Fig. 5.

Signal e.m.f. in the three coils is the same when there is modulation in one channel, but the phasing of the coils is such that the sum of the signals in right vertical coil 1 and the lateral coil appears across terminals C and R when the right channel is modulated. There is theoretically zero output from the left channel, between C and G, because the signal in vertical coil 2 is in phase opposition with that in the lateral coil, thus giving the difference function. In practice, however, a very small signal is obtained due to the crosstalk factor through leakage from other

coils.

When the other wall is modulated, the right channel is quiet and the signal in coil 1 is in phase opposition to that in the lateral coil. When both left and right are modulated together, the two stereo signals are delivered with minimal interaction between them. The Y terminal allows the lateral coil only to be used for mono replay. (Codings R, G, and Y usually refer to colours of the connecting lead, i.e. red, green, yellow. Common C is the screen.)


Other cartridges employ a pair of generators with their motional axes in V formation to correspond to the 45/45 stereo cut, where each channel is recorded 45 degrees to the surface of the disc and at right-angles to each other (Fig. 6). Sometimes the moving magnet is arranged in V formation, as shown in Fig. 7.

OTHER PICKUPS

Other pickups include one based on the photoelectric principle, where a small lamp is focused on photoelectric diodes and the stylus vibration is caused to modulate the light on the diodes. Another is based on the strain gauge principle, where d.c. is modulated by the vibrating stylus.

One uses ribbon instead of a moving coil, as in a ribbon microphone. This, as with the moving coil type, requires a booster amplifier or step-up transformer.

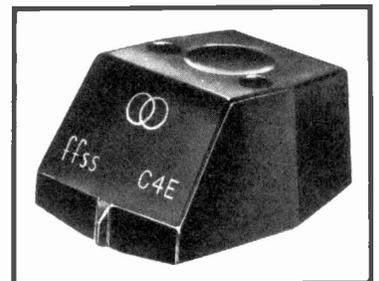Other transducer principles have been adopted, and there would appear to be an increasing interest in the electrostatic principle, resulting in the capacitor pickup.



Pickup head by Decca. This is based on the sum-and-difference principle

Audio Technica AT 1005/II pickup arm



PICKUP CHARACTERISTICS

LOW FREQUENCY RESONANCE

One problem of arm/transducer matching is low frequency resonance (i.e. the natural tendency for vibration to be excited at a particular frequency related to the characteristics of the component). This results from the dynamic mass of the arm resonating with the compliance of the stylus assembly.

The electrical analogues of mass and compliance are inductance and capacitance, so not unnaturally the resonance frequency (f_0) is equal to $1/(2\pi\sqrt{MC})$, where M is the mass and C the compliance. Thus the greater is M or C the lower will be f_0 .

At resonance the vibrations tend to magnify, as also does the pickup output, while below f_0 a high-pass filter effect occurs, in which the bass response tends to roll-off (Fig. 8).

Thus if the MC combination results in f_0 being too high the bass response suffers, while a too low f_0 encourages unstable tracking, the stylus tending to leave the groove when the resonance is excited by external vibration, such as someone walking across the room.

Moreover, if f_0 corresponds to the

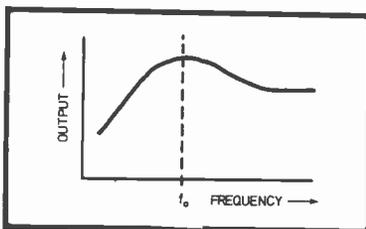


Fig. 8. Below bass resonance the output rolls off, an effect which is sometimes exploited for attenuating rumble

resonance of another connected component, such as a loudspeaker in a room, acoustic feedback can lead to howl build-up as the amplifier's volume control is advanced. If f_0 falls near the slip frequency of the drive motor (22.5Hz), turntable rumble could be aggravated. Thus it is seen that not all heads or cartridges will work with all arms without some problems arising.

Fortunately, hi fi cartridges and arms are to some extent designed for each other. Arm mass is being made as low as practicable, while stylus compliance is being made as

high as practicable. However, by going too far in these directions, other problems arise, such as inability to track properly; a proper balance between these two factors is very important.

It is known that at least one manufacturer reduced the compliance of a popular cartridge so that it could be used with budget auto-changers and decks. Consequently, high and low compliance models may be available to cater for high quality adjustable arms and medium class mass produced pickups.

In some cases i.f. resonances are tamed by arm decoupling (compliant couplings) and sometimes by viscous damping.

An f_0 between 8 and 20Hz is fairly safe, but calculation is not easy before purchase because the manufacturer's published specification rarely includes the effective mass. Mass is not the same as weight which is counterbalanced, with just sufficient turned on to the head end for tracking the groove. Nevertheless, the majority of hi fi arms will partner the best cartridges without trouble.

FREQUENCY RESPONSE

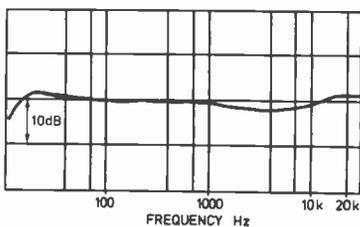


Fig. 9. Frequency response of top-flight magnetic cartridge. The mild 5.6kHz droop is normal with magnetic types

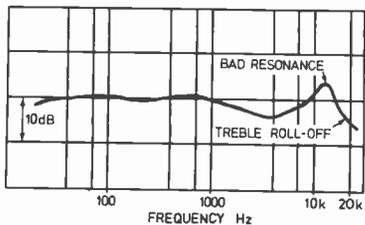


Fig. 10. Cartridge with bad h.f. resonance, possibly due to the mass at the cantilever end removed from the tip resonating with the cantilever compliance

Specifications which merely give a frequency range without reference to a nominal power level deviation of undistorted signal should be treated with suspicion. Correct frequency response relates output to frequency over the audio spectrum and usually extends beyond aural sensitivity (Fig. 9). Both channels should match very closely at all frequencies for good stereo listening quality. A good cartridge should be free from violent peaks in its characteristic which could signify undesirable resonances, particularly at the treble end.

One treble resonance is caused by the effective tip mass resonating with the compliance of the disc material (rather like a violin bow on a string), which has a value around 3×10^{-8} cm/dyne. The lower the tip mass, therefore, the higher the resonant frequency.

A low tip mass is essential for good tracking of high acceleration modulation, and a mass of 1mg or less would put the resonance outside the audio passband. However, the resonant frequency can be lower due to the mass at the end of the cantilever remote from the

stylus tip and the compliance of the stylus lever arm.

High frequency resonances yield significant energy which can damage the groove walls and hence the modulation; moreover, h.f. resonance also results in acute treble roll-off (Fig. 10). This characteristic is typical of the cheaper crystal pickups at one time common on mass produced equipment.

H.F. resonances also show up on the separation curves at close or corresponding frequencies. Internal damping reduces the mechanical Q factor and hence diminishes the peaks, thereby resulting in a "smoother" frequency response, but the intrinsic faults remain.

Many magnetic cartridges, especially those of current variable reluctance and moving magnet design, exhibit the droop around 5 to 6kHz (Figs. 9 and 10). The effect is not significant and can be tolerated since it is gradual and not a violent resonance.

Piezoelectric cartridges in general have less smooth frequency responses than magnetic cartridges.

AND PERFORMANCE

MEAN OUTPUT VOLTAGE

The output is related to velocity of modulation, usually at 1 or 5cm/s at 1kHz. Each channel should yield the same output within 1dB (even closer in top quality pickups). An average moving iron magnetic cartridge would be expected to produce about 6mV from 5cm/s, both r.m.s. values.

Moving coils and ribbon types will generate a mere 100 μ V, which is why a booster or step-up trans-

former is required. Due to this lower sensitivity and the limitations in the frequency response of small transformers, these latter types tend to lose favour.

Crystal cartridges can generate as much as 1V r.m.s. from average modulation, but better class ceramic types settle for about 20 to 50mV, with a smoother frequency response characteristic over the whole audio range.

STEREO SEPARATION

A stereo cartridge specification should give the channel separation at 1kHz or at two other frequencies. Good magnetic types often have a ratio as high as 25dB at mid-spectrum, falling possibly to 15 or 20dB at 100Hz and 10kHz.

Maximum stereo impact occurs at mid-spectrum, so the separation here must be as high as possible, but lack of stereo image stability can result if the separation ratio changes too violently in the upper treble regions.

The separation curve of a good

magnetic cartridge is given in Fig. 11, where the mid-spectrum separation is better than 25dB. Notice the mild "ripples" at the top treble end which signify well damped resonances.

It is difficult to check cartridges with separation better than 30dB owing to the disc replay noise in the "non-speaking" channel approaching the level of the breakthrough signal.


Piezoelectric cartridges have less exacting separation characteristics than most magnetic cartridges.

LOADING

Correct cartridge loading is important for the best frequency response, and the optimum load is generally given in the specification. Most magnetic cartridges work best into about 47 kilohms, the treble lifting if the load impedance is too high and drooping if it is too low (Fig. 12).

Piezoelectric cartridges, on the other hand, are load sensitive at the bass end. This is because they are capacitive in source, a high pass filter effect thus occurring when the load is too low (Fig. 13).

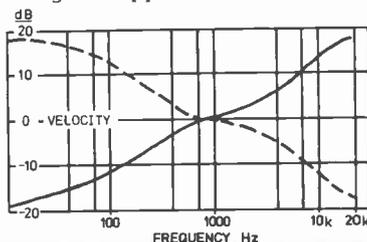Good ceramic types usually demand a load impedance of at least two megohms for extended bass response; to secure a reasonable overall frequency response from the RIAA recording characteristic inbuilt equalisation is often incorporated. The full-line curve in Fig. 14 approximates the RIAA





recording characteristic, which is projected to the amplitude modulation characteristic in Fig. 15, this clearly revealing the need for piezoelectric type of equalisation.

A piezoelectric cartridge can be made to approximate velocity characteristics by loading with a low value resistor (about 33 kilohms), the output then being similar to that of a magnetic cartridge, allowing the normal magnetic equalisation to be used.

Care is necessary, though, to avoid the relatively high output from overloading the RIAA equalised preamplifiers and causing bad distortion on signal peaks. This is not the best way of using ceramics.

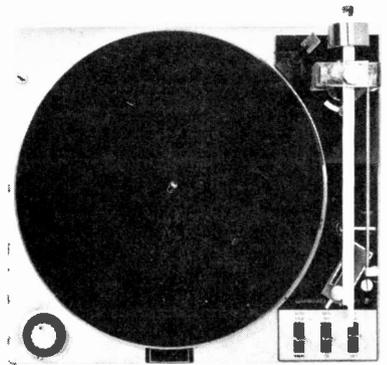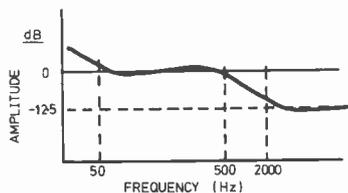Capacitance in shunt with the load has virtually no effect on piezo cartridges, but it can affect the treble response of magnetic types, especially when the coil



An example of the parallel arm type of pickup, the Garrard Zero 100. The head is pivoted to both arms to maintain tangential tracking

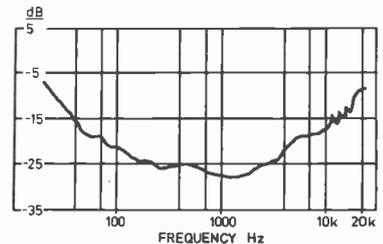


Fig. 11. Separation characteristics of a good magnetic cartridge. The mild ripples at the treble end signify well controlled resonances.

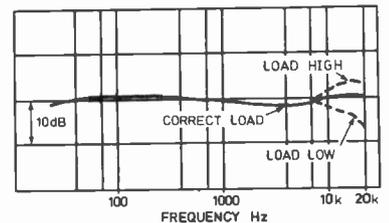


Fig. 12. Effects of incorrect loading of a magnetic cartridge


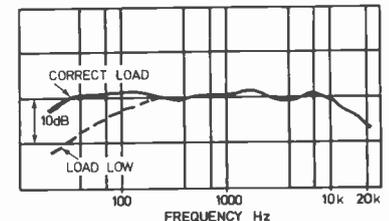


Fig. 13. Effect of incorrect loading of piezoelectric cartridge


inductance (another parameter that might be specified) is high, and incite electrical resonance with the coils within the passband.

Fig. 14 (far left). RIAA recording characteristic in full-line. The broken-line curve shows the equalisation required in the amplifier


Fig. 15 (left). The RIAA velocity recording characteristic projected in terms of amplitude. This shows the need for inbuilt equalisation of a piezoelectric cartridge.

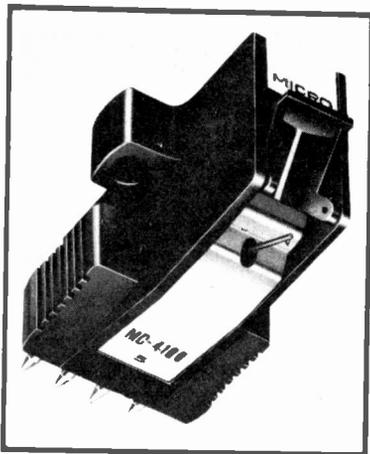

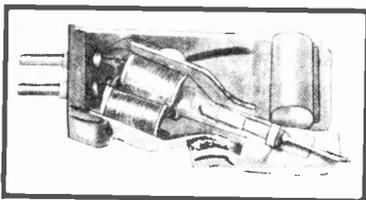Micro-Seiki MC 4100/5 cartridge with 0.5 thou radius diamond stylus



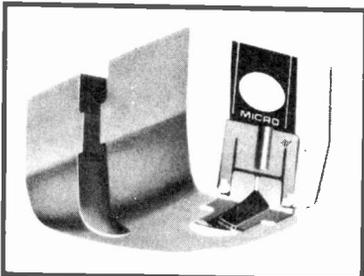Artist's sectional view of the Audio and Design induced field cartridge



Magnetic cartridge which has a removable stylus assembly

BEARING FRICTION

The lower the vertical and lateral bearing frictions the better, and to reap the full advantage from a low tracking weight cartridge they should not exceed much more than the equivalent of 50 dynes force at the stylus tip, a value which is met by most hi fi arms.

EFFECTIVE ARM MASS

This is effectively the inertia reflected at the stylus after the weight of the arm and cartridge have been counterbalanced and the required tracking weight turned on; total value must include the cartridge and headshell.

When the arm is to be used with high compliance cartridges the total value should be as small as possible to avoid a too low a low frequency resonance (see under this heading).

COMPLIANCE

Most specifications give a figure for compliance which is expressed in terms of the distance in 10^{-6} cm the stylus is displaced by a 1 dyne force (roughly equivalent to a weight of 1mg on Earth). Modern magnetic cartridges boast up to 20×10^{-6} cm dyne or more.

Static compliance is higher than the dynamic compliance, and confusion can thus arise in resonance calculations. Low frequency tracking is governed by the compliance and, since maximum recorded amplitudes are limited to about 0.005cm, from the tracking point alone there is no need for the compliance to exceed 5×10^{-6} cm dyne at a tracking force of 1 gramme. However, there are other factors, including mechanical damping and tip mass, that are related to compliance as explained earlier under Resonance.

Obviously the compliance cannot be increased to the extent where there is inadequate restoring force for the stylus assembly. Vertical and lateral compliances often differ, so there could be two main low frequency resonance factors.

MECHANICAL RESISTANCE

In any electro-mechanical device some mechanical resistance to movement is inevitable, but in pickups it is deliberately employed in conjunction with compliance and tip mass to even the tracking and to damp resonances over the audio spectrum. It takes effect more over the middle part of the spectrum,

EFFECTIVE TIP MASS

The stylus is mechanically coupled to the transducer so the inertia of the mechanical assembly including the cantilever is reflected at the stylus tip, and is taken into account in determining the tip mass M_t . For adequate high frequency response and hence high acceleration tracking, M_t has to be very small.

It is a difficult parameter to measure, which is why it is rarely found in published specifications. However, an approximation of performance can be found by calculating mass $M_t \approx F/(2\pi fV)$ where V is the velocity in cm/s, f the frequency in Hz and F is the tracking weight at the stylus for a condition of "just tracking properly". The modulus of acceleration is $2\pi fV$.

A good frequency for estimating M_t is 10kHz, and if 10cm/s velocity puts the tracking threshold at, say, 1.5 grammes, then M_t would equal approximately 2.3mgm.

The better cartridges tracking down to one or two grammes would have tip masses around 1mg. A treble resonance well within the passband indicates a relatively high tip mass.

while compliance is important at the low end and tip mass at the high end.

Again it is not a parameter that is specified, nor easily measured, but if natural resonance occurs over mid-range, it is likely that the mechanical assembly of stylus and cantilever is at fault.

TRACKING PERFORMANCE

Few specifications carry meaningful information on the tracking performance, although Shure do give a parameter in terms of "trackability", which indicates the ability of a cartridge to track recorded waveforms of high amplitude, velocity and acceleration at minimum tracking weights.

The information given under compliance and effective tip mass implies that given sufficient tracking weight any cartridge would track a given modulation. This is untrue, of course, because the groove wall would collapse. Tracking performance thus relates to tracking weight.

Modern discs carry amplitude variations up to 0.005cm, velocities up to 25cm/s (sometimes more on heavily recorded "pop" discs) and accelerations sometimes exceeding 2,000g. Thus to track these at, say, 1 or even 2 grammes tracking weight, both the cartridge and

the arm must be of high quality.

In a more advanced specification the tracking performance might be given as a curve showing the mechanical impedance of the stylus tip over the spectrum in terms of F/V , where F is the threshold tracking force in milligrammes and V the recorded velocity.

It is then possible to project a curve of maximum recorded velocities over the spectrum on to this curve as shown in Fig. 16. From these curves the tracking weight required at any frequency can be determined. At 3kHz, for example, the impedance is 50 mg/cm/s, while the maximum peak velocity is about 27cm/s, which means that a tracking weight of a little under 1.4 grammes is required.

Very few impedance curves are as smooth as this illustration, and it is only the best cartridges which can boast a tip impedance of less than 50 ohms at 2kHz.

TRACKING WEIGHT

All specifications should give a tracking weight or maximum/minimum limits. The maximum merely indicates the force that the stylus assembly can handle before running into mechanical non-linearity effects (or bottoming) while the minimum is usually a very optimistic value having no relationship to real tracking performance.

Tracking force of a specific amount is demanded, of course, to counter the reaction of the stylus in the modulated groove (see under Tracking Performance), but even

running at the maximum is no indication that the pickup will track maximum velocities accurately unless the weight refers to given levels of modulation over the spectrum (see Fig. 16).

The arm and side-thrust correction are tied in with this problem, and one way that the user can determine the approximate tracking performance of his pickup at a given tracking weight is by testing with a special record. Bands are provided on the HF69 test record for this purpose and for optimising the side-thrust correction.

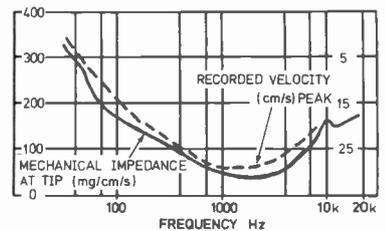


Fig. 16. Curves relating stylus tip impedance to recorded velocities

STYLUS

Modern discs have groove dimensions suitable for styli of 0.0005in tip radius. Earlier LPs called for 0.001in radius styli. A compromise dimension is 0.0007in, suitable for early and recent discs, but for the best reproduction the smallest practicable active radius is desirable. This is because the recorded high frequency waveforms, particularly at inner groove diameters where they are more compressed, can only be defined by a tip of smaller dimension than themselves.

Tracing distortion, which is a harmonic distortion resulting from the recording cutter being chisel-shaped while the replay stylus is spherical, reduces as the active tip radius is reduced.

A hemi-spherical tip cannot be reduced to much less than 0.0005in for fear of it bottoming in the groove and causing excessive noise.

This, however, is overcome by the semi-ellipsoid or biradial tip, whose active minor radius is 0.0003in or sometimes less. The major radius which falls across the width of the groove is 0.0007in, thereby preventing bottoming. Such a tip improves replay definition at inner grooves while also minimising tracing distortion.

Diamond is the only material suitable for a hi fi stylus, although sapphire is still used for mass market equipment. The life of a sapphire stylus is shorter, being a softer substance, often of a composite mixture.

Stylus replacement nowadays demands either the return of the cartridge to the maker or the replacement of the stylus assembly which sometimes pulls from the main body.

VERTICAL TRACKING ANGLE

Discs are now being cut with a 15 degree vertical tracking angle, this value being given in the specification. If the angle deviates from 15 degrees there is a rise in harmonic distortion. The angle is defined in Fig. 17.

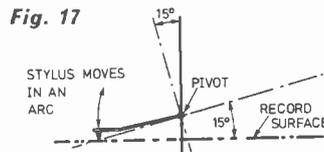


Fig. 17

LATERAL TRACKING ERROR

When a disc is cut, the cutter head follows a line of true radius of the disc, tracking along a radial rotating lathe screw. On replay the stylus follows an arc because the arm is pivoted at one point. Tracking error results because of the departure from exact tangential alignment of the replay stylus with the groove over the whole groove length.

As high harmonic distortion and disc and stylus wear result from this error, steps are taken in the arm design to correct it or at least significantly to reduce it. They consist of offsetting the axis of the cartridge from that of the arm and arranging for the stylus tip to overhang the turntable pivot at centre swing.

In Fig. 18, ϕ_2 is the offset angle and $d_3 - d_2$ the overhang. The tracking error is thus equal to 90 minus $(\phi_1 + \phi_2)$, or is zero when $\phi_1 + \phi_2 = 90$ degrees.

The following expression is useful for calculating the offset angle for zero error with overhang and effective arm length (d_3) as parameters.

$$\cos x = \frac{d_1^2 - (d_3 - d_2)^2 + 2d_3(d_3 - d_2)}{2d_3d_1}$$

whence ϕ_2 for zero tracking error is $90 - x$ degrees.

Clearly, many combinations of offset angle and overhang are possible for zero error, and it is the job of the designer to select that which yields minimum error at all arm positions relative to the effective length of the arm.

The overhang is commonly adjusted by the user with an alignment protractor for the least error at the inner groove diameter, since it is here, where the waveforms are compressed, where the distortion can be at its highest.

A well designed 8in arm with an overhang of 0.55in and an offset angle of 24 degrees would have zero error at 3.5in and 9in diameters and errors of about 2.5 and 3 degrees at diameters of 9in and 12in. The maximum errors are less with longer arms, but then there is the disadvantage of extra arm inertia.

For optimum tracking conditions ϕ_2 reduces as d_3 increases, this making d_4 , called the "linear offset", a constant. It has been determined that when d_4 is 3.47in, irrespective of arm length, the distortion due to tracking error is minimised over the swing of the disc after setting the overhang with an alignment protractor.

Distortion is proportional to the ratios of tracking error/groove radius and recorded velocity/turntable velocity. When calculations are made for the least distortion between the maximum and minimum groove diameters the parameters obtained differ slightly from those based on zero tracking error at the inner groove diameter.

Tangential arms which do not pivot in the usual way reduce the tracking error to a maximum of about 1/2 degree by using a pantograph style arm with parallel arms for adjusting the offset angle during playback.

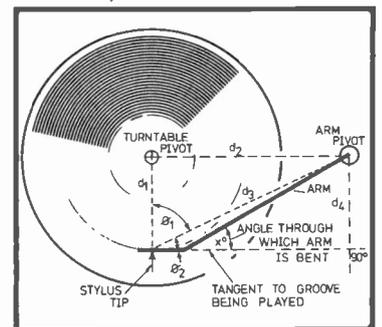


Fig. 18. Factors involved in lateral tracking

SIDE-THRUST CORRECTION

Fig. 19 shows that owing to the arm offset angle ϕ and the forward drag l of the stylus in the groove, a torque results at the arm pivot, which reflects as force F pulling the cartridge inwards.

Cancellation of this force at the arm is achieved by a dangling weight device, spring or magnetism. Actual correction value cannot be calculated for the changing modulation conditions (e.g. changing drag) and a compromise correction

is usually established by using a suitable test record.

The previously held view that F diminishes with reducing stylus-to-groove velocity (such as at the inner diameters) is currently under question, some authorities claiming that the drag due to components other than modulation remains substantially constant over the disc.

Accurately corrected side-thrust can reduce the required tracking weight by as much as 20 per cent.


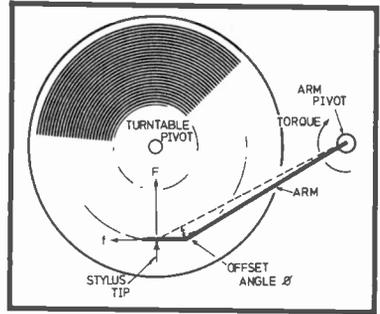


Fig. 19. Illustrating side-thrust, where force F is equal to $f \sin \phi \times \cos \phi$.

TURNTABLE REQUIREMENTS

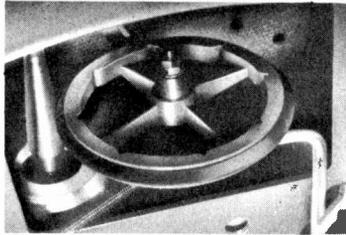

Philips GA202 uses electronic controlled d.c. motor and belt drive



Detail of the Goldring-Lenco continuously variable speed control

One design angle is for minimal mechanical noise from the turntable unit which gives rise to "rumble" superimposed on the signal from the pickup. Pickup resonance must be prevented by designing the pickup shell and arm to avoid such effects being aggravated.

The motor is mechanically decoupled from the pickup by using rubber or spring suspension, and from the turn-table by the transmission, which might be a rubber idler wheel or belt. Any noise from this source is around 22.5Hz, the slip frequency of the motor, and can be aggravated by dynamic imbalance of the motor's rotor.

The main bearing of the turntable is responsible for a lower frequency noise, discerned more by feeling than hearing in a hi fi system. Special attention is given to the removal of this noise from transcription units, the bearing generally consisting of a single ball, rather than a ball race.

WOW AND FLUTTER

Wow, which is caused by turntable speed variations below 20Hz, and flutter, which results from speed variations at a higher rate, are far more disturbing than consistent speed error.

The percentage wow and flutter is given as

$$\frac{(f_{\max} - f_{\min})}{f_{\text{av}}} \times 100 \quad \text{per cent}$$

where f_{\max} and f_{\min} are the maxi-

mum and minimum frequencies and f_{av} is the average frequency, usually based on 3kHz. Measurement is by a wow and flutter meter and the readout may be in peak or r.m.s. value.

The minimum DIN requirement is not greater than ± 0.2 per cent peak, but to be undetectable to acute hearing the wow must not be greater than 0.3 per cent and the flutter not greater than 0.15 per cent.

Drive motors are mostly a.c. mains operated and of quasi-synchronous nature. They are usually adequately decoupled from the turntable bearing by rubber buffers or springs. The whole motor board, too, may be decoupled from the plinth to reduce shock excitation of the pickup.

A fairly recent idea is the use of a Wien network oscillator for driving a synchronous motor, the motor speed thus being adjustable by varying the oscillator frequency. Servo controls have been mooted, but in general the a.c. motors and turntable units of today are well compatible with the associated components of the system and do not really justify such sophistication.

SPEED ERROR

The DIN minimum speed error tolerance of ± 1.5 per cent and -1 per cent is generally well met and is reasonable since an error of 0.2 per cent corresponds to a change in pitch of less than 1/30th of a semitone. Nevertheless, listeners blessed with perfect pitch should consider a unit with limited speed control.

RUMBLE

Rumble is quoted relative to a given level of modulation, the greater the level the greater the signal/rumble ratio. Rumble expressed as, say, 40dB below 5cm/s at 1kHz RIAA implies that the rumble is relative to a signal of that frequency and level, with the rumble itself being measured via RIAA equalisation.

Other filters may be incorporated in the readout to weight the disturbance and to eliminate high frequency noise. For meaningful comparisons the nature of the measurement must be known, and this is not always given in the specification.



Jupiter, in blue light, showing the great Red Spot, Satellite G a n y m e d e and shadow (a b o v e).
200in Hale

(Mount Wilson and
Palomar Observatories)

RADIO ASTRONOMY

TECHNIQUES

BY F. W. HYDE · PART 10

THIS is the concluding article in the present series: it is mainly concerned with a project for the detection of the decametre radiation from the planet Jupiter, but also explains how a radio map of the sky may be produced.

RADIATION FROM JUPITER

In 1955 Burke and Franklyn in America were testing a large aerial system. With the team was F. Graham-Smith, one of the original team under Martin (now Sir Martin) Ryle at Cambridge. Graham Smith and the other members of the American team had noticed that there was a regular outburst of radiation which was very like the sun in some respects. Someone jokingly said perhaps it is Jupiter and in fact Jupiter was in the beam of the aerial when the radiation appeared. A check was made and it was indeed found that the planet was radiating on frequencies around 16 to 22MHz.

When listening to these radiations the sound from the loudspeaker is very much like the sound of the ebb and flow of the sea on a shingle beach. It is quite distinctive and easily recognised in the midst of other radiation; it changes in level very rapidly and may vary by as much as a hundred times in the course of a few seconds.

As this particular part of the frequency band is full of activity, daytime observation is difficult even with an interferometer; thus the majority of observations of Jupiter are made at night. This particular problem has received a great deal of attention by Warwick and others in America but not much elsewhere, apart from the author's work in collaboration with Florida State University.

There are a number of observatories in America involved and names associated with the work are Alex G. Smith and T. D. Carr at Florida University; and recently workers at Meudon Observatory in France have taken a new approach to the problem. It is not possible to do more than give a brief account of this phenomenon of the Jupiter radiations. Various theories have been proposed over the past several years.

Obviously, there is still much to be done in the way of observation, and as the aerials and receiving equipment needed are extremely simple, Jupiter is now a worthwhile project for the amateur. Indeed, work can now be done in the back garden, because of a simple type of aerial which the author has brought into use.

Formerly, a large corner reflector was required and remembering that at 18MHz, one of the particular frequencies used, the wavelength in physical length is some 54ft, a corner reflector is quite large even with a half-wave dipole—being some 40ft high and 40ft long (one of the author's large aerials is shown in the photograph).

EQUIPMENT REQUIRED

The requirements for the Jupiter project are a suitable yet simple aerial, a pre-amplifier, a communications receiver, a d.c. amplifier, and a recording system. The block layout is shown in Fig. 10.1.

The simple aerial already alluded to is a loop which is nearly closed and it may be used in the normal way without a reflector, in which case it will have the usual figure of eight polar diagram. A reflector of mesh added gives an increase in gain

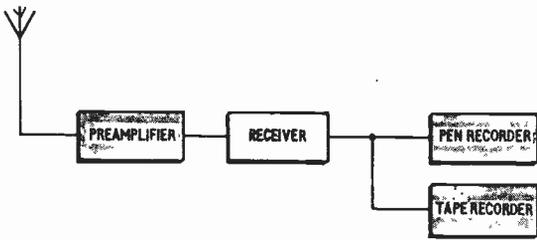


Fig. 10.1. Block diagram of Jupiter Receiving System

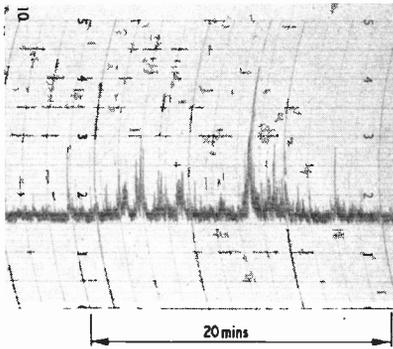


Fig. 10.2. A recording of radiations from Jupiter

with the loop facing the source of energy. This aerial is not unduly critical as to bandwidth so that an aerial designed for 20MHz will operate quite well between 18 and 22MHz. This is quite an important factor, because it may be that some radiations will appear in any part of this band. Also, if the band is somewhat crowded the tuning point can be changed to find a quiet spot.

Because of the nature of the Jupiter radiations the normal time constant of the communications receiver is used. If the pre-amplifier provides of the order of 20-30dB gain, it will be possible to use the direct output from the receiver, or to feed the d.c. amplifier direct from the second detector, with no intermediate long time constant detector section.

Much of the professional work that has been done in the past has been with high-gain receiver front-ends, and recordings made on low resistance recorders with an incorporated rectifier. If the recorder had no rectifier then a 1mA bridge rectifier such as the Westinghouse meter rectifier was used. The results of such observations are shown in the recorded chart in Fig. 10.2.

Bearing in mind the description of the sound of this radiation, it will still need some practice, both aurally and visually, to determine that which is of Jovian origin, and that which is from man-made and extraterrestrial sources. More will be said about this at the end of this article.

AERIAL CONSTRUCTION

Details of the loop aerial are given in Fig. 10.3.

The best material for the aerial element is half-inch aluminium tube of about one half inch

diameter. The reflector should be of 1in to 1½in square mesh of 16s.w.g. galvanised wire with welded joints. This is a readily available item in most hardware stores.

The frame can be of timber or metal according to choice. If metal is used then make sure that all parts of metal that touch are electrically bonded.

The mounting of the aerial can be left to choice, but this is an opportunity to make up an equatorial mounting, and the diagrams in Fig. 10.4 give some suggestions in this respect. The aerial and pre-amplifier should be mounted on the back of the reflector. It is suggested that another additional pre-amplifier be employed at the receiver.

PRE-AMPLIFIER

Two examples of suitable pre-amplifier circuits are shown in Fig. 10.5. The type of transistor can be changed to suit, provided the parameters are the same. Those shown are the types used in the original equipment and which have given reliable service.

A warning is perhaps advisable here about breakthrough. If attempts are made to use this radio telescope where there is much commercial operation, breakthrough may be troublesome and in some cases damaging. A check should be made with an aerial located at the receiver to observe the state of the band before connecting the main aerial and its pre-amplifier. Also, it is as well to have the aerial pre-amplifier switched off when not in use, for it too could suffer from overloading.

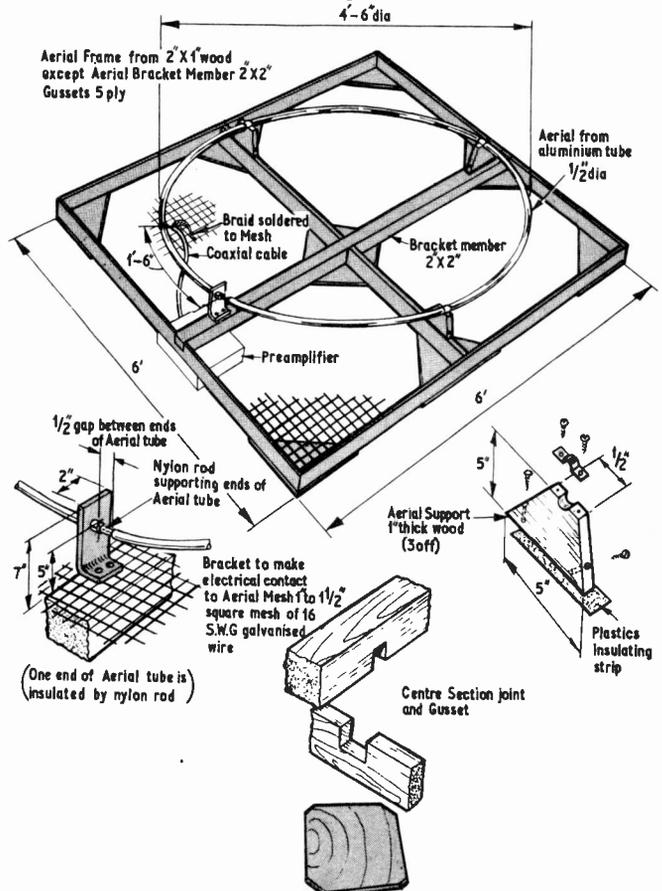


Fig. 10.3. Loop aerial constructional details

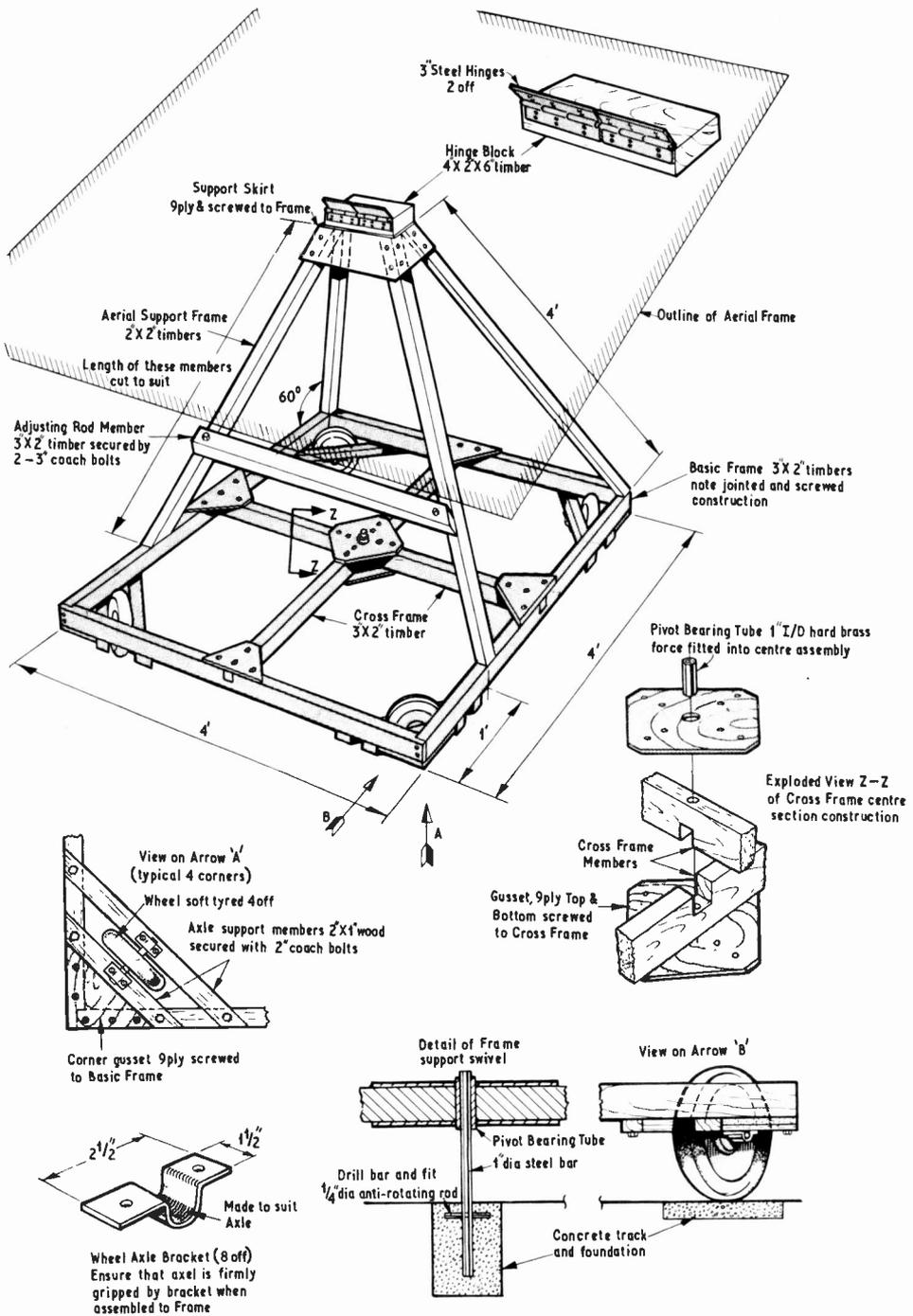


Fig. 10.4. Suggested mounting arrangement for loop aerial centred at 20MHz. This provides for equatorial and altazimuth adjustment

FORM OF OBSERVATION

After a few trial observations and recordings, it would be possible to let the system run without direct supervision. This is of course very simple in the case of the interferometer for most of the interference will be avoided. In the case of the simple one-aerial system, as just described, attendance of the observer is necessary to ensure acceptable observations and until sufficient experience has been gained in assessing the recordings obtained. If possible, the recordings should subsequently be examined by an observer who has this experience.

This is mentioned because to be useful the observations should be made over as long a period as possible, and it is not very convenient nor desirable to spend up to eight hours on direct observations.

The important times are in fact the two hours before and the two hours after the planet passes the meridian. There are special reasons why the earlier and later observations can be useful. For example: important information about the ionosphere after sunset can be obtained; and, after say 03.00 a.m., the rise of the dawn chorus can be recorded. This latter phenomenon is quite striking when first experienced, and the effect on the recording can be seen in the example given in Fig. 10.6.

MAKING A RADIO MAP OF THE SKY

The list of sources given in Part 7 is short and covers only the more powerful sources, though even some of these may be below the threshold of recording where the simple telescope is used. It is however a practical and useful exercise to make a radio map of the sky from the point of observation. There will be a considerable difference between the maps made in the northern hemisphere and those made in the southern hemisphere. Such maps could be useful where correlation of results is at intervals ranging over the two hemispheres.

The procedure for building up a useful map is simple and involves two requirements: (1) a setting in altitude; (2) a sufficiently spaced scanning programme. The altitude changes will depend on the beamwidth in the vertical direction and the value of the scans will depend on having a number of days at the same scanning position. This latter requirement is necessary in order to take care of the varying conditions of the ionosphere and other effects on the transmission of the radiation through the atmosphere. Usually a four to six day run at each altitude selected should give a reliable set of data. The sequence is then as follows:

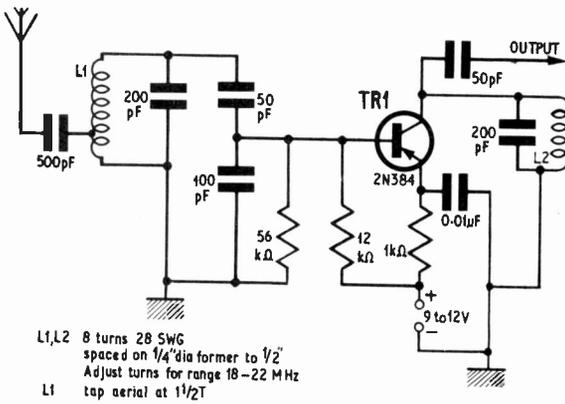


Fig. 10.5a. A simple aerial pre-amplifier

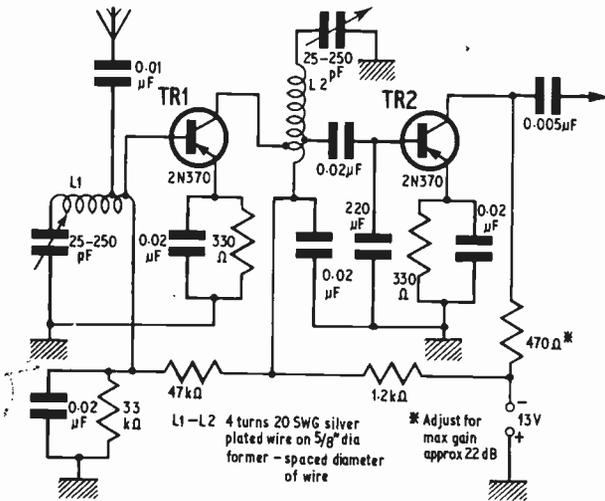


Fig 10.5b. A two transistor aerial pre-amplifier

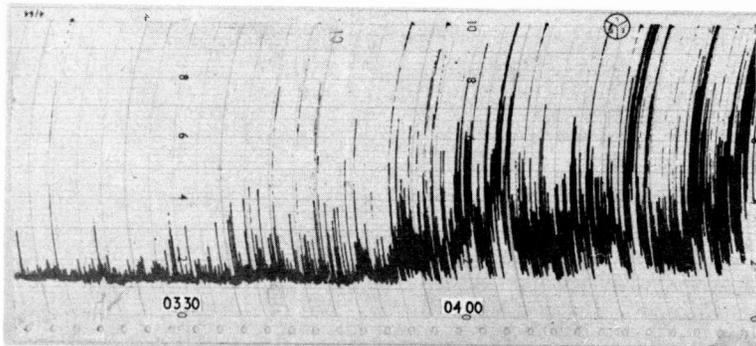


Fig. 10.6. Example of a pen recording of the dawn chorus

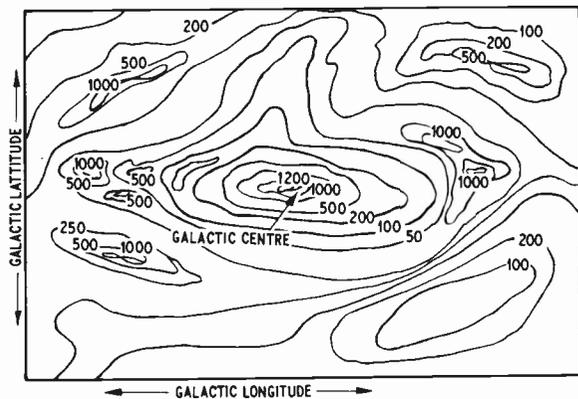


Fig. 10.7. Radio map of sky at 200MHz. Values in arbitrary units

Set the altitude; record the runs; carefully log the conditions; examine each day and compare it with the next; lay the records over each other with a bright light under to assess visually the changes.

Make careful notes of any unusual or odd items on the recording. From this it will be possible to learn the effects of satellites, man made interference, air radiation effects and, at the frequency chosen, the rain static effects.

As a normal programme, a month of scanning should yield sufficient data for a reasonably accurate map. When the map is completed it would look somewhat like that shown in Fig. 10.7. The contour lines are at the points of equal intensity, and the whole presents a kind of relief map of the part of the sky covered. The value of the lines are arbitrary in the case of this project, but there is a standard evaluation and this is given in the appendix for those who would like a little mathematical information.

POLARISATION

One point that should be mentioned here is that the energy that is received from extra terrestrial sources is polarised. Since the aerials in use are horizontally polarised, only half the energy from space is received in the horizontal mode. It might be thought reception should be set up in both planes. This is, in fact, frequently done and does offer a means of roughly determining the way in which the radiation is polarised. This might be left handed or right handed.

One reason for the more common practice of using horizontal receiving elements is that mechanically they are easier to construct but there is also another reason which relates to the electrical properties.

It is a fact that there appears to be less interference on the horizontal mode compared with the vertical mode. One reason for this is the amount of reflected radiation from the ground which also seems to carry a good deal of man-made interference.

With the corner reflector aerial there is protection from this type of reflection. If the aerial is turned so that the bottom edge of the reflector is near the ground the "spill-over" of the beam will mean that radiation from the ground is picked up. It is sometimes necessary to set another horizontal reflector to overcome this. Where the sensitivity of the system is low as in the first simple project described in this

series, the ground radiation (or temperature as it is described) will dominate in any case. The appendix also deals with this aspect.

IN CONCLUSION

If there is sufficient interest in the promotion of projects that have so far been described in this series, it could be possible to organise them on a group basis, and so make a worthwhile contribution to knowledge.

Those wishing to follow such a line of observation, whether it be solar noise and/or polarisation measurements, together with the study of the Jupiter radiations, should contact the editor. This would enable the author to arrange the correlation of data with a view to publication of the results and credits to those who take part. It could also result in an exchange of information between like minded readers. ★

APPENDIX


One method of assessing the intensity of the radiations received is based on Planck's law relating to the emission of electromagnetic energy at all frequencies from a "black body". This energy is related to the temperature of the body. For radio frequencies the Rayleigh-Jeans formula can be used and this is:

$$B = \frac{2KT}{\lambda^2}$$

This gives the brightness of the source in terms of T which is the temperature in degrees Kelvin and the wavelength λ where K is Boltzman's constant and is equal to 1.38×10^{-23} in MKS units.


The temperature of the earth radiation is of the order of 100° Kelvin and this sets the lower limit of temperature that can be measured. This is one advantage of the large dish type aerial since the aperture can be trained away from the surface of the earth and so avoid these limiting factors.

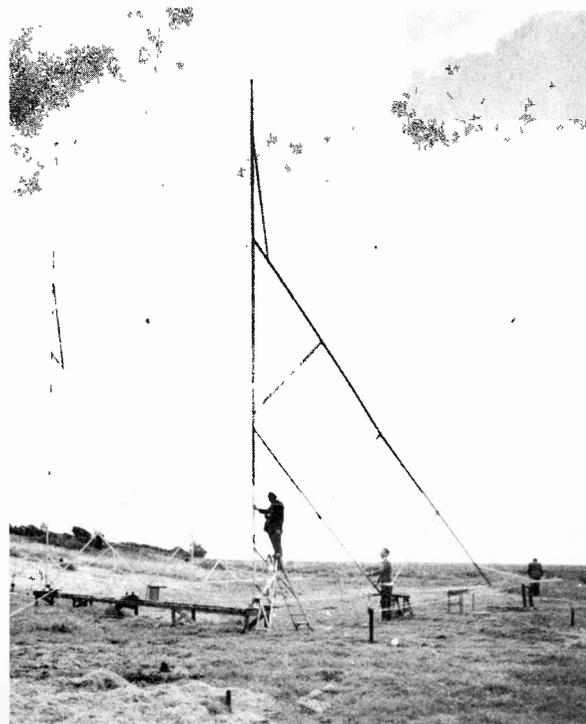Although there are not many books on Radio Astronomy there are sufficient in most libraries for the enthusiast to pursue these theoretical considerations.






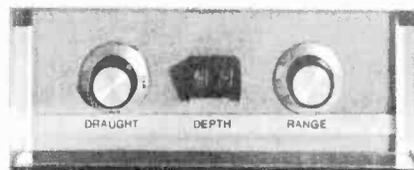This photo shows Chay Blyth at the chart table of the boat *British Steel* which uses Brooks and Gatehouse electronic instruments, including speed, depth and wind indicators; depth transducer selection switch is at bottom right of the panel. The instrument dials are often duplicated in a waterproof housing on the top of the cabin as shown on the 36ft cruiser racer below



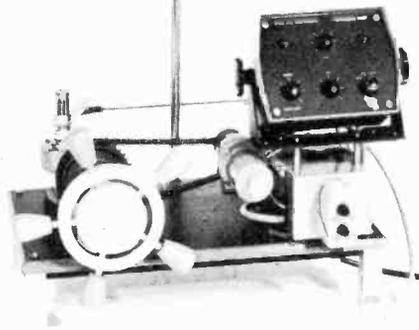Mini computer using medium integration with seven-segment displays



An electronic polar locking compass (EPL) is incorporated in this "Command Pilot" from Space Age Electronics. It is mounted on the post

ELECTRONORAMA



ANOTHER boat show—another year of marine electronic development, although quite often it is hard to find what has been developed by who. This is mainly due to the lack of organisation in the press office at the show and not the firms concerned.

Medium scale integration has now found its way into the sailing scene and is incorporated in a depth indicator with seven segment digital readout, by G. M. Systems Ltd. Having ranges from 0 to 99 feet and 0 to 99 metres the unit has no moving parts (except a range, on/off switch and a draught compensator control) and is very compact. Main disadvantages are: no facilities for remote readout and the possibility that it is more difficult to judge the rate of change of depth from a digital display than from a meter or graph readout.


The G1000-F chart recording echo sounder for inshore fishermen, yachtsmen and small coasters has been introduced by Ferrograph. The new sounder is unusual in that it uses a specially prepared paper that is marked electrically avoiding the need for a special pen and ink.

Another new product is the 050 radar from Decca. Smaller than the 101 and less expensive this new radar should be of interest to many small boat owners. Decca tell us that no corners have been cut to get the price down.

Other developments in small boat radar were announced by Kelvin Hughes (Type 17 radar developments) and EMI (new version of the Electrascan); no price increases have been made on the developed sets by either of these firms.

Brookes and Gatehouse have this year come up with no less than five new developments, admittedly one of those is a skin fitting for the existing boat speed indicator, but the other four are significant developments in the small boat electronics field. Three new B and G equipments are a sailing performance computer to calculate speed made good to windward, a "single signal" df receiver—a development of the Homer K receiver,

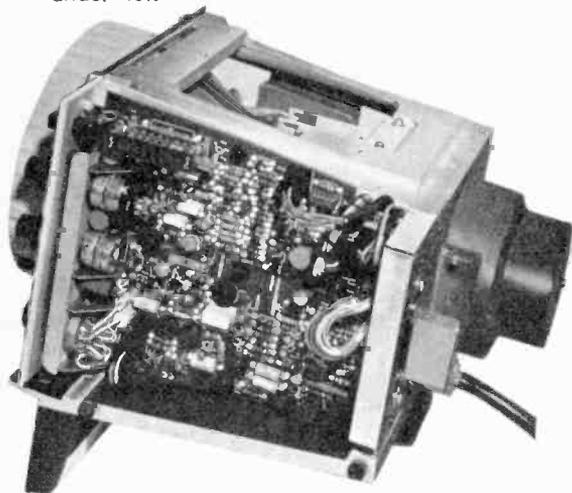The Decca 050 radar is suitable for small boats under 40ft



The interior of the Decca 050 display unit showing all the display electronics mounted on one printed circuit board

AT THE BOAT SHOW

and a long-range echo sounder (100 fathoms).


The fifth development is an improved distance-off-course computer. This computer uses a "new design" master compass which we believe has only recently been released for sale for non-military applications. This electronic polar locking (EPL) compass is also used in the "autopilots" made by Space Age Electronics. The main feature is that the bearing is unaffected by the movement of the boat however violent. The command pilot from Space Age Electronics shown on the facing page has EPL unit on the raised mounting and incorporates a remote hand held steering control unit—shown fixed to the pilot under the main control panel.

A new speedo/log that does not use an impeller or straingauge, merely a small transducer, and provides seven segment digital readout is now being offered by Detronic Ltd. The transducer is formed by an electrostrictive crystal transmitting an ultrasonic signal of 500kHz. The unit works by measuring the frequency change of the signal reflected by the water (the signal is transmitted about 9 inches) due to the doppler effect. Hence a very accurate measurement can be made—0.1 of a knot from 0—9.9 knots and 1 knot from 10—99 knots.

The Baron Squire range is new this year, the main difference from their original range seems to be the housings and sealed indicators, some of which incorporate the electronics. They had an impressive display of units working under about a foot depth of water. It is a pity that they do not improve their meter face design as this tends to be complicated and not very easy to read.

All in all plenty of new developments for the boat owner to consider and, with the advance of micro-electronics, perhaps some smaller, better equipments still to come.

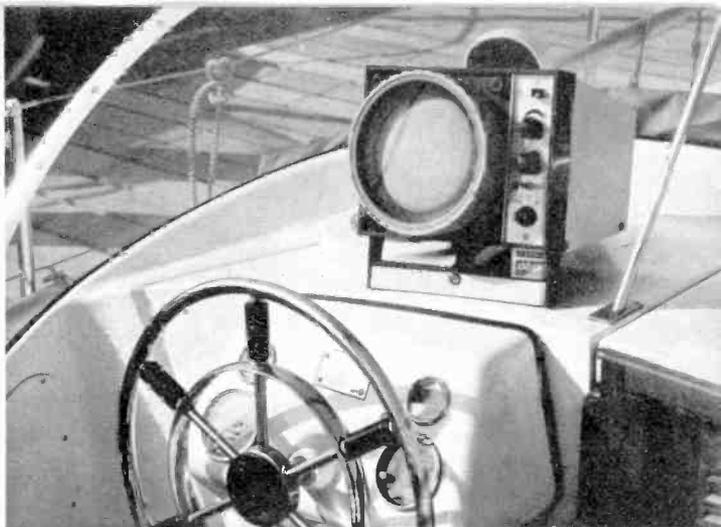The waterproof glass fibre radome houses the Decca 050 aerial and transceiver. This arrangement, fitted to a mast is most suitable to small motorised sailing boats where unshielded rotating scanners are unsuitable



Fairey Marine "Huntsman 31"





A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

UNIUNCTION TIMER

ALTHOUGH it might be argued that a monostable could perform the same function as the circuit shown in Fig. 1, it should be borne in mind that this is true for relatively short periods only. The circuit under consideration will perform happily for tens of minutes but to achieve the same time scale with a monostable would require enormously large electrolytic capacitors.

This particular circuit is also more straightforward in operation. To obtain the proper sequence from a monostable would necessitate the reversal of the initial states, i.e. the transistor which is initially off would have to be triggered initially on.

The purpose of the circuit is to manually switch on a power supply for a pre-determined period and leave it to switch itself off automatically. The power supply may be connected to a motor or some other piece of apparatus. In my project, it was used for a high-frequency transmitting oscillator.

When push switch S1 is pressed, TR1 is brought into conduction via R1 and the relay is energised. The operation of the relay closes contact RLA1 across the switch to act as a self-hold. Capacitor C1 begins to charge via R4.

When the voltage on C1 has risen to the triggering level of the unijunction TR3, C1 discharges into R3 which produces a pulse of sufficient magnitude to turn TR2 on. The base-emitter junction of TR1 now has the V_{ce} saturation voltage of TR2 across it. This voltage is lower than the requisite turn-on voltage so TR1 is turned off, the relay is de-energised and contact RLA1 opens. The supply is thus switched off.

The main requirement in the project was to consume as little power as possible since the equipment was battery operated. An RS Components, type 15, relay was therefore chosen because it requires only 60mW operating power.

The unijunction transistor TR3 is the popular GEC type 2N2646 and the values of R2 and R3 are those recommended by the manufacturer. Capacitor C1 was chosen to be 1,000 μ F so that C1, R3 has a time constant of 100ms, which is twice the release time of the type 15 relay.

The value for R4 is only a guide since there is a variation in the value of η for the 2N2646 and electrolytic capacitors have such a wide tolerance. R4 will have to be finally chosen by trial and error. In the circuit which was constructed, a time delay of 5 minutes was achieved by using 100k Ω for R4.

The ballast resistance for the Zener diode may conveniently be a suitable indicator lamp. For example, with a supply voltage of 36V one may employ an S6/8 type of lamp (RS Components) at 28V, 0.04A. A current of 40mA through the Zener diode will provide good regulation since the greatest shunt path will be the 20mA relay current.

J. Wilson, C.Eng., M.I.E.R.E.,
Reading.

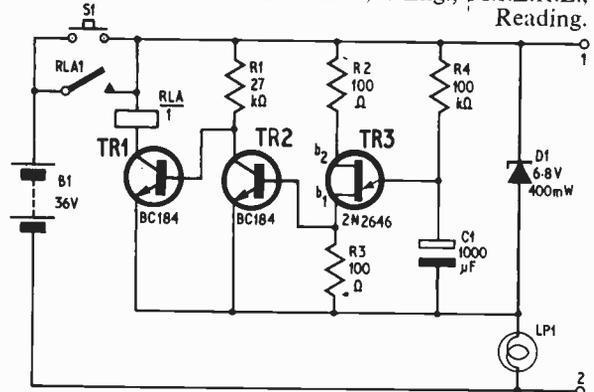


Fig. 1. Circuit diagram of the unijunction timer. Terminals 1 and 2 go to equipment

R.F. AMPLIFIER FOR CAR RADIO

BY USING a low noise transistor in the circuit shown in Fig. 1 the average car radio's performance is greatly enhanced and stations previously beneath noise level become reasonably clear.

The circuit, having a high output impedance, is effectively tuned by the input circuitry of the car radio.

The gain control VR1 should be advanced as far as possible consistent with absence of cross-modulation and car ignition interference.

Using a separate battery B1, eliminates earth loop problems, the need for elaborate decoupling and will last at least nine months with continuous use.

P. E. J. Lacey,
Crediton, Devon.

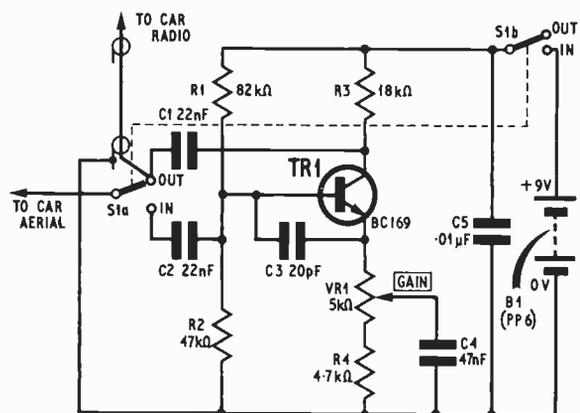


Fig. 1. Circuit diagram of the r.f. amplifier for car radio

PATENTS REVIEW

TONE GENERATORS

IN the new British Patent 1 245 714 Standard Telephones and Cables Ltd. (STC) discuss the problems inherent in constructing tone generators for telephone dialling.

Electrical oscillators can be used for this purpose but the problem in this case is that the associated switch is of necessity heavily used and its contacts may show early wear. A contact-less generator uses a reed of magnetised material which is set in vibration by plucking; but the vibration of the reed is not easily sustained and the plucking and plucked parts are also susceptible to wear.

STC have devised and patented a tone generator which uses a transducer (e.g. piezo electrical material) mounted on a reed coupled to a bowed leaf spring, Fig. 1. Once the transducer is excited a circuit keeps the reed vibrating, but this vibration is normally suppressed by a mechanical damper, see Fig. 2. As the reed is on a bowed spring, however, it can be snapped between one of two positions and it is only damped in one of these positions. In the other position it is free to vibrate and, what is more, this snapping motion serves to start the reed vibrating. Vibration is then maintained by the electric circuitry.

In Fig. 2 STC show such an arrangement in side view.

The leaf spring is snap controlled by a push button loaded by springs, and in its up-bowed position the leaf forces its reed and transducer against a mechanical damping bar. When the push button is pressed, the leaf snaps into its down-bowed position so that the transducer is brought well clear of the damper, the snapping motion mechanically jolts the reed into vibration. This vibration is then maintained by an amplifier with two high gain transistors functioning as an oscillator by

virtue of a feedback loop, Fig. 3.

Usually the reed will be formed by a tongue cut out of the spring by a U-shaped incision and the transducer by a sandwich of piezoelectric material between metal electrode layers.

NEUTRALISED AMPLIFIERS

IN BP 1 241 285 Mullard Ltd. outline the advantages and disadvantages to date of neutralised transistor amplifiers.

According to Mullard the advantages of neutralising the base-collector capacitance of a transistor in an amplifier (to minimise unwanted feedback due to such capacitance) are increased gain and stability. Such neutralisation can be achieved by a neutralising capacitor circuit.

However, as there is frequently a spread in the value of the base-collector capacitance and as a fixed value component is normally used for neutralisation, there is clearly a problem that under some circumstances the transistor may be over-neutralised and have a tendency to oscillate, while under other circumstances the transistor may be under-neutralised and have its gain seriously reduced. Ideally the neutralising capacitor would be matched to a particular transistor for the best possible compromise, but this is hardly practical for normal use.

The Mullard solution is to use a semiconductor body which has a transistor and a neutralising capacitor incorporated in the one case, the latter having a value appropriate for neutralising the capacitance of the base-collector junction.

The neutralising capacitor is formed from the same material as the transistor, but with opposite conductivity type regions as the base-collector junction. Usually this will be by the same diffusions.

BP 1 241 285

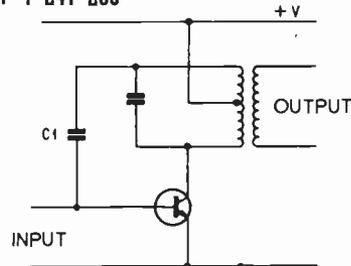


Fig. 1

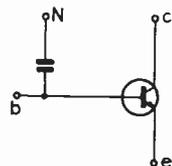


Fig. 2

The collector or base region of the transistor is connected to the region of corresponding conductivity type of the capacitor and the amplifier circuits so arranged that during operation there will always be a virtually complete cancellation of signals fed back to the base of the transistor via the two junctions.

By making the neutralising capacitor in the same semiconductor body as the transistor, it becomes possible to hold the ratio of their capacitances to within 5 per cent or better even though their actual capacitance values may vary by ± 30 per cent.

In Fig. 1 Mullard show how conventionally a neutralising capacitor C1 is connected between the base of a transistor and the side of a parallel LC tuned circuit away from the transistor collector. In Fig. 2 there is shown the manner in which the transistor and neutralising component C1 of Fig. 1 is realised as an integrated circuit.

The patent gives full details of the actual semiconductor bodies that can be used for realisation.

BP 1 245 714

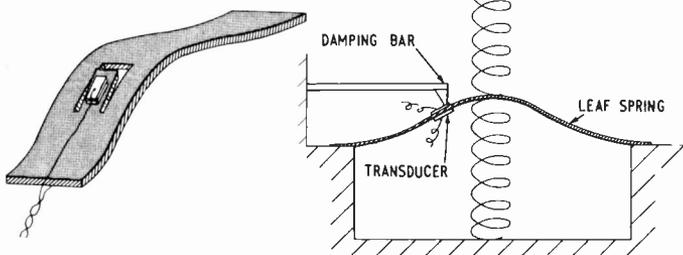


Fig. 1

Fig. 2


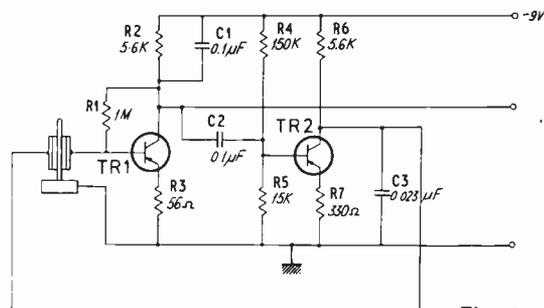
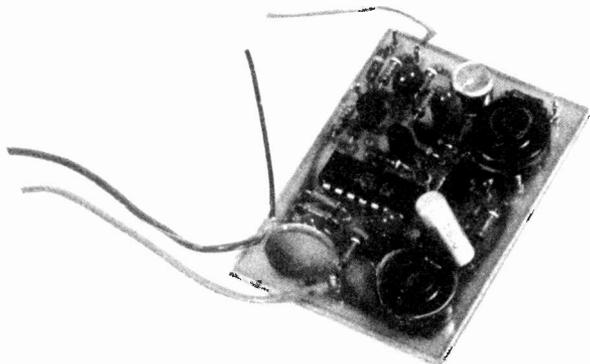


Fig. 3

Part 2

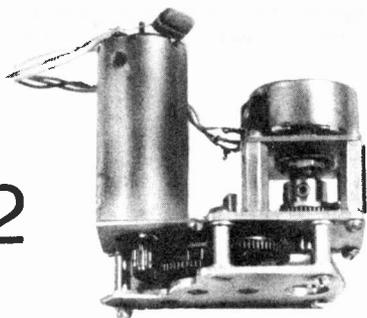

Model Servo Control

By A.J. Dunn

THE circuit of servo amplifier "B" is basically similar to that of servo amplifier "A" and with the exception of D1, C2, VR2, VR3, D2, C3 (Fig. 5) the action is the same. In this circuit TR1 is complementary to TR2 and V_{be} voltage changes with temperature are therefore eliminated. TR10 replaces the resistor R8 of the long-tailed pair in amplifier "A" and acts as a constant current source, bias being determined by R10, R8a and R9b. Note that reducing R8b increases the dead zone.

The use of a complementary emitter pair enables R2 to have a higher value and the input impedance is high. If large values of C1 and R1 are used, R2 (approximately $10 \times R1$) may be fitted to swamp the leakage effects of C1.

DEAD ZONE OPERATION

The function of D1, C2, VR2 is as follows: if the input signal is increased, TR5 conducts more and TR3 and TR4 are turned on.

The collector of TR3 (bottomed) is approximately 0.2V below the +6V supply and, according to the setting, the wiper of VR2 may be at +4V. The diode, D1 is therefore forward biased and C2 discharges to 5.2V, there being a drop of 0.6V across D1 and 0.2V across TR3. This can be considered as being equivalent to connecting a 5.2V supply to the wiper of VR2 in place of +4V; the voltages associated with all sections of VR1 are consequently increased.

If the input signal increase is not large the wiper of VR1 would have been initially not far from the

dead zone and the rapid voltage increase at VR1 would cause TR6 to conduct more, TR5 less, and TR4 and the motor to be switched "off" before it would have otherwise done without the action of D1, C2, VR2. The effect of motor inertia is therefore to carry the wiper into the normal position of the dead zone and not beyond.

When TR3 is cut off its collector is held by R5 and R6 at 0V and D1 is reverse biased. C2 therefore charges to the voltage set by the position of VR2 wiper and the voltages associated with VR1 return to the normal condition, reducing the voltage applied to the base of TR6. If the wiper of VR2 is set to more than +5.2V then D1 is not able to conduct as above and hence plays no part.

OVERCOMING HUNTING

If the wiper of VR2 is set to progressively lesser voltages than +5.2V, then the voltage change at this point and consequently at the wiper of VR1 becomes greater. If the voltage change at the wiper is made equal to the equivalent dead zone in use, the effect is to overcome hunting effects without the necessity of increasing R16 and R17, or alternatively to increase resolution. If the voltage change at

VR2 wiper is increased further, then another effect is involved.

If bottomed, TR3 and D1 discharge C2 relatively rapidly; thus in the example quoted, the motor is switched off prior to entering the "normal" position of the dead zone. On cut off, C2 is charged through VR2 relatively slowly; this time must elapse before the voltage at VR1 is restored and the motor reverse should have traversed the dead zone.

The damping effect of C2 can be tuned by means of VR2 to damp out persistent hunting. The components D2, C3 and VR3 have the complementary effect to D1, C2, VR2 and cause, by an amount set by VR3, the early cut-off of the motor in the reverse direction.

The fail safe operation is effected by changing the connection of R18 from 0V when it has no significant effect to +6V. This can be performed remotely, by using a relay. If R18 is less than R4 TR2 will cut off, and by selection the required torque unit setting can be obtained.

CONSTRUCTION AND TESTING

The components should be assembled on a printed circuit board, the pattern and layout being similar to that of Servo A (see Figs. 6 and 7). On completion VR2 and VR3 should be set to have no action.

If hunting takes place, when testing with the decoder for a given time constant for R1-C1, then VR2 and VR3 should be adjusted to damp out the hunting.

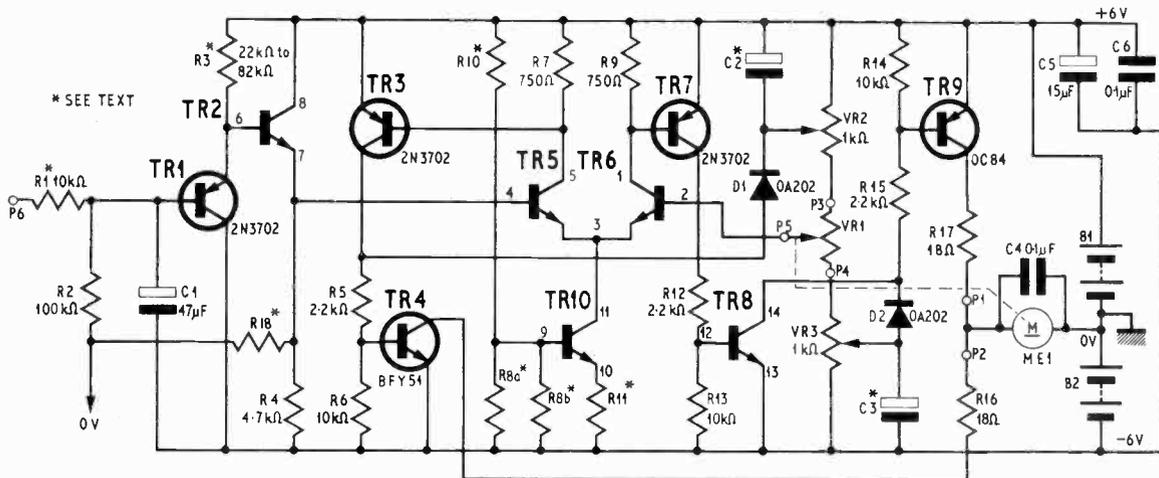


Fig. 5. Circuit diagram of servo amplifier "B". The connection to R18 should be brought out separately if "fail safe" operation is contemplated

COMPONENTS . . .

SERVO AMPLIFIER "B" (Fig. 5)

Resistors

*R1 10k Ω	*R10 9.1k Ω
R2 100k Ω	R11 680 Ω
*R3 22k to 82k Ω	R12 2.2k Ω
R4 4.7k Ω	R13 10k Ω
R5 2.2k Ω	R14 10k Ω
R6 10k Ω	R15 2.2k Ω
R7 750 Ω	R16 18 Ω
*R8a and b 2 \times 2.2k Ω	R17 18 Ω
R9 750 Ω	R18 4.7k Ω
All $\pm 10\%$ $\frac{1}{8}$ W carbon	

Potentiometers

- VR1 500 Ω linear, linked to servogearred motor
- VR2 1k Ω linear preset
- VR3 1k Ω linear preset

Capacitors

- C1 47 μ F tantalum
- *C2 47 μ F tantalum
- *C3 47 μ F tantalum
- C4 0.1 μ F polyester (mounted on motor)
- C5 15 μ F tantalum
- C6 0.1 μ F disc ceramic

Transistors

- TR2, TR5, TR6, TR8, TR10 Contained in IC1 CA3046 (RCA)
- TR1, TR3, TR7 2N3702 (3 off)
- TR4 BFY51
- TR9 OC84

Diodes

- D1, D2 OA202 (2 off)

Batteries

- B1, B2 Two 6V dry batteries

Miscellaneous

- Printed circuit board
- Solder pins
- *See text

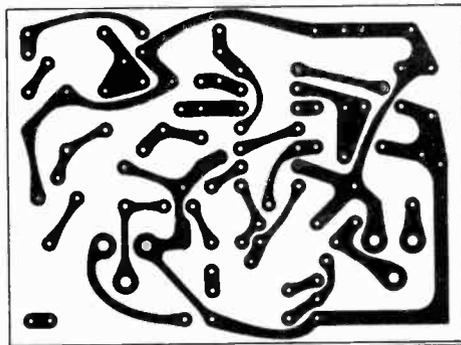


Fig. 6. Printed circuit pattern (full size) for servo amplifier "B"

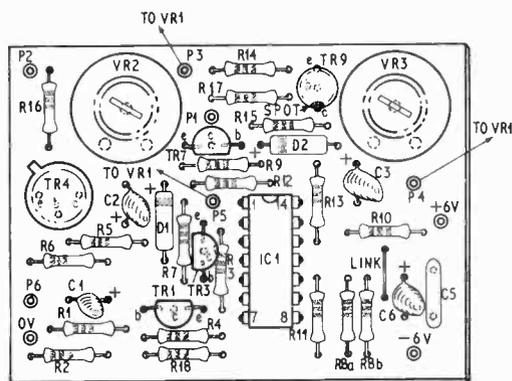


Fig. 7. Component layout for servo amplifier "B"

SERVO AMPLIFIER "C"

As shown in Fig. 8 the circuit is similar in form to servo amplifier "A" but fewer components are used. The unit is compact and may be mounted directly on the torque unit. TR1 and TR2 (not thermally coupled) operate as a long-tailed pair with R4 adjusted to define the current so that TR3 and TR4 cannot be on simultaneously.

Changes in temperature and supply voltages markedly change the width of the dead zone which should for safety be made approximately 15 per cent of the range.

TR3 is operated directly from TR1 which despite

a gain of 100 may turn on slowly in relation to TR5. The selection of component values follows as for Servo amplifier "A."

CONSTRUCTION AND TEST

The components should be assembled on a printed circuit board; the copper pattern is as in Fig. 9 and component layout Fig. 10.

The unit should be tested as for servo amplifier "A" noting the absence of "fail-safe" circuitry and that the switching action of TR3 and TR5 in Fig. 8 is reversed with respect to the motor.

COMPONENTS . . .

SERVO AMPLIFIER "C" (Fig. 8)

Resistors

R1 10k Ω	*R6 4.7k Ω
R2 750 Ω	R7 10k Ω
R3 750 Ω	R8 18 Ω
R4 6.2k Ω	R9 18 Ω
R5 2.2k Ω	*R10 100 Ω

Potentiometer

VR1 500 Ω linear, linked to servogearred motor

Capacitor

C1 47 μ F tantalum

Transistors

TR1, TR2	2N3702	(2 off)
TR3, TR4	2N3704	(2 off)
TR5	OC84	

Batteries

B1, B2 Two 6V dry batteries

Miscellaneous

Printed circuit board

Solder pins

*See text

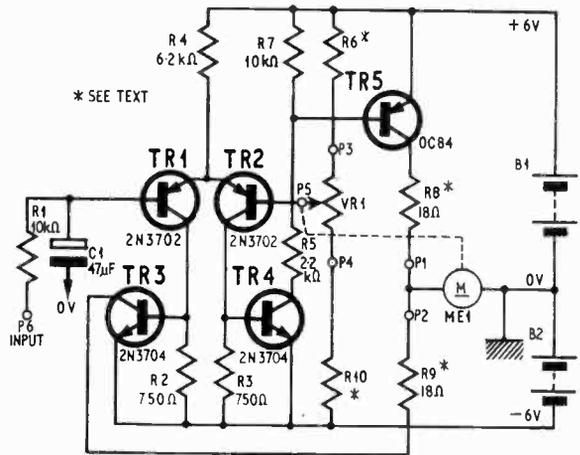


Fig. 8. Circuit diagram of servo amplifier "C"

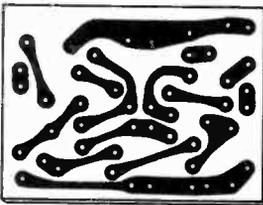


Fig. 9. Printed circuit pattern (full size) for servo amplifier "C"


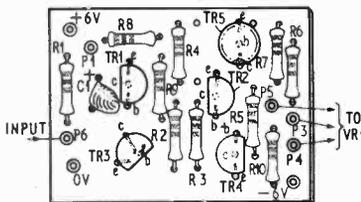


Fig. 10. Component layout for servo amplifier "C"

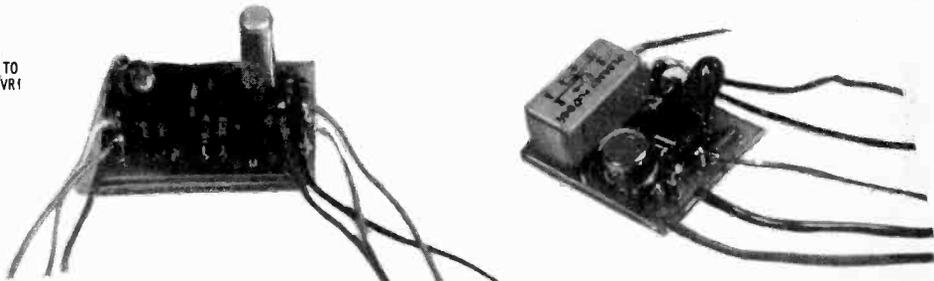

FAIL SAFE SYSTEM

As shown in the servo amplifier circuits, a means is provided to preset the torque unit rotation in the event of a transmitter or system failure. This is effected by changing the connection of grouped servo amplifier leads by means of a lightweight relay.

As shown in Fig. 11, a decoder output pulse is also applied through R1 and D1 to the base of TR1. Capacitor C1 charges rapidly during the period of the pulse, the source impedance being R1 and the collector resistance Rx of the logic unit used (approx. 4.7 kilohms).

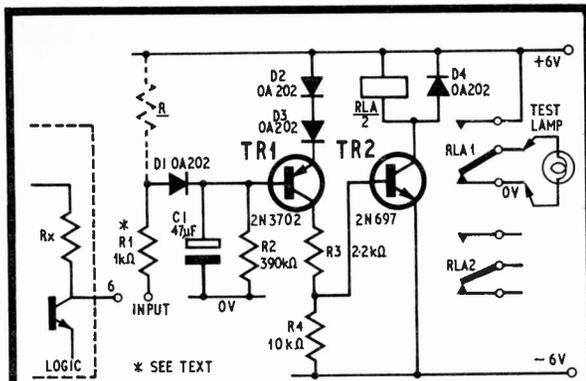


Fig. 11. Circuit diagram of "fail safe" system

COMPONENTS . . .

FAIL SAFE CIRCUIT (Fig. 11)

Resistors

R1	1kΩ	R3	2.2kΩ
R2	390kΩ	R4	10kΩ

Capacitor

C1 47µF

Transistor

TR1 2N3702
TR2 2N697

Diodes

D1, D2, D3, D4 OA202 (4 off)

Relay

RLA 12V 37mA, two sets of change over contacts (minimum resistance 240 ohms)

Miscellaneous

Printed circuit board
Solder pins
Test lamp

Assuming a gain of 50, the collector current of TR2 would be about 50mA sufficient for a small relay of more than about 240 ohms. The diode D4 is normally reverse biased but conducts when the relay is switched off protecting TR2 from the inductive back e.m.f. pulse from RLA.

CONSTRUCTION AND TEST

The components should be assembled on a printed circuit board as shown in Figs. 12 and 13 with R1 fitted and a 6V lamp connected for test, as shown. The copper strips retained under the relay must be arranged to suit the relay used.

With the -6, +6 and 0V supply lines connected, the input should be connected to +4.5V (from a battery or from a potentiometer across 0V and +6V). The time taken for the relay to operate and release on the application of +4.5V should be noted. If the "make" time is slow and the "release" time less than half second, then C1 should be checked for excess leakage current.

The unit should then be tested in connection with the working decoder, it being noted that any output could be used, but it is preferable to use one with a defined pulse-to-cycle time ratio, such as the ungated complex one previously described.

The unused contacts may be wired for servo amplifier "A" or used with any non-proportional model function. The resistor R1 forms a means to protect the logic units from accidental shorts.

The positive going logic output is derived from Rx and in certain circumstances this may produce only about 4.2V at C1.

A momentary interruption of pulses may therefore cause the fail safe device to operate after too short an interval. In this case R1 should be connected as shown. In cases where an exceptionally long interval (+5 seconds) is required before fail safe operation, D2 and D3 should be replaced by a 3.5V Zener diode. ★

CHARGE TIME CONSTANT

Diode D1 prevents discharge back through R1 and the discharge time constant is $C_1 \times R_2$. Assuming a decoder pulse of 1ms per cycle period of 40ms this ratio of 40 : 1 makes an effective charging time constant which is still greater than the discharge time and C1 steadily charges. The base of TR1 is 0.6V $V_{be} + (2 \times 0.6V)$ (D2 + D3) below the +6V rail (i.e. approx. + 4V). When C1 is charged to this value TR1 cuts off and R4 ensures that the base of TR2 goes to -6V cutting it off and allowing the relay RLA to release to the position indicated in Fig. 11 connecting the test lamp to 0V.

Referring to servo amplifier B, this is the normal working state; the fail safe acts as inoperative and no current is drawn by the circuit shown.

PULSE FAILURE MODE

In the event of pulse failure, the charge on C1 falls relatively slowly to about +4V when TR1 turns on. The base current would be $4/R_2$ and, assuming a gain of 100 for TR1, the collector current is

$$\frac{4 \times 100 \times 10^3}{390 \times 10^3} \text{ mA.}$$

or approximately 1mA base current for TR2.


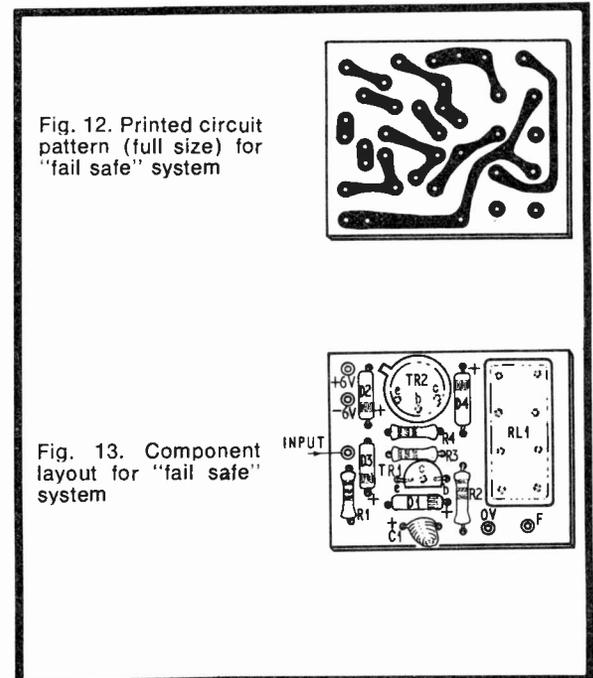


Fig. 12. Printed circuit pattern (full size) for "fail safe" system

Fig. 13. Component layout for "fail safe" system

P.E. GEMINI STEREO TUNER

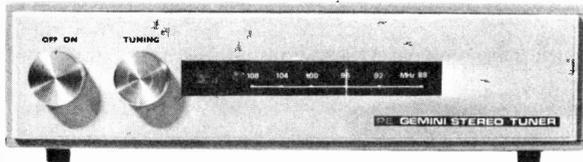

- Integrated circuit phase lock loop stereo decoder with only one easily adjusted coil
- Pre-aligned high selectivity tuner head
- Integrated circuit limiter/discriminator with one simple coil
- High selectivity ceramic filters

The P.E. Gemini Stereo Tuner is a perfect companion for the P.E. Gemini Amplifier or any other hi-fi amplifier.

I.C. SIGNAL INJECTOR

Build this rapid switching, low cost, square wave signal injector which has usable harmonics from audio to u.h.f. frequencies. Simple to make and to operate it is an ideal portable test instrument for the serviceman.

DOUBLE FLUORESCENT LAMP INVERTER

Full details are given for constructing a 12in fluorescent lamp driver which runs off a 12V battery. It can light two 8W lamps or one at 13W. Provides a high light output for low running costs—a boon to all readers who enjoy camping whether in a caravan or tent. Also useful as an emergency light.

all in APRIL'S
issue of....

**PRACTICAL
ELECTRONICS**

ON SALE FRIDAY MARCH 10



BOOK REVIEWS

RADIO AND ELECTRONIC LABORATORY HANDBOOK (8th Edition)

By M. G. Scroggie
Published by Iliffe Books (Butterworth Group)
614 pages, 9in x 6in. Price £4.75

PREVIOUS editions of this work have been referred to as "Scroggie" and one wonders whether this well-known electronics engineer, who graduated in 1922, is ever likely to retire. The amazing quality of this latest edition is the maintenance of the established down to earth style coupled with a massive quantity of technical information, updated to present day techniques.

"Scroggie" is an established technical philosophy for dedicated electronic engineers, as much as a reference work on electronics principles and practice. To newcomers from sixth form to retirement it provides almost a "bible" of sensible well planned procedures for the development laboratory. The last 100 pages or so could be treated as a book within a book, providing data, formulæ, charts and tables—"For Reference" as its chapter heading suggests. This heading reflects the practicality of working with Scroggie and we suggest that the size and price of this work should not be a deterrent to begging, borrowing or even buying. Whatever the price if you can find it, buy it!

M.A.C.

I.T.V. 1972

Published by the Independent Television Authority
240 pages, 9in x 7½in. Price 75p

THE latest edition of the guide to Independent Television is packed with information about every facet of television broadcasting from the making of a programme to audience rating techniques. There is liberal use of colour and all the statistics are presented in a clear, easy to read, manner.

This book is both a useful work of reference with a good index, and an informative insight into ITV for the average viewer.

S.R.L.

THE TECHNIQUE OF KINETIC ART

By John Tovey
Published by B. T. Batsford
144 pages, 10in x 7½in. Price £3.50

KINETIC art exploits technology to create light, colour and motion, and in this new book some of the basic techniques are discussed.

The book is divided into four main sections dealing with vision and perception, light and simple optics, mechanical and electrical control of light, and basic electrical theory. Concepts are clarified by numerous simple line drawings and photographs as well as eighteen colour plates.

For both the artist interested in engineering, and the engineer interested in art, this book provides a useful, attractive and comprehensive introduction to kinetic art.

R.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0.260V

All Types from £1.50 amp from stock.

SHROUDED TYPE
 1 amp, £7.00
 2.5 amp, £8.05
 3 amp, £11.75
 5 amp, £22.50
 15 amp, £25.00



(Panel Mounting) 2 1/2 amp, £4.75
 1 amp, £7.00, 2 1/2 amp, £8.05. All carriage paid.

L.T. TRANSFORMERS

All Primaries 220-240V	Type No.	Sec. Taps	Price	Car.
1 30, 32, 34, 36V at 5A	1	5A	£4.68	45p
2 30, 40, 50V at 5A	2	5A	£6.88	45p
3 10, 17, 18V at 10A	3	10A	£4.95	45p
4 6, 12V at 20A	4	20A	£6.43	45p
5 17, 18, 20V at 20A	5	20A	£7.28	55p
6 6, 12, 20V at 20A	6	20A	£6.88	55p
7 24V at 10A	7	10A	£5.23	45p
8 4, 6, 24, 32V at 2A	8	2A	£7.15	45p
9 6 and 12V at 10A	9	10A	£3.75	45p

RING TRANSFORMERS

Functional Versatile Educational These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. Eg. Using the RT.100 VA Model the output could be wound to give 8V, 12 1/2A, 4V, 25A, or 2V, 50A, etc. Price:

RT.100VA 3-18 turns per V. £2.25 + 28p P. & P.
 RT.300VA 2-27 turns per V. £4.20 + 38p P. & P.
 RT.1KV 1-82 turns per V. £6.50 + 58p P. & P.
 RT.2KVA 1-5 turns per V. £10.50 + 80p P. & P.
 RT.3KVA 1-5 turns per V. £14.00 + 80p P. & P.

220/240 VOLT A.C. CENTRIFUGAL FAN/BLOWER

Smooth, balanced running unit. Two pole shaded pole. Mycalex motor gives approximately 90 cubic ft./min. but draws only 240mA on run. Weight 2 1/2 lb. Case dia. 3 1/2 in, width (case only) 3 1/2 in, width overall (incl. motor) 5 2 1/2 in, aperture 3 1/2 in x 1 1/2 in. Price only £2.95 P. & P. 25p.



BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle. 0.38 amp.
 (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p. P. & P. or less transformer £2.13 plus 27p P. & P.

12 VOLT D.C. MOTOR
 Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving final speed of approx. 125 r.p.m. Size: 4 1/2 in x 2 1/2 in dia. Price 95p inc. post.



230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Hamilton or Smith. Built-in gearbox.
 1 r.p.m. cw. 1 r.p.m. a/cw. 10 r.p.h. a/cw.
 30 r.p.m. cw. 2 r.p.h. cw. 15 r.p.h. a/cw.
 60 r.p.m. cw. 3 r.p.h. a/cw. 30 r.p.h. cw.
 6 r.p.h. cw. 30 r.p.h. cw.
 cw. = clockwise rotation; a/cw. = Anticlockwise. Fraction of maker's price. All at 75p incl. P. & P.

6-12V D.C. MINI-MOTOR

Small, powerful, precision made. smooth running, reversible motor. 7,000 r.p.m. Weight only 2oz. £1 incl. P. & P.

200-250V A.C. NEON INDICATOR
 Available in red or amber £20p each. Or in green at 32p each. Minimum order 3 units. P. & P. 5p.

VENNER Electric Time Switch

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk OFF dawn. Price as above.

36V 30 AMP. A.C. OR D.C. VARIABLE L.T. SUPPLY UNIT

INPUT 220/240V a.c.
 OUTPUT CONTINUOUSLY VARIABLE 0-36V Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £58 plus £2 P. & P.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. **EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P.

NEW INDUSTRIAL KIT Ideally suited for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.
HY-LYGH T STROBE MK III This strobe has been designed and produced for use in large rooms, halls and the photographic field and utilises a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12.00, P. & P. 50p. **SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE.** For industrial or Hy-Lyght. Including reflector. £4.00 P. & P. 45p. Post paid with kit.

THE 'SUPER' HY-LYGH T KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:
 ● Heavy duty power supply.
 ● Variable speed from 1-23 flash per sec.
 ● Reactor control circuit producing an intense white light.
 Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.
ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Lyght Kit including reflector £7.00 P. & P. 45p.
7-inch POLISHED REFLECTOR Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb, 1,000V, 1,000 megohms, £34.00 carriage paid.



MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV 10 AMP

Now available **EX STOCK**. Supplied with full data and applications sheet. Price £1.05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

G.E.C. 12 WAY 15 AMP CONNECTORS

NEW in makers carton. BAKELITE £1.25 per doz. FLEXIBLE £1.50 per doz. Post paid (Minimum J doz).



PROGRAMME TIMERS

(Mfg. by Magnetic Devices Ltd.). 240V A.C. 5 r.p.m. 'Crouzet' motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW PRICE £5.75. P. & P. 25p.



D.C. AMMETERS NEW!

100mA, 200mA, £1.75, incl. P. & P.
 500mA, £1.90, incl. P. & P.



230V A.C. SOLENOID

Extremely powerful with approx. 14lb pull, 1in travel. Fitted with mounting feet. Size: 4in long, 2 1/2 in wide, 3in high. £2.00 incl. P. & P.



230-250 VOLT A.C. SOLENOID

Manufactured by Westool Ltd. (similar in appearance to above illustration). Approx. 1 1/2 lb pull. Feet size 1 1/2 in x 1 1/2 in. Price 85p incl. P. & P.

Superior Quality Products Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 5 kΩ, 140mA. Diameter 3 1/2 in. Shaft length 1/2 in, dia. 1/8 in. All at £1.50 each. P. & P. 5p.
 50 WATT. 1/5/10/25/50/100/250/500/1/1/1/5/2-5/5kΩ. All at £1.12 each. P. & P. 11p.
 25 WATT. 10/25/50/100/250/500/1/1/1-5/2-5/3-5/5kΩ. All at 78p each. P. & P. 15p.
 Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats. 18p ea.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS COMPETITIVE PRICES

Col. (1)	1	2	3	4
Coil ohms	45	6-9	2 HD M	50p
Col. (2)	185	12-18	4 c/o	73p
Working d.c. volts	280	9-12	2 c/o	73p*
Col. (3)	700	16-24	4H 2B	63p*
Contracts	700	12-24	2 c/o	63p*
Col. (4)	700	15-35	2 c/o HD	73p*
Price	700	16-24	6M	65p*
HD	1,250	24-36	4 c/o	63p*
Incl. duty	2,500	36-48	6M	63p*
Heavy duty	2,400	30-48	4 c/o	50p
Incl. Base	5,900	40-70	6M	63p*
All post paid.	9,000	40-70	2 c/o	50p*
	15k	85-110	6M	50p*

12 VOLT D.C. RELAY

Three sets c/o contacts rated at 5 amps. 78p including P. & P. (Similar to illustration below.)



'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)


Three sets c/o contacts rated at 5 amps. PRICE: 50p. P. & P. 10p. (100 lots £40 including P. & P.)

KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. Boxed PRICE: 40p. P. & P. 5p. (100 lots £32 including P. & P.)

UNISELECTOR SWITCHES

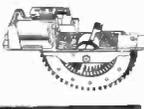NEW 4 Bank 25 Way 24V d.c. operation. £5.88, P. & P. 12p.
6 Bank 25 Way 24V d.c. £6.50, P. & P. 12p.
8 Bank 25 Way, 24V d.c. operation. £7.62 plus 22p. P. & P.



230 VOLT A.C. SOLENOID OPERATED FLUID VALVE

Adjustable flow control, all metal construction. Will handle hot or cold liquids: water, oil, paraffin, etc. Available with 1/2 in inlet/outlet or 3/8 in inlet/outlet. Either type £1.50, P. & P. 20p.



LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.75. P. & P. 18p.



LIGHT SENSITIVE SWITCHES

Kit includes ORP.12 Photocell, Relay Transistor Circuit. For 6 or 12V D.C. operation. Price £1.50 plus 12p P. & P. ORP. 12 and Circuit 63p post paid.



'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob lin. Fixing hole ONE bank 10s, TWO bank 10s, THREE bank 55p; incl. P. & P.



'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. NEW in maker's carton. PRICE: 10 for £1.90 including P. & P.



MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 inc. post. (Min. order 20).



All Mail Orders—Callers—Ample Parking
Dept. PE2, 57 BRIDGMAN ROAD
LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
 Phone 01-437 0576

Handwritten notes and signatures at the bottom of the page, including "60p x 15" and "10.5p x 10" with arrows pointing to specific items.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
 - Radio Amateurs' Examination
 - General Radiocommunications Certificate
 - C. & G. Radio Servicing Theory
 - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics
Member of the ABCC Accredited by the CACC



INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. FA25, Intertext House, Stewarts Rd., London SW8 4UJ

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME _____ AGE _____
(Block Capitals Please)

ADDRESS _____

3/72

INTERNATIONAL CORRESPONDENCE SCHOOLS

VALVES

**SAME DAY SERVICE
NEW! TESTED! GUARANTEED!**

SETS 1R5, 1S5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for £1.02. DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	-28	30C17	-76	EAF42	-50	EM81	-41	PCL84	-34	UBCA1	-32
1S5	-22	30C18	-61	EB41	-40	EM84	-32	PCL85	-38	UBF80	-34
1T4	-16	30F15	-64	EB91	-10	EM87	-34	PCL86	-38	UBF89	-32
384	-28	30F11	-61	EB33	-40	EY51	-38	PCL88	-65	UCB84	-32
3V4	-37	30FL12	-69	EBC41	-54	EY86	-29	PCL800	-75	UCB85	-35
5U4G	-31	30FL14	-68	EBC90	-22	EZ40	-43	PENA4J	-77	UCF80	-32
5U4G	-35	30L1	-29	EBF80	-32	EZ41	-43	PEN36C	-70	UCI42	-58
5Y3GT	-26	30L13	-57	EBF89	-29	EZ80	-22	PFL200	-52	UCI81	-32
5Z4G	-35	30L17	-67	ECC81	-17	EZ81	-23	PL36	-49	UCI82	-32
630L2	-54	30F14	-57	ECC82	-20	GZ30	-34	PL81	-44	UCI83	-55
6AL5	-11	30F12	-72	ECC83	-35	GZ32	-40	PL81A	-47	UCF41	-56
6AM6	-13	30F19	-57	ECC85	-34	GZ34	-48	PL82	-31	UF80	-30
6AQ5	-22	30PL1	-60	ECC804	-54	KT41	-77	PL83	-33	UL41	-57
6AT6	-20	30PL13	-89	ECCF80	-27	KT61	-55	PL84	-30	UL44	£1.00
6AU6	-20	30PL14	-65	ECCF82	-26	KT66	-78	PL500	-63	UL84	-30
6BA6	-20	33L6GT	-45	ECH45	-30	LN319	-63	PL504	-63	UM84	-22
6BE6	-21	33W4	-25	ECH42	-61	LN329	-72	PM84	-33	UY41	-42
6BJ6	-41	33Z4GT	-25	ECH81	-29	LN339	-63	PX25	-95	VP85	-25
6BW7	-52	807	-45	ECH83	-40	N78	-87	PY32	-55	VP48	-77
6F14	-40	6063	-62	ECH84	-36	P61	-40	PY38	-55	X78	£2.75
6E23	-68	AC/VP2	-77	ECL80	-30	PABC80	-34	PY81	-25	X79	£2.75
6E25	-53	B349	-65	ECL82	-31	PC86	-47	PY82	-25	Z77	-22
6K7G	-12	B729	-62	ECL86	-35	PC88	-47	PY83	-28	Transistors	
6Q7G	-35	CY31	-30	EF41	-60	PC96	-42	PY88	-33	AC107	-17
6N7GT	-30	DAF91	-22	EF80	-23	PC97	-29	PY800	-34	AC127	-18
6V6G	-28	DAF96	-38	EF85	-28	PC900	-31	PY801	-31	AD140	-37
6B8GT	-28	DF33	-38	EF86	-30	PCC84	-29	R19	-30	AF115	-20
6X4	-23	DF91	-16	EF89	-26	PCC85	-25	R20	-56	AF116	-20
6X3GT	-28	DF96	-36	EF91	-13	PCC88	-40	U25	-64	AF117	-20
12A7	-17	DK32	-33	EF98	-65	PCC89	-45	U26	-56	AF118	-48
12AU6	-20	DK91	-28	EF183	-28	PCC188	-48	U47	-64	AF125	-17
12AU7	-20	DK92	-38	EF184	-31	PCC805	-56	U49	-56	AF127	-17
12AX7	-22	DK96	-38	EFH90	-35	PCF80	-28	U50	-28	OC26	-25
19B6GG	-87	DL35	-40	EL33	-55	PCF82	-31	U52	-31	OC44	-12
20E2	-67	DL92	-26	EL34	-45	PCF86	-35	U78	-24	OC45	-12
20P3	-77	DL94	-37	EL41	-34	PCF800	-58	U191	-59	OC71	-12
20P4	-92	DL96	-38	EL84	-23	PCF805	-61	U193	-42	OC72	-12
25L6GT	-20	DY86	-24	EL90	-26	PCF808	-62	U251	-64	OC75	-12
25U4GT	-57	DY87	-24	EL95	-33	PCF808	-68	U801	-80	OC82	-12
30C1	-28	DY802	-33	EL500	-62	PCL82	-32	UABC80	-32	OC82D	-12
30C15	-58	EABC80	-32	EM80	-41	PCL83	-57	UAF42	-51	OC170	-23

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD ESSEX. Tel. 01-550 7441

Post/packing on 1 valve 6p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

LIGHT SENSITIVE

INTEGRATED CIRCUIT

ARE YOU STILL USING PHOTOTRANSISTORS, DIODES AND OTHER PHOTOCELLS?

—KEEP UP TO DATE

WE ARE OFFERING THE COMPLETE SWITCH—

PHOTODETECTOR +
AMPLIFIER +
TRIGGER +

DRIVER—ALL IN A SINGLE 4 mm. DIA. CAN

—WILL DRIVE RELAY OR TRIAC FOR AUTOMATIC LIGHT SWITCHING CONTROL. BURGLAR ALARM BEAM BREAK DETECTOR. AUTOMATIC DOOR CONTROL AND MANY OTHER APPLICATIONS.

P.O. CHEQUES payable to ELBON and crossed LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX



PRICE ONLY 65p each + 5p post and packing) with full operating instructions. 10 for £5.75 (post free).



P.E. SCORPIO IGNITION SYSTEM



Complete kit of high quality components — £10.75. p.p. 50p
All parts available separately send S.A.E. for list

AMC ELECTRONICS LTD.,
160, DRAKE ST., ROCHDALE, LANCs.

Gerry Brown . . . ON THE FRINGE



ELECTROPSYCHEDELIA ?

Flicker phenomena, discussed by many and at some length by Dr W. Grey Walter in his book "The Living Brain", is the effect which sometimes manifests itself as the result of the pulsating nature of the light from cine projectors, or the intermittent flashing of sunlight through roadside trees during a drive in the car. This phenomena is often exploited in such places as discotheques where strobed xenon lamps are employed.

The effect is difficult to describe in purely objective terms, but, for most observers, this generally seems to evidence itself as a form of pleasant swimming sensation or a feeling of moving through time. To a large extent the degree of influence appears to be related to the flicker rate of the lamp and, in this context, probably has the greatest effect when it is synchronous with the frequency of the "alpha" waveform produced by the brain.

The amplitude of this alpha rhythm seems, in most cases, to be very much suppressed so that for many individuals the phenomenon may be either just noticeable or entirely absent.

However, a method for selecting and, even, raising the intensity of the elusive rhythm has just been re-discovered. This has resulted in the brand-new craze which is currently sweeping through the U.S.A., previously called "photic" stimulation back in the 1950's, and now enjoying the title "bio-feedback".

In reality, the concept behind this bio-feedback lark is an attempt to help people teach themselves the art of controlling their brain rhythms, with the intention of encouraging an equivalent condition of that transcendental experience, only hitherto reached by masters of deep meditation!

Basic operation of a bio-feedback set-up will be seen from Fig. 1. Electrodes, dampened in saline

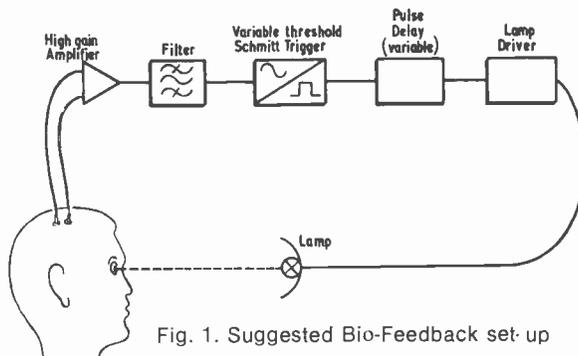


Fig. 1. Suggested Bio-Feedback set-up

solution and attached to the subject's scalp, pick up the very much attenuated signals originating in the cortex of the brain. They are then amplified several hundred thousand times and, subsequently, filtered since the required signals are almost always buried deep in either noise, or unwanted signals of greater amplitude.

The resulting output is fed to a Schmitt trigger prior to operating a simple delay circuit which either flashes a lamp into the subject's eyes, or controls an audio oscillator. In this way the flash-rate and delay can be adjusted to achieve a constant positive feedback such that the lamp flashes at the most effective point in the brain's alpha waveform.

This, essentially, instant way of "mind-travelling" could have quite exciting possibilities and, although not a therapy worthy of recommendation to epileptics, may hold some of the keys to the more arcane aspects of psi phenomena.

I notice that this rather costly form of "everyman's electroencephalography" is already beginning to catch on in this country. Anyone for back-pocket hypnosis?

FAST TALKER

For too long now the blind have been forced to contend with "talking-books" which produce far fewer words per unit time than could be read visually. Up till quite recently, unless these people were prepared to tolerate a kind of "chipmunk" sound, the speed of playback could not be increased.

The visually handicapped are not the only ones who have cause for

complaint. How about education for adults and children having high IQs and capable of absorbing data at great rates, but who are tied by the speed at which the most backward can understand the same information?

Such problems are almost as good as solved, because by next summer the Cambridge Research and Development Group in Westport, Conn., U.S.A. is scheduled to have a helpful little i.c. device available. Priced as low as \$10 (£6) the i.c. will permit normal speech rate to be electronically varied from about 100 to 500 words per minute without the annoyance of an accompanying change in pitch! (useful for solid-state echo too).

Operation of the device, Fig. 2, is, I understand, similar in principle to one developed by Phillips a short while ago. This relies on the so-called "bucket-brigade" technique employing chains of capacitors interposed between charge-transfer transistors forming an analog version of the shift-register. Data is passed from "bucket" to "bucket" in the form of charge deficits clocked through the entire register at a rate determined by an external clock-generator.

While such an idea must represent a considerable boon to the handicapped, I cannot help feeling that its total value will need to be revised if ever the disc-jockeying fraternity latch-on to its possibilities!

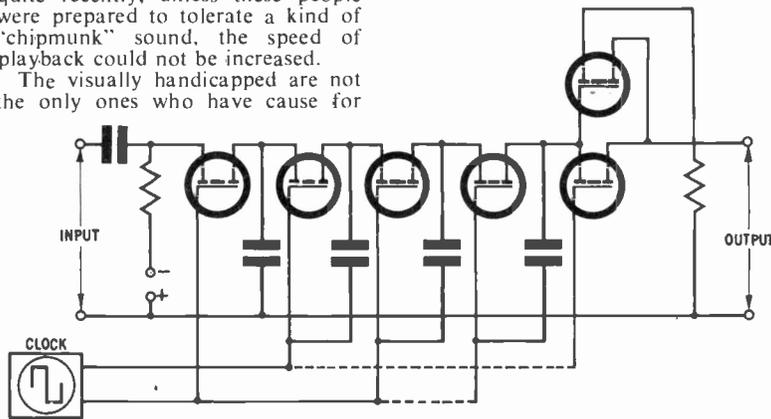


Fig. 2. Circuit diagram for varying speech rate

THE UNIJUNCTION TRANSISTOR

By E. C. Copperthwaite

ALTHOUGH it is only in the last few years that unijunction transistors have found popularity among non-professional users, they were demonstrated by Henrich Welker in France as far back as 1948. This device was made commercially available due to the efforts of I. A. Lesk of Motorola in 1952.

There is no other solid state counterpart to the unijunction transistor (UJT), nor is there any vacuum tube that is functionally similar. Its unique characteristics make it particularly suitable for use in oscillators, timing circuits and thyristor trigger circuits.

TYPES OF CONSTRUCTION

Most commercially available unijunction transistors are of the cube or bar structure (see Fig. 1), and these have been in use for many years. But as these components were not readily adaptable to automatic production methods, Motorola's design team have produced an annular construction type.

The die used to produce this annular type is fabricated using techniques similar to those used for making silicon annular transistors. This relatively new construction method is now batch-processed like conventional transistors for extensive availability and considerable lowering of costs.

Tests have proved that the resultant uniformity also simplifies various applications and intrinsic stand-off ratios (see below) are confined to a narrow range of variation.

GENERAL PRINCIPLES

The UJT (originally called a double base diode) has three terminals namely the emitter, base-one and base-two (Fig. 2a). The emitter is composed of a *p*-type junction and is positioned near the centre of a pair of dissimilar bases of *n*-type silicon (B1, B2). Between B1 and B2 the unijunction has the characteristics of an ordinary resistance; this resistance is called the interbase resistance (R_{BB}) and at a temperature of 25°C can vary between 4.7 kilohms and 9.1 kilohms for different devices.

It is simplest to describe the action of a unijunction with reference to the equivalent circuit of Fig. 2b. With no current flowing in the emitter a voltage will appear at the emitter proportional to the interbase voltage (V_{BB}). For current to flow into the emitter this voltage plus the forward voltage drop of the emitter junction (V_D) must be exceeded. When this occurs, the injection of holes into the silicon bar causes an increase in the number of electrons in the base and hence the resistance of base-1 drops, producing the negative resistance region shown in Fig. 3.

The threshold voltage is called the emitter peak point voltage (V_P). When the emitter voltage (V_E) is below V_P only a small leakage (I_{EO}) flows.

The peak voltage (V_P) of the unijunction transistor varies in proportion to the interbase voltage (V_{BB}) according to the equation

$$V_P = \eta V_{BB} + V_D$$

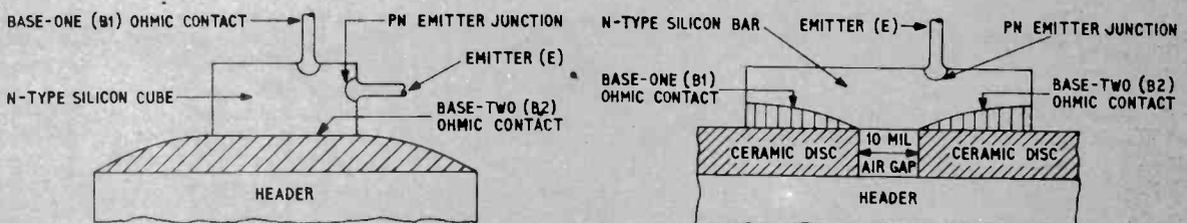



Fig. 1. Cross sectional views of unijunction structures. (a) cube structure; (b) bar structure



UBC-4
Battery Charger



CR-1 Car Radio

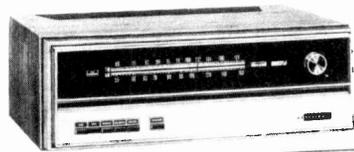

AJ-29 Tuner




MI-29
Fish Spotter



TRENT
Speaker

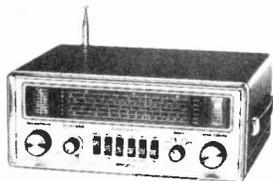*The new
HEATHKIT
catalogue is
now available
... **FREE**
on request*



GR-78 Shortwave Receiver



GD-48 Metal
Locator



The new **AR-2000** Tuner Amplifier



HEATH (Gloucester) LTD., GLOUCESTER GL2 6EE

Why not visit the Heathkit
showrooms in London or
Birmingham?

233 Tottenham Court Road
London

17-18 St. Martin's House
Birmingham

Please send me the free Heathkit Catalogue

Name

Address

PEO3

- LARGE STOCKS
 - GOOD SERVICE
 - ATTRACTIVE DISCOUNT
- Satisfaction Guaranteed

ELECTROVALUE

Electronic Component Specialists

SEMI-CONDUCTORS

Brand new, guaranteed to spec. No seconds or surplus.

1B40K10 175p	2N3055 60p	40361 55p	AF124 24p	BC184L 41p	BFY90 104p	OA95 6p
1N914 175p	2N3325 53p	40362 68p	AF125 24p	BC186 42p	B5X20 16p	OA200 9p
1N916 70p	2N3405 60p	40406 75p	AF126 22p	BC212L 16p	BY164 45p	OA202 10p
1N11763A 14p	2N3663 52p	40408 70p	AF127 22p	BC213L 16p	BY238 18p	OC19 50p
1N3754 20p	2N3702 13p	40412 67p	AF139 33p	BC214L 16p	BYX38 42p	OC25 42p
1N5399 21p	2N3703 13p	40430 140p	AF239 36p	BC257 9p	BY300 38p	OC28 70p
1N5402 28p	2N3704 13p	40432 185p	AL102 77p	BC258 9p	BY383 10p	OC29 74p
1N5407 45p	2N3705 13p	40512 195p	AS526 27p	BC259 9p	300R 38p	OC35 60p
1544 5p	2N3706 13p	40602 52p	AS727 36p	BC267 17p	C407 17p	OC36 65p
15940 5p	2N3707 13p	40669 140p	AS728 27p	BC268 15p	C762 19p	OC41 42p
2N696 17p	2N3708 10p	AC107 46p	AS729 36p	BC269 17p	C1412 102p	OC42 46p
2N697 18p	2N3709 11p	AC126 20p	AU111 97p	BC300 49p	E2512 164p	OC44 42p
2N706 12p	2N3710 13p	AC127 20p	B30C250 24p	BC301 37p	EA403 10p	OC45 38p
2N930 29p	2N3711 13p	AC128 20p	B30C550 24p	BC303 60p	EB383 10p	OC70 21p
2N1131 29p	2N3731 120p	AC141H 37p	30C 34p	BCY30 60p	EC401 18p	OC71 38p
2N1132 29p	2N3794 15p	AC141HK 37p	B1912 66p	BCY31 75p	EC402 17p	OC72 38p
2N1302 19p	2N3819 23p	AC142H 25p	B5041 72p	BCY70 18p	ER900 54p	OC75 40p
2N1303 19p	2N3820 53p	AC142HK 29p	BA102 25p	BCY71 33p	MC140 25p	OC81 25p
2N1304 26p	2N3904 35p	AC153K 22p	BA130 22p	BCY72 15p	MJ481 120p	OC81D 25p
2N1305 26p	2N4036 55p	AC176K 15p	BA145 27p	BD121 105p	MA491 135p	OC83 25p
2N1306 33p	2N4036 55p	AC176K 15p	BA155 15p	BD123 105p	MJ371 108p	OC84 25p
2N1307 33p	2N4058 13p	AC187K 17p	BA156 13p	BD124 100p	MJ521 92p	P346 26p
2N1308 36p	2N4059 10p	AC188K 23p	BAX13 13p	BD130 50p	MJE2955 165p	S2CN1 10p
2N1309 36p	2N4060 11p	*AC187K/ 40p	BB103/B 16p	BD131 79p	MJE3055 82p	SC141D 187p
2N1596 102p	2N4061 11p	188K 40p	BB103/G 16p	BD132 86p	MPF102 37p	SC146D 247p
2N1599 122p	2N4062 12p	ACV17 31p	BC145 12p	BD135 38p	MP5631 35p	SD1 13p
2N1613 23p	2N4124 18p	ACV18 19p	BC108 10p	BD136 44p	MP5634 30p	SD4 13p
2N1711 26p	2N4126 27p	ACV19 23p	BC109 12p	BD141 227p	NKT211 25p	V763 28p
2N1893 54p	2N4284 24p	ACV20 20p	BC122 21p	BDY20 92p	NKT212 25p	W106B1 45p
2N2147 95p	2N4286 15p	ACV21 21p	BC125 15p	BF115 23p	NKT213 25p	W106D1 83p
2N2218 34p	2N4289 15p	ACV22 21p	BC126 22p	BF167 18p	NKT214 23p	WO2 40p
2N2218A 44p	2N4291 15p	ACV23 63p	BC140 30p	BF173 19p	NKT217 50p	WPO2 92p
2N2219 36p	2N4292 15p	ACV40 31p	BC147 10p	BF177 25p	NKT261 21p	ZTX300 15p
2N2219A 53p	2N4440 24p	ACV41 18p	BC148 9p	BF178 31p	NKT271 18p	ZTX301 15p
2N2270 62p	2N4443 111p	ACV44 31p	BC149 70p	BF194 14p	NKT274 18p	ZTX302 22p
2N2369A 19p	2N4906 305p	AD140 63p	BC153 19p	BF195 15p	NKT275 23p	ZTX303 22p
2N2483 35p	2N4915 215p	AD142 50p	BC154 20p	BF244 30p	NKT403 65p	ZTX304 27p
2N2484 42p	2N4991 62p	AD149 58p	BC157 12p	BF254 14p	NKT404 61p	ZTX330 23p
2N2646 47p	2N5062 61p	AD150 50p	BC158 11p	BF255 15p	NKT405 79p	ZTX331 27p
2N2900 38p	2N5086 38p	AD161 33p	BC159 12p	BF258 90p	NKT603F 30p	ZTX500 18p
2N2904A 42p	2N5163 25p	AD162 36p	BC167 11p	BF259 21p	NKT613F 30p	ZTX501 21p
2N2905 44p	2N5172 18p	*AD161/ 16p	BC168 10p	BF284 35p	NKT674F 24p	ZTX502 25p
2N2905A 47p	2N5192 125p	162 16p	BC169 11p	BF285 32p	NKT677F 22p	ZTX503 22p
2N2924 20p	2N5195 147p	AF114 24p	BC177 14p	BF287 29p	NKT713 30p	ZTX504 52p
2N2925 72p	2N5457 49p	AF115 24p	BC178 13p	BF288 26p	NKT753 27p	ZTX530 27p
2N2926 72p	2N5459 49p	AF116 22p	BC179 14p	BFY50 23p	OA47 8p	ZTX531 33p
2N3053 27p	40250 71p	AF117 11p	BC182L 11p	BFY51 80p	OA90 6p	
2N3054 60p	40251 89p	AF118 82p	BC183L 10p	BFY52 73p	OA91 5p	

Appointed Distributors for SIEMENS (UK) Ltd.

CAPACITORS, I.C.'S, POT CORES, THYRISTORS, RECTIFIERS, ETC.

SIEMENS 5% TOLERANCE POLYCARBONATE CAPACITORS

250V up to 0.1mF: 100V 0.1mF and above
0-01, 0-012, 0-015, 0-018, 0-022, 0-027, 0-5p
0-033, 0-039, 0-045, 0-056, 0-068, 0-082, 0-1p
0-12, 0-15, 0-18, 0-22
0-27, 7p; 0-33, 0-39, 9d; 0-47, 10p; 0-56, 13p; 0-68, 15p.

BAXENDALL SPEAKER KIT

As originally designed and described by P. J. Baxendall in Wireless World. 10 watt/15Ω with frequency equaliser, speaker unit and special cabinet (size approx. 18" x 12" x 10") in pack-flat form. Inc. carriage paid in U.K. £13.90

MAIN LINE AMPLIFIER KITS

Very powerful 70 watt module, nett £12.60
Power supply list, nett £6.00.
Matching pre-amp Kit.
(Mag. or Xtal input), nett £3.30.
For stereo to build in your own cabinet, etc.
2 - 70W amps, control unit and angled matched controls, power unit, nett £38.40.

VEROBOARD

Copper clad, 0.1 matrix
0-1 matrix: 2.5in x 3.75in 23p; 3.75 x 3.75in, 26p; 2.5in x 5in, 26p; 3.75in x 5in, 29p.
0-15 matrix: 2.5in x 3.75in, 17p; 3.75in x 3.75, 26p; 2.5in x 5in, 26p; 3.75in x 5in, 30p.
0-2in matrix 5in x 3.4in, 37p.

ZENER DIODES 5%, full range E24 values:

400mW: 2.7V to 30V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V 60p each.
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

PUBLICATIONS

The Book of Transistor Equivalents (BP.1) 40p
Handbook of Tested Transistor Circuits by H. Ness (BP.3) 40p
Radio and Electronic Colour Code and Data Wall Chart (BP.7) 15p
Any of above ordered singly, add 3p P. & P.

DISCOUNTS

Not allowed on nett items
10% on orders for components for £5 or more.
15% on orders for components for £15 or more.

POSTAGE AND PACKING

FREE on orders over £2. Please add 10p if orders under £2.
Overseas orders welcome: carriage and insurance charged at cost.

U.S.A. Customers are recommended to get in touch with ELECTRO-VALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

CARBON TRACK POTENTIOMETERS

Long spindles. Double wiper ensures minimum noise level.
SINGLE GANG linear 100Ω to 2.2MΩ, 12p; Single gang los. 4.7K to 2.2MΩ, 12p; DUAL GANG linear 4.7KΩ to 2.2MΩ, 42p; Dual gang los. 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 42p; 1MΩ only, 42p; Dual potentiometer, 10K only, 42p Any type with 1A-D main switch, 42p extra.
Only decades of 10, 22 and 47 available in ranges quoted.
DUAL CONCENTRIC in any combination of above values, 60p. With switch 72p.

CARBON SKELETON PRE-SETS

Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

COLVERN 3 watt Wire-wound Potentiometers, 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 100K each.

INSULATED SCREW TERMINALS

In range of seven colours, each 12p. Matching plugs, 2mm 5p, 4mm 7p.

RESISTORS 10% — 5% — 2%

Code	Power	Tolerance	Range	Values available
C	1/20W	5%	82 Ω - 220K Ω	E12
C	1/20W	5%	4.7 Ω - 470K Ω	E24
C	1/4W	10%	4.7 Ω - 10M Ω	E12
C	1/2W	5%	4.7 Ω - 10M Ω	E24
C	1W	10%	4.7 Ω - 10M Ω	E12
MO	1/2W	2%	10 Ω - 1M Ω	E24
WW	1W	10% ± 1/20 Ω	0.22 Ω - 3.9 Ω	E12
WW	7W	5%	12 Ω - 10K Ω	E12
WW	7W	5%	12 Ω - 10K Ω	E12

Codes: C = carbon film high stability low noise
MO = metal oxide electrostatic TR5 ultra low noise
WW = wire-wound Plessey

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

CAPACITORS

MULLARD polyester C280 series
250V 20%; 0.01, 0.22, 0.033, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p, 10% and up to 2.2μF 24p.

MULLARD SUB-MIN. ELECTROLYTICS

C426 range, axial lead, 6p each
Values (μF/V): 0.6/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 15/10; 16/40; 20/16; 20/64; and up to 500/2.5

LARGE CAPACITORS

High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, 114p; 2500/64, 77p; 2500/70, 98p; 5000/25, 100p; 5000/50, 110p; 5000/100, 129p; 10000/50, 140p.
For full range see catalogue.

Let Electrovalue supply you with components for designs published by Practical Electronics. See the Electrovalue 64-page Catalogue 10p post free.

ELECTROVALUE

An independent company established 1965
Dept. PE372, 28 St. Judes Rd., Englefield Green, EGHAM, Surrey TW20 8NB
Phone: Egham (0784-3) 5533 and 4757. Telex 264475
Hours: 9.5.30 daily. 1 p.m. Saturday

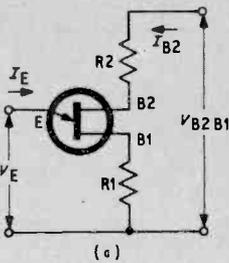


Fig. 2a. Unijunction symbol and nomenclature

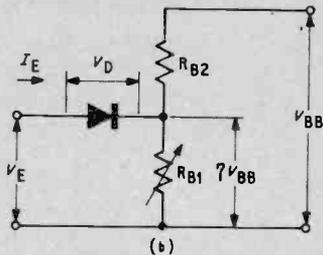


Fig. 2b. Equivalent circuit of UJT

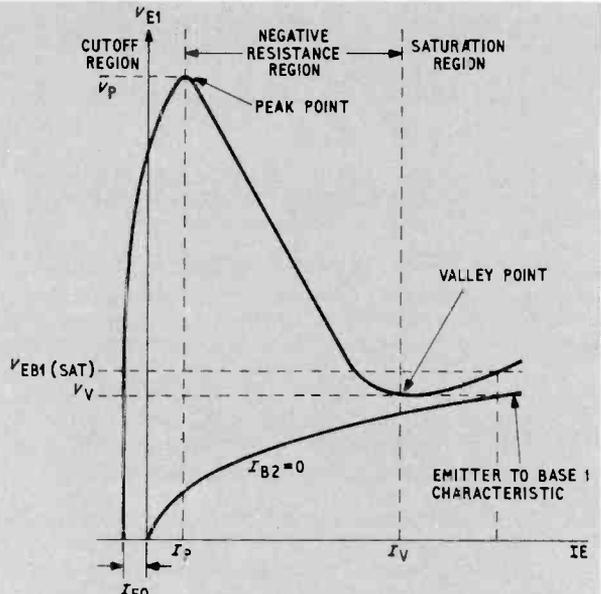


Fig. 3. Static emitter characteristic of UJT

The parameter η is a constant and is termed the intrinsic stand-off ratio. It is that fraction of the interbase voltage which appears as part of the peak point voltage, this important parameter is a constant for a given device and the value lies between 0.51 and 0.82. The equivalent diode emitter voltage (V_D) is in the order of 0.5 volts depending on the UJT and the temperature. With an increase of temperature V_P decreases, but it is possible to overcome this variation by making use of the positive temperature coefficient of R_{BB} . If a resistor R_2 is used in series with base-two (see Fig. 2) the temperature variation of R_{BB} will compensate for the original loss.

TYPES OF UJT

Fig. 4a shows the conventional type (UJT) which is a single junction device having an emitter and two dissimilar bases.

Fig. 4b is called a complementary type (CUJT) and works by applying opposite current and voltage polarities to those used in the conventional UJT. A greater circuit flexibility is now obtainable and can be comparable to *pnp* and *npn* transistors. The CUJT has shown better stability, improved uniformity and closer intrinsic stand-off ratio. It is more reliable over the specified temperature range allowing less compensation control.

TABLE 1: UJT NOMENCLATURE

SYMBOL	DEFINITION
I_E	Emitter current
I_{EO}	Emitter reverse current
I_P	Peak point emitter current. The total emitter current that can flow without permitting the UJT to go into the negative resistance region.
I_V	Valley point emitter current. Represents the current flowing in the emitter when the UJT is biased to the valley point.
R_{BB}	Interbase resistance. The resistance measured between base-two and base-one at a specified interbase voltage.
V_{BB}	Voltage existing across base-two and base-one.
V_P	Peak point emitter voltage.
V_D	Forward voltage drop of the emitter junction.
V_V	Valley point emitter voltage.
η	Intrinsic stand-off ratio.
αR_{BB}	Interbase resistance temperature coefficient. Variation of resistance between B2 and B1 over the specified temperature range.

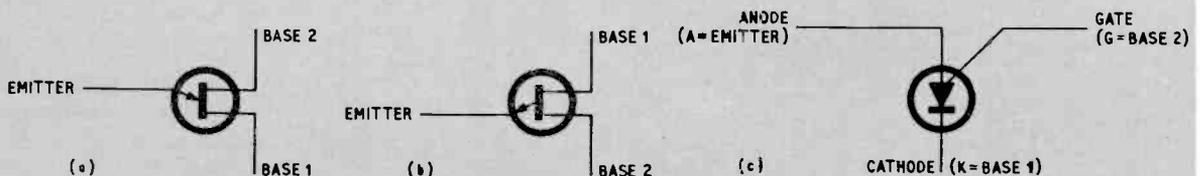


Fig. 4. Types of UJT. (a) conventional UJT; (b) complementary UJT; (c) programmable UJT (PUT)

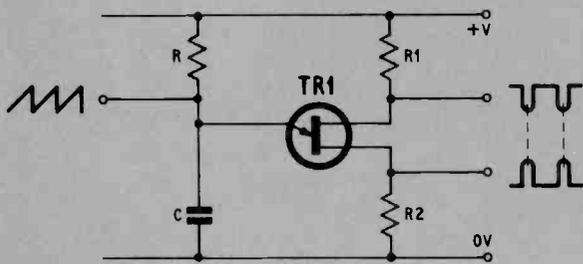


Fig. 5. Relaxation oscillator circuit showing waveforms available

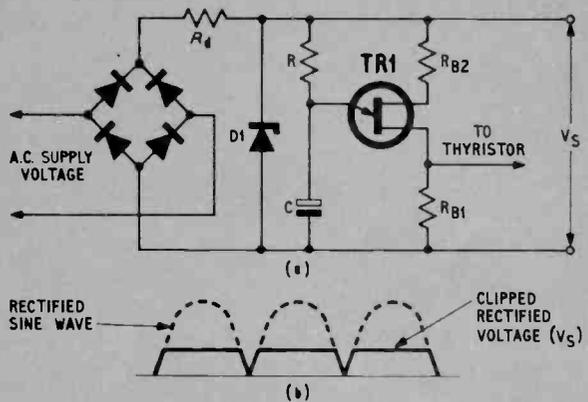


Fig. 6. (a) Full wave control circuit; (b) Zener clipped rectified voltage

Fig. 4c illustrates a third configuration, termed a programmable type (PUT). The PUT is programmable in that a number of characteristics that are set in the conventional type (i.e. valley current, peak current and interbase resistance) can be adjusted accordingly or programmed into the PUT at the designer's discretion. With careful selection of additional resistors the designer can turn the device into any one of a large number of discrete UJT's.

The PUT is a planar passivated *ppn* element and hence is not a true UJT, it is conventionally represented by a symbol similar to the SCR. The PUT's electrodes are known as the anode, gate and cathode, which correspond to emitter, base-two and base-one respectively.

FLEXIBILITY

The UJT is a unique device in that it can be used for any number of applications involving oscillation, timing circuits and triggering devices for turning-on thyristors.

UJT's offer the advantage of being excellent circuit simplifiers allowing the elimination of a number of components. For example, one UJT used in the bistable mode (see Fig. 5) can provide the function that normally would require two transistors and the associated capacitors and resistors. Outputs can be taken from any of the three electrodes: an

approximation of a sawtooth waveform from the emitter; a positive pulse from base-one and a negative pulse from base-two. A high degree of frequency stability and accuracy can be obtained by the careful selection of the timing constants RC .

APPLICATIONS

A full-wave control circuit shown in Fig. 6a with Zener clipped rectified voltage Fig. 6b. The resistor R_d is chosen to limit the current through the diode D_1 enabling this device to work within its rated specification.

Fig. 7a shows a unijunction trigger circuit for a gated thyristor and its associated waveforms Fig. 7b. As capacitor C_1 is being charged current (I_{FO}) flows through the interbase resistance (R_{BB}) of the unijunction, say of the order of $1\mu A$. Resistance R_{B1} is included in the circuit to provide a path for this current and prevent an undesirable turn-on of the thyristor through its gate. R_{B1} is calculated so that a maximum voltage developed across it will be less than 0.2 volt. For a typical UJT the resistance of R_{BB} lies between 4.7 kilohms and 9.1 kilohms, so with an applied operating voltage of 20 volts, the value of R_{B1} would be:

$$R_{B1} = \frac{0.2 \times R_{BB} (\text{min})}{V_S} = \frac{0.2 \times 4.7k\Omega}{20} = 47 \text{ ohms}$$


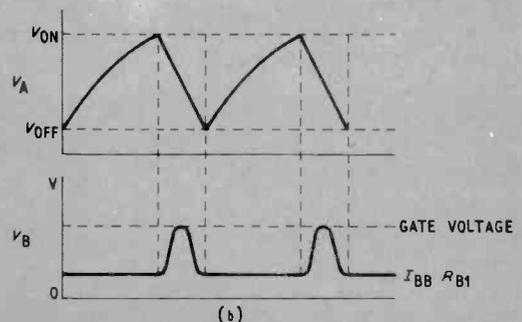
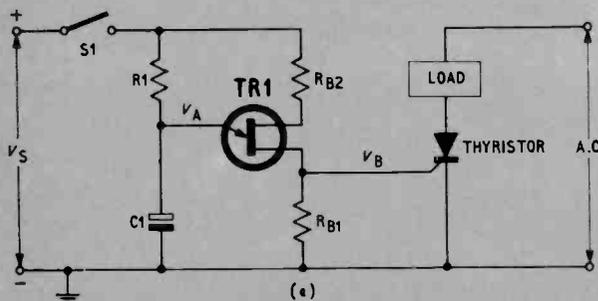


Fig. 7. Relaxation oscillator trigger circuit and associated waveforms

BSR LATEST SUPERSLIM STEREO & MONO

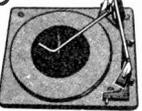
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 133 11in. Above motor board 3in. below motor board 2in.



with STEREO and MONO XTAL £7.75 Post 25p.

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 2-stage with triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer. Knobs, loudspeaker, valves ECL82, EZ80/81. Response £4 Post 25p. 50-12,000 cps. Sensitivity 200mV.

R.C.S. PORTABLE PLAYER CABINET

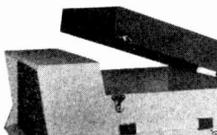

Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 x 15 8in. Metal fittings. Carrying handle. Two tone recessed covers. Popular Colours. £4 Post 25p.

GARRARD SINGLE PLAY TA Mk II. Ideal Discoboth or Hi-Fi. Stereo/Mono. £10

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond and Mono Sapphire. SP25 Mk III £16. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (state player make and model). £2.75

R.C.S. PLASTIC COVERS FOR ABOVE BASE. £2.25

EMI PICK-UP ARM. With mono xtal and stylus £1.25. HI-FI PICK UP CARTRIDGES. Diamond Stereo/Mono GTA £2.50; GP94 £2.50; GP93 £2.00; Mono GP91 £1.50; ACOS standard fitting with L.P. stylus only 50p.

E.M.I. WOOFER AND TWEETER KIT £5.75

Comprising a fine example of a Woofer 13" x 6 1/2in. with a massive Ceramic Magnet, 44oz., Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3in. square has a special lightweight paper cone and magnet flux 10,000 lines.

WEYRAD P50 - TRANSISTOR COILS

RA5W Ferrite Aerial...	85p	Spare Cores...	30p
Osc. P50/1AC...	30p	Driver Trans. LFDT4...	50p
I.F. P50/2CC 470 kc...	33p	Printed Circuit, PCA1...	50p
3rd L.F. P50/3CC...	30p	1/2 Tuning Gang...	65p
P51/1 or P51/2...	23p	Weyrad Booklet...	10p
P50/3V...	33p	OPTI...	55p
Mullard Ferrite Rod 3 x 1/2in.	20p.	6 x 3/4in. 25p.	

VOLUME CONTROLS

Long spindles. Midget Size	5K ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.	
Edge SK. SP. Transistor 25p.	Ideal 625 and colour 30p.

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10Ω to 25K. £2.50 Post 25p. 30K to 2 Meg. £4.00

VEROBORD 0-15 MATRIX

2 1/2 x 6in. 20p.	2 1/2 x 8 1/2in. 17p.	3 1/2 x 3 1/2in. 20p.	3 1/2 x 5in. 30p.
EDGE CONNECTORS 10 way 25p.	24 way 35p.		
PINS 36p per packet 21p.	FACE CUTTERS 35p.		

S.R.B.P. Board 0-15 MATRIX 2 1/2in wide 3p per lin. 3 1/2in wide 4p per lin.; 5in wide 5p per lin. (up to 17 1/2in). S.R.B.P. un drilled 1/4in. Board 10 x 8in. 15p.

BLANK ALUMINIUM-ORANISSIS. 18 s.w.g. 2 1/2in. sides 6 x 4in. 45p; 8 x 6in. 55p; 10 x 7in. 65p; 12 x 8in. 85p; 14 x 9in. 90p; 16 x 6in. 90p; 12 x 8in. 50p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 9in. 15p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 8in. 28p; 16 x 6in. 28p; 14 x 9in. 34p; 12 x 12in. 40p.

1 1/2inch DIAMETER WAVECHARGE SWITCHES. 25p. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 25p each. 1 p. 2-way or 4 p. 2-way, or 4 p. 3-way 25p.

TOGGLE SWITCHES. 3p. 14p; dp. 18p; dp. dt. 23p. SILICON REC. 40-100Ks 225500 Bridge 70s. 5 amp £1. RECTIFIERS CONTACT COOLED half wave 60mA 35p; 85mA 48p. SILICON BYZ13 30p; BY100 80p; BY127 30p.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less PLEASE STATE VOLTAGE REQUIRED. £2 Post Free Details S.A.E. Size 3 1/2 x 1 1/2in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2 x 1 1/2 in. Response 25 c.p.s. to 25 Kc/s. 26 db gain. For use with valve or transistor equipment. 90p Post 10p Full instructions supplied. Details S.A.E.

NEW TUBULAR	REGULATED	CAN TYPES
2/350V 14p	250/25V 14p	16+16/500V 55p
4/350V 14p	500/25V 20p	50+50/350V 55p
8/450V 14p	1000/25V 35p	80+100/350V 55p
16/450V 15p	2000/25V 45p	32+32/250V 13p
32/450V 20p	8+8/450V 18p	32+32/450V 33p
55/25V 10p	8+16/450V 20p	350+50/325V 50p
20/50V 10p	16+16/450V 25p	32+32+32/350V 43p
100/25V 10p	32+32/350V 25p	100+50+50/350V 48p

LOW-VOLTAGE ELECTROLYTICS. 1, 2, 4, 5, 8, 10, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 6V 25p; 25V 42p; 50V 52p. 2500mF 50V 62p; 8000mF 25V 47p; 35V 65p. 5000mF 6V 25p; 12V 22p; 25V 77p; 35V 85p; 50V 95p. CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 500V 0.1 4p, 0.1 3p; 1mF 15p; 2mF 15V 15p. 500V 0.001-0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Clear tolerance 1%; 2-500pF 5p; 500-2200pF 10p; 2.700-5.600pF 20p; 6.800pF 0.01, mfd 30p each. TWIN GANG. "0-0" 20pF+176pF. 65p; 500pF slow motion, standard 45p; 500pF 500 pF £1.60. SHORT WAVE SINGLE 10pF, 20p, 25pF. 55p, 50pF. 55p. CHROME TELESCOPIC AERIALS 23in. Swivel base 20p. NEON PANEL INDICATORS 15, 20, 25, 30, 40, 45, 50, 60. RESISTORS 1 w. 1 w. 2% 1/4, 1/2, 5p. 10Ω to 10M. HIGH STABILITY. 1 w. 2% 1/4, 1/2, 5p. 10Ω to 10M. Ditto 5%. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p.

SCOOP! METAL PLINTH AND PLASTIC COVER

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. £5.50 Post 25p

MAINS TRANSFORMERS

250-0-250 80 mA. 6.3 v. 4 amp.	All post 25p each
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£1.40
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. £2.50	
MINIATURE 20v, 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p	
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 45p	
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 in. 45p	
HEATER TRANS. 6.3 v. 3a. 60p	
Ditto tapped sec. 1.4 v. 2.3 a. 4.5. 6.3 v. 1 1/2 amp. 80p	
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.25	
1 amp., 6, 8, 10, 12, 16, 20, 24, 30, 36, 40, 48, 60. £2.25	
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £3.25	
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £2.75	

AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 150w. £2.25; 500w. £2.25; 750w. £10; 1000w. £14. CHARGER TRANSFORMERS. Input 200/250V. 6 or 12v. output. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p. All Transformers Postage 25p each

E.M.I. 13 1/2 x 8in. LOUDSPEAKERS

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 15p

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 15p

Recommended Teak Cabinet Size 16 x 10 x 9in. Post 25p. £5


LOW MINI-MODULE £3-25 LOUDSPEAKER KIT

Triple speaker system combining on ready cut baffle. 1/2 in. chipboard 15 in. 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 9in. Modern design, with fluted Wood Front. Highly recommended. £5 Post 25p

MINIMUM POST AND PACKING 15p. CUSTOMERS FREE CAR PARK. CALLERS WELCOME

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in MAJOR £9

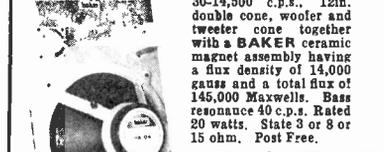

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 12in. dia. speaker 20 x 13 x 9in. £9 Post 25p. For 13 x 8in. speaker 16 x 10 x 9in. £5 Post 25p. For 10 x 6in. speaker 16 x 8 x 6in. £4 Post 25p. LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

GOODMANS 6 1/2in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambrie cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. £4

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 2 1/2 in. deep. Rating 10 watt, 3 ohm or 15 ohm models. £1-90 Post 10p

Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3. TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm, 2 1/2in. dia.; 35 ohm, 2in.; 3 in. 25 ohm, 2 1/2in. dia.; 3in. dia.; 6 1/2in.; 8 1/2in. £1 EACH 1/2 TYPE 3 or 8 or 15 ohm models £1.95 each. Post 15p. LOUDSPEAKERS P.M. 3 OHMS. 6 1/2in. £1.10; 8 x 5in. £1.25; 8 x 2 1/2in. 90p; 8in. £1.75; 10 x 6in. £1.90. 5in. WOOFER. 8 w. max. 20-10,000 cps. 8 or 15 ohm £1.80. ELAC 10in. 10w. Twin Cone. De Luxe Ceramic 8 ohm £4. RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in. dia. 4 watt; 10in. dia. 5 watt; 12 in. dia. 8 watt. 3 or 8 or 15 ohm models £1.95 each. Post 15p. OUTPUT TRANS. EL84, etc. 25p. MIKE TRANS. 50 1/2 25p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMANS OUTPUT TRANSFORMER 5 watt push pull for valves EL84, etc., 3, 8 and 15 ohms 85p. Post 20p.

BAKER 100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass Controls. Guaranteed. Details S.A.E. £39 Post Free

ALL EAGLE PRODUCTS

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and guitar with separate controls into single output. 9 volt. Stereo version of above. £4-25

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £12

BARGAIN FM TUNER as above, Chassis only, less cabinet. £7-50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3-50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES. SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p. 40 ohm or 300 ohms. JACK SOCKET Std. open-circuit 14p. closed circuit 23p. Chrome Lead Socket 45p. Phone Plugs 6p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 3-mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 5p; GANS 5p.

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA Spindle 0.187 x 0.75in. Size 3 1/2 x 1 1/2 2 1/2 x 2 1/2in. (illustrated). Post 15p. £1-25

BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1 x 3/8in. Size 2 1/2 x 2 1/2in. Post 15p. 85p

337 WHITEHORN ROAD, CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) Buses 50, 68, 159 pass door. Rail Selhurst. Tel. 01-684-1666

4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.40. P. & P. 55p extra.

INTERCOM/BABY ALARM



£3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. 25p.

Transistor TELEPHONE AMPLIFIER



£2.99

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/3)
169 KENSINGTON HIGH STREET, LONDON, W.8

1972 WORLD RADIO TV HANDBOOK

A COMPLETE DIRECTORY OF INTERNATIONAL RADIO AND TELEVISION

£2.80. Postage 10p.

COLOUR TELEVISION PICTURE FAULTS, by K. J. Bohlman. £2.50. Postage 8p.

MULLARD TRANSISTOR AUDIO AND RADIO CIRCUITS, £1.50. Postage 10p.

GUIDE TO PRINTED CIRCUITS, by Gordon J. King. £2.50. Postage 10p.

UNDERSTANDING OSCILLATORS, by I. M. Gottlieb. £1.90. Postage 10p.

HI FI YEAR BOOK 1972, £1.25. Postage 20p.

FOUNDATIONS OF WIRELESS AND ELECTRONICS, by M. G. Scroggie. £1.80. Postage 20p.

FUNDAMENTALS OF RADIO SERVICING, by B. W. Hicks. £1.50. Postage 10p.

GE SCR MANUAL, £1.25. Postage 20p.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

TRANSFORMERS

DOUGLAS GUARANTEED
12 or 24 Volts

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS*	£0.88 8p
12V x 2 500 mA x 2	MT213 CT*	£0.97 12p
12V x 2 1A x 2	MT 71 AT	£1.48 23p
12V x 2 2A x 2	MT 18 AT	£2.04 29p
12V x 2 3A x 2	MT 70 AT	£2.59 30p
12V x 2 4A x 2	MT 108 AT	£2.92 31p
12V x 2 5A x 2	MT 72 AT	£3.88 28p

30 volts. All tapped at 0-12-15-20-24-30V
Out-put Ref. No. Price P.P. Out-put Ref. No. Price P.P.

Amps.	put	£	Amps.	put	£
500 mA	MT 112 CT	1.12 14p	3A	MT 20 AT	2.64 30p
1A	MT 79 AT	1.55 28p	4A	MT 21 AT	3.10 40p
2A	MT 3 AT	2.23 28p	5A	MT 51 AT	4.31 38p

50 volts. All tapped at 0-19-25-33-40-50V
500 mA MT 102 AT: 1.45 22p 3A MT 105 AT: 3.81 39p
1A MT 103 AT: 2.00 30p 4A MT 106 AT: 5.06 39p
2A MT 104 AT: 3.10 30p 6A MT 107 AT: 7.47 39p

60 Volts. All tapped at 0-24-30-40-48-60V
500 mA MT 124 AT: 1.46 21p 2A MT 127 AT: 3.16 39p
1A MT 126 AT: 2.24 28p 3A MT 125 AT: 4.69 39p

AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	£0.89 23p
75 VA	"	MT 64 AT	£1.72 28p
150 VA	0-115-200-220-240	MT 4 AT	£2.15 30p
200 VA	"	MT 65 AT	£3.00 30p
400 V. Output at 50 Hz.	Ref. IT3 AT	Price P. & P.	

C-D Ignition system by R. M. Marston £2.25 27p
Eq.

EQUIPMENT RANGE

Sec. Output (m.a.s.)	Ref. No.	Price P. & P.
3-0-3 V.	200 mA MT 209 CS*	£2.69 6p
9-0-9 V.	100 mA MT 13 CS*	£0.91 6p
12-0-12	50 mA MT 210 CS*	£0.91 6p
20-0-20	30 mA MT 211 CS*	£0.91 6p
0-20 x 2	300 x 2 MT 214 CT*	£1.21 12p
0-8-8 x 2	500 mA x 2 MT 207 CT*	£1.46 30p
0-15-20 x 2	500 mA x 2 MT 202 AT*	£2.12 27p
0-15-27 x 2	500 mA x 2 MT 203 AT*	£2.45 27p
0-15-27 x 2	1A x 2 MT 204 AT*	£3.42 28p
10-12-0-12-20	700 mA (d.c.) MT 221 AT*	£1.11 24p

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spalls; *with interwinding screen; †untapped 240V Primary; ‡Primary tapped at 210-240V; other Primaries tapped at 200-220-240V.
Over 200 types in stock through agents or direct. Send for list.


DOUGLAS ELECTRONICS INDUSTRIES LTD., Dept. MO. 52, Thames Street, LOUTH, Lincs.



Call'em what you will...

...the best place to get them is

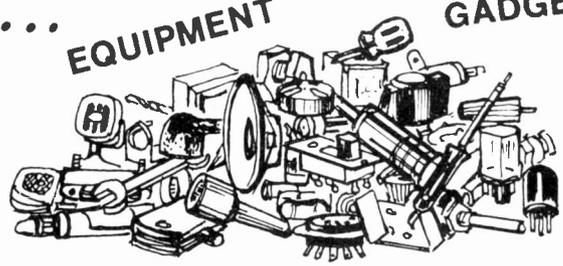COMPONENTS
BITS & PIECES PARTS
EQUIPMENT GADGETS



HOME RADIO (COMPONENTS) LIMITED

Phone 01-648 8422

Until you've tried the service provided by Home Radio (Components) Limited you've no idea how simple it can be tracking down and obtaining components. It becomes a pleasure instead of a bind! But first you need the Home Radio Catalogue, listing over 8,000 components, over 1,500 of them illustrated. At 70 pence, including p & p, it's a gift—especially as every copy contains 10 vouchers each worth 5 pence. Send coupon today.

POST THIS COUPON with your cheque or postal order for 70p

Please write in block capitals

Name _____

Address _____

HOME RADIO (COMPONENTS) LTD., Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD.

The price of 70p applies only to catalogues purchased by customers in the UK and to BFPO addresses.

To ensure the UJT remains stable during an increase of temperature an additional resistance R_{B2} is connected in series with base-2.

A half-wave trigger circuit is shown in Fig. 8, where the thyristor is acting as a rectifier and power control device. No power is supplied to the load during the negative half cycle, but a variable power is supplied to the load during the positive half cycle.

During the positive half-cycle the gated thyristor is switched on by a time (phase angle) determined by the control current. The relative power in the load can be controlled by varying the phase angle when the thyristor is switched on.

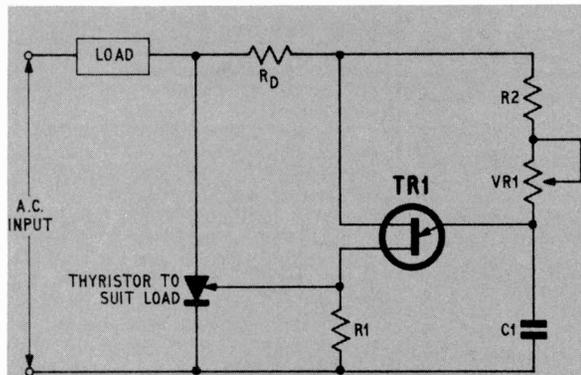


Fig. 8. Half wave UJT trigger circuit

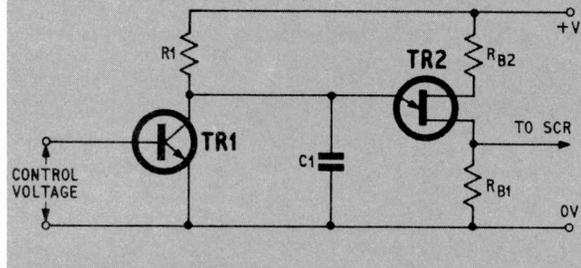


Fig. 9. Shunt transistor control of UJT

SHUNT TRANSISTOR CONTROL OF UJT

Phase control can be obtained by use of a *pnp* or *npn* transistor connected to shunt with the emitter capacitor of the unijunction. The amount of current in the base of the transistor will control the effective charging current to the capacitor, and hence will control the trigger angle of the UJT and the SCR.

Fig. 9 shows a phase control circuit and functions as follows. Transistor TR1 shunts some of the charging current supplied to capacitor C1 by resistor R1 in an amount dependent on the base drive of TR1. The more TR1 is turned-on, the later the UJT will trigger, consequently lowering the output of the SCR. Depending on the value of R1 and the base drive to TR1 the diversion of charging current from C1 will advance or retard the trigger angle accordingly. ★

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical* way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it’s as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.

FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF



POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B12, Aldermaston Court, Reading RG7 4PF
Please send books and full information — free and without obligation.

NAME AGE
BLOCK CAPITALS PLEASE
ADDRESS




SUBJECT OF INTEREST

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
Accredited by the Council for the Accreditation of Correspondence Colleges.

YEAR BS9000?

It's been a long time coming but this could be Year BS9000. Just to refresh your memory, BS9000 was the outcome of the Burghard Report or, to give its full title, "2nd Report of the Committee on Common Standards for Electronic Parts." The Report was published by H.M.S.O. in 1965.

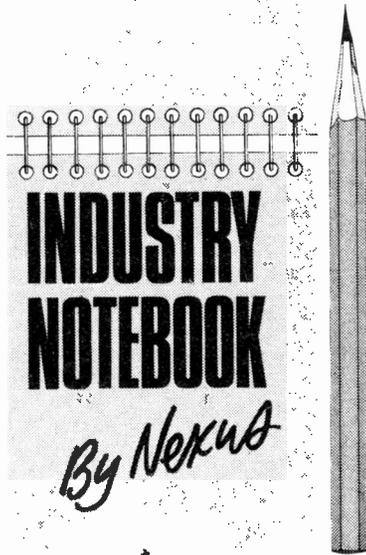The following year the Report was accepted on behalf of the electronics industry by the Conference of the Electronics Industry and the British Standards Institution was given the task of implementing the recommendations. Supervision of the operation on a practical day-to-day basis is the responsibility of the Electrical Quality Assurance Directorate of the Ministry of Defence.



The BS9000 scheme set out with the finest ideal and that was to formulate a new and up-to-date set of specifications for electronic components which would ultimately supersede the rag-bag of specifications originated in the United States and Europe over the years. Clearly this would be a major operation but few people, in my opinion, realised what a mammoth task it would become. The technical problem was big enough to begin with. Add to it the democratic process involving countless committees on which were representatives not only of BSI and the Ministries but also of manufacturers and users, all trying to reach a consensus, and you get some idea of why BS9000 has been so long on the runway, so to speak, without getting airborne. But movement is now in sight.

Mr John Hinchcliff, Assistant Director (Components), Electrical Quality Assurance Directorate, Ministry of Defence, is at the centre of BS9000. At a recent dinner

organised by component distributors he revealed a few facts and figures on progress to date.

All the basic BS9000 specifications and many supplementary specifications have now been published. Almost 200 component manufacturers, distributors and test houses have applied to join the scheme and over 80 have so far been fully approved to operate it. More than 100 components (or component families) have been or are being approved and this figure is doubling every six months. About 200 military semiconductor specifications have been brought into the system and military digital integrated circuits are soon to be included. Nevertheless, stated Hinchcliff, there is still an enormous way to go. Several thousand components will eventually be drawn in.

BS9000 has been a source of irritation to the Americans. They see it as a protectionist policy under which their long established military specifications and quality assurance procedures will become obsolete and will no longer be specified in British equipment to the detriment of American exports.

Meantime, the Europeans have not been idle. In 1967 they instituted their own Harmonised System of Quality Assessment for Electronic Components under the title CENEL 1. Britain joined CENEL 1 as a full member with France, Germany and Italy with an understanding that each country would mutually recognise standards, approvals, and methods of inspection as equal to their own. Other European countries are in process of joining.

To cap it all, the International Electrotechnical Commission (IEC) is considering a similar system to operate on a world-wide basis. Clearly, world standards would be best of all but will take many more years to achieve leaving, as one disgruntled components man remarked to me, the fall guy in the middle hacking his way through a jungle of national and international specifications as best he can.

ABSENTEES

The British contingent at this year's Paris Components Show (April 6-11) will be one of the smallest on record, numbering little over 20 companies. Last year's show was both expensive and disappointing and this, I suspect, is why so many "regulars" of previous years have decided to stay at home this year despite our imminent entry into the Common Market.

But this doesn't explain why industry giants GEC and Plessey have decided to stay away from the big IEA Show at Olympia in May. Selectivity seems to be the answer. Publicity managers with restricted

budgets have spent sleepless nights worrying over the optimum split of funds between direct mail shots, press advertising, exhibitions, and even the supply of book matches. And exhibitions seem to be losing out.

TOTAL CAPABILITY

Total capability, it's a hackneyed phrase but it still means something when attached to Decca Radar, still proudly holding the Number One Spot as world suppliers of marine radar and determined as ever to stay there in what, by any standards, is a highly competitive business.

Decca launched the biggest radar event of the year. Not half a dozen, nor even a dozen, but a dazzling two dozen new models on show for the first time, twenty of them for coastal and open sea use and four river radars. All the new radars owe a lot to the solid-state RM914, introduced just a year ago and which won the Queen's Award for technological innovation.

The RM914, already topping 3,000 sales, was a runaway success. Big features were a solid state local oscillator, solid state modulator, and wide use of integrated circuits. The same modules, or derivations of them, are in all the new models which come in a huge choice of display sizes, scanner sizes, transmitter powers and optional facilities.

Decca's competence in advancing the state of the art in marine radar is perhaps most convincingly demonstrated by one simple fact. The latest 25kW radar with a 60 mile range consumes no more power than the 3kW, 24 mile range D202 model which Decca introduced as the first commercial marine radar to use transistors in 1963.

DIVERSIFICATION

The high-powered "think-tank" at Frimley which we have known as E-A Space and Advanced Military Systems Ltd and more conveniently as EASAMS since 1962 has now officially become EASAMS Ltd.

Reason for the change of name is a change of emphasis although marketing manager R. M. French assures me that EASAMS still has plenty of military work. But the sort of systems analysis and engineering which made EASAMS famous is now being applied equally effectively in the civil field and not only in electronics. Examples are the design, construction and commissioning of new hospitals, the development of transport and distribution systems, and ports and harbour management.

At the same time there is plenty of electronic work such as studies for ESRO and on the MRCA project.

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Abysmal writing

Sir—As a regular subscriber to your normally excellent magazine, I feel that I must protest at what has become its present standard of presentation. You have excellent news columns, excellent features, and many highly interesting projects, *but* I have now become convinced that the standard of presentation of your projects has now fallen to a level where they are intelligible only to those who are experts in your pseudo-scientific jargon.

This situation was drawn to my attention about a year ago during the course of 6th Form Electronics that I teach. I use, for this, back copies of P.E. as source material for student projects, but increasingly I have been aware that these 17- and 18-year-old Grammar School pupils were just unable to understand what your projects were about. Often I am faced with the plaintive, "What on Earth are they trying to say." My initial reaction was to blame them, but now I realise that I have been quite unjust, some of what appears is quite unintelligible unless you have prior knowledge of what the project is about.

In your December 1971 issue your article about *Logical Radio Control* is the most abysmal example of semi-scientific writing I have seen in many years as a professional scientist. By pooling the resources of two physics graduates, two graduate electrical engineers, the 6th Form and myself, we have worked out how this system can be used to control six channels, but it has taken us two weeks to work it out. God help those who are less adept than ourselves—they will just move on disillusioned.

How much simpler it could have been if someone had taken the trouble to explain the significance of each pulse, the significance of each pulse length and the significance of the need to transmit pulse trains. If you search, some of this material is present, mixed up with the wonders of the technicalities. But most is absent.

In the same issue your article *I.C. Digital Dice* reduced some of my 6th Form to glassy eyed disbelief. I offer the following paragraph as an example of how this article could

be made much more intelligible to a much wider public:

"A dice generates the numbers 1 to 6 in a random order. This device achieves this in the following manner. A signal generator produces a series of electrical pulses, which are then counted in binary form. The counter counts from 1 to 6, and then returns to 1. The sequence of numbers is repeated over and over again just as long as pulses are fed to the counter.

To make the dice random, and cheat proof, we must be able to stop the counter when we do not know what the count is, and we must make the rate of counting very high.

The dice described generates pulses at 4,800 per second, so that each number from 1 to 6 appears 800 times a second, and each time it appears for only 1/4,800 second. This is too fast for the eye and hand to see, and so when ever the counter is stopped the numbers must be in a random order."

I am prepared to admit that many readers would not require such a simple approach to a project, but such an approach to presentation would take all the mystery out of electronics. If you or your staff are intent on producing working diagrams that are easy to follow, even

to the non-expert, surely it is more than worth while making the description of what a device is supposed to do, and the broad principles upon which it works as clear as possible.

In conclusion may I pass the opinion that the now defunct *Beginners Columns*, and your complimentary magazine, *EVERYDAY ELECTRONICS* also have the same problem, a pre-occupation with jargon, little thought being given to clarity.

I hope my comments are of interest and assistance.

W. G. Jones,
Lancs.

Not logic

Sir—I have noticed with considerable interest your recent articles in P.E. on *Logical Radio Control*. It does however seem to me that you appear to have contradicted yourself on the shift-register section of the decoder.

You say that following the "clear" pulse the first signal pulse "turns on" the first flip-flop and the second signal pulse causes the second output to change to "1" and the first output to revert to "0". However, in Fig. 19b the waveform for the output (Q1) of this flip-flop remains up for five of the signal pulses, not resetting to 0 after the first.

The way I see it is that following the clear pulse the first signal pulse will, as you say, set the first flip-flop to "1". The second pulse will also set to "1" the second flip-flop, but since the input conditions to the first and sixth flip-flops have not changed neither will change state and the first flip-flop will remain in the "1" condition. So after six pulses all the flip-flops will be set which will not really work as a proportional system.

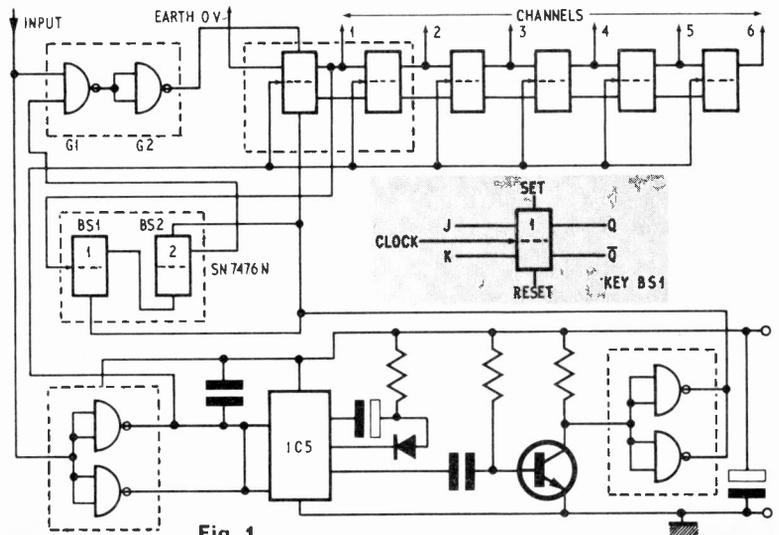


Fig. 1

Readout —

A SELECTION FROM OUR POSTBAG

Another point to note is that the master-slave type of flip-flop recommended triggers on the *trailing* edge of the clock-pulse; thus, assuming your circuit did work as you suggested, following the clear pulse the first flip-flop would not set until after the first pulse and would remain set for the interval plus the duration of the *second* pulse, thus the first channel would be "lost".

The enclosed circuit, Fig. 1, is my idea for the answer to the problem.

The clear pulse resets BS1, and sets BS2, the latter providing one input for G1 which, together with G2, forms an AND gate. Thus the leading edge of the first pulse will enable G1 and G2, and hence set the first flip-flop in the shift register for the duration of the signal impulse. The trailing edge of the pulse will reset the first flip-flop, set the second, and will also indirectly (via the first flip-flop) set BS1 which, in turn, resets BS2, closing the AND gate, preventing the setting of the first flip-flop until the next clear pulse.

The second and subsequent flip-flops in the chain will each set for the pulse length plus the interval. The clear pulse is applied to the first flip-flop in the register, to ensure correct triggering of BS1.

I hope my comments have been constructive, and look forward with great anticipation to your article on the Servo Motor Control. In fact, I was wondering whether, now you have gone so far, you might go the whole way and describe a suitable transmitter and receiver, possibly using integrated circuits as well?

M. C. Tiend,
Chelmsford.

Triggered.

Sir—First may I compliment A. J. Dunn for a very interesting series on *Logical Radio Control*. It has created a great deal of enthusiasm amongst myself and friends, but also some queries were raised.

One of these was with regard to Mr Dunn's circuit for sync detection using a retriggerable monostable, as the majority of constructors seem to prefer the Texas SN74—range of TTL i.c.s and many suppliers do not stock retriggerable monostables.

To try to alleviate this problem I have designed the following circuit. It can be used to detect long "0" or "1" pulses as required and uses

a 5-bit shift register as counting timer (see Fig. 2).

As shown here the clear signal to JK flip flops is produced when a "1" has existed at the input for a time set by the frequency of the multivibrator. This could be made up from NAND gates (see *Digital Dice* article, December P.E.) to make this circuit exclusively TTL.

To detect "0's instead of "1's merely invert the input.

L. Cook,
Lancs.

P.E. Scorpio ignition system

TACHOMETERS

A large number of constructors have enquired about the possible effects of the ignition system on electronic impulse tachometers. Unfortunately none of the cars on which the system was tested were fitted with electronic tachometers and so we have no personal experience of these. As there are a large number of different types available, differing considerably in their requirements, we obviously could not make any positive recommendations without buying a sample of every available type, which would be impractically expensive. There are, however, two basic types and we recommend that the constructor ascertain which type he has and experiments to obtain the best results.

CURRENT OPERATED

These contain a current transformer which is normally connected in series with the ignition coil, or else the SW lead is wrapped around a small magnetic pick-up on the tacho. It should be possible to operate this type with the Scorpio by connecting it into the lead from the coil to C6/7 (tag 5) as there is a 10A current pulse through this lead

VOLTAGE OPERATED

These are normally connected between the contact breaker and earth and work either on the 12V change of d.c. level when the contact points open or on the high voltage spike produced when the points open. With the Scorpio it should be possible to operate the low voltage type from the contact breaker, as normal, but the high voltage type should be connected to terminal 5 on the unit, or the tag on the ignition coil to which terminal 5 is connected.

CARS WITH MULTIPLE CONTACT BREAKERS

A number of constructors have asked about using the Scorpio with two-stroke, three-cylinder engines having a separate contact breaker and coil for each cylinder. Unfortunately as there is no distributor it would be necessary to use three separate units and in view of the high cost we cannot recommend the use of the Scorpio with this type of engine.

D. S. Gibbs & I. M. Shaw

Ferret tracker

Sir—I would be most grateful if any reader can offer any advice. I intend to start ferreting rabbits and previously I have used a ferret on a collar and line, digging up to the ferret by means of holes every 2 to 3ft.

Would it be possible to attach a device to the ferret collar which can be tracked above ground level by some kind of electronic detector?

The ferret's collar is leather $\frac{1}{4}$ in wide. The average depth we dig is 18in to 24in deep, some odd holes 36in deep.

If such equipment can be purchased would you be kind enough to forward on any details, it would be a tremendous asset.

D. Nunn,
Suffolk.


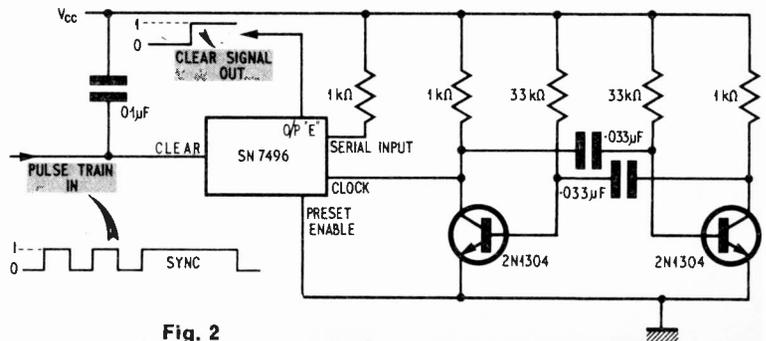


Fig. 2

new

Super IC-12

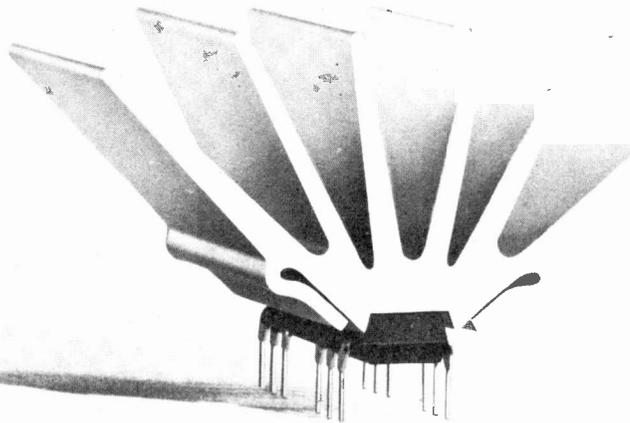

High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

Output power 6 watts RMS continuous (12 watts peak)

Frequency Response 5 Hz to 100KHz \pm 1 dB.

Total Harmonic Distortion Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

Load Impedance 3 to 15 ohms.

Input Impedance 250 Kohms nominal.

Power Gain 90dB (1,000,000,000 times) after feedback.

Supply Voltage 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

Quiescent current 8mA at 28 volts; low enough to make the IC.12 ideal also for battery operation.

Size 22 x 45 x 28 mm including pins and heat sink.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added



FREE 44 page instruction manual now included with all units. Available free on request to present IC.12 users. Gives full circuit and wiring diagrams for many applications including car-radios, oscillators, etc.



Price, inc. **FREE** printed circuit board for mounting and manual.

£2.98 Post free



SINCLAIR GENERAL GUARANTEE
Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

Sinclair Radionics Ltd, London Rd, St. Ives
Huntingdonshire PE17 4HJ
Telephone St. Ives (048 06) 4311

sinclair

Sinclair Project 60

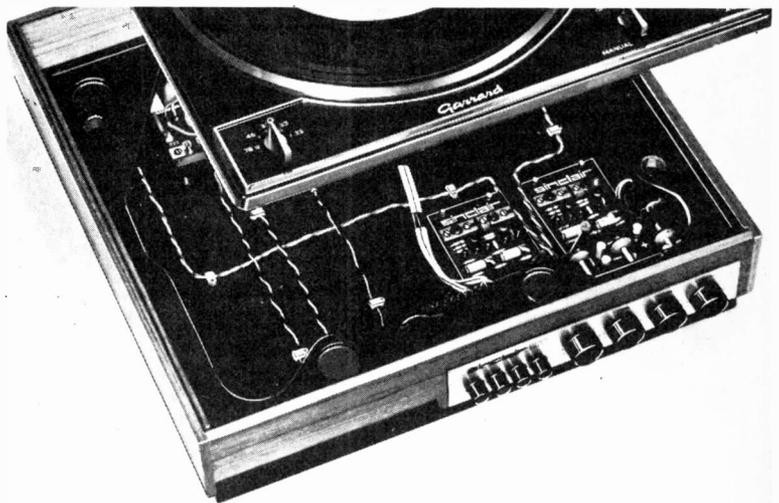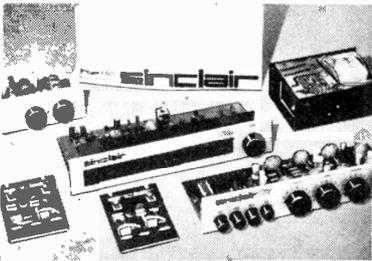The World's leading range of high fidelity modules



New! Project 605

The easy way
to buy and
build
Project 60



Project 605 is one pack containing: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**
-All you need for a superb 30 watt high fidelity stereo amplifier.

Sinclair Radionics Limited, London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.


Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
20 + 20 W. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
20 + 20 W. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
40 + 40 W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required.

from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

Z.30 & Z.50 power amplifiers

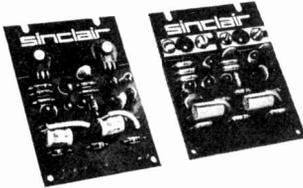

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).
Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

Frequency response: 30 to 300,000Hz \pm 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size: 14 x 80 x 57 mm.

Z.30

Built, tested and guaranteed with circuits and instructions manual. **£4.48**

Z.50

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


PZ.5 30 volts unstabilised **£4.98**

PZ.6 35 volts stabilised **£7.98**

PZ.8 45 volts stabilised

(less mains transformer) **£7.98**

PZ.8 mains transformer **£5.98**

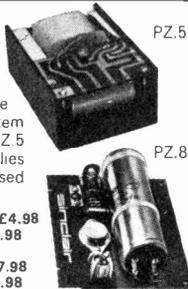

Project 60 Stereo F.M. Tuner



First in the world to use the phase lock loop principle


The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS—Number of transistors: 16 plus 20M I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 μ V for 30dB quieting; 7 μ V for lock-in over full deviation. **Squelch level:** 20 μ V. **A.F.C. range:** \pm 200 KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz - 15 KHz (\pm 1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Power on/tuning/stereo. **Size:** 93 x 40 x 207 mm.

Built and tested. Post free.

£25

Stereo 60 Pre-amp/control unit

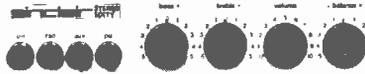

Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS—Input sensitivities: Radio - up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A curve \pm 1dB; 20 to 25,000 Hz. Ceramic p.u. - up to 3mV; Aux - up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 15 to -15dB at 10 KHz; BASS + 15 to -15dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207 mm.

Built tested and guaranteed.

£9.98

A.F.U. High & Low Pass Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less

loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages - rumble (high pass) and scratch (low pass). Supply voltage - 15 to 35V. Current - 3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed.

£5.98

The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

Name _____

Address _____

I enclose cash/cheque/money order.

PE3/72


TV'S 19" NOW £11.95

TWO YEARS' GUARANTEE ALL MODELS

405/625: 19" £25.95; 23" £35.95

FREE CATALOGUE

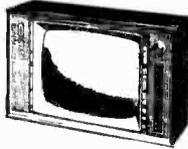DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS



COLOUR TV 19" £145 OR 25" £185
LIMITED SUPPLY. REGRET PERSONAL CALLERS ONLY

TV TUBES REBUILT
GUARANTEED 2 YEARS



14" £3.95; 17" & 19" £5.95;
21" & 23" £6.45
Exchange Bowls carr. 55p.

UHF/625 AERIAL
£1.95 10 ELEMENT
p.p. 25p

PRESS BUTTON
SWITCHING UNITS
4 BANKS 25P, 6 BANKS 35P.
p.p. 5p.

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12 Phone 01-478 6001-2-3

COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" 6 1/2" x 3 1/2". Post 15p
Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.

Precision Tape Motors: £1.95 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.

Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 15p.

Transistors 15p. each. Post free. AC126, AC128, AF114, AF117, OC45, OC71, OC81, OC81D

Valve 6XL80 30p. Only stock in the country.

Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg./100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

SIEMENS TTL EX STOCK!!

SIEMENS QUALITY PLUS BARGAIN PRICES PLUS LST SERVICE
A full design range of high quality TTL available from LST your Officially Appointed Siemens Distributors

Part No.	Description	Equal to	1-24	25-99	100 up
7400	Quadruple 2-input NAND gate	FLH 101	20p	16p	14p
7401	Quadruple 2-input NAND gate with open collector output	201	30p	16p	14p
7402	Quadruple 2-input NOR gate	191	20p	16p	14p
7403	Quadruple 2-input NAND gate with open collector output	291	20p	16p	14p
7404	Hex inverter	211	25p	21p	18p
7405	Hex inverter with open collector output	271	25p	21p	18p
7408	Quad 2-input positive AND gate Totem pole output	381	25p	21p	18p
7409	Quad 2-input positive AND gate open collector	391	25p	21p	18p
7410	Triple 3-input NAND gate	111	20p	16p	14p
7413	Schmitt Trigger	351	35p	29p	25p
7420	Dual 4-input NAND gate	121	20p	16p	14p
7430	8-input NAND gate	131	20p	16p	14p
7440	Dual 4-input NAND buffer	141	24p	20p	17p
7442	BCD to decimal decoder TTL output	281	21.15p	94p	31p
7443	Excess 3 to decimal decoder	361	21.45p	£1.20	£1.08
7444	Excess 3 gray to decimal decoder	371	£1.45	£1.20	£1.08
7450	Expandable dual 2-wide 2-input AND-OR-INVERT gate	151	20p	16p	14p
7451	Dual 2-wide 2-input AND-OR-INVERT gate	161	20p	16p	14p
7453	Expandable 4-wide 2-input AND-OR-INVERT gate	171	20p	16p	14p
7454	4-wide 2-input AND-OR-INVERT gate	181	20p	16p	14p
7460	Dual 4-input expander	FLY 101	20p	16p	14p
7470	J-K flip-flop	FLJ 101	45p	37p	32p
7472	J-K master-slave flip-flop	111	32p	27p	23p
7473	Dual J-K master-slave flip-flop	121	45p	40p	35p
7474	Dual D-type edge triggered flip-flop	141	46p	38p	33p
7475	Quad bistable latch	151	45p	40p	37p
7476	Dual J-K master-slave flip-flop with preset and clear	131	45p	40p	36p
7480	Gated full adder	FLH 221	67p	56p	48p
7482	2-bit binary full-adder	231	87p	73p	62p
7483	Four-bit binary full adder	241	£1.32	£1.16	£1.00
7486	Quadruple 2-input exclusive-OR element	341	33p	27p	23p
7490	Decade counter	FLJ 161	80p	67p	57p
7491A	8-bit shift register	221	£1.28	£1.07	92p
7492	Divide-by-12 counter	171	85p	71p	61p
7493	4-bit binary counter	181	80p	67p	57p
7494	4-bit shift register	231	£1.13	94p	81p
7495	4-bit shift register	191	87p	72p	62p
7496	5-bit shift register	261	£1.48	£1.22	£1.05
74100	Dual quadruple bistable latch	301	£1.64	£1.37	£1.17
74107	Dual J-K master-slave flip-flop with preset and clear	271	52p	43p	36p
74121	Monostable multivibrator	FLK 101	48p	40p	34p
74141	BCD to decimal decoder and nixie driver	FLL 101	£1.22	£1.02	87p
74190	Synchronous up down 4-bit decade counter with one line mode control	201	£1.80	£1.48	£1.27
74191	Synchronous up down 4-bit binary counter with one line mode control	211	£1.80	£1.48	£1.27
74192	Synchronous up down 4-bit decade counter	241	£1.74	£1.45	£1.25
74193	As above—binary counter	251	£1.74	£1.45	£1.25

TYPES MAY BE MIXED TO QUALIFY FOR PRICE BREAKS
DATA BOOKLET 20p

**CONTRACT ORDER PRICES AND BULK QUANTITY PRICES QUOTED ON REQUEST
EXTENDED RANGE AVAILABLE TO TRADE**

REEDS REEDS REEDS

We offer a comprehensive range of reed switch devices. These are not "seconds" or "job lots", but genuine manufacturers stock lines. Send S.A.E. for full data and prices.

INTRODUCTORY OFFERS

Reed Relay type 2/E 3V 25p each
Miniature Reed Switches type A 1/2A 200V 20p each
Reed Push Button Switches 1 contact 85p each

REED COILS

3, 6, 9, 12, 24V Miniature 27p
Small 27p
Standard 34p

REED SWITCHES

Large range of many sizes, types and manufactures
Popular types: E Small normally open 10 for 50p
A Miniature normally open 24p each
B Standard change over 40p each

REED RELAYS

Many versions available, popular types:
3, 6, 9, 12, 24V
Miniature 1/A normally open 56p
Small 2/E 1 contact 36p
2/EE 2 contacts 44p
2/EEE 3 contacts 52p
STD 3/B change over 87p

REED PUSH BUTTON SWITCHES

Momentary Action
1 contact £1.00
2 contacts £1.25
Illuminated 1 contact £1.30
Illuminated 2 contacts £1.55 inc. P. Tax

REELS OF ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g.
250 grams and 500 grams. Send for prices
Packing and postage 7p on all orders.

C.B.M. ELECTRONIC COMPONENTS LTD.
26 Avon Trading Estate, Avonmore Road, London, W.14



PART OF OUR CATALOGUE RANGE:

Large range of Transistors by many major manufacturers, Zener Diodes, Thermistors, Varicap Diodes, Rectifiers, Thyristors, Triacs, IC Amplifiers, Unijunctions, Opto-electronics, Tunnel Diodes, Meters, etc., etc.

2N5777 PHOTO DARLINGTON
NEW LOWEST PRICE
FANTASTIC SENSITIVITY **45p**

IF YOU HAVEN'T GOT OUR CATALOGUE WHY NOT??? **IT'S FREE!**

ULTRASONIC TRANSDUCERS



Operate at 40 kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.
FREE: With each pair our complete transmitter and receiver circuit.

PRICE **£5.90**
(Sold only in pairs)

7 SEGMENT INDICATOR 3015F

16DIL Case—0-9 plus decimal indication. £2 incl. data/circuits. FLL121 Decoder Driver £1.32 to suit.
LST are appointed distributors for the Mintron 3015F—quantity prices on request.



NEW PRODUCT ! !

LOW COST DIL SOCKETS

16 PIN DUAL IN LINE **17p**
14 PIN DUAL IN LINE **15p**

NEW LOW PRICE LINEARS!!

LIC709C/5 (T05) **40p**
LIC709C/14 (DIL) **35p**
LIC723/5 (T05) **79p**
LIC723/14 (DIL) **93p**
LIC741C/5 (T05) **43p**
LIC741C/14 (DIL) **40p**

All above are the new NEW-MARKET Linear range.

LST are Official Distributors for Newmarket Transistors Ltd.

Data and Volume prices on application.

TERMS:

Retail Mail order subject to 50p minimum order. Cash with order only.

Schools etc.: Nett MA against Official order.

Trade: Account on application.

Postage: 10p inland; 25p Europe; elsewhere—send plenty will refund.

Guarantee: All goods carry Manufacturers' warranty.

Counter sales: Same address—open Saturdays.

Trade Enquiries only: Telephone Brentwood 226470.

LOW COST I AMP BRIDGES

	1-99	100+
WO05 50piv	23	21
WO1 100piv	24	22
WO2 200piv	25	23
WO4 400piv	27	24
WO6 600piv	28	25
WO8 800piv	35	31

Sub-miniature size. Plastic encapsulated. Larger quantity prices on application.

SPECIAL OFFER IN 4000 SERIES I AMP RECTIFIERS

	p.i.v. 1-49	50+	100+
IN4001 50	070	060	050
IN4002 100	070	065	060
IN4003 200	090	085	070
IN4004 400	100	090	080
IN4005 600	120	100	090
IN4006 800	140	130	110
IN4007 1000	190	150	120

	p.i.v. 500+	1000+
IN4001 50	045	040
IN4002 100	055	045
IN4003 200	060	050
IN4004 400	070	060
IN4005 600	075	070
IN4006 800	100	085
IN4007 1000	110	100

Should any item be out of stock we reserve the right to supply a higher voltage rated item at no extra charge.

NEW LOWER PRICES

AC107 30p	BSY95A 12p	OA70 8p	40430 97p
AC126 20p	BY100 15p	OA73 8p	40432 £1.37
AC128 20p	BY210 35p	OA79 8p	40512 £1.45
AC150 20p	BY212 30p	OAB1 8p	40513 £1.70
AC176 25p	BY213 20p	OAB5 8p	IN4007 20p
AC187 25p	BZY88/ 25p	OA90 8p	IN4148 7p
AC188 25p	C3V3 15p	OA91 8p	2G302 19p
ACY17 27p	C3V6 15p	OA95 8p	2G371 15p
AC188 25p	C3V9 15p	OA200 10p	2G374 25p
AC191 20p	CA4V3 15p	OC174 10p	2N174 80p
AC192 20p	CA4V7 15p	OC202 10p	2N175 25p
AC211 19p	CA5V1 15p	OC19 60p	2N382A/ 50p
AC222 19p	CA5V6 15p	OC20 97p	2N388A 50p
AC240 15p	CA6V2 15p	OC22 47p	2N404 23p
AC241 15p	CA6V8 15p	OC23 60p	2N696 15p
AD140 55p	CA7V5 15p	OC24 60p	2N697 17p
AD149 50p	CA8V2 15p	OC25 77p	2N698 30p
AD161 36p	CA9V1 15p	OC26 93p	2N706 10p
AD162 36p	CA10 15p	OC28 60p	2N706A 12p
AF106 34p	CA11 15p	OC29 60p	2N707 12p
AF114 25p	CA12 15p	OC35 50p	2N711 37p
AF115 25p	CA13 15p	OC36 63p	2N711A 37p
AF116 25p	CA15 15p	OC42 15p	2N911 50p
AF117 25p	CA16 15p	OC44 15p	2N914 20p
AF119 25p	CA18 15p	OC45 72p	2N918 42p
AF124 25p	CA20 15p	OC71 72p	2N1090 30p
AF126 17p	CA22 15p	OC72 72p	2N1098 30p
AF139 30p	CA24 15p	OC75 72p	2N1131 30p
AF186 40p	CA27 15p	OC76 72p	2N1132 30p
AF239 36p	CA30 15p	OC77 40p	2N1302 17p
AS226 25p	CA3004 £1.80	OC81 20p	2N1303 17p
AS227 30p	CA3005 £1.17	OC81D 20p	2N1304 22p
AS228 22p	CA3011 74p	OC81Z 20p	2N1305 22p
AS229 30p	CA3013 £1.05	OC82 25p	2N1306 24p
AS221 37p	CA3014 £1.24	OC82D 15p	2N1307 24p
AUY10 £1.50	CA3018 84p	OC83 23p	2N1308 30p
BA115 8p	CA3020 £1.26	OC84 25p	2N1309 30p
BC107 10p	CA3028A 74p	OC84 25p	2N1507 23p
BC108 10p	CA3035 £1.23	OC139 25p	2N1613 15p
BC109 10p	CA3037 £1.27	OC140 25p	2N1615 15p
BC110 10p	CA3044 £1.20	OC170 25p	2N2147 75p
BC117 10p	CA3046 75p	OC171 30p	2N2148 60p
BC147 10p	CA3047 £1.37	OC200 40p	2N2160 57p
BC148 9p	CA3048 £2.05	OC201 60p	2N2368 17p
BC149 10p	CA3049 £1.60	OC202 75p	2N2369 17p
BC158 11p	CA3052 £1.65	OC202 75p	2N2369A 17p
BC167 11p	CA3090C £3.46	OC203 40p	2N2376 15p
BC168 10p	CR1/051C 09p	OC204 40p	2N2904 44p
BC169 11p	CR1/401C 60p	OC205 75p	2N2904A 49p
BC182 10p	CRS305AF £1.58	OC206 90p	2N2905 65p
BC183 9p	CRS3/40AF £1.03	OC207 75p	2N2905A 75p
BC183L 10p	CRP17/M 40p	OC207 75p	2N2806 44p
BC184 10p	CRP12 50p	ORP12 50p	2N2906A 54p
BC184L 12p	DI3T1 45p	ORP16 40p	2N2926 all colours 00p
BC212 12p	MJES20 50p	P346A 10p	2N3053 20p
BC212L 12p	MJ480 97p	PA230 £1.40	2N3054 50p
BCY30 25p	MJ481 £1.25	PA234 £1.25	2N3055 60p
BCY31 48p	MJ490 £1	PA237 £2	2N3702 10p
BCY32 30p	MJ491 £1.35	PA246 £2.63	2N3703 40p
BCY33 20p	MJ492 £1.42	PA424 £2.45	2N3704 11p
BCY34 25p	MPF103 45p	SL403D £1.50	2N3705 10p
BCY38 30p	MPF104 37p	ST140 20p	2N3706 9p
BCY70 30p	MPF105 40p	ST141 20p	2N3707 11p
BCY71 30p	NKT124 30p	TAA263 75p	2N3708 7p
BCY72 30p	NKT125 40p	TAA293 97p	2N3709 9p
BD121 65p	NKT126 37p	TAA310 £1.25	2N3710 9p
BD123 80p	NKT128 25p	TAA320 75p	2N3711 8p
BD124 75p	NKT129 25p	TAD100 £1.97	2N3819 35p
BD131 75p	NKT121 25p	TAD110 £1.97	2N3820 60p
BD132 75p	NKT213 25p	TD716 60p	2N3826 30p
BDY20 £1.05	NKT216 46p	TIP31A 62p	2N4058 15p
BF115 23p	NKT217 50p	TIP32A 74p	2N4060 12p
BF163 35p	NKT218 25p	TIS88A 45p	2N4061 15p
BF167 18p	NKT219 25p	UL900 40p	2N4062 12p
BF173 19p	NKT223 27p	UL914 40p	2N4284 15p
BF177 25p	NKT271 18p	UL923 40p	2N4287 18p
BF178 31p	NKT272 17p	V405A 46p	2N4289 15p
BF180 35p	NKT274 18p	ZTX108 11p	2N4871 15p
BF184 35p	NKT275 20p	ZTX300 13p	2N5254 45p
BF185 20p	NKT279A 12p	ZTX302 18p	3N84 £1.30
BF185 25p	NKT281 29p	ZTX303 18p	3N128 69p
BF194 17p	NKT302 87p	ZTX304 27p	3N140 76p
BF195 15p	NKT304 79p	ZTX314 11p	3N141 73p
BF196 15p	NKT351 75p	ZTX320 30p	3N152 86p
BF200 35p	NKT401 71p	ZTX330 18p	40250 55p
BFX13 25p	NKT402 77p	ZTX500 90p	40309 13p
BFX29 25p	NKT403 65p	ZTX501 16p	40310 45p
BFX84 25p	NKT404 60p	ZTX502 20p	40312 48p
BFX85 34p	NKT405 79p	ZTX503 17p	40320 47p
BFX86 25p	NKT406 62p	ZTX504 40p	40360 43p
BFX87 30p	NKT420 £1.83	IN34A 20p	40361 47p
BFX88 24p	NKT451 58p	IN60 20p	40362 55p
BFY50 42p	NKT452 52p	IN64 20p	40406 56p
BFY51 19p	NKT453 50p	IN82A 47p	40407 39p
BFY52 20p	NKT713 29p	IN914 7p	40408 51p
BFY53 17p	NKT717 44p	IN4001 7p	40409 54p
BFY90 67p	NKT773 25p	IN4002 7p	40410 62p
BSX19 16p	NKT781 29p	IN4003 7p	40464A 35p
BSX20 16p	NKT70329 31p	IN4004 7p	40600 58p
BSX21 20p	0013 31p	IN4005 7p	40601 55p
BSY27 20p	OAS 20p	IN4006 15p	40602 49p
BSY29 25p	OAI0 25p	2N5756 95p	40603 49p
	OAA7 8p	40486 95p	40673 90p

QUALITY: LST are Official Franchised Distributors for the majority of our advertised products. Members of the Association of Franchised Distributors of Electronic Components.



LST ELECTRONIC COMPONENTS LTD
Mail Order Dept. (PE)
7 COPTFOLD ROAD, BRENTWOOD, ESSEX

Great new OFFER from **DIOTRAN** TRANSISTORS

BRAND NEW FULLY GUARANTEED DEVICES

AC107	15p	AF115	17p	BC140	35p	BCY31	22p	BF272	80p	EC403	15p	ORP60	40p	2N918	30p	2N2714	25p	2N3704	15p
AC113	20p	AF116	17p	BC141	35p	BCY32	25p	BF273	30p	GET880	27p	ORP61	40p	2N929	22p	2N2904	25p	2N3705	12p
AC115	17p	AF117	17p	BC142	45p	BCY33	17p	BF274	30p	MAT100	15p	ST140	12p	2N930	25p	2N2904A	30p	2N3706	12p
AC126	17p	AF124	30p	BC143	40p	BCY34	20p	BF308	35p	MAT101	17p	ST141	17p	2N1131	20p	2N2905	25p	2N3707	13p
AC127	17p	AF125	20p	BC147	17p	BCY71	30p	BF309	37p	MAT120	15p	T1543	40p	2N1302	17p	2N2906	27p	2N3708	8p
AC128	17p	AF126	20p	BC148	12p	BCY72	15p	BF316	75p	MAT121	17p	UT46	27p	2N1303	40p	2N2906A	25p	2N3710	10p
AC141K	17p	AF127	20p	BC149	17p	BCZ11	20p	BF309	37p	MPF102	43p	V405A	25p	2N1304	22p	2N2907	35p	2N3711	10p
AC142K	17p	AF129	33p	BC150	17p	BD121	85p	BFX29	27p	MPF105	43p	Y410A	45p	2N1305	20p	2N2907A	30p	2N3819	40p
AC151	15p	AF178	30p	BC151	20p	BD123	85p	BFX85	27p	OC20	50p	ZG302	19p	2N1306	22p	2N2923	13p	2N3820	41p
AC154	15p	AF179	50p	BC152	17p	BD124	70p	BFX86	25p	OC22	30p	ZG303	19p	2N1307	22p	2N2924	13p	2N3903	25p
AC155	17p	AF180	50p	BC153	27p	BD124	80p	BFX87	25p	OC23	33p	ZK304	20p	2N1308	19p	2N2925	13p	2N3904	27p
AC156	17p	AF191	50p	BC154	30p	BD132	80p	BFX88	25p	OC24	40p	ZG306	35p	2N1309	27p	2N2926	12p	2N3905	25p
AC157	17p	AF186	45p	BC157	20p	BDY20	41	BFY50	20p	OC25	25p	ZG308	35p	2N1613	17p	(G)	11p	2N3906	27p
AC165	17p	AF239	37p	BC158	17p	BF115	22p	BFY51	20p	OC26	25p	ZG309	35p	2N1889	35p	2N2926	11p	2N4059	10p
AC166	17p	AFZ12	45p	BC159	20p	BF117	45p	BFY52	20p	OC28	80p	ZG339	17p	2N1890	45p	(O)	10p	2N4060	12p
AC167	20p	AFZ12	45p	BC167	13p	BF118	60p	BFY53	20p	OC29	40p	ZG339A	15p	2N1893	37p	2N3010	80p	2N4061	12p
AC168	20p	AL102	85p	BC168	13p	BF119	70p	BSX19	15p	OC35	33p	ZG344	15p	2N3011	60p	2N3010	80p	2N4062	12p
AC169	14p	AL103	85p	BC169	13p	BF152	35p	BSX20	15p	OC36	40p	ZG345	15p	2N3053	20p	2N5172	12p	2N4063	12p
AC176	23p	ASY26	25p	BC170	12p	BF153	35p	BSY25	15p	OC41	20p	ZG371	13p	2N3055	63p	25034	75p	2N4064	15p
AC177	20p	ASY27	30p	BC171	13p	BF154	35p	BSY26	15p	OC42	20p	ZG371B	10p	2N3056	63p	25035	75p	2N4065	15p
AC187	30p	ASY28	25p	BC172	13p	BF157	35p	BSY27	15p	OC44	15p	ZG374	17p	2N3057	20p	25036	75p	2N4066	15p
AC188	30p	ASY29	25p	BC173	13p	BF158	30p	BSY28	15p	OC45	12p	ZG377	27p	2N3058	20p	25037	75p	2N4067	15p
AC17	25p	ASY50	25p	BC174	13p	BF159	30p	BSY29	15p	OC70	15p	ZG378	27p	2N3059	20p	25038	75p	2N4068	15p
AC18	20p	ASY51	25p	BC175	22p	BF160	30p	BSY38	15p	OC71	9p	ZG382	15p	2N3060	20p	25039	75p	2N4069	15p
AC19	22p	ASY52	25p	BC177	17p	BF162	30p	BSY39	15p	OC72	12p	ZG401	12p	2N3061	20p	25040	75p	2N4070	15p
AC20	20p	ASY54	25p	BC178	17p	BF163	35p	BSY40	15p	OC74	12p	ZG414	30p	2N3062	22p	2N3402	22p	25041	75p
AC21	20p	ASY55	25p	BC179	17p	BF164	35p	BSY41	15p	OC75	15p	ZG417	25p	2N3063	22p	2N3403	22p	25042	75p
AC22	19p	ASY56	25p	BC180	20p	BF165	35p	BSY42	15p	OC76	15p	ZG418	25p	2N3064	22p	2N3404	22p	25043	75p
AC27	18p	ASY57	25p	BC181	22p	BF167	22p	BSY95A	12p	OC77	12p	ZG419	25p	2N3065	22p	2N3405	22p	25044	75p
AC28	19p	ASY58	25p	BC182	10p	BF173	22p	BU105	£3.90	OC81	15p	ZG420	25p	2N3066	22p	2N3406	22p	25045	75p
AC29	30p	ASY58	25p	BC182L	10p	BF176	35p	CI11E	60p	OC81D	15p	ZG421	25p	2N3067	22p	2N3407	22p	25046	75p
AC30	25p	ASZ21	10p	BC183	10p	BF177	35p	C400	30p	OC82	15p	ZG422	25p	2N3068	22p	2N3408	22p	25047	75p
AC31	25p	BC107	10p	BC183L	10p	BF178	45p	C407	25p	OC82D	15p	ZG423	25p	2N3069	22p	2N3409	22p	25048	75p
AC32	18p	BC108	10p	BC184	13p	BF179	50p	C424	17p	OC83	20p	ZG424	25p	2N3070	22p	2N3410	22p	25049	75p
AC33	18p	BC109	11p	BC184L	13p	BF180	30p	C425	40p	OC84	20p	ZG425	25p	2N3071	22p	2N3411	22p	25050	75p
AC35	30p	BC110	11p	BC185	27p	BF181	30p	C426	30p	OC139	15p	ZG426	25p	2N3072	22p	2N3412	22p	25051	75p
AC36	30p	BC113	35p	BC186	27p	BF182	30p	C428	20p	OC140	12p	ZG427	25p	2N3073	22p	2N3413	22p	25052	75p
AC40	15p	BC114	30p	BC187	27p	BF182	30p	C429	20p	OC170	15p	ZG428	25p	2N3074	22p	2N3414	22p	25053	75p
AC41	18p	BC115	30p	BC207	11p	BF183	30p	C441	27p	OC171	15p	ZG429	25p	2N3075	22p	2N3415	22p	25054	75p
AC44	35p	BC116	35p	BC209	11p	BF184	25p	C442	35p	OC171	15p	ZG430	25p	2N3076	22p	2N3416	22p	25055	75p
AD140	40p	BC117	35p	BC209	11p	BF185	30p	C444	37p	OC200	25p	ZG431	25p	2N3077	22p	2N3417	22p	25056	75p
AD142	40p	BC118	35p	BC212L	11p	BF186	30p	C450	17p	OC201	27p	ZG432	25p	2N3078	22p	2N3418	22p	25057	75p
AD149	35p	BC119	45p	BC213L	11p	BF194	23p	C730	12p	OC202	27p	ZG433	25p	2N3079	22p	2N3419	22p	25058	75p
AD161	35p	BC125	35p	BC213L	11p	BF195	24p	C722	25p	OC203	25p	ZG434	25p	2N3080	22p	2N3420	22p	25059	75p
AD162	35p	BC126	35p	BC214L	12p	BF196	30p	C740	25p	OC204	25p	ZG435	25p	2N3081	22p	2N3421	22p	25060	75p
AD161(1)	63p	BC132	30p	BC225	25p	BF197	35p	C742	17p	OC205	35p	ZG436	25p	2N3082	22p	2N3422	22p	25061	75p
AD161(2)	63p	BC134	30p	BC226	35p	BF200	45p	C744	17p	OC309	35p	ZG437	25p	2N3083	22p	2N3423	22p	25062	75p
AD1140	50p	BC135	30p	BC217	12p	BF222	80p	C760	17p	P346A	17p	ZG438	25p	2N3084	22p	2N3424	22p	25063	75p
ADZ11	£2.10	BC136	30p	BC318	12p	BF257	35p	C762	17p	P397	17p	ZG439	25p	2N3085	22p	2N3425	22p	25064	75p
ADZ12	£2.10	BC137	35p	BC319	12p	BF270	25p	C764	60p	ORP71	43p	ZG440	25p	2N3086	22p	2N3426	22p	25065	75p
AF114	17p	BC139	45p	BCY30	20p	BF271	17p	EC401	15p	ORP12	43p	ZG441	25p	2N3087	22p	2N3427	22p	25066	75p

DIODES & RECTIFIERS

AA119	8p	BYZ11	32p	OA81	7p
AA120	8p	BYZ12	30p	OA85	7p
BA116	22p	BYZ13	25p	OA90	6p
BA126	22p	BYZ16	35p	OA91	7p
BY100	15p	BYZ17	35p	CA95	6p
BY101	12p	BYZ18	30p	OA200	6p
BY105	15p	BYZ19	25p	SO10	4p
BY114	12p	OAS	17p	SO19	4p
BY126	15p	OAI0	22p	IN914	6p
BY127	17p	OA7	7p	IN916	6p
BY130	15p	OA70	7p	IN918	6p
BYZ10	35p	OA79	8p	IN4148	6p

500,000

SILICON PLANAR

NPN-PNP PLASTIC AND TRANSISTORS METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

TYPE STN18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSX27-95A, BSX44-76-77.
Price: 500 £9; 1,000 £15

TYPE STP18. Silicon Planar Transistors pnp TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above nnp type device type STN18.
Price: 500 £9; 1,000 £15

TYPE STN5. Silicon Planar Transistors nnp TO-5 Metal Can. Types similar to: BFY50-51-52 and 2N1292-92.
Price: 500 £9-50; 1,000 £16

TYPE STPL. As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above nnp devices type STNL.
Price: 500 £7-50; 1,000 £13

TYPE STNK. Silicon Planar Plastic Transistor nnp with TO-18 pin circular lead configuration, I.C. 200mA, 300mV and similar to BC107-B-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8.
Price: 500 £9-50; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

200,000

SILICON ALLOY

TRANSISTORS

Clearance of pnp Silicon Transistors from the 2S300 (TO-5) and 2S320 (SO-2) range and similar to the GC200-205 and BCY30-34 series. Ideal for Amateur Electronics, Radio Hams and for experimental use in Schools, Colleges and Industry.

Approximate count by weight:
100 off—75p (plus p. & p. 10p)
300 off—£1.75 (plus p. & p. 15p)
500 off—£2.50 (plus p. & p. 17p)
1,000 off—£4 (plus p. & p. 25p)
10,000 off—£35 (plus p. & p. 55p)

Large quantities quoted for on request.
EXPORT INQUIRIES WELCOME

DIOTRAN

SALES

PO BOX 5, WARE, HERTS

Full Money-Back

Guarantee

POSTAGE & PACKING 7p

10 MILLION DIODES

Silicon or Germanium

State which when ordering

200	50p	10,000	£10.00
1,000	£2.00	50,000	£30.00
5,000	£7.00	100,000	£50.00

2,000,000 SILICON

PLANAR TRANSISTORS

TO18 P.N.P. & N.P.N. TYPES

State which when ordering

DISTRIBUTION PANELS

Just what you need for work bench or lab.

4 x 13A sockets in metal box to take standard 13A fused plug and on-off switch with neon warning light. Supplied complete with 2 feet of heavy cable. Wired up ready to work. £2.95 plus £2.25 with fitted 13A plug; £2.40 with fitted 13A plug, plus 23p Post and Insurance.

MULTI-SPEED MOTOR

Six speeds are available 600, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,300 r.p.m. Shaft is 3/16" diameter and approximately 1/2" long. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 1/2" dia. x 3 1/2" long. Price 88p plus 23p postage, and insurance.

RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckon your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.

SPARTAN Portable RADIO

Long and medium wave, 7 transistor, size 6 1/2" x 4 1/2" x 1 1/2" with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, carrying and case £3.75 plus 25p post and ins.

EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 3 1/2" casing with 3 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2 plus 36p post and ins.

MAINS MOTOR

Precision made as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Ship at 50p. Postage 13p for first one then 5p for each one ordered.

TELEPHONE DIAL

Ex-G.P.O. Perfect working order. 50p each.

TELEPHONE HANDSET

Ex-G.P.O. Perfect order. 50p each plus 20p P. & P.

SELECTOR SWITCHES

Ex-G.P.O. All in good working order.
3 pole £1.25 5 pole £1.75
4 pole £1.50 6 pole £2.00
plus 20p P. & P.

QUICK CUPPA

Mini Immersion Heater, 350W, 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at hand for tea, baby's food, etc. £1.25, post and insurance 13p. 12V car model also available same price. Just call £1.50 plus P. & P. 14p.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 0V, 9V, 12V volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 83p, plus 18p postage.

MICRO SWITCH

5 amp changeover contacts. 9p each. £1 doz. 15 amp on/off Model. 10p each or £1.05 doz. 15 amp changeover 15p each 10 for 135p.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kits of parts for improved and even more efficient version (P.W. June), price £4.95. When ordering please specify whether for positive or negative systems. Plus 30p post.

ELECTRONIC IGNITION

RADIO STETHOSCOPE

Easiest way to find and trace signal from aerial to speaker when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.25 stethoscope instead of earpiece. 25p extra post and ins. 20p.

STANDARD WAFER SWITCHES

Standard size 1/2" wafer—silver-plated 5amp contact, standard 1/2" spindle 2 1/2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	70p	70p						
3 poles	40p	40p	40p	40p	70p	70p	70p	95p	95p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1.20	£1.20
5 poles	40p	40p	70p	70p	85p	85p	85p	£1.45	£1.45
6 poles	40p	70p	70p	85p	85p	85p	85p	£1.70	£1.70
7 poles	70p	70p	85p	£1.20	£1.20	£1.20	£1.20	£1.95	£1.95
8 poles	70p	70p	85p	£1.20	£1.20	£1.20	£2.20	£2.20	£2.20
9 poles	70p	70p	85p	£1.45	£1.45	£1.45	£2.45	£2.45	£2.45
10 poles	70p	70p	85p	£1.20	£1.45	£1.45	£1.45	£2.70	£2.70
11 poles	70p	85p	85p	£1.20	£1.70	£1.70	£1.70	£2.95	£2.95
12 poles	70p	85p	85p	£1.20	£1.70	£1.70	£1.70	£3.20	£3.20

TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and flower heaters costing £13 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal lined case or cabinet. Only need control switch. £3.50. 2kW. Model as above except 2 kilowatts £2.50. Don't miss this. Control Switch 35p. P. & P. 30p.

THIS MONTH'S SNIP

MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohm speakers. Infit suitable for crystal pic, or pick-up. 9V battery operated. Size 2 1/2" long x 1 1/2" wide x 1 1/2" high. SPECIAL SNIP PRICE 60p each, 10 for £5.

POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit, house wiring, car electrics. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or 2 for 50p. Post paid.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 chance-over micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 r.p.m. Some of the many uses of this timer are: Machinery control, Boiler firing, Dispensing and Venting machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £5.75 plus 25p post and insurance. Don't miss this terrific bargain.

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip (IP) amplifiers. The 5th is a monolithic 80p matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data or data. Complete parcel only £1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.

BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese-nickel-silver oxide and alkaline batteries may be tested. The meter puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2 1/2" with leads and prods. Price £1.75 plus 20p postage.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboards. Has spindle for pointer knobs. Quickly adjustable from 30-80°F. 40p. Calibrated dial 20p extra. Suitable box for wall mounting. 25p.

Type "B" 15 amp. This is a 17 1/2" long rod type made by the famous Sunvic Co. Spindle adjusts from 30-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1000°F. Suitable

heater or to make flame-stat or fire alarm. 43p plus 12p post and insurance.

Type "D" We call this the frost-stat as it cuts in and out at around freezing point. 2.3 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16yd. 50p) is wound round the pipes. 40p.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 50p.

Type "F". Glass enclosed for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (dial submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 30 to 150°F. Price 80p.

TREASURE TRACER

Complete Kit (except wooden battery) to make the metal detector as the circuit in Practical Wireless August issue. £2.95 plus 20p post and insurance.

DRILL CONTROLLER NEW 1KW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available. £2.25 plus 13p post and p.

CONTROL DRILL SPEEDS

HIGH ACCURACY THERMOSTAT Uses differential comparator I.C. with thermostat as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £5.70.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.75 plus 25p post and ins.

AUTO-LITE

as circuit in P.W. Kit of parts £1.20 post paid.

TOGGLE SWITCH

3 amp 250V with fixing ring 73p each, 75p/doz.

CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for £3.42.

ROCKER SWITCH

13 amp self-fixing into an oblong hole. size approximately 2 1/2" x 2 1/2". 6p each, 10 for 54p.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V a.c. Good British Make. Unused. Size approx. 1 1/2" x 1 1/2". Open construction. Single pole 25p each 10 for £2.25. Treble pole 40p each 10 for £3.60.

BALANCED ARMATURE UNIT

500 ohm, operates speaker or microphone, so useful in intercom or similar circuits. 33p each. £3.30 doz.

2kW FAN HEATER


Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central flow cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £3.95. Post and ins. 38p.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p. Over £1 post free. S.A.E. with enquiries please.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.) 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon.


SUPERSOUND 13 HI-FI MONO AMPLIFIER

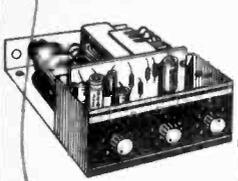

A superb solid state audio amplifier. Brand new components throughout. 3 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W rms into 8 ohm. Frequency response 12Hz-30kHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 4in wide x 7in deep. A.C. 200/250V.

PRICE £10.50 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

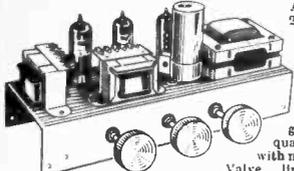

A.C. mains 200/240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2x ECL86 Triode Pentodes.

12E230 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control in stereo. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 30mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. x 4in. x Overall height including valves 5in. Ready built and tested to a high standard. Price £8.92. P. & P. 45p.

SPECIAL PURCHASE OF MANUFACTURER'S SURPLUS: All Transistor F.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. F.M. R.F. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s) transistor with optional AFC connection. Built on printed circuit panel and fully screened. Medium stable over range 88-108 Mc/s. Brand new and pre-aligned. Size 2 1/2 in H. x 1 1/4 in W. x 2 1/4 in D. For 6V D.C. @ 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. **LIMITED NUMBER.** Only £2.25 post free. Connection details supplied.

SPECIAL PURCHASE!

BRAND NEW FM MULTIPLEX STEREO DECODER UNITS. Manufactured by PHILIPS. Size 2 1/2 in x 3 1/2 in x 1 1/2 in. All transistor 24V at 6mA. Supplied pre-aligned with full circuit diagram and connection details. £4 each. Post free.

INPUT MATCHING TRANSFORMER. Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2 in high x 1 1/2 in dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick-up from low to high impedance or vice versa. 75p each. Post free.

BLACK ANODISED ALUMINIUM HEAT SINKS. For T08, complete with mica's and bushes. Size 2 1/2 in x 3 in approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER MINUTE BOARDS. Size 6 in x 4 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC ARMATURES WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to approx. 22in. Maximum diameter 1in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 12 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-30-40-60V half amp. 0-10-20-30-40-60V at 2 amps all ways. Size 3 1/2 in x 3 1/2 in W x 3 in D. Price £1.75. P. & P. 25p.

MAIN TRANSFORMER. For transistor power supplies. H.T. 200/240V. Sec. 9-0-9 at 300mA. 70p. P. & P. 3p. H.T. 200/240V. Sec. 10-0-10 at 1 amp. 85p. P. & P. 3p. H.T. 200/240V. Sec. 10-0-10 at 2 amp. £1.25. P. & P. 3p. Tapped Primary 200-220-240V. Sec. 9-0-9 at 300mA. 70p. P. & P. 3p.

1.5 AM BATTERY CHARGER TRANSFORMER. Brand new. For 6 or 12V 300V Primary. Secondary 3.5 r.m.s. off load 10 and 16.5V. Overall size approx. 2 1/2 in x 3 in. Weight 3lb. Limited number at £1.85. P. & P. 35p.

4-SPEED RECORD PLAYER BARGAINS
Main models. All brand new in maker's packing.
LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £8.97. Carr. 50p.
With stereo cartridge £7.97. Carr. 50p.
LATEST GARRARD MODELS. S.A.E. for Latest Prices!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025, 3000, 3000, 3100, SP25 II and III, SL65B, AT90, etc., or B.S.R. C109, C129, A21, etc. Choice of black leatherette or teak grain finish. Size 12 1/2 in x 14 1/2 in x 3 1/2 in high (approx. 7 1/2 in high, including rigid smoked acrylic cover). Price **£5.50** P. & P. 60p.

LATEST ACOS GP18180 Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

SONOTONE STANC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST ROHETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo 78. £1.88. P. & P. 10p.

LATEST ROHETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6h. Ready built and tested. **PRICE £3.75.** P. & P. 40p. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit cabinet below. **PRICE £4.88.** P. & P. 50p.

DE LUXE QUALITY PORTABLE E/P CABINET MK II
Output motor board size 14 1/2 in. clearance 2 in. below, 6 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT90 and SP25). Size 18 1/2 x 15 1/2 in. **PRICE £4.75.** P. & P. 50p.

SPECIAL OFFER!!

HI-FI LOUDSPEAKER SYSTEM
Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2 in high x 10 1/2 in wide x 5 1/2 in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Carr. 65p.
CABINET AVAILABLE SEPARATELY £4.50

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £6.10. Carr. 65p.

LOUDSPEAKER BARGAINS

5in 3 ohm 80p. P. & P. 15p. 7 x 4in 3 ohm £1.05. P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 3in 3 ohm with high flux magnet £1.92. P. & P. 20p. E.M.I. 13 x 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW. 12in low H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic magnet assembly £5.0. Guitar models: 25w £6.50 35w £8.50. P. & P. 35p each. E.M.I. 3in HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohm 85p each. P. & P. 13p.

12in "BA" TWIN CONE LOUDSPEAKER
10 watts peak handling. 3, 8 or 15 ohm, £2.20. P. & P. 30p. 15 ohm SPEAKERS 3". ONLY 63p. P. & P. 13p.

"POLY PLANAR" WATER-PROOF WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 1 1/2 in x 14 1/2 in x 1 1/2 in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

VYNALD & REXINE SPEAKERS & CABINET FABRIC
app. 54 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES


Adjustable headband with comfortable flexi-foam earmuffs. Wired and fitted with standard stereo 1/4 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £2.95.** P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR **PRICE £1.05.** P. & P. 8p.

GENERAL PURPOSE HIGH STABILITY TRANSMITTER PRE-AMPLIFIER. P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/240V. Frequency response 16Hz-25KHz. Gain 20. Full wave encapsulation size 12 x 1 1/2 in. Brand new - complete with instructions. Price 85p. P. & P. 13p.

GENUINE ZERO MINIATURE MOVING COIL METER. 100A for balance or tuning. Approx. size 1in x 1/2 in. Limited number 75p. P. & P. 10p.

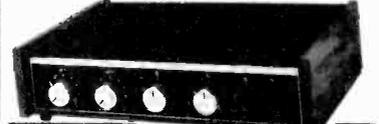HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts - no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over full amp. Power requirements 35V at 1-0 amp. Overall size - 12" wide x 8" deep x 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES AMPLIFIER KIT, £10.50 P. & P. 15p.
POWER PACK KIT, £3 P. & P. 30p.
CABINET, £3 P. & P. 30p.

(Post Free) All units purchased at same time! Full after sales service. Also available ready built and tested, £20.50. Post Free.

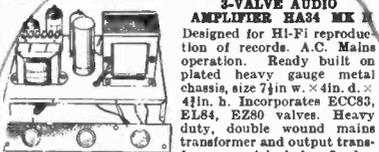Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi DiTcoque etc. etc.



3-VALVE AUDIO AMPLIFIER HA34 MK I
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. x 4 1/2 in. x 4 1/2 in. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.95. P. & P. 40p.


HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL86 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely brand new, completely wired and tested with good quality output transformer. **£5W ONLY.**

OUR ROCK BOTTOM BARGAIN PRICE **£2.75** P. & P. 35p

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished mono amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving loud lift and cut. Valve line-up 2 EL84s, ECC83, E788 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. **ONLY £7.97.** P. & P. 55p. Also available ready built and tested complete with input sockets, £9.97. P. & P. 55p.

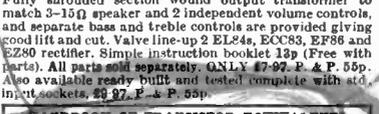

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. **ONLY 40p.** Post free.

Open 9.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.
170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



KONTAKT 60

FOR INACCESSIBLE CONTACTS—More than just a cleaner. KONTAKT 60 guarantees perfect cleaning of contacts chemically in accordance with today's technology.

KONTAKT offers the following advantages:—

1. Dissolves oxides and sulphides the safe way without attacking contact substances.
2. Contains carefully selected solvents which do not attack plastics whereas they do dissolve resinified contact greases and dirt.
3. Contains no silicone.
4. Contains a light lubricant in order to avoid the contact paths being corroded.
5. Prevents further oxidation setting in.
6. Prevents "creep" currents.

Because of these outstanding properties KONTAKT 60 is one of the best and most popular contact cleansing agents in the world.

Users include: Rolls Royce Ltd., C.E.G.B., South of Scotland Electricity Board, Trinity House Workshops, Kolster Brandes, Mullard, Plessey Cos., etc.

OTHER KONTAKT PRODUCTS ARE:

- 70 Protective Lacquer
- 72 Insulating Spray
- 75 Cold Spray For Fault Location
- 80 Special Siliconized Polish
- 100 Antistatic Agent For Plastics
- 101 Dehydration Fluid

Write for full details of above complete range of Kontakt products to:—

SPECIAL PRODUCTS DISTRIBUTORS LIMITED

81 Piccadilly, London, W.1 01-629 9556

IN 15 MINUTES YOU COULD HAVE GUNTON ELECTRONIC IGNITION FITTED TO YOUR CAR

Capacitive Discharge Ignition is recognised as being the most efficient ignition system and will give you:

- CONTINUAL PEAK PERFORMANCE
- UP TO 20% REDUCED FUEL CONSUMPTION
- EASIER ALL-WEATHER STARTING
- INCREASED ACCELERATION & TOP SPEED
- LONGER SPARK PLUG LIFE
- INCREASED BATTERY LIFE
- CONTACT BURN ELIMINATED
- PURER EXHAUST GAS EMISSION



For all petrol engines—cars,

boats, etc. Guaranteed for 5 yrs. Complete Installation Kit for 12-volt vehicles £12.95 + 45p P. & P. State earth polarity of vehicle POSITIVE or NEGATIVE earth. Unit Construction Kit also available for the radio electronics constructor £9.95 + 45p P. & P. The construction kit includes instructions and all components for wiring as positive or negative earth, and is complete with the stove enamelled steel case and aluminium base.

Money back guarantee. S.A.E. for leaflet. P.E. SCORPIO Components: Transformer and Mounting Kit £11.85 + 25p P. & P. Printed Circuit Board 60p + 10p P. & P. Case and Hardware as above £1.85 + 25p P. & P.

ELECTRONICS DESIGN ASSOCIATES

82 BATH STREET, WALSALL WS1 3DE

If you have difficulty in obtaining

PRACTICAL ELECTRONICS

Please place a regular order with your newsgent or send 1 year's subscription (£2.65) to Subscription Department, Practical Electronics, Fleetway House, Farringdon St., London, E.C.4.

MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES LARGEST RANGE

BRAND NEW FULLY GUARANTEED

MOTOROLA

We can now offer a vast range of Motorola IC's at industrial distributor prices.

Examples	£p	Data Sheets
MC724P	0.66	
MC790P	1.24	
MC1303L	2.70	20-121 extra

1-11	12-24	1-11	12-24
£p	£p	£p	£p
SN7406	0.80 0.75	SN7493	0.87 0.84
SN7407	0.20 0.18	SN7494	0.87 0.84
SN7408	0.20 0.18	SN7495	0.87 0.84
SN7409	0.20 0.18	SN7496	0.87 0.84
SN7410	0.20 0.18	SN7497	6.40 6.00
SN7411	0.23 0.21	SN74100	1.66 1.58
SN7412	0.48 0.48	SN74104	1.62 1.40
SN7413	0.40 0.38	SN74105	1.52 1.40
SN7416	0.84 0.78	SN74107	0.52 0.49
SN7417	0.84 0.78	SN74110	0.80 0.75
SN7420	0.20 0.18	SN74111	1.67 1.45
SN7423	0.51 0.47	SN74118	1.30 1.25
SN7425	0.48 0.46	SN74119	1.92 1.80
SN7427	0.48 0.45	SN74121	0.50 0.47
SN7428	0.80 0.75	SN74122	1.44 1.35
SN7430	0.23 0.15	SN74123	2.85 2.70
SN7432	0.48 0.42	SN74145	1.80 1.75
SN7433	0.80 0.75	SN74150	3.52 3.40
SN7437	0.64 0.60	SN74151	1.40 1.35
SN7438	0.64 0.60	SN74153	1.40 1.35
SN7440	0.23 0.21	SN74154	2.20 2.10
SN7441	0.87 0.83	SN74155	1.68 1.60
SN7442	0.85 0.81	SN74156	1.68 1.60
SN7443	2.86 2.70	SN74157	1.92 1.82
SN7444	2.86 2.70	SN74160	1.80 1.75
SN7445	2.50 2.40	SN74161	2.80 2.65
SN7446	1.00 0.95	SN74164	2.40 2.30
SN7447	1.00 0.95	SN74163	4.26 4.10
SN7448	1.00 0.95	SN74164	2.20 2.10
SN7449	1.00 0.95	SN74165	2.28 2.15
SN7450	0.20 0.18	SN74166	4.45 4.20
SN7451	0.20 0.18	SN74167	6.40 6.10
SN7453	0.20 0.18	SN74170	4.38 4.10
SN7454	0.20 0.18	SN74171	4.40 4.30
SN7460	0.20 0.18	SN74175	1.68 1.60
SN7470	0.40 0.38	SN74176	2.64 2.55
SN7472	0.32 0.30	SN74177	2.64 2.55
SN7473	0.45 0.41	SN74180	2.13 2.05
SN7474	0.45 0.41	SN74181	9.33 9.00
SN7475	0.45 0.41	SN74182	2.32 2.25
SN7476	0.45 0.44	SN74184	4.80 4.60
SN7480	0.70 0.65	SN74185	4.80 4.60
SN7481	1.40 1.38	SN74190	1.80 1.70
SN7482	0.87 0.82	SN74191	1.80 1.70
SN7483	0.87 0.82	SN74192	1.75 1.80
SN7484	2.00 1.95	SN74193	2.75 2.65
SN7485	3.82 3.80	SN74194	2.87 2.85
SN7486	0.33 0.30	SN74195	2.25 2.10
SN7490	0.87 0.84	SN74196	2.64 2.55
SN7491	1.21 1.10	SN74198	5.95 5.85
SN7492	0.87 0.84	SN74199	5.95 5.85

FAIRCHILD (RTL)

	1-5	6-11	12-4
	40p	37p	35p
L900	40p	37p	35p
L914	40p	37p	35p
L923	40p	37p	35p

Data sheet 121p

LINEAR

Op. Amps.	1-11	12-24	25-99
	£p	£p	£p
L702A TO5	2.80	2.70	2.60
L702C TO5	0.77	0.72	0.67
L703C TO5	0.82	0.57	0.52
L709A TO5	1.25	1.20	1.15
L709C TO5	0.47	0.42	0.37
L709E DIL	0.45	0.40	0.35
L710C DIL	0.47	0.42	0.37
L710E DIL	0.45	0.40	0.35
L711C TO5	0.49	0.44	0.39
L711E DIL	0.45	0.40	0.35
L713C TO5	1.87	1.75	1.70
L714C TO5	0.80	0.85	0.80
L714E DIL	0.80	0.75	0.65
L714C DIL	0.70	0.65	0.60
LM741C DIL	0.70	0.65	0.60
SN7209P DIL	0.45	0.40	0.35

MULLARD PLESSEY

TTL	£p	SL403D	1.50
FJH110	0.87	SL611C	1.70
FJH121	0.87	SL921C	2.60
FJH141	0.87	SL701C	1.45
FJH161	0.87	SL702C	1.25
FJH171	0.91		
FJH221	0.87		
FJH221	1.37		171p
FJH221	1.87		
FJH221	3.12		
FJH221	1.87		
FJH221	3.12		
FJK101	2.25		
FJY101	0.80		

TOSHIBA

	£p
TH9013P	£4.57
20 WATT AMP	
TH9014P	£1.50
PRE-AMP	
DATA SHEETS	20-121

MULLARD DTL

	£p
FCH101	0.87
FCH121	1.05
FCH201	1.32
FCH231	1.50
FCJ101	1.62
FCJ111	1.55
FCJ201	1.80
FCJ211	2.75
FCJ101	4.87
FCY101	1.05

MULLARD LINEAR

	£p
TAA241	1.30
	2.42
	2.63
	0.80
	2.00
	1.30
	3.20
	0.65
	2.10
	4.35
	0.73
	0.57
	1.13
	4.95
	2.60
	4.45
	0.97
	1.87
	1.87

GENERAL ELECTRIC

	£p
PA222	2.70
PA230	1.31
PA234	0.88
PA257	1.11
PA259	2.21
PA246	1.54
PA264	1.76
PA265	1.93
PA424	1.99
PA435	1.76
PA494	2.10

SGS

TAA661B	£1.32	TAA700	£3.50
TAA621	£2.03	TBA651	£1.69
All TTL IC's may be mixed to qualify for quantity discounts.			
8 Pin TO-5 I.C. Holders, £0.90			
10 Pin TO-5 I.C. Holders, £0.25			
12 Pin TO-5 I.C. Holders, £0.40			
8 Pin Dual-in-Line I.C. Holders, £0.20			
14 Pin Dual-in-Line I.C. Holders, £0.20			
16 Pin Dual-in-Line I.C. Holders, £0.25			

TTL LOGICS

1-11	12-24	1-11	12-24
£p	£p	£p	£p
SN7400	0.20 0.18	SN7403	0.20 0.18
SN7401	0.20 0.18	SN7404	0.20 0.18
SN7402	0.20 0.18	SN7405	0.20 0.18

SGS EA 1000

3 watt Audio Amplifier Module £2.10
Data Sheets 10p each

RCA

Type	1-24	25-99	Type	1-24	25-99
	£p	£p		£p	£p
CA3000	1.80	1.60	CA3033A	4.26	3.80
CA3000V1	1.80	1.60	CA3035	1.23	1.10
CA3001	2.69	2.40	CA3035V1	1.23	1.10
CA3001V1	2.69	2.40	CA3036	0.73	0.65
CA3002	1.80	1.60	CA3037	1.65	1.47
CA3002V1	1.80	1.60	CA3037A	1.99	1.80
CA3004	1.80	1.60	CA3038	2.53	2.25
CA3005	1.17	1.05	CA3038A	3.40	3.08
CA3006	2.80	2.50	CA3039	0.84	0.75
CA3007	2.63	2.34	CA3040	2.40	2.14
CA3008	1.80	1.60	CA3041	1.09	0.97
CA3008A	2.92	2.64	CA3042	1.99	1.80
CA3010	1.37	1.23	CA3043	1.37	1.25
CA3010A	2.53	2.25	CA3044	1.20	1.07
CA3011	0.74	0.65	CA3044V1	1.20	1.07
CA3011PRE			CA3045	1.23	1.09
	0.74	0.65	CA3046	0.69	0.60
CA3012	0.89	0.78	CA3047	1.37	1.23
CA3012V1	0.89	0.78	CA3047A	2.53	2.25
CA3013	1.05	0.94	CA3048	2.04	1.81
CA3014	1.24	1.10	CA3049	1.60	1.48
CA3014V1	1.24	1.10	CA3050	1.84	1.64
CA3015	2.09	1.86	CA3051	1.84	1.40
CA3015A	3.40	3.03	CA3052	1.65	1.27
CA3016	2.45	2.18	CA3053	0.46	0.41
CA3016A	3.73	3.33	CA3054	1.09	0.97
CA3018	0.84	0.75	CA3055	1.69	1.51
CA3018A	1.10	0.99	CA3056	1.20	1.07
CA3019	0.84	0.75	CA3056A	3.10	2.86
CA3020	1.25	1.13	CA3059	1.65	1.46
CA3020A	1.80	1.43	CA3060	1.70	1.51
CA3021	1.51	1.39	CA3062	2.56	2.27
CA3021V1	1.51	1.39	CA3064	1.20	1.07
CA3022	1.30	1.18	CA3065	1.20	1.07
CA3023	1.26	1.13	CA3066	2.11	1.88

LARGEST STOCKS SEMICONDUCTORS & COMPONENTS BRAND NEW WIDEST RANGE GUARANTEED

TRANSISTORS

2N301	20p	2N3405	45p	40311	35p	BC172	15p	88W70	271p	NKT238	25p
2N302	20p	2N3414	221p	40312	47p	BC175	281p	88X19	171p	NKT240	25p
2N303	20p	2N3415	221p	40313	47p	BC182	10p	88X20	171p	NKT241	25p
2N306	421p	2N3416	371p	40320	471p	BC183	9p	88X21	371p	NKT242	25p
2N308	20p	2N3417	371p	40323	371p	BC184	11p	88X22	45p	NKT243	25p
2N309	30p	2N3418	21p	40324	371p	BC185	13p	88X23	21p	NKT244	25p
2G371	16p	2N3472	971p	40328	371p	BCY30	271p	88X25	471p	NKT245	25p
2G374	20p	2N3605	271p	40329	30p	BCY31	30p	88X26	321p	NKT291	20p
2G381	221p	2N3606	271p	40344	271p	BCY32	50p	88X60	821p	NKT262	30p
2N404	221p	2N3607	221p	40347	271p	BCY33	25p	88X76	221p	NKT264	20p
2N696	20p	2N3702	11p	40348	521p	BCY34	30p	88X77	271p	NKT271	20p
2N697	20p	2N3703	10p	40360	421p	BCY38	40p	88X78	271p	NKT272	20p
2N698	20p	2N3704	11p	40361	471p	BCY40	60p	88X78	271p	NKT274	20p
2N706	121p	2N3705	10p	40362	571p	HCY42	15p	88Y10	271p	NKT281	271p
2N706A	121p	2N3706	9p	40370	371p	BCY43	15p	88Y11	271p	NKT401	871p
2N708	181p	2N3707	11p	40406	571p	BCY44	321p	88Y24	15p	NKT402	87p
2N709	621p	2N3708	7p	40407	571p	BCY58	221p	88Y25	15p	NKT403	76p
2N718	20p	2N3709	9p	40408	521p	BCY59	221p	88Y27	171p	NKT404	821p
2N726	30p	2N3710	9p	40410	621p	BCY60	671p	88Y27	171p	NKT405	75p
2N727	30p	2N3711	13p	40410	621p	BCY70	30p	88Y28	171p	NKT406	621p
2N914	171p	2N3715	£1.25	40467A	571p	BCY70	30p	88Y29	171p	NKT452	821p
2N916	171p	2N3716	£1.30	40488A	571p	BCY71	25p	88Y29	171p	NKT452	821p
2N918	30p	2N3791	06.06	06600	571p	BCY72	171p	88Y29	171p	NKT452	821p
2N929	221p	2N3819	35p	06673	85p	BCZ10	271p	88Y36	25p	NKT463	471p
2N930	221p	2N3823	371p	AC107	30p	BCZ11	171p	88Y37	25p	NKT603P	371p
2N1090	221p	2N3824	371p	AC108	30p	BCZ16	£1.22	88Y38	221p	NKT613P	321p
2N1091	221p	2N3854	271p	AC127	25p	BD121	65p	88Y39	221p	NKT614P	321p
2N1131	20p	2N3855	271p	AC128	20p	BD123	821p	88Y40	321p	NKT614P	321p
2N1132	25p	2N3856A	30p	AC154	25p	BD124	60p	88Y41	321p	NKT617P	321p
2N1302	171p	2N3856	30p	AC176	25p	BD131	75p	88Y53	371p	NKT781	30p
2N1303	221p	2N3859A	35p	AC187	621p	BD132	85p	88Y54	40p	NKT10419	30p
2N1304	221p	2N3859	25p	AC188	621p	BDY10	£1.37	88Y60	90p	NKT10439	371p
2N1305	221p	2N3859A	371p	ACV17	271p	BDY11	£1.50	88Y78	471p	NKT10519	321p
2N1306	25p	2N3859	271p	ACV18	271p	BDY18	£1.75	88Y79	45p	NKT20329	371p
2N1307	25p	2N3859A	321p	ACV19	25p	BDY19	£1.97	88Y82	521p	NKT20339	371p
2N1308	30p	2N3860	30p	ACV20	25p	BDY20	£1.12	88Y90	521p	NKT80111	771p
2N1309	30p	2N3866	£1.50	ACV21	20p	BDY38	971p	88Y95A	12p	NKT80113	72p
2N1607	171p	2N3877	40p	ACV22	20p	BDY58	10.25	C111	12p	NKT80113	72p
2N1613	20p	2N3878	40p	ACV28	20p	BDY60	10.25	C111	12p	NKT80113	72p
2N1631	30p	2N3900	371p	ACV18	20p	BDY62	£1.25	C424	271p	NKT80212	921p
2N1632	30p	2N3900A	40p	ACV40	20p	BDY62	£1.25	C425	55p	NKT80212	921p
2N1637	30p	2N3901	971p	ACV41	25p	BF115	25p	C426	40p	NKT80212	921p
2N1638	271p	2N3903	35p	ACV44	50p	BF117	471p	C428	371p	NKT80213	921p
2N1671B	£1	2N3904	35p	AD140	421p	BF163	371p	C744	30p	NKT80214	921p
2N1711	321p	2N3905	371p	AD141	521p	BF167	18p	D1E1	621p	NKT80216	921p
2N1712	321p	2N3906	371p	AD142	521p	BF167	18p	D1E1	621p	NKT80216	921p
2N1893	371p	2N4058	171p	AD150	671p	BF167	18p	D1E1	621p	NKT80216	921p
2N2147	821p	2N4059	10p	AD162	371p	BF178	30p	D1E2	371p	NKT80216	921p
2N2148	821p	2N4060	121p	AF106	421p	BF179	30p	D1E74	371p	NKT80216	921p
2N2160	571p	2N4061	121p	AF114	25p	BF180	35p	D40X1	47p	NKT80216	921p
2N2183	40p	2N4062	121p	AF115	25p	BF181	321p	GET102	30p	NKT80216	921p
2N2183A	421p	2N4044	471p	AF116	25p	BF184	25p	GET113	20p	NKT80216	921p
2N2184	30p	2N4063	121p	AF117	25p	BF185	421p	GET114	20p	NKT80216	921p
2N2217	271p	2N4286	171p	AF118	65p	BF194	171p	GET118	20p	NKT80216	921p
2N2218	25p	2N4287	171p	AF119	65p	BF195	15p	GET118	20p	NKT80216	921p
2N2219	25p	2N4288	171p	AF124	221p	BF196	421p	GET119	20p	NKT80216	921p
2N2220	25p	2N4289	171p	AF125	20p	BF197	421p	GET120	521p	NKT80216	921p
2N2221	25p	2N4290	171p	AF126	20p	BF198	421p	GET873	10p	NKT80216	921p
2N2222	30p	2N4291	171p	AF127	171p	BF200	521p	GET889	30p	NKT80216	921p
2N2267	£1.07	2N4292	171p	AF127	171p	BF204	14p	GET894	20p	NKT80216	921p
2N2267	80p	2N4303	471p	AF139	371p	BF225	19p	GET898	221p	NKT80216	921p
2N2368	171p	2N5027	521p	AF178	421p	BF237	23p	GET898	221p	NKT80216	921p
2N2369	171p	2N5028	571p	AF180	521p	BF238	23p	GET896	221p	NKT80216	921p
2N2369A	171p	2N5029	471p	AF181	521p	BF244	23p	GET897	221p	NKT80216	921p
2N2410	421p	2N5030	421p	AF182	521p	BF258	271p	GET898	221p	NKT80216	921p
2N2483	471p	2N5172	121p	AF239	421p	BF259	271p	GET898	221p	NKT80216	921p
2N2484	321p	2N5174	621p	AF279	421p	BF260	25p	MJ400	£1.07	OC75	221p
2N2529	221p	2N5175	621p	AF280	621p	BF261	471p	MJ420	£1.12	OC76	221p
2N2540	221p	2N5176	45p	AF291	321p	BFX12	221p	MJ430	£1.08	OC81	221p
2N2613	36p	2N5220A	30p	ASV26	25p	BFX13	221p	MJ440	£1.08	OC81D	221p
2N2614	30p	2N5245	45p	ASV27	271p	BFX29	30p	MJ480	971p	OC83	25p
2N2615	521p	2N5246	421p	ASV28	271p	BFX30	30p	MJ481	971p	OC83	25p
2N2696	321p	2N5249	871p	ASV29	271p	BFX43	371p	MJ481	£1.25	OC84	25p
2N2711	25p	2N5265	£3.25	ASV36	25p	BFX44	371p	MJ490	£1.01	OC139	321p
2N2712	25p	2N5286	£2.75	ASV50	25p	BFX68	671p	MJ491	£1.37	OC140	321p
2N2713	271p	2N5267	£2.82	ASV51	321p	BFX84	25p	MJ1800	£2.17	OC171	30p
2N2714	30p	2N5305	371p	ASV54	321p	BFX85	25p	MJ1800	£2.17	OC171	30p
2N2865	621p	2N5306	40p	ASV56	321p	BFX86	25p	MJ1800	£2.17	OC171	30p
2N2904	30p	2N5307	371p	ASV58	321p	BFX87	271p	MJE521	73p	OC200	60p
2N2904A	321p	2N5308	371p	ASV21	321p	BFX88	25p	MJE521	73p	OC202	75p
2N2905	371p	2N5309	621p	AU103	£1.25	BFX89	621p	MJE2955	£3.37	OC203	421p
2N2905A	371p	2N5310	421p	BC107	10p	BFX93A	70p	MJE3055	£4.15	OC204	421p
2N2906	25p	2N5354	271p	BC108	10p	BFY10	321p	MPF10	421p	OC205	85p
2N2906A	271p	2N5355	271p	BC109	10p	BFY11	421p	MPF10	421p	OC207	75p
2N2907	30p	2N5356	321p	BC110	10p	BFY17	221p	MPF104	371p	OCPT1	40p
2N2923	15p	2N5365	321p	BC113	15p	BFY18	321p	MPF104	371p	ORP21	50p
2N2924	15p	2N5366	471p	BC115	15p	BFY19	321p	MPF105	371p	ORP21	50p
2N2925	15p	2N5367	571p	BC116A	15p	BFY20	£1.60	MPS3638	321p	P346A	60p
2N2926	20p	2N5457	371p	BC118	10p	BFY21	421p	NKT0013	471p	TIP29A	50p
Green	14p	28005	75p	BC121	20p	BFY24	45p	NKT124	421p	TIP30A	50p
Yellow	181p	28020	22	BC122	20p	BFY25	25p	NKT125	421p	TIP31A	50p
Orange	181p	28021	56p	BC125	20p	BFY26	25p	NKT126	271p	TIP32A	50p
2N3011	30p	28103	25p	BC126	20p	BFY29	50p	NKT128	271p	TIP32A	50p
2N3014	30p	28104	25p	BC140	371p	BFY30	50p	NKT128	271p	TIP34A	50p
2N3053	18p	28501	321p	BC147	10p	BFY41	50p	NKT137	321p	TIS34	621p
2N3054	46p	28502	35p	BC148	10p	BFY43	621p	NKT210	30p	TIS43	621p
2N3055	62p	28503	271p	BC149	10p	BFV60	621p	NKT211	30p	TIS44	621p
2N3133	25p	28104	25p	BC152	171p	BFY32	23p	NKT212	30p	TIS45	621p
2N3134	30p	28109	25p	BC157	20p	BFY33	171p	NKT213	30p	TIS46	621p
2N3135	25p	28140	771p	BC158	11p	BFY56A	571p	NKT215	221p	TIS47	621p
2N3136	25p	28141	721p	BC159	11p	BFY75	30p	NKT216	371p	TIS48	621p
2N3390	25p	28142	55p	BC160	621p	BFY76	421p	NKT217	421p	TIS49	621p
2N3391	20p	28143	55p	BC161	621p	BFY77	571p	NKT219	30p	TIS50	621p
2N3391A	30p	28152	871p	BC167	10p	BFY90	571p	NKT223	271p	TIS51	621p
2N3392	171p	28153	871p	BC168A	10p	BFY90	571p	NKT223	271p	TIS52	621p
2N3393	15p	40050	55p	BC168B	11p	BFX25	£1.85	NKT229	271p	TIS53	621

Practical Electronics Classified Advertisements

RATES: 8p per word (minimum 12 words). Box No. 10p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

MISCELLANEOUS

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW (S.A.E. for details)
TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

DO-IT-YOURSELF... we stock a large range of audio and electronic components at very competitive prices, e.g.: Chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale and Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list. (2 x 3p stamps for fabric samples). Mail order ONLY. No callers please.

AUDIOSCAN Dept. P.E.3/72
4, PRINCES SQUARE,
HARROGATE, YORKS.

RECORD T.V. SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. CROWBOROUGH ELECTRONICS (P.E.), Eridge Road, Crowborough, Sussex.

SOLID State C.ds. Exposure Meter—save pounds! assemble our meter, all parts and simple instructions for your ease. Photo-logic module ensures accuracy over 18 light values. £3.47 or details—TRANIX, 18 Wroxham Close, Shelton Lock, Derby.

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3.30**
or in kit form **£2.90** post paid

SALOP ELECTRONICS Callers welcome
23 Wyle Cop Shrewsbury, Shropshire S.A.E. for lists

CIRCUIT BOARD ETCHING KITS, full instructions, £1.25, c.w.o. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

BUILD IT in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

MISCELLANEOUS (continued)

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACY22	BFY5	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee. P. & P. 10p.

J. M. KING (X)

17 Buckridge, Portpool Lane, London, E.C.1

ORGAN CONSTRUCTORS

A wealth of components for the home enthusiast. Many BIRD_ORGAN parts. S.A.E. for lists.

BARRY M. CHILDE
24 WORTHINGTON CRESCENT
POOLE, DORSET BH14 8BW

CHROMASONIC electronics

1972 CATALOGUE

20p. post free

36 FORTIS GREEN ROAD, LONDON N10 3HH

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**
MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN.
TRIAL KIT £1.28 Carr. Paid
No. 1 KIT £1.88 Carr. Paid
No. 2 KIT £2.39 Carr. Paid
M.P.E. Ltd. (P.E.), BRIDGE ST., CLAY CROSS DERBYS.

LOTS OF

Suppliers forget to tell you, that their metal locators won't function until you've first got a transistor radio with which to beat the locators signal. The BOFFIN TREASURE PROBE, however, comes to your doorstep with PRINTED-CIRCUIT BOARD, all ELECTRONIC COMPONENTS, a ready-drilled box to put it in plus search-coil and earphone. Think of the fun you'll have BEACHCOMBING with the sensitive TREASURE-PROBE, and the expectancy of hearing its LOUD "BEEP" tell you "YOU'RE ON TO SOMETHING" GET YOUR TREASURE-PROBE SEND £6.59 NOW! (S.A.E. for details).

BOFFIN PROJECTS

4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designed by GERRY BROWN & JOHN SALMON and presented on TV

MISCELLANEOUS (continued)

... DON'T LOOK

unless you really want to get the benefit from this collection of SUPER electronic projects. Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN. Find out more that interests YOU!

GET YOUR CATALOGUE — SEND JUST 20p NOW! (S.A.E. for details).

TO: BOFFIN PROJECTS

4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

SWITCHES UNUSUAL

PRESSURE MAT—flexible, hard-wearing plastic, mat containing 180 contacts. Contacts close when pressed, open when released. Rating 50v, 500mA. Size 30in x 24in **£2 each**

MINI MAT—size 24in x 7in. **£1.50** (Tailor made. Price on request). Suitable for burglar alarm, counter, foot switch, games. "Uses limited by imagination."

PROXIMITY SWITCH—in moulded plastic case. Rating 250v, 600mA. **£1.10**

SWITCH PROBLEM? We have multi-range, key operated, infra-red, solid state, etc., etc.

POSTAGE FREE IN U.K. C.W.O.

ELECTRONIC SWITCHING DEVICES
P.O. Box 7, Aspley, P.D.O. Nottingham
For further details send s.a.e.

Guaranteed satisfaction or money back



MICROJET WELDER
A TINY FLAME UP TO
5000°F!
WELDS BRASSES
SOLDERS

£10.99

INC 3
FLAME TIPS

A-precision tool using a combination of butane and compressed oxygen. U.S.A. manufactured. Gives two sizes of flame of pencil lead thickness. Adjustable temperatures up to 5,000°F. Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc., gold and silver. Ideal for electronics and electrical engineering, jewellers, clockmakers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 oxygen and 1 butane cylinders £1.50 inc. post. Complete with instructions. Our price **£10.99 + 31p p. & p.** Send **£11.30**.

JOHN DUDLEY & CO. LTD., Dept. PE2
301 Cricklewood Lane, Child's Hill, London, N.W.2.
Tel. 01-438 3917. Callers welcome.

HARDWARE FOR CONSTRUCTORS. Screws, nuts, brackets, spacers, etc. S.A.E. list. R. A. MARSH, 29 Shelbourne Road, Stratford-on-Avon, Warwick.

BRON ALGULATOR. Adds, subtracts, divides, calculates figures, money, sums easily and quickly. Pocket size, with full instructions, 55p. CAMERA CENTRE, Fleetwood.

FASCIA PANELS, hi-fi equipment, etc., etched aluminium to individual specifications, S.A.E. details. R. MARSH, 29 Shelbourne Road, Stratford on Avon, Warwick.

MISCELLANEOUS (continued)

GLASS FIBRE OPTIC

FLEXIBLE LIGHT PIPE, now available in any length. 150 \pm glass fibres with three times lower loss than plastic fibre. P.V.C. sheath 0.060 in. dia.

Used like wire but to convey light to remote or inaccessible positions for inspection, panel indicators, photo-electric and other applications. Prices per ft. (post free): 1-9, 25p; 10-49, 20p; 50-249, 15p. Enquiries S.A.E.

FIBRE OPTIC SUPPLIERS
P.O. BOX 702, LONDON W10 6SL

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

PERFECT SPEAKERS EX TV
P.M. 3 OHM (Minimum order 2)
8" x 2 1/2" 15p each, add 10p per speaker P. & Pkg.
100 SPEAKERS for £15 delivered
200 SPEAKERS for £25 delivered

UHF TUNERS EX TV (Complete with Valves)
£2.50 each + 50p p. & pkg.
or 10 for £23 post free

TRADE DISPOSALS (Dept. PE)
Thornbury Roundabout, Leeds Road, Bradford
Telephone 665670

MORSE MADE EASY!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Complete Course £4.50 (Overseas £1.00 extra) details only, 4p stamp. 01-660 2896.

GHBC (Box 19), 45 GREEN LANE, PURLEY, SURREY

YUKAN SELF-SPRAY 50 PROFESSIONAL THE YUKAN AEROSOL WAY -
Get these air drying GREY HAMMER OR BLACK WRINKLE NOW! (CRACKLE) Finishes

Yukan Aerosol sprays contain 45% fine quality, durable wax emulsion. No stove baking required. Hammer available in grey and blue. 90p can; 100ml. Epplet Black Wrinkle (Crackle) producing a 3D textured finish, 90p can; 100ml. Choice of 13 self-sealing paint colours. Also durable, heat and water resistant Black Matt finish (250ml self-sealing cream spray) 75p can; 100ml.

SPECIAL OFFER: One can plus optional transferable snap-on trigger handle, value 25p for 90p can; 100ml. Choice of 13 self-sealing paint colours and primer (motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:
DEPT: PE2 YUKAN, 307A EDGWARE ROAD, LONDON W2 1BN

We supply many Government Departments, Municipal Authorities, Institutes and leading Industrial Organisations - We can supply you too!

Open all day Saturday. Closed Thursday afternoons. New British. Even Better.

Send now for our:
**Illustrated Component/
Equipment Catalogue
Slide and Rotary Lamp
Dimmer Catalogue**
10p each—post Free
YOUNG ELECTRONICS
54 Lawford Road, London NW5 2LN
01-267 0201

LADDERS

LADDERS. 20ft, £7. Order C.O.D. Phone 02-993 5222. HOME SALES (Dept. PEE), Baldwin Road, Stourport, Worcs. Callers welcome.

WANTED

PRACTICAL ELECTRONICS wanted May June 1969. State Price for pair. Box No. 39.

CASH PAID for New Valves. Payment by return. **WILLOW VALE ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

HIGHEST POSSIBLE CASH prices for Akai, B. & O., Brenell, Ferragraph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

TOP PRICES PAID

for new valves and components
Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

SERVICE SHEETS

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex. Telephone, Bexhill 7097.

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. **TELRAY**, 11 Maudland Bank, Preston.

SERVICE SHEETS (continued)

RADIO, TELEVISION AND TAPE RECORDERS. 50 mixed odd sheets 50p. Also large stock of obsolete and current valves. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Road, London, W.6 (01-743 8441). S.A.E. enquiries.

EDUCATIONAL

MEN! You can earn £50 p.w. Learn computer operating. Send for FREE brochure—**LONDON COMPUTER OPERATORS TRAINING CENTRE**, E47 Oxford House, 9-15 Oxford Street, London, W.1.

GET INTO Electronics—opportunities for trained men. Learn at home. Postal courses in RTEB, City & Guilds, Radio, TV, Telecoms., etc. FREE informative guide: **CHAMBERS COLLEGE** (Dept. R.103), Aldermaston Court, Reading, RG7 4PF.

AMSE (Elec), City & Guilds, RTEB Cert. Radio Amateurs Cert. Study at home courses in all branches of Electrical Engineering, etc. Details and illustrated book—FREE—**BET** (Dept. H.5), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Welding, etc. FREE book from: **BET** (Dept. H.4), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

SITUATIONS VACANT



Established 1891

**TECHNICAL TRAINING
IN RADIO, TELEVISION AND
ELECTRONIC ENGINEERING**

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc. Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- * RADIO AMATEURS' EXAMINATION.
- * GENERAL RADIOCOMMUNICATIONS CERTIFICATE.
- * C. & G. RADIO SERVICING THEORY.

Now available, Colour T.V. Servicing.

Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ABCC

ACCREDITED BY THE CACC

**INTERNATIONAL
CORRESPONDENCE
SCHOOLS**

**A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!**

International Correspondence Schools
(Dept. FA25), Intertext House, Stewarts Road,
London SW8 4UJ

NAME
Block Capitals Please

ADDRESS

.....

.....

AGE OCCUPATION 3/72



TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: London Electronics College, Dept. B/3, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.

RECEIVERS AND COMPONENTS

nippiboard

MULTI-PURPOSE PRINTED WIRING BOARD FOR

PE TRANSISTOR CIRCUITS

	SRBP	FIBREGLASS
Photo-print Process Control Unit	4AS	4BS
Rhythmtron (Nov)	2A	2B
Life Note Generator (Ingenuity) (Nov)	2A	2B
Chart Recorder (Oct)	2A	2B
Engine Temperature Controller (Oct)	1A	1B
Rain or Water Level Alarm (Oct)	1A	1B
Timer with Digital Readout (Sept)	2A	2B

TYPE 1A 15p; 1B 18p; 2A 25p; 2B 34p; 3A 39p; 3B 43p; 4AS 44p; 4BS 52p. ALSO SUITABLE FOR MANY OTHER PROJECTS.

FREE NIPPIBOARD TYPE 1A when you buy **SL403D** SHORT CIRCUIT PROOF I.C. AMP. as specified for **EE RECORD PLAYER**

£1-99 plus 9p post & packing

NIP ELECTRONICS DEPT NBE
P.O. BOX 11, ST. ALBANS, HERTS, ENGLAND.

COMPUTER PANELS. 5-BC108 diodes, 15p, post 5p; 4-50p, post 10p. **AMERICAN PANELS** total at least 50 transistors, integrated components, 4-55p, post 10p. **ASSORTED PANELS** 6-£1, post 15p, no midjet boards, plenty of components at least 60 transistors. List of boards sent on receipt of S.A.E. **LA2 POT CORES.** 20 in all box with 20 1% capacitors, £1-50, post 27p. Singles 15p c.p. New and boxed 30p c.p. **COMPUTER RELAYS** DDDT, 700 ohm coil, weigh 1oz, carry 2 amp, 60p c.p. Same weigh 14oz silver contacts, 35p c.p. **ORP12** on panel ex equip. 35p c.p. **WIRE ENDED NEONS** bank of 20, 50p, post 7p. **COPPER CLAD PAXOLIN** single sided, 8 x 5, 10p, post 5p each. 101 x 8, 20p, 13 x 11, 30p, post 8p each. **RESETTABLE COUNTER** 5 Figure 15/22V. Will work on 12V. £1-76, post 10p. **POLYSTYRENE CAPACITORS** 125V, 160, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 15p dozen, post 10p. **ASSORTED TWIN GANG VARIABLE CAPACITORS, BRAND NEW.** 5 FOR £1-26, C.P. **ASSORTED COMPONENTS.** 7lb, £1-25 c.p. **ASSORTED COMPUTER PANELS.** 2lb, £1-25 c.p. **J.W.B. RADIO**
75 HAYFIELD ROAD, SALFORD 6, LANCAS.
MAIL ORDER ONLY

ASSORTED BRAND NEW WIRE-WOUND RESISTORS, 1-10 watts (5 x 10 different values), 50 for 60p, P. & P. 10p.

PLESSEY 50K + 50K GANGED LOG POTENTIOMETERS, 25p, P. & P. 5p.

PLESSEY ELECTROLYTIC CAPACITORS 200µF, 350V 35p, P. & P. 8p; 200µF, 500V (limited quantity) 50p, P. & P. 10p.

PLESSEY LOUDSPEAKERS, 3in, 35 ohms, 50p, P. & P. 10p.

ASSORTED CAPACITORS (no rubbish), includes Silver Mica, Ceramic and Polystyrene types, 100 for 50p, P. & P. 10p.

MAIL ORDER ONLY
XEROZA RADIO
1 EAST STREET
BISHOP'S TAWTON
DEVON

DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62p per doz.; £3-75 per 100; £27-50 per 1,000; £250 per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

P.E. GEMINI STEREO AMPLIFIER

(Dual purpose, 30W per channel)

All the components to build this high quality amplifier, as featured in "Practical Electronics," Nov. 1970—Feb. 1971, are now available from one source.

ALL PARTS CAN BE PURCHASED SEPARATELY.

Please send foolscap size S.A.E. for free complete lists. Reprint of articles available in booklet form, complete with free price list, 55p post free.

Mail Order Only
ELECTROSPARES
21 BROOKSIDE BAR
CHESTERFIELD, DERBYSHIRE
QUALITY • VALUE • SERVICE

I.C. STEREO AMPLIFIER (Plessey Design) 3W per channel into 8 ohms. Includes pre-amplifier, tone controls, power supply, £19-25. **SL403D I.C. Amplifier only, £2-20 each.**

HEAT SINKS Plain, finned.
5DN Undrilled 4in x 4in x 4in, 28p each.
5DN Drilled 2 x TO3 (OC28, etc.), 33p each.
10DN Undrilled 4in x 4in x 1in, 33p each.
10DN Drilled 2 x TO3 (OC28, OC35, etc.), 38p each. Mica washers and Insulators TO3, SO55, 5p per set.

VEROBOARD State 0-1in or 0-15in matrix. 2in x 5in, 22p. 2in x 3in, 20p. 3in x 5in, 24p. 3in x 3in, 22p. 17in x 2in x 0-15in matrix, 55p. 17in x 3in x 0-15in matrix, 70p. Veropins 0-1in or 0-15in, 50 for 20p.

ALUMINIUM BOXES. Ideal for housing "Veroboard" Projects. 2in x 5in x 1in, 35p. 2in x 4in x 1in, 35p. 4in x 5in x 1in, 45p. 4in x 4in x 1in, 35p. Complete with lid and fixing screws. P. & P. 10p for all orders under £2. S.A.E. for list.

SEPTON ELECTRONICS
P.O. BOX 15, ALDERSHOT, HANTS

Trampus electronics

Brand New, No Surplus, Fully Guaranteed.

BC107, 8p. BC108, 8p. BC109, 8p.
2N8055, 53p. BC177, 8.9p. 2N2926ov, 9p.
LIGHT EMITTING DIODES, VISIBLE
RED 1.7V 20mA, 67p. INPRA RED 1.3V 100mA, £1-49.
I.C. Photo Detector and amp. lens case, 48p.
Rectifiers: 1A 50V, 6p. BRIDGE W005, 29p.
Zeners: 400mW, 3.4, 5.6, 9, 12, 15, 18, 24, 30V, 12p.

INTEGRATED CIRCUITS
709, 34p. 741, 35p. 710, 45p.
TA4263, 58p. TA4293, 75p. PA1100 110RX, £1-67. TA4290, 55p. TA4310 £1-19. PA237 2W amp, £1-49. Plastic Power 6W, 500mA Darlington amp, 58p.
74N TTL series data booklet, 12p.
7400, 1, 2, 3, 4, 10, 20, 30, 40, 50, 51, 53, 54, 90, 16p.
7413, 70, 72, 28p. 74, 74, 76, 86, 29p. 75, 121, 57p. 7490, 92, 93, 73p. 41, 141, 42, 93, 95p. 81, 82, £1-19.
NUMERICAL INDICATOR, 7 segment 3013F DIL0-9DP 5V 8mA bar, £1-89. 7447N, £1-23.
74N and 3013F DIL SOCKETS 16 or 14 pin, 12p.
Capacitors 15V 0-01 to 100µf, 6p. 1,000µf, 25p.
FREE CATA-LIST, S.A.E., DATA SHEETS, 6p.
C.W.O. P. & P. U.K. 6p. Discount 10+ 10%.

P.O. BOX 29, BRACKNELL, BERKS.

AARVAK ELECTRONICS, 3 channel sound-light converters; 1,200 watts, £17; 3,000 watts £25; Medium Power Strobes £16. 74 Bedford Avenue, Barnet, Herts. 01-449 1268.

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 OC28) 50p, P. & P. 6p.

9 OA6, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 G.T. 72, 3 GET 872H, 1 GET 875. All long leads on panels 13in x 4in. 4 for £1, P. & P. 25p.

709C OPERATIONAL AMPLIFIER TOS
8 lead I.C. 1 off 50p. 50 off 35p. 100 off 20p.

250 MIXED RESISTORS 62p
1 & 4 watt.

150 MIXED HI STABS 62p
1, 1 & 1 watt 5% & better.

QUARTZ HALOGEN BULBS
With long leads. 12V 55W for ear spot lights, projectors, etc. 60p each. P. & P. 5p.

GPO EXTENSION TELEPHONES
with dial but without bell. 85p each. P. & P. 30p. £1-75 for 2. P. & P. 60p.

BARGAIN RELAY OFFER
Single pole change over silver contacts 25V to 50V. 2.5kΩ coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

WITWORTH TRANSFORMERS

TV Line out-put transformers

Manufacturers of the largest range in the country. All makes supplied. Free catalogue.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact London 01-948 3702

Tidman Mail Order Ltd., Dept. PE,
236 Sandycroft Road,
Richmond, Surrey.

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers also stocked.
Callers welcome.

NEW COMPONENTS — LOW PRICES

Archid 9315 (equivalent SN7441), 55p.
SN5476, 35p. SN7475, 35p. SN7495, 55p.
SN7403, 18p. SN7410, 18p. SN7400, 18p.
SN7490, 66p. SN7492, 66p.

Numerical Indicator Tubes side view with decimal points, £1-30. Metal Oxide Resistors all values from 3p each. Eric Aluminium Electrolytic Capacitors from 11p each. Metallised polyester capacitors resin moulded from 9p each. Foolscap S.A.E. plus 3pin stamps for lists. P&P 7p

AQUA-GEM ELECTRONICS, 8 Pound Lane Bowers Gifford, Basildon, Essex. Mail Order Only

ENTS

RESISTANCE METERS

Controls		W Carbon	Dials	
Line	LOG	Line	LOG	
500kΩ	5kΩ	5kΩ	1kΩ	5kΩ
1kΩ	10kΩ	25kΩ	2.5kΩ	10kΩ
5kΩ	25kΩ	50kΩ	5kΩ	25kΩ
10kΩ	50kΩ	100kΩ	10kΩ	25kΩ
25kΩ	100kΩ	250kΩ	50kΩ	500kΩ
500kΩ	500kΩ	1MΩ	100kΩ	1MΩ
1MΩ	2MΩ		2MΩ	

Skeleton 10mm preset carbon horizontal mounting following values only: 100Ω, 220Ω, 470Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 10kΩ, 22kΩ, 47kΩ, 100kΩ, 220kΩ, 470kΩ, 680kΩ, 1MΩ, 6p each.
Add 10p Packing and Postage on all orders.
BLORE-BARTON LIMITED
REEDHAM HOUSE, BURNHAM, BUCKS.

PRINTED CIRCUIT BOARDS FOR P.E. PROJECTS

All boards drilled and roller tinned complete with layout drawing.
EXAMPLES
Waa-Waa pedal Vol. 4 No. 7 14p ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 43p ea.
NEW
Scorpio Ignition Nov./Dec. '71 Fibreglass 70p.
Logical R/C Coder Dec. '71 Fibreglass 44p.
S.A.E. for List.
P.H. ELECTRONICS LTD.—Industrial Estate, Sandwich, Kent. Tel. 2517

TRANSISTORS from 1p. Silicon *npn* similar N2920, approx. 10 on panel with resistors, capacitors, diodes, etc., 17p. Panels 70p. 25 for £2.50. Mixed small components, some damaged, 65p per lb. Satisfaction or money back. Logic IC's, 10 assorted on panels, 10p. Post paid, list and data included. We now have ex-equipment hour meters, transmitters, switches, contactors, cut-outs, speakers, computer electrolytics, fans, blowers, etc. at clearance prices. Free sample transistors and enlarged list if you send 9p. In S.A.E. J. & J. PAWSON (ELECTRONICS), 114 South St. Annadale, W. Lothian.

SOUND SUPPLIES (LOUGHTON) CO. LTD.

1 Eagle International and International Rectifier Products.
TOA P.A. Equipment and Mikes.
Capacitors, Resistors, Plugs, Sockets, Cabinets, Audio Leads, Semiconductors, Valves, Vero Board, etc., for the constructor.
Electronics Dept. Tel. 01-508 2715
12 Smart Lane, Loughton, Essex
Hours: 9.30 a.m.-1 p.m. 2-5 p.m. Mon, Tues., Wed. and Fri. 9.30 a.m.-1 p.m. 2-5.30 p.m. Sat.
Closed All Day Thurs.

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25V 1, 2, 5, 10 mfd.—3p, 25, 50—4p, 100—5p. Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02—2p; 0-04, 0-05—2p; 0-068, 0-1—3p. Mullard miniature carbon film resistors third watt E12 series 1Ω-10MΩ, 8 for 5p, insured postage 8p. The G.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

MINI MAINS PACK KIT.

Safe double-wound mini transformer, silicon rectifiers, 1,000μF smoothing, instructions. Buildable to size of PP6 etc. 9V, 120mA, 90p, U.K. post 5p. Mail order only. **AMATRONIX LTD.**, 396 Selston Road, South Croxson, Surrey, CR2 0DE.

P.E. RHYTHM GENERATOR PARTS.

P.C. board, built switch. Transistors, diodes, resistors, etc. Instructions, S. IYGO, 352 Dallow Road, Luton, Beds.

OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS

Prim. 200/240V a.c. TX6, 425-0-425V, 500 Ma, 6-3V 6A CT, 6-3V 6A CT, 0-5-6-3V 3a, £12-75; TX1, 425-0-425V, 250Ma, 6-3V 4A CT, 6-3V 4A CT, 0-5-6-3V 3a, £7-50; TX2, 250-0-250V, 150Ma, 2 x 4A CT, 0-5-6-3V 3a, £4-05; TX5, 300-0-300V, 120Ma, 6-3V 2A CT, 6-3V 2A, 6-3V 1A, £4-05; TX8, 250-0-250V, 60ma, 6-3V 1.5A, £2-10; MT1, 200V, 30ma, 6-3V 1A, £1-20; MT2, 230V, 45ma, 6-3V 1.5A, £1-50; MT2A, 250V, 60ma, 6-3V 2A, £1-95; MT3 Prim. 110/240V, Sec. 250V, 100ma, 6-3V 2A, £2-25.

AUTO TRANSFORMERS

0-110-200-250-240V a.c. up or down fully shrouded fitted insulated terminal blocks. 30W £1-35; 50W £1-80; 75W £2-10; 100W £2-55; 150W £3-15; 200W £3-90; 300W £5-25; 400W £6-30; 500W £7-50; 600W £8-25; 750W £9-75; 1,000W £12-75; 1,500W £18; 2,000W £24-75; 3,000W £33; 4,000W £45.

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c. 6-3V 1.5A, 85p; 250V 2A, £1-18; 6A CT, £1-80; 12V 1.5A, £1-18; 3A CT, £1-80; 6A CT, £2-70; 18V 1.5A CT, £1-80; 24V 1.5A CT, £1-80; 3A CT, £2-70; 5A, £3-75; 8A, £6; 12A, £9; 40V 3A CT, £3-45.

MIDGET RECTIFIER TRANSFORMERS

For FW rect., size 1 1/2 x 2 1/4 in. Prim. 200/240V a.c. output, PPT1, 9-0-9V, 0.3A, PPT2, 12-0-12V, 0.25A, PPT3, 20-0-20V, 0.13A, £120-250V, ditto, size 2 x 2 1/4 x 1 1/4 in. MTV1, 9-0-9V, 1A, 88p; MTV2, 12-0-12V, 1A, MTV3, 20-0-20V, 0.75A, £1-20 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS

P.P. sec. tapped 3-7.5-15 ohms, A-A 6-6kΩ, 30W (KT66, etc.), £4-05; 50W, 3kΩ, A-A, £6-75; 100W, 3kΩ, A-A, £11-40; £11-40 and to 400W.

LOUDSPEAKERS FOR POWER AMPLIFIERS

New, famous makes, 15W with tweeter, £4-75; 25W, £5-80; 35W, £7-20; 50W, £10-00; 100W, £21-50; E.M.I. 134 x 8in 10W, 3 or 8 or 15 ohms, £2-25. Ditto to twin tweeters and Nover, £4-00; Horn Tweeters 2-16kHz 10W 8 or 16 ohms, £1-50. 111-FI, 8 x 5in 8Ω, £1-85; 10-5in 3 or 8 or 15 Ω, £2-10.

G.E.C. MANUAL OPERATED AMPLIFIERS

Governing valve, supplied with 30 to 400 watts, with price list of transformers and chokes specified, 25p.

LOUDSPEAKERS

2in 35Ω, 2 1/2in 8 or 80Ω, 2 1/2in 25Ω, 3in 30Ω, 60p each; 3 1/2in 3Ω, 4in 15Ω, 5 x 3in 3 or 15 or 25Ω, 80p each; 6 x 4in 8Ω, 7 x 4in 3Ω, 6in 3Ω, £1-08; 8 x 5in 3 or 15 or 25Ω, £1-35; 8in 3Ω, £1-85.

SPEAKER AUTO MATCHING TRANSFORMER 12W

3 to 8 or 15 ohms, up or down, 75p. P. & P. 15p.

MINIATURE MODEL RELAYS

Instant erasure, tape spools and cassettes, demagnetizes tape heads, etc. 200/250V, £2-40 plus 24p 1p & P. **AIRCRAFT BAND CONVERTERS**

PRINTED CIRCUIT ETCHING KITS

Comprehensive outfit, solutions and equipment to make your own P.C. boards, instructions, £1-36, extra p.c. Boards 8 x 6in, 15p.

TAPE RECORDER MOTORS

A variety of uses. Blowers, Fans, etc., new 110V a.c. 25p; 230/250V a.c. 50p each.

CONDENSERS

Paper: 0.01/2kV 121p; 0.22/800V a.c. 25p; 0.47/700V 15p; 0.47/1kV 25p; 4.7/500V 25p. Electrolytics: 100 + 200/275V 40p; 100 + 200/350V 50p; 100 + 60/450V 25p; 350 + 50/25V 15p; 100 + 400/275V 20p; 24/450V 10p; 2500/64V 50p.

BATTERY ELIMINATORS

(get rid of your batteries) for your transistor radio, amplifier, cassette operates from the mains 200/240V a.c., fully insulated, compact. Outputs: 6V £1-50, 9V £1-50; 7 1/2V £1-50.
Carriage extra on all orders, etc., etc.

S.A.E. INQUIRIES-LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

BEAT THIS FOR VALUE!

BRAND NEW, MARKET AND GUARANTEED

TRANSISTORS
BC107, 8p; BC109, 8p; AC126, 16p; AC127, 20p; BCY43, 10p; BFX87, 17p; BCY30, 20p; BFY51, 16p; 2N1711, 22p; 2N1305, 21p; 2N2270, 58p.
I.C.s: 709, 35p; 741, 69p.

CAPACITORS

Min. Electrolytics C426 10mF x 16V d.c., 5p; 80mF x 16V d.c., 5p; 25mF x 10V d.c., 5p.
Polyester Capacitors C280: 0.01, 2p; 0.047, 3p; 0.1, 3p.

1/2 or 1/4 watt High Stab. Carbon Film Resistors (Low Noise). All values 1p each.

10% discount on orders over £10.
Cash with Order. Post and Packing extra. Postal Business only.

R. I. RICHARDSON
30 Hayes Street, Bromley BR2 7LD

U.H.F. TV AERIALS
SUITABLE FOR COLOUR & MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.
LOFT MOUNTING ARRAYS
7 element £2-25, 11 element £2-75, 14 element £3-25, 18 element £3-75.

WALL MOUNTING c/w WALL ARM AND BRACKET. 7 element £3-25, 11 element £3-75, 14 element £4-25, 18 element £4-75.
CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT. 7 element £4, 11 element £4-50, 14 element £4-75, 18 element £5-25.

MAST MOUNTING arrays only 7 element £2-25, 11 element £2-75, 14 element £3-25, 18 element £3-75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 9p yd.
KING TELEBOOSTERS from £3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7-50. State clearly channel number required on all orders. P. & P. on all aerials 50p. accs. 15p. C.W.O. min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS

BBC (band I) Wall S/D £2. **LOFT** inverted 'T' £1-25. **EXTERNAL 'H'** array only £3-50. **ITV (band 3)** 5 element loft array £2-50, 7 element £3. **COMBINED BBC-ITV** loft 1+5 £2-75, 1+7 £3-50. **WALL AND CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from £3-75.

COMBINED U.H.F.-V.H.F. aerials 1+5+9 £4, 1+5+14 £4-50, 1+7+14 £5. **F.M. RADIO** loft S/D £1, 3 element £3-25, 4 element £3-50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p, accs. 30p. C.W.O. min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED OPEN ALL DAY SATURDAY
K.V.A. ELECTRONICS
40-41 Monarch Parade, London Rd. Mitcham, Surrey
Telephone 01-648 4884

NEW 15 Watt Hi-Fi AMPLIFIERS
£3-75 plus 25p postage

7 TRANSISTORS - GUARANTEED PRINTED CIRCUIT - TESTED DESIGN BUILT - INSTRUCTIONS
A great new 15 watt Hi-Fi amplifier is now available at the low cost of £3-75. Just look at the specification—Power 15 Watts R.M.S. Frequency response 19 cs-19000 cs., 1dB at all powers. Signal to noise ratio better than -70 dB Harmonic distortion 0.1%. Input sensitivity 750 mv into 2k. These factors make the H. Electronics Hi-Fi amplifier the best at its price—order now

H ELECTRONICS
105, Grange Road, London, S.E.25

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6V, 9V, 12V, 18V (single output) £2 each. P. & P. 15p. 9V + 9V; 6V + 6V; or 4 1/2V + 4 1/2V (two separate outputs) £2.50 each. P. & P. 15p. Please see output required. All the above unit completely isolated from mains by wound transformer ensuring 100%
R.C.S. PRODUCTS (R)
(Dept. P.E.), 31 Oliver R.

Please merge
PRACT

MAIL ORDER
DIVISION

THE POWER
HOUSE

distronic LTD

28 BURNT MILL ELIZABETH WAY
HARLOW ESSEX HARLOW 32947

Why wait weeks?

—ALL OUR ORDERS
DISPATCHED BY
RETURN OF POST!

Transistors, Diodes
and Integrated Circuits

A) DIODES & RECTIFIERS	40411 £1.95	BC107 9p	BF159 35p
IN914 3p	AC138 15p	BC108 9p	BF177 25p
IN4148 5p	AC141 20p	BC109 9p	BF178 30p
IN4001 7p	AC141H 25p	BC113 14p	BF179C 35p
IN4002 8p	AC142 15p	BC114 14p	BFX86 25p
IN4003 9p	AC187K	BC115 14p	BFX87 27p
IN4004 10p	AC188K	BC116A 14p	BFX88 25p
IN4005 12p	Matched	BC117 30p	BFY34 30p
IN4006 14p	Pair 50p	BC125 19p	BFY50 19p
IN4007 20p	AC191 15p	BC126 19p	BFY51 19p
	AC192 15p	BC132 20p	BFY52 19p
	AC193 20p	BC134 20p	ME0404-1 10p
	AC193K	BC137 30p	ME0404-2 10p
	AC194K	BC142 35p	ME1001 10p
	Matched	BC143 40p	ME1002 11p
	Pair 60p	BC144 35p	ME2001 10p
	AC194 20p	BC145 30p	ME3001 20p
WOOS 50V	AD142 50p	BC147 9p	ME3002 25p
IA Bridge	AD143 50p	BC148 9p	ME4001 10p
40p	AD262 35p	BC149 9p	ME4002 11p
WO1 100V	AD263 40p		ME6001 15p
IA Bridge	AF106 25p		ME6002 18p
45p	AF109 35p		ME8001 20p
WO4 400V	AF129 31p		ME8003 30p
IA Bridge	AF166 20p		ME9001 15p
48p	AF170 18p		ME9002 15p
	AF200 25p		MEL11 40p
	AF201 30p		MEL12 50p
	AF239 40p	BC153 30p	MEU21 40p
	AF239S 45p	BC154 35p	MEU22 50p
	AL103 60p	BC182L 9p	OC25 40p
	AU103 £1	BC183L 9p	OC28 60p
		BC184L 9p	OC35 48p

Compare our prices

WOOS 50V
IA Bridge
40p

WO1 100V
IA Bridge
45p

WO4 400V
IA Bridge
48p

Send 10p for Price List or free with order

B) TRANSISTORS	2N696 13p	2N930 25p	2N1613 22p	2N1711 23p	2N2369 15p	2N2484 30p	2N2904 30p	2N2904A 32p	2N2905 36p	2N2905A 38p	2N3053 17p	2N3054 45p	2N3055 59p	2N3442 £1.50	2N3638 25p	2N3866 £1.50	2N4347 £1.50	2N4356 35p
	AF239 40p	AF239S 45p	AL103 60p	AU103 £1	BC153 30p	BC154 35p	BC182L 9p	BC183L 9p	BC184L 9p	BC212L 12p	BC213L 12p	BC214L 12p	BCY70 18p	BCY71 20p	BCY72 17p	BF152 25p	BF153 25p	BF158 25p

Component Discounts
10% on orders over £5

C) INTEGRATED CIRCUITS
709C (TO-5) 45p
709C (DIP) 68p
741C (TO-5) 68p
741C (DIP) 68p
TBA800 SW 68p
Audio £1.50

POSTAGE AND PACKING

PLEASE ADD 10p TO YOUR ORDER

2N3055 115V 15A	59p	AD142 80V 10A TO-3	50p
2N3053 1A TO-5	17p	AU103 155V, 10A TO-3	£1
BC107 also BC108 and BC109	9p	BC147/8/9 High gain LOCKFIT	9p
AF239 UHF: SDB Noise factor at 800MHz	40p	40411 30A, 150V	£1.95
WO1 1A, 100V Bridge Rectifier	45p	BFY50, 51, 52	19p
AD262 JPNP Matched BD162 JNPN Pair 10W, Audio output pair	80p	NEW! TBA800 5W Audio IC	£1.50

ERSIN

Multicore

5 CORE SOLDER

for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75 ft. 18 gauge on plastic reel. Recommended retail price 75p
Size 12



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170 ft. 22 gauge on plastic reel. Recommended retail price 75p
Size 10



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG
19A 60/40 18 18p *
Savbit 18 18p *
(Size 5 illustrated)
15 60/40 22 22p *
* Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIG WIRE STRIPPER AND CUTTER, easily



adjustable for all standard diameters. Plastic covered handles, can also be used as wire cutter. Recommended retail price 50p

From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

C.T. ELECTRONICS

FOR REAL SERVICE WITH THE LARGEST SELECTION OF ELECTRONIC COMPONENTS AND TEST EQUIPMENT

You must visit

C.T. ELECTRONICS

267 ACTON LANE, CHISWICK, LONDON, W.4

9.30 a.m. 6 p.m. MONDAY SATURDAY

BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power 35 watts
Bass Resonance 35 c.p.s.
Flux Density 15,000 gauss
Voice coil impedance 8 or 15 ohms models
Useful response 20-14,000 c.p.s.
Nett weight 15 lbs.

£19

POST FREE

GUITAR MODEL "GROUP 50" 50 watt £19
Latest catalogue 5p with enclosure plans



Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn.

If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship
A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic
A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.
C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero
A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production
Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Stockkeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication
Sales Management

Constructional
A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General
C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education
Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T., and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT— SO COULD YOU

"My income has almost trebled... my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B4, Aldermaston Court, Reading RG7 4PF.

Accredited by the Council for the Accreditation of Correspondence Colleges.



(Write if you prefer not to cut this page)

POST THIS COUPON TODAY

To: B.I.E.T., Dept B4, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name..... Age.....
BLOCK CAPITALS PLEASE
Address.....

..... Occupation.....

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/Sia) Ltd.; South Africa - Central News Agency Ltd.; Rhodesia and Zambia - Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.65 (£2.13.0.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

PRICE
£1.85



*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

*
Write for
price list
and
catalogue

ADCOLA


ADCOLA PRODUCTS LTD.,
(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

1N4148	Signal Diode	18 for 50p
(=1N914)		
1N5060	1 Amp Rectifier 400V	
(=A14D)	avalanche protected	7 for 50p
2N2923	NPN Silicon Transistor	
	hfe 90 - 180 (25v)	7 for 50p
2N2926	NPN Silicon Transistor	
(Red)	hfe 55 - 110	8 for 50p
2N3391A	Si NPN Hi Gain (250 - 500)	
	low noise transistor	3 for 50p
2N3402	Medium power (driver)	
	900mw 25v Hfe 75 - 225	6 for 50p
C6U	1.6 amp general purpose	
	25v SCR in T05 case	3 for 50p

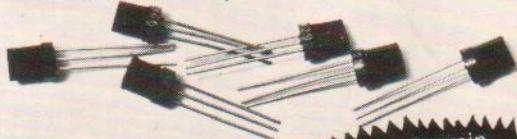Post and packing 10p for 1 or 2 packs; 3 packs or more post free.
Order any quantity, till sold (but we regret packs cannot be subdivided).




P.O. or Cheque payable
Jermyn Industries,
Vestry Estate,
Sevenoaks, Kent.

Star Bargain
Sprague (Pirgo) Triacs
PT406S (6 amp 400v)
48p each

PHOTOELECTRIC KIT

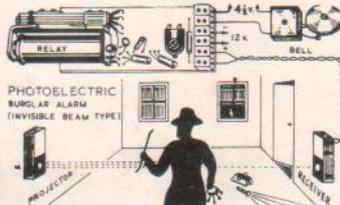CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
£2.60

Postage and Pack. 15p (U.K.)
Commonwealth:
SURFACE MAIL 25p
AIR MAIL £1.40
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photoelec Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1.25. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.85. Postage and Pack. 15p (U.K.). Commonwealth: Surface Mail 20p; Air Mail £1.15.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.
CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".
Price £1.25. Postage and Pack. 10p (U.K.). Commonwealth 20p; Airmail 50p.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photoelec receiver for use with Junior Photoelectric Kit.
Price 75p. Post and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 50p.

YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects