

PRACTICAL

ELECTRONICS

MAY 1972

20p

FREE INSIDE WALLCHART

SEMICONDUCTOR
LEAD-OUT DATA

ULTRA-SONIC

- INTRUDER ALARM
- REMOTE CONTROLLER
- SIGNALLING SYSTEM





CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. **Price £1.70**


CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. **Price £1.70**

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. **Price £1.83.**



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety: fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. **Price £1.80**

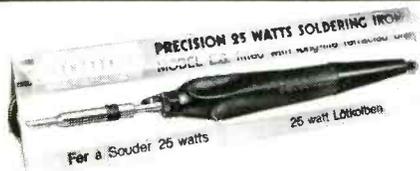CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. **Price £1.95**



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. **Price £1.80.**

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. **Price £1.83**



**SK.1
SOLDERING
KIT**

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price £2.75



**SK.2
SOLDERING KIT**

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"


Price £2.40.



MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. **Price £1.95.**

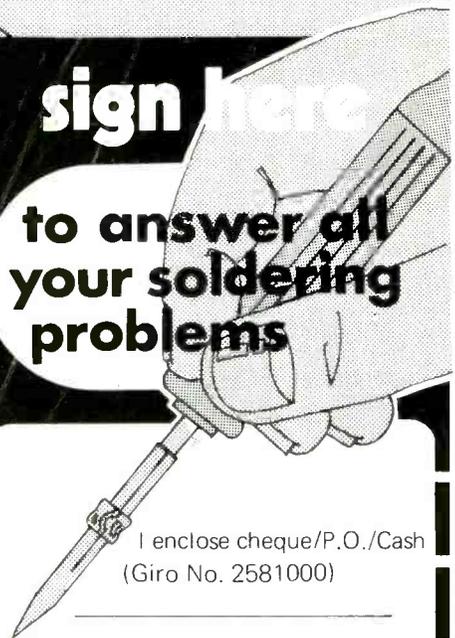sign here
to answer all your soldering problems



I enclose cheque/P.O./Cash (Giro No. 2581000)

Name _____
Address _____

PE5

Please send the Antex colour catalogue.

Please send the following:



from electrical, radio or car accessory shops or from **Antex Ltd., Freeport** (no stamp required) **Plymouth** **PL1 1BR** Telephone 0752 67377/8

Now! From EMI precision speakers and enclosures in matched money-saving kits

EMI speakers are internationally recognised—used in the highest quality sound reproduction equipment. Because of this world-wide demand, EMI matched speaker kits are available to you at a really keen price.

And now, EMI introduce the commonsense cost-saving approach to high quality speaker enclosures. Available in complete easily assembled kit form—all you need is a screwdriver—they form the ideal

combination of superb sound reproduction and good looks you'll be proud to have in your home.

There are eight kits—from compact book-shelf units to large floor standing enclosures—all finished in selected wood veneer, with matched loudspeaker kits handling from 5-35 Watts.

Realise the full fidelity of your audio system at a fraction of the cost of comparable speaker assemblies. Contact your hi-fi dealer or send to EMI for full details



A member of the
EMI Group of Companies.
International leaders in Electronics,
Records and Entertainment.



Perfection in Sound
EMI Sound Products Ltd., Hayes, Middlesex.
Telephone: 01-573 3888, Ext. 667


SYSTEM 12 STEREO

BUDGET PRICED AT ONLY **£13.95**

P&P 35p

- ★ **COMPACT —**
- EASY TO ASSEMBLE**
- ★ **LATEST SOLID-STATE ELECTRONICS**
- ★ **MONOLITHIC POWER AMPLIFIERS**
- ★ **BRITISH BUILT ★ FULLY GUARANTEED**
- ★ **COMPREHENSIVE INSTRUCTIONS**
- ★ **DIRECT FROM MANUFACTURERS**

The Bi-kits "SYSTEM 12 STEREO" is a kit form modular stereo amplifier system of modern design, providing an output of 12 watts peak (6 watts RMS minimum) from two remarkable amplifiers which have a frequency response from 20 Hz to 50 kHz. Assembled pre-amplifier and power supply module together with mains transformer plus two 8in round twin-cone speakers matched to the system are included in the kit which also contains all the necessary connecting wire and such items as the silver anodised front panel and 4 matching control knobs. Inputs for tuner or tape recorder, ceramic or magnetic cartridges are provided. Stereo balance better than 2dB, plus separate bass and treble controls are typical of the "SYSTEM 12 STEREO" specification.

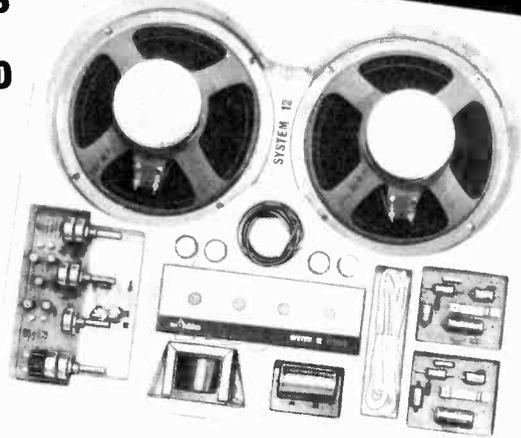


Plinths and covers, speaker cabinets and decks are easily available and your finished stereo system (built by you) will look like this.

ORDER NOW!

enclosing M.O./P.O./Cheque: Value £.....to

**BI-KITS Dept. PE, 63a High Street
Ware, Herts.**

A Member of the BI-PAK Group

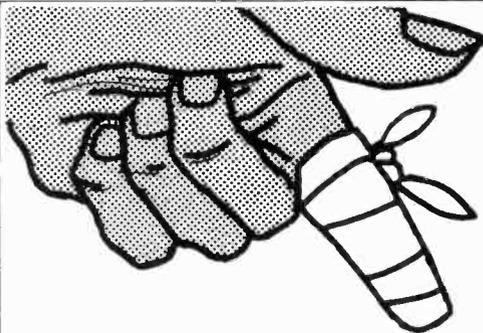

Burns and scalds can rob your fingers of the dexterity essential to your hobby. So keep Burneze close to hand for minor burns. This unique scientific aerosol cools the heat out in just 8 seconds, anaesthetizes pain, reduces swelling. Be well-equipped — buy Burneze, from chemists.



Potter & Clarke Ltd Croydon CR9 3LP

FERRANTI

SEMICONDUCTORS AT LOWEST PRICES

All semiconductors brand new and fully guaranteed.

ZTX107 10p	ZTX320 28p	BFS61 19p	ZS176 21p	KS043A 17p
ZTX108 9p	ZTX330 15p	BFS96 16p	ZS178 34p	KS047A 17p
ZTX109 10p	ZTX331 14p	BFS97 21p	ZS270 10p	KS056A 17p
ZTX114 20p	ZTX500 10p	BFS98 21p	ZS271 14p	KS062A 17p
ZTX300 10p	ZTX501 11p	2N3055 65p	ZS272 16p	KS068A 17p
ZTX301 11p	ZTX502 15p		ZS274 17p	KS075A 17p
ZTX302 15p	ZTX503 12p	Diodes	ZS276 23p	KS082A 17p
ZTX303 12p	ZTX504 39p	ZS140 23p	ZS278 33p	KS091A 17p
ZTX304 19p	ZTX510 15p	ZS141 39p		KS100A 17p
ZTX310 7p	ZTX530 19p	ZS142 30p	Zeners	KS110A 17p
ZTX311 9p	ZTX531 20p	ZS170 9p	KS030A 17p	KS120A 17p
ZTX312 9p	ZTX550 15p	ZS171 11p	KS033A 17p	KS130A 17p
ZTX313 10p	BFS59 15p	ZS172 14p	KS036A 17p	KS150A 17p
ZTX314 11p	BFS60 19p	ZS174 15p	KS039A 17p	KS180A 17p

MOTOROLA: MJE2955 £1.65, MJE3055 85p, 2N4444 £2.25

R.C.A.: CA3075 £1.13, CA3090Q £3.46

Postage & packing 10p. Free above £2. Send SAE for Ferranti data.

DAVIAN ELECTRONICS, P.O. BOX 38, OLDHAM, LANCs

C.T. ELECTRONICS

FOR REAL SERVICE WITH THE
LARGEST SELECTION OF
**ELECTRONIC COMPONENTS
AND TEST EQUIPMENT**

You must visit

C.T. ELECTRONICS

267 ACTON LANE, CHISWICK, LONDON, W.4

9.30 a.m. — 6 p.m.

MONDAY — SATURDAY

LATEST SHIPMENT JUST ARRIVED!

ONLY FROM US!

BRAND NEW

RUSSIAN WORLD BEATER!

WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!

6 WAVEBAND

10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO



WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

£9.97 BOX POST ETC. 43p

*COMPARE ITS PERFORMANCE with **£34 RADIOS!**

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

What everyone's been waiting for—THE LATEST MODEL SUPERSEDING ALL PREVIOUS MODELS—THE FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO DESIGNED FOR WORLD-WIDE RECEPTION! So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios. You can't lose. Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection! Once again the Russians have proved their fantastic ability in the field of electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover the world. Unique side-control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips, and messages from all over the world! Superb, sweet tone—controlled from a whisper to a roar that will fill a hall. Genuine push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33in length. It's also a fabulous CARRADIO, any speed, requires no additional aerial. UNIQUE! Elegant Black, White and Chrome finish case. SIZE 10in x 8in x 3in overall approx. Made to give years of perfect service. With WRITTEN GUARANTEE, manual with simple instructions and circuit diagram. ONLY £9.97 POST, ETC., 43p. Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address. Refund if not delighted. Send today or call.

FANTASTIC (even by our standards!) Brand new—the latest sensation in the world of sound! First class! Brand new—only a fabulous VHF AM/FM Radio AND Cassette Tape Recorder and Player combined, but it also runs off standard batteries or mains (simply plug in 220/240V a.c. line cord). Now you can record and play back anything, anywhere! You can even tape direct from the Radio as you listen! RECOMMENDED RETAIL PRICE GENUINELY £44 YET WE OFFER AT ALMOST HALF PRICE! Just look at these wonderful features: "Press-button Keyboard Control panel or latest MASTER SWITCH CONTROL. "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic leveller! "Separate ON/OFF, and HI-LO volume controls! Heavy duty built-in speaker! "Earphone (for personal listening or "monitoring") and extension speaker sockets! "Remote control microphone! "Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case, with carry handle (DESIGNS VARY SLIGHTLY). Takes standard 30, 60, 90 or 120 minute Philips Cassettes and mics, everywhere. But wait, the amazing built-in full circuit VHF AM/FM Radio gives you superb clarity of tone and incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC National VHF. Picks up dozens of foreign stations. Also fabulous in your car! You could pay £44's more for a Car Radio or Car Cassette Player ALONE! ONLY £23.75 CARR, etc., 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE. BONUS OFFER—Standard Batteries and Cassette Tape 25p extra. Refund g'need. It's an offer you cannot afford to miss!

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

SHOPERTUNITIES LTD. SL

***WHY PAY £40 or MORE?**

THE VERY LATEST! SENSATIONAL! COMPLETE HIGH FIDELITY PORTABLE HIGH FIDELITY

Special Transmissions & Radio Receiver

VHF WITH SPECIAL FM MW AFC AIRCRAFT WAVEBAND

MIRACLE PRICE — REDUCED TO

£7.99

POST ETC. 38p

BUT WAIT! SUPER DE LUXE AC/DC MAINS and BATTERY model with Built-in MAINS BATTERY BOOSTER ONLY £2 EXTRA IF REQUIRED



PICKS UP AIRCRAFT TRANSMISSIONS (control to aircraft, etc.). ALSO GETS TAXIS, AMBULANCES, LOCAL RADIO STATIONS, CONTINENTAL STATIONS, ALL BBC, VHF, AND MANY MORE, including fascinating public service transmissions. A miracle of advanced technology. An instrument that will bring a new dimension to your world of sound! Frequency range: MWS40-1600 KHz, FM 88-108 MHz, Air 108-136 MHz. Intermediate Frequency: MW 455 KHz, FM 10.7 MHz, Air 10.7 MHz. 18 SEMI CONDUCTORS, Transistors 11, Diodes 6 + Thermister! Automatic frequency control "locks-in" eliminating drift. Pinpoint selection. Built-in adjustable 8-section Telescopic Aerial over 30in approx. Lowest price ever! Tremendously strong leather-grained finish case with carry handle. 10in x 6in x 4in overall approx. Written guarantee. ONLY £7.99, post 38p. Also Super De-Luxe model ONLY £9.99, post 38p (incorporating VHF, AM, FM and AFC SPECIAL AIRCRAFT WAVEBAND). Runs off mains—AC 230-250V, OR off standard batteries. It's got a built-in battery booster, too! Just plug into mains whenever you wish! Compare them with sets costing £40 or more! Refund guarantee. BONUS TO EVERY PURCHASER OF EITHER MODEL: Shoulder strap, earphone for personal listening and dry batteries all for 31p ex. inc. req. NOTE—The Ministry of Posts & Telecommunications has pointed out that a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

THIS FANTASTIC OFFER ONLY FROM US! **SAVE £20.25 NOW!** **SOLID STATE** This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

RECOMMENDED RETAIL PRICE £44

OUR PRICE £23.75 CARR ETC. 35p

WITH REMOTE CONTROL MICROPHONE

Dept./PE/16 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH STORES OPEN FROM MON. TO SAT. 9-6.

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it’s as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of “**OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO**”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF

POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B12, Aldermaston Court, Reading RG7 4PF
Please send books and full information — free and without obligation.

	NAME	AGE
	BLOCK CAPITALS PLEASE	
	ADDRESS	
SUBJECT OF INTEREST		
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY <i>Accredited by the Council for the Accreditation of Correspondence Colleges.</i>		

SIEMENS TTL EX STOCK!!

SIEMENS QUALITY PLUS BARGAIN PRICES PLUS LST SERVICE
A full design range of high quality TTL available from LST your Officially Appointed Siemens Distributors

Part No.	Description	Equal to	1-24	25-99	100 up
7400	Quadruple 2-input NAND gate	FLH 101	20p	16p	14p
7401	Quadruple 2-input NAND gate with open collector output	201	20p	16p	14p
7402	Quadruple 2-input NOR gate	191	20p	16p	14p
7403	Quadruple 2-input NAND gate with open collector output	291	20p	16p	14p
7404	Hex inverter	211	25p	21p	18p
7405	Hex inverter with open collector output	271	25p	21p	18p
7408	Quad 2-input positive AND gate Totem pole output	381	25p	21p	18p
7409	Quad 2-input positive AND gate open collector	391	25p	21p	18p
7410	Triple 3-input NAND gate	111	20p	16p	14p
7413	Schmitt Trigger	351	35p	29p	25p
7420	Dual 4-input NAND gate	121	20p	16p	14p
7430	8-input NAND gate	131	20p	16p	14p
7440	Dual 4-input NAND buffer	141	24p	20p	17p
7442	BCD to decimal decoder TTL output	281	£1.16	94p	31p
7443	Excess 3 to decimal decoder	361	£1.45	£1.20	£1.08
7444	Excess 3 gray to decimal decoder	371	£1.45	£1.20	£1.08
7450	Expandable dual 2-wide 2-input AND-OR-INVERT gate	151	20p	16p	14p
7451	Dual 2-wide 2-input AND-OR-INVERT gate	161	20p	16p	14p
7453	Expandable 4-wide 2-input AND-OR-INVERT gate	171	20p	16p	14p
7454	4-wide 2-input AND-OR-INVERT gate	181	20p	16p	14p
7460	Dual 4-input expander	FLY 101	20p	16p	14p
7470	J-K flip-flop	FLJ 101	45p	37p	32p
7472	J-K master-slave flip-flop	111	32p	27p	23p
7473	Dual J-K master-slave flip-flop	121	45p	40p	35p
7474	Dual D-type edge triggered flip-flop	141	46p	38p	33p
7475	Quad bistable latch	151	45p	40p	37p
7476	Dual J-K master-slave flip-flop with preset and clear	131	45p	40p	36p
7480	Gated full adder	FLH 221	67p	56p	48p
7482	2-bit binary full-adder	231	87p	73p	62p
7483	Four-bit binary full adder	241	£1.32	£1.16	£1.00
7486	Quadruple 2-input exclusive-OR element	341	33p	27p	23p
7490	Decade counter	FLJ 161	80p	67p	57p
7491A	8-bit shift register	221	£1.28	£1.07	92p
7492	Divide-by-12 counter	171	85p	71p	61p
7493	4-bit binary counter	181	80p	67p	57p
7494	4-bit shift register	231	£1.13	94p	81p
7495	4-bit shift register	191	87p	72p	62p
7496	5-bit shift register	261	£1.48	£1.22	£1.05
74100	Dual quadruple bistable latch	301	£1.64	£1.37	£1.17
74107	Dual J-K master-slave flip-flop with preset and clear	271	52p	43p	36p
74121	Monostable multivibrator	FLK 101	48p	40p	34p
74141	BCD to decimal decoder and nixie driver	FLL 101	£1.22	£1.02	87p
74190	Synchronous up down 4-bit decade counter with one line mode control	201	£1.80	£1.48	£1.27
74191	Synchronous up down 4-bit binary counter with one line mode control	211	£1.80	£1.48	£1.27
74192	Synchronous up down 4-bit decade counter	241	£1.74	£1.45	£1.25
74193	As above—binary counter	251	£1.74	£1.45	£1.25

TYPES MAY BE MIXED TO QUALIFY FOR PRICE BREAKS
DATA BOOKLET 20p

CONTRACT ORDER PRICES AND BULK QUANTITY PRICES QUOTED ON REQUEST EXTENDED RANGE AVAILABLE TO TRADE

LST

PART OF OUR CATALOGUE RANGE:

Large range of Transistors by many major manufacturers, Zener Diodes, Thermistors, Varicap Diodes, Rectifiers, Thyristors, Triacs, IC Amplifiers, Unijunctions, Opto-electronics, Tunnel Diodes, Meters, etc., etc.

2N5777 PHOTO DARLINGTON

NEW LOWEST PRICE
FANTASTIC SENSITIVITY **45p**

IF YOU HAVEN'T GOT OUR
CATALOGUE WHY NOT??? IT'S FREE!

ULTRASONIC TRANSDUCERS




Operate at 40 kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.
FREE: With each pair our complete transmitter and receiver circuit.
PRICE **£5-90**

(Sold only in pairs)

7 SEGMENT INDICATOR 3015F

16DIL Case—0-9 plus decimal indication. £2 incl. data/circuits. FLL121 Decoder Driver £1.32 to suit.

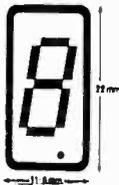LST are appointed distributors for the Minitron 3015F—quantity prices on request.



NEW PRODUCT !!

LOW COST DIL SOCKETS

16 PIN DUAL IN LINE **17p**
14 PIN DUAL IN LINE **15p**

NEW LOW PRICE LINEARS!!

LIC709C/5 (TOS) **40p**
LIC709C/14 (DIL) **35p**
LIC723/5 (TOS) **79p**
LIC723/14 (DIL) **93p**
LIC741C/5 (TOS) **43p**
LIC741C/14 (DIL) **40p**

All above are the new NEW-MARKET Linear range.

LST are Official Distributors for Newmarket Transistors Ltd.

Data and Volume prices on application.

TERMS:

Retail Mail order subject to 50p minimum order. Cash with order only.

Schools etc.: Nett MA against Official order.

Trade: Account on application.

Postage: 10p inland; 25p Europe; elsewhere—send plenty will refund.

Guarantee: All goods carry Manufacturers' warranty.

Counter sales: Same address—open Saturdays.

Trade Enquiries only: Telephone Brentwood 226470.

LOW COST 1 AMP BRIDGES

	1-99	100+
W005	50piv	.23 .21
W01	100piv	.24 .23
W02	200piv	.25 .23
W04	400piv	.27 .24
W06	600piv	.28 .25
W08	800piv	.35 .31

Sub-miniature size. Plastic encapsulated. Larger quantity prices on application.

SPECIAL OFFER IN4000 SERIES 1 AMP RECTIFIERS

	p.i.v.	1-49	50+	100+
IN4001	50	070	060	050
IN4002	100	070	065	060
IN4003	200	090	085	070
IN4004	400	100	090	080
IN4005	600	120	100	090
IN4006	800	140	130	110
IN4007	1000	190	150	120
	p.i.v.	500+	1000+	
IN4001	50	045	040	
IN4002	100	055	045	
IN4003	200	060	050	
IN4004	400	070	060	
IN4005	600	075	070	
IN4006	800	100	085	
IN4007	1000	110	100	

Should any item be out of stock we reserve the right to supply a higher voltage rated item at no extra charge.

NEW LOWER PRICES

AC107	30p	BSY95A	12p	OA70	8p	40430	97p
AC126	20p	BY100	15p	OA73	8p	40432	£1.17
AC127	25p	BYZ10	35p	OA79	8p	40512	£1.45
AC128	20p	BYZ12	30p	OA81	8p	40576	£1.70
AC151	12p	BYZ13	20p	OA85	8p	IN4007	20p
AC176	25p	BZY98/		OA90	8p	IN4148	7p
AC187	25p	C3V3	15p	OA91	8p	2G302	19p
AC188	25p	C3V6	15p	OA95	8p	2G371	15p
AC191	37p	C3V9	15p	OA200	10p	2G372	25p
AC198	20p	C4V3	15p	OA202	10p	2N174	80p
AC199	20p	C4V7	15p	OC19	37p	2N385A/	50p
ACY20	20p	CSV1	15p	OC20	97p	2N388A/	50p
ACY21	19p	CSV6	15p	OC22	47p	2N404	23p
ACY22	10p	C6V2	15p	OC23	60p	2N696	15p
ACY40	15p	C6V8	15p	OC24	60p	2N697	17p
ACY41	15p	C7V5	15p	OC25	37p	2N698	30p
AC180	35p	CBV2	15p	OC26	33p	2N706	10p
AD149	50p	C9V1	15p	OC28	60p	2N706A	12p
AD161	36p	C10	15p	OC29	60p	2N708	16p
AD162	24p	C11	15p	OC35	50p	2N711	37p
AF106	24p	C12	15p	OC36	63p	2N711A	37p
AF114	25p	C13	15p	OC41	25p	2N911	50p
AF115	25p	C15	15p	OC42	30p	2N914	20p
AF116	25p	C16	15p	OC44	15p	2N918	43p
AF117	25p	C18	15p	OC45	12p	2N1090	30p
AF118	44p	C20	15p	OC71	12p	2N1091	33p
AF124	25p	C22	15p	OC72	12p	2N1131	30p
AF126	17p	C24	15p	OC75	23p	2N1132	30p
AF139	30p	C27	15p	OC76	25p	2N1302	17p
AF186	40p	C30	15p	OC77	40p	2N1303	17p
AS211	37p	CA3004	£1.80	OC81	20p	2N1304	15p
AUY10	£1.50	CA3005	£1.17	OC81D	20p	2N1305	22p
BC107	8p	CA3011	74p	OC81Z	55p	2N1306	24p
BC108	10p	CA3013	£1.05	OC82	25p	2N1307	24p
BC109	10p	CA3014	£1.24	OC82D	15p	2N1308	30p
BC147	10p	CA3018	82p	OC83	23p	2N1309	30p
BC148	9p	CA3020	£1.26	OC84	25p	2N1309	23p
BC149	10p	CA3049	£1.60	OC139	15p	2N1310	15p
BC158	11p	CA3052	£1.65	OC140	35p	2N1711	15p
BC167	11p	CA3090Q	£3.46	OC170	25p	2N2147	75p
BC168	10p	CR1051C	40p	OC171	30p	2N2148	60p
BC169	11p	CR1401C	60p	OC200	40p	2N2160	57p
BC169C	15p	CRS305AF	£1.08	OC201	60p	2N2368	17p
BC182	10p			OC202	75p	2N2369	17p
BC182L	10p			OC202	75p	2N2369A	19p
BC183	9p			OC203	40p	2N2646	47p
BC183L	10p			OC204	40p	2N2904	44p
BC184	13p			OC205	75p	2N2904A	49p
BC184L	12p			OC206	90p	2N2905	65p
BC212	12p			OC207	75p	2N2905A	75p
BC212L	12p			OC207/M	42p	2N2806	44p
BCY30	25p			ORP12	50p	2N2906A	54p
BCY31	48p			ORP60	40p	2N2925 all	
BCY32	50p			ORP61	40p	colours	10p
BCY33	20p			ORP61	40p	2N3053	20p
BCY34	25p			P346A	19p	2N3054	50p
BCY38	30p			PA230	£1.40	2N3055	60p
BCY70	15p			PA234	£1.25	2N3702	10p
BCY71	30p			PA237	£2	2N3702	10p
BCY72	15p			PA246	£2.63	2N3704	11p
BD121	65p			PA424	£2.45	2N3705	10p
BD123	80p			SL403D	£1.50	2N3706	9p
BD124	75p			ST140	15p	2N3707	11p
BD131	75p			ST141	20p	2N3708	7p
BDY132	75p			TAA263	75p	2N3709	9p
BDY137	75p			TAA293	97p	2N3710	9p
BDY20	£1.05			TAA310	£1.25	2N3711	9p
BF115	23p			TAA320	75p	2N3819	35p
BF163	35p			TAD100	£1.97	2N3820	60p
BF167	18p			TAD110	£1.97	2N3826	30p
BF173	19p			TD716	60p	2N4058	15p
BF177	25p			TIP31A	62p	2N4061	12p
BF178	31p			TIP32A	74p	2N4062	12p
BF180	35p			TIS88A	45p	2N4284	15p
BF181	35p			µL900	40p	2N4285	15p
BF184	20p			µL914	40p	2N4287	15p
BF185	25p			µL923	40p	2N4289	15p
BF194	17p			V405A	46p	2N4370	40p
BF195	15p			NKT124	18p	2N4371	45p
BF196	15p			NKT125	40p	3N84	£1.30
BF200	35p			NKT126	37p	3N128	69p
BFX13	25p			NKT128	25p	3N140	76p
BFX29	25p			NKT211	25p	3N141	73p
BFX84	25p			NKT212	25p	3N152	80p
BFX85	34p			NKT213	25p	40250	55p
BFX86	25p			NKT216	46p	40309	33p
BFX87	30p			NKT217	50p	40312	48p
BFX88	24p			NKT218	25p	40320	47p
BFY50	22p			NKT219	25p	40360	43p
BFY51	19p			NKT223	27p	40361	47p
BFY52	20p			NKT227	18p	40407	39p
BFY53	17p			NKT272	17p	40408	51p
BFY90	67p			NKT274	18p	40409	54p
BSX19	16p			NKT277	18p	40418A	62p
BSX20	16p			NKT279A	18p	40462	35p
BSX21	20p			NKT281	29p	40406	56p
BSY27	20p			NKT302	87p	40407	39p
BSY29	25p			NKT304	79p	40408	51p
				NKT351	75p	40409	54p
				NKT401	71p	40410	62p
				NKT402	77p	40464	35p
				NKT403	65p	40500	10p
				NKT404	60p	40501	16p
				NKT405	79p	40502	20p
				NKT406	62p	40503	17p
				NKT420	£1.83	40504	40p
				NKT451	58p	IN34A	20p
				NKT452	58p	IN60	20p
				NKT453	50p	IN64	20p
				NKT454	50p	IN82A	47p
				NKT713	29p	IN914	7p
				NKT717	44p	IN4001	7p
				NKT773	25p	IN4002	7p
				NKT781	29p	IN4003	10p
				NKT20329/		IN4004	10p
				0013	31p	IN4005	12p
				OA5	20p	IN4006	15p
				OA10	25p	2N5756	95p
				OA47	8p	40486	95p

QUALITY: LST are Official Franch

units at lowest prices?..."

Compare our prices with any other unit on the hi-fi market, and you'll find you won't beat ROC unit prices. No matter where you live, London or Land's End!

Take a good look at all these super audio equipment bargains. They're all on demonstration at our Shop from 9 to 6 p.m. Monday to Saturday, late night Thursday until 7 p.m. But don't worry if you can't get there yourself. Our Mail Order service is at your disposal. With the same exclusive ROC equipment — and at the same super-value-for-money prices!

When you invest in ROC equipment, you're getting much more than an exclusive product. You're getting value for money that is literally unbeatable. ROC units are bought direct from the manufacturer, and ALL the savings ROC derive from this are passed on to you!

At ROC Electronics, we take extra care to select only the best buys. We check everything before you do — and it's fully guaranteed whether you buy at the shop or by Mail Order.



TOP VALUE • TOP QUALITY ACCESSORIES THAT EVERY HI-FI ENTHUSIAST NEEDS TO COMPLETE HIS SYSTEM

Every item shown here is the best of its kind within its price range. Buy them separately or at the same time as the other top-value audio products listed.



R.328 STEREO HEADPHONE
If you're starting in hi-fi, and you discover the need for a pair of really good stereo headphones. The R.328 is ideal, at a price you can afford. They have padded ear cushions, a 6-foot cord and jack plug. Frequency range 30-15,000 Hz. Impedance 8 ohms per channel.
ROC PRICE £2 95

EAGLE SE-30 STEREO HEADPHONE

This model is for the more discriminating listener. For a start the frequency range extends from 30 to 16,000 Hz. And you can adjust the volume of each earpiece independently. There's also a mono/stereo switch. For maximum comfort, the ear cushions are covered in soft leathers. **ROC PRICE £7 05**



EAGLE SE-80 STUDIO STEREO HEADPHONE

Here's the ultimate in headphone design! Apart from its fantastic ability to reproduce all the frequencies from 20 to 20,000 Hz, the SE-80 has eliminated the discomfort and strain associated with traditional headphone design. Eagle has designed and produced a pair of headphones which breaks with all previous concepts. You hear all the sounds crisp and clear. In fact, the reproduction is so good, that it compares favourably with the most expensive hi-fi speaker systems. Separate slider volume control on each earpiece. Impedance: 8 ohm per channel.
ROC PRICE £14 90



TEC HR-007 HEADPHONE RADIO
When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW.
Normal Price £9 45 ROC PRICE £7 65



EAGLE 8-TRACK CAR STEREO PLAYER, CS.8
Drive to the sound of music — with this fabulous 8-Track Cartridge Player. It gives you superb tone and power to fill the car with stereo sound. Ideal for use with R.151 or R.152 speakers. Complete with all mounting accessories. For negative earth electrical systems only. Output: 2.5 watts per channel. Frequency range: 70-10,000 Hz. Wow and flutter: less than 0.3%. Tape speed: 3.5 cm/sec. Channel selector: automatic with manual over-ride. Mounting dimensions: 5 1/2" x 5 1/2" x 2 1/4". **ROC PRICE £27 20**




RECORD CLEANERS
The original "Dust Bug" Automatic Record Cleaner keeps your records clean as they play. £1 20 Watts Disc Preener. Keeps new records like new — for perfect record reproduction 35p



R.307 TRANSISTORIZED STEREO PRE-AMPLIFIER
Now your amplifier that could only reproduce ceramic or crystal pick-up cartridges, can accept signals from moving-magnet cartridges! The R.307 steps up signals from between 5-20mV to 200-800 mV. Input: 5-20mV. Equalisation: RIAA. Output: 200-800mV flat. Frequency range: 20-22,000 Hz. Dimensions: 3 1/2" x 1 1/2" x 2 1/2". Supply: 240 VAC. **ROC PRICE £4 92**



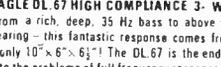15-FOOT STEREO HEADPHONE EXTENSION CORD R.362
Fitted with heavy duty 3-circuit stereo plug at one end and a matching stereo socket at the other. **ROC PRICE £1 30**



STEREO HEADPHONE "Y" ADAPTOR R.361
Enables you to use two sets of stereo headphones from a single socket. Fitted with male plug and two female sockets. **ROC PRICE £1 30**



THRENS TD150AB II Transcription Turntable
Complete with pick up arm, plinth and cover. **£52 31**



R.186 STEREO HEADPHONE JUNCTION BOX
If you want easy, fingertip control of headphones and loudspeakers, here's the ideal solution to the problem. All you do is connect it to your speakers and amplifier, plug in your headphones — and you're ready to take over! At the flick of a slide switch, you can have headphones alone, or speakers alone, or both together. Input: suitable for use with amplifiers rated up to 20 watts. [Size: 2 1/2" x 3 1/2" x 1 1/2"]
ROC PRICE £1 50



R.151 STEREO CAR SPEAKERS
Smart black, tough plastic cases, each containing a high flux 110mm diameter speaker unit. Just what you need to go with the CS.8 Cartridge Player or any other car stereo system. Fitted with over three yards of connecting cable. Dimensions: 6 1/4" x 5 1/2" x 3 1/2". Impedance: 8 ohms per speaker. Rating: 5 watts max per speaker. **ROC PRICE £3 72**



R.152 STEREO CAR SPEAKERS
These sloping front speakers match the CS.8 Cartridge Player or any other car stereo system. Fitted with high flux 110mm diameter speaker unit, and over three yards of connecting cable. Dimensions: 6 1/2" x 3 1/2" x 3 1/2". Impedance: 8 ohms per speaker. Rating: 5 watts max per speaker.
ROC PRICE £4 96



EAGLE LC.05 STEREO MAGNETIC CARTRIDGE
For fabulous reproduction at a very low price, you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: -1.5dB. Channel separation: 20dB. Recommended stylus pressure: 2-4 grams. Compliance: 9 x 10⁻⁶ cm/dyne. **ROC PRICE £4 75**



EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE
Here's your opportunity to own a transcription cartridge for the price of a ceramic! It's specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: +1dB. Channel separation: 20dB. Compliance: 12 x 10⁻⁶ cm/dyne. **ROC PRICE £6 37**



R.088 MATCHED STEREO LOUD SPEAKERS
Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9 50 pair**



EAGLE DL.67 HIGH COMPLIANCE 3-WAY TEAK SPEAKER SYSTEM
From a rich, deep, 35 Hz bass to above the limit of human hearing — this fantastic response comes from such a small size — only 10" x 6" x 6 1/2"! The DL.67 is the end product of several years' effort into the problems of full frequency response from small cabinets. The DL.67 has a dual cone high compliance bass mid range unit, and a horn tweeter. The speaker has a variable brilliance control to suit individual rooms — a feature normally only found on very expensive speaker systems. Power handling capacity: 10 watts rms, 20 watts peak. Frequency range: 35-20,000 Hz. Flux density: 11,000 gauss. Impedance: 8 ohms. Dimensions: 11 1/2" high x 8" wide x 6 1/2" deep. Finish: oiled teak. **ROC PRICE £110 80 each**

HERE'S A RANGE OF AUDIO SYSTEMS BUILT AROUND EXCLUSIVE ROC AMPLIFIERS AND TUNERS

Now run your eye over the prices, select the System nearest to your budget — and you've hit on the best value that your money can buy! Supplied with all necessary leads and plugs, ready to use.



REALISTIC SA-100B SYSTEM
Realistic SA-100B Stereo Amplifier, Garrard 2025TC Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers. Matching TM-100 Stereo Tuner £23.25 extra if required.
Normal Price £63 98 ROC PRICE £47 60



OLSON AM-395 SYSTEM
Olson AM-395 Stereo Amplifier, Garrard SP25 Mk III Record Player with Eagle LC07 Stereo Magnetic Cartridge, plinth and cover and a pair of Eagle DL.67 Speakers. Matching RA.310 Stereo Tuner £39.95 extra if required.
Normal Price £106 65 ROC PRICE £92 60




OLSON AM-357 SYSTEM
Olson AM-357 Stereo Amplifier, Garrard 2025 T/C Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.088 4 watt Speakers.
Normal Price £45 28 ROC PRICE £36 70



PALACE SYSTEM
Palace SSA-16 Stereo Tuner Amplifier, Garrard 2025 T/C autochanger with stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers.
Normal Price £84 98 ROC PRICE £66 30



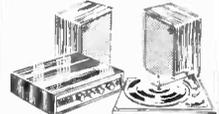
REALISTIC SA-500 SYSTEM
Realistic SA-500 Stereo Amplifier, Garrard SP25 Mk III Single Record Player with Eagle LC.07 Stereo Magnetic Cartridge, plinth and cover and a pair of Cryster CE.5b Speakers. **Normal Price £157 95 ROC PRICE £124 00**



OLSON AM-372 SYSTEM
Olson AM-372 Stereo Amplifier, Garrard 2025 T/C Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers.
Normal Price £68 18 ROC PRICE £51 53



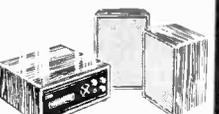REALISTIC 12-694 SYSTEM
Realistic 12-694 Stereo Tuner Amplifier with matching speakers and Garrard SP25 Mk III with Eagle LC.07 Stereo Magnetic Cartridge and plinth and cover.
Normal Price £144 05 ROC PRICE £124 50



ROC E1 SYSTEM
ROC E1 8 track Stereo Cartridge Player complete with a pair of ROC R.088 4 watt Speakers.
Normal Price £59 10 ROC PRICE £49 45

Return-of-post mail order service. Over £10 post free (UK only). Add 25p for a p to orders under £10. HP terms available for callers

ROC ELECTRONICS LTD

N. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211

CALLERS WELCOME AT THE SHOP 9-6 MON TO SAT,

LATE NIGHT THURSDAY 7 PM





ORGAN KITS

Build your own Electronic Organ, if you want the best value for your money. Yes you really save over 50% and get the best and up-to-date designs. There are four models to choose from.

- ★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, at £103.00, P/P £1.50.
- ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato built in amplifier and 50 watt 12" Goodmans speaker at £167.00, P/P £5.00.
- ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, Wah Wah, etc. at £406.00. Carr. paid on complete kit U.K. only.
- ★ Console—2 x 5 octave keyboards and 32 note pedal boards, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572.55 carr. paid on complete kit U.K. only.

We regret H.P. facilities are not available, but components can be bought separately. Trade and overseas enquiries welcomed. Send 15p for latest catalogue.


Please call in for demonstration. Business hours: 10 a.m. to 7 p.m. Monday to Saturday. Thursday closed.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE RD., LONDON
S.W.18 TEL: 01-870 4949

Bus numbers 37, 220, 225, 168 pass the door. 10 minutes walk from East Putney or 15 minutes walk from Putney Bridge Underground Stations.

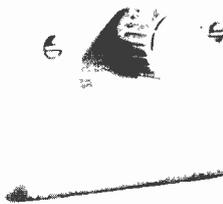Vary the strength of your lighting with a DIMMASWITCH




The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70
300 Watt £2.70. Kit Form £2.20

All plus 10p post and packing.
Please send C.W.O. to:

DEXTER & COMPANY
1 ULVER HOUSE, 19 KING STREET
CHESTER CH1 2AH Tel. 0244-25883
As supplied to H.M. Government Departments

INTER-LOCKING PLASTIC STORAGE DRAWERS

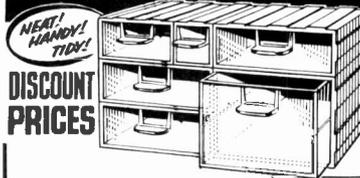

NEAT!
HANDY!
TIDY!

DISCOUNT
PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES
ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins) £1.35 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins) £2.25 DOZEN.

TREBLE (3D) £2.35 for 8.

DOUBLE TREBLE 2 draws, in one outer case (6D2), £3.65 for 8, **EXTRA LARGE SIZE (6D1)** £3.30 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £
Orders £10 and over DEDUCT 7½% in the £
Orders £20 and over DEDUCT 10% in the £
PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £5. Orders £5 and over, packing/postage/carriage free.

**QUOTATIONS FOR LARGER QUANTITIES
ALL PRICES TAX PAID**

**IVORYET
LIMITED**

(Dept. PE5) 124 Cricklewood
Broadway, London, N.W.2
Tel. 01-450 4844

4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.40. P. & P. 50p extra.

INTERCOM/BABY ALARM



£3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. 25p.

Transistor TELEPHONE AMPLIFIER




£2.99

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE1)
169 KENSINGTON HIGH STREET, LONDON, W.8



I.L.P. (Electronics) Ltd

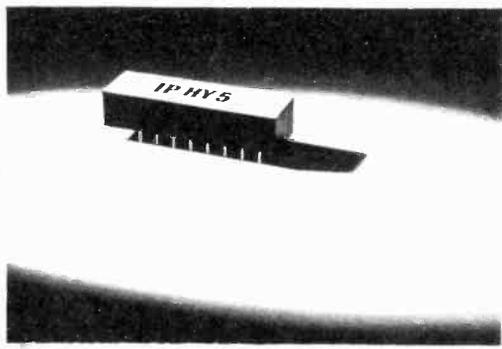

HY40 IS POWER AMP PERFECTION

Lets face it—an immediate success, the HY40 is here to stay.

HY40 means Hybrid Power, power neatly locked away inside an Integrated Circuit. Power the modern way, simply mount only five additional components on a printed circuit board (all of which are supplied with the HY40). Power not only for Hi-Fi, power for Groups, for public address, for industry, power for all.

HY40 is HI-FI POWER ILP are POWER PROUD

In addition to the P.C. board and manual supplied with the HY40 we now include the five remaining components, at minimal cost, needed to complete the assembly of a High Performance Power Amplifier.

By merely combining two HY40s with a Stereo Preamplifier (2 x HY5) and simple Power Supply (PSU45), premium quality stereo may be obtained for a very modest outlay.

The free manual supplied with the HY40 gives clear, easy build instructions for Power Supply; volume, bass, treble and balance controls, together with inputs for Ceramic and Magnetic Pick-ups, Tape, Tuner and Auxiliary functions.

Internally the HY40 is based on conventional and proven circuit techniques developed over recent years.



OUTPUT POWER British Rating 40 WATTS PEAK, 20 watts RMS continuous.

LOAD IMPEDANCE 4—16 ohms

INPUT IMPEDANCE 22Kohms at 1Khz.

INPUT SENSITIVITY 300 mV for maximum output.

VOLTAGE GAIN 30db at 1KHz.

FREQUENCY RESPONSE 5Hz-60KHz \pm 1db.

TOTAL DISTORTION less than 1% (typical 0.1%) at all output powers.

SUPPLY VOLTAGE \pm 22.5 volts D.C.

SUPPLY CURRENT 0.8 amps maximum.

PRICE: including comprehensive manual, P.C. Board and FIVE EXTRA COMPONENTS:

MONO £4-40 STEREO £8-80 all post free.

A WORLDS FIRST TO JOIN THE WORLDS BEST

The HY5 is a unique and revolutionary concept in High-Fidelity pre-amplifiers. Thanks to the latest techniques, all feedback and equalization networks are, for the first time, combined into an integrated pre-amplifier circuit.

Simply by adding volume, treble, bass potentiometers and only three stabilizing capacitors, which are supplied, your HY5 is complete and ready for use.

The HY5 provides equalization for almost every conceivable input. This years developments in equalization technique enables precise correction for both output voltage and frequency response for any crystal or ceramic cartridge. Yet another feature of the HY5 is its inbuilt stabilization circuit, allowing it to be run off any unregulated power amplifier supply.

The HY5 contains a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo preamplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY40 and PSU45 forms a completely integrated system.

INPUTS

Magnetic Pick-up (within \pm 1db RIAA curve) 2mV.

Tape Replay (external components to suit head). 4mV.

Microphone (flat) 10mV.

Ceramic Pick-up (equalized and compensatable) 20—2000mV variable.

Tuner (flat) 250mV.

Auxiliary 1 250mV.

Auxiliary 2 2—20mV.

OUTPUTS

Main Pre-amp output 500mV.

Direct tape output 120mV.

ACTIVE TONE CONTROLS

Treble \pm 12db.

Bass \pm 12db.

INTERNAL STABILIZATION

Enables the HY5 to share an unregulated supply with the Power Amplifier.

SUPPLY VOLTAGE

15—25 volt.

SUPPLY CURRENT

5mA approx.

OVERLOAD CAPABILITY

better than 28db on most sensitive input infinite on tuner and auxl.

OUTPUT NOISE VOLTAGE

0.5mV.

PRICE

Mono £3-60

Stereo £7-20

POWER SUPPLY PSU45



The PSU45 is specifically designed to supply, simultaneously, your HY40 (in mono or stereo format) and one or two HY5s.

Spec.

PSU45 \pm 22.5 volts, 2 amps simultaneously.

PRICE: £4-50 including Postage and Packing

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT
TELEPHONE: CANTERBURY 63218

DISCOUNTS UP TO

60%* ON BRANDED GOODS

ALL BRAND NEW
in manufacturer's sealed cartons.
GUARANTEED 12 MONTHS.

SPECIAL OFFER
Garrard SP25 Mk. III £18
Goldingr G800H £19.95
Teak plinth and tinted cover.
Ready wired for immediate use.
Please add £1.25 for P. & P.

TURNTABLES

Please add 75p post & packing

Garrard SP25 Mk. III	£9.95
Garrard AP76	£13.25
Garrard SL65B	£5.97
Garrard 1025T + cart.	£27.00
Garrard 401	£39.95
Garrard Zero 100 (Auto)	£37.25
Garrard Zero 100 (Single)	£10.00
BSR MP60	£22.50
Goldingr GL72	£29.25
Goldingr GL72/P	£27.50
Goldingr GL75	£35.50
Goldingr GL75/P	£55.00
Leak Delta	£27.75
Wharfedale Linton + cart.	£37.75
Thorens TD125	£90.00
Thorens TD125AB	£28.00
Thorens TD150 Mk. II	£33.75
Thorens TD150A Mk. II	

AMPLIFIERS

Please add 75p post & packing

Amstrad 8000 Mk. II	£16.95
Amstrad IC2000	£27.90
Armstrong 521 (Teak cased)	£43.95
Alpha Highgate 212	£25.00
Alpha Highgate FA300	£27.95
Alpha Highgate FA400	£31.95
Cambridge P100	£116.00
Cambridge P40	£65.95
Cambridge P50	£71.00
Ferrograph F307 Mk. II	
(Wood cased)	£47.50
(Metal cased)	£45.00
Leak Delta 30	£48.00
Leak Delta 70	£56.00
Metrosound ST20E	£24.75
Metrosound ST60	£47.25
Pioneer SA900	£92.00
Pioneer SA1000	£94.00
Rogers R/brook (Chassis)	£35.00
Rogers R/brook (Cased)	£37.00
Rogers R/bourne (Chassis)	£41.50
Rogers R/bourne (Cased)	£46.50
Scaneltra HT58	£28.75
Sinclair PR060 2	Z30/PZ5 £15.25
Sinclair PR060 2	Z30/PZ6 £17.50
Sinclair PR060 2	Z50/PZ8/Trans £21.75
Sinclair AFU (Filter Unit)	£4.40
Sinclair 605	£18.75
Sinclair 2000 Mk. II	£21.75
Sinclair 3000 Mk. II	£29.75
Sugden A21/111	£51.50
Sugden A51/CS1	£102.00
Wharfedale Linton	£39.95
Goodmans Max Amp	£37.95
Teleton SAQ206B	£21.50
Teleton SAQ306	£22.95
Euromon 10 + 10	£16.95

TUNERS

Please add 75p post & packing

Armstrong 523	£39.50
Armstrong 524	£31.00
Rogers R/brook FET4	
(Chassis)	£31.00
Rogers R/brook FET4	
(Cased)	£35.00
Rogers R/bourne FET4	
(Chassis)	£43.00
Rogers R/bourne FET4	
(Cased)	£48.00
Sinclair PR060 (Module)	£18.50
Sinclair Cased Tuner	£34.00
Philips RH690	£33.00
Leak Delta FM (Cased)	£55.50
Leak Delta AM/FM (Cased)	£66.50

TUNER/AMPLIFIERS

Please add 75p post & packing

Armstrong 525 (Teak cased)	£68.50
Armstrong 526 AM/FM	
(Teak cased)	£78.50
Leak Delta 75	£130.95
Philips RH781	£50.00
Philips RH882 (+ cass. head)	£72.00
Philips RH702	£62.50
Teleton 1515 FM	£29.95
Goodmans One Ten	£105.00
Rogers Ravensbrook	
(Teak cased)	£80.00
Rogers R/brook (Chassis)	£74.50
Scaneltra 1515 AM/FM	£102.50
Scaneltra 3030 FMG	£110.50
Scaneltra 1515 FM	£74.50

SPEAKERS

Please add £1.25 for post & packing Price per pair

Amstrad 138	£20.00
Wharfedale Denton 2	£29.00
Wharfedale Linton 2	£37.00
Wharfedale Melton 2	£47.95
Wharfedale Dovedale 3	£61.50
Celestion Ditton 120	£39.00
Celestion Ditton 15	£55.00
Celestion Ditton 25	£89.00
Goodmans Double Maxim	£48.50
Goodmans Mezzo 3	£45.75
Goodmans Magister	£120.25
Sinclair Q16	£12.50

CARTRIDGES

Please add 10p post & packing

Goldingr G850	£3.65
Goldingr G800	£6.25
Goldingr G800E	£10.35
Goldingr G800 Super E	£15.75
Shure M3D	£4.50
Shure M44E	£6.25
Shure M55E	£6.75
Shure M75E Type 2	£12.25
Sonotone 9TAHC	£1.85

£3.20*

Plus 35p P. & P.
Finished in teak veneer with tinted dust cover. (Fully assembled).
For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR, McDonald MP60 and others.
For AP76; AP75; SL72B; SL75; SL95B*, £4.20 plus 35p P. & P.
Also finished in walnut to match Japanese equipment—at no extra.




JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

1N4148	Signal Diode	18 for 50p (=1N914)
1N5060	1 Amp Rectifier 400V avalanche protected	7 for 50p (=A14D)
2N2923	NPN Silicon Transistor hfe 90 - 180 (25v)	7 for 50p
2N2926	NPN Silicon Transistor hfe 55 - 110	8 for 50p
2N3391A	Si NPN Hi Gain (250 - 500) low noise transistor	3 for 50p
2N3402	Medium power (driver) 900mw 25v Hfe 75 - 225	6 for 50p
C6U	1.6 amp general purpose 25v SCR in T05 case	3 for 50p

Post and packing 10p for 1 or 2 packs; 3 packs or more post free.

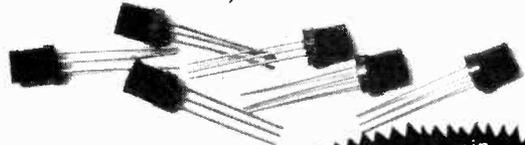Order any quantity, till sold (but we regret packs cannot be subdivided).



P.O. or Cheque payable
Jermyn Industries,
Vestry Estate,
Sevenoaks, Kent.

Star Bargain
Sprague (Pirgo) Triacs
PT406S (6 amp 400v)
48p each

Keep those Contacts CLEAN

by using a

DIACROM SPATULA

The "Diacrom" is a metal spatula upon which diamond powder has been deposited by a special process. No deep scratches are possible because density is controlled and the polishing of the contacts is achieved by a gentle brushing motion. With coloured nylon handle for complete insulation and easy size identification.



Manufactured in France
British Patents applied for

- Grain size 200, thickness 55/100 mm., both faces diamonded. For quick cleaning of industrial relays and switching equipment, etc.
- Grain size 300, thickness 55/100 mm., both faces diamonded. For smaller equipments, like telephone relays, computer relays, etc.
- Grain size 400, thickness 25/100 mm., one face diamonded. For sensitive relays and tiny contacts. Two close contacts facing each other can be individually cleaned, because only one face of the spatula is abrasive.

Sole Distributors for the United Kingdom

SPECIAL PRODUCTS (Distributors) LTD.

81 Piccadilly, London, W.1

Phone 01-629 9556

As supplied to the War Office, U.K.A.E.A., Electricity Generating Boards, British Railways and other public authorities; also to leading electronic and industrial users throughout the United Kingdom



All prices correct
at time of going
to press E. & O. E.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. PE10 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue,
Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to

6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

FANTASTIC! WHARFEDALE

SPEAKER BARGAINS DENTON 2 SAVE £8.40

Sold in matched pairs. Each Denton contains an 8in. bass unit with 3in. pressure unit, coupled by a Wharfedale crossover network. Rated input: 18 watts maximum. Frequency response: 65-17,000 Hz. Impedance: 4/8 ohms. Cabinet 9½in. 14in. 8½in.



List Price £39.90 Per Pair. C. & P. £2.00

LASKY'S PRICE **£31.00**

List Price	Lasky's Price	C & P
LINTON 2 Pair	£49.90	£38.75
FRITON 3 Pair	£65.00	£51.50
MELTON 2 each	£35.00	£25.50
DOVEDALE 3 each	£45.00	£33.00
ROSEDALE each	£65.00	£50.00
UNIT 3 each	£12.50	£9.50
UNIT 4 each	£18.00	£12.50
UNIT 5 each	£26.00	£18.50

LASKY'S DIGITAL CLOCK



The clock measures 4½ W x 4½ H x 3½ D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V, 3A. Complete with instructions. Hundreds of applications: Complete with knobs. Features: ● Mains operation ● 12-hour alarm ● Auto "sleep" switch ● Hours, minutes and seconds read-off ● Forward and backward time adjustment ● Silent operation ● Shock and vibration proof ● Built-in alarm buzzer SPECIAL QUOTES LASKY'S PRICE **£6.50** C. & P. 25p FOR QUANTITIES

BSR TD8S

8-TRACK STEREO CARTRIDGE PLAYER



The unit is switched on and off by the insertion of the cartridge. The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mW. Power requirements: 210/250V a.c., 50Hz. Frequency response: 50Hz-10kHz. 4 pole dynamically balanced synchronous motor maintains unwavering speed accuracy—Independent of mains fluctuations. Compact in size the TD8S is housed in black and woodgrain plastic cabinet. Size 8½ (W) x 3½ (H) 10½ (D) in. LASKY'S PRICE **£17.95** List Price £24.20

BELTEK C5700

8-TRACK

Stereo Car Player



Accepts all standard pre-recorded 8-track stereo cartridges. Other features include automatic head cleaner, channel select and channel repeat push buttons, slider type volume and tone controls, channel balance control. Tech. spec. max. output 10W (5 watts per channel), frequency response 50Hz-10kHz. Output imp. 4 ohms. Size 4½ (W) x 1½ (H) 6½ (D) in. Operates on 12V d.c. negative earth systems. Beautifully styled with black, ivory and chrome trim finish.

BELTEK C5700 complete with mounting brackets and 8-track pre-recorded demonstration cartridge. **£19.75** C. & P. 30p

BELTEK C5700 with pair SP24 speakers. **£24.95** C. & P. 30p

Beltek SP24 speakers are available perfectly matching the C5700 in performance and finish—specially designed for optimum performance in heavily damped car interior. Size: 7½in. (W) x 6in. (D) 4½in. rear, 2½in. front (H). Comp. with leads. **£5.95** pair. C. & P. 30p

TM-1 TEST METER

1,000 ohms/volt

Lasky's new look top value TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to +3% of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case with white and metallic red/green figuring. Ohms zero adjustment. 1,000's IN USE. SIZE ONLY 2½ x 3½ x 1½ in. ● DC/V: 0-10-50-250-1000 at 1K/ohms/V. ● AC/V: 0-10-50-250-1000 at 1K/ohms/V. ● DC Current: 0-1mA, 100mA. ● Resistance: 0-150K/ohms. ● Decibels: -10 + 22dB. ● Complete with test leads.



LASKY'S PRICE **£1.85** C. & P. 15p

TM-5 TEST METER

5,000 ohms/volt

Another pocket multimeter from Lasky's. The "slimline" impact resistant case—size 4½ x 2½ x 1½ in. fitted with extra large 2½in. square meter. Readability is superior on all low ranges, making this an excellent instrument for servicing transistorised equipment. Zero ohms adjustment. Buff finish with crystal clear meter cover. ● DC/V: 3-15-150-300-1200 at 5K/ohms/V. ● AC/V: 6-30-300-600 at 2.5K/ohms/V. ● DC Current: 0-300µA, 0-300mA. ● Resistance: 0-10K/ohms, 0-1M/ohms. ● Decibels: -10dB to 16dB. ● Complete with test leads, battery and instructions.



LASKY'S PRICE **£2.55** C. & P. 35p

BSR McDONALD MP60

High precision low-mass counter-pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.



LASKY'S PRICE **£10.95** C. & P. 50p

BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Complete wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
MP60	10.95	15.50	18.50	18.75	22.00
HT70	15.90	19.90	23.50	23.75	27.00
610	14.50	18.75	23.00	22.25	25.50
510	12.10	16.50	18.85	20.00	22.85
310	9.75	14.00	16.50	17.25	20.25

210 complete with plinth, cover and BSR cartridge. **£9.95**
MP60 TPD2 styrene base **17.50 21.00**

FANTAVOX CAR RADIO

W1/700 MW/LW



A new two waveband all transistor car radio that covers full medium and long wavebands with slide switch wave change. Large easy to grip controls. Illuminated dial with "easy to read" lining scale. Externally adjustable aerial trimmer ensures maximum output. Powerful output stage gives perfect reproduction through either one or two speakers. Operates on all 12 volt D.C. systems. Negative or positive earth. Standard size 6½ in. (W) x 4½ in. (D) 2 in. (H). Black with chrome trim. Complete with speaker, baffle, leads, mounting brackets and instructions. Fully guaranteed.

LASKY'S PRICE **£7.50** C. & P. 25p

TAPE SCOOP

EMI 2,400ft Professional Tape on 10½in metal NAB spools. Fully guaranteed brand new. Today's value over **£5.00** each.

£1.25 each **5 for £5.00** C. & P. each 20p. 5 for 50p

SONY TV SCOOP

TV-730UK—the world in 7in

This miniature portable TV can be operated by household currents, rechargeable power pack or 12V car/boat battery. The special anti-glare screen gives a perfect picture even in sunlight. Brief Spec. ● Screen size 7in. measured diagonally. ● System: 625 UHF. ● Antenna system: Built-in loop aerial. External 300 and 75 ohm switchable. ● 23 transistors, 15 diodes, 3 thermistors, 1 EHT rectifier (selenium). ● Power source: AC 240V, 50Hz; DC 12V. ● Power consumption: AC17W, DC11W. ● Dimensions: 9in. x 9½in. x 11½in. ● Weight: 8lb. 13oz. ● Accessories: Earphone; loop aerial; polishing cloth.



List Price **£59.75** C. & P. £1.50 LASKY'S PRICE **£42.00**

CAR RADIOS FROM PHILIPS

MODEL RN 214/15

The RN214 is a triumph of micro-miniaturisation. So compact and light, mounted on its spindles only, it needs no real support. The RN214 can be fixed quickly and easily. Spec.: Power supply: 13 volt D.C. negative earth operation only. Power output: 5 watts. Wave ranges: Medium wave: 185m-585m (1622-512kHz). Long wave: 1030m-2000m (290-150kHz). Intermediate frequency: 470kHz. Size: 7in. x 6in. x 3½in. EN8893/05 general purpose mounting kit with loudspeaker **£2.70** extra.



List Price **£19.25** LASKY'S PRICE **£15.50** C. & P. 25p


MODEL RN 314/15

The RN314 gives you big sound because of the high sensitivity from the tuned RF stage. Due to its compact size it can be mounted without any rear support. Spec.: Power supply: 12V D.C. neg. earth only. Power output: 5 watts RMS. Wave ranges: Medium: 185m-585m (1622-512kHz); Long: 1030m-2000m (290-150kHz). Intermediate frequency: 170kHz. Size: 7in. x 6in. x 1½in. EN8893/05 general purpose mounting kit with loudspeaker **£2.70** extra. LASKY'S PRICE **£21.00** C. & P. 25p



BARGAIN SCOOP

High quality transistorised and ultra compact Shortwave Converter for use with any suitable MW (AM) Car Radio. Self-powered for use on 12V positive or negative earth systems. The model 2649 is simply connected to the radio via the aerial socket and provides shortwave coverage in 9 push-button selected band spread ranges (13, 16, 19, 25, 31, 41, 49, 60 & 90 MHz) combined with the normal radio tuning to give full coverage from 3.2MHz-21.75MHz. On/off switch and by-pass switch for normal M.W. radio use. Complete with mounting bracket fitting and alignment instructions. Black hammer crackle finished case—size: 6(W) 1½(H) x 3½(D) in. Made to sell at approx. **£20**.

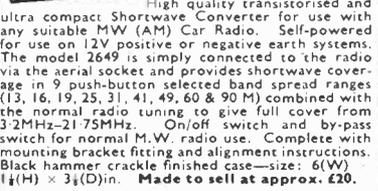

LASKY'S PRICE **£8.75** C. & P. 20p

OUT NOW! 1972

AUDIO-TRONICS NEW REVISED EDITION

The great new 1972 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1,000's of items for the Radio and Hi-Fi enthusiasts, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and don't miss LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday


ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST. TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821



READY-BUILT?—OR D.I.Y? SAXON ENTERTAINMENTS HAVE IT!!

STANDARD & CUSTOM BUILT SOUND EQUIPMENT

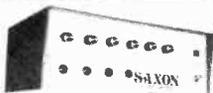100 WATT FULL RANGE AMPLIFIER £48.50 carr. free



100 Watt RMS for all musical and P.A. applications
 * FOUR individually mixed high impedance inputs
 * 20Hz-20,000Hz response
 * FULLY short and open circuit proof
 * 8ohm load for full output
 * Four 15 amp output transistors—all silicon
 IDEAL FOR GROUPS—DISCOTHEQUES—CLUBS, ETC.
 FULL 12 MONTHS GUARANTEE.

50 WATT VERSION Identical to above but 50 Watt output
£37.75

GOODMANS 12P 50W 8 or 15ohm
 £12.37 (rec. R.P.). **Our Price £10.90**
HUGE DISCOUNTS ON CRESCENDO'S

SUPER HIGH EFFICIENCY 20,000 GAUSS
 MAGNET (state impedance required)



(rec. R.P.) **Our Price**
 12in 100 Watt RMS £28.75 £21.50
 15in 100 Watt RMS £35.90 £26.80
 18in 150 Watt RMS £45.90 £36.75
 Larger discounts for quantities

MUSICAL INSTRUMENTS NEW & SECONDHAND

100 WATT MODULE



- * Fibre-glass p.c. board
- * All silicon transistors
- * Short/open circuit proof
- * 8ohms load for 100 Watt

Needs only power supply components—input sensitivity 200mV 10k.

£13.50 + 20p carr.

IDEAL FOR YOUR CUSTOM BUILT SYSTEM.

Or complete with power supply and transformer. **£18.75 + 40p carr.**

20 WATT INTEGRATED MODULE



- * Two mixed inputs
- * Fibre-glass p.c. board
- * Baxandall treble and bass controls
- * All power supply components mounted less transformer


Excellent Value and Reliability for only **£8.60 + 20p carr.**

D.J.'s Fader unit with built-in Pre-fade listen and tone controls. This unit plus two decks makes an economical Disco-control panel **£6.50 + 20p carr.**

SAXON ENTERTAINMENTS
 327-331 WHITEHORSE ROAD
 WEST CROYDON CR0 2HS 01-684 6385

SAFEBLOC

of robust construction

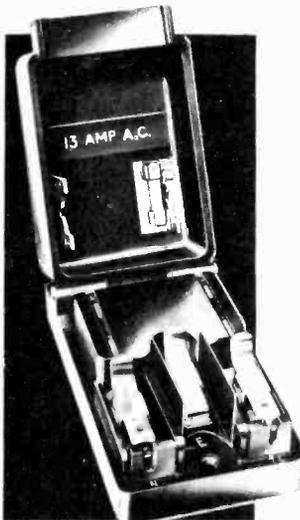

Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.

If ordering by post, send cash with order.

PRICE £2.60+10p P&P EACH

Special bulk order wholesale and industrial rates on application



RENDAR®

Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642

The most accurate
 pocket size
CALCULATOR
 in the world



The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4.50 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

CARBIC LTD. (Dept. PE 40)
 54 Dundonald Road, London SW19 3PH

FREE
 BOOKLET ON
 REQUEST

IN 15 MINUTES YOU COULD HAVE GUNTON ELECTRONIC IGNITION FITTED TO YOUR CAR

Capacitive Discharge Ignition is recognised as being the most efficient ignition system and will give you:

- CONTINUAL PEAK PERFORMANCE
- UP TO 20% REDUCED FUEL CONSUMPTION
- EASIER ALL-WEATHER STARTING
- INCREASED ACCELERATION & TOP SPEED
- LONGER SPARK PLUG LIFE
- INCREASED BATTERY LIFE
- CONTACT BURN ELIMINATED
- PURER EXHAUST GAS EMISSION
- RADIO INTERFERENCE SUPPRESSED



For all petrol engines cars, boats, etc. Guaranteed for 5 yrs.
 Complete Installation Kit for 12-volt vehicles **£9.95 + 35p P. & P.** State earth polarity of vehicle POSITIVE or NEGATIVE earth. Unit Construction Kit also available for the radio electronics constructor **£7.95 + 35p P. & P.** The construction kit includes instructions and all components for wiring as positive or negative earth, and is complete with the stove enamelled steel case and aluminium base. S.A.E. for leaflet, or call in for a demonstration.
P.E.'SCORPIO Components: Transformer and Mounting Kit **£1.85 + 25p P. & P.** Printed Circuit Board **60p + 10p P. & P.** Case and Hardware as above **75p + 20p P. & P.** **P.E. INVERTER TRANSFORMERS**, 20 watt **£1.85 + 25p P. & P.**

ELECTRONICS DESIGN ASSOCIATES 82 BATH STREET, WALSALL WS1 3DE

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK • OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

TYPE SW. 100 100 x 80 mm	TYPE S-80 80 mm square fronts
500μA \$3-20	50μA \$3-20
1mA \$3-10	50-0-50μA \$3-10
20V d.c. \$3-10	100μA \$3-10
50V d.c. \$3-10	100-0-100μA \$3-00
300V d.c. \$3-10	1mA \$3-00
1A d.c. \$3-10	100μA \$3-60
5A d.c. \$3-10	5A d.c. \$3-60
300V a.c. \$3-10	50V d.c. \$3-60
300V a.c. \$3-10	300V a.c. \$3-60
100-0-100μA \$3-35	VU Meter \$3-37

"SEW" CLEAR PLASTIC METERS

Type MR. 85P. 4 1/2in x 4 1/2in fronts.	Type MR. 83P. 1 21/32in square fronts.
50μA \$3-60	150mA \$1-60
50-0-50μA \$3-10	200mA \$1-60
100μA \$3-10	300mA \$1-60
100-0-100μA \$3-00	500mA \$1-60
200μA \$2-90	750mA \$1-60
500μA \$2-90	1A \$1-60
500-0-500μA \$2-80	2A \$1-60
1mA \$2-80	5A \$1-60
1-0-1mA \$2-80	10A \$1-60
5mA \$2-80	3V d.c. \$1-60
10mA \$2-80	10V d.c. \$1-60
	20V d.c. \$1-60
	50V d.c. \$1-60
	150V d.c. \$1-60
	300V d.c. \$1-60
	500V d.c. \$1-60
	15V a.c. \$1-60
	50V a.c. \$1-70
	150V a.c. \$1-70
	300V a.c. \$1-70
	500V a.c. \$1-70
	15A a.c.* \$2-80
	50A a.c.* \$2-80
	100A a.c.* \$2-80
	20A a.c.* \$2-80
	30A a.c.* \$2-80
	S Meter \$2-80
	VU Meter \$2-80

Type MR. 85P. 3in x 3 1/4in fronts.	Type MR. 45P. 2in square fronts.
50μA \$3-10	50μA \$2-25
50-0-50μA \$2-75	10V d.c. \$1-50
100μA \$2-75	20V d.c. \$1-50
100-0-100μA \$2-65	50V d.c. \$1-50
200μA \$2-65	300V d.c. \$1-50
500μA \$2-65	500V d.c. \$1-50
500-0-500μA \$2-50	15V a.c. \$1-80
1mA \$2-50	50V a.c. \$1-80
1-0-1mA \$2-50	150V a.c. \$1-80
5mA \$2-50	300V a.c. \$1-80
10V d.c. \$2-50	S Meter \$1-85
	1mA \$1-70
	VU Meter \$2-25
	1A a.c.* \$1-70
	5A a.c.* \$1-70
	10A a.c.* \$1-70
	20A a.c.* \$1-70
	30A a.c.* \$1-70
	S Meter \$1-70
	VU Meter \$1-70

"SEW" BAKELITE PANEL METERS

Type MR. 85 3 1/2in square fronts.

25μA \$3-50	100μA \$2-35
50-0-50μA \$2-37	100-0-100μA \$2-25
100μA \$2-35	500μA \$2-20
100-0-100μA \$2-25	1mA \$1-95
500μA \$2-20	1-0-1mA \$1-95
1mA \$1-95	5mA \$1-95
1-0-1mA \$1-95	50mA \$1-95
5mA \$1-95	100mA \$1-95
50mA \$1-95	
100mA \$1-95	
5V d.c. \$1-95	
20V d.c. \$1-95	
50V d.c. \$1-95	
150V d.c. \$1-95	
300V d.c. \$1-95	
50V a.c.* \$1-95	
150V a.c.* \$1-95	
300V a.c.* \$1-95	
500mA a.c.* \$1-95	
1A a.c.* \$1-95	
5A a.c.* \$1-95	
10A a.c.* \$1-95	
20A a.c.* \$1-95	
50A a.c.* \$1-95	
VU meter \$3-10	

*** MOVING IRON — ALL OTHERS MOVING COIL**
 Please add postage

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA \$4-00	20V d.c. \$4-40
100μA \$4-45	50V d.c. \$4-40
1mA \$4-40	300V d.c. \$4-40
50-0-50μA \$4-45	
1-0-1mA \$4-40	
1A d.c. \$4-40	
5A d.c. \$4-40	
10V d.c. \$4-40	

EDGEWISE METERS

PE.70 3 17/32in x 1 15/32in x 3/4in deep.

50μA \$3-10	500μA \$2-75
50-0-50μA \$3-00	1mA \$3-45
100μA \$3-00	300V a.c. \$3-45
100-0-100μA \$3-00	VU meter \$3-40
200μA \$3-00	

MULTIMETERS for EVERY purpose!

ROUND SCALE TYPE PENCIL TESTER MODEL TS.68

Completely portable, simple to use, pocket sized tester. Ranges 0/3/30/300V A.C. and DC at 2,000 ohms. Resistance 0-20K ohms. ONLY \$1.97. P. & P. 13p.

SKYWOOD SW-500

50 KΩ/Volt. Mirror scale DC Volts 0.5/1/2/3/30/300/600. AC Volts 3/30/300/600. DC Current 20mA/6/60/600mA. Resistance 10K/100 K/1Meg/10 Meg. Decibels -20 to +57dB. \$7.50. P. & P. 10p.

370 WTR MULTIMETER

Features AC current ranges. 20,000 o.p.v. 0/5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50μA/1/10/100mA/1/10 Amp DC. 0/100MA/1/10 Amp AC. 0/5K/50K/500K/5MEG/50MEG. -20 +82db. \$15. P. & P. 25p.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20c/s to 200 k/s on 4 bands. Square: 20c/s to 30 k/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. \$17.50. Carr. \$7.1p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120K/1.5-300Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$15. Carr. \$7.1p. Size 140 x 215 x 170 mm.

TO-3 PORTABLE OSCILLOSCOPE

3in tube. Y amp. Sensitivity 0.1V p-p/CM. Bandwidth 1-5 cps-5MHz. Input Imp. 2MegΩ 25pF. X amp. sensitivity 0.9V 800KHz. Input Imp. 2 megΩ 20pF. Time base, 5 ranges 10cps-300KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 13 1/2lb 220/240V a.c. Supplied brand new with handbook. \$40. Carr. \$9p.

240° WIDE ANGLE 1mA METERS

MW1-6 60mm square \$2.97. MW1-8 90mm square \$4.97. P. & P. extra.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. 6 Ranges ±1%. L1 μH - 1 1/1 HENRY'S. 6 Ranges -2%. C. 10pF ±11.10 nF d. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. \$20. P. & P. 25p.

230/240V S.M.T.H.S. SYNCHRONOUS MOTORS

Built in gearbox. All brand new and boxed. 60BPM CW; 30RPM CW; 2R/HR ACW; 2R/HR CW; 8R/DAY CW; 10RPM CW; 20R/HR ACW; 60p each. Post 12p

HIKOKI MODEL 780X 20,000 O.P.V.

Overhead protection. 5/25/100/500/1000V D.C. 10/50/250/1000V A.C. 30μA/250mA. 20K/2 meg ohm. -20 to + 62db. \$4.97. P. & P. 15p.

Model S-100TR MULTIMETER/TRANSISTOR TESTER

100,000 o.p.v. MIRROR SCALE/OVERLOAD PROTECTION

0/12/6/3/12/30 120/600 VDC. 0/6/30/120/600 VAC. 0/12/600A/12/300MA/12 AMP DC. 0/10K/1 MEG/100 MEG. -20 to +50 db. 0-0.1 - 2 MFD. Transistor tester measures Alpha, Beta and Ico. Complete with batteries, instructions and leads. \$18.50. P. & P. 25p.

TME MODEL TW-50K 46 RANGES, MIRROR SCALE, 50K/VOL. D.C. 5K/VOLT A.C. D.C.: Volts 125, 25, 125, 250, 5, 10, 25, 50, 125, 500, 1000V. A.C. Volts: 1 1/2, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50μA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +41.5dB. \$2-80. P. & P. 17 1/2p.

HT100BA MULTIMETER

Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection. 0/5/2.5/10/50/250/500/1000V D.C. 0/2.5/10/50/250/1000V A.C. 0/10/50μA/25/250/500MA/10 Amp D.C. 10AMP A.C. 0/20K/200K/2MEG/20MEG. -20 +82db. \$12-50. P. & P. 25p.

RUSSIAN 22 RANGE MULTIMETER Model U437, 10,000 o.p.v.

A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V. A.C. 2.5/10/50/250/500/1000V a.c. D.C. current 10mA/1/10/100mA/1A. Resistance 300 ohms/3/30/300KΩ/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OVR PRICE \$5-97. P. & P. 25p.

BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine Hz to 100KHz. Square 20c/s to 20KHz. Output max. +10dB (10kΩ). Operation 220/240V a.c. Size 215mm x 160mm x 120mm. Price \$27-50. Carr. \$2p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures v.d.c. but can be used to measure a wide range of a.c. and d.c. volt, current and ohms with optional plug-in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. No. of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V d.c. Input: Fully floating (3 poles). Input power: 110-230V a.c. 50/60 cycles. Overall size: 3 1/2in. x 2 1/8in. x 8 3/16in. AVAILABLE IN BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$49-97 1/2 Carr. \$9p

G. W. SMITH & CO (RADIO) LTD.
 Also see next two pages

SEMI-CONDUCTORS/VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415		2N5458		BC114		BFW90		NKT219		30p	
2G301	80p	2N3416	37p	2N5459	40p	BC115	15p	BFW91	20p	NKT223	27p		
2G302	80p	2N3417	37p	2N5460	40p	BC116	15p	BFX12	20p	NKT224	27p		
2G303	80p	2N3438	130p	2N5103	25p	BC118	15p	BFX13	20p	NKT225	27p		
2G304	80p	2N3439	130p	2N5104	25p	BC119	15p	BFX14	20p	NKT226	27p		
2G306	42p	2N3564	17p	2R3010	50p	BC121	20p	BFX20	25p	NKT237	25p		
2G308	30p	2N3565	15p	2R3012	50p	BC122	20p	BFX37	30p	NKT238	25p		
2G309	30p	2N3566	22p	2R3013	50p	BC125	15p	BFX44	37p	NKT240	27p		
2G371	15p	2N3568	25p	2R3014	50p	BC126	20p	BFX68	67p	NKT241	27p		
2G374	30p	2N3569	25p	2R3015	50p	BC134	12p	BFX84	25p	NKT242	20p		
2G381	22p	2N3570	122p	2R3016	50p	BC135	12p	BFX85	30p	NKT243	20p		
2N388A	40p	2N3572	27p	2R3017	50p	BC137	17p	BFX87	25p	NKT245	17p		
2N404	20p	2N3607	22p	2R3018	50p	BC138	15p	BFX88	20p	NKT261	20p		
2N696	15p	2N3608	22p	2R3019	50p	BC139	15p	BFX89	20p	NKT262	20p		
2N697	15p	2N3609	22p	2R3020	50p	BC140	15p	BFX89	20p	NKT263	20p		
2N698	25p	2N3638	18p	2R3021	50p	BC141	15p	BFX93A	70p	NKT264	20p		
2N699	30p	2N3638A	20p	2R3022	50p	BC147	10p	BFY11	42p	NKT271	20p		
2N706	12p	2N3641	18p	2R3023	50p	BC148	87p	BFY18	25p	NKT262	20p		
2N708A	12p	2N3642	18p	2R3024	50p	BC149	12p	BFY19	25p	NKT274	20p		
2N709	15p	2N3643	20p	2R3025	50p	BC152	17p	BFY21	42p	NKT275	20p		
2N709	62p	2N3644	25p	2R3026	50p	BC153	20p	BFY24	45p	NKT275	20p		
2N718	25p	2N3645	25p	2R3027	50p	BC154	20p	BFY29	40p	NKT281	27p		
2N718A	30p	2N3691	15p	2R3028	50p	BC157	15p	BFY30	40p	NKT401	87p		
2N726	30p	2N3692	18p	2R3029	50p	BC158	11p	BFY41	50p	NKT402	90p		
2N727	30p	2N3693	15p	2R3030	50p	BC159	35p	BFY43	82p	NKT403	75p		
2N914	17p	2N3694	18p	2R3031	50p	BC160	35p	BFY50	20p	NKT404	55p		
2N918	30p	2N3703	10p	2R3032	50p	BC167	20p	BFY59	25p	NKT405	75p		
2N929	22p	2N3704	11p	2R3033	50p	BC168B	10p	BFY52	20p	NKT406	82p		
2N930	20p	2N3705	10p	2R3034	50p	BC168C	11p	BFY53	15p	NKT451	62p		
2N987	40p	2N3706	9p	2R3035	50p	BC169B	11p	BFY56A	57p	NKT452	62p		
2N1060	22p	2N3707	11p	2R3036	50p	BC169C	12p	BFY76	42p	NKT453	47p		
2N1091	22p	2N3708	7p	2R3037	50p	BC170	12p	BFY77	57p	NKT173	20p		
2N1131	25p	2N3709	6p	2R3038	50p	BC171	20p	BFY80	65p	NKT174	20p		
2N1132	25p	2N3710	9p	2R3039	50p	BC172	20p	BFY81	65p	NKT174	20p		
2N1302	17p	2N3711	12p	2R3040	50p	BC173	20p	BFY82	20p	NKT173	20p		
2N1303	17p	2N3713	187p	2R3041	50p	BC178	20p	BFY82	20p	NKT173	20p		
2N1304	22p	2N3714	200p	2R3042	50p	BC179	20p	BFY82	20p	NKT173	20p		
2N1305	22p	2N3715	123p	2R3043	50p	BC182	10p	BFY82	20p	NKT173	20p		
2N1306	22p	2N3716	102p	2R3044	50p	BC182L	10p	BFY82	20p	NKT173	20p		
2N1307	22p	2N3717	102p	2R3045	50p	BC183	10p	BFY82	20p	NKT173	20p		
2N1308	22p	2N3719	208p	2R3046	50p	BC183L	9p	BFY82	20p	NKT173	20p		
2N1309	25p	2N3819	34p	2R3047	50p	BC184	11p	BFY82	20p	NKT173	20p		
2N1507	17p	2N3820	55p	2R3048	50p	BC184L	11p	BFY82	20p	NKT173	20p		
2N1613	20p	2N3823	50p	2R3049	50p	BC186	25p	BFY82	20p	NKT173	20p		
2N1631	35p	2N3854	27p	2R3050	50p	BC187	27p	BFY82	20p	NKT173	20p		
2N1632	30p	2N3854A	27p	2R3051	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1637	30p	2N3859	30p	2R3052	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1638	27p	2N3855A	30p	2R3053	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1639	27p	2N3856	30p	2R3054	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1701	162p	2N3856A	35p	2R3055	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1711	24p	2N3858	25p	2R3056	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1869	32p	2N3858A	30p	2R3057	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N1893	37p	2N3859	27p	2R3058	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2172	72p	2N3901	37p	2R3059	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2160	57p	2N3902	30p	2R3060	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2193	40p	2N3966	150p	2R3061	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2193A	42p	2N3967	40p	2R3062	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2194	27p	2N3977A	40p	2R3063	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2194A	30p	2N3990	37p	2R3064	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2217	72p	2N3990A	25p	2R3065	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2218	30p	2N3991	37p	2R3066	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2219	30p	2N3992	30p	2R3067	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2220	25p	2N3993	20p	2R3068	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2221	25p	2N3994	25p	2R3069	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2222	25p	2N3995	30p	2R3070	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2222A	25p	2N3996	25p	2R3071	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2222B	25p	2N4008	12p	2R3072	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2297	30p	2N4062	12p	2R3073	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2368	15p	2N4063	12p	2R3074	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2369	15p	2N4064	12p	2R3075	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2369A	15p	2N4065	12p	2R3076	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2410	42p	2N4244	47p	2R3077	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2483	27p	2N4248	15p	2R3078	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2484	32p	2N4249	15p	2R3079	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2539	22p	2N4250	15p	2R3080	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2540	22p	2N4251	15p	2R3081	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2613	35p	2N4252	15p	2R3082	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2614	30p	2N4253	15p	2R3083	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2644	40p	2N4254	15p	2R3084	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2711	25p	2N4255	15p	2R3085	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2712	25p	2N4256	15p	2R3086	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2713	25p	2N4257	15p	2R3087	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2714	30p	2N4258	17p	2R3088	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2904	20p	2N4259	17p	2R3089	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2904A	25p	2N4260	15p	2R3090	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2905	25p	2N4261	15p	2R3091	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2905A	25p	2N4262	15p	2R3092	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2906	25p	2N4263	15p	2R3093	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2906A	25p	2N4264	15p	2R3094	50p	BC187L	27p	BFY82	20p	NKT173	20p		
2N2907	25p	2N4265	15										

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!



RECORD DECKS

B.S.R.			
UA50 Mono	\$4-97		
C1291	\$6-50		
MP60	\$10-40	GOLDRING	
610	\$14-07	GL69/2	\$18-97
510	\$11-50	GL69/2/P	\$24-20
310	\$9-40	GL72	\$23-25
810	\$33-95	GL72/P	\$29-05
MP60 TPD1	\$17-12	GL75	\$23-83
MP60 TPD2	\$16-40	GL75/P	\$24-95
610 TPD1	\$20-35	LID75	\$3-83
510 TPD1	\$18-20	LID72	\$3-65
210 Package*	\$9-55	G99	\$19-30
HT70	\$14-99	GL85	\$48-50
HT70 Package	\$21-60	GL85P	\$54-30
GARRARD		LD85	\$4-60
2025TC*	\$8-50	G101	\$21-95
40B*	\$9-25	PIONEER	
5-300*	\$8-50	PL12AC	\$35-15
SP25 III	\$10-50	PL15C	\$20-25
SL65B	\$13-45	PLA25	\$22-85
AP76	\$18-95	THORENS	
AP76 with		TD125	\$57-85
G800*	\$22-50	TD125AB	\$91-15
SL72B	\$23-25	TX25	\$6-40
SL75B	\$26-00	TD150	\$27-90
SL95B	\$32-50	TD150A II	\$33-20
401	\$28-60	TD150AB II	\$37-80
ZERO 100A	\$41-65	TD150 Plinth	\$3-47
ZERO 100B	\$40-70	TX11	\$3-65

*Mono cart. *Stereo cart. All others less cartridge. Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied with cartridge ready wired in teak veneered plinth with cover.

Garrard 2025TC/9TAHCD	\$12-95
Garrard SP25 III/9TAHCD	\$15-95
Garrard SP25 III/G800	\$18-50
Garrard SP25 III/M73-6	\$19-50
Garrard SP25 III/M44-7	\$20-35
Garrard SP25 III/M55-E	\$22-30
Garrard SP25 III/G800 (Play on Plinth and Cover)	\$18-75
Garrard AP76/G800	\$29-50
Garrard AP76/M75-6	\$30-25
Garrard AP76/M55-E	\$32-95
Garrard AP76/M75-E	\$34-90
BSR McDonnell MP60/AT55	\$19-25
Golding GL72/G800	\$24-50
Golding GL75/G800	\$29-70
Golding GL75/G800E	\$44-15

Carriage 50p any item

SINCLAIR EQUIPMENT

Project 60 Package offers: 2 x Z30 amplifier, stereo 60 pre-amp, P25 power supply, \$15-95. Carr. 37p. Or with P26 power supply, \$18-00. Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, P28 power supply, \$20-25. Carr. 37p. Transformer for P28, \$2-97 extra. Add to any of the above \$4-45 for active filter unit and \$13-90 for pair of Q16 speakers. Project 60 FM Tuner \$18-95. Carr. 37p. New Project 605 \$20-97. Carr. 37p. All Sinclair products in stock. IC12 \$1-80. P. & P. 10p. 2,000 amplifier, \$23-50. Carr. 37p. 3000 Amplifier, \$30-95. Carr. 37p. Neoteric amplifier, \$48-95. Carr. 37p.

TAPE CASSETTES

Top quality in plastic library boxes.

C80	60 min.	30p.	3 for \$8p
C80	90 min.	42p.	3 for \$11-10
C120	120 min.	52p.	3 for \$11-35

Cassette Head Cleaner 30p. Post Extra.

LATEST CATALOGUE

SEND NOW—STILL ONLY 37p P. & P. 10p

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and containing thousands of items at bargain prices.

TELETON SAQ-206B STEREO AMPLIFIER

Latest exciting release. Beautifully styled with walnut case. 6 + 6 watts r.m.s. Switched inputs for Mag. Xtal, aux, tape. Incorporates volume, bass, treble, sliding balance, scratch filter and loudness controls. Our price \$18-50. Carr. 37p.

TELETON SPECIAL OFFER!

CRIOI AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR OF SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception, AFC, built-in MPX. Cer/XtAL Input. OTR PRICE \$22-50. Carr. 62p.

Also available with Garrard 2025TC Record Changer, Plinth, cover and stereo cartridge. Rarely wired \$35-50. Carr. £1.

LAFAYETTE LA. 324 STEREO AMPLIFIER 12.5 + 12.5 watt R.M.S. Mag/Cer/Tuner /Tap/Imp. Excellent performance.

Compares with amplifiers up to £40. OUR PRICE £24. Carr. 37p.

★ **TRANSISTORISED FM TUNER** ★ 6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6.4 x 4.2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 MHz. Ready built ready for use. Fantastic value for money. £6-37p. P. & P. 12p. Stereomultiplex adaptors £4-97p.

E.H.T. TESTER E-30KV

Completely self-contained with built-in voltmeter. Easy to read, very accurate, robust construction. An essential for colour television servicing, etc. Size 360mm long, 50mm dia. \$6-95. P. & P. 25p.

TEK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 28 ranges. Large 4in mirror scale. Size 3 1/2in x 4 1/2in x 2 1/2in. D.C. volts 0-2, 1,200V. A.C. volts 3-300V R.M.S. 6.0-500V P-P. D.C. current 0.12-12mA. Resistance up to 2,000 ohm. Decibels -20 to +51dB. Complete with leads/instructions. \$17-50. P. & P. 20p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand New. 3 sets of changeover contacts at 5 amp rating, 50p each. P. & P. 10p (100 lots £40). Quantities available.

HOMER INTERCOMS

Ideal for home, office, store, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station \$2-97, P. & P. 15p.
3 Station \$4-25, P. & P. 15p.
4 Station \$6-62, P. & P. 17p.

EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000Hz. 15 watt R.M.S. Available 8 or 15 ohms. \$7-50 each. P. & P. 37p.

Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000Hz. 8 watt R.M.S. Available 8 or 15 ohms. \$3-50 each. P. & P. 23p.

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft earpads, adjustable headband. Magnetic, impedance 600 ohms. \$1-97, P. & P. 15p.

MP7 MIXER PREAMPLIFIER

5 microphone inputs with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mic 1 x 3mV 50K, 2 x 3mV 600 ohms. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 520mV 100K. \$8-97. P. & P. 20p.

1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". \$2-25. P. & P. 10p.

SH55 STEREO HEADSET

Outstanding value. Soft earpads. Adjustable headband. 8-16 ohms. 29-50, 20,000Hz. Complete with cable and stereo jack plug. \$1-87. P. & P. 15p.

MCA. 220 AUTOMATIC VOLTAGE STABILISER

Input 220-250V a.c. or 176-230V a.c. Output 120V a.c. or 240V a.c. 200VA rating. \$11-97. Carr. 50p.

TE-16A Transistorised Signal Generator. 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2 x 5 1/2 x 3 1/2. Complete with instructions and leads. \$7-97. P. & P. 20p.

SPECIAL OFFER! SINCLAIR PROJECT STEREO FM TUNER



The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 87.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2µV. AFC range ± 200KHz. Signal to noise ratio: 66dB. Output voltage 2 x 150mV. Operating voltage 25-30V D.C. Size: 93 x 40 x 207mm. REC. LIST PRICE \$22.

OUR PRICE £16-95 P. & P. 25p
Unrepeatable offer—buy now and save over £8.

U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/1-5/7.5/30/60/150/300/600/900 VDC and 75mV. 0/1-5/7.5/30/60/150/300/600/900 VAC. 0/300mA/1.5/6/15/60/150/600MA/1-5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%, AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-50 plus P. & P. 25p.

FR8-2 PHOTO ELECTRIC RELAY

Inexpensive warning or counting system consisting of an exciter and relay unit. Relay unit has variable sensitivity control and automatic intermittent alarm operation. Exciter unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V A.C. Complete with cables and instructions. \$9-97. P. & P. 25p.

UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 55KHz-30MHz FET, 8 Meter. Variable BFO for SSB. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in x 4 1/2in x 7in. Brand new with instructions. £25. Carr. 37p.

LAFAYETTE HA-600 RECEIVER

General coverage 150-400KHz, 550KHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, S Meter, Bandspread. RF Gain. 15in x 9 1/2in x 8 1/2in. 18lb. 220/240V a.c. or 12V d.c. Brand new with instructions \$50. Carr. 50p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wear. Continuous rating. Wide range ex-stock Single hole fixing, 1/2in. dia. shafts. Bulk quantities available.

35 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms, 72p. P. & P. 7p.
50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, \$1-05. P. & P. 7p.
100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms, \$1-37. P. & P. 7p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS
Excellent quality • Low price • Immediate delivery

S-260 General Purpose Bench Mounting		S-260B Panel Mounting	
1A	\$7-00	1A	\$7-00
2-5A	\$8-05	2-5A	\$8-05
5A	\$11-75		
8A	\$15-90		
10A	\$22-50		
12A	\$23-60		
20A	\$49-00		

Please add postage

ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES. OUTPUT VARIABLE 0-260 VOLTS
Special discounts for quantity

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to—
11-12, Paddington Green,
London, W.2
Tel: 01-262 6562

MAIL ORDER DIVISION

THE POWER HOUSE

distronic LTD

28 BURNT MILL ELIZABETH WAY
HARLOW ESSEX HARLOW 32947

Why wait weeks?

—ALL OUR ORDERS
DISPATCHED BY
RETURN OF POST!

Transistors, Diodes
and Integrated Circuits

A) DIODES & RECTIFIERS	Price	Part No.	Price	Part No.	Price	Part No.	Price
IN914	5p	40411	£1.95	BC107	9p	BF159	35p
IN4148	5p	AC138	15p	BC108	9p	BF177	25p
IN4001	7p	AC141	20p	BC109	9p	BF178	30p
IN4002	8p	AC142	25p	BC113	14p	BF179C	25p
IN4003	9p	AC187K	15p	BC114	14p	BFX86	35p
IN4004	10p	AC188K	15p	BC115	14p	BFX87	37p
IN4005	12p	Matched		BC116A	14p	BFX88	25p
IN4006	14p	Pair	50p	BC117	30p	BFY34	30p
IN4007	20p	AC191	15p	BC125	19p	BFY50	19p
		AC192	15p	BC126	19p	BFY51	19p
		AC193	20p	BC132	20p	BFY52	19p
		AC193K	20p	BC134	20p	ME0404-1	10p
		AC194K	20p	BC137	30p	ME0404-2	10p
		Matched		BC142	35p	ME1001	10p
		Pair	60p	BC143	40p	ME1002	11p
		AC194	20p	BC144	35p	ME2001	10p
		AD142	50p	BC145	30p	ME3001	20p
		AD143	50p	BC147	9p	ME3002	25p
		AD262	35p	BC148	9p	ME4001	10p
		AF106	25p	BC149	9p	ME4002	11p
		AF109	35p			ME6001	15p
		AF139	31p			ME6002	18p
		AF166	20p			ME8001	20p
		AF170	18p			ME8003	30p
		AF200	25p			ME9001	15p
		AF201	30p			ME9002	15p
		AF239	45p			ME111	40p
		AF239S	45p			ME112	50p
		AL102	60p			MEU21	40p
		AL103	50p			MEU22	50p
		AL103	£1			OC25	60p
						OC28	60p
						OC35	48p

Compare our prices

WOOS 50V IA Bridge	40p
WO1 100V IA Bridge	45p
WO4 400V IA Bridge	48p

Send 10p for Price List or free with order

B) TRANSISTORS	Price	Part No.	Price	Part No.	Price	Part No.	Price
2N696	15p	BC153	30p	ME2001	10p	ME3001	20p
2N930	25p	BC154	35p	ME3002	25p	ME4001	10p
2N1613	22p	AL102	60p	ME4002	11p	ME6001	15p
2N1711	23p	AL103	50p	ME6002	18p	ME8001	20p
2N2369	15p	£1	£1	ME8003	30p	ME9001	15p
2N2484	30p			ME9002	15p	ME111	40p
2N2904	30p			ME112	50p	MEU21	40p
2N2904A	32p			MEU22	50p	OC25	60p
2N2905	36p			OC28	60p	OC35	48p
2N2905A	38p						
2N3053	17p	AU106	95p	BC212L	12p	709C (TO-5)	45p
2N3054	45p	AU107	70p	BC213L	12p	709C (DIP)	68p
2N3055	59p	AU108	65p	BC214L	12p	741C (TO-5)	68p
2N3442	£1.50	AU110	£1	BCY70	18p	741C (DIL)	68p
2N3638	25p	AU111	70p	BCY71	20p	TBA800 5W	68p
2N3866	£1.50	AUY21A	60p	BCY72	17p	Audio £1.50	
2N4347	£1.50	AUY22A	70p	BF152	25p		
2N4356	35p	AUY35	45p	BF153	25p		
		AUY37	60p	BF158	25p		

Component Discounts 10% on orders over £5

C) INTEGRATED CIRCUITS	Price
709C (TO-5)	45p
709C (DIP)	68p
741C (TO-5)	68p
741C (DIL)	68p
TBA800 5W	68p
Audio £1.50	

POSTAGE AND PACKING PLEASE ADD 10p TO YOUR ORDER

2N3055 115W 15A	59p	AD.142 80V 10A TO-3	50p
2N3053 IA TO-5	17p	AU103 155V, 10A TO-3	£1
BC107 also BC108 and BC109	9p	BC147/8/9 High gain LOCKFIT	9p
AF239 UHF, 5DB Noise factor at 800MHz	40p	40411 30A, 15V	£1.95
WO1 IA, 100V Bridge Rectifier	45p	BFY50, 51, 52	19p
AD262 PNP Matched BD162 NPN Pair 10W, Audio output pair	80p	NEW! TBA800 5W Audio IC	£1.50

THE ULTIMATE IN COMMUNICATIONS RECEIVERS

WORLD MASTER 8 WAVE BANDS + WORLD MAP & TIME ZONE DIAL

Brings INSTANT WORLD-WIDE RECEPTION at the press of a button. Sensational scoop purchase of this just-released model enables us to offer a truly advanced communications receiver at a previously unheard-of price! (Similar models can cost £120 or more!) The 8 WAVEBANDS enable you to cover the world at the press of a button. You might even pick up a world scoop on your world-wide receiver! As well as all the usual BBC Programmes you can pick up Local Radio Stations (including new stations yet to be introduced). *Pop Pirates, *Aircraft (control to pilot-pilot to control), *Shipping, *Taxis, *RAC, *AA, *Fire and Ambulances; even EAVESDROP ON BANK RAIDS IF YOU'RE LUCKY! *Continental and 100s more too numerous to list, from Australia, Africa, America, India, Europe. You'll get hour after hour of enjoyable listening on this superb receiver 24 hours a day—7 days a week. A complete hobby in itself. Enjoy the exciting cross-talk between control towers and airline pilots. Listen to the progress of an ambulance on its way to an accident—hear the deep-sea trawler captain's ship-to-ship and ship-to-shore conversations. PLUS many more exciting and absorbing Public Service Band transmissions we are not allowed to mention. This set has been manufactured by one of the most advanced companies in radio and electronic communications and carries their FULLY WRITTEN GUARANTEE. Attractively finished in Leatherette and stainless steel to add quality and distinction to any living-room. Completely portable using standard batteries (obtainable anywhere)—or can be plugged directly into mains. 14 Transistors, 9 diodes, 1 thermistor, internal ferrite rod antenna and external Telescopic Antenna. Tone, volume and tuning controls. Very latest keyboard push-button waveband selector. Dial light (enabling use in darkness). Special WORLD-WIDE DIAL and WORLD MAP enables you to tell the correct time in any country of the world (essential for long listening). Hi-fidelity earphone automatically cuts out main speaker when in use. Freqs.: Long Wave 150-350Kcs. Medium 535-1805Kcs. Marine 1.6-4.2Mc. Short Wave 4-12Mc. Short Wave 12-24Mc. FM/VHF 88-108Mc. AIRCRAFT 108-135Mc. PUBLIC SERVICE BANDS 135-174Mc.



CASH PRICE £35.50 +50p p. & p. or sent for £7.50 deposit and 50p p. & p. and 8 monthly payments of £5.60 (Total £41.10).

SCIENTIFIC AND TECHNICAL (PE5), 507-511 LONDON ROAD, WESTCLIFF, ESSEX

ERSIN Multicore SOLDER

5 SCORE SOLDER

for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

EASY-TO-USE DISPENSERS

Size 5 (Savbit) 18swg, 18p (illustrated)

Size 19A (60/40 alloy) 18swg, 18p

Size 15 (60/40 alloy) 22swg, 22p


BIB WIRE STRIPPER AND CUTTER

Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4&6BAspanner ends, ground cutting edges Price 32p. Also available, de Luxe Model 8. Price 58p.

NEW!

From Electrical and Hardware Shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

BUDGET HIGH-FIDELITY STEREO SYSTEMS

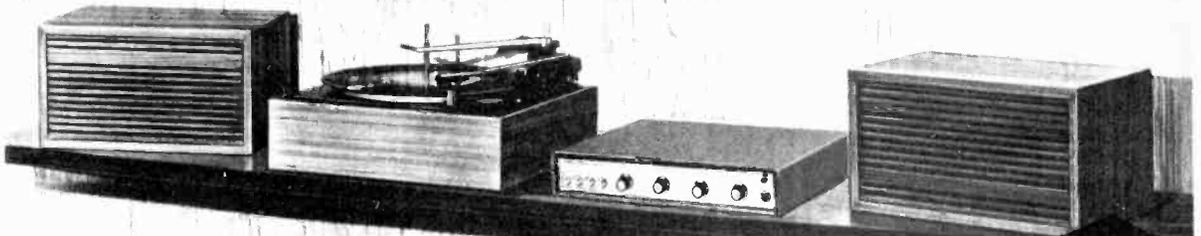

FREE
leads and plugs
supplied with all
systems

PREMIER STEREO SYSTEM "ONE" consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo/mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Headphone socket. Power on/off. Black leatherette cabinet with aluminium front panel. Size: 12 1/2in x 6in x 2 1/2in. (Amplifier available separately if required £18.25. Carr. 50p.)

PREMIER STEREO SYSTEM "TWO", as above but with Garrard SP25 Mk. III and magnetic cartridge **ONLY £48.** Carr. £1.75.

ONLY
£40-95
carr. £1.75

METER BARGAINS



MODEL GT800 MULTIMETER
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries.

Ranges: D.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). A.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). D.C. current: 1mA, 100mA. Resistance: 0-150 kohms. Decibels: -10 to +22dB (at A.C. 10V range). £2.47. P. & P. 25p



MULTIMETER 20,000 O.P.V. MULTIMETER
Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4 1/2in x 3 1/2in x 1 1/2in.

Ranges: D.C. voltages: 0-5-25-50-250-500-2,500V. A.C. voltages: 0-10-50-100-500-1,000V. D.C. current: 0-50µA-2.5mA-250mA. Resistance: 0-6,000 ohms, 0-6 meg ohms (300 ohms and 30 kohms at centre scale). Capacity: 10uf to 100uf, 100uf to 1uf. Decibels: -20 to +22dB. £4.90. P. & P. 25p



MODEL CT620 MULTIMETER
Ranges: D.C. voltages: 0, 5, 25, 100, 500, 1,000V (20,000 ohms/V). A.C. voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). D.C. current: 0, 50µA, 0mA, 5mA, 50mA, 500mA. Resistance: 0, 6kΩ, 600kΩ, 6MΩ, 60MΩ. Decibels: -20 to +62dB in 3 ranges. £5.62. P. & P. 25p



"WELLER EXPERT" SOLDER GUN
Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dial heat 100/140 watt. 240 volt A.C. £3.95 P. & P. 50p



"Weller Marksman" Soldering Iron
Lightweight, 3/4in pencil bit, 25 watt. 240 volt A.C. £1.50 P. & P. 16p



VERITAS V-313 TAPE HEAD DEFLUSER
A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds. £1.72. P. & P. 13p

PREMIER HI-FI OFFERS!

Rogers Ravensbrook 11 Stereo Amplifier in teak case (List £52.50) **£38.50**


Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49.00**

Metrosound ST20E Stereo Amplifier in teak case (List £39.50) **£28.50**

Thorens TD150A/11 Transcription unit with arm Garrard SP25 111 with Goldring G800 cartridge (List £28.35) **£31.00**

£15.50

SP25 Mk III SPECIAL!

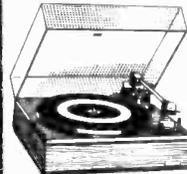

Garrard SP25 Mk. III Single Record Player. Fitted Goldring G800 Magnetic Stereo Cartridge. Complete in Teak Plinth with Cover.

Total list Price over £34.
PREMIER PRICE £18.90
P. & P. 50p

GARRARD AP78 WITH G800, READY WIRED TO 5-PIN DIN IN PLINTH WITH COVER £29.95


Garrard AP78 less cartridge **£19.50**

GARRARD 401 TRANSCRIPTION UNIT (LIST £40-15) £28.00

Garrard 2025 T/C with Stereo Ceramic Cartridge **£9.97**

Garrard 2025 T/C with Stereo Ceramic Cartridge ready wired in teak plinth with cover **£12.45**
Carriage and Insurance 60p extra any item.

PREMIER 800 STEREO AMPLIFIER

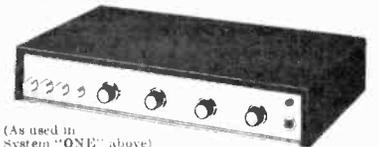

(As used in System "ONE" above)

A truly high quality stereo amplifier compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000Hz ± 2db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.V.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Stereo Headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12 1/2in x 6 1/2in x 2 1/2in **ONLY £16.25** Carr. 50p



HI-FI STEREO HEADPHONES
Designed to the highest possible standard. Fitted 2 1/2in speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft lead and stereo jack plug. **£2.47** P. & P. 25p

STEREO STETHOSCOPE SET Low imp. £1.25. P. & P. 10p
MONO STETHOSCOPE SET Low imp. 52p. P. & P. 10p

E.M.I. 13x8in. HI-FI SPEAKERS
Fitted two 2 1/2in tweeters and crossover network. Available with 8 or 16 ohm impedance. Handling capacity 10W. Brand new. **£3.47** P. & P. 50p

VERITAS V-49 MIXER
Battery operated 4-channel audio mixer providing four separate inputs. Size 6in x 3in x 2in suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phono plug output. Attractive teak wood grain finish case. Mono £3 Stereo £3.47 P. & P. 15p



TAPE CASSETTES
C60 (60 min.) 37p 3 for £1.05
C90 (90 min.) 62p 3 for £1.80
C120 (120 min.) 87p 3 for £2.55
P. & P. 5p

FREE Cassette Head Cleaner with every 10 cassettes
All cassettes can be supplied with library cases at 3p extra each.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped - attractively boxed.

LP3 3' 250' P.V.C.	28p	LP6 5 1/2' 1200' P.V.C.	75p
TT3 3' 450' POLYESTER	37p	DT6 5 1/2' 1800' POLYESTER	£1.12
DT3 3 1/2' 600' POLYESTER	57p	TT6 5 1/2' 2400' POLYESTER	£1.87
SP5 5' 600' P.V.C.	42p	SP7 7' 1200' P.V.C.	62p
LP5 5' 900' P.V.C.	50p	LP7 7' 1800' P.V.C.	75p
DT5 5' 1200' POLYESTER	75p	DT7 7' 2400' POLYESTER	£1.25
		TT7 7' 3600' POLYESTER	£2.50

TAPE SPOOLS 3' 5p, 5', 5 1/2', 7' 9p.
Post and Packing 3' 5p, 5', 5 1/2', 7' 10p. (3 reels and over Post Free.)



PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



Eavesdrop on the exciting world of Aircraft Communications—

V.H.F. AIRCRAFT BAND

CONVERTER ONLY £2-85

Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground, approach control, airport tower. Hear for yourself the disciplined noises hiding tenseness on talk down. Be with them when they take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard P3 battery. All you do is extend rod aerial, place close to an ordinary medium wave radio (even tiny portables) NO CONNECTIONS WHAT-EVER NEEDED. SEND ONLY £2-85 + 25p p & p for kit including case, nuts, screws, wire, etc. etc. (Parts available separately.)

SLEEP INDUCER
ONLY £3-25

Do you wake up in the night and can't get off to sleep again? Would you like to be gently soothed off to satisfying sleep every night? They build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing music. The loudspeaker sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. All transistor. No knowledge of electronics or radio needed. Step-by-step instructions. No soldering necessary. Kit includes case, nuts, wire, screws, etc. SEND £3-25 + 25p p & p. (Parts available separately.)

FIND BURIED TREASURE!

Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES, ETC. ETC. Extremely sensitive. Will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy-to-follow, step-by-step, fully illustrated instructions—uses standard P3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2-85 + 25p p & p. (Sectional handle as illustrated 95p extra.) Parts available separately. Made up looks worth £15!

SHORTWAVE TRANSISTOR RADIO
ONLY £2-75

Anyone from 9 years up can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 75 stations logged on rod aerial in 30 minutes—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses P3 battery. Size only 3in x 4in x 1 1/2in. Only £2-75 + 20p p & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately.)

BUILD 5 RADIO AND ELECTRONIC PROJECTS

ONLY £2-45

Amazing Radio Construction set! Become a radio expert for £2-45. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send £2-45 + 20p p & p.

ELECTRONIC ORGAN

ONLY £3-25

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Fully transistorised. SELF-CONTAINED LOUD-SPEAKER. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering necessary, simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions. ONLY £3-25 + 25p p & p for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHES YOUR NERVES! The RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. IF YOU WORK IN A NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard P3 batteries (current used so small that battery life is almost self-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components nuts, screws, wire, etc., no soldering. Send only £2-75 + 25p p & p. (Parts available separately.)

READY BUILT AND TESTED TREASURE LOCATOR MODULE

ONLY £4-95

FULLY TRANSISTORISED DETECTOR MODULE. Ready built and tested—just plug in a P3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! EXTREMELY SENSITIVE—PENETRATES EARTH, SAND, ROCK, WATER, ETC. EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! £4-95 + 30p carr. etc.

SLEEP INDUCER

ONLY £3-25

Do you wake up in the night and can't get off to sleep again? Would you like to be gently soothed off to satisfying sleep every night? They build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing music. The loudspeaker sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. All transistor. No knowledge of electronics or radio needed. Step-by-step instructions. No soldering necessary. Kit includes case, nuts, wire, screws, etc. SEND £3-25 + 25p p & p. (Parts available separately.)

SHORTWAVE TRANSISTOR RADIO

ONLY £2-75

Anyone from 9 years up can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 75 stations logged on rod aerial in 30 minutes—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses P3 battery. Size only 3in x 4in x 1 1/2in. Only £2-75 + 20p p & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately.)

CONCORD ELECTRONICS LTD. (PESU), 8 Westbourne Grove, London, W.2. Callers Welcome 9 a.m.-6 p.m. inc. Saturday

TRANSFORMERS

DOUGLAS GUARANTEED 12 or 24 Volts			
Output V. & Amps.	Ref. No.	Price P. & P.	
12V x 2 250 mA x 2	MT111 CS**	£0-91	9p
12V x 2 500 mA x 2	MT213 CT**	£0-97	13p
12V x 2 1A x 2	MT 71 AT	£1-48	24p
12V x 2 2A x 2	MT 18 AT	£2-04	30p
12V x 2 3A x 2	MT 70 AT	£2-59	32p
12V x 2 4A x 2	MT 68 AT	£2-82	33p
12V x 2 5A x 2	MT 72 AT	£3-33	34p
30 volts. All tapped at 0-12-15-20-24-30V			
Out-put Ref. No.	Price P. & P.	Out-put Ref. No.	Price P. & P.
500 mA MT 112 CT:	1-12 15p	3A MT 20 AT	£-04 32p
1A MT 79 AT:	1-55 29p	4A MT 21 AT	£-10 42p
2A MT 3 AT:	2-23 36p	5A MT 51 AT	£-31 42p
50 Volts. All tapped at 0-10-25-33-40-50V			
500 mA MT 102 AT:	1-45 24p	3A MT 105 AT	£-91 41p
1A MT 103 AT:	2-00 32p	4A MT 106 AT	£-98 41p
2A MT 104 AT:	£-10 32p	6A MT 107 AT	£-47 50p
60 Volts. All tapped at 0-24-30-40-48-60V			
500 mA MT 124 AT:	1-46 21p	2A MT 127 AT	£-31 41p
1A MT 126 AT:	£-24 28p	3A MT 125 AT	£-49 41p
AngUTO-WOUND RANGE			
Power output	Wind (tapped at)	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	£0-89 15p
75 VA		MT 64 AT	£1-72 30p
150 VA	0-115-200-220-240	MT 4 AT	£2-15 31p
200 VA		MT 65 AT	£2-00 32p
400 V. Output at 50 HZ.	Ref. ITS AT		Price P. & P.
C-D Ignition system by R. M. Marston Esq.			£2-25 29p
EQUIPMENT RANGE			
Sec. Output (r.m.s.)	Ref. No.	Price P. & P.	
3-0-3 V. 200 mA	MT 209 CS**	£0-91	8p
9-0-9 V. 100 mA	MT 13 CS**	£0-91	8p
12-0-12 50 mA	MT 210 CS**	£0-91	8p
20-0-20 30 mA	MT 211 CS**	£0-91	8p
0-20-20 300 mA x 2	MT 214 CT**	£1-21	14p
0-8-8 x 2 500 mA x 2	MT 207 CT**	£1-46	20p
0-15-20 x 2 500 mA x 2	MT 205 AT*	£2-12	23p
0-15-20 500 mA	MT 204 AT*	£2-45	29p
0-15-27 x 2 1A x 2	MT 204 AT*	£2-42	30p
10-12-10-12-20 700 mA (d.c.)	MT 221 AT*	£1-11	25p

AT Indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; * with interwinding screen; † untapped 240V Primary; ‡ Primary tapped at 210-240V; other Primaries tapped at 200-220-240V.
Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.
(Dept. MO. 54), Thames Street, LOUTH, Lincs.

U.H.F. TV AERIALS

SUITABLE FOR COLOUR & MONOCHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS
7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75.

WALL MOUNTING c/w WALL ARM AND BRACKET. 7 element £3-25. 11 element £3-75. 14 element £4-25. 18 element £4-75.

CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT. 7 element £4. 11 element £4-50. 14 element £4-75. 18 element £5-25.

MAST MOUNTING arrays only 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd.

KING TELEBOOSTERS from £3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7-50. State clearly channel number required on all orders. P. & P. on all aerials 50p accs. 15p. C.O.D. min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS
BBC (band 1) Wall S/D £2. LOFT inverted 'T' £1-25. EXTERNAL 'H' array only £3. ITV (band 3) 5 element 'loft' array £3-50. 7 element £3. COMBINED BBC-ITV left 1+5 £2-75. 1+7 £3-50. WALL AND CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from £3-75.

COMBINED U.H.F.-V.H.F. aerials 1+5+9 £4. 1+5+14 £4-50. 1+7+14 £5. F.M. RADIO loft S/D £1. 3 element £3-25. 4 element £3-50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p accs. 30p. C.O.D. min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS
40-41 Monarch Parade, London Rd. Mitcham, Surrey Telephone 01-648 4884

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

2 METRE CONVERTER KIT
9V Neg. earth feeding 28-30 MHz. Consisting of: RF BF180, Fet. mixer, crystal osc. BF180, and multiplier BF180. Complete with all components, instructions and aluminium box.
Not for beginners. Price £4-75 P. & P. 18p

TRANSISTOR EQUIVALENT BOOK
FEB 1971. 78 pages. 40p P. & P. 3p

RADIO and TV VALVE and TUBE EQUIVALENTS BOOK
JULY 1971. 60 pages, in CV types. 40p P. & P. 3p
Series 74N. Data booklet 14p Post Paid
930 Series. Data booklet 14p Post Paid
900, 914, 923. Data booklet 12p Post Paid

R.T.L. IC's
µL 900 Buffer, 40p; µL 914, 40p; µL 923, 45p. P. & P. 5p

LINEAR IC's
µA 703 45p (TO.5), µA 709 50p (DIL). P. & P. 5p

DUAL IN LINE SKTS.
14 pin, 25p; 16 pin, 30p. P. & P. 3p

AIRCRAFT BAND CONVERTER
Circuit and instructions and components. All you need is a tobacco tin. £1-20 P. & P. 7p

B.F.O. FOR ANY RADIO
Circuit and instructions and components. All you need is a tobacco tin. £1-05 P. & P. 5p

TAPE RECORDER LEVEL METERS.
500 micro amp. Size 50p P. & P. 5p
lin - lin - 3in

WE STOCK Numicator Tubes XN3 and GR 10/MU.
WE STOCK "Weco" Television Tubes.
CATALOGUE 5p POST FREE

**FOR
RAPID
SERVICE**

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

TRANSISTORS

AC127	17p	BFX29	38p
AC128	18p	BFX84	25p
AC176	24p	BFX88	30p
AC187	28p	BFY50	21p
AC188	27p	BFY51	21p
AC199	23p	BFY52	22p
AD149	47p	MAT100	25p
AD161/162	72p	MAT101	29p
ADT140	62p	MAT120	25p
AF118	45p	MAT121	29p
AF124	22p	OC28	58p
AF125	19p	OC35	48p
AF126	25p	OC44	12p
AF127	19p	OC45	11p
AF178	67p	OC71	12p
AF179	66p	OC72	12p
AF180	45p	OC75	20p
AF239	32p	OC200	27p
BC107	11p	OC201	38p
BC108	11p	OCP71	60p
BC109	11p	ST140	15p
BC147	12p	ST141	23p
BC148	12p	UT46	35p
BC149	12p	2N696	15p
BC157	15p	2N706A	12p
BC158	14p	2N2926G	14p
BC159	14p	2N2926Y	13p
BD131	75p	2N2936C	12p
BD132	75p	2N3053	25p
BF115	25p	2N3054	60p
BF178	32p	2N3055	72p
BF179	56p	2N3702	15p
BF180	30p	2N3703	14p
BF181	32p	2N3704	15p
BF184	30p	2N3705	14p
BF185	32p	2N3706	14p
BF194	14p	2N3711	14p
BF195	14p	2N3819	35p
BF196	28p	2N4058	17p
BF197	15p	2N5459	60p
BFV10	70p		

DIODES

AA119	11p	OA202	10p
OA47	7p	BY100	15p
OA50	7p	BY127	22p
OA91	6p	BY212	22p

ZENER DIODES

From 2 to 33 volts.
400mW, 15p; 1.5W, 22p

SILICON BRIDGE RECTIFIERS

40 P.I.V., 1.5A **50p**
200 P.I.V., 2.0A

FUSES AND HOLDERS

1 1/2in glass—2 1/2p
60, 100, 150, 250, 500, 750mA; 1, 1.25, 1.5, 2, 2.5, 3, 5, 7.5, 10, 15 amp.
1/2in glass—2 1/2p
100, 250, 500mA; 1, 2.5 amp.
Anti-surge 1 1/2in—8p
250, 500, 750, 850mA; 1, 1.5, 2, 3 amp.
Anti-surge 20mm—5p
80, 125, 200, 315, 400, 500, 630, 800mA; 1, 2 amp.

PANEL FUSEHOLDERS

For 1 1/2in fuses 18p
For 20mm fuses 15p

CONTROLS, Log. or Lin.

Single, less switch, 15p
Single, D.P. switch, 24p
Tandem, less switch, 40p
5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ

RESISTORS

Carbon
All 5%, high-stability, E12 values.
1/2W, 1p; 1W, 4p; 2W, 6p
Wire-wound
5W, 10p; 10W, 12p

ELECTROLYTICS

1μF	450V	19p	1,000μF	25V	27p
2μF	500V	20p	1,000μF	50V	39p
4μF	500V	14p	2,000μF	25V	36p
8μF	450V	16p	2,000μF	50V	53p
16μF	450V	17p	2,500μF	25V	45p
25μF	50V	8p	2,500μF	50V	60p
32μF	450V	24p	3,000μF	25V	48p
50μF	50V	10p	5,000μF	25V	55p
100μF	25V	10p	5,000μF	50V	98p
100μF	50V	10p	8-8μF	450V	18p
250μF	25V	12p	8-16μF	450V	20p
250μF	50V	17p	16-16μF	450V	27p
500μF	25V	18p	16-32μF	450V	63p
500μF	50V	25p	32-32μF	450V	49p
			50-50μF	350V	38p

MINIATURE ELECTROLYTICS

1μF	25V	10μF	64V
2 1/2μF	64V	16μF	40V
4μF	40V	25μF	25V
5μF	64V	30μF	15V
8μF	15V	50μF	15V
8μF	40V	100μF	15V
10μF	15V		

ALUMINIUM BOXES with lids and screws

Type	Length	Width	Depth	Price
GB7*	2 1/2in	5 1/2in	1 1/2in	38p
GB8*	4in	4in	1 1/2in	38p
GB9*	4in	2 1/2in	1 1/2in	38p
GB10*	4in	5 1/2in	1 1/2in	44p
GB11	4in	2 1/2in	2in	38p
GB12	3in	2in	1in	33p
GB13	6in	4in	2in	52p
GB14	7in	5in	2 1/2in	63p
GB15	8in	6in	3in	81p
GB16	10in	7in	3in	92p

* These sizes fit standard Veroboards

VEROBOARD

Size	0.1 matrix	0.15 matrix
2 1/2in x 3 1/2in	22p	16p
2 1/2in x 5in	24p	25p
3 1/2in x 3 1/2in	24p	25p
3 1/2in x 5in	27p	29p
1 7/8in x 2 1/2in	75p	57p
1 7/8in x 3 1/2in	£1	75p

Pins—both sizes: packet of 36, 18p

VARIABLE POWER SUPPLY

Input: 240V, a.c.
Output: Switched 3, 4.5, 6, 7.5, £4.20
9, 12 volts d.c. at 500mA

CASSETTE OWNERS!

For Philips and similar cassette recorders.
PU12 Power unit for connection to 12V + or - e.c. electrical systems, £3.25
giving 7 1/2V, stabilised output.
PP75 Mains power supply, output £1.95
7 1/2V d.c.
Both units are complete with cable and 5 pin D.I.N. plug

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18lin wide, 1in thick. The ideal lining for speaker enclosures. 25p per yard

MISCELLANEOUS ITEMS

B9A valve bases, 2p
5kΩ edge control, fits most small, imported radios, 7p
20Ω volume control for 3Ω speakers, 20p
Antex CN240, 15W miniature soldering iron, £1.70
Valve and Transistor Data book, 9th edition, 75p
Transistor equivalent book, BPI, 40p

LOW-OHM RESISTORS

2 1/2 watt wire-wound, 1Ω, 1.8Ω, 2.7Ω, 3.3Ω, 3.9Ω, 4.7Ω, 5.6Ω, 6.8Ω, 8.2Ω **11p**

CAPACITORS

2.2pF	500V	S/M	7p	0.0027μF	500V	S/M	15p
3.3pF	500V	S/M	7p	0.0033μF	500V	Cer.	5p
5pF	500V	S/M	7p	0.0033μF	1,000V	MDC	6p
10pF	125V	P.S.	5p	0.0036μF	500V	S/M	15p
10pF	500V	S/M	7p	0.0047μF	125V	P.S.	9p
15pF	125V	P.S.	5p	0.0047μF	500V	Poly.	6p
15pF	500V	Cer.	4p	0.0047μF	500V	S/M	20p
18pF	500V	S/M	7p	0.0047μF	1,000V	MDC	6p
22pF	125V	P.S.	5p	0.0051μF	100V	Mylar	3p
22pF	500V	S/M	7p	0.0051μF	500V	Cer.	5p
25pF	500V	S/M	7p	0.0068μF	125V	P.S.	10 1/2p
27pF	500V	Cer.	4p	0.0068μF	500V	S/M	30p
33pF	125V	P.S.	5p	0.0068μF	500V	Poly.	6p
33pF	500V	S/M	7p	0.0082μF	500V	S/M	10 1/2p
39pF	500V	S/M	7p	0.0082μF	500V	S/M	30p
47pF	125V	P.S.	5p	0.01μF	12V	Disc	4p
47pF	500V	Cer.	4p	0.01μF	125V	P.S.	10 1/2p
50pF	500V	S/M	7p	0.01μF	160V	Poly.	4p
56pF	500V	S/M	7p	0.01μF	250V	M.F.	3p
68pF	125V	P.S.	5p	0.01μF	400V	Poly.	3p
68pF	500V	S/M	7p	0.01μF	500V	Cer.	5p
75pF	500V	S/M	7p	0.01μF	500V	S/M	3p
82pF	500V	S/M	7p	0.01μF	600V	MDC	7p
100pF	125V	P.S.	5p	0.01μF	1,000V	MDC	9p
100pF	500V	S/M	7p	0.015μF	160V	Poly.	3p
100pF	500V	Cer.	5p	0.015μF	400V	Poly.	3p
120pF	500V	S/M	7p	0.02μF	100V	Mylar	3p
150pF	125V	P.S.	5p	0.022μF	18V	Disc	5p
150pF	500V	S/M	7p	0.022μF	250V	M.F.	3p
150pF	500V	Cer.	5p	0.022μF	400V	Poly.	3p
180pF	500V	S/M	7p	0.022μF	600V	MDC	7 1/2p
200pF	500V	S/M	7p	0.022μF	1,000V	MDC	9p
220pF	500V	P.S.	5p	0.033μF	250V	M.F.	4p
220pF	500V	Cer.	5p	0.033μF	400V	Poly.	4p
250pF	500V	S/M	8p	0.047μF	12V	Disc	6p
270pF	500V	Cer.	5p	0.047μF	160V	Poly.	3p
300pF	500V	S/M	10p	0.047μF	500V	S/M	3p
330pF	125V	P.S.	5p	0.047μF	400V	Poly.	4p
330pF	500V	S/M	8p	0.047μF	600V	MDC	8p
390pF	500V	S/M	8p	0.047μF	1,000V	MDC	10p
470pF	125V	P.S.	5p	0.1μF	30V	Disc	6p
470pF	750V	Disc	5p	0.1μF	250V	M.F.	4p
500pF	500V	S/M	8p	0.1μF	400V	Poly.	5p
560pF	500V	S/M	8p	0.1μF	500V	MDC	10p
680pF	125V	P.S.	5p	0.1μF	1,000V	MDC	13p
680pF	500V	S/M	8p	0.15μF	250V	M.F.	5p
820pF	500V	S/M	8p	0.22μF	160V	Poly.	6p
0.001μF	100V	Mylar	3p	0.22μF	250V	M.F.	5p
0.001μF	125V	P.S.	6p	0.22μF	400V	Foil	10p
0.001μF	400V	Poly.	3p	0.22μF	1,000V	MDC	15p
0.001μF	500V	S/M	10p	0.33μF	250V	M.F.	3p
0.001μF	500V	Cer.	5p	0.47μF	250V	Foil	8p
0.001μF	1,000V	MDC	6p	0.47μF	400V	Foil	15p
0.0015μF	400V	Poly.	3p	0.47μF	1,000V	MDC	20p
0.0015μF	500V	S/M	10p	1.0μF	250V	M.F.	15p
0.0015μF	500V	Cer.	5p				
0.0018μF	500V	S/M	10p				
0.002μF	100V	Mylar	3p				
0.002μF	500V	Cer.	5p				
0.0022μF	125V	P.S.	6p				
0.0022μF	500V	S/M	10p				
0.0022μF	1,000V	MDC	6p				

Note: S/M=silver mica 1% tol.
P.S.=polystyrene 2 1/2% tol.
MDC—a.c. rating=300V.
M.F.=Mullard min. foil.
Cer.=ceramic.

PLUGS




Car aerial
Co-axial
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 4 pin
D.I.N. 5 pin, 180
D.I.N. 5 pin, 240
D.I.N. 6 pin
Jack, 2 1/2mm unscreened
Jack, 2 1/2mm screened
Jack, 3 1/2mm unscreened
Jack, 3 1/2mm screened
Jack, 4 1/2mm unscreened
Jack, 4 1/2mm screened
Jack, stereo, unscreened
Jack, stereo, screened
Phono, plastic top
Phono, plated metal
Phono, fitted 4 ft lead
Wander, red or black
Banana 4mm, red or black



SOCKETS

Car aerial
Co-axial, surface
Co-axial, flush
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 5 pin, 180
D.I.N. 5 pin, 240
Jack, 2 1/2mm
Jack, 3 1/2mm
Jack, 4 1/2mm
Jack, 4 1/2mm unscreened
Jack, 4 1/2mm switched
Jack, stereo, switched
Phono, single
Phono, 2 on a strip
Phono, 3 on a strip
Phono, 4 on a strip
Wander, single, red or black
Wander, twin strip
Banana 4mm red, or black

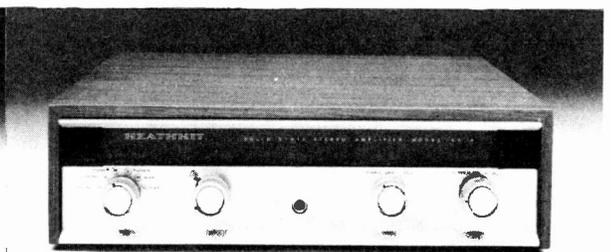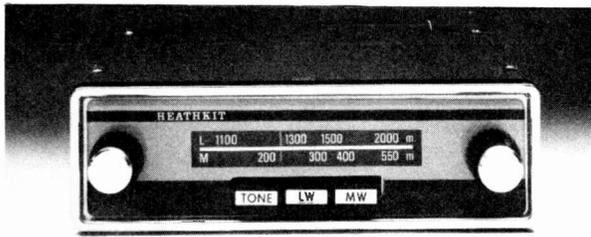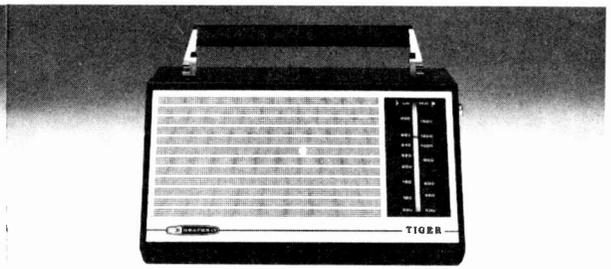MAIL ORDERS: C.W.O. only. Please include 10p P. & P. (Air mail extra). S.A.E. with all enquiries please. Telephone 01-692 4412



If you can use a soldering iron and follow simple instructions, you can assemble any of these high performance products in a few hours. And save a lot of money.

Heathkit have the world's widest range of top quality electronic products designed specifically for home assembly.

Of which we show just 4 above.

The AD110 is our new stereo cassette recorder. It gives you cassette convenience, reel performance and Heathkit quality. Designed to complement various other Heathkit Hi Fi products, it costs only £74.80 + £8.45 for twin matched stereo mikes.

Another new product, the Tiger transistor radio kit

costs £10.90. It gives long life from every large PP9 battery, weighs just 3 lbs, and gives really good reception on Long & Medium wavebands.



And, as you can see, it looks pretty good too.

Costing just £18.45 complete with speaker and aerial, the CR1 car radio gives unsurpassed reception. A 6 transistor, 2 diode circuit gives 4 watts output, pre-assembled and aligned tuning unit makes assembly easy, and push-button controls give instant selection.

The AA14 30 watt stereo amplifier is an established

product, proven in use by thousands of satisfied customers. Featuring a 17 transistor, 6 diode circuit, it costs £30.00 less cabinet.

These products and all the others in the Heathkit range are easily assembled by anyone who can use a soldering iron and follow our superbly clear, step-by-step instructions. Furthermore, in the unlikely event that you get stuck, we guarantee to help you out.

Find out more. Send for our free 1972 catalogue. Now.



You can make it if you try.

Please send me the FREE New 1972 Heathkit catalogue. PW05/72

Name

Address

HEATH (Gloucester) Ltd., Gloucester GL2 6EE



Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial D. BARRINGTON G. GODBOLD S. R. LEWIS B.Sc. (Eng.)
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY R. J. GOODMAN
Advertisement Manager D. W. B. TILLEARD

ESSENTIAL SERVICE

WITH commendable boldness and confidence in the future growth of telecommunications for domestic purposes, the Post Office is currently involved in the installation of a "communication main" system in the new city of Milton Keynes, now arising in Buckinghamshire. Every house in the new city will be linked to this communication system. The cables will, so far as possible, be laid in a communal trench, with the other essential services, water, gas, electricity, and drainage.

A standard telephone pair forms part of this "main". This cable is accompanied throughout, right up to every front door, by a high performance coaxial cable. Besides being capable of carrying radio and television signals, this wideband coaxial cable provides for the transmission of two-way signals such as could be employed to operate viewphones and computer data terminals, and permits the carrying out of other useful functions, like the remote reading of gas and electricity supply meters.

What happens in Milton Keynes *may* become the pattern for the future throughout the country. At any rate, this pioneer installation is worth noting and musing upon.

The advancement of computerised data techniques makes it fairly safe to conjecture that the day will come when every home will be able to have access to a wide range of data services, via sophisticated readout devices. But in the meanwhile, it would seem that further technical improvements are necessary, mainly to overcome the shortcomings of human operators, to make these advanced amenities fully acceptable to the general user.

At present, many people have a rather jaundiced view of computers, usually based upon their experience of incorrect statements of account issued by public supply authorities and other business concerns. The prevailing public mistrust of computerisation (however falsely based) does not provide the ideal climate for introducing more extensive and more complex computerised data systems; especially if these are to be linked directly with our homes to perform (above all!) such functions as the remote reading of domestic gas and electricity meters.

Elevation of the "communication main" to an essential domestic service status would certainly provide a great fillip to the electronics industry. It could herald another technological explosion making direct impact upon the domestic or "consumer" section. We don't doubt that fertile minds will seize eagerly the opportunity it promises for further imaginative and useful exploitation of electronics.

F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

ULTRASONIC TRANSMITTER—RECEIVER	374
SOLID STATE SNAP	392
FUZZ BOX	396
P.E. GEMINI STEREO TUNER	400

SPECIAL SERIES

ALPHA-NUMERIC DISPLAYS — 3	383
----------------------------	-----

GENERAL FEATURES

SMALL POWER TRANSFORMERS	404
INGENUITY UNLIMITED	417

NEWS AND COMMENT

EDITORIAL	373
SPACEWATCH	382
BOOK REVIEWS	388
ON THE FRINGE	391
ELECTRONORAMA	398
NEW BRIEFS	399
INDUSTRY NOTEBOOK	413
MARKET PLACE	414
PATENTS REVIEW	418
READOUT	421

SPECIAL DATA SHEET

SEMICONDUCTOR LEAD-OUT IDENTICHART

*Our June issue will be published on
Friday, May 12*

© IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65 (£2 13s. 0d).
Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

ULTRASONIC TRANSMITTER RECEIVER

By J. B. DANCE, M.Sc.

ONE might expect that it would be very expensive to generate and detect ultrasonic waves. However, this article shows that simple circuits can be used to construct a portable low-power system which has many applications for both the amateur and industrial user.


TRANSDUCERS

The transducers used with the circuits described in this article contain piezo-ceramic elements which resonate at the ultrasonic frequency to be employed. They are essentially like loudspeakers which operate at one particular narrow band of frequencies above the audible range and they are therefore given the same circuit symbol as a loudspeaker.

The equipment to be described employs two similar transducers, one in the transmitter and the other in the receiver. These two transducers must resonate approximately the same frequency, but they do not have to be specially selected so that they match one another in frequency.

The transducers chosen for the prototype equipment are the relatively new type 808-40 which operate at about 40kHz. When an electrical signal of about this frequency is applied to a transducer,

SOME TYPICAL
APPLICATIONS—

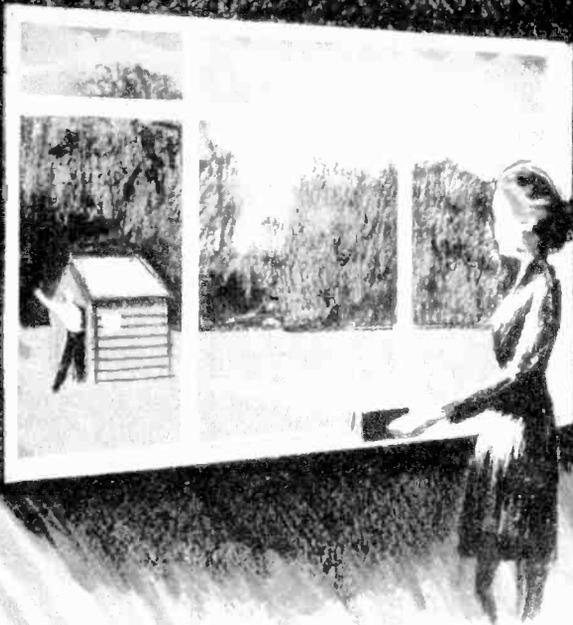

Ultrasonic waves of the same frequency are emitted through the small metal grille in the face of the transducer. If these waves fall on another transducer, a 40kHz electrical signal will be generated across the terminals of the second transducer. This signal may be amplified, rectified and used to operate a relay. The relay contacts can then be used to actuate any other type of device.

THE TRANSMITTER

The circuit of a simple transmitter which will generate an ultrasonic beam is shown in Fig. 1. It consists of a simple astable multivibrator which employs two low current *npn* silicon transistors.

The preset potentiometer, VR1, can be used to adjust the frequency of oscillation of the circuit so that it matches the resonant frequency of the transducer; maximum power output is then obtained from the unit. Details of the adjustment of this potentiometer will be discussed later.

The circuit shown applies a rectangular waveform of about 8.5V amplitude to the transducer. This is quite suitable for most applications, but the use of a higher supply voltage with suitable transistors in the same circuit will provide a greater power output

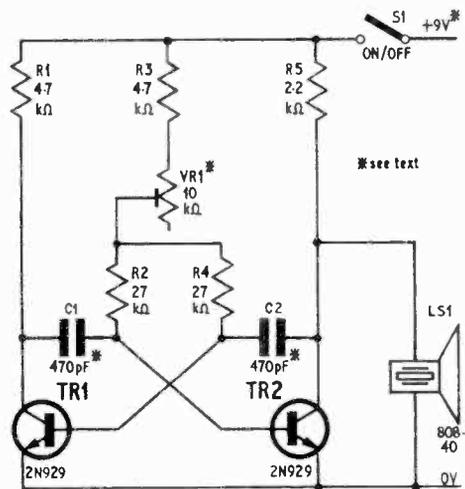


Fig. 1. Circuit diagram of the ultrasonic transmitter. The values of the components are those for a 40kHz transducer

* Intruder Alarm

* Remote Controller

* Signalling Systems

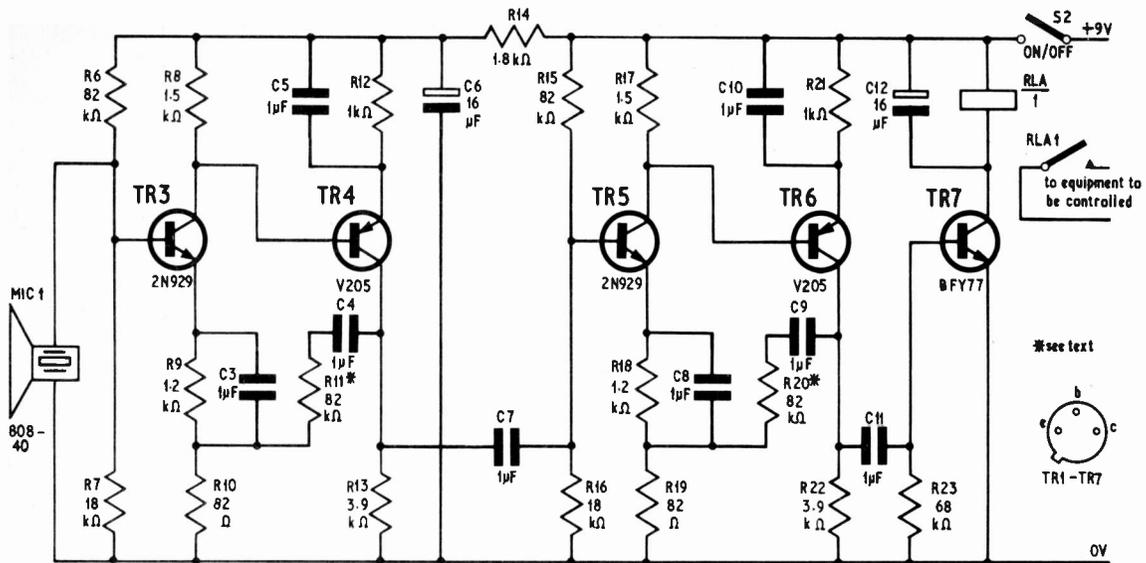


Fig. 2. Circuit diagram of the ultrasonic receiver. The values of the components marked with an asterisk can be altered if a reduced range is required

and therefore an increased range of operation. The maximum permissible voltage which can be applied to the "808" transducers is 20V r.m.s. with continuous operation or 30V r.m.s. under pulsed conditions.

The prototype took a current of 3.7mA from a 9V supply, but with an 18V supply the current was 7.5mA.

THE RECEIVER

The circuit of the receiver used in the prototype equipment is shown in Fig. 2. It is not necessary to employ a frequency selective amplifier, since the transducer itself will respond only to those ultrasonic frequencies which are near to its resonant frequency. The receiver is quite insensitive to loud audible noise.

The transducer converts the incoming energy into a signal which is amplified by transistors TR3 and TR4 in the first amplifier stage. The output from this circuit is coupled through C7 to a second similar amplifier stage containing TR5 and TR6. The output from TR6 is an alternating signal of the same frequency as the incoming ultrasonic waves. This signal is applied to the base of TR7 through C11.

Positive going parts of the signal drive TR7 into conduction and cause a current to pass through the reed relay coil in the collector circuit of this transistor. No bias is applied to TR7; the collector current of this transistor is therefore normally very small and it will be unaffected by negative going pulses applied to its base.

The circuit of TR7 thus acts as a rectifier or demodulator of the amplified 40kHz signal. When ultrasonic energy falls on the receiver transducer, the rectified current passes through the relay coil and TR7. If the intensity of the ultrasonic waves exceeds a certain limiting value, this current is great enough to cause the relay to close. The value of the limiting intensity is set by the sensitivity of the transducer, the gain of the two amplifier stages, the current gain of TR7 and the relay sensitivity.

FEEDBACK RESISTORS

The gain of each amplifier stage is determined by the current gain of the two transistors used and by the value of the feedback resistor (R11 or R20). If a value of 82 kilohms is employed for each of these feedback resistors, the amplification obtained with high gain transistors will approach the maximum which can be obtained with stability.

Lower values, such as 27 kilohms, can be used if the transmitter and receiver are to be used with a maximum separation of some 10 to 15 feet. Indeed, if the units are to be placed fairly close together, a lower value of feedback resistor may be necessary to prevent the operation of the relay by stray scattered radiation from the transmitter.

When no ultrasonic energy was incident upon the transducer in the receiver, the first two stages of amplification (TR3 to TR6) consumed a total of 2.4mA, whilst the current in the output transistor was very small. However, if the receiver transducer was placed very close to the transmitter transducer, the first two amplifier stages passed a total of 3.7mA, whilst the total receiver current increased to about 10.5mA.

COMPONENTS

Five *npn* and two *pnp* small signal silicon transistors are required. All of the transistors used in the receiver should have a fairly high current gain (at least about 50, but preferably over 100).

The *npn* transistors used in the prototype at first were the medium gain type 2N929, but many other types (such as those shown in the components list) are equally suitable. Similarly two medium gain *pnp* transistors type V205 were employed in the prototype, but other possible type numbers are given in the components list.

The medium gain transistors were subsequently replaced with transistors of a far higher gain (the *npn* type 2N2484 and the *pnp* type 2N2605) in order to carry out experiments on the maximum reliable

range of operation. The circuit worked well with both sets of transistors.

The two capacitors C1 and C2 in the transmitter may be mica or polystyrene types, but it is best to avoid the uses of ceramic types intended for decoupling applications in this position, since they may have a value of 50% or more above their marked value.

THE REED RELAY

The reed relay used in the prototype is fully encapsulated in a moulded outer case for use in the temperature range 0 to 70°C. The contacts close with 3.5V or less across the coil, so one may take 4.5V as being the minimum operating voltage in order to allow for tolerances or a low battery voltage.

It was found that the contacts of the CPR1/J closed at a current of 2.8mA and re-opened when the current fell to 1.8mA; this difference prevents the relay "chattering" when minor fluctuations take place in the ultrasonic beam intensity.

The CPR1/J has one pair of normally open contacts which can switch up to 10W of power to a device which does not require more than 200V nor more than 0.5A.

It should be noted that tungsten filament lamps have a much lower resistance when cold than when hot and therefore a relatively large current flows when they are first switched on. Thus relay contacts rated at 0.5A maximum should not be used to switch on a lamp rated at more than about 0.05 to 0.1A of normal running current unless a suitable thermistor is placed in series with the lamp to reduce the current surge at switch-on. Care should also be taken to suppress transient voltages or currents if the load is a reactive one, since the relay contacts may be damaged.

HIGHER POWER CONTROL

If it is necessary to control more power than the miniature reed relay in the receiver is capable of switching, it is only necessary to use the contacts of the reed relay to control the current to a larger relay in an auxiliary circuit. (It would also be possible to re-design the output stage of the receiver so that a suitable transistor is used to control a larger relay, but in this case more current would be taken from the receiver battery.)



CONSTRUCTION

The transmitter was constructed on a small piece of Veroboard as shown in Fig. 3.

In the case of the receiver board, see Fig. 4, it is obviously necessary to keep the input circuit well away from the output section, hence the layout follows the theoretical circuit fairly closely. The row of cuts down the centre of the board is to provide some isolation between the input and output stages.

It is not essential to place each of the units in metal boxes but some form of box will normally be used for convenience.

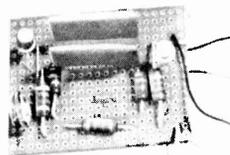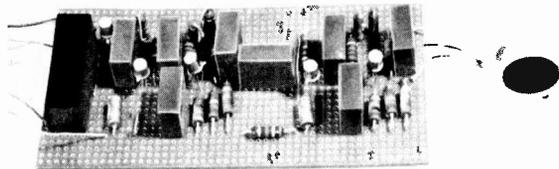The transmitter was placed in a diecast box together with a large battery. This enables the transmitter to be used for long periods without frequent replacement of the battery. If the transmitter is to be used in remote control applications where it will only be on for a few minutes a day, then a small battery (say a PP3) and hence a smaller box (e.g. a plastic torch case) will be more convenient.



The transmitter and receiver boards with the transducers before installation in their cases

STRAY PICKUP BY RECEIVER

If the receiver is not placed in a metal enclosure it has been found that about 0.5mA will pass through the relay even when the transmitter is not near. This is due to stray pickup by the high gain receiver circuit. Thus it is advisable to use a metal case with the negative line of the battery connected to the case. The quiescent current in the relay should then be very small. Incidentally the prototype receiver became unstable when the transducer was disconnected from the input even when a metal enclosure was used.

A flexible copper strip was used to hold the transducers in place. The holes in the lids of both units were made slightly smaller than the transducer so that some protection is given. Reasonable care should be taken when soldering to the transducers. It is important that the grounded pin of the transducer (shown by the adjacent metal tab) should be connected to the negative supply line; this is doubly important if a metal box is used as the transducer may be shorted out.

A small piece of foam rubber on the battery was found to be enough to hold the battery firmly when the lid is screwed down.

TESTING AND ADJUSTMENT

When the two units have been assembled, the system should be tested by placing the transducers in the two units face to face and close together. The relay in the receiver should close when both units are switched on. If it does not do so, the potentiometer VR1 should be adjusted (fairly coarsely) until the relay closes. (An ohm-meter may be connected to the relay contacts to ascertain when they close.)

If the relay still will not operate, some tests of the following type may be carried out in order to localise the fault. The transmitter unit may be tested by disconnecting the output of the circuit from the transducer and feeding this output to an a.c. voltmeter (or, preferably, an oscilloscope).

If it is found that the transmitter circuit is working, the negative power supply lines of the two units may be joined and C11 disconnected from TR6. If the output from the collector of TR2 is fed to C11

(and hence to TR7), the relay should close when both units are switched on; in this case the transmitter circuit and the output circuit of the receiver are satisfactory.

With the negative power supply lines still connected, the output from TR2 may be fed through a $0.01\mu\text{F}$ capacitor to the junction of C7 and R16; if the relay closes, the circuits of TR5, TR6 and TR7 are probably satisfactory.

If the whole receiver is functioning, the relay will close if the input wire is held between the fingers.

TRANSMITTER ADJUSTMENTS

The adjustment of the potentiometer in the transmitter is carried out more easily if a 0 to 10mA meter is connected in series with the relay coil. The transmitter and receiver should be separated and/or the transducers placed at an angle to one another so that a reading of 1 to 3mA is obtained. The potentiometer should then be adjusted so that the meter reading increases.

If necessary the units should be separated further to keep the meter current at 1 to 3mA and the potentiometer again adjusted for maximum sensitivity. Finally the transmitter should be switched off and then on again to check that the oscillator starts to function at the chosen potentiometer setting. If it does not do so, a small adjustment of the potentiometer should be made towards a lower resistance value.

OPERATING RANGE

When medium gain transistors were employed in the prototype and the value of the feedback resistors were both 82 kilohms, it was found that the maximum distance for reliable operation was some 15 feet in the open air. However, this distance was increased to some 45 feet in the open when using transistors of higher gain.

If the equipment is used in a room or in a corridor, it is found that the range of reliable operation is considerably increased. This is mainly accounted for by reflections of ultrasonic energy from the walls towards the receiver, but effects due to wind are normally avoided inside a building and this reduces random fluctuations of the current in the relay coil.

The maximum range of reliable operation inside a building may easily be double that in the open air, but much depends on the arrangement of the objects in the building and of the ability of the walls, etc. to reflect ultrasonic energy.

Still greater ranges may be obtained by applying a higher power supply voltage to the transmitter circuit provided that the transistors used in the transmitter are suitable. For example, the writer has found that an operating range of up to about 60 feet can be obtained in the open by using an 18V transmitter supply with the Fig. 1 circuit and transistors of moderately high gain in the receiver.

SHORT RANGE OPERATION

The writer has found that the first amplifier stage (TR3 and TR4) of the receiver may be omitted if the distance between the two units is to be very small. In this case C7 is disconnected from the base circuit of TR5 and the non-earthly lead of the transducer is connected to the junction of R15, R16 and the base of TR5. The decoupling components C6 and R14 can then also be omitted.

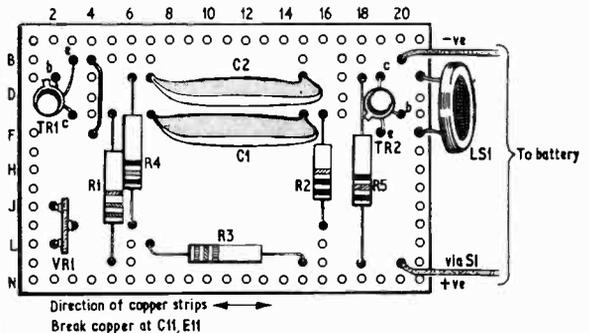
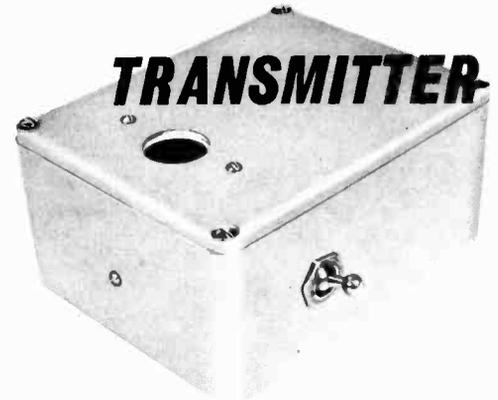


Fig. 3. Layout of the components on the transmitter board

COMPONENTS . . .

ULTRASONIC TRANSMITTER

Resistors

- R1 4.7k Ω
- R2 27k Ω
- R3 4.7k Ω
- R4 27k Ω
- R5 2.2k Ω
- All $\pm 10\%$, $\frac{1}{4}$ watt carbon

Potentiometers

- VR1 10k Ω miniature skeleton preset

Capacitors

- C1, C2 470pF silver mica or polystyrene

Transistors

- TR1, TR2 2N929 or any similar npn high gain, low current type (e.g. BC108, BC148, BC184L, BFY77, 2N2484, ZTX108, ZTX109) (2 off)

Transducer

- LS1 808-40 type 40kHz transducer (Hall Electronics, 48 Avondale Rd., Leyton, London, E.17) or Gulton type 1404 (from LST Components Ltd., Coptfold Road, Brentwood, Essex)

Miscellaneous

- S1 Single pole on/off switch
- 0.1in matrix Veroboard $2\frac{1}{2}$ in \times $1\frac{1}{2}$ in
- 9 volt battery
- $4\frac{1}{2}$ in \times $3\frac{1}{2}$ in \times 2in diecast metal box

RECEIVER

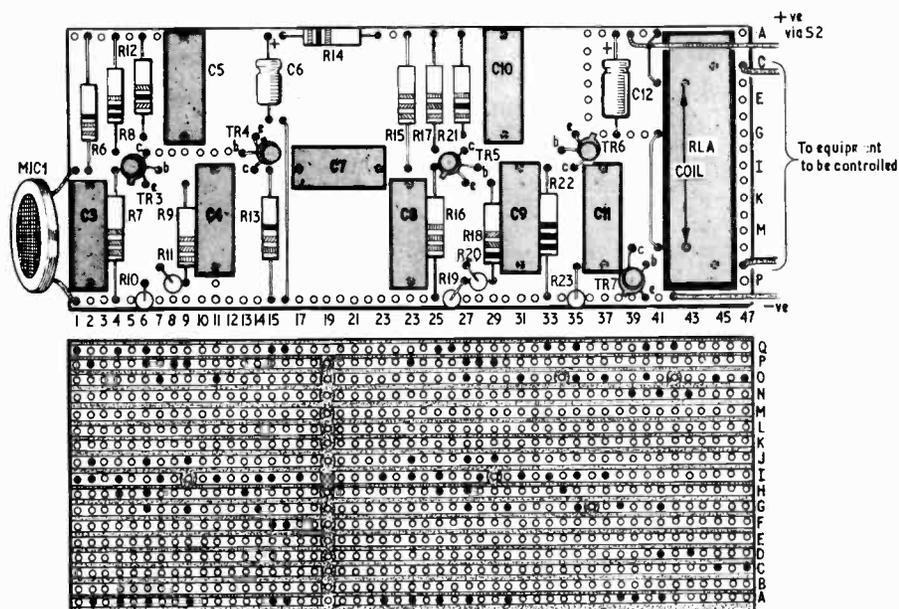
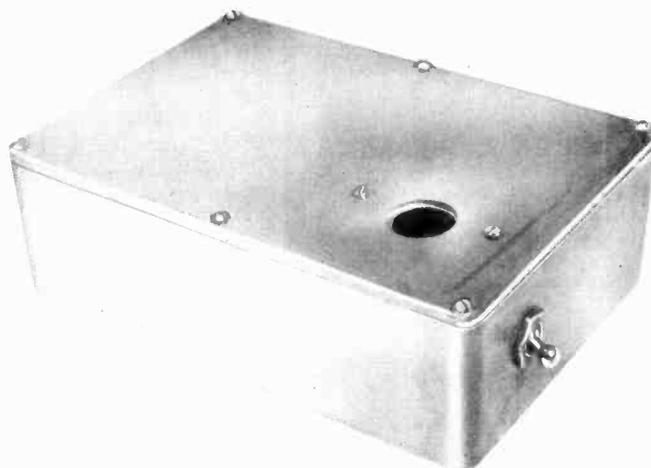


Fig. 4. Layout of the components on the receiver board

COMPONENTS . . .

ULTRASONIC RECEIVER

Resistors

R6	82k Ω	R15	82k Ω
R7	18k Ω	R16	18k Ω
R8	1.5k Ω	R17	1.5k Ω
R9	1.2k Ω	R18	1.2k Ω
R10	82 Ω	R19	82 Ω
R11	82k Ω	R20	82k Ω
R12	1k Ω	R21	1k Ω
R13	3.9k Ω	R22	3.9k Ω
R14	1.8k Ω	R23	68k Ω

All $\pm 10\%$, $\frac{1}{4}$ W carbon

Capacitors

- C3 to C5 1 μ F polyester (3 off)
- C6 16 μ F, electrolytic 10V
- C7 to C11 1 μ F polyester (5 off)
- C12 16 μ F electrolytic 10V

Transistors

- TR3, TR5 2N629 or similar (see TR1, TR2 in transmitter) (2 off)
- TR4, TR6 V205 or any similar *npn* high gain, low current type (e.g. BC158, BC214L, 2N2605, 2N3798, 2N3964, 2N4062, ZTX501, ZTX530) (2 off)
- TR7 BFY77 or similar high gain, low current *npn* type

Transducer

- MIC1 808-40 type 40kHz transducer

Miscellaneous

- RLA Reed relay close current 2.8mA at 3.5V. Type CPR1/J (Alma Components)
- S2 Single pole on/off switch
- 0.1in matrix Veroboard 4.8in \times 1.8in
- 9 volt battery
- 6 $\frac{3}{8}$ in \times 4 $\frac{1}{8}$ in \times 2 $\frac{1}{2}$ in diecast metal box

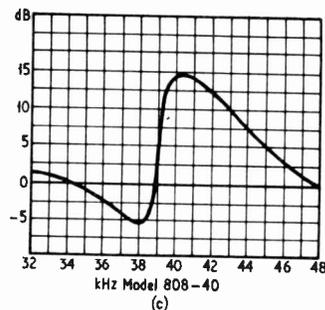
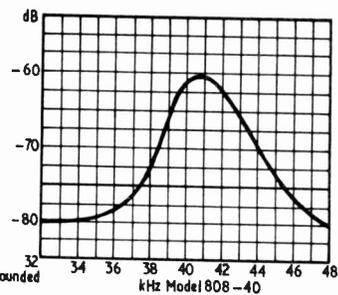
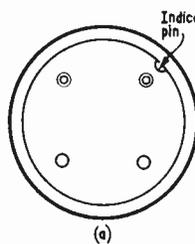
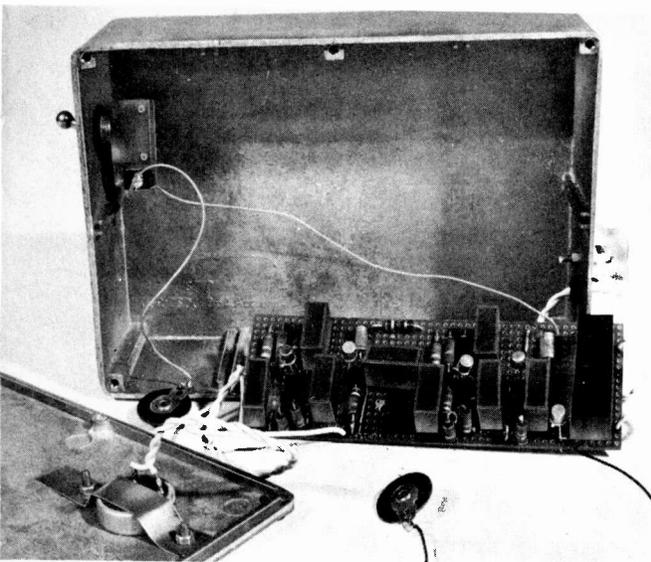


Fig. 5. The 808-40 transducer. (a) The metal tab indicates the grounded side of the transducer; (b) The acoustic response of the 808-40; (c) The electrical response of the 808-40

It was found that the maximum working range with such a simplified receiver is about 9 inches with medium gain transistors in the receiver and about 2 to 3 feet with high gain transistors.

If an 18V transmitter power supply is used, the maximum range is increased to 4 to 5 feet with the simplified receiver. It is assumed that readers will normally wish to construct the full receiver circuit of Fig. 2, since it is far more versatile than the simplified version.

Ultrasonic waves are much more directional than waves of audible sound, since they have a shorter wavelength. It has been found that if a receiver with high gain transistors is employed, the relay will close when a transmitter is placed almost anywhere in the same small room even if the two transducers are not facing one another. This is due to the reflection of waves from the walls of the room. When used in the open air, the transmitter and receiver can be placed quite close together without the relay closing, provided that the transducers do not face one another (nor nearly face one another).

TYPES OF TRANSDUCER

The circuits described in this article can also be used with the 1405 type of transducer for 40kHz operation, in which case standard phone plugs will be required as connectors for each transducer. However, the 808-40 transducer was chosen for the prototype, since it is smaller and of more recent design than the 1404 and has a somewhat greater sensitivity (about 6db) when used as a receiver. Thus the 1404 should be used only when a plug-in transducer is required.

If it is desired to work at a lower frequency, the type 808-25 transducers may be used for 25kHz operation. This type is similar to the 808-40, but the value of each of the capacitors in the transmitter circuit must be increased to about 820pF so that the oscillator can operate at the correct frequency. No other circuit changes are required for 25kHz operation. The beam is not so directional as a 40kHz beam.

The acoustic response (i.e. sensitivity as a receiver) of the 808-40 is shown in Fig. 5b, whilst the electrical response (i.e. output power when used as a transmitter) is shown in Fig. 5c. It can be seen that bandwidths of the order of 1kHz can be obtained.

APPLICATIONS

Ultrasonic systems can operate over greater distances than most photoelectric equipment and they have the advantage that their operation is unaffected by smoke or by dirt collecting on the transducers. In addition ultrasonic beams can detect transparent objects.


Although the range of ultrasonic equipment is less than that of radio control systems, no radio transmitting licence is required and the associated circuits are very simple. In general the ultrasonic beam will be found to be more directional than a radio beam but not so directional as the light or infra-red beam used in photoelectric equipment.

INTRUDER ALARM

Ultrasonic waves do not pass through people. If the beam from a transmitter is directed onto the receiver, the relay in the latter will close. However, when a person's body interrupts the beam, the relay will open and this can be used to sound an alarm.

This type of alarm has the same advantage as that of an infra-red alarm, namely that the intruder cannot sense the radiation from the transmitter. Such a system will give a warning if the transmitter or receiver is moved appreciably by the intruder, if either unit is switched off or if either battery is disconnected.

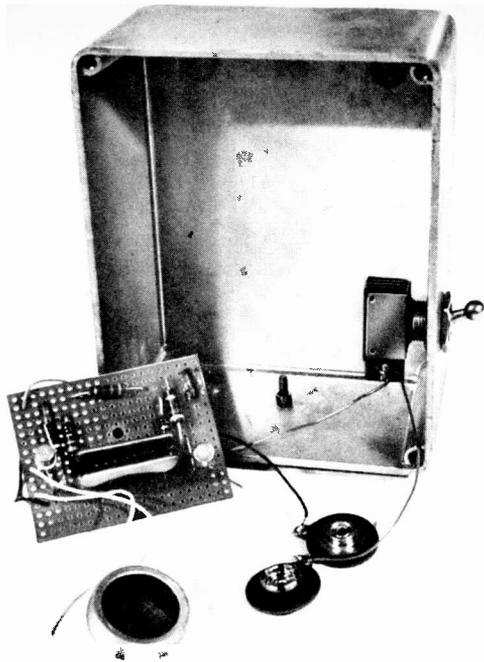In a practical intruder alarm of this type, the transmitter and receiver may be fairly close together. For example, the system may be used to monitor



a corridor. In such cases it may be necessary to use smaller values of the feedback resistors (R11 and R20) in the receiver circuit so that the sensitivity is insufficient for stray reflections from the walls to keep the relay closed when an intruder interrupts the main beam.

REMOTE CONTROL

In general the units described earlier can perform any remote switching operation over a distance within their operating range. The lazy man can use such a system to switch a radio or television receiver on and off without getting up from his chair.

The reed relay in the ultrasonic receiver can be used to operate a stepping switch which alternately switches the radio or television receiver on and off.

More complicated remote control applications can be devised for use in the home of the amateur experimenter. For example, one could have a receiver in a shed in the garden and use an ultrasonic beam to operate an aerial change over relay or any other device from the house.

A good practical man could mount a transmitter unit under the front bumper of his car and a receiver near to his garage door so that a pulse of the ultrasonic beam would cause the garage door to open automatically. When the motorist takes his car away next day, a similar pulse could be used to close the garage door after the car has been reversed out.

COMMUNICATION

If a morse key is connected in the power supply line of the transmitter, the equipment can be used for communication over short distances, for example, to a house across the other side of the road. The relay in the receiver could be used to control the current to an oscillator which produces the morse signal.

The bandwidth of the beam provided by the circuits described is too narrow for it to be possible to modulate this beam with speech, but it is presumably

possible to use more complex equipment operating at a high frequency to carry speech by means of an amplitude modulated ultrasonic wave. However, the range may be very limited.

RANGING

Ultrasonic systems can be used to measure the range of objects which are not too far away. The time taken for a pulse from the transmitter to travel to the object and to be reflected back to a second transducer near to the transmitter is a measure of the distance of the object. Ultrasonic beams are employed in this way in the aids used by blind people.

Although the prototype equipment has not been used for range finding, there appears to be no reason why the transmitter should not be pulsed with power and the time interval between the transmitted and reflected pulses measured with a digital counter.

LEAK TESTING

The simple transmitter and receiver described in this article can be used to detect holes or leaks in the rubber sealing of objects such as car bodies and refrigerators. The transmitter is placed in the object to be tested and the door is closed. A detector employing a milliammeter in series with the relay is moved around the edges of the doors, windows, etc. to detect any leakage of ultrasonic energy.

INDUSTRIAL APPLICATIONS

The receiver of Fig. 2 can be used without any transmitter for the detection of leaks in either pressure or vacuum pipes, since such leaks generate ultrasonic waves. Leaks can be detected in this way even in the presence of the loud noise and vibration often found in industrial plant.

Ultrasonic beams can be used to detect the presence of an object, such as an item passing along a production line. Each item can be made to interrupt the beam to produce electrical pulses which can be counted. Alternatively the ultrasonic beam may be reflected off each object in turn. The circuits of Figs. 1 and 2 are very suitable for this application.

EDUCATIONAL APPLICATIONS

Numerous experiments can be carried out with ultrasonic waves which are suitable for educational use. For example, one may investigate the transmission and reflection of the waves by various materials.

The writer used the transmitter and receiver (at fairly low gain) on a bench top with the transducers facing each other and separated by a distance of about two feet. When an object such as one's hand was moved slowly towards the mid-point of the two transducers, a milliammeter connected in series with the relay coil of the receiver showed rapid fluctuations in its reading according to the position of the reflecting object.

This is due to interference between the waves travelling directly from the transmitter to the receiver and those taking the longer path to the reflecting object and then to the receiver. Maximum intensity occurs at the receiver when these two path lengths differ by a whole number of wavelengths. An experiment could be devised to measure the wavelength of the radiation.





SOVIET AND AMERICAN CO-OPERATION

As a result of the co-operation in the exchange of samples of moon-dust from *Luna 16*, for *Apollo* samples, a considerable amount of new data has been obtained. It would appear that the dust forming the regolith at the landing site of *Luna 16* had not been disturbed for 3,000 million years. This site was in the Mare Fecunditatis and the dust shows an age (by radiation dating) nearly twice that of the dust recovered by *Apollo 11*. Some mechanism must exist for the transportation of dust if these measurements are reliable.

The specimens from the Soviet mission were from depths of 8cm and 28 to 32cm. There is evidence to indicate that this is about the thickness of the moon-dust in this area. The different teams working on this dust have produced a large number of papers and all seem in close agreement on their findings.

It seems from the electron microscopy and electron diffraction examination, that the radiation bombardment at the *Luna 16* site is very much greater than any of the material recovered from each of the *Apollo* missions.

One clue is that since the moon passes through the earth's magnetic tail for about four days every month, the right conditions could arise. The high energy electrons are sufficient to cause considerable disturbance of small grains. From this it follows that the most intense bombardment by the solar wind and other radiation would show on the other side of the moon, and that it could be there, that there would be least disturbance. If this is so, then the most disturbed area which

has been noted for the *Apollo* sites offers new data about the earth's magnetic field and magnetosphere.

THE OTHER MOON

Little Toro, the earth's other moon, is in the limelight again. It will be making one of its near approaches in the next few years when it will come to within nine million miles from earth. Its period of orbit is some eight years.

It has been under close observation since it was discovered in 1964 and computers have been used to track its behaviour. Being only one mile in diameter it is not visible to the naked eye, even though it does reflect sunlight.

It could be very useful to astronomers if there was a possibility of examining its surface. Since it is not likely to attract meteoritic impact or collect cosmic debris because of its extremely low gravity, the surface should be little different from what it was early in the life of the solar system.

It is possible to get such information by using a remote controlled spacecraft. Such a craft would take about six months to make the trip. Support for such a venture has come from Nobel Prizewinner Hannes Alfvén and he has suggested to NASA that this is a worth while project. If this should become a mission it would be suitable for early 1975.

As an exercise, the computer used to study the behaviour of Little Toro has checked the orbital behaviour for 200 years ahead and this shows little possibility of the moonlet getting out of hand and crashing into the earth.

NEWS FROM MARS

The wealth of information now being returned from *Mariner 9* has more than justified the project even though *Mariner 8* was lost. Many conjectures and theories regarding the red planet have had to be adjusted as a result of the present studies.

With more than 4,000 pictures already returned, much new data is revealed. The widely differing terrain is very apparent and consists of smooth craters and rough craters, large areas of furrowed and rugged surface, with many faults, channels and scarps. There are also signs of extensive and smooth lava flows.

The topography is such that it is difficult to explain the condition of branching channels which start in featureless areas, except by water erosion. It would seem that there is a continuing activity which suggests that the opinions of scientists based on the information of the previous *Mariners* have been radically revised.

After the results of 1969, Mars became of secondary interest to the

moon. However, now it is back in favour. Its cratered surface shows young volcanoes and lava flows which have overlaid existing craters both volcanic and impact.

The ultraviolet spectrometer and the radiometer measurements have indicated that carbon dioxide is the predominant gas in the upper atmosphere and that the south pole is too warm for there to be a solid cap of carbon dioxide. It is also clear that the north pole could be cold enough to support solid carbon dioxide clouds which might precipitate carbon dioxide snow. At the present time the north polar cap controls the atmosphere.

MARS IN ICE AGE?

There is little similarity between the Martian atmosphere and the atmosphere of the earth. There is some atomic oxygen and some atomic hydrogen. The whole planet is surrounded by a cloud of hydrogen extending for about 25,000 miles from the surface. At heights of 90 to 100 miles the temperature is much lower than that at the same heights on earth.

The hydrogen envelope surrounding the planet increases as solar activity becomes more intense and consequently the sun must draw some 100,000 gallons of water from Mars through photodissociation.

It is possible that the planet may be in an ice age and so would have large quantities of water stored in the form of permafrost. Certainly, there is much more information to be disclosed during the years that it will take to process the data so far acquired. It is to be hoped that this will spur on the missions of manned landings to round off the knowledge accumulated from remote sensing.

As *Apollo 15* has demonstrated, in the final analysis it is the human direct observations which enable more precise conclusions to be drawn.

ORBITING SOLAR OBSERVATORY


The first photographs of a solar flare on the far side of the sun was recorded by *OSO-7*. The flare which was of type Class 2 projected some four million miles out from the sun. The photographs show the progress of the flare till its plasma clouds were sent into space at a speed of 600 miles a second.

Each cloud, more than 150,000 miles in extent causes havoc to communications and triggers off auroral displays and magnetic storms when directed toward the Earth.

Even though the event recorded was in the opposite direction, some of its effects spilled round and was observed by Soviet, Australian and Phillipine radio telescopes.

ALPHA NUMERIC DISPLAYS

Part
By R.W. Coles

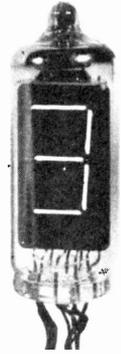

Incandescent Filament Displays

IN THE last two months we have seen how cold cathode tubes work and how their decoding and driving circuits are used. Whilst this type of tube has been the most widely used for many years, new technologies are now coming to the forefront of display systems design. Among these is the incandescent filament display. This type of display in its various forms is the subject of this month's article.

INCANDESCENT FILAMENT DEVICES

Many years of experience with incandescent filament bulbs, and the technology on which these are based, has led, not surprisingly, to some very cheap and practical alpha-numeric readout systems, in a wide variety of ingenious designs.

Filament lamps have many advantages to fit them for display purposes: high brightness which can be controlled at will (unlike gas filled devices); long life (100,000 hours is now obtainable); and a wide

range of working voltages making them simple to drive, especially important when i.c. drivers are contemplated.

Of course, there are a few disadvantages, of which heat generation is about the most serious, but all in all, filament lamps are so versatile and inexpensive that displays based on them are likely to continue in popularity for some time, despite competition from more advanced technologies.

As far as amateurs are concerned, there are already a fair number of device types available, and attention will be concentrated on these as far as possible.

DISCRETE CHARACTER TYPES

The discrete character format is very suitable for use with individual miniature bulbs, and there are many variations available. This format is preferred because of its inherent legibility, but all indicators employing it are more complex in construction than those using other schemes, and are also restricted in the character set which can be displayed.

PROJECTION TYPE

Fig. 3.1 shows a sectioned view of a typical projection type indicator, which can display twelve separate letters, numerals or symbols, depending on the transparency employed. Transparencies can be easily changed, as can the bulb holder which contains twelve individual i.e.s. lamps, the voltage ratings of which can be selected to suit the application.

In operation the selected character is illuminated by its associated lamp which may be driven by relay contacts or transistors, the illuminated section is then projected onto a ground glass screen at the front of the device where it gives a well defined image of reasonable brightness which can be in colour if required.

The complete indicator is rather long, though its frontal dimensions are very compact, making it possible to assemble multi-digit readouts with the minimum of panel space.



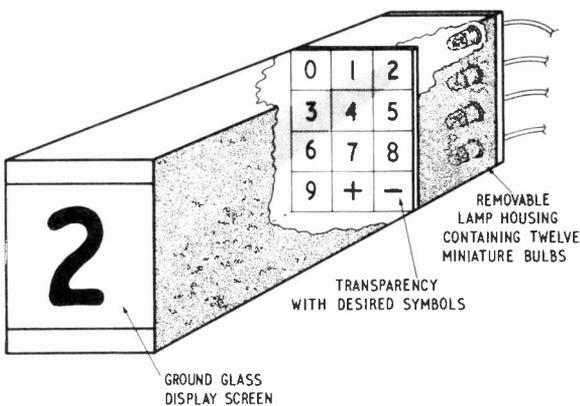


Fig. 3.1. A sectioned view of a typical projection type indicator. Light from the selected bulb projects the image of the transparency onto the ground glass screen

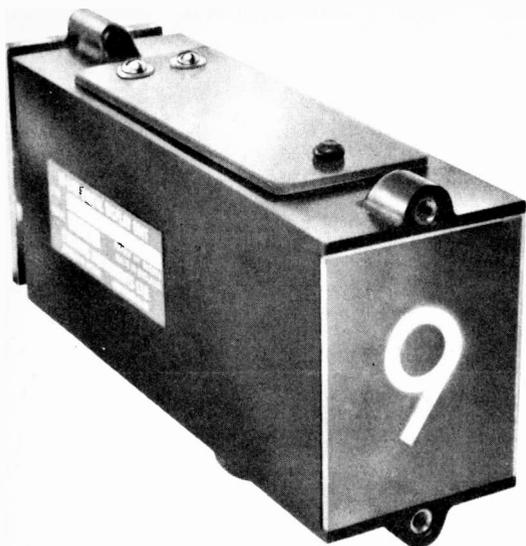

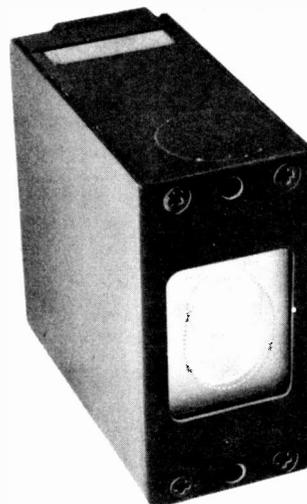A rear projection type display unit. This type gives 1in characters using 6.3V pilot lamps. It will give all the numerals and a decimal point (supplied by Electronic Brokers Ltd.)



A digital indicator using the Perspex light-guide technique as described in Fig. 3.2 (supplied by Electronic Brokers Ltd.)

EDGE-LIT TYPE

Again using a battery of individual i.e.s. lamps, the edge-lit Perspex indicators really do seem clever. These indicators utilise the fact that Perspex can be made to act as a "light-pipe", transmitting the bulb illumination over quite long distances and round corners before directing it towards the observer.

Fig. 3.2 gives a rough idea of the layout of these devices, though only one Perspex sheet (and hence one character) is shown; the side view shows how the other sheets are arranged in their respective slots.

When the selected lamp is illuminated, some of the light is directed onto the edge of the high quality Perspex, and this is channelled over the top of the bulb holder block and down to the viewing area.

The light does not escape in any appreciable amount because of the difference in the refractive index between the Perspex and air, and because the angles of refraction inside the Perspex sheet are too shallow for much light to exceed the critical angle and escape.

The character to be displayed is formed on the Perspex sheet by etching a series of holes of the correct layout, and these discontinuities in the sheet cause the channelled light to be refracted out towards the observer at these points.

Note that a series of dots rather than a continuous figure must be used so that some of the channelled light can pass through the upper parts of the figure and be available to interact with the lower parts.

One noteworthy point is the obvious difference in path length between the front and the rear bulb slit, and its effect on the brightness of the rear sheet; this is neatly compensated by the fact that although the front bulb has to transmit over a short path in the Perspex, once it has been refracted at the dots it has to travel through ten or so other sheets to reach the observer; the long path length on the other hand does not travel through any other sheets after interacting with the dots.

These devices are similar in length to the projection type, but are rather taller, the display is reasonably bright and easily interpreted, but parallax problems restrict the viewing angle, a problem not shared by the previous type.

GENERAL ADVANTAGES

Both the discrete character types discussed have the advantage of almost unlimited life since if a lamp fails it can be speedily replaced, a factor


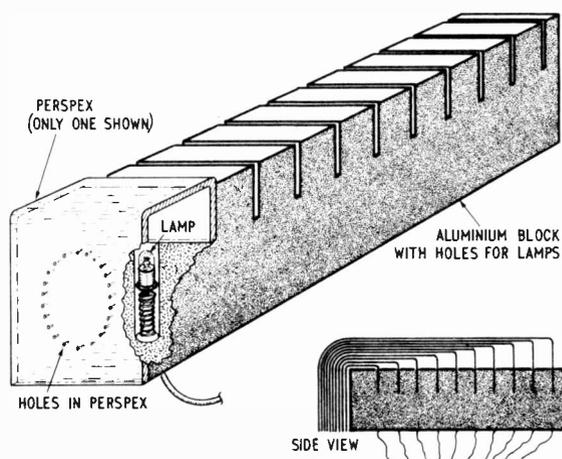
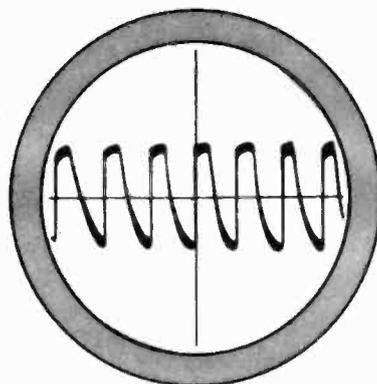


Fig. 3.2. An edge-lit indicator. Light from the selected bulb passes along the Perspex sheet and is refracted by the etched holes for viewing. The smaller drawing shows how the Perspex sheets are arranged

look! electronics really mastered

... practical
... visual
... exciting!

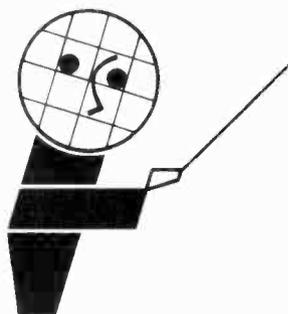no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

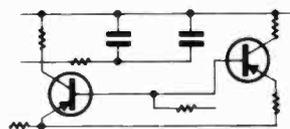2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE P.W.6

special free gift also to all our students

- LARGE STOCKS
 - GOOD SERVICE
 - ATTRACTIVE DISCOUNT
- Satisfaction Guaranteed

ELECTROVALUE

Electronic Component Specialists

SEMI-CONDUCTORS Brand new, guaranteed to spec. No seconds or surplus.

1B40K10	175p	2N3055	60p	40361	55p	AF124	24p	BC184L	11p	BFY90	104p	OA95	6p
1N2914	15p	2N3405	53p	40362	68p	AF125	24p	BC186	42p	BSY22	16p	OA200	9p
1N916	10p	2N3405	53p	40406	75p	AF126	22p	BC112L	16p	BY164	45p	OA202	10p
1N1763A	24p	2N3663	52p	40408	70p	AF127	22p	BC121L	16p	BY23B	18p	OC19	50p
1N3754	20p	2N3702	13p	40412	67p	AF139	33p	BC214L	16p	BYX38-	16p	OC25	42p
1N5399	21p	2N3703	13p	40430	140p	AF239	36p	BC257	9p	300	38p	OC28	78p
1N5402	28p	2N3704	13p	40432	185p	AL102	77p	BC258	8p	BYX38-	30p	OC29	76p
1N5407	45p	2N3705	13p	40512	195p	ASV26	27p	BC259	9p	300R	38p	OC35	60p
1S44	9p	2N3706	13p	40602	52p	ASV27	36p	BC267	17p	C407	17p	OC36	65p
1S940	5p	2N3707	13p	40659	140p	ASV28	27p	BC268	15p	C462	19p	OC41	42p
2N696	17p	2N3708	10p	AC107	46p	ASV29	16p	BC269	17p	CI412	102p	OC42	46p
2N697	18p	2N3709	11p	AC126	20p	AU111	97p	BC300	49p	E2512	164p	OC44	42p
2N706	12p	2N3710	13p	AC127	20p	B30C250	24p	BC301	37p	EA403	10p	OC45	38p
2N930	21p	2N3711	13p	AC128	20p	B30C550	24p	BC303	60p	EB383	10p	OC70	21p
2N1131	29p	2N3731	120p	AC141H	34p	306	34p	BCY30	60p	EC401	18p	OC71	38p
2N1132	29p	2N3774	15p	AC141HK	37p	B1912	66p	BCY31	75p	EC402	17p	OC72	38p
2N1202	19p	2N3801	60p	AC142H	25p	B5041	72p	BCY70	18p	ER900	54p	OC73	38p
2N1303	19p	2N3820	63p	AC142HK	29p	BA102	26p	BCY71	33p	MC140	25p	OC81	25p
2N1304	26p	2N3904	35p	AC153K	22p	BA130	22p	BCY72	15p	MJ481	120p	OC81D	25p
2N1305	26p	2N3906	35p	AC176	16p	BA145	27p	BD121	105p	MJ491	135p	OC83	25p
2N1306	33p	2N4036	55p	AC176K	17p	BA155	15p	BD123	105p	MJ371	108p	OC84	25p
2N1307	33p	2N4058	13p	AC187K	17p	BA156	13p	BD124	100p	MJE521	92p	P346A	26p
2N1308	36p	2N4059	10p	AC188K	23p	BA157	13p	BD130	50p	MJE2735	165p	S2CNI1	10p
2N1309	36p	2N4060	11p	*AC187K/	16p	BB103B	16p	BD131	79p	MJE3055	83p	SC141D	187p
2N1596	102p	2N4061	11p	188K	40p	BB103G	16p	BD132	86p	MPF102	37p	SC146D	247p
2N1599	122p	2N4062	12p	ACV17	31p	BC107	12p	BD135	38p	MPS6531	35p	SD1	10p
2N1613	23p	2N4124	18p	ACV18	19p	BC108	11p	BD136	44p	MPS6534	30p	SD4	12p
2N1711	26p	2N4126	27p	ACV19	23p	BC109	12p	BD141	227p	NKT211	25p	V763	28p
2N1893	54p	2N4284	24p	ACV20	20p	BC122	21p	BDY20	92p	NKT212	25p	WI06B1	45p
2N2147	95p	2N4286	15p	ACV21	21p	BC125	15p	BF115	23p	NKT213	25p	WI06D1	83p
2N2218	44p	2N4291	15p	ACV22	21p	BC126	22p	BF167	18p	NKT214	23p	WC2	40p
2N2218A	44p	2N4291	15p	ACV29	63p	BC130	30p	BF173	19p	NKT217	50p	WPO2	95p
2N2219	38p	2N4292	15p	ACV40	17p	BC147	10p	BF177	25p	NKT261	21p	ZTX300	14p
2N2219A	53p	2N4410	24p	ACV41	18p	BC148	9p	BF178	31p	NKT271	18p	ZTX301	16p
2N2270	62p	2N4443	11p	ACV44	31p	BC149	10p	BF194	14p	NKT274	18p	ZTX302	22p
2N2369A	19p	2N4906	305p	AD140	63p	BC153	19p	BF195	15p	NKT275	23p	ZTX303	22p
2N2483	35p	2N4915	215p	AD142	50p	BC154	20p	BF244	30p	NKT403	65p	ZTX304	27p
2N2484	42p	2N4921	62p	AD149	58p	BC157	14p	BF254	14p	NKT404	61p	ZTX304	23p
2N2646	47p	2N5062	31p	AD150	30p	BC158	11p	BF255	15p	NKT405	79p	ZTX331	27p
2N2904	38p	2N5088	38p	AD161	33p	BC159	12p	BF25X	19p	NKT603F	30p	ZTX500	18p
2N2904A	42p	2N5163	25p	AD162	36p	BC167	11p	BFX29	31p	NKT613F	30p	ZTX501	21p
2N2905	44p	2N5172	18p	*AD161/	60p	BC168	10p	BFX84	25p	NKT674F	24p	ZTX502	25p
2N2905A	47p	2N5192	125p	162	60p	BC169	11p	BFX85	22p	NKT677F	22p	ZTX503	22p
2N2924	20p	2N5195	147p	AF114	24p	BC177	14p	BFX87	39p	NKT713	30p	ZTX504	52p
2N2925	23p	2N5457	49p	AF115	24p	BC178	13p	BFX88	26p	NKT773	25p	ZTX530	37p
2N2926	11p	2N5459	9p	AF116	22p	BC179	9p	BFY50	23p	OA47	8p	ZTX531	33p
2N3053	27p	40250	71p	AF117	22p	BC182L	11p	BFY51	20p	OA90	6p		
2N3054	60p	40251	89p	AF118	82p	BC183L	10p	BFY52	23p	OA91	5p		

Minitron DIGITAL INDICATOR

Type 3015F seven segment indicator compatible with standard logic modules and power supplies. Shows 0-9 by filament segments (8mA from 5V d.c. per seg.)
Suitable BCD decoder driver FLL 1217 £1.45
DIL socket, 16 lead 30p
TYPE 3015G to show + or -, fig. 1 and decimal point £2

SOLDERSTAT SOLDER IRON

As appointed distributors for Eremco-Wolf "Solderstat" irons, we offer this model HMS in 16 or 24 watt, a.c. mains, for **£1.70**

RIVLIN PRECISION RESISTORS

0.1% to 0.01% TOLERANCE. Prices and delivery on request. £1-£2 for values up to 100k

NEW ELECTROVALUE CATALOGUE (No. 6)

1972 Edn. Bigger and better than ever. More lines, more bargains, more information, more diagrams. Post free 10p

BAXANDALL SPEAKER KIT

As originally designed and described by P. J. Baxandall in Wireless World. 10 watt/15Ω with frequency equaliser, speaker unit and special cabinet (size approx. 18" x 12" x 10") in pack-flat form. Inc. carriage paid in U.K. £13.90

PUBLICATIONS

The Book of Transistor Equivalents (BP.1) 40p
Handbook of Tested Transistor Circuits by H. Ness (BP.3) 40p
Radio and Electronic Colour Code and Data Wall Chart (BP.7) 15p
Any of above ordered singly, add 3p P. & P.

DISCOUNTS

Not allowed on NETT items
10% on orders for components for £5 or more.
15% on orders for components for £15 or more.

Prices subject to alteration without prior notice. Terms of business as published in catalogue.

POSTAGE AND PACKING FREE

on orders over £2. Please add 10p if orders under £2.

Overseas orders welcome: carriage and insurance charged at cost.

U.S.A. Customers should get in touch with **ELECTROVALUE AMERICA**, P.O. Box 27, Swarthmore, PA 19081.

CARBON TRACK POTENTIOMETERS

Long spindles. Double wiper ensures minimum noise level.
SINGLE GANG linear 100Ω to 2.2M. 12p; Single gang log. 47KΩ to 2.2MΩ, 12p; **DUAL GANG** linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log. 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 47K, 1MΩ only 42p; Dual antilog, 10K only, 42p Any type with 2A D.P. mains switch, 12p extra.
Only decades of 10, 22 and 47 available in ranges quoted.
DUAL CONCENTRIC in any combination of above values, 60p. With switch 72p.

CARBON SKELETON PRESETS

Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

SIEMENS 5% TOLERANCE POLYCARBONATE CAPACITORS 250V up to 0.1mF; 100V 0.1mF and above; 0.01, 0.012, 0.015, 0.018, 0.022, 0.027, 0.033, 0.039, 0.045, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22 6p; 0.27, 7p; 0.33, 0.39, 9p; 0.47, 10p; 0.56, 13p; 0.68, 15p.

ZENER DIODES 5% full range E24 values: 400mV: 2.7V to 36V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V 60p each.
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

CAPACITORS

MULLARD polyester C280 series
250V 20%; 0.01, 0.022, 0.033, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p; 10%; 0.33 7p; 0.47 8p; 0.68 11p; 1μF 14p; 1.5μF 21p; 2.2μF 24p.

MULLARD SUB-MIN. ELECTROLYTICS

C436 range, axial lead... 6p each
Values (μF): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/10; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/25; 40/16; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 100/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/25.

LARGE CAPACITORS
High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91; 10000/50, £2.40.

RESISTORS 10% — 5% — 2%

Prices are in pence each for some ohmic value and power rating, NOT mixed values. (Ignore fractions of 1p on total value of resistor order.)

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	9	8	7
C	1/8W	5%	4.7 Ω-470K Ω	E24	1	0.8	0.7
C	1/4W	10%	4.7 Ω-10M Ω	E12	1	0.8	0.7
C	1/2W	5%	4.7 Ω-10M Ω	E24	1.2	1	0.9
C	1W	10%	4.7 Ω-10M Ω	E12	2.5	2	1.9
MO	1/2W	2%	10 Ω-1M Ω	E24	4	3.5	3
WW	1W	10% ± 1/20	0.22 Ω-3.9 Ω	E12	7	7	6
WW	3W	5%	12 Ω-10K Ω	E12	7	7	6
WW	7W	5%	12 Ω-10K Ω	E12	9	9	8

Codes: C = carbon film high stability low noise
MO = metal oxide ElectroSil TR5 ultra low noise
WW = wire-wound Plessey

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

ELECTROVALUE An independent company established 1965

Dept. PE572, 28 St. Judes Rd., Englefield Green, EGHAM, Surrey TW2 0HB
Phone: Egham (0784-3) 5533 and 4757. Telex 264475
Hours: 9-5.30 daily. 1 p.m. Saturday

which in some applications makes up for the slightly higher cost compared with, say, cold cathode tubes.

These indicators are also more reliable than some of their incandescent cousins which involve moving parts, a technique widely used in the early days of display design, but no longer competitive, and therefore not treated here.

DOT MATRIX INDICATORS


Dot matrix indicators are the second type of format mentioned in the introductory article, and it is obviously possible to build this type of display with filament lamps. There are no commercially available display devices of this type, however, and in view of the problems of mechanical design (all those bulb holders!) and the more complex decoding required, such devices are not practical in miniature form.

The general principle is used however for large moving newsreel displays where the programming can be achieved simply by controlling the matrix with punched tape.

Further examples of large displays using this principle are the motorway traffic information boards, Guinness clocks, and sports scoreboards.

This is an area amenable to "do-it-yourself" techniques, the important points to remember being: keep it big, and keep the character set simple to ease decoding problems. Of course, if there is no objection to employing complex electronics such as commutators and read-only memories, then any desired character set can be built.

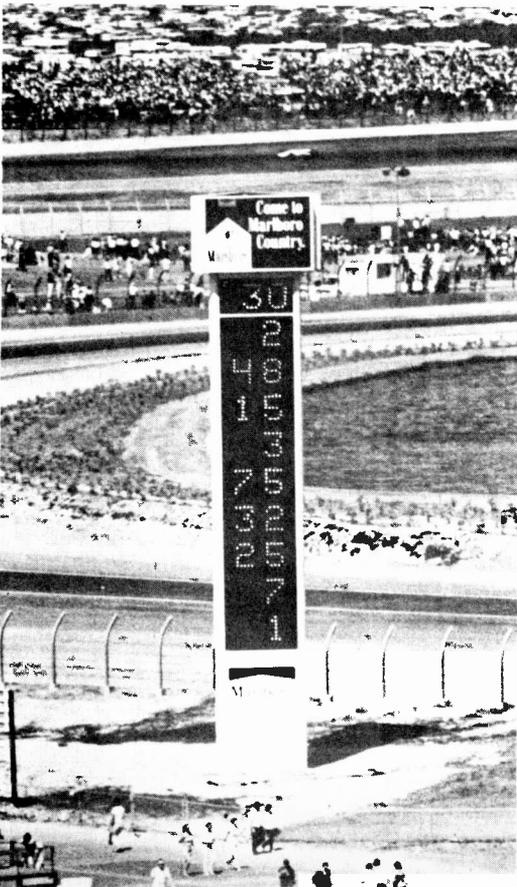A large display system using filament bulbs in a dot-matrix arrangement



A seven segment incandescent filament indicator tube. Almost any colour filter can be used unlike the cold cathode tubes which are either red or orange

BAR MATRIX DISPLAYS

The simple bar matrix display format, and in particular the "seven-segment" arrangement, is an ideal layout for use with incandescent device technology and a wide range of indicators have emerged using this combination, most of them championed in the U.S.A.

It is again possible to use individual lamps for each segment, but the real area where incandescent technology has come into its own is in the production of a complete seven segment indicator inside a single evacuated package.

These devices, often housed inside a valve type glass envelope, are capable of being mass produced, and large numbers are now being imported from Japan where most examples are manufactured.

This suitability for mass production combined with the inherent filament advantages quoted earlier and the availability of cheap decoder driver i.c.s will in future make these indicators the best choice for most amateur applications, such as digital clocks, counters, and calculators, a position held by the gas filled tubes at present.

OPERATION

A typical example of this type of device is shown in Fig. 3.3; this particular indicator has been chosen since it represents one of the types advertised for amateur use at present. Its type number is DA 133 (or DA 133D with decimal point) and it is available from West Hyde Developments under the trade name of Atron.

This indicator is housed in a glass envelope about half the size of a B7G valve, and produces characters 12mm in height. The coiled filaments are supported by wire pegs protruding from a ceramic base, and these pegs are interconnected at the rear of the ceramic according to the wiring shown, the segment, common, and decimal point each have an individual leadout through the nine pin base.

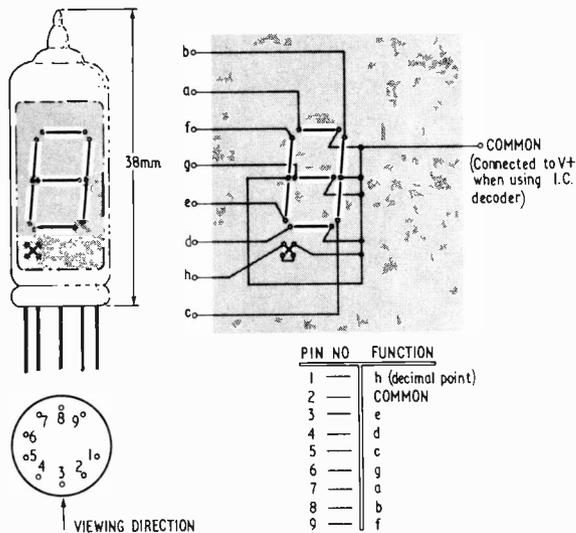



Fig. 3.3. The internal construction of a seven segment incandescent filament tube (Atron, available from West Hyde Developments)

The filaments are made of an advanced long-life, high brightness, material which gives a typical life of 100,000 hours. Each segment consumes about 120mW at the nominal supply voltage of 5V, making i.c. drivers eminently suitable, another advantage being that only one supply rail (V_{cc}) is necessary in a system using DTL or TTL.

The colour of the illuminated filament is of course the white normally associated with incandescent lamps, and this means that a filter can be positioned in front of the indicator to select any desired colour.

A filter is necessary in any case to improve contrast, but the possibility of selecting any colour is an advantage over, say, cold cathode tubes where a red or orange filter is mandatory. Green, blue, red, daylight, and neutral are the colours specifically available for use with the Atron.

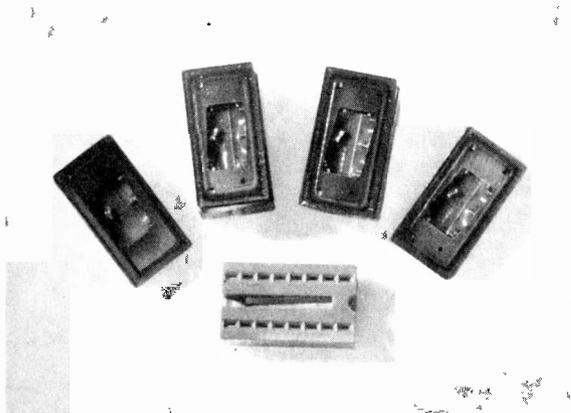Next month: Decoding and driving circuits for incandescent filament displays



Seven segment incandescent filament indicators in dual-in-line packages (Minitron 3015F, available from A. Marshall & Son)

BOOK REVIEWS

GUIDE TO PRINTED CIRCUITS

By Gordon J. King
Published by Fountain Press
140 pages, 8½in × 5½in. Price £2.50

NOT only does this book give a guide to printed circuit making for the amateur, it also describes industrial manufacture, printed circuit substitutes (i.e. Veroboard, S-Dec, and similar arrangements), soldering techniques, the use of printed circuit methods in i.c. manufacture, and applications of i.c.s.

Whilst some of the information is interesting I can find very little of any real use to the amateur. The techniques of making printed circuits could easily be described in a few paragraphs and the rest of the book seems merely to fill out the space. Are the "enthusiastic amateurs," for whom Mr. King professes to be writing, really interested in a chapter on the construction of soldering irons and desoldering methods?

At £2.50 this book is by no means cheap and I do not feel the content warrants such an outlay by the average enthusiast.

S.R.L.

INTRODUCTION TO VIDEO RECORDING

By W. Oliver
Published by W. Foulsham & Co Ltd
109 pages, 8½in × 5½in. Price £1.50

THE recording of events and entertainments, until fairly recently restricted to sound and cine film, promises great things for the future through the various media of electronic video processing. This book takes an outsider's view of the state of the art of video tape, disc, and hologram with ample reference to commercially exploited principles.

Although the author admits to taking a "semi-layman's" viewpoint he does describe in fundamental terms how the different systems work without becoming too embedded in technicalities. So much so that some of the earlier chapters could make rather boring reading to those already well informed on the principles of waveform propagation.

I, personally, found the section on video disc recording the most interesting as it seems that this is likely to become the commonly used technique for domestic applications—when all of the bugs have been ironed out. Tape is at present being used to a large extent, but as with sound recording, there are the attendant risks of erasure unless scrupulous precautions are taken. Bulk is also another commercial problem as is mass recording on tape.

This book is very readable but its price precludes its purchase value. Since it can be read in a couple of hours (there are many large illustrations) it is perhaps best suited to the lending and technical libraries.

M.A.C.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT
VARIABLE 0.260V

All Types:
from 1/2 to 50 amp from stock.

SHROUDED TYPE

1 amp, £7.00	20 amp, £49.00
2.5 amp, £8.05	25 amp, £58.00
5 amp, £11.75	37.5 amp, £82.00
10 amp, £22.50	50 amp, £98.00



(Panel Mounting) 1/2 amp, £4.75. OPEN TYPE
1 amp, £7.00. 2 1/2 amp, £8.05. All carriage paid.

L.T. TRANSFORMERS

All primaries 220-240V	Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36V at 5A		£4.68	45p
2	30, 40, 50V at 5A		£6.88	45p
3	10, 17, 18V at 10A		£4.95	45p
4	6, 12V at 20A		£6.43	45p
5	17, 18, 20V at 20A		£7.28	55p
6	6, 12, 20V at 20A		£6.88	55p
7	24V at 10A		£5.23	45p
8	4, 6, 24, 32V at 12A		£7.15	45p
9	6 and 12V at 10A		£3.75	45p

COMPLETE NI. CAD. BATTERY OUTFIT (EX W.D.)

2 metal carrying cases each containing 10 x 1.2V 7AH (12V) batteries, also 10 x 1.2V 22AH (12V) batteries (24 batteries in all).
1 Dual voltage, dual meter, thyristor controlled charging unit. Designed for charging the 7AH and 22AH batteries simultaneously. Input voltage can be adjusted between 100-250V a.c. Built to ministry specification. Ideal power supply for field work. Offered at fraction of makers' price. 2 sets of batteries, 1 charging unit. The set £45, P. & P. £1.50.



220/240 VOLT A.C.

CENTRIFUGAL FAN/BLOWER

Smooth, balanced running unit. Two pole shaded pole Mylex motor gives approximately 90 cubic ft./min. but draws only 240mA on run. Weight 2 1/2 lb. Case dia. 3 1/2 in, width (case only) 3 1/2 in, width overall (inc. motor) 5 2 1/2 in, aperture 3 1/2 in. 1.85in. Price only £2.95. P. & P. 25p.



BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible, 1/70th inch. stroke, 0.38 amp. (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible, 1/80th inch. stroke, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p. P. & P. or less transformer £2.13 plus 27p. P. & P.



12 VOLT D.C. MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size 4 1/2 in. x 2 1/2 in. dia. Either type price 95p inc. post.



230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox.
1 r.p.m. cw. 1 r.p.h. a/cw. 10 r.p.h. a/cw.
60 r.p.m. cw. 2 r.p.h. a/cw. 15 r.p.h. a/cw.
30 r.p.h. cw. 20 r.p.h. a/cw.
6 r.p.h. cw. 30 r.p.h. a/cw.
cw. = clockwise rotation; a/cw. = anticlockwise. Fraction of makers' price. All at 75p incl. P. & P.



100-250V A.C. NEON INDICATOR

Available in red or amber at 20p each. Or in green at 32p each. Minimum order 3 units. P. & P. 5p.



MINIATURE UNISELECTOR

3 banks of 11 positions, plus housing bank, 40 ohm coil. 24.36V d.c. operation. Carefully removed from equipment and tested. £1.15, plus 15p P. & P.



UNISELECTOR SWITCHES

NEW 4 Bank 25 Way
24V d.c. operation. £5.88, P. & P. 12p. 6 Bank 25 Way
24V d.c. £6.50, P. & P. 12p.
8 Bank 25 Way, 24V d.c. operation. £7.62 plus 22p P. & P.



36V 30 AMP. A.C. or D.C. VARIABLE L.T. SUPPLY UNIT

INPUT 220/240V a.c.
OUTPUT CONTINUOUSLY VARIABLE 0-36V Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £68 plus £2 P. & P.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.
EXPERIMENTERS' ECONOMY KIT Speed adjustable 1 to 36 flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P.

NEW INDUSTRIAL KIT Ideally suitable for schools, laboratories, etc. Roller trim printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.
HY-LYGT STROBE MK III This strobe has been designed and produced for use in large rooms, halls and the photographic field and utilises a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 150 joules. £12.00. P. & P. 50p. SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE. For industrial or Hy-Lyght. Including reflector. £4.00 P. & P. 45p. Post paid with kit.

THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:
● Heavy duty power supply.
● Variable speed from 1-23 flash per sec.
● Reactor control circuit producing an intense white light.

Never before a Strobe Kit with so HIGH an output at so LOW a price. Only £20 plus 75p P. & P.
ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Lyght Kit including reflector £7.00 P. & P. 45p.

7-inch POLISHED REFLECTOR Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.

6 INCH COLOUR WHEEL

As used for disco lighting effects, etc. £5.75 incl. P. & P. can be operated from our one r.p.m. synchronous motor price 75p incl. P. & P.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34.00 carriage paid.



MOTOROLA MIC 11/6 PLASTIC TRIAC 400 PIV. 10 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1.05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

240V A.C. SOLENOID FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1/2 in b.s.p. inlet/outlet. Precision made, British mfg. PRICE: £1.75. P. & P. 20p. Special quotation for quantity. (New in makers' carton)



PROGRAMME TIMERS

(Mfg. by Magnetic Devices Ltd.) 240V A.C. 5 r.p.m.
"Crouzet" motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment; for chaser lights, animated displays, etc. NEW PRICE £5.75. P. & P. 25p.



230V A.C. SOLENOID

Extremely powerful with approx. 14lb pull, 1in travel. Fitted with mounting feet. Size: 4in long, 2 1/2 in wide, 3in high. £2.00 incl. P. & P.



230-250 VOLT A.C. SOLENOID

Manufactured by Westool Ltd. (similar in appearance to above illustration). Approx. 1 1/2 lb pull. Feet size 1 1/2 in. Price 85p incl. P. & P.

18-24 VOLT D.C. SOLENOID

Size: O.A.L. 3 1/2 in. 1 1/2 in. Max. push 1/2 at 1lb. approx. PRICE: 75p incl. P. & P.

Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 5 kΩ, 140mA. Diameter 3 1/2 in. Shaft length 1 1/2 in, dia. 1/8 in. All at £1.65 each. P. & P. 7 1/2 p.
50 WATT. 1/5/10/25/50/100/250/500/1/1/1-5/2-5/5k.Ω. All at £1.15 each. P. & P. 7 1/2 p.
25 WATT. 10/25/50/100/250/500/1/1-5/2-5/5/5k.Ω. All at 90p each. P. & P. 7 1/2 p.
Black Silver Skirted knobs calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats. 18p ea.

RELAYS SIEMENS, PLESSEY, Etc.

MINIATURE RELAYS


Col. (1)	1	2	3	4
Coil ohms	280	9-12	2 c/o	73p*
Coil (2)	410	10-18	4 c/o	73p*
Working d.c. volts	700	16-24	4M 2B	63p*
Coil (3)	700	16-24	4 c/o	78p*
Contr'ts	700	12-54	2 c/o HD	63p*
Coil (4)	700	16-24	6M	65p*
Price	1,250	24-36	4 c/o	63p*
HD =	2,500	36-45	6M	63p*
Heavy duty	2,400	30-48	4 c/o	50p*
Incl. Base	9,000	40-70	2 c/o	50p
Post paid	15k	85-110	6M	50p*

12 VOLT D.C. RELAY

140 ohm coil
Three sets c/o contacts rated at 5 amps. 78p including P. & P. (Similar to illustration below.)

'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

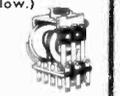Three sets c/o contacts rated at 5 amps. PRICE: 50p. P. & P. 10p. (100 lots £40 including P. & P.)



230 VOLT A.C. RELAYS MFG. KEY SWITCH

One set c/o contacts rated at 7.5 amps. PRICE: 40p. P. & P. 5p. (100 lots £32 including P. & P.)

MINIATURE RELAYS

9-12V d.c. operation. Two c/o 500 M.A. contacts. Size only 1 in x 1/2 in x 1/2 in. Price 58p post paid.
30-36V d.c. operation. Two c/o 500 M.A. contacts. 3.200 ohm coil. Size only 1 in x 1/2 in x 1/2 in. 43p post paid.

VENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set 2 on, 2 off every 24h. Override switch; 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.



G.E.C. 12 WAY 15 AMP CONNECTORS

NEW in makers carton. BAKELITE £1.25 per doz. FLEXIBLE £1.50 per doz. Post paid (Minimum 1 doz).



LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.75. P. & P. 18p.



LIGHT SENSITIVE SWITCHES

Kit includes ORP.12 Photocell, Relay Transistor Circuit. For 6 or 12V D.C. operation. Price £1.50 plus 12p P. & P.
ORP.12 and Circuit £6.3p post paid.
220/240V A.C. MAINS MODEL Mains transformer, rectifier, relay, 1 make 1 break H.D. contacts. price incl. circuit £2.65. P. & P. 20p.



"HONEYWELL" PUSH BUTTON PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amp 240V A.C. Black knob in. Fixing hole 1/2 in. ONE bank 30p; TWO bank 40p; THREE bank 55p; incl. P. & P.



"HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contact. NEW in maker's carton. PRICE: 10 for £1.90 including P. & P.



D.C. AMMETERS NEW!

1A, 5A, 15A, 20A, £1.75, incl. P. & P. 0-3000V a.c., £1.90, incl. P. & P.



All Mail Orders—Callers—Ample Parking
Dept. PE4, 57 BRIDGMAN ROAD
LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

INTEGRATED CIRCUIT POCKET BOOK

by R. G. Hibberd

£2.50 Postage 10p.

RADIO TECHNICIAN'S BENCH MANUAL by H. W. Hellyer. £3. Postage 12p.

AUDIO TECHNICIAN'S BENCH MANUAL by John Earl. £3. Postage 12p.

SERVICING TRANSISTOR RADIO RECEIVERS by F. R. Pettit. 75p. Postage 7p.

1972 WORLD RADIO-TV HANDBOOK. £2.80. Postage 15p.

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. £1.20. Postage 10p.

PRACTICAL TRANSISTOR SERVICING by W. C. Caldwell. £1.90. Postage 12p

RADIO DATA REFERENCE BOOK by G. R. Jessop. £1. Postage 12p.

THE MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal. £3.50. Postage 15p.

THE MODERN BOOK CO.


BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

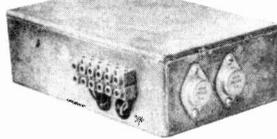PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision. Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2 in x 4 1/2 in x 2 in approx. Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.90 plus 50p P. & P. S.A.E. with all enquiries.

PSYCHEDELIC LIGHTING UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9 in x 7 in x 3 in. Price £25 carr. paid. S.A.E. with all enquiries.

DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET, WALSALL
STAFFS WS1 1UZ
WALSALL 34365
MAIL ORDER ONLY

SOLDERSOKE Solder Absorbing Wick 4 feet for 40p ^{post free} Orientation Ltd

MAIFIELD, COVERACK,
CORNWALL.

OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6, 425-0-425V, 500 Ma, 6.3V 6A CT, 6.3V 6A CT, 0-5-6.3V 3a, £12-75; TX1, 425-0-425V, 250Ma, 6.3V 4A CT, 6.3V 4A CT 0-5-6.3V, 3A, £7-50; TX2, 250-0-250V, 150mA, 6.3V 4A CT, 0-5-6.3V, 3A, £4-05; TX5, 300-0-300V, 120mA, 6.3V 2A CT, 6.3V, 2A, £3V, 1A, £4-05; TX8, 250-0-250V, 65mA, 6.3V, 1.5A, £2-10; MT1, 200V, 30mA, 6.3V, 1A, £1-20; MT2, 230V, 40mA, 6.3V, 1.5A, £1-50; MT2A, 250V, 60mA, 6.3V, 2A, £1-95; MT3 Prim. 110/240V, Sec. 250V, 100mA, 6.3V, 2A, £2-25.

AUTO TRANSFORMERS
0-110-200-220 240V a.c. up or down fully shrouded fitted insulated terminal blocks. 30W £1-35; 50W £1-80; 75W £2-10; 100W £2-55; 150W £3-15; 200W £3-80; 300W £5-25; 400W £6-30; 500W £7-50; 600W £8-25; 750W £9-75; 1,000W £12-75; 1,500W £18; 2,000W £24-75; 3,000W £33; 4,000W £45.

MULTIVOLT TRANSFORMERS
Prim. 200/240V a.c. OMT4/1 tapped sec. 0-60V 1A, £2-25; OMT4/2, ditto 2A, £3-40; OMT4/3, tapped sec. 0-110V 1A, £3-45; D10 sec. 12V 4A-12V 4A, £3-60; D10 sec. tapped, 0-10-20-25V 2A-0-10-20-25V 2A, £3-60.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V, 1.5A, 85p; 3A, £1-13; 6A CT, £1-80; 12V, 1.5A, £1-13; 3A CT, £1-80; 6A CT, £2-70; 15V, 1.5A CT, £1-80; 24V, 1.5A CT, £1-80; 30V CT, £2-70; 5A, £3-75; 8A, £8; 12A, £9; 40V, 3A CT, £3-45.

MIDGET RECTIFIER TRANSFORMERS
For FW rect., size 1 1/2 x 2 x 1 1/2 in. Prim. 200/240V a.c. output, PPT1, 9-0-9V, 0.3A, PPT2, 12-0-12V, 0.25A, PPT3, 20-0-20V, 0.16A, £1-20 each; ditto, size 2 x 2 1/2 x 1 1/2 in. MTV1, 9-0-9V, 1A, 85p; MTV2, 12-0-12V, 1A, £1.00; MTV3, 20-0-20V, 0.75A, £1.00 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3-7.5-15 ohms, A-A 6.6kΩ, 30W (KT66, etc.), £4-05; 50W, 3kΩ, A-A, £6-75; 100W, 3kΩ, A-A, EL34 (KT88, etc.) £11-40 and to 400W.

LOUDSPEAKERS FOR POWER AMPLIFIERS
New, famous make, 15W with tweeter, £4-95; 25W, £5-60; 30W, £7-20; 50W, £10-50; 100W, £22-50; E.M.I. 1 1/2 x 8 in 10W, 3 or 8 or 15 ohms, £2-25. Ditto with two tweeters and Xover, £4-00; Horn Tweeters 2-16kHz 10W 8 or 16 ohms, £1-60. HI-FI, 8 x 5 in 8Ω, £1-85; 10 6 in 3 or 8 or 15Ω, £2-10.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30 to 400 watts, with price list of transformers and chokes specified. 25p.

LOUDSPEAKERS
2 1/2 in 16Ω, 2 1/2 in 8Ω, 2 1/2 in 25Ω, 3 in 8 or 30Ω, 80p each; 3 1/2 in 8 or 15Ω, 4 in 8 or 15Ω, 5 in 3, 15 or 25Ω, 5 x 3 in 3, 8, 15 or 25Ω, 90p each; 6 x 4 in 25Ω, 7 x 4 in 3 or 6 1/2 in 3Ω, £1-08; 8 x 5 in 3, 8, 15 or 25Ω, £1-50; 8 in 3Ω, £1-95.

SPEAKER AUTO MATCHING TRANSFORMER 12W
3 to 8 or 15 ohms, up or down, 75p. P. & P. 15p.

MINIATURE RELAYS FOR MODELS, ETC.
1 x 2 x 3 in 1oz, with transparent cover, 2 C.O. in 9; 15; 20 or 30V d.c. 50p each.

BULK TAPE ERASERS
Instant erasing, tape spools and cassettes, demagnetizes tape heads, a.c. 200/250V, £2-40 plus 24p P. & P.

PRINTED CIRCUIT ETCHING KITS
Complete outfit: solutions and equipment to make your own P.C. boards instructions, £1-40, P. & P. 21p. Extra p.c. Boards 8 6 in, 15p each.

TAPE RECORDER MOTORS
A variety of uses, Blowers, Fans, etc., new. 230/250V a.c. 50p each.

CONDENSERS
Paper: 0-01/2kV 12p; 0-1/1kV 12p; 0-22/1kV 20p; 0-22/800V a.c. 25p; 0-47/700V 15p; 0-47/1kV 25p; 4/500V 25p; Electrolytics: 100 + 200/275V 40p; 100 + 200/350V 50p; 100 + 60/450V 25p; 350 + 50/325V 15p; 100 + 400/275V 20p; 24/50V 10p; 25/00/4V 50p

BATTERY ELIMINATORS/POWER UNITS
To operate battery equipment from mains 200/240V a.c. Outputs, 6V, £1-50; 9V, £1-50; 7-5V (for cassettes), £2-00; 12V 1A, £3-00; 40V 1A, £4-50.

Carriage extra on all orders, etc., etc.

S.A.E. INQUIRIES-LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

BATTERY ELIMINATORS
The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) £2 each. P. & P. 15p.

9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) £2.50 each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17

GY-NORMOUS RADIO BARGAINS!

*3 types, all superhets with push-pull output to internal loudspeaker. Supplied complete with carrying case, earphone and batteries.

Type A—Very neat little set, still only £1.50 + p & p 20p.

Type B—Large battery operated model, full LW and MW coverage. Ideal for kitchen or car. Complete with swivelling telescopic aerial. £5-80 + p & p 45p.

Type C—Large portable radio as sold nationally. A.M. and F.M. coverage (Yes F.M.—88—108MHz). Horizontal pointer tuning scale. Operates from own dry batteries or a.c. mains from internal transformer isolated power pack, with provision for rechargeable cells (not supplied). £8 + p & p 50p.

All these sets are BRAND NEW and complete in manufacturers original cartons, but may require slight attention—hence bargain prices—cheaper than kits!

***CASSETTE PLAYERS**—last few only—uses standard musicassettes—possible conversion to full recorder. Deck alone worth our price of £8-99 + p & p 55p.

***C120 Cassettes**. Top quality. 75p + p & p 7p.

***SAVE £££'s ON BATTERIES**, run your transistor, etc., from the mains with our 9V eliminator, £1.50 + p & p 15p.

***LABGEAR** "Magic Circle" indoor UHF aerial only £1-25 + p & p 15p.

T.V.'s: T.V.'s: T.V.'s: T.V.'s: T.V.'s: T.V.'s: *4 Channel 19in UHF T.V.'s Despatched tested, and in full working order. £20.

*19in Slimline, only requires UHF tuner for BBC2, untested, complete, £8.

*As above but with UHF tuner, £12.

*2 Channel (with 405/625 Timebase) 19in 110" tube, untested, £5.

(Carriage £1-50 extra all models.)

SUMIKS

7 High Street
Langley, Warley, Worcs.

Callers Welcome

Gerry Brown . . . ON THE FRINGE



OCCULTAPHONICS

Stick your neck out, my old man used to say, and some willing cove will come along and lop it off. True to form, and human nature being the readily predictable thing it so often is, some willing cove very nearly succeeded a month or so back! Stuart White, at that time reporting for one of the big "Sundays", brought to the attention of the public his judgements about the efficacy of an unusual electronic device then available.

Somewhat embarrassingly, this device owed its very inception to me and, to boot, represented about the nearest thing to the "popular" definition of an electronic crystal-ball that you could wish to find!

Preparation for this mis-guided event began "yonks ago" while I was yet a callow youth in the RAF. One soon discovers at an air-base, however, what a monotonous business life in a control tower can be; particularly so when all the lads have nipped off on a sortie and the only remaining company are a couple of card-playing "a/c plonks" and the idle hiss from a temporarily inactive air-radio. It was this very hiss that had, at one time or another, given rise to an effect that had both interested and perplexed us all.

As I have said, you would be sitting there contemplating your next week-end off, or maybe the one just gone, when suddenly you would be aware that through the background hash from the radio there was a signal feebly breaking through. "Unidentified aircraft, say again," you would call back, but somehow you almost knew that there would be no response, other than the steady rushing sound from the receiver. Any number of operators had witnessed this effect and, indeed, some were convinced that the voices they heard were for real!

Obviously, we must preserve a meaningful perspective and it is probably true to say that since white noise (hiss) contains just about every sound that has ever been produced (but all at once) there's a fair chance that if you listen to it long enough you might ultimately hear speech too. But

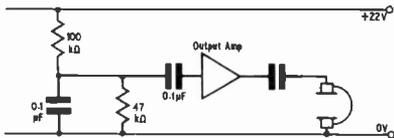


Fig. 1

there are even technical reasons for disputing this, so, apart from that "old chestnut" imagination being the culprit, from where *do* these effects originate?

It was in November 1971 with many of these unsolved questions still uppermost in my mind, that I built a simple little set-up, Fig. 1, in an attempt to discover more. The results were relatively inconclusive, although sufficiently thought provoking for work to continue. The circuit is included for your interest only; it's really nothing special, just a white-noise generator followed by an amplifier. Try it if you will.

Only days after White's report, I noticed that a sister newspaper, in direct contradiction to the apparent ethics of the one mentioned earlier, carried almost an entire page on Flying Saucers. Maybe there are "fairies at the bottom of their garden" after all!



STUDENT IC

There's an integrated circuit on the market at the moment which you can actually *teach!* This MOS device is an adaptive-logic gate, MC901, produced by the Motorola Corporation and designed, primarily, for feature-extraction in pattern-recognition applications.

In essence (Fig. 2) the MC901 comprises a 4-bit binary to 1-out-of-16 decoder, plus sixteen individual flip-flop memories and associated output gating.

Each gate also has a common connection with a "teach" input such that if it is taken to logical

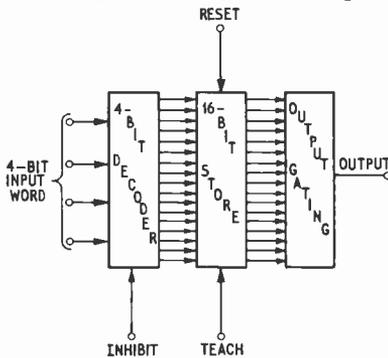


Fig. 2

"1" (for a brief moment during the time that the decoder input is present) the relevant gate will cause its associated flip-flop to change state. Since each flip-flop controls an output gate (which is also connected to the decoder) any subsequent application of the original 4-bit number will result in "recognition" and the output going to "1". A "0" at the teach input resets the memory.

The MC901 additionally embodies an inhibit facility which allows several devices to be inter-linked and so accept expansion in the size of input word. An integrated circuit of this kind would, without doubt, obviate almost all the tedium associated with building a complete learning network; trouble is you'll need seven pounds to make the idea a going proposition.

GREEN FINGERS

It shouldn't be long before G. W. Millard of the Reddiglade Nurseries in Kent publishes his paper relating to the effects of manipulation of bio-potentials in trees.

Early in 1971 he was conducting some rather interesting experiments pointing to the fact that trees sometimes increase their rate of growth



when an electric current is passed through them. Of course, rate of growth is largely dependent on the rate at which the organisms' food supplies can reach the sites of actual growth. Since, however, the nutrients are abundant in molecules having electrical charges, an applied current could exert quite a profound influence on a tree's development.

Millard, as yet, has not announced the magnitude of the potentials which need to be applied; indeed workers in several parts of the world have had no luck in establishing the validity of his claims.

It is difficult to say whether the effect is a load of old nonsense or really genuine, nevertheless, I recall some years ago hearing about a similar effect involving the control of sap by electrical potential. At that time, the voltage used was about a couple of volts or so, with negative applied to the top of the tree and positive earth to make the sap rise.

Now don't quote me on this, but I heard a tale that someone who employed this scheme last year succeeded in bringing some simply beautiful Cox's Orange to maturity real early. Trouble was they got too cute and reversed the current. The "windfalls" made great cider!!



SOLID STATE SNAP

By J. S. GRICE B.A.

SNAP is an unusual game in that mainly it tests speed of response; we have all played the game as children. There are two good reasons why the game is confined largely to children. One, it is not always easy to determine who did shout first, and two, the face of the turning card is not necessarily presented to both contestants simultaneously. For adults such uncertainty and imprecision spoil the game for serious contest.

The apparatus to be described here provides an electronic analogue of the game in which these deficiencies have been overcome. Essentially what is needed is a sudden signal presented simultaneously to the two contestants, and a mode of response such that the priority can be determined infallibly.

GENERAL DESCRIPTION

Snap consists of a small metal case, which contains the circuitry, mounted on a wooden baseboard, and two morse-keys (S1 and S2) also mounted on the baseboard—one on each side of the case. On the top panel of the case are an on/off switch (S4), the reset button (S3) and a centre-zero meter (M1), which indicates the winner.

The apparatus is switched on, the contestants take up their positions one to each key, and the reset button is pushed down and released. After a delay

of about ten seconds the machine emits a high-pitched note, and the players respond by depressing their keys as quickly as possible. The meter pointer swings over towards the key which was depressed first. It is only necessary to depress and release the reset button again to initiate another "round". Perhaps ten "rounds" may be taken to constitute a game.

DESIGN POINTS

An audible signal was chosen since there is no difficulty in ensuring that such a signal is presented to both players simultaneously; also the sound can be produced with due economy of current consumption. A delay of about ten seconds between the operation of the reset button and the sounding of the signal was found to be the most effective period.

Some safeguard is necessary against the inadvertent (or deliberate) premature depressing of a key. It is therefore arranged that if a key is depressed during the delay period the signal will not sound. Nevertheless the meter indicates which key was depressed, and it is suggested that in such circumstances the point is awarded to the other side.

A minor refinement is the automatic cessation of the signal note some ten seconds after a key has been legitimately depressed.

For simplicity of control, one push of the reset button resets and recycles everything; that is, stops the signal note if necessary, initiates the ten second delay, and re-centres the meter.

BLOCK DIAGRAM

The two bistables shown in the block diagram (Fig. 1) are cross-coupled; the pulse required to reverse the condition of bistable one is obtained, via

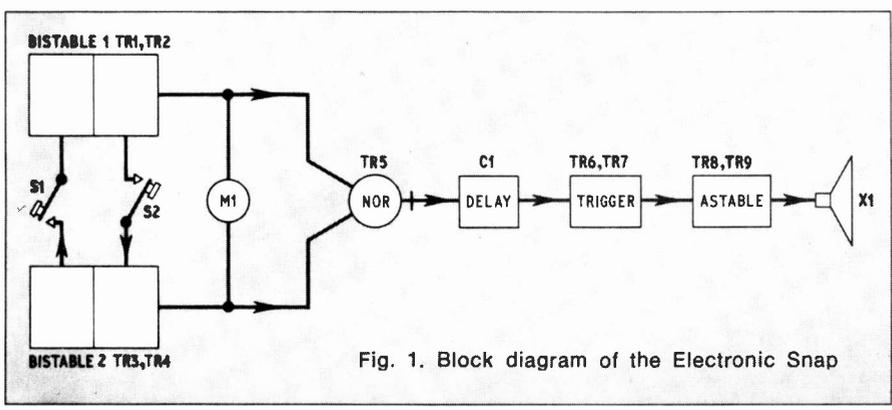


Fig. 1. Block diagram of the Electronic Snap

a morse-key (S2), from bistable two; and the pulse required to reverse the condition of bistable two is obtained, via a second morse-key (S1), from bistable one. However, as soon as the initial condition of either bistable is reversed it is unable to supply a pulse to reverse the condition of the other bistable. It is the two bistables then which determine which key was depressed first. The action is explained more fully in the next section.

Both bistables are linked with the NOR gate. The NOR gate produces an output voltage only when both inputs are zero. This is the case when both bistables are in their initial condition.

Assuming that the bistables remain undisturbed in their initial condition for a while so that the NOR gate maintains its output voltage, then the delay capacitor will slowly charge up.

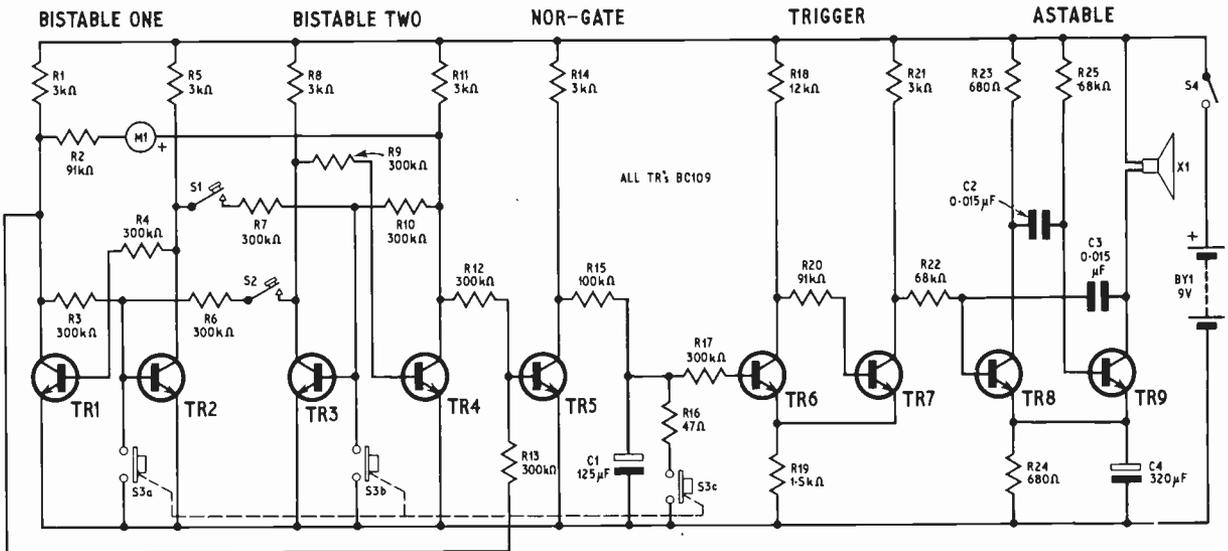
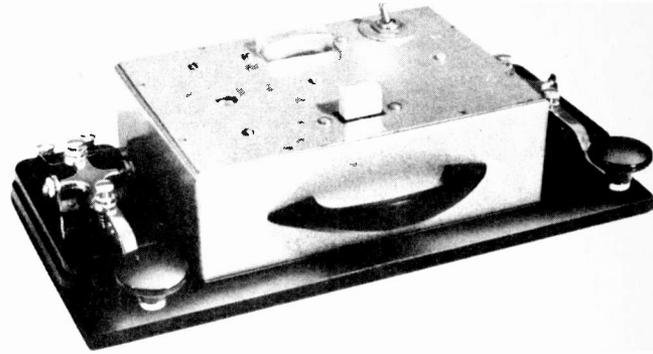


Fig. 2. Complete circuit diagram of the Electronic Snap

The slowly increasing voltage at the delay capacitor is passed to the trigger. The trigger has only two output states: a low voltage which prevents the astable from oscillating, and a high voltage which permits the astable to oscillate. When the input voltage of the trigger rises to a certain level the output switches suddenly from the low voltage to the high voltage, thus producing the signal.

If a key is depressed before the input voltage of the trigger reaches this particular level, then the signal will not be produced. This is because depressing a key reverses the initial state of a bistable thereby causing an input voltage to the NOR gate and hence no output voltage from it, so that the delay capacitor will be discharged.


BISTABLES

Transistors TR1 and TR2 (Fig. 2) form bistable one; TR3 and TR4 form bistable two. The bistable is a familiar building-block in logic circuitry. Here it consists of two transistors, one fully conducting, the other cut-off. A pulse applied at an appropriate point reverses the roles of the transistors, and they remain reversed until another pulse is applied at an appropriate point.

When the apparatus is switched on the state of the bistables is indeterminate. The reset switch (S3) serves to establish the desired initial condition in each bistable. When S3a is temporarily closed the emitter-base junction of TR2 is shorted and this ensures that TR2 is the cut-off transistor in bistable one. Similarly the closing of S3b ensures that TR3 is the cut-off transistor in bistable two.

So, when the play cycle is initiated, in bistable one TR1 is fully conducting and TR2 is cut-off, and in bistable two TR3 is cut-off and TR4 is fully conducting. This means that the collectors of TR1 and TR4 are at near zero voltage, and the collectors of TR2 and TR3 are at approximately full supply voltage. The centre-zero meter M1 connected between the collectors of TR1 and TR4 will not register.

Now we can reverse the state of bistable one by supplying a positive pulse to the base of TR2 via S2 and R6. This will cause TR2 to become fully conducting and TR1 cut-off. Once this is done, however, it is not possible to reverse the state of bistable two in a similar manner by depressing S1 because the voltage at the collector of TR2 is now near zero. The meter pointer will swing to the left indicating that the collector voltage of TR1 is at the supply

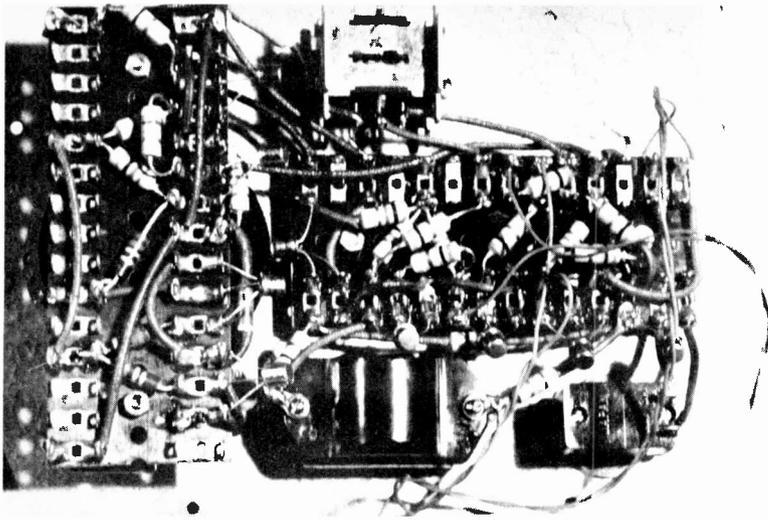

Showing the layout of components and tag boards mounted inside the case

voltage while the collector voltage of TR4 remains near zero.

Of course, had we depressed S1 first, reversing the condition of bistable two, then the subsequent depressing of S2 would have had no effect on bistable one, and the meter pointer would have swung to the right indicating the collector of TR4 is at the supply voltage.

The two bistables measure which key was depressed first, and since the switching time of the circuitry is much faster than human reaction times, the measurement is entirely reliable.

NOR GATE

The bistables have one subsidiary function. It will be seen that the state of the collectors of TR1 and TR4 determines the state of the collector of TR5. When a play cycle is initiated the collectors of TR1 and TR4 are at near zero volts, so that there is near zero voltage supply to the base of TR5. Consequently TR5 is cut-off and its collector is at full supply voltage. Should, however, the collector of either TR1 or TR4 go positive, as happens when a key is depressed, then TR5 will become fully conducting and its collector voltage will drop to near zero. Transistor TR5 is then in effect a NOR gate, giving an output only when it has no input.

The purpose of this arrangement has already been explained. The delay capacitor (C1), which determines when the signal will sound, charges from the TR5 collector voltage. If this voltage is cut off during the build-up period, C1 starts to discharge and there is no signal. Thus the premature depressing of a key is detected. It will be noted, however, that the meter will still register in the usual way which key was depressed first.

Assuming no interruption, C1 will charge up in ten seconds to a voltage sufficient to fire the trigger.

TRIGGER

Transistors TR6 and TR7 comprise the trigger circuit. When a play cycle is initiated C1 is discharged completely by S3c so that there is zero voltage at the base of TR6; this means that TR6 is cut-off. The collector of TR6 is therefore at the supply voltage, and TR7 is fully driven via R20. Although TR7 is fully conducting, its collector is at approximately 3V

because of the voltage drop across the emitter resistor, R19.

As the play cycle continues the voltage at C1 builds up until a point is reached where TR6 is conducting sufficiently for its collector voltage to fall to such a level that TR7 is less than fully driven. Then a very rapid regenerative switching action occurs so that TR6 becomes fully conducting and TR7 cut-off. The collector of TR7 is now at the supply voltage, and TR8 is driven via R22 so that the astable oscillates.

Depressing a key as already explained causes C1 to start discharging. When the voltage on C1 has fallen to such a level that TR6 is just less than fully driven, then another regenerative switching action occurs, and the trigger circuit reverts to its former state, so that the signal stops. The voltage on C1 which causes the trigger to switch off is considerably lower than the voltage on C1 which causes the trigger to switch on. It takes C1 approximately ten seconds to discharge from the higher to the lower voltage, so that there is a delay of about ten seconds between the depressing of a key and the cessation of the signal.

ASTABLE

The signal note is produced by a conventional astable multivibrator formed by TR8 and TR9. The only unusual feature is that the emitters are connected to the negative line through R24, which is bypassed for a.c. signals by C4. This establishes a voltage platform of 4.5V above which the astable works. This is necessary because the base of TR8 must be held negative with respect to the emitter when the trigger is in its off condition if the astable is not to oscillate and, as has been shown, the trigger actually outputs 3V in its off condition.

The collector load of TR9 is the transducer (X1) which produces the sound. This transducer is an ear-piece from a pair of headphones—the d.c. resistance was measured at 700 ohms.

CONSTRUCTION

With this kind of circuitry there is nothing critical about component layout or wiring. The neat metal case, complete with hammer-grey finish and handle, can be obtained from Henry's Radio. All the components are mounted on the top panel except the

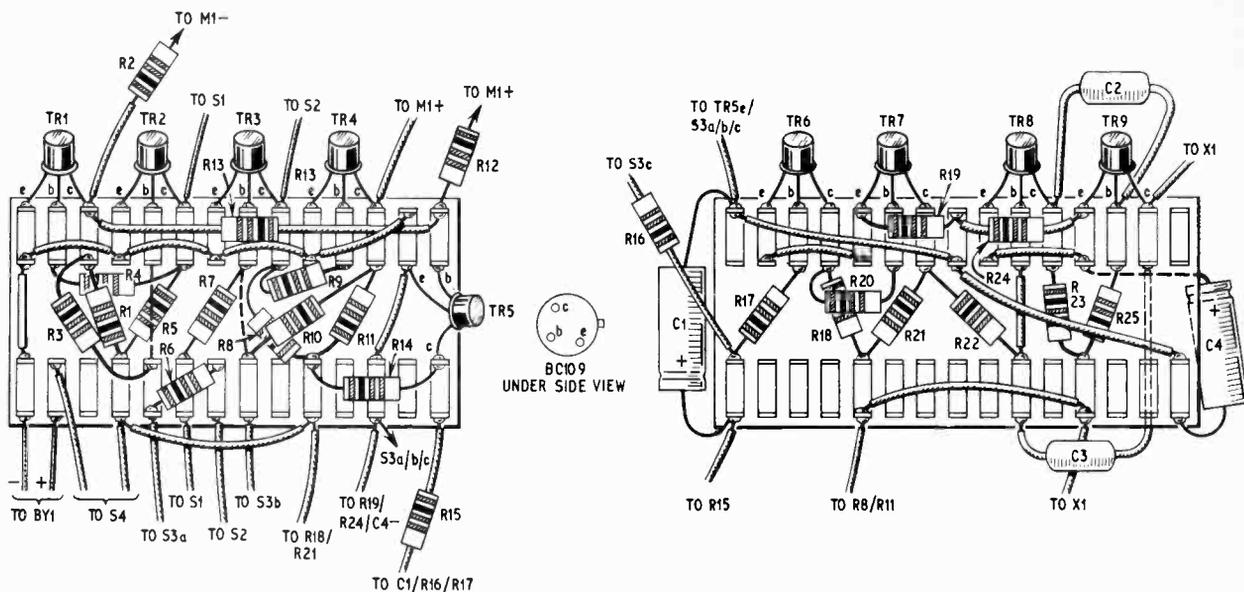


Fig. 3. Tag board wiring diagram

COMPONENTS . . .

Resistors

R1	3k Ω	R14	3k Ω
R2	91k Ω	R15	100k Ω
R3	300k Ω	R16	47 Ω
R4	300k Ω	R17	300k Ω
R5	3k Ω	R18	12k Ω
R6	300k Ω	R19	1.5k Ω
R7	300k Ω	R20	91k Ω
R8	3k Ω	R21	3k Ω
R9	300k Ω	R22	68k Ω
R10	300k Ω	R23	680 Ω
R11	3k Ω	R24	680 Ω
R12	300k Ω	R25	68k Ω
R13	300k Ω		

All $\frac{1}{2}$ W, $\pm 5\%$ carbon

Capacitors

C1	125 μ F elect. 10V
C2	0.015 μ F polyester
C3	0.015 μ F polyester
C4	320 μ F elect. 6.4V

Transistors

TR1-9 BC109 (9 off)

Switches

S1	Morse key
S2	Morse key
S3	3 pole push-to-make pushbutton
S4	S.P.S.T. toggle

Miscellaneous

M1	100-0-100 μ A moving coil balance meter
X1	700 Ω earpiece
BY1	PP6 9V battery
Case	6 $\frac{1}{8}$ in \times 4 $\frac{1}{8}$ in \times 2 $\frac{1}{8}$ in
Wooden base	11in \times 5 $\frac{1}{2}$ in \times $\frac{1}{2}$ in
Tag strips	14-way and 15-way (2 off)
Wire and 4B.A. fixings	

battery S1 and S2. With a total current requirement of about 18 milliamps it was found necessary to use a fairly large 9V battery; a PP6 is the largest that can be accommodated. The battery can be cemented down inside the box, taking care that there is sufficient clearance for the top panel components.

Most of the circuitry is constructed on two tag strips, shown in Fig. 3, one for the bistables and NOR gate, the other for the trigger and astable. The one for the trigger and astable is mounted over X1 and the two boards are wired to the remaining components as shown in the photograph.

A convenient small meter was found in the form of an edgewise-reading balance meter. This is all that is necessary since it is only the direction of the pointer swing that needs to be observed. The meter must have a 100-0-100 microamp movement. Keys S1 and S2 are mounted on the right and left sides of the box respectively. The case and the keys are screwed to a piece of $\frac{1}{2}$ inch thick wood that forms a solid base. The underside of the base can be covered with material to prevent it scratching polished surfaces.


CONCLUSION

Some people are naturally quicker in their responses than others. However, nobody is entirely consistent, and with most contestants quite a number of "rounds" are necessary before one begins to establish a definite superiority. Even with ill-matched contestants, the mismatch is not evident until put to the test.

With well-matched contestants games can be very tense. Concentration appears to be the key to success.

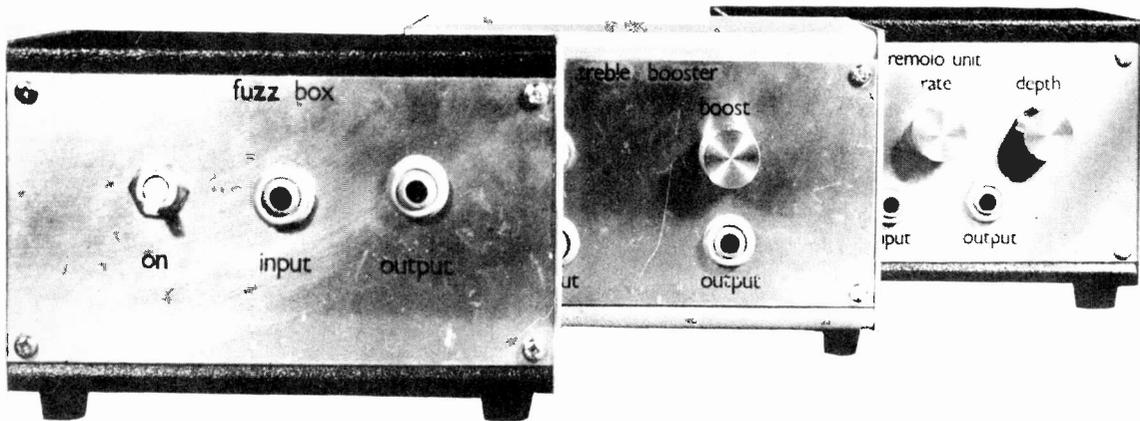Overall then electronic snap is an exciting game, inheriting from its predecessor the unique property, among competitive games, of testing primarily speed of response.





FUZZ BOX

The last of three articles on special effects units for guitars

By A. Russell

THE effect of fuzz is to provide change in the tone produced of a guitar or other sound source so adding colour or interest to a particular musical statement.

The particular unit to be described uses cheap and readily available components and compares very favourably, both in cost and performance, with its commercial counterpart.

FUZZ PRODUCTION

In the fuzz unit circuit of Fig. 1 the pre-amplifier TR1 magnifies the incoming signal via the socket JK1 and this is passed in turn to a Schmitt trigger consisting of TR2 and TR3.

The action of this circuit is to amplify and square

up the signal thus adding distortion to give the characteristic fuzz sound.

To protect the base/emitter junction of TR2 from reverse bias breakdown a diode, D1, is connected.

TONAL VARIATIONS

To introduce some variation in tone a low pass filter C3 is connected to the negative line from C4. The function of this is to shunt some of the higher frequency components of the square wave and so the tone of the output depends upon its value.

In the prototype a 0.22 μ F capacitor was used to provide a fairly mellow tone. If the value of this is decreased to 0.1 μ F or lower, the tone becomes harsher. Obviously, the choice here will depend on personal requirement.

CONSTRUCTION


Small circuit components are mounted and wired on a 3 $\frac{1}{2}$ in \times 2 $\frac{1}{4}$ in piece of Veroboard as shown in Fig. 2.

It should be noted that input and output leads from the control panel sockets are screened so as to prevent hum pick-up which might cause unwanted triggering of the Schmitt circuit.

THE UNIT IN USE

When using the unit, it should be borne in mind that while the guitar volume control will not affect the level of fuzz produced, if it is set too low the Schmitt will not trigger and there will be no output to the amplifier at JK2 at all.

It is possible to make a lot of unpleasant noise with a fuzz unit. This can be avoided by never playing "fuzzed" chords or over indulging in the effect in musical passages where fuzz just does not fit in. ★

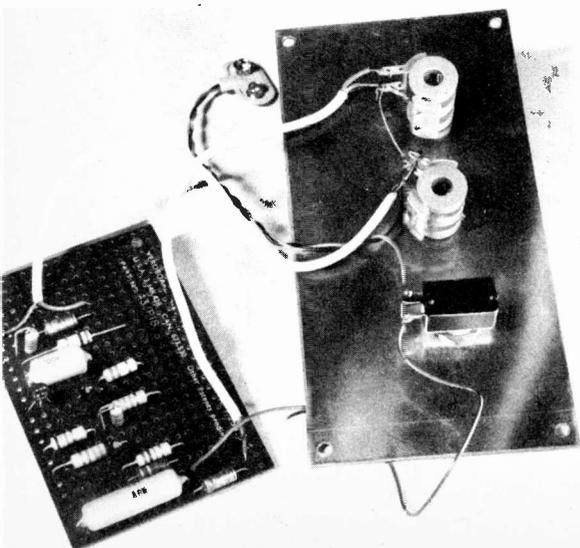

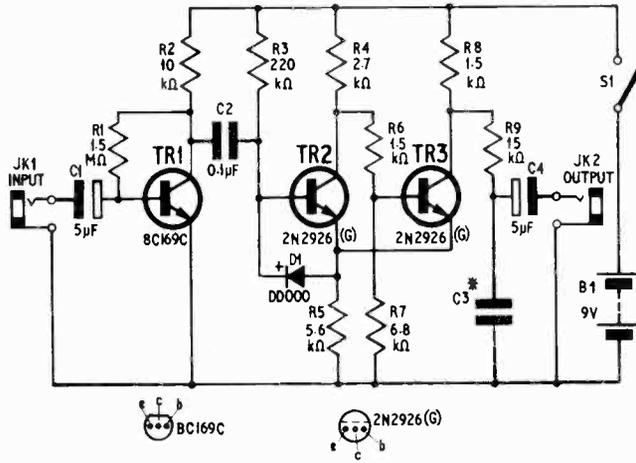


Fig. 1. Circuit diagram of Fuzz Box

COMPONENTS . . .

Resistors

R1	1.5M Ω	R6	1.5k Ω
R2	10k Ω	R7	6.8k Ω
R3	220k Ω	R8	1.5k Ω
R4	2.7k Ω	R9	15k Ω
R5	5.6k Ω		

All 10%, $\frac{1}{4}$ watt carbon

Capacitors

C1	5 μ F elect. 25V
C2	0.1 μ F polyester
C3*	See text
C4	5 μ F elect. 25V

Transistors

TR1	BC169C
TR2/TR3	2N2926 (G) (2 off)

Diodes

D1	DD000
----	-------

Miscellaneous

JK1, JK2 Standard jack sockets (2 off)
 S1 On/off toggle switch. Control knobs
 Veroboard $3\frac{1}{2}$ in \times $2\frac{1}{2}$ in 0.15in matrix, B1-PP3
 9V battery. Battery connectors

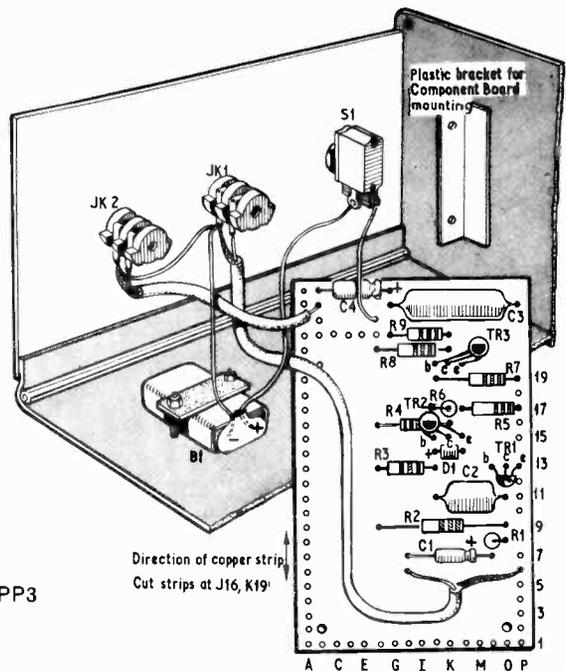


Fig. 2. Veroboard component assembly details and control panel interwiring

ELECTRONORAMA

In Search of the Quark

Two of these 75in flash tubes from the English Electric Valve Company are used at Leeds University to photograph the tracks of cosmic rays as they pass through a 100 cubic ft cloud chamber. From these photographs it is hoped to identify minute particles of matter called "quarks".



Computer Helps Conservation

DIGITAL Equipment Computers are being used by the Natural Environment Research Council in their fight to conserve British wildlife.

Installed at the Marlewood Research Station in Lancashire, the computer is used to process data, particularly in connection with research into soil chemistry, Dutch Elm Disease, and a nationwide survey of woodland.



Atomic Pacemaker

SURGICAL care is needed in the assembly of electronic modules for a new heart pacemaker at the Raytheon Company. Powered by nuclear energy, the new pacemaker will have a life expectancy of ten years as compared with the two years of the present type powered by mercury batteries.

Fluoridation Control

A NEW type of meter relay from Sifam is to be used to control fluoridation by the South Derbyshire Water Board. The meter monitors the water flow and has two extra pointers which can be preset so that if the flow drops below the lower setting, fluoridation is stopped. When it again reaches the upper setting, fluoridation is resumed.



NEWS BRIEFS

Electro-Optics International '72

ALTHOUGH this year's exhibition at Brighton brought no startling new breakthroughs, it did highlight the rapid developments going on in this relatively new field.

Present in profusion were GaAsP light emitting diodes (LEDs) reduced in size from the clumsy packaging of only a few years ago to their present size, no larger than a transistor.

LEDs are now finding applications particularly in the field of communications. ITT showed how LEDs could be combined with low-loss fibre-optic cable to provide an efficient information transmission system even in noisy environments such as an aeroplane.

LEDs also appeared in a wide variety of alphanumeric displays. ITT, Monsanto, Motorola and Ferranti all had their latest devices on show.

Liquid crystals are also being developed for alphanumeric displays and in the next few months they should emerge as strong competition to the LED displays.

Vacuum tubes are still holding their own in area of low-level light detection. Also on show were thermal imaging devices which give a T.V. picture of the temperature distribution of the objects they are viewing. Useful both for medical diagnosis and night security.

Lasers also abounded in applications too numerous to mention. Solartron showed a novel use for them in the form of their Simfire system. The laser is used to simulate a gun providing accurate and safe determination of a marksman's skill.

It was clear from the show that there can no longer be any clear dividing line between the two areas of optics and electronics, so readers should be prepared to find more light creeping into their future projects.

Exhibition Dates

I.E.A. (Instruments Electronics and Automation) will be held at Olympia, London, May 8 to 12.

International Audio Festival and Fair will be held in the Grand Hall, Olympia, London, October 23 to 28.


Fly Fishing

A NEW RCA low-light level TV camera that can detect from an aircraft the dim glow of sea plankton being disturbed by fish is being used for night-time ocean surveys.

The camera, which employs an imaging tube similar to the one used in *Apollo* moon cameras, is being flown at altitudes up to 6,000 feet by the U.S. National Marine Fisheries Service in a new approach to the detection and assesment of ocean fish.

Besides detecting fish from the plankton glow, the camera can record the outline of the school. By analysing the size and shape of the outline, scientists hope to be able to determine the species of the school.

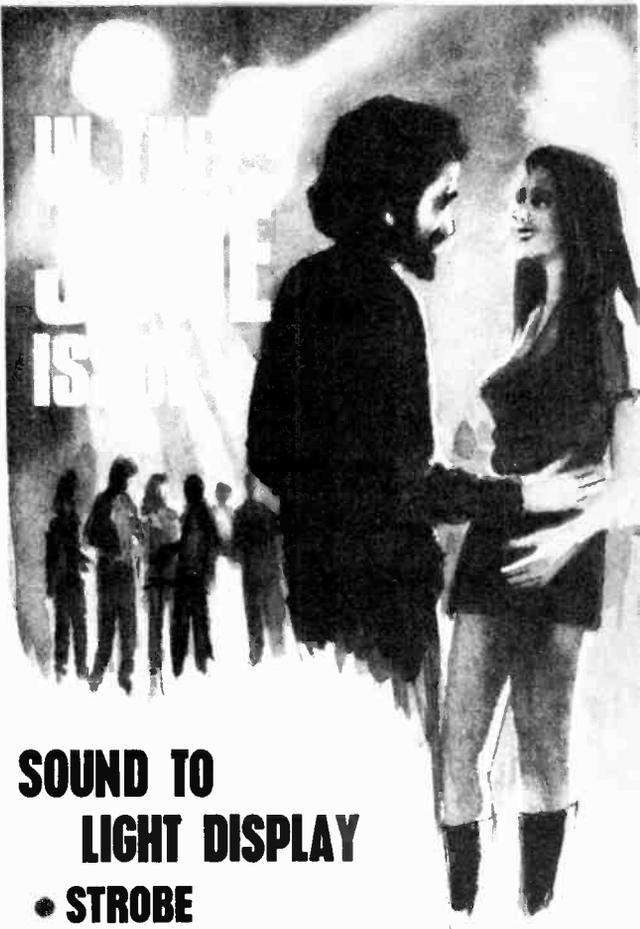The new method of detecting fish is expected to provide scientists with a means of tracking and analysing the distribution and abundance of many types of marine resources. If tests are successful, a commercial version of this camera could one day be used by the fishing industry. One aircraft equipped with such a device might guide a large fleet of boats to the most productive fishing grounds.



SOUND TO LIGHT DISPLAY

- STROBE
- SOUND SYNC
- STROBE + SOUND SYNC

A versatile light effects unit for driving one lamp channel from one sound source; this unit adds an extra "strobe" dimension to dances, discos and parties. It will handle banks of lamps up to 750 watts in three modes using a thyristor controller.

2 TO 20 MINUTE PROCESS TIMER

This useful timer can be used for a multitude of timing operations where a 2 to 20 minute period is required. It can also be arranged to provide a delay of a preset period before switching on any apparatus.

ALSO a special feature on

STEREO RECEPTION


PRACTICAL
ELECTRONICS

June issue on sale May 12

P. E. GEMINI

PART TWO

STEREO TUNER

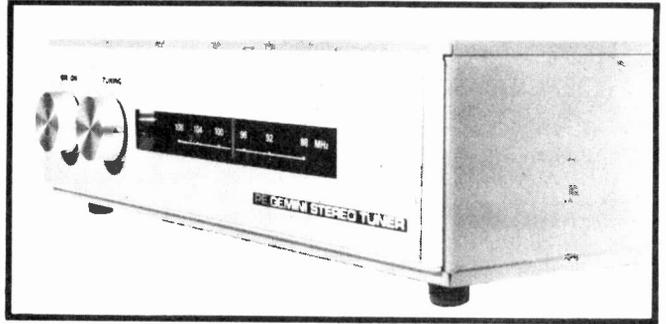


BY D.S.GIBBS & I.M.SHAW

LAST month complete circuit details were given with components list. This month the mechanical assembly of the case and tuning drive is given.

METALWORK

The Gemini Tuner is housed in a Contil Mod-2 case, size G; the front and rear grey panels should be cut and drilled as shown in Figs. 13a and 13b. Two extra panels, a dummy front panel and an inner front panel, are required and these should be cut from 18 s.w.g. aluminium as shown. Note that the slot in the dummy front panel is $\frac{1}{4}$ inch narrower and $\frac{1}{4}$ inch shorter than the slot in the case itself to facilitate the mounting of the Perspex tuning scale.

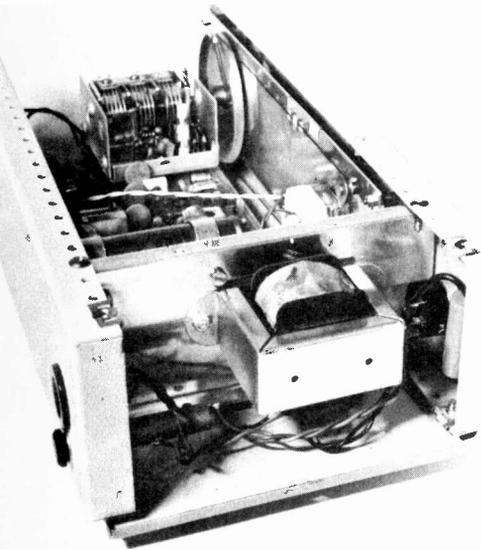

This is glued to the back of the dummy front panel and protrudes through the hole in the case. When the holes have been cut the edges of the panel should be smoothed off and it can then either be rubbed with wire wool (using soap and water) to give a "brushed" finish or sand blasted to give a "satin" finish.


The aluminium inner front panel (Fig. 14) supports the tuning drive, the tuning meter and the stereo indicator lamp. The rectangular hole with the two fixing holes on either side are specifically for the type of tuning meter used in the prototype (Type MH-25B) and modifications will be necessary if a different tuning meter is used. The same applies to the $\frac{1}{8}$ inch hole for the stereo indicator lamp. The prototype used a Thorn 6V 60mA miniature pilot lamp, but any similar lamp can be used if the mounting hole is changed to suit. A 12V 40mA lamp can be used if R32 is omitted. The finished panel should be cleaned and can then be sprayed black with matt black car aerosol paint, or alternatively, brush painted with blackboard paint. Don't forget to cover up the meter fixing screws with a dab of paint. The tuning meter is mounted with two countersink 8B.A. screws. A piece of 2 inch wide matt black adhesive tape can be used instead of paint, if desired.

Two small brackets are required to hold the scale lamps in position and these should be cut from 18 s.w.g. aluminium as shown in Fig. 15.

The tuner head spindle should be cut down to $\frac{1}{16}$ inches taking great care not to allow the filings to get into the tuner head assembly. The tuning drum should be positioned on the shaft so that the slot travels through the arc shown in Fig. 16. The fixing screws on the drum should be facing the tuner head case.

TUNING SCALE AND LABELLING

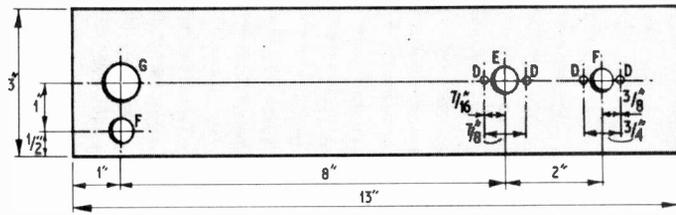The scale is cut from a piece of $\frac{1}{16}$ inch clear Perspex and is labelled on the front with white Letraset or on the inside with "reverse lettering" Letraset, to contrast with the black background. The calibration is shown in Fig. 17. After lettering the scale should be protected by applying two *light* coats of Letracote



DRILL SIZES

- C $\frac{1}{8}$ in dia.
- D No. 34 drill
- E $\frac{3}{8}$ in dia.
- F $\frac{1}{2}$ in dia.
- G $\frac{1}{2}$ in dia.

Fig. 13a. Rear grey panel looking at inside

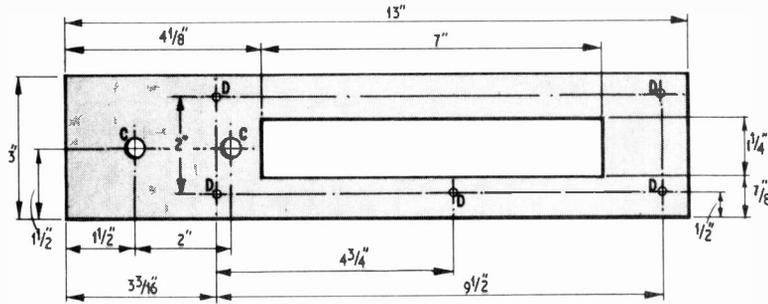


Fig. 13b. Front grey panel looking at inside

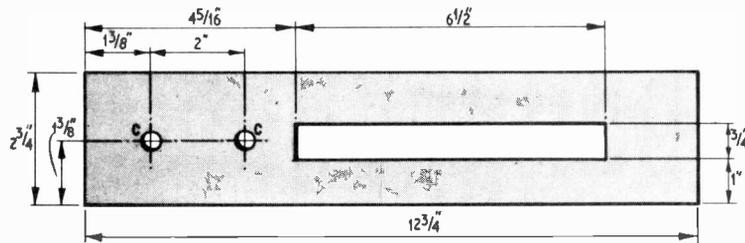


Fig. 13c. Front aluminium escutcheon plate

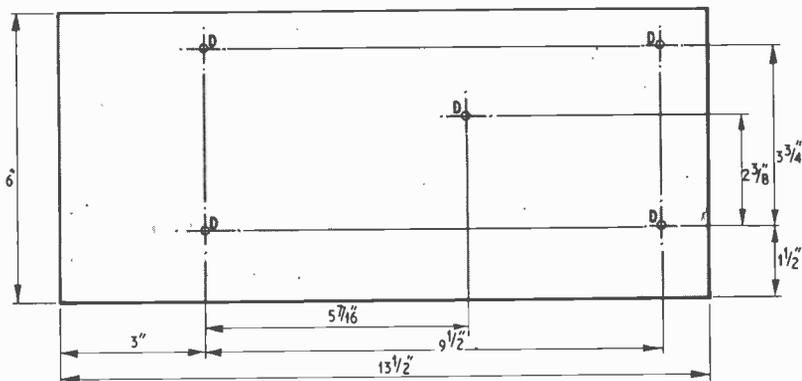


Fig. 13d. Blue base-plate looking at inside

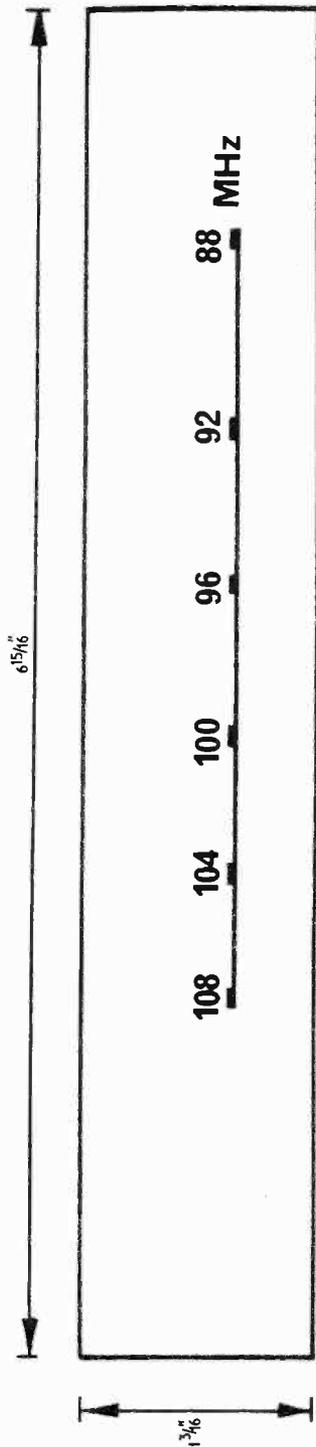


Fig. 17. Full size drawing of the tuning scale made from Perspex

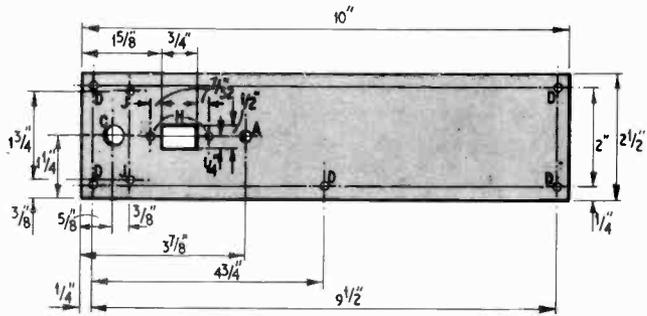


Fig. 14. Tuning drive assembly is mounted on this aluminium plate (front view)

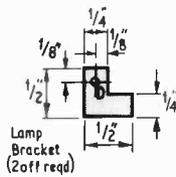


Fig. 15. Two of these aluminium brackets are required to mount the dial lamps

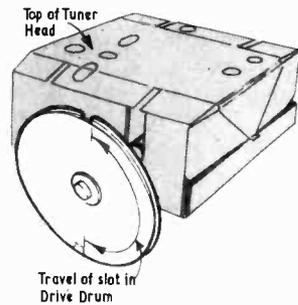


Fig. 16. Position of drum on tuner head

DRILL SIZES

- A $\frac{1}{8}$ in dia.
- B No. 27 drill
- C $\frac{1}{4}$ in dia.
- D No. 34 drill
- H No. 44 drill
- J $\frac{1}{16}$ in dia.

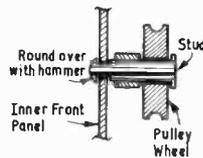


Fig. 18. Section through the pulley assembly riveted to holes J in the plate in Fig. 14

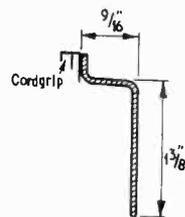


Fig. 19. The cursor is bent and trimmed to length as shown here


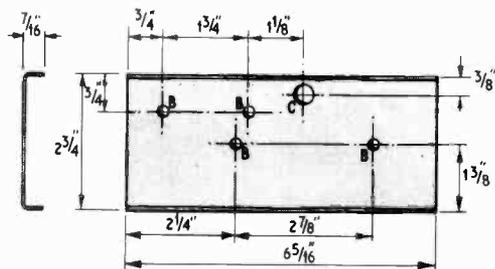


Fig. 20. This screening plate (available with the case) is drilled as shown here

The finished tuning drive assembly

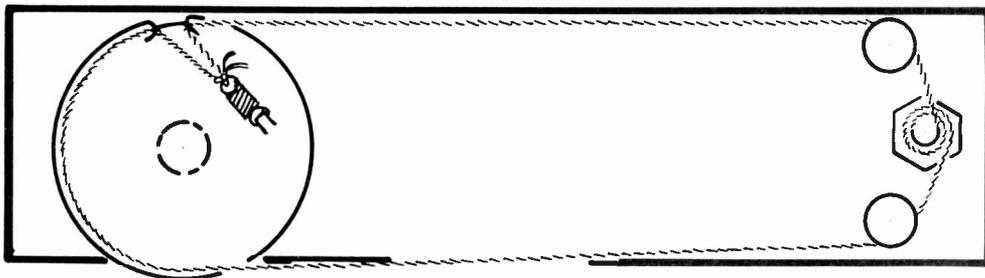

gloss spray. Do not use heavy coats or household varnish as this will cause unpleasant discolouration of the scale.

The dummy front panel should be carefully cleaned and given one coat of Letracote spray before applying the lettering. This gives the panel a smooth surface which the lettering can adhere to better than the bare aluminium. After applying the lettering the panel should be given two further light coats of spray to protect it.

(Letraset and Letracote spray are available from most shops specialising in artist's and drawing materials, and also from some stationers.)

DIAL DRIVE ASSEMBLY

The Perspex scale can now be glued to the rear of the dummy front panel with "Clear Bostik". Take great care not to allow the adhesive to show on the front face and place the scale so that it can pass through the hole in the case.

The scale lamps (i.e.s. with nylon holders) can now be fitted to the inside top of the front panel, using the existing perforated holes to fix the two brackets at each end of the slot. The two lamps are then wired in series, using a length of very thin ((7/0076) twin twisted wire, ready for connection to the printed circuit board later.

The two pulleys for the drive cord should be fixed to the inner front panel as shown in Fig. 18 (note: do this before painting the panel) and then the tuning meter, cord drive spindle, and stereo indicator lamp should be fitted to the finished panel. This panel is mounted on five $\frac{1}{4}$ inch spacers to the rear of the front panel of the case, using 6 B.A. counter-sink screws. Make sure that the heads of the screws are properly recessed, otherwise they will interfere with the fitting of the dummy front panel. The dummy front panel can then be glued into position on the front of the case, taking great care to align the holes correctly. Use clear Bostik, Evostik, or double sided adhesive tape.

The mains transformer and capacitor C39 can now be mounted on the small internal chassis supplied with the case, and the sockets, fuse holder, and switch mounted on the rear and front panels of the case, as shown in the photographs. The box can then be assembled except for the two sides and the top.

POINTER

The Jackson type SL6 pointer is supplied straight, and to avoid parallax error it must be carefully cut and bent as shown in Fig. 19. After bending, fit it on to the inner front panel and make sure that it can slide along the top edge freely. Any fouling can be rectified at this stage by bending to suit. The pointer should be as close to the front

panel as possible without touching. This pointer is supplied with a white finish, but it can be made to stand out very brightly by giving it a coat of "Fire Orange" fluorescent paint.

CHASSIS PLATE

The chassis plate shown in Fig. 20 is supplied with the case and needs drilling. This plate is used to screen the a.c. power section from the rest of the tuner.


MORE ABOUT COMPONENTS

The slide pointer dial drive assembly is made up from components made by Jackson Bros. They are as follows:

- Pointer type SL6, No. 4580
- Drum $2\frac{1}{4}$ in dia., No. 3955
- Pulley assembly $\frac{1}{2}$ in dia. (2 off), Nos. 4534, 4879, 4880
- Cord drive spindle, Type H, No. 5081
- Spring for drum, No. 4587
- Nylon cord

The Tuner Head is a pre-aligned unit which should never be altered or tampered with; it can be obtained from A.M.C. Electronics Ltd. The coil L2 and Vernitron transfilters are generally available through component suppliers including Home Radio. Neosid coil formers are also generally available through component specialists who advertise in this magazine.

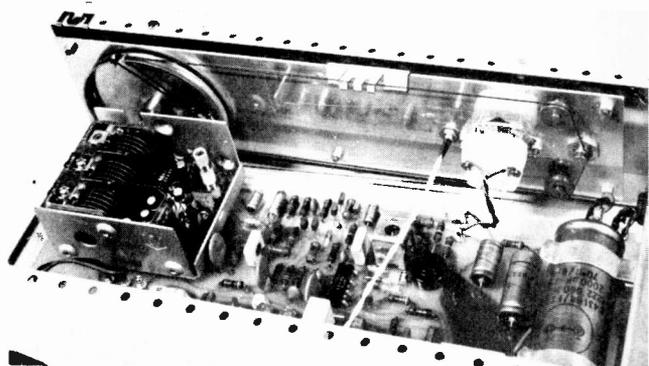We regret that due to space restrictions the full details of the component assembly and printed circuit board is held over to next month.



SMALL POWER

TRANSFORMERS

How to design and construct

By P. Duncan

A SMALL power transformer is constructed by winding a coil of insulated copper wire and assembling a treated iron laminated core into it.

The coil can be wound without the aid of a winding machine if certain simplified hand methods are adopted. Assembling the core is no trouble. Wire, core laminations, and other constructional material can be obtained either from clean discarded transformers or new from stockists.

It is feasible, therefore, for the electronics constructor to wind and assemble his own transformers, if the basic principles are grasped.

Before any winding is attempted, however, it is necessary to determine the number of turns, the gauge of wire, and the size of core. A method will be described in this article that reduces the electrical design of transformers to a few calculations.

It is also feasible, therefore, for the constructor to originate his own transformer designs. And when

he does theoretical work in addition to doing the winding, he has the deep satisfaction of completely creating at least one component in his equipment.

THE BOBBIN

The easiest coil winding method employs a flanged bobbin. Bobbins may be made from any stiff insulating material such as cardboard or s.r.b.p. The thickness of this material should not exceed $\frac{1}{16}$ in. Six pieces of the material are cut, two large pieces for the cheeks, and four smaller pieces for the former. An assembled bobbin is shown in Fig. 1. Polystyrene cement or impact adhesive may be used to hold the bobbin together, but must not be allowed to come into contact with the enamel insulation on the copper wire.

Dimensions for the various bobbin pieces are given in Table 1. A slot should be cut, or a line of holes drilled, in each cheek before assembly to

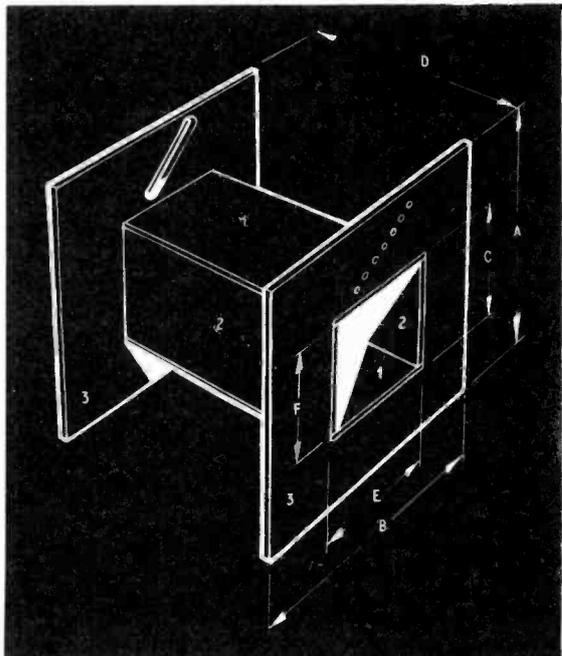


Table 1. DIMENSIONS OF BOBBIN PARTS (inches)

Lamination	A	B	C	D	E	F
$\frac{1}{4}$	Stack +1.250	1.47	Stack +0.187	1.094	0.906	Stack +0.062
$\frac{1}{8}$	Stack +1.500	1.72	Stack +0.187	1.281	1.031	Stack +0.062
1	Stack +1.625	1.97	Stack +0.187	1.469	1.156	Stack +0.062
$1\frac{1}{4}$	Stack +2.000	2.47	Stack +0.187	1.844	1.406	Stack +0.062
$1\frac{1}{2}$	Stack +2.375	2.97	Stack +0.187	2.219	1.656	Stack +0.062
$1\frac{3}{4}$	Stack +2.750	3.47	Stack +0.187	2.594	1.906	Stack +0.062

Fig. 1. The bobbin is made up from pieces cut from $\frac{1}{16}$ in s.r.b.p. sheet or thick cardboard and glued together. Slots or holes in the cheeks (3) are to allow lead-out wires to be passed out

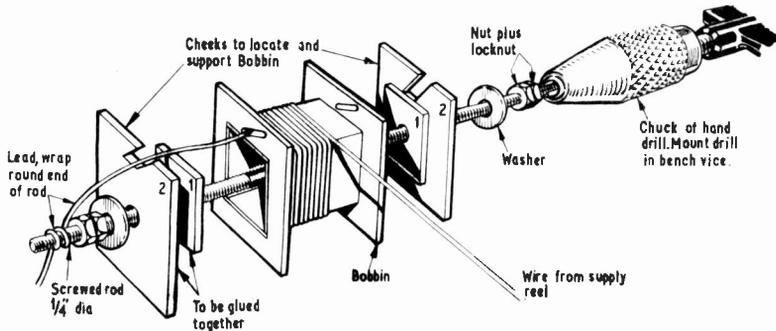


Fig. 2. A winding jig is made up so that Parts 1 fit inside the bobbin and the Parts 2 prevent the cheeks bulging. Studding and nuts clamp the two ends onto the bobbin; both pairs of Parts 1 and 2 are glued together. Tightness is very important, without damaging the bobbin, to prevent the bobbin assembly slipping. Spigotted washers or key-ways would help

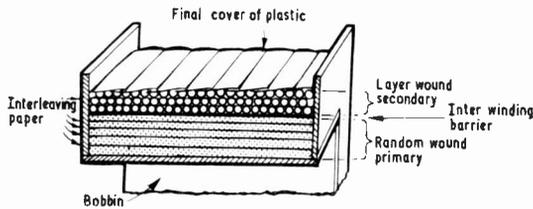


Fig. 3. Cross-section view of a transformer winding

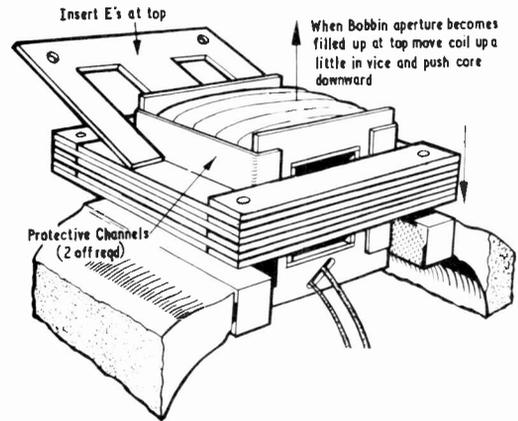


Fig. 5. Method of inserting laminations alternately. The insulating coating should face the same way throughout

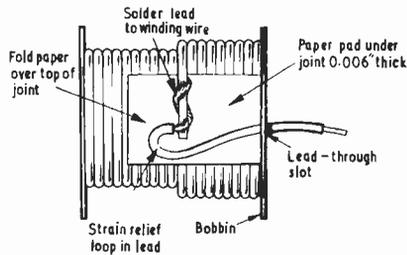


Fig. 4. Method of terminating the winding wire with very thin flexible p.v.c. covered wire. Remove about $\frac{1}{2}$ in of enamel from winding with very fine emery paper. Do not allow paper pad, lead wire, or soldered joint to slide from top end of winding down the side of the winding where it would take up vital space and prevent the E's from fitting over the sides of the completed coil

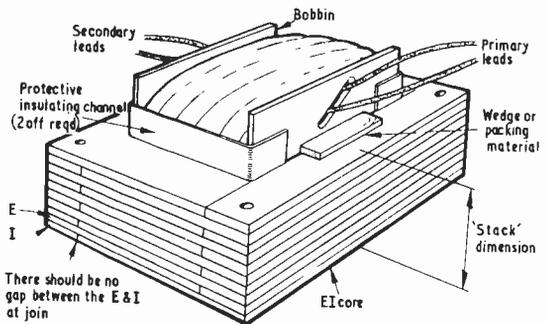


Fig. 6. The finished winding and lamination assembly

allow the connecting leads (or taps) to be brought out from the windings. If a cardboard bobbin lacks rigidity it may be strengthened by brushing with varnish and allowing to dry. Any sharp corners on the former should be rounded with a fine file to avoid damage to wire insulation.

WINDING DEVICE

The bobbin may be wound with the help of a hand drill supported in a bench vice. The bobbin is held in the chuck by a piece of studding or a long bolt. The set up is shown in Fig. 2. The supporting cheeks shown in Fig. 2 are cut from plywood. Part 1 of each cheek should just fit inside the bobbin; part 2 of each supporting cheek is cut as large as the bobbin cheek but must have a notch adjacent to the lead-out slot. Parts 1 and 2 are glued together.

Keeping count of the number of turns during winding is simplified if only the revolutions of the drill handle are noted. The count must then be multiplied by the gear ratio of the drill to find the number of turns on the bobbin.

The number of turns need not be exact. Even professional manufacturers with automatic machines only work to a turns accuracy of $\pm 2\frac{1}{2}$ per cent. That is, a winding that should have 1,500 turns is

considered satisfactory if it actually contains anything from 1,463 to 1,537 turns.

THE WINDING

The wire should be close wound on to the bobbin in flat even layers, each layer being filled out until the end turn of wire touches and is supported by the bobbin flange. After each layer of wire, a turn of paper the full width of the bobbin and 0.001 to 0.003in thick is inserted. "Bank" grade typing paper is suitable. The paper should also touch the bobbin flanges at each side, and it should go round the coil $1\frac{1}{4}$ times so that the overlap may be glued. A coil may therefore be built up from alternate layers of wire and paper. Pile winding and crossed turns of thick wire should be avoided if possible to prevent the risk of shorted turns. The secondary winding shown in Fig. 3 illustrates this method.

The method of winding, however, depends on the gauge of wire. It is easy to wind 20 s.w.g. wire with every turn lying neatly alongside its neighbour, but it is not as easy to achieve this with a fine wire such as 30 s.w.g.

RANDOM WINDING

Fine wires may be random wound (Fig. 3). In random winding the wire is filled into the bobbin in much the same way that thread is filled into a sewing machine shuttle, except that it is essential not to allow hills and valleys to form on the surface of the winding, otherwise all the turns will not fit into the bobbin.

From insulation requirements a random winding must be divided into sections. There is a maximum number of turns that can be included in each section. Table 3, column 10, gives the maximum number of turns for each core size.

A section in a random winding is created by inserting a turn of the same thin interleaving paper (0.001 to 0.003in) that is used in layer winding. The interleaving paper thickness suggested for use with the various wire gauges in Table 2, column 4, should therefore be used whether the coil is to be layer or random wound. All thin wire windings start and finish with very thin flexible wire connections that are well insulated. Do not use self-adhesive clear tape for insulation or the enamel is likely to be corroded by the adhesive. Tapped windings should also be connected to terminating wire and insulated. Finely soldered joints are always recommended, the enamel being removed with fine emery paper.

LEADS

Transformer windings must be connected to the source of power and to the load circuit. This is best accomplished by flexible leads whether a terminating tag strip is used or not. Leads should provide a good electrical connection and should also be strong enough to withstand handling.

Winding wires of 25 s.w.g. and thicker are strong enough, yet flexible enough in themselves to form lead-out connections. Such a lead may, therefore, be made by extending the winding wire out through the slot in the cheek of the bobbin. This extension may then be covered with sleeving for extra protection. The sleeving should be passed back through the slot so that it becomes anchored within the winding.

If the winding wire is 26 s.w.g. or thinner, then an insulated flexible lead should be soldered on to the first and last turns of the winding. The method

Table 2. SIZES OF ENAMELLED WIRES AND INTERLEAVING PAPER THICKNESS

1 Area sq in	2 Dia. over Enamel	3 Layer Height	4 Paper Thickness	5 S.W.G.
0.000015205	0.0056	0.0066	0.001	41
0.000018096	0.0061	0.0071	0.001	40
0.00002124	0.0066	0.0076	0.001	39
0.00002827	0.0074	0.0084	0.001	38
0.00003632	0.0084	0.0094	0.001	37
0.00004536	0.0093	0.0103	0.001	36
0.00005542	0.0102	0.0122	0.002	35
0.00006648	0.0111	0.0131	0.002	34
0.00007854	0.0120	0.0140	0.002	33
0.00009161	0.0129	0.0149	0.002	32
0.00010568	0.0137	0.0157	0.002	31
0.00012076	0.0146	0.0166	0.002	30
0.00014527	0.0159	0.0179	0.002	29
0.00017203	0.0171	0.0191	0.002	28
0.0002324	0.0190	0.0210	0.002	27
0.0002545	0.0207	0.0227	0.002	26
0.0003142	0.0228	0.0258	0.003	25
0.0003801	0.0249	0.0279	0.003	24
0.0004524	0.0270	0.0300	0.003	23
0.0006158	0.0312	0.0342	0.003	22
0.0008042	0.0353	0.0383	0.003	21
0.0010179	0.0396	0.0426	0.003	20
0.0012566	0.0437	0.0467	0.003	19
0.0018096	0.0519	0.0549	0.003	18
0.002463	0.0602	0.0632	0.003	17
0.003217	0.0683	0.0713	0.003	16

Notes for use with Table 2.

All dimensions are in inches.

Column 1 gives the bare copper area for each wire gauge.

Column 2 gives the overall diameter including the enamel covering.

Column 3 gives the combined layer height of one layer of the wire plus one layer of the suggested interleaving paper from Column 4.

Column 4 suggests the thickness of interleaving paper for use with the respective wire gauge.

of connection to the last turn is shown in Fig. 4. At the start of a winding, the lead is connected to the first turn of the winding wire in the same way, except that the pad of 0.006in paper is placed over the joint. The soldered joint should have no sharp points or edges that would puncture the paper pad.

TAPS

If taps are required on a winding, the winding wire need not be cut. The wire should be scraped clean of enamel with fine emery paper for a short distance and a flexible lead soldered on. The insulating pad of paper must now be folded round the soldered joint so that it insulates the joint from the other turns in the winding both above and below.

It is not essential for a stranded flexible lead wire to have a total copper area equal to the copper area of the winding wire to which it is connected. As a general rule, a popular lead wire such as 7/36

(7/0076), that is, a lead built up from seven strands of 36 s.w.g. tinned copper wire, may be used with all thin winding wires.

THE HEIGHT CHECK

Design Table 3 gives, for each core size (assuming a 1in former), the wire gauge and the number of turns for a 250 volt primary winding. This primary leaves a certain space in the bobbin into which the secondary must fit. Normally, if the bobbin is not overloaded, the secondary will indeed fit.

Unfortunately, for certain combinations of secondary volts and amperes, the secondary will not fit. The build up of winding height for the secondary should therefore be checked before a transformer is wound.

The method of checking the secondary build up is explained in Step 5 of the practical example that follows later.

Table 3. TRANSFORMER DESIGN TABLE, 50Hz

1	2	3	4	5	6	7	8	9	10	11
VA	Lam Size	Lam Stack	Primary Wire	Turns	Turns per Volt Sec	Sq In Per Amp	Bobbin Width	Bobbin Height	Random Turns	Weight lbs
10.0	0.75	0.75	42	2720	13.2	0.000313	0.969	0.105	545	0.19
13.3	0.75	1.0	40	2045	9.65	0.000313	0.969	0.105	410	0.21
16.6	0.75	1.25	39	1635	7.55	0.000313	0.969	0.105	328	0.23
20.0	0.75	1.5	38	1362	6.20	0.000313	0.969	0.105	273	0.25
25.0	0.875	1.0	37	1750	8.22	0.000313	1.156	0.125	351	0.36
31.3	0.875	1.25	36	1400	6.46	0.000313	1.156	0.125	281	0.40
36.5	0.875	1.5	36	1167	5.30	0.000321	1.156	0.125	234	0.43
41.6	0.875	1.75	35	1000	4.50	0.000329	1.156	0.125	200	0.46
41.9	1.0	1.0	35	1532	7.20	0.000325	1.344	0.150	307	0.50
49.3	1.0	1.25	34	1225	5.60	0.000337	1.344	0.150	245	0.54
56.5	1.0	1.5	33	1020	4.60	0.000353	1.344	0.150	204	0.59
63.2	1.0	1.75	32	875	3.88	0.000367	1.344	0.150	175	0.63
70.0	1.0	2.0	30	765	3.36	0.000380	1.344	0.150	153	0.67
85	1.25	1.25	29	1025	4.47	0.000432	1.719	0.195	205	1.00
98	1.25	1.5	28	854	3.68	0.000439	1.719	0.195	171	1.07
112	1.25	1.75	28	734	3.13	0.000451	1.719	0.195	147	1.15
124	1.25	2.0	27	638	2.71	0.000463	1.719	0.195	128	1.22
135	1.25	2.25	26	568	2.41	0.000478	1.719	0.195	114	1.28
147	1.25	2.5	25	512	2.15	0.000492	1.719	0.195	103	1.36
160	1.5	1.5	25	740	3.14	0.000518	2.094	0.242	148	1.90
182	1.5	1.75	24	634	2.68	0.000532	2.094	0.242	127	2.10
202	1.5	2.0	23	555	2.35	0.000543	2.094	0.242	111	2.20
223	1.5	2.25	23	493	2.06	0.000558	2.094	0.242	99	2.30
241	1.5	2.5	22	444	1.95	0.000573	2.094	0.242	89	2.40
276	1.5	3.0	22	370	1.53	0.000602	2.094	0.242	74	2.50
285	1.75	1.75	22	544	2.29	0.000608	2.469	0.289	109	3.30
316	1.75	2.0	21	476	1.99	0.000627	2.469	0.289	96	3.45
344	1.75	2.25	21	420	1.75	0.000648	2.469	0.289	84	3.62
374	1.75	2.5	21	382	1.58	0.000663	2.469	0.289	77	3.80
420	1.75	3.0	19	318	1.31	0.000702	2.469	0.289	64	4.10

Notes for use with Table 3

All dimensions are in inches.

Column 1 is the maximum volt-amp rating for the core given in Columns 2 and 3.

Column 2 gives the size of the centre tongue of the required lamination. This is dimension "A" in the lamination table, Table 4.

Column 3 gives the stack of laminations required. The stack is shown in Fig. 6.

Columns 4 and 5 give the wire gauge (s.w.g.) and turns for a 250V 50Hz primary.

Column 6 gives the turns per volt for the secondary. The secondary voltage should not be greater than 500V.

Column 7 gives the wire area in square inches per ampere for use with any secondary.

Columns 8 and 9 give the space that is available in the bobbin for the secondary winding after the given primary has been wound.

Column 10 gives the maximum number of turns that may be wound in a random section without the insertion of interleaving paper.

Column 11 gives the total weight of wire required for the transformer. The weight of wire required for either a primary or a secondary winding will be one half of this figure.

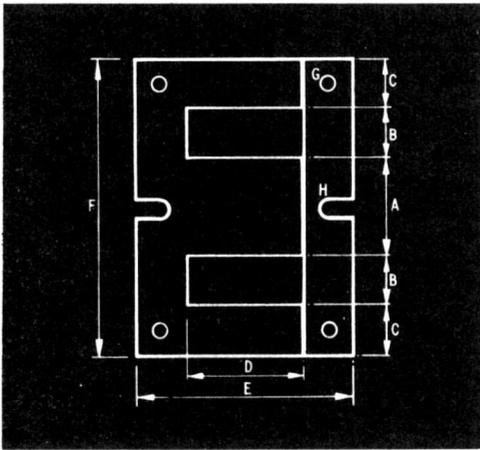


Table 4. DIMENSIONS OF STANDARD EI LAMINATIONS (inches)

A	B	C	D	E	F
0.75	0.375	0.375	1.125	1.875	2.25
0.875	0.437	0.437	1.312	2.187	2.625
1.00	0.5	0.5	1.5	2.5	3.00
1.25	0.625	0.625	1.875	3.125	3.75
1.5	0.75	0.75	2.25	3.75	4.5
1.75	0.875	0.875	2.625	4.375	5.25

Note: Holes G and notches H are provided for mounting purposes.

In calculating the build up, the layer height from Column 3, Table 2, should be used whether the secondary is to be layer or random wound. A layer wound secondary of, say, ten layers of 25 s.w.g. would have a total winding height of $10 \times 0.0258 = 0.258$ in. If the same winding were to be random wound then the same height calculation should be made.

Although the layer of paper that normally follows every layer of wire is omitted in a random winding, it is found that the build up of a random winding is approximately equal to the build up of a layer winding. A random winding has less paper in it, but it becomes untidy as the winding progresses and therefore uses space inefficiently compared to a neat layer winding.

In the case of a high current secondary it is permissible to wind with two or three wires in parallel, but when the height is checked it must be remembered that the winding consists of side by side turns of a multiple wire.

CORE ASSEMBLY

The core laminations are insulated one from the other to prevent the circulation of eddy currents that could overheat the core and damage the transformer.

The most common arrangement for transformer laminations is the pairing of "E" and "I" pieces. Table 4 lists the dimensions of typical EI laminations. For use on 50Hz supplies the lamination thickness should be in the range 0.010 to 0.025 in.

Laminations are usually referred to by the width of their centre tongue which passes through the bobbin. In Table 4, a 1 in lamination is the lamination with dimension "A" equal to 1 in.

When the winding is complete the core laminations are stacked into the bobbin by first inserting the E lamination then the I lamination alternately (Fig. 5). The insulated surface on all laminations must face the same way. The bobbin is filled with E's and I's until it is full, the last piece being a firm fit otherwise excessive hum will result when the transformer is energised. If necessary, the correct degree of tightness can be obtained by tapping a thin card wedge, or some other non-metallic packing material, in at the top of the stack as shown in Fig. 6.

It is necessary to hold the two outside I's in place with the mounting brackets or clamps.

With the E's and I's all in place, the core should be finally squared up by tapping on a flat surface with a small block of wood.

OVERSIZE COILS

It may be found that after a coil is wound the E laminations will not fit into the bobbin because the windings have built up until they bulge beyond the edge of the bobbin cheeks.

An oversize coil is either caused by there being too much wire and paper in the bobbin or it is caused by insufficient tension having been applied to the wire during winding. If the present design method is followed, an oversize coil due to excessive wire and paper should not occur.

Insufficient winding tension merely results in the coil being loose and spongy, and such a coil can be used if the winding is gently compressed before the insertion of the laminations. The vice method is shown in Fig. 5, but is not to be recommended unless extreme care is exercised to prevent the laminations chafing the winding. The best solution really is to strip and rewind the bobbin.

INSULATION

Enamelled winding wire should be used. The enamel, however, is usually only about 0.0005 in thick. Where two wires touch, therefore, the total thickness of insulation between them is 0.001 in (or one thou). The maximum working stress that can be placed on the insulation in a home constructed transformer is about 50 volts per 0.001 in. Hence the reason for splitting a random winding into sections. The sections ensure that not more than 50 volts will ever occur between adjacent wires.

A barrier of insulation 0.010 in thick should be wound on top of the primary winding before the secondary is started. It is usual to build up this barrier from three turns of 0.003 in paper (e.g. thickness of bond typing paper). Fig. 3 shows the location of the insulation barrier between a primary and a secondary winding.

The outer surface of the secondary winding may be protected by covering with one or two layers of insulating paper tape or, better still, cambric. The tape should be pulled tight so that it holds the windings firm within the bobbin.

There is a possibility of the sharp corners on the legs of the E laminations to cut into the surface of

the coil during assembly of the core. It is advisable, therefore, to fit stiff paper channels, 0.010 thick, on each side of the completed coil before inserting the E's. The channels can be seen in Fig. 6. There is no need to put adhesive on the channels; the first E will hold them in place.

Small quantities of electrical insulating paper are difficult to obtain and the enthusiast must improvise. Thin brown wrapping paper, clean writing paper, typewriter paper, office file covers, all are possible alternatives. A matt finish paper is better than a gloss paper because the wire beds into it better.

A dry unprotected transformer will give years of service in a domestic indoor location. But if a transformer is for use in portable equipment, or a damp location, then protection against the ingress of moisture is necessary. Such protection can be obtained by dipping the completed transformer in wax, or by brushing it with varnish. Before dipping or brushing, the transformer should be dried out by warming for two hours in a moderate oven set to 212°F.

There is the possibility, particularly with mains and audio power transformers, for buzzing to occur. This is usually the wire or laminations vibrating in sympathy with the a.c. supply. The best cure is wax dipping using beeswax or paraffin wax.

SPECIFICATION

Before a transformer can be designed the following electrical parameters must be known: (a) the volt-amp rating (VA); (b) the primary voltage; (c) the secondary voltage; (d) the secondary current; (e) the voltage of any taps that are required on either the primary or secondary.

For most small power transformer applications the VA rating of the transformer is equal to the rating of the load in watts.

DESIGN

By making use of Table 3, the design is reduced to the following six steps.

1. A core with a VA rating equal to or greater than the VA rating of the proposed transformer is chosen via column 1.

2. The wire size and the number of turns for the primary are copied from columns 4 and 5.

3. The number of secondary turns is determined by multiplying the secondary voltage by the turns per volt figure from column 6.

4. The area of wire required for the secondary is found by multiplying the secondary current by the current density from column 7. The first wire gauge with an area in excess of this calculated area is then chosen from column 1, Table 4.

5. A height check is made to ensure that all the secondary turns of the chosen wire gauge will fit into the bobbin. Columns 8 and 9, Table 3, give the winding width and height that remains for the secondary winding.

6. If taps are to be included in the windings, the location of each tap is determined and space should be allowed for the extra bulk at terminations.

The complete design procedure is illustrated by the flow diagram in Fig. 7.

EXAMPLE

A transformer was required to power a piece of equipment that was rated at 115 volts, 50/60Hz,

70 watts from 250V 50Hz mains supply. The following specification was required:

Rating: 70VA.

Primary: 250 volts, 50Hz, with taps at 210 volts and 230 volts.

Secondary: 115V, 0.61A, with a tap at 110 volts.

(Note: 0.61 amps = 70VA/115 volts)

The design went as follows.

Step 1. From columns 1, 2 and 3 of Table 3, the first core capable of delivering 70VA is built up from a lin lamination with a stack of 2in.

Step 2. From columns 4 and 5, the primary wire size is 30 s.w.g. and the primary turns are 765.

Step 3. In column 6, the secondary turns per volt is 3.36. Therefore, for 115 volts, the number of secondary turns is $3.36 \times 115 = 386$.

Step 4. The required wire area for the secondary is found by multiplying 0.61A by the current density in column 7. The wire area is therefore $0.61 \times 0.000380 = 0.000232$ square inches. And from Table 2, a wire gauge of 27 s.w.g. is required to meet this area.

Step 5. From column 8 of Table 3, the available winding width between the cheeks of the bobbin is 1.344in (see dimension "A" Fig. 8). From column 2, Table 2, the overall diameter of 27 s.w.g. is 0.019in. Therefore $1.344/0.019 \approx 70$, is the number of turns that may be wound in each layer of the secondary.

If 70 turns go on each layer, and if the total secondary turns are 386, then $386/70 = 5.5$ layers

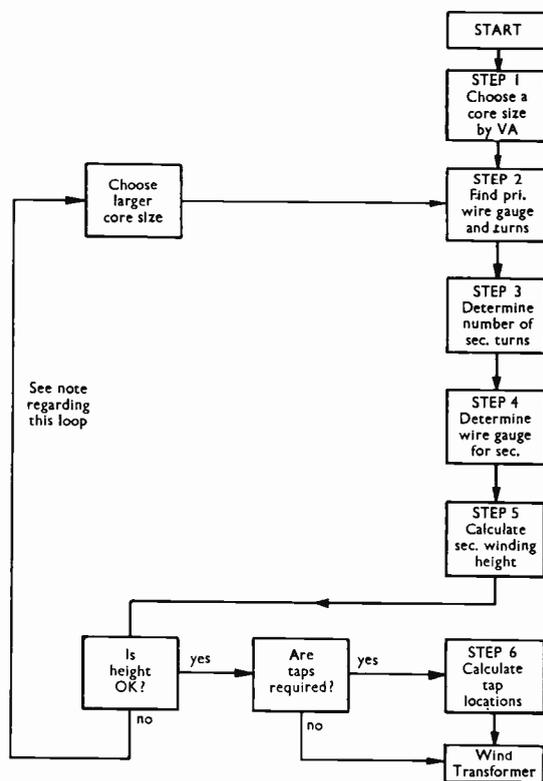


Fig. 7. Flow diagram of design procedure using Table 3. If the winding height calculated for the secondary in Step 5 exceeds the available height given in column 9, Table 3, then the next larger core size should be chosen and the design procedure repeated by looping back to Step 2.

are required to accommodate the secondary winding. But since 0.5 of a layer occupies the same build up in height as a whole layer, then the number of secondary layers must be considered as six.

From column 3, Table 2, the height of each layer of 27 gauge is 0.021in, therefore $6 \times 0.021 = 0.126$ in will be the total build-up in height for the secondary winding. From column 9, Table 3, the height available for the secondary winding is 0.150in (see dimension "B" Fig. 8). There should therefore be plenty of room for the secondary on top of the primary.

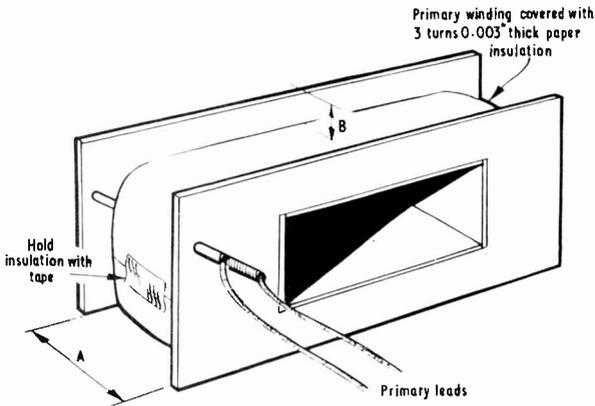


Fig. 8. Designing for optimum bobbin size. Dimension "A" is the available winding width between the flanges of the bobbin for both the primary and the secondary windings. The value of "A" for each core size can be found in column 8, Table 3. Dimension "B" is the winding height remaining for the secondary after the primary has been wound. The value of "B" for each core size can be found in column 9, Table 3

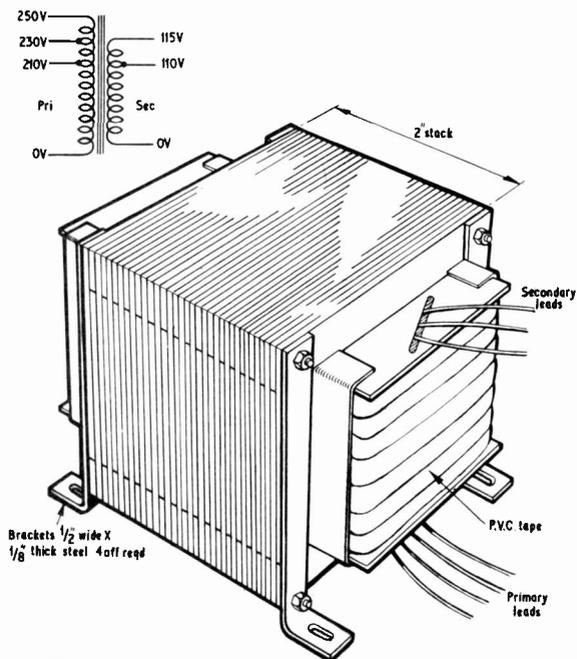


Fig. 9. Finished transformer with mounting clamps

Step 6. The location of a tap is determined by dividing the total number of turns in a winding by the full winding voltage and then multiplying the result by the voltage at which the tap is required.

In this design, the 230 volt primary tap must be made at $(765/250) \times 230 = 704$ turns. The primary 210 volt tap must be made at $(765/250) \times 210 = 643$ turns. And the secondary tap must be made at $(386/115) \times 110 = 369$ turns for 110 volts.

The final design was therefore:

Core: 1in lamination with a 2in stack.

Primary: 765 turns of 30 s.w.g. wire tapped at 704 and 643 turns.

Secondary: 386 turns of 27 s.w.g. wire tapped at 369 turns.

CONSTRUCTION

The bobbin was made from 1/4in cardboard. The primary was random wound in five sections, which required the insertion of a turn of interleaving paper every 153 turns (or every 41st turn of the drill handle since the gear ratio of the hand drill used in the winding was 3.73:1).

Interleaving paper was cut from sheets of new typewriter paper that was 0.0025in thick. P.V.C. insulated lead wire, 7/36, was used for all taps and also at the start and finish of both primary and secondary.

On completion of the primary winding the height remaining for the secondary measured 0.125in. That is, dimension "B" Fig. 8, measured 0.125in. Column 9, Table 3, states that there should be 0.150in remaining for the secondary after the primary has been wound. The primary winding was therefore over-size and occupying more space than it should.

To reduce the excessive coil build up, the secondary was wound as tightly as possible in three random sections. The turns of interleaving paper being inserted at the 128th and at the 256th turn of wire.

On completion of the secondary winding the finished coil was over-size and the E laminations would not go in. The laminating method shown in Fig. 5, however, enabled the insertion of the E's and the core was successfully assembled.

The 0.001in channels that protect the windings during the laminating operation were made from an office folder.

Four lengths of 1/4in steel strap are cut and shaped into mounting brackets. The brackets can be seen in Fig. 9, which shows the final appearance of the completed transformer. Before testing, wire up the primary winding to the 250V a.c. supply via a 3A fuse. Use a reliable meter for checking a.c. voltage tappings.

TESTING

On test, with 250 volts applied to the whole primary winding, the primary taps measured 232 and 211 volts. The open circuit secondary voltage measured 125 volts, with the tap at 119.5 volts.

After allowing two hours running to warm up, the secondary full load voltage measured 116 volts.

In the author's opinion the most exacting part of the construction is the making of the bobbin. The winding, which at first may be thought the major problem, proved easy, and only required about half an hour for each winding.



BI-PRE-PAK



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 50p

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Rec. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts.	50p
H15	30	Top Hat Silicon Rectifiers, 750mA Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

£p		£p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G301	0-13
ACY17	0-20	2G303	0-13
AF239	0-30	2N711	0-50
AF186	0-20	2N1302-3	0-15
AF139	0-30	2N1304-5	0-17
BC154	0-20	2N1306-7	0-20
BC107	0-10	2N1308-9	0-22
BC108	0-10	2N3819FET	0-45
BC109	0-10		
BF194	0-15	Power Transistors	
BF274	0-20	OC20	0-50
BFY50	0-15	OC23	0-30
BSY25	0-13	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-35
BSY29	0-10	OC36	0-37
BSY95A	0-10	AD149	0-30
OC41	0-15	AUY10	1-25
OC44	0-13	25034	0-25
OC45	0-10	2N3055	0-50
OC71	0-10		
OC72	0-10	Diodes	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-09
OC83	0-18	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-15	IN914	0-07

F.E.T. PRICE

BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device.
1-10 30p each, 10-50 25p each, 50+ 20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, 8AY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 3p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 3p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.
IN4004, 500+ at 5p each; 1,000+ at 4p each.
IN4006, 500+ at 6p each; 1,000+ at 5p each.
IN4007, 500+ at 8p each; 1,000+ at 7p each.

FREE CATALOGUE FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS



8 RELAYS FOR VARIOUS TYPES P. & P. 25p £1

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested	Unmarked		
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

Quantity	1-10	10-50	50+
SL403D Audio Amp. 3-Watts	2.00	1.95	1-80
709C Linear Opp. Amp	25p	20p	15p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
SN7490 Decade Counter	50p	45p	40p
UL914 Dual 2 1/2 P Gate	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes; 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.
The Iiffe Radio Valve & Transistor Data Book 9th Edition; 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS


MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

BSR LATEST SUPERSLIM STEREO & MONO

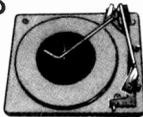Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2" x 11 1/2". Above motor board 3 1/2". Below motor board 2 1/2".



with STEREO and MONO XTAL £8-75 Post 25p.


MONO-COMPATIBLE £7-75 Post 25p. Plays all records

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 2-stage triode pentode valve UCL82, 3 watts output. Tone and volume controls. Rectifier valve UY85. Knobs, with high performance loudspeaker. £4 Post 25p. Response 50-12,000 cps. Sensitivity 200mV.

R.C.S. PORTABLE PLAYER CABINET

£4

Post 25p

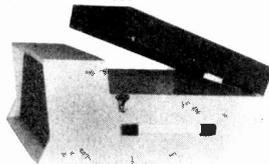

Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 x 15 x 8in Metal fittings. Carrying handle. Popular Colours. Two-tone rexine covered. £10

GARRARD SINGLE PLAY TA Mk II. Ideal Discotheque or Hi-Fi. Complete with stereo/mono plug-in head. £10

GARRARD AUTOCHANGERS with Sonotone Cartridges. Stereo Diamond and Mono Sapphire. Model 1025 £10. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER. Turntable. 4-speed motor and separate pick-up. £4-50

HI-PICK UP ARM. With mono xtal and stylus £1-25. EMI-FI PICK UP CARTRIDGES. Diamond LP/Stereo, Stereo/Mono STA £2-50; GP84 £2-50; GP93 £2. Sapphire Mono GP81 £1-50; Powerpoint LP/78 60p.

E.M.I. WOOFER AND E.M.I. TWEETER KIT

£5-75 POST 25p

Comprising a fine example of a Woofer 10 1/2" 6 1/2" with a massive Ceramic Magnet, 45oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2" square has a special lightweight paper cone and magnet flux 10,000 lines.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9in. £9. POST 25p.

WEYRAD P50 - TRANSISTOR COILS

RA2W Ferrite Aerial... 72p Spare Cores... 3p
Osc. P50/LAC... 33p Driver Trans. LFDT4... 58p
I.F. P50/ACC 470 kc/s... 33p Printed Circuit, PCAL... 58p
3rd I.F. P50/ACC... 33p T.B. Tuning Gang... 65p
P51/1 or P51/2... 33p Weyrad Booklet... 10p
P50/3V... 33p OPT1... 58p
Mullard Ferrite Rod 8 x 1/2in. 20p. 6 x 1/2in. 20p.

VOLUME CONTROLS

Long spindles. Midget Size 8 K. Ohms to 2 Meg. LOG or L.N. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p.

80ohm Coaxial 4p. yd.

BRITISH AERIALS AERAXIAL-AIR SPACED 40 yd. £1-40; 60 yd. £2. PRINGE LOW LOSS 10p. Ideal 825 and colour

8in. ELAC HI-FI SPEAKER

Dual cone plasticated roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 56 cps. 8 ohm impedance. 10 watts music power. £4-80



BLANK ALUMINIUM CHASSIS. 18 a.w.g. 2 1/2in. sides 6 x 4in. 45p; 8 x 6in. 58p; 10 x 7in. 65p; 12 x 8in. 85p; 14 x 9in. 90p; 16 x 10in. 90p; 18 x 10in. £1. ALUMINIUM PANELS 18 a.w.g. 8 x 4in. 9p; 8 x 6in. 15p; 14 x 3in. 16p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 8in. 25p; 16 x 8in. 28p; 14 x 9in. 34p; 12 x 12in. 40p; 16 x 10in. 50p.

1 1/2inch DIAMETER WAVELENGTH SWITCHES. 25p. 2 p. 2-way, or 2 p. 8-way, or 3 p. 4-way 25p each. 1 p. 2-way, or 4 p. 2-way, or 4 p. 3-way 25p. TOGGLE SWITCHES. 8p. 14p; dp. 18p; dp. 23p.

"THE INSTANT" BULK TAP ERASER & HEAD DEMAGNETISER 200/250 v. A.C. £2-35 Post Leaflet S.A.E. 15p

HI-FI STOCKISTS. RETURN OF POST DESPATCH.

RADIO COMPONENT SPECIALISTS

Radio Books & Component Lists 5p. Written guarantee. (Export: Remit cash and extra postage.)

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 8 or 12 or 15 or 18 or 20V d.c. at 100mA. D.C. operation. Size 1 1/2" x 1 1/2". Response 25 c.p.s. to 25 Kc/s, 26 db gain. PLEASE STATE VOLTAGE REQUIRED. £2 Post Details S.A.E. Size 3 1/2" x 1 1/2".

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2". Response 25 c.p.s. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. 90p Post Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS	CAN TYPES
2/350V 14p 250/25V 14p	50-50/350V 85p
4/350V 14p 500/25V 20p	60-100/350V 58p
8/450V 14p 1000/25V 35p	32-32/250V 18p
18/450V 15p 1000/50V 47p	32-32/450V 33p
32/450V 20p 8-8/450V 18p	350-50/325V 50p
50/25V 10p 8-18/450V 20p	32-32-32/350V 43p
50/50V 10p 18-18/450V 25p	100-50-50/350V 48p
100/25V 10p 32-32/350V 25p	

LOW VOLTAGE ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 60, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 6V 25p; 25V 42p; 50V 57p. 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 85p.

CERAMIC. 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0.5 15p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%. 2-2-500pF 8p; 560-2.20mF 10p; 2,700-5,600pF 20p; 6,800pF-0.01, mid 30p each. TWIN GAMES. 200mF 25V 17p; 470p 65p; Slow motion drive 365pF+365pF with 25pF+25pF. 50p; 500pF slow motion, standard 45p; small 3-gang 500 pF £1-80. SHORT WAVE SINGLE. 10pF, 30p, 25pF, 55p, 50pF, 55p. NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1 w, 1/2 w, 1/4 w, 20p; 1/2 w, 5p. 10 to 10M. HIGH STABILITY. 1 w, 2 w, 10 ohms to 1 meg. 10p. Ditto 5%. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2 1/2 watt, 1 ohm to 8.2 ohms 10p.

DECCA DECADEC GARRARD MOTOR UNIT Mk. II

Single play Stereo Mono Deram transcription head and arm. Four speeds. 10 1/2in. turntable. Anti-rumble filter. Bias compensation. Laboratory motor.



SPECIAL PRICE £18-50 Post 25p

METAL PLINTH AND PLASTIC COVER

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest Design. Covered in black leatherette. Antimagnetic. £5-50 Post 25p

MAINS TRANSFORMERS

All post 25p each
250-0-250 80 mA. 6.3 v. 4 amp. £1-50
100-0-100 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a, or 5 v. 2 a. £2-50
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a, or 5 v. 2 a. £3
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. £3-25
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2in. 75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2in. 90p
HEATER TRANS. 6.3 v. 3a. 1 1/2 x 1 1/2in. 60p
Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6.3 v. 1 1/2 amp. 80p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-25
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. £2-25
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. £2-25
5 amp. 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. £2-75
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 150w. £2-25; 500w. £2-25; 750w. £1-20; 1000w. £1-4.
CHARGER TRANSFORMERS. Input 200/250v. 10r 6 or 12v. 1 1/2 amp. £1-30; 2 amp. £1-40; 4 amp. £2-50
FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.
LUCAS 2D5800 Bridge 70v. 5 amp. £1.


E.M.I. 13 1/2 x 8in. TWIN SPEAKERS

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 15p £4-25

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 15p £2-75

Teak Cabinet. Size 18 x 10 x 9in. Post 25p. £5

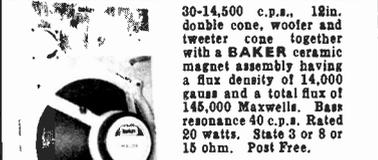ALL MODELS "BAKER SPEAKERS" IN STOCK BAKER 12in MAJOR £9



30-14,500 c.p.s., 18in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

BAKER "BIG-SOUND" SPEAKERS		
'Group 25'	'Group 35'	'Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt 3 or 8 or 15 ohm	35 watt 3 or 8 or 15 ohm	50 watt 8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 12in. dia. or 10in. speaker 20" x 13" x 8in. £8 Post 25p. For 13" x 8in. or 8in. speaker 18" x 10" x 8in. £8 Post 25p. For 10" x 6in. or 8in. speaker 18" x 8" x 8in. £4 Post 25p. LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft.

GOODMANS 6 1/2in. HI-FI WOOFER 8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. £4

ELAC CONE TWEETER The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2in. deep. Rating 10 watt, 3 ohm or 15 ohm models. £1-90 Post 10p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-18Kc/s, 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm 25p. TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm. 2in. 2in. 2in. 35 ohm. 2in. 3in. 15 ohm, 3 1/2in. dia.; 3in. dia.; 6 1/2in.; 8 1/2in. £1 EACH 15 ohm, 3 1/2in. dia.; 6 1/2in.; 7 1/2in.; 3 ohm, 2 1/2in. 3in. 5in. 5 1/2in. LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in. £1-25; 6 1/2in. £1-50; 8 x 8in. £1-80; 8 x 2 1/2in. 90p; 8in. £1-75; 10 x 6in. £1-90. ELAC 10in. 10w. Twin Cone. De Luxe Ceramic 8 ohm £4. RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt, 3 or 8 or 15 ohm models £2 each. Post 15p. VALVE OUTPUT TRANS. 25p. MIKE TRANS. 50:1 25p. 5 WATT WATT RATIO, 3, 8 and 15 ohms 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £39 Post Free



BARGAIN AM TUNER. Medium Wave. £4-50 Transistor Superhet. Ferrite aerial. 9 volt.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recording. Will mix Microphone, records, tape and tuer with separate controls into single output. 9 volt. Stereo version of above £4-50

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £12-50

BARGAIN FM TUNER as above. £8-85 Chassis only, less cabinet.


BARGAIN 3 WATT AMPLIFIER. 4 Transistor £3-50 Push-Pull Ready built, with volume control. 9v.

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES. SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p yd. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p. closed circuit 25p. Crown Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 8p; CAN 5p.

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.1875" x 7/16". Size 3 1/2 x 2 1/2 x 2 1/2in. (Illustrated). Post 15p. £1-25

BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/8" x 3/16". Size. 85p 2 1/2 x 2 1/2 x 1 1/2in. Post 15p

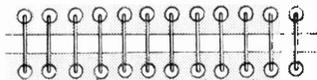CUSTOMERS FREE CAR PARK. CALLERS WELCOME 337 WHITEHORE ROAD, CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) Buses 50, 68, 159. Rail Selhurst. Tel. 01-884-1668



INDUSTRY NOTEBOOK

By Nexus

ELECTRO-OPTICS

Early in 1971 Milton S. Kiver launched his first Electro-Optics exhibition and conference in the UK. It was a smash-hit. Everything was good about it. The venue at Brighton was popular, the technical conference was above suspicion with many world authorities speaking and listening, the turn-out of trade exhibitors was first-class, the attendance figures for such a specialised show were little short of fantastic.

This year we had a repeat performance and although the number of exhibitors was down the attendance seemed as good as ever. Laser Instrumentation Ltd wittily supplied a match with their hand-out literature with the invitation "Strike a match and read this!"—an allusion, of course, to the aftermath of the miners' strike which was still causing problems although Kiver had seen to it that plenty of emergency power was available to keep the large number of live demonstrations ticking over.

What makes Kiver's shows so popular is the quality of the technical sessions. This year, as last, he won the co-operation of the SIRA Institute who acted as a technical filter for the 50 or so technical papers presented.

At a time of general misery and rising prices it was good to see Integrated Photomatrix Ltd announcing big price reductions at the show. IPL had only just celebrated their third birthday and what a lusty infant the company is. Peter Noble, managing director, told me that greatly increased production had enabled him to cut prices of some IPL light activated switches by almost half in 100+

quantities. But the highlight of IPL exhibits was a line scan camera incorporating up to 256 optical devices.

Low light TV systems were abundantly on view with exhibitors keen to show that their own systems were most sensitive. The big rush to sell these systems commercially came only after declassification of some military equipment last year. Apart from obvious applications like prison security, low light TV could penetrate into completely new fields.

Sad note at the closing of Electro-Optics '72 was that there will be no exhibition next year. In future it will take place every two years, the reason given by the organisers being that the rate of development of new technology is no longer such that an annual event is justified.

NEW HOME FOR "PHYSOC"

So we have seen the last of the Physics Exhibitions at Alexandra Palace, N. London. Next year it will be teaming up with the Laboratory Equipment Exhibition (Labex) at Earls Court. I welcome the change to a more central location and it will now be possible to take in two exhibitions in a single day—at least for those who are content with a quick spin-round.

A big disappointment this year was the failure of the Scandinavian countries to mount their own display. An invitation was extended but was declined. I understand, at comparatively short notice.

UNHAPPY IRISH

Ireland's electronics industry has been expanding nicely. In the past five years some high technology companies, mainly US-based, have become established and started making an increasing contribution to the country's exports as well as providing the foundation for training the first generation of home-grown Irish electronics engineers.

The Irish Government has been offering good incentive schemes for investment of foreign capital and a ten-year tax-holiday for all profits from exports. Everything was going fine—until the troubles.

I recently visited nine electronics plants in Ireland ranging in size from tiny Gow-Mac employing only ten people up to the 1,000-strong Ecco Ltd which is a wholly owned subsidiary of US General Electric turning out 200 million diodes, transistors and rectifiers a year.

Irish industrialists are worried—and they have good reason. Wage-inflation has been high, eroding many of the advantages of operating in what used to be a comparatively low-cost labour area. Tourism, on which so much of the country's economic prosperity depends, will be very hard hit this year. And few industrialists are likely to be tempted to make any new investment until a greater level of stability has been achieved.

It is hard to see how any real growth in Irish electronics can be sustained this year although most manufacturers are putting a brave face on things and trying not to talk themselves into a depression. Most, too, would like to see an end to bitterness and a long period of tranquility in which Irish electronics can build its strength and play a leading role in bringing the country forward into our technological age.

BUILT-IN SERVICES

Two cheers for the Post Office for announcing that every house in the new town of Milton Keynes is to have piped-in services. We should have adopted such systems on the widest scale years ago. But better late than never.

Each house will have not only its own telephone pair but also a high-performance coaxial cable for piping in radio and TV services and, eventually, for piping out the data from your own computer terminal, your viewphone, even your North Sea gas meter readings.

Both v.h.f. and u.h.f. will be used on the system, the v.h.f. for trunk circuits and u.h.f. over local lines. Everything will be underground so there will be no need for forests of TV aerials and last-minute overhead telephone cables. The Post Office has already had some experience in other new towns but Milton Keynes is the biggest and the forecast is that over 2,000 houses will be wired in to the system in the next twelve months.

CHIPS HAVE EVERYTHING

Those single chip large scale integrated circuits (LSI) have certainly got going commercially in a big way. And they must be real cheap, too. Latest rock-bottom price I have heard of for an electronic desk calculator using a single Texas Instruments LSI and an eight digit readout is about £36 in the Japanese supermarkets.

The desk calculator market is one the Japanese have now sewn up so tightly that no-one else has a chance. Which product line is next on their list?

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

ELECTRONIC CALCULATOR

The time when housewives will soon be doing their shopping with the aid of an electronic pocket calculator is fast approaching; only price seems the deterrent.

The latest calculator to be marketed by **West Hyde Developments** under the trade name of **Tobicom**, measures only $7\text{in} \times 9\frac{1}{2}\text{in} \times 3\frac{1}{2}\text{in}$ and costs only £99.

Weighing only $3\frac{1}{2}\text{lb}$, the calculator adds, subtracts, multiplies and divides. Also, the arithmetic can be mixed, i.e. $2 + 6 - 3 \times 5 - 6 \div 2 + 4.5 = 14$. The decimal place can be set with 0 to 7 digits to the right and the machine automatically clears after the equals sign is pressed. Zero suppression is included to make easier reading.

Built around six MOS LSI (Large Scale integration) chips the calculator will give up to a 16-digit answer for up to an 8-digit entry. It will multiply a negative number by a positive number. As each entry is displayed it can be checked and cleared if incorrectly entered. Only the last entry is acted on.

The keys are in three colours and arranged in three groups for ease of operation. For repetitive multiplication or division a constant factor key is depressed.

GAS DETECTOR

For some unexplained reason the reported number of accidents that have been attributed to gas leaks has been increasing over the last nine months.

For companies who rely on gas for producing their respective products the **Gasmarker** from **Crowcon (Instruments) Ltd.** would seem a reasonable investment. Perhaps, even private individuals may consider the investment a worth while one, since the unit is portable.

The **Gasmarker** sells for approximately £25 and operates on the thermal conductivity principle and gas detection is through a sintered bronze diffusion head. It can be supplied calibrated for "town" or natural gas (methane). Operation is by a single pushbutton, percentage gas by volume being indicated on a large-scale moving-coil meter.

A particular feature is the special meter scale, the lower end of which has been expanded so that 0-25 per cent concentrations occupy approximately half the scale width and 25-100 per cent the remainder. This is of special significance in locating a leak, because it allows accurate comparative measurements of very low gas concentrations in the early stages of a search; the higher end of the scale then being used to trace the leak to its source.

Additional information on the **Gasmarker** is available from **Crowcon (Instruments) Ltd.**, The Common, Stokenchurch, Bucks.

AUDIO KITS

Just as someone had to be first to break the "sound barrier", it would seem that **Radio and TV Components (Acton) Ltd.** have broken the "price barrier" for home entertainment and the motorist. With the introduction of their **Unisound** system and the **Tourist PB** car radio they have certainly struck a blow for the reader.

At £25 the **Unisound 505** must surely be the best value for money in the audio field, especially as their kit comes complete with turntable, stereo ceramic cartridge and a pair of **EMI** dual-cone elliptical loudspeakers. Also included in the kit is a simulated teak plinth, with a tinted cover, to house the amplifier and changer, plus two matching loudspeaker enclosures.

Based on the well known **Mullard Unilux** modules, the output stages have been modified and improved by the addition of integrated circuits which provide an output power of 5 watts per channel, ample for living rooms.

The pre-amplifier module has separate bass, treble controls and two separate volume controls.

The complete kit can be easily assembled, with a screwdriver, in approximately 40 minutes and R &

TV claim that any novice or housewife who can wire up a three-pin plug can successfully assemble a **Unisound 505** kit.

Once again the joy of sitting and listening to reproduction of good music has been achieved without prohibitive cost.

The new **Tourist PB** car radio kit is claimed to be the first in the UK to feature an integrated circuit combined with push-button station selection.

The radio covers both the medium and long wavebands and the five push-buttons can be tuned in the conventional manner or set to pre-selected stations. Four of the push-buttons operate on the medium waveband and the fifth selects stations on the long waves.

Permeability tuning and the inclusion of longwave coils ensure excellent tracking, sensitivity and selectivity on both wavebands. R.F. sensitivity at 1MHz is claimed better than $15\mu\text{V}$.

The power output of the car radio is 2.5W into an 8 ohm loudspeaker.

Retailing at only £7 the kit contains full step-by-step instructions and the company claims that anyone who can solder should be able to complete the kit in an evening.

Both the **Unisound** system and the **Tourist PB** car radio are backed by an excellent after sales service. For approximately £2 R & TV will undertake to "trouble shoot" any returned unit provided that a genuine attempt has been made to construct a unit following their instructions.

HEATSINKS


A new range of heatsinks which, it is claimed, will improve the performance and life of transistors is announced by **J. W. Sales**.

Further details and information can be obtained from **J. W. Sales**, 6 Russet Road, Cox Green, Maidenhead.



Tobicom calculator marketed by West Hyde Developments

Gasmarker detector from Crowcon Ltd.

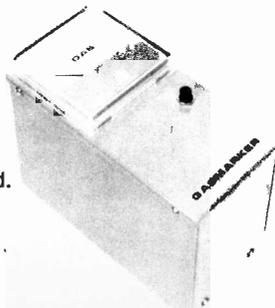

Completed car radio and Unisound 505 kit from Radio & TV Components Ltd.



Great new OFFER from DIOTRAN

TRANSISTORS

BRAND NEW FULLY GUARANTEED DEVICES

AC107	15p	AF115	17p	BC140	35p	BCY31	22p	BF272	80p	EC403	15p	ORP60	40p	2N918	30p	2N2714	25p	2N3704	15p
AC113	20p	AF116	17p	BC141	35p	BCY32	22p	BF273	30p	GET880	27p	ORP61	40p	2N929	22p	2N2904	25p	2N3705	12p
AC115	23p	AF117	17p	BC142	45p	BCY33	17p	BF274	30p	MAT100	15p	ST140	12p	2N1131	25p	2N2905	20p	2N3706	12p
AC125	17p	AF118	30p	BC143	40p	BCY34	20p	BF308	35p	MAT101	17p	ST141	17p	2N1132	22p	2N2906	25p	2N3707	13p
AC126	17p	AF124	21p	BC145	45p	BCY70	17p	BF309	37p	MAT120	15p	TIS43	40p	2N1302	17p	2N2906A	25p	2N3708	8p
AC127	17p	AF125	20p	BC147	17p	BCY71	30p	BF316	75p	MAT121	17p	UT46	27p	2N1303	17p	2N2907	27p	2N3709	8p
AC128	17p	AF126	20p	BC148	12p	BCY72	15p	BFW10	55p	MPF102	43p	V405A	25p	2N1304	20p	2N2907A	27p	2N3710	10p
AC141K	17p	AF127	20p	BC149	17p	BCZ11	20p	BFX29	27p	MPF105	43p	V410A	45p	2N1305	22p	2N2907A	30p	2N3711	10p
AC142K	17p	AF139	33p	BC150	17p	BD121	85p	BFX84	20p	OC15	30p	2G301	19p	2N1306	22p	2N2923	20p	2N3819	40p
AC151	15p	AF178	50p	BC151	20p	BD133	85p	BFX85	27p	OC20	50p	2G302	19p	2N1307	22p	2N2924	3p	2N3903	25p
AC154	15p	AF179	50p	BC152	17p	BD124	75p	BFX86	22p	OC22	30p	2G303	19p	2N1308	27p	2N2925	13p	2N3904	27p
AC155	17p	AF180	50p	BC153	27p	BD131	80p	BFX87	25p	OC23	33p	2G304	20p	2N1309	27p	2N2926	12p	2N3905	25p
AC156	17p	AF191	50p	BC154	30p	BD132	80p	BFX88	22p	OC24	45p	2G306	35p	2N1613	17p	(G)	12p	2N3906	27p
AC157	17p	AF186	45p	BC157	20p	BDY20	£1	BFY50	20p	OC25	25p	2G308	35p	2N1711	20p	2N2926(Y)	11p	2N4058	15p
AC165	17p	AF239	37p	BC158	17p	BF115	22p	BFY51	20p	OC26	25p	2G309	35p	2N1889	35p	2N2926	(O)	2N4059	10p
AC166	17p	AF211	37p	BC159	20p	BF117	45p	BFY52	20p	OC28	40p	2G339	35p	2N1890	45p	2N3010	80p	2N4060	12p
AC167	20p	AF212	45p	BC167	13p	BF118	60p	BFY53	17p	OC29	40p	2G339A	15p	2N1893	37p	2N3011	80p	2N4061	12p
AC168	20p	AL102	85p	BC168	13p	BF119	70p	BSX19	15p	OC35	33p	2G344	15p	2N1897	75p	2N3053	20p	2N4062	12p
AC169	14p	AL103	85p	BC169	13p	BF152	35p	BSX20	15p	OC36	40p	2G345	15p	2N2147	75p	2N3054	50p	2N5172	12p
AC176	23p	AS22	25p	BC170	12p	BF153	35p	BSY25	15p	OC41	20p	2G371	13p	2N2148	60p	2N3054	50p	2N5459	43p
AC177	20p	AS27	30p	BC171	13p	BF154	35p	BSY26	15p	OC42	22p	2G371B	10p	2N2192	30p	2N3055	63p	25034	75p
AC187	30p	AS28	25p	BC172	13p	BF157	45p	BSY27	15p	OC44	15p	2G374	17p	2N2193	30p	2N3391	17p	25035	50p
AC188	30p	AS29	25p	BC173	13p	BF158	25p	BSY28	15p	OC45	12p	2G377	17p	2N2194	27p	2N3391A	20p	25036	45p
AC197	25p	AS50	25p	BC174	13p	BF159	30p	BSY29	15p	OC70	15p	2G378	15p	2N2217	20p	2N3392	17p	25037	45p
AC198	20p	AS51	25p	BC175	22p	BF160	30p	BSY38	15p	OC71	9p	2G382	15p	2N2218	25p	2N3393	15p	25038	60p
AC199	22p	AS52	25p	BC177	17p	BF162	30p	BSY39	15p	OC72	12p	2G401	30p	2N2219	27p	2N3394	15p	25039	£1-10
AC200	20p	AS54	25p	BC178	17p	BF163	35p	BSY40	30p	OC74	12p	2G414	30p	2N2220	22p	2N3395	20p	25040	£1
AC211	20p	AS55	25p	BC179	17p	BF164	35p	BSY41	35p	OC75	15p	2G417	25p	2N2221	22p	2N3402	22p	25041	£1-10
AC222	19p	AS56	25p	BC180	20p	BF165	35p	BSY45	13p	OC76	15p	2N388	30p	2N2222	27p	2N3403	22p	25042	£1-10
AC227	18p	AS57	25p	BC181	22p	BF167	23p	BSY45A	13p	OC77	25p	2N388A	30p	2N2223	17p	2N3404	32p	25043	60p
AC228	19p	AS58	25p	BC182	10p	BF173	22p	BU105	£3-90	OC81	15p	2N404	22p	2N2224	15p	2N3405	45p	25044	50p
AC229	30p	AS58	25p	BC182L	10p	BF176	35p	CI11E	60p	OC82D	15p	2N404A	30p	2N2225	15p	2N3414	20p	25045	£1-20
AC230	25p	AS21	40p	BC183	10p	BF177	35p	C400	30p	OC82	15p	2N524	55p	2N2226	60p	2N3415	20p	25046	£1-20
AC231	25p	BC107	10p	BC183L	10p	BF178	45p	C407	25p	OC82D	15p	2N527	60p	2N2227	12p	2N3416	37p	25047	£1-20
AC234	18p	BC108	10p	BC184	13p	BF179	50p	C424	17p	OC83	20p	2N696	12p	2N2228	12p	2N3417	37p	25048	£1-20
AC235	18p	BC109	11p	BC184L	13p	BF180	30p	C425	40p	OC84	20p	2N697	15p	2N2229	12p	2N3418	37p	25049	£1-20
AC236	30p	BC113	25p	BC186	27p	BF181	30p	C426	30p	OC89	15p	2N698	24p	2N2230	15p	2N3419	37p	25050	£1-20
AC240	15p	BC114	30p	BC187	27p	BF182	30p	C428	20p	OC140	17p	2N699	55p	2N2231	15p	2N3420	37p	25051	£1-20
AC241	18p	BC115	30p	BC207	11p	BF183	30p	C441	27p	OC170	15p	2N706	7p	2N2232	15p	2N3421	37p	25052	£1-20
AC244	35p	BC116	35p	BC209	11p	BF184	25p	C442	35p	OC171	15p	2N706A	7p	2N2233	15p	2N3422	37p	25053	£1-20
AD140	40p	BC117	35p	BC209	11p	BF185	30p	C444	37p	OC200	25p	2N708	12p	2N2234	15p	2N3423	37p	25054	£1-20
AD142	40p	BC118	25p	BC212L	11p	BF188	30p	C450	17p	OC201	27p	IN709	45p	2N2235	15p	2N3424	37p	25055	£1-20
AD149	45p	BC119	45p	BC213L	11p	BF194	23p	C720	12p	OC202	27p	2N711	40p	2N2236	15p	2N3425	37p	25056	£1-20
AD161	35p	BC125	35p	BC213L	11p	BF195	24p	C722	25p	OC203	25p	2N717	42p	2N2237	15p	2N3426	37p	25057	£1-20
AD162	35p	BC126	35p	BC214L	12p	BF196	30p	C740	25p	OC204	25p	2N718	24p	2N2238	15p	2N3427	37p	25058	£1-20
AD161/162(MP)	63p	BC134	30p	BC225	25p	BF197	35p	C742	17p	OC205	35p	2N718A	50p	2N2239	15p	2N3428	37p	25059	£1-20
AD140	50p	BC135	30p	BC317	12p	BF222	80p	C760	17p	OC309	35p	2N726	27p	2N2240	15p	2N3429	37p	25060	£1-20
ADZ11	£2	BC136	30p	BC318	12p	BF257	35p	C762	17p	P346A	27p	2N727	27p	2N2241	15p	2N3430	37p	25061	£1-20
ADZ12	£2	BC137	30p	BC319	12p	BF270	25p	C764	60p	OCPT1	45p	2N743	17p	2N2242	15p	2N3431	37p	25062	£1-20
AF114	17p	BC139	45p	BCY30	20p	BF271	17p	EC401	15p	ORP12	43p	2N914	17p	2N2243	15p	2N3432	37p	25063	£1-20

DIODES & RECTIFIERS

8p	AA119	8p	BYZ11	32p	OA81	7p
12p	AA120	8p	BYZ12	30p	OA85	7p
45p	BA116	22p	BYZ13	25p	OA90	6p
40p	BA126	22p	BYZ16	35p	OA91	7p
42p	BY100	15p	BYZ17	35p	OA92	7p
24p	BY101	12p	BYZ18	30p	OA200	6p
50p	BY105	15p	BYZ19	25p	OA202	7p
17p	BY114	12p	OA5	17p	SO10	4p
15p	BY126	15p	OA10	22p	SO19	4p
17p	BY127	17p	OA47	7p	IN914	6p
17p	BY130	15p	OA70	7p	IN916	6p
17p	BYZ10	35p	OA79	8p	IN4148	6p

500,000

SILICON PLANAR NPN-PNP PLASTIC AND METAL CAN TYPES TRANSISTORS

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

TYPE STN18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77.
Price: 500 £9; 1,000 £15

TYPE STP18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18.
Price: 500 £9; 1,000 £15

TYPE STN5. Silicon Planar Transistors npn TO-5 Metal Can. Types similar to: BFY50-51-52 and 2N2192-92.
Price: 500 £9-50; 1,000 £16

TYPE STPL. As above but in npn and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL.
Price: 500 £7-50; 1,000 £13

TYPE STNK. Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, i.c. 200mA, 300mW and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8.
Price: 500 £9-50; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

200,000

SILICON ALLOY TRANSISTORS

Clearance of npn Silicon Transistors from the 2S300 (TO-5) and 2S320 (SO-2) range and similar to the GC200-205 and BCY30-34 series. Ideal for Amateur Electronics, Radio Hams and for experimental use in Schools, Colleges and Industry.

Approximate count by weight:
100 off—75p (plus p. & p. 10p)
300 off—£1.75 (plus p. & p. 15p)
500 off—£2.50 (plus p. & p. 17p)
1,000 off—£4 (plus p. & p. 25p)
10,000 off—£35 (plus p. & p. 55p)

Large quantities quoted for on request. EXPORT INQUIRIES WELCOME

DIOTRAN

SALES

PO BOX 5, WARE, HERTS

Full Money-Back Guarantee

POSTAGE & PACKING 7p

10 MILLION DIODES

Silicon or Germanium			
State which when ordering			
200	50p	10,000	£10-00
1,000	£2-00	50,000	£30-00
5,000	£7-00	100,000	£50-00

2,000,000 SILICON PLANAR TRANSISTORS

TO18 P.N.P. & N.P.N. TYPES			
State which when ordering			
100	£1-50	10,000	£90-00
500	£6-00	50,000	£400-00
1,000	£10-00	100,000	£625-00

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

**COMPONENTS AND HI FI
FOR THE HOME CONSTRUCTOR**
OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

EA1000 3 WATT AUDIO AMPLIFIER

An Audio Amplifier designed around the TAA621 Linear I.C. —
Supply Voltage 9-24V
Speaker Imp. 8-16 ohm
Frequency 50Hz-25kHz
Overall Size 2in x 3in x 2in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at



£2-63
+ 5p P. & P.

MINI STROBE

Another Bargain from Crescent. 1 joule output, speed variable from 2-10 flashes per sec. and powered from a.c. mains 220V-250V. Housed in its small attractive fibreglass case (size approx 6in x 4in x 4in high). Makes an ideal Strobe Unit for Discos, Experimental Work, Photography and many other uses.



£16-50 plus 38p P. & P.

74 Series I.C.s.

7400	15p
7401	15p
7402	15p
7410	15p
7430	15p
7441	67p
7473	37p
7474	37p
7490	67p

Please include 5p P. & P. per 3 I.C.s.



7"x4" LOUDSPEAKER
A top quality speaker ideal where small size is important. Manufactured by F.M.I. for a well known hi-fi set maker. Size: 7in x 4in. Impedance: 15 ohm. Flux: 38,000 Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable Price: **£1-60**. Free postage on this item.



CRESCENT CASSETTES

Best quality LOW NOISE Cassettes, complete in standard storage case. Please note our new low price.

C60	28p
C90	38p
C120	48p

Please include 5p P. & P.



EMI LOUDSPEAKER 450

10W 13in 8in & two 2 1/2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp.

£3-25 plus 38p P. & P. each.

PRINTED CIRCUIT KIT

Everything for producing your own Printed Circuits. **£1-40**, plus 10p P. & P.

NKE CALIBRATED KNOB

0-10 calibrated plastic knob with metal insert and skirt. Fixing size 6.35mm. Skirt dia. 36mm. Our price **20p** each plus 2p P. & P.

HIGH QUALITY IMPORTED HEADPHONES

1,000 Ω per phone **80p**
2,000 Ω per phone **88p**
Plus 10p P. & P. per pair.



TTC
G1105

BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price **£2-75** plus 8p P. & P. each.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7.5 or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Our Price **£2-75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.

INTEGRATED CIRCUIT SOCKETS

A must for the experimenter interested in I.C.S. 14 pin, **20p** each, 16 pin, **20p** each. Please include 5p P. & P. per 3 sockets.



MINI LOUDSPEAKERS

2in 8 ohm	38p
2in 25 ohm	38p
2in 40 ohm	38p
3in 8 ohm	48p

Please include 5p P. & P. on each L.S.

2N3055

Popular power transistor now at our low price — **50p** each. Please include 5p P. & P.

IB40K05

Bridge Rectifier (Texas). Plastic encapsulated 50V at 4A. Approx. size 1 1/2in x 1 1/2in. Our Price **60p** each.

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and plus 25p Control Switch. **£5.50** P. & P.



BARGAIN S.C.R.

Tested Thyristor. 400V, 8amp. **45p** each. 5 for **£2**. 5p P. & P.

"CRESCENT" D.J. PARTY AMPLIFIER "P100"

A completely new style 100W Amplifier especially designed for the D.J. who expects his equipment to look and sound really good, and still keep a moderate price. 10-30,000Hz response. All loudspeaker systems suitable. Pull out front to 4 ohm. All silicon transistors. F.E.T. at front end. Real value at **£42** plus **£1 P. & P.** and insurance.

PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18-50** plus 38p P. & P. If you require more information please send S.A.E.


TV'S 19" NOW £11.95

TWO YEARS' GUARANTEE ALL MODELS

405/625: 19" £25.95; 23" £35.95

FREE CATALOGUE

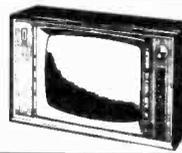DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS



COLOUR TV 19" £145 OR 25" £185
LIMITED SUPPLY. REGRET PERSONAL CALLERS ONLY

TV TUBES REBUILT GUARANTEED 2 YEARS



14" £3.95; 17" & 19" £5.95; 21" & 23" £6.45.
Exchange Bowls carr. 55p.

RECORD PLAYER CABINETS **£3.75**. Designed for the modern autochanger. Size 17" x 15" x 7 1/2". p.p. 55p.

PRESS BUTTON SWITCHING UNITS
4 Banks 25p, 6 Banks 35p. p.p. 5p.

COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 15p.

Speakers: 35p. 2 1/2" 8 Ω . Brand new. Post 15p.

Precision Tape Motors: £1.95 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.

Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.

Transistors 15p. each. Post free. AC126, AC128, AF114, AF117, OC45, OC71, OC81, OC81D.

Valve EL80 50p. Only stock in the country.
Pots: 25p each. Post 5p. D.S.W 500/500 K Ω . D.S.W 500/100 K Ω . D.S.W 1 meg./100 K Ω . S.S.W 500/500 K Ω . S.S.W 500/1 meg.

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS		1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DL92, DL94, Set of 4 for £1-02. DAF96, DF96, DK96, DL96. 4 for £1-48.	
1R5	28	30C15	58
185	22	30C17	78
1T4	16	30C18	61
384	26	30E5	64
3V4	37	30E11	61
DAF91	29	30FL12	69
5V4G	35	30FL14	68
5Y3GT	26	30L1	29
5Z4G	35	30L15	57
6X02L	54	30L17	67
6AL5	11	30P4	57
6AM6	35	30P12	72
6AQ5	22	30P19	57
6AT6	20	30PL1	60
6BA6	20	30PL13	89
6BA8	20	30PL14	85
6BE6	21	35L6GT	45
6BJ6	41	35W4	25
6BW7	52	35Z4GT	25
6P14	40	807	45
6P23	88	6063	62
6P25	53	ACV12	77
6P7G	24	B349	65
6K7G	12	B729	62
6X8G	17	OC135	67
6X4T	35	CY31	30
6887GT	30	DAF91	28
6V6G	28	DAF96	36
6V6GT	28	DF96	36
6X4	23	DF91	18
6X5GT	28	DF96	36
10P13	58	D177	20
20P4	92	DL92	17
12A6	20	DK91	28
12A7	20	DK92	38
12A7X	22	DK96	38
10B6GG	80	DL35	40
20E2	87	DL92	26
30P3	77	DL94	37
20P4	92	DL96	38
25L6GT	19	DY86	24
50Y4GT	57	DY87	24
30C1	28	DY802	33
EM80	38	PCL83	57
EM81	38	PCL84	34
EM84	32	PCL86	38
EM87	34	PCL88	65
EY51	33	PCL88	65
EV96	34	PC800	75
EZ40	43	PEN44	77
EZ41	43	PEN36G	70
EZ80	22	PFL200	52
EZ81	22	PL36	49
EZ82	22	PL81	44
EZ83	24	PL82	31
EZ84	22	PL83	33
EZ85	22	PL84	30
EZ86	22	PL85	47
EZ87	22	PL86	33
EZ88	22	PL87	33
EZ89	22	PL88	33
EZ90	22	PL89	33
EZ91	22	PL90	33
EZ92	22	PL91	33
EZ93	22	PL92	33
EZ94	22	PL93	33
EZ95	22	PL94	33
EZ96	22	PL95	33
EZ97	22	PL96	33
EZ98	22	PL97	33
EZ99	22	PL98	33
EZ00	22	PL99	33

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12 Phone 01-478 6001-2-3

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Post/Packing on 1 valve 6p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

IC DICE

READERS may be interested in a modification I have made to J. D. Croft's, "IC Digital Dice" published in the December 1971 edition of P.E.

I had also been thinking along the same lines but decided against using an SN7492 ÷ 12 counter. The output "000" of the counter greatly increases the amount of decoding circuitry required.

The circuit design shown in Fig. 1 uses only four packages and requires no decoder. The counter was built from two dual JK flip-flops (SN7473). The gate G1 is used to set the counter back to the "001" state after a final count of "110".

It can be seen from the truth table that if the lamps are connected directly to the counter outputs A, B, C and if the lamps are arranged as in Fig. 2, a suitable display will result. If the lamp drivers shown in the December article are used it may be necessary to use two to drive the four lamps LP4-LP7. Alternatively, a higher power transistor could be used.

The major disadvantage of the circuit is the failure to use all packages completely: there remains a flip-flop and a 3-input NAND gate unused. The flip-flop might be incorporated as a "Head or Tails" device, or could be used to indicate a "+" or "-" sign on the display to give a forwards or backwards move. It could also be used to control a bulb lighting the legend "Add Six" thus extending the dice throw to twelve. The latter will not, however, indicate doubles, for which purpose the unit must be duplicated.

No doubt readers will be able to think of other ingenious uses for the "left-overs".

A. J. Jacobs,
Beaconsfield,
Bucks.

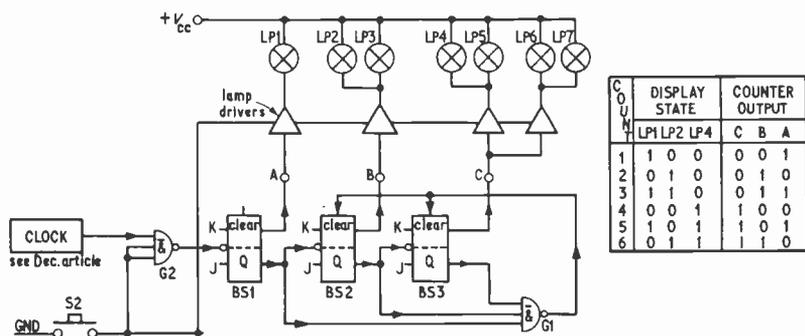


Fig. 1. Circuit diagram for the modified i.c. digital dice. The truth table is shown on the right

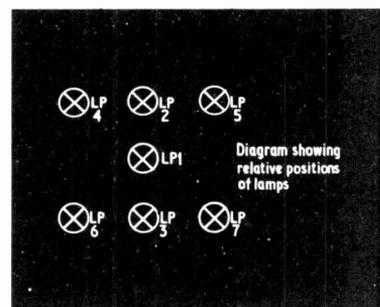


Fig. 2. Suggested layout for the indicator lamps

BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

June to August 1968

Mr. R. Henderson, 79, Glencroft Road, Croftfoot, Glasgow, S.4.

December 1970

Mr. J. F. Glavin, North Lodge, Northlands, Salthill, Chichester, Sussex.

April, May 1968

Mr. M. Martin, 29, Hillingdon Road, Stretford, Manchester.

August 1968

Mr. L. H. Maul, 11, Shrublands Avenue, Croydon, CRO 8JD.

January 1965

Mr. T. Webster, 41, George Street, Great Yarmouth, Norfolk.

June 1971

Mr. T. F. Gillies, 247, Brownlow Drive, Rise Park, Bestwood, Nottingham.

April, May 1971

Mr. R. Barrett, The Midland Bank, Nailsworth, Stroud, Glos.

November, December 1967

Mr. C. J. Gummer, 31 Palace Road, Tulse Hill, London, SW2 3EA.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

December 1971

Mr. C. E. H. Morgan, 53, Midland Road, Bramhall, Cheshire.

January to April 1970 and January 1971

Mr. M. Palmer, 9, Trenance Gardens, Greetland, Halifax, Yorks.

November 1964, July 1965, October 1968, August 1970

Mr. D. Carter, 12, Martins Lane, Bracknell, Berks.

PATENTS REVIEW...

ELECTRICAL DAMP COURSE

A CERTAIN degree of mystery surrounds the electrode methods for providing a damp-proof course in buildings prone to rising damp. A new British patent originating from Rumania (BP 1 248 441) clears up some of this mystery.

In this field there are so-called "active" methods and "passive" methods.

In the passive methods, electrodes are fixed in the damp zone of the wall and then connected in groups to grounding electrodes. Usually, pairs of electrodes made of different metals are coupled together and then connected in groups to the grounding electrodes, the more electro-negative metal being in the lowest row. No external source of current is provided.

In a known active method a continuous current is provided in the circuit, the wall electrodes being connected to the positive pole and the grounding electrodes to the negative pole.

Humidity is removed through the electro-osmotic migration from the capillaries of the building into the soil where the grounding electrodes are placed. The disadvantages are that corrosion of the electrodes will take place over the years and that little moisture is removed directly by the air.

The Rumanian proposal is that in the active method the positive, as well as the negative, electrodes should be fixed in a horizontal row in the wall without any grounding electrodes. The positive electrodes are made of solid metallic bars and the negative electrodes are perforated metallic tubes. The interior of each tubular electrode is hollow and open to the air. The positive and negative electrodes are connected alternately as two separate circuits at a distance from the ground level equal to 0.86 of the distance between the electrodes.

By the use of tubular negative electrodes, humidity from the walls can escape direct into the air. To avoid corrosion the electrodes are formed of depolarising compositions appropriate to the nature of the wires associated with them.

The theory becomes a little clearer by reference to Fig. 1. Solid metallic positive electrodes and perforated metallic tube negative electrodes are fixed alternately in the building wall. No

BP 1 248 441



Fig. 1

grounding electrodes are provided and the water migrates directly into the air with the assistance of the electro-osmotic current which drains it to the negative tubular electrodes. Experiments have shown that optimum drying is obtained when the quoted circumstance is met; namely when the height of the electrodes above ground level is equal to 0.86 of the distance between the electrodes.

The patent gives calculations to substantiate this and suggests suitable depolarising compositions for the electrodes. For instance for copper electrodes the depolarising mixture is 50 per cent clay powder, 20 per cent copper sulphate powder and 30 per cent Portland cement.

Readers interested in more of these and other details should refer to the patent specification.

LOUDSPEAKER DESIGN

THE diaphragm of a loudspeaker, outlined in a new patent (BP 1 250 640) by the Japanese firm of Nippon Gakki Seizo Kabushiki Kaisha, resembles a cross between an ordinance survey map and a ceiling tile.

It is known to use foamed plastics, such as polystyrene, as a loudspeaker diaphragm, but the usual principle of suspending a symmetrical cone or circular sheet of the polystyrene at its periphery has been shown to produce a non-linear frequency response and attempts have been made to improve on it by using an asymmetrical diaphragm. One shape tried, for example, is similar to a grand piano, with a near conical area in the central region.

Kaisha now suggest that problems arise with asymmetrical diaphragms because strong resonances may be produced due to the relatively large flat portion which is formed between the asymmetric periphery and the outer lines of the conical portion.

The flat portion gives reduced flexural rigidity and this in turn gives rise to excessive peaks and dips in the frequency response curve, especially in the middle and low frequency ranges.

The suggested answer is an asymmetrical diaphragm with an initially truly conical trumpet shaped central driven portion smoothly merging into an outer asymmetrical flat portion of uniform width all around the periphery of the diaphragm. The resultant diaphragm thus looks rather like a contour model of an asymmetric hill with a circular peak and a flat base surround region of uniform width. See Fig. 2. This uniform surround and absence of large flat lands apparently improves linearity quite dramatically.

TIMELY REMINDER

Now seems a timely point to remind readers of the points made in the introductory *Patents Review* published in the November 1971 issue—e.g. copies of all specifications are available at 25p each from the British Patent Office in Southampton Buildings, Chancery Lane, London, E.C.4. (Back numbers of Practical Electronics are also available there for reference.)

Readers should always, of course, bear in mind the points made in the November issue on the legal aspect of the protection which a granted patent offers its owner against infringers.

BP 1 250 640

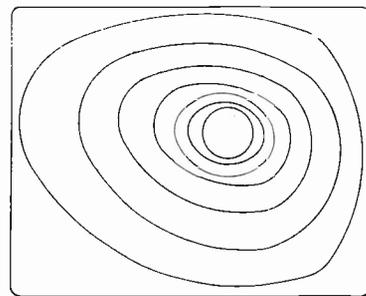


Fig. 2

Would YOU pay 50 pence for a components catalogue?



You'll be glad you did when you get THIS one!

A components catalogue is so vital to any keen constructor that it simply does not pay to make do with less than the best. True, the best may cost a little more... but it's the cheapest in the end. So invest in a Home Radio Components Catalogue, listing over 8,000 items, more than 1,500 of them illustrated. If you call at our shop the catalogue is yours for just 50 pence. If you order by post—70 pence, including postage and packing. You also get 10 Vouchers, each worth 5 pence when used as instructed—so you can get the cost of the catalogue back in any case!

Send the coupon today with your cheque or P.O. for 70p.

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. PE.
234-240 London Road, Mitcham, Surrey CR4 3HD 01-648 8422

PRACTICAL ELECTRONICS

Specify

CONTIL MOD-2 CASES



PRACTICAL ELECTRONICS specify CONTIL MOD-2 CASES for housing the P.E. GEMINI STEREO TUNER, P.E. GEMINI AMPLIFIER, P.E. AURORA LIGHT DISPLAY SYSTEM, P.E. DIGITAL CLOCK. Also available ready punched for Sinclair Project 60, with or without active filter unit. Full kit of hardware is also available, including capacitors, for use with Z30 or Z50 at £3.68.

PVC COATED

MATERIALS. PVC's
easy to clean surface is scuff resistant.

PVC/ALUMINIUM FOR FRONT AND BACK PANELS. PVC/STEEL FOR SIDES, TOP AND BOTTOM. LOW COST.

	X	Y	Z	I	off p	& p		X	Y	Z	I	off p	& p
A	4.5	3.6	5.2	2.0	18p		N	4.5	7.1	3.4	2.0	28p	
B	4.5	7.6	5.2	5.0	28p		O	4.5	10.1	3.4	4.0	35p	
C	4.5	10.6	5.3	0.5	28p		P	9	3.1	3.4	4.0	28p	
D	9	3.6	5.3	0.5	28p		Q	9	7.1	3.4	4.0	35p	
E	9	7.6	5.3	4.0	28p		R	9	10.1	3.5	4.0	35p	
F	9	10.6	5.4	0.0	28p		S	13	3.1	3.4	4.0	35p	
G	13	3.6	5.3	4.0	28p		T	13	7.1	3.5	4.0	35p	
H	13	7.6	5.4	0.0	28p		U	13	10.1	3.6	6.0	45p	
I	13	10.6	5.4	4.0	35p		V	18	3.1	3.5	4.0	35p	
J	18	3.6	5.4	0.0	28p		W	18	7.1	3.6	6.0	45p	
K	18	7.6	5.4	0.0	35p		X	18	10.1	3.8	6.0	45p	
L	18	10.6	5.6	6.0	45p		G	Woodgrain	4.0	4.0	28p		
M	4.5	3.1	3.2	5.0	28p							Sizes in inches	

ATRON READOUT TUBES

As mentioned in the PRACTICAL ELECTRONICS article entitled ALPHA NUMERIC DISPLAYS

1. 5V 23mA per segment AC or DC
2. Large, bright 12mm high display
3. Compatible with I.C. decoder driver 7447
4. Rugged construction, sub-miniature size, compact design
5. Long life expectancy (100,000 hour accelerated life test)
6. Any desired colour with filters red, green, blue, daylight, neutral
7. Visibility curve ideally suited to the human eye
8. Bright daylight viewing from any angle up to 140°
9. Atron P.C. boards including I.C.'s available



ATRON READOUT TUBES

DA-133	1 off	10 off	100 off	1000 off
DA-133D Decimal	1.75	1.65	1.55	1.40
DA-133S +, -, I.	1.80	1.70	1.60	1.45
	1.65	1.55	1.45	1.30

4 for £6.00 CWO including Filter Samples 4 DA-133 or 2 DA-133, 1 DA-133D 1 DA-133S. Filter Sections 5in x 2in—5p each

Postage and Packing any quantity 5p

WH WEST HYDE

Minimum order £1

WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRESCENT
NORTHWOOD, MIDDX. HA6 1NN
Telephone: Northwood 24941/26732 Telex 923231 WEST HYDE NTHWD

HENRY'S FOR **LOW COST** **FIRST GRADE** **BRAND NEW** **GERMANIUM** and **SILICON TRANSISTORS, DIODES, RECTIFIERS, TRIACS, FETS, ZENERS, BRIDGES and INTEGRATED CIRCUITS**
 BY **ATES** · **EMIHUS** · **FAIRCHILD** · **FERRANTI** · **I.T.T.** · **MULLARD** · **NEWMARKET** · **PHILIPS** · **R.C.A.** · **TEXAS**

TRANSISTORS

A SELECTION FROM OUR LIST

AAV30 10p	BD115 75p	OC16 50p	2N1303 18p
AAV42 15p	BD123 85p	OC20 50p	2N1304 22p
AAZ13 10p	BD124 80p	OC22 50p	2N1305 22p
AAZ15 10p	BD131 75p	OC23 50p	2N1306 25p
AAZ17 10p	BD132 80p	OC24 60p	2N1307 25p
AC107 35p	BDY11 1.00	OC25 40p	2N1307 25p
AC126 30p		OC26 25p	2N1308 25p
AC127 25p	BDY17 1.00	OC28 80p	2N1309 25p
AC127Z 50p		OC29 60p	2N1613 20p
AC128 20p	BDY29 1.50	OC35 50p	2N2147 75p
AC176 20p	BDY80 1.00	OC36 50p	2N2140 60p
AC187 25p		OC42 40p	2N2217 20p
AC188 25p		OC43 50p	2N2218 20p
AC197 20p	BF116 25p	OC44 18p	2N2219A 1.00
ACY18 25p	BF154 20p	OC45 18p	
ACY19 25p	BF156 18p	OC70 18p	2N2219 1.00
ACY20 20p	BF159 65p	OC71 18p	2N2220 20p
ACY21 20p	BF180 25p	OC72 90p	2N2221 20p
ACY22 10p	BF194 18p	OC75 25p	2N2220 20p
ACY29 55p	BF195 18p	OC76 25p	2N2221 20p
ACY40 20p	BF196 18p	OC77 40p	2N2221A 1.00
ACY41 15p	BF197 18p	OC79 20p	
AD44 25p	BFX13 25p	OC81D 20p	2N2222 20p
AD140 40p	BFX29 25p	OC82 25p	2N2222A 1.00
AD149 50p	BFX30 25p	OC83 25p	
AD161 30p	BFX84 25p	OC84 25p	2N2369 15p
AD162 35p	BFX85 20p	OC139 25p	2N2369A 1.00
AF114 25p	BFX88 25p	OC140 40p	
AF115 25p	BFX87 25p	OC141 40p	2N2646 40p
AF118 25p	BFY90 65p	OC170 20p	2N2647 20p
AF117 20p	BFY18 25p	OC171 80p	2N2904A 1.00
AF118 60p	BFY30 20p	OC200 40p	
AF124 25p	BFY51 20p	OC201 75p	2N2905 25p
AF125 20p	BFY52 20p	OC202 80p	2N2905A 1.00
AF126 20p	BFY63 15p	OC206 80p	
AF127 20p	BFY100 15p	OC211 75p	2N2906 25p
AF139 30p	BRX20 18p	ORP12 50p	2N2906A 1.00
AF180 50p	BRX21 20p	ORP60 40p	
AF181 45p	BRX27 18p	RT140 15p	2N2907 25p
AF185 50p	BRX28A 12p	RT141 20p	2N2907A 1.00
AF186 40p	BRX95 12p	TIP29A 50p	
AF259 40p	BU105 42.25	TIP30A 60p	2N2995 15p
ARV24 20p	BY100 15p	TIP31A 75p	2N2926 10p
ARV27 30p	BY124 12p	TIP32A 70p	2N3011 20p
ARV28 25p	BY124 15p	TIP33A 70p	2N3053 20p
ARV29 30p	BY182 90p		2N3054 50p
ARZ21 55p	BYZ10 85p	TIP34A 1.00	2N3055 20p
BA100 15p	BYZ11 80p		2N3055A 1.00
BA102 30p	BYZ12 85p	TIB43 1.00	
BA110 25p	BYZ13 85p	TIB50 12p	2N3614 55p
BA115 7p	BZY78A1.00	TIB51 10p	2N3702 10p
BAX13 5p	GET102 35p	TIB52 10p	2N3703 10p
BAX16 7p	GET103 25p	TIB60 18p	2N3704 12p
BAY31 7p	GET111 45p	TIB61 18p	2N3705 10p
BAY58 12p	GET112 25p	TIB62 25p	2N3707 12p
BC107 10p	GET114 20p	V405A 25p	2N3708 10p
BC108 10p	GET115 50p	VR525 35p	2N3714 1.00
BC109 10p	GET116 55p	W01 80p	
BC109C 12p	GET116 55p	W06 45p	2N3715 1.00
BC109C 12p	GET116 55p	ZTX107 15p	
BC114 10p	GET117 20p	ZTX108 12p	2N3716 1.00
BC115 20p	GET118 20p	ZTX109 15p	2N3717 1.00
BC116 20p	GM378A 50p	ZTX300 12p	2N3771 1.00
BC116A 20p	MAT101 25p	ZTX301 15p	
BC117 20p	MAT121 25p	ZTX302 20p	2N3772 1.00
BC118 20p	MC724P 60p	ZTX303 20p	
BC119 30p	MJ420 80p	ZTX304 25p	2N3773 1.00
BC120 20p	MJ430 80p	ZTX305 15p	
BC135 15p	MJ2801 1.00	ZTX501 15p	2N3791 1.00
BC136 20p		ZTX502 20p	2N3792 1.00
BC137 20p	MJ2901 1.00	ZTX503 17p	2N3819 35p
BC138 20p		ZTX504 40p	2N3820 55p
BC147 12p	MJE340 50p	ZTX531 26p	2N3823 50p
BC148 10p	MJE370 20p	1N814 7p	2N3924 50p
BC149 12p	MJE371 80p	1N816 10p	2N3903 20p
BC154 20p	MJE520 70p	1N4148 7p	2N3906 25p
BC155 20p	MJE521 70p	1N44 7p	2N4058 12p
BC167 15p	MJE2955 1.00	1N821 7p	2N4061 12p
BC169 12p		1N822 8p	2N4062 12p
BC169C 15p	MJE3055 1.00	2G301 25p	2N4280 12p
BC177 20p		2G302 30p	2N4290 12p
BC178 20p	MPSA06 25p	2G303 35p	2N4871 35p
BC179 20p	MPSA56 20p	2N404 20p	2N5457 30p
BC182L 10p	MPSA70 18p	2N696 15p	2N5458 35p
BC183L 10p	MPSB106 50p	2N897 18p	2N5459 50p
BC184L 12p	MPSB136 55p	2N898 30p	40250 40p
BC192L 12p	NKT214 20p	2N706 10p	40360 40p
BC193L 12p	NKT216 85p	2N708A 12p	40361 40p
BC214L 12p	NKT403 75p	2N708 15p	40362 50p
BCY30 35p	NKT404 55p	2N930 20p	40430 1.00
BCY31 40p	OAS 25p	2N987 40p	40543 60p
BCY32 60p	OAI0 20p	2N131 25p	40594 1.00
BCY33 80p	OAA7 10p	2N132 25p	40595 1.00
BCY34 80p	OA70 10p	2N130Z 18p	40636 1.00
BCY38 1.00	OAA81 8p		
BCY45 50p	OAA90 8p		
BCY70 15p	OAA95 7p		
BCY71 20p	OAA20 7p		
BCY72 15p	OAA202 10p		

Full transistor list available—send for free copy today!

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL74 SERIES
BRANDED FAIRCHILD, I.T.T. AND TEXAS
 DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICING

No.	Description	1-11	12-24	25-99	100+	250+
7400	Quad 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	14p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7404	Hex inverters	20p	18p	14p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	14p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	14p	14p	12p
7413	Dual 4-input Schmitt triggers	20p	18p	14p	14p	12p
7430	Dual 4-input NAND gates	20p	18p	14p	14p	12p
7432	Single 8-input NAND gates	20p	18p	14p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	14p	14p	12p
7441	BCD-Decimal decoder/Nixie driver	75p	75p	70p	60p	65p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	75p	70p	60p	65p
7443	Excess 3-Decimal decoder TTL outputs	1.00	90p	90p	80p	70p
7447	BCD-Decimal 7 seg. decoder/Indicator driver	1.25	1.00	1.45	1.30	1.15
7448	BCD-Decimal 7 seg. decoder/Indicator driver TTL O/P	1.75	1.40	1.45	1.30	1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7453	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7454	4-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7460	Dual 4-input expanders	20p	18p	14p	14p	12p
7470	Single J-K flip-flop (gated inputs)	20p	27p	25p	22p	20p
7472	Single J-K flip-flop (gated inputs)	20p	27p	25p	22p	20p
7473	Dual J-K flip flop	40p	37p	35p	32p	30p
7474	Dual J-K flip flop	40p	37p	35p	32p	30p
7475	Quad J-K flip-flops with Preset and Clear	40p	37p	34p	31p	28p
7480	Gated Full Adder	40p	37p	34p	31p	28p
7481	16-bit read/write memory	1.25	1.15	1.10	1.00	90p
7482	2-bit binary Full Adder	87p	80p	70p	65p	60p
7483	4-bit binary Full Adder	1.00	90p	85p	80p	73p
7484	16-bit RAN with gated write inputs	90p	85p	80p	75p	71p
7488	Quad 2-input Exclusive OR gates	45p	41p	38p	35p	33p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	80p	75p	70p	65p	60p
7492	Divide twelve counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	75p	70p	65p	60p	55p
7494	Dual entry 4-bit shift register	80p	75p	70p	65p	60p
7495	4-bit up-down shift register	80p	75p	70p	65p	60p
7496	5-bit parallel/serial in/out shift register	1.00	87p	85p	80p	73p
74100	8-bit bistable latch	22.50	22.00	22.00	21.50	21.50
74118	Hexuple 8-bit Reset latches	1.00	95p	90p	80p	75p
74121	Monostable multivibrators	80p	55p	50p	40p	41p
74141	BCD-Decimal decoder/Nixie driver	1.00	90p	90p	80p	70p
74145	BCD-Decimal decoder (1-4 line) TTL O/P	1.50	1.40	1.30	1.10	1.10
74150	16-bit data selector/multiplexer	23.35	23.20	22.95	22.15	22.05
75181	8-bit data selector/multiplexer	1.10	95p	90p	80p	70p
74153	Dual 4-line to 1-line data selector multiplexer	1.00	90p	85p	80p	70p
74154	16-bit decoder/demultiplexer	22.00	21.75	21.55	21.30	21.05
74155	Dual 2-line to 4-line decoder/demultiplexer	1.55	1.47	1.35	1.10	1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	1.55	1.47	1.35	1.10	1.05
74190	Sync decade up-down counter, 1-line mode	1.95	1.85	1.75	1.60	1.50
74191	Sync 4-bit up-down counter, 1-line mode	1.95	1.85	1.75	1.60	1.50
74192	Sync decade up-down counter, 2-line mode	2.00	1.90	1.80	1.65	1.55
74193	Sync 4-bit up-down counter, 2-line mode	2.00	1.90	1.80	1.65	1.55
74196	Asynchronous presettable decade counter	1.50	1.40	1.30	1.10	1.00
74197	Asynchronous presettable 4-bit binary counter	1.50	1.40	1.30	1.10	1.00

Texas I.C. Handbook. Complete information on 100 types, 40p. Post 10p. Complete data on the above in booklet 20 pages. Ref. 29, issue 2 at 15p post paid. Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

INTEGRATED CIRCUITS

MFC4000P 55p
MFC4010P 60p
IC12 22.50
PA24E 1.50
TAD100 1.00
TAD110 1.50
MC724P 50p
702C (T05) 75p
709C (T05) 45p
709C (D.I.L.) 45p
723C(T05) 1.00
MC1303P 22.00
MC1304P 22.25
8L103D 1.50
914(T05) 75p
923(T05) 40p
TO8H1A 40p
20 watt amp. 44.47
TO8H1BA 40p
Pre amp 1.50

PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier

SL4008
Complete with 8-pair booklet, circuits and data
£1.50

TRIACS

Stud with accessories
P.I. Current 1-11
Type volts
BC35A 100 3 amps 80p
BC35B 200 3 amps 85p
BC35D 400 3 amps 90p
BC40A 100 6 amps 90p
BC40B 200 6 amps 1.05
BC40C 400 6 amps 1.05
BC45A 100 10 amps 1.05
BC45B 200 10 amps 1.15
BC45D 400 10 amps 1.25
BC50A 100 15 amps 1.35
BC50B 200 15 amps 1.45
BC50C 400 15 amps 1.75
BC40E 500 6 amps 1.25
BC48E 600 10 amps 1.45
BC50E 600 15 amps 1.95
DIAC 8D2 35p

SILICON RECTIFIERS				BRIDGE RECTIFIERS			
1 AMP MINIATURE PLASTIC WIRE ENDED				Miniature Potted Silicon 1" x 1" x 1"			
Type	P.I.V.	1-49	50+	100+	500+	1000+	
IN4001	50	5p	5p	4p	4p	3p	
IN4002	100	7p	6p	5p	4p	4p	
IN4003	200	8p	7p	6p	5p	4p	
IN4004	400	9p	8p	7p	6p	5p	
IN4005	600	10p	9p	8p	7p	6p	
IN4006	800	12p	10p	9p	8p	7p	
IN4007	1000	15p	12p	10p	9p	8p	

QUANTITY OFFERS! FROM STOCK

AF117 Mullard 20p	25 + 17p
	100 + 15p
	500 + 12p
	1000 + 10p
2N2646 Motorola 40p	25 + 35p
	100 + 32p
	500 + 25p
	1000 + 25p
OC170 Mullard 25p	25 + 20p
	100 + 18p
	500 + 15p
	1000 + 13p
BY127 Mullard 15p	25 + 12p
	100 + 10p
	500 + 9p
	1000 + 8p
OC35 Mullard 50p	25 + 45p
	100 + 40p
	500 + 35p
	1000 + 30p
2N2926 Green 10p	25 + 9p
	100 + 8p
	500 + 6p
	1000 + 5p
BC107 All Makes 10p	25 + 8p
	100 + 7p
	500 + 6p
	1000 + 5p
2N3055 Fairchild 75p	25 + 65p
	100 + 50p
	500 + 40p
</	

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Light guide

Sir—I have read with interest the article by Mr M. K. Titman on *Fibre Optics* published in your February edition. My Company is actively engaged in the field of fibre optics on behalf of JENAer Glaswerk Schott & Gen., of Mainz, Western Germany, who are one of the major suppliers and manufacturers of fibre optics and are world renowned for the range of high quality optical glasses.

I would like to draw the author's attention to some minor inaccuracies in the paragraph headed "Present Limitations". Schott produce a vast range of fibres, some of which will cater for infra-red transmission and, more especially, for ultra-violet light transmission. In both cases, these fibres are not currently available from any other European source and, indeed, the ultra-violet light transmitting fibre optic is unique to Schott and is not available from any other manufacturer.

With regard to the author's comments on long distance communications, I would like to take this opportunity of informing you that Schott are actively engaged both with the Post Office Research and various other commercial telecommunication companies here in the United Kingdom on the use of fibre optic light guides for long distance communication systems.

Existing fibres are used in aircraft communication links, because these light guides are not subject to noise and other electronic interference and this makes them ideal as signal transmission mediums within the aircraft.

The whole point I wish to make on this subject is really that the distance of 6 to 10 feet mentioned by Mr Titman in his article, would generally seem to indicate that this is the maximum length over which adequate signals can be transmitted, whereas signal lengths of 30 metres are quite normal.

One final item I would like to mention is the suggested use of fibre optics for the monitoring of vehicle lights. I wholeheartedly agree with him on this subject and believe that this positive signal indication is highly desirable for vehicles. I personally have had a

vehicle equipped and it has been running on the road for approximately two years now and I derive a great deal of satisfaction from being able to check from the driver's position that my lights are operating. The beauty of the fibre optic system is that it is fail-safe and will monitor all light conditions.

I sincerely hope that you find my comments of interest and I hope that they help to clarify one or two inaccuracies in the article mentioned.

A. Hardy,
Fibre Optics Division,
H. V. Skan Ltd.,
Solihull,
Warks.

Long distance optical communication is indeed an exciting prospect for the future since the bandwidth using light is very wide. Indeed this system is the only practical arrangement for the introduction of domestic video-phones.

At present fibre optics are not as acceptable as line of sight or mirrored circular waveguide systems, but development will reduce this gap. Bell Laboratories and ITT/STC in the U.S.A. are also actively working in this field using laser projectors with solid state photomultiplier detectors.

Present practical limitations on distance are governed primarily by the complexity of the projector/detector system and the 6 to 10ft I quoted assumed the simplest arrangement. As Mr Hardy points out, longer runs are feasible but care must be taken over projector/detector stability and sensitivity, or a modulated light system adopted.

I welcome the development of fibres for use in the infra-red and ultra-violet spectrum and also the low loss guides, and look forward to the widespread use of fibre optic guides in the future.—M.K.T.

Dogmatic

Sir,—With reference to the letter of Mr (or is it Mrs?) W. G. Jones (Abysmal Writing), published last month, I would like to make the following comments, partly in defence of a periodical to which I have subscribed since its inception,

and partly as a protest against the dogmatic criticism of a person entrusted with the education of tomorrow's technocrats.

To a person of such self claimed ability, the task of understanding and relating in his own words the underlying principles of *Logical Radio Control* should not have required such tremendous powers of concentration.

A dice is essentially a passive device and in itself "generates" nothing.

Hands do not "see".

When the counter is stopped the "numbers" cannot be in a random condition. Also, a previous statement made it clear that the count was cyclic from 1 to 6, and therefore not random. The randomness is achieved only as a function of probability with respect to time.

It is worth noting that within industry all explanations accompanying new circuitry are not crystal clear and textbook fashion. It is therefore almost a pre-requisite that persons operating with the presented information must be capable of salvaging the salient features and reconstructing these into realistic representation of the phenomena in question.

As an educator of sixth form students, Mr Jones might well be better employed in preparing his charges for such eventualities, instead of composing uninteresting letters. If, however, he is bent on writing low-level semi-technical jottings, perhaps he would be good enough to iron out his own ambiguities and fantasy phrases before attacking professionals.

J. P. T. Travers,
Poole,
Dorset.

Good vet needed

Sir,—I have just read Mr W. G. Jones' letter regarding the standard of writing in *PRACTICAL ELECTRONICS*. His general comments are, in my opinion, quite correct even though I would say the standard is slightly higher than the abysmal standard he gave it. The digital dice explanation of Mr Jones was definitely far easier to understand, but even then there was no reason given as to why it was necessary to run the digital dice at *forty-six thousand times* per second when the limit of visual observation is *fifteen times* per second even with the bulbs illuminated, which they are not in the digital dice.

May I therefore suggest that a standard instructional technique is employed as advocated by the D.E.S. in which each subject or project is divided into "Must Knows", "Should Knows" and "Could

Readout—

A SELECTION FROM OUR POSTBAG

Knows" and these are presented in a logical sequence. Obviously the circuit, components employed and method of construction are all "Must Knows" in order that the project can be completed but the internal functions of an integrated circuit are only a "Could Know" which could be omitted if, for example, space was short.

One further point on a similar path is that I am of the opinion that projects that are intended for use on a vehicle should be vetted by some good auto electricians.

Similarly, with ignition systems the authors appear to be quite unaware that the present h.t. lead is a bit of carbon string not copper wire and a capacitor discharge unit will give you an awful lot of trouble if you use the standard type h.t. lead.

May I suggest that future projects aimed specifically at car owners could be a Zenon tube timing light, an exhaust gas analyser, a dwell meter and how to connect a standard oscilloscope to a car along with the interpretation of the pattern. I know all these are commercially available but at £1,200 per set.

I trust that you will accept these comments as being constructive and if only part are incorporated in your excellent magazine I am sure you will find an ever increasing interest and increase in readership.

H. D. Briggs,
Telford, Salop.

Baby alarm

Sir,—I have just read with interest the article "Child Care" in the Gerry Brown column *On The Fringe*, January 1972 issue, and would like to say that it is about time a device was available on the market to help prevent the abduction of babies from their prams. To this end my company has marketed a product which electronically senses a baby's weight, and sounds an alarm bell should the baby be removed from its pram. The complete unit does not need to be permanently attached to the pram in question, but remains free to be used in a carry-cot or push-chair.

I would, however, disagree that one needs to sense pram movement, since statistics have shown that only a small percentage of baby abductions actually involve the taking of the pram, and to manufacture a device that senses brake position is

difficult, in so much that every pram manufacturer seems to have his own idea on braking.

One method that can be used is to have a small magnet attached to one of the spokes of one wheel that operates a reed switch during the first revolution of the wheel. This pulse triggers a self-latching switch, preferably an electronic one, because of the current drain involved in relays, and the alarm is sounded.

B. Naylor,
Bournemouth,
Hants.

Mind travelling

Sir—I read with great interest Gerry Brown's piece on "Brainwave Reinforcement" in the March issue of P.E. Perhaps you could pass on to him the message that the arrangement he shows does not actually work, for the following reasons. Alpha rhythms (of 8–12Hz, which are present in *all* normal persons) are generated when the eyes are closed and the subject is resting with mind blank and no distractions. The rhythms disappear on falling asleep. Any attempt to visualise mental pictures or watch a flashing light, even with the eyes closed, will tend to break up the Alpha rhythm.

The system in vogue in America operates by sound, that is to say the subject listens to gentle white noise or a low audio tone which is modulated by his own Alpha waves. The trick is not to listen too intently, but let the sound lull one into a state akin to that commonly experienced just prior to falling asleep. With a certain amount of practice it is possible to attain a high Alpha output and thus enforce complete relaxation. In effect the gadget tells you when you are relaxed and when you are not.

A possibility I have not investigated with Gerry's set-up is that the equipment actually handles Beta waves from the front of the head (18–25Hz) which result from minute motor movements of the eye during normal vision. It could be that the flashing light then interacts with eye movements and causes some kind of "way out" effect.

If Gerry wants an unusual experience though, he should try feeding the output from an audio oscillator to electrodes on his head. The oscillator *must*, of course, be battery powered otherwise he might find he is undergoing unwanted shock therapy! A mere 2–4V r.m.s. at 5–20Hz is sufficient to cause pronounced visual strobing in broad daylight and a wealth of coloured patterns when the eyes are closed.

D. Bollen,
Cornwall.

Poor bunnies!

Sir—With reference to Mr D. Nunn's enquiry as to an electronic ferret tracker: no doubt such a device would be entirely feasible. However, I would suggest that if Mr Nunn is so intent on hunting poor little bunnies with his nasty little ferrets, he reads a book on electronics and designs one himself.

May it take him a long while.

G. J. Rounce,
Grays,
Essex.

Collared

Sir—Reading the March *Readout* as promised, I noticed Mr D. Nunn's letter on ferret tracking. The Heath Co. Model GD-48 metal locator would be an excellent device for him. He could detect a piece of iron attached to the collar with good reliability from my experience.

Brice Ward,
Kidsgrove,
Stoke-on-Trent.

Scorpio shake-up

Sir—May I suggest that any readers who are building the P.E. Scorpio car ignition might find it advisable to tie down capacitors C6 and C7 to the board as the leads could possibly fracture under the low frequency conditions in a car.

G. Boyd,
Basingstoke,
Hants.

Lost components

Sir—Some time ago, the question of availability of components was commented on by dealers and constructors in your magazine.

Since that time, several well-known firms have closed down, merged with others, or reduced their range of products. I have to hand, two larger component suppliers' catalogues and various other smaller ones, yet not one of them lists items which were once easily obtainable.

The "Electroniques" (now defunct) 10 μ H to 10mH range or r.f. chokes and the Painton encapsulated chokes; the temperature compensating ceramic capacitors in the NPO (zero change), N and P types (i.e. the popular N750) were once available for frequency stabilisation of r.f. oscillators against temperature drift. Where have these items gone?

Perhaps a dealer who can supply these items would contact us.

M. J. Shepherd, BRS 25625,
72 Westerland Avenue,
Canvey Island, Essex.

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS AND AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated telescopic aerial, for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. Switched earpiece socket complete with earpiece. 10 transistors plus 3 diodes. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser with VHF section. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS


£8-50

P. P. & INS. 50p
(OVERSEAS P. & P. £1)



ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

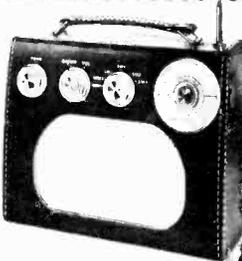


7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6-98** P. P. & INS. 41p (OVERSEAS P. & P. £1)

ROAMER SEVEN Mk. IV

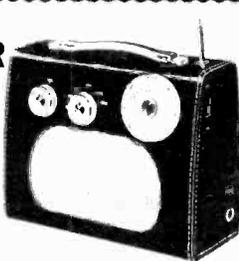
7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra



medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

TOTAL BUILDING COSTS **£5-98** P. P. & INS. 41p (OVERSEAS P. & P. £1)


ROAMER SIX

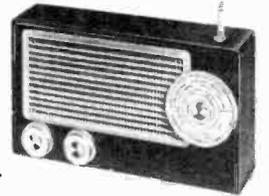

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£3-98** P. P. & INS. 26p (OVERSEAS P. & P. £1)

POCKET FIVE

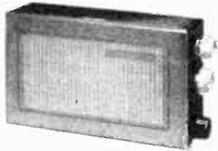

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2in x 1 1/2in x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£2-23** P. P. & INS. 21p (OVERSEAS P. & P. 63p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£2-50** P. P. & INS. 22p (OVERSEAS P. & P. 63p)

TRANS EIGHT

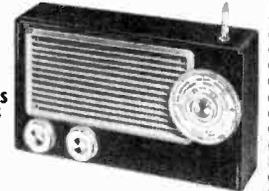

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£4-48** P. P. & INS. 31p (OVERSEAS P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; 4" x 2 1/2" Speaker; Terminal Strip; Ferrite Rod Aerial; 3 Plugs and Sockets; Battery Clips; 4 Tag Boards Balanced Armature Unit; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

ALL PARTS INCLUDING CASE AND PLANS **£5-50** P. P. & INS. 31p (OVERSEAS P. & P. £1)

FULL AFTER SALES SERVICE

★ Callers side entrance Barratts Shoe Shop
★ Open 10-11, 2.30-4.30 Monday-Friday, 9-12 Saturday

RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD.

Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for.....

Name

Address

P. E. 41

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A TO-5	3A TO-66	7A TO-66	10A TO-48	16A TO-48	30A TO-48
50	0-23	0-25	0-47	0-50	0-53	1-15
100	0-25	0-33	0-58	0-58	0-63	1-40
200	0-35	0-37	0-57	0-61	0-75	1-60
400	0-43	0-47	0-67	0-75	0-93	1-75
800	0-53	0-57	0-77	0-87	1-25	
1000	0-63	0-70	0-90	1-20	1-50	4-00

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0-04	0-05	0-05	0-07	0-14	0-21	0-47
100	0-04	0-06	0-05	0-13	0-16	0-23	0-75
200	0-05	0-08	0-06	0-14	0-20	0-24	1-00
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25
600	0-07	0-18	0-10	0-23	0-34	0-45	1-85
800	0-10	0-17	0-13	0-25	0-37	0-55	2-00
1000	0-11	0-25	0-15	0-30	0-46	0-83	2-50
1200	—	0-33	—	0-33	0-57	0-75	—

TRIACS

VBOM	2A TO-1	6A TO-66	10A TO-58
100	0-50	0-63	1-00
200	0-70	0-80	1-25
400	0-90	1-00	1-60

DIACS

FOR USE WITH TRIACS
BR100 D32... 37p each

UNIJUNCTION

UT46. Eqvt. 2N2646, Eqvt. T1843. BEN3000 27p each, 25-99 25p 100 UP 20p.

NPN SILICON PLANAR
BC107/106, 10p each;
50-99 9p; 100 up
8p each; 1,000 off
7p each. Fully tested
and coded TO-18 case.

FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

SPECIAL OFFER

2N2996 (Y) (0). 10 for 50p, 25 for \$1. 20,000 TO CLEAR.

CADMIUM CELLS

ORP12 40p
ORP60, ORP61 40p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM.

TO 2N706/8, BSY27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.
2p
20 For 0-50
50 For 1-00
100 For 1-75
500 For 7-50
1000 For 13-00

PHOTO TRANS.

OC71 Type 43p

SIL. G.P. DIODES 50p
300mV 30 5p
40pIV (Min.) 100... 1-50
Sub-Min. 500... 5-00
Full Tested 1,000... 9-00
Ideal for Organ Builders.

DI8D1 Silicon Unilateral switch 50p each.

A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

FULL RANGE OF ZENER DIODES
2-33V. 400mV (DO-7 Case) 13p ea. 11W (Top-Hat) 18p ea. 10W (80-10 Stud) 25p ea. All fully tested, 1/2 tel. and marked. State voltage required.

10amp POTTED BRIDGE RECTIFIERS on heat sink. 100 PIV. 80p each.

JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS
Exceptionally good value

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P. & P. \$1.50 only

Plus your satisfaction or money back guarantee.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed
Pak No. EQVT
T1 8 2G371B OC71
T2 8 D1374 OC75
T3 8 D1370 OC81D
T4 8 2G381T OC81
T5 8 2G382T OC82
T6 8 2G344B OC44
T7 8 2G345B OC45
T8 8 2G378 OC78
T9 8 2G393A 2N1302
T10 8 2G417 AF117
All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699

TEXAS. Our price 25p each.

120 VCB NIXIE DRIVER TRANSISTOR. Sim. B5X21 & C407, 2N1893 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 5p each. Any Qty.

NEW LINE

PLASTIC ENCAPSULATED 2 AMP BRIDGE RECTS.

Each
50V RMS 32p
100V RMS 37p
400V RMS 46p
Size 15mm x 6mm

KING OF THE PAKS Unequaled Value and Quality SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0-50
U2	60 Mixed germanium transistors AF/RF	0-50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0-50
U4	40 Germanium transistors like OC81, AC128	0-50
U5	60 200mA sub-min. Sil. diodes	0-50
U6	30 Silicon planar transistors NPN sim. B8Y95A, 2N706	0-50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0-50
U8	50 Sil. planar diodes 250mA, OA/200/202	0-50
U9	20 Mixed volts 1 watt Zener diodes	0-50
U11	25 PNP silicon planar transistors TO-5 sim. 2N1132	0-50
U13	30 PNP-NPN sil. transistors OC200 & 2N104	0-50
U14	150 Mixed silicon and germanium diodes	0-50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0-50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0-50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0-50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0-50
U19	25 Silicon NPN transistors like BC108	0-50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0-50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	0-50
U23	30 Mads' like MAT series PNP transistors	0-50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0-50
U25	25 300Mc/s NPN silicon transistors 2N708, BSY27	0-50
U26	30 Fast switching silicon diodes like IN914 micro-min	0-50
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CRS1/25-600	1-00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0-50
U32	25 Zener diodes 400mV DO7 case mixed volts, 3-18	0-50
U33	15 Plastic case 1 amp silicon rectifiers IN4000 series	0-50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	0-50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0-50
U36	25 Sil. planar NPN trans. TO-5 BFY50/51/52	0-50
U37	30 Sil. alloy trans. 80-2 PNP, OC200 28322	0-50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0-50
U39	30 RF germ. PNP trans. 2N1303/3 TO-5	0-50
U40	10 Dual trans. 6 lead TO-5 2N2906	0-50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0-50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF117	0-50
U43	25 Sil. trans. plastic TO-18 A.F. BC113/114	0-50
U44	20 Sil. trans. plastic TO-5 BC115/116	0-50
U45	7 3A SCR's TO-66 up to 600 PIV	1-00

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

POWER TRANSISTOR BONANZA!

GENERAL PURPOSE GERM. PNP
Coded GPM100. BRAND NEW TO-3 CASE. POSS. REPLACE.—OC25-28-29-30-35-36. NKT 401-403-404 405-406-430-451-452-453. T13027-3028. 2N250A, 2N456A 457A-458A, 2N511 A & B. 2G220-222, ETC. VCEO 80V VCE0 50V IC 10A PT. 30 WATTS Hfe 30-170
PRICE
1-24 25-99 100 up
43p each 40p each 38p each

SILICON High Voltage 250V NPN
TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCEO 250V VCEO 100/IC 6A/30 Watts. HFE type 20/IT 5MHZ.
OUR PRICE EACH:
1-24 25-99 100 up
50p 45p 40p

EX-STOCK TYPE EACH AS PRICED
OC20 50p OC28 40p AD149 43p BD131 70p BD139 75p
OC29 30p OC29 40p AL109 85p BD132 80p BD140 85p
OC23 35p OC35 33p AL103 85p BD135 70p BD135 75p
OC24 45p OC36 40p BD121 80p DR136 80p BU105 25
OC25 25p AD14040p BD123 75p BD137 70p 2N3054 45p
OC26 25p AD14240p BD124 70p BD138 80p

RTL MICROLOGIC CIRCUITS

Price each
Epoxy TO-5 case 1-24 25-99 100 up
uL900 Buffer 35p 33p 27p
uL914 Dual 2 1/2p
Gate 35p 33p 27p
uL923 J-K flip-flop 50p 47p 45p
Data and Circuits Booklet for I.C.'s Price 7p.

NEW QUALITY TESTED PAKS

Pak	Description	Price
Q1	20 Red spot trans. PNP AF	0-50
Q2	16 White spot R.F. trans. PNP	0-50
Q3	4 OC77 type trans.	0-50
Q4	6 Matched trans. OC44/45/81/81D	0-50
Q5	4 OC75 trans. MAT 101 & 1 MAT 121	0-50
Q6	4 OC72 transistors	0-50
Q7	4 AC128 trans. PNP high gain	0-50
Q8	4 AC126 trans. PNP	0-50
Q9	7 OC81 type trans.	0-50
Q10	7 OC71 type trans.	0-50
Q11	2 AC127/128 comp. pairs PNP/NPN	0-50
Q12	8 AC116 type trans.	0-50
Q13	3 AF117 type trans.	0-50
Q14	3 OC171 H.F. type trans.	0-50
Q15	5 2N2926 sil. epoxy trans.	0-50
Q16	2 GET880 low noise germ. trans.	0-50
Q17	3 NPN 1 ST141 & 2 ST140	0-50
Q18	4 Mads' 2 MAT 100 & 2 MAT 120	0-50
Q19	3 Mads' 2 MAT 101 & 1 MAT 121	0-50
Q20	OC44 germ. trans. A.F.	0-50
Q21	3 AC127 NPN germ. trans.	0-50
Q22	20 NKT trans. A.F. R.F. coded	0-50
Q23	10 OA202 sil. diodes sub-min.	0-50
Q24	8 OA81 diodes	0-50
Q25	6 IS914 sil. diodes 75PIV 75mA	0-50
Q26	8 AF116 germ. diodes sub-min. IN69	0-50
Q27	2 10A 600PIV sil. rectis. IS45R	0-50
Q28	2 Sil. power rect. BYZ13	0-50
Q29	4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0-50
Q30	7 Sil. switch trans. 2N706 NPN	0-50
Q31	6 Sil. switch trans. 2N708 NPN	0-50
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0-50
Q33	3 Sil. NPN trans. 2N1711	0-50
Q34	7 Sil. NPN trans. 2N2369, 500MHZ.	0-50
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2N2905	0-50
Q36	7 2N3046 TO-18 plastic 300MHZ NPN	0-50
Q37	3 2N3053 NPN sil. trans.	0-50
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702	0-50
Q39	7 PNP trans. 4 x 2N3704, 3 x 2N3705	0-50
Q40	7 NPN amp. 4 x 2N3707, 3 x 2N3708	0-50
Q41	3 Plastic NPN TO-18 2N3904	0-50
Q42	8 NPN trans. 2N5172	0-50
Q43	7 BC107 NPN trans.	0-50
Q44	7 NPN trans. 4 x BC108, 3 x BC109	0-50
Q45	3 BC113 NPN TO-18 trans.	0-50
Q46	3 BC115 NPN TO-5 trans.	0-50
Q47	6 NPN high gain 3 x BC107, 3 x BC108	0-50
Q48	4 BCY70 NPN trans. TO-18	0-50
Q49	4 NPN trans. 2 x BFY51, 2 x BFY52	0-50
Q50	7 BSY28 NPN switch TO-18	0-50
Q51	7 BSY95A NPN trans. 300MHZ.	0-50
Q52	8 BY100 type sil. rect.	1-00
Q53	25 Sil. & germ. trans. mixed all marked new	1-50

PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards \$3. P. & P. 30p.

SILICON PHOTO TRANSISTOR.

TO-18 Lens end. NPN Sim. to BPX 25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty. 1-24 25-99 100 up
Price each 45p 40p 35p

FET'S
2N3819... 35p 2N5458... 50p
2N3820... 50p 2N5459... 40p
2N3821... 35p BFW10... 40p
2N3823... 30p MPF105... 40p

NEW EDITION

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each. Red Cover Edition.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX-STOCK. SEND FOR FREE LIST.

OUR STOCKS of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductor. All available Ex-Stock at very competitive prices.

-the lowest prices!

74 Series T.T.L. I.C's DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C's. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.

BI-PAK Order No.	Price and qty. prices			BI-PAK Order No.	Price and qty. prices		
	1-24	25-99	100 up		1-24	25-99	100 up
BP00=8N7400	0-15	0-14	0-12	BP86=8N7486	0-32	0-30	0-28
BP01=8N7401	0-15	0-14	0-12	BP90=8N7490	0-67	0-64	0-58
BP02=8N7402	0-15	0-14	0-12	BP91=8N7491AN	0-67	0-64	0-78
BP03=8N7403	0-15	0-14	0-12	BP92=8N7492	0-67	0-64	0-58
BP04=8N7404	0-15	0-14	0-12	BP93=8N7493	0-67	0-64	0-58
BP05=8N7405	0-15	0-14	0-12	BP94=8N7494	0-77	0-74	0-68
BP07=8N7407	0-18	0-17	0-16	BP95=8N7495	0-77	0-74	0-68
BP08=8N7408	0-18	0-17	0-16	BP96=8N7496	0-77	0-74	0-68
BP09=8N7409	0-18	0-17	0-16	BP100=8N74100	1-75	1-65	1-55
BP10=8N7410	0-15	0-14	0-12	BP104=8N74104	0-97	0-94	0-88
BP13=8N7413	0-29	0-28	0-24	BP105=8N74105	0-97	0-94	0-88
BP16=8N7416	0-43	0-40	0-38	BP107=8N74107	0-40	0-38	0-36
BP17=8N7417	0-43	0-40	0-38	BP110=8N74110	0-55	0-53	0-50
BP20=8N7420	0-15	0-14	0-12	BP111=8N74111	1-25	1-15	1-00
BP30=8N7430	0-15	0-14	0-12	BP118=8N74118	1-00	0-95	0-90
BP40=8N7440	0-15	0-14	0-12	BP119=8N74119	1-35	1-25	1-10
BP41=8N7441	0-67	0-64	0-58	BP121=8N74121	0-67	0-64	0-58
BP42=8N7442	0-67	0-64	0-58	BP141=8N74141	0-67	0-64	0-58
BP43=8N7443	1-85	1-85	1-75	BP145=8N74145	1-50	1-40	1-30
BP44=8N7444	1-85	1-85	1-75	BP146=8N74146	1-80	1-70	1-60
BP45=8N7445	1-95	1-85	1-75	BP151=8N74151	0-05	0-05	0-00
BP46=8N7446	0-97	0-94	0-88	BP153=8N74153	1-20	1-10	0-95
BP47=8N7447	0-97	0-94	0-88	BP154=8N74154	1-80	1-70	1-60
BP48=8N7448	0-97	0-94	0-88	BP155=8N74155	1-40	1-30	1-20
BP50=8N7450	0-15	0-14	0-12	BP156=8N74156	1-40	1-30	1-20
BP51=8N7451	0-15	0-14	0-12	BP160=8N74160	1-80	1-70	1-60
BP53=8N7453	0-15	0-14	0-12	BP161=8N74161	1-80	1-70	1-60
BP54=8N7454	0-15	0-14	0-12	BP164=8N74164	2-00	1-90	1-80
BP60=8N7460	0-15	0-14	0-12	BP165=8N74165	2-00	1-90	1-80
BP70=8N7470	0-29	0-28	0-24	BP181=8N74181	2-75	2-60	2-40
BP72=8N7472	0-29	0-28	0-24	BP182=8N74182	0-97	0-94	0-88
BP73=8N7473	0-37	0-35	0-32	BP190=8N74190	3-50	3-25	3-00
BP74=8N7474	0-37	0-35	0-32	BP191=8N74191	3-50	3-25	3-00
BP75=8N7475	0-47	0-45	0-42	BP192=8N74192	2-10	1-95	1-75
BP76=8N7476	0-43	0-40	0-38	BP193=8N74193	2-10	1-95	1-75
BP80=8N7480	0-67	0-64	0-58	BP125=8N74195	1-10	1-05	0-95
BP81=8N7481	0-97	0-94	0-88	BP196=8N74196	1-80	1-70	1-60
BP82=8N7482	0-97	0-94	0-88	BP197=8N74197	1-80	1-70	1-60
BP83=8N7483	1-10	1-05	0-95	BP198=8N74198	5-50	5-00	4-00
				BP199=8N74199	5-50	5-00	4-00

PRICE-MIX. Devices may be mixed to qualify for quantity prices.

PRICES for quantities in excess of 500 pieces mixed, on application.

Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442.

LINEAR I.C's - FULL SPEC.

Type No.	Price		
	1-24	25-99	100 up
BP 201C - 8L201C	83p	53p	45p
BP 701C - 8L701C	83p	50p	45p
BP 702C - 8L702C	83p	50p	45p
BP 702C - 8L702C	53p	45p	40p
BP 709F - μ A709C	53p	45p	40p
BP 710 - 72710	53p	45p	40p
BP 711 - μ A711	58p	50p	45p
BP 741 - 72741	75p	60p	55p
μ A 703C - μ A703C	43p	35p	27p
TAA 263	70p	60p	55p
TAA 293	90p	75p	70p
TAA 350	170p	158p	150p

S.C.S. EA 1000 £2-63.

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C's

Type No.	Price		
	1-24	25-99	100 up
BP930	12p	11p	10p
BP932	13p	12p	11p
BP933	13p	12p	11p
BP935	13p	12p	11p
BP936	13p	12p	11p
BP944	13p	12p	11p
BP945	25p	24p	22p
BP946	12p	11p	10p
BP948	25p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP9983	40p	38p	35p
BP9984	40p	38p	35p
BP9997	40p	38p	35p
BP9999	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only.)

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR116	3013F
Anode voltage (Vdc)	170 min	175 min	5 min
Cathode current (uA)	2.3	14	8
Numeral height (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12 wide
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
Price each	£1.70	£1.55	£1.90

All indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.

STOP PRESS! NOW OPEN

BI-PAK'S NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices.

18 BALDOCK ST. (A10) WARE, HERTS. Tel. 61593
OPEN 9.15-6 TUES. to SATS. FRIDAYS UNTIL 8 p.m.


BI-PAK DO IT AGAIN!

50W pk 25W (RMS)

0.1% DISTORTION!

HI-FI AUDIO AMPLIFIER

THE AL50

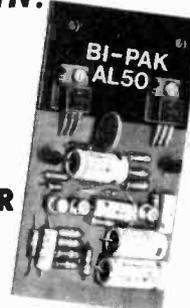

- ★ Frequency Response 15Hz to 100,000 Hz.
- ★ Load—3, 4, 8 or 16 ohms.
- ★ Distortion—better than 0.1% at 1kHz.
- ★ Signal to noise ratio 80dB.

ONLY

£3.25p each

- ★ Supply voltage 10-35 volts.
- ★ Overall size 63mm x 105mm x 13mm

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p.

STABILISED POWER MODULE SPM80 £2.95

TRANSFORMER BMT80 £1.95 p. & p. 25p

SPECIAL COMPLETE SET COMPRISING

2 AL50's, 1 SPM80 & 1 BMT80. ONLY £11 FREE P. & P.

DTL AND TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C's and experimental work.

Pak No.	Price	Pak No.	Price
UIC930 = 12 x μ A 930	50p	UIC948 = 8 x μ A 948	50p
UIC932 = 12 x μ A 932	50p	UIC951 = 5 x μ A 951	50p
UIC933 = 12 x μ A 933	50p	UIC961 = 12 x μ A 961	50p
UIC935 = 12 x μ A 935	50p	UIC963 = 5 x μ A 963	50p
UIC936 = 12 x μ A 936	50p	UIC964 = 5 x μ A 964	50p
UIC944 = 12 x μ A 944	50p	UIC967 = 5 x μ A 967	50p
UIC945 = 8 x μ A 945	50p	UIC909 = 5 x μ A 909	50p
UIC946 = 12 x μ A 946	50p	UICX 9 25 Assorted 930 Series	£1.50

Paks cannot be split but 25 Assorted Pieces (our mix) is available as PAK UIC9. Data Booklet available for the BP930 Series, PRICE 13p.

UIC00 = 12 x 7400N	50p	UIC46 = 5 x 7446N	50p	UIC81 = 5 x 7481N	50p
UIC01 = 12 x 7401N	50p	UIC47 = 5 x 7447N	50p	UIC82 = 5 x 7482N	50p
UIC02 = 12 x 7402N	50p	UIC48 = 5 x 7448N	50p	UIC83 = 5 x 7483N	50p
UIC03 = 12 x 7403N	50p	UIC50 = 12 x 7450N	50p	UIC86 = 5 x 7486N	50p
UIC04 = 12 x 7404N	50p	UIC51 = 12 x 7451N	50p	UIC90 = 5 x 7490N	50p
UIC05 = 12 x 7405N	50p	UIC53 = 12 x 7453N	50p	UIC91 = 5 x 7491N	50p
UIC10 = 12 x 7410N	50p	UIC54 = 12 x 7454N	50p	UIC92 = 5 x 7492N	50p
UIC13 = 8 x 7413N	50p	UIC60 = 12 x 7460N	50p	UIC93 = 5 x 7493N	50p
UIC20 = 12 x 7420N	50p	UIC70 = 8 x 7470N	50p	UIC94 = 5 x 7494N	50p
UIC40 = 12 x 7440N	50p	UIC72 = 8 x 7472N	50p	UIC95 = 5 x 7495N	50p
UIC41 = 5 x 7441AN	50p	UIC73 = 8 x 7473N	50p	UIC96 = 5 x 7496N	50p
UIC42 = 5 x 7442N	50p	UIC74 = 8 x 7474N	50p	UIC121 = 3 x 74121N	50p
UIC43 = 5 x 7443N	50p	UIC75 = 8 x 7475N	50p	UICX1 = 25 x Assorted	74's £1.80
UIC44 = 5 x 7444N	50p	UIC76 = 8 x 7476N	50p		
UIC45 = 5 x 7445N	50p	UIC90 = 5 x 7480N	50p		

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

Viscount III

Solid State Stereo Amplifier



The Specification sounds fine the System sounds great

Viscount III Audio Suite complete £49

**14 + 14 watts r.m.s. 40 Hz to 40kHz
3dB. Total distortion at 10 watts at
1 kHz - 0.1%**

This is real value for money! We have designed 3 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. It is available in 2 versions—R100 for ceramic cartridges and R101 for magnetic and ceramic. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For all systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with simulated teak plinth and dust cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES SYSTEM 1

Viscount III R101 amplifier £22.00 + 90p p&p
2 x Duo Type II speakers £14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover £23.00 + £1.50 p&p
Total £59.00

Available complete for only £52 - £3.50 p&p

SYSTEM 2

Viscount III R101 amplifier £22.00 + 90p p&p
2 x Duo Type III speakers £32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover £23.00 + £1.50 p&p
Total £77.00

Available complete for £69 + £4 p&p

SYSTEM 3

Viscount III Amplifier R100 £17.00 + 90p p&p
2 x Duo Type II speakers, pair £14.00 + £2 p&p
Garrard SP25 Mk. III with CER, diamond cartridge, plinth and cover £21.00 + £1.50 p&p
Total £52.00

Available complete for only £49 + £3.50 p&p

SPEAKERS

Duo Type II


Size approx. 17in 10in 6in. Drive unit 13in 8in with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

Duo Type III

Size approx. 23in 11in 9in. Drive unit 13in 8in with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms. Total distortion 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 10kHz into 47K equalised within 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivity given at full power). Tape out facilities: headphones socket, power out 250mW per channel. Tone controls and filter characteristics: Bass: ±12dB to 17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: Treble ±12dB to 17dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio 65dB. P.U.2—58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13in x 9in x 3in.

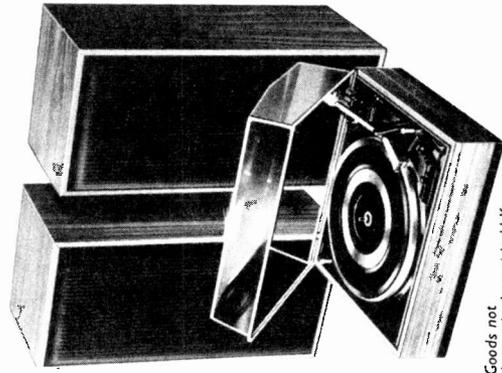

Goods not despatched outside U.K.



S.A.E. for fully illustrated leaflet.
Radio and TV Components (Acton) Ltd.
21d High Street, Acton, London W3 6NG
323 Edgware Road, London, W2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

We'll give you the chance you didn't take at school.



'O level standard in Maths, and Science or English, or a good C.S.E. in selected subjects could get you a great career in today's Navy. We'll train you to be one of our top technicians, working on space-age equipment and earning over £2,000 a year. If you're 15½-21 send for our free book.

APPRENTICESHIPS

Name

Address

Date of birth

(Enquiries from U.K. residents only)

Royal Naval Careers Service
(877QN2), Old Admiralty Bldg.,
Whitehall, London, SW1A 2BE.
Please send me, without obligation,
your free booklet, "Royal Navy
Technician Apprenticeships".



TOURIST

MARK 3 CAR RADIO ALL TRANSISTOR



Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

Circuit diagram 13p. free with parts Speaker, baffle and fixing kit
£1.25 extra plus P. & P. 25p

SET OF PARTS

£6.30 Plus P. & P. 50p

Speaker postage free when ordered with parts



DUETTO MK. II I.C. STEREO AMPLIFIER

Sophisticated styling combined with up-to-date electronics means Hi-Fi. This is what the Duetto Mk. II offers at a

realistic price. Mullard built stereo pre-amplifier/ tone control module and the highly efficient I.C. monolithic power chips ensure: reliability, very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum, etc.

Inputs: P.U. 150mV @ 2.2 Meg. (for cer. cartridge).
Auxiliary 100mV @ 1 Meg. (for radio, tape, etc.).

Outputs: 5 watts rms per channel into 8-15Ω speakers.
Switched stereo headphone socket with power correction.

Controls: Mono/stereo switch, selector switch, treble, bass, volume, balance and on/off switch. Neon indicator.

Tone Controls: Treble 14dB @ 15kHz.
Bass 14dB @ 60 Hz.

Power Bandwidth: ± 2db 20Hz - 25kHz.

£10.50 plus P. & P. 60p



RELIANT MK. IV

The Reliant Mk. IV provides a high standard of sound reproduction, with full mixing facilities. Its versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate bass and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry
- ★ Attractive Styling

1. Crystal Mic. or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 and 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

CONTROLS: 3 Volume controls. Bass control range 13dB @ 60 Hz. Treble control range ± 12dB @ 15KHz. Separate ON/OFF Switch. Neon Indicator.

POWER OUTPUT: 12 Watts R.M.S. into 3 to 4 ohms speaker.

SIGNAL/NOISE: Better than -60dB on inputs 3, 4 and 5 and -50dB on 1 and 2.

SUPPLY: 220 to 250V A.C. Mains.

SIZE: 12½in x 6in x 3½in.

PRICE

£9.50


Plus P. & P. 60p

CONTINENTAL 4-TRACK, 3-SPEED TAPE DECK

with high impedance heads

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ i.p.s. 4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7in. The R.C. 74 is driven by a powerful 200/250V 50-cycle a.c. motor. A heavy, accurately balanced flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ i.p.s. Fast rewind in both directions. Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

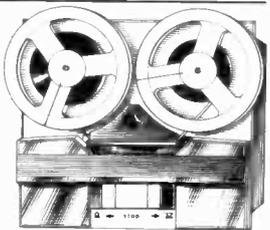The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6in. Every single deck fully tested before dispatch. Spools not supplied. £15. Plus 75p P. & P.



See opposite page for addresses

TRANSFORMERS

MAINS ISOLATING SERIES
 Primary 200-250 Volts Secondary 240 Volts Centre
 Tapped (120V) and Earth Shielded
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 11	7.0 x 6.0 x 6.5	1-61 30
100	60	3 8	8.9 x 8.0 x 7.7	2-39 36
61	100	5 12	10.2 x 8.9 x 8.3	2-62 52
30	200	9 8	12.0 x 10.3 x 10.0	4-39 52
62	250	12 4	9.5 x 12.7 x 11.4	5-80 67
55	350	15 0	14.0 x 10.8 x 12.4	7-77 82
63	500	27 0	17.1 x 11.4 x 15.9	11-20 * *
92	1000	40 0	17.8 x 17.1 x 21.6	20-63 * *
128	3000	63 0	24.1 x 21.6 x 15.2	34-10 * *

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 11	7.3 x 4.3 x 4.4	0-15-210-240	0-85 22
64	75	1 14	7.0 x 6.4 x 6.0	0-15-210-240	1-66 30
4	150	3 0	8.9 x 6.4 x 7.6	0-15-200-220-240	2-00 36
66	300	6 0	10.2 x 10.2 x 9.5	3-89 52
67	500	12 8	14.0 x 10.2 x 11.4	5-78 67
84	1000	16 0	11.4 x 14.0 x 14.0	10-49 82
93	1500	28 9	13.5 x 14.9 x 16.5	15-20 * *
95	2000	40 0	17.8 x 16.5 x 21.6	19-84 * *
73	3000	45 8	17.4 x 18.1 x 21.3	26-99 * *

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
 115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £7.87, P & P 67p.
 Also available a 20 Watt version, £1.67, P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	12V 24V	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5 0.25	1 12	7.6 x 5.7 x 4.4	0-12V at 0.25A x 2	0-85 22
213	1.0 0.5	1 0	8.3 x 5.1 x 5.1	0-12V at 0.5A x 2	1-01 22
71	2 2	1 0	7.0 x 6.4 x 5.7	0-12V at 1A x 2	1-33 22
18	4 2	2 4	8.3 x 7.0 x 7.0	0-12V at 2A x 2	1-86 36
70	6 3	3 12	10.2 x 7.6 x 8.6	0-12V at 3A x 2	2-24 42
108	8 4	5 4	10.0 x 8.3 x 8.2	0-12V at 4A x 2	2-48 52
72	10 5	6 3	7.9 x 10.8 x 10.2	0-12V at 5A x 2	2-94 52
17	16 8	7 8	12.1 x 9.5 x 10.2	0-12V at 8A x 2	4-54 52
115	20 10	11 13	12.1 x 11.4 x 10.2	0-12V at 10A x 2	5-78 67
187	30 15	16 12	13.3 x 12.1 x 12.1	0-12V at 15A x 2	10-67 82
226	60 30	34 0	17.0 x 14.5 x 12.5	0-12V at 30A x 2	19-61 * *

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5 1	4 4	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	1-01 22
79	1-0 2	0 7	7.0 x 6.4 x 6.0	1-35 36
3	2-0 3	2 2	8.9 x 7.0 x 7.6	2-01 36
20	3-0 4	6 0	10.2 x 8.9 x 8.6	2-48 42
21	4-0 6	0 0	10.2 x 10.0 x 8.6	2-94 52
51	5-0 6	8 8	12.1 x 10.0 x 8.6	3-66 52
117	6-0 7	8 12	12.1 x 10.0 x 10.2	4-36 52
88	8-0 10	0 0	14.0 x 11.7 x 10.0	5-64 67
89	10-0 12	2 2	14.0 x 10.2 x 11.4	7-14 67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5 1	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1-33 30
103	1-0 2	1 0	8.3 x 7.3 x 7.0	1-94 36
104	2-0 5	0 0	10.2 x 8.9 x 8.6	2-69 42
105	3-0 6	0 0	10.2 x 10.2 x 8.6	3-65 52
106	4-0 9	4 4	12.1 x 11.4 x 10.2	4-83 52
107	6-0 12	4 4	12.1 x 11.1 x 13.3	7-14 67
118	8-0 18	9 9	13.3 x 13.3 x 12.1	9-32 97
119	10-0 19	12 2	16.5 x 11.4 x 15.9	11-68 97

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5 2	4 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1-35 36
126	1-0 3	0 0	8.9 x 7.6 x 7.6	1-88 36
127	2-0 5	6 0	10.2 x 8.9 x 8.6	2-94 42
125	3-0 8	8 8	11.9 x 9.5 x 10.0	4-48 52
123	4-0 10	6 6	11.4 x 9.5 x 11.4	5-78 67
120	6-0 16	12 12	13.3 x 12.1 x 12.1	8-37 82
122	10-0 23	2 2	16.5 x 12.7 x 16.5	13-85 * *

LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Amps.	Weight lb oz	Size cm.	P & P £ p
45	1-5 1	9 9	7.0 x 6.0 x 6.0	1-34 30
5	4-0 3	11 11	10.2 x 7.0 x 8.3	2-03 42
86	6-0 5	12 10	8.3 x 8.9 x 8.3	3-07 52
146	8-0 6	4 4	8.9 x 10.2 x 10.2	3-49 52
50	12-5 11	14 14	13.3 x 10.8 x 12.1	5-20 67

All ratings are continuous. Standard construction; open with solder tags and wax impregnation. Enclosed styles to order.
TRANSISTORS FULL SPEC.
 BC107/108/109 9-0p each 2N 3055 68p each AD 161/162 60p pair
 25+ 7.5p with mica and bushes 25+ 55p with mica and bushes 100+ 45p 100+ 50p
 100+ 6.5p
 Minimum order 10 pieces this range.

AVOMETERS · MAINS KEYNECTOR ELECTROSIL RESISTORS

*Carriage via BRS

BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY
 LONDON W2 4AH Tel: 01-229 6681/2
 NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

RST VALVE MAIL ORDER CO.

BLACKWOOD HALL
 16a WELLFIELD ROAD, LONDON SW16 2BS
 SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p				
1N91	0-17	AC126	0-80	BF173	0-25	GJ4M	0-88	OC43	0-40
1N23	0-20	AC127	0-85	BF181	0-35	GJ5M	0-88	OC44	0-17
1N85	0-88	AC128	0-80	BF184	0-20	GJ7M	0-87	OC44M	0-17
1N263	0-60	AC187	0-25	BF185	0-20	HG1005	0-60	OC45	0-12
1N266	0-60	AC188	0-25	BF194	0-17	H8100A	0-60	OC46M	0-18
1N645	0-25	ACY17	0-30	BF195	0-15	MAT100	0-25	OC46	0-27
1N726A	0-80	ACY18	0-25	BF196	0-15	MAT101	0-30	OC57	0-60
1N914	0-07	ACY19	0-25	BF197	0-15	MAT120	0-25	OC58	0-60
1N4007	0-80	ACY20	0-20	BF861	0-28	MAT121	0-30	OC59	0-60
18021	0-20	ACY21	0-20	BF898	0-28	MJE250	0-87	OC66	0-60
18113	0-16	ACY22	0-10	BFX12	0-20	MJE255	1-87	OC70	0-12
18130	0-18	ACY23	0-26	BFX13	0-25	MJE3055	0-87	OC71	0-12
18131	0-18	ACY28	0-17	BFX29	0-25	NKT128	0-85	OC72	0-20
18202	0-23	ACY39	0-50	BFX30	0-25	NKT129	0-80	OC73	0-20
2G240	1-07	ACY40	0-15	BFX35	0-08	NKT211	0-25	OC74	0-30
2G301	0-20	ACY41	0-15	BFX63	0-60	NKT213	0-25	OC75	0-25
2G302	0-22	ACY44	0-25	BFX84	0-25	NKT214	0-16	OC76	0-25
2G305	0-30	AD140	0-60	BFX85	0-30	NKT216	0-37	OC77	0-40
2G371	0-22	AD149	0-60	BFX86	0-25	NKT217	0-25	OC78	0-25
2G381	0-25	AD181	0-27	BFX87	0-25	NKT218	1-13	OC79	0-22
2G414	0-30	AD182	0-37	BFX88	0-20	NKT219	0-88	OC81	0-20
2G417	0-22	AF106	0-80	BFY10	1-00	NKT222	0-20	OC81D	0-20
2N214	0-43	AF114	0-25	BFY11	1-25	NKT224	0-22	OC81M	0-20
2N247	0-25	AF116	0-25	BFY17	0-25	NKT251	0-84	OC81DM	0-18
2N250	0-60	AF116	0-25	BFY18	0-25	NKT271	0-25	OC817	0-40
2N270	0-40	AF117	0-25	BFY20	0-17	NKT272	0-25	OC82	0-25
2N697	0-15	AF118	0-02	BFY24	0-45	NKT273	0-15	OC82D	0-20
2N698	0-40	AF119	0-20	BFY44	1-00	NKT274	0-20	OC83	0-25
2N706	0-10	AF124	0-25	BFY50	0-22	NKT275	0-25	OC84	0-25
2N706A	0-12	AF125	0-20	BFY51	0-20	NKT277	0-20	OC114	0-30
2N708	0-16	AF126	0-17	BFY62	0-22	NKT278	0-25	OC122	0-60
2N709	0-25	AF126	0-17	BFY63	0-17	NKT279	0-25	OC123	0-60
2N711	0-37	AF139	0-30	BFY64	0-42	NKT304	0-75	OC139	0-25
2N987	0-58	AF178	0-58	BFY90	0-65	NKT403	0-75	OC140	0-85
2N1090	0-30	AF179	0-65	B8X27	0-60	NKT404	0-55	OC141	0-60
2N1091	0-38	AF180	0-62	B8X60	0-93	NKT678	0-30	OC169	0-20
2N1131	0-25	AF181	0-42	B8X76	0-18	NKT713	0-25	OC170	0-25
2N1132	0-25	AF186	0-40	BSY26	0-15	NKT773	0-25	OC171	0-25
2N1302	0-18	AFY19	1-18	BSY27	0-17	NKT777	0-25	OC200	0-40
2N1303	0-18	AFZ11	0-90	BSY51	0-60	078B	0-88	OC201	0-70
2N1304	0-22	AFZ12	1-00	BSY95A	0-12	0A5	0-20	OC202	0-80
2N1305	0-22	BSY26	0-25	BSY95	0-12	0A6	0-12	OC203	0-40
2N1306	0-25	BSY27	0-32	BT102/500R	0-75	0A7	0-10	OC204	0-40
2N1307	0-25	BSY28	0-25	BTY42	0-92	0A71	0-10	OC205	0-75
2N1308	0-25	BSY29	0-30	BTY79/100R	0-75	0A73	0-10	OC206	0-90
2N1309	0-25	BSY36	0-25	0A75	0-74	0A74	0-10	OC460	0-20
2N1420	0-93	BSY60	0-17	0A79	0-10	0A79	0-10	OC470	0-30
2N1507	0-28	BSY51	0-40	BTY79/400R	1-25	0A81	0-08	OCPT71	0-97
2N1626	0-38	BSY33	0-20	BY100	0-15	0A85	0-12	ORP12	0-60
2N1909	2-25	BSY55	0-20	BY126	0-16	0A86	0-15	RRP60	0-40
2N2147	0-75	BSY62	0-25	BY127	0-17	0A91	0-07	S19T	0-30
2N2148	0-60	BSY66	0-38	BY182	0-65	0A95	0-07	SAC40	0-25
2N2160	0-60	ASZ21	0-60	BY213	0-25	0A200	0-07	SFT308	0-38
2N2218	0-20	ASZ23	0-75	BY210	0-35	0A202	0-10	ST722	0-38
2N2219	0-20	AU Y10	0-80	BY211	0-32	0A210	0-25	ST723	0-68
2N2287	1-03	AU101	1-50	BY212	0-30	0A211	0-30	SX68	0-20
2N2287	0-20	BC107	0-10	BY213	0-25	0A220	0-65	SX831	0-30
2N2369A	0-16	BC108	0-10	BY215	0-20	0A2201	0-50	SX835	0-40
2N2444	1-99	BC109	0-30	BY216	1-00	0A2202	0-42	SX640	0-50
2N2613	0-28	BC113	0-25	BY216	0-62	0A2203	0-42	SX641	0-55
2N2646	0-45	BC116	0-20	BY288C3V3	0-60	0A2204	0-30	SX642	0-60
2N2712	0-25	BC116	0-25	BY288C3V3	0-15	0A2205	0-42	SX644	0-75
2N2784	0-60	BC116A	0-60	BY288C3V3	0-15	0A2206	0-42	SX645	0-75
2N2846	0-75	BC118	0-25	CH11	0-20	0A2207	0-47	V15/30P	0-50
2N2848	0-42	BC121	0-20	CRS1/05</					

MULTI-SPEED MOTOR

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000; 12,000 and 15,500 r.p.m. shaft is 1/2 in dia. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor, size approx. 2 1/2 in dia. x 3 in long. Price 89p plus 23p postage and insurance.



RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen. Specify 3, 10 or 15 amp—simply fit in place of switch.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 85p, plus 20p postage.

MICRO SWITCH

5A changeover contacts, 9p each. £1 doz. 15 amp Model 10p each or £1.05 doz.




EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 3 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, main connector, and fixing brackets, £2 plus 30p post and ins.



MAINS MOTOR

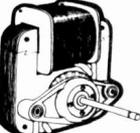Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one, then 5p for each one ordered.



THERMOSTAT

Continuously variable 30-90°C. Has sensor bulb connected by 33in of flexible tubing. On operation a 15A 250V switch is opened and in addition a plunger moves through approx. 1/2 in. This could be used to open valve on ventilator, etc. £1.50 plus 23p post and insurance.



FLUORESCENT INVERTER PE GEMINI AMPLIFIER WIDE BAND SIGNAL INJECTOR FUZZ BOX ULTRA-SOUND TRANSMITTER RECEIVER

as featured this last month

Send S.A.E. for parts list

We reserve the right to substitute components should deliveries be protracted so as to avoid undue delay.

MAINS OPERATED SOLENOIDS

Model 77E—small but powerful. 1/2 in pull—approx. size 1 1/2 in x 1 1/2 in 60p.
Model 400/1—1/2 in pull. Size 2 1/2 in x 2 in x 1 1/2 in 75p.
Model TT10 1 1/2 in pull. Size 3 in x 2 1/2 in x 2 1/2 in £1.80 plus 20p post and insurance.



TELESCOPIC AERIAL

For portable, car, radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 38p. KNUCKLED MODEL FOR F.M. 50p.



3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made by the famous "Cyclon" Company for the equally famous Radionobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra as required) with a frequency coverage 1,620kHz-525kHz and intended to operate with an I.F. value of 470kHz. Extremely compact (size only 2 1/2 x 2 1/2 in thick) with reduction gear for fine tuning. Snip price this month 65p, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post free.




CAPACITOR DISCHARGE CAR IGNITION

This system has proved to be amazingly efficient. We offer a Kit of Parts as PW circuit, £5.95 plus 20p postage. De-luxe model with prepared circuit board £6.95. When ordering please state whether for positive or negative systems.

ELECTRONIC IGNITION

RADIO STETHOSCOPE

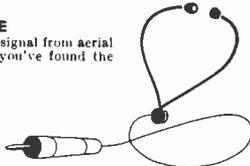Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal cartridge. £2—with stethoscope instead of earpiece 70p extra—post and ins. 20p.



STANDARD WATER SWITCHES

Standard Size 1 1/2 wafer—silver-plated 5-amp contact, standard 1/2" spindle 2 in long—with locking washer and nut.


No. of Poles	2	3	4	5	6	8	9	10	12
1 pole	40p								
2 poles	40p								
3 poles	40p								
4 poles	40p								
5 poles	40p								
6 poles	40p								
7 poles	70p								
8 poles	70p								
9 poles	70p								
10 poles	70p								
11 poles	70p								
12 poles	70p								

Dial Thermometer. Reading from 200-525°F used on Tricity and other cookers. This has a flange and can be mounted through a 1 1/2 in hole or alternatively it can just be rested on the object whose temperature it is required to measure. Size 2 1/2 in x 1 in overall dia. Depth 1/2 in below and 1/2 in above mounting panel. Price 80p each or 10 for £7.20.



THIS MONTH'S SNIP

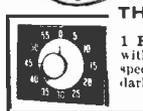1 HOUR MINUTE TIMER. Made by Smiths complete with control knob and calibrated dial. This month's special bargain at 50p. Useful in the kitchen, office and dark-room, etc.



THYRISTOR LIGHT DIMMER

For any lamp up to 1kW. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £1.99 plus 20p post and insurance.



MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohm speakers. Input suitable for crystal mic. or pick-up. 9V battery operated. Size 2 in long x 1 1/2 in wide. SPECIAL SNIP PRICE 80p each. 10 for £5.




POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit, house wiring, car, electricies. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or 2 for 60p. Post paid.



HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with 70p which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 r.p.m. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £5.75 plus 25p post and insurance. Don't miss this terrific bargain.

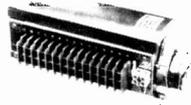

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect. First-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic μ PS matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only £1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.

BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nickel—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £1.75 plus 20p postage.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

Thermostat with Probe. Made by the famous Ranco Thermostat Co. Covers the range from approx. 0°-200°C variable by a control spindle, handles currents up to 16A. Length of capillary and sensor tube approx. 3ft 6in. These are ideal for ovens and all general purpose thermostat. Price 60p each or 10 for £4.50.

Small Tuning Condenser as fitted to many imported Japanese and Hong Kong radios. Two gang about 200pF per gang. Size approx. 1 1/2 in with a 1/2 in dia. spindle with dust cover. 25p each or 10 for £2.25.

Best Bink. Small type as used with OC81, etc. Price 5p each or 10 for 45p.

High Voltage Condenser. 0.265 mfd 1500V RMS which means that these have a d.c. rating of over 4,000V. 75p each or 10 for £6.75.

125W Starter. For 8ft fluorescent tubes. Mazda 1 1/2 in canister 4 pin base. Price 80p each or 10 for £1.80.

IT Transformers. 465 K.C. double tuned and made for transistor circuits. 35p per set of 3. 10 sets for £3.15.

Spectacle Frames (No lenses). With built-in hearing aids. The amplifier and battery being housed in the arms. Although these are complete hearing aids we are selling them purely for the sub miniature component they contain. We give no guarantee that they are in working order also these may be secondhand. Price £2.50 each.

Foot Switch. Twin levers each of which operates a 10A QMB change over switch. Price 90p each.

9V Gram Unit. On unit plate with 33-45 change lever, complete with turntable price £2.25 each, plus 20p post and insurance.

18 Watt Plug and Socket. 15p per pair. 10 pairs for £1.35.

Programmers. 5 r.p.m. Made by Magnetic Devices, Ltd. The contacts may be set to trigger anywhere around the shaft, ideal for motivated lighting displays, sequential switching, etc.

Drive motors are 200-240V 50Hz, 23A. Has 2 changeover contacts. Price £1.50. Model B has 11 changeover contacts. Price £2.80.

Black Heat Elements. Copper clad 1/2 in tubular construction replacements in Tricity and many other cookers also suitable if connected in series to heat airing cupboards and for other low temperature applications. The following types are available: 900W model, 1 1/2 in long x 1 1/2 in wide. Made by Backer. Price 75p or 10 for £6.75.

2,200W model, W shaped, 1 1/2 in long x 9 in wide. 85p each or 10 for £7.65.

Radiant Cooker Rings. As fitted to Tricity and many other popular cookers. We have two types. These are copper clad 1/2 in tubular construction. Both models having an external diameter of 6 1/2 in and the elements have been slightly flattened to increase radiation. Backer Type 7D1, 2,000W has a metal cover, size approx. 3 in x 1 1/2 in x 1 1/2 in over the element connections. So in addition to being a replacement this could also quickly be made into a boiling ring as it only needs mounting on a simple iron frame. This element is rated 2,000W but it is perfectly safe on 240V and as these are usually simmerstat controlled the lower voltage rating is not all that important. Price 75p each or 10 for £6.75.

Backer Model 7D1 MK.II again 2,000W rated but 230-240V, has no cover over element ends. Price 65p each or 10 for £5.65.

Tricity Cooker Elements. We have quite an assortment of these and will describe them in future issues—but if in the meantime you are needing these then please let us have a sketch, we may have the exact one in stock.

Slide Switch. 2-pole changeover panel mounting by two 6BA screws. Size approx. 1 in x 1 in rated 250V lamp. 6p each, 10 for 54p, 100 for £5.10, 500 for £24.

Sub Miniature Slide Switch. DPDT 19mm (1 in approx.) between fixing centres. 18p each or 10 for £1.08.

Thermal Trip. Bakelite encased called the "Klixon". Current passes through the heater coil and bi-metal strip clicks the circuit open should the current exceed 3A. Quite small and with lag and lead connections, ideal for protecting transformers or motors. Price 25p each or 10 for £2.25.

Mains Transformer. Primary 240V tapped 220V. Secondary 20V 1A. Price 60p each or 10 for £4.40.

Transformer. Primary 230-240V. Secondary 6.5-0-6.5V 1A. With fitted primary screen. 65p each or 10 for £5.85.

Small Croc. Clips. Suitable for instruments, etc. 5p each or 10 for 45p.

Bell Transformer. Normal mains input 4, 6, 8V output, normal bakelite case with protective connections. 75p each.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

24 HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.) 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon.

Sinclair Project 60



Project 605

The easy way to buy and build Project 60



Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier.

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
12 W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag P.U., F.M. Tuner, etc.	£23.90
25 W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80 W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60 W. RMS into 8 ohms)	2 x Z.50s, Stereo 60 PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311

sinclair

Project 60 Stereo F.M. Tuner

Built and tested. Post free. **£25**



The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** $7\mu\text{V}$ for lock-in over full deviation. **Squelch level:** $20\mu\text{V}$. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ($\pm 1\text{dB}$). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** $2\mu\text{V}$. **Cross talk:** 40dB. **Output voltage:** $2 \times 150\text{mV}$ R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Stereo on, tuning. **Size:** $93 \times 40 \times 207\text{mm}$.

Stereo 60 Pre-amp/control unit

Built, tested and guaranteed. **£9.98**



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A curve $\pm 1\text{dB}$: 20 to 25,000 Hz. Ceramic p.u. – up to 3mV. Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 12 to –12dB at 10KHz. BASS + 12 to –12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** $66 \times 40 \times 207\text{mm}$.

A.F.U. High & Low Pass Filter Unit


Built tested and guaranteed. **£5.98**



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off (–3dB) variable from 28KHz to 5KHz. L.F. cut-off (–3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. **Size:** $66 \times 40 \times 90\text{mm}$.

Z.30 & Z.50 power amplifiers

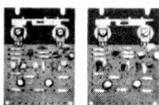Built, tested and guaranteed with circuits and instructions manual. **Z.30 £4.48** **Z.50 £5.48**



The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8 Ω) and all lower outputs. Whether you

use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts

20 watts R.M.S. into 3 ohms using 30 volts

Z.50 40 watts R.M.S. into 3 ohms using 40 volts

30 watts R.M.S. into 8 ohms using 50 volts

Frequency response: 30 to 300,000Hz $\pm 1\text{dB}$.

Distortion: 0.02% into 8 ohms.


Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms (for 15w into 8 Ω)

For speakers from 3 to 15 ohms impedance.

Size: $14 \times 80 \times 57\text{mm}$.

Power Supply Units

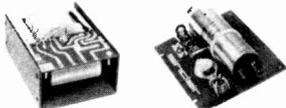

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ.5 30 volts un stabilised £4.98

PZ.6 35 volts stabilised £7.98

PZ.8 45 volts stabilised

(less mains transformer) **£7.98**

PZ.8 mains transformer £5.98

Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

sinclair

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

PE5

YATES ELECTRONICS

(FLITWICK) LTD.

RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction, 1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W Erie wire wound. 1/4W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7Ω-2.2MΩ	E24	1-99 100+
	10%	3.3MΩ-10MΩ	E12	1-0p 0-8p
	2%	10Ω-1MΩ	E12	1-0p 0-8p
	10%	1Ω-3.9Ω	E12	1-0p 0-8p
	5%	4.7Ω-1MΩ	E12	1-0p 0-8p
1/2	5%	1Ω-10Ω	E12	6p 5-5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ. E12 pack 325 resistors £2-40. E24 pack 650 resistors £4-70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2V, lin 1/2V). Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix). Sub-miniature 0-1V, 5p each. Miniature 0.25W, 6p each.

SEMICONDUCTORS

AC107 15p	BC108 10p	BFY52 22p	OC71 12p	1N4006 12p
AC126 12p	BC109 10p	BY127 12p	OC72 12p	1N4007 12p
AC127 12p	BC147 13p	BZ110 20p	OC81 12p	2N2926B 9p
AC128 12p	BC148 13p	BZ113 20p	OC82 12p	2N2926C 9p
AC131 12p	BC149 13p	OA85 7p	OC82D 12p	2N2926Y 9p
AD140 50p	BC157 14p	OA90 5p	ORP12 50p	2N2926G 10p
AF114 20p	BC158 14p	OA91 5p	1N4001 6p	2N3055 60p
AF115 20p	BC159 14p	OA202 7p	1N4002 10p	2N3702 13p
AF116 20p	BC179 32p	OC26 45p	1N4003 10p	2N3703 11p
AF117 20p	BFY50 22p	OC44 12p	1N4004 10p	2N3707 13p
BC107 10p	BFY51 22p	OC45 12p	1N4005 12p	2N3711 10p

ZENER DIODES

400mW 5% 3.3V to 30V, 15p. LINEAR I.C.'s (D.I.L.) DIL Socket 14 and 16 pin. 16p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p.

ELSTOW STORAGE DEPOT,
KEMPSTON HARDWICK,
BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2. Catalogue which contains data sheets for most of the components listed will be sent free on request. 5p stamp appreciated. 10% DISCOUNT TO ALL CALLERS ON SATURDAYS

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7 1/2p, 0.33μF, 11p, 0.47μF, 13p, 160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3 1/2p, 0.15μF 4 1/2p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7 1/2p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 3 1/2p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6 1/2p, 0.47μF, 8 1/2p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2 1/2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

6p each. (μF/V) 10/2.5, 40/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6.4/6.4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64, 20/64, 32/64.

ELECTROLYTIC CAPACITORS—MULLARD C437

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p, 100/64, 160/40, 250/25, 400/16, 640/10, 1000/6.4, 1600/2.5, 12p, 160/64, 250/40, 400/25, 640/16, 1000/10, 1600/6.4, 2000/4, 2500/2.5, 15p, 250/64, 400/40, 640/25, 1000/16, 1600/10, 2500/6.4, 3200/4, 4000/2.5, 18p.

ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25. 5p each.

VEROBOARD

0.1	0.15
22p	16p
24p	24p
24p	24p
3 1/2 x 3 1/2	24p
3 1/2 x 5	27p
17 x 2 1/2	75p
17 x 3 1/2	100p
17 x 5 (plain)	78p
17 x 3 1/2 (plain)	82p
17 x 2 1/2 (plain)	60p
2 1/2 x 5 (plain)	42p
2 1/2 x 3 1/2 (plain)	12p
Pin insertion tool	52p
Spot face cutter	42p
Pkt. 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Stereo socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin Plug 12p. Socket 8p. 4 way screened cable, 15p/metre. 6 way/screened cable 22p/metre.

BATTERY ELIMINATOR

£1.50 9V mains power supply. Same size as PP9 battery.

Component Factors

ALL GOODS NEW AND GUARANTEED
BARGAIN PRICES

P.O. BOX No. 18
LUTON • BEDS.
LU1 1SU

SPECIAL RESISTOR OFFER

Due to the enormous response to our last offer, here is another bargain. **250 FOR £1**
E24 Series 4.7Ω 10MΩ 1/4W and 1/2W, 5% and 10% mixed. Your selection, but subject to a maximum of 20 different values, and no more than 50 of any one value. If any value is out of stock the nearest will be sent. Note: No quantity discount allowed.

Miniature Ceramic Lemco All 750V

10%
3PF, 5PF, 10PF, 20PF, 25PF, 40PF, 75PF, 100PF, 120PF, 180PF, 220PF.
Price: 2 1/2p each or 10 for 20p (same value).

Latest Transistor Equivalents Book, 40p

1000MFD 12V	12p
2500MFD 6V	10p
2500MFD 12V	12p
1000MFD 50V	35p
1000MFD 25V	25p
100MFD 50V	10p

DIODES

100V 1A Bridge	50p
100V 20A Plastic Case Rectifier	50p
OA5	20p
OA47	5p
IN5054 (1KV)	10p
IN914	6p
OA202 equiv.	5p

TUNNEL DIODES

IN3717	£1
TD715	50p
TD716	40p
TD717	50p
TD719	50p

ZENER DIODES

3V3 BZ Y88C	10p
3V9 BZ Y88C	10p
4V3 BZ Y88C	10p
5V1 MZ5-IT5	10p
5V6 IN752A	15p
6V8 BZ Y96C	15p
7V5 BZ Y96C	15p
10V K54A	10p
13V BZ Y94C	15p
20V BZ X22	12p
24V BZ Y88C	12p
39V IN5259	15p

S.G.S. EA1000 Amplifier Module with Manual, £2.60.

Large range of Tantalum, Polycarbonate and Polyester capacitors available.

IC-12	£2.60
μL914	30p
MC1027	£2
SN7400N	15p
SN7410N	15p
2N706	10p
BFY51	10p
2N3866	80p
2N3055	60p
BSX21	12p

Mains Transformer 32-0.32 at 150mA 50p
Mains Transformer 150V at 20mA, 8V at 650mA 75p

1/2 Black Knob with Silver Disc 1/2in hole 3p
P.V.C. Wire 14/0076 100yd 50p or 1p per yd
Miniature RF chokes 0.22, 1, 1.5, 2.2, 12, 15, 22μH 8p each
Red Panel Neon, 15p
Neon lamp A230, 5for 20p. Strikes at 70V

TERMS: Cash with order. Post and packing free on orders above £5. For smaller orders please add 10p. DISCOUNT: orders above £10—10%, above £20—15%. All goods subject to a money refund guarantee if not satisfied. We have many components not advertised, and enquiries are welcome. Price list 5p. Data sheets 5p. Trade enquiries welcome.

REEDS REEDS REEDS

We offer a comprehensive range of reed switch devices. These are not "seconds" or "job lots", but genuine manufacturers stock lines. Send S.A.E. for full data and prices.

INTRODUCTORY OFFERS

Reed Relay type 2/E 3V .. 25p each
Miniature Reed Switches type A 1/2A 200V .. 20p each
Reed Push Button Switches I contact .. 85p each

REED COILS

3, 6, 9, 12, 24V Miniature .. 27p
Small .. 27p
Standard .. 34p

REED SWITCHES

Large range of many sizes, types and manufactures
Popular types: E Small normally open .. 10 for 50p
A Miniature normally open .. 24p each
B Standard change over .. 40p each

REED RELAYS

Many versions available, popular types:
3, 6, 9, 12, 24V
Miniature 1/A normally open .. 56p
Small 2/E I contact .. 36p
2/EE 2 contacts .. 44p
2/EE 3 contacts .. 52p
STD 3/B change over .. 87p

REED PUSH BUTTON SWITCHES


Momentary Action
1 contact .. £1.00
2 contacts .. £1.25
Illuminated 1 contact .. £1.30
Illuminated 2 contacts .. £1.55

REELS of ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g.
50, 100, and 200 grams. Send for prices
Packing and postage 7p on all orders.

C.B.M. ELECTRONIC COMPONENTS LTD.
26 Avon Trading Estate, Avonmore Road, London, W.14

SUPERSOUND 13 HI-FI MONO AMPLIFIER

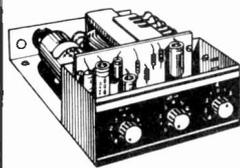


A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz - 30KHz ± 3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, etched-on panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. P. & P. 25p.

PRICE £10.50

DE LUXE STEREO AMPLIFIER

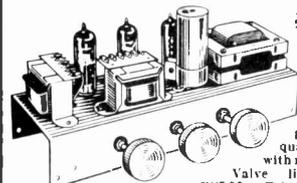

A.C. mains 200-240 volts, 50/60Hz. Heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2-2 ECL86 Triode Pentodes.

1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in x 4in x 4in. Overall height including valves 5in. Ready built and tested to a high standard. Price £2.92. P. & P. 45p.

SPECIAL PURCHASE OF MANUFACTURER'S SURPLUS! All Transistor F.M. tuner head with win A.M. Gang incorporated. Beautifully engineered with precision gear reduction drive. F.M. R.F. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional AFC connection. Built on printed circuit board and fully screened. Extremely stable over range 88-108 Mc/s. Brand new and pre-aligned. Size 2 1/2 in. H. x 1 1/2 in. W. x 2 1/2 in. D. For 6V D.C. or 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2.25 post free. Connection details supplied.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2 in x 3 in approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS 8in x 6in x 1/8in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to approx. 22 1/2 in. Maximum diameter 1/2 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL 3 1/2inW x 3inD. Price £1.75. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.38. P. & P. 30p. Tapped Primary 200-220-240V. Sec. 21.5V at 500mA. 65p. P. & P. 13p.

4 AMP BATTERY CHARGER TRANSFORMER Brand new. For 6 or 12V. 240V Primary. Secondary volts r.m.s. off load 10 and 16.5V. Overall size approx. 2 1/2 in x 2 1/2 in x 3 in. Weight 3lb. Limited number at £1.35. P. & P. 35p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 6p.

4-SPEED RECORD PLAYER BARGAINS Mains models. All brand new in maker's packing. **LATEST B.S.R. C108/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £8.97. Carr. 50p. With stereo cartridge £7.97. Carr. 50p. **LATEST GARRARD MODELS. S.A.E. for Latest Prices!**

PRECISION ENGINEERED PLINTHS Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025/TC, 2500, 3000, 3500, 5100, 8P25 11 and 111, SL65B, AT60, etc., or B.S.R. C109, C129, A21, etc. Choice of black leatherette or oak grain finish. Size 12 1/2 in x 14 1/2 in x 3 1/2 in high (approx. 7 1/2 in high, including rigid smoked acrylic cover). Price £5.50 P. & P. 60p.

LATEST ACOS GP91/1SC Mono Compatible Cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

SONOTONE 9TACH COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1.63. P. & P. 10p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. £1.60. P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II A top-quality record player amplifier employing heavy duty double wound mains transformer, EC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3d. x 6h. Ready built and tested. Price £3.75. P. & P. 40p. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit cabinet below. Price £4.88. P. & P. 50p.

DE LUXE QUALITY PORTABLE R/P CABINET MK II Uncut motor board size 14 1/2 in. clearance 2in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD record or Single Player (except AT60 and SP25). Size 18 x 15 x 8 in. Price £4.75. P. & P. 50p.

SPECIAL OFFER!! HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Ynair front. Size 16 1/2 in high x 10 1/2 in wide x 5 1/2 in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Carr. 65p.

CABINET AVAILABLE SEPARATELY £4.50. Carr. 60p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £8.50. Carr. 65p.

LOUDSPEAKER BARGAINS

5in 3 ohm £1.05, P. & P. 15p. 7 x 4in 3 ohm £1.15, P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1.62, P. & P. 20p. E.M.I. 13 1/2 x 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two built-in tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW. 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflex ceramic ferrobar magnet assembly £8.25. Guitar models: 25w £8.50, 35w £8.50. P. & P. 38p each. E.M.I. 3in HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohm 85p each. P. & P. 13p.

12in "RA" TWIN CONE LOUSPEAKER 10 watts peak handling, 3, 8 or 15 ohm. £2.20. P. & P. 30p. 35 ohm SPEAKERS 3". ONLY 63p. P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2 in x 1 1/2 in x 1 1/2 in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. (Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £2.75 each. P. & P. 25p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually 1 1/2 yd. only, our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES


Adjustable headband with comfortable flexiform earmuffs. Wired and fitted with standard stereo 3 1/2 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. Price £2.95. P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1.05. P. & P. 8p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/2 in. Brand new - complete with instructions. Price 85p. P. & P. 13p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100A for balance or tuning. Approx. size 1 1/2 in x 1 1/2 in. Limited number 75p. P. & P. 10p.

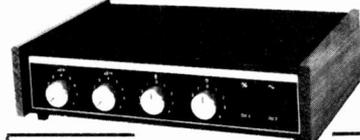HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 6 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts - no extra to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response ±3dB 12-30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ±3dB 12-15,000Hz. Bass boost approx. to ±12dB. Treble cut approx. to -16dB. Negative feedback 18dB over 1m amp. Power requirement 35V at 1.0 amp. Overall size - 12" wide x 8" deep x 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES AMPLIFIER KIT. £10.50 P. & P. 16p. POWER PACK KIT. 23 P. & P. 30p. CABINET. 23 P. & P. 30p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested. £20.50. Post Free.

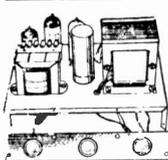Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER BASE MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. x 4in. d. x 4 1/2 in. h. Incorporates EC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 44 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.


HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 8 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 8in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY. **OUR ROCK BOTTOM BARGAIN PRICE** £2.75 P. & P. 35p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Full section wound output transformer to match 8-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7.97. P. & P. 55p. Also available ready built and tested complete with std. input sockets, £8.97. P. & P. 55p.

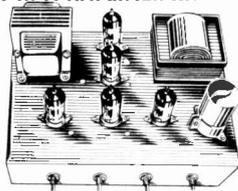

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985


SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

PHOTOELECTRIC KIT

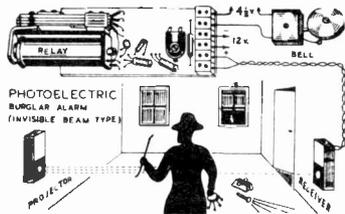CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT

£2-60

Postage and Pack, 15p (U.K.).
Commonwealth:
SURFACE MAIL 25p
AIR MAIL £1 40
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1-25. Postage and Pack, 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1-85. Postage and Pack, 15p (U.K.). Commonwealth: Surface Mail 20p; Air Mail £1-15.

JUNIOR PHOTOELECTRIC KIT

Versatile invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.
CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".
Price £1-25. Postage and Pack, 10p (U.K.). Commonwealth 20p; Airmail 50p.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.
Price 75p. Post and Pack, 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 50p.

YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

A.M.C. ELECTRONICS LTD.

SCORPIO ELECTRONIC IGNITION

Complete kit of parts and comprehensive constructional data giving answers to most of the questions concerning operation, installation and fault finding.

KIT AS ABOVE—£11-25 post paid.

CONSTRUCTION DATA—10p.

COMPONENT PRICE LIST—S.A.E. Please.

GEMINI TUNER

Please ask to be put on our mailing list (U.K. only). Components available to date include Tuner Head, Drive Components, Dial, Front Panel, P.C.B., L1, L2, F1, F2, T1, sets of Resistors, Capacitors and Semiconductors.

AMCEL, MAIL ORDER, 160 DRAKE ST., ROCHDALE

Tel. 0706-46234

MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES LARGEST RANGE
BRAND NEW FULLY GUARANTEED

MOTOROLA

We can now offer a vast range of Motorola IC's at industrial distributor prices.

FAIRCHILD (RTL)

Op. Amps. 1-11 12 24 25-99

Op. Amps.	1-11	12	24	25-99
L702A	T05	2-80	2-70	2-60
L702C	T05	0-77	0-72	0-67
L703C	T05	0-62	0-57	0-52
L709C	T05	0-38	0-36	0-31
L709C	D1L	0-33	0-31	0-27
L710C	T05	0-47	0-42	0-37
L710C	D1L	0-45	0-40	0-35
L711C	T05	0-49	0-44	0-39
L711C	D1L	0-45	0-40	0-35
L716C	T05	1-87	1-75	1-70
L723C	T05	0-75	0-72	0-66
L739		1-86		
L741C	T05	0-40	0-38	0-34
L741C	D1L	0-38	0-36	0-32
LM741C	D1L	0-70	0-65	0-60
SN72709F	D1L	0-45	0-40	0-35

MULLARD PLESSEY

TTL	8L403D	1-50
FJH101	SL011C	1-70
FJH121	SL021C	2-60
FJH141	SL701C	1-45
FJH161	SL702C	1-25
FJH171		0-91
FJH221		0-87
FJH101		1-37
FJH121		1-87
FJH141		3-12
FJH191		1-87
FJH251		3-12
FJK101		2-25
FJY101		0-80

TOSHIBA

TH9013P £4-57
20 WAIT AMP
TH9014P £1-50
PRE-AMP

MULLARD

DATA SHEETS £0-12

DTL

FCH101	1-50	FCH121	1-05	FCH201	1-32	FCH231	1-50	FCJ101	1-62	FCJ111	1-55	FCJ201	1-80	FCJ211	2-75	FCK101	4-37	FCY101	1-05

GENERAL ELECTRIC

PA239	2-21	PA246	1-54	PA264	1-76	PA285	1-93

SIEMENS

TAA151	0-88	TAD100	1-97	TAA435	0-73	TAD110	1-97

SGS

TAA661B	£1-32	TAA700	£3-50	TAA621	£2-03	TBA651	£1-69

All TTL IC's may be mixed to qualify for quantity discounts.

8 Pin TO-5 I.C. Holders	20-20
10 Pin TO-5 I.C. Holders	20-25
12 Pin TO-5 I.C. Holders	20-40
8 Pin Dual-in-Line I.C. Holders	20-20
14 Pin Dual-in-Line I.C. Holders	20-17
16 Pin Dual-in-Line I.C. Holders	20-20

TTL LOGICS

1-11	12-24	1-11	12-24
SN7400	0-20-0-18	SN7403	0-20-0-18
SN7401	0-20-0-18	SN7404	0-20-0-18
SN7402	0-20-0-18	SN7405	0-20-0-18

1-11 12-24

SN7406	0-80-0-75	SN7483	0-87-0-84
SN7407	0-80-0-75 <td>SN7484</td> <td>0-87-0-84</td>	SN7484	0-87-0-84
SN7408	0-20-0-18 <td>SN7485</td> <td>0-87-0-84</td>	SN7485	0-87-0-84
SN7409	0-20-0-18 <td>SN7486</td> <td>0-87-0-84</td>	SN7486	0-87-0-84
SN7410	0-20-0-18 <td>SN7487</td> <td>0-84-0-60</td>	SN7487	0-84-0-60
SN7411	0-23-0-21 <td>SN74100</td> <td>1-65-1-53</td>	SN74100	1-65-1-53
SN7412	0-48-0-46 <td>SN74104</td> <td>1-52-1-40</td>	SN74104	1-52-1-40
SN7413	0-80-0-78 <td>SN74105</td> <td>1-52-1-40</td>	SN74105	1-52-1-40
SN7414	0-84-0-75 <td>SN74107</td> <td>0-52-0-49</td>	SN74107	0-52-0-49
SN7417	0-84-0-78 <td>SN74110</td> <td>0-80-0-75</td>	SN74110	0-80-0-75
SN7420	0-20-0-18 <td>SN74111</td> <td>1-57-1-45</td>	SN74111	1-57-1-45
SN7423	0-51-0-47 <td>SN74118</td> <td>1-30-1-25</td>	SN74118	1-30-1-25
SN7425	0-48-0-45 <td>SN74119</td> <td>1-92-1-80</td>	SN74119	1-92-1-80
SN7427	0-48-0-45 <td>SN74121</td> <td>0-60-0-47</td>	SN74121	0-60-0-47
SN7428	0-80-0-78 <td>SN74122</td> <td>1-44-1-35</td>	SN74122	1-44-1-35
SN7430	0-23-0-15 <td>SN74123</td> <td>0-52-0-70</td>	SN74123	0-52-0-70
SN7432	0-48-0-42 <td>SN74145</td> <td>1-80-1-75</td>	SN74145	1-80-1-75
SN7433	0-80-0-75 <td>SN74150</td> <td>3-52-3-40</td>	SN74150	3-52-3-40
SN7437	0-84-0-60 <td>SN74151</td> <td>1-40-1-35</td>	SN74151	1-40-1-35
SN7438	0-84-0-60 <td>SN74153</td> <td>1-40-1-35</td>	SN74153	1-40-1-35
SN7440	0-23-0-21 <td>SN74154</td> <td>2-20-2-10</td>	SN74154	2-20-2-10
SN7441	0-87-0-83 <td>SN74155</td> <td>1-65-1-60</td>	SN74155	1-65-1-60
SN7442	0-85-0-81 <td>SN74156</td> <td>1-65-1-60</td>	SN74156	1-65-1-60
SN7443	0-86-0-70 <td>SN74157</td> <td>1-92-1-82</td>	SN74157	1-92-1-82
SN7444	0-86-0-70 <td>SN74160</td> <td>1-80-1-75</td>	SN74160	1-80-1-75
SN7445	0-20-0-18 <td>SN74161</td> <td>2-60-2-55</td>	SN74161	2-60-2-55
SN7446	1-00-0-95 <td>SN74162</td> <td>4-28-4-10</td>	SN74162	4-28-4-10
SN7447	1-00-0-95 <td>SN74163</td> <td>4-28-4-10</td>	SN74163	4-28-4-10
SN7448	0-80-0-78 <td>SN74164</td> <td>2-20-2-10</td>	SN74164	2-20-2-10
SN7449	1-00-0-95 <td>SN74165</td> <td>2-28-2-15</td>	SN74165	2-28-2-15
SN7450	0-20-0-18 <td>SN74166</td> <td>4-48-4-20</td>	SN74166	4-48-4-20
SN7451	0-20-0-18 <td>SN74167</td> <td>6-40-6-10</td>	SN74167	6-40-6-10
SN7453	0-20-0-18 <td>SN74170</td> <td>4-38-4-10</td>	SN74170	4-38-4-10
SN7454	0-20-0-18 <td>SN74174</td> <td>2-40-2-30</td>	SN74174	2-40-2-30
SN7455	0-20-0-18 <td>SN74175</td> <td>1-65-1-60</td>	SN74175	1-65-1-60
SN7470	0-40-0-38 <td>SN74176</td> <td>2-84-2-65</td>	SN74176	2-84-2-65
SN7472	0-32-0-30 <td>SN74177</td> <td>2-64-2-55</td>	SN74177	2-64-2-55
SN7473	0-43-0-41 <td>SN74180</td> <td>2-18-2-08</td>	SN74180	2-18-2-08
SN7474	0-43-0-41 <td>SN74181</td> <td>9-38-9-00</td>	SN74181	9-38-9-00
SN7475	0-43-0-41 <td>SN74182</td> <td>2-03-1-95</td>	SN74182	2-03-1-95
SN7476	0-43-0-41 <td>SN74184</td> <td>4-80-4-60</td>	SN74184	4-80-4-60
SN7477	0-43-0-41 <td>SN74185</td> <td>4-80-4-60</td>	SN74185	4-80-4-60
SN7481	1-40-1-38 <td>SN74190</td> <td>1-80-1-70</td>	SN74190	1-80-1-70
SN7482	0-87-0-82 <td>SN74191</td> <td>1-80-1-70</td>	SN74191	1-80-1-70
SN7483	0-87-0-82 <td>SN74192</td> <td>1-75-1-65</td>	SN74192	1-75-1-65
SN7484	2-00-1-85 <td>SN74193</td> <td>1-75-1-65</td>	SN74193	1-75-1-65
SN7485	3-62-3-40 <td>SN74194</td> <td>2-67-2-55</td>	SN74194	2-67-2-55
SN7486	0-35-0-30 <td>SN74195</td> <td>2-28-2-25</td>	SN74195	2-28-2-25
SN7490	0-87-0-84 <td>SN74196</td> <td>2-64-2-55</td>	SN74196	2-64-2-55
SN7491A	1-21-1-10 <td>SN74198</td> <td>5-95-5-85</td>	SN74198	5-95-5-85
SN7492	0-87-0-84 <td>SN74199</td> <td>5-95-5-85</td>	SN74199	5-95-5-85

SGS EA 1000

3 watt Audio Amplifier Module £2-10
Data Sheets 10p each

RCA

Type	1-24 25-99	Type	1-24 25-99
CA3000	1-80-1-60	CA3033A	4-28-4-06
CA3000V1	1-80-1-60	CA3033	3-25-3-10
CA3001	2-69-2-40	CA3035V1	1-23-1-10
CA3001V1	2-69-2-40	CA3036	0-78-0-65
CA3002	1-80-1-60	CA3037	1-65-1-47
CA3002V1	1-80-1-60	CA3037A	2-53-2-25
CA3004	1-80-1-60	CA3038	2-53-2-25
CA3005	1-17-1-05	CA3038A	1-65-1-47
CA3006	2-80-2-50	CA3039	0-84-0-75
CA3007	2-63-2-34	CA3040	0-42-0-14
CA3008	1-80-1-60	CA3041	1-09-0-97
CA3008A	2-96-2-64	CA3042	1-10-0-97
CA3010	1-37-1-23	CA3043	1-37-1-23
CA3010A	2-53-2-25	CA3044	1-20-1-07
CA3011	0-74-0-65	CA3044A	1-20-1-07
CA3011PRE		CA3045	1-23-1-09
CA3012	0-74-0-65	CA3046	0-69-0-60
CA3012V1	0-89-0-79	CA3047	1-37-1-23
CA3013	1-05-0-94	CA3047A	2-53-2-25
CA3014	1-24-1-10	CA3048	2-04-1-81
CA3014V1	1-24-1-10	CA3049	1-30-1-17
CA3015	2-09-1-86	CA3051	1-34-1-20
CA3015A	3-40-3-03	CA3052	1-65-1-47
CA3016	2-46-2-19	CA3053	0-46-0-41
CA3016A	3-78-3-33	CA3054	1-09-0-97
CA3018	0-84-0-75	CA3055	1-69-1-51
CA3018A	1-10-0-99	CA3056	1-30-1-17
CA3019	0-84-0-75	CA3056A	3-19-2-85
CA3020	1-26-1-13	CA3059	1-65-1-46
CA3020A	1-60-1-43	CA3060	4-91-4-37
CA3021	1-56-1-39	CA3062	2-55-2-27
CA3021V1	1-56-1-39	CA3064	1-30-1-07
CA3022	1-30-1-10	CA3065	1-30-1-07
CA3023	1-28-1-13	CA3066	2-1-1-88
CA3026	1-00-0-90	CA3067	2-18-1-94
CA3026PRE		CA3068	2-43-2-16
	1-00-0-90	CA3070	1-70-1-51
CA3028A	0-74-0-65	CA3071	1-62-1-44
CA3028B	1-05-0-94	CA3072	1-62-1-44
CA3029	0-87-0-77	CA3073	1-62-1-44
CA3029A	1-05-1-47	CA3076	1-30-1-10
CA3030	1-37-1-23	CA3078	3-19-2-85
CA3030A	2-53-2-25	CA3080	0-79-0-70
CA3033	2-53-2-25	CA3090Q	3-46-3-06

LARGEST STOCKS WIDEST RANGE SEMICONDUCTORS & COMPONENTS BRAND NEW GUARANTEED

TRANSISTORS

2G301	20p	2N3405	45p	40311	35p	BC172	15p	BSW70	27p	NKT238	25p
2G302	20p	2N3414	22p	40312	47p	BC175	22p	BSX19	17p	NKT240	27p
2G303	20p	2N3415	22p	40314	47p	BC182	10p	BSX20	17p	NKT241	27p
2G306	20p	2N3416	27p	40320	47p	BC183	9p	BSX21	37p	NKT242	27p
2G308	30p	2N3417	37p	40323	38p	BC184	11p	BSX22	45p	NKT243	27p
2G309	30p	2N3570	11-25	40324	47p	BC21L	13p	BSX23	47p	NKT244	27p
2G371	15p	2N3572	27p	40328	37p	BCY30	27p	BSX28	47p	NKT245	27p
2G374	20p	2N3605	27p	40329	30p	BCY31	30p	BSX28	47p	NKT261	20p
2G381	22p	2N3606	27p	40344	27p	BCY32	50p	BSX61	62p	NKT262	30p
2N404	22p	2N3607	22p	40347	57p	BCY33	25p	BSX76	62p	NKT264	30p
2N696	22p	2N3607	22p	40347	57p	BCY34	30p	BSX77	27p	NKT271	20p
2N697	20p	2N3703	11p	40348	52p	BCY38	40p	BSX78	27p	NKT272	20p
2N698	20p	2N3704	11p	40360	48p	BCY39	60p	BSX78	27p	NKT274	20p
2N706	18p	2N3705	10p	40361	47p	BCY40	50p	BSX78	27p	NKT275	20p
2N706A	18p	2N3706	9p	40370	57p	BCY42	15p	BSY10	27p	NKT281	27p
2N708	18p	2N3707	11p	40406	57p	BCY43	15p	BSY11	27p	NKT401	87p
2N709	68p	2N3708	7p	40407	40p	BCY64	32p	BSY24	15p	NKT402	90p
2N718	20p	2N3709	9p	40408	52p	BCY68	22p	BSY26	17p	NKT403	75p
2N726	80p	2N3710	10p	40408	52p	BCY69	22p	BSY26	17p	NKT404	82p
2N727	80p	2N3711	12p	40410	68p	BCY69	22p	BSY26	17p	NKT405	82p
2N914	17p	2N3715	11-23	40467A	57p	BCY70	20p	BSY28	17p	NKT406	82p
2N916	17p	2N3716	11-30	40468A	57p	BCY71	25p	BSY29	17p	NKT451	62p
2N918	18p	2N3719	22-06	40600	57p	BCY72	17p	BSY32	25p	NKT452	62p
2N929	22p	2N3791	35p	40774	65p	BCZ10	27p	BSY36	25p	NKT453	47p
2N930	87p	2N3857	37p	AC107	30p	BDY1	42p	BSY37	25p	NKT603F	32p
2N1090	22p	2N3854	27p	AC126	25p	BDY11	42p	BSY38	22p	NKT713F	30p
2N1091	22p	2N3864A	27p	AC127	25p	BDY12	65p	BSY39	22p	NKT714F	30p
2N1131	25p	2N3855	27p	AC128	25p	BDY13	75p	BSY40	22p	NKT715F	30p
2N1132	25p	2N3856	30p	AC128	25p	BDY14	60p	BSY41	22p	NKT716F	30p
2N1302	17p	2N3856	30p	AC176	25p	BDY15	65p	BSY42	22p	NKT717F	30p
2N1303	17p	2N3857	35p	AC187	65p	BDY16	65p	BSY43	22p	NKT718F	30p
2N1304	22p	2N3858	27p	AC188	37p	BDY17	65p	BSY44	40p	NKT719	30p
2N1305	22p	2N3858A	30p	ACY17	27p	BDY18	65p	BSY45	40p	NKT10439	37p
2N1306	25p	2N3859	27p	ACY18	27p	BDY19	65p	BSY46	40p	NKT10519	37p
2N1307	25p	2N3860A	32p	ACY19	25p	BDY20	65p	BSY47	40p	NKT20329	47p
2N1308	30p	2N3860	30p	ACY20	25p	BDY21	65p	BSY48	40p	NKT20339	47p
2N1309	30p	2N3861	30p	ACY21	25p	BDY22	65p	BSY49	40p	NKT80111	77p
2N1607	17p	2N3862	11-60	ACY22	25p	BDY23	65p	BSY50	40p	BSY95A	12p
2N1613	25p	2N3877	40p	ACY28	20p	BDY24	65p	BSY51	40p	C111	22p
2N1631	35p	2N3900	37p	ACY40	20p	BDY61	21-25	BSY52	40p	C424	22p
2N1632	30p	2N3900A	40p	ACY41	20p	BDY62	21	BSY53	37p	C425	55p
2N1637	30p	2N3901	97p	AD144	40p	BF115	25p	BSY54	40p	C426	40p
2N1638	27p	2N3903	35p	AD140	52p	BF117	47p	BSY55	40p	C428	37p
2N1671B	41p	2N3904	35p	AD149	67p	BF163	37p	BSY56	40p	C444	30p
2N1711	25p	2N3905	37p	AD149	67p	BF167	18p	BSY57	40p	D13T	62p
2N1889	38p	2N3906	37p	AD150	67p	BF173	19p	BSY58	40p	D16P1	37p
2N1893	37p	2N4058	17p	AD161	37p	BF177	30p	BSY59	40p	D16P2	37p
2N2147	88p	2N4059	10p	AD162	37p	BF178	30p	BSY60	40p	D16P3	37p
2N2148	57p	2N4060	12p	AF106	42p	BF179	30p	BSY61	40p	D16P4	37p
2N2160	57p	2N4061	12p	AF114	25p	BF180	30p	BSY62	40p	D46N1	50p
2N2193	42p	2N4062	12p	AF116	25p	BF181	32p	BSY63	40p	GET102	30p
2N2194A	42p	2N4247	17p	AF116	25p	BF182	32p	BSY64	40p	GET113	20p
2N2195A	42p	2N4285	17p	AF117	25p	BF183	42p	BSY65	40p	GET114	20p
2N2217	27p	2N4286	17p	AF118	63p	BF194	17p	BSY66	40p	GET118	20p
2N2218	23p	2N4287	17p	AF119	20p	BF195	15p	BSY67	40p	GET120	20p
2N2219	23p	2N4288	17p	AF124	22p	BF196	42p	BSY68	40p	GET121	20p
2N2220	23p	2N4289	17p	AF125	20p	BF197	42p	BSY69	40p	GET122	20p
2N2221	23p	2N4290	17p	AF126	20p	BF198	42p	BSY70	40p	GET123	20p
2N2222	23p	2N4291	17p	AF127	17p	BF200	52p	BSY71	40p	GET124	20p
2N2287	11-07A	2N4292	18p	AF127	17p	BF224	14p	BSY72	40p	GET125	20p
2N2297	20p	2N4303	47p	AF139	37p	BF225	19p	BSY73	40p	GET126	20p
2N2388	17p	2N6027	62p	AF179	78p	BF237	23p	BSY74	40p	GET127	20p
2N2389	17p	2N6028	67p	AF180	62p	BF238	23p	BSY75	40p	GET128	20p
2N2389A	17p	2N6029	67p	AF181	42p	BF244	23p	BSY76	40p	GET129	20p
2N2401	42p	2N5030	42p	AF181	42p	BF258	27p	BSY77	40p	GET129	20p
2N2483	37p	2N5172	12p	AF239	42p	BF259	27p	BSY78	40p	GET129	20p
2N2484	38p	2N5174	62p	AF279	47p	BF260	25p	BSY79	40p	GET129	20p
2N2539	22p	2N5175	62p	AF280	62p	BF261	47p	BSY80	40p	GET129	20p
2N2540	22p	2N5176	62p	AF281	62p	BF262	47p	BSY81	40p	GET129	20p
2N2541	22p	2N5177	62p	AF282	62p	BF263	47p	BSY82	40p	GET129	20p
2N2542	22p	2N5178	62p	AF283	62p	BF264	47p	BSY83	40p	GET129	20p
2N2543	22p	2N5179	62p	AF284	62p	BF265	47p	BSY84	40p	GET129	20p
2N2544	22p	2N5180	62p	AF285	62p	BF266	47p	BSY85	40p	GET129	20p
2N2545	22p	2N5181	62p	AF286	62p	BF267	47p	BSY86	40p	GET129	20p
2N2546	22p	2N5182	62p	AF287	62p	BF268	47p	BSY87	40p	GET129	20p
2N2547	22p	2N5183	62p	AF288	62p	BF269	47p	BSY88	40p	GET129	20p
2N2548	22p	2N5184	62p	AF289	62p	BF270	47p	BSY89	40p	GET129	20p
2N2549	22p	2N5185	62p	AF290	62p	BF271	47p	BSY90	40p	GET129	20p
2N2550	22p	2N5186	62p	AF291	62p	BF272	47p	BSY91	40p	GET129	20p
2N2551	22p	2N5187	62p	AF292	62p	BF273	47p	BSY92	40p	GET129	20p
2N2552	22p	2N5188	62p	AF293	62p	BF274	47p	BSY93	40p	GET129	20p
2N2553	22p	2N5189	62p	AF294	62p	BF275	47p	BSY94	40p	GET129	20p
2N2554	22p	2N5190	62p	AF295	62p	BF276	47p	BSY95	40p	GET129	20p
2N2555	22p	2N5191	62p	AF296	62p	BF277	47p	BSY96	40p	GET129	20p
2N2556	22p	2N5192	62p	AF297	62p	BF278	47p	BSY97	40p	GET129	20p
2N2557	22p	2N5193	62p	AF298	62p	BF279	47p	BSY98	40p	GET129	20p
2N2558	22p	2N5194	62p	AF299	62p	BF280	47p	BSY99	40p	GET129	20p
2N2559	22p	2N5195	62p	AF300	62p	BF281	47p	BSY00	40p	GET129	20p
2N2560	22p	2N5196	62p	AF301	62p	BF282	47p	BSY01	40p	GET129	20p
2N2561	22p	2N5197	62p	AF302	62p	BF283	47p	BSY02	40p	GET129	20p
2N2562	22p	2N5198	62p	AF303	62p	BF284	47p	BSY03	40p	GET129	20p
2N2563	22p	2N5199	62p	AF304	62p	BF285	47p	BSY04	40p	GET129	20p
2N2564	22p	2N5200	62p	AF305	62p	BF286	47p	BSY05	40p	GET129	20p
2N2565	22p	2N5201	62p	AF306	62p	BF287	47p	BSY06	40p	GET129	20p
2N2566	22p	2N5202	62p	AF307	62p	BF288	47p	BSY07	40p	GET129	20p
2N2567	22p	2N5203	62p	AF308	62p	BF289	47p	BSY08	40p	GET129	20p
2N2568	22p	2N5204	62p	AF309	62p	BF290	47p	BSY09	40p	GET129	20p
2N2569	22p	2N5205	62p	AF310	62p	BF291	47p	BSY10	40p	GET129	20p
2N2570	22p	2N5206	62p	AF311	62p	BF292	47p	BSY11	40p	GET129	20p
2N2571	22p	2N5207	62p	AF312	62p	BF293	47p	BSY12	40p	GET129	20p
2N2572	22p	2N5208	62p	AF313	62p	BF294	47p	BSY13	40p	GET129	20p
2N2573	22p	2N5209	62p	AF314	62p	BF295	47p	BSY14	40p	GET129	20p
2N2574	22p	2N5210	62p	AF315	62p	BF296	47p	BSY15	40p	GET129	20p
2N2575	22p	2N5211	62p	AF316	62p	BF297	47p	BSY16	40p	GET129	20p
2N2576	22p	2N5212	62p	AF317	62p	BF298	47p	BSY17	40p	GET129	20p
2N2577	22p	2N5213	62p	AF318	62p	BF299	47p	BSY18	40p	GET129	20p
2N2578	22p	2N5214	62p	AF319	62p	BF300	47p	BSY19	40p	GET129	20p
2N2579											

Practical Electronics Classified Advertisements

RATES: 8p per word (minimum 12 words). Box No. 10p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW (S.A.E. for details) TO: 'BOFFIN PROJECTS' DEPT. KE2010 4 CUNLIFFE ROAD STONELEIGH, EWELL, SURREY

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

CHEAP FAST LOGIC EX-ICT. 2, 4, 6 DTL gates per board, suit 100ns clock (1MHz rate) Circuits, write-ups 50p. Free with order. 10 Boards £1-50. CHAPLIN, 14 Warminster Road, London, S.E.25.

SOUND/LIGHT—POWER DIMMERS SPECIAL LIGHTING EFFECTS

Choose from our range of versatile units specially designed for DISCOS, CLUBS, DANCE HALLS, etc. Prices range from £6-50 to £22 per unit. Send for free catalogue to:

D & D ELECTRONICS (P.E.)
20 Lodge Road, Wallington, Surrey

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3-30** or in kit form **£2-90** post paid

SALOP ELECTRONICS Callers welcome
23 Wyle Cop Shrewsbury, Shropshire S.A.E. for lists

CONSTRUCTION AIDS. Fascia panels, dials, nameplates in etched aluminium to individual specification. Sheet aluminium, printed circuits—drafting tapes, negatives supplied, boards manufactured, singles or small runs. Copper clad laminate supplied. Hardware for constructors. S.A.E. details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwick.

RECORD T.V. SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included, £1 post free. CROWBOROUGH ELECTRONICS (P.E.), Eridge Road, Crowborough, Sussex.

MISCELLANEOUS

R.E.

TREMOLO

TREBLE BOOSTER

FUZZ

Build these three simple and extremely effective P.E. sound effects units easily on one Type 3A or each one on Type 1A or 1B

Nippiboard

ON TYPES 1A or 1B Fibreglass Wiring connections also provided (State which)

NIP ELECTRONICS P.O. BOX 11 ST. ALBANS

also P.E. GENERAL PURPOSE AMPLIFIER on Type 3A or 3B See our advert in classified pages

SPECIAL SL403D i.e. amp. OFFER with circuits £1-20 TWO for £2-25

PROFESSIONAL CONTROL PANELS with FASCIA KIT

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN.

TRIAL KIT £1-28 Carr. Paid
No. 1 KIT £1-88 Carr. Paid
No. 2 KIT £2-39 Carr. Paid

M.P.E. Ltd. (P.E.), BRIDGE ST., CLAY CROSS DERBYS.

BINOCULAR MAGNIFIER



FOR PRECISION CLOSE-UP WORK—LEAVES BOTH HANDS FREE

See close up work with less eye strain and fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glassworks.

Can be worn over normal glasses. An essential aid in electronics, modelling, industry, Home and Workshop. Stamp collecting, Jewellers, Watchmaking and any fine work. 2½x magnification. £4-95 + 35p P. & P. Send £5-30. 3x model 50p extra. State model. TWIN-BEAM SPEC-LAMP—Worn just like a pair of spectacles. Two powerful spot lamps illuminate working area. Can be worn with Binocular Magnifier. Batt. operated. Only £1-90 + 10p P. & P. Send £2.

JOHN DUDLEY & CO. LTD., Dept. PE.3
301 Cricklewood Lane, Child's Hill, London, N.W.2
Tel. 01-458 5917. Callers welcome.

BUILD IT in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

PROFESSIONAL BUILT 2 manual and pedal organ console, 61 note manuals with thumb pistons under each, and shaped 30 note pedal board. R. H. MEREDITH, 104 Bournbrook Road, Birmingham, B29 7BU.

MAYFAIR ORGAN. 49 note, 16", 8", 5½", 4", 11 tones, vibrato, reverb, £55 o.n.o. LYGO, 352 Dallow Road, Luton, Beds.

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to—METER REPAIRS, 39 Chesholm Road, London, N16 0DS.

P.E. GEMINI. Etched aluminium fascia panels as detailed in latest publication. Printed circuit boards and other items. S.A.E. details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwick.

CIRCUIT BOARD ETCHING KITS, full instructions, £1-25, c.w.o. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

... DON'T LOOK

unless you really want to get the benefit from this collection of SUPER electronic projects. Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN. Find out more that interests YOU!

GET YOUR CATALOGUE — SEND JUST 15p NOW!

TO: BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

ELECTRONIC MUSIC

Build your own units or even a complete sound machine from our circuit assemblies. These include I-C Ring Modulator, Phasing amps, White Sound effects, auto Waa-Waa, an amazing V-C oscillator, and many others. Send 10p for catalogue; mail order only.

TAYLOR ELECTRONIC MUSIC DEVICES
Greyfriars House, Chester

SWITCHES UNUSUAL

PRESSURE MAT—flexible, hard-wearing plastic mat containing 180 contacts. Contacts close when pressed, open when released. Rating 50v, 500mA. Size 30in x 24in **£2 each**

MINI MAT—size 24in x 7in. **£1-50** (Tailor made. Price on request). Suitable for burglar alarm, counter, foot switch, games. "Uses limited by imagination."

PROXIMITY SWITCH—in moulded plastic case. Rating 250v, 600mA. **£1-10**

SWITCH PROBLEM? We have multi-range, key operated, infra-red, solid state, etc., etc.

POSTAGE 15p PER ITEM. C.W.O.

ELECTRONIC SWITCHING DEVICES
P.O. Box 7, Aspley, P.D.O. Nottingham

For further details send s.a.e.
Guaranteed satisfaction or money back

DAILY UFO flight pattern, 38p. UFO wave pattern and prediction, 45p. TV notes on UFO detection, 2 optical circuits, 50p. UFO map (S. England), 38p. R. & E. PUBLICATIONS, Highlands, Needham Market, Suffolk.

SERVICE SHEETS

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex. Telephone, Bexhill 7097.

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

RADIO, TELEVISION AND TAPE RECORDERS. 50 mixed odd sheets 50p. Also large stock of obsolete and current valves. JOHN GILBERT TELEVISION, 1b Shepherds Bush Road, London, W.6 (01-743 8441). S.A.E. enquiries.

TELEVISION TRAINING (MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing September 11th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. B/5, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**



AMSE (Elec), City & Guilds, RTEB Certs Radio Amateurs Cert. Study at home course. In all branches of Electrical Engineering, etc. Details and illustrated book—FREE—BIET (Dept. H.5), Aldermaston Court, Reading RG7 4PF. *Accredited by CACC.*

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Building, etc. FREE book from: BIET (Dept. H.4), Aldermaston Court, Reading, RG7 4PF. *Accredited by CACC.*

GET INTO Electronics—opportunities for trained men. Learn at home. Postal courses in RTEB, City & Guilds, Radio, TV, Telecoms., etc. FREE informative guide: CHAMBERS COLLEGE (Dept. R103), Aldermaston Court, Reading, RG7 4PF.

OPTICS. "How to use Lenses and Mirrors". 112p. 100 ills. Hardback. Best book on the market for the newcomer to optics. £1 each on 14 days, approval against cash. New and ex-Gov. optical equipment of all types. 48 page illustrated catalogue free for 3p stamp. H. W. ENGLISH, 469 Rayleigh Road, Hutton, Brentwood, Essex. Dept. P.E.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

YUKAN SELF-SPRAY 50 PROFESSIONAL THE YUKAN AEROSOL WAY—

Get these air drying GREY HAMMER OR BLACK WRINKLE NOW! OR (CRACKLE) finishes

Yukan Aerosol spray contains 45g. Fine quality durable easy maintain spray. No stove heating required. Hammer available in grey and black. 90c can and Modern Toilet Black Wrinkle (Crackle) producing a 3D textured finish. 50c can and 100c per litre. Both finish well, easy care all day. Also durable, neat and water resistant Black Matt finish. 100g per litre. (See only) 75c per litre.

Other Yukan Air Drying Aerosols: 45g in 50c can and 100c per litre. 100g in 1.00 can and 2.00 per litre. 200g in 2.00 can and 4.00 per litre. 500g in 5.00 can and 10.00 per litre. 1kg in 10.00 can and 20.00 per litre. 2kg in 20.00 can and 40.00 per litre. 5kg in 50.00 can and 100.00 per litre. 10kg in 100.00 can and 200.00 per litre. 20kg in 200.00 can and 400.00 per litre. 50kg in 500.00 can and 1000.00 per litre. 100kg in 1000.00 can and 2000.00 per litre. 200kg in 2000.00 can and 4000.00 per litre. 500kg in 5000.00 can and 10000.00 per litre. 1000kg in 10000.00 can and 20000.00 per litre.

SPECIAL OFFER: One can plus optional transferable strap on luggage. (Value 25p) for 99c only. Choice of 13 matt spray pen in colour and primer, motor car quality. Also available.

Please fill in coupon or request P.O. for full information to: DEPT: P.E. YUKAN, 307A EDGWARE ROAD, LONDON W2 1BN. We supply to: Home, Government Departments, Municipal Authorities, Institutes and leading Industrial Organisations. We can supply you too. Now British Own Air Dry. Standard. Choose Transferable strap.

PERFECT SPEAKERS EX TV
P.M. 3 OHM (Minimum order 2)
8" - 2 1/2" 15p each, add 10p per speaker P. & Pkg.
100 SPEAKERS for £15 delivered
200 SPEAKERS for £25 delivered

UHF TUNERS EX TV (Complete with Valves)
£2-50 each + 50p p. & pkg.
or 10 for £23 post free

TRADE DISPOSALS (Dept. PE)
Thornbury Roundabout, Leeds Road, Bradford
Telephone 665670

MORSE MADE EASY!!
FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed. Complete Course £4-50 (Overseas £1-00 extra) details only, 4p stamp. 01-060 2598. **GSHC (Box 19), 45 GREEN LANE, PURLEY, SURREY**

Send now for our:
**Illustrated Component/
Equipment Catalogue
Slide and Rotary Lamp
Dimmer Catalogue**
10p each—post Free
YOUNG ELECTRONICS
54 Lawford Road, London NW5 2LN
01-267 0201

BACK ISSUES. First Thirty P.E. Any Offers? Bradley 01-643 4288.

POTTED BRIDGE RECTIFIERS small size. 400 PIV ZA 65p each, discount on quantity. Ring Yateley 83048.

PRACTICAL ELECTRONICS. Vols. 1-5. Mint. 01-504 3256 after 7.

LADDERS

LADDERS. 20ft. £7-80. Callers Welcome. Carr. 80p. Leaflet. (Dept. PEE), HOME SALES, Baldwin Road, Stourport, Worcs. Phone 02-993 2574/5222. Ansaphone installed 5222. Open Sunday 8-12 noon.

SITUATIONS VACANT

MEN!
£50 p.w.
can be yours

Now for the first time anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a computer operator in only 4 weeks—and can earn £2,500+ p.a. **JOBS GALORE!** 144,000 new computer personnel will be needed over the next 5 years alone! Write without obligation, for FREE details or telephone TODAY!
London Computer Operators Training Centre
E80, Oxford House, 9/15 Oxford Street, London, W.1
Telephone 01-734 2874
127 The Piazza, Dept. E80 Piccadilly Plaza, Manchester 1
Telephone 061-236 2935

ICS TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

Established 1891

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc. Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
 - RADIO AMATEURS' EXAMINATION.
 - GENERAL RADIOCOMMUNICATIONS CERTIFICATE.
 - C. & G. RADIO SERVICING THEORY.
- Now available, Colour T.V. Servicing.

Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES
Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. **All under expert guidance.**

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ABCC ACCREDITED BY THE CACC

**INTERNATIONAL
CORRESPONDENCE
SCHOOLS**

**A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!**

International Correspondence Schools
(Dept. JA25), Intertext House, Stewarts Road,
London SW8 4UJ

NAME
Block Capitals Please

ADDRESS

.....

.....

AGE OCCUPATION

PICTURE BOOK WAY OF LEARNING

BASIC ELECTRICITY 5 Vols. £4.50 post paid
 BASIC ELECTRONICS 6 Vols. £5.40 post paid

SELRAY BOOK COMPANY, 60 Hayes Hill, Bromley BR2 7HP

OVER 1,000,000 PARTS ALREADY SOLD

Available on our 100% Guarantee Money back if not completely satisfied

Illustrated Prospectus Free on Request

BASIC PRINCIPLES OF ELECTRONICS

by Jenkins and Jarvis—Pergamon
 Vol. I: Thermionics, including theory and practicals to beyond A and S level;
 Vol II: Semiconductors. Many modern practicals; questions from recent examinations. Hard or limp. All booksellers.

This advertisement inserted by the authors.

WANTED

CASH PAID for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

HIGHEST POSSIBLE CASH prices for Akai, B. & O., Brenell, Ferrograph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

TOP PRICES PAID

for new valves and components
 Popular T.V. and Radio types
KENSINGTON SUPPLIES
 (B) 367 Kensington Street
 Bradford 8, Yorks.

GYRO'S small pair of motor driven gyros wanted. Phone Kettering 3060.

RECEIVERS AND COMPONENTS

New Branded Guaranteed Top Quality MICROCIRCUITS & TRANSISTORS
 All Complete with Data

2N2926, Red and Orange 6p, Green 8p, BC109C 9p, 2N3055 48p, 741 36p, 723 75p, BFY50/51/52 10p, ME0412 19p, ME4101 10p, MP8111 33p. Soldercon I.C. Pin Sockets 0.7p per pin.

JEF ELECTRONICS (P.E.5)

York House, 12 York Drive, Grappenhall Warrington WA4 2EJ

Mail Order Only. C.W.O. P. & P. 7p per order. Overseas 65p. Money back if not satisfied. Discounts begin at 10 off.

List free on application.

GROUP POWER AMPS

100 watt, 60 watt, Trany Sets suitable for EL34, KT88

60 Mains: Pri. 0-110-200-220-240V. Secy. 1 350V-0-350V at 350MA. Secy. 2 6.3 CT. at 4AM. £11.

60 O/P: Secy. impd. 2.75-7-15 ohms. A-A 4kΩ. £9.

60 Choke: 1H at 350MA. £3.75.

100 Mains: Pri. 0-110-200-220-240V. Secy. 375V at 400MA., Secy. 88V CT. at 100MA. Secy. 6.3 CT. 6 AMP. £12.

100 O/P: Secy. impd. 2.75-7-15 ohms. A-A 2kΩ. £11.

100 Choke: 1H at 500MA. £3.75.

High quality material used throughout manufacture. Fully shrouded. State upright or drop through mounting on mains. Post, packing free of charge.

Trade enquiries ROYAL AUDIO 43 PINNER ROAD SHEFFIELD S11 8UG

WITWORTH TRANSFORMERS

TV Line out-put transformers

Manufacturers of the largest range in the country. All makes supplied. Free catalogue.

Modern

BAIRD, BUSH, GEC, PHILIPS

Replacement types ex-stock.

For "By-return" service, contact London 01-948 3702

Tidman Mail Order Ltd., Dept. PE, 236 Sandycroft Road, Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers also stocked.

Callers welcome.

SOUND SUPPLIES (LOUGHTON) CO. LTD.

for Eagle International and International Rectifier Products.

TOA P.A. Equipment and Mikes.

Capacitors, Resistors, Plugs, Sockets, Cables, Audio Leads, Semiconductors, Valves, Vero Board, etc., for the constructor.

Electronics Dept. Tel. 01-508 2715

18 Smarig Lane, Loughton, Essex
 Hours: 9.30 a.m.-1 p.m. 2-6 p.m. Mon, Tues, Wed. and Fri. 9.30 a.m.-1 p.m., 2-5.30 p.m. Sat. Closed All Day Thurs.

EX COMPUTER PRINTED CIRCUIT PANELS
 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Core, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 20p.

709C OPERATIONAL AMPLIFIER T05
 8 lead I.C. 1 off 50p. 50 off 35p. 100 off 20p.

250 MIXED RESISTORS 62p
 1/2 & 1/4 watt.

150 MIXED HI STABS 62p
 1/2, 1/4 & 1 watt 5% & better.

QUARTZ HALOGEN BULBS
 With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES
 with dial but without bell. 95p each. P. & P. 30p. £1.75 for 2. P. & P. 50p.

BARGAIN RELAY OFFER
 Single pole change over silver contacts 25V to 50V. 2.5kΩ coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
 44 EARLS COURT ROAD
 LONDON, W.8 01-478 8499

BRAND NEW copperclad fibreglass laminate printed circuit board, two 2 x 8in or one 4 x 8in. 19p. Add 10p for double sided. C.W.O. plus P. & P. 10p. H.R. CIRCUITS, 44 Wattyhall Road, Wibsey, Bradford.

SHARPEN YOUR RESPONSES with Vernitron ceramic i.f. resonators. Set of four TF-04 442, 455kHz, with associated capacitors for bandwidth 2, 4, 5.7, 7.5, 10 or 12kHz (state which), £1.85. U.K. post 5p. Mail order only. AMATRONIX LTD., 306 Selsdon Road, South Croydon, Surrey, CR2 0DE.

ELEKON SPECIAL OFFERS

Twin Power Supply Panels (Semi-stabilised). Contains 2 x Texas 1 B10 J10 Silicon Bridge Rectifiers, 100 P.I.V. at 1A; 1 x Mullard OAZ225 Zener Diode, 7.5V at 10W; 1 x I.T.T. Zener Diode, 5-1V at 1W; 5 x Texas IS121 Silicon Diodes 150 P.I.V. at 200mA. Electrolytic Capacitors, 2 x Plessey 1,000µF, 25V; 2 x 50µF, 50V; 2 x Mullard 250µF, 25V; 2 x Mullard 640µF, 25V. Circuit details supplied. Exceptionally good bargain, £1, post 10p.

Bargain Component Parcels. Includes Resistors, Plugs, Sockets, etc. 4lb nett weight, £1, post 30p.

Assorted Potentiometers. Mostly Plessey types, 10 for 50p, post 10p.

Electrolytic Capacitors. At reduced prices. µF/V. 1,000/60-70, 1,500/50, 2,000/25, 2,500/15, 3,000/15, 5,000/15, 10,000/15, 32 x 32/350, 100 x 32/350, 100 x 200/300, 100 x 400/275, 150 x 350/300, 1,000 x 1,000/18, 40 x 40 x 10/350, 32 x 32 x 50/350, 600 x 600 x 600/35. All above one price, 30p each, 10p post; or any 4 £1. 3,000/150, 6,600/50, 8,000/50, 10,000/70, 13,500/38, 33,000/25, 1,000 x 1,000/40, 150 x 50 x 150/350, 100 x 100 x 47/320, 100 x 100 x 200/275, 150 x 200 x 250/300, 200 x 200 x 100/275. All one price 50p, post 10p; any 5 £2.

Special Bargain Electrolytics. 8/350, 32/450, 50/350, 60/450, 80/300, 100/450, 150/300, 250/100, 500/12, 500/60, 600/150, 1,000/10-15. Each pack contains one each of above, £1.50, post 25p.

ELEKON ENTERPRISES

12A TOTTENHAM STREET, LONDON W1P 9PQ
 Telephone 01-580 7391

LIGHT SENSITIVE INTEGRATED CIRCUIT

ARE YOU STILL USING PHOTOTRANSISTORS, DIODES AND OTHER PHOTOCELLS?

—KEEP UP TO DATE

WE ARE OFFERING THE COMPLETE SWITCH—

PHOTODETECTOR +
 AMPLIFIER +
 TRIGGER +
 DRIVER—ALL IN A SINGLE 4mm. DIA. CAN



—WILL DRIVE RELAY OR TRIAC FOR AUTOMATIC LIGHT SWITCHING CONTROL: BURGLAR ALARM BEAM BREAK DETECTOR: AUTOMATIC DOOR CONTROL AND MANY OTHER APPLICATIONS.

PRICE ONLY 65p each + 5p post and packing; with full operating instructions. 10 for £5.75 (post free).

P.O. CHEQUES payable to ELBON and crossed
 LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX

RECEIVERS AND COMPONENTS

PRECISION POLYCARBONATE CAPACITORS

Fresh Stock — Fully tested

Close tolerance capacitors by well-known manufacturer. Good stability and very low leakage. All 63V d.c.

0.47µF:	±5%	80p:	±2%	40p:	±1%	50p
1.0µF:	±5%	40p:	±2%	50p:	±1%	60p
2.2µF:	±5%	50p:	±2%	80p:	±1%	75p
4.7µF:	±5%	70p:	±2%	90p:	±1%	£1.15
10µF:	±5%	£1.10:	±2%	£1.40:	±1%	£1.80
15µF:	±5%	£1.80:	±2%	£2.10:	±1%	£2.70

P.E. SCORPIO IGNITION SYSTEM

Special 1µF 440 V a.c. capacitor for use in place of two existing 0.47µF 1,000V d.c. units (C6 and C7). Does the job of both. Size 2 in × 3/4 in. Price — 45p each. Post and packing 5p on all orders

V. ATTWOOD, P.O. BOX 8, ALRESFORD, HANTS

COMPUTER PANELS 3-BC108, Diodes 15p, post 5p; 4 for 50p, Post 10p. ASSORTED PANELS, 6 for 75p, Post 20p. Send large S.A.E. for list of panels, etc. LA2 POT CORES 20 in all box with 20 1% capacitors £1.70, post 30p. UNIT WITH 4 LA2 POT CORES plus 11 2% capacitors, 60p, post 16p. Singles 20p c.p. New and boxed 30p c.p.

WIRE ENDED NEONS, bank of 20 50p, post 10p. COPPER CLAD PAXOLIN single sided, 8 × 5, 10p, post 5p each. — 13 × 11, 30p, post 10p each.

ORP12 ON PANEL ex equip. 35p c.p. 22 POSITION STEPPING SWITCH, A.C. mains operated with reset 80p post 15p. RESETTABLE 5 FIGURE COUNTER 18/22V. Will work on 12V. £1.75 post 10p. LOUDSPEAKERS 2 1/2 in 25 ohms 50p c.p. UNIT WITH 25 V.D.C. MOTOR, 2 relays, 2 motorised switches, mass of gears, etc. £1.75 c.p.

POLYSTYRENE CAPACITORS 125V, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0.01, 0.012, 15p dozen post 10p. 0.015, 0.018, 0.022, 0.027, 0.033, 24p dozen post 10p.

ASSORTED COMPONENTS. 7lb, £1.30 c.p. ASSORTED COMPUTER PANELS. 2lb, £1.30 c.p. J.W.B. RADIO 75 HAYFIELD ROAD, SALFORD 6, LANCAS. MAIL ORDER ONLY

Mixed component parcels contain Toggle, Wafer, Slide Switches, Plugs, Sockets, Electrolytic Capacitors, Valveholders, Tag Strips, Transistors, Diodes, Potentiometers, Trimmers, plus a good selection of other components. Save yourself £5's on these well-sorted parcels. 6lb nett weight, £1. P. & P. 40p.

Assorted Capacitors (no rubbish), includes Silver Mica, Ceramic and Polystyrene types. 100 for 50p. P. & P. 10p.

Assorted brand new wire-wound Resistors, 1-10 watts. 100 for £1, post free.

P.v.c. connecting wire, 10 different colours, 30 × 1 yard lengths. 30p, post free.

Electrolytic Capacitors, 32µF, 500V, 25p. Also 100µF, 500V (limited quantity), 35p.

Mixed wire-wound Potentiometers, good selection. 10 for 50p. P. & P. 10p.

Mail Order only

XEROZA RADIO

1 EAST STREET

BISHOP'S TAWTON, DEVON

P.E. transistor circuits look better

BUILD THESE ON NIPPIDBOARD

SRBP or FIBREGLASS

1A 15p 1B 18p GENERAL PURPOSE AMPLIFIER 3A or 3B

2A 28p 2B 34p TREMOLO 1A or 1B

3A 36p 3B 43p PHRE BOOSTER 1A or 1B

2AS 28p 34p TROCELL THYRISTOR SWITCH 1A or 1B

4AS 44p 4BS 52p RHYTHMETRON 2A or 2B

6AS 60p 6BS 70p

SEND TO DEPT NEW PLEASE STATE WHICH PROJECT

NIP ELECTRONICS P.O. Box 11, St. Albans, Herts.

CHROMASONIC electronics

SL403D £1.50, SN76013 £1.25, MFC4000 52p, AD161/162 pair 60p. A.M. Coil set with ferrite rod £1 (p. & p. all orders). Carbon Track pots 12p + Switch 24p. Fully illustrated 1972 Catalogue 20p post free. 56 Fortis Green Road, London N10 3HN

Trampus electronics

Brand New. Money Back Guarantee

NUMERICAL INDICATORS

3015F 7 bar 5 volt 8mA bar

0-9DP £1.89. S.A.E. free data.

Socket 35p. 7447 driver, £1.23

NIXIE type 0-9DP 180V, £1.23

LIGHT EMITTING DIODES. Infra-

red 1.3V, £1.49. Visible red 1.6V,

3/4 in dia. panel clip, 67p.

I.C. Photo Detector and amplifier,

lens case, 44p.

1A RECTIFIERS. 50V, 6p; 400,

9p; IN914/916, 7p.

ZENERS. BZY88 400mW, 3 3V

to 30V, 12p

TRANSISTORS

BC107, 8p; BC108, 8p; BC109, 8p; BC177/8, 12p.

2N3055, 49p; 2N3053, 19p; 2N2926, 8p.

ME0404-2, 18p; FET2N3819, 29p; T1843, 33p;

2N3702/3/4/5/6/7, 11p. 2N3708/9/10/11, 9p.

INTEGRATED CIRCUITS

Op Amps 709, 31p and 741, 34p; TAA263, 60p.

TAD100 Receiver, £1.75. 703 R.F. amp., 65p.

3-5 WATT AUDIO AMP. and data, £1.49.


PLASTIC POWER 6W 500mA Darlington Amp.,

67p.

FREE CATA-LIST S.A.E., DATA SHEETS, 6p.

C.W.O. P. & P. U.K. 6p. Discount 10+ 10%.

P.O. BOX 29, BRACKNELL, BERKS.

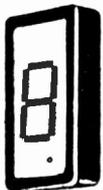

If you have difficulty in
obtaining

PRACTICAL ELECTRONICS

Please place a regular
order with your
newsagent or send 1
year's subscription
(£2.65) to Subscription
Department, Practical
Electronics, Tower House
Southampton Street
London WC2E 9QX

P.E. GEMINI STEREO AMPLIFIER

(Dual purpose, 30W per channel)

All the components to build this high quality amplifier, as featured in "Practical Electronics," Nov. 1970—Feb. 1971, are now available from one source.

ALL PARTS CAN BE PURCHASED SEPARATELY.

Please send foolscap size S.A.E. for free complete lists. Reprint of articles available in booklet form, complete with free price list, 55p post free.

Mail Order Only

ELECTROSPARES

21 BROOKSIDE BAR

CHESTERFIELD, DERBYSHIRE

QUALITY • VALUE • SERVICE

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts, 62p per doz.; £3.75 per 100; £27.50 per 1,000; £250 per 10,000. All carriage paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex BN9 0B3

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25V 1, 2, 5, 10 mfd—34p. 25, 50—4p. 100—5p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p; 0.04, 0.05—24p; 0.068, 0.1—3p. Mullard miniature carbon film resistors third watt E.12 series 1Ω-10MΩ, 8 for 5p. Insured postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

New, At Last

HEATSINKS, a new range, never before available, gives decreased leakage current, longer transistor life and greater circuit reliability, lower costs.

FAN, TOP TOS LB TO66 UP TO3, TO8



Only 10p Only 20p Only 35p

Please include 5p P. & P. on all orders.

AUDIO CABLE, graphite loaded thermo-plastic screen gives flexibility, less noise, designed for all audio applications, ideal for DIN plug use. Price: 1 core, 5p; 2 core, 10p; 3 core, 15p; 4 core, 20p per yd. Please include 10p for 10yd or less, 15p over.

J. W. SALES, 6 Russet Road
Cox Green, Maidenhead

NEW

15 watt Hi-Fi
£3.75 plus 25p
postage
packing
AMPLIFIERS


7 TRANSISTORS - GUARANTEED
PRINTED CIRCUIT - TESTED
DESIGN BUILT - INSTRUCTIONS

A great new 15 watt Hi-Fi amplifier is now available at the low cost of £3.75. Just look at the specification—Power 15 Watts R.M.S. Frequency response 15 cs-19000 cs, ±1dB at all powers. Signal to noise ratio better than -70 dB. Harmonic distortion 0.1%. Input sensitivity 750 mv into 2k. These factors make the H. Electronics Hi-Fi amplifier the best at its price—order now

H. ELECTRONICS.

105, Grange Road, London, S.E. 25

BUILD A PROJECT 'X' SYNTHESISER

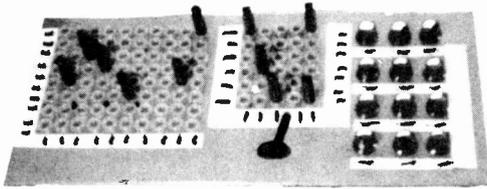

MAN-SIZED ROBUST PATCHBOARD

MAKE A "PATCH" AS IF YOU MEAN IT. "K-L-O-N-K" and it's MADE!

No fiddling with fragile patch pins. No cables. Countless possible combinations giving **FULL RANGE EFFECTS**. Keyboards available for versatile "live" use.

VOLTAGE CONTROL

Voltage-controlled filters, oscillators, amplifiers and . . . *P-H-A-S-E*.

Yes, Dewtron have perfected **voltage-controlled phase** in module form.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group. Send s.a.e. for synthesiser details or send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES

CASH SAVINGS

by buying modules and parts in bulk! All modules are available separately: Ring Modulator RM2, £7. Voltage-controlled Oscillator VC01, £9.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £12.50. White noise type WN1, £6. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £4.50.

MULTIMETER IT12, 20,000 ohm/V, £4.20. 10W TRANSISTOR AMPLIFIER, £3.75. STEREO HEADPHONES, 8 ohm, £1.95. HIGH IMPEDANCE (2,000 ohm), 80p. TELESCOPIC AERIALS, 47in, 45p. RECORDING TAPE: 5in L.P. 900ft, 45p; 5½in L.P. 1,200ft, 60p; 7in L.P. 1,800ft, 80p; C60, 39p; C90, 60p. MICROPHONES: Lapel, 28p; ACOS Mic. 45, 90p; Mic. 60, 92p; Dual Impedance, 600 ohm and 50kΩ, £4.50. 5kΩ Potentiometers with Switch, 16p. Bridge Rectifiers, 40V, 1.5A, 36p. Rotary Switches, 250V, 2A, 9p. PLUGS: Jack Standard, 10p; SCREENED, 13p; 2.5mm and 3.5mm, 6p; SCREENED, 8p. BALANCE AND TUNING METER, 500µA, 38p. 100 MIXED RESISTORS, 45p. MINIATURE INDICATOR LAMPS (5 colours), 11p; 6V or 12V BULBS for above, 4p. CARTRIDGES: COMPATIBLE ACOS GP91-3SC, 90p; STEREO GP93-1, £1.15. MAINS NEONS panel mounting (red, green, clear), 13p. TELEPHONE AMPLIFIER, £2.62. MINIATURE SKELETON PRESETS, 6p. CAPACITORS: 400-200-50-16mF, 300V, 30p. A range of miniature CERAMICS 50V and Miniature ELECTROLYTICS. FIBRE GLASS cut to size, ½p per sq. in.

Special prices for quantity. S.A.E. for list. Add 10p for P. & P. on orders under £5.

M. DZIUBAS

158 Bradshawgate, BOLTON, Lancs

FOR THE AMATEUR AND CRAFTSMAN ALIKE . . .

PRACTICAL WOODWORKING

The invaluable magazine for detailed how-to-do-it features covering every aspect of working with wood.

Place a regular order now . . . they sell out fast! Out every month . . . 25p

BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power	35 watts
Bass Resonance	35 c.p.f.
Flux Density	15,000 gauss
Voice coil impedance	8 or 15 ohms models
Useful response	20-14,000 c.p.s.
Nett weight	15 lbs.


£19

POST FREE

GUITAR MODEL "GROUP 50" 50 watt £19
Latest catalogue 5p with enclosure plans

Baker Reproducers Ltd

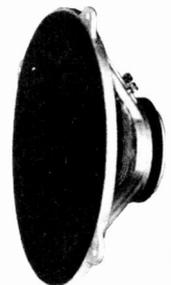Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665



In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn.

If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing

Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication
Sales Management

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT— SO COULD YOU

"My income has almost trebled... my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B4, Aldermaston Court, Reading RG7 4PF.

POST THIS COUPON TODAY

To: B.I.E.T., Dept B4, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name _____
BLOCK CAPITALS PLEASE
Address _____

Age _____

Subject of Interest _____

Accredited by the Council for the Accreditation of Correspondence Colleges.



(Write if you prefer not to cut this page)

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/asia) Ltd.; South Africa - Central News Agency Ltd.; Rhodesia and Zambia - Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.65 (£2.13.0.). Practical Electronics is sold subject to the following conditions, namely: that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

