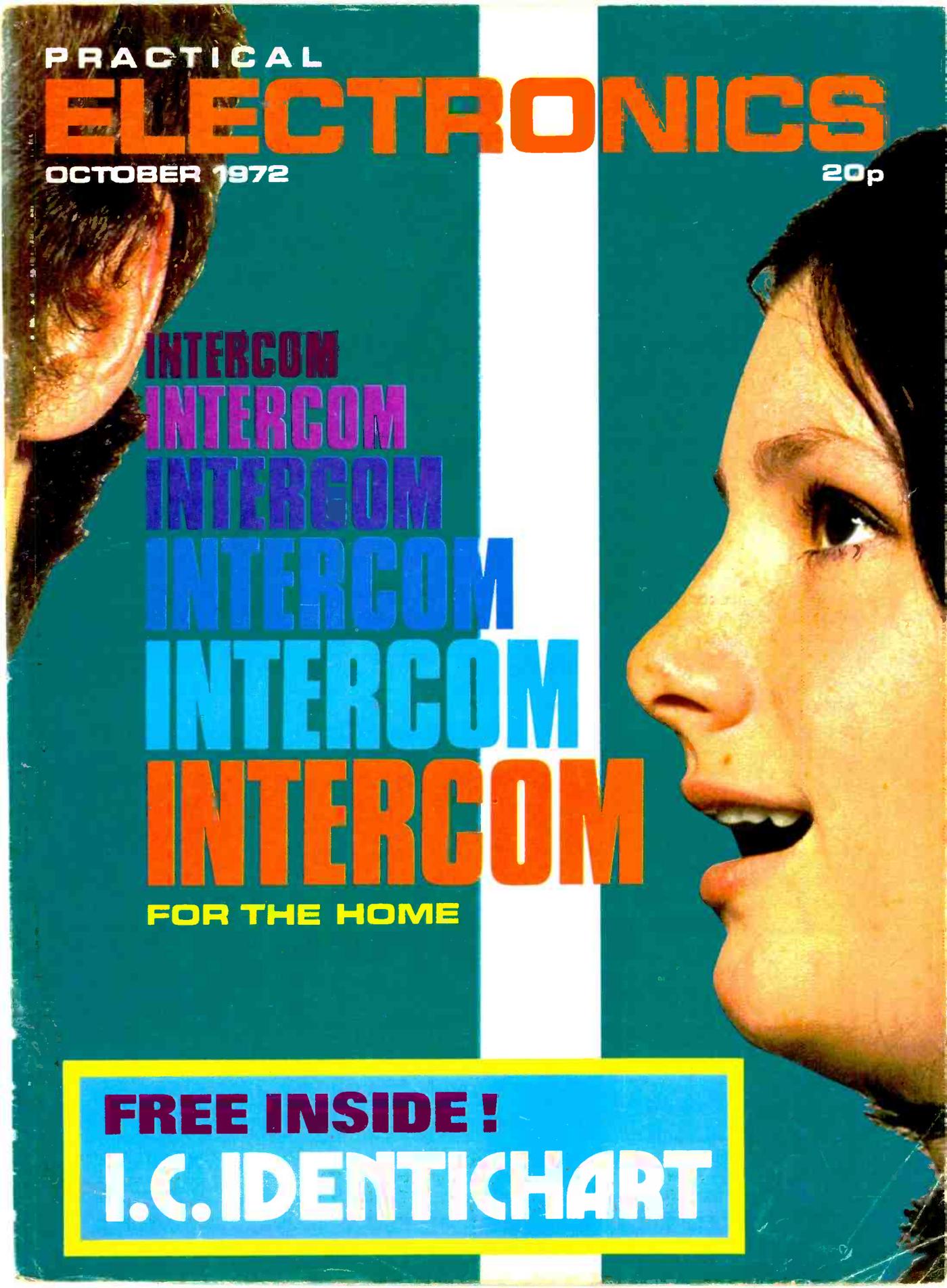


PRACTICAL

# ELECTRONICS

OCTOBER 1972

20p



INTERCOM  
INTERCOM  
INTERCOM  
INTERCOM  
INTERCOM  
INTERCOM

FOR THE HOME

**FREE INSIDE!**

**I.C. IDENTICHART**

# Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

## Use Antex low-leakage soldering irons



220-240 Volts or  
100-120 Volts

### Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".

Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8"

2 other bits available 3/32" and 3/16"

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be removed

PRICE: £1.75 (rec. retail)

Suitable for production work and as a general purpose iron

### Model CCN 220 volts or 240 volts

The 15 watt miniature model CCN. also has negligible leakage.

Test voltage 4000v. A.C.

Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available

1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

## A SELECTION OF OTHER SOLDERING EQUIPMENT.



### MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 1/16" to 3/16". Voltages 240, 220, 110, 50 or 24

PRICE: £1.70 (rec. retail)

### MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.

PRICE: £1.70 (rec. retail)



### MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.

PRICE: £1.83 (rec. retail)

### MODEL SK.1 KIT



contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75

(Rec. retail)

### MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32",

heat sink,

solder and

booklet "How to Solder"



PRICE £2.40

(Rec. retail)

### MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong

plastic wallet with booklet "How to Solder." PRICE £1.95

(Rec. retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from:-

**ANTEX LTD. FREEPOST**

(no stamp required) **Plymouth**

**PL1 1BR Tel: 0752 67377**

- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_



## The other pocket calculators fit neatly into your briefcase.

The Sinclair Executive is the world's smallest and lightest electronic calculator.

How light? Just 2½ oz. Less than the bunch of keys you're probably carrying now.

And how small? It's 5½ inches long, 2½ inches wide, and an incredible ⅜ inch thick – same as a cigarette.

Yet this featherlight wafer of British technology offers more than some desk-top models.

With its brilliant 8-digit display it adds and subtracts, of course. It multiplies and divides – and by a constant figure over and over again, if you want it to (to work out discounts for example, for currency conversions, or for percentages). It works to 2, 4 or 6 decimal places – or it allows the decimal point to float. It rounds off automatically to the nearest decimal place.

### The Secret of the Sinclair Executive

The Executive's 'brain' is an electronic marvel – a 7,000-transistor integrated circuit (the largest ever produced for commercial use).

But the real genius lies in the circuitry linking the brain, the batteries, the keyboard and the display. Circuitry soaks up power, which is why other pocket calculators have to use large batteries – and that, in turn, makes them bulky.

In the Executive, the Sinclair flair for miniaturisation has developed circuitry which absorbs virtually no power. Tiny hearing-aid batteries take up the minimum space, allow an elegantly slim case, and

give a full three-months average life.

Yet small though it is, the Executive is far from frail. Every one is covered by an unbeatable five-year guarantee.

### Smallest... lightest... and quite exceptionally powerful!

The easiest way to test the Executive's full performance is to try it for yourself.

You'll find the Executive at

**HENRY'S  
RADIO LTD.**

354 Edgware Road,  
London, W.2.  
Tel: 01-402 5854

**ELECTRONIC AND  
AUDIO SPECIALISTS  
FOR 30 YEARS.**

**Highly recommended  
calculator by us  
for all trades and  
professions.**

FROM STOCK

**£79**

POST PAID



**10 DAY MONEY  
BACK GUARANTEE**

Also full back-up  
service facilities  
and guarantee.

**HENRY'S RADIO LTD. AUDIO-ELECTRONICS  
SPECIALISTS**

303, 309, 354, 356, 404 and 406 EDGWARE ROAD, LONDON, W.2.  
Open 9 a.m. - 6 p.m. 6 days a week.

THE MIDLAND  
**NATIONAL**  
 AMATEUR  
 RADIO  
 &  
 ELECTRONICS  
 EXHIBITION  
 AT THE  
**GRANBY HALLS**  
**LEICESTER**  
 OCTOBER  
 26th to 28th, 1972

SPONSORED BY THE AMATEUR  
 RADIO RETAILERS' ASSOCIATION

COME AND SEE THE LATEST  
 DEVELOPMENTS IN RADIO  
 COMMUNICATIONS AND  
 ELECTRONICS

WORLD-WIDE CONTACTS FROM  
 THE EXHIBITION  
 LARGE CAR PARKS  
 EASY ACCESS FROM  
 M1 MOTORWAY  
 ADMISSION 20p  
 THIS INCLUDES A CHANCE TO  
 WIN A PIECE OF THE BEST IN  
 RADIO EQUIPMENT

OPENING TIMES:



THURSDAY 26th and FRIDAY 27th |  
 12 noon to 9 pm

SATURDAY 20th — 10 am to 7 pm

OVERSEAS VISITORS FROM PARIS  
 FRANKFURT, AMSTERDAM AND BRUSSELS

PLEASE CONTACT:

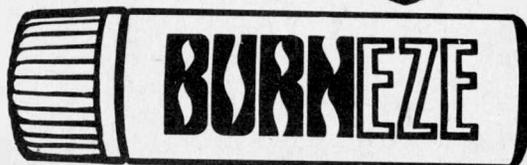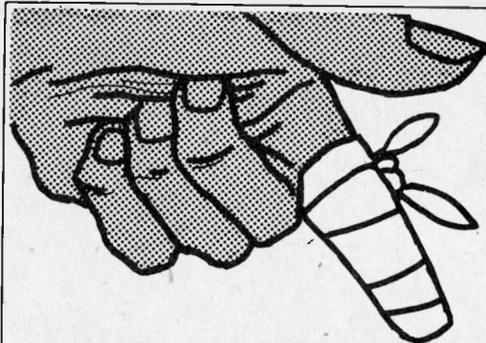MIDAWAY LTD., 40a HILLSIDE, CASTLE  
 DONNINGTON, nr. DERBY, FOR INFORMATION  
 REGARDING INCLUSIVE AIR CHARTER  
 FLIGHTS TO AND FROM THE SHOW



Burns and scalds can rob your fingers of the dexterity essential to your hobby. So keep Burneze close to hand for minor burns. This unique scientific aerosol cools the heat out in just 8 seconds, anaesthetizes pain, reduces swelling. Be well-equipped — buy Burneze, from chemists.



Potter & Clarke Ltd Croydon CR9 3LP



for fast, easy  
 reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

IDEAL FOR HOME  
 CONSTRUCTORS



Size 1 cartons all at 25p each  
 in 40/60, 60/40,  
 or Savbit alloys in 7 gauges.

EASY-TO-USE  
 DISPENSERS



Size 5  
 (Savbit) 18swg,  
 18p (illustrated)

Size 19A  
 (60/40 alloy)  
 18swg. 18p

Size 15  
 (60/40 alloy)  
 22swg. 22p

**BIB WIRE STRIPPER AND CUTTER**



**Model 3A.** Strips insulation from cable or flex without nicking wire. 4 different settings. 4 & 6 BA spanner ends, ground cutting edges Price 32p. Also available, de luxe Model 8. Price 58p.

**NEW!**

From Electrical and Hardware Shops. If unobtainable, write to:  
 Multicore Solders Ltd., Hemel Hempstead, Herts.

introducing

## ARROW ELECTRONICS LTD.

an associate Company of LST ELECTRONIC COMPONENTS LTD.

**'Service the way it ought to be'**

When it comes to retail distribution we're head and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way.

Here at Arrow Electronics fast, reliable service is law!

We offer a rapid, same day turn round on all mail received up to 3 pm on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

Our no fuss, no bother ordering system is a joy to behold. We'll give you all the forms and envelopes you could possibly need. Combine them with our simple Catalogue Coding and hey presto, you can order and order, time and time again without the slightest error or mistake.

You'll always be up to date with us—we're continually adding to our high quality stock range and we're always updating our catalogue.

Get to know us and you'll soon raise your hat to our customer discount—it's tops with a total order value discount of 10% on orders exceeding £4.00.

Now's your chance to get to know us better. Our brand new Catalogue is now awaiting you, hot from the presses.

### NEW PRODUCTS

Products featured in the Arrow Electronics Mail Order Catalogue include the following:

- Extended ranges of Bridge Rectifiers, and Capacitors including Variable Capacitors
- Low cost Integrated Circuit Mounting Pins
- Instrument Knobs.
- Light Emitting Diodes.
- Magneto Resistors.
- Optically Coupled Isolators
- Extended Range of Potentiometers.
- Medium current and High current Rectifiers.
- Temperature controlled Soldering Irons.
- Extended Range of Thyristors.
- Many new types of Passive Components.
- Hardware and Accessories including tools, Chassis.
- Aluminium Boxes.
- An extended range of Opto Electronic Devices.
- A very wide range of new Semiconductors.
- Test Meters.

and many other items of great interest to the home constructor.

Arrow Electronics Limited  
Dept PE2  
7 Coptfold Road  
Brentwood Essex  
Tel: Brentwood 219435

### NEW PRODUCT

The unique test instrument illustrated gives an instantly visible display of the Logic State of DIL Integrated circuits. The device automatically selects its power supply from the terminals of the IC's being inspected. Each Logic Checker is supplied complete with a set of clip-on Logic plates. For fuller details see the new Arrow catalogue.



### NEW PRODUCT

Arrow are the first to offer the new double wound ring core chokes designed for RF interference suppression in Bi-Polar SCR and TRIAC circuits. The chokes are supplied as a kit including a Delta Capacitor. For details see the new catalogue



Shoot me  
your  
catalogue

I enclose PO/Cheque for 10p  
Name .....  
Address .....  
Arrow Electronics Limited  
Dept. PE2  
7 Coptfold Road  
Brentwood, Essex


# Connoisseur

## B.D.2 Press button speed change turntable



Now, a new development on the well established Connoisseur BD2 belt drive turntable - press button speed change. This new development is exciting news for the enthusiast and comes as part of an integrated turntable and pickup arm assembly which also features a special version of the popular SAU 2 arm. This is now fitted with a new lifting device which gives improved lowering characteristics, the headshell allowing for lateral adjustment of the cartridge. The BD2 is supplied as a chassis unit or spring mounted on a wood plinth with dust cover.

## B.D.1 Turntable kit

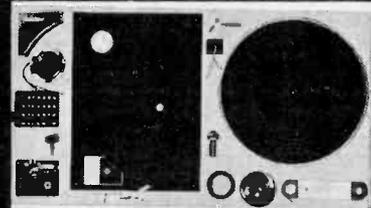

The B.D.1 well known for its superb performance and quality two speed working through a flexible belt drive system is now available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.


## A.R. SUGDEN & CO. (ENGINEERS) LTD.

Market Street, Brighouse HD6 1DX, Yorkshire. Telephone: 2142.

## INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!  
HANDY!  
TIDY!

DISCOUNT PRICES

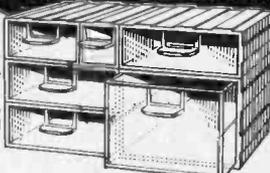

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

### BUY AT TRADE PRICES!

**SINGLE UNITS (1D)** (5ins x 2½ins x 2½ins) £1.35 DOZEN.

**DOUBLE UNITS (2D)** (5ins x 4½ins x 2½ins) £2.25 DOZEN.

**TREBLE (3D)** £2.35 for 8.

**DOUBLE TREBLE 2** draws, in one outer case (6D2), £3.65 for 8, **EXTRA LARGE SIZE (6D1)** £3.30 for 8.

### PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £  
Orders £10 and over DEDUCT 7½% in the £  
Orders £20 and over DEDUCT 10% in the £  
**PACKING/POSTAGE/CARRIAGE:** Add 35p to all orders under £5. Orders £5 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID

**IVORYET LIMITED**

(Dept. PE10) 124 Cricklewood Broadway, London, N.W.2  
Tel. 01-450 4844

## MULTI MINI VICE AND STAND

£5.90

26p P. & P.



This unique all purpose vice is just like a 'third hand' countless uses for the electronics enthusiast —assembly, soldering, gluing, wiring, drilling, etc. Firm base, positive grip for all shapes of work, with independently adjustable twin jaws.

Truly a precision made bargain.

Also: single jaw model £3.37 (22p P. & P.)

**FREEBORN LTD. (Dept. PE10)**  
Beechfield House • West Bar  
Banbury • Oxon

## 4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

### MAINS INTERCOM

No batteries—20 wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.40. P. & P. 55p extra.

## INTERCOM/BABY ALARM



£3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. 25p.

### Transistor TELEPHONE AMPLIFIER




£2.99

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 14p extra. P. & P. 25p. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (PE/1)**  
169 KENSINGTON HIGH STREET, LONDON, W.8

## LEAK AMPLIFIER BARGAN

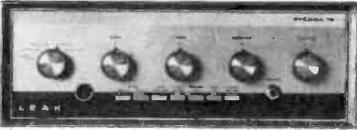

STEREO 70 Amp. (Cased). LIST PRICE £75-00  
**LASKY'S PRICE £49-50**

STEREO 30 plus Amp. (Cased). LIST PRICE £62-50  
**LASKY'S PRICE £39-75**  
 C & P £1

## LEAK TEAK CASES

Teak or Walnut case for Stereofetic tuner only.

LIST PRICE £7-37  
**LASKY'S PRICE £2-50** C & P 25p

Double case to hold Stereo 30 or Stereo 70 and Stereofetic tuner in Teak or Walnut.

LIST PRICE £10-37  
**LASKY'S PRICE £4-95** C & P 35p



## LEAK TRUSPEED

2-speed 45 and 33 1/2 rpm belt drive turntable complete with plinth, cover and Shure cartridge.

LIST PRICE £69-50

**LASKY'S PRICE £47-50** C & P £1-50

## SINCLAIR PHASE LOCK LOOP STEREO FM TUNER



Incorporates varicap diodes, printed circuit, coils, squelch circuit I.C. Decoder, etc., supplied completely built and tested and ready to be mounted into any cabinet you choose. It may be used with any High Fidelity Amplifier. Power requirements 25/30V DC.

LIST PRICE £25-00  
**LASKY'S PRICE £15-75** C & P 25p

## BSR TAPE DECK SCOOP



Reels not supplied

### BSR TD2

FANTASTIC VALUE, ONLY Lasky's can offer you a tape deck at such an amazing price. The BSR TD2 tape deck operates by a simple reliable mechanism using the minimum of controls.

With 1/2 track mono heads. Incorporates fast wind and fast rewind, records at 3 1/2 ips. giving up to 3 hrs playing time, takes up to 5 1/2 in. spools. Size 1 3/4 in. x 8 1/2 in. front to rear, 2 1/4 in. below plate, 1 1/4 in. above plate.

ALSO SUITABLE FOR USE AS A TAPE TRANSPORTER

**LASKY'S PRICE £8-95** C & P 35p

## BELTEK C5700 8 TRACK

### Stereo car Player

Accepts all standard pre-recorded 8 track stereo cartridges. Features include automatic head cleaner, channel select and channel repeat push buttons, slider type volume and tone controls, channel balance. Output 5 watts per channel, frequency response 50Hz-10KHz. Output imp. 4 ohms, size 4 1/2 (W) x 1 1/4 (H) x 6 1/2 (D) in. Operates on 12V DC negative earth. Beautifully styled with black ivory and chrome trim.

**BELTEK C5700** complete with mounting brackets and 8 track pre-recorded demonstration cartridge. C & P 30p

**£19-75**

### BELTEK R5310 FM TUNING ADAPTOR

Matches the C5700, the ideal car stereo system.

**LASKY'S PRICE £18-95** C & P 25p

Add £3-75 to any BELTEK car player for pair of FANTAVOX KS701 car speakers.



## AKAI TAPE RECORDER SCOOP!

(C & P 75p on all Tape Decks.)

**AKAI 4000D** illustrated List Price £93-65 Lasky's Price £61-50

**AKAI 1720L** List Price £87-36 Lasky's Price £58-95

**AKAI X1800SD** List Price £162-79 Lasky's Price £111-50

**AKAI X200D** List Price £157-93 Lasky's Price £106-50

**2 CSS-8 Speakers** List Price £25-00 (pair) Lasky's Price £15-95 C & P 50p


**2 ADM 11/8 mics.** Suitable for use on all Akai tape recorders. List Price £11-90. Lasky's Price (pair) £7-50. C & P 15p.

## FANTASTIC VALUE WHARFEDALE SCOOP!

**10" BRONZE C/S**  
 10 in. cloth surround 15 ohms.  
**LASKY'S PRICE £2-45** C & P 20p



## STEREOSOUND SPEAKERS

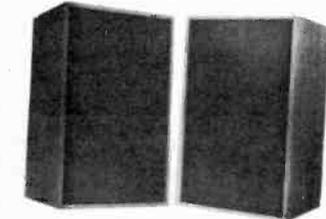

An attractive bookshelf speaker system with teak veneer finish. Imp. 8 ohms. Max. Power 12W. Size 1 1/4 (H) x 9 (W) x 7 1/2 (D) in.  
**LASKY'S PRICE (PAIR) £15-75** C & P 25p

## LEAK SPEAKERS

150 Speakers (pair) .. .. . £38-95 C & P  
 250 " " " " " " " " " " £48-95 £2-50  
 600 " " " " " " " " " " £68-75

## DIGITAL CLOCK

### EXCLUSIVELY FROM LASKY'S

The clock measures 5 1/2 (W) x 2 1/2 (H) x 3 1/2 (D) (overall from front of drum to back of switch). SPEC.: 210/240V a.c. 50Hz operation; switch rating 250V, 3A. Complete with instructions. NOW WITH ILLUMINATED DIAL COMPLETE WITH KNOBS  
**FEATURES:** ● MAINS OPERATION ● 12-HOUR ALARM ● AUTO "SLEEP" SWITCH ● HOURS, MINUTES AND SECONDS READ-OFF ● FORWARD AND BACKWARD TIME ADJUSTMENT ● SILENT OPERATION ● SHOCK AND VIBRATION PROOF ● BUILT IN ALARM BUZZER  
**SPECIAL QUOTES LASKY'S £6-75** C & P FOR QUANTITIES PRICE 25p




## BSR TD8S

### 8 TRACK STEREO CARTRIDGE PLAYER

The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mW. Power requirements: 210/250V AC, 50Hz. Frequency response: 50Hz-10KHz. 4 pole dynamically balanced synchronous motor. Black and woodgrain plastic cabinet. Size: 8 1/2 (W) x 3 1/2 (H) x 10 1/2 (D) in.  
**LASKY'S PRICE £17-95**  
 Price £24-20



## Garrard Record Players

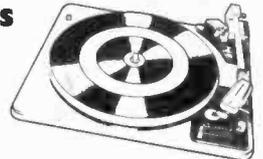

SP25 Mk. III Deck Only

4 speed

Automatic Single Player

Lasky's price **£11-50**

Garrard SL95B Deck	£35-00
Add £9-00 for Garrard Base and Cover	
Garrard AP76 deck only	£18-85
Garrard 40B deck only	£9-50
complete with stereo cartridge	£11-50
Garrard SL55B deck only	£9-00
Garrard 2025TC deck only	
complete with K540A stereo ceramic cartridge	£7-95
Garrard ZERO 100 Automatic	£43-50*
Garrard ZERO 100S Single Player	£42-75*
	*C & P £1-50

## Garrard Plinths & Covers

WB4 Mk. II Plinth	£5-45
SPC4 Mk. II cover	£4-25
Price together	£8-70
WB1 Plinth	£3-70
SPC1 cover	£3-60
Price together	£6-50

## SP 25 Package

SP25 Mk. III Single Player	List	£15-85
AD76K stereo magnetic cartridge	List	£4-35
Lasky's teak plinth and cover	List	£4-75

Total List Price .. .. . £24-95

**Package Price £18-50**

## AP 76 Package

AP76 Single Player	List	£29-26
SHURE M44E Cartridge	List	£8-59
Lasky's Base and Cover	List	£5-95

Total List Price .. .. . £43-80

**Package Price £35-00**

## CARRIAGE—all units

DECK ONLY 50p. PLINTH & COVER ONLY 25p. DECK WITH PLINTH AND COVER 75p.

# Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

**NEW CITY BRANCH NOW OPEN**

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST. TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821



# RTVC THE

## THE FABULOUSLY SUCCESSFUL VISCOUNT III AUDIO £52 complete

14 + 14 watts r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10 watts at 1kHz — 0.1%.

This is real value for money! We have designed 2 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For both systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with simulated teak plinth and dust cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

### SPEAKERS

**Duo Type II** Size approx. 17in. x 10½in. x 6½in. Drive unit 13in. x 8in. with parasitic tweeter. Max power 10 watts, ohms. Simulated Teak cabinet. £14 pair + £3 p & p.

**Duo Type III** Size approx. 23½in. x 11½in. x 9½in. Drive unit 13½in. x 8½in. with H.F. speaker. Max power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p & p.

### SPECIFICATION

14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0-1%. P.U.1. (for Ceramic cartridges) 150mV into 3 Meg. P.U.2. (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within ±1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal-to-noise ratio: (all controls at max) —P.U.1. and radio —65dB, P.U.2 —58dB. Cross talk better than —35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13½in. x 9in. x 3½in. Send S.A.E. for fully illustrated brochure. 12 MONTH'S WRITTEN GUARANTEE.

PRICES: SYSTEM 1	
Viscount III R 101 amplifier	£22.00 + 90p p&p
2 x Duo Type II speakers	£14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
<b>Total</b>	<b>£59.00</b>

Available complete for only £52 + £3.50 p & p

PRICES: SYSTEM 2	
Viscount R 101 amplifier	£22.00 + 90p p&p
2 x Duo Type III speakers	£32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
<b>Total</b>	<b>£77.00</b>

Available complete for £69 + £4 p & p

— ONLY FROM US



# MUSIC MAKERS

## UNISOUND FOR THE NEW SOUND

AT £25

The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds!

Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13in. X 8in. EMI Twin-cone speakers ready for mounting in their elegant cabinets, which simply need screwing and glueing together. All glue and screws supplied.

Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.


£25 complete plus £2.80 p. & p. Diamond Stylus £1.25 extra.

Power output: 4 watts per channel into 8 ohms. Inputs: 120 mV (for ceramic cartridges). Stereo headphones with adaptor £4.00.
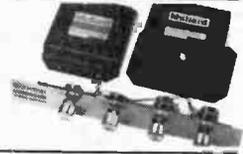
### UNISOUND MODULES ONLY £6.95

If you prefer, you can buy the three modules—pre-amplifier power supply/dual power amplifier, and control panel—for themselves for only £6.95. P. & P. 50p extra.

No soldering, just simply screw together with screwdriver supplied. Their overall specification is the same as shown for the complete Unisound console, using the high efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum.



AN **R T V C** EXCLUSIVE DESIGN

## A 'NATURAL' ONLY FROM **R T V C** THE TOURIST PB CAR RADIO KIT

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms. Power consumption is less than 1 amp.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale for easy reading at night. Chassis size is: 7in wide, 2in. high and 4 1/8 in. deep (excluding front panel, etc.).

★ Circuit diagram and comprehensive instructions 50p, free with parts.

★ Fully retractable lockable car aerial £1.25 post paid.

PRICE ONLY £7 + p & p 50p

8 ohm speaker with baffle and fixing strips £1.50 + 25p p & p, post free if brought with the kit.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

ONLY  
**£7.00**



## RELIANT MK.IV

★ 5 Electronically Mixed Inputs. ★ 3 Individual Mixing Controls. ★ Separate bass and treble controls common to all 5 inputs. ★ Mixer employing F.E.T. (Field Effect Transistor). ★ Solid State Circuitry. ★ Attractive Styling.

**INPUTS:**—1. Crystal Mic. or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram., Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

**CONTROLS:**—3 Volume controls. Bass control range: 13dB @ 60Hz. Treble control range: ± 12dB @ 15KHz. Separate ON/OFF Switch. Neon indicator. **POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker. **SIGNAL NOISE:**—Better than -60dB on inputs 3, 4 and 5 & -50dB on 1 & 2. **SUPPLY:**—220-250 A.C. Mains. **SIZE:**—12 1/2 in. X 6 in. X 3 1/2 in.

**£10.50**  
plus p & p 60p

VISIT OUR SHOWROOM

**R T V C**

S.A.E. for fully illustrated leaflet

Radio and TV Components (Acton) Ltd.  
21D High St., Acton, London W3 6NG  
323 Edgware Road, London, W.2

Mail orders to Acton • Terms C.W.O. • All enquiries S.A.E.

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it’s as fascinating as a hobby.**

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

### New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of “**OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO**”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF

## POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B12, Aldermaston Court, Reading RG7 4PF  
Please send books and full information — free and without obligation.



NAME ..... AGE .....  
BLOCK CAPITALS PLEASE  
ADDRESS .....

SUBJECT OF INTEREST.....

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**  
Accredited by the Council for the Accreditation of Correspondence Colleges.

**MICROJET WELDER**  
A TINY FLAME UP TO 500°F WELDS BRASS & SOLDER

**£11-50**

**INC. 3 FLAME TIPS**  
A precision tool using a combination of butane and compressed oxygen. U.S.A. manufactured. Gives two sizes of flame temperatures up to 5,000°F. Adjustable of pencil lead thickness. Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc., gold and silver. Ideal for electronics and electrical engineering, jewellers, clock-makers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 oxygen and 1 butane cylinders £1-50 inc. post. Complete with instructions. Our price **£11-50 + 31p P. & P.** Send **£11-81.**

**TWIST FREE STORAGE**  
WITH THE SAFE-WAY MAINS EXTENSION LEAD

**£1-69**

Store cable tidily. Heavy duty 3-core cable fitted under breakable rubber standard 13 amp fused 3-pin plug and 3-pin socket. Saves trouble fitting yourself. For Domestic Appliances, Garden Power Tools, Hedge Trimmers, Mowers, etc. 30ft. app. cable and **FREE** storage reel **£1-00 + 41p P. & P.** Send **£2-10.** 15ft. app. **£1-20 + 35p P. & P.** 50ft. app. **£2-20 + 41p P. & P.** 75ft. app. **£2 + 50p P. & P.** 100ft. app. **£2-75 + 55p P. & P.** 50ft. app. “**Everpoint**” cable with winder reel, socket, plug, carry handle **£3-00 + 41p P. & P.**

**BINOCULAR MAGNIFIER**  
FOR PRECISION CLOSE-UP WORK—LEAVES BOTH HANDS FREE

**£4-95**

See close-up work with less eye strain and fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glassworks. Can be worn over normal glasses. An essential aid in modelling, industry, home and workshop. Stamp collecting. Jewellers, watchmakers and any fine work. 2 1/2 x magnification. **£4-05 + 35p P. & P.** Send **£5-30.** 3 x model 50p extra. State model.

**TWIN-BEAM SPEC-LAMP**—Worn just like a pair of spectacles. Two powerful spot lamps illuminate working area. Can be worn with Binocular Magnifier. Battery operated. Only **£1-00 + 10p P. & P.** Send **£2.**

**13 AMP DISTRIBUTION PANEL**

**From Only £2-40**

Safe and quick. **FOUR** 13 amp 3-pin shuttered Socket. Outlets Red neon warning indicator operates when in use. Only **£2-40 + 35p P. & P.** Total **£2-75.** Also De Luxe Model (illus.) **PLUS** On/Off switch **PLUS** Magnetic Contact Breaker —If you draw too much current it switches off automatically. **PLUS** 30ft (9 metres) approx. lead. **£6-75 + 40p P. & P.** Total **£7-15.** Bonus offer: if required, set of four fused 13 amp plugs 50p extra. Post free if ordered with above.

**JOHN DUDLEY & CO. LTD.** Dept. PE5, 301 Crickwood Lane, Childs Hill, London, N.W.2. Tel. 01-458 5917. Callers welcome.

**Mini-Drill**

**ONLY £2 P. & P. 0p**

## AMAZING MINI-DRILL

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with **MINI-DRILL**. Super Kit (extra power, interchangeable chuck) **£4-95** p.p. 13p. De Luxe Professional Kit with 17 tools **£7-65** p.p. 23p. Money Ref. Guarantee.

**FOR PRECISION MODEL WORK**

**+ 6 TOOLS**

ABRASIVE  
SPAR DRILL  
BURR  
NIP  
BRUSH

**MERLIN SUPPLY CO.**  
Dept. PE10D, Nailsea, Bristol BS19 2LP

## PARKER'S SHEET METAL FOLDING MACHINES HEAVY VICE MODELS

**With Bevelled Former Bars** Carr. free

No. 1.	Capacity 18 gauge mild steel × 36in. wide	... ..	£17
No. 2.	Capacity 18 gauge mild steel × 24in. wide	... ..	£12
No. 3.	Capacity 16 gauge mild steel × 18in. wide	... ..	£12

Also new bench models. Capacities 36in. × 18 gauge **£35.** 24in. × 16 gauge **£32.** Carriage free.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 27 1/2p per ft. Other models 17 1/2p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

# Jermyn Cash Sales

All goods supplied are manufacturers' branded.  
We neither stock nor supply manufacturers' rejects.

Popular types ex stock.

Devices marked with an \* available in bargain corner.

Diodes/Rectifiers	*General Purpose Transistors	Unijunction Transistors	SCR's (Thyristors)
<p>*1N4148 (= 1N914) 5p each</p> <p>1N5060 400v 2.5A 11p each</p> <p>1N4001 7p each</p> <p>1N4005 14p each</p> <p>Comprehensive range of Zener Diodes in stock—too many to list.</p>	<p>*2N2926 mixed colours 27p each</p> <p>*2N2926 (red) 3p each</p> <p>*2N3390 hfe 400-800 25p each</p> <p>*2N5355 complement to 2N2926 22p each</p>	<p>2N2646 46p each</p> <p>D5E29 low cost version 32p each</p> <p>2N4870 39p each</p> <p>2N4871 34p each</p>	<p>C13F complementary 50V 0.25A 44p each</p> <p>TAG06 TO18 60V 0.6A 26p each</p> <p>TAG1-400 TO5 400V 1A 55p each</p> <p>TAG2-5-400 TO5 400V 2.5A 65p each</p> <p>C106B plastic 200V 4A 43p each</p> <p>C106B (400) plastic 240V ac 3A 47p each</p> <p>*C20D † stud 400V 7.5A £1.34 each</p> <p>C22D/1057/2 400V 7.5A with heatsink £1.57 each</p>
Photo Transistor (High Gain)	Power Transistors	Power Darlingtons	SEMICONDUCTOR CATALOGUE lists over 10,000 devices 60p
<p>*2N5777 28p each</p> <p>2N3904 } complementary pair 21p each</p> <p>2N3906 } 21p each</p>	<p>D40D1 1A NPN 26p each</p> <p>D41D1 1A PNP 27p each</p> <p>D42C1 3A NPN 31p each</p> <p>D43C1 3A PNP 34p each</p> <p>MJ481 4A NPN £1.09 each</p> <p>MJ491 4A PNP £1.31 each</p> <p>2N3055 10A NPN 60p each</p> <p>MJ2955 10A PNP £1.06 each</p>	<p>D40C1 0.5A NPN 44p each</p> <p>MJ4000 4.0A NPN £1.10 each</p> <p>MJ4010 4.0A PNP £1.51 each</p> <p>MJE1100 5A NPN £1.12 each</p> <p>MJE1101 5A PNP £1.23 each</p> <p>MJ1000 8.0A NPN £1.12 each</p> <p>MJ900 8.0A PNP £1.34 each</p> <p>MJ4034 16.0A NPN £3.66 each</p> <p>MJ4031 16.0A PNP £3.89 each</p>	<p>Price list of over 4,000 devices normally in stock 12p</p>
*Triacs	Diac	IC and Transistor Sockets	Plugs (Pin Headers) for DIL Sockets
<p>TAG302/400 400V 2A TO5 59p each</p> <p>MAC11-6 (2N6155) 400V 10A plastic £1.27 each</p> <p>Isolated types and many others from stock</p>	<p>D32 21p each</p> <p>ST4 Hysteresis free 46p each</p>	<p>Full range of Jermyn Manufacturing Divisions products</p> <p>TO18 Socket A23-2044 9p each</p> <p>TO5 Socket A23-2045 9p each</p> <p>TO99 Socket A23-2013 27p each</p> <p>TO100 Socket A23-2015 30p each</p> <p>TO110 Socket A23-2014 30p each</p> <p>DIL 14-Pin Skt A23-2066Y 31p each</p> <p>DIL 16-Pin Skt A23-2067Y 42p each</p>	<p>A23-2048 14 pin 27p each</p> <p>A23-2049 16 pin 30p each</p> <p>Add suffix TC if deep cover required 4p extra</p>
Integrated Circuits	*Tunnel Diodes	Operational, etc.	Digital
<p><b>Audio</b></p> <p>PA230 Low noise mono-pre-amp £1.31 each</p> <p>MC1303 Stereo pre-amp £2.19 each</p> <p>PA263/A1286 3.5w rms amp with PC board £1.75 each</p> <p>MFC6040 Electronic attenuator 86p each</p> <p>MC1310 Monolithic FM Stereo Decoder</p>	<p>1N3716 4.7mA peak point £1.78 each</p>	<p>RF</p> <p>*PA189 RF up to 50 MHz £1.48 each</p> <p>MC1304 Stereo De-modulator £3.50 each</p> <p>MC1350 Limiting FM IF amp 94p each</p> <p>MC1310 Coil-less stereo de-mod £2.77 each</p>	<p>Full range of DTL, TTL and ECL Typical prices—</p> <p>MIC 7400J 25p each</p> <p>MIC 7413J 40p each</p> <p>Dual schmitt</p>
		<p>RC709D 84p each</p> <p>RC741D 68p each</p> <p>JA424 Zero-voltage S/W £1.48 each</p>	<p>A23-2048 14 pin 27p each</p> <p>A23-2049 16 pin 30p each</p> <p>Add suffix TC if deep cover required 4p extra</p>
		<p>Based on a unique phase-locked loop circuit (originally developed for aerospace), the Motorola MC1310 requires no external tuning inductors and is far more stable than previous IC decoders. Automatic stereo-mono switching is built-in, as well as a lamp-drive circuit. Thus a complete decoder can be built using very few discrete components and may be set up without using instruments. Stereo channel separation 40dB at 1 kHz can be readily achieved with total harmonic distortion around 0.3% for 560mV composite input. Price £2.77 plus 15p p. &amp; p.</p>	
<b>Bargain Corner</b>		<b>Tried and Tested Kits</b>	<b>Power Controller:</b>
<p>1S2120 12V Zener 7 for 50p</p> <p>1N4148 12 for 50p</p> <p>TD710 Tunnel Diode 66p each</p> <p>2N2926 mixed 25 for 200p</p> <p>2N2926 (red) 8 for 50p</p> <p>2N3390 3 for 50p</p> <p>2N5777 4 for 50p</p> <p>C20B (our devices) 30p each</p> <p>SC35D 50p each</p>	<p>SC46D 86p each</p> <p>SCR Manual previous edition £1.00 including post and packing.</p> <p>PA189 2 for £2.00</p> <p>2N5355 complement to 2N2926 3 for 50p</p>	<p><b>Hot Ignition:</b> Electronic ignition kit as described in <i>Practical Wireless</i> June/July issues 1972. £7.75 complete. State positive or negative earth 6 or 12 volt.</p> <p><b>Cool Lighting:</b> A new version of our popular light dimmer. 300 watt capacity. £2.80 complete with trendy knob.</p>	<p>A drill speed controller using an SCR and SUS giving continuously variable control featuring: (1) very high torque down to under 250 rpm due to back emf feedback; (2) conservatively rated up to 1,000 watts; (3) may be used for 1kW electric fire control; (4) equivalent to units costing £20. £5.00 complete.</p>

All prices except kits subject to 15p handling post and packing.  
Minimum order £1 add 25% if below.

Jermyn Industries, Sevenoaks, Kent

# BUILD A PROJECT 'X' SYNTHESISER



Typical Simplified Synthesiser

## MAN-SIZED ROBUST PATCHBOARD

MAKE A "PATCH" AS IF YOU MEAN IT. "K-L-O-N-K" and it's MADE!

No fiddling with fragile patch pins. No cables. Countless possible combinations giving **FULL RANGE EFFECTS**. Keyboards available for versatile "live" use.

## NEW BREAKTHROUGH

VCO-2 gives SINE, TRIANGULAR and SQUARE outputs, and is stable! 1 volt/octave control. Single £20 each. Matched and tracked £23 each.

SHE-1 SAMPLE, HOLD and ENVELOPE module gives sustain and variable env. to VCO signal. £11.50.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group. Our modules are used in professional equipment! Send s.a.e. for synthesiser details or send 15p for full catalogue of our famous musical effects.

## D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

## Dewtron

using (Regd. Trademark)

## PROFESSIONAL MODULES

### CASH SAVINGS

by buying modules and parts in bulk!

All modules are available separately:

Ring Modulator RM2, £7. Voltage-controlled Oscillator VC01, £9.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £12.50. White noise type WN1, £6. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £4.50.

## SOUND BARGAINS




## GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM  
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10.50  
+40p P. & P.

THIS NEW 1972 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHERBAND. Frequency ranges: MW 540-1600kHz, FM 88-108MHz, Airband 108-135 MHz, VHF 143-175 MHz, 23 semiconductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31in telescopic aerial. Runs off mains a.c. 230/240V or off 4 1.5 batteries, or one re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2 in x 6 1/2 in. 3 1/2 in. Written guarantee. Special magnetic ear-piece for personal listening, dry batteries free. **HURRY!** Limited quantity only from Markytme.

OUR PRICE £28.95  
+50p P. & P.

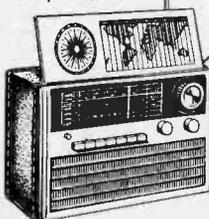


Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with Stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240V domestic mains supply. 14 transistors: 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350 kHz. Medium 330-1605 kHz. Marine 1.6-4.5 MHz. Short Wave 12-24 MHz. FM/VHF 88-108 MHz. Aircraft 108-135 MHz. PUBLIC SERVICE BANDS 135-174 MHz. Fully guaranteed.

N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

## MARKYTME

(Dept. PES), 372 EDGWARE ROAD  
LONDON, W.2. Tel. 01-723 0094  
Callers welcome Mon. to Sat. 9 a.m.-6 p.m.

# Are you alright for Jacks?

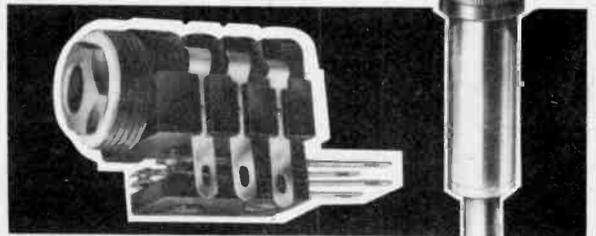

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes... plugs in both screened and unscreened versions... socket bodies in high melting point thermoplastic... several unique features (some protected by UK and US Patents)... Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



## RENDAR®

Rendar Instruments Ltd., Victoria Road  
Burgess Hill, Sussex. Tel. Burgess Hill 2642-4  
Cables: Rendar, Burgess Hill

# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-20	AD162	0-33	BC148	0-10	BD137	0-45	BF188	0-40	OC19	0-35	2G371	0-18	2N2219	0-20	2N3054	0-46	2N4059	0-10
AC113	0-20	AD161 &		BC149	0-12	BD138	0-50	BF194	0-12	OC20	0-38	2G373B	0-12	2N2220	0-22	2N3055	0-50	2N4060	0-12
AC115	0-23	AD162 (MP)		BC150	0-18	BD139	0-55	BF195	0-12	OC22	0-42	2G374	0-17	2N2221	0-20	2N3056	0-14	2N4061	0-12
AC117K	0-20		0-55	BC151	0-20	BD140	0-60	BF196	0-14	OC23	0-46	2G375	0-20	2N2222	0-20	2N3057	0-18	2N4062	0-12
AC122	0-12	ADT140	0-50	BC152	0-17	BD155	0-80	BF197	0-14	OC24	0-56	2G377	0-30	2N2268	0-17	2N3392	0-14	2N4284	0-17
AC125	0-17	AF114	0-24	BC153	0-28	BD175	0-60	BF200	0-45	OC25	0-38	2G378	0-16	2N2369	0-14	2N3393	0-14	2N4285	0-17
AC126	0-17	AF115	0-24	BC154	0-30	BD176	0-60	BF222	0-95	OC26	0-25	2G381	0-16	2N2369A	0-14	2N3394	0-14	2N4286	0-17
AC127	0-17	AF116	0-24	BC157	0-18	BD177	0-60	BF257	0-45	OC28	0-50	2G382	0-16	2N2411	0-24	2N3395	0-14	2N4287	0-17
AC128	0-17	AF117	0-24	BC158	0-12	BD178	0-65	BF258	0-60	OC29	0-42	2G414	0-30	2N2412	0-24	2N3402	0-21	2N4288	0-17
AC132	0-14	AF118	0-35	BC159	0-12	BD179	0-70	BF259	0-85	OC36	0-50	2G401	0-30	2N2456	0-47	2N3403	0-21	2N4289	0-17
AC134	0-14	AF124	0-30	BC160	0-45	BD180	0-70	BF262	0-55	OC37	0-50	2G417	0-25	2N2456A	0-21	2N3404	0-28	2N4290	0-17
AC137	0-14	AF125	0-25	BC161	0-50	BD185	0-65	BF263	0-55	OC41	0-20	2N388	0-35	2N2712	0-21	2N3405	0-42	2N4291	0-17
AC141	0-14	AF126	0-28	BC167	0-12	BD186	0-65	BF270	0-35	OC42	0-24	2N388A	0-55	2N2714	0-21	2N3414	0-15	2N4292	0-17
AC141K	0-17	AF127	0-28	BC168	0-12	BD187	0-70	BF271	0-30	OC44	0-15	2N404	0-20	2N2904	0-17	2N3415	0-15	2N4293	0-17
AC142	0-14	AF139	0-30	BC169	0-12	BD188	0-70	BF272	0-80	OC46	0-12	2N404A	0-28	2N2904A	0-21	2N3416	0-28	2N4293A	0-17
AC142K	0-17	AF178	0-50	BC170	0-12	BD189	0-75	BF273	0-75	OC70	0-35	OC70	0-10	2N2905	0-21	2N3417	0-28	2N4294	0-17
AC151	0-15	AF179	0-50	BC171	0-14	BD190	0-75	BF274	0-35	OC71	0-35	OC71	0-10	2N2906	0-15	2N3418	0-28	2N4295	0-17
AC154	0-20	AF180	0-50	BC172	0-14	BD195	0-85	BF275	0-60	OC72	0-14	2N598	0-42	2N2906A	0-18	2N3702	0-10	2N4296	0-17
AC156	0-20	AF181	0-45	BC173	0-14	BD196	0-85	BF276	0-27	OC74	0-14	2N599	0-45	2N2907	0-20	2N3703	0-10	2N4297	0-17
AC156	0-20	AF186	0-45	BC174	0-14	BD197	0-90	BF284	0-22	OC75	0-15	2N696	0-12	2N2907A	0-20	2N3704	0-10	2N4298	0-17
AC157	0-24	AF229	0-37	BC176	0-22	BD198	0-90	BF285	0-22	OC76	0-15	2N697	0-13	2N2907A	0-22	2N3705	0-11	2N4299	0-17
AC165	0-20	AL102	0-65	BC177	0-19	BD200	0-95	BF287	0-22	OC77	0-25	2N698	0-24	2N2920	0-14	2N3706	0-10	2N4300	0-17
AC166	0-20	AL103	0-65	BC178	0-19	BD200	0-95	BF287	0-22	OC77	0-25	2N699	0-24	2N2924	0-14	2N3706	0-09	2N4304	0-17
AC167	0-20	ASB26	0-25	BC179	0-19	BD205	0-80	BF288	0-22	OC81D	0-15	2N706	0-09	2N2924A	0-14	2N3707	0-11	2N4305	0-17
AC168	0-24	ASB27	0-25	BC180	0-24	BD206	0-80	BF290	0-20	OC82	0-15	2N706A	0-09	2N2926 (G)	0-12	2N3708	0-07	2N4306	0-17
AC169	0-14	ASB28	0-25	BC181	0-24	BD207	0-95	BF291	0-20	OC82D	0-15	2N708	0-12	2N2926 (Y)	0-12	2N3709	0-09	2N4307	0-17
AC176	0-24	ASB29	0-25	BC182	0-10	BD208	0-95	BF292	0-20	OC83	0-20	2N711	0-30	2N2926 (Y)	0-10	2N3710	0-09	2N4308	0-17
AC177	0-24	ASB30	0-25	BC192L	0-10	BDY20	1-00	BFY53	0-17	OC84	0-20	2N717	0-35	2N2926 (O)	0-11	2N3711	0-09	2N4322A	0-17
AC178	0-28	ASB51	0-25	BC183L	0-10	BF117	0-45	BSX19	0-15	OC140	0-20	2N718	0-24	2N2926 (R)	0-10	2N3820	0-50	2N4323	0-17
AC179	0-28	ASB52	0-25	BC183L	0-10	BF117	0-45	BSX19	0-15	OC140	0-20	2N718A	0-50	2N2926 (R)	0-10	2N3821	0-35	2N4324	0-17
AC180	0-17	ASB54	0-25	BC184	0-12	BF118	0-70	BSX20	0-15	OC169	0-25	2N726	0-28	2N2926 (B)	0-10	2N3822	0-50	2N4325	0-17
AC180K	0-20	ASB56	0-25	BC184L	0-12	BF119	0-70	BSY25	0-15	OC170	0-25	2N727	0-28	2N2926 (B)	0-10	2N3823	0-28	2N4325	0-17
AC181	0-17	ASB56	0-25	BC186	0-28	BF121	0-45	BSY26	0-15	OC171	0-25	2N743	0-20	2N2926 (B)	0-10	2N3903	0-28	2N4326	0-17
AC181K	0-17	ASB57	0-25	BC187	0-28	BF123	0-45	BSY27	0-15	OC200	0-25	2N744	0-20	2N2926 (B)	0-10	2N3904	0-30	2N4327	0-17
AC187	0-22	ASB59	0-25	BC187	0-11	BF125	0-45	BSY28	0-15	OC201	0-28	2N914	0-14	2N3011	0-10	2N3905	0-28	2N4328	0-17
AC187K	0-20	ASB21	0-40	BC208	0-11	BF127	0-50	BSY29	0-15	OC202	0-28	2N918	0-30	2N3011	0-14	2N3906	0-27	2N4361	0-17
AC188	0-22	BC107	0-09	BC209	0-12	BF152	0-55	BSY38	0-18	OC203	0-25	2N920	0-21	2N3053	0-17	2N4058	0-12	40362	0-45
AC188K	0-20	BC108	0-09	BC212L	0-11	BF153	0-45	BSY39	0-18	OC204	0-25	2N920	0-21						
ACY17	0-25	BC109	0-10	BC213L	0-11	BF154	0-45	BSY40	0-28	OC205	0-35	2N1131	0-20						
ACY14	0-20	BC113	0-10	BC214L	0-14	BF155	0-70	BSY41	0-28	OC309	0-40	2N1132	0-22						
ACY19	0-20	BC114	0-15	BC225	0-25	BF156	0-48	BSY45	0-12	P346A	0-20	2N1302	0-14	AA119	0-08	BY133	0-21	OA10	0-35
ACY20	0-20	BC115	0-15	BC226	0-35	BF157	0-45	BSY55A	0-12	P397	0-42	2N1303	0-14	AA120	0-08	BY164	0-50	OA47	0-07
ACY21	0-20	BC116	0-15	BCY30	0-24	BF158	0-55	Bu105	2-00	OC71	0-43	2N1305	0-17	AA129	0-08	BYX38/30	0-42	OA79	0-07
ACY22	0-16	BC117	0-15	BCY31	0-28	BF159	0-60	CI11E	0-50	ORP12	0-43	2N1307	0-21	AA130	0-09		0-42	OA79	0-07
ACY27	0-18	BC118	0-10	BCY32	0-30	BF160	0-40	C400	0-30	ORP60	0-40	2N1306	0-21	AA131	0-09	BYZ10	0-35	OA81	0-07
ACY28	0-19	BC119	0-30	BCY33	0-22	BF162	0-40	C407	0-25	ORP61	0-40	2N1307	0-21	BA100	0-10	BYZ11	0-30	OA85	0-09
ACY29	0-35	BC120	0-80	BCY34	0-25	BF163	0-40	C424	0-20	RT140	0-12	2N1308	0-23	BA106	0-10	BYZ12	0-30	OA89	0-06
ACY30	0-28	BC125	0-12	BCY70	0-14	BF164	0-40	C425	0-60	RT141	0-17	2N1309	0-23	BA116	0-21	BYZ21	0-30	OA90	0-06
ACY31	0-28	BC126	0-18	BCY71	0-18	BF165	0-40	C426	0-35	T843	0-30	2N1613	0-20	BA126	0-22	BYZ23	0-25	OA91	0-06
ACY34	0-21	BC132	0-12	BCY72	0-14	BF167	0-22	C428	0-20	UT46	0-20	2N1711	0-20	BA148	0-14	BYZ16	0-40	OA95	0-07
ACY35	0-21	BC134	0-18	BCZ10	0-20	BF173	0-22	C441	0-30	2G301	0-09	2N1889	0-32	BA154	0-12	BYZ17	0-35	OA200	0-04
ACY36	0-28	BC135	0-12	BCZ11	0-25	BF176	0-35	C442	0-30	2G302	0-19	2N1890	0-35	BA155	0-14	BYZ18	0-35	OA202	0-05
ACY40	0-17	BC136	0-15	BCZ12	0-25	BF177	0-35	C444	0-35	2G303	0-19	2N1893	0-47	BA156	0-13	BYZ19	0-28	SD10	0-06
ACY41	0-18	BC137	0-15	BD121	0-60	BF178	0-30	C460	0-22	2G304	0-24	2N2147	0-72	BY100	0-15	CG62		SD19	0-05
ACY44	0-35	BC139	0-40	BD123	0-65	BF179	0-30	MAT100	0-19	2G306	0-40	2N2148	0-57	BY101	0-12	(Eq) OA91		IN34	0-07
AD130	0-38	BC140	0-30	BD124	0-60	BF180	0-30	MAT101	0-20	2G308	0-35	2N2160	0-60	BY105	0-17		0-05	IN34A	0-07
AD140	0-48	BC141	0-30	BD131	0-50	BF181	0-30	MAT120	0-19	2G309	0-35	2N2192	0-35	BY114	0-12	CG651	0-05	IN34A	0-07
AD142	0-48	BC142	0-30	BD132	0-60	BF182	0-40	MAT121	0-20	2G339	0-20	2N2193	0-35	BY126	0-14	(Eq) OA70		IN316	0-06
AD143	0-38	BC143	0-30	BD133	0-65	BF183	0-40	MFF102	0-42	2G339A	0-16	2N2194	0-35	BY127	0-15	OA79	0-06	IN414B	0-06
AD149	0-50	BC145	0-45	BD135	0-40	BF184	0-25	MFF104	0-87	2G344	0-18	2N2217	0-22	BY128	0-15	OA5	0-35	I8021	0-10
AD161	0-33	BC147	0-10	BD136	0-40	BF185	0-30	MFF105	0-37	2G345	0-16	2N2218	0-20	BY130	0-16	OA58L	0-21	I8651	0-06

### DIODES AND RECTIFIERS

AA119	0-08	BY133	0-21	OA10	0-35
AA120	0-08	BY164	0-50	OA47	0-07
AA129	0-08	BYX38/30	0-42	OA79	0-07
AA130	0-09		0-42	OA79	0-07
AA131	0-09	BYZ10	0-35	OA81	0-07
BA100	0-10	BYZ11	0-30	OA85	0-09
BA116	0-21	BYZ21	0-30	OA90	0-06
BA126	0-22	BYZ23	0-25	OA91	0-06
BA148					

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	16A	30A
705	T068	T066	T064	T048	T048	T048	T048
50	0-23	0-23	0-35	0-35	0-47	0-50	0-53
100	0-35	0-35	0-47	0-47	0-50	0-53	0-53
200	0-35	0-35	0-49	0-49	0-57	0-61	0-75
400	0-43	0-47	0-56	0-56	0-67	0-75	0-93
600	0-53	0-57	0-68	0-68	0-77	0-85	1-05
800	0-63	0-70	0-80	0-80	0-90	1-20	1-40

## SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0-04	0-06	0-05	0-07	0-14	0-21	0-30
100	0-04	0-06	0-05	0-07	0-14	0-21	0-30
200	0-05	0-09	0-06	0-14	0-20	0-24	0-10
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25
600	0-07	0-16	0-10	0-22	0-34	0-45	1-86
800	0-10	0-17	0-11	0-25	0-37	0-55	2-00
1000	0-11	0-25	0-14	0-30	0-46	0-63	2-50
1200		0-33		0-38	0-57	0-75	

TRIAC		
VBO	2A	10A
TO-1 TO-86 TO-88		
5p	5p	5p
100	80	76
200	60	90
400	70	75

**DIACS**  
**FOR USE WITH TRIACS**  
 BR100 (D39) 37p each

**FREE**  
 One 50p Pak of your own choice free with orders valued \$4 or over.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
 Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC44
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC44
T8	8 2G378 OC78
T9	8 2G399A 2N1202
T10	8 2G417 AF117

All 50p each pak

**2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS.** Our price 25p each.

**120 VCB MIXIE DRIVER TRANSISTOR.** 8im. B5X21 & C407, 2N1893 FULLY TESTED AND CODED ND 120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 5p each.

## POWER TRANS BONANZA!

**GENERAL PURPOSE GERM. PNP**  
 Coded GPI00. BRAND NEW TO-3 CASE. POSS. REPLACE.—OC25-28-29-30-35-36. NKT 401-403-404-405-406-430-451-452-453. T13027-3028, 2N280A, 2N456A-457A-458A, 2N511 A & B. 2G220-222. ETC. VCB0 50V VCB0 50V 10A PT. 30 WATTS Hic 30-170.  
 PRICE 1-24 25-99 100 up 43p each 40p each 36p each

**SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications.** Brand new Coded R 2400 VCB0 250V/VC0 100/1C 6A/30 Watta. HFE type 20/1F 5MHZ.  
 OUR PRICE EACH: 1-24 25-99 100 up 50p 45p

**ADI61/162 PNP M/P COMP GERM TRANS.** OUR LOWEST PRICE OF 55p PER PAIR

**FULL RANGE OF ZENER DIODES**  
 TO-1 TO-86 TO-88  
 2-33V 400mV (DO-7 Case) 13p ea. 11W (Top Hat) 18p ea. 10W (SG-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

**10 amp POTTED BRIDGE RECTIFIER** on heat sink. 100PIV. 90p each

**NEW LINE Plastic Encapsulated 2 Amp BRIDGE RECTS.**  
 50 v RMS 32p each  
 100 v RMS 37p each  
 400 v RMS 46p each  
 Size 15 mm x 6 mm.

**UNIJUNCTION**  
 U18 Eqvt. 2N2646, 2N1843, BEN3000  
 27p each 25-99 25p 50p up 30p

**CADMIUM CELLS**  
 ORP12 43p  
 ORP60, ORP61 40p each

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N705/8, B5Y-27/28/95A.** All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.  
 20 For 0-50  
 50 For 1-00  
 100 For 1-75  
 500 For 7-50  
 1000 For 18-00

**SIL. G.P. DIODES**  
 300mV 30 0-50  
 40PIV (Min.) 100 1-00  
 Sub-Min. 500 5-00  
 Full Tested 1,000 9-00  
 Ideal for Organ Builders.

**2N3055**  
 115 WATT SIL POWER NPN 50p EACH

**ALARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.**

**SILICON 50 WATTS MATCHED NPN/PNP**  
 BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCB0 100V/VC0 50/1C 10A. HFE type 100/1F 3mHZ.  
 OUR PRICES PER PAIR: 1-24 prs. 60p 25-99 prs. 55p 100 prs. 50p

## KING OF THE PAKS Unequaled Value and Quality

# SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-50
U 2	60 Mixed Germanium Transistors AF/RF	0-50
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-50
U 4	40 Germanium Transistors like OC81, AC128	0-50
U 5	80 200mA Sub-Min. Silicon Diodes	0-50
U 6	30 Sil. Planar Trans. NPN like B5Y95A, 2N706	0-50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V 0-50	
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-50
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-50
U10	20 BA550 charge storage Diodes DO-7 Glass	0-50
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-50
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-50
U13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0-50
U14	160 Mixed Silicon and Germanium Diodes	0-50
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-50
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-50
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-50
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 800 PIV	0-50
U19	25 Silicon NPN Transistors like BC108	0-50
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-50
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0-50
U23	30 MADT's like MHz Series PNP Transistors	0-50
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-50
U25	25 300 MHz NPN Silicon Transistors 2N708, B5Y27	0-50
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-50
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0-50
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	0-50
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0-50
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-50
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-50
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-50
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0-50
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-50
U36	25 Silicon Planar NPN Transistors TO-5 BFY60/51/52	0-50
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0-50
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-50
U39	30 RF GERM. PNP Transistors 2N1303/5 TO-5	0-50
U40	10 Dual Transistors 6 lead TO-5 2N2060	0-50
U41	25 RF Germanium Transistors TO-5, OC45, NKT72	0-50
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0-50
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-50
U44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-50
U45	7 3A SCR. TO66 up to 600V 1-00	

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

**SILICON PHOTO TRANSISTOR.** TO-18 Lens end NPN Sim. to BP x 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

**F.E.T.'S**  
 2N3819 35p 2N5458 50p  
 2N3820 50p 2N5459 40p  
 2N3821 85p BFW10 40p  
 2N3823 80p MPF105 40p

**NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

## INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Out" which include Functional and Part-Functional Units. These are classed as "out-of-spec" because they do not meet very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	-12 x 7400	0-50	UIC46	-5 x 7446	0-50	UIC86	-5 x 7486	0-50
UIC01	-12 x 7401	0-50	UIC47	-5 x 7447	0-50	UIC87	-5 x 7487	0-50
UIC02	-12 x 7402	0-50	UIC48	-5 x 7448	0-50	UIC88	-5 x 7488	0-50
UIC03	-12 x 7403	0-50	UIC50	-12 x 7450	0-50	UIC92	-5 x 7492	0-50
UIC04	-12 x 7404	0-50	UIC51	-12 x 7451	0-50	UIC93	-5 x 7493	0-50
UIC05	-12 x 7405	0-50	UIC53	-12 x 7453	0-50	UIC94	-5 x 7494	0-50
UIC06	-8 x 7406	0-50	UIC54	-12 x 7454	0-50	UIC95	-5 x 7495	0-50
UIC07	-8 x 7407	0-50	UIC60	-12 x 7460	0-50	UIC96	-5 x 7496	0-50
UIC10	-12 x 7410	0-50	UIC70	-8 x 7470	0-50	UIC100	-5 x 74100	0-50
UIC13	-8 x 7413	0-50	UIC72	-8 x 7472	0-50	UIC121	-5 x 74121	0-50
UIC20	-12 x 7420	0-50	UIC73	-8 x 7473	0-50	UIC141	-5 x 74141	0-50
UIC30	-12 x 7430	0-50	UIC74	-8 x 7474	0-50	UIC151	-5 x 74151	0-50
UIC40	-12 x 7440	0-50	UIC75	-8 x 7475	0-50	UIC154	-5 x 74154	0-50
UIC41	-5 x 7441	0-50	UIC76	-8 x 7476	0-50	UIC193	-5 x 74193	0-50
UIC42	-5 x 7442	0-50	UIC80	-5 x 7480	0-50	UIC199	-5 x 74199	0-50
UIC43	-5 x 7443	0-50	UIC81	-5 x 7481	0-50			
UIC44	-5 x 7444	0-50	UIC82	-5 x 7482	0-50			
UIC45	-5 x 7445	0-50	UIC83	-5 x 7483	0-50			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC.X1.

**BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593. OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.**

All mail orders please add 10p post and packing. Send all orders to BI-PAK P.O. Box 6, WARE, HERTS.  
 All mail orders please add 10p post and packing.  
 Send all orders to BI-PAK P.O. BOX 6, WARE, HERTS.

# - the lowest prices!

## 74 Series T.T.L. I.C's


BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS



	1	25	100+		1	25	100+
SN7400	0.15	0.14	0.12				
SN7401	0.15	0.14	0.12				
SN7402	0.15	0.14	0.12				
SN7403	0.15	0.14	0.12				
SN7404	0.15	0.14	0.12				
SN7405	0.15	0.14	0.12				
SN7406	0.35	0.31	0.28				
SN7407	0.35	0.31	0.28				
SN7408	0.18	0.17	0.16				
SN7409	0.18	0.17	0.16				
SN7410	0.15	0.14	0.12				
SN7411	0.25	0.24	0.23				
SN7412	0.35	0.31	0.28				
SN7413	0.29	0.28	0.24				
SN7416	0.43	0.40	0.38				
SN7417	0.43	0.40	0.38				
SN7420	0.15	0.14	0.12				
SN7422	0.15	0.14	0.12				
SN7423	0.50	0.48	0.45				
SN7425	0.50	0.48	0.45				
SN7427	0.45	0.42	0.40				
SN7428	0.70	0.65	0.60				
SN7450	0.15	0.14	0.12				
SN7432	0.45	0.42	0.40				
SN7433	0.80	0.75	0.70				
SN7437	0.64	0.62	0.60				
SN7438	0.64	0.62	0.60				
SN7440	0.15	0.14	0.12				
SN7441	0.67	0.64	0.58				
SN7442	0.67	0.64	0.58				
SN7443	£1.30	£1.25	£1.20				
SN7444	£1.30	£1.25	£1.20				
SN7445	£1.30	£1.25	£1.20				
SN7446	0.97	0.94	0.88				
SN7447	£1.00	0.97	0.95				
SN7448	£1.00	0.97	0.95				
SN7450	0.15	0.14	0.12				
SN7451	0.15	0.14	0.12				
SN7453	0.15	0.14	0.12				
SN7454	0.15	0.14	0.12				
SN7460	0.15	0.14	0.12				
SN7470	0.29	0.28	0.24				

## BI-PAK DO IT AGAIN!

### 50W pk 25w (RMS)

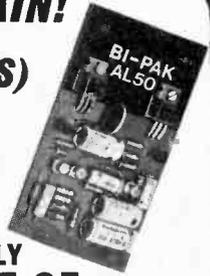


0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER

### THE AL50

- ★ Frequency Response 15Hz to 100,000—1dB.
  - ★ Load—3, 4, 8 or 16 ohms.
  - ★ Distortion—better than 1% at 1KHz.
  - ★ Signal to noise ratio 80dB.
- ONLY £3.25p each**
- ★ Supply voltage 10-35 Volts.
  - ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.  
FULLY BUILT — TESTED — GUARANTEED.

### STABILISED POWER MODULE SPM80

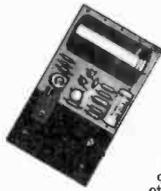

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2.95**

TRANSFORMER BMT80 £1.95 p. & p. 25p.

### STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

#### SPECIFICATION

Frequency Response	20Hz - 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs : 1. Tape Head	1-25 mV into 60K Ω
2. Radio, Tuner	35 mV into 60K Ω
3. Magnetic P.U.	1.5 mV into 60K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than - 65dB
Input overload	+ 20dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm



**SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23.00 FREE p. & p.**

All prices quoted in new pence Giro No. 388-7006  
Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

### ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C's

Type No.	Price	1-24	25-99	100 up
BP930	12p	11p	10p	10p
BP932	13p	12p	11p	11p
BP938	13p	12p	11p	11p
BP935	13p	12p	11p	11p
BP936	13p	12p	11p	11p
BP941	13p	12p	11p	11p
BP946	25p	24p	22p	22p
RP946	12p	11p	10p	10p
BP948	25p	24p	22p	22p
BP951	65p	60p	55p	55p
BP962	12p	11p	10p	10p
BP9093	40p	38p	35p	35p
BP9094	40p	38p	35p	35p
BP9097	40p	38p	35p	35p
BP9099	40p	38p	35p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### LINEAR I.C's—FULL SPEC.

Type No.	Price	1-24	25-99	100 up
BP 201C—SL201C	63p	53p	45p	45p
BP701C—SL701C	63p	50p	45p	45p
BP 702C—SL702C	63p	50p	45p	45p
BP 702—72702	63p	45p	40p	40p
BP709—72709	80p	34p	30p	30p
BP 709P—µA709C	80p	34p	30p	30p
BP 710—72710	44p	42p	40p	40p
BP 711—µA711	45p	42p	40p	40p
BP 741—72741	75p	60p	50p	50p
µA703C—µA703C	28p	26p	24p	24p
TAA 285	70p	60p	55p	55p
TAA 293	80p	75p	70p	70p
TAA 350	170p	158p	150p	150p

B.G.S. EA1000 B-68

## NUMERICAL INDICATOR TUBES



MODEL	CD86	GR116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2.3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All Indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.

### RTL MICROLOGIC CIRCUITS

	Price each	1-24	25-99	100 up
Epoxy TO-5 case				
uL900 Buffer	35p	33p	27p	27p
uL914 Dual 2 1/p gate	35p	33p	27p	27p
uL923 J-K flip-flop	50p	47p	45p	45p

Date and Circuits Booklet for IC's Price 7p.

### DUAL IN LINE SOCKETS.

14 & 16 Lead Sockets for use with DUAL-IN-LINE I.C's. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-99 100up.

T50 14 pin type	30p	27p	25p
T50 16 " " "	35p	32p	30p

LOW COST No.

BPS 14	16p	13p	11p
BPS 16	16p	14p	12p

# DISCOUNTS UP TO 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

**SPECIAL OFFER**  
Garrard SP25 Mk. III £17.75  
Goldring G800  
Teak plinth and tinted cover.  
All leads supplied.  
Please add £1.25 for P. & P.

## TURNTABLES

**Please add 75p post & packing**

Garrard SP25 Mk. III £9.45  
Garrard AP76 £18.50  
Garrard SL65B £12.65  
Garrard 1025T + cart. £5.97  
Garrard 2025TC, Sonotone 9TACH cart. £8.75  
Garrard Zero 100 (Auto) £26.50  
Garrard Zero 100 (Single) £38.75  
BSR MP60 £36.55  
£9.65  
Goldring GL72 £21.75  
Goldring GL72/P £27.95  
Goldring GL75/P £34.25  
Goldring GL85/P £55.50  
Goldring 101/P.C. £20.00  
Leak Delta £54.00  
Wharfedale Linton + cart. £27.25  
Thorens TD125 £57.00  
Thorens TD125AB £88.50  
Thorens TD150 Mk. II £26.00  
Thorens TD150A Mk. II £33.50

## AMPLIFIERS

**Please add 75p post & packing**

Amstrad 8000 Mk. II £16.25  
Amstrad IC2000 £27.50  
Amstrad Integra 4000 £21.95  
Armstrong 52 I (Teak cased) £43.90  
Alpha Highgate 212 £26.00  
Alpha Highgate FA300 £29.50  
Alpha Highgate FA400 £34.50  
Leak Delta 30 £47.65  
Leak Delta 70 £56.50  
Metrosound ST20E £24.45  
Metrosound ST60 £45.95  
Pioneer SA900 £92.00  
Pioneer SA1000 £94.00  
Rogers R/brook (Chassis) £35.00  
Rogers R/brook (Cased) £37.00  
Rogers R/bourne (Chassis) £41.95  
Rogers R/bourne (Cased) £47.50  
Rotel RA210 £24.50  
Rotel RA310 £33.00  
Rotel RA610 £49.95  
Scanetra HT58 £29.75  
Sinclair PR060 2 x Z30/PZ5 £14.95  
Sinclair PR060 2 x Z30/PZ6 £17.00  
Sinclair PR060 2 x Z50/PZ8 £17.00  
Trans £21.25  
Sinclair AFU (Filter Unit) £4.40  
Sinclair 605 £18.50  
Sinclair 2000 Mk. II £21.50  
Sinclair 3000 Mk. II £29.25  
Wharfedale Linton £37.50  
Goodmans Max Amp £37.95  
Eagle TSA149 £24.95  
Eagle TSA151 £34.50  
Teleton SAQ 206B £20.50  
Teleton SAQ 306 £22.50

## TUNERS

**Please add 75p post & packing**

Amstrad Multiplex 3000 £27.95  
Armstrong 523 £39.50  
Armstrong 524 £30.95  
Rogers R/brook FET4 (Chassis) £31.00  
Rogers R/brook FET4 (Cased) £35.00  
Rogers R/bourne FET4 (Cased) £43.00  
Rogers R/bourne FET4 (Cased) £48.00  
Sinclair PR060 (Module) £17.95  
Sinclair 2000/3000 Tuner £32.75  
Philips RH690 £33.00  
Leak Delta FM (Cased) £54.75  
Leak Delta AM/FM (Cased) £64.50

## TUNER/AMPLIFIERS

**Please add 75p post & packing**

Armstrong 525 (Teak cased) £67.95  
Armstrong 526 AM/FM (Teak cased) £77.75  
Leak Delta 75 £127.95  
Philips RH781 £50.00  
Philips RH702 £82.50  
Teleton 2100 £29.95  
Goodmans One Ten £99.50  
Rogers Ravensbrook £78.50  
Rogers R/brook (Chassis) £72.75  
Scanetra 1515 AM/FM £102.50  
Scanetra 3030 FMG £110.50  
Scanetra 1515 FM £74.50

## SPEAKERS

**Please add £1.25 for post & packing** Price per pair

Amstrad I38 £15.95  
Wharfedale Denton 2 £28.40  
Wharfedale Linton 2 £35.95  
Wharfedale Melton 2 £47.45  
Wharfedale Dove Dale 3 £39.50  
Celestion Ditton 120 £53.50  
Celestion Ditton 25 £87.00  
Goodmans Double Maxim £48.25  
Goodmans Mezzo 3 £44.95  
Goodmans Magister £74.00  
Sinclair Q16 £12.50

## CARTRIDGES

**Please add 10p post & packing**

Goldring G850 £3.39  
Goldring G800 £5.90  
Goldring G800E £8.95  
Goldring G800 Super E £14.95  
Shure M1D £3.95  
Shure M1E £5.65  
Shure M55E £5.85  
Shure M75E Type 2 £10.35  
Sonotone 9TACH £1.55

£3.20\*

Plus 35p P. & P.  
Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for McCord MP60 and others. For AP76; AP75; SL72B; SL75; SL95B\*. £4.20 plus 35p P. & P. Also finished in walnut to match Japanese equipment—at no extra.



# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. PE141 174 Pentonville Road, London, N1. Telephone 01-278 1759  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.  
MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

## UHF-AERIALS

Suitable for colour and monochrome reception.  
PLANAR folded dipoles + MESH reflectors



ILLUSTRATED UHF.50  
Aerial Arrays designed for fringe area reception UHF.50 £3.90  
UHF.18 £2.60

Without alochrome process for loft/window sill mounting UHF.10 £1.95  
chm Bkt & 5' angled mast C,5 £1.50  
wall Bkt & 5' angled mast W,5 £1.00  
(Available by mail order only when ordering UHF.50-UHF.18 or FM Aerials)

## VHF/FM AERIALS

Aerial Array single-dipole B,21 £1.30  
Aerial Array dipole-reflector B,22 £1.65

## CAR-AERIALS

Wing mounting spring Aerial 3-section extends to 48 1/2" A,6 £1.60  
Motorised electric Aerial complete with details & switch. 12V poss or neg. 5-section extends to 40" A,7 £6.00

## PRE-AMPLIFIERS

Suitable for colour and monochrome, freq coverage 40-860 MHz-14dB Gain  
Weather proof Pre-Amplifier T1 £5.25  
240V.A.C. Power Unit T1/PU £4.25

Low-Loss co-axial cable sold in multiples of 5 meters at 40p, nylon cable clips per 100 at 30p. Aerial switches at 90p Co-axial plugs at 8p.  
P & P. UHF & VHF/FM Aerials 50p, Car Aerials-Amps & cable etc. 25p.

When ordering UHF Aerials, please state channel combination or transmitter location. S.A.E. with enquiries please.  
Terms P.O./Cheque with order. U.K. Mainland only.

## AVEE (COMMUNICATIONS) LTD

Dept P.E.1. 96a Plains Avenue, Maidstone, Kent  
Telephone Maidstone 56962

## VALVES SAME DAY SERVICE

SETS 1R5, 1R6, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for £11.2. DAF96, DF96, DK96, DL96. 4 for £1.55.

1R5	-28	30C17	-78	EB91	-10	EM80	-38	PCF806	-56	U329	-68
1R5	-22	30C18	-61	EB3C3	-40	EM81	-38	PCF808	-68	U501	-80
1T4	-18	30F5	-64	EB3A1	-54	EM84	-39	PCF809	-38	UABC80	-32
384	-28	30FL1	-65	EB3C1	-30	EM87	-60	PCLR3	-57	UAF42	-50
3V4	-47	30FL12	-69	EB3C0	-22	EY61	-36	PCLR4	-34	UBC41	-52
5V4G	-31	30PL14	-68	EBF80	-82	EY86	-29	PCL85	-38	UBF80	-34
5V4G	-35	30L1	-29	EBF83	-39	EY87	-29	PCL86	-38	UBF89	-32
5Y3GT	-34	30L15	-70	EBF89	-29	EZ40	-42	PCL88	-65	UCC94	-32
6Z4G	-35	30L17	-67	EC081	-17	EZ41	-43	PCL800	-75	UCC95	-38
6Y80L2	-54	30P4	-65	EC089	-20	EZ60	-22	PCL805	-38	UCF80	-32
6AL5	-11	30P12	-72	EC083	-35	EZ61	-23	PENA4	-77	UCH42	-32
6AM6	-13	30P19	-65	EC085	-34	EZ90	-25	PEN36C	-70	UCH81	-32
6AQ5	-22	30PL1	-60	EC080A	-54	GZ30	-34	PFL200	-52	UCL82	-32
6AT6	-20	30PL13	-89	ECF80	-31	GZ32	-40	PL36	-49	UCL83	-55
6AU6	-20	30PL14	-66	ECF82	-82	GZ34	-48	PL81	-44	UF41	-56
6BA6	-20	35L6GT	-45	ECB36	-55	KT41	-77	PL81A	-47	UF60	-30
6BE6	-21	33V4	-25	ECH42	-59	KT61	-55	PL82	-31	UL41	-57
6BJ6	-41	35Z4GT	-25	ECH81	-29	KT66	-78	PL83	-33	UL84	-30
6BW7	-52	40C6D	-68	ECH83	-40	LN319	-63	PL84	-30	UM84	-22
6F14	-40	807	-45	ECH84	-36	LN329	-72	PL500	-63	UY41	-30
6E23	-68	AC/VP2	-77	ECL80	-35	LN389	-63	PL504	-63	UY85	-22
6F26	-63	B349	-66	ECL82	-31	N78	-87	PM84	-38	VF4B	-77
6J7G	-34	B729	-62	ECL86	-35	F61	-40	FX25	-95	W77	-43
6K7G	-19	CCH35	-87	EFL89	-38	PCB80	-34	PY32	-55	Z77	-22
6K8G	-17	CY31	-30	EF41	-60	PC86	-47	PY33	-55	Transistors	
6Q7G	-35	DAF91	-22	EF80	-23	PC88	-47	PY81	-25	AC107	-17
68N7GT	-30	DAF96	-36	EF85	-28	PC86	-42	PY82	-25	AC127	-18
6V8G	-28	DF91	-16	EF86	-30	PC97	-39	PY83	-28	AD140	-37
6V6GT	-28	DF96	-36	EF89	-28	PC90	-31	PY88	-35	AP116	-20
6X4	-23	DH77	-20	EF91	-13	PC94	-29	PY800	-34	AP116	-20
6X5GT	-23	DK32	-33	EF92	-30	PC85	-23	PY801	-34	AF117	-20
10L13	-58	DK91	-28	EF98	-65	PC98	-38	R19	-30	AF125	-17
12A8B	-296	DK92	-50	EF183	-28	PC99	-45	R20	-56	AF127	-17
12A77	-17	DK96	-45	EF184	-31	PC0189	-48	R25	-84	OC26	-25
12A7U	-20	DL35	-40	EH90	-35	PC805	-56	U26	-56	OC44	-12
6X4	-23	DH77	-20	EF91	-13	PCF80	-28	U47	-84	OC45	-12
19BG6G	-80	DL94	-47	EL34	-45	PCF82	-33	U49	-58	OC71	-12
20F2	-67	DL96	-38	EL41	-54	PCF86	-48	U52	-31	OC72	-12
20P3	-77	DY86	-24	EL84	-23	PCF800	-58	U78	-24	OC75	-12
25L6GT	-19	DY87	-24	EL90	-26	PCF801	-28	U91	-59	OC81	-12
25U4GT	-57	DY802	-33	EL95	-33	PCF802	-40	U28	-64	OC82	-12
30C1	-28	EAPC50	-32	EL98	-33	PCF805	-61	U301	-88	OC82D	-12
30C15	-58	EAP42	-30	EL500	-82	PCF805	-61	U301	-88	OC170	-28

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD  
ESSEX Tel. 01-550 7441

Minimum post/packing on 1 valve 7p, on each additional valve (3p per valve extra)

Any parcel insured against damage in transit 3p extra.



Eavesdrop on the exciting world of Aircraft Communications—  
**V.H.F. AIRCRAFT BAND**

**CONVERTER ONLY £2.85**

Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices riding tenements on talk down. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including **HEATHROW GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL.** This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables) **NO CONNECTIONS WHATSOEVER NEEDED. SEND ONLY £2.85 + 25p p & p for kit including case, nuts, screws, wire, etc. etc.** (Parts available separately.)

**SLEEP INDUCER**  
**ONLY £3.25**

Do you wake up in the night and can't get off to sleep again? Would you like to be gently soothed off to satisfying sleep every night? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether. The effect it has on people is amazingly very similar to hypnosis. All transistor. No knowledge of electronics or radio needed. Step-by-step instructions. No soldering necessary. Kit includes case, nuts, wire, screws, etc. **SEND £3.25 + 25p p & p.** (Parts available separately.)



**FIND BURIED TREASURE!**  
Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES, ETC. ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anyone from nine years of age upwards, with the clear, easy-to-follow, step-by-step, fully illustrated instructions—uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2.85 + 25p p & p.** (Sectional handle as illustrated 95p extra.) Parts available separately. Made up looks worth £15!

**ONLY £2.85**

Can be built with ease in one short evening by anyone from nine years of age upwards, with the clear, easy-to-follow, step-by-step, fully illustrated instructions—uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2.85 + 25p p & p.** (Sectional handle as illustrated 95p extra.) Parts available separately. Made up looks worth £15!

**SHORTWAVE TRANSISTOR RADIO**  
**ONLY £2.75**

Anyone from 9 years up can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3in x 4in x 1 1/2in. **Only £2.75 + 20p p & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately.)



**BUILD 5 RADIO AND ELECTRONIC PROJECTS**  
**ONLY £2.45**

Amazing Radio Construction set. Become a radio expert for £2.45. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. **Send £2.45 + 20p p & p.**

**SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON**

CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! The RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TRUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components nuts, Screws, Wire, etc., no soldering. **Send only £2.75 + 25p p & p.** (Parts available separately.)




**ELECTRONIC ORGAN**  
**ONLY £3.25**

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Fully transistorised. **SELF-CONTAINED LOUD-SPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary, simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions. **ONLY £3.25 + 25p p & p** for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

**READY BUILT AND TESTED TREASURE LOCATOR MODULE**  
**ONLY £4.95**

**FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE.** Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR. **EASILY WORTH ABOUT £20!** EXTREMELY SENSITIVE—PENETRATES EARTH, SAND, ROCK, WATER, ETC. EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN: £4.95 + 30p carr. etc.

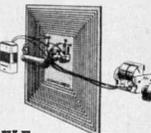

**CONCORD ELECTRONICS LTD. (PEI0U), 8 Westbourne Grove, London, W.2. Callers welcome.**

**BEDFORD ELECTRONICS**  
2 GROVE PLACE, BEDFORD  
(continuation of Lurke Street)

**MULLARD C296 POLYESTER FILM CAPACITORS**  
400V: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 2ip, 0.0068, 0.01, 0.015, 0.022, 0.033, 3p, 0.047, 0.068, 0.1, 4p, 0.15, 5ip, 0.22, 7p, 0.33, 10ip, 0.47, 12p, 160V: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 3p, 0.1, 3ip, 0.15, 4p, 0.22, 4ip, 0.33, 5ip, 0.47, 7p, 0.68, 10p, 1.0, 12p.

**MULLARD C280 METALLISED FILM CAPACITORS 250V**  
0.01, 0.015, 0.022, 3p, 0.033, 0.047, 0.068, 3ip, 0.1, 4p, 0.15, 0.22, 4ip, 0.33, 6p, 0.47, 7ip, 0.68, 10p, 1.0, 12p, 1.5, 18p, 2.2, 21p.

**CERAMIC CAPACITORS 50V (Square plaquette body)**  
E12 Series 22pF-1,000pF, 1ip, 0.0015-0.01, 2p, 0.015-0.047, 2ip.

**HIGH VOLTAGE CAPACITORS 1000V d.c. (300V a.c.)**  
0.001, 0.0022, 0.0033, 0.0047, 7p, 0.0068, 0.01, 0.022, 10p, 0.047, 0.1, 12p, 0.22, 20p, 0.47, 22p.

**ISKRA POLYSTYRENE CAPACITORS 160V, 2 1/2%**  
Values in pF: 5, 10, 15, 22, 33, 47, 56, 68, 100, 150, 220, 330, 470, 560, 680, 820, 1000, 3ip.

**SOLID TANTALUM RESIN DIPPED BEAD CAPACITORS**  
µF/V: 0.1/35, 0.22/35, 0.47/35, 1.0/35, 2.2/35, 4.7/35, 10/6.3, 10/16, 10/25, 22/16, 47/6.3, 100/3, 15p.

**MULLARD 015/016/017 ELECTROLYTICS (Replaces C426/C437)**  
µF/V: 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/63, 10/25, 10/63, 15/10, 15/63, 22/25, 22/63, 33/16, 33/40, 47/10, 68/16, 100/4, 100/10, 100/25, 150/16, 220/16, 5p, 47/63, 470/6.3, 5ip, 68/63, 330/16, 9p, 100/63, 150/63, 680/16, 1500/6.3, 11p, 220/63, 470/40, 1000/16, 15p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 18p.

RESISTORS	Type	Tolerance	Range	Values	Price each
ISKRA 1/2W	5%	4R7-2M2	E24	1p	
ISKRA 1/2W	10%	3M3-10M	E12	1p	
MULLARD 1/3W	10%	1R-3R9	E12	1p	
ISKRA 1/5W	5%	4R7-1M	E24	1p	
WIREWOUND 2.5W	10%	R22-R47	E12	9p	
WIREWOUND 2.5W	5%	1R-270R	E12	7p	
PRESETS 100R, 250R, 500R and Decades to 5M, 0.1W, 5p, 0.25W, 6p.					

Post and packing 10p on orders under £2.  
FULL CATALOGUE ON REQUEST.

**LOW COST BRIDGE RECTIFIERS**

DC output	Type Nos.	
Amps	Volts	
10	60	PM7A1
	125	PM7A2
	250	PM7A4
when mounted	375	PM7A6
15	60	PM7A1Q
	125	PM7A2Q
	250	PM7A4Q
when mounted	375	PM7A6Q

AMP tags electrically isolated from mounting bracket. Mount them on a chassis, the equipment box, transformer housing etc.

**AVAILABLE EX STOCK**  
**AEI SEMICONDUCTORS**  
AEI Semiconductors Limited  
Carholme Road Lincoln

**STEREO IC DECODER**  
HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72)  
**MOTOROLA MC1310P**  
**EX STOCK DELIVERY**

Specn. Separation: 40dB 50Hz-15kHz. Distortion: 0.3%. I/P Level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED.

**KIT COMPRISES FIBREGLASS PCB** (Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. & Instructions. Only £3.50 post free.

**LIGHT EMITTING DIODE (Red)**  
Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only 35p + p.p.

**MC1310P only £2.77 + p.p. 6p**

**Fi-Comp Electronics**  
**BURTON ROAD, EGGINOTON, DERBY DE6 6GY**




"Where can I get exclusive units at lowest prices?..."
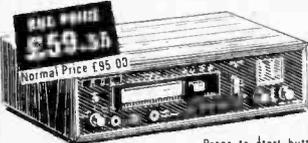
# ROC ELECTRONICS!



**ROC PRICE £10.50**  
Normal Price £15.70

**OLSON AM-357 4-WATT STEREO AMPLIFIER**  
Here's a marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 20-20,000 Hz  $\pm$  3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2 1/4" high, 4 1/2" wide.



**ROC PRICE £59.50**  
Normal Price £95.00

**8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST**  
The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual over-ride. Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed 3 1/2 ips (9.5 cms). Frequency response: playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect on a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut, including connecting leads.



**ROC PRICE £28.00**  
Normal Price £30.70

**A-3000 36-WATT SOLID STATE STEREO AMPLIFIER**  
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz ( $\pm$  2db). Inputs: Magnetic, Ceramic, Tuner, Tape, Aux. Tape Play. Size: 345mm x 300mm x 130mm.

**REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500**  
A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner, aux, mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz  $\pm$  1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono - 50db; tuner/aux - 65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



**ROC PRICE £35.20**  
Normal Price £55.50

**OLSON RA-310 AM/FM/MPX STEREO TUNER**  
This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as it's good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz; AM: 525-1605 kHz. FM Sensitivities: FM, 3uV; AM, 250uV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.



**ROC PRICE £31.20**  
Normal Price £50.00

**REALISTIC SA-100B 6-WATT STEREO AMPLIFIER**  
Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide, 3" high x 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are alled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz  $\pm$  3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.



**ROC PRICE £12.45**  
Normal Price £21.00

**EAGLE LC 07 STEREO MOVING-MAGNET CARTRIDGE**  
Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance:  $\pm$  1.5dB. Channel separation: 20dB. Compliance: 12 x 10.9 cm/dyne. ROC PRICE £6.37



**ROC PRICE £24.10**  
Normal Price £39.60

**OLSON AM-395 40-WATT STEREO AMPLIFIER**  
An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for tapping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz  $\pm$  3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3.0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!



**ROC PRICE £17.80**  
Normal Price £25.00 per pair.

**R.446 3-WAY MATCHED SPEAKERS**  
These will do justice to your amplifier - and to your pocket. At only £17.80 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.




**"WATTS" RECORD CLEANERS**  
The original "Dust Bug" Automatic Record Cleaner keeps your records like new - for perfect record reproduction. 35p

**R.307 TRANSISTORIZED STEREO PRE-AMPLIFIER**  
Now your amplifier that could only reproduce ceramic or crystal pick-up cartridges, can accept signals from moving-magnet cartridges! The R.307 steps up signals from between 5-20mV to 200-800 mV. Input: 5-20mV. Equalisation: RIAA. Output: 200-800mV flat. Frequency range: 20-22,000 Hz. Dimensions: 3 1/2" x 1 1/2" x 2 1/4". Supply: 240 Vac. ROC PRICE £4.92




**ROC PRICE £27.55**  
Normal Price £42.00

**PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16**  
This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to "Stereo"! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz; AM 525-1605 kHz. Frequency response: 50-10,000 Hz  $\pm$  3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

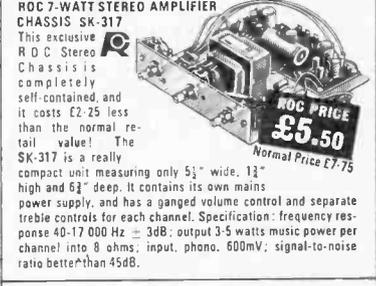

**ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317**  
This exclusive R.O.C. Stereo Chassis is completely self-contained, and it costs £25.55 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 12" high and 6 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz  $\pm$  3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 60mV; signal-to-noise ratio better than 45dB.

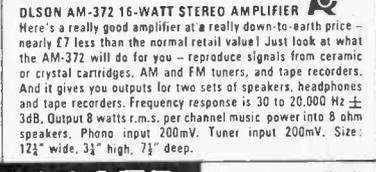

**ROC PRICE £15.10**  
Normal Price £25.20

**OLSON AM-372 16-WATT STEREO AMPLIFIER**  
Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz  $\pm$  3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

**ROCELECTRONICS LTD**  
N. JORY Esq., 193 EDGWARE RD, LONDON, W2 1ET. 01-723 8211  
CALLERS WELCOME 9-6 MON TO SAT,  
LATE NIGHT THURSDAY 7 PM

Return-of-post mail order service. Orders over £10 post free (UK only). Add 25p for p & p to orders under £10. HP terms available for callers



## BSR LATEST SUPERSLIM STEREO & MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13½ x 11½ in. Above motor board 3½ in. Below motor board 2½ in.



With STEREO and MONO XTAL £8-75 Post 25p.  
MONO-COMPATIBLE £7-75 Post 25p.  
Plays all records

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made, tested. Printed circuit. 3 watts output. Tone and volume controls. Complete with output valve and rectifier, two knobs, and high performance loudspeaker. Double wound fully isolated mains transformer. A.C. mains 200/250V. Response 50-12,000 cps. Sensitivity 300mV. £4 Post 25p

## GARRARD DISCO DECK

£10 Post Free

4 speeds. Plays all sizes of records. 4 pole heavy duty motor. 9 in. steel turntable. Plug in head complete with stereo/mono cartridge. Adjustable stylus pressure. Auto-stop. Brown and Cream finish. AC mains 110/240V. Base plate size 12½ in. 8 in. Operating area 14 in. x 12½ in. Above motor board 3 in., below motor board 2½ in. Ideal for Home Hi-Fi or Discoteque.



GARRARD AUTOCHANGERS with Sonotone Cartridges. Stereo Diamond and Mono Sapphire. Model 1025 £10. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

## BSR JUNIOR

### SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono £4-50 cartridge



HI-FI PICK UP CARTRIDGES. Diamond LP/Stereo, Stereo/Mono 9TA £2-50; GP84 £2-50; GP83 £2. Sapphire Mono GP91 £1-50; Powerpoint LP/78 60p.

## GARRARD DECCADEC SP25 Mk. II RECORD PLAYER

Single play Stereo/Mono Derram transcription head and arm. Four speeds. 10½ in. turntable. Anti-rumble filter. Bias compensation. Laboratory motor.



SPECIAL PRICE £18-50 Post 25p

## METAL FINISH AND PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position. Latest Design. Covered in black leatherette. Antimagnetic. 12½ x 14½ x 7½ in. high. Post 25p

£5-50

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH AT SAME PRICE

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES. SURFACE OR FLOORS 25p.  
BALANCED TWIN FEEDERS 80 ohms or 300 ohms. 5p yd.  
JACK SOCKET Std. open-circuit 14p. closed circuit 23p.  
Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p.  
JACK PLUGS Std. Chrome 15p; 3.5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p. CERAMIC 8p; CANS 5p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½ in. sides 6 x 4 in. 45p; 8 x 8 in. 53p; 10 x 7 in. 65p; 12 x 8 in. 85p; 14 x 8 in. 90p; 16 x 8 in. 90p; 12 x 8 in. 50p; 16 x 10 in. 21p.  
ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 9p; 8 x 6 in. 15p; 14 x 3 in. 18p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 16 x 6 in. 28p; 14 x 8 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p

## RADIO BOOKS (Post Paid)

Handbook of transistor equivalents 46p  
Radio valve guide, Book 1, 2, 3, 4, 5 (each) 30p  
Master colour code folder 13p  
Boy's book of crystal sets and simple circuits 20p  
Universal gram motor speed indicator 10p  
High fidelity loudspeaker enclosures 42p  
Practical Stereo handbook 22p  
Transistor superhet receivers 42p  
Coil design and construction manual 30p  
Radio, TV and electronics data book 28p  
Transistor circuits manual, No. 4 20p  
Practical transistor audio amplifier Book 1 25p  
Transistor subminiature receivers 30p  
Manual of transistor audio amplifiers Book 2 35p  
Resistor colour code disc calculator 10p  
Engineers' reference tables 10p  
TV fault finding 55p

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. Post PLEASE STATE VOLTAGE REQUIRED. £2 Free Details S.A.E. Size 3½ x 1½ in.

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 13½ x 11½ x 1½. Response 25 c.p.s. to 25 Kc/s. 28 db gain. Post For use with valve or transistor equipment. £10 Post Full instructions supplied. Details S.A.E. 90p 10p

NEW TUBULAR ELECTROLYTICS CAN TYPES  
2/350V 14p 250/25V 14p 50-50/350V 35p  
4/350V 14p 500/25V 20p 80-100/350V 58p  
8/450V 14p 1000/25V 35p 32-32/250V 18p  
18/450V 15p 1000/50V 47p 32-32/450V 33p  
32/450V 20p 8+8/450V 18p 350+50/325V 45p  
25/25V 10p 8+18/450V 20p  
50/50V 10p 16+18/450V 25p 32+32+32/350V 43p  
100/25V 10p 32+32/350V 25p 100+50+50/350V 48p

LOW VOLTAGE ELECTROLYTICS  
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 15p; 25V 20p; 50V 20p.  
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.  
2000mF 6V 25p; 25V 42p; 50V 57p.  
2500mF 50V 62p; 5000mF 25V 47p; 50V 65p.  
5000mF 6V 25p; 12V 42p; 25V 75p; 50V 95p.

CERAMIC, 1pF to 0.01µF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 50V 0.1µF, 0.1µF, 1µF 15p; 2mF 150V 15p. 500V 0.001 to 0.05µF, 0.1µF, 0.25µF, 0.47µF, 25p. SILVER MICA. Close tolerance 1%, 2.2-500pF 8p; 560-2,200pF 10p; 2,700-5,800pF 20p; 8,000pF-0.01, mid 30p each. TWIN GANG. "0-0" 208pF+176pF, 65p; Slow motion drive 365pF+365pF with 25pF+25pF, 50p; 500pF slow motion, standard 45p; small 3-gang 300 pF £1-60. SHORT WAVE SINGLE 10pF, 30p, 25pF, 55p, 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. 50p each Values up to 100pF. Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS 1 w., ½ w., ¼ w. 20p; 10; 2 w. 5p. 10Ω to 10M. HIGH STABILITY. 25, 10 ohms to 1 meg. 10p. Diode 5p. Preferred values 10 ohms to 1 meg. 4p. WIRE WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2½ watt, 1 ohm to 8 ohms 10p.

## MAINS TRANSFORMERS

250-0-250 80 mA. 8.3 v. 4 amp. £1-50  
250-0-250 80 mA. 8.3 v. 3.5 a. 8.3 v. 1 a. or 5 v. 2 a. £2-50  
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3  
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.: 6.3 v. 2 a. £3-25  
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2½ x 2½ in. 75p  
MIDGET 220 v. 45 mA. 8.3 v. 2 a. 2½ x 2½ in. 90p  
MINI-MAINS 20v. 100mA. 11 x 11 x 1½ in. 50p  
HEATER TRANS. 6.3 v. 3a. 25 ohms to 1 meg. 60p  
Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1½ amp. 95p  
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30v. £2-25  
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £2-25  
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £3-25  
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £8-75  
3 amp. 5, 8 and 13V £1-20  
5 amp. 5, 8 and 13V £1-20  
3 amp. 3, 5, 8, 10, 13 and 5-0-5V £1-40  
5 amp. 3, 5, 8, 10, 13 and 5-0-5V £1-40  
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 15w. £2-25; 500w. £6-25; 750w. £10; 1000w. £14.  
CHARGER TRANSFORMERS. Input 200/250V. 10r 6 or 12v. 1½ amp. £1-50; 2 amp. £1-80; 4 amp. £2-50  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1½ amp. 40p; 2 amp. 55p; 4 amp. 85p.  
LUCAS 2DS500 Bridge 70v. 5 amp £1.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3 amp. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. £10 Carriage Famous make. BARGAIN OFFER £10 50p

## WETRAD P50 TRANSISTOR COILS

RA2W Ferrite Aerial... 72p Spare Cores... 3p  
O.C. P50/1AC... 33p Driver Trans. LFDT4... 58p  
I.F. P50/2CC 470 kc/s... 38p Printed Circuit, PCA1... 58p  
3rd I.F. P50/3CC... 38p J.B. Tuning Gang... 85p  
P51/1 or P51/2... 38p Weyrad Booklet... 10p  
P50/3V... 38p OPT... 58p  
Mullard Ferrite Rod 8 x ½ in. 20p. 6 x ½ in. 20p.

## VOLUME CONTROLS 80ohm Coax 4p yd.

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 3K. S.P. Transistor 27p.  
1½ in. DIAMETER WAVECHANGE SWITCHES. 25p. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 25p each. 1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way 25p.  
TOGGLE SWITCHES. sp. 14p; dp. 18p; dp. dt. 23p.

## HI-FI STOCKISTS. RETURN OF POST DESPATCH.



## E.M.I. 13½ x 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p  
£4-25  
With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-80 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p  
£2-25

## TEAK CABINET 16 x 10 x 9in. Fluted Front £5 Post 25p

GOODMANS 6½ in. HI-FI WOOFER 8 ohm. 10 watt. Large ceramic magnet. Special Cambrie cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. £4

ELAC CONE TWEETER The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3½ x 3½ x 2½ in. deep. Rating 10 watt. 3 ohm or 15 ohm models. £1-90 Post 10p

GOODMANS 8 in WOOFER 8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. £4-50

SPECIAL OFFER! 80 ohm. 2½ in. 2½ in. 35 ohm. 2½ in.; 3 in. 25 ohm. 2½ in. dia.; 3 in. dia.; 8 x 4 in.; 8 x 5 in. £1 EACH 15 ohm. 3½ in. dia.; 6 x 4 in.; 7 x 4 in.; 3 ohm. 2½ in. 3 in. 5 in. 5 x 3 in. LOUDSPEAKERS P.M. 3 OHMS. 7 4 in. £1-25; 6 in. £1-50; 8 x 6 in. £1-60; 8 x 2½ in. £1-50; 11 x 7½; 10 x 6 in. £1-50. RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8 in. dia. 4 watt; 10 in. dia. 5 watt; 12 in. dia. 8 watt. 3 or 8 or 15 ohm models £2 each. Post 15p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kcs, 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 Kcs, 15W, 15 ohm £3. TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 95p.

TWO-WAY CROSSOVER NETWORK 3,000 c/s With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5½ in. x 4 in. with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm impedance. £1-90 Post 10p

VALVE OUTPUT TRANS. 25p. MIKE TRANS. 50.1 25p. 5 WATT MULTI RATIO, 3, 8 and 15 ohms 80p. HEAVY DUTY PUSH-PULL OUTPUT TRANSFORMERS. 50 watt £9-50 100 watt £12-50

## STEREO/MONO HEADPHONES

Model 6000 with new type slider volume controls. Stereo/Mono switch. 8 ohms. £10. High quality with tweeters and volume controls. 8 ohm. £7. Budget Model. 8 ohm. £3-25. Stereo Stethoscope 8 ohm £1-98. HEADPHONE JUNCTION BOX with switch £1-50. ACOS H.R. 1000 ohms. 53p. Mono Stethoscope 8 ohms. 53p. EAR PIECES. Crystal 25p. Magnetic 8 ohms. 15p. Magnetic 250 ohms. 23p.

## BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2½ x 6½ x 1½ in. Pre-aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100V FM input. Full instructions for any FM Tuner. Some technical experience essential. £6-50  
DIPOLE LOFT AERIAL £1-50. CABLE 4p yard.

## AM-FM/VHF TUNING GANG

Super quality small size 1½ x 1½ x 1½ in., plus spindle 1½ x ½ in. 365 + 365 pF with 25 + 25 pF. British made. Geared slow motion drive 6:1. Plastic dust cover. 6BA tapped front fixing. Cast aluminium frame. 50p Post free

# RADIO COMPONENT

Radio Books & Component Lists 5p. Written guarantee with all orders.

## E.M.I. WOOFER AND TWEETER KIT

**£5.75** POST 25p

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 in. square has a special lightweight paper cone and magnet flux 10,000 lines. With Crossover condenser.

Impedance Standard 8 ohms  
Maximum power 12 watts  
Useful Response 35 to 18,000 cps  
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in. **£9** Pos 25p

MODERN TEAK DESIGN



## 8in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts music power. **£3.75**

## TEAK HI-FI SPEAKER CABINETS


MODEL "A". 20 x 13 x 9 in. For 12in. dia. or 10in. speaker. **£9** Post 25p

MODEL "B". 16 x 10 x 9 in. For 13 x 8in. or 8in. speaker. **£5** Post 25p

MODEL "C". 16 x 8 x 6 in. For 10 x 6in. or 6in. speaker. **£4** Post 25p

LOUDSPEAKER CABINET WADDING 18in. wide, 15p 11

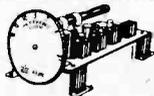BARGAIN AM TUNER. Medium Wave. Transistor Superhet **£4.50** Ferrite aerial. 9 volt.



BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. battery operated. **£3.50**



STEREO VERSION OF ABOVE £4.50.

BARGAIN FM TUNER 88-106 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. **£12.50**



BARGAIN FM TUNER **£8.85** as above less cabinet

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9 volt battery operated. **£3.50**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£2.35** Post 15p



## WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 1 1/2 x 8 1/2 x 1/8 in. Operating voltage 200/250V. a.c. 350 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying. Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seedraising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series or parallel.

ONLY **40p** EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

## BAKER 12in MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11.50**

## BAKER "BIG-SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8**  
12in. 25 watt  
3, 8 or 15 ohms. Post Free

GROUP "35" **£9**  
12in. 35 watt  
3, 8 or 15 ohms. Post Free

GROUP "50" **£20**  
15in. 50 watt  
3, 8 or 15 ohms. Post Free



## BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. **£49** Post Free



CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. Valve version. Limited number! **£55**

## Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

1/2 in. Round	88p	1/2 in. Round	88p	Key "B" for	
3/4 in. Round	75p	1 1/4 in. Round	98p	above	8p
1 in. Round	5p	1 1/2 in. Round	98p	2 1/2 in. Round	£2.05
1 1/4 in. Round	83p	1 3/4 in. Round	£1.05	2 3/4 in. Round	£2.30
1 1/2 in. Round	83p	1 3/4 in. Round	£1.05	Key "C" for	
1 3/4 in. Round	83p	1 3/4 in. Round	£1.05	above	18p
1 3/4 in. Round	88p	1 3/4 in. Round	£1.10	2 1/2 in. Round	£4.10
2 in. Round	88p	1 3/4 in. Round	£1.10	2 1/2 in. Round	£5.25
2 in. Round	90p	1 3/4 in. Round	£1.10	3 in. Round	£5.10
2 in. Round	90p	1 3/4 in. Round	£1.25	Key "E" for	
Key "A" for		1 3/4 in. Round	£1.43	above	18p
above	5p	1 3/4 in. Round	£1.50	1 1/2 in. Square	
		1 3/4 in. Round	£1.50	with key	£1.83

## SLIDER VOLUME CONTROLS



Available in both LOG and LINEAR type. Size 3 1/2 x 1 x 1/8 in. with knobs. 5K, 10K, 25K, 50K, 100K. 250K, 500K, 1 MEG. 2 MEG. **65p** EACH



E.M.I. TAPE MOTORS. 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. Size 3 1/2 x 2 1/2 x 2 1/2 in. (illustrated). Post 15p. **£1.25**

BALFOUR GRAM. MOTORS. 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/20. Size. 85p 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p

E.M.I. GRAM. MOTORS. 120V or 240V a.c. 2,400 rpm. 2-pole 70mA. **75p** Post 15p

## BAKER HI-FI SPEAKERS

HIGH QUALITY — BRITISH MADE

### REGENT

12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver. Bass Resonance 45cps  
Flux Density 12,000gauss  
Useful response 45-13,000cps  
3 or 8 or 15 ohm models




**£8** Post Free
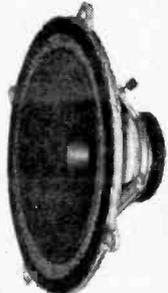
### DE-LUXE Mk II

12in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone. Bass Resonance 30cps  
Flux Density 14,000gauss  
Useful response 25-16,000cps  
8 or 15 ohms models



**£10** Post Free

### SUPERB

12in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps  
Flux Density 16,500gauss  
Useful response 20-17,000cps  
8 or 15 ohms models



**£15** Post Free

### AUDITORIUM

12in. 25 watts

A full range reproducer for high power. Electronic Guitar, public address, multi-speaker systems, electronic organs. Ideal for H-FI and Discoteques. Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 20-17,000cps  
8 or 15 ohms models



**£14** Post Free

### AUDITORIUM

15in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 3,000 cps. Ideal for Public Address, Discoteques, Electronic instruments and the home. Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 20-14,000cps  
8 or 15 ohms models



**£20** Post Free

Hi-Fi Enclosure Manual containing 20 plans, crossover data and cubic tables. 42p. Post Free.

CALLERS WELCOME CUSTOMERS FREE CAR PARK

# SPECIALISTS

(Export: Remit cash and extra postage.)

337 WHITEHORSE ROAD • CROYDON

OPEN 9-6 p.m. (WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

# 1000's OF TEST EQUIPMENT BARGAINS!



**A PROFESSIONAL DIGITAL MULTIMETER BRAND NEW AT A FRACTION OF THE ORIGINAL PRICE!**

3 digit plus polarity indicator. Its 17 positions allow it to measure in the following ranges: d.c. volts 100 $\mu$ V to 999V; a.c. volts 100 $\mu$ V to 420V; d.c. current 100 $\mu$ A; a.c. current 100 $\mu$ A. Resistance 0-1 $\Omega$  to 999k $\Omega$ . Operates from 230V 50Hz. 12V d.c. external. Dry cells or Ni-Cad batteries. Original Price £89. **OUR PRICE £55** P. & P.

## BRAND NEW DIGITAL PANEL VOLTMETERS

10mV to 1-99V, 199 measuring points. Input Z=100M $\Omega$ . Automatic zeroing. Dimensions 72mm H x 72mm W x 155mm D. Original Price £52. **OUR PRICE £24-50** P. & P.

### CANNON XLR AUDIO SERIES

XL3-11 3-pole socket (free, line mounting), XL3-32 3-pole plug (chassis mounting), £1-25 per pair

XL6-32 6-pole (chassis mounting), XL6-11 6-pole socket (free, line mounting), £1-50 per pair

XL3-32 3-pole plug, 75p each

### BARGAIN OFFER—LOW VOLTAGE STABILISED POWER SUPPLIES

\*Voltage Range 16-24V.

\*Current Range to 6A.

\*Full over-voltage and Current protection.

\*AC Ripple content better than 5mA.

These PSUs are constructed to exacting standards and incorporate the very best of components and circuit design for long life and reliability. Employs Silicon transistors, thyristors, C-Core transformer, etc. Offered in perfect condition, carefully checked before despatch. List price over £125. Our price only £26-50. Carriage £1.

### 5 MULLARD OC36 TRANSISTORS

Mounted on plug in P.C. Board. Absolutely brand new unused. Size 6 x 5 in. Our price only £1-25. P. & P. inclusive.

### 10 MULLARD GET 113 TRANSISTORS+10 diodes, resistors, etc.

Size 6 x 5 in. Brand new boards. Only 55p. P. & P. inclusive.

### HELICAL POTENTIOMETERS

STC Relcon, 10-turn, Type No. HEL/07-10/1001/A. Following values supplied ex-stock.

Res. 500 $\Omega$   $\pm$  1% 1k $\Omega$  5k $\Omega$  20k $\Omega$

All above Helicals are brand new stock. Quantities available. Price £1-25 each. P. & P. 5p for one.

Beckman Type A Helical pots. 5W. 10 turn. Resistances available. 30k $\Omega$  and 50k $\Omega$ . Brand new and boxed. Price £1-75 each.

Bournes Helical pots. Miniature type. Resistance 10k $\Omega$ . Brand new. Price £1-50.

### LUCAS POWER DIODES

Type DD 716

P.I.V. 400 max. 35A (gold plated) stud mounting. In sets of four. Only £2. P. & P. 10p.

### MULLARD FERROX-CUBES

Type LA4. Brand new boxed. Price 95p. P. & P. inc.

## AERIAL CHANGEOVER RELAYS

of current manufacture designed especially for mobile equipments, coil voltage 12V, frequency up to 250kHz at 50W. Small size only, 2 in. x 1/4 in. Offered brand new, boxed. Price £1-50, inc. P. & P.

## ADVANCE AUDIO OSCILLATOR TYPE J.I.

15Hz to 50kHz in 3 ranges. Output 0-25V into 600 $\Omega$ . In good, serviceable condition. PRICE £18-50. P. & P. 50p.

## WE SPECIALISE IN SUPPLYING NEW AND USED TEST EQUIPMENT . .

to industry, educational establishments and private enthusiasts. Whatever your requirements: signal generators, audio oscillators, frequency meters, oscilloscopes (by Tektronix and other leading makers), high and low voltage power supply units, relays (simple or special), panel meters, chart recorders, etc.—a telephone call to us could save you pounds!

# P. F. RALFE

10 CHAPEL STREET, LONDON, N.W.1

Tel. 01-723 8753

## PCB's and KITS

for designs published in P.E.  
All PCB's Fibreglass, Drilled, Roller-Tinned

### AURORA—Multichannel Frequency Controlled Sound to Light

Designer Approved PCB's and Kits  
Semiconductors incl. SCR's (1A), 8 Ch., £11-40; 4 Ch., £6-45  
R's, C's, Pots, Ferrite Cores, 8 Ch., £10-10; 4 Ch., £5-70  
Power Supply (will supply 8 channels), £2-85  
PCB (4 1/2 in x 1 1/2 in) holds Pre-amp and 4 chans. incl. pots, £1-80  
PCB (4 1/2 in x 6 1/2 in) holds PSU, Sync. Gen., 8 Ferrite Cores, 8 SCR's, £1-35

### CALLERCORD—Automatic Answering Machine

Designer Approved PCB and Kit  
Semiconductor Set, £4-80  
R's, C's, Pots, Switches, Relays, Transformer, £7-20.  
PCB (4 in x 7 1/2 in) also holds edge-con. and relays, £1-50

### DIGI-CAL-PCB's—Details on request

### DOOR BELL YODELLER

S/C's, R's, C's, Pots, £4-65. PCB (3 in x 3 1/2 in), 60p

### GEMINI PRE-AMP

PCB (3 1/2 in x 10 1/2 in) Stereo. Specially designed to also hold rotary or slider pots and rotary switches, £1-65  
R's, C's, Rotary pots and Sw's to match PCB (Stereo set), £8-55

### GEMINI 30W MAIN AMP

PCB (3 1/2 in x 5 1/2 in) Stereo £1-40. R's, C's, Pots (Stereo), £4-20

### GEMINI POWER SUPPLY

PCB (2 in x 4 in), 60p. R's, C's, Pot, £3-20

### MICROPHONE MIXER UNIT—2 Mic. and 4 High Level Inputs

S/C's, R's, C's, Pots, £2-85. PCB (3 1/2 in x 4 1/2 in) also holds pots, £1-20

### TAPE NOISE LIMITER

S/C's, R's, C's, Pot, £1-60. PCB (1 1/2 in x 3 in), 60p

### VERSATILE LIGHT EFFECTS UNIT—Single Channel Sound Controlled Light

S/C's, R's, C's, Pots, T/formers, Keyswitch. (SCR excl.), £8-55  
PCB (5 1/2 in x 5 1/2 in) also holds Pots, Sw, T/former, £1-35

Other Designs Available. S.A.E. for List. P. & P. 10p any order

## PHONOSONICS

25 Kentish Road, Belvedere, Kent. Mail Order Only

## NEW COMPONENTS

Post and Package free for orders over £1-50. Include 10p P. & P. for each single pack under £1-50.

200 Mixed Resistors, all types, 50p.

100 Mixed Modern and Miniature Resistors, 50p.

10mF 64V Electrolytic Caps, 5 for 25p; 12 for 50p.

640mF 16V Electrolytic Caps, 3 for 30p; 7 for 60p.

100 New Mixed Caps, 60p.

10mF 63V Wima non-Electrolytic, 15p each.

## TRANSISTORS

Any 6 of the following 50p or 10p each. OC71, BFY50, 2N3702, CV8615 (BS179A), NTC885.

## CONSTRUCTORS' ITEMS

P. & P. free for orders over £3-50. Half-hour timers—consisting of: 12.0/12 T/F Transistors, Diodes and Capacitors, 40p each, P. & P. 16p; or 3 for £1, P. & P. 20p.

Subminiature Omron 12V d.c. Relays. Mounted on CCT Board, 3 for 60p, P. & P. 9p. Mounted on CCT Board with components, 2 for 60p, P. & P. 7p.

G.P.O. Relays various, 200 $\Omega$ -7,000 $\Omega$ , 30p each. Uniselectors, 10 pole, 25-way, £1 each. P. & P. 25p. Dictating Machines Working with Mic. etc., £6-50. P. & P. 75p. Requiring attention, £2-50. Ideal for spares Motor, power pack, rec./play electronics.

## THIS MONTH'S HI-FI BARGAINS

Quadraphonic cartridge player with slider controls plus 4 speakers. Cartridges available. List on application, our price £100.

GARRARD SP25, SP27 Mk. 3, £11; SONOTONE 9TAHCD, £2-10;

GOLDRING G800, £8-65; GOLDRING G850, £5-70; GOLDRING G101/PT/T UNIT, £22-50.

ALL ABOVE POST FREE.

## EX COMPUTER CIRCUIT BOARDS

10 Boards, 50p, P. & P. 8p.

25 Boards, £1, P. & P. 18p.

2 Boards with 2 Power Transistors, i.e. 4 x OC28 type, 50p, P. & P. 7p.

## LAWBAK ELECTRONICS

18 High Road, Swaythling, SOUTHAMPTON

Telephone: Southampton 58479

NO HALF DAY CLOSING

**FOR RAPID SERVICE**

# GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

**TRANSFORMERS**  
all with 0-250 Volt primaries

**Miniature**  
MM6 6V, 500mA + 6V, 500mA  
MM12 12V, 250mA + 12V, 250mA  
MM20 20V, 150mA + 20V, 150mA  
£1.29 plus 13p p. & p.

**L.T.**  
LT1 6-3V, 1.5A—75p plus 18p p. & p.  
LT2 6-3V, 3A—80p plus 26p p. & p.  
LT3 12V, 1.5A—80p plus 26p p. & p.  
LT4 12V, 3A—£1.32 plus 30p p. & p.  
LT5 9-0-9V, 0.5A—75p plus 21p p. & p.  
LT6 12-0-12V, 1A—95p plus 26p p. & p.  
LT7 30-0-30V, 1A—£1.87 plus 30p p. & p.

**Multi-tapped**  
MT60/2 0-12-15-20-24-30V, 2A—£1.95 plus 30p p. & p.  
MT60/1 0-5-20-30-40-60V, 1A—£2.99 plus 30p p. & p.  
MT60/3 0-5-20-30-40-60V, 2A—£2.90 plus 34p p. & p.

**Charger**  
CT/01 1A—£1.50 plus 30p p. & p.  
CT/02 2A—£1.25 plus 30p p. & p.  
CT/03 4A—£1.50 plus 30p p. & p.  
Secondaries—0-5-11-17V.

**SEMICONDUCTORS, etc.**  
Zeners—400mW, 15p; 1-5W, 22p  
L.D.R.—ORP12, 56p  
S.C.R.—400 P.I.V., 3-0A, 57p  
Bridge rectifier—40 P.I.V., 1.5A, 50p  
Bridge rectifier—200 P.I.V., 2-0A, 50p  
Transistor sockets—6p  
D.I.L. I.C. sockets—14 pin, 25p; 16 pin, 25p  
IN4001—50 P.I.V., 1-0A, 6p  
IN4002—100 P.I.V., 1-0A, 7p  
IN4003—200 P.I.V., 1-0A, 8p  
IN4004—50 P.I.V., 1-0A, 8p  
IN4005—600 P.I.V., 1-0A, 12p

**ALUMINIUM BOXES**  
with lids and screws

Type	L	W	D	Price p. & p.
GB7*	5 1/2 in	2 1/2 in	1 1/2 in	38p 15p
GB8*	4 in	4 in	1 1/2 in	38p 15p
GB9*	4 in	2 1/2 in	1 1/2 in	38p 13p
GB10*	5 1/2 in	4 in	1 1/2 in	44p 18p
GB11	4 in	2 1/2 in	2 in	38p 13p
GB12	3 in	2 in	1 in	33p 13p
GB13	6 in	4 in	2 in	52p 18p
GB14	7 in	5 in	2 1/2 in	63p 19p
GB15	8 in	6 in	3 in	81p 26p
GB16	10 in	7 in	3 in	92p 26p

\* These sizes fit standard veroboards

**EQUIPMENT CASES**  
with sloping front panel

Type	H	W	D	Price p. & p.
SF1	2 in	5 1/2 in	2 1/2 in	45p 12p
SF2	2 in	7 1/2 in	3 1/2 in	60p 16p
SF3	2 in	9 1/2 in	4 1/2 in	75p 19p

Plain aluminium.  
Stove - enamelled silver-grey hammer finished, 20p extra.

**CONSOLE CASES**  
in plain aluminium, ideal for mixers, instruments, etc.

Type	W	A	B	C	D	Price p. & p.
GB20	8	9	3 1/2	3	1	£1.42 30p
GB21	10	9	3 1/2	3	1	£1.58 30p
GB22	12	9	3 1/2	3	1	£1.72 30p

**VEROBOARD**

Size	0-1 matrix	0-15 matrix
2 1/2 in x 3 1/2 in	22p	16p
3 in x 5 in	24p	25p
3 1/2 in x 3 1/2 in	24p	25p
3 1/2 in x 5 in	27p	29p
1 7/8 in x 2 1/2 in	75p	57p
1 7/8 in x 3 1/2 in	41p	78p

Pins—either size; packet of 36, 18p

**ELECTROLYTICS**

1µF 450V	19p	1,000µF 25V	27p
2µF 500V	20p	1,000µF 50V	39p
4µF 350V	14p	2,000µF 25V	36p
6µF 450V	16p	2,000µF 50V	53p
16µF 450V	17p	2,500µF 25V	45p
25µF 25V	7p	2,500µF 50V	60p
25µF 50V	8p	3,000µF 25V	48p
32µF 450V	24p	5,000µF 25V	55p
50µF 50V	10p	5,000µF 50V	98p
100µF 25V	10p	8-8µF 450V	18p
100µF 50V	10p	8-16µF 450V	20p
250µF 25V	12p	16-16µF 450V	27p
250µF 50V	17p	16-32µF 450V	63p
500µF 25V	18p	32-32µF 450V	49p
500µF 50V	25p	50-50µF 350V	38p

**MINIATURE ELECTROLYTICS**

1µF 63V	6p	47µF 16V	7p
2.2µF 63V	6p	47µF 25V	6p
3.3µF 63V	6p	68µF 16V	6p
4.7µF 63V	6p	100µF 10V	6p
6µF 40V	7p	220µF 16V	7p
10µF 25V	6p	330µF 16V	11p
10µF 64V	7p	470µF 10V	11p
16µF 40V	7p	1,000µF 16V	19p
30µF 15V	7p	1,500µF 16V	23p

**CASSETTE OWNERS!**

For Philips and similar cassette recorders.  
PU12 Power unit for connection to 12V + or - E car electrical systems, giving 7 1/2V, stabilised output. **£3.25**

PU14 As above but switched for 6V, 7 1/2V or 9V output. **£5.10**

PP75 Mains power supply, output 7 1/2V d.c. **£1.95**

All units are complete with cable and plug.

**VARIABLE POWER SUPPLY**

Input: 240V, a.c.  
Output: Switched 3, 4.5, 6, 7.5, 9, 12 volts d.c. at 500mA **£4.20**

**BATTERY ELIMINATORS**  
suitable for transistor radios and similar light current equipment

PP6 Input 240V a.c. Output 6V d.c.  
PP9 Input 240V a.c. Output 9V d.c.  
Price £1.50 plus 12p p. & p.

**NEW ILLUSTRATED 1972-73 CATALOGUE**  
Post Free 15p

**CONTROLS, Log. or Lin.**

Single, less switch, 15p  
Single, D.P. switch, 24p  
Tandem, less switch, 40p  
5KΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ

**SLIDER CONTROLS, 87mm.**  
complete with knobs.

Single, 44p; Tandem, 55p. 10kΩ, 25kΩ, 50kΩ, 100kΩ, log. or lin.

**RESISTORS**

Carbon  
All 5%, high-stability, E12 values. ±W, 1p; ±W, 1p; 1W, 4p; 2W, 6p

Wire-wound  
5W, 10p; 10W, 12p

**LOUDSPEAKERS**

7 in x 4 in, 3Ω—£1.12, 8Ω—£1.12, 15Ω—£1.40.  
8 in x 5 in, 3Ω—£1.85, 8Ω—£1.77, 15Ω—£1.70.  
10 in x 6 in, 3Ω—£2.32, 8Ω—£2.32, 15Ω—£2.32.  
Bin round, 3Ω—£2.10, 8Ω—£2.50, 15Ω—£2.10.  
Adastr "Hi-Ten", 10in, 10W, 8 or 15Ω—£3.40.  
Please add 20p p. & p. to all speakers.

**BONDED ACRYLIC FIBRE**  
B.O.F. wadding, 18in wide, lin thick. The ideal lining for speaker enclosures. 25p per yard.

**PLUGS**

Car aerial 14p  
Co-axial 9p  
D.I.N. 2 pin (speaker) 10p  
D.I.N. 3 pin 13p  
D.I.N. 4 pin 14p  
D.I.N. 5 pin, 180° 13p  
D.I.N. 5 pin, 240° 15p  
D.I.N. 6 pin 15p  
Jack, 2 1/2mm unscreened 9p  
Jack, 2 1/2mm screened 10p  
Jack, 3 1/2mm unscreened 8p  
Jack, 3 1/2mm screened 12p  
Jack, 4 1/2mm unscreened 12p  
Jack, 4 1/2mm screened 20p  
Jack, stereo, unscreened 20p  
Jack, stereo, screened 35p  
Phono, plastic top 5p  
Phono, plated metal 12p  
Phono, fitted 4 ft lead 8p  
Wander, red or black 3p  
Banana 4mm, red or black 6p



**SOCKETS**

Car aerial 8p  
Co-axial, surface 8p  
Co-axial, flush 10p  
D.I.N. 2 pin (speaker) 9p  
D.I.N. 3 pin 9p  
D.I.N. 5 pin, 180° 9p  
D.I.N. 5 pin, 240° 9p  
Jack, 2 1/2mm 10p  
Jack, 3 1/2mm 10p  
Jack, 4 1/2mm unscreened 15p  
Jack, 4 1/2mm screened 24p  
Co-axial 17p  
Jack, 4 1/2mm switched 15p  
Jack, stereo, switched 25p  
Phono, single 16p  
Phono, 2 on a strip 16p  
Phono, 3 on a strip 16p  
Phono, 4 on a strip 10p  
Wander, single, red or black 5p  
Wander, twin strip 7p  
Banana 4mm red, or black 6p

**LINE SOCKETS**

Car aerial 14p  
Co-axial 17p  
D.I.N. 2 pin (speaker) 15p  
D.I.N. 3 pin 16p  
D.I.N. 5 pin, 180° 16p  
D.I.N. 5 pin, 240° 16p  
Jack, 3 1/2mm 10p  
Jack, 4 1/2mm screened 49p  
Jack, stereo, screened 30p  
Phono, plated metal 14p

**CAPACITORS**

2.2pF	500V	S/M	71p	0.0027µF	500V	S/M	15p
3.3pF	500V	S/M	71p	0.003µF	500V	Cer.	5p
5pF	500V	S/M	71p	0.0033µF	1,000V	MDC	6p
10pF	125V	P.S.	5p	0.0036µF	500V	S/M	15p
10pF	500V	S/M	71p	0.0047µF	125V	P.S.	9p
15pF	125V	P.S.	5p	0.0047µF	500V	Poly.	6p
15pF	500V	Cer.	4p	0.0047µF	500V	S/M	20p
18pF	500V	S/M	71p	0.0047µF	1,000V	MDC	6p
22pF	125V	P.S.	5p	0.005µF	100V	Mylar	3p
22pF	500V	P.S.	71p	0.005µF	500V	Cer.	5p
22pF	500V	S/M	71p	0.0068µF	125V	P.S.	10p
27pF	500V	Cer.	5p	0.0068µF	500V	S/M	30p
33pF	125V	P.S.	5p	0.0068µF	500V	Poly.	6p
33pF	500V	S/M	71p	0.0082µF	125V	P.S.	10p
39pF	500V	S/M	71p	0.0082µF	500V	S/M	30p
47pF	125V	P.S.	5p	0.01µF	18V	Disc	4p
47pF	500V	Cer.	4p	0.01µF	125V	P.S.	10p
50pF	500V	S/M	71p	0.01µF	160V	Poly.	4p
56pF	500V	S/M	71p	0.01µF	250V	M.F.	3p
68pF	125V	P.S.	5p	0.01µF	400V	Poly.	3p
68pF	500V	S/M	71p	0.01µF	500V	Cer.	5p
75pF	500V	S/M	71p	0.01µF	500V	S/M	30p
82pF	500V	S/M	71p	0.01µF	500V	MDC	7p
100pF	125V	P.S.	5p	0.015µF	1,000V	MDC	9p
100pF	500V	S/M	71p	0.015µF	160V	Poly.	3p
100pF	500V	Cer.	5p	0.015µF	400V	Poly.	3p
120pF	500V	S/M	71p	0.02µF	100V	Mylar	3p
150pF	125V	P.S.	5p	0.022µF	18V	Disc	5p
150pF	500V	S/M	71p	0.022µF	250V	M.F.	3p
150pF	500V	Cer.	5p	0.022µF	400V	Poly.	3p
180pF	125V	P.S.	5p	0.022µF	600V	MDC	71p
200pF	500V	S/M	71p	0.022µF	1,000V	MDC	9p
220pF	125V	P.S.	5p	0.033µF	250V	M.F.	4p
220pF	500V	Cer.	5p	0.033µF	400V	Poly.	4p
250pF	500V	S/M	8p	0.047µF	12V	Disc	6p
270pF	500V	Cer.	5p	0.047µF	160V	Poly.	3p
300pF	500V	S/M	8p	0.047µF	250V	M.F.	3p
330pF	125V	P.S.	5p	0.047µF	400V	Poly.	4p
330pF	500V	S/M	8p	0.047µF	600V	MDC	8p
390pF	500V	S/M	8p	0.047µF	1,000V	MDC	10p
470pF	125V	P.S.	5p	0.1µF	30V	Disc	6p
470pF	750V	Disc	5p	0.1µF	250V	M.F.	4p
500pF	500V	S/M	8p	0.1µF	400V	Poly.	5p
560pF	500V	S/M	8p	0.1µF	600V	MDC	13p
680pF	125V	P.S.	5p	0.1µF	1,000V	MDC	13p
680pF	500V	S/M	8p	0.15µF	250V	M.F.	5p
820pF	500V	S/M	8p	0.22µF	160V	Poly.	6p
0.001µF	100V	Mylar	3p	0.22µF	250V	M.F.	5p
0.001µF	125V	P.S.	6p	0.22µF	400V	Foil	10p
0.001µF	400V	Poly.	3p	0.22µF	1,000V	MDC	15p
0.001µF	500V	S/M	10p	0.33µF	250V	M.F.	8p
0.001µF	500V	Cer.	5p	0.47µF	250V	M.F.	8p
0.001µF	1,000V	MDC	6p	0.47µF	400V	Foil	15p
0.0015µF	400V	Poly.	3p	0.47µF	1,000V	MDC	20p
0.0015µF	500V	S/M	10p	1.0µF	250V	M.F.	15p
0.0015µF	500V	Cer.	5p				
0.0018µF	500V	S/M	10p				
0.002µF	100V	Mylar	3p				
0.002µF	500V	Cer.	5p				
0.0022µF	125V	P.S.	6p				
0.0022µF	500V	S/M	10p				
0.0022µF	1,000V	MDC	6p				

Note:  
S/M = silver mica 1% tol.  
P.S. = polystyrene 2 1/2% tol.  
MDC—a.c. rating = 300V.  
M.F. = Mullard min. foil.  
Cer. = ceramic.

**MAIL ORDERS:** Some items have a post and packing charge shown against them. Where p. & p. is not shown the charge is 12p for any selection. When both classes of goods are ordered the charge is 12p plus 20p p. & p. charges shown. (Overseas extra.) Telephone 01-692 4412

# FERRANTI

PROFESSIONAL  
GRADE  
SEMICONDUCTORS

## New Low Prices!

All devices Top grade, Brand new, Fully guaranteed

BFS59 13p	ZTX304 19p	ZTX503 12p	ZS142 30p	KSO36A 17p
BFS60 18p	ZTX310 8p	ZTX504 39p	ZS170 9p	KSO39A 17p
BFS61 18p	ZTX311 9p	ZTX510 15p	ZS171 11p	KSO43A 17p
BFS96 13p	ZTX312 9p	ZTX530 19p	ZS172 14p	KSO47A 17p
BFS97 21p	ZTX313 10p	ZTX531 20p	ZS174 15p	KSO51A 17p
BFS98 18p	ZTX314 11p	ZTX550 15p	ZS176 21p	KSO56A 17p
ZTX107 8p	ZTX320 28p	ZTX551 15p	ZS178 34p	KSO62A 17p
ZTX108 7p	ZTX330 13p	2N3055 65p	ZS270 10p	KSO68A 17p
ZTX109 10p	ZTX331 14p		ZS271 14p	KSO75A 17p
ZTX114 20p	ZTX382 11p	<b>*DIODES*</b>	ZS272 16p	KSO82A 17p
ZTX212 12p	ZTX383 13p	ZS120 7p	ZS274 17p	KSO91A 17p
ZTX213 12p	ZTX384 16p	ZS121 9p	ZS276 23p	KS100A 17p
ZTX214 13p	ZTX450 15p	ZS122 11p	ZS278 33p	KS110A 17p
ZTX300 10p	ZTX451 15p	ZS123 14p		KS120A 17p
ZTX301 11p	ZTX500 10p	ZS124 16p	<b>*ZENERS*</b>	KS130A 17p
ZTX302 15p	ZTX501 11p	ZS140 22p	KSO30A 17p	KS150A 17p
ZTX303 12p	ZTX502 15p	ZS141 39p	KSO33A 17p	KS180A 17p

### GEMINI AMPLIFIER

Set of Main Amp. semiconductors (stereo)	£5-60
Set of Pre-amp. semiconductors (stereo)	£1-55
Set of Power Supply semiconductors	£2-15
Main amp. printed circuit board	£1-45
Pre-amp. printed circuit board	£1-95
Power Supply printed circuit board	£0-60
(P.C.B.'s are glass fibre and are roller tinned and drilled)	
Set of GEMINI TUNER semiconductors	£6-60

### P. E. ELECTRONIC PIANO

350 ZS170	£20-00	110 ZTX300	£9-50
24 ZN7474E	£14-40	14 KSO47A	£2-30

Postage & packing 10p. Free over £2. Send SAE for Ferranti data.

WE CAN SUPPLY ANY FERRANTI DEVICE. Send SAE for quotation.

DAVIAN ELECTRONICS . P O BOX 38 . OLDHAM . LANC S

## CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER  
DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

## COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY  
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY  
(WE CLOSE ALL DAY THURSDAY)  
13 SOUTH MALL, EDMONTON, N.9 803 1685

### LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high I.M.P. input this amplifier will work as a record player, baby alarm, etc. amplifier.



£1-75

### TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7 1/2 or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2 in x 2 1/2 in x 3 1/2 in. Our Price £2-75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.



### DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £22-50 + 50p P. & P. Please send S.A.E. if you require more information.



### EA1000 3 WATT AUDIO AMPLIFIER

An Audio Amplifier designed around the TAA821 Linear I.C.:-  
Supply Voltage . . . . . 9-24V  
Speaker Imp . . . . . 8-16 ohm  
Frequency . . . . . 50Hz-25kHz  
Overall Size . . . . . 2in x 3in x 1 1/2in  
Ideal Amplifier for radios, record players, stereo units, etc.  
Full technical data and diagrams with each module. All guaranteed and a bargain.



£2-63

+ 5p P. & P.

### BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a M.K. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price £2-75 plus 8p P. & P. each



### TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3 1/2in. x 1 1/2in. This converter supplies 6, 7 1/2 and 9 volt and is transistor regulated. A real money saving device for £2-50 plus 10p P.

3 volt 70 ohm.  
Single Pole Changeover . . . . . 40p plus 5p P. & P.  
Approx. size = 1 1/2in. x 1 1/2in. x 1 1/2in.

### MINIATURE RELAY



1B40K05  
Bridge Rectifier (Texas)  
Plastic encapsulated 50V  
at 4A. Approx. size 1 1/2in. x 1 1/2in. x 1 1/2in. Our Price 80p each.

### MINI LOUSPEAKERS

2 1/2in 8 ohm . . . . . 50p  
2 1/2in 80 ohm . . . . . 50p  
2 1/2in 40 ohm . . . . . 50p  
Please include 5p P. & P. each L.S.



PRINTED  
CIRCUIT  
KIT  
Everything for  
producing your  
own Printed  
Circuits. £1-40  
plus 10p P. & P.

BARGAIN S.C.R.  
Tested Thyristor.  
400V, 3amp.  
40p each. £2.  
5p P. & P.

### ADD LUXURY TO YOUR CAR

#### WITH A MOTOR DRIVEN CAR AERIAL

Spec: 5 Section  
Extended Length 100cm  
Length under Fender 40cm  
Cable Length 120cm  
Supplied complete with Fixing  
Bracket and . . . . . plus 25p  
Control Switch. £5-75 P. & P.



EMI LOUSPEAKER 450  
10W 13in x 8in ± two 2-2 1/2in  
tweeters and cross-over. All wired  
and ready for use. This ever-  
popular 450 in 3-8-16 ohm imp.  
£3-50 plus 38p P. & P. each.

### CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C80 28p, C90 38p, C120 48p plus 5p P. & P.



### PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18-50 plus 38p P. & P.



If you require more information please send S.A.E.

### HIGH QUALITY IMPORTED HEADPHONES

1,000 Ω per phone . . . . . 95p TTC  
2,000 Ω per phone . . . . . £1-05 G1105  
Plus 10p P. & P. per pair.



### CRESCENT 100W STEREO

A new style 100 watt per channel stereo amplifier. All loudspeaker systems, 8-16 ohm are suitable. This amplifier is designed for the D.J. and group who must have good looking and reliable equipment. A bargain at £82. We also have a mono 100 watt at £42. Please include £1 P. & P. and insurance. If you require more information please send S.A.E.



### 7" x 4" LOUSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in. x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1-60. Free postage on this item.



**ALMOST UNBELIEVABLE!** Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £80 radios! Test 7 days, we'll refund instantly if you are not astounded! Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day including all normal transmissions, VHF, AM, FM, MW, LW, USW, plus local & new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial, plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions & circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra). **BOX, POST, ETC. 50p.** \***BUT WAIT**, for only 55p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard 'longlife' batteries **PLUS** ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY!** Send today or call at either store.

**JUST ARRIVED!** **THIS YEAR'S NEW \* COMPUTERISED?**  
**RUSSIAN MIRACLE!**

**BRAND NEW 'SPACE AGE' model**  
—SO FAR AHEAD OF ITS  
TIME IT WILL STILL  
BE MAKING MANY  
LOOK OUT OF DATE  
IN 1984!

**THE FABULOUS**  
**ASTRAD 17**

**PORTABLE RADIO & COMMUNICATIONS RECEIVER**

**THIS OFFER ONLY £20.75!**

**WORLD WIDE RECEPTION**  
THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!



\*COMPARE ITS PERFORMANCE with **£80** RADIOS!

**28 TRANSISTORS AND DIODES!**  
**WAVEBANDS:**  
STANDARD LONG and MEDIUM  
**Plus 5 SHORT WAVEBANDS**  
**Plus ULTRA SHORT WAVES**  
(V.H.F. AM, FM, MW, LW, USW.)

**BATTERY MODEL £20.75** **BOX POST ETC. 50p**  
**MAINS/BATTERY ELIMINATOR £1.48 extra**

**FIRST TIME EVER!**  
\*NOW AVAILABLE WITH **fabulous "COMPUTERISED" WORLD TUNING GUIDE!**  
**NO MORE GUESSWORK—**  
**INSTANT DATA** at your fingertips—enables you to **TUNE IN A FLASH** to transmissions the world over!

**ANOTHER EAST EUROPEAN MIRACLE!**

**Fantastic 2-in-1 PERSONAL PORTABLE and CAR RADIO**

**NOW WORLD WIDE RECEPTION IN YOUR CAR TOO!** (RUNS OFF 12V CAR BATTERY)

Position it for **CAR RADIO**, results will justify! OR detach & use carry handle for **PORTABLE** with its own batteries!

**4 WAVEBAND VHF AM/FM/ LONG & SHORT WAVEBANDS**

**FANTASTIC PRICE £9.95** **TRY AND MATCH IT FOR UNDER £35!**  
BOX, POST ETC. 45p.

**FANTASTIC!** Brand spanking new from East Europe — we bring you this incredible 2-in-1 Radio! First class makers — because of our crazy price, contract stipulates we must **NOT** mention name! Beautifully made, 9x5x2 1/2 inches overall approx. Every up-to-date technological improvement, **15 SEMI-CONDUCTORS!** 9 Transistors, 5 Diodes and Stabiliser!

**F O U R W A V E B A N D S!** Yes, VHF model with AM/FM Long and Short wavebands! get stations around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in internal ferrite aerial plus 5 section 26in. swivel telescopic aerial. On/off/volume and tone controls. Clear Station Selector Dial. Waveband selector! Equally wonderful in CAR or HOME! **TWO** Tuning Dials for flat or upright use as illustrated. **RUNS OFF 12 VOLT BATTERY!** (AS A PORTABLE it runs on standard batteries.) **PLUG IN 12 VOLT ADAPTOR JACK PROVIDED** and automatically cut out internal batteries, using car battery only! Don't you think it's miraculous? Span the Oceans and pull in hundreds of transmissions day and night, including short wave—even in car! **BUT WAIT—** simply remove Radio from car, "snap on" optional carry handle **AND YOU HAVE A DELUXE PORTABLE**, with additional upright tuning dial. **WRITTEN GUARANTEE. ONLY £9.95** box, post 45p. \*Sprung all metal matching detachable carry handle (as illus.), batteries only 25p ex. if required. Match with sets costing £35 or more. Test 7 days. Refund if not delighted. Order by post to Uxbridge Road address, or call at either store.

**THIS FANTASTIC OFFER ONLY FROM US!** **SAVE £20.25 NOW!**

**fabulous BRAND NEW SOLID STATE** This equipment's got EVERYTHING!

**BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

**WITH REMOTE CONTROL MICROPHONE**

**OUR PRICE £23.75** **CARR. ETC. 35p** **RECOMMENDED RETAIL PRICE £44**

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!) We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V. AC line cord.) Record and play back anything, anywhere! Even tape direct from the Radio—as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: \* Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** \* "MAGIC EYE" Visual AND Battery checking recording level indicator or built-in automatic Leveller! \* Separate ON/OFF and HI-LO volume controls! \* Heavy duty built-in speaker! \* Earphone (for personal listening or "monitoring") and extension speaker sockets! \* Remote control microphone! \* Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes: obtainable everywhere. **AND** Battery checking built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player **ALONE!** £23.75, **CARR. ETC. 35p.** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send today or call at either store. Test 7 days, refund if not delighted. **BONUS OFFER:** Batteries and Cassette Tape 25p extra if required.

around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in internal ferrite aerial plus 5 section 26in. swivel telescopic aerial. On/off/volume and tone controls. Clear Station Selector Dial. Waveband selector! Equally wonderful in CAR or HOME! **TWO** Tuning Dials for flat or upright use as illustrated. **RUNS OFF 12 VOLT BATTERY!** (AS A PORTABLE it runs on standard batteries.) **PLUG IN 12 VOLT ADAPTOR JACK PROVIDED** and automatically cut out internal batteries, using car battery only! Don't you think it's miraculous? Span the Oceans and pull in hundreds of transmissions day and night, including short wave—even in car! **BUT WAIT—** simply remove Radio from car, "snap on" optional carry handle **AND YOU HAVE A DELUXE PORTABLE**, with additional upright tuning dial. **WRITTEN GUARANTEE. ONLY £9.95** box, post 45p. \*Sprung all metal matching detachable carry handle (as illus.), batteries only 25p ex. if required. Match with sets costing £35 or more. Test 7 days. Refund if not delighted. Order by post to Uxbridge Road address, or call at either store.

COMMERCIAL TRAVELLERS NOTE: Merchandising office at Holborn Store.

**SHOPERTUNITIES LTD.**

Dept. PE/21, 164 UXBIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) **BOTH STORES OPEN FROM MONDAY TO SATURDAY FROM 9 A.M. UNTIL 6 P.M.**

**That's Summer that was!!**



Summer was so late arriving this year that it nearly slipped by without our noticing it! Already we are tucking the lawn mower in for its winter hibernation, and once again "the nights are drawing in" HOORAY! —that means we can really get cracking on those electronic projects that have been buzzing around at the back of our minds.

The first step is to get the *components* lined up. And the best way to do that? Simple—get a copy of the Home Radio Components Catalogue. Then we can quickly and clearly see what we need and how much it costs. We'll know too that either by sending an order or by calling in at the Mitcham shop, we can get just what we want "off the shelf". The catalogue costs 70p, including post and packing, or 50p over the counter. Every copy contains 10 vouchers, totalling a value of 50p when used as instructed—so you can soon get back the cost of the catalogue. Over 8,000 items are listed, over 1,500 of them illustrated, and free supplements are supplied regularly to keep you up to date.

Post the coupon today, or call at our shop S.A.P.—we're open 9 to 5.30 Monday to Saturday, except Wednesday, 9 to 1.

It would help us considerably if we knew whether this was your first Home Radio Components Catalogue. If it is, please place a tick in the box.

**POST THIS  
COUPON  
with your  
cheque or  
postal order  
for 70p**

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

## Our CREDIT ACCOUNT SERVICE makes it so simple to purchase

Our customers find this service a very simple and convenient way of purchasing all their radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one

payment per month. There are several other advantages too—full details and entry forms are included in our catalogue.

**24-hr. Phone Service  
Ring 01-648 8422**



This is my first H.R. Components Catalogue

Name.....

Address.....



**HOME RADIO (Components) LTD.**

**Dept. PE, 234-240 London Road, Mitcham CR4 3HD**

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial D. BARRINGTON G. GODBOLD S. R. LEWIS B.Sc. (Eng.)  
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY R. J. GOODMAN  
Advertisement Manager D. W. B. TILLEARD

## PROBLEMS OF PROGRESS

THE pace of technical progress has become so accelerated that many interesting developments and techniques, especially in the field of integrated circuits, hardly see the light of day before their demise is threatened by yet another new development. Innovation leap-frogs innovation, and consequently valuable and thought-provoking devices become redundant long before they have been fully exploited. This poses problems to industrial users of such components, and despite crystal-ball gazing and shrewd planning ahead, many equipment makers have been caught out by this explosive state of the art.

The break-through in small calculator designs based on the single-chip i.c. is an outstanding case at this particular time. Commercial desk calculators costing in the region of £250 have been replaced overnight by new instruments selling at one third the price. Business people who purchased their calculator last year must be wringing their hands and wishing they had waited until the spring of '72. But it is easy to be wise after the event.

The same problem, although on a smaller scale, affects a magazine such as ours, catering for the private constructor. Does one sit back neglecting contemporary and readily available devices, just waiting for the "ultimate" one to turn up? For example, to have knowledge of impending changes in i.c. design that are likely to revolutionise the commercial calculator in the near future is one thing; it is quite a different thing, though, to predict with any certainty if and when these new l.s.i. chips will be made available to private individuals—and if so at what cost.

In such circumstances the P.E. Digi-Cal desk calculator was commissioned. The abundance of cheap TTL devices seemed to justify such a project being presented to the private constructor. The total cost of material for this project made it a most favourable proposition in view of the then prevailing cost of a comparable commercial instrument. However, between the completion of this design and the publication of the first article, the big break-through in cheap commercial calculators occurred.

Though "priced out of the market" the Digi-Cal remains a unique and valuable contribution to the record of design information published expressly for the benefit of private constructors and electronics enthusiasts. As an education exercise, the real worth of this project cannot be denied. Certainly it offers the technically inquisitive far more than the mere assembly of any commercial kit can possibly provide.

F.E.B.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

I.C. INTERCOM	818
NOUGHTS AND CROSSES GAME	832
P.E. ELECTRONIC PIANO—2	840
P.E. DIGI-CAL—4	848

### SPECIAL SERIES

DESIGNING WITH I.C.s	829
----------------------	-----

### GENERAL FEATURES

INGENUITY UNLIMITED	825
---------------------	-----

### NEWS AND COMMENT

EDITORIAL	817
SPACEWATCH	824
POINTS ARISING	855
NEWS BRIEFS	855
REPORT FROM AUSTRALIA	856
INDUSTRY NOTEBOOK	858
PATENTS REVIEW	861
MARKET PLACE	862
READOUT	865

### SPECIAL DATA SHEET

#### I.C. LEAD-OUT IDENTICHART

We apologise for any slight loss of quality of print in this month's issue. Supplies of the normal paper were not available due to the Docks Dispute.

*Our November issue will be published on  
Friday, October 13*

**M**OST of the cheaper intercoms on the market at the present time have a low output which can be very distorted. In order to overcome these difficulties it was decided to build a battery powered intercom using an integrated circuit chosen from the General Electric range of audio amplifiers.

The i.c. chosen was the PA234 which has a quoted output of just under one watt when working from an 18V supply with a typical distortion of three per cent. A preamplifier is needed to drive this i.c. and a simple, one transistor, common base type is used.

Even though the basic system described here is only a simple master/slave one it is very easy to extend it to master/master or master and two or more slaves, with or without call facilities; the necessary alterations for these additions are given at the end.

As no commercial cases could be found which looked right, it was decided to build these as well.

### CIRCUIT OPERATION

The amplifier circuit diagram is shown in Fig. 1. It will be seen that TR1 is connected in the common base mode which is relatively rare.

In this configuration the signal is applied to the emitter producing the advantages of low input impedance—of the order of approximately 50 ohms, and a high output impedance, thus making it ideally suited to its purpose.

The microphone/speaker is a 25 ohm loudspeaker and this is easily matched to the preamplifier stage, another advantage being that this configuration prevents inductive pickup from TV sound. Whilst experimenting with the prototype a standard high gain common emitter preamplifier was used and the TV pickup drowned all other signals.

The purpose of C1 is to filter out any TV or other radiated interference; the final version gives

no mains hum even though the cables run alongside mains leads for some distance.

The biasing for TR1 is provided by R1, R2 and C2 which ensures that the base is near earth potential as far as alternating signals are concerned. R3 serves a dual purpose in that it reduces the supply of 18V down to 9V for the preamplifier and in conjunction with C3 decouples the two stages preventing any feedback via the supply.

Potentiometer VR1 is a volume control and should be adjusted to give the best output. The signal is then fed via C4 and R4 to the input terminal, pin 3, of the i.c. The ratio of R5 to R6 is determined from the manufacturer's data sheet and controls the correct biasing of the i.c., whilst the gain is determined by the ratio R5 to R4.

The output is stabilised against oscillation by the capacitor C5, and C7 further stabilises the arrangement.

The circuit for the call oscillator is given in Fig. 2 and it will be seen that it is a conventional multi-vibrator working at about 1kHz. Other frequencies can be selected by varying R8, R9 and C8, C9.

The power supplies are two PP6 batteries connected in series to give 18 volts.


### MASTER/SLAVE SWITCHING

Fig. 3 shows a simple master/slave set up. S1 is a miniature lever key switch having four sets of changeover contacts on each side. This switch is wired so that when the key is in the central position the master loudspeaker is in the listen mode. If now S2 is operated then power is applied to the amplifier and the slave can talk to the master.

Should the master wish to call the slave then pushing the key one way the oscillator which provides the calling tone and the amplifier are both powered and the output is fed to the slave speaker.

Pushing the key the other way switches the slave to the listen position thus enabling the master station to speak. This arrangement of switching ensures that privacy is enjoyed by the slave station—the master can not easily listen in, though, if desired, by mounting S2 at the master end one can control all functions from the one position.

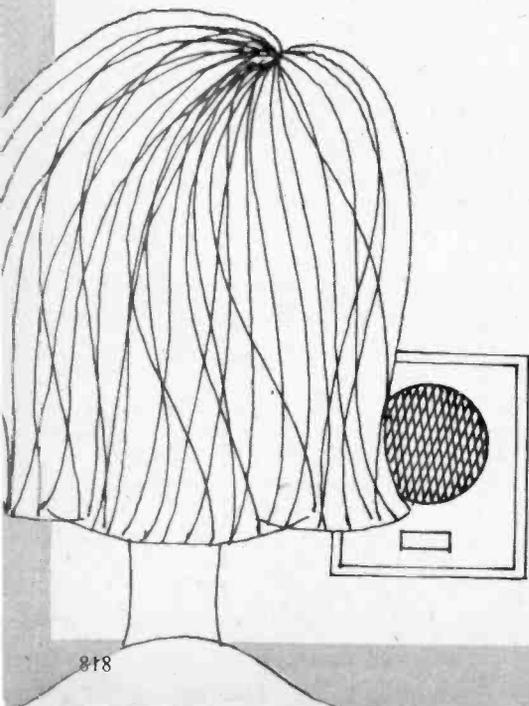The wiring of the switch is shown in Fig. 7.



# I.C. INTERCOM

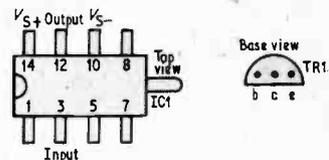
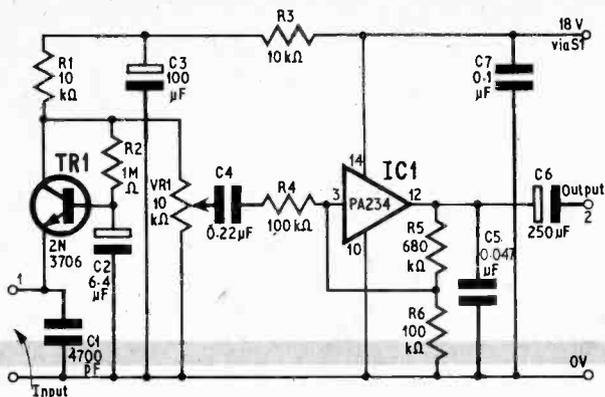


Fig. 1. Circuit diagram of the main amplifier

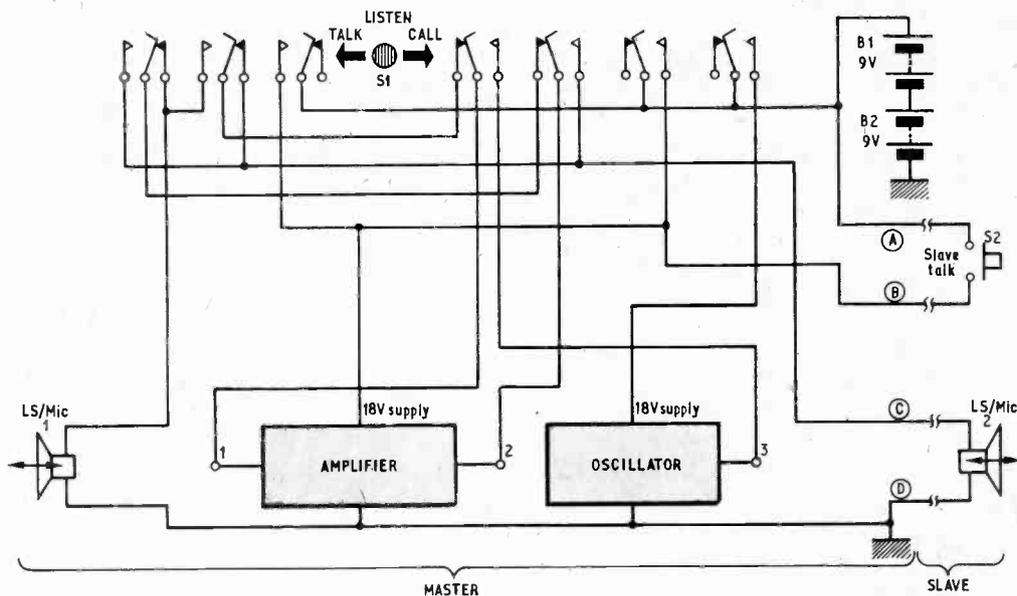


Fig. 3. Diagram showing the switching arrangement for a simple master/slave system. Only four wires connect the master to the slave (labelled A, B, C, D). Switch S2 and loudspeaker LS/MIC2 are in the slave


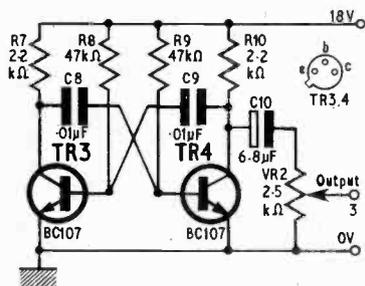


Fig. 2. Circuit diagram of the call oscillator

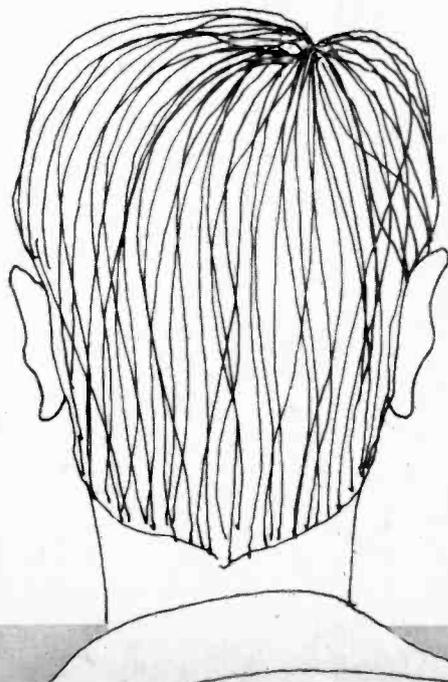

By R. A. PENFOLD

# COMPONENTS . . .

## AMPLIFIER BOARD

### Resistors

- R1 10k $\Omega$
- R2 1M $\Omega$
- R3 10k $\Omega$
- R4 100k $\Omega$
- R5 680k $\Omega$
- R6 100k $\Omega$
- All  $\pm 10\%$ ,  $\frac{1}{4}$ W carbon

### Potentiometer

- VR1 10k $\Omega$  log.

### Capacitors

- C1 4,700pF
- C2 6.4 $\mu$ F 25V elect.
- C3 100 $\mu$ F 25V elect.
- C4 0.22 $\mu$ F
- C5 0.047 $\mu$ F
- C6 250 $\mu$ F 30V elect.
- C7 0.1 $\mu$ F

### Semiconductors

- TR1 2N3706
- IC1 PA234 (General Electric)

### Speakers

- LS/MIC1, LS/MIC2 22 $\Omega$  3in (2 off)

### Switches

- S1 Miniature lever Keyswitch, 4 pole changeover in each position
- S2 Push on, release off push button

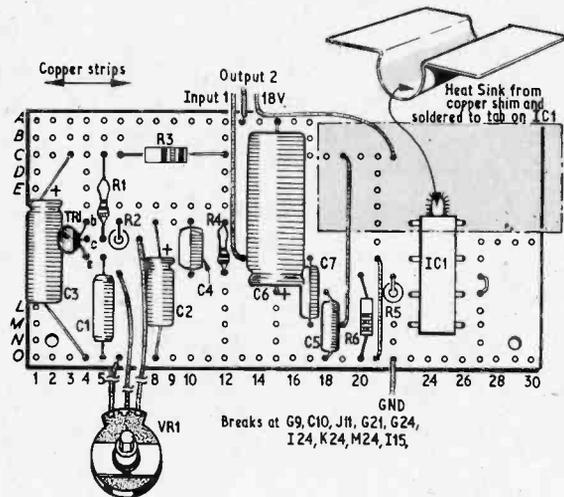


Fig. 4. Layout of the components on the amplifier board. The copper heatsink is carefully soldered to the i.c. tab

## COMPONENT ASSEMBLY

The components are mounted on 0.1-in pitch Vero-board as shown in Fig. 4 and Fig. 5, and special care is needed to ensure that no solder bridges are formed between adjacent strips. No real trouble should be encountered in the construction providing the diagrams showing the layout are followed carefully and that all breaks are made.

When soldering the i.c. in position do not leave the iron in place for too long. The i.c. needs a heat sink of at least 1 sq in and this can be made from an offcut of phosphor bronze draught strip though any copper or tin sheet will do. This heat sink, which should be bent so that it does not touch other components, is soldered directly onto the tab attached to the i.c.—take great care not to bend this tab too much or else it will break off and render the i.c. useless.


## CASE CONSTRUCTION

The case for the master station was made from 20 gauge aluminium sheet. Fig. 6 gives the various details of sizes and cuts to be made.

A number of home constructors are put off making their own cases by the thought that it is too difficult and that the finished job will look "home made". Provided that the aluminium is marked out accurately and carefully before any cuts or bends are made no difficulty should be encountered.

When all the various bits have been cut out an Abra-file can be used to cut the hole for the loud-speaker and key switch. The exact size of these will depend on the actual components obtained. The holes for fixing the key switch should be drilled at the same time.

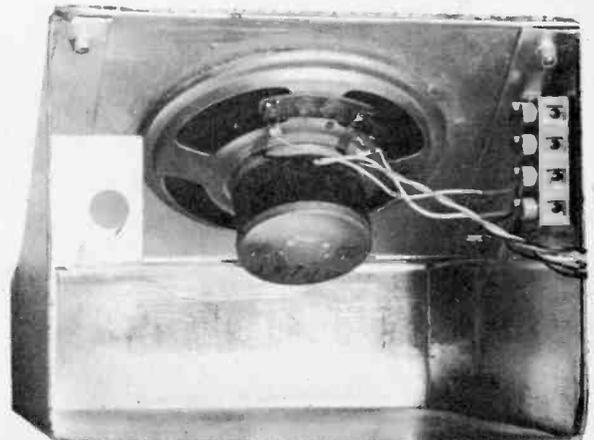The inside of the master box is seen here with the components removed from their positions. The brackets which hold the potentiometer and the call oscillator board can be seen fixed to the inside



# COMPONENTS . . .

## OSCILLATOR BOARD

### Resistors

- R7 2.2kΩ
- R8 47kΩ
- R9 47kΩ
- R10 2.2kΩ
- All ±10%, ¼W carbon

### Potentiometer

- VR2 2.5kΩ miniature skeleton preset

### Capacitors

- C8 0.01μF
- C9 0.01μF
- C10 6.8μF 35V elect.

### Transistors

- TR3, TR4 BC107 or similar

### Miscellaneous

- B1, B2 9V battery (2 off)
- 0.1in matrix Veroboard (see text for sizes)
- Aluminium for cases
- Terminal block, copper for heatsink, four way connecting wire

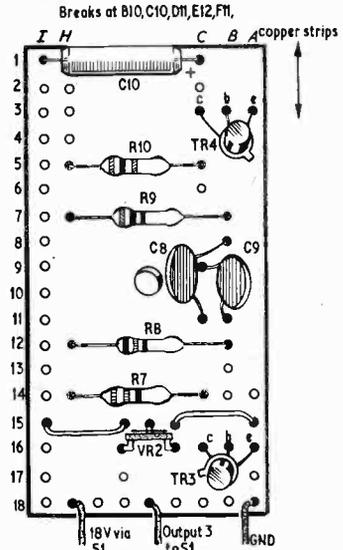


Fig. 5. Layout of the components on the call oscillator board


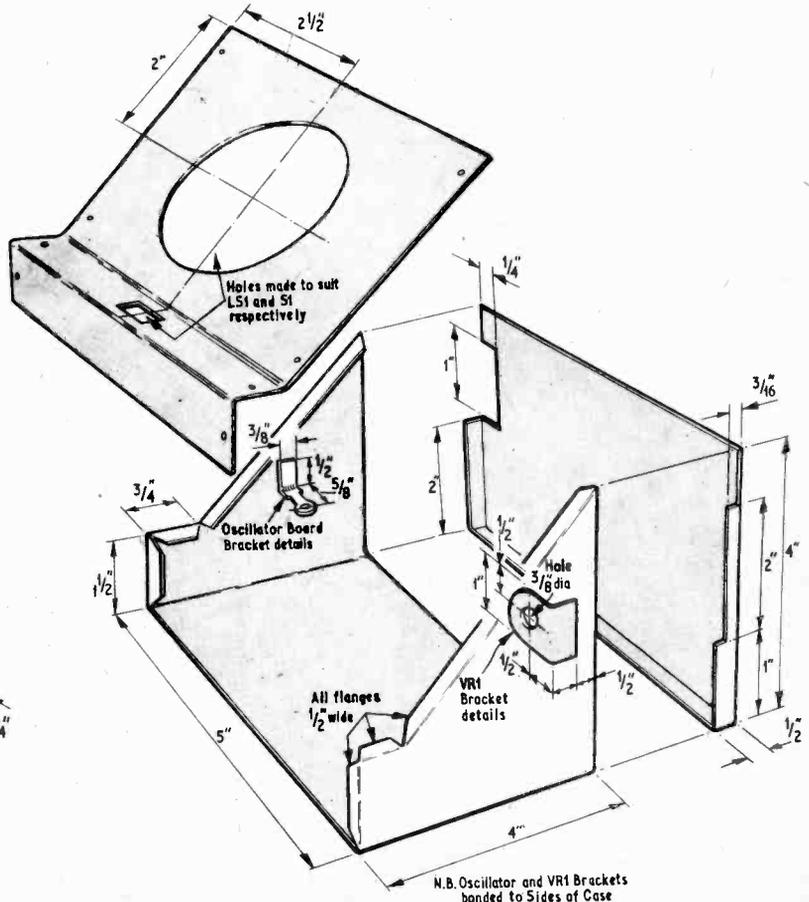


Fig. 6. Construction of the case for the master. 20 s.w.g. aluminium should be used and cut and bent to the sizes shown

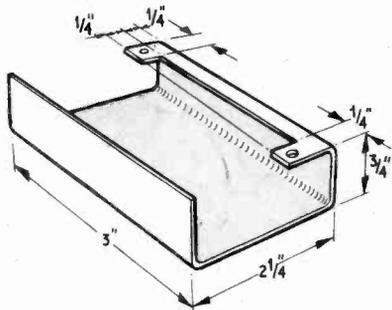


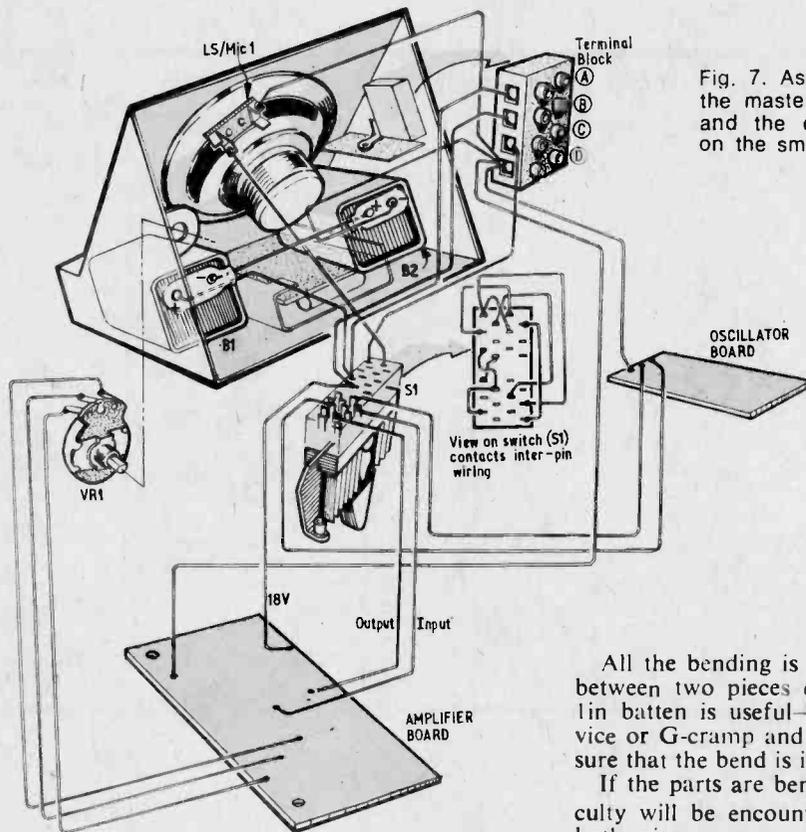


Fig. 7. Assembly and interwiring of the master box. The potentiometer and the call oscillator are mounted on the small brackets as shown

All the bending is done by placing the aluminium between two pieces of suitable sized wood—2in × 1in batten is useful—clamping the ends either in a vice or G-cramp and then carefully bending, making sure that the bend is in the correct direction!

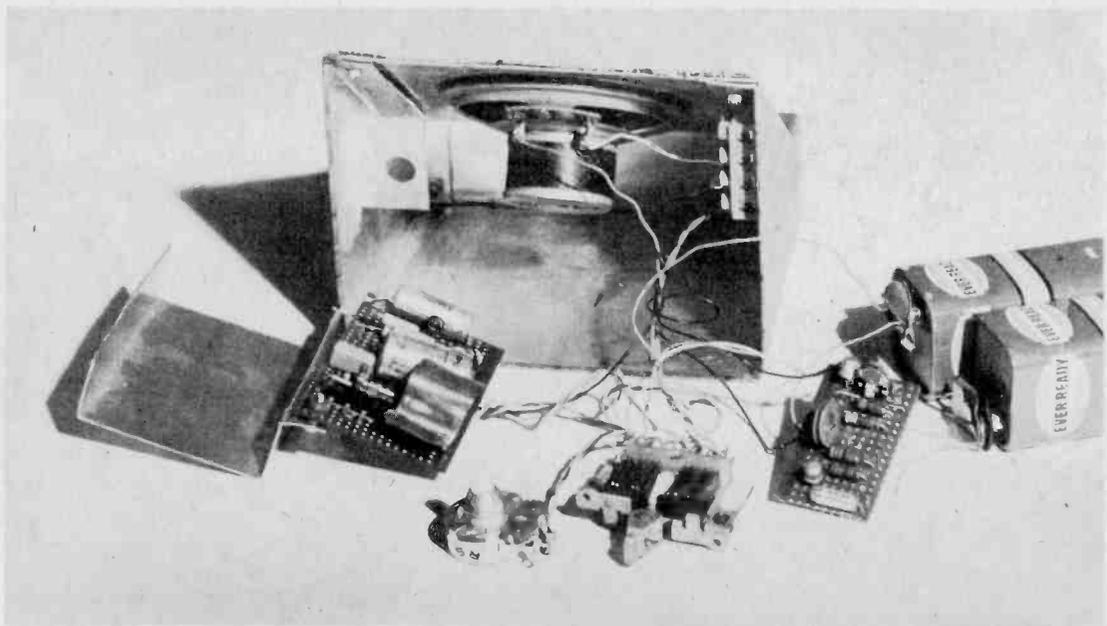If the parts are bent in a logical sequence no difficulty will be encountered with the overlaps. When both pieces are completed offer them up together and hold in place whilst you drill suitable holes for holding them together; self tapping screws or pop rivets are ideal. Then cover the sloping front with speaker cloth and the rest with Fablon or similar.



## ASSEMBLY OF THE UNIT

When fitting the switch it is necessary to wire it up first and then fit it in position.

Any offcuts left can be used to make the bracket for VR1 which is glued in position using Evostick or Araldite. Other pieces can be used to make the circuit board support. The terminal block is also glued to the inside of the case on the opposite side to VR1 as shown in Fig. 7.

The case for the slave station can be purchased, adapted from an available tin or constructed from aluminium. It should be covered in the same way as the master station.

The amplifier circuit board should then be

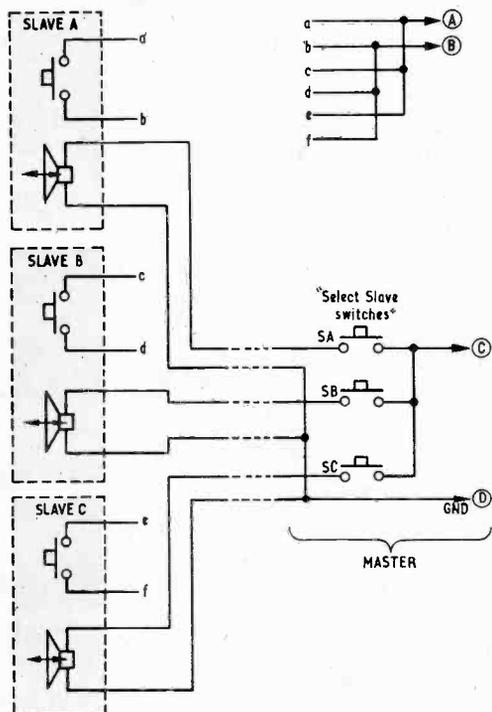



Fig. 8. Switching arrangement to give multiple slave operation, though none of the slaves has a call facility. The "select slave" switches are push buttons mounted on the master box

mounted on the bracket shown using insulating washers to ensure that the Veroboard strip is not shorted. The call oscillator can be mounted on its bracket which is then glued to the inside of the case behind the terminal block; to aid adjustment it helps if the preset on this board is easily accessible.
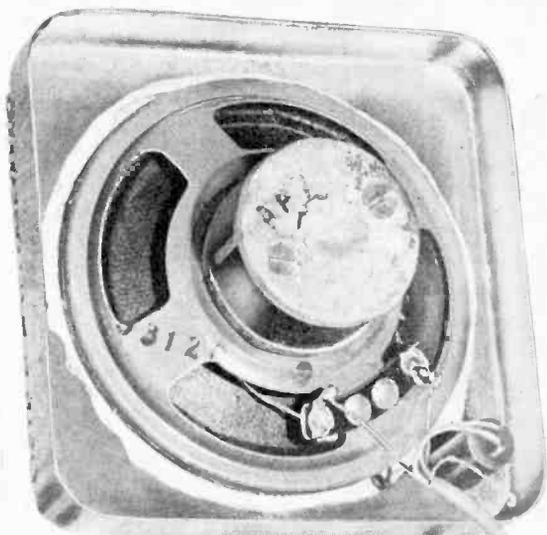
## TESTING THE FINISHED UNIT

Before commencing testing ensure that all components are in the correct position, that their values and polarities are as in the diagram and also that you have made all the breaks. Trace all wires to see that they do go to the right terminals and most important that no solder bridges are present.

When you are completely satisfied connect the external speaker and plug the batteries in. It helps




The internal construction of the slave showing the speaker and the push button in place

if a working transistor radio is placed near the slave station, when the switch is pushed one way you should hear the radio—adjust VR1 to give the best results. If testing is carried out with the stations too close together, feedback will occur giving an almighty howl.

Should you have no helper available you can short the two terminals taking power to the slave button at the master terminal block, this will be the same as pressing the "talk" button at the slave. Should there be a lot of distortion occurring when the slave talk button is pressed and the only cure is to reduce the volume you can try decoupling the two power lines going to the slave with a capacitor—say 50 $\mu$ F—connected across the appropriate terminals at the station end. When the lever key is pushed towards "call" the tone should sound in the slave speaker. The volume and quality can be adjusted to some extent by altering the value of the preset on the oscillator board.

*continued on page 839*

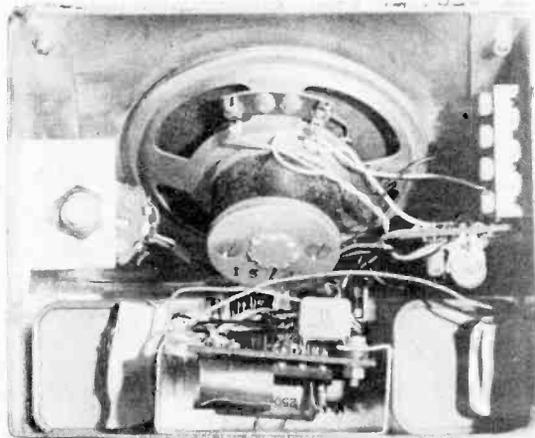

Completed master unit



## GRAVITATIONAL WAVES

Some time ago details of an experiment to detect gravitational waves by radio was described. This experiment, which was originally suggested by Dr John Jelley, made some stir when the results were reported in *Nature*. There were two series of the experiments but the results were negative. There were certain difficulties mainly due to the high level of noise on the frequency of operation.

The original paper on gravitational waves was put forward by Joseph Weber in 1969. He claimed at that time that he detected these waves as coming from the centre of the Galaxy.

The possibility of these waves was predicted by Einstein in 1916 but nothing much was attempted in the way of investigation. The principle which underlies the theory is that gravitational waves are a form of radiation which affects mass. Small displacements of mass are caused by the radiation setting up a definite vibration. If they are in line with the radiation the masses do not move with respect to each other.

Professor Weber's experiment was made with two huge aluminium cylinders deep down in the earth. Though Weber is satisfied that his results are positive, and indicate quite definitely that these waves come from the galactic centre, not all the scientific community accepts this.

## SOURCE CONFIRMED

It is, therefore, quite a move forward when independent experimenters confirm the source of the waves. Three physicists from Israel have published some work on their

experiments and it seems to be a big step forward in this field. They are using the earth itself as the detector. Its great mass is much more sensitive than arrays of discs or cylinders.

If these waves are in fact coming from a specific point in the galaxy, then using the earth as a detector, all those points in line with the waves would vibrate the earth. Since the earth revolves on its axis this particular point on the earth would show a peak of activity twice in a sidereal day.

This effect will occur every 11hr 58min and has been detected by Dr Sadeh of Tel Aviv and Dr A. Ben-Menahem of the Weizmann Institute. They have set up a seismometer in the fairly noise free area on the Gulf of Aqaba.

The team set out to discover if pulsars were the cause of the gravitational waves; pulsars are dense stars and revolve very rapidly. Since it is unlikely that they are completely homogeneous, there will be angular moments which will show as a variation of the gravitational effect. In other words there will be a certain frequency of change which could be detected.

## FIRST EVIDENCE

The first evidence that this was right thinking came in 1971. The Israeli physicists found that there was a peak in the recording which corresponded to a periodicity of 0.53-0.60 seconds. Moreover, as each day passed the event came a little earlier in time. This was a clear indication that the origin of this event was outside the earth.

The twice a day response confirmed that the position of the source was at a celestial longitude of Right Ascension 11hr 33min. This position corresponded to the pulsar known as CP 1133.

As a check on this the team have examined the radio period of the pulsar and find that their events are in agreement. According to the present model of the pulsar, the radio pulses occur once with each revolution of the star. Gravity waves however would be emitted twice every revolution. Measurements confirmed that the seismometer events did occur at twice the rate of the radio pulses from CP 1133. The actual period of the gravitational waves is 0.594 seconds.

It would seem that there is a chance for confirmation of Weber's untiring efforts in this field. Certainly the benefits to astrophysics will be very great.

## EARLY LINK-UP

It would seem possible that the planned space link-up exercises between America and Russia will be undertaken earlier than was previously expected. While the main

exercise remains set for 1975 between a *Soyuz* and *Apollo* vehicle, it is possible that a *Salyut* orbital station might be used.

The problems that have to be solved are many. Not the least of these is that of communications. The languages are different, the mode of procedures between the crews and ground will have to be rationalised to name two aspects.

There is also the problem of the airlock system. The *Apollo* atmosphere is nearly pure oxygen, at a pressure of 5lbs per square inch, while the Russians use a mixture of nitrogen and oxygen at the normal atmospheric pressure of sea level.

## LUNA-20

Some new evidence about the lunar rock formation has been brought back by *Luna-20*, the automatic probe sent by the USSR to collect samples from the Moon.

The samples came from the highland area between the Mare Crisium and the Mare Fecunditatis. The soil in this region is much lighter and contains fragments of minerals and crystalline rocks. It is rich in aluminium, calcium and magnesium oxide and the surfaces are well preserved. The iron and titanium content is less than that brought back from the actual maria by *Luna-16*.

Altogether some 70 elements have been detected in the lunar soil by Soviet scientists. They are particularly interested in the nature of the lunar iron.

It seems that the lunar iron is even more rust proof than the meteoritic iron, and attempts are being made to simulate lunar conditions on earth with the possible benefits to industry. Already some success has resulted from the sublimation of iron from basalts which have been heated to a high temperature in a vacuum.

## MYSTERY MOON

There are some rather puzzling features about Titan, Saturn's largest moon. Theoretically the gases should have boiled off, since this body has a low escape velocity.

The present low density atmosphere of molecular hydrogen and methane, from which the gases must be escaping quite rapidly into space, must have come into being long after the solar system was formed. This means that there must be a constant replenishing probably by evaporation and gassing from the solid surface.

Measurements made by L. Tafton of the McDonald Observatory suggest that there is some other major constituent in the atmosphere. It also seems probable that methane is present in the solid as well as in the gaseous state.

# INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

## TTL EQUIVALENT GATE

	A	B	output
same	0	0	0
different	1	0	1
different	0	1	1
same	1	1	0

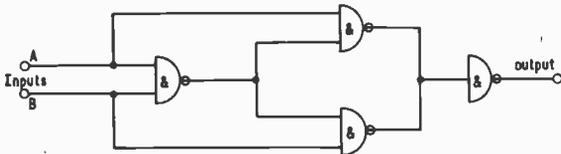


Fig. 1. TTL equivalence gate and truth table

I HAVE built and tested an equivalence gate for use in TTL circuitry, see Fig. 1. It uses one inexpensive integrated circuit package, type SN7400, a quadruple 2-input NAND gate.

If the inputs *A*, *B* are the same, the output goes low ("0" in positive logic). If the inputs are different the output goes high ("1" in positive logic), see truth table in Fig. 1.

S. L. Thompson,  
Rainham.

## VARIABLE ATTACK AND DECAY

ANY audio circuit which produces a simulation of an instrument has not only to copy the frequency and waveform produced by the instrument but also has to emulate the general shape of the envelope, because the sound produced from any instrument, when it is played, does not immediately attain full volume but is a gradual build up. It also dies away slowly afterwards. It is in this respect that most simple electronic devices are inaccurate, as they produce an envelope with virtually no rise or decay time.

The circuit shown in Fig. 1 will produce a note with a rise and decay time variable between two limits. With the values given the note produced is approximately 830Hz.

The first stage TR1 and TR2 are in the normal multivibrator configuration and the waveform which should be obtained from point A is shown in Fig. 2. Transistor TR3 is an overdriven amplifier to produce a good square wave and Fig. 3 shows the waveform that should be obtained at the output, point B. Transistor TR4 acts as an attenuator and is controlled by C3, VR1 and VR2 connected to its base.

The output from the circuit is taken from TR4 collector ( $R_L$ ), and if a resistive load is used its value should be 5.6k $\Omega$ , but other loads can be used to give different tones. An inductive load gives a sawtooth waveform and has a peculiar metallic tone. Other loads, such as capacitive, could be tried.





The envelope produced is shown in Fig. 4;  $t_r$  is the rise time, which will occur if S1 is pressed at time 0. Potentiometer VR2 gives a rise time variable between 0.50 milliseconds. The decay time  $t_d$  is controlled by VR1 and starts at point (a) in Fig. 4 and can be varied between 0.200 milliseconds.

The output should be attenuated before (if desired) it is amplified as it is in the region of 7V.

Switch S1 should be of the push-on, release-off type with position 1 normally closed and position 2 normally open. The switch should be the break-before-make type because if the rise and decay time were both set at 0, the battery could be shorted out.


N. R. Adams,  
Colehill,  
Dorset.

Fig. 1. Circuit of variable attack and decay

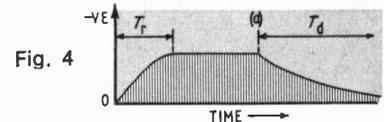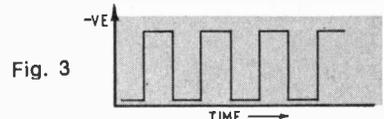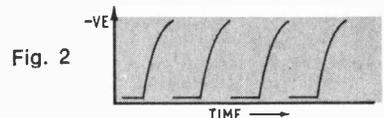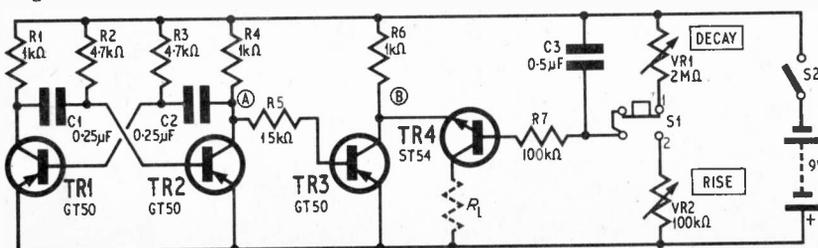



## COMBINATION LOCK

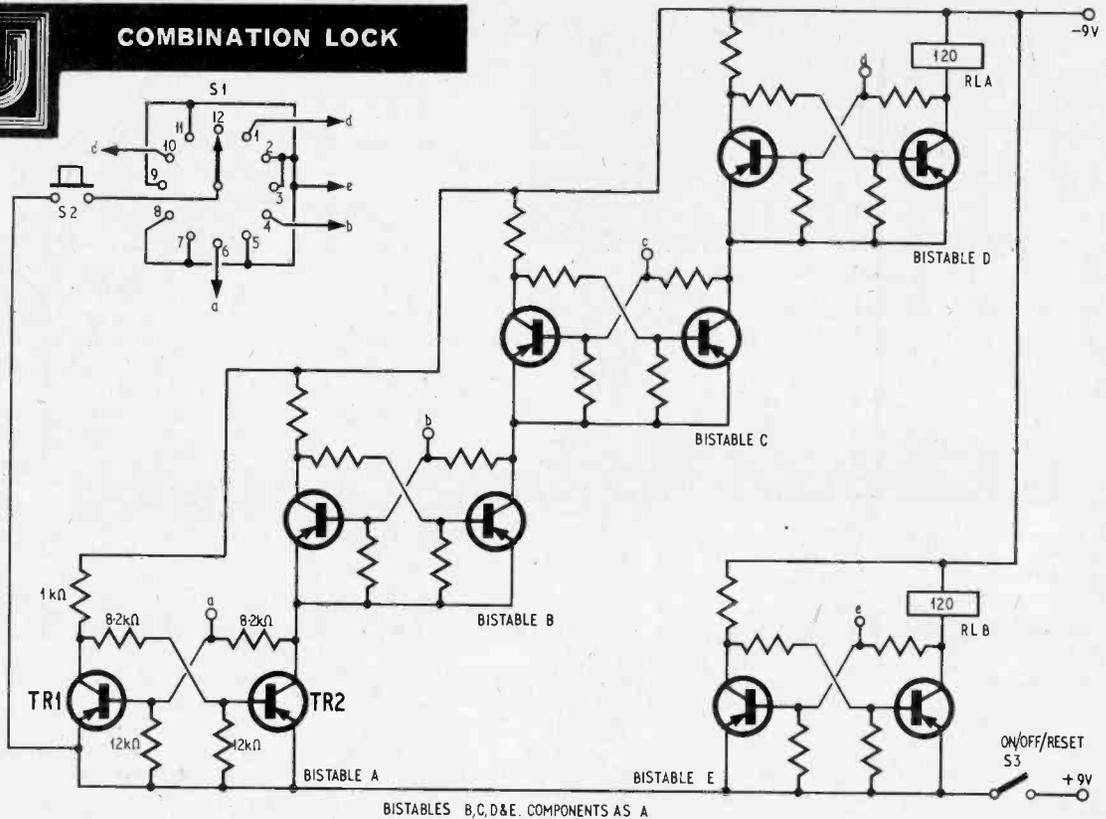

BISTABLES B,C,D&E COMPONENTS AS A

**T**HE circuit shown above is a 4-digit combination lock, against which the chances of finding the correct sequence of operation is 1 in 19,958,400, which is about 0.000 000 05, making it quite hard to pick!

Fundamentally, it consists of a four stage binary computer, the fifth stage being the alarm flip-flop which is only activated when the wrong digits are dialled. Each flip-flop, when switched, provides the power supply for the preceding flip-flop and so on up the chain until the relay is activated, and thus driving the lock mechanism.

The flip-flops of the computer are simple bistables, i.e. it has two stable states. When one transistor is conducting the other one is not. The non-conducting transistor is made to conduct by applying a pulse to the base of conducting transistor.

In the combination lock this is accomplished by shorting the base of the first transistor of each stage to the positive line. When the power supply to a flip-flop is switched on, one transistor will always conduct first. This must be the first in each stage (due to inequalities in the circuit).

Operation of the combination lock is quite simple. The first number is dialled in this case number 6, and the pushbutton switch S2 is pressed momentarily switching on bistable A. The second number is dialled and the procedure is repeated. This procedure is repeated with the last two numbers till the lock is operated.

Resetting of the bistable is accomplished by disconnecting the power supply and then reconnecting it.

G. E. Kaparnick,  
Swindon, Wilts.

## BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

### November 1968

Mr. E. J. Holt, Serenje Secondary School, P.O. Serenje, Central Province, Zambia.

### January to October 1968

Mr. M. Swire, Apt. 2K, 277 Eastern Parkway, Brooklyn, New York, 11238, USA.

### July 1968

Mr. B. J. Carling, 15 Hillary Drive, Crowthorne, Berkshire, RG11 6QF.

### March, April 1971

Mr. R. Brown, P.O. Box 926, Chingola, Zambia.

### July 1968, March 1972

Mr. N. Harvey, 47 Goffs Park Road, Crawley, Sussex, RH11 8AX.

### March 1966

Mr. N. Sherwood, 1 Aspen Grove, Scunthorpe, Lincolnshire, DN16 2EW.

### July 1967

Mr. H. Anderson, Verites, Charterhouse, Godalming.

### April 1972

Mr. R. Ellsmore-Creed, Seal House, Seal Square, Selsey.

### June, July, September 1970 and April 1971

Mr. S. T. Bartley, 41 Braemar Road, London, E13 8EH.


### September, November 1970, February 1971, February 1972

Mr. C. P. Newton, Broadmead House, Broadmead Road, Send, Woking, Surrey.
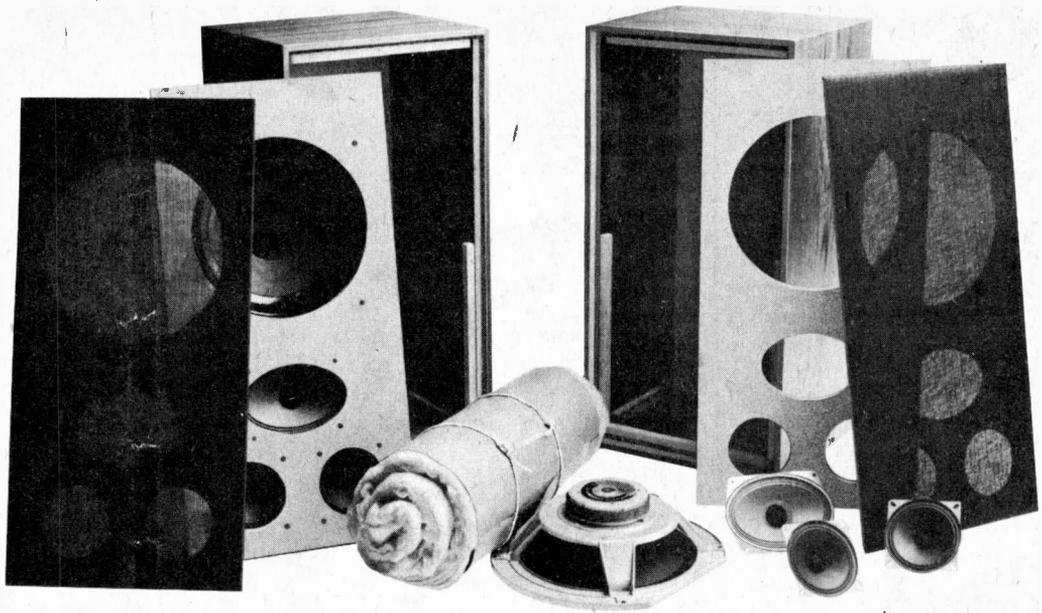
### January, February 1969, January, April 1970, January 1972

Mr. M. B. Firth, Pine Cottage, Pontardulais Road, Gorseinon, Swansea, Glam.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.



# If you want a job done properly, do it yourself.

Incredibly, almost half the money you spend on a speaker system simply goes to pay for the package it comes in: the cabinet.

As a result, if you're on a tight budget, the quality of the speaker drive unit suffers.

At Eagle, we've a simple solution to the problem, do-it-yourself.

Stereo speaker systems are easy to build and cost very little.

Yet you'll end up with the same quality as a lot of the higher priced systems you'll find in the shops. (You can even match them to your furniture.)

Have a look at the chart below and you can see how many good quality Eagle speaker drive units there are to choose from.

You'll find all full range speaker drive units come with full cabinet working drawings.\*

And all accessories come with complete installation instructions.

Once the job's done, you'll find you can go on adding to your system too.

Since all Eagle drive units are compatible, adding in a mid range speaker or tweeter is no problem.

After that, of course, you'll have nothing more to do but sit back and enjoy the music.

With the extra satisfaction of knowing there are still a few people around who can do a job properly.

## Eagle International<sup>®</sup>

Eagle International Precision Centre Heather Park Drive  
Wembley HA0 1SU Telephone 01-903 0144

MODEL	TYPE	PRICE	MODEL	TYPE	PRICE
<b>Bass/Full Range Units</b>			<b>Mid Range Units</b>		
FR4	Cone	4.90	AA12	Cone	4.23
FR65	Dual Cone	6.80	<b>High Frequency Units</b>		
FR8	Dual Cone	8.90*	CT5	Cone	1.20
<b>Crossover Networks</b>			CT10/8	Horn	2.40
CN23	2 way	1.10	CT10/16	Horn	2.40
CN28	2 way	1.10	HT15	Horn	3.50
CN216	2 way	1.10	MHT10	Horn	3.60
SN75	2 way	2.20	HT21	Horn	4.20
FF5	3 way	2.60	DT33	Dome	5.20


\*Please send me your free advance copy of full cabinet details.

Name

Address

PE 1



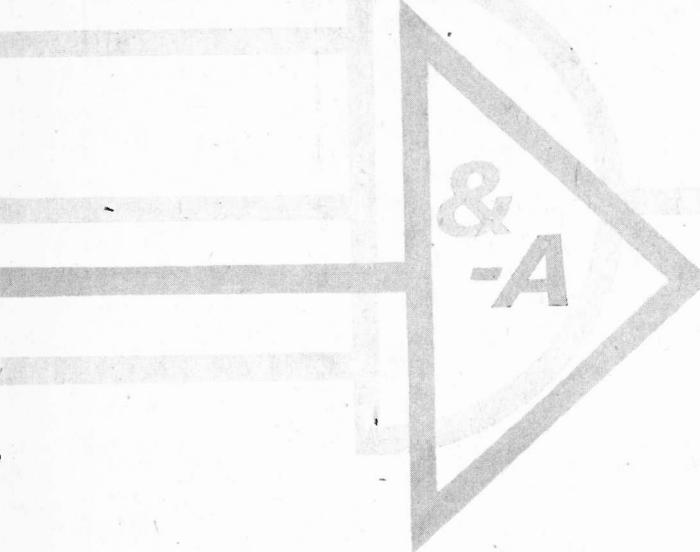

# Designing with Integrated circuits

BY A. FOORD

*A new series designed to help the experimenter to use I.C.s in practical applications. The circuits provided are not intended as definitive designs, but rather as a basis on which to experiment further.*

## 1 The 741 as an ASTABLE

THERE are literally thousands of different integrated circuits on the market, and it would take every page of every issue of the magazine to make any impression in reviewing the complete field. Integrated circuits can be divided into two very broad categories, those intended for general applications and those designed with a specific function in mind.

The state of the art is such that many integrated circuits are so complex as to prohibit experimentation. Those for TV signal processing, for example, cannot adequately be used unless we are prepared to rewire a TV! Where appropriate such i.c.s usually appear in constructional articles.

In general research and development a selection of TTL and a few linear circuits allows much "routine" work to be achieved quickly. Manufacturers short form catalogues show where to go for "state-of-the-art" circuits if they become necessary.

Rather than extract up to the minute information from data sheets and application notes, we hope to show how the "standard" integrated circuits can be used in many cases. We will place the emphasis on designing circuits using integrated circuits and not necessarily on reviewing a different one each month. We feel that this is more useful for the reader who wishes to experiment because he will often be able to use the same integrated circuit more than once.

Readers requiring further details of individual i.c.s and their performance, are recommended to consult manufacturers' data sheets.

### OPERATIONAL AMPLIFIERS

The first generation of linear integrated circuits were the  $\mu$ A702 and 709 operational amplifiers and the 710

comparator. Both the 702 and 709 have their own disadvantages. The 702 has the limited input voltage range of +1.5V to -6V and can "latch up" if this is exceeded. It can however be used for many feedback applications from d.c. to 30MHz.

The 709 is an improvement on the 702's performance by providing a higher input impedance, a large input common mode range of  $\pm 10$ V and a high output swing. It has its own characteristics (cross-over distortion, for example) and is not short-circuit proof. It can be used for high performance applications from d.c. to 5MHz or so.

Both the 702 and 709 require several external components to provide frequency compensation so that they are stable under closed loop conditions, and do not become unstable when overall feedback is applied. This compensation can be chosen to obtain the best bandwidth for a given closed loop gain.

The first of the "second generation" of integrated circuits was the  $\mu$ A741 which overcomes many of the disadvantages of the 702 and 709 series. It is very suitable for general work where a wide bandwidth and a fast slew rate are not required.

This month we introduce the 741C amplifier and will use it again later in the series. Although it is convenient for demonstration purposes its bandwidth restricts its use and the 702 or 709 circuits can be used, within their limitations, when we wish to work outside the frequency limit of the 741.

The 702, 709, 741 integrated circuits are available, under slightly different numbers, from many manufacturers. (Some guidance on these numbers can be seen in the table on the P.E. I.C. Identichart in this issue.)

**THE 741C OPERATIONAL AMPLIFIER**

The 741C is a high performance operational amplifier intended for a wide range of analogue applications from d.c. to 1MHz. Its high common mode range and absence of "latch up" make it ideal for a voltage follower.

It requires no external components for frequency compensation and is stable under closed loop conditions including unity gain and integrator applications. It is protected against an indefinite short circuit to ground or to either supply rail. The input offset voltage is typically 2mV and this may be nulled by a simple circuit.

Its connections are shown in the diagrams for the various package outlines. Typical parameters are shown in the Table 1.1. Versions without the "C" suffix have slightly improved parameters, such as working temperature range.

**LOW FREQUENCY MULTIVIBRATOR**

To start the series, let us look at the 741 wired in an astable multivibrator configuration. Although not necessarily the best application for the 741, it does illustrate how very simple the external circuitry of an i.c. can be to provide a useful application.

Fig. 1.1 shows a basic astable multivibrator suitable for generating a fixed frequency square wave for test purposes. It has a negative feedback loop from the output to the inverting input via R3 and a positive feedback loop from the output to the non-inverting input via R1 and R2. The circuit changes state regeneratively each time the two inputs are at the same potential.

If we assume that the circuit is operating and that the output has just switched to +V<sub>o</sub> (the positive saturated output level) then the voltage V<sub>1</sub> at the non-inverting input (marked +) will depend on R1 and R2. The voltage V<sub>2</sub> at the inverting input (marked -) will be rising exponentially towards +V<sub>o</sub> from an initial negative value.

Let constant  $k = \frac{R_1}{R_1 + R_2}$  Initially  $V_1 = +kV_o$   
 $V_2 = -kV_o$

When V<sub>2</sub> reaches V<sub>1</sub> the amplifier will change state with the output switching to -V<sub>o</sub>, V<sub>1</sub> switching to -kV<sub>o</sub>, while V<sub>2</sub> now falls exponentially towards -V<sub>o</sub> from its initial value of +kV<sub>o</sub>. When V<sub>2</sub> reaches V<sub>1</sub> (which is now -kV<sub>o</sub>) the circuit changes state again and the cycle repeats.

**Table 1.1: Typical Characteristics of the 741C**

Large signal open loop gain	100dB
Input resistance	1 Megohm
Differential input offset voltage	2mV
Differential input offset current	30nA
Input voltage range	±13V
Maximum output voltage swing	±13V
Common mode rejection ratio	90dB
Input bias current	200nA
Output resistance	75 ohms
Supply voltages	±15V
Slew rate at unity gain	0.5V/μs

**ANALOGUE COMPUTING** Computing system where continuous signals represent mechanical (or other) parameters.

**COMMON MODE REJECTION RATIO** A common mode input is one applied to both inputs of an operational amplifier. In theory this should produce no output, since only the difference between the inputs is amplified. The CMRR is a measure of this rejection to a common input signal, and should be large.

**COMPARATOR** An amplifier designed for comparing two inputs and giving a 0 or 1 output. Usually the output is compatible with logic levels.

**DIFFERENTIAL INPUT** An input applied between two terminals, neither of which is at earth potential.

**DIFFERENTIAL INPUT RATING** The maximum differential input which may be applied between the two terminals.

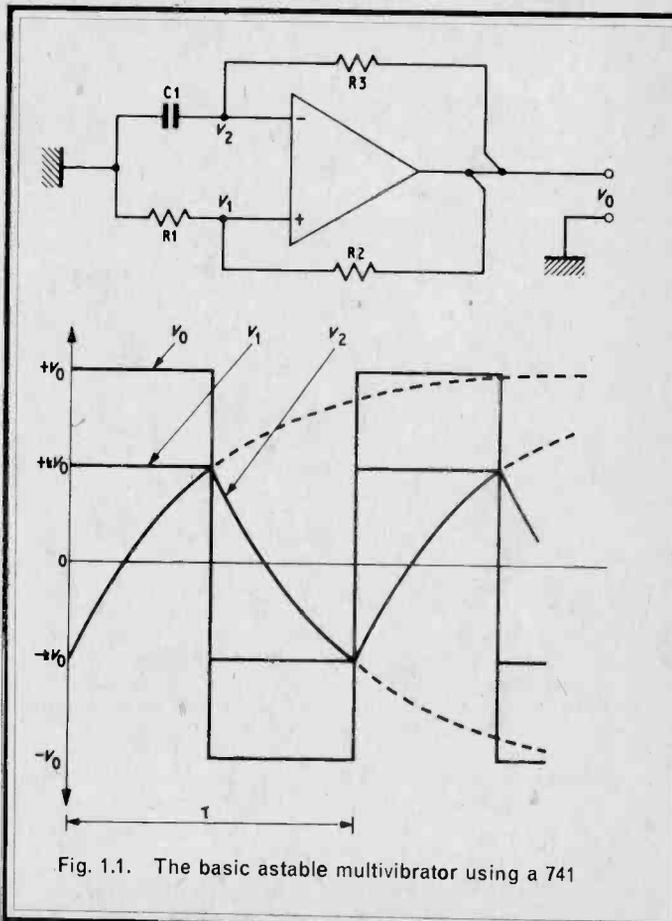


Fig. 1.1. The basic astable multivibrator using a 741

**DIGITAL COMPUTING** Computing system where two valued signals represent mechanical (or other) parameters.

**FREQUENCY COMPENSATION** The compensation required in feedback amplifiers to ensure stability and prevent unwanted oscillations.

**INPUT COMMON MODE RANGE** The maximum input which can be applied to either input without causing damage or abnormal operation.

**INPUT OFFSET CURRENT** The difference in input bias current requirements for the two inputs.

**INPUT OFFSET VOLTAGE** That voltage which must be applied between the input terminals to obtain a zero output voltage.

**INTEGRATED CIRCUIT** An electronic device containing several elements, active or passive, which perform all or part of a circuit function.


**LATCH UP** The switching of an electronic circuit to an unintended mode by improper voltage application.

**OFFSET ERRORS** Errors produced by input offset voltage and input offset current.

**OPEN LOOP GAIN** The gain of an amplifier before negative feedback is applied.

**OPERATIONAL AMPLIFIER** Originally a direct coupled high performance amplifier used in analogue computing to perform mathematical operations (summation, scaling, subtraction, integration, etc.). Today a low frequency packaged amplifier (about d.c. to 1MHz)

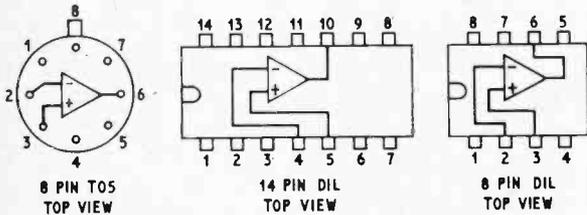**SLEW RATE** The maximum rate of change of the output voltage for large signals. Usually in  $V/\mu s$ .



Basic connections (looking at top) of inputs and output for the 741. For details of other connections, see the I.C. Lead-out Identichart

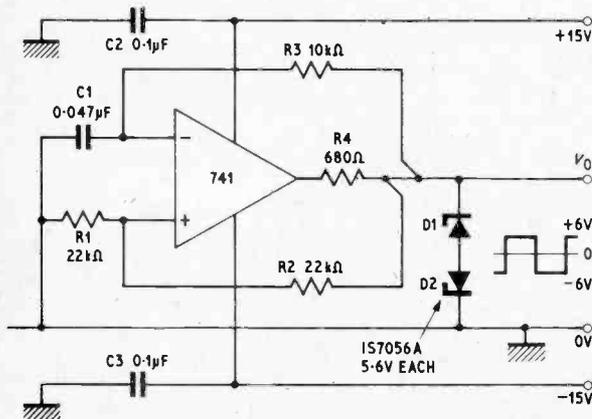


Fig. 1.2. A practical circuit for 1kHz operation

## PERIOD OF OSCILLATION

If we assume that the inputs of the amplifier draw no current and that the positive and negative saturation levels are equal, then the period of oscillation is given by:

$$\tau = 2C_1 R_3 \log_e \left( \frac{1+k}{1-k} \right)$$

For  $R_1$  equal to  $R_2$ , this becomes  $\tau = 2.2C_1 R_3$  secs.

Although there is no need to do so, it is convenient to make  $R_3$  equal to the parallel combination of  $R_1$  and  $R_2$  to minimise offset errors. The maximum allowable value for  $k$  depends on the differential input rating of the amplifier. For the 741, values for  $k$  of up to 0.9 are suitable. For a 709 with  $\pm 12V$  supplies a  $k$  of 0.2 would be used.

## PRACTICAL CIRCUIT

A practical circuit for a nominal 1kHz operation is shown in Fig. 1.2. The Zener diodes clip the output level at  $\pm 6V$  to aid slew rate slightly. The measured frequency was 844Hz. This is 13 per cent lower than the nominal value, probably due to the 20 per cent tolerance of the capacitor.

Rise and fall times were  $10\mu s$ , equivalent to a bandwidth of 35kHz. Although this is noticeable for a 1kHz square wave, it is still good enough for simple audio testing to illustrate the effects of tone controls, instability and ringing, or filters. For higher frequencies a 709 can be used with a value of 0.2 for  $k$ .

At frequencies lower than 1kHz, or if slightly longer rise and fall times can be tolerated, the Zener diodes may be removed and  $R_4$  shorted out, so that the circuit relies on the symmetrical limiting characteristics of the amplifier.

**Part 2 Next month: Introduction to basic logic gates**

# NOUGHTS & CROSSES

By R. K. Johnson B.Sc.

*A novel entertainment for parties and fêtes*

**N**OUGHTS and crosses is a simple but fascinating game whose rules can be understood even by young children. Two players alternately place noughts and crosses in a three by three grid in an attempt to obtain a complete line of their own symbol either diagonally, horizontally or vertically.

With this machine the player is given the advantage of starting first and makes his play by using a pen to "write" a nought on to a colourful illuminated screen. The computer instantly replies by displaying a cross. Two anti-cheat devices are included to foil baffled players.

Most of the 945 different games that can be played against the computer will be drawn or lost, but in two per cent of the games the player can get three noughts in a line. Finding these winning

games is not easy and presents an interesting problem in logic for the player. Schoolchildren will play for hours trying to find one or more ways of beating the computer.

## ANALYSIS OF THE GAME

The object of the game is to obtain a row (horizontally, vertically or diagonally) of three noughts, while preventing the computer from obtaining a row of three crosses.

In the usual game using pencil and paper the first player has a choice of nine places, his opponent then has a choice of eight places, and so on. Thus there are  $9 \times 8 \times 7 \times 6 \times 5 \times 4 \times 3 \times 2 \times 1 = 362,880$  ways of filling the places. Though not all of these represent interesting games, the number is too large for a simple computer and so must be reduced.

This is done by allowing the player any choice of position, but limiting the machine to just one reply. The total is then  $9 \times 1 \times 7 \times 1 \times 5 \times 1 \times 3 \times 1 = 945$  possible games, a number which allows simplified circuitry but still provides variety of play.

For further analysis of the game the squares are numbered 1 to 9 as in Fig. 1.


Square 5 is the most important because it controls four of the eight possible rows of three. Squares 1, 3, 7 and 9 each control three rows. Least important are squares 2, 4, 6 and 8 because each can only block two rows.


## TACTICS OF THE MACHINE

The first basic principle of play is that if the player's first move is in one of squares 1, 2, 3, 4, 6, 7, 8 or 9, then the computer's best reply is square 5. If the player's first move is square 5, then the computer's reply should be either 1, 3, 7 or 9, but in practice it is made to be always square 1.

The player's first move determines the computer's reply for each successive move in that game. These moves and the corresponding replies are shown in Fig. 2(a) to (i).

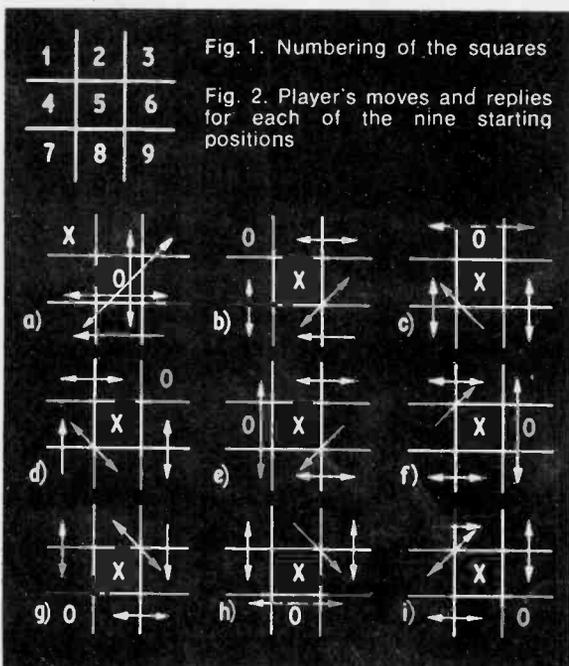Consider Fig. 2(a). The player has started with square 5 and the computer has replied with square 1.



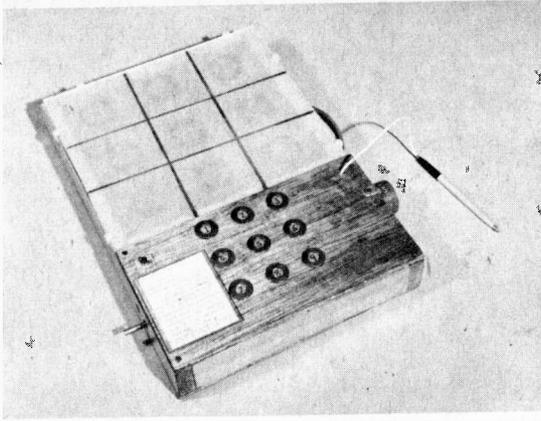

The completed prototype showing the general appearance of the unit with the "how to play" notice in position

The double-headed arrows indicate reversible positions; for example if the player plays square 2 the computer answers with square 8 (to block the row), while if the player plays square 8, the computer replies with square 2 (to block the row).

This illustrates the second design principle: when the player fills in a second "0" in any line, the computer should block the line with an "X".

It will be seen in Fig.2(a) that one of the arrows is single-headed indicating an irreversible play. If the player plays square 9 the reply is square 7, whereas if square 7 is played the reply is not square 9, but square 3.

This illustrates the third principle: if the player is just about to start a line of "0"s, the computer should reply with a second "X" in a line so as to force the player on to the defensive.

If these three principles are followed in the usual pencil and paper game then the player cannot lose.

Possible moves and replies for the eight other starting positions can be followed by reference to Figs. 2(b) to (i).

### INPUT UNIT

The player makes each move by touching the pen to one of nine 1in diameter brass washers (corresponding to the nine squares). Each washer is connected to the gates of two thyristors (SCRs).

When a washer is touched, one of these thyristors switches on a lamp indicating the player's "0", and the other thyristor, by means of the memory store, switches on the computer's reply "X".

Once on, the thyristors will stay on until the power supply is interrupted. Thus the use of thyristors has the important advantage that once a move is made, it cannot be changed either accidentally or deliberately. If toggle switches were used instead, players could cheat by flicking the switches to find the best move at each stage.

Fig. 3 shows the circuit diagram for these thyristors and Fig. 4 shows how they may be mounted on a piece of Veroboard. Eighteen 50 p.i.v. 1A SCRs were used in the prototype, but thyristors with other ratings may be used providing they are all of the

same type to ensure that the lamps light equally brightly.

Also needed for the input unit is the pen and a resistor which may be fitted inside the pen. The resistor should be the highest value that will give reliable triggering of the thyristors. A 150 ohm 1/4W resistor was suitable in the prototype.

The pen is a plastic ballpoint of the kind that unscrews in the middle and has a retracting button at the top end. With the ink tube and button removed, flexible cable may be led in at the top hole, knotted, and soldered to the resistor which in turn is soldered to a thick wire which is then soldered or glued with "Araldite" epoxy resin, so as to protrude through the lower hole as in Fig. 5.

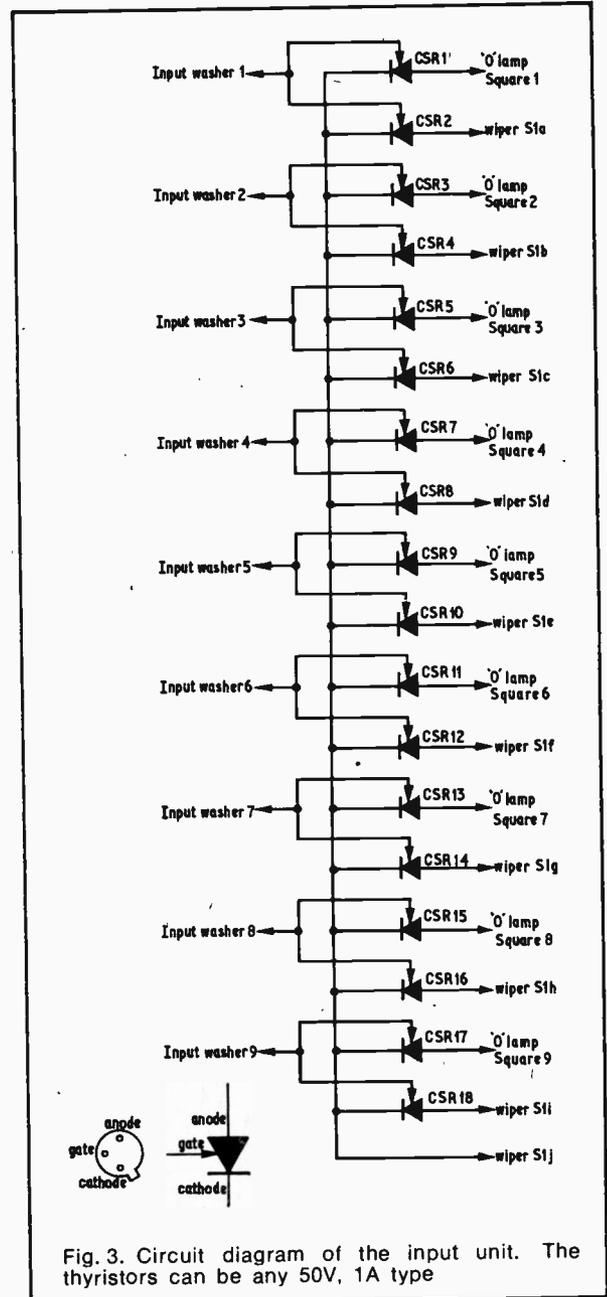


Fig. 3. Circuit diagram of the input unit. The thyristors can be any 50V, 1A type

# COMPONENTS

## Resistor

R1 150Ω ¼W carbon (see text)

## Thyristors

CSR1-CSR18 Any 50V 1A type (18 off)

## Switches

S1 10 pole 10 way wafer switch (1 wafer must be a break-before-make type)

S2 Push-to-break push button switch

## Lamps and holders

LP1-LP18 M.E.S. lamps and holders (for voltage ratings see text) (18 off)

## Miscellaneous

1in dia. brass washers (9 off), ballpoint pen, large knob, mirror clips (6 off), two pieces of glass or Perspex, plywood or hardboard, 2in×1in softwood, red and green cellophane or cinemoid, tracing paper, Araldite (for details of these materials see text), 5in×1½in 0.15in matrix Veroboard

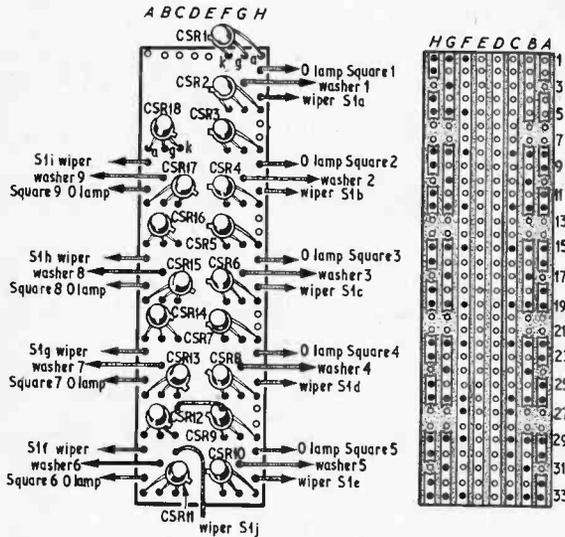


Fig. 4. Layout of the thyristors on the Veroboard panel


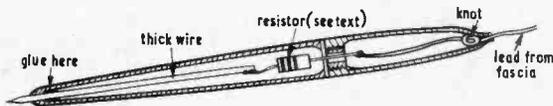


Fig. 5. Internal construction of the "pen"

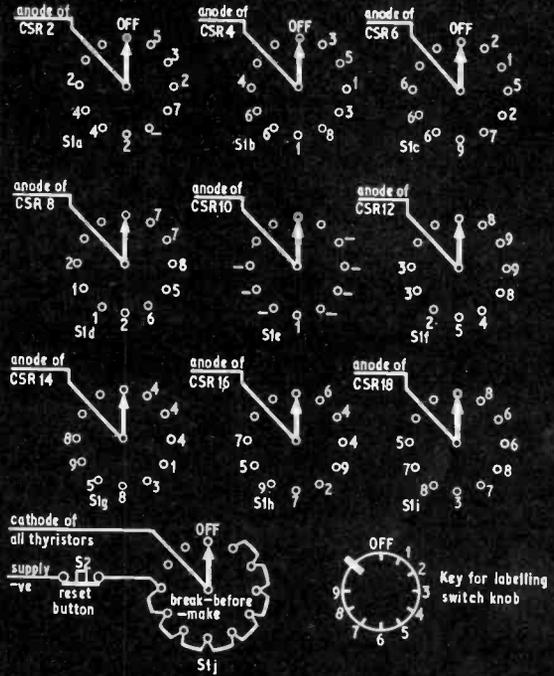

## MEMORY SWITCH

The memory switch consists of a 10 pole 10 way wafer switch. One way is used as an "off" position and the other nine positions of the switch are used to set the initial play number (i.e. select the required programme).

Nine of the wafers are used to route current to the correct lamps and the tenth wafer forms another anti-cheat device. This tenth wafer must be "break-before-make" type. This ensures that if a player tries to cheat by turning to a different programme part way through a game, the power supply to the thyristors is cut off momentarily and the display unit is wiped clean.

Fig. 6 shows the ten wafers. Wafers S1a to S1i must be wired together by reference to the numbers shown round each wafer in Fig. 6. All the contacts marked "1" must be wired together (for connection later to the "X" lamp in square 1 of the display unit). Similarly all the contacts marked "2" are wired together (for connection later to the "X" lamp in square 2 of the display unit), and so on. Great care should be taken at this stage to ensure correct wiring.

All except one of the contacts of wafer S1j are wired together, as shown in Fig. 6.



## OUTPUT DISPLAY UNIT

This consists basically of 18 m.e.s. lamps in lamp-holders under a translucent screen. Nine lamps (green) are used to indicate the "0"s and the other nine (red) to indicate the "X"s using filters as described later.
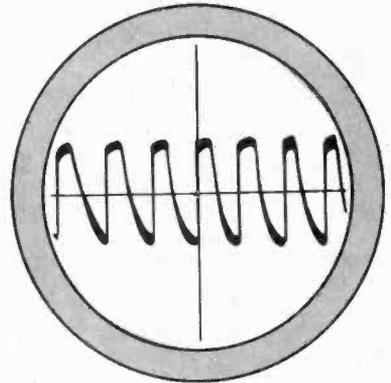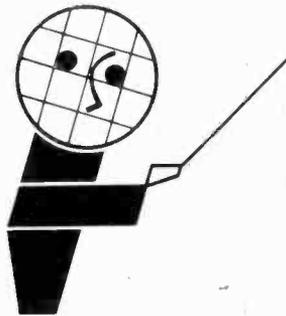
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
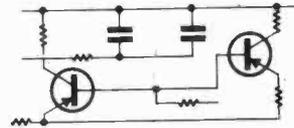
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL102

**special free gift also to all our students**



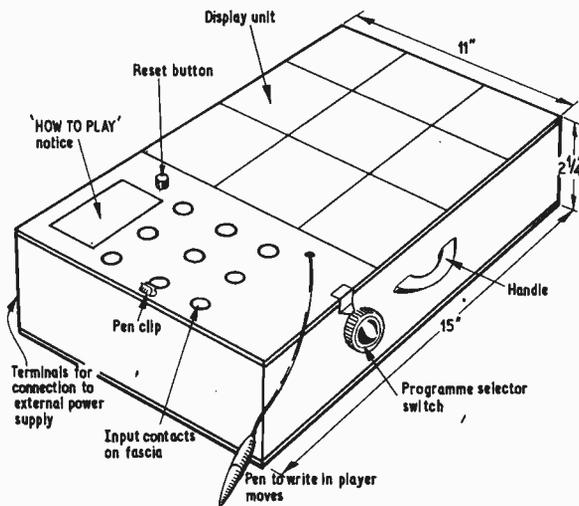


Fig. 7. General layout and dimensions of the complete unit (above)

Fig. 8. Construction of the cabinet and display unit (right)

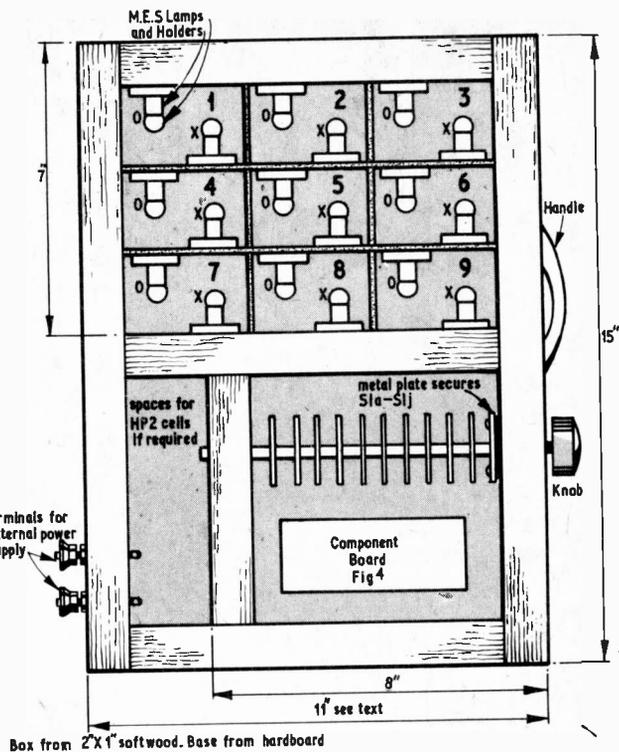


Fig. 9. Arrangement of the "0" and "X" filters under the tracing paper (bottom right)

## CONSTRUCTION OF CABINET AND DISPLAY UNIT

Fig. 7 shows the general layout. Fig. 8 shows the fascia and glass panels removed.

The dimensions are not critical except that the cabinet must be deep enough (at least 2 1/4 in) to take the wafer switch with all its wiring.

The lamp compartments should be as small as possible to give a bright display while ensuring that there is enough room to unscrew and replace lamps.

If a compartment is needed for HP2 cells (see "Power Supply" section below) then a maximum size of 11 in × 15 in overall may be used. If an external power supply is to be used then 8 in × 15 in will give a better, brighter display.



The cabinet may be made by glueing and pinning four pieces of 2 in × 1 in softwood to each other and to a rectangular (11 in × 15 in) hardboard base, see Fig. 8.


Four slotted partitions for the lamp compartments can be cut as shown, the m.e.s. lampholders screwed in position and the partitions slotted together and held in position by a 9 in crosspiece.

A metal plate, drilled to take the fixing bolt of the wafer switch can be screwed in position as shown. A short piece of softwood may be necessary to steady the end of the switch shaft if a battery compartment is required. Terminals or a power lead may be fitted for connection to an external power supply.
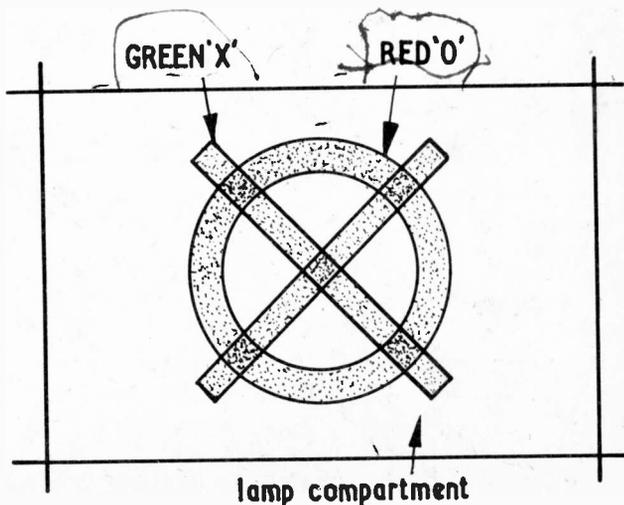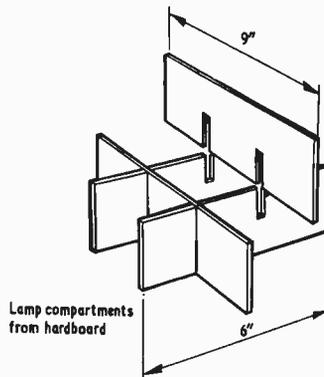
## NOUGHTS AND CROSSES

The nine "0" lamps are each wrapped in one or more layers of green cellophane and the nine "X" lamps



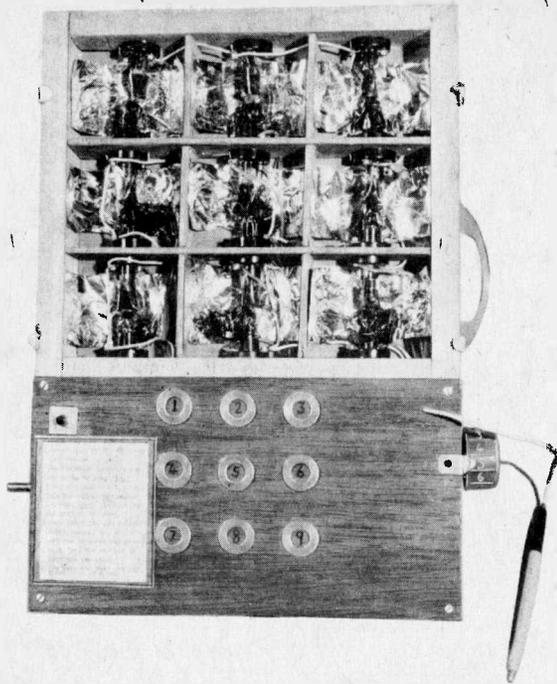

lamps are similarly wrapped in red cellophane or cinemoid. (Cellophane is obtainable from artists' supply shops and cinemoid, used in stage lighting, is obtainable from large electrical lighting shops.)

The lamp compartments are covered by two sheets of glass or Perspex which sandwich a sheet of tracing paper between them. Also sandwiched (under the tracing paper) are nine large red "0"s and nine large green "X"s cut out of cellophane, one of each over each lamp compartment (see Fig. 9). Thus when a green "0" lamp lights, it illuminates that square with green light except where the red "0" shape absorbs the green light and so appears as a black "0". Similarly when a red "X" lamp lights, a red square with a black "X" appears.

The cellophane or cinemoid should be chosen so that when a red and a green piece are overlapped and held to the light, it should appear as dark as possible without the individual colours being too dense for the lamps. In the prototype it was found that six layers of pale green cellophane and one layer of primary-red cinemoid were most suitable.

The brightness of the display is improved by fitting reflectors of aluminium kitchen foil behind the lamps, taking care not to cause a short circuit between the lampholder terminals.

The two sheets of glass may be held in place by mirror clips.

### FASCIA PANEL

The fascia is cut from  $\frac{1}{4}$ in or  $\frac{1}{2}$ in plywood or hardboard. Nine holes are drilled under the positions of the nine brass 1in washers (see Fig. 7). Leads are soldered to the washers, passed through the holes and the washers are glued in position using "Araldite" epoxy resin. They should be numbered 1 to 9 as in Fig. 1.

The "push-to-break" reset switch is fixed to the fascia. A hole is also drilled for the lead to the pen. The wood may be finished with varnish or stain. A carrying handle, and a pen clip may be added.

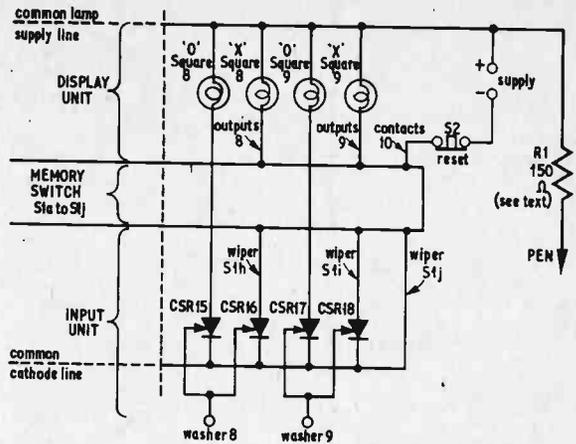


Fig. 10. Part of the complete circuit to show the method of interwiring the display, memory and input units

A large 12-faced plastic knob is needed for the wafer switch. The knob should be marked from 1 to 9 plus an "off" position corresponding to the switch positions shown in Fig. 6. A small metal pointer may be fixed to the fascia to facilitate reading the knob.

### INTERWIRING OF THE UNITS

Fig. 10 shows part of the complete circuit.

One side of all the lamps is connected to the positive terminal using thick wire and a circuit similar to a ring main to keep the resistance to a minimum.

The pen lead is also connected to the positive terminal.

The negative terminal is connected through the reset switch to all the contacts on the tenth wafer, using thick wire.

The wiper of the tenth wafer is connected to the common cathode lines on the Veroboard (Fig. 4) again using thick wire.

The lead from washer 1 is connected to the gates of thyristors CSR1 and CSR2 (Fig. 4 and 10) and similarly with the leads from the other eight washers. Heat shunts should be used to protect the thyristors while soldering.

The anode of thyristor CSR2 is connected to the wiper of wafer S1a (see Figs. 4 and 10). The anodes of the eight other even numbered thyristors are similarly connected. If possible colour coded wire should be used here.

A lead from all the switch contacts marked 1 in Fig. 8 is connected to lamp 1 "X" (i.e. the red lamp in square 1). Similarly all the contacts marked 2 are wired to lamp 2 "X" and so on.

Finally each of the anodes of the "0" thyristors is wired to the corresponding green "0" lamp (Fig. 4).

### POWER SUPPLY

This must be capable of lighting up to nine lamps in parallel, with least reduction in brightness.

Lead-acid accumulators or a tapping off a car battery or Nife alkaline cells give a bright display and can be re-charged.

**Table 1: POWER SUPPLIES AND LAMPS**

POWER SUPPLY	LAMPS
1 lead-acid accumulator (2.2V)	1.25V, 0.25A
2 lead-acid accumulators (4.4V)	2.5V, 0.3A or 3.5V, 0.3A
3 lead-acid accumulators (6.6V)	5.5V, 0.3A or 6V, 0.3A
2 NiFe cells (2.4V)	1.25V, 0.25A
4 HP2 dry cells (2 pairs in parallel) (3V)	1.25V, 0.25A
Mains driven d.c. power pack	bulb to suit voltage (allow 1V drop across thyristors)

**Table 2: "TRUTH TABLE" FOR CHECKING COMPUTER'S REPLIES**

SWITCH POSITION	WASHER TOUCHED WITH PEN								
	1	2	3	4	5	6	7	8	9
1	5	3	2	7	-	8	4	6	8
2	3	5	1	7	-	9	4	4	6
3	2	1	5	8	-	9	4	4	6
4	7	3	2	5	-	8	1	9	8
5	-	8	7	6	1	4	3	2	7
6	2	1	9	2	-	5	8	7	3
7	4	6	6	1	-	2	5	9	8
8	4	6	6	1	-	3	9	5	7
9	2	4	6	2	-	3	8	7	5

Table 1 shows which lamps to use depending on the available power supply. If more powerful lamps are used, make sure that the thyristors can carry the necessary current.

If a power-pack is used, it must have a low internal resistance and be capable of delivering enough current for nine lamps.

High power U2 dry cells can be used, but have a limited life and the display will not be very bright.

### TESTING

Table 2 shows the "truth table" for checking the computer's replies. For example with the switch set to position 1, if the pen is touched to washer 1 the green lamp in square 1 and the red lamp in square 5 should light. If the pen is then touched to washer 2, the green lamp in square 2 and the red lamp in square 3 should light. In this way the circuit should be carefully and methodically tested for each switch position, using the reset button where necessary.

### METHOD OF PLAY

The player decides at the beginning of a game which position he will play initially and then moves the memory switch to indicate that position. This switch must be left in that position for the rest of the game. The player then uses the pen to write in his initial play and carries on with the rest of the game.

A notice suitable for fixing to the fascia near the reset button is shown in the photographs. The aim of the game should be given as "to get three noughts in a line".

It is left to the constructor to find the 18 winning games. ★

## I.C. INTERCOM

continued from page 823

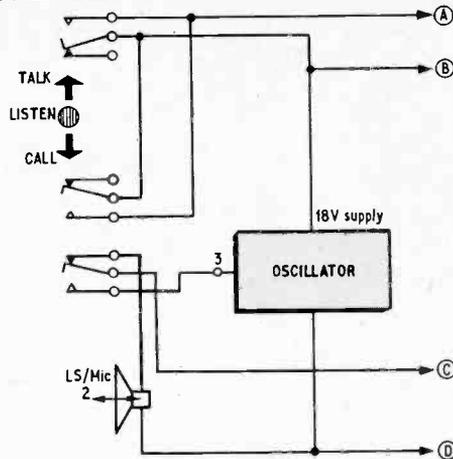


Fig. 9. A call oscillator identical to the one in the master can be used to give the slave a call facility. The switch is a miniature lever switch as used in the master. The letters to the right show how the modified slave is connected to the master


### MODIFICATIONS TO THE BASIC SYSTEM

The basic system can easily be extended by connecting slaves in parallel. Fig. 8 shows a typical set up with three slaves none of which have call facilities to the master; in this case it is the master station which has to initiate any communication by pressing the relevant button. If it is wished to give the slave a call facility then Fig. 9 shows the arrangement and this can easily be wired in if the master/slave set up is sufficient.

If any of the configurations using two or more slaves are built then the cases may have to be redesigned. For example, if it is decided to build the master/two slaves with call facilities then the slaves will have to have a case large enough to accommodate the speaker, the call oscillator and the lever key whilst the master will need to be enlarged so that the multi-button switch and the indicator lights can be fitted.

Depending on what loudspeaker is finally used will dictate the method of fixing; the easiest is to glue them to the case making the hole a little smaller than the speaker. ★

The completed intercom

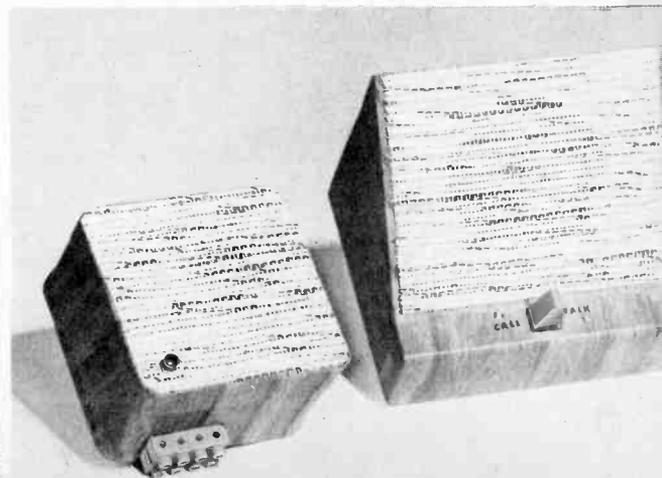



## PART 2

POWER SUPPLY...

PRE-AMPLIFIER...

TREMOLO...

# ELECTRONIC PIANO

By A. J. Boothman B.Sc.

To achieve a logical building sequence the order of construction presented will be the power supply unit, pre-amplifier and tremolo unit, main amplifier and pitch printed circuit boards. The mounting of the keyboard and other assembly details will round off the series.

To assist in lining up the p.c.b.s the power unit and amplifier are used as test gear, hence the order of construction.

### POWER SUPPLY CIRCUIT

The circuit of the power supply is shown in Fig. 2.1 and is based on well established design principles. A transformer using the 20 volt secondary tap produces an open circuit voltage of approximately 30 volts across a large reservoir capacitor, and this reduces to about 26 volts at 2 amps. Two 6.8 volt Zener diodes connected in series act as the reference voltage with which a portion of the output voltage at the emitter of a ZT3055 is compared. Any error is amplified and fed to the output transistor, thus regulating the output voltage. Capacitor C4 produces a slow rise in output voltage at switch on, whilst C3 and R3 give high negative feedback of any ripple voltage which might be developed at the output.

The output voltage range of the supply is 16-21 volts, controlled by VR1, and the maximum output

current is 2 amps. Worst case dissipation in the output transistor TR3 is 18W with 700mW in the driver transistor TR2. Two Zener diodes are used rather than one high voltage type in order to reduce the power requirement in one package. TR1 and each Zener diode have maximum power dissipation levels of approximately 75mW.

The earth connector allows the earth to the piano circuits to be disconnected in the event of any instabilities which might occur when the piano is connected to a self earthed external amplifier.

### P.S.U. ASSEMBLY

The small components for the power supply unit are mounted on a simple printed circuit an etching and drilling pattern for which is given in Fig. 2.2.

With the p.c.b. completed and terminal pins inserted first the pre-set potentiometer is mounted, then the resistors, diodes, transistors, capacitors and finally the a.c. input terminal strip as in Fig. 2.3.

The two regulator transistors are mounted on a heatsink and the assembly completed using the transformer for mounting the board. The large capacitors, heatsink and transformer are mounted on a baseboard as seen in the photograph.

After assembly the power supply can be checked for correct operation by measurement of voltage at

# POWER SUPPLY

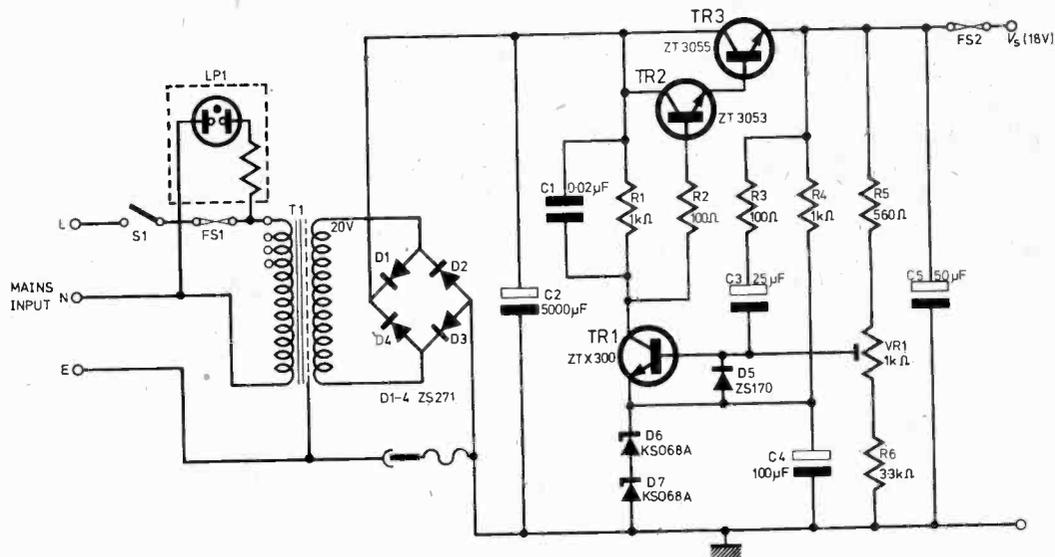


Fig. 2.1. Circuit diagram of power supply unit

a number of points. The voltage across the 5000 $\mu$ F capacitor (two 2,500 $\mu$ F capacitors, connected in parallel, were used in the prototype) on no load should be approximately 29 volts with a voltage on load of 25V at 1.5A. The emitter voltage of TR1 is 13 volts, with 18.5 volts at the collector for an output voltage of 17 volts.


The voltage on the slider of the preset potentiometer is 14 volts. This component should be of high quality as severe damage could be caused by a faulty condition. After experiencing some difficulties with cheap skeleton potentiometers the author decided to use a multi-turn linear track potentiometer which is probably at the other extreme on cost.

## PRE-AMPLIFIER CIRCUIT

The pre-amplifier circuit is shown in Fig. 2.4 and consists of three stages. The input impedance is very low, and allows an unscreened signal interconnection between the pitch boards.

It is essential that the amplifier should be able to handle a wide range of signals, since the peak level for one note is approximately 80mV peak-to-peak on maximum attack. The maximum input signal which can be presented at the input is approx. 2.6 volts peak-to-peak which represents 32 notes in the maximum attack position.

Perspective view of power supply module

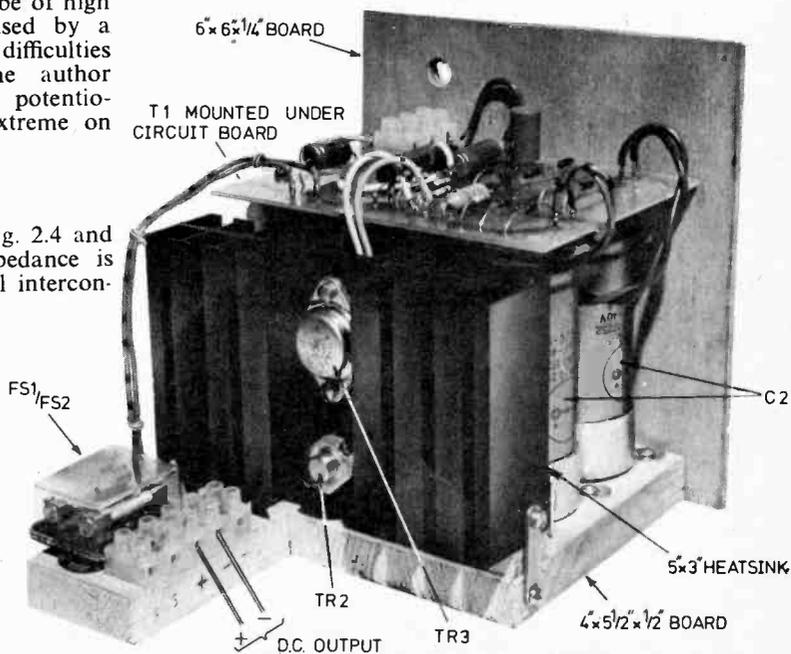

# POWER SUPPLY BOARD

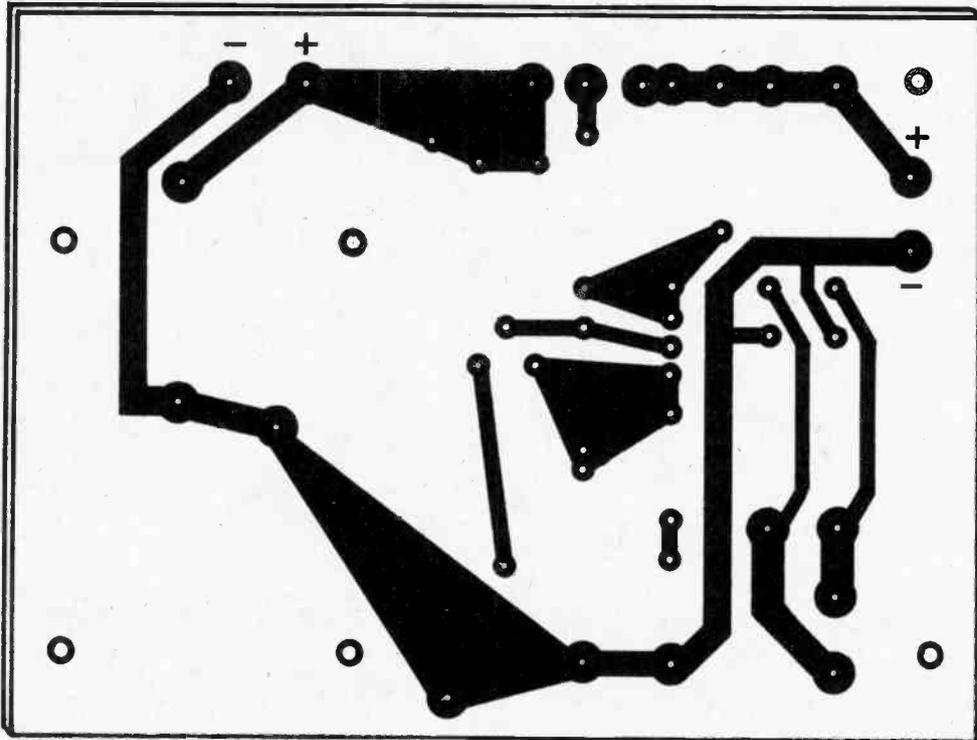


Fig. 2.2. Etching and drilling details for p.s.u. printed circuit board (full size)

## COMPONENTS . . .

### POWER SUPPLY UNIT

#### Resistors

R1 1k $\Omega$	R4 1k $\Omega$
R2 100 $\Omega$	R5 560 $\Omega$
R3 100 $\Omega$	R6 3.3k $\Omega$

All 5%  $\frac{1}{2}$ W carbon

#### Potentiometer

VR1 1k $\Omega$  preset

#### Capacitors

C1 0.02 $\mu$ F polyester 125V	C4 100 $\mu$ F elect. 15V
C2 5,000 $\mu$ F elect. 35V	C5 50 $\mu$ F elect. 25V
C3 25 $\mu$ F, elect. 15V	

#### Diodes

D1-D4 ZS271 (Ferranti) 4 off
D5 ZS170 (Ferranti)
D6-D7 K5068A (Ferranti) 6.8V 400mW Zener (2 off)

#### Transistors

TR1 ZTX 300 Ferranti	TR3 ZT 3055 Ferranti
TR2 ZT 3053 Ferranti	

#### Transformer

T1 Mains transformer, Douglas type MT3AT

#### Miscellaneous

FS1 — 200mA fuse, FS2 — 1.5A fuse, S1 — Main toggle switch, heatsink, LP1 — Mains neon

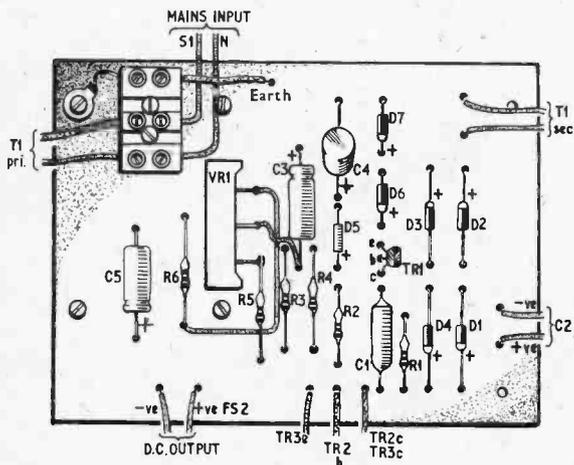


Fig. 2.3. Component assembly on p.s.u. printed circuit board

The output from the first stage is fed via a resistor network to a compound emitter follower containing two transistors (TR5, TR6). The design of this portion of the circuit is determined by the condition required for the tremolo effect. The tremolo circuit, which is described later, acts as a shunt modulator by presenting a variable impedance across VR2, so giving a variable degree of attenuation of the signal between the first and second stages.

Output from the emitter follower is again at low impedance and the nominal attenuation (tremolo off)

for the second stage is a factor of two. Thus the overall voltage gain to the output of the emitter follower is approximately 1.5.

### LEVEL CONTROL SETTINGS

The second stage is followed by the two level determining elements, the first being the foot soft pedal control, whilst the second is the keyboard level control. The latter item consists of a five position switch with fixed resistors giving stepped attenuation levels.

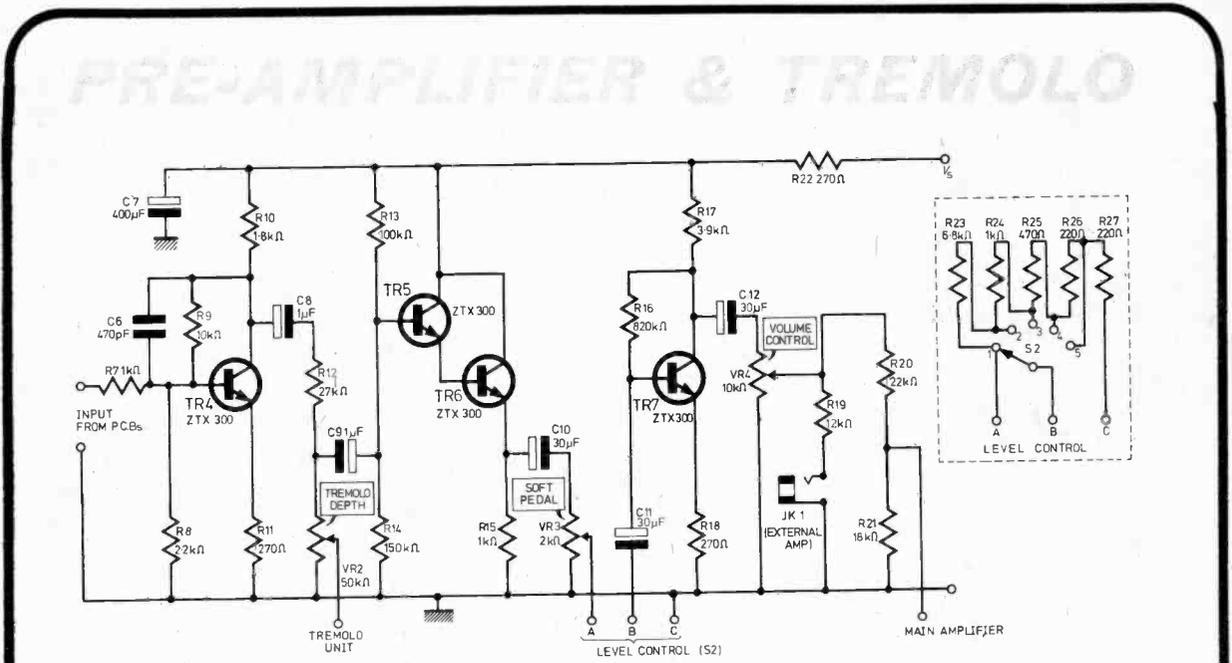


Fig. 2.4. Circuit diagram of pre-amplifier

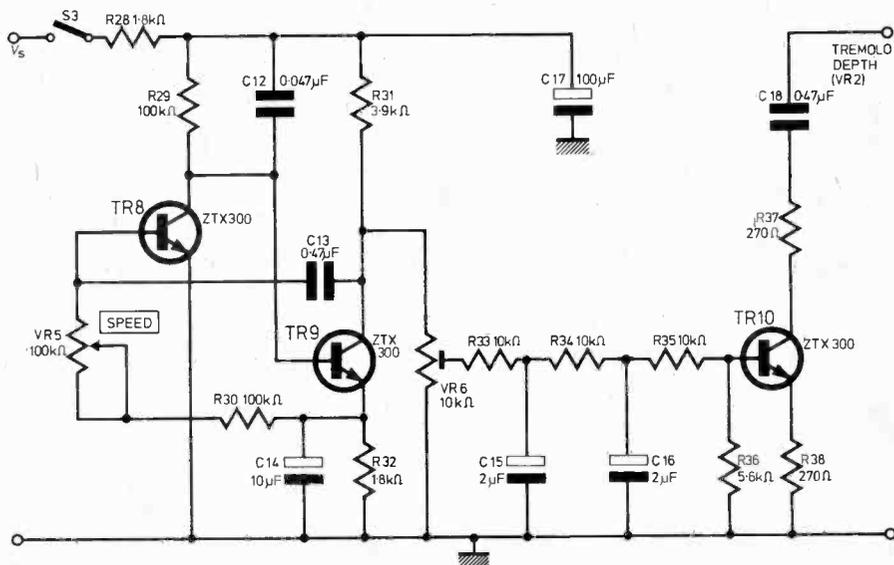


Fig. 2.5. Circuit diagram of tremolo unit, S3 is the keyboard on/off control switch

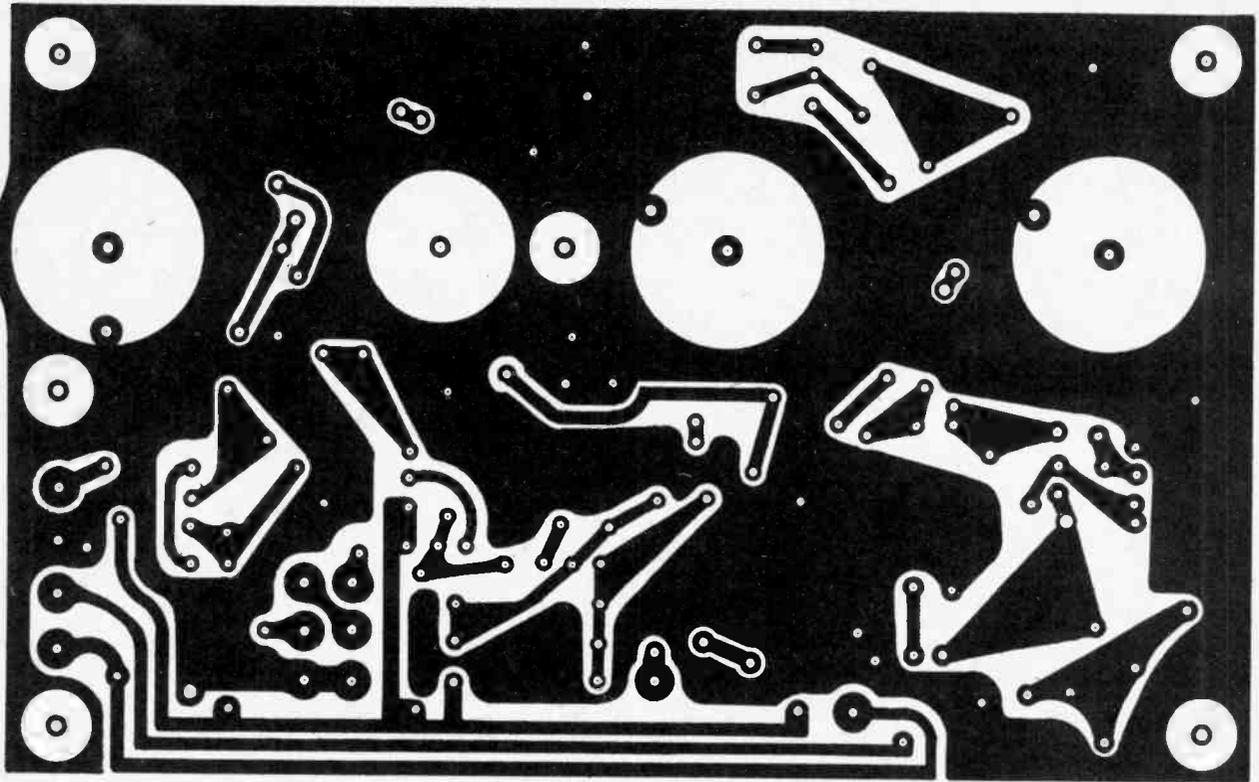


Fig. 2.6. Etching and drilling details for pre-amplifier and tremolo printed circuit board (full size). The white circles for JK1, VR2, VR4 and VR5 should be only  $\frac{3}{8}$ in diameter

## COMPONENTS . . .

### PRE-AMPLIFIER

#### Resistors

R7 1k $\Omega$	R18 270 $\Omega$
R8 2.2k $\Omega$	R19 12k $\Omega$
R9 10k $\Omega$	R20 22k $\Omega$
R10 1.8k $\Omega$	R21 18k $\Omega$
R11 270 $\Omega$	R22 270 $\Omega$
R12 27k $\Omega$	R23 6.8k $\Omega$
R13 100k $\Omega$	R24 1k $\Omega$
R14 150k $\Omega$	R25 470 $\Omega$
R15 1k $\Omega$	R26 220 $\Omega$
R16 820k $\Omega$	R27 220 $\Omega$
R17 3.9k $\Omega$	

All resistors  $\pm 5\%$   $\frac{1}{2}$ W carbon

#### Capacitors

C6 470pF polyester 125V
C7 400 $\mu$ F elect. 15V
C8-C9 1 $\mu$ F elect. 15V (2 off)
C10-C12 30 $\mu$ F elect. 15V (3 off)

#### Transistors

TR4-TR7 ZTX300 (Ferranti) (4 off)

#### Potentiometers

VR2 50k $\Omega$ carbon lin.
VR3 2k $\Omega$ carbon log.
VR4 10k $\Omega$ carbon log.

#### Miscellaneous

S2—5-way single pole rotary switch
JK1—Standard jack socket

### TREMOLO UNIT

#### Resistors

R28 1.8k $\Omega$	R34 10k $\Omega$
R29 100k $\Omega$	R35 10k $\Omega$
R30 100k $\Omega$	R36 5.6k $\Omega$
R31 3.9k $\Omega$	R37 270 $\Omega$
R32 1.8k $\Omega$	R38 270 $\Omega$
R33 10k $\Omega$	

All resistors  $\pm 5\%$   $\frac{1}{2}$ W carbon

#### Capacitors

C12 0.047 $\mu$ F polyester 125V
C13 0.47 $\mu$ F polyester 125V
C14 10 $\mu$ F elect. 15V
C15 2 $\mu$ F elect. 15V
C16 2 $\mu$ F elect. 15V
C17 100 $\mu$ F elect. 25V
C18 0.47 $\mu$ F polyester 160V

#### Transistors

TR8-TR10 ZTX 300 (Ferranti) (3 off)

#### Potentiometers

VR5 100k carbon lin.
VR6 10k $\Omega$ preset

#### Switch

S3—On/off switch

Normal setting is position 2 which gives the nominal output, on maximum master volume, for a five note input. Position 1 gives the nominal output when a single note is played and is only for special single note solo effects.

Positions 3, 4 and 5 give quick operation attenuated levels as required. In position 2 the attenuation between stages two and three is a factor of five.

The single transistor third stage has a gain of approximately ten, and again has a high dynamic range, such that the maximum output swing capability is 8V peak-to-peak.

Overall pre-amplifier voltage gain with the level control in position 2 totals a factor of three, and is followed by a master volume control which feeds the external amplifier jack socket, and a fixed attenuation network prior to the main internal amplifier.


### TREMOLO CIRCUIT

The tremolo circuit is shown in Fig. 2.5. and consists of a multivibrator (TR8, TR9) supplying a square wave output across a preset potentiometer in the range of 5-10Hz. The output from the preset feeds two low pass filters to give a ramp waveform at the base of TR10.

Preset adjustment ensures that the transistor operates from the off condition and provides maximum voltage change at the collector. In turn the degree of voltage swing is controlled by VR2 when applied to the pre-amplifier.
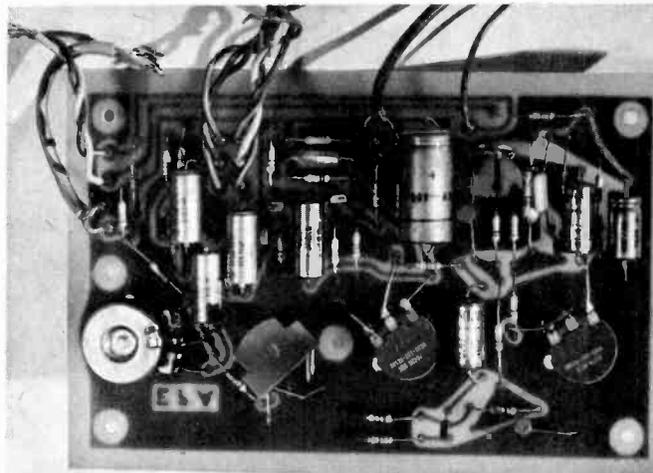
### PRE-AMPLIFIER AND TREMOLO ASSEMBLY

The pre-amplifier and tremolo circuits are mounted on the same printed circuit board, which



Photograph of the completed pre-amplifier and tremolo board

also acts as the panel to hold the external amplifier output socket, the master volume control, and the tremolo rate and depth controls.

Figs. 2.6 and 2.7 give details of the printed circuit board and component assembly. As before all holes should first be checked against the diagrams, and any missed holes should be drilled before proceeding. This may be particularly necessary in the case of the potentiometer peg location holes which will vary in position for different types and sizes of potentiometer.

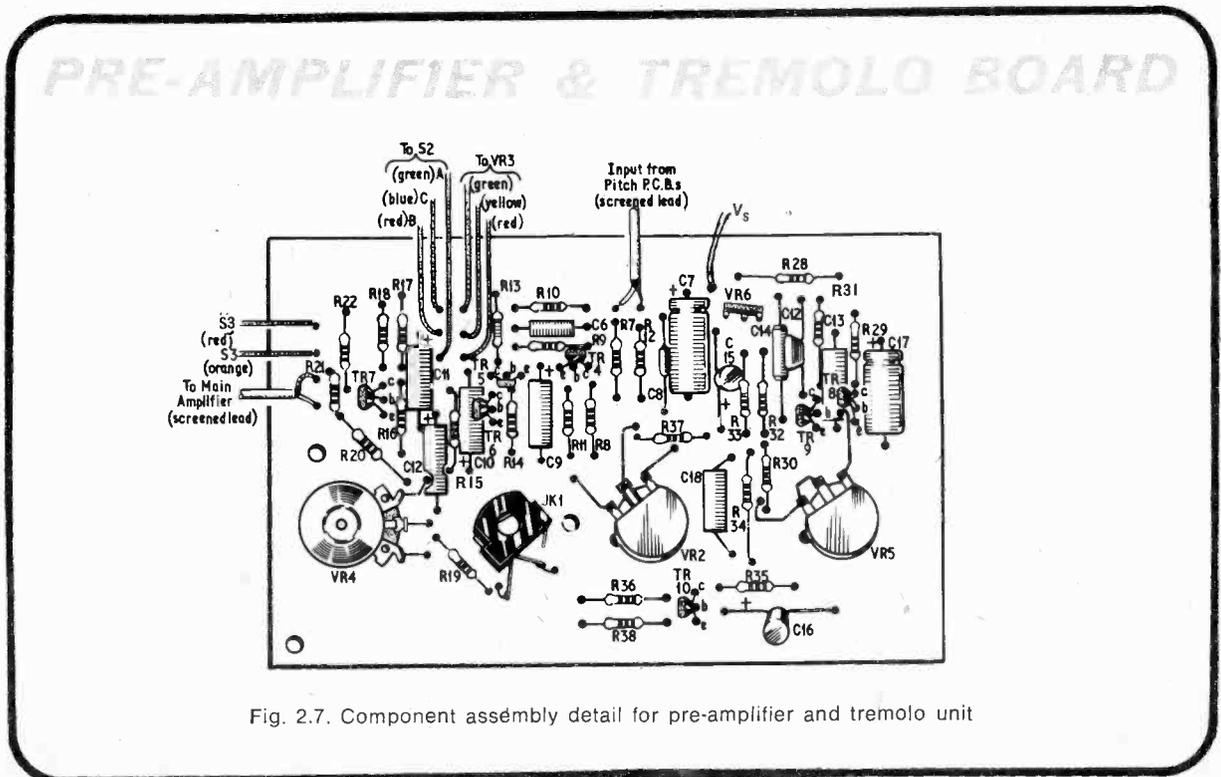


Fig. 2.7. Component assembly detail for pre-amplifier and tremolo unit

Next the terminal pins should be fitted, followed by the potentiometers, jack socket, and preset potentiometer. Fit the resistors, transistors and capacitors in that order, and finally wire the potentiometers and output socket.

### MAIN AMPLIFIER

The circuit of the main amplifier is shown in Fig. 2.8 and is based on the Sinclair integrated circuit type IC-12.

The amplifier is intended as a low power unit to drive the two small internal loudspeakers, or the headphones. Whilst the power is adequate for home use in a small or medium size room, an external amplifier is recommended for any serious use of the instrument outside the domestic circle.

The circuit within the package is fully explained in the Sinclair booklet which is supplied with the unit. If you should purchase a unit which includes the earlier simple two page leaflet the booklet can be obtained by writing to Sinclair Radionics Limited.

### COMPONENT CHANGES

A printed circuit card is supplied with each unit and the photograph shows the assembled unit. Some of the component values have been changed from those suggested by Sinclair for the average application. The components affected are marked with an asterisk in Fig. 2.8 and the associated components list.

C19 (0.5 $\mu$ F) has been chosen for the input coupling capacitor since, as explained later, the input impedance has been reduced such that bass response could suffer if this capacitor were not increased. C20 (0.01 $\mu$ F) has been used to provide a small amount of treble cut as a form of tone shaping on the internal amplifier setting. C25 (400 $\mu$ F) prevents any possible instabilities due to the length of the supply lines.

### MAXIMUM BASS


To provide maximum bass response a 1,000 $\mu$ F coupling capacitor (C27) is connected at the output. Due to the large size of this capacitor it has been removed from the p.c.b. as supplied by Sinclair. It will also be noted that the connection of this capacitor within the circuit has been removed from the live side of the speakers and inserted on the ground side. This prevents the possible shorting out of C27 to earth by the insertion of a jack plug into the headphone socket where the jack plug is connected to some other equipment which is earthed.

This rearrangement means, that it is necessary to connect a wire link across the connections intended for C27, thus making pin F an earth point.

The input impedance is reduced by the choice of R39 which minimises pick-up between the pre-amplifier board and main amplifier. R41 (470 $\Omega$ ) is used to hold the amplifier gain at 60. This gives an input sensitivity of approximately 200mV peak-to-peak for a 3 watt output into 6 ohms.

Sinclair Radionics state that it is very important that the i.c. only be used mounted on the printed circuit board which is supplied with it. Due to the very high gain of the device, the slightest coupling between output and input can cause trouble in the way of distortion and instability.

Next month: Pitch Board

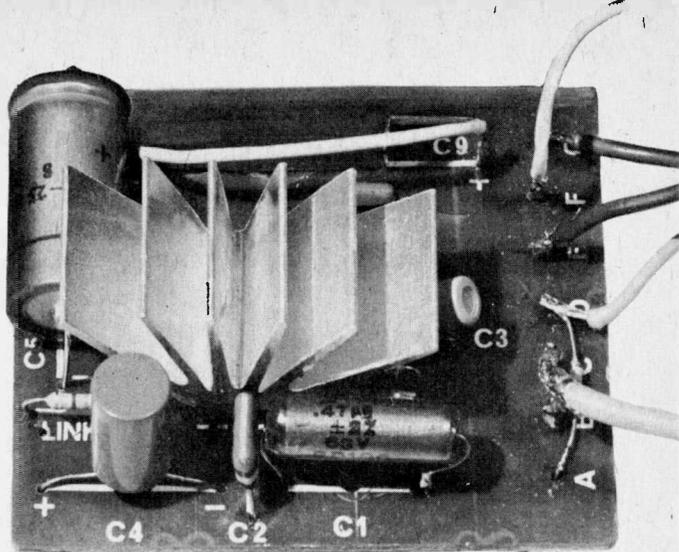

Proprietary board assembly for the main amplifier

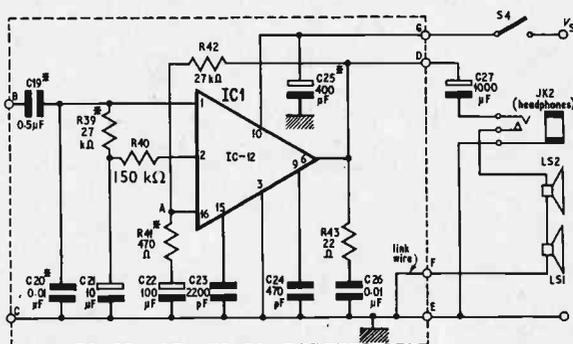


Fig. 2.8. Circuit diagram of main amplifier

## COMPONENTS . . .

### MAIN AMPLIFIER

#### Resistors

- R39\* 27k  $\Omega$
- R40 150k  $\Omega$
- R41\* 470  $\Omega$
- R42 27k  $\Omega$
- R43 22  $\Omega$
- All resistors  $\pm 5\%$   $\frac{1}{4}$ W carbon

#### Capacitors




- C19\* 0.5 $\mu$ F polyester 125V
- C20\* 0.01 $\mu$ F polyester 125V
- C21 10 $\mu$ F elect. 15V
- C22 100 $\mu$ F elect. 15V
- C23 2,200pF polyester 125V
- C24 470pF polyester 125V
- C25\* 400 $\mu$ F elect. 25V
- C26 0.01 $\mu$ F polyester 125V
- C27 1,000 $\mu$ F elect. 15V

#### Integrated Circuit

- IC1—Super IC-12 with printed circuit board. (Sinclair Radionics Ltd.).
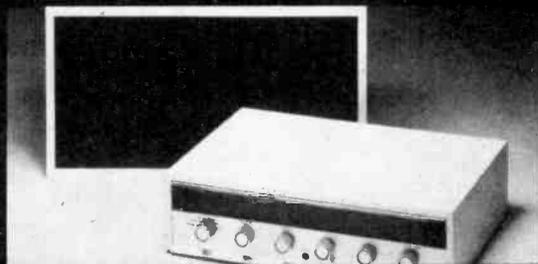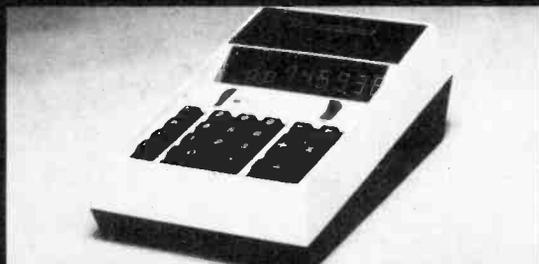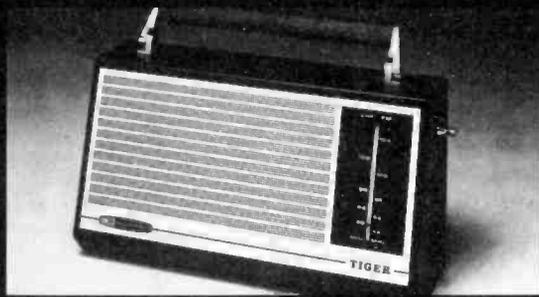
#### Miscellaneous

- JK2—Jack socket to match headphones
- LS1-LS2 3  $\Omega$  elliptical loudspeakers 8in  $\times$  2 $\frac{1}{2}$ in.
- S4—On/off switch



## You can make any of these just as well as we can. And save yourself money into the bargain.

We at Heathkit do all the donkey-work – the rest is up to you. If you're handy with a soldering iron, pliers and screwdrivers you'll have no difficulty putting the bits and pieces together in a few hours. Even if you're not used to soldering you can still do it. Because we tell you how in an introductory booklet. And we give you bits and pieces to practise on before you take the plunge.

Just think what you could make yourself this weekend.

How about building the world's first electronic calculator kit? It's easier than you think. The new Heathkit IC-2008 desk-top calculator adds, subtracts, multiplies and divides up to eight digits. Electronically. You can multiply or divide a series of numbers by a pre-selected figure; fix the decimal point in one of eight positions or in a floating decimal mode. And a ninth display tube indicates overflow. It's smart.



highly sophisticated – and shows a big saving over the ready-built price.

Or you could make yourself an IB-1101 frequency counter. New from Heathkit, it has a range from 1 Hz to over 100 MHz – and an input frequency that'll accept levels from below 50 mV to over 2000V. The decimal point is automatically placed with range selection. A truly professional piece of equipment.



Maybe radio is more in your line. Well, you could make our new version of the successful Tiger transistor portable – the Tiger FM. Designed specifically for the high-quality sound of VHF broadcasts (BBC radio 2, 3, 4 and local stations), it's particularly easy to build. Ideal for beginners.

And if you're bored with teak or walnut finishes on audio equipment, you'll be glad to know that we do Hi Fi in colour. You can choose from snow white or sunshine orange, besides the usual teak or walnut. That goes

for our AA14 30 watt stereo amp, AR14 tuner/amp, and Trent speakers.

If you want a demonstration of any Heathkit equipment we'll be pleased to see you at either of our showrooms – 233 Tottenham Court Road, London W.1 (open 9–6, six days a week), and 17–18 St. Martin's House, Bull Ring, Birmingham (open Tues-Sat, 9–6).

Like we said, you can make them all as well as we can. But if, by any remote chance, you do manage to go wrong with your assembly, we'll put you right again. In fact, that's a firm guarantee.

You simply can't fail.

Want to know more? Mail the coupon for our free catalogue – it's packed with Heathkit goodies.



Please send me the FREE 1972 Heathkit catalogue.

Name .....



Address .....

HEATH (Gloucester) Ltd., Gloucester GL2 6EE.

PE 10/72



We won't let you fail.

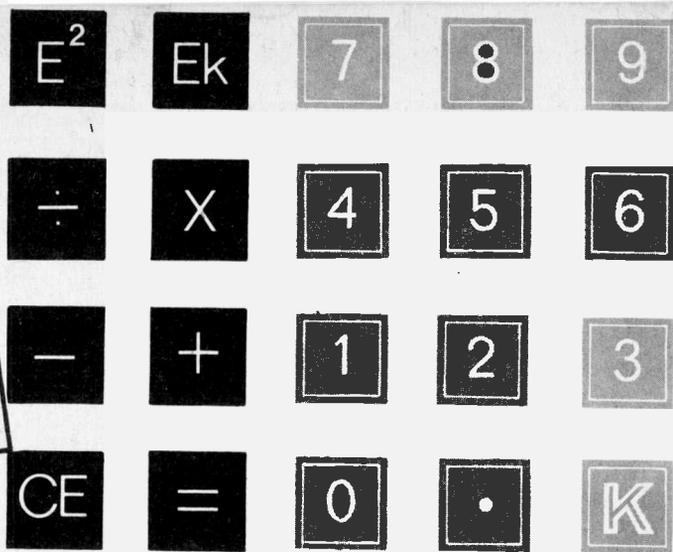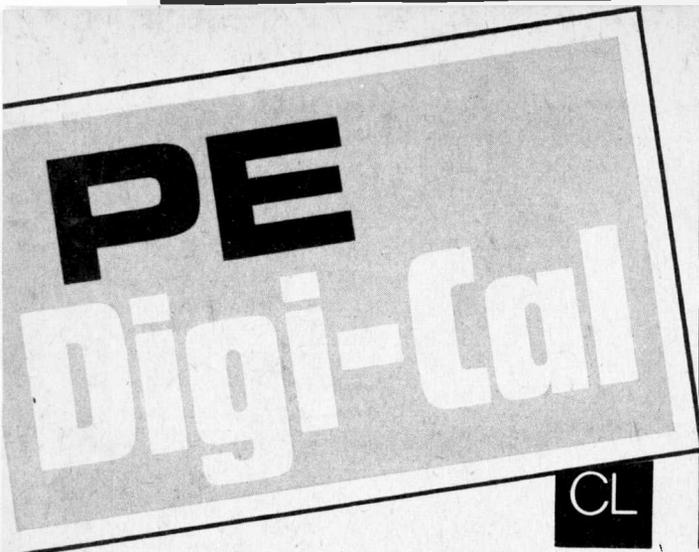

By R.W.COLES PART 4

## KEYBOARD LOGIC AND HARDWARE

**S**ATISFACTORY functioning of the keyboard is vital for correct calculator operation and to make things as easy as possible for the user, a great deal of thoughtful design has been carried out as regards key-top labels, keyboard layouts, the required function of each of the keys, and compensation for possible "finger-trouble"! The author's solutions to these problems are embodied in the Digi-Cal keyboard, but should any constructor wish to alter either the physical layout or the logic there is plenty of scope for modifications to produce a "custom" design.

### KEYBOARD DEFINITION

The keyboard circuitry can be split up into a number of independent or interlocking sub-circuits, and each of these performs a different function, corresponding to one of the following list of keyboard requirements:

1. Convert figure key depressions into a four bit B.C.D. code and generate a single coincident clock pulse to enter the B.C.D. data into the (separate) entry register.
2. Convert arithmetic key depressions into a static two bit code suitable for use by the programme and arithmetic sections.
3. Record the number of decimal places in each figure entry and control the final alignment of the number so that it has the correct number of decimal places as entered on the thumb-wheel switch.
4. Produce a three bit code representing the number of decimal places to be displayed, dependent upon whether entries or answers are being read out.
5. Generate a single pulse to start the programme when the EQUALS key is pressed.
6. Switch on the overflow lamp when an OVERFLOW input is received from the arithmetic section.

### BLOCK DIAGRAM

The circuit of the keyboard panel can be subdivided into a number of relatively straightforward logic groups.

Fig. 4.1 shows these groups laid out in the form of a functional block diagram and it is best to understand the keyboard using this diagram before studying the full circuit in detail.

In the block diagram the circuit has been simplified as far as possible and the symbol consisting of a switch in a box with an arrowed input is used to represent gating functions which control the switched path, the arrow showing the input which has control.

### ARITHMETIC KEYS

Starting at the top of the diagram, the four main arithmetic keys are fed to an encoding circuit which generates a unique binary code for each depression. This code is "staticised" in two latch flip-flops so that the code remains on the output wires until over-ridden by a future (different) arithmetic selection.

The  $E^2$  key is in parallel with the "MULTIPLY" key since squaring is simply a modified multiplication sequence; a separate  $E^2$  output is also produced to modify the programme.

The narrow START pulse required by the programme is generated by a monostable triggered by the EQUALS key, and this monostable is also used to start the second half of the multiply and divide sequences on command from the arithmetic section.

### NUMERAL KEYS

The number keys are encoded to their B.C.D. equivalent in a diode matrix, the outputs of which are also staticised by four flip-flops so as to present a steady logic output during the clock pulse which enters the data into the entry register, the data in the latches remaining until either a different number key is pressed, or the EQUALS key is pressed in which

# KEYBOARD LOGIC

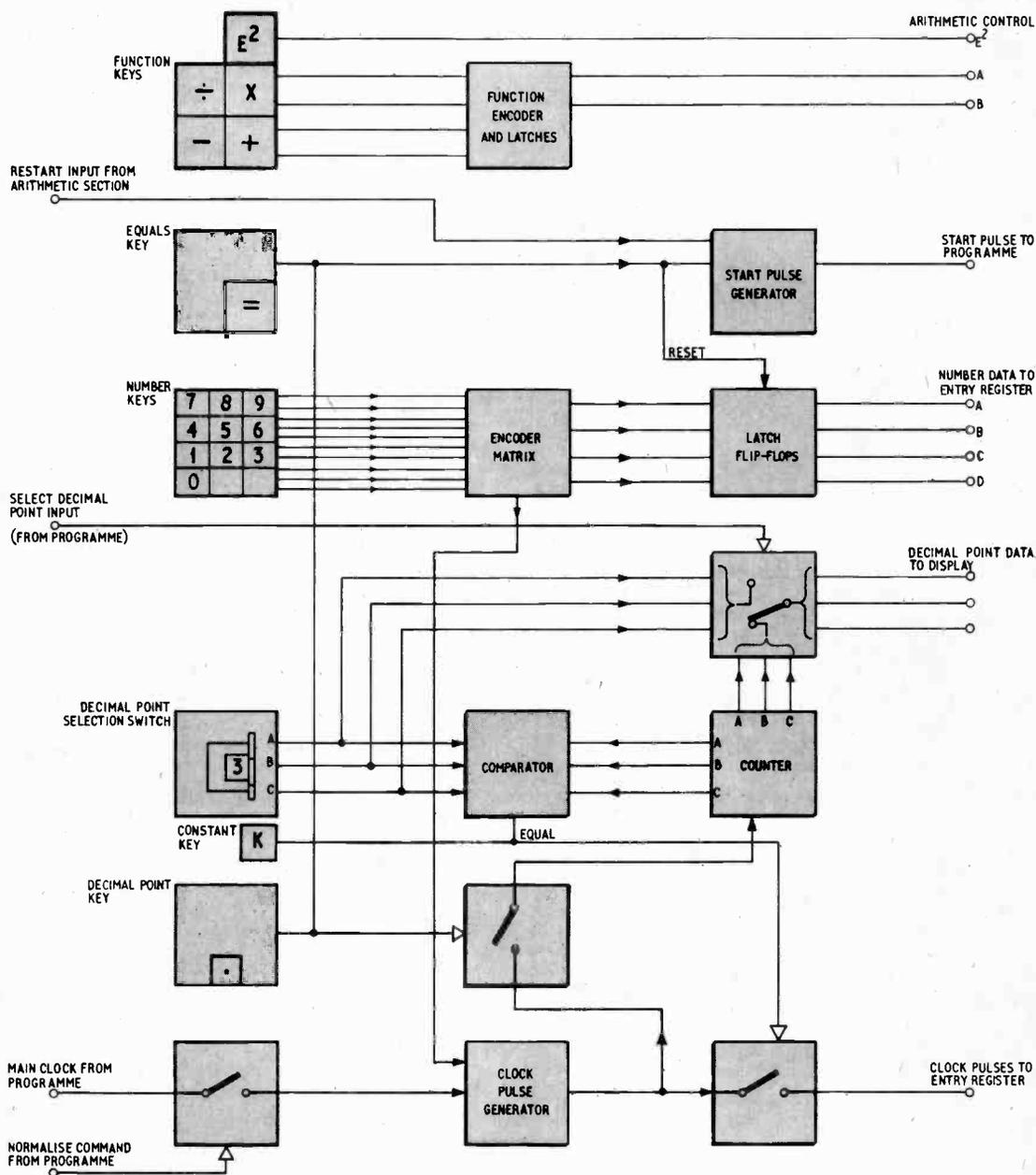


Fig. 4.1. Simplified block diagram of the keyboard logic. The symbol of a switch in a box with an arrowed input represents a group of logic gates, the arrow being the input which has control

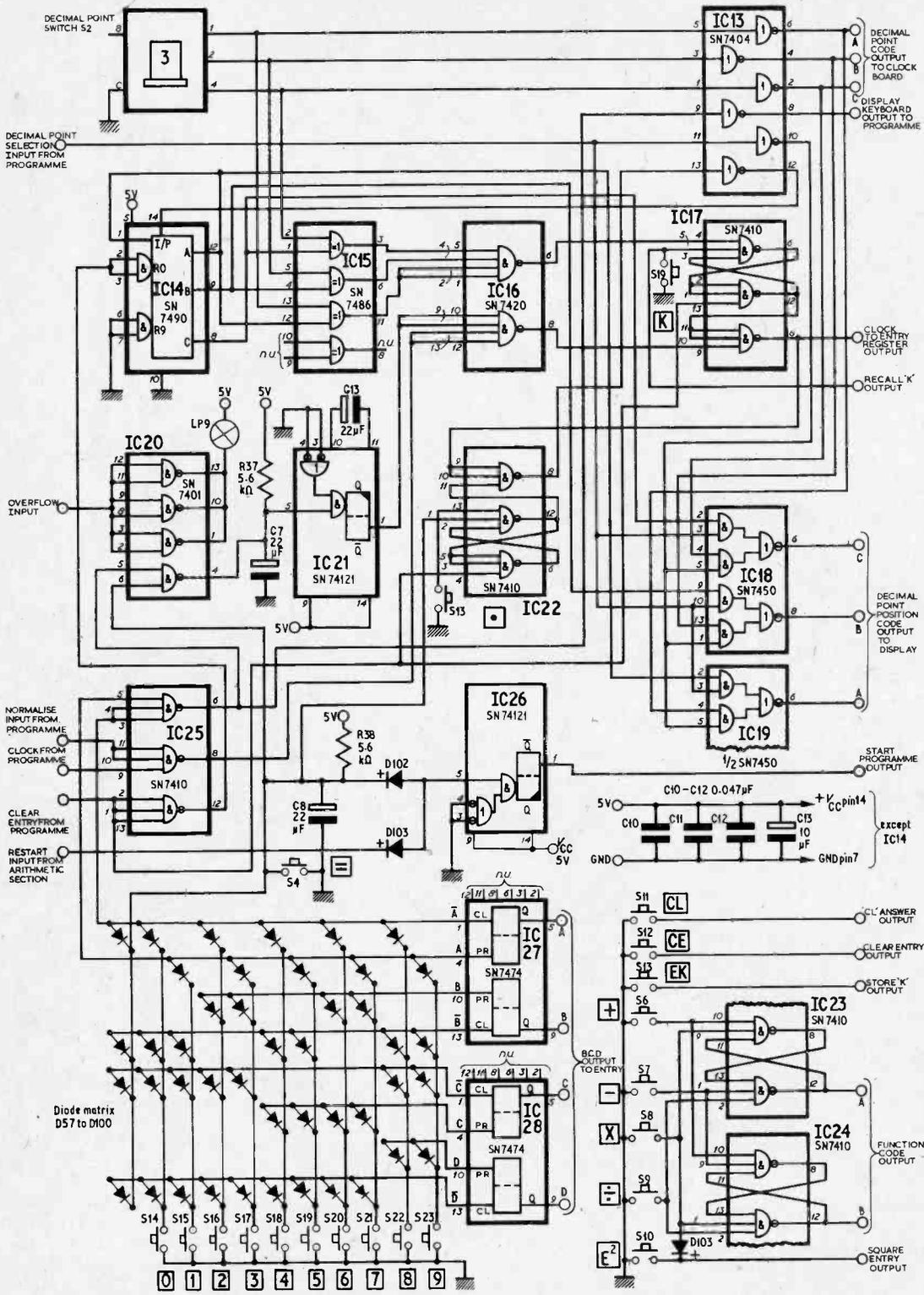


Fig. 4.2. The complete circuit diagram of the keyboard logic panel. All i.c.s have pin 7 as ground and pin 14 as 5V except IC14 whose power supplies are shown

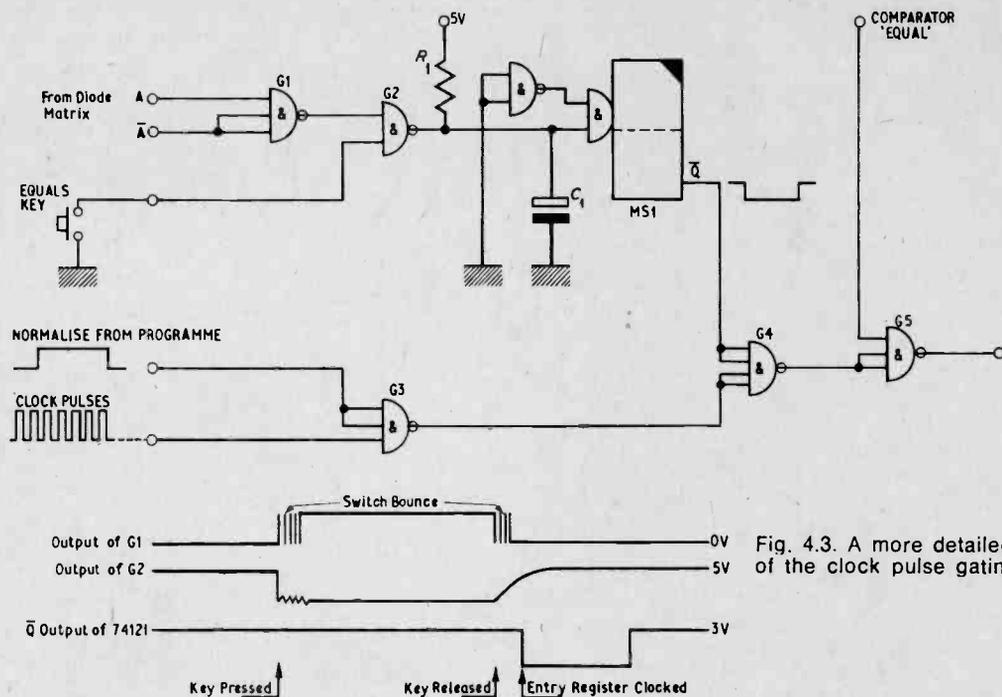


Fig. 4.3. A more detailed diagram of the clock pulse gating circuit

case the latches are cleared. An output is also generated from the matrix whenever any key is pressed, and this signal is used to trigger the clock pulse generator, but more of this later.

### DECIMAL POINT POSITIONING

If the decimal point key is pressed during an entry then a latch is set which in turn opens a gate to allow any subsequent clock pulses through to a counter. This counter counts the clock pulses after the point entry and gives an output which is compared with the setting of the decimal point thumbwheel in a comparator circuit.

When the correct number of decimal places have been entered the comparator registers the equality and shuts off the clock pulses from the clock pulse generator. It is this mechanism which prevents entry of too many decimal places in any figure entry.

If the number entered has too few decimal places then when the programme is started a NORMALISE command from the programme allows the main calculator clock pulses through to the clock generator in the keyboard, and the entry register data is rapidly shifted along until the comparator again registers equality then shuts off the clock.

This process ensures that all numbers can be entered without regard to the position of the point, normalisation being automatically carried out by the calculator itself.

### OTHER FUNCTIONS

There are two additions to the clocking circuit to allow for special conditions. The EQUALS key is allowed to close the path connecting the clock pulses to the counter, this being done to cater for the occasions when only whole numbers are entered, the decimal point being unused.

Also, the RECALL CONSTANT (K) key is allowed to shut off the clock path to the entry register so as to inhibit normalisation, this being necessary because the constant in store is correctly aligned to start with.

The three bit output of the thumbwheel switch is used to define decimal point position when the answer to a calculation is being displayed, and the three bit output of the counter is used to define it when an entry is being displayed. Switching between the two sources is carried out by a gating arrangement controlled primarily by the programme.

Any keys not shown on the simplified diagram have no associated logic circuitry and are passed out to the rest of Digi-Cal as switch closures to earth.


The full circuit of the keyboard is given in Fig. 4.2, and with the knowledge of its operation gained from the simplified diagram it should be possible to pick out the various logic groups previously discussed. One particular group may still be a little difficult to trace out, and that is the clock generation and gating.

To see this circuit in a clearer light it has been redrawn in Fig. 4.3 in an integrated way, and because this section is so important we can go through it step by step.
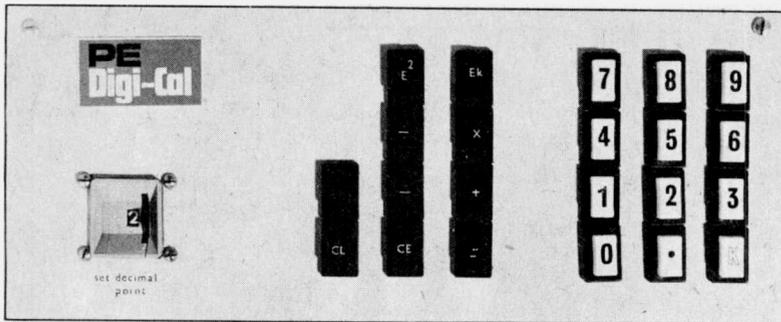
### CLOCK CIRCUIT

The clocking is initiated by detecting any output from the diode matrix which is an indication of a key depression. Because the normally high A, B, C, and D outputs of the matrix will always have either their true or their complement output active (i.e. low) for any one of the ten relevant key depressions a detection circuit can be made by "ORing" together the true and complement version of any one of them.

In Fig. 4.3 G1 performs the detection by using the two "A" outputs from the matrix. The "logic 1"



The upper side of the keyboard showing the arrangement of the switches in the slots

output from G1 is applied to G2 which is an open collector gate with  $R_1$  and  $C_1$  in its collector circuit to give a slow "0" to "1" transition. The other input to G2 is an inhibiting input from the EQUALS key which prevents a clock pulse being generated by the latch reset when the EQUALS key is pressed.

The output of G1 is shown for a typical key depression and as you can see it carries with it a faithful (though inverted) representation of the switch bounce which is a feature of all mechanical switch operations, and which must be removed before the signal is used to trigger the monostable.

The output of G2 is "cleaned-up" by  $R_1$  and  $C_1$  to give the output pulse shown, and the slow transition after the key is released is used to activate the level sensitive trigger input of the SN74121. The fairly long negative going pulse from the monostable is "ORed" with the possible output of G3 and fed out to the entry register via G5 which is controlled by an inhibitory input from the COMPARATOR EQUAL latch. Gate G3 is used to control the main clock input used during the normalising cycle, being enabled by a long pulse from the programme.

## DIODE MATRIX

The diode matrix used to encode the figure keys into their binary equivalent is so named because of its physical construction, the logic it performs being simply that of eight multi-input OR gates, the number of inputs to each gate being set by the number of diodes connected to its output line.

In the circuit diagram the eight horizontal lines represent the gate outputs, the requisite inputs being made by the diode links to the eleven vertical lines from the number keys and the reset line.

The matrix is built using the same technique as was employed for the display matrix (Part 3) with a small piece of Veroboard providing the vertical output lines to the latches and the key inputs being wired to the horizontal strips on the mother board.

Remember that it is necessary to make guide funnels on the blank side of the small piece of Veroboard to ease the location of the diodes prepriated to the mother board, and most important, the cathode end of the diodes should be mounted next to the mother board.

The outputs from the matrix drive the PRESET and CLEAR inputs of the four latch bistables, which do not use their D inputs or CLOCK inputs in this application (IC27, IC28).

The use of SN7474 flip-flops in this position is a bit extravagant, since a couple of SN7400s cross coupled to form four latches would work just as

well and can be incorporated if desired, the more versatile SN7474s being used in the prototype to allow for possible future modification to enter data automatically from a source such as a tape reader.

## FUNCTION CODER

Unlike the number coder and latches, the function coder and latches do not need a separate set of coding gates, the latches being built from SN7410 three input NAND gates, ICs 23 and 24, and the two inputs to each gate left after making the latch coupling are sufficient to provide the gating required to encode the arithmetic keys.

The E<sup>2</sup> key is coded in the same way as MULTIPLY and a diode D103 is used to facilitate this.

## EQUALS KEY

Pressing the EQUALS key is the signal to start the selected arithmetic programme, and as may be expected, when it is pressed several things happen at once.

The earth appearing on the EQUALS line:

- resets the number latches via the matrix;
- inhibits the generation of a clock pulse which would normally result from the previous reset (see G2, Fig. 4.3);
- sets the decimal point latch IC22 to allow subsequent clock pulses through to the counter (this latch may have already been set by operation of the DECIMAL POINT key during figure entry).

When the key is released and the earth disappears the resulting positive going signal on the line is "debounced" and used to trigger the START PROGRAMME monostable IC26 via a simple diode gate D101, D102. The output from the monostable is a very narrow pulse which is used to initiate the programme sequence. The diode gate is required so that the programme can also trigger the monostable to generate a "RESTART" pulse required in some arithmetic sequences.

## DECIMAL POINT NORMALISATION

When the decimal point latch is set clock pulses are allowed through to the SN7490 decade counter IC14, which in effect counts the number of figures after the point in a number entry. The contents of this counter are continually compared with the decimal point switch output so as to detect a state of equality.

The thumbwheel switch output is already in a binary code though of an inverted form so that a logic "1" is represented by an earth connection and

# COMPONENTS...

## KEYBOARD PANEL

### Resistors

R37, R38 5.6kΩ ¼W ±10% carbon

### Integrated Circuits

IC13 SN7404  
 IC14 SN7490  
 IC15 SN7486  
 IC16 SN7420  
 IC17 SN7410  
 IC18, IC19 SN7450 (or SN7451) (2 off)  
 IC20 SN7401  
 IC21 SN74121  
 IC22, 23, 24, 25 SN7410 (4 off)  
 IC26 SN74121  
 IC27, IC28 SN7474 (2 off)

### Capacitors

C7, C9 22µF 15V elect. (2 off)  
 C8, C13 10µF 15V elect. (2 off)  
 C10, C11, C12 0.047µF (3 off)

### Switches

S2 Birch Stolec EB10N 1248 and a pair of end plates  
 S3-S23 On/off push button (Bulgin type MP22, white 12 off, black 9 off)

### Lamp and holder

LP9 6V 40mA lamp and holder (Bulgin type D22)

### Diodes

D57-D103 West Hyde type "red" (47 off)

### Miscellaneous

9.5in×3.3in 0.1in matrix Veroboard


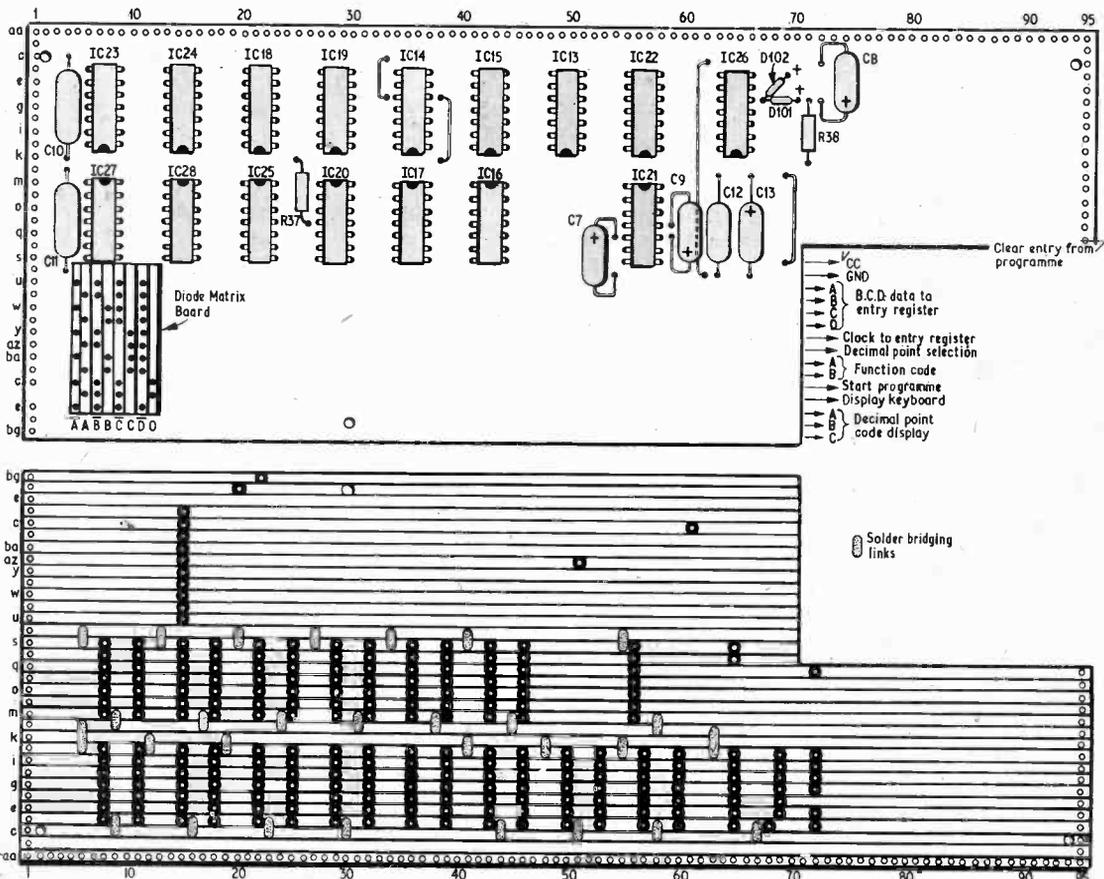


Fig. 4.4. Layout of the components on the Veroboard panel and the cuts which must be made in the copper strips. The links shown are for the power supply lines only and can either be made above or below the board. The black dots on the "diode matrix" board show the positions of the diodes which are arranged with the cathodes towards the main panel

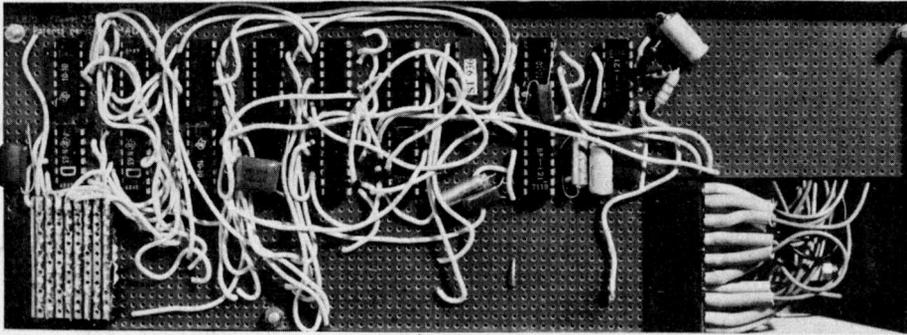

A photograph of the keyboard logic panel in the prototype. The edge connector is an optional extra as wires can be soldered directly to the board

logic "0" by an open circuit. This suits our purpose admirably since the SN7486 used as a comparator, IC15, gives a "1" from each of its gates when its inputs are exactly opposite.

By comparing the true counter outputs with the complement switch outputs a comparator is formed which gives three "1" outputs when the count equals the switch setting. These three ones are used to enable a gate IC16, which in turn sets a latch, IC17, the output of which forms the input to G5 of Fig. 4.5 and serves to shut off the supply of clock pulses to the entry register.

### DISPLAY CONNECTIONS

The position of the decimal point in the display can be governed either by the contents of the counter, IC14, or by the thumbwheel switch setting depending on a command from the programme.

Switching between these two sources is carried out by the AND OR INVERT gates IC18 and IC19, but note that for this purpose the outputs from the thumbwheel switch are inverted by IC13, to make them compatible with the counter outputs. The selected point data is fed to the display via a three line bus.

### OVERFLOW INDICATION

If an OVERFLOW condition is detected during an arithmetic operation a "1" input on the OVERFLOW line drives three SN7401, IC20, gates in parallel to switch on the panel indicator bulb. The correct procedure is then to use the CLEAR key to erase all data and then re-enter the problem in a rescaled form. It is necessary to parallel connect three gates for this job because of the current requirements of the bulb.

### PROGRAMME RESET

To return the keyboard to its correct state for a further calculation it is necessary to rest the DECIMAL POINT and EQUALS latches and the decimal point position counter. This is carried out by a CLEAR ENTRY command from the programme which, as its name implies, also clears the contents of the entry register.

### CONSTRUCTION

The layout of the Veroboard panel is shown in Fig. 4.4, the panel itself being cut to size from a West Hyde type 122 board.

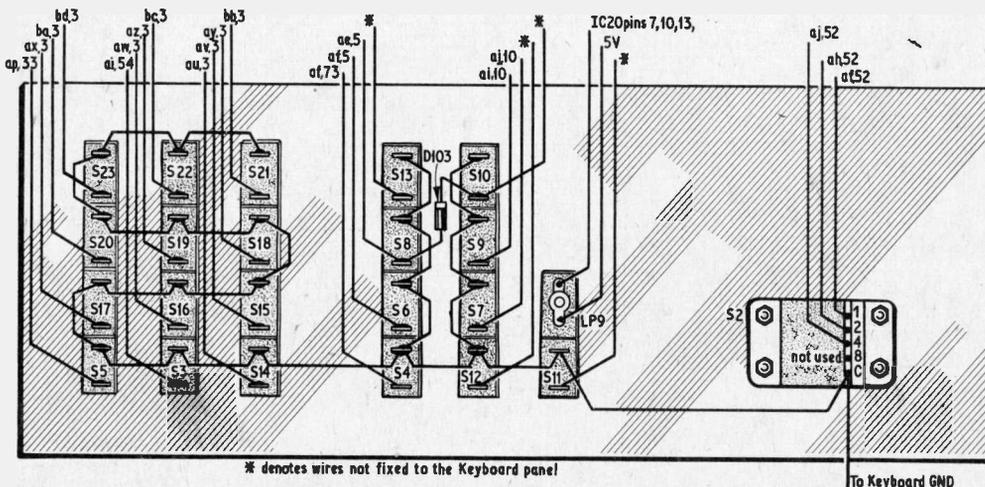


Fig. 4.5. The switches are wired as shown. All wires except those with an asterisk go to the panel shown in Fig. 4.4

The finished panel will be mounted upside down under the keyboard proper, affixed to the recessed wooden blocks either by means of wood screws, or, as in the prototype, by captive 6B.A. bolts cemented into the blocks with Araldite.

Needless to say, it is advisable to make all the board fixing arrangements before commencing the wiring.

Wiring up is carried out as before with thin single core wire, using terminal pins where necessary to increase the wire handling capacity of a particular pad.

Off board wiring is achieved with thin flexible stranded wire left long enough that the board can be easily removed for access, but not too long that stray pick-up could become a problem.

An edge connector was used to carry some of the off-board wiring in the prototype to help with development, this would not be necessary, or even advantageous to any significant extent with later versions, due to the very large number of interconnections required in all.

The switches are wired up as shown in Fig. 4.5.

## TESTING

As with the display board last month it is advisable to wire up the keyboard logic a section at a time, testing each block before proceeding. In this way small mistakes can be easily discovered and dealt with before they become buried in several different circuit blocks.

Almost all the logic can be tested at the wiring stage without undue complication, outputs being monitored with a multimeter or by connecting them temporarily to the display board input if desired. If the latter course is chosen remember that the display board requires an inverted B.C.D. input, which while easily accommodating the decimal point outputs and function code outputs, will require temporary connection to the  $\bar{Q}$  rather than the Q outputs of the figure latches for correct display.

The clock pulse output is long enough to be detected on a meter which is an advantage for tests of this type, the EQUALS triggered START pulse is however far too short to be detected in this way but fortunately this part of the circuit is quite simple and can be left unchecked at this stage.

**Next month: Entry Register (constant store, entry register and multiplexer)**

# POINTS ARISING

## SQUARE WAVE GENERATOR (Sept. 1972)

In the lower half of Fig. 6, the connections for the switch should read as follows reading from top to bottom:

- (a) Top group is S1b numbered 1,2,3,W,4;
- (b) Bottom group is S1a numbered 4,3,2,1;
- (c) S1b wiper should read S1a wiper.

# NEWS BRIEFS

## TECHNICAL INFORMATION SERVICE

A NEW technical information service, aimed at giving firms, corporate bodies, instructors, students, and others engaged in educational work, advice on correct electrical installation practice according to I.E.E. "Regulations" has been established by the National Inspection Council for Electrical Installation Contracting.

The service is confined to technical matters and excludes advice on commercial or trading aspects, industrial or labour relations, and information relating to manufacturers' products.

The aim is to promote a high standard of installation and maintenance safety of electrical wiring and appliances. The subscription fee is £3.50 per year to cover the services offered. Further information is available from the Council at Trafalgar Buildings, 1 Charing Cross Road, London SW1A 2DT.

## NEW POCKET CALCULATOR

WHAT is claimed to be the world's smallest electronic calculator has just been announced by the British company Sinclair Radionics Ltd. At only just over  $\frac{1}{2}$ in thick and  $5\frac{1}{2}$ in  $\times$  2in this can really claim to be a pocket sized calculator.


Known as the Sinclair Executive this calculator embodies many new techniques. Firstly the single MOS chip which forms the calculator consumes a mere 20 mW of power making it possible to run the whole machine from three mercury cells of the type used in hearing aids. This is made possible by switching off the i.c. completely between clock pulses relying on the capacitance of the MOS elements to store the information. Secondly the clock rate is reduced when the calculator is not performing a calculation so as to conserve power.

The battery voltage is just sufficient to drive the display thus eliminating the usual dropper resistors which consume power.

The keyboard was specially developed for the calculator being only 4mm in depth. The contacts are gold plated and the keys are arranged so that it is virtually impossible to touch two at the same time.

The L.E.D. display has a capacity of eight digits. The calculator can perform all the usual arithmetic functions as well as automatic squaring, reciprocals and can operate in either fixed or floating decimal point mode. It also has a memory for calculations with a predetermined factor.

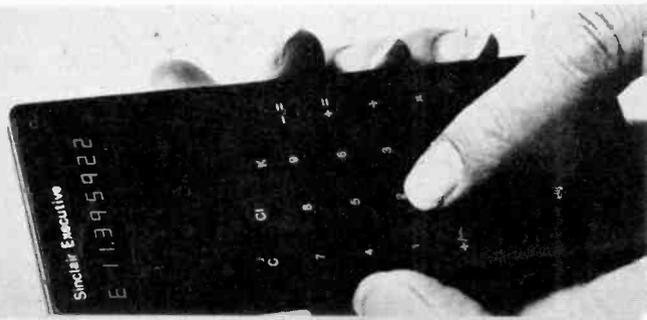Although, at £79 this calculator is not the cheapest on the market, it must pose quite a threat to the present Japanese domination of the calculator field.



# report from AUSTRALIA

BY J.M.WALDIE

In this report, the main theme will be the audio scene, which again should be of interest to intending migrants and visitors.

Audiophiles here have a very large range of components from which to choose; it is likely that the range encountered in the average store will be greater than in a similar situation in the U.K. The possession of a respectable audio system, at least in the large cities, appears to be the rule rather than the exception, despite the "outdoor life" philosophy of the average Australian.

## LOCAL PRODUCTS

The number of companies producing audio systems is relatively small. There are about six brands of Australian-made amplifiers (including Leak and Philips); only two very simple belt-driven turntables are produced here; I understand that there are only two locally produced reel-to-reel recorders and only one cassette system. There are, of course, several brands of "mid-Fi" modular grams and radiograms, including such brands as Kreisler (division of Philips); AWA (Amalgamated Wireless Australia), Thorn, Pye and HMV.

## IMPORT TRADE

However, there is sufficient industry to warrant relatively high import surcharges—designed to protect local manufacturers (which, in some areas, are non-existent). Despite this, Japanese equipment dominates the retail trade, followed by British, German, Scandinavian and—to an increasing degree—American audio components.

For example, of the 30,000 reel-to-reel mains-operated recorders and decks imported in 1970-71, 26,000 came from Japan. Some \$A 2 million worth (F.O.B. values) of amplifiers also arrived in the same period, of which well over half also came from Japan, and approximately one-quarter (in terms of value) from the U.K.

The British, however, have the lion's share of the turntable market: of the 200,000 units imported in the year ending June 1971, 176,000 came from the U.K. This is largely due to the practice of installing Garrard and BSR decks in mass-produced "unit-audio" systems.

There is a very wide range of loudspeakers—both imported and home-grown—available, and the Australian audiophile has a bewildering selection from which to choose. There are three locally-made brands of any consequence, and some very presentable designs have been issued. Japanese cabinets again dominate the imported systems. It is in this area that the Americans have been active, promoting the more expensive brands such as JBL, A.R., Marantz and Advent.

## QUADRAPHONY

Largely due to the Japanese dominance in Australia in the audio field (Japan is one of Australia's largest customers for ore and coal; consequently the trade relations between the companies are maintained at a very close level), the current interest among audiophiles is the idea of 4-channel sound.

The battle between proponents for the CD-4 discrete system of quadraphonic disc reproduction (JVC/National/RCA) and the various matrix methods for obtaining more or less the same result (dominated by Sony's SQ system), is now in full swing.

Records produced by both methods are now available; the record manufacturers appear to be taking sides but showing apparent preference for the matrix method. It has been announced, for example, that EMI, with CBS, have opted for the Sony SQ system, but the decision to market SQ records will depend on demand. This demand will presumably originate from new owners of SQ equipment, but who would buy such equipment without a guaranteed source of quadraphonic records?

This chicken-and-egg situation is likely to delay still further the final decision. On the other side of the fence, aurally speaking, RCA have announced, in America, that eventually all records issued by that particular stable will be "in discrete" quadraphony, a move that must be followed not only here but worldwide. And to confuse matters even more, according to local sources of information, A&M records are being matrixed to the Sansui QS method (not necessarily compatible with Sony's SQ) and two big German companies, Polydor and Deutsche Grammophon, are opting for a discrete system not necessarily similar to JVC/Nivico.

Record manufacturers I spoke to locally all indicated that the outlook was in such confusion that nobody really knows what is happening next.

## ORIENTAL CUSTOM

Australian audiophiles may have an extensive selection of audio equipment available but they don't grow on trees. For English equipment, the list retail price is likely to be double that in the U.K. For example, a Garrard Zero 100 deck has a list price here of \$A 269 (about £120) which compares with the U.K. list price of £54. On the other hand, the difference in price of Japanese equipment is very much less; a Sansui SD 5000 deck is listed here at \$A 756 (£345) which compares to £328 in the U.K.

This, of course, explains to some extent why Japanese equipment is so popular. However, we not only import oriental equipment but, to some extent, their methods of selling; it is usual to "haggle" over prices and the published list prices are something of a myth. Moreover, it is always possible to "trade-in" an article, which might not even be electrical.

## COLOUR TELEVISION

It was recently announced that Australia will "go colour" in March 1975. The system to be adopted will be the 625-line PAL format and all four Sydney stations (1 national, 3 commercial) are in the process of preparing their studios and transmitting equipment.

The manufacturers, however, are treating the news with some trepidation; on the one hand, it could be regarded as a shot in the arm for the electronics industry, but a real concern is being expressed regarding imported receivers which, at the current import rates, could possibly be landed and sold at prices below those expected for locally-produced sets.

The matter will be discussed with the Tariff Board, who decide the magnitude of import duties applicable to any imports. And there are a number of critics who feel that, at an anticipated price of £500 for a 25in set, the sales to Australians, who for the most part regard television as a distraction rather than as a necessary part of life, may just not warrant the large initial outlay.

# NEXT MONTH

## SPECIAL SUPPLEMENT

### Electronic MUSICAL INSTRUMENTS

A SURVEY OF THE COMMERCIAL SCENE

♫ ORGANS

♫ GUITARS

♫ EFFECTS UNITS



# SYNTHESISERS


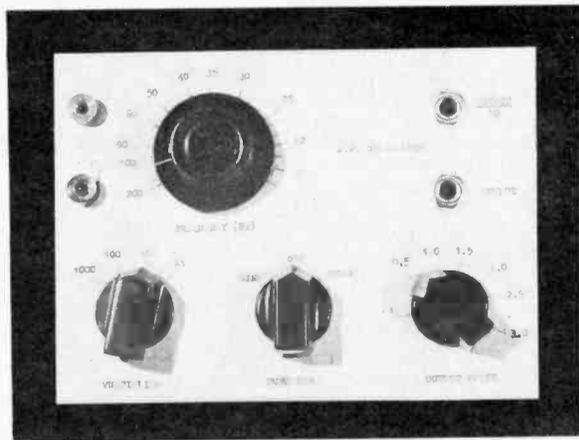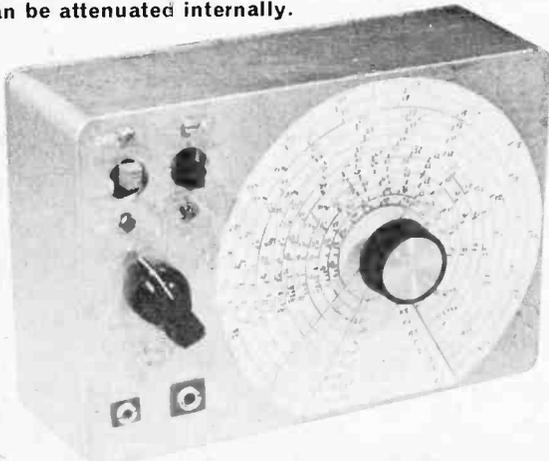
## A.F. SIGNAL GENERATOR

For checking and measuring the characteristics of audio equipment, including frequency response, distortion, power output, signal to noise ratio, and dynamic range, one of the most important aids is an a.f. signal generator.

This instrument provides a sine wave output in the frequency range 19Hz to 200kHz in four bands. Square wave pulses from 19Hz to 20kHz are also available. Maximum output is just over 1V r.m.s. and can be attenuated internally.



## SIMPLE C-R BRIDGE

Ever had the frustration of finding a capacitor or resistor whose only fault is that the marked value is indecipherable? Now your problems can be over with this simple C-R Bridge.


Values of resistor or capacitors can be determined simply by turning a pointer until the signal from an audio generator is reduced to a minimum.

There is no meter so the unit is inexpensive and robust. The components are readily available and the instrument is easy to construct.

PRACTICAL

# ELECTRONICS

NOVEMBER ISSUE ON SALE OCTOBER 13

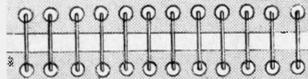

# INDUSTRY NOTEBOOK

By Nexus



## VALUE ON THE BRIDGE

There was a bumper gathering of 300 delegates at the I.E.E. conference on *Advances in Marine Navigational Aids*. They came from all over the world to hear and discuss 55 papers.

It was a heady occasion embracing just about every navigation technique all the way from visual aids (the earliest known lighthouse was at Alexandria about 265 B.C.) to such twentieth century exotica as "System of location of balloons, ships or buoys by means of a low-orbiting satellite".

For the student of marine electronics the occasion was fascination itself. For the practical mariner, expected to foot the bill for equipment as well as understand and evaluate all the rival and complementary systems available, it was more like a nightmare.

The Chief Marine Superintendent of the B.P. Tanker Company Ltd., Mr R. Maybourn, put his finger on the shipowner's problem in his paper "Cost benefit and related factors—a shipowner's point of view". A navigation outfit for a modern tanker has an installed cost of almost £45,000 using fairly conventional equipment. Using some of the sophisticated systems described at the conference could result in a doubling of the cost with only dubious advantages.

## EXOTIC IDEAS

Mr Maybourn criticised the electronics industry for developing expensive and exotic ideas without adequate reference to the shipowners, and which are not clearly related to adequately defined problems or needs. He suggested that we often seem to have the solution first and the problem becomes one of finding a need to which to match it.

On computerised anti-collision systems, he wondered whether the problem had been adequately identified or even if the current problem is being solved. He referred to the computer as something which mesmerises the electronics engineer "itching to use its spare capacity in much the same way as an idle hand does a work study practitioner".

What Mr Maybourn asked of the industry was for far more reliability in existing equipment, and some element of standard design in equipment in regard to dimensions, methods of fitting and presentation of data which, he said, was chaotic and certainly would not be tolerated in the aircraft industry.

This point of view deserves some sympathy but should be examined in an historical perspective. Most of the exciting new concepts such as satellite navigation and the v.l.f. Omega system have their origin in military developments as, indeed, did marine radar and Decca Navigator before them. These last two items are now accepted as standard fit and comparatively inexpensive aids. What Mr Maybourn and the shipping industry are getting is the best of both worlds.

## HIGH RELIABILITY

If the electronics industry demonstrated anything at all at the Conference it was that today's technology is available with high reliability and at a bargain price, while tomorrow's technology is being seriously considered and will be available in due course to merchant shipping at a fair price.

Timing is terribly important. The Marconi "Predictor" anti-collision radar system has been available for four years, yet less than a dozen have been sold. It was, and is, a brilliant example of electronic engineering and necessarily expensive. Decca Radar brought out a simple anti-collision radar with limited capability about the same time at about half the price and have sold some 700 equipments. It was what the shipowner wanted at a price he could afford. But the outlook for "Predictor" remains bright and Marconi still expect it to do well. It was only the timing that was seriously adrift.

## TOUGH COMPETITION

On the other hand, you don't need to invent new technology to invent new systems. I was at the inauguration of the Southampton Harbour Radar system, said to be the finest in Europe if not in the whole world. I searched in vain for completely new technology in both the operations room and the equipment areas. Decca Radar, the prime contractors, had done a wonderful systems engineering job

using off-the-shelf equipment freely available on the open market.

I was also at the unveiling of a new marine radar display concept introduced by Kelvin Hughes and reviewed at the Conference by marine consultant Captain J. P. Stewart. The system uses television techniques and is a notable advance, yet the only device in any way unusual for a radar is a light-sensitive "image retaining panel". This panel has been commercially available for ten years but nobody had apparently thought of using it in a radar application until Kelvin Hughes originated the idea.

What is worrying the marine electronics industry is an unrealistic pricing policy. Competition is so severe that few companies are making sufficient money to support future civil (as distinct from naval) R and D at a reasonable level.

## TXE2 TAKES TO THE ROAD

The Post Office is always fair game for the knockers and I have knocked away in my time with the best of 'em. SDS Components Ltd, the Portsmouth-based component distributors have gone one step further than knocking by abandoning postal delivery and employing Securicor to make all deliveries.

But the Post Office is not all that bad, although you might still think so when out driving and you get stuck behind one of the eighty or so 27ft long trailers now being built to house mobile electronic telephone exchanges. Each of these will house a Plessey TXE2 equipment and will be on the move to a site where 1,000 would-be telephone subscribers can stop biting their nails with frustration and get hooked into the network.

The Post Office already has 250 mobile exchanges of conventional types but these can only handle 400 lines each. The TXE2 electronic exchange in two trailers can handle 1,000 and a dual installation housed in three trailers will serve 2,000 subscribers.

Deliveries commence next May and the investment by the Post Office is £3 million. At least they are trying to keep pace with a demand that seems insatiable.

## GOONHILLY 3

I was sorry to see that the 10th anniversary of the Post Office satellite station at Goonhilly Downs passed with so little notice. The occasion was marked by the inauguration of Goonhilly 3 making the station the busiest satellite terminal in Europe.

It seems more than ten years since we were all startled by *Telstar 1* and *Relay* before *Early Bird*, the first of the *Intelsat* satellites, really got going with a full commercial service.

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS AND AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated telescopic aerial, for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. Switched earpiece socket complete with earpiece. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser with VHF section. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS

**£8.50**

P.P. & INS. 50p  
(OVERSEAS P. & P. £1)




### ROAMER EIGHT Mk. I NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.98** P.P. & INS. 41p (OVERSEAS P. & P. £1)


### ROAMER SEVEN Mk. IV

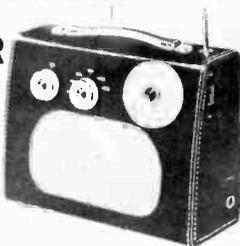

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxemburg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.

TOTAL BUILDING COSTS **£5.98** P.P. & INS. 41p (OVERSEAS P. & P. £1)

### ROAMER SIX

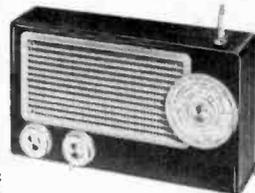

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£3.98** P.P. & INS. 30p (OVERSEAS P. & P. £1)

### POCKET FIVE



3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2in x 1 1/2in x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£2.29** P.P. & INS. 21p (OVERSEAS P. & P. 63p)

### TRANSONA FIVE



5 TRANSISTORS AND 2 DIODES  
3 TUNABLE WAVEBANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


TOTAL BUILDING COSTS **£2.50** P.P. & INS. 22p (OVERSEAS P. & P. 63p)
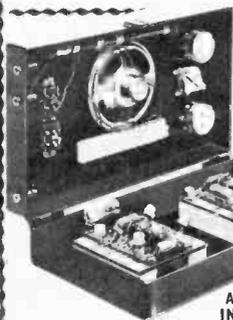
### TRANS EIGHT



8 TRANSISTORS AND 3 DIODES  
6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£4.48** P.P. & INS. 31p (OVERSEAS P. & P. £1)



### NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; 3" Speaker; Terminal Strip; Ferrite Rod Aerial; 3 Plugs and Sockets; Battery Clips; 4 Tag Boards; Balance Armature Unit; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

ALL PARTS INCLUDING CASE AND PLANS **£5.50** P.P. & INS. 31p (OVERSEAS P. & P. £1)

## RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- |               |                          |              |                          |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN    | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT  | <input type="checkbox"/> | TRANS EIGHT  | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX   | <input type="checkbox"/> |
| POCKET FIVE   | <input type="checkbox"/> | EDU-KIT      | <input type="checkbox"/> |

Parts price list and plans for.....

Name .....

Address .....

P.E. 46

FULL AFTER SALES SERVICE

- ★ Callers side entrance Barratts Shoe Shop
- ★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday



# PATENTS REVIEW...

## MOVEMENT DETECTOR

BP 1 267 194

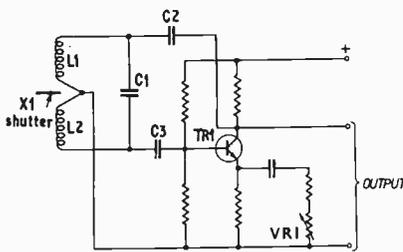


Fig. 1

British Patent 1 267 194 from Rotameter Manufacturing Co Ltd describes a simple but probably very effective circuit for sensing and registering very small physical movements of objects.

The basic circuit is shown in Fig. 1 and relies on a Hartley oscillator with two magnetically coupled inductors L1, L2, a bridging capacitor C1 and d.c. blocking capacitors C2, C3. The variable resistor VR1 controls, along with the mutual inductance of inductors L1, L2, the amplitude of the circuit oscillations. The frequency of the oscillations depends upon the values chosen for the inductors L1, L2 and capacitor C1.

A small shutter X1, formed from non-magnetic but electrically conductive material (e.g. copper, brass, etc.), is movable into and out of a small gap which is left between the magnetically coupled ends of the inductors L1, L2.

If the object whose movement is to be sensed is mechanically coupled to the shutter, then any movement, however slight, will cause a change in the amplitude of oscillation. This change may in some cases be reasonably linear.

By amplifying TR1 output a direct dial readout can be obtained or, alternatively, the amplified output can be fed to a "pot coil" electromagnet arranged to apply a restoring force to the object which has moved. This restoring force will tend to move everything back to the original or null position, i.e. seek equilibrium in this state.

Component values are suggested which will detect and register a 0.025mm movement with a transistor output change of 200 millivolts.

## ELECTRONIC SPEEDOMETER

In conventional electronic speedometers there is sometimes a problem in raising sufficient control voltage to not only display the speed, but also record the maximum speed obtained. Mechanical systems can introduce an inaccuracy of around 15 per cent which can be hopeless when the engine speeds are in the order of 10,000 r.p.m.

Porsche KG now claim (BP 1 254 486) a form of electronic speedometer which should be free from such problems. In Fig. 1 Porsche show how pulses derived from the ignition coil (at a frequency directly proportional to the engine speed) are shaped, integrated by the filter circuit and fed via the servo amplifier to a reversible servo motor. This motor drives the speedometer pointer through gearing to provide a direct readout indication of speed.

The car battery voltage is fed to the stabiliser to give a stabilised output voltage which is fed to the shaper and is also tapped by the servo motor to provide a feedback voltage to the servo amplifier. The servo motor also drives a maximum speed indicator through a ratchet which can be released for zeroing by a spring loaded button.

If it is thought wise, and safe, to provide an automatic switch-off for the engine, e.g., to avoid stripping the car gears, the speed voltage signal at the filter can be compared by the critical speed circuit with a predetermined limiting value to operate an ignition interrupter switch.

Instead of sensing pulses derived from the ignition coil, an

independent inductor associated with the engine shaft can be used to produce the necessary pulses.

## PATENT ACTIVITY IN THE OPTICAL FIBRE FIELD

At least two different uses for light fibres in motor cars have now been patented by Joseph Lucas (Industries) Ltd.

In the first patent, published a few months ago (BP 1 258 395) Lucas described and claimed as novel the use of a light fibre with one end set in the door frame and the other behind a dashboard warning indicator. The door itself carries a mirror which is arranged so that light is reflected from a lamp into the doorframe end of the fibre only when the door is closed. Light thus emerges from the other end of the fibre to illuminate the dashboard indicator when the door is safe.

In their more recent patent (BP 1 264 325) Lucas claim as novel the use of fibres extending variously from all the crucial car driving lights (headlights, sidelights, etc.) to various dashboard instruments. Thus any unlit instrument on the dashboard is a fail-safe signal of an extinguished driving light.

The above patents are only reported briefly, because they are technically simple. But in view of recent published correspondence on this topic they may be interesting references for anyone working in the field. Incidentally, it should be borne in mind that although the patents have only recently been published, they were applied for several years ago.

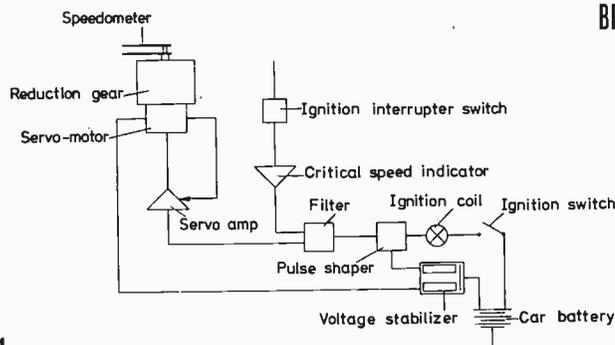


Fig. 1

BP 1 254 486

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## FIRE ALARM KIT

The new fire regulations require all properties which provide overnight accommodation for more than six people to be fitted with an acceptable fire alarm system. To meet this need **Ramick Security Services** have developed a new "Fire Alarm Kit" complete with instruction and wiring diagram to enable the handyman or an electrician to install a system for the smaller size hotel or boarding house.

The kit costs £30 complete and comprises a Control Unit; Heat-switch; Preswitch; Testswitch and a 12V d.c. 4in gong alarm bell.

The control unit operates from the mains a.c. supply but the voltage to the sensors is only 12V d.c. A battery is incorporated in the unit together with an automatic change-over circuit so that in the event of a mains failure the installation remains operative and changes back to a.c. supply when reconnected.

Whenever the alarm bell rings it continues until the control unit is reset manually. The control unit is contained in a pressed steel case, suitable for wall mounting, and has a mains indicator light and an on/off switch on the front panel.

The Heatswitch is a bi-metallic switch with a combined rate of rise and fixed temperature automatic fire detector to B.S. 3116. The contacts close when the temperature reaches 135°F (57°C) or if there

is an unusually rapid increase in temperature. The unit can be mounted in any position and provides coverage of approximately 500 square feet per heatswitch.

The Preswitch is a push button unit with a cast aluminium front plate and can be supplied for surface mounting or flush mounting. Breaking the glass front operates the button which activates the alarm.

The Testswitch has a manually biased push button and indicator light complete with housing and is designed for fitting at the end of the twin wire circuit connecting the sensors to the control unit. When the switch is operated the indicator light is energised (and remains energised until the control unit is reset) and the control circuit, external wiring and alarm bell is checked.

Further details can be obtained from **Ramick Security Services**, The Lodge, Randalls Road, Leatherhead, Surrey.

## PRINTED CIRCUIT BOARDS

Sometime ago we mentioned a versatile printed circuit board called **Nippiboard** marketed by **NIP Electronics**.

Although these boards have proved very successful, from the response of users they seem to suffer from two limitations. These limitations are that the boards are not pre-drilled and, more important, do not take integrated circuits.

Now, **NIP Electronics** have introduced a new range of boards called "NIP-E-Boards." These boards are available pre-drilled and are suitable for transistor circuits, integrated circuit designs or a combination of both.

The integrated circuit range of boards were designed in order to cater for the vast expansion of component manufacture in standardised DIL packages, such as relays, readout devices, as well as integrated circuits and transistor arrays.

All boards are made from s.r.b.p. or glass fibre and are available pre-drilled or undrilled according to choice.

The designs of the boards are such that they will all accept edge connectors; a range of card handles, stand-off mounting pillars, and edge connectors is also available.

Further details and prices of the **NIP-E-System** can be obtained from **NIP Electronics**, P.O. Box 11, St. Albans, Herts.

## POCKET METER

Readers should find the **TS-60R Multimeter** from **West Hyde Developments** an excellent purchase.

This pocket multimeter makes no pretensions to be up to professional standard but still covers most ranges needed for checking out the majority of circuits published in this magazine.

The meter movement is a 1000Ω/V type and the ranges covered are: a.c. voltages 0-15V, 0-150V, 0-1000V; d.c. voltages 0-15V, 0-150V, 0-1000V; d.c. current 1mA, 150mA; resistance 100kΩ. A feature of the meter is the "printed circuit" rotary switch.




The meter costs only £2 and in the event of a meter breakdown it is probably cheaper to throw it away and buy a replacement, whereas with the more expensive counterpart it would cost more to repair than the purchase price of the **TS-60R**.

Further details of the **TS-60R** multimeter can be obtained from **West Hyde Developments Ltd.**, Ryefield Crescent, Northwood Hills, Northwood, Middlesex.

Whilst on meters, a comprehensive range of **Avometer** spare parts is always held in stock by **Instrument Services** and they are able to offer a rapid **Avometer** repair and recalibration service.

Complete refurbishing to "as new" is claimed to take approximately seven days. The company also offers a similar service to users of **G.E.C.** "Selectest" and "Minitest" instruments.

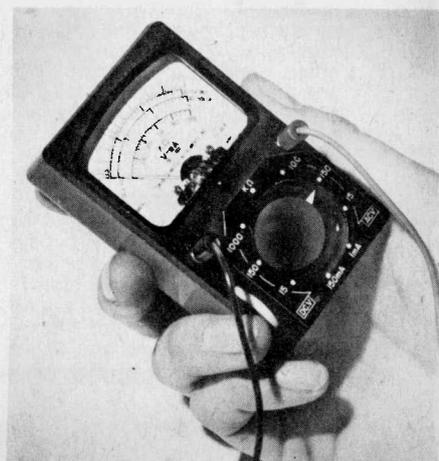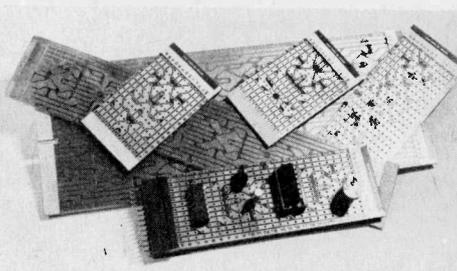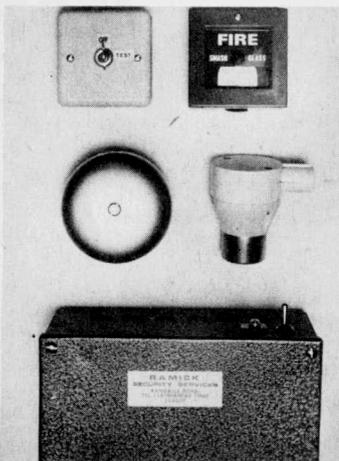Further information of the meter repair service can be obtained from **Instrument Services Company (London) Ltd.**, 208 Maybank Road, London E18.



(above) NIP-E-Boards from NIP Electronics  
(left) Ramick Fire Alarm Kit  
(right) TS-60R Multimeter from West Hyde

# AUDIO SUPPLIES THE BIG DISCOUNT HOUSE

WE HAVE **SLASHED** PRICES AS NEVER BEFORE ON THE FOLLOWING TOP QUALITY MAKES OF EQUIPMENT  
**BOWERS & WILKINS • BSR • AMSTRAD • ADC • AUDIO TECHNICA • CAMBRIDGE  
 AKAI • ROLA CELESTION • DECCA • EAGLE • EMPIRE • FIDELITY • FERROGRAPH  
 GARRARD • GOLDRING Lenco • KOSS • KEF • HOWLAND & WEST • METRO SOUND  
 LEAK • WHARFEDALE • QUAD • ROGERS • SINCLAIR • VICEROY • PHILIPS • PIONEER  
 ROTEL • REVOX • SANSUI • SCAN ELTRA • TRANSCRIPTORS • SONAB • SME  
 PEERLESS • SONATONE • SHURE • ORTOFON • KORTING • NEAT • SENNHEISER etc..**

**ADC  
10E MKIV**  
PRICE  
**£20.50**  
p.p.10p.

**SYSTEM  
AS 2000**



OUR PRICE  
**£69** p.p. £1-50  
SAVE OVER £53

**GOLDRING  
G 800 E**  
PRICE  
**£8-99**  
p.p.75p

**BOWERS  
& WILKINS  
DMI SPEAKERS**  
PRICE PER PAIR  
**£54**  
p.p.75p.

**GARRARD  
SP 25 MKIII**  
with Goldring G800  
Deluxe Plinth & Cover  
PRICE  
**£17.50**  
p.p.75p

AUDIO SUPPLIES LTD., Dept. PE10, 50 STAMFORD HILL, LONDON, N.16. Tel: 01-806 3611

**ALSO AT:—**

12 London Road, North End,  
Portsmouth, Hants.  
120 Notting Hill Gate,  
London, W.11

OPENING IN TOTTENHAM  
COURT ROAD, W.1, DURING  
AUGUST AND IN BIRMINGHAM  
DURING SEPTEMBER

WE SPECIALISE IN MAIL ORDER/PERSONAL CALLERS WELCOME. Send Cheques, Money Orders, P/O, Giro, Bank Draft or Cash (Registered). 24-Hour Securicor delivery £1-50 extra to Postage and Packing. Personal Callers: Note: We are easy to get to by Public Transport. Open: Mon., Tue., Wed., Thur., 9.30 to 6.00 p.m. LATE NIGHT FRIDAY: 9.30 to 7.30 p.m. Sat.: 9.30 to 5.00 p.m. Send large stamped addressed envelope with all correspondence (except orders). Cheques are only accepted from Personal Callers

if backed by a relevant bank cheque card. Payment by Barclaycard accepted by arrangement. All prices are subject to changes as and when necessary. Credit facilities available on purchases of £50 or more for Personal Callers only. Send for further details. For any information on goods write to manufacturer or importer concerned NOT US. This advertisement is a small selection from our most comprehensive quality range. Send 5p and large S.A.E. for our complete price list.

# TECHNICAL TRAINING

*in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunication Techns'. Certs.
  - Radio Amateurs' Examination
  - General Radiocommunications Certificate
  - C. & G. Radio Servicing Theory
  - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

**Examination Students coached until successful**

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics  
Member of the ABCC Accredited by the CACC

## ICS

EST. 1891

## INTERNATIONAL CORRESPONDENCE SCHOOLS

**Dept. TA25, Intertext House, Stewarts Rd., London SW8 4UJ**

Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam.)

**NAME** \_\_\_\_\_ **AGE** \_\_\_\_\_  
(Block Capitals Please)

**ADDRESS** \_\_\_\_\_


3/72

INTERNATIONAL CORRESPONDENCE SCHOOLS

## PRINTED CIRCUIT KIT

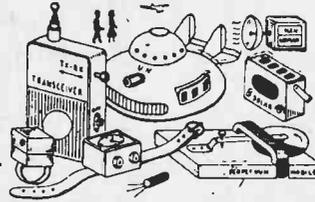**BUILD 50 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX**

**CONTENTS:** (1) 2 Copper Laminate Boards 4 1/2in x 2 1/2in. (2) 1 Board for Match-box Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 50 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



**EXPERIMENTER'S  
PRINTED CIRCUIT KIT**  
**60p**

Postage & Pack. 40p (UK)  
Commonwealth:  
**SURFACE MAIL 15p**  
**AIR MAIL 60p**  
Australia, New Zealand,  
South Africa, Canada

- (1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photo-cell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. (10) Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62in x 0-95in x 0-25in. (11) Wristwatch Radio 1-15in x 0-80in x 0-55in. (12) Ring Radio 0-70in x 0-70in x 0-55in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transmitter (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector Modulators, etc.

**YORK ELECTRICS, Mail Order Dept.**  
**335 BATTERSEA PARK ROAD, LONDON, S.W.11**

*Send a S.A.E. for full details and a brief description of all kits and Projects.*

### P.E. 'GEMINI' STEREO AMPLIFIER

30 watts (R.M.S.) per Channel into 8 ohms!  
Total Harmonic Distortion 0-02%!  
Frequency Response (-3 dB) 20Hz-100kHz!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but is well within the capabilities of the ambitious constructor.

WE CAN NOW SUPPLY A REPRINT OF THE ARTICLES IN BOOKLET FORM. PRICE 55p PLUS 4p POSTAGE. WITH FREE COMPLETE COMPONENT PRICE LIST.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

ALL PARTS AVAILABLE SEPARATELY



**ELECTRO SPARES**

21 BROOKSIDE BAR  
CHESTERFIELD, DERBYSHIRE

QUALITY • SERVICE • VALUE

#### REED COILS

3, 6, 9, 12, 24V Miniature 27p  
Small 27p  
Standard 34p

P. & P. 7p on all orders.

#### REED PUSH BUTTON SWITCHES

Momentary Action  
1 contact £1-00  
2 contacts £1-25  
Illuminated 1 contact £1-30  
Illuminated 2 contacts £1-55

#### REED SWITCHES

Large range of many sizes, types and manufacture  
Popular types:  
E Small n/o 10 for 50p  
A Miniature n/o 24p each  
B Standard c/o 40p each

#### REED RELAYS

Many versions available, popular types: 3, 6, 9, 12, 24V  
Miniature 1/A normally open 56p  
Small 2/E 1 contact 36p  
2/EE 2 contacts 44p  
2/EEE 3 contacts 52p  
STD 3/B change over 87p

#### REELS OF ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g. 50, 100 & 200 grams, Send for prices

**C.B.M. ELECTRONIC COMPONENTS LTD.**  
26 Avon Trading Estate, Avonmore Road, London, W.14

# Readout —

## A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

### Strong objection

Sir—I object strongly to the article *Digi-Cal*. Whilst I can understand people building their own electric organ or colour TV, I am sure nobody with any sense will build this machine at £110. These calculators can be purchased from about £60. Further to this, the cost of a simple counter with Nixie tube readout is approx. £5 per unit, i.e. with a six digit readout this section is approx. £30. Careful design should therefore give a complete calculator for £60. Still not worth making.

As a "Practical" magazine the very least I would expect is for articles to be practical propositions.

G. A. Bobker,  
Unsworth, Bury, Lancs.

I am sorry to hear that Mr Bobker objects so strongly to the *Digi-Cal* series, and though in the light of the latest developments in the field of m.o.s. technology I can sympathise with his comments on price differential, his letter does point to one very important advantage of these current articles.

The logic operations involved in any calculator are necessarily complex, and the new "single-chip" devices are valuable simply because the complex logic has been "wired-up" entirely by the i.c. manufacturer. Mr Bobker's concept of a calculator made from SN7490's and Nixies shows, I am afraid, a lamentable grasp of the way machines of this type operate, and since he himself is active in the circuit design field he could learn a tremendous amount about logic in general and calculating circuits in particular by following the *Digi-Cal* series. I am sure many readers will be glad of the chance to delve into this interesting and relevant field of electronics before the rapid march of technology reduces us all to mindless "wirer-upper" of a circuit which can be built in half an hour but which is

far too involved to be explained to "mere amateurs".

It does seem to be true that calculators are going the way of medium-wave transistor pocket radios, where the vast quantities which can be sold reduce prices to a level where amateur designs are difficult to justify on economic grounds, and to those readers who want a cheap calculator to use immediately without knowing what makes it tick, I can thoroughly recommend the new ready made machines available from retailers at low cost.

For those of us who also want to know what's going on inside, I hope *Digi-Cal* will help. After all, now that single-chip organs, f.m. tuners, and even computers are with us, it may be our last chance.

—R. W. Coles.

### What is the point?

Sir—Over the years I have successfully constructed many of the circuits published in P.E. The amount of enjoyment derived from assembling these projects has been twofold. Firstly, the satisfaction of building something with one's hands and seeing it working and secondly, knowing you have saved quite a bit doing it.

Therefore when you announced the P.E. *Digi-Cal*, which is the sort of project right up my street, I could hardly wait for the August issue to get cracking. Imagine my dismay at seeing the total cost as being approx. £110 when one can buy a ready built article to the same specification for £43.25.

Even if your design had cost the same I would have built it for the satisfaction to be obtained, but I cannot see anyone wanting to construct *Digi-Cal* with such a price difference. So really, what is the point of publishing a design like that.

This is my only criticism so far of an otherwise excellent magazine which I have taken since it first came out.

Brian Harrison,  
Settle, Yorks.

### Beyond reason

Sir—I have been reading PRACTICAL ELECTRONICS since its inception in November 1964 and on average consider about 50 per cent of the constructional projects of interest to me (not that that figure relates to the quantity constructed!). But aren't we getting a little above ourselves with the introduction of a project to build an electronic calculator?

Now I am not one to decry the technical capabilities of your readers (quite the opposite) but what astounds me is the cost. Your author quotes a bulk component cost £110 yet one can buy an equally sophisticated machine (with all the trimmings like leading zero suppression, floating DP, constant key, etc.) for £56 and no extras like replacing over-soldered transistors or mis-wired ic's!

My point, to which I laboriously come, is *what is the function of the constructional feature?* I think it should be a medium through which constructors can promulgate their brainchildren so that readers can build a piece of equipment which is impossible to buy either because it is prohibitively expensive or because no manufacturer's specification matches that of the constructors. The intrinsic pleasure of building is enhanced when one notices that there are still pennies in the pocket.

Come on P.E. Continue to disseminate the superb features that you do but let us keep our exuberant competition with the pros within the bounds of reason.

J. E. Barrett,  
London, S.W.6.


We recognise and understand the bewilderment caused to some readers because of the relatively high cost of building the P.E. *Digi-Cal*. This very creditable project provides a dramatic illustration of the far-reaching effects of rapid and stupendous advances in technology. See Editorial Comment, page 817.

### Advance information

Sir—Could you please inform me if it is possible to purchase a full copy of PRACTICAL ELECTRONICS,



## PREMIER 800 STEREO AMPLIFIER

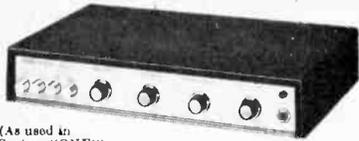

(As used in System "ONE")

A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000Hz  $\pm$  2db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A.

Magnetic 5mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Stereo Headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12 1/2in x 6 1/2in x 2 1/2in

**ONLY £15.00**

Mk. II Version available with Teak Finish Cabinet. £16.25. Carr. 50p.

## PREMIER HI-FI STEREO SYSTEMS

### SYSTEM "ONE"

consists of the Premier 800 all transistor stereo amplifier, Garrard auto/manual record player unit fitted stereo/mono cartridge with diamond stylus and mounted in teak finish plinth with cover and two cloth front loudspeaker systems.

Absolutely complete and supplied ready to plug in and play. The 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Headphone socket. Power on/off. Black leatherette cabinet with aluminium front panel. Size: 12 1/2in x 6 1/2in x 2 1/2in.

**£35** Carr. £1.75



### SYSTEM "TWO"

as above but with slotted front teak finish loudspeakers, Garrard SP25 Mk. III and magnetic cartridge.

**£45**  
Carr. £1.75

### SYSTEM "THREE"

This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and Ceramic pick-up, tuner, tape in and out. Stereo headphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of I.M.F. Speakers size 10 1/2in x 10 1/2in x 9in fitted EMI units complete the matching system.

**£57.75**  
Carr. £1.75

**FREE**

leads and plugs supplied with all systems

## METER BARGAIN

### MODEL GT800 MULTIMETER

A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. Ranges—D.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). A.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). D.C. current: 1mA, 100mA. Resistance: 0-100 Kohms. Decibels: -10 to +22dB at A.C. 10V rms. £2.47. P. & P. 25p.



## CASSETTE TUNER PACK

Aids radio reception to your cassette tape recorder—just slip in this AM tuner pack and select the station required. Medium waveband coverage. 4 transistorised circuit. Same size as compact cassette. Complete with D23 1.5v. battery. Suitable for most top loading cassette recorders. Only £1.50. P. & P. 15p.



### "WELLER EXPERT" SOLDERING GUN

Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat 100/140 watt. 240 volt A.C. £3.95 P. & P. 50p.



"Weller Marksmen" Soldering Iron Lightweight. Air pencil bit, 25 watt. 240 volt A.C. £1.50 P. & P. 16p.



## VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds. £1.72. P. & P. 16p.



## E.M.I. 13 x 8in. HI-FI SPEAKERS

Fitted two 2 1/2in tweeters and crossover network. Available with 8 or 15 ohm impedance. Handling capacity 10W. Brand new. £3.47 P. & P. 50p.



## PREMIER HI-FI OFFERS!

- Rogers Ravensbrook 11 Stereo Amplifier teak **£38.50**
- Rogers Ravensbourne Stereo Amplifier teak **£49.00**
- Metrosound ST20E Stereo Amplifier teak **£25.50**
- Goldingr GL72 less cartridge **£22.00**
- Garrard SP25 111 with Goldring G800 cartridge **£15.00**



Garrard SP25 Mk. III Single Record Player. Fitted Goldring G800 Magnetic Stereo Cartridge. Complete in Teak Plinth with Cover.

Total list Price over £34.

PREMIER PRICE **£18.50**  
P. & P. 50p

**GARRARD AP76 WITH G800, READY WIRED TO 5-PIN DIN IN PLINTH WITH COVER £29.50**

Garrard AP76 less cartridge **£18.80**

**GARRARD 401 TRANSCRIPTION UNIT £27.40**

Garrard 2025 T/C with Stereo Ceramic Cartridge **£8.50**

Garrard 2025 T/C with Stereo Ceramic Cartridge ready wired in teak plinth with cover **£12.45**


Carriage and Insurance 60p extra any item.

### CARTRIDGE BARGAINS!

GOLDRING G800H £5.00; G800 £5.50; G800E £9.50. SHURE M3D £4.00; 3144E £5.75; M55E £8.50; M75EII £10.90.

## SPECIAL OFFER!
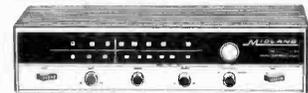
## MIDLAND MODEL 19-520 AM/FM STEREO TUNER AMPLIFIER



A fantastic all solid state stereo receiver at a realistic price. Beautifully styled in streamline design cabinet. Covers AM 535-1,635 kHz and FM 88-108 MHz with built-in stereo multiplex decoder. Input for ceramic phono. Output 2 1/2 watts r.m.s. per channel. Controls: Volume, tone, balance, tuning, AFC, stereo indicator. Speaker impedance 4-8 ohms. Size: 15in x 8 1/2in x 3 1/2in.

**ONLY £25** Carr. 50p



### HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2in speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft lead and stereo jack plug. £2.47 P. & P. 25p.

### VERITAS V-49 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6in x 3in x 2in suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phono plug output. Attractive teak wood grain finish case. Mono Model £3 Stereo Model £3.47 P. & P. 15p.



## GENUINE EMI-TAPE COMPACT CASSETTES LOW NOISE BRAND NEW IN LIBRARY CASES

C60 (List 71p) 53p  
C90 (List 98p) 86p  
C120 (List £1.48) 90p P. & P. 10p each.



## "VERITONE" CASSETTES

In library cases—fully guaranteed.

C60 29p each  
C90 40p each  
C120 52p each  
P. & P. (3 for £1.11) (3 for £1.40) 10p each (3 and over 15p)



## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped— attractively boxed.

TT3 3' 450' POLYESTER	37p	LP8 5 1/2' 1200' ACETATE	75p
DT3 3 1/2' 600' POLYESTER	57p	DT8 5 1/2' 1800' POLYESTER	£1.12
SP5 5' 600' P.V.C.	42p	TT5 5 1/2' 2400' POLYESTER	£1.87
LP5 5' 900' ACETATE	50p	SP7 7' 1200' P.V.C.	82p
DT5 5' 1200' POLYESTER	75p	LP7 7' 1800' ACETATE	75p
		DT7 7' 2400' POLYESTER	£1.25
		TT7 7' 3600' POLYESTER	£2.50

TAPE SPOOLS 3" 5p, 5", 5 1/2", 7" 9p.  
Post and Packing 3" 5p, 5", 5 1/2" 8p, 7" 10p. (3 reels and over Post Free.)

# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



# NEW FROM SAXON.....

STANDARD & CUSTOM-BUILT SOUND EQUIPMENT      MUSICAL INSTRUMENTS, NEW & SECOND-HAND

THREE LOW-PRICED AUDIO MODULES — 100W — 35W — 25W (all rms ratings)

**SA100 £10.90** carr. free

11 transistors—8 diodes  
4½" x 4" x 1"

**SA35 £4.45** carr. free

7 transistors—7 diodes  
4" x 3" x 1"


**SA25 £2.95** carr. free

7 transistors—7 diodes  
4" x 3" x 1"

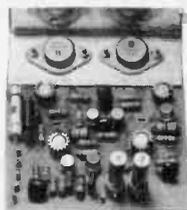**COMPLETELY BUILT AND TESTED — SATISFACTION GUARANTEED**

Employing the latest silicon devices these three modules excel in the field of low-cost high quality audio. All three modules are short and open circuit proof and the 100 watt module has further protection against overheating and faulty inductive loads. All modules may be used with a wide range of supply voltages and loads.

ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRAORDINARILY LOW PRICES POSSIBLE.



**BRIEF SPEC. FOR ALL THREE MODULES**

Response	15–40,000 Hz ± 1 dB
Distortion	0.2% @ 1 kHz
Loads	4–8–16 ohms
Quiescent current	15 mA
Noise	Better than –75 dB
Supply voltage	25–45 volts SA25/35 40–70 volts SA100

**ALL MODULES ARE CONSTRUCTED ON GLASS FIBRE P.C. BOARD**

## STABILIZED SUPPLIES

**PS45**—supplies two SA25 or two SA35. Fully assembled and tested, **£2.85**. MT45 to suit the above module **£2.85**. Carr. PS45 free, MT45 20p.

**PU70** (Unstabilized) drives two SA100, **£6.75**, carriage 35p. **PS70**—Stabilized module for 2SA100, **£4.90**, carriage free. **MT70** transformer for above, **£4.25**, carriage 35p.

## SOUND to LIGHT CONVERTER

This single channel light unit is the ideal low-priced addition to the D.J.'s equipment. It will operate from the bass notes thus flashing lights up to 1000 watts in time with the music. Complete with control and attractive case—fully tested and guaranteed.

**£8.90**

Carr. Free

**120 WATT MODULE** for 8 ohm systems.

Rugged transformer driver stage. **£13.90** carr. 20p or with supply **£18.95** carr. 40p.



**GOODMANS 12P**  
12" 50W 8/15Ω  
only **£10.90** carr. 30p  
Famous British  
25W 12" loudspeaker  
only **£4.95** carr. 20p



**CSE AMPLIFIER £32** carr. free. 70W cont. R.M.S. 100W music. Two inputs, bass, treble. **FULLY GUARANTEED.**

## ANOTHER SAXON PRICE BREAK-THROUGH!

**STEREO CONTROL UNIT** only **£15.80** Carr. Free

**MONO VERSION** with P.F.L. still available at **£6.50**, carr. 20p  
**SATISFACTION GUARANTEED**

**A UNIT TO SATISFY ALL THE NEEDS OF A HIGH QUALITY DISCOTHEQUE**

LOOK AT THESE FEATURES

- ★ Left/right fader, treble and bass controls for decks.
- ★ Microphone input with own volume, treble and bass controls.
- ★ Headphone monitoring (P.F.L.) with 100mW undistorted output.
- ★ Master volume control—output levels up to 1 volt.
- ★ Suitable with all power amplifiers or with the SAXON SA series of amplifier modules.



- ★ Built-in mains operated power supply, or may be battery operated.
- ★ 20–25,000Hz response.
- ★ –65dB noise level.
- ★ Accepts all ceramic cartridges.
- ★ 26dB tonal variation.
- ★ Smart black panel.

(Illustration shows Mono Unit only)

**S.A.E. WITH ALL ENQUIRIES PLEASE — TELEPHONE ORDERS & EXPORT ENQUIRIES WELCOME**

CALLERS AND MAIL ORDER:

327-331 Whitehorse Road,  
West Croydon CR0 2HS. 01-684 6385

**SAXON ENTERTAINMENTS**

CALLERS ONLY:  
6a Delce Road, Rochester, Kent.  
Medway 404199

## GUNTON ELECTRONIC IGNITION KIT

**£7.95** + 35p P. & P.

★ ALL HIGH QUALITY COMPONENTS ★  
Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- Continual Peak Performance
- Up to 20% reduced fuel consumption
- Easier All-weather Starting
- Increased Acceleration and Top Speed
- Longer Spark Plug Life
- Increased Battery Life
- Elimination of Contact Breaker Burn
- Purer Exhaust Gas Emission

12 volt only—take pos. or neg. earth. Supplied with illustrated assembly and fitting instructions, with details for fitting all types of tachometers. Can be built in an evening and fitted in 15 minutes. Spare snap-on connectors for coil, etc. Call in for a demonstration. S.A.E. all enquiries please. Ready built unit, guaranteed 5 years—£9.95 + 35p P. & P.

"SCORPIO" COMPONENTS: Transformer £1.85 + 25p P. & P. Fibreglass printed circuit board 65p + 10p P. & P. Silver-grey stove enamelled steel and aluminium case with heat sink 75p + 20p P. & P.



**ELECTRONICS DESIGN ASSOCIATES**  
82 BATH STREET, WALSALL WS1 3DE

## BUILD YOUR OWN LIQUID OIL WHEEL PROJECTOR

SUITABLE FOR DISCO OR HOME ENJOYMENT  
**TOP QUALITY**

6 inch dia. MULTICOLOURED OIL WHEEL  
PLUS

1 R.P.M. MINIATURE GEARED MOTOR

Complete Kit **£6.50** inc. postage

## C.T. ELECTRONICS

267 ACTON LANE, LONDON, W.4 01-994 6275

SURPLUS ELECTRONICS WAREHOUSE NOW OPEN AT

20-24 BEAUMONT ROAD, LONDON, W.4

Thousands of component and equipment bargains

# ATTRACTIVE DISCOUNTS

ON VERY MANY ITEMS  
WHEN YOU BUY FROM US

# ELECTROVALUE

Electronic Component Specialists

## TRANSISTORS

Wide range. Up to date. Brand new —no "seconds" or surplus. Highest quality and reliability.

IN 4148	2p	AF139	3p
IN5999	0-04	AF239	0-38
2N2646	0-37	BC107	0-13
2N3055	0-85	BC108	0-12
2N3702	0-10	BC109	0-14
2N3703	0-10	BC148	0-09
2N3704	0-10	BC177	0-15
2N3819	0-25	BC184L	0-11
2N4286	0-15	BC212L	0-14
2N4289	0-15	BD130	0-85
2N4443	0-88	BD131	0-77
2N5062	0-42	BD132	0-81
2N5088	0-46	BD135	0-25
2N5192	0-77	BD136	0-27
2N5195	0-80	BDY20	0-87
2N5457	0-30	BFY51	0-20
40361	0-45	BRV39	0-30
40392	0-45	BY164	0-45
40432	1-60	MJ481	1-20
40512	1-79	MJ491	1-35
40669	1-20	MJE3055	0-68
AC128	0-26	OA91	0-06
AD142	0-50	OC35	0-63
AD149	0-68	SCGN1	0-12
AD161	0-42	SD4	0-09
AD162	0-40	TO3 Transistor covers, ea. 7p	

## RESISTORS 10%—5%—2%

Code	Power	Tolerance	Range in ohms	Values 1 to 9	10 to 99	100 up (see note below)
C	1/20W	5%	82-220K	E12	9	8
C	1/8W	5%	4.7-470K	E24	1	0-8
C	1/4W	10%	4.7-10M	E12	1	0-8
C	1/2W	5%	4.7-10M	E24	1-2	0-9
C	1W	5%	4.7-10M	E12	2-5	2-9
MO	1/2W	2%	10-1M	E24	4	3
WW	1W	10%	0-22-3.9	E12	7	2 net
WW	3W	5%	±1/20Ω	1-10K	E12	7
WW	7W	5%	1-10K	E12	9	8

Codes: C = carbon film high stability low noise  
MO = metal oxide ElectroSil TR5 ultra low noise  
WW = wire wound Pleseey

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 72, 91 and their decades. Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1p on total value of resistor order.)

## Minitron DIGITAL INDICATOR




TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 6-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V d.c. per segment. A limited number of alphabetical symbols also available. In 16 lead DIL case.

Suitable BCD decoder driver type FLL121T net £1-36  
DIL Socket: 16 lead 30p. No. 3015G showing + or - and fig. 1 and decimal point 2£.

## PRECISION COMPONENTS

Resistors by Rivlin, 0.1% to 0.01%, £1 to 2£.  
Capacitors by MFD, 0.1 μF to 22 μF, 70p to £3-50. Prices and delivery times on request.

## SLIDE POTENTIOMETERS

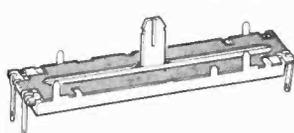

Robust construction, smooth silent action. In values from 4k7Ω to 1MΩ, linear or log. 28p each. Escutcheon, light grey, 10p.  
Knobs, flat, grip type, in black/red/green/yellow/blue/light grey/dark grey or white, 5p each.

## SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Eimco-Wolf "Solderstat" irons, we offer this model HMS 16 or 24 watt, a.c. mains, net £1-87

INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON 20  
DE-SOLDER BRAID  
Per 6ft length, net 50p.

NIPPBOARDS  
A useful board for circuit building.  
Type 1A. Single basic pattern 2 1/2" x 1 7/8", 15p.  
Type 2A. Two ptns. side by side, 28p.  
Type 2AS. Dual channel, 28p.  
Type 3A. 3 ptns. side by side, 36p.  
Type 4AS. Dual channel, 2 above 2, 44p.  
Many others in stock up to 10 patterns.

## PUBLICATIONS

Handbook of Transistor Equivalents, 40p. Handbook of Tested Transistor Circuits (H. Ness), 40p. Radio & Electronics. Colour codes & data wall chart, 15p. Engineers Reference Handbook & Tables, 20p. (Add 3p for postage on each of above if bought separately.)

## SIEMENS TTL INTEGRATED CIRCUITS

Part No.	Price	Part No.	Price
FLH101 (7400)	20p	FLJ121 (7473)	45p
FLH201 (7401)	20p	FLJ141 (7474)	45p
FLH191 (7402)	20p	FLJ151 (7475)	45p
FLH291 (7403)	20p	FLJ131 (7476)	45p
FLH211 (7404)	25p	FLH221 (7480)	88p
FLH271 (7405)	25p	FLH231 (7483)	87p
FLH381 (7408)	25p	FLH241 (7485)	1-38
FLH391 (7409)	25p	FLH341 (7486)	33p
FLH111 (7410)	20p	FLJ161 (7490)	80p
FLH351 (7413)	35p	FLJ221 (7491A)	1-28
FLH121 (7420)	20p	FLJ171 (7492)	85p
FLH181 (7430)	20p	FLJ181 (7493)	80p
FLH141 (7440)	24p	FLJ231 (7494)	1-13
FLH101 (7414)	1-22	FLJ191 (7495)	87p
FLH281 (7442)	1-16	FLJ261 (7496)	1-48
FLH361 (7443)	1-45	FLJ301 (74100)	1-64
FLH371 (7444)	1-45	FLJ281 (74104)	45p
FLH151 (7450)	20p	FLJ271 (74107)	53p
FLH161 (7451)	20p	FLK101 (74121)	48p
FLH171 (7452)	20p	FLY101 (7466)	20p
FLH181 (7454)	20p	FLJ101 (7470)	45p
FLY101 (7466)	20p	FLJ211 (74191)	1-80
FLJ101 (7470)	45p	FLJ241 (74192)	1-74
FLJ111 (7472)	32p	FLJ251 (74193)	1-74

## BAXANDALL SPEAKER

As designed by P. J. Baxandall and originally described in "Wireless World". Complete kit inc. spkr., equaliser and special cabinet kit (18in x 12in x 10in) cut to size. 60p. 10 watt RMS/15Ω loading. Part cost carr. in U.K. 60p.  
Net £1-81  
Speaker unit and equaliser kit, net. Post free 24-81.  
Pack flat cabinet assembly (all cut to shape), natural teak finish with instructions, 28 net. Part cost carr. in U.K. 60p.

## SIEMENS THYRISTORS

0-8A-400V, 55p. 600V, 70p.  
3A-400V, 60p. 600V, 85p.

## CARBON SKELETON PRE-SETS

Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

## ZENER DIODES

3% full range, E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.3V to 82V, 27p each; 1.5W: 4.7V to 75V, 48p each.  
Clip to increase 1.5W rating to 3 watts (type 260F) 4p.

## MINIATURE TOGGLE SWITCHES

2A/250V. DP/DT, 48p.

## MAINLINE AMPLIFIER KITS

70 watt power amp module kit, £12-60 net. Power supply kit, 28-50 net.

## SIEMENS CAPACITORS

POLYCARBONATE—5% TOLERANCE  
250V up to 0.1μF: 100V/0.1μF and above.  
0.01, 0.012, 0.015, 0.018, 0.022, 0.027, 0.033, 0.047, 0.056, 4p each.  
0.068, 0.082, 0.1, 0.12, 0.15, 4p each.  
0.18, 0.22, 5p each.  
0.27, 0.33, 6p; 0.39, 7p; 0.47, 8p; 0.56, 10p; 0.68, 11p; 1μF, 13p.

## ELECTROLYTIC CAPACITORS

(Values in μF/V)  
0.47/100, 1/100, 2.2/63, 4.7/35, 10/25, 22/16, 47/10, 47/25, 100/10, 220/3, 7p each.  
10/63, 22/35, 47/35, 100/16, 100/25, 220/6, 220/10, 220/16, 470/3, 7p each.  
47/50, 47/63, 100/35, 220/16, 8p each; 100/50, 220/35, 10p each; 100/63, 470/25, 1000/10, 12p each; 220/63, 470/35, 1000/16, 17p each; 1000/25, 20p each; 470/63, 1000/35, 23p each; 2200/25, 36p each; 1000/63, 2200/35, 4700/16, 40p each.

Tantalum and other capacitors, etc. see latest 1972 catalogue—issue No. 6.

## 1972 ELECTROVALUE CATALOGUE (No. 6)

Third printing with latest price and information details. Contains 96 pages plus cover. More items, more information, more diagrams than ever. Post free in U.K. 10p.

## NEWMARKET LINEAR I.C.s

LIC 709C/14 dual in line, 34p. | 709C/5, TO5 39p.  
LIC 741C/14 dual in line, 40p. | 741C/5, TO5 42p.

## CARBON TRACK POTENTIOMETERS

CARBON TRACK POTENTIOMETERS, long spindles. Double wipers.  
SINGLE GANG linear 100Ω to 2.2MΩ, 12p; Single gang log, 4.7kΩ to 2.2MΩ, 12p; Dual gang linear 4.7kΩ to 2.2MΩ, 42p; Dual gang log, 4.7kΩ to 2.2MΩ, 42p; Log/antilog, 10kΩ, 22kΩ, 47kΩ, 1MΩ only 42p; Dual antilog, 10kΩ only, 42p. Any type with 2A.D.F. mains switch, 12p extra.  
Only decades of 10, 22 and 47 available in ranges quoted.  
DUAL CONCENTRIC in any combination of P.20 values, 60p; with switch, 72p. Knobs, pair 24p.

## DISCOUNTS

10% on orders £5 to £15.  
15% on orders over £15. No discount on items marked Net. Prices subject to alteration without notice.

## POSTAGE AND PACKING

FREE, unless otherwise stated. Handling surcharge 10p on mail orders under 2£. Overseas orders: cart. and insurance charged at cost. U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.


ENQUIRIES FROM TRADE AND OTHER LARGE QUANTITY BUYERS INVITED.

# ELECTROVALUE

(Dept. PE 1072) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 (STD 0784-3). Telex 264475  
ELECTROVALUE LTD.—AN INDEPENDENT COMPANY SINCE ITS ESTABLISHMENT IN 1965

# Sinclair Project 60

## Stereo 60

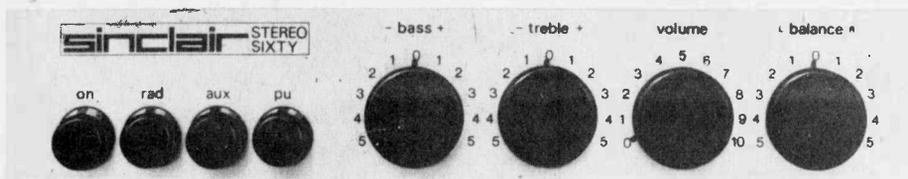

Built and tested post free  
**£9.98**


### pre-amplifier/control unit

The versatility of Project 60 high-fidelity modules is well demonstrated in this excellent unit. It provides the facilities essential to good stereo and will enhance the quality of any system it is used with, whether Project 60 or any other top line power amplifiers. Compact, yet robustly constructed, the unit is easily panel mounted and will operate satisfactorily from 18 to 35 volts supply. Silicon epitaxial transistors are used throughout to achieve a very high signal to noise ratio with excellent separation between channels. Distortion at maximum output is barely 0.02% with magnetic p.u. input. Accurate equalisation is provided for all inputs, which are selected by push buttons. For maximum effectiveness, the Sinclair A.F.U. is recommended for use with the Stereo 60 pre-amp/control unit. A comprehensive manual supplied with Project 60 modules makes installing and connecting easy and ensures best possible results from your system.

#### SPECIFICATIONS

**Input sensitivities:** Radio – up to 3mV. Mag. p.u. 3mV correct to R.I.A.A. curve  $\pm 1\text{dB}$ , 20 to 25,000 Hz. Ceramic p.u. – up to 3mV. Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE  $\pm 12$  to  $-12\text{dB}$  at 10KHz; BASS  $+12$  to  $-12\text{dB}$  at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.
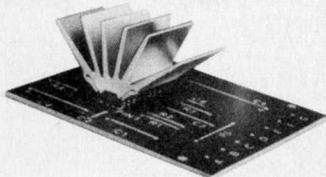
### Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

#### SPECIFICATIONS

**Output power:** 6 watts RMS continuous (12 watts peak). 6–8 $\Omega$ . **Frequency Response:** 5Hz to 100KHz  $\pm 1\text{dB}$ . **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

**£2.98** Post free

### Project 605



The easy way to buy and build Project 60

Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

Everything you need to assemble a superb 30 watt high fidelity stereo amplifier without having to solder.

# sinclair

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311

# the world's most advanced high fidelity modules

## Z.30 & Z.50 power amplifiers


Built, tested and guaranteed with circuits and instructions manual. Z.30 £4.48 Z.50 £5.48

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to provide unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and are intended for use principally with other units in the Project 60 range. Their performance and design are such, however, that Z.50s and Z.30 may be used in a far wider range of applications.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).— Power Outputs:** Z.30 15 watts R.M.S. into 8 ohms using 35 volts: 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts: 30 watts R.M.S. into 8 ohms using 50 volts.

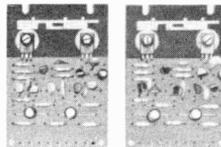**Frequency response:** 30 to 300,000Hz ±1dB. **Distortion:** 0.02% into 8 ohms. **Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω). For speakers from 3 to 15 ohms impedance. **Size:** 14 x 80 x 57mm.



## Project 60 Stereo F.M. Tuner

Built and tested. Post free. £25

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7μV for lock-in over full deviation. **Squelch level:** Typically 20μV. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz – 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2μV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.



## A.F.U. High & Low Pass Filter Unit

Built, tested and guaranteed. £5.98

For use between Stereo 60 unit and two Z.30s or Z.50s. The unit is very easily mounted and is unique in that the cut-off frequencies are continuously variable. As attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. There are two filter sections – rumble (high pass) and scratch (low pass). H.F. cut-off (–3dB) variable from 28KHz to 5KHz. L.F. cut-off (–3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. Operating voltage from 15 to 35V. Current 3mA. **Size:** 66 x 40 x 90mm.



## Power Supply Units

Designed specifically for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 or PZ.8 where a stabilised supply is essential.

PZ.5 30 volts un stabilised £4.98  
 PZ.6 35 volts stabilised £7.98  
 PZ.8 45 volts stabilised £7.98  
 (less mains transformer) £7.98  
 PZ.8 mains transformer £5.98



### Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

## Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

SINCLAIR RADIONICS, ST IVES, HUNTINGDONSHIRE PE1072

Please send

I enclose cash/cheque/money order.

Name \_\_\_\_\_

Address \_\_\_\_\_

# sinclair

# JOHN D. ADAMS INDUSTRIAL ELECTRONICS

219 GLOUCESTER ROAD  
CROYDON CR0 2DW



WE ARE PLEASED TO ANNOUNCE WE ARE STOCKING A SELECTED RANGE OF METAL DETECTORS.

Special Offer for Limited Period Only. Free with each Metal Detector a copy of "Fortune under Your Feet".

This informative book gives useful advice and hints on treasure hunting. THE FAMOUS "CONCORD" well known for reliability and sensitivity, £24 + P&P 50P

THE "RETRIEVER" super lightweight detector. Search coil can be immersed in water. Good sensitivity at a modest price, £19.50 + P&P 45P

THE "MAGPIE", similar to the Retriever but with earpiece output, only £14.90 + P&P 45P

THE "PUP", one of the smallest detectors of our range, very easy to use. Very lightweight. Ideal for the children, £12.25 + P&P 40P

THE "ATLANTA". British made. Ready to use, ultra lightweight, good sensitivity, £9.95 + P&P 40P

THE "PUP"

THE "ATLANTA"

Send cheque with order and don't forget to ask for your free copy of "Fortune at your Feet" free with any of the above metal detectors

ALL OUR DETECTORS ARE BACKED BY A 12 MONTH GUARANTEE

### STOCK TAKING CLEARANCE SPECIAL £1 BARGAIN PACKS

- A 10 OC74 PNP Germ. O/P D 10 2N744 NPN Sil. 300mV similar to OC81 300mhz
- B 40 OC71 PNP Germ. LF AMP unmarked E 10 1N47Z Diodes 1200V 1 amp
- C 12 2N1303 PNP Germ. Gen./ Purpose F 25 OA81 Diodes unmarked

\* Please add 10p to orders under £2

### BRAND NEW GUARANTEED TRANSISTORS

2G304 20p	2N3053 20p	ASY32 20p	BCJ10 20p	NKT221 25p
2G271 10p	2N3134 30p	ASY76 20p	BCZ11A 30p	OC28 45p
2N697 12p	2N3135 20p	AS220 30p	BF194 14p	OC45 10p
2N744 17p	2N3702 10p	BC107 10p	BF200 30p	OC71 10p
2N1303 15p	2N3707 12p	BC108 10p	BFY51 16p	OC74 20p
2N1305 20p	2N4036 55p	BC109 10p	BFY52 20p	OC139 25p
2N1309 25p	25002 50p	BC148 10p	BFX87 25p	OC200 25p
2N1596 15p	25323 60p	BC187 27p	BFX88 20p	OC201 50p
2N1613 15p	25324 18p	BCY30 35p	GET25 10p	V30/30P 30p
2N1711 24p	AC128 18p	BCY32 45p	GET875 12p	
2N1997 30p	AD149 30p	BCY34 35p	GET875 12p	
2N2270 60p	ASY29 20p	BCY43 15p	GET882 10p	

### SPECIALS

ISKRA RESISTORS 1/4W carbon film low noise all values 1p each  
ON/OFF TOGGLE SWITCH 10p  
GRELCO 5-WAY SCREW CONNECTOR 13p  
2 POLE SW STANDARD JACK SOCKETS 9p  
RED PUSH BUTTON SWITCH SP. ROUND hole fix 10p

SUB MIN ELECTROLYTIC CAPACITORS, 5p each  
Values µF/V: 6.4/25; 10/16; 20/64; 80/25; 125/10; 125/16; 25/6.4; 4/10  
POLYSTYRENE CAPACITORS 3p each  
0.033; 0.047; 0.1  
LOUDSPEAKERS, 2 1/2in 8 ohm, 45p  
BATTERY CLIPS. PP3 with leads, 6p, PP1, 7p pair  
\*Please add 10p to orders under £2.

# MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES LARGEST RANGE  
BRAND NEW FULLY GUARANTEED

### MOTOROLA

We can now offer a vast range of Motorola IC's at industrial distributor prices.

Examples	£p	Data Sheets
MC724P	0.68	
MC790P	1.24	£0.12
MC1303L	2.70	extra

### FAIRCHILD (RTL)

L900	L923	1-5	6-11	12+
40p	40p		37p	35p
Data sheet 121p				

### LINEAR

Op. Amps.	1-11	12-24	25-90
	£p	£p	£p
L702A TO5	2.80	2.70	2.60
L702C TO5	0.77	0.72	0.67
L703C TO5	0.62	0.57	0.52
L709C TO5	0.38	0.36	0.31
L709C DIL	0.33	0.31	0.27
L710C TO5	0.47	0.42	0.37
L710C DIL	0.45	0.40	0.35
L711C TO5	0.49	0.44	0.39
L711C DIL	0.45	0.40	0.35
L716 TO5	1.87	1.75	1.70
L723C TO5	0.75	0.72	0.66
L739	1.95	—	—
L741C TO5	0.40	0.38	0.34
L741C DIL	0.38	0.36	0.32
LM741CN DIL	0.70	0.65	0.60
SN72700P DIL	0.45	0.40	0.35

### RCA COSMOS PLESSEY

£p	£p
SL403D 1.50	SL611C 1.70
SL621C 2.60	SL701C 1.45
SL702C 1.25	
CD4001AE 0.93	DATA SHEETS
CD4009AE 1.98	
CD4011AE 0.93	17p
CD4013AE 1.88	
CD4015AE 4.38	
CD4017AE 4.42	
CD4018AE 3.95	
CD4020AE 5.50	
CD4024AE 2.98	

TH9013P £4.57  
20 WATT AMP  
TH9014P £1.50  
PRE-AMP  
DATA SHEETS £0.12

### MULLARD DTL

£p	£p
FCH101 0.874	FCH121 1.05
FCH201 1.384	FCH31 1.50
FCJ101 1.824	FCJ111 1.55
FCJ201 1.80	FCJ211 2.75
FCK101 4.374	FCY101 1.05
TAA241 1.30	TAA241 1.30
300 2.00	310 1.30
320 0.85	320 0.85
350 2.10	435 0.73
521 0.57	522 1.13
570 2.60	530 4.95
700 3.50	811 4.45
TAB101 0.974	TAD100 1.974
TAD110 1.974	

### MULLARD LINEAR

TH9013P £4.57  
20 WATT AMP  
TH9014P £1.50  
PRE-AMP  
DATA SHEETS £0.12

### GENERAL ELECTRIC

£p	£p
PA238 2.81	PA246 1.54
PA284 1.78	PA265 1.93
570 2.60	700 3.50
811 4.45	TAB101 0.974
TAD100 1.974	TAD110 1.974

### SIEMENS

TAA151 0.88  
TAA435 0.73  
TAB101 0.974  
TAD100 1.974  
TAD110 1.974

### SGS

TAA661B £1.32  
TAA821 £2.03  
TAA700 £3.50  
TBA651 £1.89

### TTL LOGIC

1-24 25-99	£p	£p	1-24 25-99	£p	£p
SN7400	0.20	0.18	SN7407	0.56	0.05
SN7401	0.20	0.18	SN7408	0.22	0.20
SN7403	0.20	0.18	SN7410	0.22	0.20
SN7404	0.22	0.20	SN7411	0.22	0.20
SN7405	0.22	0.20	SN7412	0.48	0.42
SN7406	0.58	0.50	SN7413	0.35	0.32

### 1-24 25-99

£p	£p	£p	£p
SN7416 0.45	0.40	SN7496 1.00	0.90
SN7417 0.45	0.40	SN7497 0.40	0.50
SN7420 0.20	0.18	SN74100 1.80	1.60
SN7421 0.22	0.20	SN74104 1.52	1.33
SN7422 0.48	0.42	SN74105 1.52	1.33
SN7423 0.52	0.45	SN74107 0.43	0.38
SN7425 0.48	0.42	SN74109 1.06	0.93
SN7426 0.32	0.28	SN74110 0.80	0.70
SN7427 0.48	0.42	SN74111 1.57	1.38
SN7428 0.71	0.62	SN74118 1.45	1.27
SN7430 0.20	0.18	SN74119 1.82	1.68
SN7432 0.48	0.42	SN74120 1.06	0.93
SN7433 0.71	0.62	SN74121 0.43	0.38
SN7437 0.52	0.45	SN74122 0.52	0.47
SN7438 0.52	0.45	SN74123 0.90	0.80
SN7439 0.52	0.45	SN74128 0.80	0.70
SN7440 0.20	0.18	SN74141 0.90	0.80
SN7441A		SN74443 0.80	0.80
SN7442 1.04	0.88	SN74150 1.19	1.05
SN7443 1.04	0.88	SN74151 1.18	1.00
SN7444 1.04	0.88	SN74153 1.18	1.00
SN7445 1.82	1.70	SN74154 1.89	1.75
SN7446 1.30	1.20	SN74155 1.55	1.35
SN7447 1.30	1.20	SN74156 1.30	1.15
SN7447 1.30	1.20	SN74157 1.30	1.15
SN7448 1.04	0.92	SN74158 1.40	1.15
SN7449		SN74160 1.80	1.70
SN7450 0.20	0.18	SN74161 2.60	2.50
SN7451 0.20	0.18	SN74162 2.60	2.50
SN7452 0.20	0.18	SN74163 3.52	3.08
SN7453 0.20	0.18	SN74164 4.48	3.90
SN7454 0.20	0.18	SN74165 4.48	3.90
SN7460 0.20	0.18	SN74166 4.25	3.72
SN7470 0.38	0.34		
SN7472 0.38	0.31	SN74170 4.38	3.83
SN7473 0.45	0.39	SN74174 2.08	1.82
SN7474 0.45	0.39	SN74175 1.44	1.28
SN7475 0.60	0.55	SN74176 1.30	1.10
SN7476 0.47	0.42	SN74177 1.30	1.10
SN7480 0.70	0.65	SN74178 1.80	1.55
SN7481 1.45	1.27	SN74179 1.80	1.55
SN7482 1.28	1.00	SN74180 1.37	1.20
SN7483 1.30	1.05	SN74181 5.60	4.75
SN7484 1.19	1.05	SN74182 1.48	1.34
SN7485 2.50	2.30	SN74190 1.80	1.55
SN7486 0.45	0.40	SN74191 1.95	1.75
SN7488 12.40	11.80	SN74192 1.70	1.50
SN7489 4.97	4.40	SN74193 1.70	1.50
SN7490 0.80	0.75	SN74194 2.00	1.80
SN7491 1.20	1.00	SN74195 2.00	1.80
SN7492 0.80	0.75	SN74196 1.48	1.38
SN7493 0.80	0.75	SN74197 1.60	1.38
SN7494 0.85	0.79	SN74198 3.00	2.75
SN7495 0.85	0.79	SN74199 3.00	2.75

### 14-08 12-32

Type	1-24 25-99	Type	1-24 25-99
CA3000	2.28 1.88	CA3044V1	4.42 3.17
CA3001	3.38 2.79	CA3045	1.50 1.24
CA3002	2.28 1.88	CA3048	0.86 0.71
CA3004	2.28 1.88	CA3047	1.59 1.31
CA3005	1.50 1.24	CA3048A	2.92 2.41
CA3006	3.47 2.86	CA3049	2.34 1.93
CA3007	3.28 2.71	CA3049A	1.46 1.32
CA3008	1.98 1.64	CA3050	2.78 1.88
CA3008A	3.24 2.87	CA4051	1.23 1.43
CA3010	0.58 0.47	CA4052	1.73 1.43
CA3011	0.89 0.57	CA4052	1.80 1.48
CA3011A	0.92 0.76	CA3053	0.52 0.43
CA3012	1.11 0.91	CA3054	1.19 0.98
CA3013	1.30 1.07	CA3058	3.32 2.74
CA3014	1.52 1.28	CA3059	1.84 1.52
CA3015	1.40 1.15	CA3060A	
CA3015A	1.82 1.50		3.47 2.86
CA3016	2.61 2.15	CA3060BD	
CA3016A	3.80 3.22		5.93 4.89
CA3018	0.88 0.72	CA3060D	4.70 3.88
CA3018A	1.19 0.92	CA3060E	2.74 2.26
CA3019	0.94 0.78	CA3062	2.91 2.45
CA3020	1.55 1.28	CA3064	1.42 1.17
CA3020A	2.01 1.65	CA3065	1.42 1.17
CA3021	1.90 1.57	CA3066	2.61 2.15
CA3022	1.81 1.33	CA3067	2.72 2.24
CA3023	1.55 1.28	CA3068	3.01 2.48
CA3026	2.82 2.41	CA3070	2.15 1.78
CA3028A	0.88 0.72	CA3071	2.41 1.85
CA3028B	1.17 0.97	CA3072	2.07 1.71
CA3029	0.52 0.43	CA3075	1.46 1.21
CA3029A	0.63 0.52	CA3076	1.67 1.38
CA3030	1.08 0.89	CA3078A	
CA3030A	1.64 1.35		4.88 3.86
CA3033	4.93 4.07	CA3078T	2.80 2.31
CA3035	1.52 1.28	CA3079	2.91 2.45
CA3035V1	1.52 1.28	CA3080	0.58 0.48
CA3036	0.90 0.74	CA3081	1.80 1.48
CA3037	1.68 1.39	CA3082	1.80 1.48
CA3037A	2.60 2.14	CA3083	1.38 1.12
CA3038	2.60 2.14	CA3084	3.41 2.85
CA3039A	3.40 2.80	CA3085B	3.78 3.12
CA3039	1.00 0.83		

# LARGEST STOCKS SEMICONDUCTORS & COMPONENTS BRAND NEW GUARANTEED

## TRANSISTORS

2N301	15p	2N2923	12p	2N4900	£2.25	AF115	25p	BC301	34p	BF255	15p
2G302	12p	2N2924	12p	2N4901	£2.70	AF116	25p	BC302	27p	BF257	41p
2G303	25p	2N2925	12p	2N5172	9p	AF117	20p	BC303	54p	BF258	40p
2G306	30p	2N2926	12p	2N5174	22p	AF118	50p	BC304	43p	BF259	48p
2G309	30p	Green	10p	2N5175	28p	AF121	22p	BC307	9p	BF261	25p
2G344	25p	Yellow	10p	2N5176	32p	AF124	22p	BC307A	9p	BF264	25p
2G345B	25p	Orange	10p	2N5246	48p	AF125	20p	BC307V1	9p	BF270	25p
2G371	15p	2N3003	15p	2N5100	48p	AF126	20p	BC306	8p	BF271	21p
2G374	15p	2N3004	15p	2N5101	48p	AF127	20p	BC308A	8p	BF272	53p
2G381	15p	2N3005	60p	2N5192	£1.24	AF139	33p	BC308B	8p	BF273	25p
2G417	20p	2N3390	20p	2N5193	£1.01	AF170	25p	BC309	9p	BF274	28p
2N109	48p	2N3391	20p	2N5194	£1.10	AF172	25p	BC309A	9p	BF457	40p
2N174	£1.40	2N3391A	22p	2N5195	£1.48	AF173	25p	BC309B	9p	BF458	57p
2N176	76p	2N3392	13p	2N5245	43p	AF179	65p	BC313	30p	BF459	57p
2N177	76p	2N3393	12p	2N5447	35p	AF180	50p	BC327	21p	BF821	£2.10
2N183	76p	2N3394	12p	2N5448	33p	AF186	40p	BC328	18p	BF821A	£2.30
2N185	76p	2N3402	17p	2N5450	33p	AF200	35p	BC337	17p	BF828	92p
2N187	76p	2N3403	19p	2N128	63p	AF239	38p	BC338	17p	BF881	27p
2N188	93p	2N3404	24p	2N138	£1.37	AF240	63p	BCY30	30p	BF888	30p
2N388A	40p	2N3405	27p	2N139	£1.38	AF279	47p	BCY31	40p	BF910	61p
2N404	23p	2N3414	10p	2N140	76p	AF280	47p	BCY32	60p	BF911	61p
2N406	75p	2N3415	10p	2N142	76p	AF281	47p	BCY33	60p	BF915	75p
2N456	75p	2N3416	10p	2N144	59p	AF211	45p	BCY34	35p	BF913	23p
2N457A	80p	2N3417	21p	2N143	64p	AL102	75p	BCY38	40p	BF920	25p
2N491	£3.25	2N3570	£1.25	2N192	79p	AL103	70p	BCY39	80p	BF929	25p
2N584	34p	2N3571	£1.12	2N193	74p	AS926	25p	BCY40	50p	BF937	33p
2N591	26p	2N3572	97p	2N194	74p	AS927	30p	BCY42	15p	BF938	30p
2N696	15p	2N3702	11p	2N199	£1.50	AS928	30p	BCY58	18p	BF939	£2.45
2N697	15p	2N3703	10p	2N187	£1.50	AS929	30p	BCY59	18p	BF938	30p
2N698	25p	2N3704	10p	2N207	£1.05	AS930	30p	BCY59	18p	BF938	30p
2N699	25p	2N3705	10p	2N201	£1.05	AS935	35p	BCY66	58p	BF935	29p
2N706	10p	2N3706	80p			AS931	55p	BCY67	82p	BF936	24p
2N706A	12p	2N3707	11p			AI103	£1.25	BCY70	17p	BF937	27p
2N708	13p	2N3708	70p			BC107	12p	BCY71	22p	BF938	25p
2N709	38p	2N3709	90p			BC108	11p	BCY72	22p	BF938	25p
2N711	30p	2N3710	80p	40050	50p	BC109	12p	BCY73	22p	BF938	25p
2N718	21p	2N3711	80p	40051	58p	BC110	12p	BCY74	22p	BF938	25p
2N718A	30p	2N3712	95p	40309	28p	BC111	12p	BCY75	22p	BF938	25p
2N720	50p	2N3713	£1.08	40310	29p	BC112	12p	BCY76	22p	BF938	25p
2N721	55p	2N3714	£1.15	40360	35p	BC116	15p	BCY77	22p	BF938	25p
2N914	15p	2N3715	£1.23	40361	37p	BC116A	15p	BD111	75p	BFY29	40p
2N916	17p	2N3716	£1.30	40362	40p	BC117	21p	BD112	75p	BFY29	40p
2N918	10p	2N3773	£2.40	40363	61p	BC118	11p	BD121	82p	BFY41	43p
2N919	20p	2N3774	£3.33	40369	37p	BC119	27p	BD123	82p	BFY41	43p
2N929	14p	2N3775	£4.19	40394	58p	BC121	20p	BD124	60p	BFY43	65p
2N930	14p	2N3776	£5.95	40395	59p	BC123	25p	BD130	60p	BFY40	18p
2N1090	30p	2N3777	£4.84	40406	40p	BC125	15p	BD131	75p	BFY41	18p
2N1091	32p	2N3778	£2.25	40407	31p	BC126	20p	BD132	75p	BFY42	50p
2N1131	20p	2N3779	£3.15	40408	43p	BC129	30p	BD133	38p	BFY33	15p
2N1132	20p	2N3780	£4.50	40409	49p	BC134	11p	BD136	44p	BFY64	34p
2N1184	£1.27	2N3781	£3.67	40410	45p	BC135	11p	BD137	47p	BFY64	41p
2N1302	16p	2N3782	£3.37	40411	£1.40	BC136	15p	BD138	55p	BFY75	40p
2N1303	16p	2N3789	£1.76	40454	57p	BC137	15p	BD139	62p	BFY76	22p
2N1304	20p	2N3790	£1.80	40468A	53p	BC138	24p	BD140	70p	BFY77	24p
2N1305	20p	2N3791	£2.06	40600	57p	BC140	30p	BDY11	£1.50	BFY60	55p
2N1306	22p	2N3792	£2.20	40601	55p	BC141	34p	BDY11	£1.50	BFY60	55p
2N1307	22p	2N3794	£2.40	40602	49p	BC142	18p	BDY17	£1.50	FRY39	38p
2N1308	25p	2N3819	28p	40603	49p	BC143	21p	BDY18	£1.75	B8X19	13p
2N1309	25p	2N3820	48p	40604	49p	BC144	24p	BDY19	£1.87	B8X20	14p
2N1483	30p	2N3823	62p	40636	35p	BC145	21p	BDY20	£1.87	B8X21	20p
2N1507	30p	2N3824	75p	40673	30p	BC147	10p	BDY38	65p	B8X26	34p
2N1613	20p	2N3826	23p	AC107	65p	BC149	9p	BDY60	65p	B8X27	34p
2N1631	38p	2N3854	16p	AC113	16p	BC153	10p	BDY62	75p	B8X28	25p
2N1637	38p	2N3854A	16p	AC115	16p	BC154	11p	BF115	25p	B8X29	27p
2N1638	35p	2N3855	16p	AC117	20p	BC154	11p	BF117	43p	B8X30	68p
2N1671	£1.10	2N3855A	16p	AC121	11p	BC157	9p	BD117	43p	B8X39	68p
2N1701	£1.10	2N3856	16p	AC126	20p	BC158	10p	BF119	58p	B8X39	68p
2N1702	£2.15	2N3856A	16p	AC127	20p	BC159	10p	BF121	21p	B8X41	27p
2N1711	17p	2N3858	16p	AC128	20p	BC160	11p	BF123	27p	B8X61	62p
2N1893	34p	2N3858A	16p	AC141K	30p	BC161B	11p	BF125	27p	B8X76	25p
2N2102	30p	2N3859	16p	AC142K	25p	BC168B	10p	BF127	27p	B8X77	25p
2N2144	60p	2N3859A	16p	AC151V	12p	BC168C	10p	BF152	20p	B8X78	25p
2N2148	60p	2N3860	16p	AC152V	15p	BC169B	11p	BF153	20p	B8W70	28p
2N2192	40p	2N3866	70p	AC153	15p	BC169C	11p	BF154	18p	B8Y24	20p
2N2192A	40p	2N3877	25p	AC153K	22p	BC170	11p	BF156	22p	B8Y25	20p
2N2193	58p	2N3877A	20p	AC154	20p	BC171	13p	BF159	27p	B8Y26	20p
2N2194	21p	2N3878	16p	AC176	15p	BC171	15p	BF160	23p	B8Y27	20p
2N2194A	30p	2N3900	20p	AC176K	17p	BC182	10p	BF161	35p	B8Y28	15p
2N2195	37p	2N3900A	21p	AC187K	17p	BC182L	10p	BF163	20p	B8Y38	15p
2N2195A	18p	2N3901	32p	ACV17	25p	BC183	8p	BF166	35p	B8Y39	15p
2N2196	18p	2N3903	22p	ACV18	15p	BC184	11p	BF167	18p	B8Y61	25p
2N2197	18p	2N3904	22p	ACV19	20p	BC184L	11p	BF172	19p	B8Y62	25p
2N2198	20p	2N3905	22p	ACV20	20p	BC186	25p	BF178	31p	B8Y64	30p
2N2219	20p	2N3906	22p	ACV21	18p	BC187	25p	BF179	38p	B8Y66	78p
2N2220	20p	2N3906A	22p	ACV22	13p	BC204	11p	BF180	35p	B8Y65	78p
2N2221	20p	2N4036	40p	ACV22	13p	BC204	11p	BF181	34p	B8Y78	40p
2N2221A	20p	2N4037	35p	ACV28	18p	BC205	10p	BF182	40p	B8Y79	40p
2N2222	20p	2N4038	12p	ACV30	42p	BC206	11p	BF183	40p	B8Y79	40p
2N2222A	32p	2N4039	90p	ACV39	55p	BC207	10p	BF184	17p	B8Y95A	9p
2N2268	11p	2N4060	11p	ACV40	17p	BC208	9p	BF185	17p	BU104	£1.42
2N2309	12p	2N4061	11p	ACV41	17p	BC209	10p	BF186	18p	BU105	£2.25
2N2368A	15p	2N4062	11p	ACV44	31p	BC211	30p	BF194	14p	BU105	£2.25
2N2646	45p	2N4302	25p	AD136V	84p	BC212K	10p	BF196	15p	C111	53p
2N2647	£1.20	2N4303	32p	AD140	55p	BC212L	12p	BF196	15p	C407	18p
2N2711	12p	2N4918	80p	AD142	50p	BC2141	14p	BF197	15p	C424	15p
2N2712	12p	2N4914	87p	AD143	45p	BC236	10p	BF198	18p	C425	15p
2N2713	17p	2N4915	95p	AD149V	85p	BC237	8p	BF199	18p	C426	25p
2N2714	17p	2N4916	11p	AD149V	£1.24	BC238	8p	BF200	40p	C428	25p
2N2714	17p	2N4917	17p	AD150	55p	BC239	8p	BF2243	14p	C444	20p
2N2904	18p	2N4918	50p	AD161	33p	BC251	20p	BF2251	19p	D40N1	50p
2N2904A	28p	2N4919	53p	AD162	36p	BC252	18p	BF237	22p	D40N3	62p
2N2905	28p	2N4920	60p	AD161 PR	35p	BC253	28p	BF238	22p	GET111	45p
2N2905A	28p	2N4921	50p	AD162	60p	BC257	8p	BF244	18p	GET114	20p
2N2906	18p	2N4922	55p	ADZ11	£1.50	BC258	11p	BF245	38p	GET115	50p
2N2906A	23p	2N4926	90p	ADZ12	£1.75	BC261	20p	BF246	48p	GET119	35p
2N2907	18p	2N4927	£1.00	AF106	18p	BC282	18p	BF247	48p	GET120	40p
2N2907A	28p	2N4928	£1.80	AF109R	35p	BC283	23p	BF247	48p	GET133	20p
2N2913	75p	2N4929	£2.23	AF114	25p	BC296	24p	BF254	14p	GET336	20p

# everyday electronics makes it simple!



This companion magazine to PRACTICAL ELECTRONICS has been devised to introduce complete novices to this fascinating hobby. EVERYDAY ELECTRONICS offers a wide range of simple-to-build projects that will be of interest to men and women of all ages. The October issue of EVERYDAY ELECTRONICS will be on sale from Friday, 15th September with these special features:

**CASSETTE TAPE POWER SUPPLIES.** See how to build two separate power supplies that will enable a cassette recorder to be used on mains electrical supply or car battery.

**ELECTRONIC MOUSE TRAP.** This humane mouse trap enables mice to be caught unharmed so that they may be released outside the home.

**REACTOMATIC.** An intriguing unit which can be used for testing reflexes or for TV-type quiz game answering!

**ON SALE EVERY MONTH — PRICE 15p**

## TRANSFORMERS

DOUGLAS GUARANTEED  
18 or 24 Volts

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS**	£0-91 3p
12V x 2 500 mA x 2	MT213 CT**	£0-97 13p
12V x 2 1A x 2	MT 71 AT†	£1-48 24p
12V x 2 2A x 2	MT 18 AT	£2-04 30p
12V x 2 3A x 2	MT 70 AT	£2-69 32p
12V x 2 4A x 2	MT 108 AT	£2-92 35p
12V x 2 5A x 2	MT 72 AT	£2-38 34p

30 volts. All tapped at 0-12-15-20-24-30V

Out. put Amps.	Ref. No.	Price P.P.	Out. put Amps.	Ref. No.	Price P.P.
500 mA	MT 112 CT†	1-12 15p	3A	MT 20 AT	2-64 32p
1A	MT 79 AT†	1-55 25p	4A	MT 21 AT	3-10 40p
2A	MT 3 AT	2-23 30p	5A	MT 51 AT	4-31 42p

50 volts. All tapped at 0-19-25-33-40-50V

500 mA	Ref. No.	Price P. & P.	3A	Ref. No.	Price P. & P.
MT 102 AT†	1-45 24p	3A	MT 105 AT	3-91 41p	
1A	MT 103 AT†	2-00 32p	4A	MT 106 AT	5-08 41p
2A	MT 104 AT†	3-10 32p	6A	MT 107 AT	7-47 50p

60 volts. All tapped at 0-24-30-40-48-60V

500 mA	Ref. No.	Price P. & P.	2A	Ref. No.	Price P. & P.
MT 124 AT†	1-46 21p	2A	MT 127 AT	3-18 41p	
1A	MT 126 AT†	2-24 28p	3A	MT 125 AT	4-59 41p

**AUTO-WOUND RANGE**

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	£0-89 16p
75 VA	"	MT 64 AT	£1-72 30p
150 VA	0-115-200-220-240	MT 4 AT	£2-15 31p
200 VA	"	MT 65 AT	£2-00 32p

400 V. Output at 50 HZ. Ref. ITS AT Price P. & P. £2-25 29p

C.D. Ignition system by R. M. Marston

**EQUIPMENT RANGE**

Sec. Output (r.m.s.)	Ref. No.	Price P. & P.
3-0-3 V.	200 mA MT 209 CS**	£0-89 8p
9-0-9 V.	100 mA MT 13 CT*	£0-91 8p
10-0-12	50 mA MT 210 CS**	£0-91 8p
20-0-20	30 mA MT 211 CS**	£0-91 8p
0-20 x 2	300 x 2 MT 214 CT**	£1-21 14p
0-8-8 x 2	500 mA x 2 MT 207 CT*	£1-46 20p
0-15-20 x 2	500 mA x 2 MT 205 AT**	£2-12 29p
0-15-27 x 2	500 mA x 2 MT 203 AT*	£2-45 29p
0-15-27 x 2	1A x 2 MT 204 AT**	£2-42 30p
10-12-0-12-20	700 mA (d.c.) MT 221 AT*	£1-11 25p

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spalls; \* with interwinding screen; † untapped 240V Primary; ‡ Primary tapped at 210-240V; other Primaries tapped at 200-220-240V.

Over 800 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.  
(Dept. MO. 58), Thames Street, LOUTE, Lincs.

## BASIC TELEVISION

3 Vols. combined edition

£3-50.

Postage 25p.

A NEW PICTURE BOOK MANUAL  
IN THE COMMON CORE SERIES

**PRACTICAL TRANSISTOR NOVELTY CIRCUITS**, by H. Ness. 40p. Postage 5p.

**ELECTRONICS EXPERIMENTERS CIRCUIT MANUAL**, by General Electric. £1. Postage 10p.

**DIGITAL LOGIC BASIC THEORY AND PRACTICE**, by J. H. Smith. £1-50. Postage 10p.

**FOUNDATIONS OF WIRELESS AND ELECTRONICS**, by M. G. Scroggie. £1-80. Postage 20p.

**THE MAZDA BOOK OF PAL RECEIVER SERVICING**, by D. J. Seal. £3-50. Postage 20p.

**TRANSISTOR POCKET BOOK**, by R. G. Hibberd. £1-40. Postage 10p.

**MAKING AND REPAIRING TRANSISTOR RADIOS**, by W. Oliver. £1. Postage 10p.

**RADIO VALVE AND TRANSISTOR DATA**, by A. M. Ball. 75p. Postage 10p.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books  
19-21 PRAED STREET  
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 876. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

**709C OPERATIONAL AMPLIFIER TO6**  
8 lead I.C. 1 off 50p. 50 off 35p.  
100 off 20p.

**250 MIXED RESISTORS** 62p  
‡ & † watt.

**150 MIXED HI STABS** 62p  
‡, † & ‡ watt 5% & better.

**QUARTZ HALOGEN BULBS**  
With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

**GPO EXTENSION TELEPHONES**  
with dial but without bell. 90p each. P. & P. 30p.  
£1-76 for 2. P. & P. 50p.

**BARGAIN RELAY OFFER**  
Single pole change over silver contacts 25V to 50V. 2-5kΩ coil. 8 for 60p. P. & P. 5p.

**KEYTRONICS** mail order only  
44 EARLS COURT ROAD  
LONDON, W.8 01-478 8499

# HENRY'S - Your complete Semi-Conductor Store!

## INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. **BRANDED FROM TEXAS I.T.T. FAIR-CHILD**



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
8N7400	0.20	0.18	0.16	8N7450	0.20	0.18	0.16	8N74145	1.50	1.40	1.30
8N7401	0.20	0.18	0.16	8N7451	0.20	0.18	0.16	8N74150	3.35	3.05	2.15
8N7402	0.20	0.18	0.16	8N7452	0.20	0.18	0.16	8N74151	1.10	0.95	0.90
8N7403	0.20	0.18	0.16	8N7454	0.20	0.18	0.16	8N74153	1.35	1.27	1.20
8N7404	0.20	0.18	0.16	8N7460	0.20	0.18	0.16	8N74154	2.00	1.75	1.55
8N7405	0.20	0.18	0.16	8N7470	0.30	0.27	0.25	8N74155	1.55	1.47	1.35
8N7406	0.30	0.27	0.25	8N7472	0.30	0.27	0.25	8N74156	1.55	1.47	1.35
8N7407	0.30	0.27	0.25	8N7473	0.40	0.37	0.35	8N74157	1.80	1.70	1.50
8N7408	0.20	0.18	0.16	8N7474	0.40	0.37	0.35	8N74160	2.60	2.40	2.25
8N7409	0.42	0.38	0.35	8N7475	0.55	0.41	0.38	8N74161	2.60	2.40	2.25
8N7410	0.20	0.18	0.16	8N7476	0.45	0.42	0.39	8N74162	3.40	3.25	2.70
8N7411	0.23	0.22	0.20	8N7480	0.80	0.75	0.67	8N74163	3.40	3.25	2.70
8N7412	0.42	0.40	0.35	8N7481	1.25	1.15	1.10	8N74164	2.75	2.30	2.10
8N7413	0.30	0.27	0.25	8N7482	0.87	0.80	0.70	8N74165	4.00	3.50	3.00
8N7416	0.30	0.27	0.25	8N7483	1.00	0.90	0.85	8N74167	6.25	5.40	5.10
8N7417	0.30	0.27	0.25	8N7484	0.90	0.85	0.80	8N74170	4.10	3.55	3.05
8N7422	0.48	0.40	0.40	8N7486	0.90	0.75	0.65	8N74172	2.00	1.75	1.30
8N7423	0.48	0.44	0.40	8N7491	1.00	0.85	0.90	8N74175	1.35	1.27	1.15
8N7425	0.48	0.40	0.35	8N7492	0.75	0.70	0.65	8N74176	1.60	1.35	1.20
8N7427	0.42	0.39	0.35	8N7493	0.75	0.70	0.65	8N74177	1.60	1.35	1.20
8N7428	0.50	0.45	0.42	8N7494	0.80	0.75	0.70	8N74180	1.55	1.30	1.20
8N7430	0.20	0.18	0.16	8N7495	0.85	0.75	0.70	8N74181	1.00	0.80	1.00
8N7432	0.42	0.38	0.35	8N7496	1.00	0.70	0.65	8N74182	2.00	1.80	1.80
8N7433	0.70	0.61	0.44	8N7497	0.25	0.50	0.50	8N74184	2.40	2.00	1.80
8N7437	0.65	0.60	0.50	8N74100	2.50	2.30	2.00	8N74185A	2.40	2.00	1.80
8N7438	0.65	0.60	0.50	8N74104	1.45	1.35	1.20	8N74190	1.95	1.85	1.75
8N7440	0.20	0.18	0.16	8N74105	1.45	1.35	1.20	8N74191	1.95	1.85	1.75
8N7441A	0.75	0.72	0.70	8N74107	0.50	0.45	0.40	8N74192	2.00	1.80	1.80
8N7442	0.75	0.72	0.70	8N74110	0.80	0.70	0.65	8N74193	2.00	1.80	1.80
8N7443	1.00	0.95	0.90	8N74118	1.00	0.95	0.90	8N74194	2.50	2.25	1.90
8N7445	2.00	1.75	1.60	8N74119	1.90	1.78	1.65	8N74195	1.85	1.70	1.60
8N7446	2.00	1.75	1.60	8N74121	0.60	0.55	0.50	8N74196	1.50	1.40	1.30
8N7447	1.75	1.60	1.45	8N74122	1.35	1.25	1.10	8N74197	1.50	1.40	1.30
8N7448	1.75	1.60	1.45	8N74123	2.70	2.55	2.47	8N74198	4.60	3.70	3.35
				8N74141	1.00	0.95	0.90	8N74199	4.80	3.70	3.35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX  
 LARGER QUANTITY PRICES PHONE (01) 402 4891  
 TEXAS HANDBOOK DATA 2, H.C. 700 PAGES DATA 60p. POST 20p.  
 HIGH POWER SM 74 HOO } None in stock - send  
 LOW POWER SM 74 LOO } for list No. 36

## A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA130	10p	BC147	12p	BU105	2.25	OC44	15p	T1843	35p	2N3055	55p
AAY42	10p	BC169C	12p	BU100	15p	OC45	15p	2N3440	25p	2N3440	1.25
AAZ13	10p	BC182	10p	BY126	15p	OC57	50p	ZTX108	12p	2N3444	1.25
AC107	35p	BC214	10p	BY127	15p	OC71	15p	ZTX300	12p	2N3455	75p
AC196	25p	BCY32	75p	BY213	35p	OC72	25p	ZTX301	15p	2N3614	50p
AC127	25p	BCY34	35p	CI06D	85p	OC77	45p	ZTX302	18p	2N3615	75p
AC128	25p	BCY39	1.00	GET111	55p	OC81	25p	ZTX341	20p	2N3702	10p
AC176	25p	BCY42	30p	GET115	55p	OC83	25p	ZTX500	15p	2N3704	10p
AC187	25p	BCY43	25p	GET880	45p	OC140	55p	ZTX503	17p	2N3705	10p
AC188	25p	BCY45	2.50	LM309K		OC170	25p	2G301	30p	2N3714	1.80
ACY17	30p	BCY70	1.50	(T03)	1.87	OC171	30p	2N404	20p	2N3771	1.75
ACY20	20p	BCY72	20p	M4712	25p	OC200	45p	2N527	35p	2N3772	2.00
ACY21	20p	BCY72	15p	MJE340	50p	OC201	75p	2N696	15p	2N3790	2.25
ACY39	55p	BCY87	2.00	MJE370	70p	OC202	80p	2N697	15p	2N3819	35p
AD140	50p	BCZ11	50p	MJE520	75p	OC203	50p	2N706	10p	2N3820	25p
AD149	50p	BD124	80p	MJE2955		OC217	1.25	2N930	20p	2N3866	85p
AD181	35p	BD131	75p		1.10	ORP12	50p	2N987	45p	2N3904	15p
AD192	35p	BD132	80p	MJE3055		ORP60	40p	2N131	25p	2N3906	12p
AF117	20p	BF115	25p			P346A	20p	2N182	25p	2N4061	12p
AF118	50p	BF167	25p	MPP105	40p	RA8310AF		2N1302	18p	2N4062	12p
AF124	25p	BF173	25p	NKT214	20p		45p	2N1304	22p	2N4126	15p
AF139	30p	BF179	30p	NKT216	40p	RA8508AF		2N1305	22p	2N4871	35p
AF186	40p	BF180	30p	NKT217	40p		55p	2N1307	25p	2N5457	30p
AF239	40p	BF194	15p	NKT403	70p	TA2963	75p	2N1308	25p	2N5777	55p
AS127	30p	BF195	25p	NKT404	50p	TIL209	38p	2N1613	20p	2S001	1.00
AS228	25p	BF261	25p	OA5	50p	TIP29A	50p	2N1671	1.00	2S012	1.00
BA102	30p	BF898	25p	OA10	35p	TIP30A	60p	2N2147	75p	2S018	6.25
BA115	7p	BFX13	25p	OA81	10p	TIP31A	60p	2N2160	50p	2S026	8.50
BA143	15p	BFX34	75p	OA91	7p	TIP32A	70p	2N2217	25p	2S301	50p
BA1316	7p	BFY37	30p	OA900	7p	TIP33A		2N2221	20p	2S303	65p
BC107	10p	BFY50	20p	OA92	10p		1.00	2N2224	25p	2S324	95p
BC108	10p	BFY51	20p	OC16	75p	TIP34A			25p	40250	50p
BC109	10p	BFY52	20p	OC20	90p		1.50	2N2369A		40360	40p
BC109C	12p	BFY54	50p	OC25	40p	TIP35A			15p	40361	40p
BC113	15p	BFY90	80p	OC28	65p	TIP36A		2N2906	20p	40362	50p
BC117	20p	BLY38	8.00	OC35	50p		3.00	2N2926	(all	40368	50p
BC143	35p	BSY27	15p	OC38	15p	TIP41A	75p	2N3053	20p	40636	1.10
				OC42	40p	TIP42A	85p	2N3054	50p	40430	1.00

## INTEGRATED CIRCUIT SOCKETS LOW PROFILE PLATED PINS

(16 Lead) D.I.L. 17p	(14 Lead) D.I.L. 15p	(8 Lead) D.I.L. 15p

## QUANTITY DISCOUNTS

10% 12+ : 15% 25+ : ANY ONE TYPE  
 20% 100+ : 25% 250+

From above sections except Integrated Circuits and Special Offers where discounts are included.  
 Minimum order value £1 please.  
 Postage 7p on all orders.

## SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC/S		All Colours	
25 + 20p		25 + 9p	
100 + 17p		100 + 8p	
500 + 15p		500 + 6p	
		1000 + 5p	

AFI17 Mullard	25p
25 + 17p	
100 + 15p	
500 + 12p	

2N3819 Texas	35p
100 + 25p	
500 + 20p	
1000 + 15p	

OC170 Mullard	25p
25 + 20p	
100 + 18p	
500 + 15p	
1000 + 13p	

BC107, BC108, BC109	10p each
All Makes	
25 + 8p	
100 + 7p	
500 + 6p	
1000 + 5p	

BY127 Mullard	15p
25 + 12p	
100 + 9p	
500 + 8p	

AD161, AD162	35p each
25 + 32p	
100 + 28p	
500 + 25p	
1000 + 22p	

OA202	10p
25 + 8p	
100 + 7p	
500 + 6p	
1000 + 5p	

2N3053	20p
25 + 18p	
100 + 15p	
500 + 12p	
1000 + 10p	

OC35 Mullard	50p
25 + 45p	
100 + 40p	
500 + 35p	
1000 + 30p	

# INST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS  
SPECIAL EXPRESS MAIL ORDER SERVICE  
Express postage 1p per transistor, over ten post free  
INTEGRATED CIRCUITS 5p + 1p each added

Sp	Sp	Sp	Sp	Sp	Sp
1N21	0-17	AFZ12	1-90	BYZ16	0-85
1N22	0-20	ASV26	0-25	BYZ17	0-82
1N23	0-28	ASV27	0-25	BYZ18	0-80
1N24	0-50	ASV28	0-25	BYZ19	0-25
1N25	0-50	ASV29	0-25	BYZ15	1-00
1N26	0-25	ASV36	0-25	BYZ16	0-62
1N725A	0-20	ASV50	0-17	BYZ28C3V3	
1N914	0-07	ASV51	0-40		
1N4007	0-20	ASV53	0-20		
18113	0-15	ASV55	0-20	C111	0-65
18130	0-13	ASV62	0-25	CRS105	0-25
18131	0-18	ASV68	0-33	CRS140	0-45
18202	0-23	ASZ21	0-42	CS4B	2-50
2G371	0-22	ASZ23	0-75	CS10B	3-13
2G381	0-25	AUY10	0-28	DD000	0-15
2G414	0-20	AU101	1-50	DD003	0-15
2G417	0-20	BC107	0-10	DD006	0-18
2N404	0-20	BC121	0-10	DD007	0-10
2N697	0-15	BC109	0-10	DD008	0-40
2N698	0-40	BC113	0-15	GD3	0-33
2N706	0-10	BC115	0-20	GD4	0-05
2N708	0-15	BC116	0-25	GD5	0-33
2N709	0-15	BC116A	0-20	GD8	0-25
2N709	0-15	BC118	0-25	GD12	0-05
2N901	0-20	BC121	0-10	GET102	0-20
2N1131	0-25	BC122	0-20	GET103	0-20
2N1132	0-25	BC125	0-68	GET113	0-20
2N1302	0-18	BC126	0-65	GET114	0-15
2N1303	0-18	BC140	0-55	GET115	0-45
2N1304	0-22	BC147	0-15	GET116	0-80
2N1305	0-22	BC148	0-13	GET120	0-25
2N1306	0-20	BC149	0-15	GET872	0-80
2N1307	0-25	BC157	0-12	GET876	0-20
2N1308	0-25	BC158	0-16	GET880	0-37
2N2147	0-75	BC160	0-63	GET881	0-25
2N2148	0-75	BC169	0-18	GET892	0-25
2N2180	0-60	BCY31	0-35	GET895	0-25
2N2181	0-60	BCY32	0-65	GET844	0-08
2N2219	0-20	BCY32	0-65	GET846	0-10
2N2369A	0-15	BCY33	0-25	GET841	0-15
2N2444	1-99	BCY34	0-30	GJ3M	0-25
2N2413	0-28	BCY38	0-40	GJ4M	0-28
2N2456	0-45	BCY39	1-00	GJ5M	0-25
2N2904	0-20	BCY40	0-20	GJ7M	0-27
2N2904A	0-25	BCY42	0-25	HG1005	0-50
2N2906	0-20	BCY70	0-15	HJ100A	0-20
2N2907	0-23	BCY71	0-20	MAT100	0-25
2N2924	0-23	BCZ10	0-35	MAT101	0-30
2N2925	0-15	BCZ11	0-60	MAT120	0-25
2N2926	0-10	BD121	0-65	MAT121	0-30
2N3054	0-50	BD123	0-60	MAT129	0-87
2N3055	0-75	BD124	0-75	MJE2955	1-87
2N3702	0-10	BDY11	1-62	MJES055	0-37
2N3705	0-10	BF115	0-25	NKT128	0-35
2N3706	0-23	BF117	0-50	NKT129	0-30
2N3707	0-12	BF167	0-25	NKT211	0-25
2N3709	0-10	BF173	0-25	NKT213	0-25
2N3710	0-10	BF181	0-25	NKT214	0-15
2N3711	0-10	BF184	0-20	NKT216	0-37
2N3819	0-25	BF185	0-20	NKT217	0-35
2N5027	0-53	BF194	0-17	NKT218	1-13
2N6088	0-33	BF195	0-15	NKT219	0-33
28501	0-50	BF196	0-18	NKT222	0-20
28502	0-75	BF197	0-15	NKT224	0-22
28501	0-87	BF891	0-28	NKT221	0-24
28702	0-62	BF898	0-28	NKT271	0-25
AA129	0-20	BFX12	0-20	NKT262	0-25
AAZ12	0-30	BFX13	0-25	NKT273	0-15
AAZ13	0-10	BFX29	0-25	NKT274	0-20
AC107	0-37	BFX30	0-25	NKT275	0-25
AC126	0-20	BFX32	0-25	NKT277	0-25
AC127	0-25	BFX63	0-60	NKT278	0-25
AC128	0-20	BFX84	0-25	NKT301	0-40
AC187	0-25	BFX85	0-30	NKT304	0-75
AC189	0-25	BFX86	0-25	NKT403	0-75
AC171	0-80	BFX87	0-25	NKT404	0-55
ACY18	0-25	BFY06	0-25	NKT678	0-30
ACY19	0-25	BFY10	1-00	NKT713	0-25
ACY20	0-20	BFY11	1-25	NKT773	0-25
ACY21	0-20	BFY17	0-25	NKT777	0-88
ACY22	0-10	BFY18	0-25	O79B	0-38
ACY27	0-25	BFY19	0-25	O45	0-20
ACY28	0-17	BFY24	0-45	O48	0-12
ACY39	0-50	BFY44	1-90	O47	0-10
ACY40	0-15	BFY50	0-22	O470	0-10
ACY41	0-15	BFY51	0-20	O471	0-10
ACY44	0-25	BFY62	0-22	O473	0-10
AD140	0-50	BFY63	0-17	O474	0-10
AD149	0-50	BFY64	0-42	O479	0-10
AD181	0-37	BSX09	0-65	O481	0-08
AD182	0-87	BSX27	0-60	O485	0-12
AF106	0-20	BSX80	0-93	O486	0-15
AF114	0-25	BSX76	0-15	OA90	0-08
AF115	0-25	BSY26	0-18	OA91	0-07
AF116	0-25	BSY27	0-17	OA95	0-07
AF117	0-40	BSY95	0-10	OA202	0-20
AF118	0-62	BSY95A	0-12	OA202	0-20
AF119	0-20	BSY95	0-12	OA210	0-25
AF124	0-25	BT102/600R		OA211	0-50
AF125	0-20			AZ200	0-55
AF126	0-17	BTY42	0-92	AZ201	0-60
AF127	0-17	BTY79/100R		AZ202	0-45
AF128	0-40			AZ203	0-42
AF178	0-55	BTY79/400R		AZ204	0-30
AF179	0-65			AZ205	0-42
AF180	0-52	BY100	0-15	AZ206	0-42
AF181	0-42	BY126	0-15	AZ207	0-47
AF186	0-40	BY127	0-17	AZ208	0-38
AFY19	1-13	BY182	0-55	AZ209	0-32
AFZ11	0-40	BY213	0-25	AZ210	0-32

## THE ULTIMATE IN COMMUNICATIONS RECEIVERS

# WORLD MASTER 8 WAVE BANDS

+ WORLD MAP & TIME ZONE DIAL



Brings INSTANT WORLD-WIDE RECEPTION at the press of a button. Sensational scoop purchase of this just-released model enables us to offer a truly advanced communications receiver at a previously unheard-of price! (Similar models can cost £120 or more!) The 8 WAVEBANDS enable you to cover the world at the press of a button. You might even pick up a world scoop on your world-wide receiver! As well as all the usual BBC Programmes you can pick up Local Radio Stations (including new stations yet to be introduced). \*Pop Pirates. \*Aircraft (control to pilot—pilot to control). \*Shipping. \*Taxis. \*RAC. \*AA. \*Fire and Ambulances; \*Continental and 100s more too numerous to list, from Australia, Africa, America, India, Europe. You'll get hour after hour of enjoyable listening on this superb receiver 24 hours a day—7 days a week. A complete hobby in itself. Enjoy the exciting cross-talk between control towers and airline pilots—listen to the progress of an ambulance on its way to an accident—hear the deep-sea trawler captain's ship-to-ship and ship-to-shore conversations. PLUS many more exciting and absorbing Public Service Band transmissions we are not allowed to mention. This set has been manufactured by one of the most advanced companies in radio and electronic communications and carries their FULL WRITTEN GUARANTEE. Attractively finished in Leatherette and stainless steel to add quality and distinction to any living-room. Completely portable using standard batteries (obtainable anywhere)—or can be plugged directly into mains. 14 Transistors, 9 diodes, 1 thermistor, internal ferrite rod antenna and external Telescopic Antenna. Tone, volume and tuning controls. Very latest keyboard push-button waveband selector. Dial light (enabling use in darkness). Special WORLD-WIDE DIAL and WORLD MAP enables you to tell the correct time in any country of the world (essential for world listening). Hi-fidelity earphone automatically cuts out main speaker when in use. Freqs.: Long Wave 150-350Kcs. Medium 535-1605 Kcs. Marine 1.6-4.5Mcs. Short Wave 4-12Mcs. Short Wave 12-24Mcs. FM/VHF 88-108Mcs. AIRCRAFT 108-135Mcs. PUBLIC SERVICE BANDS 135-174Mcs.

**CASH PRICE**  
**£28-50** + 50p p. & p. or send £7-50 deposit + 50p p. & p. and 6 monthly payments of £4-40 (Total £23-90).

Note: Ministry of Posts and Telecommunications state that a licence not generally available to the public is required for the reception of Aircraft, Fire-brigade, Shipping, etc. BUT THERE'S NO LICENCE NEEDED TO BUY!

Send 5p for comprehensive brochure of specialised frequency radios  
**SCIENTIFIC AND TECHNICAL (PE10)**  
**507-511 LONDON ROAD, WESTCLIFF, ESSEX**

1/2W TRANSISTOR AMPLIFIER, £1; 10W, £3-75, 1W VALVE AMPLIFIER, £3. STEREO HEADPHONES, 8 ohm £1-95, with Volume Control, £6. HIGH IMPEDANCE (2,000 ohm), 80p. RECORDING TAPE, 5in L.P. 900ft, 45p; 5 1/2in L.P. 1,200ft, 60p; 7in L.P. 1,800ft, 80p. MICROPHONES: Lapel, 28p; ACOS Mic, 45, 90p; Dual Impedance 600 ohm and 50kΩ, £4-50. ROTARY SWITCHES 250V 2A, 9p. PLUGS: Jack Standard, 10p; Screened, 13p; 2-5mm and 3-5mm, 6p; Screened, 8p. TUNING METERS, 500μA, 38p. 100 MIXED RESISTORS, 45p. MINIATURE INDICATOR LAMPS (5 colours), 11p; 6V or 12V BULBS for above, 4p. MAINS NEONS panel mounting (red, green, clear), 15p. TELEPHONE AMPLIFIERS, £2-62. INTERCOMS, 2 way, £2-50. CARTRIDGES: COMPATIBLE ACOS GP91-3SC, 90p; STEREO GP93-1, £1-15. CAPACITORS: 100mF, 25V, 5p; 0-047, 630V, 2 1/2p; 400-200-50-16mF, 300V, 30p. TRANSISTORS AND DIODES: AC107, 13p; AC126, 11p; AC127, 11p; AC128, 15p; AC176, 11p; AD140, 39p; AD149, 39p; AD161, 35p; AD162, 35p; AF117, 18p; BC107, 10p; BC108, 10p; BC109, 10p; OC26, 25p; OC44, 11p; OC45, 11p; OC71, 11p; OC81, 11p; OC35, 39p; 2N2926G, 13p; 1N4004, 8p; 1N4006, 12p; OA81, 7p; SILICON BRIDGE RECTIFIER B40, C1500/1000, 33p.

Special Prices for quantity quoted on request. Large S.A.E. for list. Add 10p for P. & P. on orders under £5.

**M. DZIUBAS**  
**158 Bradshawgate, Bolton, Lancs**

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.  
Valves, Tubes and Transistors - Closed Sat. 1 p.m.-3 p.m.  
Terms C.W.O. only Tel. 01-677 2424-7



# SEMI-CONDUCTOR DEVICES/VALVES

## ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415		2N4548		35p		BC114		15p		BFW90		22p		NKT219		30p	
2G301	20p	2N3417	37p	2N4548	35p	BC114	15p	BFW90	22p	NKT219	30p	2G302	20p	2N3417	37p	NKT219	30p	2G303	20p
2G303	20p	2N3439	130p	2N4548	35p	BC116	15p	BFW91	22p	NKT224	25p	2G304	20p	2N3440	97p	NKT224	25p	2G305	20p
2G306	42p	2N3540	17p	2N4548	35p	BC118	15p	BFX12	25p	NKT225	25p	2G306	42p	2N3544	17p	NKT225	25p	2G307	20p
2G308	42p	2N3565	15p	2N4548	35p	BC121	15p	BFX29	25p	NKT228	25p	2G308	42p	2N3565	15p	NKT228	25p	2G309	20p
2G309	20p	2N3566	15p	2N4548	35p	BC122	15p	BFX30	25p	NKT230	30p	2G310	20p	2N3568	15p	NKT230	30p	2G311	20p
2G311	20p	2N3568	15p	2N4548	35p	BC126	15p	BFX37	37p	NKT240	27p	2G312	20p	2N3570	15p	NKT240	27p	2G313	20p
2G313	20p	2N3570	15p	2N4548	35p	BC134	12p	BFX48	47p	NKT242	27p	2G314	20p	2N3572	15p	NKT242	27p	2G315	20p
2G315	20p	2N3572	15p	2N4548	35p	BC136	12p	BFX65	30p	NKT243	65p	2G316	20p	2N3575	15p	NKT243	65p	2G317	20p
2G317	20p	2N3575	15p	2N4548	35p	BC138	15p	BFX86	25p	NKT244	17p	2G318	20p	2N3577	15p	NKT244	17p	2G319	20p
2G319	20p	2N3577	15p	2N4548	35p	BC137	15p	BFX88	25p	NKT245	20p	2G320	20p	2N3580	15p	NKT245	20p	2G321	20p
2G321	20p	2N3580	15p	2N4548	35p	BC140	15p	BFX89	25p	NKT262	20p	2G322	20p	2N3582	15p	NKT262	20p	2G323	20p
2G322	20p	2N3582	15p	2N4548	35p	BC141	15p	BFX93A	70p	NKT271	20p	2G324	20p	2N3584	15p	NKT271	20p	2G325	20p
2G324	20p	2N3584	15p	2N4548	35p	BC147	10p	BFY11	42p	NKT272	20p	2G326	20p	2N3586	15p	NKT272	20p	2G327	20p
2G326	20p	2N3586	15p	2N4548	35p	BC148	10p	BFY18	25p	NKT282	20p	2G328	20p	2N3588	15p	NKT282	20p	2G329	20p
2G328	20p	2N3588	15p	2N4548	35p	BC149	10p	BFY21	25p	NKT273	20p	2G330	20p	2N3590	15p	NKT273	20p	2G331	20p
2G330	20p	2N3590	15p	2N4548	35p	BC152	17p	BFY21	25p	NKT275	20p	2G332	20p	2N3592	15p	NKT275	20p	2G333	20p
2G332	20p	2N3592	15p	2N4548	35p	BC153	20p	BFY24	45p	NKT278	25p	2G334	20p	2N3594	15p	NKT278	25p	2G335	20p
2G334	20p	2N3594	15p	2N4548	35p	BC154	20p	BFY29	40p	NKT281	27p	2G336	20p	2N3596	15p	NKT281	27p	2G337	20p
2G336	20p	2N3596	15p	2N4548	35p	BC157	15p	BFY30	40p	NKT282	20p	2G338	20p	2N3598	15p	NKT282	20p	2G339	20p
2G338	20p	2N3598	15p	2N4548	35p	BC158	15p	BFY41	50p	NKT283	20p	2G340	20p	2N3600	15p	NKT283	20p	2G341	20p
2G340	20p	2N3600	15p	2N4548	35p	BC159	12p	BFY43	62p	NKT403	75p	2G342	20p	2N3602	15p	NKT403	75p	2G343	20p
2G342	20p	2N3602	15p	2N4548	35p	BC160	35p	BFY50	20p	NKT404	55p	2G344	20p	2N3604	15p	NKT404	55p	2G345	20p
2G344	20p	2N3604	15p	2N4548	35p	BC167	11p	BFY51	20p	NKT406	62p	2G346	20p	2N3606	15p	NKT406	62p	2G347	20p
2G346	20p	2N3606	15p	2N4548	35p	BC168H	10p	BFY53	15p	NKT451	82p	2G348	20p	2N3608	15p	NKT451	82p	2G349	20p
2G348	20p	2N3608	15p	2N4548	35p	BC168L	10p	BFY53	15p	NKT452	82p	2G350	20p	2N3610	15p	NKT452	82p	2G351	20p
2G350	20p	2N3610	15p	2N4548	35p	BC169	10p	BFY53	15p	NKT453	82p	2G352	20p	2N3612	15p	NKT453	82p	2G353	20p
2G352	20p	2N3612	15p	2N4548	35p	BC170	12p	BFY77	57p	NKT713	20p	2G354	20p	2N3614	15p	NKT713	20p	2G355	20p
2G354	20p	2N3614	15p	2N4548	35p	BC171	15p	BFY77	57p	NKT717	42p	2G356	20p	2N3616	15p	NKT717	42p	2G357	20p
2G356	20p	2N3616	15p	2N4548	35p	BC172	15p	BFY90	65p	NKT717	42p	2G358	20p	2N3618	15p	NKT717	42p	2G359	20p
2G358	20p	2N3618	15p	2N4548	35p	BC175	22p	BFY90	65p	NKT734	27p	2G360	20p	2N3620	15p	NKT734	27p	2G361	20p
2G360	20p	2N3620	15p	2N4548	35p	BC175	22p	BFY90	65p	NKT736	35p	2G362	20p	2N3622	15p	NKT736	35p	2G363	20p
2G362	20p	2N3622	15p	2N4548	35p	BC176	20p	BFY90	65p	NKT773	25p	2G364	20p	2N3624	15p	NKT773	25p	2G365	20p
2G364	20p	2N3624	15p	2N4548	35p	BC178	20p	BFY90	65p	NKT773	25p	2G366	20p	2N3626	15p	NKT773	25p	2G367	20p
2G366	20p	2N3626	15p	2N4548	35p	BC179	20p	BFY90	65p	NKT773	25p	2G368	20p	2N3628	15p	NKT773	25p	2G369	20p
2G368	20p	2N3628	15p	2N4548	35p	BC182	10p	BFY90	65p	NKT773	25p	2G370	20p	2N3630	15p	NKT773	25p	2G371	20p
2G370	20p	2N3630	15p	2N4548	35p	BC182L	10p	BFY90	65p	NKT773	25p	2G372	20p	2N3632	15p	NKT773	25p	2G373	20p
2G372	20p	2N3632	15p	2N4548	35p	BC183	9p	BFY90	65p	NKT773	25p	2G374	20p	2N3634	15p	NKT773	25p	2G375	20p
2G374	20p	2N3634	15p	2N4548	35p	BC183L	9p	BFY90	65p	NKT773	25p	2G376	20p	2N3636	15p	NKT773	25p	2G377	20p
2G376	20p	2N3636	15p	2N4548	35p	BC184	7p	BFY90	65p	NKT773	25p	2G378	20p	2N3638	15p	NKT773	25p	2G379	20p
2G378	20p	2N3638	15p	2N4548	35p	BC184L	11p	BFY90	65p	NKT773	25p	2G380	20p	2N3640	15p	NKT773	25p	2G381	20p
2G380	20p	2N3640	15p	2N4548	35p	BC186	25p	BFY90	65p	NKT773	25p	2G382	20p	2N3642	15p	NKT773	25p	2G383	20p
2G382	20p	2N3642	15p	2N4548	35p	BC187	27p	BFY90	65p	NKT773	25p	2G384	20p	2N3644	15p	NKT773	25p	2G385	20p
2G384	20p	2N3644	15p	2N4548	35p	BC187L	27p	BFY90	65p	NKT773	25p	2G386	20p	2N3646	15p	NKT773	25p	2G387	20p
2G386	20p	2N3646	15p	2N4548	35p	BC188	20p	BFY90	65p	NKT773	25p	2G388	20p	2N3648	15p	NKT773	25p	2G389	20p
2G388	20p	2N3648	15p	2N4548	35p	BC188L	20p	BFY90	65p	NKT773	25p	2G390	20p	2N3650	15p	NKT773	25p	2G391	20p
2G390	20p	2N3650	15p	2N4548	35p	BC189	20p	BFY90	65p	NKT773	25p	2G392	20p	2N3652	15p	NKT773	25p	2G393	20p
2G392	20p	2N3652	15p	2N4548	35p	BC190	20p	BFY90	65p	NKT773	25p	2G394	20p	2N3654	15p	NKT773	25p	2G395	20p
2G394	20p	2N3654	15p	2N4548	35p	BC190L	20p	BFY90	65p	NKT773	25p	2G396	20p	2N3656	15p	NKT773	25p	2G397	20p
2G396	20p	2N3656	15p	2N4548	35p	BC191	20p	BFY90	65p	NKT773	25p	2G398	20p	2N3658	15p	NKT773	25p	2G399	20p
2G398	20p	2N3658	15p	2N4548	35p	BC191L	20p	BFY90	65p	NKT773	25p	2G400	20p	2N3660	15p	NKT773	25p	2G401	20p
2G400	20p	2N3660	15p	2N4548	35p	BC192	20p	BFY90	65p	NKT773	25p	2G402	20p	2N3662	15p	NKT773	25p	2G403	20p
2G402	20p	2N3662	15p	2N4548	35p	BC192L	20p	BFY90	65p	NKT773	25p	2G404	20p	2N3664	15p	NKT773	25p	2G405	20p
2G404	20p	2N3664	15p	2N4548	35p	BC193	20p	BFY90	65p	NKT773	25p	2G406	20p	2N3666	15p	NKT773	25p	2G407	20p
2G406	20p	2N3666	15p	2N4548	35p	BC194	20p	BFY90	65p	NKT773	25p	2G408	20p	2N3668	15p	NKT773	25p	2G409	20p
2G408	20p	2N3668	15p	2N4548	35p	BC194L	20p	BFY90	65p	NKT773	25p	2G410	20p	2N3670	15p	NKT773	25p	2G411	20p
2G410	20p	2N3670	15p	2N4548	35p	BC195	20p	BFY90	65p	NKT773	25p	2G412	20p	2N3672	15p	NKT773	25p	2G413	20p
2G412	20p	2N3672	15p	2N4548	35p	BC196	20p	BFY90	65p	NKT773	25p	2G414	20p	2N3674	15p	NKT773	25p	2G415	20p
2G414	20p	2N3674	15p	2N4548	35p	BC196L	20p	BFY90	65p	NKT773	25p	2G416	20p	2N3676	15p	NKT773	25p	2G417	20p
2G416	20p	2N3676	15p	2N4548	35p	BC197	20p	BFY90	65p	NKT773	25p	2G418	20p	2N3678	15p				

# HI-FI EQUIPMENT

## SAVE UP TO 33 1/3% OR MORE

### SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!

#### RECORD DECKS

B.S.E.		
UA50 Mono:	\$4-97	
C129:	\$6-50	
MP60	\$10-40	
610	\$14-07	
610	\$11-50	
610	\$9-40	
610	\$8-45	
MP60/G800*	\$12-90	
MP60 TPD1	\$17-12	
MP60/TPD1/		
G800*	\$19-50	
MP60 TPD2	\$15-40	
610 TPD1	\$20-35	
610 TPD1	\$18-20	
210 Package*	\$9-55	
HT70	\$14-99	
HT70/G800*	\$17-85	
HT70 Package*	\$21-60	
G800*	\$23-95	

GARRARD		
2025TC*	\$8-50	
40B*	\$10-25	
SP25 III	\$10-25	
SL65B	\$13-45	
AP76	\$18-85	
SL72B	\$22-95	
SL95B	\$32-50	
401	\$32-60	
ZERO 100A	\$39-95	
ZERO 100B	\$37-50	
ZERO 100S	\$37-50	

\*Mono cart. \*Stereo cart. All others lens cartridge. Carriage 50p extra any model.

Garrard 2025TC/STAHCD	\$12-95
Garrard SP25 III/STAHCD	\$16-95
Garrard SP25 III/G800	\$18-50
Garrard SP25 III/M76-6	\$19-50
Garrard SP25 III/M44-7	\$19-75
Garrard SP25 III/G800 (Play on Plinth and Cover)	\$19-75
Garrard AP76/G800	\$22-75
Garrard AP76/M76-6	\$23-25
Garrard AP76/M50E	\$24-25
Garrard AP76/M76BJ	\$24-25
Garrard AP76/G800E	\$24-25
BSR McDonald MP60/G800	\$19-95
BSR McDonald MP60/M44-7	\$20-95
BSR McDonald MP60/M44-E	\$21-50
Golding GL72/G800	\$21-60
Golding GL75/G800	\$21-95
Golding GL75/G800E	\$24-95

Carriage 50p any item

#### SINCLAIR EQUIPMENT



Project 60. Package offers. 2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply, \$15-95. Carr. 37p. Or with PZ6 power supply, \$18-00. Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply, \$20-25. Carr. 37p. Transformer for PZ8, \$2-97 extra. Add to any of the above \$4-45 for active filter unit and \$13-80 for pair of Q16 speakers. Project 60 FM Tuner \$15-75. Carr. 37p. New Project 605 \$20-97. Carr. 37p. All Sinclair products in stock. IC12 \$1-80. P. & P. 10p. 2,000 amplifier, \$21-95. Carr. 37p. 3000 Amplifier, \$28-50. Carr. 37p. Neoteric amplifier, \$48-95. Carr. 37p.


#### LATEST CATALOGUE

Our 7th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 320 pages, fully illustrated and detailing thousands of items at bargain prices.

SEND NOW ONLY 40p P. & P. 10p



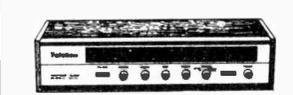
#### TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/ Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/ Cer phono inputs. AFC/Built-in MPX. OUR PRICE \$28-25. Carr. 50p.
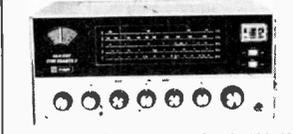
#### SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and 0-55 to 30 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO. AVC. ANL. 'S' meter. AM/CW/SS B. Integrated speaker and phone socket. Operation 220/240V AC or 12V DC. Size 3 1/2 x 2 1/2 x 1 1/2 inch. Complete with instructions and circuit. \$28-50. Carr. 50p.

#### WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet. 20 watts r.m.s. Brand new. \$1-50. Carr. 37p.

#### ★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 1/2 x 4 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 MHz. Ready built ready for use. Fantastic value for money. \$6-75. P. & P. 12p. Stereo multiplex adaptors \$4-97.

TAPE CASSETTES. Top quality Hi Fi Low Noise in Philips Library cases. C80 3 for 75p 10 for \$2-35 P. & P. C90 3 for \$1-05 10 for \$2-30 10p C120 3 for \$1-35 10 for \$4-20 extra Tape Head Cleaner 80p each

#### TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER



Battery operated, 11 meg input. 28 ranges. Large 4 1/2 in mirror scale. Size 5 1/2 in x 4 1/2 in x 2 1/2 in. D.c. volts 0-3-1,200V. A.c. volts 3-300V R.M.S. 8-0-800V P.P. D.c. current 0-10-12mA. Resistance up to 2,000,000 Ohms. Decibels -20 to +51dB. Complete with leads/instructions. \$17-50. P. & P. 20p.

#### TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.c. volts 1-5-1,500V. A.c. volts 1-5-1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation. Complete with probe and instructions. \$17-50. P. & P. 30p. Additional Probes available: R.P. \$2.12. H.V. \$2-50

## SINCLAIR IC-12



List Price £2-98  
OUR PRICE  
£1-80 P. & P. 10p.

#### HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.  
2 Station £2-97, P. & P. 15p.  
3 Station £5-25, P. & P. 15p.  
4 Station £6-62, P. & P. 17p.

#### EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000Hz. 15 watt R.M.S. Available 8 or 15 ohms. £7-50 each. P. & P. 37p.  
Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000Hz. 8 watt R.M.S. Available 8 or 15 ohms. £8-50 each. P. & P. 25p.

#### TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1-97. P. & P. 15p.

#### MP7 MIKER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 3 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K; 2 x 3mV 500 ohms. Phono meg. 4mV 50K. Phono 1 meg. 100mV 1 meg. Output 520mV 100K. £8-97. P. & P. 20p.

#### 1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo/headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2-25. P. & P. 15p.

#### MCA 220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC. Output 120 VAC or 176-250V input output 240 VAC. 200 VA rating. £11-97. Carr. 50p.

#### 230 VOLT A.C. 50 CYCLES RELAYS

Brand New. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

## SPECIAL OFFER! SINCLAIR PROJECT STEREO FM TUNER



The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 87.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2µV. AFC range ± 200KHz. Signal to noise ratio: 65dB. Output voltage 2 x 150mV. Operating voltage 25-30V D.C. Size: 93 x 40 x 207mm. REC. LIST PRICE £25.

OUR PRICE **£15-75** P. & P. 25p ONLY

Unrepeatable offer—buy now and save over £9.

#### U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 ohm V. Automatic stereo indicator. Sensitivity: 2µV. AFC range ± 200KHz. Signal to noise ratio: 65dB. Output voltage 2 x 150mV. Operating voltage 25-30V D.C. Size: 93 x 40 x 207mm. REC. LIST PRICE £25.



#### PRS-2 PHOTO ELECTRIC RELAY SYSTEM

Inexpensive warning or counting system consisting of an encoder and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Encoder unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V A.C. Complete with cables and instructions. £9-97. P. & P. 25p.



#### UNR-30 RECEIVER

4 Bands covering 550KHz-30MHz B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £15-75. Carr. 37p.



#### LAFAYETTE HA-600 RECEIVER

General coverage 150-400KHz, 550KHz-30MHz. PET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, S Meter, Bandspread. RF Gain. 15in x 9in x 8 1/2in. 18lb. 220/240V a.c. or 12V d.c. Brand new with instructions £50. Carr. 50p.



## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock Single hole fixing, 1/2 in. dia. shafts. Bulk quantities available.  
25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms. 90p. P. & P. 7p.  
50 WATT. 10/25/50/100/250/500/1,000/1,500 or 5,000 ohms. £1-15. P. & P. 7p.  
100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms. £1-65. P. & P. 7p.

#### "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality Low price Immediate delivery	
S-260 General Purpose Bench Mounting	
1A	£7-00
2-5A	£8-05
5A	£11-75
8A	£15-90
10A	£22-50
12A	£23-80
20A	£49-00


ALL MODELS INPUT 230 VOLTS. 50/60 CYCLES. OUTPUT VARIABLE 0-280 VOLTS. Special discounts for quantity

# G.W. SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-637 2232  
27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
257/258 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-580 0670  
3 LITTLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LITTLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387


CALLERS WELCOME MONDAY TO SATURDAY 9AM-6PM  
All Mail Orders to— 11-12, Paddington Green, London, W.2 Tel: 01-262 6562

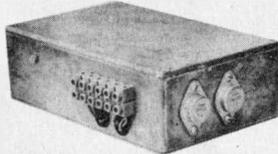**PRACTICAL ELECTRONICS**  
**"SCORPIO"**  
**ELECTRONIC IGNITION**  
**SYSTEM**



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12v ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required. Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision. Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2in x 4 1/2in x 2 1/2in approx. Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P. S.A.E. with all enquiries.

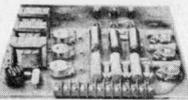**PSYCHEDELIC LIGHTING.**  
**UNIT Mk. 3**



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source. The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid. S.A.E. with all inquiries.

**DABAR ELECTRONIC PRODUCTS**  
 98a LICHFIELD STREET, WALSALL  
 STAFFS WS1 1UZ  
 WALSALL 34365  
 MAIL ORDER ONLY

**OSMABET LTD.** We make transformers amongst other things

**MAINS TRANSFORMERS**  
 Prim. 200/240V a.c. TX6, 425-0-425V, 500 Ma, 6-3V 6A CT, 6-3V 6A CT, 0-5-6-3V 3a, £12-75; TX1, 425-0-425V, 250Ma, 6-3V 4A CT, 6-3V 4A CT 0-5-6-3V 3a, £7-50; TX2, 250-0-250V, 100Ma, 6-3V 4A CT, 0-5-6-3V 3a, £4-05; TX5, 300-0-300V, 120Ma, 6-3V 2A CT, 6-3V 2A, 6-3V 1A, £4-05; TX8, 250-0-250V, 60Ma, 6-3V 1.5A, £2-10; MT1, 200V, 30Ma, 6-3V 1A, £1-20; MT2, 230V, 45Ma, 6-3V 1.5A, £1-50; MT2A, 250V, 60Ma, 6-3V 2A, £1-95; MT3 Prim. 110/240V, Sec. 250V, 100Ma, 6-3V 2A, £2-25.

**AUTO TRANSFORMERS**  
 0-110-200-220-240V a.c. up or down fully shrouded fitted insulated terminal blocks. 30W £1-35; 50W £1-80; 75W £2-10; 100W £2-55; 150W £3-15; 200W £3-80; 300W £5-25; 400W £6-30; 500W £7-50; 600W £8-25; 750W £9-75; 1,000W £12-75; 1,500W £18; 2,000W £24-75; 3,000W £33; 4,000W £45.

**MULTIVOLT TRANSFORMERS**  
 Prim. 200/240V a.c. OMT4/1 tapped sec. 0-60V 1A, £2-25; OMT4/2, ditto 2A, £3-45; OMT5/1 tapped sec. 0-110V 1A, £3-45; Duo sec. 12V 4A-12V 4A, £3-80; Duo sec. tapped, 0-10-20-25V 2A-0-10-20-25V 2A, £3-60.

**LOW VOLTAGE TRANSFORMERS**  
 Prim. 200/240V a.c. 6-3V 1.5A, 35p; 3A, £1-13; 6A CT, £1-80; 12V 1A, £1-13; 3A CT, £1-80; 6A CT, £2-70; 18V, 15A CT, £1-80; 24V, 1.5A CT, £1-50; 36V CT, £2-70; 6A, £2-75; 8A, £2; 12A, £2; 40V, 3A CT, £2-45.

**MIDGEE RECTIFIER TRANSFORMERS**  
 For FW rect. size 1 1/2 x 2 x 1 1/2in, Prim. 200/240V a.c. output, PPT1, 0-9V, 0-3A, PPT2, 12-0-12V, 0-25A, PPT3, 20-0-20V, 0-15A, £1-20 each; ditto, size 2 x 2 1/2 x 1 1/2in MTV1, 9-0-9V, 1A, 88p; MTV2, 12-0-12V, 1A, MTV3, 20-0-20V, 0-75A, £1-80 each.

**O/P TRANSFORMERS FOR POWER AMPLIFIERS**  
 P.P. sec. tapped 3-7-5-15 ohms, A-A 6-6kΩ, 30W (KT66, etc.), £4-05; 50W, 3kΩ, A-A, £6-75; 100W, 3kΩ, A-A, £13-4 (KT68, etc.) £11-40 and to 400W.

**LOUDSPEAKERS FOR POWER AMPLIFIERS**  
 New, famous makes, 15W with tweeter, £4-99; 25W, £6-50; 35W, £7-80; 50W, £10-50; 100W, £22-50; E.M.I. 131 x 8in 10W, £2-00 or £1-60 each.

**DIITTO WITH TWO TWEETERS AND XOVER, £4-00.**  
 Speakers 2-16kHz 10W 8 or 16 ohms, £1-50. Hi-Fi 8 x 3in 8Ω, £1-95; 6in 3Ω or 15Ω, £2-10.

**G.E.C. MANUAL OF POWER AMPLIFIERS**  
 Covering valve amplifiers of 30 to 400 watts, with price list of transformers and chokes specified, 25p.

**LOUDSPEAKERS**  
 2 1/2in 16Ω, 2 1/2in 25Ω, 3in 8 or 30Ω, 60p each; 3 1/2in 3 or 15Ω, 4in 8 or 15Ω, 5in 3, 15 or 25Ω, 6in 3, 3.8, 15 or 25Ω, 6in 8, 4in 8 or 25Ω, 7 x 4in 3Ω 6 1/2in 3Ω, £1-08; 8 x 3in 3, 8, 15 or 25Ω, £1-50; 8in 3Ω, £1-85.

**SPEAKER AUTO MATCHING TRANSFORMER 12W**  
 3 to 8 or 15 ohms, up or down, 75p. P. & P. 15p.

**MINIATURE RELAYS FOR MODELS, ETC.**  
 1 x 1 x 1 1/2in box, with transparent cover, 2 C.O. in 9; 15; 20 or 30V d.c. 50p each.

**BULK TAPE ERASERS**  
 Instant erasure, tape spools and cassettes, demagnetize tape heads, a.c. 200/250V, £2-40 plus 24p P. & P.

**PRINTED CIRCUIT ETCHING KITS**  
 Complete outfit; solutions and equipment to make your own P.C. boards instructions, £1-40, P. & P. 21p. Extra p.c. Boards 8 x 6in, 15p each.

**TAPE RECORDER MOTORS**  
 A variety of uses, Blowers, Fans, etc., new. 230/250V a.c. 50p each.

**CONDENSERS**  
 Paper: 0.01/2kV 121p; 0.1/1kV 121p; 0.22/1kV 80p; 0.22/800V a.c. 25p; 0.47/700V 15p; 0.47/1kV 25p; 4/500V 25p. Electrolytics: 100 + 200/275V 40p; 100 + 200/350V 50p; 100 + 60/450V 25p; 350 + 50/325V 15p; 100 + 400/275V 20p; 24/450V 10p; 2500/64V 50p

**BATTERY ELIMINATORS/POWER UNITS**  
 To operate battery equipment from mains 200/240V a.c. Outputs, 6V, £1-50; 9V, £1-50; 7.5V (for cassettes), £2-00; 12V 1A, £3-00; 40V 1A, £4-50. Carriage extra on all orders, etc., etc.

**S.A.E. INQUIRIES-LISTS. MAIL ORDER ONLY**  
 46 Kealworth Road, Edgware, Middx. HA8 5TG  
 Tel. 01-958 9314

**U.H.F. TV AERIALS**  
 SUITABLE FOR COLOUR & MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
 7 element £2.25, 11 element £2.75, 14 element £3.25, 18 element £3.75.

**WALL MOUNTING c/w WALL ARM AND BRACKET.** 7 element £3.25, 11 element £3.75, 14 element £4.25, 18 element £4.75.

**CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT.** 7 element £4, 11 element £4.50, 14 element £4.75, 18 element £5.25.

**MAST MOUNTING** arrays only 7 element £2.25, 11 element £2.75, 14 element £3.25, 18 element £3.75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd.


**KING TELEBOOSTERS** from £3.75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7-50. State clearly channel number required on all orders. P. & P. on all aerials 50p accs. 15p. C.W.O. min. C.O.D. charge 25p.

**BBC-ITV-FM AERIALS**  
 BBC (band 1) Wall S/D £2. LOFT inverted 'T' £1.25. EXTERNAL 'H' array only £3. ITV (band 3) 5 element loft array £2-50. 7 element £3. COMBINED BBC-ITV left 1 + 5 £2.75. 1 + 7 £3.50. WALL AND CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from £3.75.

**COMBINED U.H.F.-V.H.F. aerials** 1 + 5 + 9 £4, 1 + 5 + 14 £4.50, 1 + 7 + 14 £5. F.M. RADIO loft S/D £1. 3 element £3.25. 4 element £3.50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p, accs. 30p. C.W.O. min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

**CALLERS WELCOMED OPEN ALL DAY SATURDAY**  
**'K.V.A. ELECTRONICS**  
 40-41 Monarch Parade, London Rd.  
 Mitcham, Surrey  
 Telephone 01-648 4884

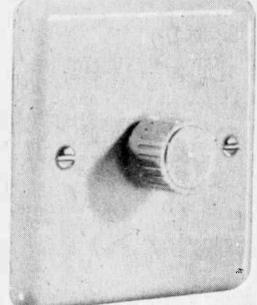Vary the strength of your lighting with a **DIMMASWITCH**



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:  
 600 Watt—£3.20. Kit Form £2-70  
 300 Watt—£2.70. Kit Form £2-20  
 All plus 10p post and packing.  
 Please send C.W.O. to:—

**DEXTER & COMPANY**  
 1 ULVER HOUSE, 19 KING STREET  
 CHESTER CH1 2AH Tel. 0244-25883  
 As supplied to H.M. Government Departments

Please mention **PRACTICAL ELECTRONICS** when replying to **ADVERTISEMENTS**

### DRILL CONTROLLER

#### NEW 1KW MODEL

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. \$1.50 plus 13p post and insurance. Made up model also available. \$2.25 plus 13p post and p.



### MAINS OPERATED CONTACTOR

220/240V. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 1/2 in. \$1.50 each. 10 for \$13.50.



### NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic pusher suitable for operating, 5p each, 45p doz.



### MICRO SWITCH

5 amp changeover contacts, 6p each. \$1 doz. 15 amp Model 10p each or \$1.05 doz.




### MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 2 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 20p each, \$1.80 for ten, your assortment.

### WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

### 15 AMP ELECTRICAL PROGRAMMER

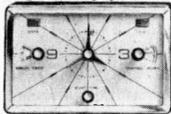

Have radio playing and kettle boiling as you awake, switch on lights to ward off intruders, have warm house to come home to. All possible with electrical programmer clock by famous maker with 15 amp on/off switch. Switch on time can be set anywhere to stay on up to 8 hours. Independent 60 minute memory jogger. A beautiful unit. Price \$1.95 + 20p p. & p. or with glass front chrome bezel 75p. extra.



### TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless, August issue. \$2.95 plus 20p post and insurance.

### SNAP ACTION SLIDE SWITCH

Rated 5a. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. 5p each, 10 for 45p.



### NUMICATOR TUBES

For digital, instruments counters, timers, clocks, etc. Hi-vac XN. 3. Price \$1.45 each. 10 for \$13.

### 12 WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper cores each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 80p per yard.



### LIGHT CELL

Almost zero resistance in sub light increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in dia. by 1/2in thick. Rated at 500 Mw, wire ended. 48p with circuit. Also ORP12 light cell 45p.

Miniature Tubes. These are approx. 1/2in diameter and need miniature pin and connectors. 3 sizes available: 9in 6 watt, 12in 8 watt, 21in. 13 watt. All are 55p each. Less 10% on 10 or more.

A.C. Mains Buzzer. These are open constructions intended for fitting into instruments, etc. Size approx. 1 1/2in high x 1 1/2in deep x 1/2in wide. Price 10p + 20p.

5 Watt Mains Transformer. As fitted into our heavy duty power pack—this has tapped primary screen and four 10V secondaries—these may be loaded to a maximum of 250 watt a.c. output. Voltage available 10-20-30 and 40V, also 20-0-20 and 10-0-10V. This transformer weighs 7 1/2lb. Price \$3 plus 45p post.

Panel Mounting Changeover Switch. With centre on position. Rated at 5 amp d.c. These switches easily handle up to 15 amp a.c. 15p each; 7 for \$1.25.




### GOOD COMPANION

We can now offer these again in modular version using Mullard A.F. and I.F. Modules and Radiomobile Permeability Tuner. Should not take more than an evening to make. Cabinet size approx. 1 1/2in wide x 8in. high x 3 1/2in. deep. Complete assembly instructions—\$4.75 plus 25p post and ins.
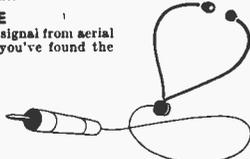
### RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. \$2—twin stethoscope instead of earpiece 75p extra—post and ins. 20p.



### STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact standard 1/2" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	40p							
3 poles	40p	40p							
4 poles	40p	40p							
5 poles	40p	40p							
6 poles	40p	40p							
7 poles	40p	40p							
8 poles	40p	40p							
9 poles	40p	40p							
10 poles	40p	40p							
11 poles	40p	40p							
12 poles	40p	40p							

### THYRISTOR LIGHT DIMMER

For any lamp up to 1kW. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price \$2.50, plus 20p post and insurance.



### THIS MONTH'S SNIP

**REPEATING TIME SWITCH.** 1 or 2 on/off per 24 hours. Repeats until reprogrammed. Switches up to 15 amp. Switching time completely adjustable through 24 hours. Precision made with 24-hour dial. Miniature—will fit into 2in. cube. Mains operated clock but switch may be isolated for switching battery sets. Ideal for: shop window lighting, anti-theft devices, central heating control and many other automatic processes. Price with instructions \$2 each plus 20p post and insurance.



### MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 500mW into ohm speakers. Input suitable for crystal mic. or pick-up. 9V battery operated. Size 2in long x 1 1/2in wide x 1in high. SPECIAL SNIP PRICE 65p each. 10 for \$5.90.

### HORSTMANN'S "TIME & SET" SWITCH

(A 50 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around \$5. Special snip price \$1.50. Post and ins. 25p.



### HONEYWELL THERMOSTAT

Made by Honeywell for normal air temperatures 40-80°F (5-25°C). This is a precision instrument with a differential which can be adjusted to better than 1.5°F. A mercury switch breaks on temp. rise—the switch is operated by a coiled bimetal element and an adjustable heater is incorporated for heat anticipation. Elegantly styled and encased in an ivory plastic case with clear plastic windows, thermometer above and switch setting scale below—size approx. 3-8in x 3-2in x 1-4in deep—can be mounted on conduit box or directly on wall. Price \$1.25 each or ten for \$11.25.



### ZPM MODULATION MOTOR

Could also be used to open ventilators, doors, valve, damper, etc. particularly suitable for remote control. Made by Satchwell. Essentially a reversible geared motor fitted with internal limit switches to stop it at the end of its travel. Size approx. 6in x 6in x 3 1/2in, and weighing approx. 3 1/2 lb. This is extremely powerful and would lift a heavy door or open a long line of ventilators. To operate this motor you put the 50 cycle supply through a changeover switch. For instance a thermostat with changeover contacts could automatically regulate the temperature in a growing house, chicken hatchery, etc. An indicator on the motor graduated 0-10 shows the state of open or close. Also internally fitted is a variable resistor, wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if built direct from Satchwell, our price complete with step down Transformer is \$15.




### INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over \$5. Full circuit details of the IC's are included and in addition you will receive a list of many different IC's available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only \$1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.
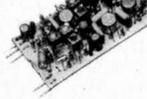
### MULLARD I.F. MODULE


This is a fully screened intermediate frequency module for amplification and detection of i.f. signals at 10.7MHz and a.m. signals at 470KHz. The first stage is used as an i.f. amplifier for i.f. and a self-oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 85p each; 10 for \$7.95. With connection dig.



Where postage is not stated then orders over \$5 are post free. Below \$5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

### EDUCATIONAL KITS

#### all with pictorial instructions

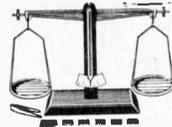

### THIS BALANCE KIT FREE

Eagle educational kits. Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits more we give FREE an accurate 1 1/2 lb. balance kit. Price of kits 40p each post paid. Special price for all 7 kits \$2.50 with free balance kit.

**KA2 Lens Kit.** Eleven parts, including candle, one concave lens, one convex lens, stage and slit frame, etc. Watch light rays bend as they pass through different lenses.

**KA3 Water Pump Kit.** Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Three types of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle.

**KA4 Buzzer Kit.** Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.

**KA5 2-Pole.** Including enamel wire, armature and pole piece, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.

**KA7 Electro-Magnet Kit.** Fifteen parts, includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.

**KA8 Current and Resistance Kit.** Twenty-nine parts, including bench and light bulb. Concise interesting and educational projects to learn the application of "OHMS LAW" and see the difference in current and resistance with different types and lengths of wire.

**KA9 Bell Kit.** Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.

**KA10 Morse Key Buzzer and Bell Kit.** 25 part kit easy to construct, simple to operate.

**4 Watt Amplifier Module.** Made by Mullard Ref. No. EP9000. Part of the Unix system. This has an output of 4 watt speech and music into a 12-15 ohm speaker. A powerful amplifier with a thousand uses—completely enclosed. Size approx. 3 1/2in x 2 1/2in x 1 1/2in. Screw down input and output terminals. Price \$1.45 each; 10 for \$13.05.

**Pre-Amplifier Module.** 2 channel for Stereo. Input sensitivity 320mV. Part of the Mullard Unix system and completely enclosed. Size 4in x 4in x 4in. Screw down input and output terminals. Price \$1.80 each; 10 for \$16.20.

**Stereo Power Module.** Mullard Ref. No. EP9002. Rated at 12V 5VA. This has 2 separate outputs to eliminate cross talk. Again part of the Mullard Unix system but suitable for many other purposes. Completely encased with screw down input and output terminals. Size 3 1/2in x 2 1/2in x 2 1/2in. approx. Price \$2.30 plus 20p post; 10 for \$20.70.

**Heavy Duty Mains Power Pack.** Output voltage adjustable from 15-40V in steps—maximum load 220W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price \$5.75 plus 65p post.

**Coloured Fluorescent Tubes.** Unless otherwise stated all tubes are standard diameter and have normal bi-pin ends. 18in. 15 watt, pink, green, gold/yellow, blue, red. 2ft 20 watt, red, radar red. 2ft 40 watt, peach and red. 3ft 30 watt, peach. 4ft 40 watt, rose.

5ft 80 watt, radar red, radar blue. 5ft 80 watt, B.C. ends, pink, blue, green, peach. Up to 3ft 40p each; 4ft 50p each; 5ft 60p each. All less 10% on 10 or more.

**Flex Connecting Wire.** Various colours P.V.C. insulated. Very thin—7/0076 pink only, 100yd coils 50p each. Thin—14/0076 black, white, red, violet, 100yd coils 60p each. Medium Thick—23/0076 black, red, violet and pink, 100yd coils 70p each; 300 yards \$3. Heavy—40/0076 red/brown, 100yd coils \$1.50 each.

Extra Heavy—70/0076 yellow, black and yellow/red, 500yd coils \$1.0 each; 100 yd coils, blue, black, \$2.50 each.

Very Heavy—110/0076 100yd coils, blue, \$3 each. Screened Cable. Single P.V.C. insulated 14/96 conductor, covered by woven copper screen. P.V.C. insulated 100yd coils \$2 each. Ditto: but without outer P.V.C. sleeving \$3 each.

**Coiled Leads.** Extend to about 2yd—as fitted to telephones, etc., the flex conductors of these use a tinsel wire which makes them virtually unbreakable with normal usage. 3 core 15p; 4 core 20p; 6 core 25p per lead. All less 10% in lots of 10 or more.

## J. BULL (ELECTRICAL) LTD.

(Dept. P.E.) 7 Park Street, Croydon CRO 1YD  
Callers to 102 1/3 Tamworth Road, Croydon.

# gspk

(sales)  
quite simply — the best

## RESISTORS

### FULL RANGE OF CARBON FILM RESISTORS

1/2W (range 4.7 ohms to 470K) 1p each  
 1/4W and 1/8W (range 4.7 ohms to 10 Megs) 1p each  
 1W, (range 4.7 ohms to 10 Meg) 2p each  
 2W (range 4.7 ohms to 10 Meg) 3p each

These Miniature High Stability carbon Film Resistors have negligible noise factor.

All Resistors  $\pm 5$  per cent (except values over 4.7 Megs). These Resistors are even lower in price than most 10 per cent and older carbon composition types.

## PRE-SET POTENTIOMETERS

Standard values of pre-sets from 100 ohms to 5 Meg—  
 Standard/miniature ..... 7p each Sub-miniature ..... 5p each

## SIEMENS PROFESSIONAL CAPACITORS

### POLYCARBONATE AND POLYESTER

Voltage	Capacitance	Price
100V	0.1 $\mu$ F	6p
100V	0.15 $\mu$ F	6p
100V	0.22 $\mu$ F	6p
100V	0.33 $\mu$ F	9p
100V	0.47 $\mu$ F	10p
100V	0.68 $\mu$ F	15p
250V	0.01 $\mu$ F	5p
250V	0.015 $\mu$ F	5p
250V	0.022 $\mu$ F	5p
250V	0.033 $\mu$ F	6p
250V	0.047 $\mu$ F	6p
250V	0.068 $\mu$ F	6p
250V	0.1 $\mu$ F	6p

### ELECTROLYTIC

Voltage	Capacitance	Price
10V	22 $\mu$ F	7p
10V	470 $\mu$ F	11p
16V	47 $\mu$ F	7p
25V	10 $\mu$ F	9p
25V	100 $\mu$ F	11p
25V	220 $\mu$ F	14p
25V	470 $\mu$ F	14p
25V	1,000 $\mu$ F	22p
25V	2,200 $\mu$ F	42p
35V	4.7 $\mu$ F	7p
35V	220 $\mu$ F	14p
100V	10 $\mu$ F	8p
100V	22 $\mu$ F	9p
100V	47 $\mu$ F	14p

## SPECIAL INTRODUCTORY OFFER

# FREE

with all orders value £5 or over we will give absolutely free one GSPK P.C. Kit for making your own printed circuits (normal retail price £1.95).

Hurry! Offer valid for limited period only.



## SEMICONDUCTORS

Here are just a few examples of our LOW Semiconductor prices... Many more semicons available all at equally sensational prices... NOW

1+	25+	1+	25+	1+	25+
AC127	24p	BZY88C Series	10p	OC76	22p
AC128	19p	E12 (2.7V-30.0V)	9p	OC170	24p
AC176	15p		10p	IN4001	6p
AD161	18p	NKT210	24p	IN4002	6p
AD162	27p	NKT211	24p	IN4003	7p
AF139	28p	NKT212	24p	IN4004	8p
BC107	9p	NKT213	24p	IN4005	10p
BC108	8p	NKT214	19p	IN4006	12p
BC109	9p	NKT218	24p	IN4007	18p
BC147	8p	NKT219	24p	IN4148	4p
BC148	8p	NKT223	26p	2N1302	16p
BC149	8p	NKT224	21p	2N1304	21p
BCY70	14p	NKT242	14p	2N1613	14p
BCY71	20p	NKT243	51p	2N1711	15p
BCY72	14p	NKT401	70p	2N2904	29p
BFX29	24p	NKT402	75p	2N2905	24p
BFY30	19p	NKT403	64p	2N2906	18p
BFY51	18p	NKT453	41p	2N2907	22p
BFY52	19p	OA47	6p	2N3053	17p
		OA79	6p	2N3054	47p
		OA90	5p	2N3055	57p
		OC70	12p	(BD130)	

## NUMEROUS OTHER ITEMS AVAILABLE INCLUDE:

Switches. Comprehensive range of N.S.F. Toggle switches and Rotary Wafer switch kits (to enable you to make your own switch to your own specification).  
 Copper laminate and all materials available to make your own printed circuit boards.  
 Lamps and lampholders for every requirement. Ready Built Circuits and Modules.  
 Freezer and Cleaner aerosol sprays.  
 Jack plugs and sockets.  
 Variety of speciality products.  
 Recording Tape.

All orders value £2 or over post free. Other orders please add 10p P. & P. We only sell new products—do not confuse with "seconds" or surplus stock. Because of our keen prices we regret the prices apply to U.K. and B.F.P.O. addresses only.

To GSPK (Sales) Limited

Dept. P.E., Head Office, Hookstone Park, Harrogate, Yorkshire HG2 7BU

ALL  
CALLERS  
WELCOME

Please fill in the coupon and send with 10p (refundable on ordering) for catalogue

Name .....

Address .....

MON. TO FRI.

9-5.00

P.E.

## FM TUNER THOUSANDS NOW IN USE

### NELSON-JONES Reduced prices

Approved parts for this outstanding design (W.W. April 1971). Featuring 0.75  $\mu$ V sensitivity, Mosfet front end, Ceramic I.F. strip. Triple gang tuning, 1/2V r.m.s. output level, suitable for phase locked decoder, as below. Designer's own P.C.B. NEW Solid State Tuning Indicator and Dial-Chassis Kit. Tuner parts with box. Less than £12, S.A.E. please for lists.

## PHASE LOCKED STEREO DECODER PORTUS AND HAYWOOD

Approved kit for this superb decoder (W.W. September 1970). Featuring 40dB separation up to 10kHz. NO COILS. Negligible spurious tones (birdies). Simple setting up. Suitable for wide variety of tuners including the NELSON-JONES TUNER as above. Now with free LED 'stereo on' light. Complete kit reduced from £8.97 to £7.68 p.p. 16p.

NEW IC Stabilised PSU. SC, overload protected, low ripple. £3.55 p.p. 19p.

## LIGHT EMITTING DIODES (Red)

Improved Type panel or PCB mounting with free mounting clip—clear or black. Order LED1A. Monsanto miniature PCB mounting with radial leads. Order LED2. Please add postage. NOW ONLY 35p each with connection data.

RESISTORS. 1/2W 5% Low Noise Carbon Film, 10 ohms-4.7M E12. 1-9 1p, 10-99 0.9p each. Please add postage.

## INTEGREX LIMITED

P.O. BOX 45, DERBY DE1 1TW. Tel. 0283 89 3580.

## B.H. COMPONENT FACTORS LTD.

DEPT. P.E., P.O. BOX 18, LUTON, BEDS. LU1 1SU

### POLYESTER CAPACITORS MULLARD C280 250V

$\mu$ F. 0-0.1, 0-0.15, 0-0.22, 0-0.33, 0-0.47, 3p each. 0-0.68, 0-1, 0-1.5, 4p each. 0-2.2 5p 0-3.3, 7p, 0-4.7, 8p, 0-6.8, 10p, 1-0, 13p, 1-5, 20p, 2-2, 23p.

### POLYESTER CAPACITORS MULLARD C296 160V

$\mu$ F. 0-0.1, 0-0.15, 0-0.22, 2p each. 0-2.2, 0-3.3, 0-4.7, 4p each. 0-6.8, 1-0, 6p each.

### MINIATURE ELECTROLYTIC MULLARD C426

$\mu$ F/V. 4/40, 8/40, 10/16, 16/40, 25/25, 100/6.4, 32/10, 4p each. 200/6.4, 320/6.4, 64/10, 200/10, 40/16, 80/16, 125/16, 5p each. 80/25, 180/25, 0-64/64, 10/64, 20/64, 32/64, 5p each.

Electrolytic Capacitors		OC36		43p		pF		V	
mF	V	mF	V	4L914	30p	40	750	2p	
2	15	2	15	7400/01/10/	30p	40	750	2p	
2.5	50	1000	3	30	15p	100	750	2p	
4	10	1000	16	MC1027	£2	120	750	2p	
6.4	50	1000	25	Disc Ceramics		1000	50	21p	
10	40	1000	35p	pF	V	1	500	2p	0-01 30p
16	15	2000	12	5	750	2p	0-01	350p	2p
25	15	2500	25	10	750	2p	0-022	30p	2p
32	25	2000	25	25	750	2p	0-047	30p	2p
40	6	Panel Neon Red							
50	10	Int. Res. 240V							
50	50	15p							
64	10								
64	15	IN4001	6p						
64	25	IN4002	7p						
64	40	IN4003	7p						
100	6	IN4004	9p						
100	50	IN914	11p						
250	6	2N706	6p						
250	10	2N708	13p						
250	15	2N1303	17p						
250	25	2N3866	80p						
400	10	2N3055	57p						
500	10	BC108	11p						
500	12	BCY30	11p						
500	25	BFY51	20p						
500	50	BSX21	10p						
640	10	OC35	40p						

### BARGAIN PACKS

14/0076 PCV wire 5 x 10 yds 30p  
 7/0076 PVC wire 5 x 10 yds 30p  
 70V Neon wire ends 5 for 20p  
 Miniature Pushbutton 2 for 20p  
 Transformer 32-0-32 at 150mA 50p  
 Transistor Electrolytics 25 for 50p

### MINIATURE R.F. CHOKES

0-22 $\mu$ H, 2.2 $\mu$ H, 12 $\mu$ H,  
 15 $\mu$ H, 22 $\mu$ H, 8p each

1/2W, 5% Resistors 1p each  
 10 $\Omega$ -1M $\Omega$  60p per 100

TRANSISTOR EQUIVALENTS BOOK 40p  
 OTHER BOOKS IN STOCK

TERMS: Cash with order. P. & P. please add 10p for orders below £5. Overseas extra. Discount: £10-10%. All goods carry our money back guarantee if not satisfied. We have many components not listed, enquiries welcome. List 5p stamp. Trade enquiries welcome.

## VARIABLE VOLTAGE TRANSFORMERS

**INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V**

All Types from ½ to 50 amp from stock.

### SHROUDED TYPE

1 amp, £7.00	20 amp, £49.00
2.5 amp, £8.05	25 amp, £58.00
5 amp, £11.75	37.5 amp, £82.00
10 amp, £22.50	50 amp, £98.00
15 amp, £25.00	



2.5 amp OPEN TYPE

(Panel Mounting) ½ amp, £4.75. 1 amp, £7.00. 2½ amp, £8.05. All carriage paid.

## L.T. TRANSFORMERS

All primaries 220-240V

Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36V at 5A	£4.68	45p
2	30, 40, 50V at 5A	£6.88	45p
3	10, 17, 18V at 10A	£4.95	45p
4	6, 12V at 20A	£6.43	45p
5	17, 18, 20V at 20A	£7.28	55p
6	6, 12, 20V at 20A	£6.88	55p
7	24V at 30A	£5.23	45p
8	4, 6, 24, 32V at 12A	£7.15	45p
9	6 and 12V at 10A	£3.75	45p

## 220/240 VOLT A.C. CENTRIFUGAL FAN/BLOWER



Smooth, balanced running unit. Two pole shaded pole Mylar motor gives approximately 90 cubic ft./min. but draws only 240mA on run. Weight 2½lb. Case dia. 3-in., width (case only) 3-1/2-in., width overall (inc. motor) 5-25-in., aperture 3-1/2-in. x 1-85-in. Price only £2.95. P. & P. 25p.

## 12 VOLT D.C. MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size: 4 1/2 in. x 2 1/2 in. dia. Either type price 95p inc. post.



## PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £1.75. P. & P. 25p.



**600 WATT DIMMER SWITCH.** Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 incl. P. & P.




## CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

Seven pole armature, ballrace bearing, 2,750 r.p.m. Length 2 1/2 in. Shaft length 1/2 in., shaft dia. 5/64 in. No load 40 mA. Normal load 350 mA. Ideal for portable recorders, etc., etc. Price £1.25 P. & P. 10p.


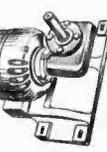
## PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. £6.30. P. & P. 50p.



## INSULATION TESTERS

NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34.00 carriage paid. 500V, 500 megohms, £28 incl. P. & P.



## UNISELECTOR SWITCHES

NEW 4 Bank 25 Way 24V d.c. operation. £5.88. P. & P. 25p. 6 Bank 25 Way 24V d.c. £6.50. P. & P. 25p. 8 Bank 25 Way 24V d.c. operation. £7.62 plus 25p. P. & P.



## 230V A.C. SOLENOID

Extremely powerful with approx. 14lb pull, 1in travel. Fitted with mounting feet. Size: 4in long, 2 1/2in wide, 3in high. £2.00 incl. P. & P.



## 230-250 VOLT A.C. SOLENOID

Manufactured by Westwood Ltd. (similar in appearance to above illustration). Approx. 1 1/2lb pull. Feet size 1 1/2in x 1 1/2in. Price 85p incl. P. & P.

## 18-24 VOLT D.C. SOLENOID

Size: O.A.L. 3 1/2in x 1 1/2in x 1in. Max. push 1/2 at 1lb approx. PRICE: 75p incl. P. & P.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard, 5 C.R., Uni-junction Xenon Tube and instructions £6.30, plus 25p P. & P.

**NEW INDUSTRIAL KIT**  
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

**HY-LIGHT STROBE MK II**  
Designed and produced for use in large rooms, halls and the photographic field and utilises a silica tube, printed circuit, also a special trigger coil. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12.00. P. & P. 50p. SPECIALLY DESIGNED.

## THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe. Incorporating:

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Reactor control circuit producing an intense white light.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P. ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Light Kit including reflector £7.00 P. & P. 45p.

For Hy-Light Kit including reflector. £4.00. 7-inch **POLISHED REFLECTOR** Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

## 6 INCH COLOUR WHEEL

As used for disco lighting effects, etc. £5.75 incl. P. & P. can be operated from our one r.p.m. synchronous motor price 75p incl. P. & P. Motor available with wheel.

## 'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. Types N39, N95, N100, N101 NEW in maker's carton. PRICE: 10 for £1.90 incl. P. & P.



## 36V 30 AMP. A.C. or D.C. VARIABLE L.T. SUPPLY UNIT

INPUT 220/240V a.c. OUTPUT CONTINUOUSLY VARIABLE 0-36V. Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £68 plus £2 P. & P.



## VENNER ELECTRIC TIME SWITCH

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.



## PROGRAMME TIMERS

240V A.C. 5 r.p.m. motor. 2 models available with either 10 cams or 15 cams. Each cam operating a 10 amp c/o micro switch. Cams are individually variable allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW 10 cam £4.75 P. & P. 25p. 15 cam £5.75 P. & P. 25p.



## SIMPLE 9 CAM PROGRAMMER

9 by 5 amp 1 make 1 break micro switches. Driven by heavy duty 'Crouzet' 115 V/230 V A.C., 15 r.p.m. motor. Solid fibre cams may be profiled and adjusted to individual requirements. Price £3.50. P. & P. 25p.

## MOTOROLA MAC 11/6 PLASTIC TRIAC 400 PIV. 10 AMP.

Now available EX STOCK. Supplied with full data and applications sheet. Price £1.05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

## Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 3.5kΩ, 5 kΩ, 140mA. Diameter 3 1/2in Shaft length 3in, dia. 1/2in. All at £1.65 each. P. & P. 71p.  
50 WATT. 1/5/10/25/50/100/250/500/1/1/1 5/2 5/5kΩ. All at £1.15 each. P. & P. 71p.  
25 WATT. 10/25/50/100/250/300/500/1/1 5/2 5/3/5/5kΩ. All at 90p each. P. & P. 71p.  
Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats, 18p. inc.

## RELAYS SIEMENS, PLESSEY, Etc.

MINIATURE RELAYS				
Col. (1)	1	2	3	4
Coil ohms	52	3-6	2 c/o	63p*
Col. (2)	410	10-18	4 c/o	73p*
Working d.c. volts	600	12-24	4 c/o	78p*
	700	16-24	4M 2B	63p*
	700	16-24	4 c/o	78p*
Col. 3 Contracts	700	16-24	6 c/o	65p*
Col. (4)	700	16-24	1 c/o HD	50p*
Price	700	20-30	6 c/o	78p*
	1,250	24-36	4 c/o	63p*
HD =	2,500	36-45	6M	63p*
Heavy duty	2,400	30-48	4 c/o	50p*
*Incl. Base	9,000	40-70	2 c/o	50p*
Post paid.	15k	85-110	6M	50p*

## 12 VOLT D.C. RELAY 140 ohm coil

Three sets c/o contacts rated at 5 amps. 78p including P. & P. (Similar to illustration below.)

## 'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 50p. P. & P. 10p. (100 lots £40 including P. & P.)



**230 VOLT A.C. RELAYS MFG. KEY SWITCH**  
One set c/o contacts rated at 7.5 amps. Boxed. PRICE: 40p. P. & P. 5p. (100 lots £32 inc. P. & P.)

**MINIATURE CLARE-ELLIOTT RELAY**  
Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 1/2" high, 3/4" wide, 1/2" thick. Complete with 3' leads. New 73p, incl. P. & P.

### ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3. P. & P. 22p.

### 50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

### G.E.C. 12 WAY 15 AMP CONNECTORS

NEW in makers carton. BAKELITE £1.25 per doz. FLEXIBLE £1.50 per doz. Post paid (Minimum 1 doz).

### LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take 1MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.75. P. & P. 18p.

### LIGHT SENSITIVE SWITCHES

Kit includes ORP.12 Photocell, Relay Transistor Circuit. For 6 or 12V D.C. operation. Price £1.50 plus 12p P. & P. ORP. 12 and Circuit 63p post paid. **220/240V A.C. MAINS MODEL** Mains transformer, rectifier, relay, 1 make 1 break H.D. contacts. price incl. circuit £2.65. P. & P. 20p.

### Very special offer MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 inc. post. (Min. order 20.)

### D.C. AMMETERS NEW!

1A, 5A, 15A, 20A, £1.75, incl. P. & P. 0-300V a.c., £1.90, incl. P. & P.

All Mail Orders—Callers—Ample Parking  
Dept. PE10, 57 BRIDGMAN ROAD  
CHISWICK, LONDON W4 5BB  
Phone 01-995 1560  
Showroom open Mon.-Fri.

# SERVICE TRADING CO.

Personal callers only. Open Sat.  
**9 LITTLE NEWPORT STREET**  
LONDON WC2H 7JJ  
Phone 01-437 0576



## £2500 career Yours in 6 weeks?

Yes. That's all the time it takes ACT to turn a person with the aptitude into a qualified Computer Programmer. Able to hold down a responsible, well-paid job in the world of computers. And our own exclusive appointments agency will introduce you to all the right connections. FREE. We've already trained vast numbers of people; pointed them in the direction of success and life-long security. Write or phone TODAY for FREE details without obligation.

### ACADEMY OF COMPUTER TRAINING.

E81, Oxford House  
9-15, Oxford Street, W.1.  
Telephone: 01-734 2874

127, The Piazza, Dept. E81,  
Piccadilly Plaza, Manchester 1.  
Telephone: 061-236 2935

## EDUCATIONAL

**ENGINEERS**—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Building, etc. FREE book from: BIET (Dept. H.4), Aldermaston Court, Reading, RG7 4PF. Accredited by C.A.C.C.

**GET INTO** Electronics—opportunities for trained men. Learn at home. Postal courses in RTEB, City & Guilds, Radio, TV, Telecoms., etc. FREE informative guide: CHAMBERS COLLEGE (Dept. R.103), Aldermaston Court, Reading, RG7 4PF.

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

**HIGHEST POSSIBLE CASH** prices for Akai, B. & O., Brenell, Ferragraph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

## TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types

**KENSINGTON SUPPLIES**

(B) 367 Kensington Street  
Bradford 8, Yorks.

## LADDERS

**LADDERS.** 20ft, £7-80. Callers Welcome. Carr. 80p. Leaflet. (Dept. PEE), HOME SALES, Baldwin Road, Stourport, Worcs. Phone 02-993 2574/5222. Ansafone installed 5222. Open Sunday 8-12 noon.

## RECEIVERS AND COMPONENTS

**BRAND NEW COMPONENTS BY RETURN.** Electrolytics 15V or 25V, 1, 2-2, 4-7, 10 mfd., 3½p, 22, 47, 4p, 100, 5p, 50V, ½p extra, Subminiature bead-type tantalums, 0-1/35V, 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 10/16V, 8p. Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02, 2p, 0-04, 0-05, 2½p, 0-068, 0-1, 3p. Polystyrene 63V, 10p, 10-000pF, E12 series, 2p. Mullard miniature Carbon Film Resistors, E12 series, three watt 1Ω—10 MΩ, 8 for 5p. Insured postage, 8p. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8.

## NEW

### 15 watt Hi Fi AMPLIFIERS

Frequency response 15 to 19000cs. Signal to noise > 70db. Input sens. 750mV into 2k.

**IHI ELECTRONICS**  
105, GRANGE ROAD, LONDON S.E. 25.

## NEW FULL SPEC.

### DEVICES BY RETURN

### MONEY BACK GUARANTEE

**MICROCIRCUITS:** 700 30p; 710 30p; 723 71p; 741 32p; 748 37p; SN76013 £1.24; 74 SERIES TTL: 00 16p; 02 18p; 04 18p; 10 16p; 11 21p; 20 16p; 30 19p; 40 16p; 47 £1.35; 51 18p; 72 30p; 73 41p; 74 38p; 75 44p; 81 £1.28; 86 41p; 90 72p; 91 £1.21. **TRANSISTORS:** 2N2924 red 8p; orange 7p; yellow 8p; green 9p; 2N3004 35p; 2N3053 48p; 2N3055 48p; BC107 6p; BC108 6p; BC109 6p; BFY305/3132 10p. **RESISTORS:** 0411 18p; 0412 19p; 0413 14p; 1002 10p; 4101 10p; 4102 11p; 4103 30p; 6002 14p; 6104 14p; 6102 15p; 8003 15p; MP8111 32p; MP8112 42p; OC44 12p; OC45 12p; OC71 12p; OC72 12p; OCA1 19p; MEF 104 42p; 2N3819 28p; MEF 11 35p; MEL 12 44p; D40C1 56p. **1 AMP RECTIFIERS:** 50V 31p; 100V 4p; 200V 5p; 400V 6p; 600V 9p; 800V 12p; 1000V 14p; W005 28p; W01 24p; W02 25p; W04 27p. **400mW 5% ZENERS:** 4-7; 5-1; 6-2; 6-8; 8-2; 9-1; 10; and 12 VOLT 1½p each. **1 WATT 5% ZENERS:** 15V & 30V; 17p each. **DIODES:** 1N914 3p; 1N916 4p; 1N4148 4p; OA5 17p; OA47 7p; OA90 6p; OA91 5p; OA200 7p; OA202 8p; SCR: 600V 1-6A, BTX30-600 75p; LED PANEL LAMP 46p. **FERRITE BEADS** 1p. **SOLDERCON PC PIN SOCKETS** 0-7p per pin and length. **PC RESIST PENS** 5p. **34 PIN DIL SOCKETS** 14p. **MICROHM Resistors** 4½p.

## JEF ELECTRONICS (P.E. 10)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ. Mail Order Only. C.W.O. P. & P. 9p per order. O/seas 65p. Discounts start at 10% for 10+

## DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts, 62½p per doz.; £3-75 per 100; £27-50 per 1,000; £250 per 10,000. All carriage paid.

G.W.H. RADIO LTD.

40/42 Portland Road, Worthing, Sussex BN9 0QS 34897

**COMPUTER PANELS,** 5-BC108s, diodes, etc., 4 for 50p, post 10p. **AMERICAN PANELS,** 4 for 55p, post 12p. Panel type 3838, 12 silicon trans. 15p; 219B, 21 silicon trans., 30p, post 6p each. For lists of other types and components send large S.A.E. **UNIT WITH 4 LA2 POT CORES + CAPS,** 50p, post 15p. LA2 ex equipt., 20p, C.P. New and boxed 30p, C.P. ORP18 on panel ex equipt., 35p, C.P. **WIDE ENDED HEATERS,** fitted resistor for mains use, 10 for 45p, 20 for 75p, post 8p. **M.C. METERS,** 2-3in, three assorted £1.05, post 25p. **MIXED POLYSTYRENE/SILVER MICA CAPS,** 100 for 40p, C.P. I.C.s 7400 series on panel(s), 10 assorted 75p, post 10p. Transistor and I.C. fall outs 100 (approx.) 15p, C.P. **VELODYNE UNIT,** 7 min. valves, w.w. res. caps, etc., 35p, post 15p. **NEW COIL PACK,** 8 piano key, no dope, 50p, post 20p. **COPPER CLAD PAXOLIN,** single sided, 12x12in, 30p, post 10p each; 8½x5½in, 10p, post 4p each; 5½x5½in, 6 for 30p, post 10p. **ASSORTED COMPONENTS,** 7lb, £1-30, C.P. **ASSORTED COMPUTER PANELS,** 2lb, £1-30, C.P.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs.

Mail Order only

## 100 WATT AMPLIFIER

Fully protected, transformerless, 9 transistor circuit. Input 500 mV. Output into 8 ohms. 0-1% distortion. Printed circuit board and full instructions. £1-45p + 10p P. & P. S.a.e. for list of component bargains.

**EDMUNDS COMPONENTS, 134 NORTH END ROAD, LONDON, W14.** (Mail order only)

2N404, VCB25, IC-200, HFE 40, 7p. P.C. pins, 40 for 10p. XB113-OC71, 4p. 470Ω, 1W 5%, polythene packed, 10 for 5p. Anti surge fuses, 14", 200-600 MA—2-2.5A, 5 for 20p. All items new coded perfect. Plus 5p postage per order. S.A.E. lists. N. F.R.E.A.R., 1 Newton Street, Ulverston, Lancs.

## PRECISION

### POLYCARBONATE CAPACITORS

Fresh Stock — Fully tested

Close tolerance. High stability. All 63V d.c.  
0.47µF: ±5% 30p; ±2% 40p; ±1% 50p  
1.0µF: ±5% 40p; ±2% 50p; ±1% 60p  
2.2µF: ±5% 50p; ±2% 60p; ±1% 75p  
4.7µF: ±5% 70p; ±2% 80p; ±1% 115p  
6.8µF: ±5% 80p; ±2% 115p; ±1% 150p  
10µF: ±5% 110p; ±2% 140p; ±1% 180p  
15µF: ±5% 160p; ±2% 220p; ±1% 270p

**TANTALUM BEAD CAPACITORS.** Values available 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V. All at 5p each; 6 for 50p; 14 for £1. Special pack 6 off each value (72 capacitors) £5.

**NEW 1-TRANSISTORS.** BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to quantity for quantity prices.

**POMERAN DIODES.** IN914, 9p each; 8 for 50p; 18 for £1. IN916, 9p each; 6 for 50p; 14 for £1. 1N914, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

**SPECIAL OFFER—400 mW ZENERS.** Values available 6-8, 7-5, 8-2, 9-1, 10, 11, 12, 13-5, 15V. Tol. ±5% at 5mA. All new and marked. Price 12p each; 5 for 50p; 12 for £1.

**RESISTORS.** Carbon film ±W 5%. Range from 2-20 to 2-2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 of each value 2-20 to 2-2MΩ (70 resistors) £5.

**440V A.C. CAPACITORS.** 0.1µF, size 1½in x ½in, 25p; 0.2µF, size 1½in x ½in, 30p; 0.47µF, size 1½in x ½in, 35p; 1.0µF, size 2in x ½in, 45p; 4.0µF, size 2in x ½in, 75p.

**POLYCARBONATE CAPACITORS** listed above is recommended by the Author for use in place of 2 x 0.47µF 1000V d.c. discharge capacitors C6 and C7. Improved reliability. Alternatively, 2 x 0.47µF 440V a.c. may be supplied at 35p each.

5p post and packing on all orders below £5.  
**V. ATTWOOD, DEPT. B5, P.O. BOX 8, ALRESFORD, HANTS**

## Trampus electronics

All Brand New. Money Back Guaranteed. Fast Service.

5V DIGITAL INDICATOR

0-9DP, with socket and red Filter. £1.55. 7447 £1.49.

IG GAS DETECTOR. Smoke, Butane, Vapour, etc. £2-19.

data 9p. **ULTRASONIC TRANSDUCER.** Transmit or receive.

22. **LIGHT EMIT DIODES.** Visible red panel clip/diode. 39p.

INVISIBLE BEAD. £1.19.

IC CALCULATOR CHIP-TMS1019. 4 function, 8 digit, 3 register storage, ROM and RAM memory. 28 pin DIL. £23. data 65p. LED DISPLAYS to suit. 1 DIGIT £4-49 each. 5 DIGITS with magnifier. DIL case, £17-49. KEYBOARD. 12 way reel switch, £14-97.

**INTEGRATED CIRCUITS:** with data.

741 op. amp. TO3 or DIL. 81p; 709 TO3, 28p; 709 DIL, 29p; 710, 36p; 723, 59p; 748, 39p.

**PHOTO DETECTOR & AMPLIFIER,** lens case, 44p.

**AUDIO AMP.** 3-5W Hi-Fi, etc., £1-24. Stereo: Dual Pre-amp, £1-49. FM MPX Decoder, £1-49. 748: Data Booklet, 5p; gates 7400, etc., 15p; 7470/72, 28p; 7473, 39p; 7490, 63p; 7492, 78p. DIL SOCKETS low profile 14 or 18 pin, 18p.

**TRANSISTORS:**

2N3055, 30p; BC107, 6p; BC108, 7p; BC109, 8p; AC127/175, £1.27/1.75; AC177/8, £1.77/1.80; AD161/2, 35p; BC167/8/9, 17p; BC177/8/9, 15p; BC182/8/4, 11p; BC212/8/4, 11p; BCY70, 16p; BFY305/132/17p; T1843 UJT, 20p; 2N706A, 18p; FET 2N3819, 28p; 2N2926 U.C., 20p; 2N3053, 17p; 2N3702/3/4/5, 11p; 2N3708/9/10/11, 9p.

**DIODES:**

1N914/6, 5p; OA47/91, 5p; OA200/202, 10p. 1A RECTS. 50V, 4p; 400V, 5p; 50V Bridge, 29p.

**ZENERS:** 500mW, 12p; 5-1V/10W, 29p.

1MVA SCR 4A/400V, 55p. TRIAC 8A/400V, 87p.

**CAPACITORS:** 25/30V Electrolytic.

10/50/100µF, 5p; 200/500µF, 8p; 1,000µF, 15p.

DISC: 22pF thro' to 0.047µF, 3p; 100 to 1000pF, 6p.

RESISTORS ±W 5%, 1p. PRESETS 0-25W, 5p.

VERO 16p/28p, etc., 1p. PLUGS 15p; sockets, 5p.

Stereo Amp. in case, £14. 12p. Dimmer, 24.

**ELECTRONIC CAR IGNITION KIT,** £6-67.

FREE: CATALOGUE, S.A.E., DATA SHEETS, 6p each. C.W.O. P. & P. 7p. Overseas 85p. Discount 10+10%.

**P.O. BOX 29, BRACKNELL, BERKS.**

**AARYAK ELECTRONICS.** Spotlight. Converters 3 channel 1-2kW £17, 3kW £25. Strobes, 1 Joule £16, 4 Joule £25. Mail or call, 74 Bedford Avenue, Barnet, Herts. Tel. 01-449 1268.

## TV Line out-put Transformers

Replacement types ex-stock.  
For "By-return" service, contact London  
01-948 3702

Tidman Mail Order Ltd., Dept. PE,  
236 Sandycroft Road,  
Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors, Rectifiers  
and Frame out-put Transformers also stocked.  
Callers welcome.

**METERS**, Motors, Relays, Valves, Electronics.  
At **ROGERS FASCINATING ESTABLISHMENT**, 31 Nelson Street, Southport.

**SHARPEN YOUR RESPONSES** with Vernitron  
ceramic i.f. resonators. Set of four **TF-04 442**,  
455kHz, with associated capacitors for band-  
width 2, 4, 5-7, 7-5, 10 or 12kHz (state which),  
**£1-85**, U.K. post 5p. Mail order only. **AMATRONIX LTD.**, 396 Selsdon Road, South  
Croydon, Surrey, CR2 0DE.

**RADIO SPARES (R.S.) COMPONENTS** specified  
for projects in this, and other magazines  
supplied on request. S.A.E. with all enquiries.  
The Hobbies Shop, 32 The Parade, Cwmbran  
Town Centre, Cwmbran, Mon.

### SOUND SUPPLIES

(Electronics) Co. Ltd.

**P.A. EQUIPMENT**. Marshall amps, instruments  
and guitars, etc. TOA and Eagle amps and  
accessories, Reslo mics, etc.  
**COMPONENTS**. Resistors, capacitors, plugs,  
sockets, cables, audio leads, semiconductors,  
valves, vero board, etc., for the constructor.  
Power packs and car droppers for the cassette  
recorder or radio.

S.A.E. for list and enquiries. P.A. list 15p.  
12 Smarts Lane, Loughton, Essex  
Tel. 01-508 2715 Closed all day Thursday

### MISCELLANEOUS

## 12 VOLT FLUORESCENT LIGHTS

(as illustrated)



Beat power cuts. Be independent. Ideal  
for caravans, tents, emergency lighting, etc.  
Works anywhere where 12v is available.  
Guaranteed for six months. Ready to use at:

12ins. 8 watt £3-60 post paid

21ins. 13 watt £4-60 post paid

**SALOP ELECTRONICS**, 23 WYLE COP  
SHREWSBURY, SHROPSHIRE. Callers  
welcome. For lists or enquiries, large.s.a.e.

### PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT,  
ANODISED, SELF-ADHESIVE ALUMINIUM.  
NO SPECIAL EQUIPMENT NEEDED.  
EASY TO FOLLOW INSTRUCTIONS.  
CHOICE OF SILVER OR BLACK, RED,  
BLUE, GREEN.

TRIAL KIT £1-28 Carr. Paid  
No. 1 KIT £1-88 Carr. Paid  
No. 2 KIT £2-39 Carr. Paid

**M.P.E. Ltd.**, BRIDGE ST., CLAY CROSS, DERBYS.

**CONSTRUCTION AIDS**. Fascia panels, dials,  
nameplates in etched aluminium to individual  
specification. Sheet aluminium, printed cir-  
cuits—drafting tapes, negatives supplied,  
boards manufactured, singles or small runs.  
(Copper clad laminate supplied. Hardware  
for constructors. S.A.E. details. **RAMAR  
CONSTRUCTOR SERVICES**, 29 Shelbourne  
Road, Stratford-on-Avon, Warwks.

## NIP-E-BOARD

FOR DISCRETE COMPONENTS  
AND INTEGRATED CIRCUITS



This unique and versatile range of ready made  
strips and glass fibre drilled and undrilled boards  
are now recognised as the best and easiest  
circuit building base currently available.

**NIP ELECTRONICS** P.O. BOX 11, BEACONSFIELD ROAD, ST ALBANS, HERTS

## PRINTED CIRCUIT SYSTEMS

### PLUG-IN PRINTED CIRCUIT CARDS

UNDRIILLED SRP from 16p; Glass fibre from 19p  
DRILLED SRP from 30p; Glass fibre from 35p

### EDGE CONNECTORS

GOLD PLATED Single sided  
14way 35p, 50way 60p

### MOUNTING PILLARS

For box or chassis mounting  
most wiring boards, from 3p.

### HANDLES

For card frames, 5p, with write on labels.  
REDUCTIONS FOR QUANTITIES OF 10 or more NIP-E-BOARDS

**METER REPAIRS**. Ammeters, voltmeters,  
multi-range meters, etc. Send to **METER  
REPAIRS**, 39 Chesholm Road, London,  
N16 0DS.

**CHROMASONIC ELECTRONICS** is well and  
living at 56 Fortis Green Road, London,  
N10 3HN. 40-page illustrated catalogue 20p  
post free.

**CIRCUIT BOARD ETCHING KITS**, full  
instructions, £1-25, c.w.o. **ARVIN SERVICE  
COMPANY**, 12 Cambridge Road, St. Albans,  
Herts.

### COMPONENT CATALOGUE

### AND DISCOUNT VOUCHERS

25p Post FREE (U.K.)

**W.E.C. LTD.**

HIGH STREET, RIPLEY, SURREY

**REGORD T.V. SOUND** using our loudspeaker  
isolating transformer. Provides safe con-  
nection to recorder. Instructions included,  
£1 post free. **CROWBOROUGH ELEC-  
TRONICS (P.E.)**, Bridge Road, Crowborough,  
Sussex.

### ELECTRONIC DIGITAL CLOCK KIT

- ★ Four numeric time display.
  - ★ Mains operated and synchronised.
  - ★ 74 Series TTL integrated circuits.
  - ★ Independent hour and minute resets.
  - ★ High quality epoxy glass P.C.B.
  - ★ Easy to follow constructional details.
- COMPLETE KIT PRICE £19-75 + 20p P. & P.  
Distributors: Collins, NW, 13 Chestnut St.  
Sheepridge, Huddersfield, Yorks.

Versatile

## 10 in ONE



### MINI-LAB

Comprising:

- AC and DC Voltmeter • Audio  
Generator • Ohm Meter • Resistance  
Substitution • Capacitance Substitu-  
tion • DC Ammeter • Battery Supply  
• RF Signal Generator • RF Field  
Strength Indicator.

This new, unique instru-  
ment combines all you need for testing. Guar-  
anteed, money back if not satisfied.  
Cash with order or write for illustrated data  
sheet to:

**R.S.L. COMPONENTS (Dept. PE)**  
Cricketfield Lane, Bishop's Stortford, Herts

**CLEARING LABORATORY**, scopes, V.T.V.M's,  
V.O.M's, H.S. recorders, transcription  
turntables, electronic testmeters, calibration  
units, P.S.U.'s, pulse generators, D.C. null-  
potentiometers, bridges, spectrum analysers,  
voltage regulators, sig-gens, M/C relays,  
components, etc. Lower Beeding 236.

**P.E. GEMINI**. Etched aluminium fascia  
panels as detailed in latest publication.  
Printed circuit boards and other items.  
S.A.E. details. **RAMAR CONSTRUCTOR  
SERVICES**, 29 Shelbourne Road, Stratford-  
on-Avon, Warwicks



**BEST EVER—INTERNATIONAL  
230 VOLT A.C. "MAINS" PER-  
FORMANCE** from 12 volt car battery.  
**R.C.A. INTERNATIONAL 230 volt  
A.C. POWER UNIT**. Wonderful  
230 volt a.c. performance with low  
battery drain. Marvellous for A.C.  
**FLUORESCENT LIGHTING** and  
hundreds of makes and types of 200/240  
volt a.c. and **UNIVERSAL A.C./D.C.  
APPLIANCES**. Can be used for re-  
charging battery by using an ordinary  
motorist's 4 amp battery charger.  
Total weight of unit 21 lbs. Price  
ONLY £4-90, plus £1 delivery. Money  
back if not delighted. C.O.D. with  
pleasure. S.A.E. full details.

Dept. PM **BROADWAY DISTRIBUTORS**, The  
Generator Centre, House of Time, 273  
Broadway, Rossall, Fylde, Lancs.

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver  
kit does not use R.F. and you can get one easily.  
Your transmissions will be virtually SECRET since  
they won't be heard by conventional means.  
Actually it's TWO KITS IN ONE because you get  
the printed-circuit boards and components for both  
the transmitter AND receiver. You're going to find  
this project REALLY FUN-TO-BUILD with the  
EASY-TO-FOLLOW instructions. An extremely  
flexible design with quite an AMAZING RANGE—  
has obvious applications for SCHOOL PROJECTS,  
LANGUAGE LABORATORIES, SCOUT CAMPS,  
etc.

GET YOURS! SEND £5-50 NOW (S.A.E. for details)

TO: 'BOFFIN PROJECTS'  
DEPT. KE2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

## FIBRE OPTICS

**FLEXIBLE LIGHT PIPE** used to convey light to  
inaccessible positions for inspection, panel  
indicators, photo-electric and other applications.  
**FIBROFLEX** Type I glass fibre flexible light  
conduit 1.14mm active dia. bundle sheathed in  
P.V.C. Prices per metre (U.K. post free): 1-4,  
70p; 5-9, 55p; 10+, 40p. 25 metres £6 per reel.  
**CROFON** (Trade mark of Du Pont) Type 1610  
plastic flexible light conduit now available.  
64 filaments. Active dia. 1.80mm.  
Prices per metre: 1-4, £1-20; 5-9, £1; 10+, 80p.  
25 metres £16 per reel.  
Send S.A.E. for full range of products, price list  
and literature.

### FIBRE OPTIC SUPPLIERS

P.O. BOX 702, LONDON W10 6SL

## RUN YOUR TAPE RECORDER OFF

### A.C. MAINS

Mains unit supplied complete  
and ready to plug into your  
cassette recorder. (State vol-  
tage, model and plug required.) P. & P. 15p  
Also available for single outputs 6V, 9V, 12V,  
18V, £2. P. & P. 15p.

**R.C.S. PRODUCTS (RADIO) LTD.**  
(Dept. P.E.), 31 Oliver Road, London, E.17



£2-50

## YOUNG SCIENTISTS

and not-so-young, whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW! (S.A.E. for details).

**TO: BOFFIN PROJECTS**  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL  
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

**SURPLUS ELECTRIC CABLE.** 3-core rubber covered 28/0076 (100yd coils), **£4** per roll. 50p postage. 3-core rubber covered 28/0076 (500yd coils), **£15-50** per roll. Free. 3-core PVC Black 14/0076 (100yd coils), **£3-50** per roll. 25p. Single core PVC clat. 14/0076 (100yd coils), **60p** per roll. 10p. 3-core PVC Black flat 28/0076 (100yd coils), **£3-50** per roll. 25p. Single core PVC Black 14/36 (100yd coils), **50p** per roll. 10p. Instrument (case Strap, 3/4in wide nylon Black (100yd coils), **50p** per roll. 10p. New 1/20 H.P. Fraemo Motor type P3371/2BD-W51 with capacitor, **£4-50**. BROXBORNE ENG. CO., Salisbury Road, Hoddesdon, Herts. Telephone, Hoddesdon 63866.

## IT'S OLYMPICS YEAR!

**36 STAMPS** AND WITH THESE 36 STRIKING OLYMPICS STAMPS YOU TOO CAN JOIN IN THE FUN!

Up-to-the-minute Munich and Sapporo issues, plus Grenoble and earlier historic Games stamps, to introduce you to the ever-popular Sport on Stamps collecting hobby, and accompanied by a selection of our bargain approvals.

All 36 stamps for ONLY 10p

**ONLY 10p** ASK FOR LOT PE 1 THE OLYMPICS SCOOP OF THE CENTURY!

**BROADWAY APPROVALS**  
50 DENMARK HILL, LONDON, S.E.5

NEW

## 15 watt Hi Fi AMPLIFIERS

Frequency response 15 to 19,000cs. Signal to noise > 70db. Input sens. 750mv into 2k.

**HI ELECTRONICS**  
105, GRANGE ROAD, LONDON S.E. 25

£3.75 each plus 25p p&pd

## IT COSTS NO MORE

To use guaranteed professional components. Don't risk failure in your building projects by using suspect junk-box items. We are able to supply, mostly by return of post, the entire range distributed by R. S. Components Ltd.



Printed Circuit type, CAPACITORS, electrolytic, low voltage, small size, in the following:  $\mu$ FV. 0.47/63, 1/63, 4.7/40, 10/63, 22/40, 100/10, at 7p each, 47/40 at 10p each, 100/63, 220/40, 470/16 at 13p each, 1000/16 at 16p each.

Phenolic Resin Boards, 172 x 133 x 1.57mm, punched 6.3mm grid, as used for Demo Deck, at 22p each. Turret Tags for above Boards, at 95p per pack of 144.



Miniature Moulded Bridge RECTIFIERS for printed circuit mounting, REC 60 800 volts 0.9 amp, 38p each. REC 65, 800 volts, 1.3 amps, 45p each.

All of the above and many, many other high grade components, are shown in our CATALOGUE. Price 25p by return of post.

All prices POST FREE in U.K.  
Mail Order Only From—

Dept. EE, P.O. Box No. 1, Llanwrtyd Major, Glamorgan CF6 9YN

CELECTRON-E

## DIMMIT

range of light dimmers  
standard wall mounting models

Rotary: 400W £3.10 1KW £3.95  
module only: 400W £2.80 1KW £3.60  
Slider: 400W £4.35 1KW £4.95  
module only: 400W £3.50 1KW £4.05

Send 10p for complete catalogue of Dimmits and components, 28 types available. Orders: add 10p P. & P. for each dimmer.

**YOUNG ELECTRONICS**

54 Lawford Rd., London NW5 2LN 01-267 0201

## FERRANTI

SEMICONDUCTORS ... COMPARE OUR PRICES

Transistors	ZTX320	28p	BFS61	19p	ZS176	21p	
ZTX107	10p	ZTX330	13p	BFS96	16p	ZS178	34p
ZTX108	9p	ZTX331	14p	BFS97	21p	ZS270	10p
ZTX109	10p	ZTX500	10p	BFS98	21p	ZS271	14p
ZTX114	20p	ZTX502	15p			ZS272	16p
ZTX300	10p	ZTX504	39p	DIODES		ZS274	17p
ZTX302	15p	ZTX510	15p	ZS140	22p	ZS276	23p
ZTX304	19p	ZTX530	19p	ZS141	39p	ZS278	33p
ZTX310	7p	ZTX531	20p	ZS142	30p		
ZTX311	9p	ZTX550	15p	ZS170	9p	ZENERS	
ZTX312	9p	BFS59	15p	ZS171	11p	K5030A series	
ZTX313	10p	BFS60	19p	ZS172	14p	ALL TYPES	17p
ZTX314	11p	BFS61	19p	ZS174	15p		

Postage and Packing 10p. Free above £2. S.A.E. for full list

## VALENCE ELECTRONICS

134 UNION STREET, ASHTON-U-LYNE, LANCs.

## COLOUR T.V.

19" Tube £125 — 25" Tube £160

COMPLETELY OVERHAULD — VARIETY OF MAKES AND MODELS

FABULOUS WINTER VIEWING:

### MONOCHROME

UHF — SINGLE STANDARD — PUSH BUTTON TUNER

20" Tube £34.95 — 24" Tube £44.95

Carr. + ins. £2-50. Famous make dis chassis—Thoroughly overhauled—Fitted with "Square Screen" tube—Transistorised "Push Button" tuner—Fitted in an attractive cabinet, refinished in a choice of oiled teak, walnut, or mahogany veneers (state 1st and 2nd choice)

12 month written guarantee with every set—Leaflet and copy guarantee sent on receipt of your stamped, self addressed envelope.

The above models can be seen working in our Langley showroom.

Working and overhauled BBC 2 TV'S (Ferguson 900 and similar sets) £20 Carr £2

**SUMIKS (P.E.), 7 HIGH STREET  
LANGLEY, WARLEY, WORCS.**



## Brunel Technical College, Bristol

Ashley Down, Bristol BS7 9BU

Department of Marine and Aero-Electronics

### Marine Radio and Electronic Officers

The Department offers the following Courses:

- For prospective Radio Officers in the Merchant Navy a Course of two years and one term leading to the MPT General Certificate in Radiocommunications and the DoTI Radar Maintenance Certificate. Commences September and January.
- For qualified Marine Radio or Electronic Officers the MNTB Additional Certificate in Marine Electronics, in two modules of three months each.
- Short advanced technique Courses for serving Radio Officers.
- MPT R/T-Licences—

### Licensed Aircraft Radio Engineers

The Department provides a 2-year Full-time Course leading to a career in Civil Aviation. The Course is fully approved by the ARB so that successful students may obtain a full Category R Licence at the end of the Course. The Department's aircraft, workshops and laboratories cover:

- 1:1 Airborne Communication Systems
- 1:2 Airborne Navigation Systems
- 1:3 Airborne Pulse and FM Systems

Courses are also provided for Aeronautical R/T Licences and Category X Compass Licences.

Courses commence each September.

For further information apply to Head of Department of Marine and Aero-Electronics, Brunel Technical College, Ashley Down, Bristol BS7 9BU. Tel. 41241

# YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

## RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction.  
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.  
2% ELECTROSIL TRS

Power watts	Tolerance	Range	Values available	Price
1	5%	4-7Ω-22MΩ	E24	1p
1	10%	3-31MΩ-10MΩ	E12	1p
1	2%	10Ω-1MΩ	E24	3p
1	10%	1Ω-3Ω	E12	1p
1	5%	4-7Ω-1MΩ	E12	1p
4	10%	1Ω-10Ω	E12	6p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4-7Ω to 1MΩ.  
E12 pack 325 resistors £2-40. E24 pack 650 resistors £4-70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/4W, lin 1/4W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0-1 matrix).  
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 6p each.

## TRANSISTORS

AC107 15p	BC108 10p	BFY51 22p	OC71 12p	OC21D 12p	OC22D 12p	OC24D 12p	OC25D 12p	OC26D 12p	OC99D 12p	OC100D 12p
-----------	-----------	-----------	----------	-----------	-----------	-----------	-----------	------------

## ZENER DIODES

400mW 5% 3.3V to 30V, 15p. LINEAR I.C.'s (D.I.L.) DIL Socket 14 and 16 pin. 16p

## DIODES

DIODES	RECTIFIER	1A	12p	SIGNAL	7p
BY127	1250V	1A	12p	OA85	7p
BZV10	800V	6A	25p	OA90	5p
BZY13	200V	6A	20p	OA91	5p
IN4001	50V	1A	7p	OA202	5p
IN4004	400V	1A	8p	IN4148	5p
IN4007	1000V	1A	12p	BA114	8p

## BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p.

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm  
SINGLE 10kΩ, 25kΩ, 50kΩ, 100kΩ, log or lin  
DUAL GANG 10kΩ + 10kΩ, etc, log or lin  
Knob for above  
FRONT PANEL  
20 gauge panel 12in x 4in with slots cut for use with slider pots.  
Grey or matt black finish, complete with fixings for 4 pots.

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7 1/2p. 0.33μF, 11p. 0.47μF, 13p.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF 3 1/2p. 0.15μF 4 1/2p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7 1/2p. 0.68μF, 11p. 1.0μF, 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3 1/2p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6 1/2p. 0.47μF, 8 1/2p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p. 2.2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2 1/2p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

(μF/V) 10/2.5, 40/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6.4/6.4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64, 20/64, 32/64.

## MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p. 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1000/6.4, 1600/2.5, 12p. 160/64, 250/40, 400/2.5, 640/16, 2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p. 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/6.4, 4000/2.5, 18p.

## ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25. 5p each.

## VEROBOARD

0-1	0-15	Standard screened	18p	2.5mm insulated	8p
2 1/2 x 3 1/2	22p	Standard insulated	12p	3.5mm insulated	8p
2 1/2 x 5	24p	Stereo screened	35p	3.5mm screened	13p
3 1/2 x 3 1/2	24p	Standard socket	15p	2.5mm socket	8p
3 1/2 x 5	27p	Stereo socket	18p	3.5mm socket	8p
4 1/2 x 2 1/2	75p				
17 x 3 1/2	100p				
17 x 5 (plain)	82p				
17 x 3 1/2 (plain)	60p				
17 x 2 1/2 (plain)	42p				
2 1/2 x 5 (plain)	11p				
2 1/2 x 3 1/2 (plain)	12p				
Pin insertion tool	52p				
Spot face cutter	42p				
Pkt. 50 pins	20p				

## JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 15p/metre.  
6 way screened cable 22p/metre.

## BATTERY ELIMINATOR £1.50

9V mains power supply. Same size as PP9 battery.

## THERMISTORS

VA10555 15p; VA10665 15p; VA1077 15p; R53 £1.35.

## COMPACT CASSETTES—IN PLASTIC LIBRARY BOX

C90 65p C120 85p.

## LARGE (CAN) ELECTROLYTICS

1600μF 8V	74p	2000μF 16V	50p
2500μF 40V	74p	1500μF 16V	30p
2500μF 30V	58p	4000μF 25V	£1.68
2500μF 64V	80p	5000μF 16V	£1.10
2800μF 100V	£3.00		

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p 0.047μF 13p 0.22μF 20p  
0.022μF 12p 0.1μF 13p 0.47μF 22p

## POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

## NEW LIGHT SENSITIVE SWITCHES

TWO NEW LITE-IC'S—  
COMPLETE LIGHT SWITCHES  
CONSISTING OF  
PHOTODETECTOR + AMPLIFIER  
+ TRIGGER + DRIVER—All in a  
single 4mm. dia. can.

NEW FEATURES: WIDER  
VOLTAGE SUPPLY RANGE—  
LITE-IC 2 11V to 20V  
LITE-IC 3 20V to 30V  
HIGHER OUTPUT CURRENT  
DRIVE—to 40mA.



APPLICATIONS INCLUDE: Relay, Tricac Drive, Automatic  
Light Switching and Door Control, Beam/Break Detection—Burglar  
Alarm, Batch Counting and Code Reading.

PRICE ONLY 95p each with full operating instructions. 10 off for  
80p each. Postage free in the U.K. P.O./CHEQUES made payable to  
ELBON and crossed (with order).

LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX

## BAKER 15in. AUDITORIUM

A high wattage loudspeaker of excep-  
tional quality with a level response to  
above 8,000 cps. Ideal for Public Address,  
Discotheques, Electronic instruments and  
the home.

Maximum Power 35 watts  
Bass Resonance 35 c.p.s.  
Flux Density 15,000 gauss  
Voice coil impedance 8 or 15 ohms models  
Useful response 20-14,000 c.p.s.

GUITAR MODEL "GROUP 50"  
15 in. Heavy Duty. 50 watt £19

20 PLANS, CUBIC TABLES,  
CROSSOVER DATA AND  
CATALOGUE 42p POST FREE  
CATALOGUE ONLY 5p

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665



£19

POST  
FREE

# FREE!

## Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. B38, Aldermaston Court, Reading RG7 4PF



To B.I.E.T., Dept. B38, Aldermaston Court, Reading RG7 4PF

B38

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

SUBJECT OF INTEREST \_\_\_\_\_

AGE \_\_\_\_\_

Accredited by the Council for the Accreditation of Correspondence Colleges.

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

- |   |   |
|---|---|
| <p><b>MECHANICAL</b><br/>A.M.S.E. (Mech.)<br/>Boiler Inspection &amp; Operation<br/>C &amp; G Eng. Crafts<br/>C &amp; G Fabrication<br/>Diesel Eng.<br/>Eng. Inspection<br/>Eng. Metallurgy<br/>Inst. Eng. &amp; Tech.<br/>Inst. Motor Ind.<br/>Maintenance Eng.<br/>Mechanical Eng.<br/>Sheet Metal Work<br/>Welding</p> <p><b>ELECTRICAL &amp; ELECTRONIC</b><br/>A.M.S.E. (Elec.)<br/>C &amp; G Elec. Eng.<br/>C &amp; G Elec. Inst.<br/>C &amp; G Elec. Tech.<br/>Computer Elect.<br/>Elec. Maths<br/>Elec. Science<br/>Electronic Eng.<br/>Electrical Eng.<br/>Install. &amp; Wiring<br/>Meters<br/>&amp; Measuring Instruments</p> <p><b>MANAGEMENT &amp; PRODUCTION</b><br/>Automatic Control<br/>Computer Prog.<br/>Electronic Data Processing<br/>Estimating<br/>Foremanship<br/>Inst. Cost &amp; Works<br/>Accountants<br/>Inst. Marketing<br/>Management<br/>Metrication<br/>Motor Trade Man.<br/>Network Planning<br/>Numerical Control<br/>Operational<br/>Research<br/>Personnel Man.<br/>Planning Eng.<br/>Production Eng.<br/>Quality Control</p> <p><b>Man. Prod.—cont.</b><br/>Salesmanship<br/>Storekeeping<br/>Work Study<br/>Works<br/>Management</p> <p><b>DRAUGHTSMANSHIP</b><br/>A.M.I.E.D.<br/>Design of Elec. Machines<br/>Die &amp; Press Tool Design<br/>Electrical Draughtsmanship<br/>Gen. Draughtsmanship<br/>Jig &amp; Tool Design<br/>Technical Drawing</p> <p><b>RADIO &amp; TELECOMMUNICATIONS</b><br/>Colour TV<br/>C &amp; G Radio/TV/Electronics<br/>C &amp; G Telecomm. Tech.<br/>Prac. Radio &amp; Elec. (with kit)<br/>Radio Amateurs Exam.<br/>Radio Servicing &amp; Repairs<br/>Radio &amp; TV Eng.<br/>Transistor Course<br/>TV Main. &amp; Serv.</p> <p><b>AUTO &amp; AERO</b><br/>Aero Eng.<br/>A.M.I.M.I.<br/>A.R.B. Cert.<br/>Auto Engineering<br/>Auto Repair<br/>C &amp; G Auto. Eng.<br/>Garage Management<br/>M.A./IMI Diploma<br/>Motor Vehicle Mechanics</p> <p><b>CONSTRUCTIONAL</b><br/>A.M.S.E. (Civil)<br/>Architecture<br/>Building</p> <p><i>Coaching for many major exams, including HNC, ONC, C &amp; G, etc.</i></p> | <p><b>Constructional-cont.</b><br/>Building Drawing<br/>Building Foreman<br/>Carpentry &amp; Join.<br/>Civil &amp; Municipal Engineering<br/>Constructional Engineering<br/>Construction Surveyors<br/>Inst. of Builders<br/>Clerk of Works<br/>Council Eng.<br/>Geology<br/>Health Eng.<br/>Heat &amp; Vent.<br/>Hydraulics<br/>Inst. of Builders<br/>Inst. Clerk of Works<br/>Inst. Works &amp; Highway Supers.<br/>Painting &amp; Dec.<br/>Public Hygiene<br/>Road Engineering<br/>Structural Eng.<br/>Surveying</p> <p><b>GENERAL</b><br/>Agricultural Eng.<br/>Council of Eng. Inst.<br/>Farm Science<br/>General Education<br/>Gen. Plastics<br/>Pract. Maths<br/>Pract. Slide Rule<br/>Pure &amp; Applied Maths<br/>Refrigeration<br/>Rubber Technology<br/>Sales Engineers<br/>Tech. Report Writing<br/>Timber Trade University Ent.</p> <p><b>G.C.E.</b><br/>58 'O' &amp; 'A' LEVELS SUBJECTS<br/>Over 10,000 group passes</p> |
|---|---|

## POST TODAY FOR A BETTER TOMORROW


Published approximately on the 15th of each month by ITC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel Press, Andover, Hants. Sole Agents for Australia and New Zealand: Gordon & Gotch (A.S.) Ltd., South Africa: Central News Agency Ltd., Rhodesia and Zambia: Kingstons Ltd., East Africa: Stationery and Office Supplies Ltd. Subscription Rate (including postage) for one year to any part of the world £2.65 (42/13.0). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade, at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# U.K.'s LARGEST ELECTRONICS CENTRES! HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.

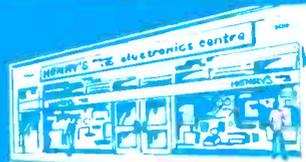**NOW OPEN!**

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381/8382  
354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736  
309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963  
303 BARGAIN STORE SPECIAL OFFERS 01-723 1008 All Mail to: 303, Edgware Rd., London, W.2.

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.




## BUILD THE TEXAN

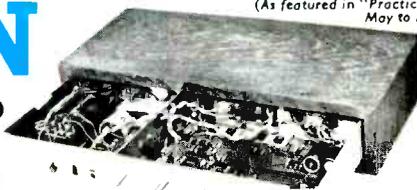**20 + 20 WATT INTEGRATED D.C. STEREO AMPLIFIER**

★ **FREE TEAK CASE** with complete kits!

**FEATURES:** New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 resistors, 2 resistors, Special Gardners low field, slim line transformer. Fibre glass PC panel. Complete chassis work.  
**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES**—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.  
**FACILITIES:** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic. Tape, Tape head, etc. (Parts list Ref. 20 on request)



(As featured in "Practical Wireless" May to August 1972)

**SPECIAL KIT PRICE**

**£28.50** P. & P. 45p

**SLIM DESIGN WITH SILVER TRIM**

Overall chassis size 14 1/2 in. x 6 in. x 2 in. high

**COMPLETE WITH FREE TEAK CABINET**

Designer approved kits only available from Henry's!

### RECORD DECKS

CHASSIS (Post 50p)  
SP25/3, £10.75 HT70, £15.00  
MP60, £10.40 MP610, £14.15  
AP76, £18.95 GL72, £22.25  
WITH PLINTH/COVER (Post 70p)  
MP60, £17.20 TD150AB, £41.75  
HT70, £21.60 PL12AC, £35.25  
HL(GL75), £35.25 BD2, £32.25  
MP610, £20.35  
CART/PLINTH/COVER (Post 70p)  
(HL) AP76/G800/PC £29.95  
(HL) SP25-3/G800H/PC £18.95  
HT70/G800/PC £27.00  
(HL) 2025TC/9TAHCD/PC £13.50  
MP60/SC5MD/PC £17.25  
(HL) GL75/G800E/PC £44.15  
(HL) GL72/G800/PC £354.0

### ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.  
PRICE PER PAIR £5.90. Post 10p.

### MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO  
"17" High Impedance £2.00  
"18" Med Impedance £2.00  
"36" Med-Low Imp. £3.50  
Erase Heads for above 75p  
"63" 2 track mono — High Impedance £1.75  
"43" Erase Head for above 75p

### POWER INTEGRATED CIRCUITS

Plessey SL403D—3 watt with 8-page data layouts and circuits £1.50, P.C. Board 60p; Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1.80.  
TH9013P—20 watt Power Amp Module £4.57.  
TH9014P—IC Pre-amplifier £1.50, Data/Circuits (No. 42) for above 10p.

### 7 SEG. & NIXIE TUBES

(Post 15p per 1 to 6)  
XN3, XN13, GN6 0-9 side view with data, 85p.  
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.  
3015F 7 seg. £2 each, £7 per 4 with data, 12 and 24 hour clock circuits for above. Ref. No. 31 15p.

### MINIATURE AMPLIFIER

5 transistor, 300mW o/p. Fitted volume and sensitivity control 9 volt operated. £1.75 each, p.p. 15p.

### QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 500kΩ, 1 meg. Log and Lin. 45p each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, Log and Lin ganged, 75p each.

### HI-FI AND TAPE EQUIPMENT

Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 Months Guarantee. Write or call for FREE 16 page lists (Ref. 16/17).

### LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2 in x 8 1/2 in and Ceramic Magnet

**TYPE 150** 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.

**TYPE 150T** Twin cone version £2.75. Post 22p.

**TYPE 450** 10 watt with twin tweeters and crossover, 8 or 15 ohms. £3.85. Post 25p.  
**TYPE 350** 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.



**POLISHED CABINETS** 150, 150T, 450 £4.60. Post 30p.

### ML3 MW/LW TUNER TO BUILD



Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7 in x 2 1/2 in x 3 1/2 in. TOTAL COST TO BUILD £4.85. Post 15p. All parts sold separately—Leaflet No. 6.

### "BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7.98, p.p. 32p (Bact. 22p). All parts sold separately—Leaflet No. 2.


### CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

**PRICE 55p** Post paid (40p FOR CALLERS)

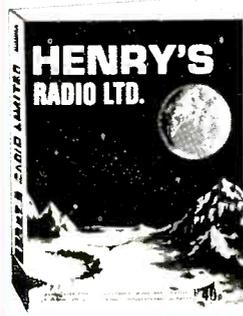**PLUS! FIVE 10p VOUCHERS**

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see below.



### TEST EQUIPMENT

SE250B Pocket Pencil Signal Injector, £1.90  
SE500 Pocket Pencil Signal Tracer, £1.50  
TE15 Grid Dip Meter 440 KHz—280 MHz, £13.45  
500 30 K/Volt Multimeter, £9.25;  
with leather case, £10.50  
200M 20K/Volt Multimeter, £4.20;  
with case £4.95  
AF105 50K/V Multimeter, £8.50; with case, £9.50  
U431 AC/DC Multimeter with transistor tester with steel case, £10.50  
TE20D RF Generator 120KHz—500MHz, £15.95. Carr. 35p  
TE22D Audio Generator 20Hz—200KHz, £17.50. Carr. 35p  
TO3 3in Scope 1 1/2Hz—1 1/2MHz, £39.00. Carr. 50p  
CI-5 3in Pulse Scope 10Hz—10MHz, £39.00. Carr. 50p  
TE65 Valve Voltmeter 28 ranges, £17.50. Carr. 40p



### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

Free Leaflet No. 3 & 7. TOTAL £6.97, p.p. 20p.  
Decoder Kit £8.97. Tuning meter unit £1.75.  
Mains unit (optional) Model PS900 £2.47. Post 20p.  
Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p.



### PA-DISCO-LIGHTING

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

DJ30L 3 Channel sound to light unit, 3kW, £28.50  
DJ40L 3 Channel Mic (Built-in) to light, 3kW, £37.50  
DJ70S 70 watt Disco amp/mixer, £49.75  
DISCOAMP 100 watt Disco amp/mixer, £67.50  
DJ105S 30 watt Disco amp/mixer, £31.00  
Anti-Feedback Quality Mic, £11.50  
SDL 12in 50 watt 8 ohm Full range Speaker, £12.95  
DECKS. Use MP60 or SP25/3 see above. Matching cartridge SC5M, £2.62



FIBRE OPTICS LIGHTING EFFECTS PROJECTORS SPOTS DIMMERS MIXERS. Everything for PA — Disco — Lighting. FREE Stock List Ref. No. 18.

### SINCLAIR PROJECT 60 MODULES —SAVE POUNDS

Z30 £3.57 Z50 £4.37  
STEREO 60 £7.97, PZ5 £3.97  
PZ6 £6.37 PZ8 £4.77.  
Transformer for PZ8 £2.95.  
Active Filter Unit £4.45.  
Stereo FM Tuner £16.95.  
IC12 £1.80 Q16's £15 pair.  
Post, etc. 20p per item.



PACKAGE DEALS Post 25p  
2 x Z30, Stereo 60, PZ5 £15.95  
2 x Z30, Stereo 60, PZ6 £18.00  
2 x Z50, Stereo 60, PZ8 £20.25  
Transformer for PZ8 £2.95  
NEW PROJECT 605 KIT £19.95

TRANSISTORS—ICs—SCRs—RECTIFIERS—TRIACS, etc.  
NEW FREE LISTS Ref. No. 36 on request.

### MORE OF EVERYTHING ALWAYS AT HENRY'S

All the parts you need plus Data and Circuits. Get a Catalogue—it's all in there! Prices subject to change without notice. F. & O.F.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

**H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H**