

PRACTICAL

# ELECTRONICS

OCTOBER 1973

20p



## SEMICONDUCTOR TESTER

**FREE INSIDE!**

**P.E. AUDIO I.C.  
IDENTICHART**

ALSO: PE **RODDO** QUADRAPHONIC SYSTEM  
Important New Series; PHASE LOCKED LOOPS

# NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT  
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN —PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loud-speaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio.
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- Complete with parts price list and plans.



TOTAL BUILDING COSTS

**£7-23** P.P. & INS. 44p  
(Overseas P.P. £1.05p)

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten.

Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9 1/2 in X 5 in X 2 1/2 in approx. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£6-95** P.P. & INS. 44p (OVERSEAS P. & P. £1-05)



## NEW EVERYDAY SERIES

Build this exciting New series of designs

**EV5** 5 Transistors and 2 diodes MW/LW. Powered by 4V Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9 in X 5 1/2 in X 2 1/2 in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£2-73** P.P. & INS. 30p (OVERSEAS P. & P. 70p)

**EV6** Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, loudspeaker, etc., MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£3-60** P.P. & INS. 30p (OVERSEAS P. & P. 85p)

**EV7** Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. Parts price list and easy build plans 20p. Free with parts.


TOTAL BUILDING COSTS **£4-08** P.P. & INS. 31p (OVERSEAS P. & P. £1-05p)

## ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 in X 7 in X 4 in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

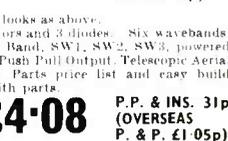TOTAL BUILDING COSTS **£6-98** P.P. & INS. 47p (OVERSEAS P. & P. £1-05)



## ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS, ALSO AIR-CRAFT BAND

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9 in X 7 in X 4 in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£8-50** P.P. & INS. 52p (OVERSEAS P. & P. £1-05)





## POCKET FIVE

3 Tunable wavebands. MW/LW and Trawler Band 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5 1/2 in X 1 1/2 in X 3/4 in approx. Plans and parts price list 15p (FREE with parts).

Total Building Costs

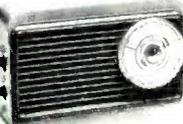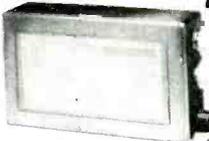**£2-28** P.P. & Ins. 24p (Overseas P.P. 65p)



## TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).


Total Building Costs **£2-50** P.P. & Ins. 25p (Overseas P. & P. 65p)

## TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 in X 5 1/2 in X 2 1/2 in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

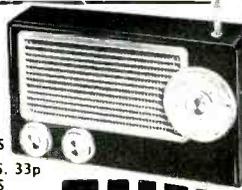**£4-48** P.P. & INS. 33p (OVERSEAS P. & P. £1-05)



## ROAMER SIX 6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC.

Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages, 6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 in X 5 1/2 in X 2 1/2 in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS

**£3-98** P.P. & IN. 31p (OVERSEAS P. & P. £1-05)

## EDU-KIT

Built Radios, Amplifiers, etc., from easy stage diagrams. Five



units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls; 2 Slider Switches; Fine tone moving coil Speaker; Terminal Strip; Ferrite Rod Aerial; 2 Plugs and Sockets; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2 in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£5-50** P.P. & INS. 33p (OVERSEAS P. & P. £1-05)

## RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0284 52387 Reg. No. 798372

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA

I enclose £ \_\_\_\_\_ for \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Please add 10% for VAT INC. P. & P.

# PRACTICAL ELECTRONICS

VOLUME 9 No. 10 OCTOBER 1973

---

## CONSTRUCTIONAL PROJECTS

- SEMICONDUCTOR TESTER—1** *by J. H. Perkin*  
A general purpose discrete semiconductor tester 852
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—2** *by R. A. Cole*  
Construction of pre-amplifiers, tone and balance controls and 20W amplifiers 866
- P.E. SOUND SYNTHESISER—9** *by G. D. Shaw*  
Voltage controlled output amplifiers and differential amplifier 882
- WIND AND RAIN EFFECTS** *by P. J. Tyrrell*  
A simple sound effects unit 888

## GENERAL FEATURES

- NEW DEVICES . . . APPLICATIONS**  
New integrated circuits for use in cars 856
- INGENUITY UNLIMITED**  
Series Regulator—Events Timer with Readout—Two Tone Audio Alarm Oscillator 857
- LOGIC TUTOR EXPERIMENTS—6** *by M. J. Hughes*  
The wired-OR function 862
- PHASED LOCKED LOOPS—1** *by J. B. Dance, M.Sc.*  
Phase locked loop principles and definitions 876

## NEWS AND COMMENT

- EDITORIAL—Amateur Radio Jubilee** 851
- SPACEWATCH** *by Frank W. Hyde*  
Red Planet Probes—Venus Probe—Skylab Results 861
- POINTS ARISING**  
Wide Range Pulse Generator—The 555 Timer—Audio Compressor—  
Lighting Control Unit—Phasing Unit—P.E. Sound Synthesiser—  
550 Volt Megohmmeter 879
- PATENTS REVIEW**  
Stereo Amplifier A.V.C.—Four Channel Volume and Balancing Control 894
- INDUSTRY NOTEBOOK**  
What's happening inside industry 897
- READOUT**  
More on the P.E. Sound Synthesiser—Back Numbers Wanted 898

## SPECIAL DATA SHEET

- AUDIO I.C. IDENTICHART**  
At-a-glance information on over 80 different devices

Our November issue will be published on Friday, October 12, 1973

---

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, to any part of the world, £2-85. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

# You'll hardly be able to believe your ears!

Can you  
really get  
sound quality  
like this for  
less than £18?

Yes you can!  
with the new

STEREO  
**21**



Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable £17.95, you can have Stereo 21—audio for the connoisseur.

Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!

And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience! Top-quality amplifier, BSR 8 record automatic changer turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit, no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins, all parts supplied including full instructions—all for £17.95 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money-back Guarantee if your pleasure in STEREO 21 is not complete!

Just think—In only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Personal shoppers and mail order price

**£17.95**

Plus £1.50 P&P.

Diamond styli, if required, £1.37 extra

Just write your order giving your credit card number. Do not send your card.



RADIO AND TV COMPONENTS (ACTON) LTD.  
21d High Street, Acton, London W3 6NG  
323 Edgware Road, London W2

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.



# RTVC VISCOUNT III

## a boost in the output.

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back. And the teak finish will harmonise and enhance virtually any style of interior decor!

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have *never* experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

**SPEAKERS:** Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 6in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair, £2.20 p. & p. Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit 13½in x 8½in with HF speaker. Max. power 20 watts 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

#### PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20 + £1 p. & p.
2 Duo Type II speakers	£14.00 + £2.20 p. & p.
Garrard SP25 Mk III with	
MAG. cartridge plinth & cover	£18.00 + £1.75 p. & p.
<b>total</b>	<b>£56.20</b>

Available complete for only £49.00 + £3.50 p. & p.

#### PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20 + £1 p. & p.
2 Duo Type III speakers	£32.00 + £3.30 p. & p.
Garrard SP25 Mk III with	
MAG. cartridge plinth & cover	£18.00 + £1.75 p. & p.
<b>total</b>	<b>£74.20</b>

Available complete for £65.00 + £4 p. & p.

STILL ONLY **£49** COMPLETE



### THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles it covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep.


\* Circuit diagram and comprehensive instructions 55p free with parts.

\* Fully retractable and lockable car aerial £1.37 post paid.
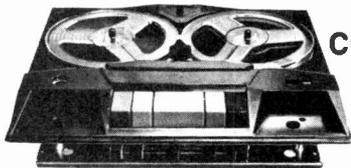
#### CAR RADIO KIT £6.60 p. & p. 55p


Speaker with baffle and fixing strips £1.65. 23p p. & p., post free if bought with the kit. Send stamped addressed envelope for leaflet.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.


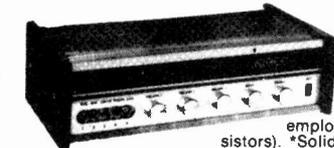
### PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, **less heads**. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty. **£4.00** £1 p. & p.



### RELIANT Mk IV £13.50


\*5 Electrically Mixed Inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12½ x 6 x 3½ ins. **£13.50 p. & p. 60p.**
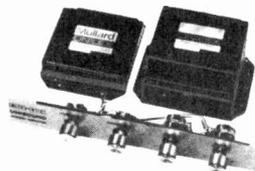
### UNISOUND MODULES

ONLY £7.64 + 55p p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



### IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.



The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit. **£9.90 p. & p. 80p** simply connect up.

**ALL PRICES INC. VAT**

SEE OPPOSITE PAGE FOR ADDRESS DETAILS

# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are already engaged in the industry, ICS can help you. We can further your technical knowledge and provide the specialized training so essential to success, or prepare you for a recognised examination. ICS have helped thousands of ambitious men to move up into higher paid jobs – we can do the same for you.

Take one of these courses . . .

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- C & G Radio Amateurs
- MPT General Certificate in Radio Telegraphy
- Audio, Radio and TV Engineering and Servicing
- Electronic Engineering Maintenance, Engineering systems
- Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances

### **NEW self-build radio courses**

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

### **POST THIS COUPON TODAY**

for full details of ICS courses in Radio, T.V. and Electronics

#### **To: INTERNATIONAL CORRESPONDENCE SCHOOLS**

Dept. No. 230U, Intertext House, Stewarts Road, London SW8 4UJ or telephone 01-622 9911.

Please send me the ICS prospectus – free and without obligation.

(State Subject or Exam.)

Block Capitals Please

NAME

ADDRESS


OCCUPATION

AGE

**ICS** your key to a brighter, better future

Accredited by the Council for the Accreditation of Correspondence Colleges.

## P.E. SOUND SYNTHESISER

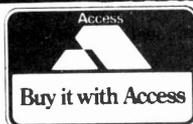

SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

### DESIGNER APPROVED KITS

ITEM 'X' TEMPORARILY OUT OF STOCK

The 'RING MODULATOR' I.C.

**SG 3402N**

£1-74 each

ELECTRONIC ATTENUATOR

**MFC 6040**

£1-00 each

**ZIJ NOISE DIODE**

43-5p each

mini D.I.L.

**741's 32p each**

while stocks last

4p stamp brings

latest lists

Attractive discounts on quantity purchases.

We stock a full range of professional quality components as specified for this exciting project.

ADD A TOUCH OF PRECISION TO V.C.O's, ETC., BY INSTALLING 10 TURN POTS AND COUNTING DIALS. 10 turn pots by BOURNS. 1/2" dia. 0-25% linearity. 0-02% resolution or better. £3 each.

10 turn indicating dial and knob by AMPHENOL. 22mm dia. Resolution better than 0-1%. With brake and zero backlash gearing. £2 each.

"AS FITTED" ITEMS ON OUR CUSTOM BUILT INSTRUMENTS.

Full range of resistors, capacitors, modular hardware and regulated power supplies. Individual component/module kits from date of publication.

## EATON AUDIO P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.

# Candis Ltd.

P.O. BOX 25, CANTERBURY, KENT

Red L.E.D. 30p; Green L.E.D. 75p (approx. 5mm diam.). Minitron 7-segment display, £1-50 OR complete with a 7447 decoder-driver £2-50

Integrated circuits in 8-14 pin D.I.L. packages

741 36p; 748 38p; 709 36p

HI-FI Stereo pre-amps. TBA231 £1-43; CA3052 £1-30

555 timer (microseconds to hours) 80p

#### Transistors

BC182L 9p

BC212L 11p

BFY51 19p

TIP29B 50p

TIP30B 60p

TIP41A 70p

TIP42A 85p

TIP35C £3

TIP36C £4

2N3055 45p

2N3053 22p

BC107/8/9 8p

1N4001 10 for 40p

1N4004 10 for 50p

#### Zeners 400 mw 5% full range 12p

Slide Switch DPDT 10p

P.C. Mounting Stereo

T05 Heat Sinks 10 for

Pots 100K Lin. 100K Log.

40p

10K Log. all at 35p

T03 Heat Sinks 25p

Miniature Toggle

Bridge Rectifiers

Switch

W005 50 P.I.V. 1A 23p

S.P.C.O. at 35p

W02 200 P.I.V. 1A 25p

Neon, panel mounting

W04 400 P.I.V. 1A 27p

amber, mains voltage

W08 800 P.I.V. 1A 34p

15p

#### Test Equipment

Digital Frequency Meters/Counters

Multimeters—Please state requirements

#### Special Offer

Spend £4 and receive FREE a red L.E.D.

Please add 10% VAT to total cost

**YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"!** ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! \*Send quickly, from receipt of goods test on mail order 7 day approval, refund if not delighted. Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pinpoint" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space-ship and satellite communications. **Yes, EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves, cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF, FM/USW, AM-LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for perfect reproduction and tone! **Press-button dial illumination!** Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39in approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 13in x 10in x 4in overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** ultra sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2.25 extra). **BOX, POST, ETC. 45p. NO MORE TO PAY!** BUT WAIT! For only 75p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard 'longlife' batteries and Converter Plug. (Sorry—We cannot change these new radios for any earlier model purchased.) Send quickly to Uxbridge Road address, or call at either Store. **But HURRY! SHOPERTUNITIES SAVE YOU £££'s.**

## THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! COMPUTERISED?

**THIS FANTASTIC  
EARTH SHRINKER**



**YES, 24,901 miles  
SHRUNK TO ONLY 13" x 10" x 4 1/2"  
inches approx?**

**BRAND NEW  
FABULOUS ASTRAD 17**  
PORTABLE RADIO & COMMUNICATIONS  
RECEIVER



**28 TRANSISTORS  
AND DIODES!**  
**WAVEBANDS:**  
STANDARD LONG and MEDIUM  
**Plus 5 SHORT WAVEBANDS**  
**Plus ULTRA SHORT WAVES**  
(V.H.F. AM, FM, MW,  
LW, USW.)

**BATTERY  
MODEL** **£18.50** **BOX  
POST  
ETC.  
45p**  
**MAINS/BATTERY  
ELIMINATOR** £2.25 extra

**FIRST TIME EVER!**  
\*NOW AVAILABLE WITH  
fabulous **COMPUTERISED**  
**WORLD TUNING GUIDE!**  
**NO MORE GUESSWORK!**  
INSTANT DATA at your fingertips—  
enables you to **TUNE IN A FLASH** to  
transmissions the world over!

**THIS  
OFFER  
ONLY  
FROM  
US!**

**BUY ONE FROM US!** **SAVE £23.03 NOW!**

Fabulous **BRAND NEW** **SOLID STATE** This equipment's got **EVERYTHING!**

**BATTERY/MAINS AC**  
**Combined**  
**V.H.F. AM/FM**  
**RADIO and**  
**CASSETTE**  
**TAPE RECORDER**  
**& PLAYER**



**WITH REMOTE CONTROL MICROPHONE**

**RECOMMENDED RETAIL PRICE £44**

**OUR PRICE £20.97** **CARR. ETC. 43p**

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord). Record and play back anything, anywhere! **RECOMMENDED RETAIL PRICE GENEROUSLY LOW OFFER AT ALMOST HALF PRICE!** Wonderful features: \* Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** \* "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! \* Separate ON/OFF and HI-LO volume controls! \* Heavy duty built-in speaker! \* Earphone (for personal listening or 'monitoring') and extension speaker sockets! \* Remote control microphone! \* Built-in swivel telescopic extension aerial (24in approx.). Magnificently made case with carry handle. (**DESIGNS VARY SLIGHTLY**.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND** the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £££'s more for a Car Radio or Car Cassette player **ALONE!** £20.97, carr. etc. 43p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required. Callers: **ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES**

**FIRST TIME EVER! SAVE £16.02!**

**BRAND NEW AC/DC BATTERY/MAINS**

**Cassette**  
**TAPE**  
**RECORDER**  
**& PLAYER**



**FIRST CLASS MAKERS**

With remote control microphone.

**WE COULD CHARGE UP TO £26.97!**

**OUR PRICE £10.95** **POST ETC. 50p**

**THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW** a superb de luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £10.95**. Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "PIANO KEYBOARD" CONTROL PANEL (for latest **MASTER SWITCH** control) and **AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Recommended selling price £26.97!) **OUR PRICE ONLY £10.95**, post, etc. 50p. **NO MORE TO PAY!** \*Send quickly, from receipt of goods test on mail order 7 day approval—refund if not delighted. Or call at either of our stores. **BONUS OFFER—**Cassette tape, Standard batteries AND microphone stand 55p extra if required.

Order by post to Uxbridge Road address or call at either store.  
Bargains galore at both stores.—(COMMERCIAL TRAVELLERS PLEASE  
**NOTE:** Merchandising office at Holborn Store)

**SHOPERTUNITIES LTD.**

Dept. PE/NC/31, 164 UXBURGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

# MAPLIN ELECTRONIC SUPPLIES

★RETURN OF POST SERVICE



1973 CATALOGUE

3rd EDITION NOW AVAILABLE

SEND NOW FOR YOUR COPY OF THIS BEAUTIFULLY PRODUCED FULLY ILLUSTRATED CATALOGUE AND WE WILL FORWARD IT TO YOU BY RETURN OF POST. PLEASE SEND 9p IN STAMPS.

EVERYTHING GUARANTEED BRAND NEW MARKED BY THE MANUFACTURER

MAPLIN: Projected site of London's third airport.

**RESISTORS**  
Carbon film 5% from 1Ω to 1MΩ, 10% from 1.2MΩ to 10MΩ. E12 series. 1W 1p. 1/2W 12p.  
Metal Oxide 2% 10Ω to 1MΩ. E24 series 1/4W 4p.  
Also 1W, 2 1/2W, 5W, 10W types stocked.

**POTENTIOMETERS**

Miniature carbon track with 2in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.  
Log or lin (and 1kΩ lin). 12p.  
Log or lin with switch 23p.  
Dual gang less switch 38p.

**7 SEGMENT DISPLAY**  
Minitron 3015F  
£1.98 each.

**P.E. SOUND SYNTHESISER**

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Verobords.

Send S.A.E. NOW for our detailed price lists.

YOU SIMPLY MUST SEE OUR PRICES!

8 pin DIL OP AMP  
741C 36p.  
14 pin 741C 45p.

**McMURDO**  
Socket, R58, 52p  
Plug, RPB, 36p.  
(As used in P.E. Sound Synthesiser.)

Diodes IN914 4p.  
OA91 6p. BAX 13 5p.  
IN4001 6p. IN4002 6 1/2p. IN4003 7p.  
IN4004 7 1/2p. IN4005 8p. IN4006 8 1/2p. IN4007 9p.

**SEMI-CONDUCTORS**

We stock a large range of transistors and I.C.s, for details please see our catalogue. LOOK! These popular devices at amazingly low prices. BC107/8 9 10p each. BC147/8 10p. BC149 12p. BC169C 12p. BF75 16p. T1543 28p. 2N706 10p. 2N2646 45p. 2N3055 49p. 2N3819 24p.

**DIN PLUGS**. 3 pin, 9p. 5 pin A (180°), 5 pin B (240°), 10p each.

**DIN SOCKETS**. 3 pin, 5 pin A, 5 pin B, 7p each.

**DIN LOUDSPEAKER**. 2 pin plug, 8p. Socket 6p.

**JACK PLUGS** standard 1/2in plastic barrel, 13p. Stereo, 25p. Bright metal barrel, 17p. Stereo, 29p.

**JACK SOCKETS** standard 1 1/2in open type, 10p. Moulded 2 break, 13p. Moulded stereo 3 break, 18p.

**ROTARY SWITCHES**

Adjustable stop. 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only 24p each.

**SPECIAL IC**, for organ builders, 7 stage frequency divider in one 14 pin DIL package, £2.63 or special price for pack of 12, £25.

Why not ask us to slip a data sheet in with your catalogue.

**NUDES!**

Clothe those naked projects with our superb instrument cases. We are sole distributors of the

**Centurion**

range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.

**HARDWARE**

Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc.  
**SOLDER** 10 metres of 22 gauge multicore, 20p.  
Insulating sleeving 3 sizes, 6 colours.

**MISCELLANEOUS**

LT700 Eagle sub-miniature O/P transformer 1200/5Ω 200mW max., 35p. Slide switch DPDT, 12p.  
Miniature push to make non-locking switch 12p.  
Silicon grease in special dispenser, 20ml, 38p.

SEE OUR CATALOGUE for details of how you can obtain £1 worth of components.


ABSOLUTELY FREE

V.A.T. Please add 10% V.A.T. to final total.

Orders and enquiries for catalogues to


**MAPLIN ELECTRONIC SUPPLIES**  
P.O. Box 3, Rayleigh, Essex SS6 8LR  
Telephone: Rayleigh (037 42) 79033

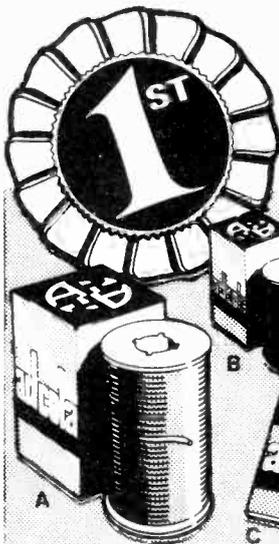Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.



# ADCOLA

the champions of soldering equipment

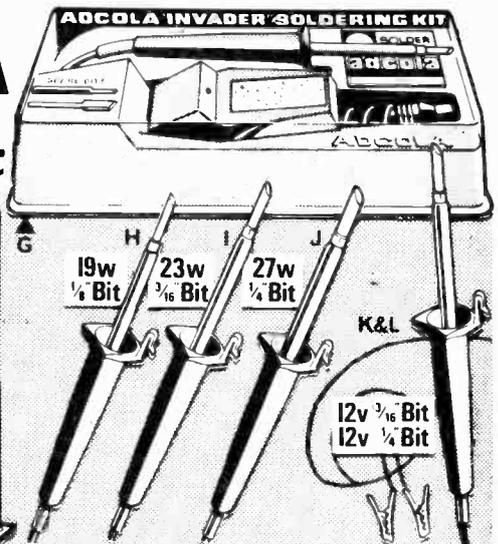

Please send me the following items

PRINT NAME .....

PRINT ADDRESS .....



PE4

- |                          |       |                          |
|--------------------------|-------|--------------------------|
| A SOLDER REEL 1/2 KILO   | £1.40 | <input type="checkbox"/> |
| B SOLDER REEL 3 OZ       | £0.48 | <input type="checkbox"/> |
| C SOLDER PACK            | £0.07 | <input type="checkbox"/> |
| D DE-SOLDERING BRAID     | £0.75 | <input type="checkbox"/> |
| E L686 SOLDERING STATION | £1.88 | <input type="checkbox"/> |
| F L68 PROTECTIVE SHIELD  | £1.08 | <input type="checkbox"/> |
| G INVADER SOLDERING KIT  | £4.39 | <input type="checkbox"/> |
| H L706 INVADER           | £2.23 | <input type="checkbox"/> |
| I L646 INVADER           | £2.42 | <input type="checkbox"/> |
| J L1076 INVADER          | £2.48 | <input type="checkbox"/> |
| K BL646 BATTERY MODEL    | £3.05 | <input type="checkbox"/> |
| L BL1076 BATTERY MODEL   | £3.17 | <input type="checkbox"/> |

ADCOLA PRODUCTS LTD ADCOLA HOUSE GAUDEN ROAD LONDON, SW4 6LH  
V A T REGD. No 235 6153 72 REGD No 442762

New Catalogue  
All prices include 10% V.A.T. Please tick items required.

# FREE

## HEATHKIT Electronic kit Catalogue

SAVE ON OVER 130 KITS  
YOU CAN BUILD

HOME APPLIANCES such as Pocket and Desk Top Electronic Calculator Kits, Electronic Digital Clock, Ultrasonic Burglar Alarm, Indoor/Outdoor Intercoms.

AUTOMOTIVE Testers, Engine Analysers, Tune-Up Meters, CD Ignition System, Timing Lights, Battery Charger.

PORTABLES Radios for Medium, Medium/LW, FM reception.

INSTRUMENTS for Test and Service, Transistor/Diode Checkers, Chart Recorders, Scientific.

SHORTWAVE AND AMATEUR RADIO includes:— Complete Stations, Receivers, Transceivers, Transmitters, a wide range of ancillary/auxiliary equipment.

STEREO Hi-Fi Systems, Compacts, Separates, Cassette, Loudspeakers, Transcriptors, Cartridges.

### METAL DETECTORS

All models offer Kit savings—outstanding performance. Enjoyable leisure activities. Payment is so easy—choose cash or low deposit terms (from £2 per month for £40 credit).

May we have your enquiries today!



### Visit your Heathkit Centres

LONDON showroom  
233 Tottenham Court Road  
Tel 636 7349


GLOUCESTER showroom & factory  
Bristol Road, Gloucester  
Tel 0452 29451

Practical Electronics October 1973

Please send me a FREE Heathkit catalogue	
Name	_____
Address	_____ _____ _____
<b>HEATH</b> <b>Schlumberger</b>	Heath (Gloucester) Limited, Dept: PE/10/73 Gloucester GL2 6EE. Telephone 0452 29451

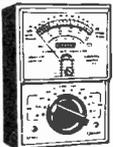
## AUDIOTRONIC MODEL ATM.1

Top value 1,000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1,000V. A.C. and D.C. D.C. Current 0-1mA/100mA. Resistance: 0/150 Kohms. Decibels: -10 to +22dB. Size: 90 x 60 x 22mm. Complete with test leads. £2-50. Post 15p.


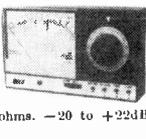
## LT 601 MULTI-METER

New style 20,000 O.P.V. pocket multimeter. 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 50µA/250A. 6K/16 meg ohms. -20 to +22dB. £3-75. Post 20p.



## MODEL TH-12

20,000 O.P.V. Overload protection. Slide switch selector. 0/0-25/2-5/10/50/250/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50µA/25/250mA d.c. 0/5K/30K/300K/3 meg. -20 to +50dB. £4-97. Post 15p.




## RUSSIAN 22 RANGE MULTIMETER

Model V437 10,000 O.P.V. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1,000V d.c. 2.5/10/50/250/500/1,000V a.c. D.C. current 100µA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3mΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £5-97. Post 20p.



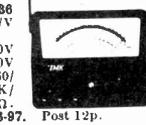
## MODEL FL486

20kΩ/V d.c. 8kΩ/V a.c. Mirror scale. 0-6/3/12/30/120/600V d.c. 3/30/120/600V a.c. 50/500µA/100/600mA. 10/100K/1 Meg/10 MegΩ. -20 to +46dB. £2-97. Post 12p.


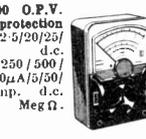
## MODEL 500 30,000 O.P.V. with overload protection

mirror scale 0/0-2/5/20/25/100/250/500/1,000V d.c. 0/2-5/10/25/100/250/500/1,000V a.c. 0/50µA/5/50/500mA. 12 amp. d.c. 0/60K/6 Meg/60 MegΩ. Leather case £1-75.




## U4812 MULTIMETER

Extremely sturdy instrument for general electrical use, 667 O.P.V. 0/0-3/1-5/7-5/30/60/150/300/600/900V d.c. and 75mV. 0/0-3/1-5/7-5/30/60/150/300/600/900V a.c. 0/300µA/1-5/6/15/60/150/300mA/1-5/6 amp. a.c. 0/200/3k/30kΩ. Accuracy Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-50. Post 25p.



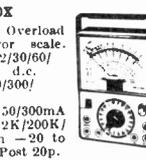
## HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 0-3/0-6/1-2/1-5/8/12/30/60/120/300/600/1,200V d.c. 1-5/3/6/12/30/60/150/300/600/1,200V a.c. 15/30µA/3/6/30/60/150/300mA/6/12 amp. d.c. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. £13-50. Post 20p.


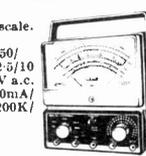
## MODEL C-7080 EN

Giant 6in mirror scale. 20,000 O.P.V. 0/0-25/1/2-5/10/50/250/1,000/5,000V d.c. 0/2-5/10/50/250/1,000/5,000V a.c. 0/50µA/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg. -20 to +60dB. £13-95. Post 30p.



## 870 WTR MULTIMETER

Features a.c. current ranges. 20,000 O.P.V. 0/0-5/2-5/10/50/250/500/1,000V d.c. 0/2-5/10/50/250/500/1,000V a.c. 0/50µA/1/10/100mA/1/10 amp. d.c. 0/100mA/1/10 amp. a.c. 0/5K/50K/500K/5MEG/50MEG. -20 to +62dB. £16. Post 25p.



## TMK LAB TESTER

100,000 O.P.V. 6in scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5Volt a.c. D.c. volts: 0-5, 2-5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100µA, 10, 100, 500mA, 2-5, 10A. Resistance: 1K, 10K, 100K, 10 meg. 200 meg. Decibels: -10 to +49dB. Plastic case with carrying handle. Size 7 1/2 x 6 1/2 x 3 1/2 in. £18-95. P. & P. 25p.



## Models-100TR MULTIMETER/TRANSISTOR TESTER.

100,000 O.P.V. mirror scale/overload protection. 0/0-2/0-6/3/12/30/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600µA/12/300mA/12 amp. d.c. 0/10 K/1 MEG/10 MEGΩ. -20 to +60dB. 0-01-2 MFD. Transistor tester measures Alpha beta and Ico. Complete with batteries, instructions and leads. £13-50. Post 25p.



## LBS TRANSISTOR TESTER

Tests Ico and B. Pnp/npn. Operates from 9V battery. Complete with all instructions, etc. £2-95. Post 20p.



## LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1-5V batteries. Complete with all instructions, etc. £4-50. Post 20p.



## MODEL 449A IN-CIRCUIT TRANSISTOR TESTER

Checks true a.c. beta in/out. Checks Ico. Checks diode in/out. Checks SCR, etc. Beta HI 10-5000 LO 2-50 Ibc0 0-6000µA. 220/240V a.c. operation. £17-50. Post 25p.




## KAMODEN HM-350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of PNP, PNP, transistors, diodes, SCRs, etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.


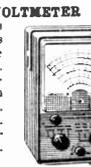
## TE-05 VALVE VOLTMETER

28 ranges. D.c. volts 1-5, 1-500V a.c. volts 1-5, 1-500V. Resistance up to 1,000 megohms. 200/240V a.c. operation. Complete with probe and instructions. £17-50. Post 30p. Additional probes available: R.F. £2-12; H.V. £2-50.



## KAMODEN 72.200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0-06/0-3/3/30/120/600/1,200V d.c. 0/3/12/60/300/1,200V a.c. 0/15µA/12mA/120mA/600mA/12A d.c. 0/12A a.c. -20 to +63dB. 0/2kΩ/200kΩ/2MΩ/200MΩ. £16-95. Post 30p.




## MODEL G4811 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 230 ohms/Volt a.c. and d.c. Accuracy 0-5% d.c. 1% a.c. Scale length 165mm. 0/300/750µA/1-5/3/7-5/150/75/150/300/750mA/1-9/3/7-5 amp. d.c. 0/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5 amp. a.c. 0/75/150/300/750mV/1-5/3/7-5/15-30/75/150/300/750V d.c. 0/750mV/1-5/3/7-5/15/30/75/150/300/750V a.c. Automatic cut out. Supplied complete with test leads, manual and test certificates. £49. Post 50p.


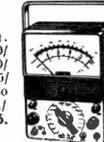
## KAMODEN HM720B F.E.T. V.O.M.

Input impedance 10MΩ. Ranges: 0/0-25/1/2-5/10/50/250/1,000V d.c. 0/25µA/2-5/25/250mA d.c. -20 to +22dB. 0/5k/50k/500k/5MΩ/500MΩ. £14-95. Post 30p.



## TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1-003/1-1/3/1/3/10/30/100/300V. R.M.S. 4cps.-1.2 Mc/s. Decibels -40 to +50dB. 80µA brand new complete with leads and instructions. Operation 230V. a.c. with instructions. £24-25. Carr. 25p.



## TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery-operated, 11 meg input, 20 ranges. Large 4 1/2 in mirror scale. Size 5 1/2 x 4 1/2 x 2 1/2 in. D.c. volts 0-3-1,200V. A.c. volts 3-300V R.M.S. 8-0-800V P-P. D.c. Current 0-12-12mA. Resistance up to 2,000Ω ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17-60. P. & P. 20p.



## MODEL L-55 FET V.O.M.

Input impedance 10 meg ohms 0/0-3/1-2/6/30/120/600V d.c. 0/3/12/60/120/600V a.c. 0/120µA/1/20mA d.c. 0/1K/100K/10 meg/100 meg ohms. £15-97. Post 25p.



## KAMODEN HMG-500 INSULATION RESISTANCE TESTER

3 ranges 0-1,000 Megohms, 500 Volt. Battery operated. Wide range clear meter 4 1/2 x 4". Complete with deluxe carrying case, batteries, instructions. £12-95. Post 30p.



## MODEL TE16 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-280MHz in 6 coils. 500µA meter. 9V battery operation. Size 180mm x 80mm x 40mm. £12-50. Post 20p.



## TO-3 PORTABLE OSCILLOSCOPE

8in tube Y amp. Sensitivity 0-1V p-p/CM. Bandwidth 1-5cps-1-5MHz. Input amp. 2 meg Ω 25pF X amp. sensitivity 0-9V. p-p/CM. Bandwidth 1-5cps-800kHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10cps-300kHz. Synchronisation. Internal/external. Illuminated scale 140mm x 215mm x 330mm. Weight 15lb. 220/240V a.c. Supplied brand new with handbook. £52-50. Carr. 50p.



## CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100kHz V. RMS/mm. 0-1-25. HORIZONTAL. Bandwidth 500kHz. Sensitivity at 100kHz. V. RMS/mm. 0-3-25. Pre-set triggered sweep in nine ranges. free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm x 360mm x 430mm, 115-230V a.c. operation. £28. Carr. paid.



## RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in x 4in C.R.T. Calibrated triggered sweep from 0-2µsec to 100 mill-sec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. £27. Carr. paid.



## TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output, 8-pin socket for calibration. 220/240V a.c. Brand new with instructions. £17-50. Carr. 37p. Size 140mm x 215mm x 170mm.



## TE22 SINE SQUARE WAVE AUDIO GENERATORS

Size: 20cps to 200 kc/s on 4 bands. Square wave. 20cps to 30 kc/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.




## ARF-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10V. P-P. RF 100 KHz to 200 MHz. Output 1V. maximum. Operation 220/240V. A.C. Complete with instructions and leads. £29-95. Post 50p.



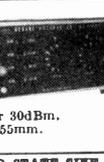
## MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200kHz. Attenuator 0-11dB. 0-1dB step. Impedance 600 ohms. Max. Input power 30dBm. Size 180mm x 90mm x 55mm. £12-50. Post 37p.


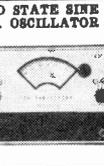
## BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Size 18-200,000 Hz. Square 18-50,000 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7 1/2 x 5 1/2 x 2 1/2 in. Price £17-50. Carr. 17p.



## AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

90W	£2-35	P. & P. 18p
150W	£3-00	P. & P. 18p
300W	£4-00	P. & P. 23p
500W	£5-80	P. & P. 33p
1000W	£8-25	P. & P. 38p
1500W	£11-25	P. & P. 45p
2250W	£19-00	P. & P. 50p
5000W	£40-00	P. & P. £1

## MCA-220 AUTOMATIC VOLTAGE STABILISER

Input 88-125V a.c. or 176-250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. £11-97. Post 50p.



ALL PRICES ARE SUBJECT TO 10% VAT



**HIGH QUALITY CONSTRUCTION KITS**  
Appointed stockists at all branches  
Complete with comprehensive, easy to follow instructions, and covered by full guarantee  
Post and packing 15p per kit

AF20 Mono transistor amplifier	£4.80
AF30 Mono transistor pre-amplifier	£2.81
AF310 Mono amplifier (see two for stereo)	£3.91
ATS Automatic light control	£2.58
AT30 Photo cell switching unit	£2.58
AT50 400W Triac light dimmer/speed control	£4.80
AT56 1.300W Triac light dimmer/speed control	£5.70
AT66 2.200W Triac light dimmer/speed control	£6.50
AT80 Psychedic light control, single channel	£7.80
AT88 Psychedic light control, 3 channel	£14.95
HF81 Medium news transistor radio	£3.33
HF75 FM transistor receiver	£2.88
HF325 De-luxe FM tuner unit	£18.81
HF330 Stereo decoder for HF310/HF325	£9.86
HF396 Aerial amplifier for AM/FM bands I, II, III	£1.77
GP310 Stereo pre-amp for use with Z4 AF310	£21.27
GU330 T-remote unit for guitars etc.	£7.50
NT10 Power supply 100 mA via 5V stab. 12V unstab.	£8.15
NT300 Professional stabilizes power supply	
2x 30 Volt, 2.2 Amp	£12.61
NT305 Transistor converter 12/15V AC/DC to 5V, 7.5V or 9V DC	£4.50
NT310 Power supply 240V AC to 2x 18V DC	£4.80
NT315 Power supply 240V AC to 4.5-15V DC 500 mA	£3.57

### "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V. 50/60 c/s. Variable output 0-260V.

#### MODEL S-260 GENERAL PURPOSE BENCH MOUNTING



1 amp.	£7.00
2.5 amp.	£8.05
5 amp.	£11.75
8 amp.	£15.50
10 amp.	£22.50
12 amp.	£23.60
20 amp.	£49.00
25 amp.	£58.00
40 amp.	£82.50

#### MODEL S-260B Panel mounting Carriage and Packing Extra




1 amp.	£7.00
2.5 amp.	£8.05

#### RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V d.c. up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V a.c. Size 185 x 85 x 105mm. £28.97. Post 25p.



#### PS.200 REGULATED P.S.U.

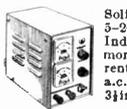

Solid state. Variable output 5-20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V a.c. Size 7 1/2in. x 5 1/2in. x 3 1/2in. £19.95. Post 25p.


#### PS.1000B REGULATED POWER SUPPLY



Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4 1/2in. x 3 1/2in. x 3 1/2in. £11.97. Post 25p.
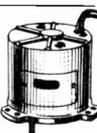
#### 230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RPH CW. 50p each, Post 12p.



#### POWER RHEOSTATS



High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/4in dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000 ohms. 95p. P. & P. 10p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.35. P. & P. 10p.

100 WATT. 1-5/10/25/50/100/250/500/1000 or 2500 ohms. £1.95. P. & P. 15p.


# SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

#### TYPE SW.100 100mm x 80mm Fronts

50µA	£4-15
50-0-50µA	£3-95
100µA	£3-95
100-0-100µA	£3-90
500µA	£3-70
1mA	£3-60
20V d.c.	£3-60
50V d.c.	£3-60
300V a.c.	£3-70
1 amp. d.c.	£3-60

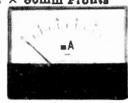

#### Type SD.830 82.5mm x 110mm Fronts

10mA	£3-10
50mA	£3-10
100mA	£3-10
500mA	£3-10
1 amp.	£3-10
5 amp.	£3-10
10 amp.	£3-10
5V d.c.	£3-10
10V d.c.	£3-10
20V d.c.	£3-10
50V d.c.	£3-10
300V d.c.	£3-10
15V a.c.	£3-80
300V a.c.	£3-80
5mA	£3-10
10mA	£3-10
50mA	£3-10
100mA	£3-10



#### Type SD.640 63.5mm x 85mm Fronts

50µA	£3-05
50-0-50µA	£3-05
100µA	£3-00
100-0-100µA	£3-00
200µA	£3-00
500µA	£2-95
1mA	£2-90
5mA	£2-90
10mA	£2-90
50mA	£2-90
100mA	£2-90

#### Type SD.460 46mm x 59.5mm Fronts

50µA	£2-80
50-0-50µA	£2-80
100µA	£2-75
100-0-100µA	£2-75
200µA	£2-70
500µA	£2-65
1mA	£2-60
5mA	£2-60
10mA	£2-60
50mA	£2-60
100mA	£2-60



### "SEW" EDGewise METERS

Type PE.70. 3 1/2 x 1 1/2	£3-40
50µA	£3-75
50-0-50µA	£3-60
100µA	£3-60
100-0-100µA	£3-50
200µA	£3-40

**\*MOVING IRON— ALL OTHERS MOVING COIL**  
Please add postage

#### 240° Wide Angle 1mA Meters

MW1-6 60mm square	£2-97
MW1-8 80mm square	£2-87


#### 230 VOLT A.C. 50 CYCLES RELAYS



Brand new. 3 sets of changeover contacts at 5 amp. rating. 40p each. Post 10p (100 lots 230). Quantities available.

#### Type MR.85P. 4 1/2in. x 4 1/2in. Fronts

50mA	£3-90
100mA	£3-90
500µA	£3-90
5 amp.	£3-90
15 amp.	£3-90
30 amp.	£3-95
20V d.c.	£3-90
50V d.c.	£3-90
150V d.c.	£3-90
300V d.c.	£3-90
15V a.c.	£3-85
300V a.c.	£3-85
8 Meter 1mA	£3-90
VU Meter	£4-55

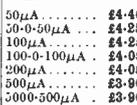


#### Type MR.52P. 2 1/2in. square Fronts.

50µA	£2-50
50-0-50µA	£2-50
100µA	£2-50
100-0-100µA	£2-50
500µA	£2-50
1mA	£2-50
5mA	£2-50
10mA	£2-50
50µA	£2-50
50-0-50µA	£2-50
100µA	£2-50
100-0-100µA	£2-50
500µA	£2-50
1mA	£2-50
5mA	£2-50
10mA	£2-50

#### Type MR.65P. 3 1/2in. x 3 1/2in. Fronts

50µA	£3-70
50-0-50µA	£3-15
100µA	£3-15
100-0-100µA	£3-10
500µA	£3-05
500-0-500µA	£2-80
1mA	£2-80
5mA	£2-80
10mA	£2-80
50mA	£2-80
100mA	£2-80
500µA	£2-80
1mA	£2-80
5mA	£2-80
10 amp.	£2-80
20 amp.	£2-80
30 amp.	£2-80
50 amp.	£2-80
5V d.c.	£2-60

### "SEW" EDUCATIONAL METERS

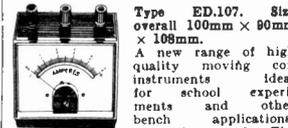

Type ED.107. Size overall 100mm x 90mm x 19mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3 1/2in. mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50µA	£2-80
100µA	£2-40
50-0-50µA	£2-40
1mA	£2-55
1-0-1mA	£2-55
1A d.c.	£2-55
5A d.c.	£2-55
10V d.c.	£2-95
20V d.c.	£2-95
50V d.c.	£2-95
300V d.c.	£2-95
Dual range	
1A d.c.	£2-95
5A d.c.	£2-95
500mA/3A d.c.	£2-70
5V/50V d.c.	£2-70

#### Type MR.88P. 1 1/2 x 3 1/2in. square Fronts.

200mA	£2-25
300mA	£2-25
500mA	£2-25
750mA	£2-25
1 amp.	£2-25
2 amp.	£2-25
5 amp.	£2-25
10 amp.	£2-25
3V d.c.	£2-25
10V d.c.	£2-25
15V d.c.	£2-25
20V d.c.	£2-25
25V d.c.	£2-25
100V d.c.	£2-25
150V d.c.	£2-25
300V d.c.	£2-25
750V d.c.	£2-25
15V a.c.	£2-30
150V a.c.	£2-30
500V a.c.	£2-30
1000V a.c.	£2-30
100mA	£2-25
150mA	£2-25
200mA	£2-25
300mA	£2-25
500µA	£2-55
50-0-50µA	£2-50
100µA	£2-45
100-0-100µA	£2-40
500µA	£2-35
1mA	£2-30
1-0-1mA	£2-25
2mA	£2-25
5mA	£2-25
10mA	£2-25
20mA	£2-25
50mA	£2-25
100mA	£2-25
150mA	£2-25

#### Type MR.45P. 2in. square Fronts.

50µA	£2-70
50-0-50µA	£2-65
100µA	£2-60
100-0-100µA	£2-50
500µA	£2-45
1mA	£2-40
5mA	£2-40
10mA	£2-40
50µA	£2-40
50-0-50µA	£2-40
100µA	£2-40
100-0-100µA	£2-40
500µA	£2-40
1mA	£2-40
5mA	£2-40
10mA	£2-40
50µA	£2-40
100µA	£2-40
500µA	£2-40
1 amp.	£2-40

### "SEW" BAKELITE PANEL METERS

#### Type MR.65. 3 1/2in. square Fronts.

1 amp.	£2-60
5 amp.	£2-60
15 amp.	£2-60
30 amp.	£2-60
50 amp.	£2-60
5V d.c.	£2-60
10V d.c.	£2-60
20V d.c.	£2-60
50V d.c.	£2-60
100V d.c.	£2-60
300V d.c.	£2-60
500V d.c.	£2-60
1000V d.c.	£2-60
30V a.c.	£2-60
50V a.c.	£2-60
150V a.c.	£2-60
300V a.c.	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60
50mA	£2-60
100mA	£2-60
500µA	£2-60
100µA	£2-60
50-0-50µA	£2-60
100µA	£2-60
100-0-100µA	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60
50µA	£2-60
100µA	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60
50µA	£2-60
100µA	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60
50µA	£2-60
100µA	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60

#### Type MR.65. 3 1/2in. square Fronts.

25µA	£4-60
50µA	£3-55
50-0-50µA	£3-05
100µA	£3-00
100-0-100µA	£2-70
500µA	£2-60
500-0-500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60
50µA	£2-60
100µA	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60
50µA	£2-60
100µA	£2-60
500µA	£2-60
1mA	£2-60
1-0-1mA	£2-60
5mA	£2-60
10mA	£2-60

#### Type 8-80 80mm square Fronts

50µA	£3-50
50-0-50µA	£3-40
100µA	£3-40
100-0-100µA	£3-30
500µA	£3-25
1mA	£3-20
1-0-1mA	£3-20
5mA	£3-20
10mA	£3-20
50µA	£3-20
100µA	£3-20
500µA	£3-20
1mA	£3-20
1-0-1mA	£3-20
5mA	£3-20
10mA	£3-20
50µA	£3-20
100µA	£3-20
500µA	£3-20
1mA	£3-20
1-0-1mA	£3-20
5mA	£3-20
10mA	£3-20

Send S.A.E. for new 8-page list of Semiconductor and Valves

ALL PRICES ARE EXCLUSIVE OF 10% V.A.T.



ALSO SEE FOLLOWING PAGES

# G.W. SMITH & CO (RADIO) LTD

## UNR 30 RECEIVER




4 Bands covering 550kHz-30MHz. BFO Built-in Speaker 220/240V a.c. Brand new with instructions.  
**OUR PRICE £15.75** Carr. 37p

## UR-1A RECEIVER



4 Bands covering 550kHz-30MHz. FET, 8 Meter. Variable BFO for 88B. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 121 x 47in x 7in. Brand new with instructions.  
**OUR PRICE £25.00** Carr. 37p

## SKYWOOD CX203 RECEIVER

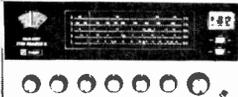


Solid state. 5 bands covering 200-420kHz and 0.55 to 30MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO. AVC. ANL. 'S' meter. AM/CW/88 B. Integrated speaker and phone socket. 220/240V a.c. or 12V d.c. Size 325 x 266 x 150mm. Complete with instructions and circuit.  
**OUR PRICE £32.50** Carr. 50p

## LAFAYETTE HA-600 RECEIVER



General coverage 150-400kHz. 550kHz-30MHz. FET front end. 2 mech. filters, product detector, variable BFO, noise limiter, 8 Meter Bandspread. RF Gain. 15in x 9 1/2in x 8 1/2in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.  
**OUR PRICE £50.00** Carr. 50p

## TRIO 9R59DS RECEIVER

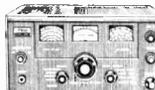

4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 88B-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 445kHz audio output 1.5W. Variable RF and AF gain controls 115/250V a.c. Size: 7in x 13in x 10in with instruction manual.  
**OUR PRICE £49.50** Carr. Paid  
**FULL RANGE OF TRIO STOCKED**

**OUR PRICE £49.50** Carr. Paid  
**FULL RANGE OF TRIO STOCKED**



ALSO SEE PREVIOUS PAGES

## EMI LOUDSPEAKERS



Model 350. 13in x 8in with single tweeter/crossover. 20-20,000 Hz. 15W RMS. Available 8 or 15 ohms. £7.95 each. P. & P. 37p.  
 Model 450. 13in x 8in with twin tweeters/crossover. 55-13,000 Hz. 8W RMS.

Available 8 or 15 ohms. £3.82 each. P. & P. 25p.

## SPECIAL OFFER!



**STEREO SPEAKERS**  
 Matched pair of bookshelf speakers. De luxe teak veneered finish. Size 14 1/2 in x 9in x 7 1/2 in. 8 ohms. 8W RMS. 16W peak. Complete with DIN lead.

**OUR PRICE £12.95** Carr. 50p

## HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MT/100MT. Output 50mW.

**OUR PRICE £6.97** P. & P. 20p

## MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2in x 5in x 3in. Inputs: Mics: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

**OUR PRICE £8.97** P. & P. 20p

## 1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets 6in x 4in x 2 1/2in.

**OUR PRICE £2.25** P. & P. 20p

## EA.41 REVERBERATION AMPLIFIER



Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverb control. Beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in.

**OUR PRICE £7.50** P. & P. 15p

## AUDIOTRONIC

### ACD660 STEREO CASSETTE DECK

A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chronic tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/DIN line input sockets, 3.5mm jack input sockets, etc. Frequency response 100-8kHz (100-12kHz (CrO2)). S/N -45dB. Crosstalk -45dB. Separation -35dB. Noise limiter -6dB at 10kHz. Complete with phone connecting leads.

**OUR PRICE £39.50** Carr. & Ins. 50p

### AHP8A 8 TRACK STEREO TAPE PLAYER

Incorporates built in amplifiers giving 22 + 22W r.m.s. output. Push-button track selector. Illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. 220/240V a.c.

**OUR PRICE £17.25** P. & P. 50p, plus V.A.T.

### AHP8D 8 TRACK STEREO TAPE DECK

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. 220/240V a.c.

**OUR PRICE £11.95** P. & P. 50p, plus V.A.T.

## STEREO HEADPHONES

LSH20. Individual volume controls. Stereo mono switch. 8 ohms. 40-18,000Hz.  
**£3.50** P. & P. 30p

LSH30. Open back type. Individual volume and volume controls. 8 ohms. 30-20,000Hz.  
**£5.50** P. & P. 30p

LSH40. Two way speaker system. Individual volume controls. 8 ohms. 20-20,000Hz.  
**£6.95** P. & P. 30p

LSH60. 3in speaker units. 8 ohms. 20-20,000Hz. Complete with zipped carrying case.  
**£8.50** P. & P. 30p

LQH400. 4-channel dynamic headphones. Each earpiece has 4 drive units. 4-32 ohms. 20-20,000Hz.  
**£9.95** P. & P. 30p

LSH50. Electrostatic with self powered energiser and control unit with headphone speaker selector. 4-32 ohms. 20-24,000 Hz.  
**£15.95** P. & P. 30p

## HIGH QUALITY EQUIPMENT

### DOLBY 'B' NOISE REDUCTION UNITS



Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16 1/2in x 8in x 3 1/2in. a.c. 00/250V2.

**PROCESS TWO**  
 For use with cassette and tape recorders. Freq. res. 301Hz-20kHz-2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

**OUR PRICE £34.50** P. & P. 50p

**PROCESS FOUR**  
 For use with semi professional tape recorders. Freq. res. 30Hz-20kHz ±2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

**OUR PRICE £50.00** P. & P. 50p

**ACR14 BATTERY MAINS CASSETTE RECORDER**  
 Portable two track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.

**OUR PRICE £10.50** P. & P. 50p

**AMR-9000 GLOBAL AM/FM PORTABLE**  
 10 wavebands covering A.M.: 535-1065kHz; F.M.: 88-108MHz; A.I.R.: 108-135MHz; P.B.: 147-174MHz; W.B.: 162-5MHz Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M. A.F.C. 3in speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 x 79 x 219mm. Battery/mains operation.

**OUR PRICE £36.00** P. & P. 50p

## AR1000 Sportsman AM/FM Portable



5 wavebands covering A.M.: 535-1065kHz; F.M.: 88-108MHz; A.I.R.: 108-135MHz; P.B.: 147-174MHz; W.B.: 162-5MHz Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M. A.F.C. 3in speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 x 79 x 219mm. Battery/mains operation.

**OUR PRICE £11.50** P. & P. 35p


## AMB500 MULTI BAND RADIO



5 wavebands covering MW 535-1605kHz and F.M. 88-175MHz. All transistor. Battery or mains operation. Built-in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.

**OUR PRICE £6.95** P. & P. 35p

## ACR14 BATTERY MAINS CASSETTE RECORDER

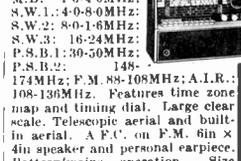

Portable two track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.

**OUR PRICE £10.50** P. & P. 50p

**ACR3500 CAR RADIO**  
 Manual tuning of Medium and Long waves. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.  
**OUR PRICE £6.50** P. & P. 50p

**ACR1 PUSH BUTTON CAR RADIO**  
 Push button tuning of one LW and five MW stations of your choice. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.  
**OUR PRICE £8.95** P. & P. 50p

**ACP8 8-TRACK CAR PLAYER**  
 12V neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with pilot lamp. With speakers, mounting brackets and instructions.  
**OUR PRICE £12.50** P. & P. 40p

**ACA55E ELECTRIC CAR AERIAL**  
 5 section. Fully automatic. 12V d.c. Extends to approx. 40in. Complete with switch, all leads and instructions.  
**OUR PRICE £5.95** P. & P. 50p

**LOW NOISE TAPE CASSETTES**  
 Top Hi-Fi quality in library cases


TYPE	5	10	25
C60	£1.29	£2.53	£5.99
C90	£1.85	£3.02	£5.59
C120	£2.29	£4.45	£10.65

P. & P. 15p Post Free  
**CASSETTE TAPE HEAD CLEANER** 30p each. P. & P. 50p.

# SAVE UP TO 33 1/3% OR MORE! GWS

## SUPER AKAI HI-FI BARGAINS

### CS35 STEREO CASSETTE RECORDER

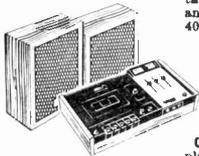

For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CrO2 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CS88 speakers. Rec. Price £96-10. **OUR PRICE £56-50** P. & P. 50p

**CS35D STEREO DECK** 4 track record/playback deck. Accepts chrome/regular tape cassettes. Rec. Price £44-45 P. & P. £28-30. **GWS PRICE £44-45** 50p.

**CASSETTE, P. & P. 60p.**

GXC40D Deck	£57-20
GXC40 Recorder	£87-20
GXC40T Deck/Receiver	£99-05
GXC45 Deck	£74-30
GXC46D Dolby Deck	£83-55
GXC46 Recorder	£89-95
GXC60D Deck	£87-65
GXC65D Dolby Deck	£92-65

**CARTRIDGE (P. & P. 50p)**

CR81 Deck with amps.	£65-40
CR81D Deck	£59-60
CR81T Recorder/Receiver	£92-75
CR8088 4 channel Recorder	£114-25
CR80DS8 4 chan. Recorder	£93-65

**TAPE (P. & P. 75p)**

4000DS Deck	£59-95
4000DS Dust Cover	£3-95
1721L Recorder	£60-35
X5000 Recorder	£82-50
X201D Deck	£108-20
GX220D Deck	£123-95
GX221D Deck	£138-40
GX280D Deck	£196-60
GX370 Deck	£211-50

**TAPE CASSETTE (P. & P. 75p)**

GX1900D Deck	£144-50
--------------	---------

## RECORD DECK PACKAGES



**Carriage and Packing 75p**  
Complete units with Stereo cartridge ready wired in plinth and cover.

**GARRARD**

2025 TC/STAHCD	£10-65
SP25 111/G800	£16-90
SP25 111/M44E	£17-40
SP25 111/M44-7	£18-95
SP25 111/M55E	£17-85
SP25 111 Module/M75-6	£19-45
AP76/G800	£25-55
AP76/G800E	£28-10
AP76/M44E	£27-05
AP76/M44-7	£26-80
AP76/M55E	£27-50
AP76/M75DE	£31-70
AP76/M75EJ	£30-30
AP76 Module M75-6	£29-10
AP96 Module M75-6	£33-20
ZERO 1008 Module/M93E	£44-15

**B.S.R. McDONALD**

Z10/SC7M	£7-40
MP60/G800	£15-00
MP60/TPD1/G800	£15-80
MP60/M44-7	£16-60
HT70/TPD1/G800	£19-20

**GOLDRING**

GL72/G800	£31-50
GL75/G800	£36-65
GL75/G800E	£39-15

**GOODMANS**

TD100/G800 Teak	£48-85
TD100/G800 White	£48-60

**LEAK**

Delta/M75-6	£47-20
Trusped	£35-95

**PHILIPS**

GA105/GP200	£13-80
GA160/GP200 Teak	£19-50
GA212/GP400	£45-25
GA308 (less cartridge)	£23-95
GA308 P.U.	£32-75

**PIONEER**

PL12D (Less cartridge)	£31-75
PL15C (Less cartridge)	£44-25
PL41D (Less cartridge)	£104-75
PL50 (Less cartridge)	£98-80
PL61 (Less cartridge)	£110-30
PLA35 (Less cartridge)	£81-55

**THORENS**

TD160C/Ortofon M15E Super	£70-35
TD125 AB/11/Ortofon M15E	£92-05
TD165/Ortofon M15E Super	£82-55

**WEARFEDALE**

Linton/M44-7 Teak	£23-55
Linton/M44-7 White	£24-70

## SPECIAL PURCHASE!

### BSR 8-TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model T D 8 S complete with silver and black escutcheon ready to fit into cabinet. Output 125mV A.C. 240V. Overall size approx. 185 x 215 x 80mm.

**OUR PRICE £8-95** P. & P. 50p



## RECORD DECKS



**Carriage & Packing 50p**

**B.S.R. McDONALD**

C114 Mini	£3-95
C129 Mono	£5-60
C137	£7-00
510/TPD1	£13-95
610	£10-55
610/TPD1	£16-45
710	£21-15
810	£28-30
MP60	£25-25
MP60/G800	£10-90
MP60/TPD1	£13-20
MP60/TPD2	£11-25
HT70	£11-60
HT70/G800	£14-25
HT70/TPD1	£10-55

## CONNOISSEUR

B1 Kit	£9-10
B1 Chassis	£11-85
B2/SAU2/Chassis	£22-70
B2/SAU2/Plinth/Cover	£28-20

**GARRARD**

2025 T/C Stereo	£6-35
SP25 III/Acos GP104	£9-25
SP25 III/G800	£9-50
SP25 III/M75-6	£10-95
SP25/M75-6	£13-90
AP76	£18-00
SL65B	£11-15
SL72B	£17-75
SL95B	£21-15
401	£24-35
ZERO 100	£34-10
ZERO 1008	£21-40

**GOLDRING**

G99	£22-50
G101/P/C	£22-50
G101/P	£15-75
GL69/2	£15-75
GL72	£25-45
GL72/P	£33-75
GL75	£32-20
GL75/P	£41-65
GL78 P/C	£35-25
GL85/P/C	£72-00

**GOODMANS**

TD100/G800 Teak	£48-85
TD100/G800 White	£48-60

**LEAK**

Delta/M75-6	£47-20
Trusped	£35-95

**PHILIPS**

GA105/GP200	£13-80
GA160/GP200 Teak	£19-50
GA212/GP400	£45-25
GA308 (less cartridge)	£23-95
GA308 P.U.	£32-75

**PIONEER**

PL12D (Less cartridge)	£31-75
PL15C (Less cartridge)	£44-25
PL41D (Less cartridge)	£104-75
PL50 (Less cartridge)	£98-80
PL61 (Less cartridge)	£110-30
PLA35 (Less cartridge)	£81-55

## THORENS

TD160C/Ortofon M15E Super	£70-35
TD125 AB/11/Ortofon M15E	£92-05
TD165/Ortofon M15E Super	£82-55

**WEARFEDALE**

Linton/M44-7 Teak	£23-55
Linton/M44-7 White	£24-70

## SPECIAL PURCHASE!


### BSR 8-TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model T D 8 S complete with silver and black escutcheon ready to fit into cabinet. Output 125mV A.C. 240V. Overall size approx. 185 x 215 x 80mm.

**OUR PRICE £8-95** P. & P. 50p



## FM TUNER CHASSIS

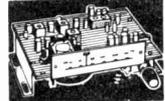

**6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6in x 4in x 2 1/2in** 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use.

**OUR PRICE £5-95** P. & P. 20p  
Stereo Multiplex Adaptor £4-97.

## SPECIAL PURCHASE!

### FERGUSON EXPORT MODELS



## 3408 STEREO TUNER AMP.

Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape, etc. Separate bass, treble, balance and volume controls.

**OUR PRICE £31-50** Carr. 50p

## 3416 STEREO TAPE DECK



4 track 7 1/2, 9 1/2, 11 i.p.a. Stereo/mono record/play. 7in reels. Inputs for dynamic mikes, radio gram. Complete with cover.

**OUR PRICE £41-95** Carr. 75p

## SINCLAIR PROJECT 60 PACKAGE DEALS



2 x Z30/Stereo 60/PZ3 £16-95. P. & P. 37p.

2 x Z30/Stereo 60/PZ6 £18-00. P. & P. 37p.

2 x Z50/Stereo 60/PZ8 £20-85. P. & P. 37p.

Transformer for PZ8 £3 extra.

Active Filter Unit £4-45.

Pair of Q16 Speakers £10-70.

Sinclair Project 605 £90-97. P. & P. 37p.

All Sinclair Products in stock: 2006 Stereo Amplifier, £22-95; 3000 Stereo Amplifier, £28-95; 2000/3000 Stereo Tuner, £26-30.

Q830 Speakers, £29-99 pair, P. & P. 60p extra on above items.

## SPECIAL GARRARD OFFERS!



**STEREO 1025T**

4 speed autochanger unit fitted with stereo ceramic cartridge.

**OUR PRICE £4-95** Carr. & Ins. 50p

## SP25 III WITH ACOS GP 104

4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.

**OUR PRICE £8-50** Carr. & Ins. 50p

## HOMER INTERCOMS

Ideal for home offices, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2-97. P. & P. 15p.

3 Station £5-25. P. & P. 15p.

4 Station £6-62. P. & P. 17p.

with batteries, cable and free instructions.

2 Station £2-97. P. & P. 15p.

3 Station £5-25. P. & P. 15p.

4 Station £6-62. P. & P. 17p.

## LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY-

- ARMSTRONG
  - CAMBRIDGE
  - KEF-LUX-NIKKO
  - SANSUI-SANYO
  - SONY-TEAC
  - TRANSCORPTORS
  - TRIO-UBER
  - YAMAHA
- Prices on request or send S.A.E. for Full Discount List

**ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!**

# G.W.SMITH & CO (RADIO) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

- |   |  |  |
|---|--|--|
| <b>CENTRAL LONDON</b>                         | 257/8, Tottenham Court Rd, W.1. Tel: 01-580 0670 | 311, Edgware Road, W.2. Tel: 01-262 0387 |
| 10, Tottenham Court Rd, W.1. Tel: 01-637 2232 | 382, Edgware Road, W.2. Tel: 01-723 4194         |  |
| 27, Tottenham Court Rd, W.1. Tel: 01-636 3715 | 152/3, Fleet Street, E.C.4. Tel: 01-353 2833     |  |
| 87, Tottenham Court Rd, W.1. Tel: 01-580 3739 | 378, Harrow Road, W.9. Tel: 01-286 9530          |  |
| 21, Old Compton Street, W.1. Tel: 01-437 9369 | <b>ESSEX</b>                                     |  |
| 3, Lisle Street, W.C.2. Tel: 01-437 8204      | 86, South Street, Romford. Tel: Romford 20218    |  |
| 34, Lisle Street, W.C.2. Tel: 01-437 9155     | <b>SURREY</b>                                    |  |
| 118, Edgware Road, W.2. Tel: 01-723 9789      | 1046, Whitgift Centre, Croydon. Tel: 01-881 3027 |  |
| 193, Edgware Road, W.2. Tel: 01-723 6211      | 27, Eden Street, Kingston. Tel: 01-547 0465      |  |
|   | 32, Hill Street, Richmond. Tel: 01-948 1441      |  |

**ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY**

HEAD OFFICE AND MAIL ORDER DEPARTMENT  
UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ  
TELEPHONE 01-205 3735

## PRICES SUBJECT TO 10% VAT

Order with confidence by Post but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.



TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS

CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over)

All prices correct at 20.8.73 but subject to change without notice. E & O

# P.C. BORED?

— not with the

# decon-dalo 33PC



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB. A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

## NO MESS— NO MASKING

### A perfect circuit every time!

The Decon-Dalo 33 PC marker is now available in France, Germany, Italy, Switzerland, Austria and all Scandinavian countries. Send for details of local supplier.

Please send me further details on the 33PC:

Name .....

Address .....

Post to: **DECON LABORATORIES LTD.**  
**FREEPOST**  
**PORTSLADE, BRIGHTON, ENGLAND**  
 (No Stamp Needed) Phone 0273 414371

# KONTAKT 60

FOR INACCESSIBLE CONTACTS—More than just a cleaner. KONTAKT 60 guarantees perfect cleaning of contacts chemically in accordance with today's technology.

KONTAKT offers the following advantages:—

1. Dissolves oxides and sulphides the safe way without attacking contact substances.
2. Contains carefully selected solvents which do not attack plastics whereas they do dissolve resinified contact greases and dirt.
3. Contains *no silicone*.
4. Contains a light lubricant in order to avoid the contact paths being corroded.
5. Prevents further oxidation setting in.
6. Prevents "creep" currents.

Because of these outstanding properties KONTAKT 60 is one of the best and most popular contact cleansing agents in the world.



Users include: Rolls-Royce Ltd., C.E.G.B., South of Scotland Electricity Board, Trinity House Workshops, Kolster Brandes, Mullard, Plessey Cos., etc.

#### OTHER KONTAKT PRODUCTS ARE:

- 70 Protective Lacquer
- 72 Insulating Spray
- 75 Cold Spray for Fault Location
- 80 Special Siliconized Polish
- 100 Antistatic Agent for Plastics
- 101 Dehydration Fluid

Write for full details of above complete range of Kontakt products to:—

**SPECIAL PRODUCTS DISTRIBUTORS LIMITED**  
 81 Piccadilly, London, W.1 01-629 9556

#### TRANSISTORS

AC126 14p	AF180 45p	BC158 14p	BF180 32p	BFY51 21p
AC127 16p	AF181 43p	BC159 14p	BF181 32p	2N3053 23p
AC128 14p	AF239 42p	BC177 20p	BF184 35p	2N3054 37p
AC141K 24p	BC107 12p	BC183L 14p	BF185 35p	2N3055 60p
AC142K 24p	BC108 10p	BC184L 12p	BF186 45p	TIP29 66p
AC176 20p	BC109 12p	BC187 22p	BF194 15p	TIP30 75p
AC187 18p	BC113 25p	BC294 16p	BF195 15p	TIS91 48p
AC187K 24p	BC114 30p	BC440 50p	BF196 15p	
AC188K 24p	BC115 20p	BC460 68p	BF197 15p	
AD142 45p	BC116 20p	BD124 80p	BF200 32p	
AD149 45p	BC117 15p	BD131 60p	BF258 40p	
AD161 34p	BC125 14p	BD132 60p	BF259 40p	
AD162 34p	BC142 25p	BD139 63p	BF337 23p	
AF115 21p	BC143 25p	BDX32 £2.00	BFT42 44p	
AF116 21p	BC147 13p	BF115 25p	BFT43 44p	OA91 7p
AF117 21p	BC148 13p	BF121 35p	BFX84 40p	OA202 9p
AF118 49p	BC149 13p	BF158 20p	BFX88 30p	IN4148 4p
AF139 40p	BC154 20p	BF167 20p	BFX89 67p	BY127 11p
AF178 45p	BC157 14p	BF179 39p	BFY50 21p	IN4006 8p

#### DIODES AND RECTIFIERS

#### RESISTORS METAL FILM

5% TOL.  
 1/2W, 1W, 1/2W, E12 values to 27M all 1p each.  
 1W to 10M E12 values 3p each;  
 2W to 10M E12 values 4p each;  
 5W wire wound, 10W wire wound 8p and 9p each. See Cat. for values.

#### POTENTIOMETERS-CARBON TRACK

5K, 10K, 25K, 50K, 100K, 250K, 500K, 1M.  
 Log or lin less switch 11p  
 Log or lin with switch 23p  
 Dual log less switch 250K, 500K, 1M, 2M, only 39p  
 Dual lin less switch 5K, 10K, 25K, 50K, 100K, only 39p  
 Dual log with switch 10K, 100K, 250K, 500K, 1M only 55p

#### JACK PLUGS AND SOCKETS

Standard insulated 11p; Standard screened 18p;  
 Stereo insulated 22p; Stereo screened 30p;  
 3.5mm insulated 8p; 3.5mm screened 12p;  
 Standard socket switched 17p; Stereo socket switched 21p; 3.5mm socket switched 6p;  
 Standard line socket 15p; Stereo line socket 22p;  
 3.5mm line socket 10p.

#### CABLES AND SCREENED WIRES

Min. mike cable single 7p/metre; Min. twin mike cable 11p/metre; Pick up wire single 7p/metre; Pick up wire twin 11p/metre; Stereo screened twin 10p/metre; 4 core individually screened 14p/metre; Speaker wire twin coded 6p/metre.

#### PHONO-D.I.N. PLUGS AND SOCKETS

Phono plug insulated 7p; Phono plug screened 11p; Phono line socket screened 12p; Metal coax plug 8p; 2, 3, 5 pin 180°, 240°, D.I.N. plugs 12p; 4, 6, 7 pin plugs 15p; 2, 3, 5 pin 180° line sockets 13p; 2, 3, 5 pin 180° chassis sockets 7p.

## E. A. HALL (ELECTRONICS)

The Manse, Little Brinton, Northampton NN7 4HX

Mail Order Only. C.W.O. Postage and packing 10p per order. Detailed Catalogue 6p. Please add V.A.T. on total order incl. postage and packing. Many other items in our catalogue.

# MORE JOSTY STOCKISTS FOR YOU

THIS FASCINATING RANGE OF QUALITY ELECTRONIC KITS ARE NOW AVAILABLE FROM:

## CENTRAL LONDON

G. W. Smith & Co. (Radio) Ltd., 257/8 Tottenham Court Road, W.1. 10 Tottenham Court Road, W.1. 27 Tottenham Court Road, W.1. 87 Tottenham Court Road, W.1. 21 Old Crompton Street, W.1. 3 Lisle Street, W.C.2. 34 Lisle Street, W.C.2. 118 Edgware Road, W.2. 193 Edgware Road, W.2. 311 Edgware Road, W.2. 382 Edgware Road, W.2. 152/3 Fleet St., E.C.4. 378 Harrow Rd., W.9.

## ESSEX

86 South Street, Romford.

## SURREY

1046 Whitgift Centre, Croydon. 27 and 21 Eden St., Kingston. 32 Hill St., Richmond.

**G. W. SMITH MAIL ORDER ADDRESS**  
G. W. Smith & Co., Unit 4, The Hyde Industrial Estate, The Hyde NW9 6JJ.

Newmart Electronics, 30-32 Shude Hill, Manchester; 4 Newmarket Street, Leeds; 20 Pinstone Street, Sheffield; 15 Whitechapel, Liverpool.

## NEWMART MAIL ORDER ADDRESS

Newmart Electronics, Altham House, Belmont St., Monton, Eccles, Manchester.

T. Pattison, 5 Maritime Terrace, Blandford Street, Sunderland.

Red Radio Shop, 31 Crowtree Road, Sunderland.

J. R. Gough, 27 East Smithy Street, South Shields.

Payne & Hornsby Ltd., 3 Andrews House, Gallowgate, Newcastle-on-Tyne.

Richley & Freeman Ltd., 100 Percy Street, Newcastle-on-Tyne.

Aitken Bros. Ltd., 35 High Bridge, Newcastle-on-Tyne.

Hamilton Music Store, Corporation Road, Middlesbrough, Teesside.

B. Williams, 16 Borough Road, Middlesbrough, Teesside.

Mckenna & Brown Ltd., 135 High Street, Redcar, Teesside.

Jaytron Ltd., 178/9 Phitsborough Road, Dublin, 7, Ireland.

Bond & Mason, 94 Church Road, Stockton, Teesside.

T. Jaques, Waterdale Wood, Doncaster, Yorks.

Modern Electronics, 5 Sunny Bar, Doncaster, Yorks.

Mitsons, Citadel Row, Carlisle, Cumberland.



Television Rentals, 414 Catcote Road, Hartlepool, Co. Durham.

Lectro-Mec, 45 Roxborough Street, Greenock, Renfrewshire

Ian Strachan, 7 Bridge Gate, Irvine, Ayrshire.

F. Brown & Co., 44-46 George IV Bridge, Edinburgh.

R.M.E. Surplus Supplies, 143 Stockwell Street, Glasgow, G.1.

Aberdeen Radio & Co., 11 Backwynd, Aberdeen.

Radiocraft (Huddersfield) Ltd., 38 King Street, Huddersfield.

Scunthorpe Audio & Hi-Fi Centre, 15 Dunstall Street, Scunthorpe.

Alpha Sound Services, 50 Stuart Road, Waterloo, Liverpool, 22.

CALL IN AT ANY OF THESE STOCKISTS AND SEE FOR YOURSELF THE VERY HIGH STANDARDS TO WHICH THESE JOSTY KITS ARE MANUFACTURED. THEY ARE GUARANTEED FOR ONE YEAR FOR ALL PARTS AS WELL AS THE CORRECT FUNCTION OF THE ASSEMBLED KITS.


# JOSTY

## JOSTY KIT RETAIL PRICE LIST (APRIL, 1973)

Model No.	Description	RRP Excluding V.A.T.	V.A.T.	Total RRP incl'd. V.A.T.
AF20	Mono Transistor Amplifier	4.80	0.48	5.28
AF30	Mono Transistor Pre-Amplifier	2.61	0.26	2.87
AF310	Mono Amplifier (for Stereo use two)	5.91	0.59	6.50
AT5	Automatic Light Control	2.58	0.26	2.84
AT30	Photo Cell Switching Unit	5.70	0.57	6.27
AT50	400W Triac Light Dimmer Speed Control	4.80	0.48	5.28
AT55	1,300W Triac Light Dimmer Speed Control	5.70	0.57	6.27
AT56	2,200W Triac Light Dimmer Speed Control	6.90	0.69	7.59
AT60	Psychedelic Light Control, Single Channel	7.80	0.78	8.58
AT65	Psychedelic Light Control, 3 Channel	14.55	1.45	16.00
HF61	Medium Wave Transistor Radio	3.33	0.33	3.66
HF75	F.M. Transistor Receiver	2.88	0.28	3.16
HF310	F.M. Tuner Unit	15.81	1.58	17.39
HF325	De-Luxe F.M. Tuner Unit	24.12	2.41	26.53
HF330	Stereo Decoder for use with HF310 or HF325	9.96	0.99	10.95
HF395	Aerial Amplifier for AM/FM Bands I, II and III	1.77	0.17	1.94
GP310	Stereo Pre-Amp to use with 2, AF310	21.27	2.12	23.39
GU330	Tremolo Unit for guitars, etc.	7.50	0.75	8.25
NT10	Power Supply 100mA/9V Stabilised, 12V Unstabilised	6.15	0.61	6.76
NT300	Professional Stabilised Power Supply 2 x 30V, 2.2A	12.51	1.25	13.76
NT305	Transistor Converter 12/15V, a.c./d.c. to 6V, 7.5V, or 9V d.c.	4.50	0.45	4.95
NT310	Power Supply 240V a.c. to 2 x 18V d.c. at 2A	4.80	0.48	5.28
NT315	Power Supply 240V a.c. to 4.5-15V d.c. 500mA	9.57	0.95	10.52

## AT65

## PSYCHEDELIC LIGHT CONTROL

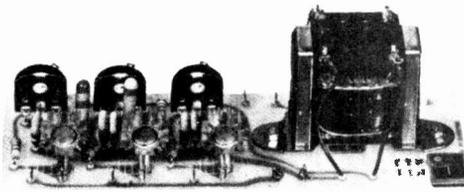

Psychedelic light control with 3 channels for treble, medium and bass. Maximum load 1,200 Watt or 400 Watt on each channel. May also be used as a triac with 3 independent controls.

Sole UK Distributors

# RADIO SUPPLIES

(Components) Ltd.  
HARTLEPOOL

# ELECTRONIC KITS


# Connoisseur

## B.D.2 Press button speed change turntable



The Connoisseur BD2 belt drive turntable with press button speed change is an integrated turntable and pickup arm assembly, the raise/lower device of which is operated by the knob at the front right hand corner. The head shell allows for the lateral adjustment of the cartridge. The BD2 is supplied as a chassis unit or spring mounted on a wood plinth complete with dust cover.

## B.D.1 Turntable kit

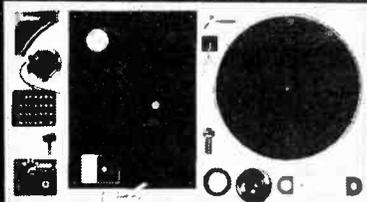

The B.D.1 well known for its superb performance and quality two speed working through a flexible belt drive system is now available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

### A.R. SUGDEN & CO. (ENGINEERS) LTD.

Atlas Mill Road, Brighouse, Yorkshire  
HD6 1ER Telephone 2142

## ZIGGY'S 2001 ELECTRONICS Co. Ltd.



**SPECS. MULTIMETER U4324.** Sensitivity 20,000 OPV DC. Usually high current ranges. 3 amps a.c./d.c. Voltages AC3 to 900V d.c. 0.6 to 1200V. Resistance 500 ohms—20,200—2,000Ω. Transmission level —10 to +12dB. This high quality instrument has diode protection. Complete with test leads, batteries, etc. £8.80 plus 25p P. & P.

**MULTIMETER 4313.** Similar to above but special features include 3 amp current range and instrument is housed in metal case with carrying handle. (Illustrated leaflet sent on request.) ONLY £10.45 plus 30p P. & P.



**SANWA JP-5D SPECS.** 2000 OPV 1000V A.C.-D.C. 500 mA current D.C. A robust instrument with diode protection. Only £6.64. P. & P. 20p.

### MAINS TRANSFORMER

Eagle MT6, 6-0-6, 100 M/A, 95p plus 6p P. & P.  
MT12, 12-0-12, 50 M/A, 95p plus 10p P. & P.  
Eagle Type MT280 6-0-6, 250 M/A } All  
MT150 12-0-12, 150 M/A } £1.43 plus  
MT100 24-0-24, 100 M/A } 12p P. & P.  
R/S 13V 0.5 Amp C.T. } £1.40  
16.3V 0.3 Amp C.T. } plus 12p P. & P.  
Charger Types 9V, 17V  
1 Amp £1.20 P. & P. 12p  
2 Amp £1.65 P. & P. 12p  
4 Amp £1.95 P. & P. 20p  
6 Amp £2.62 P. & P. 35p

### POTENTIOMETERS

5-10, 11p each. 10 plus 10p each.  
5kΩ 50kΩ 500kΩ  
10kΩ 100kΩ 1mΩ  
25kΩ 250kΩ 2mΩ  
log or lin less switch (& 1kΩ lin) 1-5 12p

log or lin with switch 1-52 4p. 5-10 23p. 10 plus 20p.  
dual less switch 1-5 39p. 5-10 37p. 10 plus 35p.  
Any mix for Quantity Prices. P. & P. 7p.

### MINI LOUDSPEAKERS

2in 8Ω 50p, 5p P. & P.  
3in 8Ω 50p, 5p P. & P.

### ENAMELLED COPPER WIRE

S.W.G. 16, 18, 20, 22, 24, 26, 2oz reels, 26p.  
28, 30, 32, 34, 36, 38, 40, 2oz reels, 36p.  
Postage 1-5, 10p. 5 plus, 15p.

### ANTEX SOLDERING IRON BITS

Chrome Type for 15 watt Models.  
3/8in, 1/2in, 3/4in. All 26p each. Postage 5p.

### TELESCOPIC AERIAL

Six Section, Swivel Base. Only 20p. P. & P. 5p.

### TURNTABLE SERVICES

**Headshells**  
Garrard SP25 Mk.I & II. Type M7 £1-10  
S.M.E. S2 Shell £2-77  
Thorens TP50 for TD150 £3-30  
Thorens TP60 for TD160 £3-30  
Goldring PH7 for GL85 £3-80  
**Head Slides** Postage 5p. per item  
Gerrard C1 for SL75 etc. 50p  
Gerrard C2 for SP25 Mk.III, SL95 etc. 50p  
B.S.R. for MP60, 310, 510, 610 50p  
**Jockey Wheels**  
Garrard SP25 Type etc. 55p  
McDonald MP60 etc. 50p  
Stylli Diamonds for Sonotone  
9TA/HC LP/78 65p  
9TA/HC LP/LP 95p

### ACoustic WADDING

B.A.F. 1in Thick Superior Quality, 50p per sq. yard.  
Any length cut x 36in width, postage 5p.

### EAGLE LT700 TRANSFORMER

40p. P. & P. 5p.  
**NEW MULLARD DATA BOOK 1973/74**  
30p. P. & P. 5p.

**FOR SPEEDY DELIVERY OF THESE MINT CONDITION COMPONENTS PLEASE SEND C.W.O. TO ZIGGY'S 2001 ELECTRONICS CO. LTD., DEPT. P.E.3, 34 MABLEY STREET, LONDON, E.9.**

All prices include VAT, please add postage where indicated.

Do you suffer from tired eyes due to bright lights, or need a softer light for watching television in comfort? Well, we have the answer, a

### GREENBANK DIMMER SWITCH

Just look at these features:

- ★ Velvet dim to full brightness at the touch of a finger
- ★ Positive off position
- ★ Built-in radio interference suppression
- ★ Controls up to 300 watts
- ★ Easy replacement for a standard light switch

All this for only  
**£3.75**  
complete

(500 watt model also available)

This price includes V.A.T., also P. & P. Why not write or phone now? Please send C.W.O. to:

**GREENBANK ELECTRONICS**  
94 New Chester Road  
New Ferry, Bebington  
Cheshire L62 5AG  
Tel. 051-645 3391

**COMPREHENSIVE HOME CONSTRUCTOR KITS**  
**AS SPECIFIED IN THE P.E. RONDO**  
**COMPLETE QUADRAPHONIC HI-FI SYSTEM**

**CBS SQ\* MATRIX DECODER**

\*REGD. CBS INC.

COMPLETE KIT **£8.00** POST FREE INCLUDING CBS LICENCE FEE  
 + 80p V.A.T.

**PREAMPLIFIER BOARD**

COMPLETE KIT **£3.00** POST FREE + 30p V.A.T.

**MASTER VOLUME/TONE CONTROLS/4 CHANNEL  
 BALANCE CONTROL BOARD**

COMPLETE KIT **£8.50** POST FREE + 85p V.A.T.

**POWER AMPLIFIER BOARDS AND HEATSINKS**

(EACH BOARD CONTAINS A STEREO PAIR OF AMPLIFIERS)

COMPLETE KIT PER BOARD **£7.50** POST FREE + 75p V.A.T.

ALL OTHER KITS AND COMPONENTS USED IN THE P.E. RONDO WILL BE AVAILABLE AS THEY APPEAR IN THIS SERIES.

KITS ARE COMPLETE IN EVERY DETAIL (RIGHT DOWN TO THE SOLDER) AND USE ONLY TOP QUALITY COMPONENTS AND FIBREGLASS P.C.Bs.

\* TRADE ENQUIRIES WELCOME

**SONAX ELECTRONICS**

SPENCER HOUSE, BRETENHAM ROAD, EDMONTON  
 LONDON, N.18 TEL. 01-807 5544

Please send me:

CBS SQ DECODER  
 PREAMPLIFIER BOARD  
 MASTER VOL/TONE/4 CHANNEL BOARD  
 POWER AMPLIFIER BOARD(S)

Please tick

CHEQUE  
 P O  
 MONEY ORDER  
 MONEY ENCLOSED £ .....

NAME .....

ADDRESS .....

Block capitals please P.E.10

# NEW VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.

## 74 Series TTL

INTERNATIONALLY KNOWN BRANDS  
1st GRADE DEVICES AT NEW  
ROCK BOTTOM PRICES

SN7400	16p	SN7473	40p
SN7401	16p	SN7474	40p
SN7402	18p	SN7475	50p
SN7410	17p	SN7476	44p
SN7413	30p	SN7490	69p
SN7420	16p	SN7492	74p
SN7447	99p	SN7493	74p

This range will be increased continuously. Please enquire about any devices not listed.

## PRICE BARRIER SLASHED

# LED READOUTS



£1.99 + 20p VAT = £2.19



	Copperclad	Plain	Extra
2pin x 1in	61p	61p	—
2pin x 3in	22p	26p	11p
2pin x 5in	26p	23p	—
3pin x 3in	29p	23p	—
3pin x 5in	30p	30p	19p
17in x 2in	74p	55p	41p
17in x 3in	99p	77p	57p
17in x 5in	—	—	82p

## I.C. SOCKETS



Dual-in-Line		
8 pin	13p	16 pin 17p
14 pin	15p	24 pin 26p
		36 pin 39p
		40 pin 44p
		28 pin 30p

## HEAT SINKS

TV2 for TO-66	15p	5F for TO-5	—
TV3 for TO-3	16p	18F for TO-18	—




TV4 for TO-126	—	DIP10 2 for SL403D	—
TV5 for TO-220	—	DIP14, 5 for EA1000	—



10DN400	46p	4Y-1	35p
---------	-----	------	-----

## BRIDGE RECTIFIERS

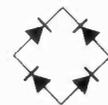


P.I.V.	1 amp	R.M.S.	2 amp
100V	20p	50V	35p
200V	22p	100V	40p
600V	25p	200V	45p
1000V	38p	600V	50p

## RECTIFIERS

P.I.V.	1 amp	3 amp
50	1N4001 63p	1N5400 15p
100	1N4002 71p	1N5401 16p
200	1N4003 9p	1N5402 17p
400	1N4004 9p	1N5404 22p
600	1N4005 11p	1N5406 26p
800	1N4006 13p	1N5407 30p
1000	1N4007 16p	1N5408 33p

BY100	163p	BY133	23p
BY103	22p	BY164	55p
BY105	163p	BY176	£1.65
BY126	16p	BY182	£1.65
BY127	163p	BY250	25p

## OR FILAMENT INDICATOR

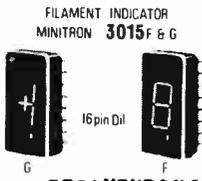

at **BREAKTHROUGH PRICE £1.49**

## Cheapest Opto yet

Goasp LED's



Remember **Vat Inclusive Prices**

## DIGITAL CLOCK



on a chip

Just imagine, one MOS LSI I.C. eliminating 15 MSI I.C.s. and numerous other components. Either 12 or 24 hour, 4 or 6 digit 50 or 60Hz operation leading zero suppression single voltage supply similar to DIGITRONIC in P.W. March 1973. Only **£6.99**

With 4 LED's £15.59  
With 6 LED's £19.75

# CHROMASONIC electronics

## RESISTORS

Rating	Type	Tolerance	Range	Price Each
1/4 watt	Metal Glaze	±5%	E12 Series 51Ω to 100KΩ	5p
1/2 watt	Carbon Film	±5%	E24 Series 51Ω to 330KΩ	11p
1 watt	Metal Oxide Film	±2%	E24 Series 10Ω to 1MΩ	11p
1/2 watt	'Cermet' Thick Film	±2%	E12 Series 56Ω to 150KΩ	8p
1 watt	Carbon Film	±5%	E24 Series 10Ω to 10MΩ	14p
1 watt	Carbon Composition	±0.5Ω	2.2Ω, 2.7Ω, 3.3Ω, 3.9Ω, 4.7Ω	44p
1 watt	Carbon Composition	±10%	5.6Ω, 6.8Ω, 8.2Ω	54p
2 watt	Carbon Film	±10%	E12 Series 10Ω to 10MΩ	3p
2 watt	Carbon Film	±10%	E12 Series 10Ω to 10MΩ	6p
2 1/2 watt	Wire Wound	±5%	E12 Series 0.22Ω to 0.47Ω	10p
2 1/2 watt	Wire Wound	±10%	E12 Series 10Ω to 270Ω	10p
5 watt	Wire Wound	±5%	0.5Ω to 8.2KΩ	10p
10 watt	Wire Wound	±10%	0.5Ω to 6.8KΩ	11p
10 watt	Wire Wound	±5%	10KΩ, 15KΩ, 20KΩ, 25KΩ	17p
15 watt	Wire Wound	±5%	10Ω to 6.8KΩ	13p

DISCOUNTS 10% on any 100 Mixed Values or wattages, 25% on any 100, same value, same wattage. Postage and Packing—Extra 8p any quantity.

## CAPACITORS

Value	Price
MULLARD C333, 629 and 630 series	—Ceramic Plate, E12 series from 1.8pF to 0.022μF, 53p.
CERAMIC DISC—LOW VOLTAGE—	0.01μF, 0.022μF, 0.047μF, 53p; 0.04μF, 0.22μF, 0.47μF, 63p.
POLYSTYRENE (160V)—From 10pF to 0.01μF in multiples of 10pF, 15pF, 22pF, 33pF, 47pF and 68pF 53p.	
MYLAR PLATE (100V)—1000 pF, 2000pF, 5000pF, 21p; 0.01μF, 0.02μF, 0.04μF, 0.05μF, 33p; 0.068μF, 0.1μF, 5p; 0.2μF, 63p.	
MULLARD C280 (250V POLYESTER)	—0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 33p; 0.022μF, 0.1μF, 0.15μF, 43p; 0.22μF, 53p; 0.33μF, 7p; 0.47μF, 9p; 0.68μF, 12p; 1.0μF, 14p; 1.5μF, 22p; 2.2μF, 26p.

## new stabilised

### POWER PACK/ CONVERTER

Switched 3, 6, 7 1/2 or 9 volts. Up to 400mA Output



Our Price £3.99 + P. & P. 16p. Unstabilised Version of above

Output	Price
6 volts at up to 50mA	£1.65
9 volts at up to 50mA	£1.65
9 volts (miniature) up to 50mA	£2.09
6 + 6 volts at up to 50mA	£2.75
9 + 9 volts at up to 50mA	£2.75
7 1/2 volts for Cassette Players (small)	£2.20
3, 4 1/2, 6, 7 1/2, 9, 12 volts up to 1A	£3.75
Fully Stabilised* Car Battery Converter, giving switched outputs of 6, 7 1/2 or 9 volts	£5.49

## ZENERS

Value	Price
BZY88, 400mW, 3.3V to 33V	11p
1ZS, 1W, 3.3V to 100V	18p
BZX70, 2.5W, 7.5V to 75V	27p

## TRANSISTORS and DIODES

Part No.	Price	Part No.	Price
AC107	16p	AF179	71p
AC126	13p	AF238	41p
AC127	13p	ASV26	33p
AC128	13p	BC107	9p
AC176	15p	BC108	9p
AC187	20p	BC114	15p
AC187K	20p	BC115	15p
AC188	20p	BC117	22p
AC188K	20p	BC147	9p
AC174	24p	BC172	12p
AC198	21p	BC149	9p
AC198K	21p	BC157	13p
AC199	22p	BC158	12p
AC199K	22p	BC159	14p
AD146	30p	BC168B	30p
AD161	25p	BC169	12p
AD162	25p	BC171	20p
AD161/2 PR	25p	BC172	17p
AD140	40p	BC173	14p
AF114	14p	BC174B	78p
AF115	14p	BC177	22p
AF116	14p	BC178	22p
AF117	14p	BC179	24p
AF118	9p	BC203	11p
AF124	9p	BC183L	9p
AF125	22p	BC184	9p
AF126	22p	BC184L	9p
AF127	35p	BC187	27p
AF172	25p	BC213L	11p
BF177	26p	BSX20	18p
BF178	26p	BSX21	22p
BF179	33p	BSY55A	13p
BF180	33p	BU105	£1.75
BF181	35p	BU105/02	£1.92
BF184	27p	BU105	£2.10
BF185	27p	MJ4000	£1.49
BF194	15p	MJ4010	£1.49
BF195	17p	MJE340	52p
BF196	16p	MJE355	36p
BF197	16p	MJE365	82p
BF200	35p	MPF102	27p
BF220	27p	MPF103	41p
BF228	£1.91	MPF104	45p
BF263	25p	MPF105	45p
BF263	25p	MPF106	45p
BF272	£1.21	OC28	36p
BF380	37p	OC35	38p
BF328	£1.91	OC36	38p
BFW10	13p	OC44	13p
BFW11	87p	OC45	13p
BFW87	38p	OC71	13p
BFX25	43p	OC72	13p
BFX30	37p	OC75	15p
BFX88	26p	OC81	13p
BFY50	18p	OC83	22p
BFY51	16p	OC94	22p
BR100	43p	OC170	27p
BRY39	44p	OC171	33p
TC44	46p	TC220D	£1.87
TP14A	81p	TP42A	99p
2N3054	55p	2N3055	55p
2N3055	55p	2N3056	18p
2N3056	18p	2N3057	11p
2N3057	11p	2N3058	11p
2N3058	11p	2N3059	11p
2N3059	11p	2N3060	11p
2N3129	11p	2N3130	11p

# VAT INVOICES ON REQUEST

UNLESS SHOWN OTHERWISE P&P ON U.K. ORDERS IS 8p. OVERSEAS ORDERS AT COST



<p><b>Mullard LP1186</b> Varactor diode tuned F.M. tuning heart. £4-15, as described in P.E. May 1973. LP1185 matching I.F. strip. £4-85.</p>	<p><b>THE TEXAN</b> 20 + 20 Watt Integrated Stereo Amplifier Kit. Superb state-of-the-art design by engineers of Texas Instruments. £31-35 + P &amp; P 49p.</p>	<p><b>SGS EA1000</b> 3 watt amplifier module. Price including handbook and FREE heatsink. Our price £2-49. Quantity discounts.</p>	<p><b>A10055</b> F.M. tuner chassis fully transistorised. 9 Volt positive earth operation. Our Price £6-35.</p>	<p><b>A1018</b> F.M. tuner, similar to A10055 but in oiled walnut cabinet, etc. Our Price £9-38.</p>	<p><b>A1005MS</b> Multiplex Stereo Decoder, fully built and aligned, to match A10055. Our Price £5-95.</p>
---	---	--	---	--	--


## AUDIO I.C.'S

Audio I.C. Leaflet No. 12. FREE (only with I.C.'s—10p separately).

- Pre-Amplifiers**  
Dual. MC1303L £1-89  
Low Noise Dual. MC1339P £1-29
- Amplifiers**  
250mW. MFC4000A 49p
- 1 watt. TAA300 £1-79  
2 watt. LM380 £1-59  
3 watt. SL403D £1-65  
5 watt. TBA800 £1-59  
15 watt. BHA0002 £3-95  
35 watt driver. NE540L £1-32



## 3 1/2 decade DVM

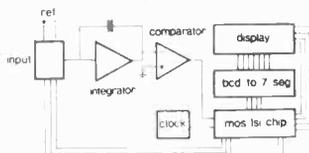


Supplied with complete data. All this on a single 16 pin DIL packed MOS LSI integrated circuit.

A State-of-the-Art Digital Voltmeter I.C. for only £7-79

- Maximum Display - or - 1.999V
- Minimum Display - or - 1mV
- Can be scaled up to read 1.999V
- Automatic Polarity Detection
- Dual Ramp Integration
- Automatic Overrange Indication
- Up to 50 readings per second
- Chopper Output provided

## Linears

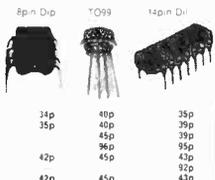

709	35p	40p	35p
710	35p	40p	39p
711	45p	39p	39p
723	96p	96p	96p
741	42p	45p	43p
747			93p
748	42p	45p	43p
CA3046	95p	MVR5V(L005)	£1-65
CA3075	£1-85	MVR12V(L036)	£1-65
CA3082	£1-65	MVR15V(L037)	£1-29
LM101H	£1-99	NE555	92p
LM301H	£1-15	NE560B	£4-99
LM4031	£1-05	NE561B	£4-92
LM307N	86p	NE562B	£4-92
LM108N	£1-45	NE565	£3-49
LM109K	£2-68	NE568	£2-75
LM1300	77p	NE567	£3-49
MC1330	89p	SQ3402N	£3-08
MC1350	83p	SL440	£2-29
MC1351	£1-10	TAA263	99p
MC1352	£1-10	TAA293	99p
MC1357	£1-59	TAA310	£1-27
MC1358	£1-69	TAA320	99p
MC1586CP	£1-75	TAA350	£2-54
MC1496N	77p	TA1000	£5-15
MC1495	£5-65	TAA570	81p
MC1498N	£1-49	TAA570	£1-85
MC3001	77p	TA1000	£4-49
MFC4010A	51p	TAD100	£1-65
MFC4060	78p	TAD110	£1-65
MFC5030A	83p	TA568	£1-65
MFC6040	£1-10	ULN2111A	£1-59

## Coil-less Phase-Locked Loop I.C. Stereo Decoder

MC1312 decodes CBS SQ. Free leaflet No. 11 gives full circuit and details. Our Price £6-49

Motorola MC1310, supplied complete with our FREE leaflet No. 11. Our Price £3.05

# QUADRISONICS

inc. all parts for decoder. inc. Veroboard, V.A.T., P & P (Leaflet alone 10p.)

the component people

Dept. 2.  
56, Fortis Green Road, London, N10 3HN.  
telephone: 883 3705

## INDUCTORS

MULLARD block filter LP1175 as used with TAD100 now only £1-49

R.F. CHOKES, 0.1µH to 19mH. For full details ask for List No. 5. P & P 5p.

## DENCO COILS

**Transistor Range:** Series 1T to 5T inclusive. Blue, Yellow, Red and White all 44p each.

**I.F. Transformers:** IFT13, 14, 16 and 17. 55p each. IFT 15, 76p; IFT18, 73p.



**Dual Purpose Range:** Series 1 to 7 inc. Blue, Yellow, Red and White. 44p each. 1 to 5 Green. List No 5 gives full details.

**Ferrite Aerials:** Medium and Long—state 300pF or 500pF tuning. 87p each.

## Tuning Gangs



Type C804  
5pF 61p 50pF 66p 365pF  
10pF 61p 60pF 79p 365 - 365pF  
15pF 61p 75pF 79p  
20pF 66p 100pF 75p  
25pF 61p

Type 0  
80p  
96p

Type 00  
208 - 176pF with screen and trimmers  
99p

P & P all types 10p

## NEW FERRANTI RANGE

### ZN414

The Radio I.C. in a TO18 can. Supplied with our data leaflet No. 10. Giving circuits and component information. (Leaflet alone 10p.)

BFS59	15p	ZTX302	17p	ZTX450	17p	ZS121	10p	ZS272	18p
BFS60	20p	ZTX303	14p	ZTX451	17p	ZS122	13p	ZS274	19p
BFS61	20p	ZTX304	21p	ZTX500	12p	ZS123	16p	ZS276	26p
BFS96	15p	ZTX310	9p	ZTX501	13p	ZS124	18p	ZS278	37p
BFS97	23p	ZTX311	10p	ZTX502	17p	ZS140	25p		
BFS98	20p	ZTX312	10p	ZTX503	14p	ZS141	43p		
		ZTX313	11p	ZTX504	43p	ZS142	33p		
		ZTX314	13p	ZTX510	17p	ZS170	10p		
ZTX107	9p	ZTX320	31p	ZTX530	21p	ZS171	13p		
ZTX108	8p	ZTX330	15p	ZTX531	22p	ZS172	16p		
ZTX109	11p	ZTX331	16p	ZTX550	17p	ZS174	17p		
ZTX212	14p	ZTX341	22p	ZTX551	17p	ZS176	23p		
ZTX213	14p	ZTX382	13p			ZS178	38p		
ZTX214	15p	ZTX383	15p			ZS270	11p		
ZTX300	12p	ZTX384	18p			ZS120	8p		
ZTX301	13p								

Our Price £1.32

KSO30A Zener Series BZV88 Series 11p each.

## ELECTROLYTICS

µF	-4V	6.3V	10V	16V	25V	40V	63V	100V
1							61p	8p
1.5							61p	8p
2.2							61p	8p
3.3							61p	8p
4.7							61p	8p
6.8							61p	9p
10							61p	9p
15							61p	11p
22							61p	11p
33							61p	11p
47	61p						61p	11p
68	61p	61p					10p	
100	61p	61p	61p				10p	23p
150	61p	61p	61p	61p			10p	31p
220	61p	61p	61p	8p	10p		11p	31p
330	61p			8p	19p	22p	22p	39p
470		61p	10p	10p	19p	26p	48p	47p
680		10p	10p	11p	20p	23p	59p	59p
1000		10p	12p	20p	22p	25p	44p	79p
1500								
2200		18p	20p		36p	44p	79p	149p
3300		20p						
4700	29p				44p	68p	79p	252p
6800					75p	93p		
10000							299p	333p

## Potentiometers

5kΩ	250kΩ	
10kΩ	500kΩ	
25kΩ	1MΩ	
50kΩ	2MΩ	
100kΩ		

Log or lin less switch (and 1kΩ lin) 13p  
Log or lin with switch 26p  
Dual less switch 44p  
Dual with switch 10kΩ, 100kΩ and 1MΩ. log only 57p  
10kΩ log + 10kΩ antilog less switch 44p

10kΩ	Single
25kΩ	33p
50kΩ	Dual
100kΩ	55p

New Silver and Black Knob 16p

## Presets

0.1 watt	51p	0.25 watt	7p
100Ω	1kΩ	10kΩ	100kΩ
250Ω	2.5kΩ	25kΩ	250kΩ
500Ω	5kΩ	50kΩ	500kΩ

Germet Type to 1MΩ only 41p.

## VDR's & Thermistors

A15B	82p	GL23	£1-10
C21	161p	RS3	£1-49
C24	141p	RS4	£1-61
C213A	141p	VA1005	161p
CZ19	141p	VA1026	141p
E298CD A258	11p	VA1033	11p
E298ED A258	11p	VA1034	11p
E298ED A260	11p	VA1039	161p
E298ED A262	11p	VA1040	11p
E298ED A265	11p	VA1053	11p
E298ED P268	11p	VA1055S	11p
E298Z 05	13p	VA1096S	11p
E298Z 06	11p	VA1065S	11p
E299DD P336	11p	VA1067S	11p
E299DD P338	11p	VA1077	141p
E299DD P342	11p	VA1098	21p
E299DD P348	11p	VA1104	25p
GL16	£1-10	VA1107	29p

Other types obtainable upon application

# DISCOUNTS UP TO

# 60%

## FULL 12 MONTH AFTER SALES SERVICE

with probably the best discounts offered in the U.K.

ALL PRICES ARE INCLUSIVE OF V.A.T.

### FANTASTIC OFFER

#### GARRARD SP25 Mk. III

Goldring G800 Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1.75 for P. & P. and Ins.

**£15.20**

### TURNTABLES

Please add 95p P. & P. & Ins.

B5R MP60	£9.15
Garrard SP25 Mk.III	£9.50
Garrard SL65B	£13.25
Garrard AP76	£17.95
Garrard 401	£24.85
Garrard Zero 100 single	£33.55
Garrard Zero 100 auto	£36.50
Goldring G185P & C	£59.35
Goldring G101P P & C	£19.40
Goldring GL72	£21.95
Goldring GL72/P	£28.55
Goldring GL75	£27.40
Goldring GL75P	£33.90
Goldring GL75 Lid	£3.85
Leak Delta	£44.20
Pioneer PL12D	£35.10
Thorens TD12S	£58.55
Thorens TD12S AB Mk.II	£89.50
Thorens TD160 AB & C	£49.30
Wharfedale Linton with cart.	£25.00

### TUNERS

Please add 93p P. & P. & Ins.

Alpha Highgate FT150	£33.30
Amstrad Multiplex 3000	£24.90
Leak Delta FM (Cased)	£47.45
Leak Delta AM/FM	£35.90
Metrosound FMS 20 Mk.II	£38.35
Rogers R/brook FET4 (Cha)	£29.50
Rogers R/brook FET4 (Cased)	£31.90
Rogers R/bourne FET4 (Cased)	£41.25
Sinclair PRO60 Mod	£14.90
Sinclair cased tuner	£26.15

### TUNER AMPLIFIERS

Please add £1.10 P. & P. & Ins.

Alpha FR3000	£61.35
Goodmans Module 80	£59.90
Goodmans Mod 80 Com	£106.00
Goodmans Mod 90	£74.65
Goodmans One-Ten	£86.65
Leak Delta 75	£107.75
Rogers R/Brook cha	£62.30
Rotel 150A	£45.90
Rotel 200A	£58.95

All prices correct at time of press. E. & O.E. and are subject to alterations.

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE10), 174 Pentonville Road, London, N.1. Tel. 01-278 1769  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue Ilford, Essex. Tel. 01-550 1086

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

### PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc. of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2in x 4 1/2in x 2 1/2in approx.

Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £12.10.

### PSYCHEDELIC LIGHTING UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £27.50 carr. paid.

ALL PRICES INCLUDE V.A.T. AND U.K. POST

### DABAR ELECTRONIC PRODUCTS

98a Lichfield Street, Walsall, Staffs. WS1 1UZ

TELEPHONE: WALSALL 34365

TELEGRAMS: DABELEC Walsall Staffs.

## STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72) MOTOROLA MC1310P

### EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz-15kHz, Distortion: 0.3%, I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED. Simple to build.

**KIT COMPRISES FIBREGLASS PCB** (Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only £3.40 post free + V.A.T.

**LIGHT EMITTING DIODE (Red)** Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only 29p + p.p. + V.A.T.

**MC1310P only £2.77 + p.p. 6p + V.A.T.**  
**14 PIN DIL SOCKETS. 16p each + V.A.T.**

**NOTE**—As the supplier of the original decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

### Fi-Comp Electronics

BURTON ROAD, EGGINTON, DERBY DE6 6GY

## WINDSCREEN WIPER DELAY KIT

Complete kit of parts including drilled and tinned fibreglass printed circuit board.

The unit provides intermittent wiper operation with a delay up to approximately 60 seconds which can be varied to optimise visibility in conditions of light rain, spray, etc. The original wiper switch overrides when normal operation is required.

Suitable for most British cars

£2.86 inc. V.A.T. and P.&P.

ESSEX X-RAY CO. LTD.

Cash with order

57 THEYDON PARK RD.

THEYDON BOIS, EPPING, ESSEX CM16 7LR

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

## COMPLETE TELEPHONES



EX G.P.O. NORMAL  
HOUSEHOLD TYPE

**ONLY £1.05**

POST & PACKING 45p EACH



## TELEPHONE DIALS

Standard Post Office type.  
Guaranteed in working order.

**ONLY 27½p**

POST & PACKING 16½p

## TESTED AND GUARANTEED PAKS

B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long dia. Highspeed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight Post & packing 15p.	55p
H4	250	Mixed Resistors. Approx. quantity counted by weight Post & packing 15p.	55p
H7	40	Wirewound Resistors. Mixed types and values	55p
H9	2	OCPT1 Light Sensitive Photo Transistor	55p
H28	20	OC2001/2/3 PNP Silicon uncoded TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short Lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon uncoded TO-5	55p
H41	2	BD131/BD132 Complimentary Plastic Transistors	55p

## UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Recti- fiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Recti- fiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1.10 each**



OVER  
**1,000,000**

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

## SILICON PLANAR PLASTIC TRANSISTORS

Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44.

P & P 11p per 1,000

## OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.  
TYPE "G" NPN Silicon, similar ZTX300 range.  
TYPE "H" PNP Silicon, similar ZTX500 range.

RELAYS FOR  
8 VARIOUS TYPES **£1.10**  
P & P 27½p

## Our famous PI Pak is still leading in value for money

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors NPN and PNP, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P.I. Only 55p. 11p P & P on this Pak.



## A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

**This complete kit of parts costs £3.85, post paid.**

**A MUST for Colour T.V. Alignment.**

## Electronic Transistor Ignition

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

**Complete kit including P. & P. £7.92**  
**Ready built & tested unit £3.02 EXTRA**

## FREE CATALOGUE FOR



TRANSISTORS,  
RECTIFIERS,  
DIODES,  
INTEGRATED  
CIRCUITS,  
FULL PRE-PAK  
LISTS

## PLASTIC POWER TRANSISTORS NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min. 15	HFE Min. 15	1-12	13-25	26-50
40 watt	22p	20p	18p		
90 watt	26½p	24½p	22p		
Range 2	VCE Min. 40	HFE Min. 40	1-12	13-25	26-50
40 watt	33p	31p	29p		
90 watt	38½p	36½p	33p		

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

**INTEGRATED CIRCUITS.** We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

**METRICATION CHARTS** now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

## LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each } Now new low  
16 pin type at 18p each } profile type.

## BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:  
**B.P.I. Transistor Equivalents and Substitutes:** 40p  
This includes many thousands of British, U.S.A., European and C.V. equivalents.  
**The Hi-Fi Radio Valve & Transistor Data Book 9th Edition:** P & P 23½p 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications.

**N.B.—Books are void of V.A.T.**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....

ADDRESS .....

**ALL PRICES INCLUDE 10% V.A.T.**

**MINIMUM ORDER 55p. CASH WITH ORDER PLEASE.** Add 11p post and packing per order. **OVERSEAS ADD EXTRA FOR POSTAGE.**

# BI-PRE-PAK LTD

Co. Reg. No. 820919

DEPT. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344



GIRO NO. 331 7056  
C.W.O. only P. & P. 10p on orders below £5  
Discount: £10-10%, £20-15% (except net items)  
Export Order enquiries welcome (VAT free)

Official Orders accepted from  
Educational & Government Departments  
**ALL PRICES INCLUDE VAT**

**SPECIAL RESISTOR KITS**

10E12 1/2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3-10 net  
10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3-20 net  
25E12 1/2W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7-20 net  
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7-35 net  
20E12 1/2W KIT: 20 of each E12 value, 10 ohms—1M, a total of 1220 (METAL FILM 5%), £7-50 net  
15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £8-15 net  
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £12-65 net

**MULLARD POLYESTER CAPACITORS C280 SERIES**

250V P.C. Mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 3½p. 0-068µF, 0-1µF, 4½p. 0-15µF, 4½p. 0-22µF, 5½p. 0-33µF, 8p. 0-47µF, 9p. 0-68µF, 11p. 1µF, 15p. 1-5µF, 22p. 2-2µF, 25p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**

400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2½p. 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3½p. 0-047µF, 4½p. 0-068µF, 0-1µF, 4½p. 0-15µF, 6½p. 0-22µF, 8½p. 0-33µF, 12p. 0-47µF, 14p.  
160V: 0-01µF, 0-015µF, 0-022µF, 2½p. 0-047µF, 0-068µF, 3½p. 0-1µF, 0-15µF, 4½p. 0-22µF, 5p. 0-33µF, 6p. 0-47µF, 7½p. 0-68µF, 11p. 1µF, 12½p.

**MINIATURE CERAMIC PLATE CAPACITORS**

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0-01, 0-015, 0-022, 0-033, 0-047, 2½p. each. 0-1, 30V, 4½p.; 0-1, 100V, 5½p.

**POLYSTYRENE CAPACITORS 160V 5%**

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p. 6800, 10,000, 4½p.

**RESISTORS**

CF—High Stab Carbon Film, 5%	MF—High Stab Metal Film, 5%
W, Type Range	1-9 10-49 50-99 100-249 250-499 500-999 1000+
1/2 CF 22-2M2	1 0-8 0-65 0-62 0-55 0-5 0-45 3-9x10-5
1/2 CF 22-2M2	1 0-8 0-65 0-62 0-55 0-5 0-45 5-5x16
1/2 MF 10-2M7	1 0-9 0-8 0-7 0-65 0-65 0-6 3x7
1/2 MF 10-2M2	1 0-9 0-8 0-7 0-65 0-65 0-6 4-2x10-8
2 MF 10-10M1	5 1-25 1-25 1 1 0-95 0-88 6-6x13
2 MF 10-10M3	2 5 2 5 1 1-75 1 75 1-6 8x17-5

For value mixing prices, please refer to our catalogue (price in pence each)  
VALUES AVAILABLE—E12 Series only

**PRESET SKELETON POTENTIOMETERS**

MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω  
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each

**B. H. COMPONENT FACTORS LTD.**

(P.W.) 61 CHEDDINGTON ROAD, PITSTONE,  
NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ  
Tel.: Cheddington 668446 (Std. Code 0296)  
PLEASE WRITE FOR FREE CATALOGUE

**Miniature Mullard Electrolytics**

1-0µF 63V 6p	68µF 16V 6p
1-5µF 63V 6p	68µF 63V 12p
2-2µF 63V 6p	100µF 10V 6p
3-3µF 63V 6p	100µF 25V 6p
4-0µF 63V 6p	100µF 63V 14p
4-7µF 63V 6p	150µF 16V 6p
6-8µF 63V 6p	150µF 63V 15p
8-0µF 40V 6p	220µF 6V 4p
10µF 16V 6p	220µF 10V 6p
10µF 25V 6p	220µF 16V 8p
10µF 63V 6p	220µF 63V 21p
15µF 16V 6p	330µF 16V 12p
15µF 63V 6p	330µF 63V 25p
16µF 40V 6p	470µF 6-4V 9p
22µF 25V 6p	470µF 40V 20p
22µF 63V 6p	680µF 16V 15p
32µF 10V 6p	680µF 40V 25p
33µF 16V 6p	1000µF 16V 20p
33µF 40V 6p	1000µF 25V 25p
32µF 63V 6p	1500µF 6-4 15p
47µF 10V 6p	1500µF 16V 25p
47µF 25V 6p	2200µF 10V 25p
47µF 63V 8p	3300µF 6-4 26p

**VEROBOARD 0-1-0-15**

2½ x 5"	28p 28p
2½ x 3½"	24p 19p
3½ x 5"	32p 33p
3½ x 3½"	28p 28p
2½ x 1"	7p 7p
2½ x 5" (Plain)	— 14p
2½ x 3½" (Plain)	— 12p
5 x 3½" (Plain)	— 22p
Insertion tool 59p 59p	
Track Cutter 44p 44p	
Pins, Ckt. 25 10p 10p	

**TRANSISTORS**

AC127 16½p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	TI543 23p
BC183L 12p	2N2926 11p
BC184L 13p	2N3702 11p

**POTENTIOMETERS**

Carbon Track 5K Ω to 2M Ω, log or linear. Single, 16½p Dual Gang 46p. Log Single with DP switch 26p

**DIODES**

IN4001 6½p
IN4002 7½p
IN4003 9p
IN4004 9½p
IN4005 12p
IN4006 14p
IN914 7p
IN916 7p
BA100 10p
OA5 45p
OA47 9p
OA81 11p
OA200 8p

**PLUGS**

DIN 2 Pin 12p
3 Pin 13p
5 Pin 180° 15p
Std. Jack 14½p
2.5mm Jack 11p
Phono 5½p

**SOCKETS**

DIN 2 Pin 10p
3 Pin 10p
5 Pin 180° 12p
Std. Jack 14½p
2.5mm Jack 11p
Phono 5½p

**ELECTROLYTIC CAPACITORS. Tubular & Large Cans**


(µF/V): 2-2/25, 2-2/63, 4-7/10, 4-7/25, 4-7/63, 22/10, 22/25, 22/63, 5p. 210, 50/10, 50/10, 100/10, 100/25, 50/25, 10/50, 5½p.  
200/10, 100/25, 50/50, 6½p. 500/10, 200/25, 100/50, 9p. 1000/10, 500/25, 200/50, 11p. 2000/10, 1000/25, 500/50, 16½p. 1000/50, 39p. 1000/100, 66p. 2000/25, 27p. 2500/12, 17p. 2500/25, 33p. 2500/50, 62p. 3000/50, 72p. 5000/25, 66p. 5000/50, 94p. 7000/50, 60p. 25,000/25, 74p. HI-VOLT: 8/350, 14p. 16/350, 19p. 32/350, 25p. 50/250, 18p. 100/500, 33p.

**METALLISED PAPER CAPACITORS**

250V: 0-05µF, 0-1µF 4½p, 0-25µF, 5½p, 0-5µF, 6½p, 1µF, 9p.  
500V: 0-025µF, 0-05µF, 4½p, 0-1µF, 5½p, 0-25µF, 6½p, 0-5µF, 9p.  
1000V: 0-01µF, 10p, 0-022µF, 12p, 0-047µF, 0-1µF, 16p, 0-22µF, 37p, 0-47µF, 39p.

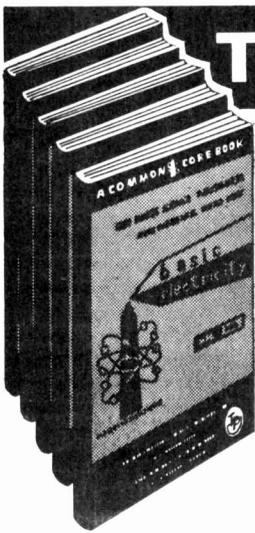**QUANTITY DISCOUNT**

SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS AND TRADE



**The Pictorial Method**

**BASIC ELECTRICITY (5 vols)**  
**BASIC ELECTRONICS (6 vols)**  
**TELEVISION (3 vols)**

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR 100% GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

**WHAT READERS SAY**

Having studied the first volume I find that learning about a subject which seemed almost out of reach has now become a relatively simple matter.  
*H.F., Coventry*

I am extremely satisfied with these fine books.  
*C.K., Swindon*

I would like to say how easy your books are to study.  
*B.B., London*

I purchased Basic Electricity and I have found them to be the best books of their kind that I have ever read. Will you please send Basic Electronics.  
*G.S., Portsmouth*

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £4.50
- BASIC ELECTRONICS 6 parts £5.40
- BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

**YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.**

NAME .....

BLOCK LETTERS

FULL POSTAL.....

ADDRESS .....

**POST NOW FOR THIS OFFER!**

# SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT. NEW & SECONDHAND MUSICAL INSTRUMENTS. DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES

## Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.



To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.

**SA35** 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

### A NEW ADDITION IS THE SA50 at £5.65

Carr. paid. A rugged, well built unit, capable of 50W RMS out, with all the advantages of Saxon Amplifier design and quality. Ready now.

## SA100 makes an ideal unit in disco assemblies

A real gluton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10.90**

### BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0.2% at 1kHz	
Loads	4 to 16 ohms	
Quiescent current	15mA	
Noise	Better than -75dB	
Supply voltage	SA25-45V SA50 45/65V SA100 40-70V	
Size	4 1/2 in × 4 in × 1 in (SA100) 4 in × 3 in × 1 in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's	£4.90
PU70	Unstabilised supply for one or two SA100	£7.75 carr. 40p
PS45	Stabilised module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

## TWO NEW PA/MIXER CONTROL UNITS

Built for hard work!

In extra slimline easy-fit case.

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

- HIGH AND LOW IMPEDANCE INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL ON OUTPUT

### CONTROL UNITS

Mono (as shown). **£6.50**  
Carr. 20p.  
Stereo. **£15.80**  
Carr. 30p.



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2 in × 3 in × 4 in deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic. Input.)

● **M4H**  
4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" × 8" and only 2 1/2 in deep. Carr. paid. **£18.50 + V.A.T.**

● **M6HL**  
12 inputs (6 high Z, 6 low Z). Carr. paid 18" × 8" × 2 1/2". **£27.50 + V.A.T.**

Channel section modules, for building your own: gain—16 × (24dB) Tone controls—18dB swing. Carr. paid. **£3.50 + V.A.T.**

PLEASE ADD 10% FOR V.A.T. TO TOTAL VALUE OF YOUR ORDER

S.A.E. brings Saxon equipment and bargains list

● 160 watts version with power supply (Carr. 50p) **£27.90**

### 120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

<b>SPECIFICATION</b>	
Power output, 120W into 8 ohms	Module only <b>£13.90</b>
Freq. response, 20-20,000Hz ± 2dB	(Carr. 20p)
Input sensitivity, 200mV into 10K	
(Construction, Fibreglass board)	
Size, 8 in × 4 in × 4 in (5 in with supply)	Module and power supply <b>£18.95</b>
Low distortion parallel push-pull output stage.	(Carr. 40p)



### 3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for splice leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p. **£19.75**

### SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.


### SINGLE CHANNEL UNIT

Operates from 5-100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£8.90**
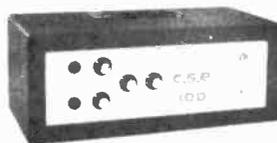
### COMPLETE AMPLIFIERS

**CSE 100** £34.90 carr. free

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.



### SAXON 100

£48.50 carr. free



With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

### LOUDSPEAKERS British made bargains!!

12 in 25W 8/15 ohms £5.95 carr. 30p. 15 in 50W 8/15 ohm £14.50 carr. 30p. 12 in 40W 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p. 600 Watt 3 colour Light Boxes Smart Roxine finish £15 carr. free.

### A.K.G. MICROPHONES

D11 DHL IDEAL DISCO MIKE ONLY £9.45 (rrp £11.00). S.A.E. for special price list.

Order and personal shoppers to:  
**SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS**  
Telephone 01-684 6385  
From 9.30 a.m.-5.30 p.m.  
Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T.  
**TRADE AND EXPORT ENQUIRIES INVITED**

### TERMS OF BUSINESS

Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.

# Henry's

**UK'S LARGEST RANGE OF TRANSISTORS, IC'S  
RECTIFIERS, ALL SEMICONDUCTOR DEVICES  
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL**

## FREE BOOKLET

All types of  
TRANSISTORS · RECTIFIERS  
BRIDGES · SCR'S · TRIACS  
INTEGRATED CIRCUITS  
F.E.T. · LIGHT DEVICES  
OVER 1500 DIFFERENT DEVICES  
ENTIRELY NEW 1973 EDITION



MORE DEVICES  
NEW PRICES  
NEW RANGES  
THIS IS A MUST  
FOR ALL  
SEMI-CONDUCTOR  
USERS!

(ask for Booklet No. 36)

SEND FOR YOUR FREE COPY TODAY!

## INTEGRATED CIRCUITS

VERY IMPORTANT—ONLY BRANDED I.C.'S ARE TO THE FULL MANUFACTURERS' SPECIFICATIONS. ALL OTHERS ARE NOT. HENRY'S SELL ONLY BRANDED INTEGRATED CIRCUITS FROM THE MOST FAIRLY PRICED SIGNIFICANT SOURCES. SO WHY BUY ALTERNATIVES OR UNDER SPEC. DEVICES WHEN YOU CAN PURCHASE THE GENUINE ARTICLE FROM US EX STOCK... NEED WE SAY MORE!

Type	1-	12-	30-	Type	1-	12-	30-
SN7400N	20	18	16	SN7441AN	1.50	1.27	1.13
SN7401N	20	18	16	SN7442N	85	79	73
SN7401AN	38	38	33	SN7443N	1.50	1.27	1.13
SN7402N	20	18	16	SN7444N	1.50	1.27	1.13
SN7403AN	38	38	33	SN7445N	2.16	2.16	1.89
SN7404AN	24	21	18	SN7447AN	1.80	1.80	1.57
SN7405N	20	18	16	SN7448N	1.50	1.27	1.13
SN7406AN	44	44	38	SN7450N	20	18	16
SN7407N	40	38	35	SN7453N	20	18	16
SN7408N	25	22	19	SN7456N	20	18	16
SN7409N	33	33	28	SN7460N	20	18	16
SN7409AN	44	44	38	SN7470N	33	30	27
SN7410N	20	18	16	SN7472N	38	38	34
SN7411N	25	23	21	SN7473N	44	41	37
SN7412N	28	28	25	SN7474N	48	48	42
SN7413AN	38	38	33	SN7475N	59	55	51
SN7414N	30	27	25	SN7476N	45	38	32
SN7416N	30	27	25	SN7480N	80	70	50
SN7417N	30	27	25	SN7481N	1.25	1.10	95
SN7420N	20	18	16	SN7482N	87	80	72
SN7422N	28	28	25	SN7483N	1.20	1.10	1.00
SN7423AN	38	38	33	SN7485N	1.87	1.87	1.63
SN7425N	37	34	32	SN7486N	50	50	44
SN7425N	37	37	32	SN7489N	4.32	4.32	3.78
SN7427N	37	37	32	SN7490N	75	70	63
SN7428N	43	43	37	SN7491AN	1.10	1.00	90
SN7429N	20	18	16	SN7492N	75	70	63
SN7430N	37	37	32	SN7493N	75	70	63
SN7431AN	38	38	33	SN7494N	85	80	75
SN7432AN	37	37	32	SN7495N	50	50	44
SN7433AN	57	57	50	SN7496N	1.00	90	83
SN7437N	43	43	37	SN74100N	2.16	1.89	1.89
SN7438AN	43	43	37	SN74104AN	60	53	45
SN7438AN	57	57	50	SN74105N	60	53	45
SN7440N	20	18	16	SN74107N	51	51	45

PRICING OF SN7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX  
SN74 (HIGH POWER), SN74 (LOW POWER) series in stock. Send for List 36 free on request. Low Profile Sockets, 14 pin, 15p, 16 pin, 17p, 8 pin, 14p.

## TRANSISTORS—A selection

For full list send for booklet 36 today

£ p	£ p	£ p	£ p	£ p	£ p	£ p	£ p
AAZ13	10 BC169C	14 BY100	15 OC36	65 V405A	25 2N3614	59	
AC107	35 BC182	12 BY127	15 OC44	18 ZTX108	10 2N3702	11	
AC128	20 BCY32	85 BYZ13	35 OC45	18 ZTX300	14 2N3714	1.60	
AC187	20 BCY39	1.00 C106D	35 OC71	15 ZTX302	18 2N3771	1.75	
ACV17	35 BCY45	2.50 GET111	55 OC72	25 ZTX500	15 2N3773	2.25	
ACV39	65 BCY70	15 GET115	75 OC77	55 ZG300	15 2N3789	2.25	
AD149	50 BCY71	20 GET880	55 OC81	28 2N697	15 2N3819	35	
AD161	39 BCY72	13 LM309K1	87 OC83	25 2N706	10 2N3866	75	
AD162	39 BD124	80 MAT121	25 OC140	65 2N930	20 2N3903	15	
AF117	20 BD131	45 MJE340	50 OC170	25 2N987	45 2N4062	14	
AF118	50 BF115	22 MJE520	65 OC200	55 2N1132	25 2N4126	15	
AF139	33 BF180	33 MJE3055	75 OC202	90 2N1304	22 2N4271	35	
AF186	40 BF194	13 MPF105	46 OC271	50 2N1613	20 2N4547	36	
AF239	44 BFX13	25 NKT217	45 OP12	55 2N1671	1.00 2S001	3.00	
AS272	30 BFX34	55 NKT404	60 OP660	45 2N2147	75 2S026	8.90	
BA115	10 BFX88	22 OA5	60 P346A	20 2N2160	69 2S303	7.00	
BAX13	5 BFY50	20 OA81	10 TIL209	25 2N2925	10 40250	45	
BC107	12 BFY51	20 OA200	8 TP29A	49 2N3052	20 40361	45	
BC108	33 BFY84	45 CA205	75 TP30A	58 2N3054	45 40412	40	
BC109	12 BFY90	75 OC16	85 TP31A	61 2N3055	45 40408	50	
BC109C	14 BLF36	6.25 OC20	1.25 TP41A	74 2N3440	50 40486	75	
BC113	16 BSX20	15 OC28	65 TP42A	90 2N3442	1.00 40636	1.00	
BC147	12 BXU10	2.20 OC35	55 TIS43	26 2N3525	80 40430	85	

All types offered subject to availability. Prices correct at time of press. E. & O.E.

**TBA 800'S WATT I.C.**  
Suitable alternative to SL403D, 5/30 volt operated. 8/16 ohm 5 watt output. With circuits and data £1.50.



### SINCLAIR IC12

With circuits and data. 6 W IC with printed circuit board 28V operated. £1.80.



### ZN414 IC

Integrated circuit radio as featured by many magazines. (FVW Jan. 73 Reprint Ref. No. 19 for 10p), £1.20.



### TOSHIBA POWER AND PREAMPLIFIER MODULES

**TH9013P** 20W power amplifier 22-0-22 or single 45V operated. £4.57.  
**TG9014P** Stereo on two channel preamplifier, £1.50. (Circuit book No. 42 price 10p).



### ULTRASONIC TRANSDUCERS

Operate at 40KHz up to 100 yds. Ideal remote switching and signalling, complete with data transmitter and receiver, new I.C. circuits. Per pair, £5.90.

### 3015F 7 SEC.

IC size complete with data price £2 each or 4 for £7. (Digital clock circuits Ref. No. 31, 15p).



### TRANSISTORS—SPECIAL OFFERS

2N3055		BY127	
25	47p each	25	12p each
100	43p each	100	10p each
500	39p each	500	9p each
1000	34p each	1000	8p each

AF117		OC35	
25	15p each	25	46p each
100	13p each	100	42p each
500	12p each	500	38p each
1000	10p each	1000	34p each

### ZENER DIODES

400m/w BZ288/ BZ283 From 3V—33V, 10p each. 723C (T099) 90 1.3W 5% Miniature Tubulars IN4700 series. From 3.3V—33V, 18p each. 10W. Send. Mounting. ZS series 6.8V—100V 5%, 40p each.

### LINEAR I.C. £ p

702C (T05)	75
709C (T05)	39
709C (DIL)	39
723C (T099)	90
723C (DIL)	90
728C (DIL)	45
728C (T099)	45
741C (T05)	50
741C (DIL)	50
747C (T099)	1.00
747C (DIL)	1.00
748C (DIL)	61

### SILICON RECTIFIERS

1 amp series. IN4001 to IN4007. From 6p each. 1.5 amp. PL4001 to PL4007. From 8p each. 3 amp. PL7001/IN5400. From 14p each. Send for full list 36.

### SEMI-CONDUCTOR QUANTITY DISCOUNTS

10%, 12+, 15%, 25+, 20% 100+ All one type except where quantity discounts shown. Min. order £1.00 please.

### 10% VAT

TO BE ADDED TO ALL ORDERS

MORE OF EVERYTHING AT HENRY'S See pages 847, 848, and Back Cover of this magazine. BEST VALUE

### TRIACS—Scud Mounting with accessories

Type	P.I.V.	Price ea.
3 AMP RANGE	1-11	
SC40A	100V	85p
SC35B	200V	85p
SC35D	400V	90p
SC35E	500V	£1.20
6 AMP RANGE		
SC40A	100V	90p
SC40B	200V	95p
SC40C	400V	£1.20
SC40E	500V	£1.50
10 AMP RANGE		
SC45A	100V	£1.05
SC45B	200V	£1.15
SC45D	400V	£1.45
SC45E	500V	£1.85
15 AMP RANGE		
SC55A	100V	£1.45
SC50B	200V	£1.65
SC50D	400V	£1.65
SC50E	500V	£2.25



TRIACS—Additional Types  
40430 TRIAC (T066) 85p  
40669 TRIAC (Plastic) 90p  
40486 TRIAC (T05) 75p

### NEW RANGES BRIDGE RECTIFIERS

Type	P.I.V.	Price ea.
B025/05	50	16p
B025/10	100	18p
1 AMP		
B05/05	50V	20p
B05/10	100V	22p
B05/20	200V	23p
B05/40	400V	25p
B05/60	600V	27p
1.5 AMP		
B1/05	50V	25p
B1/10	100V	25p
B1/20	200V	28p
B1/60	600V	30p
2 AMP		
W005	50V	29p
W01	100V	30p
W02	200V	32p
W06	600V	35p
2.5 AMP		
B2/05	50V	35p
B2/10	100V	40p
B2/20	200V	45p
B2/60	600V	50p
B2/100	1000V	55p
3 AMP		
B4/100	100V	55p
B4/200	200V	59p
B4/400	400V	65p
B4/600	600V	75p
B4/800	800V	£1.00
6 AMPS		
B6/05	50V	65p
B6/10	100V	70p
B6/20	200V	80p
B6/40	400V	90p
B6/60	600V	£1.00

### SILICON CONTROLLED RECTIFIERS


Type	P.I.V.	1-11
CRS 1/05AF	50V	30p
CRS 1/20AF	100V	35p
CRS 1/40AF	200V	35p
CRS 1/60AF	400V	55p
3 AMP (T048)		
CRS 3/05AF	50V	40p
CRS 3/10AF	100V	40p
CRS 3/20AF	200V	45p
CRS 3/40AF	400V	55p
CRS 3/60AF	600V	65p
5 AMP		
CRS	400V	60p
CRS	5/400V	60p
7 AMP (T048)		
CRS 7/100	100V	60p
CRS 7/200	200V	67p
CRS 7/400	400V	85p
CRS 7/600	600V	95p

**Henry's RADIO LIMITED**  
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
354
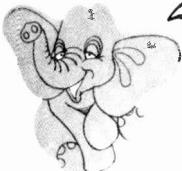
# Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS  
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS  
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's  
**LARGEST RANGE  
 OF KITS &  
 GADGETS**



## TEST EQUIPMENT MULTIMETERS

(carr., etc. 30p)

- 200M (M210) 20k/V Slimline with case, £4.95
- THL33D 2k/V Robust with case, £4.95
- U437 10k/V Steel case, A.C. up to 40kHz, £4.95
- U4324 20k/V with A.C. current ranges, £8.00
- AF105 50k/V with leather case, £9.50
- U4313 20k/V A.C. current. Steel case, £10.50
- U4341 plus built in transistor tester, £10.50
- Model 900 30k/V, £9.95

## OTHER EQUIPMENT

- SE250B Pocket Signal Injector, £1.90. Carr. 15p
- SE500 Pocket Signal Tracer, £1.50. Carr. 15p
- TE15 Grid Dip Meter 440kHz—280MHz, £13.45. Carr. 30p
- TE40 A.C. Millivoltmeter 1-2MHz, £18.75. Carr. 35p
- TE65 28 Range Valve Voltmeter, £19.25. Carr. 40p
- TE20D 120kHz—500MHz RF Generator, £16.95. Carr. 40p
- TE22D 20Hz—200kHz Audio Generator, £18.75. Carr. 40p
- SE350A Deluxe Signal Tracer, £9.95. Carr. 20p
- SE400 Volts/ohms/R-C sub./RF field/RF gen., £11.25. Carr. 20p

## A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester, £5.50. P. & P. 15p
- E1300 Mono mag cart preamp, £1.95. P. & P. 15p
- E1310 Stereo mag cart preamp, £4.95. P. & P. 25p
- Easiphone telephone amplifier, £6.15. P. & P. 25p
- DI203 Teleamp with PU coil, £3.60. P. & P. 20p
- LLI Door Intercomm. and chime, £11.95. P. & P. 25p
- Chattalite (lights as you talk), £13.90. P. & P. 20p
- 1kV Dimmer/contoller, £3.00. P. & P. 10p
- 9in Twin spring unit, for Reverbs, £2.75. P. & P. 15p
- 16in Twin spring unit, for Reverbs, £6.50. P. & P. 25p
- Car Tachometer Electronic, £7.50. P. & P. 15p

- VHF 205 Marine band converter, £3.95. P. & P. 15p
- B2005 4 Ch. mic. mixer, £2.95. P. & P. 15p
- B2004 2 Ch. stereo mixer, £4.75. P. & P. 15p

## BUILD THIS RADIO



**PORTABLE MW/LW RADIO KIT** using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7.98 (battery 22p). Carr. etc. 32p.



## BUILD THIS TUNER

MW/LW Radio tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7in x 2½in x 3½in. All parts £4.85. Carr. 15p.

## FIBRE OPTICS

- 0-01 Diam Mono Filament, £1.50 per 25 metre reel.
- 0-13 Diam 64 Fibres Sheathed, £1.00 per metre.
- SPRAYS 15mm Diam Mares Tails, £9.50.





UK LTD

EASY TO BUILD—  
 EVERYTHING SUPPLIED

Model No.	£
310 Radio control receiver	3.00
300 4-channel R/C transmitter	5.75
345 Superhet R/C transmitter	5.08
450 TV sweep generator	10.24
455 AM signal generator	9.25
460 FM signal generator	9.91
65 Simple transistor tester	1.18
115 8W amplifier	2.87
120 12W amplifier	3.88
125 Stereo control unit	4.20
130 Mono control unit	3.52
605 Power supply for 115	3.88
610 Power supply for 120	4.08
615 Power supply for 2 x 120	4.85
230 AM/FM aerial amplifier	2.79
240 Auto packing light	5.18
275 Mic. preamplifier	5.83
480 Electronic voltmeter	17.51
485 0-12V 300mA STAB. supply	9.68
570 LF generator 10Hz—1mHz	12.60
575 Sq. wave generator 20Hz—20kHz	12.87
590 SVR meter	10.24
620 Ni-CAD Charger 1-12V	7.47
630 STAB. Power supply 6-12V 0.25-0-1A	7.65
690 D.C. motor speed Gov.	2.63
700 Electronic Chaffinch	5.96
705 Windscreen wiper timer	5.56
760 Acoustic switch	8.87
780 Metal Detector (electronics only)	7.27
790 Capacitive burglar alarm	6.16
810 Dynamic Compressor	6.79
835 Guitar preamp	3.23
840 Delay car alarm	5.20
875 CAP. Discharge ignition for car engine (-Ve Earth)	10.68
80 Scope calibrator	1.98
255 Level indicator	5.50
430 3mHz Millivoltmeter	18.22
525 120-160mHz VHF timer	9.33
715 Photo cell switch	6.93
795 Electronic continuity tester	3.88
860 Photo timer	12.04
871 Slide projector auto feed control	8.72
235 Acoustic alarm for driver	6.96
465 Quartz XTAL checker	7.89



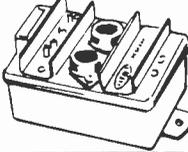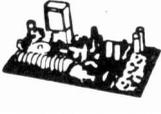ALL KITS OFFERED  
 SUBJECT TO STOCK  
 AVAILABILITY



## MULTI-USE AND RADIONIC KITS

10-1 10 Projects	£ 6.00
50-1 50 Projects	8.00
150-1 150 Projects	13.20
Telephone Communicator	7.20
X20 20 (Elec) Projects	4.95
X40 40 (radio) Projects	9.45
(Carr./Packing 40p)	

## ALL TRANSISTOR CIRCUITS WITH HANDBOOKS

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post, etc. 15p per order.



## GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4in spools. Brand new complete with head circuits, £9.50. Carr. 30p.

## TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post. etc. 15p any quantity).  
 Singles Log and Lin 5kΩ, 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1 Meg, 45p each.  
 Ganged Log and Lin 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 65p each. (Quantity discounts available). Complete with knobs.  
 R730/E73 2 Track Mono Record Erase Low Imp., 75p pair.

## MARRIOTT TAPE HEADS


4 TRACK MONO or 2 TRACK STEREO '17' High Impedance, £2.00; '18' Med. Impedance, £2.00; Erase Heads for '17' and '18', 75p; '63' 2 track mono-imp., £1.75; '43' Erase Head for '63', 75p (Post. etc. 15p any quantity).

## SINCLAIR AND MINIATURE AMPLIFIERS

AMPLIFIERS (Carr. etc. 20p).	£
A-300 0-3 watt 9 volt	1.75
104 1 watt 9 volt	2.20
304 3 watt 9 volt	2.50
555 3 watt 12 volt	2.85
E1208 5 watt 12 volt	4.50
608 10 watt 24 volt	4.10
410 10 watt 28 volt	4.95
Z30 15 watt 30 volt	3.57
E1206 30 watt 45 volt	9.75
Z50 30 watt 50 volt	4.37
E1210 24 + 21 watts 112 volt	5.25
RE500 5 watt IC mains operated Amplifier with controls	6.30
SAC14 7 + 7 watt Stereo with controls	8.00
SAC30 15 + 15 watt Stereo with controls	11.00


SINCLAIR UNITS (Carr. 20p)	£
Z30 3.57	4.37
Stereo 60 Preamplifier	7.97
PZ5	3.97
PZ6	6.37
PZB (for Z50)	4.77
TRANS.	2.95
AFU	4.45

SINCLAIR PACKAGE DEALS. Post 25p	£
2 x Z30, Stereo 60, PZ5	13.95
2 x Z30, Stereo 60, PZ6	18.00
2 x Z50, Stereo 60, PZ8	20.25
Transformer for PZ8	2.99
PROJECT 605 KIT	19.99

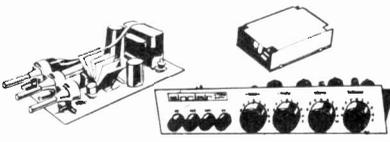
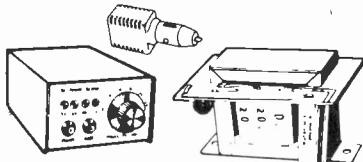
## POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)  
 470C 6.7½/9V 300mA. (Includes Multi-Adaptor for Tape Recorders etc.), £1.95. Post 20p  
 Car Lighter Voltage Adaptors 300mA (State Voltage 6V, 7½V, 9V), £1.95 each. Post 25p  
 SC202 3.6/7½/9V 400mA, £3.25. Carr. 30p  
 HC244R Stabilised version, £4.25. Carr. 30p  
 P500 9V 500mA, £2.80. Post 20p  
 P11 24V 500mA (chassis), £2.80. Post 20p  
 P15 26/28V 1 amp (chassis), £2.70. Post 20p  
 P1080 12V 1 amp (chassis), £3.25. Post 20p  
 P1081 45V 0.9 amp (chassis), £4.40. Post 20p  
 P12 4½-12V 0.4-1 amp, £6.75. Post 30p  
 SE101A 3.6/9/12V 1 amp (Stab.), £9.15. Post 25p  
 RP164 6.7½/9/12 1 amp (Stab.), £9.95. Post 30p



# Henry's RADIO LIMITED

EDGWARE ROAD, W2

SEE FACING  
 PAGE FOR  
 ADDRESSES

# Henry's

## DISCOUNT HI-FI, TV, TAPE AND CAR ENTERTAINMENT

Low prices means less VAT Henry's give full guarantees and demonstrations for callers. Plus big savings. Also at Modern Electrics (Retail) Ltd., 120 Shaftesbury Avenue, W.1.—Your Sony dealer.

**BEST VALUE  
IN U.K.**



STEREO AMPLIFIERS	
(Carr./packing 50p)	£
AKAI: AA5200	61.70
AA5500	78.50
AA5800	117.50
AMSTRAD: IC2000 Mk. II	29.50
4000	23.10
EAGLE: TSA149	25.10
TSA151	34.85
AA2	30.80
AA4	42.45
AA6	55.95
HOWLAND WEST: DA1000	22.45
HENELEC TEXAN: Kit	28.50
HENELEC TEXAN: Built	35.00
NIKKO: TRM300	25.95
TRM400	32.50
PIONEER: SA500A	34.25
ROTEL: RA310	36.95
RA610	54.95
RA810	75.75
RA1210	92.50
SINCLAIR: 2000	22.95
3000	28.95
TANDBERG: TA300	66.10
TELETON: SAQ206B	22.50
SAQ307	22.50
G202	28.50

STEREO RADIO TUNERS	
(Carr./packing 50p)	£
AKAI: AT550	60.50
AT580	94.50
AMSTRAD: 3000	23.55
EAGLE: AAB	40.50
RT512	29.45
HENELEC: Stereo Kit	21.00
Built	24.95
HOWLAND WEST: DA1000T	25.35
PIONEER: TX500A	48.75
ROTEL: RT320	36.95
RT620	57.95
SINCLAIR: 2000	26.95
3000	26.95
TELETON: GT202	30.50

DECODERS/SYNTHESIZERS	
(Carr. etc. 30p)	£
AKAI: S51	39.70
DYNACO QUADRATOR	16.90
EAGLE: AA10	12.00
AA2	16.35
TATE 1	7.95
TATE 3 Chassis	15.75
TATE 4	19.95
TATE 7 Boxed	25.95

MATCHED SPEAKER SYSTEMS	
Recommended pairs 8ohms	£
MARSDEN HALL	19.95 pair
I10, I0V	25.30 pair
150, 15W	25.30 pair
200, 20W	33.50 pair
AMSTRAD	
Acousta, 1500 15W	24.90 pair
Acousta, 2500 20W	28.50 pair
DYNACO	
A10	41.00 pair
A25 20-60W	65.00 pair
A35	78.00 pair
WHARFEDALE	
Denton 2, 18W	24.40 pair
Linton 2, 20W	31.00 pair
Triton, 25W	37.75 pair
LEAK	
150, 18W	33.50 pair
250, 18W	42.50 pair
CELESTION	
I20/20V	35.95 pair
County, 25W	31.50 pair
15, 30W	47.95 pair
44, 44W	79.95 pair

U.K.'s largest stockists for KEF Acoustic Research, Mordaunt Short and Cambridge audio speakers. In stock and on demonstration. Phone for keenest price

STEREO MAGNETIC CARTRIDGES	
(Carr. etc. 15p)	£
SHURE	
M3Dm £3.20; M44.7 £3.95; M44E £4.25; M55E £4.95; M44G £4.20; M75/6/11B £6.75; M75ED/11 £8.50; M75E/11 £7.95; M75G/11 £7.25.	
GOLDRING	
G850 £2.85; G800 £3.75; G800H £3.50; G800E £5.75; G800SE £10.00; G820 £6.70; G820E £10.00; G820SE £13.35.	
ADC	
Q36 £10.70; Q32 £8.70; Q30 £5.90.	
GRADO	
FTR £5.25; F3E £11.25; FTE £8.25; MZ £18.75.	
EMPIRE	
909EX £7.25; 999EX £9.25; 999SEX £10.75; 999TEX £14.95.	

10% VAT to be added to ALL ORDERS. Prices and description correct at time of press E & OE. All goods offered subject to stock availability.

RECORD DECK PACKAGES	
(Carr./packing 75p)	£
(HL): SP25 III/800 or H	15.95
(M): SP25 III/M756S	19.45
(HL): AP76/G800	24.75
(M): AP76/M756S	27.35
(HL): GL75 P/C	32.50
(HL): GL75 P/C G800	35.50
(HL): GL75 P/C G800E	37.50
(HL): MP60 PC G800 or H	16.25
HT70(TPD1) G800	19.50
Pioneer PL12D	31.75
Thorens TD165	43.50

STEREO COMPACTS complete with speakers	
(Carr./packing £1 25)	£
Fidelity UA3	39.90
Sony G2601KL	125.50
Sony G2615N	71.50
Sony GXT4520KL	103.50
Sony GXT4730KL	97.50

8 TRACK STEREO HOME UNITS	
(Carr./packing 70p)	£
Amerlex ACR301	£48.00
(With MW/FM stereo radio).	

PORTABLE TV BATTERY—MAINS	
(Carr./packing £1 00)	£
Elizabean T9 (9in)	43.50
Crown 9TV (9in)	46.50
Elizabean T12 (12in)	43.95
Teleton TW12 (12in)	46.95
Sony IOT150 (12in)	49.95

CARRY YOUR MUSIC ANYWHERE

### CASSETTE PLAYER

FOR CAR—HOME AND AROUND

Actually the price far below the quality of the superb player. It is of beautiful quality both in sound and looks.

Features wind, rewind volume and tone controls. Speaker is very good indeed. Comes complete with earphone, batteries Full guarantee. Optional adaptor to run off car or mains.

MADE TO ORDER OUR PRICE **£7.25** (VAT INCL)

BAR LIGHTER PLUG-IN ADAPTOR £1.95  
MAINS ADAPTOR £1.95

DOLBY/NRU	
(Carr./packing 30p)	£
Teleton SNR100D	29.50
Philips N6720	15.00
Teak AN60/AN80/AN180 stocked.	

BATTERY CASSETTE RECORDERS	
(Carr. etc. 30p)	£
Amerex 100	11.00
Wien ET100B	11.00
Philips EL3302	14.40
N2203	16.60
N2211	19.95
Sony M1101	13.90
M1102	12.95

BATTERY/MAINS CASSETTE	
(Carr. etc. 35p)	£
Wien RT452	13.65
Amerex AC101	12.00
Elizabean LZ315	12.25
Amerex AC104	16.00
Philips N2204	20.75
N2205	29.50
Pye 9115	27.75
9118	21.20
Hitachi TRQ291	27.50
Sony M2000G	23.25
MR4010	28.95
M4000G	49.50
BASF CC9201	37.25
Hitachi TRQ2335	49.50

BATTERY/MAINS RADIO CASSETTE RECORDERS	
(Carr. etc. 30p)	£
Amerex ACR200	22.00
ACR201	30.00
Elizabean LZ416	27.25
LZ516	29.10
BASF CC9301	50.75
RR413	28.75
RR412	33.90
RR712	48.30
Sony M4141	49.50
M2400W	31.50
M2400FG	31.50
M4400FG	62.50
Grundig C250	47.95
Hitachi TRK1240E	29.50
M400161	35.00
KCT1210L	33.50

STEREO RECORDER DECKS	
(Carr./packing 50p)	£
Cassette	
Philips N2506	44.50
Pye 9145	44.50
Tandberg TCD3000	112.00
Akai GX40D	57.75
GXC45D	74.00
GXC46D	84.30
GXC65D	93.40
TEAC: A250/A350/A450 stocked.	
Reel to Reel	
Akai 400DS	59.95
Tandberg 3321X/3341X	102.80
Large range Akai/Tandberg/Revox/Teac stocked.	
8 Track	
Akai CR81D	54.10
CR80DS5	94.95

STEREO RECORDERS	
(Carr./packing 70p)	£
Akai I721L	60.35
Cassette	
Akai GX40	67.95
GXC46	90.75
Philips N2400/RH411	63.75
N2401/RH411	74.50
N2401S/RH411	79.95
N2405/RH401	49.50
N2510	88.75
8 Track	
Akai, CR81	66.20
8 Track Player Decks	
(Carr./packing 35p)	£
Elizabean B/LZ1	13.40
McDonald/BSR TDBS	12.75
TDB3V	15.25

### STEREO PHONES AT SPECIAL PRICES

(carr./packing 20p)

AKAI: ASE95 £5.80; ASE20 £7.30; ASE22 £8.25.

Dulci: SH650D £2.25; SH850GX £3.95; SH1300VS £5.25.

AKG: K60 £9.25.

Rotel: RH630 £4.85; RH700 £6.75.

Senheisser: HD414 £10.95.

Wharfedale: DD1 £9.50; ISODYN £14.35.

Koss: K6 £9.95; K6/LC £11.25; K711 £7.95; KR711 £7.95; HV1 £17.50; K072B £12.45; K074 £15.95; PR04AA £21.95; PR05LC £23.95.

Howland West: CIS200 £2.75; CIS250 £5.25; CIS1000 £7.50; CIS2000 £15.25.

TTC: G3000 £6.60; G2222 £5.95; Low Cost: MD802 £1.95; MD806 £3.75.

Pioneer: SE20A £5.30; SE30A £8.90; SE50 £15.20; SEL20 £7.40; SEL25 £10.90; SEL40 £12.50.

Accessories: H1012/JB3 Junction Box £1.40; IB3DE Din Junction Box £1.60; JB11D DeLuxe Junction Switch £4.75.

Control Boxes: G1301 (two phones) £2.62; G1305 Controller £2.15; FF17 2-pairs (Sliders) £6.25; Koss T4A £4.20; Koss TSA £4.95; Koss T10A £8.90; HW Mk.III Controller £6.90.

YOU CAN PAY BY BARCLAYCARD OR ACCESS

For callers or by phone 01-402 4736

Easy credit terms for callers to 309 and 354-356

ALSO STOCKED AND DEMONSTRATED

Armstrong — Acoustic Research — Cambridge Audio — Leak — Lux — Marantz — Quad — Revox — Sansui — Tandberg — Sugden — Wharfedale — Goodmans — Celestion — Grundig — Kef — Teac — Bose — Sherwood

Call or phone 01-402 4736 for best prices

# Henry's RADIO LIMITED


EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
354-356 High Fidelity and Tape Equipment 01-402 5854/4736  
309 PA-Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW

Open: 9am-6pm 6 days a week All stores open all day Saturday

# AT LAST!! RINGBOARD

## Something new in electronics

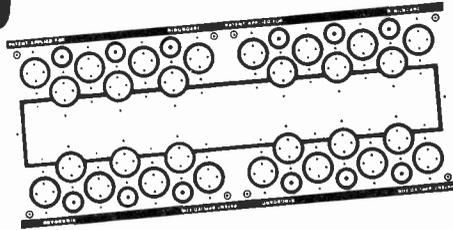

Size of full board  
6½" × 2½"

A standard printed circuit board that really works and is quicker than any other standard P.C. Board, plus a method that applies to any discrete circuit you wish to make (I.C. Ringboard to follow). Simple as A.B.C. Ringboard is a fantastic breakthrough in standard P.C. Boards... just simply ring round all joints on a circuit with a pencil and you are on your way to laying out the components on Ringboard... If you don't understand the method we will give you your money back. Who can make a claim like that?

Ringboards are made of fibreglass to enable the rings to be seen from the back, and are supplied ready drilled.

Ringboards can be cut into ½ and ¼ boards and still retain all the characteristics of a full board.

Special Opening  
Price

Ringboards Cost	55p	Full board	47p
(P. & P. 7p extra)	33p	Half board	26p
(over £1 free)	22p	Qtr. board	16p

Or ask your local trader

### STAR POINTS OF RINGBOARD

- ★ Neat and professional finish
  - ★ Simple to use
  - ★ Little or no planning
  - ★ Little or no looping
  - ★ As compact as any similar sized standard P.C. Board
  - ★ Money back guarantee
  - ★ Full instructions of the method with each RINGBOARD purchased.
- Quantity Discounts

**RINGBOARD** 259 Chesterfield Road, Sheffield S8 0RT, Yorkshire

# LASKYS 1974 CATALOGUE

## FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

AUDIOTRONIC HOUSE, THE HYDE, LONDON, NW9 6JJ


## Multicore Solder Cream for high quality joints in the Electronics Industry

New Multicore Solder Cream was designed for jobs where second best will just not do. Like manufacturing diodes for instance. Or making a tuner chassis, or soldering thick-film circuits. Multicore Solder Cream, a finely graded solder alloy powder in a thixotropic organic vehicle, is easier, quicker, more economic and more reliable than conventional techniques.

Multicore Solder Cream is different. It doesn't spit or need stirring. It can be applied by syringe, automatic dispensers or screen printing—giving instant soldering with


good spread, strong joints with low contact angles. Suitable as a temporary adhesive during assembly, the clear colour flux residue—without solder globules—makes inspection easier. There are three types of Multicore Solder Cream—one of them may be just what you're looking for.

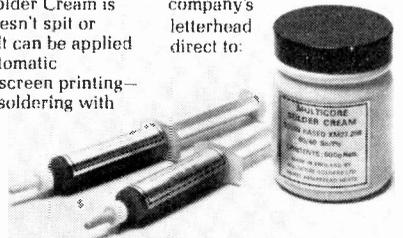For full information on this or any other Multicore products, please write on your company's letterhead direct to:



Multicore Solders Ltd., Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP. Tel: Hemel Hempstead 3636. Telex: 82363.

# The Catalogue you **MUST** have!

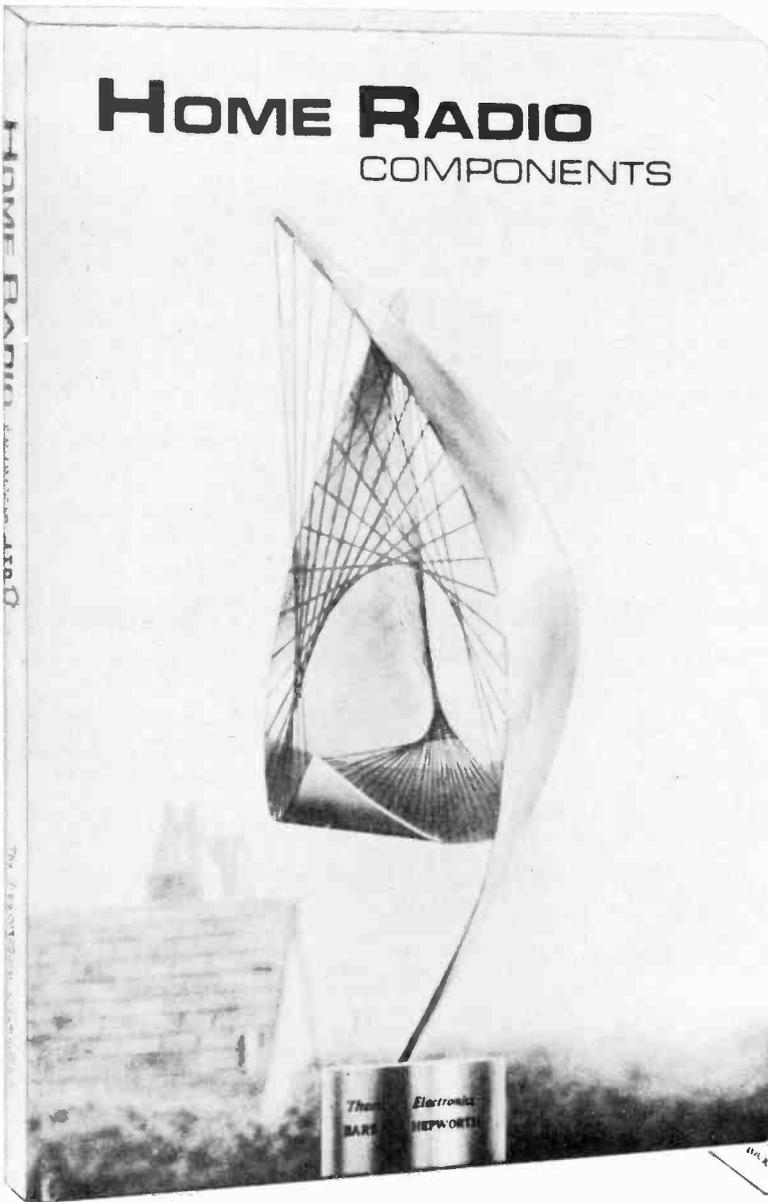

250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

*Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.*

**Only 55p.** plus 22p **POST AND PACKING**

**POST THIS COUPON**  
with cheque or P.O. for 77p.

The price of 77p applies only to customers in the U.K. and to BFPO addresses.

Name \_\_\_\_\_

Address \_\_\_\_\_

HOME RADIO (Components) LTD. Regd. No. 912966, London  
Dept. PE, 234-240 London Road, Mitcham CR4 3HD



## AMATEUR RADIO JUBILEE

**R**ADIO provided the original sturdy stock from which a host of branches have since proliferated, giving a variegated countenance to the lusty and profusely spreading technology now known as electronics. Digging back to the roots, one finds the amateur enthusiast playing his part right from the earliest times of wireless communication. This then new field offered exciting possibilities and attracted the interest of thousands of individuals possessed of a scientific bent and an urge to experiment with home-made equipment.

No doubt the community spirit engendered through contacts established by wireless between individuals and groups was responsible for the rapid formation of wireless clubs throughout the country. On September 23, 1913 the London Wireless Club held its first general meeting in London. This was a momentous event, because this body was later to be reconstituted as the Radio Society of Great Britain.

At this time when the RSGB is celebrating its Diamond Jubilee, it is well to record the event and acknowledge the vital part this body has played in furthering the interests of the radio amateur, not only within the U.K., but on an international level as well.

It has to be admitted that, in the popular eye, the radio amateur has become typified as a somewhat odd character living for much of his time in a peculiar world of his own, peopled only by other kindred spirits identified by call signs rather than names. That he *can* become so totally engrossed in his hobby as to be oblivious of all other affairs is a fact that many wives and acquaintances will affirm! It is also a fact that in recent times he has succumbed more and more to the sophisticated products offered by the communications equipment manufacturers, and his chief role now is likely to be that of an operator of a radio station equipped largely with commercial apparatus.

Nowadays the opportunities for making significant contributions to radio science are limited. Commercial interests have always quickly and eagerly followed up past pioneering achievements by amateurs (often to the latter's ultimate cost). Exploitation of all kinds of radio communication with the very latest electronic techniques has for long been a prime concern of professionals working for industry and government agencies.

But the radio amateur still has his own fascinating hobby. No one who has experienced the thrill of that first over-the-air contact will dispute the attractive force of electromagnetic waves. When the bug bites, it usually bites deep. And, of course, not all amateurs are as single-minded as we might have suggested. Not for all the time, at any rate! Most are likely to be avid followers of electronics in its widest sense, and no doubt become involved from time to time in the building of equipment entirely foreign to a radio shack.

Today's amateur constructor and experimenter, whatever his field of specialisation within electronics, is continuing a fine tradition of individual enterprise where financial gain is not the goal; a tradition established by that pioneering band in the early days of wireless. We offer best wishes to the Radio Society of Great Britain and to their members, a fraternity which through usage over the last 60 odd years has acquired its own special kind of proprietary right to that honourable term "amateur."

F.E.B.

**Editor**  
F. E. BENNETT

**Editorial**  
R. D. RAILTON *Assistant Editor*  
D. BARRINGTON *Production Editor*  
G. GODBOLD  
S. R. LEWIS B.Sc.

**Art Dept.**  
J. D. POUNTNEY *Art Editor*  
J. A. HADLEY  
R. J. GOODMAN  
K. A. WOODRUFF

**Advertisement Manager**  
D. W. B. TILLEARD  
Phone: 01-634 4202

P. J. MEW  
Phone: 01-634 4210

C. R. BROWN, *Classified*  
Phone: 01-634 4301

*Editorial & Advertising Offices:*  
Fleetway House, Farringdon St.,  
London EC4A 4AD  
Phone: *Editorial* 01-634 4452  
*Advertisements* 01-634 4202

# Semiconductor TESTER

BY J. H. PERKIN



THE semiconductor tester is an invaluable aid to the experimenter since it allows him to not only detect faulty components in both building and servicing but to select or match components for specific circuit requirements and, bearing in mind the availability of untested components, purchase and sort such devices.

However, to effect all these usually requires a number of different instruments because of the inherent differences between the devices to be tested.

The present tester removes this objection to a great extent by being able to cope with a wide range of discrete components and identify their main parameters.

It was designed so as to be of low cost and reasonable ease of construction, to be portable and easy to operate, and of course to be as versatile as possible.

## SEMICONDUCTOR THEORY

### Transistors

These have the ability to provide current gain, i.e. the application of a small change in base current of a transistor gives a larger change in collector current, giving current amplification. This may be converted to voltage amplification by use of external components.

The magnitude of this amplification is referred to as  $h_{te}$  where:—

$$h_{te} = \frac{\text{The change in collector current}}{\text{The change in base current}}$$

Ideally, when no base current flows no collector current should flow but in fact this is not so in practice. Even when the base is completely disconnected a small amount of current flows in the collector/emitter circuit. This current is known as  $I_{ceo}$  or leakage current.

### Diodes

Basically a diode is a device which allows current to flow in one direction only. Again, as with

the transistor, such devices are not perfect and, under some conditions of applied voltage, current can indeed flow in either direction through a diode.

Fig. 1 shows the curve of current to voltage for a diode, identifying the two conditions of forward and reverse bias.

When the diode is forward-biased very little current flows until voltage  $V_1$  is reached. In practice the value of  $V_1$  depends very largely on the nature of the semiconductor. If it is germanium  $V_1$  will be 0.2 volts and if silicon it will be 0.6 volts.

Incidentally, this holds true of the base/emitter junction of a transistor.

When  $V_1$  is exceeded the current rises rapidly for small increases in voltage and the slope of the graph (a tangent to the line at any given point) is the forward a.c. resistance of the diode which is approximated by using the formula:—

$$R_{tac} = \frac{26}{I_e} \text{ where } I_e \text{ is the diode current in mA.}$$

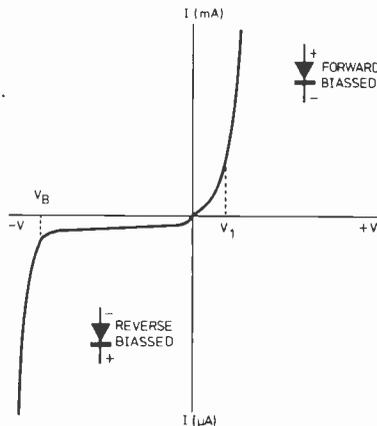


Fig. 1 Graph showing a typical voltage/current relationship for a diode

When the diode is reverse-biased little current flows and it is called the leakage current. This increases as the breakdown voltage  $V_B$  is reached and exceeded. Above  $V_B$  the current increases rapidly for small increases in voltage.

This region of the curve is known as the Zener region and the slope of the curve in the Zener region is known as the a.c. resistance or  $R_{ac}$ .

### Thyristors

Basically a thyristor is an electrically controlled switch in which a small gate current can trigger a very much larger anode/cathode current. One drawback of this device is that once anode current is flowing it can be turned off only by either removing the voltage or breaking the circuit externally to the thyristor.

The current through the thyristor in its untriggered state is known as the leakage current,  $I_{l0}$  when the thyristor is forward-biased and  $I_{r0}$  when it is reverse biased.

The magnitude of the current required to "trigger" the thyristor via the gate is known as the "gate trigger current" and the magnitude of the current required to switch the thyristor "on" is known as the "gate trigger voltage," measured with respect to the cathode.

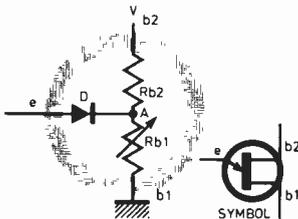


Fig. 2. Diagram of the equivalent circuit of a unijunction transistor with its usual symbol

As the current through a thyristor is reduced it reaches a state where further reduction would switch the thyristor "off." This level of current is known as the "holding" current.

### Unijunction Transistors

The diagram of Fig. 2 shows the pictorial representation of a unijunction transistor.

The voltage at point A with the emitter disconnected is given by the formula:—

$$\frac{V \times R_{b1}}{R_{b1} + R_{b2}}$$

where the ratio  $\frac{R_{b1}}{R_{b1} + R_{b2}}$  is known as  $\pi$ , the

intrinsic standoff ratio (considering  $R_{b1}$  and  $R_{b2}$  in series).

The emitter connection is isolated from b2 and b1 unless the potential at the emitter (e) is greater than  $A + 0.6V$ , when the diode will be forward-biased and thus conduct. In this condition the resistance  $R_{b1}$  decreases and the voltage at A drops as the current increases, thus producing a negative resistance region.

A point is reached where the emitter current ceases,  $R_{b1}$  returns to its initial value and the diode is reverse-biased until it attains a sufficiently high potential for the process to repeat.

## CIRCUIT OPERATION

### Transistor Testing

The block diagram of the system used to test transistors is as shown in Fig 3. To measure  $I_{ceo}$  only a meter and a meter switch S2 (see Fig. 4 which is the complete circuit diagram) are used, and the meter monitors the current through the transistor with the base disconnected. R12 is a meter shunt which is switched out by the f.s.d.  $\div 20$  switch S4. (See Fig. 4.)

$h_{fe}$  is measured as follows. The output of a multivibrator consisting of components R1, R2, R3, R4, C1, C2, TR1, TR2, oscillating at approximately 400Hz is fed via R5 to a calibrated attenuator VR1 and also to the comparator circuit. VR1 is calibrated to read  $h_{fe}$  directly and R15 is included to expand the  $h_{fe}$  scale.

The attenuated oscillation from the slider of VR1 is fed via R19 which compensates for differing input impedances of the transistors to be checked. The signal is then fed via C5, a d.c. blocking capacitor through S1e and S2d to the base of the transistor under test.

The transistor connected in the common emitter mode amplifies and inverts the signal at its base. The amplified signal is fed via R7 and C4 to the base of TR3 where it combines with the non-inverted

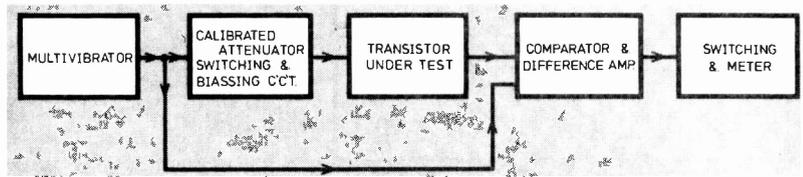



Fig. 3. Block diagram of the Semiconductor Tester as used to measure transistor characteristics

oscillation from the multivibrator which has been fed via R16 and C3; VR2a and R17 compensate for attenuation made by the network R19, VR2b and R10. If VR1 is correctly adjusted the two signals cancel at the base of TR3. Any uncancelled oscillation is amplified by TR3, TR4 and R6, R18 biasing TR3. The amplified signal is passed by C6 and R21, rectified by D7 and D3 and causes a deflection on the meter when the meter switch is set to  $h_{fe}$ . VR2 is set to the required no signal current in the transistor which is being checked. D4 and D5 provide a path for collector current when  $I_c$  is not being monitored.

### Diode and Zener Testing

Diode testing is accomplished by connecting the diode to the power supply through an internal resistor R11. The current through the diode is monitored by the meter both when the diode is forward and reverse biased. Reverse biasing is accomplished by reversing the polarity of the supply voltage.

The voltage across the diode can be measured by utilising a meter as a voltmeter, this is accomplished using the meter switch and a multiplier resistor R23, which converts the meter to read 25V f.s.d. The breakdown voltage (Zener voltage) of a Zener diode can be measured using the meter as a voltmeter. A

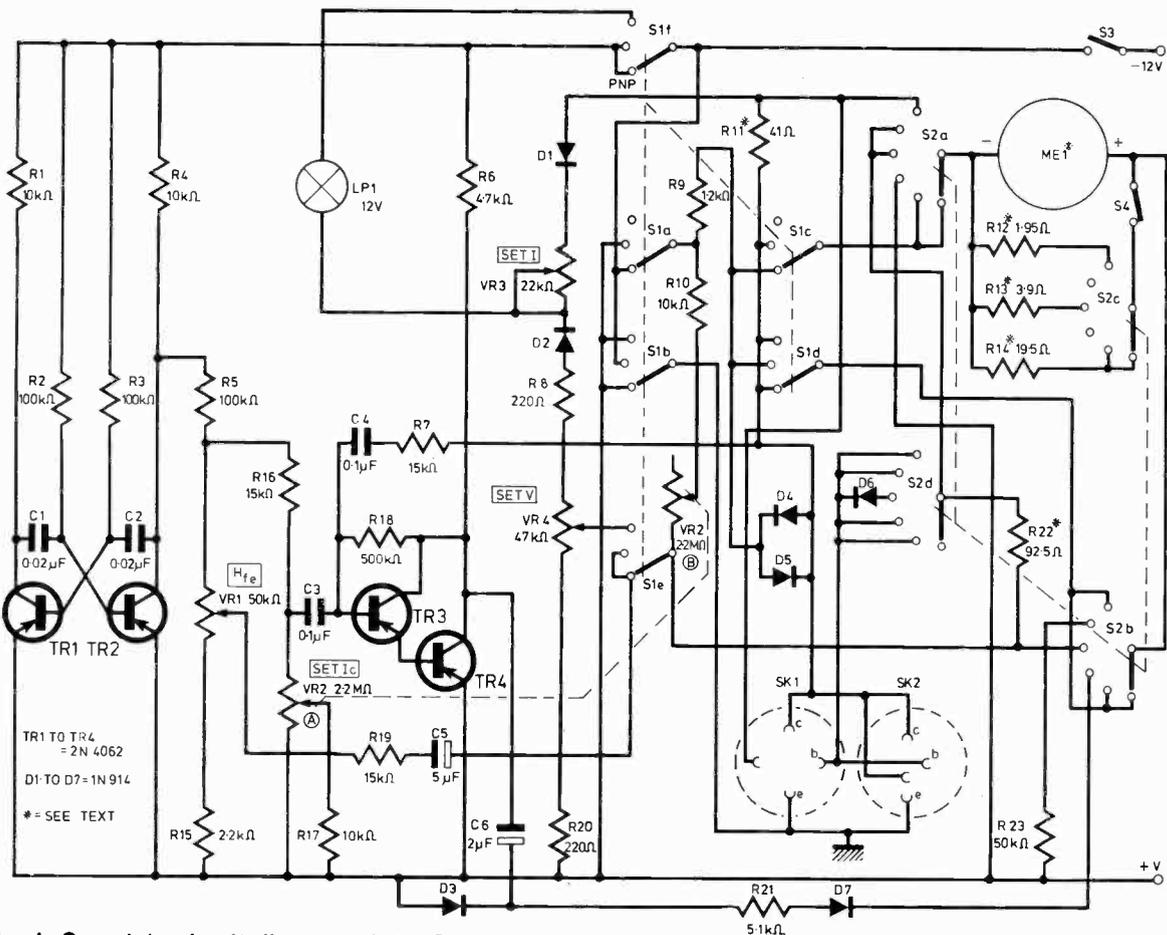

**Fig. 4. Complete circuit diagram of the Semi-conductor Tester.** The resistors marked with an asterisk are made from two or more in parallel. Switch S1 is shown in the PNP position and S2 in the  $I_{FO}$ ,  $I_{RO}$  position, other switch positions being shown right

## COMPONENTS . . .

### Resistors

R1	10k $\Omega$	R6	4.7k $\Omega$
R2	100k $\Omega$	R7	15k $\Omega$ 2%
R3	100k $\Omega$	R8	220 $\Omega$
R4	10k $\Omega$	R9	1.2k $\Omega$
R5	100k $\Omega$	R10	10k $\Omega$
R11	41 $\Omega$ (43 $\Omega$ 2% in parallel with 910 $\Omega$ 2%)		
R12	1.95 $\Omega$ (5.4 $\Omega$ in parallel with 5.1 $\Omega$ and 8.2 $\Omega$ all 2%)		
R13	3.9 $\Omega$ 2%		
R14	19.5 $\Omega$ (22 $\Omega$ 2% in parallel with 180 $\Omega$ 2%)		
R15	2.2k $\Omega$	R18	500k $\Omega$
R16	15k $\Omega$ 2%	R19	15k $\Omega$ 2%
R17	15k $\Omega$ 2%	R20	220 $\Omega$
R22	92.5 $\Omega$ (100 $\Omega$ 2% in parallel with 1.2k $\Omega$ 2%)		
R23	50k $\Omega$ 2%		

All  $\frac{1}{2}$ W 5% carbon unless otherwise stated

### Potentiometers


VR1	50k $\Omega$ log moulded track
VR2	2.2M $\Omega$ + 2.2M $\Omega$ linear double ganged
VR3	22k $\Omega$ linear
VR4	47k $\Omega$ linear

### Capacitors

C1, C2	0.02 $\mu$ F (2 off)	C5	5 $\mu$ F 25V elect
C3, C4	0.1 $\mu$ F (2 off)	C6	2 $\mu$ F 35V elect

### Diodes

D1 to D7 1N914 or similar (7 off)

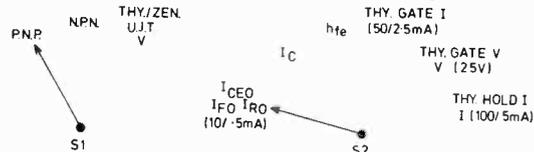

### Transistors

TR1 to TR4 2N4062 or similar high gain *pn*p silicon (4 off)

### Switches

- S1 6-pole 3-way (R.S. Components Miniature Maka-switch. Shaft assembly plus 2  $\times$  4-pole 3-way wafers)
- S2 4-pole 6-way (Maka-switch shaft assembly plus 2  $\times$  2-pole 6-way wafers)
- S3 Single pole on/off
- S4 Single pole on/off biased on

### Plugs and sockets

- SK1 4 pin transistor socket
- SK2 3 pin DIN socket
- PL1-3 3 pin DIN plugs (3 off)

### Miscellaneous

- ME1 500 $\mu$ A f.s.d. (SEW type MR45P)
- LP1 12V 0.1A (with holder)
- B1, B2 6V PP1 or equivalent with battery connectors
- West Hyde MOD303 case with rubber feet
- Veroboard 3 $\frac{3}{8}$ in  $\times$  1 $\frac{1}{4}$ in 0.15in matrix
- 4BA  $\frac{1}{2}$ in bolts, nuts and washers (4 off)
- 6BA  $\frac{1}{4}$ in bolts, nuts and washers (4 off)
- Crocodile clips (7 off)
- Screened double cored cable (6ft)

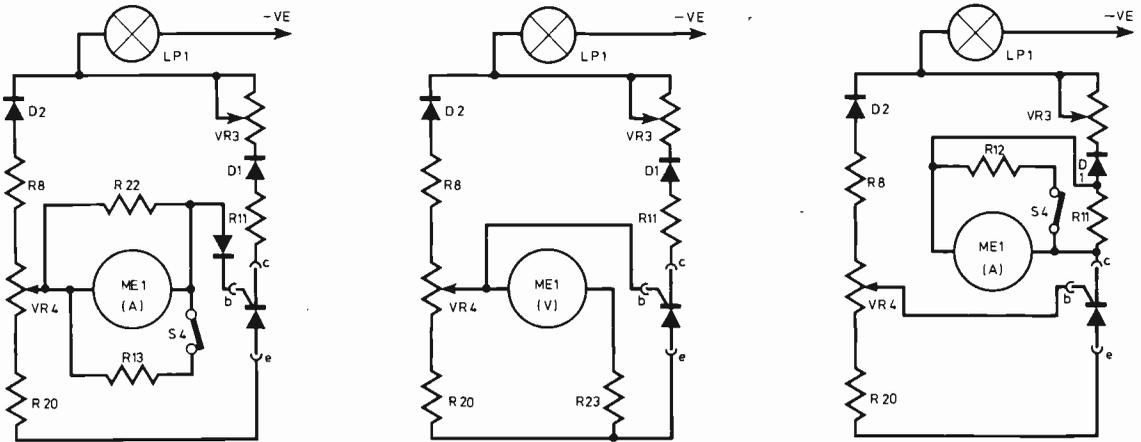


Fig. 5 (a) (left). The equivalent circuit when the switch is set to measure gate trigger current, (b) (centre) shows the switch in the gate trigger voltage position and (c) (right) in the holding current position

measure of  $R_{ac}$  and  $R_{fac}$  can be found by varying the current through the diode by adjusting VR3 and monitoring the change in voltage across the diode.

#### Thyristor testing

The circuits used in thyristor testing are as shown in Fig. 5a, b and c. The "gate trigger current" is found by increasing the voltage applied to the gate with respect to the cathode by adjusting VR4 until the thyristor switches on. The thyristor "ON" condition is indicated by the meter reading falling to zero and the lamp LP1, lighting (if VR3 is set to minimum resistance). R13 and R22 act as meter shunts and S4 is the f.s.d.  $\div 20$  switch. Diode D6 protects the meter from reverse currents which would flow through the meter when the thyristor is in the "ON" condition. The gate trigger voltage is found by setting the meter switch S2 so that the meter plus the multiplier resistor are connected across the gate and the positive supply line.

The leakage currents  $I_{T0}$  and  $I_{T0}$  through the thyristor can be found in the same way as the leakage currents for *nnp* and *pnnp* transistors.

Thyristor holding current is found by setting the meter switch to THY HOLD I which places the meter in the cathode circuit of the thyristor. Increasing VR4 (SET I) towards maximum decreases the current through the thyristor until a point is reached

where the thyristor switches off. The diodes D1 and D2 isolate the resistor line VR3, R8, VR4, R20 to 0V when the semiconductor tester is operating in the *pnnp* on *nnp* mode. Resistors R11 and R12 act as meter shunts giving two holding current ranges of 5mA and 100mA.

#### Unijunction Testing

The basic circuit used to test unijunction transistors is shown in Fig. 6. The voltage with respect to base of the emitter can be increased by VR4 (SET V) by adjusting it from maximum to minimum until at a certain point the unijunction and the semiconductor components behave as an oscillator; this point is indicated by a rise in the meter voltage.

#### Voltmeter and Ammeter

The above semiconductor tester components are used in this mode of operation. Resistor R23 acts as a meter multiplier.

When the meter switch is set to THY HOLD I the meter can be used as a two range ammeter when the ammeter plug is used, R11 and R12 acting as meter shunts.


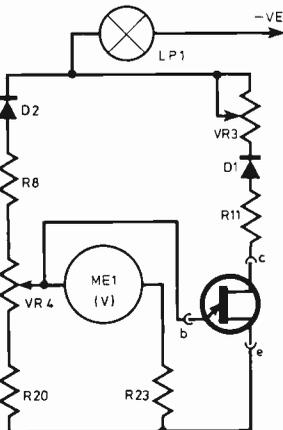


Fig. 6. The circuit used when the switches are set to measure unijunction intrinsic standoff ratio

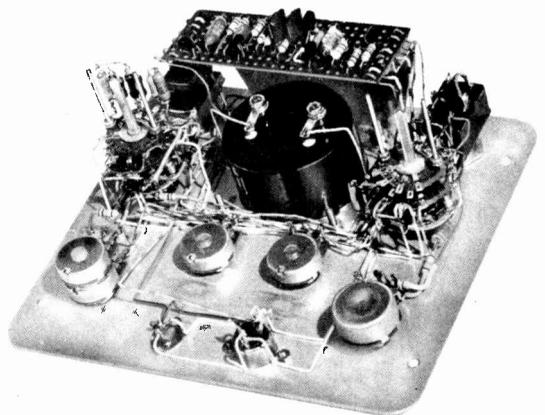

Next month: Constructional details and operating instructions.

# NEW DEVICES ... APPLICATIONS

## Automobile Integrated Circuit

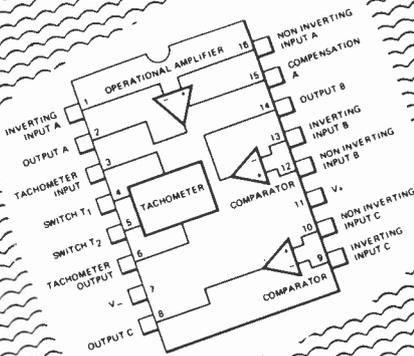


Fig.1.

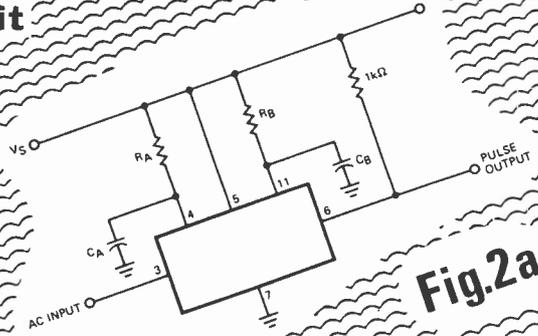


Fig.2a.

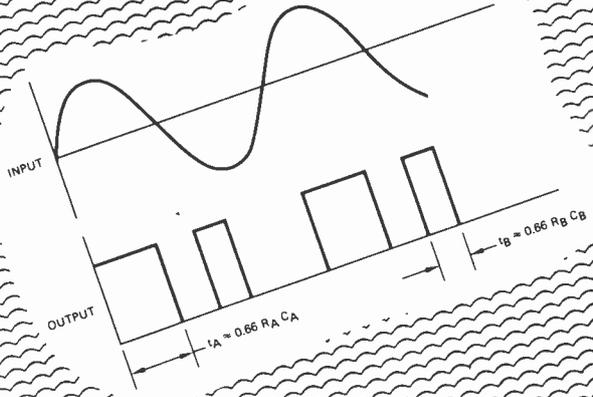


Fig.2b.

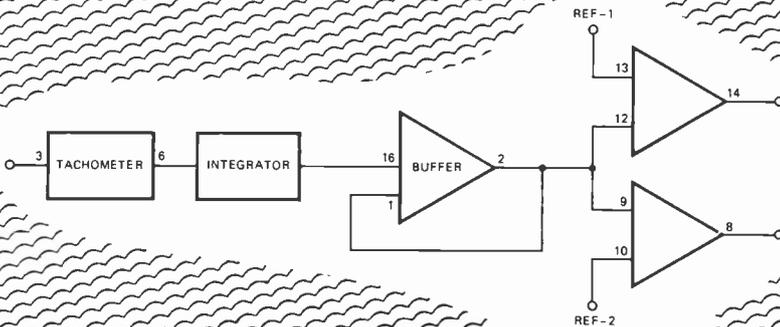


Fig.3.

In this section we present a selection of both new devices and applications, with news of applications developed for existing devices.

Generally only basic circuit details will be given sufficient for the experimenter to create his own equipment.

JUST coming on to the market are two integrated circuits from Fairchild, both designed with the Automobile market in mind. The first is the  $\mu A7350$  a complete tachometer subsystem, and the second is a triple operational amplifier, the  $\mu A7351$ .

The  $\mu A7350$  is a monolithic i.c. which includes a tachometer, an operational amplifier and two comparators. The tachometer produces fixed width pulses at the zero crossings of a ground reference a.c. input signal.

Each pulse width is individually determined by the choice of an external resistor and capacitor. The output stage of the tachometer section is a common emitter *npn* transistor with an uncommitted collector.

The operational amplifier and comparators are of identical design except that the comparators have no provision for external compensation. Their output stages consist of class A *pnp* amplifiers with uncommitted collectors which allow a variety of loads for general purpose applications.

In addition, the outputs of the comparators may be wired-OR for use as a dual level sense device.

Typical applications of this chip include over- and under-speed and frequency sensing, servo control, tone detection and a variety of timing functions.

Power requirements can be met by a single or a dual supply with an absolute supply voltage maximum of 24V. The chip is short-circuit protected.

Figure 1 shows the block schematic of the 7350 whilst Fig. 2 is a circuit of the tachometer section in application.  $R_A$  and  $R_B$  are 27k $\Omega$  and  $C_A$  and  $C_B$  are 5.670pF (all at 1%) for an output pulse width of between 900 $\mu$ s and 110 $\mu$ s. Fig. 2b shows the output in graphic form.

Figure 3 shows the block diagram of a complete system.

### TRIPLE OPERATIONAL AMPLIFIER

The second i.c. the  $\mu A7351$  shown in block form in Fig. 4, is again a monolithic device carrying three identical operational amplifiers. Each two-stage amplifier uses a class A *pnp* common emitter output stage with an uncommitted collector, providing a variety of loads for general-purpose applications.

The chip is designed specifically to operate from a single supply and is thus ideal for automotive applications or any portable battery-type environment. In fact, the power requirements run from +4V to +16V single supply or  $\pm 2V$  to  $\pm 8V$  double.

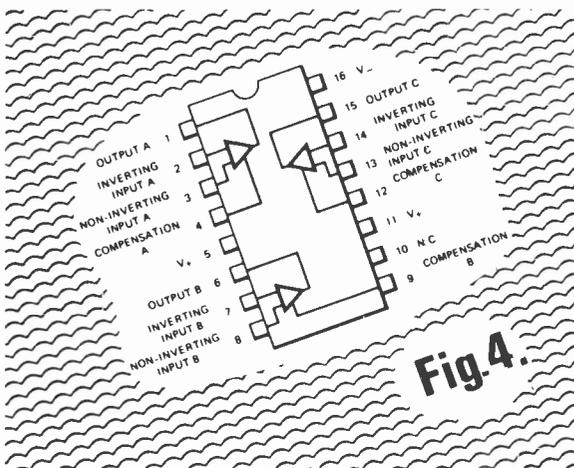


Fig. 4.



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

### SERIES REGULATOR

IN Fig. 1, the operational amplifier acts as a differential amplifier controlling the base current of the Darlington pair arrangement in series with  $V_{in}$ . The Darlington pair used came in one package (TIP140). This has a high gain and a current capability of 10A.

TR2 across R2 acts as a current limit. When the voltage across R2 is greater than  $V_{BE}$  of TR2, it will conduct and cause TR1 to turn off until the voltage across R2 is equal to  $V_{BE}$ .

The present circuit is capable of withstanding a continuous short circuit across its output. The line voltage used was 12V and was adjusted for 5V output. The circuit will regulate the output to 5V from anything from the maximum operating voltage of the op-amp down to 7V.

A very simple input can be used consisting of just a transformer, bridge rectifier and smoothing capacitor.

A. Belka,  
Bletchley.


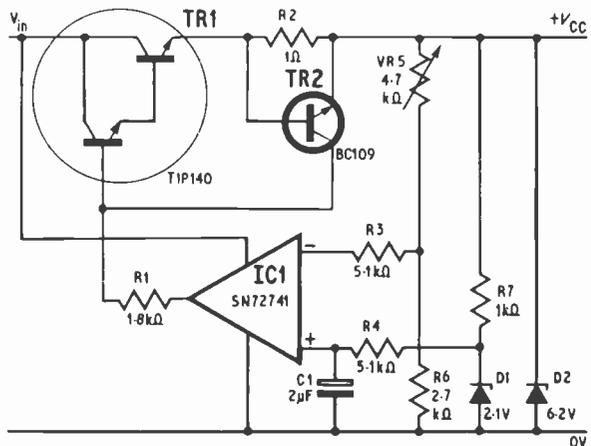


Fig. 1. Circuit diagram of Series Regulator using a Darlington pair transistor

## EVENTS TIMER WITH READOUT

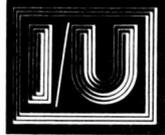

THE TIMER in Fig. 1 uses an electromechanical readout device which is not capable of actuating faster than 10 times per second. Thus the speed of operation is similarly limited.

In basis, an oscillator section, TR1 and TR2 form a multivibrator which can run at 1 or 10Hz dependent on the selection of C1 and C3 or C2 and C4.

Thus C1 and C3 are made 10 $\mu$ F for 10Hz and R2, R3 about 7k $\Omega$  each. The exact value is adjusted by VR1. A lower value of C1, C3 may be necessary as the voltage change produced at the base of TR3 may be insufficient to turn the counter off.

For the second range S1 is switched to bring in C2, C4, 100 $\mu$ F to give a frequency of 1Hz and again VR1 may need to be adjusted.

In practice capacitance adjustment was found to be much better than varying R2, R3 as too high a value for these resistors when lowering the frequency can reduce the voltage at the base of TR3 too far.

The output via TR3 is straightforward; a positive pulse at the base causes a large change in voltage at the emitter to activate the counter.

The diode D1 deals with back e.m.f. induced in the counter coil.

Basically the current drawn depends on the counter coil resistance as very little is drawn by TR1 and TR2. Indeed this can be further reduced by increasing R1, 4.

Several counters are available but if the resistance falls below 500 $\Omega$ , R5 should be reduced, increasing current drain.

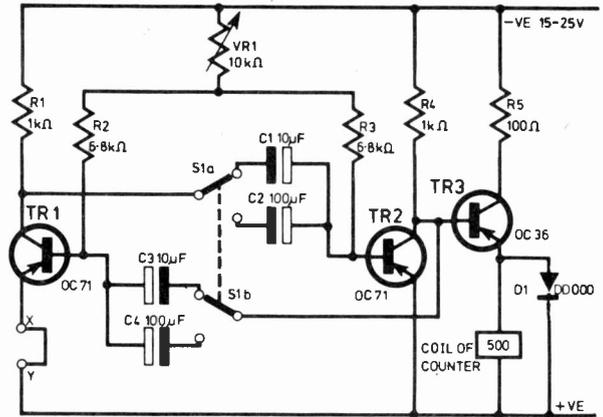


Fig. 1. Events Timer with Readout

For accuracy of timing the supply should be stabilised. Calibration could be by comparison with the Greenwich "pips" and resetting is not needed if a note is made of the reading each time it is used.

If it is required to synchronise the timer to some event such as a photocell switch then the trigger should be connected between X and Y in the emitter lead of TR1. This holds one capacitor discharged when the circuit is not oscillating so as to ensure fast and short-lived events can be handled.

Accuracy is not up to crystal-controlled standards and probably most applications will require only, say, about 5 per cent accuracy. However, the original exhibited a loss of only 3 seconds during one hour, an accuracy of better than 1 per cent.

G. Bachelor,  
Coventry.

## TWO-TONE AUDIO ALARM OSCILLATOR

FIGURE 1 shows the circuit diagram for a two-tone audio alarm oscillator, using two TTL i.c. packages.

IC1 is an SN7404N, its inverters wired in pairs to form three astable multivibrators, two oscillating at different audio frequencies, the other switching at a slow rate.

The output of one audio oscillator is gated with an output of the switching oscillator, the complementary output of the latter being separately gated with the second audio frequency. The two resultant outputs pass through a third gate, which drives a single transistor amplifier. The three NAND gates are contained in the SN7410 package.

If the two unused inputs to the first two gates are linked, a logical 1 at point X will cause the alarm to sound; a logical 0 turning it off. If these inputs are left open, the alarm sounds on connection of the power supply. The latter should be between 4.5 and 6V.

To alter the frequencies of the audio oscillators, change the values of C1 and C2; C5 and C6. Their associated resistors must NOT be altered.

This circuit was intended for use as an alarm in a digital clock, but for other purposes where a greater output is required a more powerful amplifier is needed.

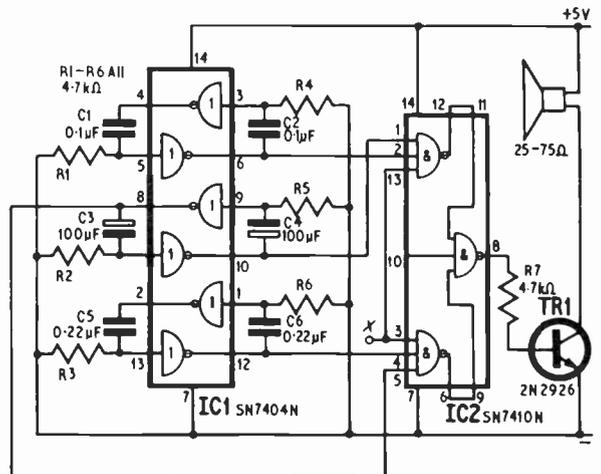


Fig. 1. Circuit diagram of the Two-tone Audio Alarm


If a transformer is to be used to power the alarm, then its output must be Zener stabilised.

B. Woodland,  
London, S.W.6.



**I.L.P. (Electronics) Ltd**

# 100 WATTS!

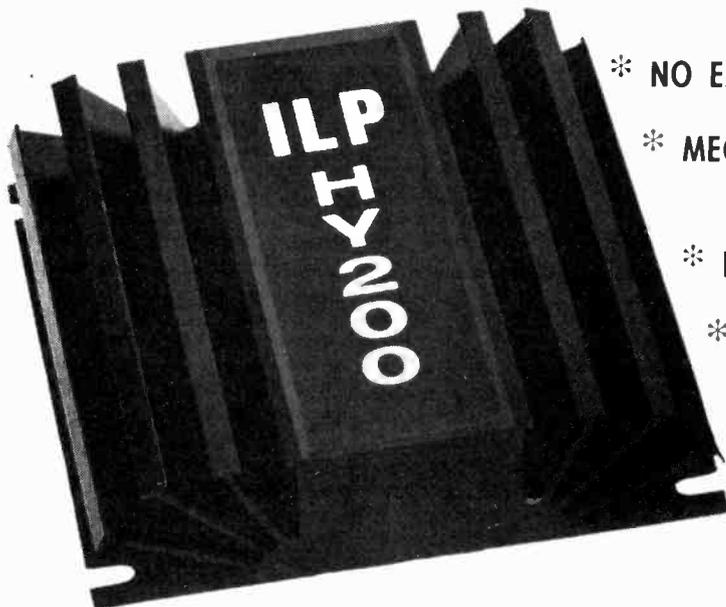

- \* NO EXTERNAL COMPONENTS
- \* MECHANICALLY & ELECTRICALLY ROBUST
- \* INTEGRAL HEATSINK
- \* HERMETICALLY SEALED UNIT
- \* ATTRACTIVE APPEARANCE
- \* LOW COST
- \* BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

**COMPLETE:** because the HY200 uses no external components!

**COMPLETE:** because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

**OUTPUT POWER:** 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k $\Omega$ . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 $\Omega$ . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz  $\pm$ 1Db. **SUPPLY VOLTAGE:**  $\pm$ 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

# SPECIAL INTRODUCTORY OFFERS-IMPORTER TO CONSUMER!

## ALL NEW GOODS—FULLY GUARANTEED—PLEASE ADD VAT TO PRICES SHOWN

**HILLS HEADPHONE JUNCTION BOX MODEL JB-3**



Designed to connect headphone to amplifier previously not fitted with headphone socket, or alternatively for remote switching. 3 position switch allows instant switching between speakers and headphones or both simultaneously.

Rec. Retail £1.75  
**OUR PRICE £1.25** P & P 15p

**HILLS DYNAMIC HEADPHONE MODEL H-707 VS DE-LUXE**



An extremely high quality headphone supplied with Padded Headphone and Earcups together with SLIDER volume controls for precise listening levels. Specially offered at an unbeatable price 8 ohms 20-20 000Hz.

Rec. Retail £7.95  
**OUR PRICE £5.75** P & P 25p

**CAR STEREO SPEAKERS MODEL CRB-200**



These dual purpose Car Speakers can be used for either shelf mounting or converted to door mounting. 5 watt Speakers ensure a brilliant audio performance.

Rec. Retail £5.25 \*Per pair  
**OUR PRICE £3.50\*** P & P 25p\*

Antex Soldering Iron CCN240, Rec. Retail £2.15. Our Price £1.60. P & P 10p.  
Antex Soldering Iron X25, Rec. Retail £1.93. Our Price £1.40. P & P 10p.  
Ferranti Radio Chlp ZN414, Our Price £1.10. P & P 5p.  
Hills Coiled Headphone Extension Cable 15ft. Rec. Retail £2.25. Our Price £1.45. P & P 10p.

**"HOMER" INTERCOM**



One of the leading makes ideal for home office factories etc. This 2 station intercom includes volume control and on-off switch. Supplied with 66ft. cable and batteries.

Rec. Retail £3.50  
**OUR PRICE £2.75** P & P 15p

**HILLS DYNAMIC HEADPHONE MODEL H-101 VSM**




Offered at a remarkably low price supplied with padded Headband and Earcups adjustable volume controls with stereo and mono switch 8 ohms imp. 30-18 000Hz.

Rec. Retail £5.25  
**OUR PRICE £3.15** P & P 25p

**PLINTH AND COVER FOR GARRARD Sp-25 III BSR MP-60.** Our Price £2.75, plus 65p P & P.  
**ELAC SPEAKER, 8in 8 ohm CERAMIC AND TWEETER.** £2.70, plus 20p P & P.


OTHER ITEMS AT BARGAIN PRICES OFFERED IN OUR AUDIO COMPONENTS CATALOGUE PLEASE WRITE FOR A FREE COPY (ENCLOSING 3p STAMP)

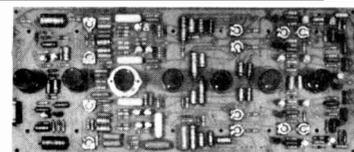**HILLS COMPONENTS LTD.**  
UNIT No. 6, MELNITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 27711



# PHONONICS
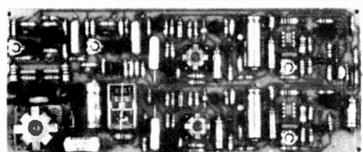
## NEW LOW PRICES FOR MANY PCB'S AND KITS



**AURORA**  
Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCR's) Rs, Cs, Pots, Cores—8 ch. £17.50; 4 ch. £9.95. Reg. PSU £3.65. PCB—4 ch. control (4 1/2in x 10 1/2in) Mk. 2—also holds rotary or slider pots £2.20. PCB (4 1/2in x 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCR's, £1.10. SCR's—1A, 50p, 3A, 55p.

**HI-FI TAPE LINK**  
(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot. Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, £11.80; Stereo, £18.70. PSU, £2.50. PCB—Main Circuit (3 1/2in x 9in) (Stereo) also holds 7 rotary or slider pots £1.85. PCB—Sub-Assembly. (2 1/2in x 6 1/2in) (Stereo) Mk. 2 holds Sw, Rs, Cs, Presets and mounts on Sw's, 80p.

**A. F. SIGNAL GENERATOR**  
(PE Nov. 72) S/c's, Rs, Cs, Pots, Sw's, PCB (2 1/2in x 4in) also holds Sw's, £3.15.

**BIOLOGICAL AMPLIFIER**  
(PE Jan./Feb. 73). P/A Sec.—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1 1/2in x 3 1/2in), £3.50. O/P Stages (S/c's, Rs, Cs, Pots and Sw's as req'd.), Alphaphone 53p, Cardiophone 66p, Freq. Meter £1.60, Vis-Feedback 55p. Audio Amp PC7 avail to order £5.20.

**REVERBERATION UNIT**  
(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, £6.80. PCB (2in x 1 1/2in) also holds sliders, £1.20. 9in Spring Unit avail to order, £3.75.

**RONDO**  
(PE CURRENT SERIES) DETAILS ON REQUEST

**ELECTRONIC PIANO**  
(PE Sep. 72 Jan. 73). PCB PRICES DOWN. Details in lists.

**VIBRASONIC GUITAR PRE-AMP**  
(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, £6.65. PSU, £2.80. PCB (3 1/2in x 10 1/2in) Mk. 2, also holds 7 rotary or slider pots, £1.75.

**TAPE NOISE LIMITER**  
(PE Feb. 72). S/c's, Rs, Cs, Pot. PCB (1 1/2in x 3in), £2.20. Reg. PSU and PCB (1 1/2in x 2 1/2in), £3.10.

**DOOR BELL YOPELLER**  
(PE Apr. 71). S/c's, Rs, Cs, Pots, PCB (3in x 3 1/2in), £4.40. L. sprk £1.30.

**GEMINI STEREO AMPLIFIER**  
(PE Nov. 70/Mar. 71) Stereo Sets & PCBs. Pre-amp—Rs, Cs, Pots, Mks—5w's—with jW MO Rs, £10.90—with jW or jW CF Rs, £8.90. PCB (3 1/2in x 10 1/2in) for sets with MO and jW Rs, also holds rotary or slider pots and Mks—Sw's, £1.90. Main Amp—Rs, Cs, Pots, £5.20. PCB (3 1/2in x 5in), £1.15. PSU—Rs, Cs, Pot, £3.70. PCB (2in x 4in), 65p.

**ULTRASONIC TRANSMITTER-RECEIVER**  
(PE May 72). S/c's, Rs, Cs, Pot. Relay, Dual PCB (2in x 5 1/2in), £3.90. T/ducers avail to order, £6.30 per pair.

**VERSATILE LIGHT EFFECTS UNIT**  
Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, £8.85. PCB (3 1/2in x 7 1/2in) Mk. 2, also holds pots, Sw, T/T T/fmr, £1.50. SCR's—1A, 50p, 3A, 55p.

**LOGICAL RADIO CONTROL**  
(PE Apr./Jun. 72)—Details in lists

**MODEL SERVO CONTROL**  
(PE Feb./Mar. 72)—Details in lists

**ALSO**  
PCBs as published (while stocks last) for:  
DIGITAL PSU (PE Aug. 72), 50p  
OSCILLOSCOPE P/A (PE Aug. 72), 33p  
SCORPIO (PE Nov./Dec. 71), 60p  
TRIFFID (PE Feb. 73), 60p

**PHOTOPRINT PROCESS CONTROL**  
(PE Jan./Feb. 72). For colour and B & W—finds exposure, controls timing, stabs, mains voltage, S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, £7.50. PCB (3 1/2in x 5 1/2in) also holds pots, Sw, relay, £1.20.

**GEMINI STEREO TUNER**  
(PE Apr./Jun. 72). Rs, Cs, Pot, £3.80. PCB as publ., £1.50.

**8 WATT AMPLIFIER**  
(PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, £2.50; Stereo, £5.20. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots and Sw, £1.50. Main Amp—S/c's, Rs, Cs, Pot—Mono, £3.65; Stereo, £7.30. PCB (2 1/2in x 3in) Mono, 60p.

**AND**  
DIGITRONIC (PW Mar. 73). Read-out PCB (1 1/2in x 3 1/2in), 60p.

**SOUND SYNTHESISER**  
(PE 1973)  
Details of PCB's & Components in lists. SOME PRICES DOWN.

**SEMICONDUCTORS**

AC128	20p	ZTX531	22p
AC176	20p	2N706	12p
AD161	40p	2N914	23p
BC107	9p	2N1304	20p
BC108	9p	2N2905	23p
BC109	9p	2N2907	22p
BC147	11p	2N3704	10p
BC148	11p	2N3704	10p
BC149	11p	2N3823E	31p
BC157	12p	2N5777	40p
BC158	12p	1N914	4p
BC159	12p	1N4001	6p
BC204	14p	1N4002	7p
BCY71	22p	1N4004	8p
BFY51	16p	1N4005	10p
BSY95A	12p	BA145	17p
OC28	45p	OA91	7p
OC71	12p	OA200	6p
OC84	24p	Z1J	50p
ORP12	48p	741s	36p
TIS471	24p	(8-pin DIL)	100p
ZTX107	9p	µA7815	£2.47
ZTX503	14p	(TO3 can)	150p

**CAPACITORS**

ELECTROLYTIC		TANTALUM BEAD		POLYESTER	
	(µF/V)		(µF/V)		C280AE
6p	220/10	6p	0.1/35	12p	0.01
6p	220/16	6p	0.1/35	12p	0.022
6p	220/25	10p	0.22/25	12p	0.033
6p	220/40	12p	0.47/35	12p	0.047
6p	226/63	18p	1.0/25	12p	0.068
6p	330/10	6p	1.0/35	16p	0.1
6p	470/6.3	6p	1.5/35	16p	0.15
6p	470/25	12p	2.2/16	12p	0.22
6p	500/64	40p	2.2/35	12p	0.33
6p	680/6.3	10p	4.7/35	12p	0.47
6p	680/25	18p	10/16	12p	0.68
6p	1000/10	12p	10/25	16p	1.0
6p	1000/25	20p	15/6.3	14p	1.0
6p	1000/40	40p	22/16	16p	1.0
6p	2200/25	45p	47/6.3	16p	1.0
6p	2200/40	50p	47/16	25p	1.0
6p	3300/63	110p			
6p	3300/100	£3			
6p	4700/16	60p			
6p	4700/25	75p			
12p	4700/40	93p			

**SWITCHES**

Makaswitch:	
Shaft assembly:	48p
Wafers:	33p
Screens (per pk of 5):	12p
Spacers (per pk of 10):	8p
Rotary:	
3P4W:	30p
Multipole Lever:	5p
4CL/ACL £1.30	
9CL/ACN £1.30	
Knobs:	6p
Slide:	14p
DPDT:	24p

**RELAYS**

2PCO 12V £1	
4PCO 12V £1.30	
Relay base & slip:	20p
Reed Relay:	85p
6-9V:	

**TRANSFORMERS (MAINS)**

Sub-min 12V-0-12V 50mA	£1.50
Min 0-6V 0-6V 6VA	£1.30
Min 0-12V 0-12V 6VA	£1.30
Min 0-20V 0-20V 6VA	£1.30
17V 1.6A	£1.88
0.25-30 0.25-30V 1.5A	£3.60

**POTENTIOMETERS**

Rotary:		Sliders—	
Dual:	12p	as and when available—	
Mono:	40p	most popular values with PCB mounting pins.	
Presets:			
Knobtrim:	or		
Mouldtrim—			
100Ω to 470Ω			
1K to 1M:	31p	Mono:	40p
Min Horiz.:	6p	Dual:	60p
Cermet Horiz.:		Knobs:	13p

**POST & PACKING**  
U.K. 10p per order. EXPORT at cost—please allow for this when ordering and state whether air or surface mail required—kit weights are shown in our list.

**V.A.T.**  
U.K. Orders only—add 10% to total cost or order.

**LIST**  
S.A.E. for free itemised list and with all enquiries please.

**GENERAL**  
All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published", PCBs are designed by Phononics. Pots are rotary unless stated as slider. All components are brand new, top quality, guaranteed. Prices and deliveries of individual components subject to stock availability.

**PHONONICS, DEPT. PE10, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW** **MAIL ORDER ONLY**

## RED PLANET PROBES

MARS is again coming to the forefront of space exploration. With the two new probes from Russia now well on their way, the plans for the fly-by by the USA in 1976, and the final *Viking* missions of landing craft as a prelude to the manned missions in the next decade, there is much to be done in preparation. A number of problems will need to be resolved for distant direct control of landed vehicles. If it is the case that the Russians intend to land a similar vehicle on Mars as they did on the moon, then the control from a distance will be somewhat difficult. Even at a close approach between the earth and Mars the controllers will be *seeing* their vehicle on the surface as it was four minutes earlier. Any guidance or correction will take a similar time to reach operation points.

There will be some areas which, though of great scientific interest, are too hazardous for landings. It therefore follows that the majority of the experiments will be automatic. Already a number of ingenious instruments have been designed for the *Viking* landing craft. These will sample the soil for biological activity.

The very ambitious search for life on Mars can only begin with instrumental techniques. Even so the instruments devised will only work if the basic chemistry of any Martian life that there may be, is similar to the basic chemistry of earth life. Should it be of a different chemistry then it may well be that any realistic search for life will have to wait until the 1980's for manned exploration. No one has succeeded in establishing a model of life chemistry that is entirely different from the carbon based system of earth life.

The final goal must of course be by manned exploration. The *Apollo* missions to the moon have more than made this point. It is only by this means that it will be possible to determine the other puzzles that need to be resolved. For example whether life on Mars may have developed from non living chemicals and whether the apparently lifeless planet may once have enjoyed a rich variety of life that has disappeared. Any relics of this could only be determined by live exploration.

## SPECULATIONS

There are a number of people who believe that there was once an abundance of water on the planet, though it is dry today. It is therefore possible that any form of life that developed, when the conditions were warm and the climate resembled that of the earth, would have had millions of years in which to grow hardy. Sufficiently so, in fact, that as the vital gases in the



BY FRANK W. HYDE

atmosphere escaped from the surface including water vapour, the life adapted to the severe conditions. As on earth the successive generations would exhibit the survival of the fittest and it could well be that there does exist a hardy plant life or something similar.

Some who have been thinking on these lines feel that with the possible colonisation of Mars the first platform will have been reached in space travel. Meanwhile Professor Carl Sagan has speculated that Mars is not dead but sleeping, and suggests that the climatic variations might well be extreme enough for there to be running water at times and the means for life, as we know it on earth, a possibility. These ideas are based on the presence of huge amounts of carbon dioxide frozen into the polar caps. Released as gas the density of the atmosphere would increase. The result could be a greenhouse effect which, with the prevailing meteorological conditions, could well support life.

## THE LUSTROUS PLANET

Venus will be having a visit from a USA probe in early 1978. This will be some 840 pounds in weight. When it arrives at Venus the four smaller vehicles will be ejected to penetrate the Venusian atmosphere. These four probes will consist of one large one with a 60 pound payload and three smaller ones of about 3 pounds. The big one will take about an hour and a half to reach the surface of the planet and the smaller ones about 75 minutes. The carrying vehicle will enter the atmosphere of the planet sending back data until it burns up. While all this is going on a sister probe will have been launched to arrive and orbit the planet at about the same time as the multiple probe. Thus the benefits of two observa-

tion vehicles will be available.

The discovery that there are vast vertical movements of the atmosphere of Venus presents another problem for astronomers. This pulsing of the clouds was detected by infra red telescopes. The indications are that the distance over which this pulsing takes place is about one kilometre.

At the present time there is no clue to the mechanism of this activity. Certainly enormous energy is indicated but where it originates is not known. Some further information may well be gathered by the spacecraft which will fly-by on its way to Mercury sometime next year.

## SOVIET AND FRENCH CO-OPERATION

The co-operation between France and Russia in some of the lunar activities is having a special orientation to geodasy. The laser reflectors, placed on the moon and on the earth in an attempt to measure accurate distances and changes, have provided important data. In consequence the techniques of this system has been developed to a stage where the satellites are to be brought into the picture.


Next year a launch is planned for a special satellite which will carry 60 corner reflectors for use with laser beams. It will have a purely passive role to play being in fact an orbiting reflector with a known position. The satellite will be known as *Starlette* with reflectors that will be grouped in threes on the outer surface on twenty plates making a total of sixty. It will have a very high density of 18.7 to ensure good dynamic stability. It will be some 26cm in diameter and be made largely of uranium. The orbit will be 50 degrees at a height of between 800 and 1,000km. It is hoped that the accuracy of the measurements will be of the order of 20cm over a period of 12 hours.

## SKYLAB RESULTS

One of the principal activities designed for *Skylab* was the detailed photography of the Sun. The results obtained in the first mission have been rewarding. In fact it would seem that the same situation exists on this venture as on so many others in space exploration, namely that a whole new vista opens up. In the case of these preliminary solar results the films show detailed structure of the Sun's atmosphere and the special changes that have been brought about by the magnetic field and the plasma which streams out from the Sun. In the X-ray part of the spectrum many small flares that were observed, developed in a few seconds. None of this type of phenomenon is observed from the ground.

# LOGIC TUTOR EXPERIMENTS..

## WIRED OR

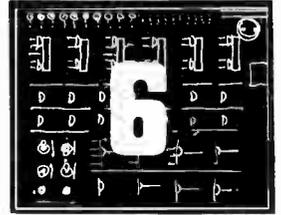

THE problem of last month was of rather a theoretical nature—to prove that the output of the four NAND gates (Fig. 5.4) was EXCLUSIVE OR. From the circuit layout and writing down the functions at each node we arrived at an output which was:

$$Q = \overline{\overline{A \cdot B}} + \overline{\overline{B \cdot A}}$$

The two double negates cancel and we are left with:

$$Q = A(\overline{B}) + B(\overline{A})$$

By applying De Morgan's Theorem to the A.B terms we get

$$Q = A(\overline{A + B}) + B(\overline{A + B})$$

There is a rule in Boolean Algebra known as the Distributive Rule which allows us to expand bracketted functions—rather like multiplying out brackets in conventional algebra:

$$Q = A \cdot \overline{A + B} + B \cdot \overline{A + B}$$

But  $A \cdot \overline{A}$  is always 0—if A is 1, NOT A must be 0; 1 AND 0 gives 0. We would get nought if A was nought and NOT A was one. Likewise  $B \cdot \overline{B}$  is always 0; so our expression becomes:

$$Q = (0 + 0) + (A \cdot \overline{B} + B \cdot \overline{A})$$

Note we have changed the sequence of the terms—this is permitted by the Boolean Commutative Rule—and grouped the functions (Associative Rule). Nought OR nought is always nought so the expression now becomes:

$Q = (0 + A \cdot \overline{B}) + B \cdot \overline{A}$  (again we have done a bit of re-grouping) 0 OR A.B is always  $A \cdot \overline{B}$ —you can prove this with a little truth table so we are left with the final expression that:

$Q = A \cdot \overline{B} + B \cdot \overline{A}$ —the EXCLUSIVE OR expression we arrived at last month.

### WIRED OR

The WIRED OR function is extremely valuable for economising on the number of gates used in a piece of equipment. To use the function you are limited to a logic type that uses passive pull up resistors in the output stages (such as DTL); it is not possible to apply the principle to conventional TTL gates which use the two output transistors in totem pole configuration but there are a number of TTL modules now available with open collectors and passive pull up which can be used. If you have made the Logic Tutor exactly as specified you will have used DTL and so can carry out this month's experiment; if you have used standard TTL please do not attempt the experiments as you will damage your gates.

Fig. 6.1. shows that WIRED OR is obtained by shorting together the outputs of two gates. If points X and Y were both at level 1 the output at node Q will obviously be 1.

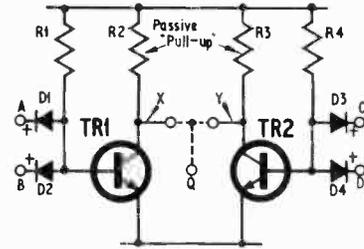


Fig. 6.1. The WIRED OR function is obtained by shorting the outputs of two NAND gates together

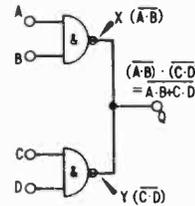


Fig. 6.2. The NAND gates showing the Boolean expressions at each node

If, however, the inputs A with B were such that TR1 was non conducting (i.e. the output from the left hand gate wanted to go to 1) but the inputs C with D forced an output of 0 from the right hand gate the combined output Q will have to be 0 because TR2 will act as a sink for current flowing through R2.

If you think about it you should see that the output Q has a level that can be specified by ANDing the levels the individual gates would have given had they not been connected together. If X wanted to be 1 but Y was 0 Q is nought and vice versa. Q will be 1 only when both X and Y want to be 1. Thus shorting the outputs of two DTL gates together effectively gives an AND function between the two outputs—a logic function obtained with no extra gates.

It might seem strange to call this WIRED OR but the name is derived from the overall function from inputs A with B and C with D to the output Q. Fig. 6.2 shows the functions ANDed for the combined output. The final expression is an INVERTED OR of the ANDed forms of the two pairs of inputs.

This function could be obtained by using the basic logic gates shown in Fig. 6.3—AND followed by OR followed by INVERT. The effect produced by wiring together two outputs of two NANDS to give WIRED OR is sometimes called

# LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

# ELECTROVALUE

## Electronic Component Specialists

### TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p
AC153K pnp germanium low power	32p
AC176K npn germanium low power	32p
AD161 npn germanium medium power	42p
AD162 pnp germanium medium power	40p
AF139 pnp germanium UHF	49p

PNP: BC107 13p, BC108 12p, BC109 13p, BC167 11p, BC168 10p, BC169 11p.

PNP: BC177 21p, BC178 19p, BC179 21p, BC257 12p, BC258 11p, BC259 13p.

Standard groupings available.

BD135 npn medium power	37p
BD136 pnp medium power	38p

### DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.


Other semiconductors: AC128, 17p; AF117, 32p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

Send S.A.E. for latest supplement of additional lines and price amendments to our No. 6 Catalogue

**ZENER DIODES** full range E24 values: 400mV: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

### DIN PLUGS AND SOCKETS

by Hirschmann, 4A rating

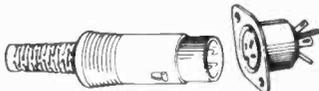


2 way LS —socket 10p, plug 12p  
3 way scr.—socket 10p, plug 12p  
5 way scr.—socket 11p, plug 15p

### TRANSISTOR ACCESSORIES

TO3 cover, 7p; Heat sinks 1°C/W, type 6W1, undrilled, 60p.
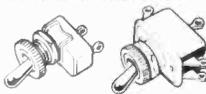
### SWITCHES

1011 SP5T toggle, 20p; 409 DPDT toggle, 29p (these are chrome plated, 2.5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.



### ROTARY SWITCHES

Radiospares Miniature Maka-switch (in assembly kit form). Shaft, 48p. Wafers: MBB-2P5V, 1P11W; BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, 32p each.

### WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 413W, 24p each.



### ELECTROLYTIC CAPACITORS

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V	AXIAL LEAD
Capacity $\mu$ F	0.47	—	—	—	—	—	—	—	10p
1.0	—	—	—	—	—	10p	—	—	7p
2.2	—	—	—	—	—	10p	—	—	7p
4.7	—	—	—	10p	—	—	—	—	8p
10	—	—	—	—	7p	8p	—	—	7p
22	—	—	—	—	7p	8p	—	—	8p
47	7p	—	7p	7p	—	7p	—	—	9p
100	8p	7p	7p	7p	7p	9p	—	—	11p
220	7p	8p	8p	8p	9p	10p	17p	—	27p
470	8p	9p	9p	10p	12p	17p	24p	—	43p
1,000	10p	12p	12p	17p	20p	24p	—	—	—
2,200	14p	17p	22p	25p	36p	40p	—	—	—
4,700	25p	28p	37p	41p	54p	—	—	—	—
10,000	40p	43p	—	—	—	—	—	—	—

Prices subject to amendment by the manufacturer.

### RESISTORS — 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 $\Omega$ –220K $\Omega$	E12	9	(see note below)	7.5
C	1/8W	5%	4.7 $\Omega$ –470K $\Omega$	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 $\Omega$ –10M $\Omega$	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 $\Omega$ –10M $\Omega$	E24	1	1	0.95 nett
C	1W	5%	4.7 $\Omega$ –10M $\Omega$	E12	2.5	1	1.6 nett
MO	1/2W	2%	10 $\Omega$ –1M $\Omega$	E24	4	3	2 nett
WW	1W	10%	1/20 $\Omega$ 0.22 $\Omega$ –3.9 $\Omega$	E12	7	7	6
WW	3W	5%	1 $\Omega$ –10K $\Omega$	E12	7	9	6
WW	7W	5%	1 $\Omega$ –10K $\Omega$	E12	7	9	8

Codes: C = carbon film, high stability, low noise. MO = metal oxide, Electroslit TR5, ultra low noise. WW = wire wound, Plesexy.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

### POLYCARBONATE—5% TOLERANCE


250V up to 0.1  $\mu$ F; 100V, 0.1  $\mu$ F and above.  
0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; 4p each. 0.068; 0.1; 0.12; 0.15; 4p each. 0.18; 0.22; 5p each. 0.27; 0.33; 6p. 0.39 7p. 0.47 8p. 0.56 10p. 0.68 11p. 1  $\mu$ F 13p. Prices subject to amendment by the manufacturer.

**Minitoron Digital Counter**  
Type 3015F. Seven Filament segment indicators to make 0.9 + decimal point. Compatible with standard logic modules, nett £2. Decoder driver type FLL 121T nett £1.36. DIL socket, nett £2.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.)

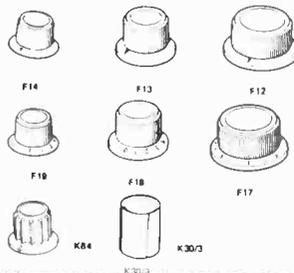
### KNOBS

All grub screw fitting for  $\frac{1}{16}$  shafts. Black. For other types —see Catalogue No. 6, p. 54.  
F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; K.B.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.


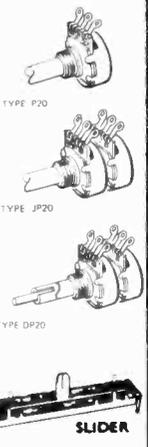
### POTENTIOMETERS

**Rotary, carbon track, double wiper**  
SINGLE P20 lin. 100  $\Omega$  to 2.2M  $\Omega$ , 12p; P20 log. 4.7K  $\Omega$  to 2.2 Meg. 12p; JP20 log. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 12p; Dual gang lin. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 42p; Dual log. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 42p; Log/antilog. 10K, 22K, 47K, 1M  $\Omega$  only, 42p; Dual antilog. 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.  
Only decades of 10, 22 and 47 available in ranges quote in pence.  
**DUAL CONCENTRIC DP20** in any combination of P20 values, 60p; with switch, 72p.  
**SLIDER**  
Lin. or log. 10K to 1 Meg. in all popular values, each 26p.  
Control knobs blk/white/red/yel./gr./blue/dk. grey/lt. grey, 5p each.  
**CARBON SKELETON PRE-SETS**  
Small high quality, PR lin. 100  $\Omega$ , 220  $\Omega$ , 470  $\Omega$ , 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M  $\Omega$ . Vertical or horizontal mounting, 5p each.



### TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps £2.85  
MT103 50V/1A plus 4 taps £2.55  
MT104 50V/2A plus 4 taps £3.50  
MT127 60V/2A plus 4 taps £3.80  
13T05 13V/1A, CT £1.25  
28T05 12+12V, 2-0-2V £1.65

### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS. 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90 Plus 60p part cost of carr.

Equaliser Assembly, £2.  
Loudspeaker Unit 59RM109, £2.45.  
Cabinet Kit (to Baxandall design), £10.45.


### DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request.  
Not allowed on nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more. Prices subject to alteration without prior notice. Prices quoted DO NOT include V.A.T. Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T. Overseas orders are exempt.

**POSTAGE AND PACKING FREE**  
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost. U.S.A. CUSTOMERS please contact ELECTROVALUE AMERICA, P.O. BOX 27, Swarthmore, PA 19081.
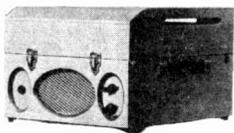
# ELECTROVALUE

(Dept. PE9), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 Telex 264475  
Eng. Reg. No. 1047769 Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB



## CASED AMPLIFIERS

Polished wooden cabinet 14x13x9in with hinged lid containing a sensitive (20 $\mu$ V) 4 valve amplifier with tone and volume controls, giving about 3 watts output to the 7x4in 3 $\Omega$  speaker. Also included

is a non-standard single motor tape deck. Easily converted to record player, guitar practice, baby alarm, etc. Supplied in good working condition with circuit diagram. Mains operated. Only £3 (£1 up to 200 miles, £1.20 over). Special cassettes, £1 (25p). Spare heads, 40p. Damaged machines from £1.50 to callers only. Discounts on quantity. Amplifier chassis, 2x ECC83, EL84, EZ80, £1-65 (35p).

## 71b BARGAIN PARCELS

Hundreds of new components—capacitors, resistors, switches, crystals, pots, PC boards, etc., etc. Outstanding value, £1-65 (37p). **COMPUTER PANELS:** Type E: 4 OC29, 4 ACY19, 8 other transistors, 35 diodes, etc., £1 (10p). Type H: 12 ASZ20+176 R's, C's & D's, 60p (10p). Parcel of 12 top quality boards, inc. power transistors, trim pots, IC's, etc., £2 (25p); 100 for £15 (£1); 1,000 £75 (£3); 3lb of lower quality, £1 (25p); 7lb, £2 (40p); 56lbs, £12 (c.p.d.). Pack of boards containing at least 500 components including 50 transistors, 60p (15p).

**NEW COMPONENTS:** 741C TO99 or 8 pin DIL, 32p; BC107-9, 8p or 14 for £1; 2N3055, 35p; 10+, 32p; 50+, 29p. OC140 25p; OC170 15p; BFY18 12p; BCY72 8p.

**PANEL METERS:** Clearing 200 meters from 10p each to callers only. Oscilloscopes available, also lots of odd units for spares. TF144G sig. gen. 85kHz-25MHz, from £12-£22. BFO No. 8 audio oscillator 50Hz-20kHz, £10. 10x crystals, 25 asstd., 75p (25p); 4p8w switches, 40p (10p); 2-8pF beehive trimmers, 5p; 3x 2 $\frac{1}{2}$ in 15A thermocouple meters, £1 (10p); delay line unit, operating around 1MHz with 7 transistor amplifier. Short delay, 40p; long delay, 60p (10p each). 1M $\Omega$  pots, 5p. 500 asstd. resistors £1 (15p); 20,000 £25 (£1); 100,000 £80 (£2); 300 asstd. capacitors £1 (25p).

Post in brackets, small parts 3p. VAT NOT INCLUDED—ADD 10% TO TOTAL. S.A.E. list, enquiries.

## GREENWELD ELECTRONICS (PE5)

All mail to 24 Goodhart Way, West Wickham, Kent, BR4 0ES. Shop at 21 Deptford Broadway, SE8 (next to old cinema). Tel. 01-692 2009. Callers most welcome.

## FM TUNER

NELSON-JONES

## PUSH BUTTON VARICAP

Tuning now available.

Six Position variable push button unit with individual frequency scales. Teak case and full metalwork matches the Texan amp.

Approved parts of this outstanding design. Featuring 0.75 $\mu$ V sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning. S.A.E. please for lists.

## PE RONDO

We are kit stockists for this excellent design

## LIGHT EMITTING DIODES

RED only 29p each 10 + 23p

GREEN only 69p each 10 + 59p

## 7 SEGMENT LED DISPLAY

0.325in Characters 0-9 and nine letters. TTL, DTL compatible. ONLY £2.46 each, p.p. 10p.

Please add 10% V.A.T. for U.K. orders.

## INTEGREX LIMITED, DEPT. P.E.

P.O. BOX 45, DERBY DEI ITW

Tel.: Repton (0283 89) 3580

Which of these 161 career opportunities could earn you £10... £15...even £30 extra a week?

In a job you really enjoy

How to qualify in your spare time for a better job

Make yourself worth more and you'll earn more. It's as simple as that. There are always plenty of people to do the routine work—but, right now, key jobs are going begging for lack of suitably qualified men to fill them. *The basic qualification is technical know-how.* When you've got that, you're in demand—out in front.

Are you ambitious—willing to set aside about 60 minutes a day for home study? If you are, B.I.E.T. can give you the technical knowledge you need

—change your entire future prospects.

It's easier than you think...

Make no mistake about it—you could do it. Most people have unused ability. A low-cost B.I.E.T. course helps you discover this hidden ability—makes learning enjoyable and so much easier than it used to be. The B.I.E.T. simplified study system gets results fast.

We've successfully trained thousands of men at home—equipped them for higher pay and better, more satisfying jobs, steered them safely through City and Guilds examinations—enabled many of them to put letters after their name.

With the help of B.I.E.T., you too could soon be on your way to better things.

## ACT NOW - DISCOVER FOR YOURSELF

It costs no more than a stamp to find out how we can help you. Tick the subject that interests you. Then post the coupon (or write). We'll send you an interesting 76-page book that will open up for you a whole new world of opportunity—and it's FREE

B.I.E.T., Aldermaston Court, Reading RG7 4PF.

## FREE 76-PAGE BOOK

can put you on the road to success through a B.I.E.T. Home Study Course. It's yours for the asking, without obligation. Post coupon for your FREE COPY TODAY!



## Choose from this list

- |  |  |
|--|--|
| <input type="checkbox"/> MECHANICAL                            | <input type="checkbox"/> Radio Servicing & Repairs |
| <input type="checkbox"/> A.M.S.E. (Mech.)                      | <input type="checkbox"/> Radio & TV Eng.           |
| <input type="checkbox"/> C & G Agric.                          | <input type="checkbox"/> Trans. Course             |
| <input type="checkbox"/> Mechanics                             | <input type="checkbox"/> TV Main. & Serv.          |
| <input type="checkbox"/> Diesel Eng.                           | <input type="checkbox"/> <b>AUTO &amp; AERO</b>    |
| <input type="checkbox"/> Eng. Inspection                       | <input type="checkbox"/> Aero Eng.                 |
| <input type="checkbox"/> Eng. Metallurgy                       | <input type="checkbox"/> A.M.I.E.                  |
| <input type="checkbox"/> Inst. Eng. & Tech.                    | <input type="checkbox"/> A.E.C. Cert.              |
| <input type="checkbox"/> Inst. Motor Ind.                      | <input type="checkbox"/> Auto Engineer.            |
| <input type="checkbox"/> Mainten. Eng.                         | <input type="checkbox"/> Auto Repair               |
| <input type="checkbox"/> Mechanical Eng.                       | <input type="checkbox"/> C & G Auto. Eng.          |
| <input type="checkbox"/> Sheet Metal Work                      | <input type="checkbox"/> Garage                    |
| <input type="checkbox"/> Welding                               | <input type="checkbox"/> Management                |
| <input type="checkbox"/> <b>ELECTRICAL &amp; ELECTRONIC</b>    | <input type="checkbox"/> MAA 1M Dipl.              |
| <input type="checkbox"/> A.M.S.E. (Elec.)                      | <input type="checkbox"/> Motor Vehicle             |
| <input type="checkbox"/> C & G Agric.                          | <input type="checkbox"/> Mechanics                 |
| <input type="checkbox"/> Mechanics                             | <input type="checkbox"/> <b>CONSTRUCTIONAL</b>     |
| <input type="checkbox"/> C & G Elec. Eng.                      | <input type="checkbox"/> A.M.S.E. (Civil)          |
| <input type="checkbox"/> C & G Elec. Inst.                     | <input type="checkbox"/> Architecture              |
| <input type="checkbox"/> C & G Elec. Tech.                     | <input type="checkbox"/> Building                  |
| <input type="checkbox"/> Computer Elect.                       | <input type="checkbox"/> Building Drawing          |
| <input type="checkbox"/> Elec. Maths                           | <input type="checkbox"/> Build. Foreman            |
| <input type="checkbox"/> Elec. Science                         | <input type="checkbox"/> C & G Agric.              |
| <input type="checkbox"/> Electronic Eng.                       | <input type="checkbox"/> Mechanics                 |
| <input type="checkbox"/> Electrical Eng.                       | <input type="checkbox"/> Carpentry & Join.         |
| <input type="checkbox"/> Install & Wiring                      | <input type="checkbox"/> Civil & Municipal         |
| <input type="checkbox"/> <b>MANAGEMENT &amp; PRODUCTION</b>    | <input type="checkbox"/> Engineering               |
| <input type="checkbox"/> Auto. Control                         | <input type="checkbox"/> Construction              |
| <input type="checkbox"/> Computer Prog.                        | <input type="checkbox"/> Surveyors                 |
| <input type="checkbox"/> Electronic Data                       | <input type="checkbox"/> Institute                 |
| <input type="checkbox"/> Processing                            | <input type="checkbox"/> Clerk of Works            |
| <input type="checkbox"/> Estimating                            | <input type="checkbox"/> Geology                   |
| <input type="checkbox"/> Foremanship                           | <input type="checkbox"/> Health Eng.               |
| <input type="checkbox"/> Inst. Cost & Man.                     | <input type="checkbox"/> Hydraulics                |
| <input type="checkbox"/> Accountants                           | <input type="checkbox"/> Inst. of Builders         |
| <input type="checkbox"/> Inst. Marketing                       | <input type="checkbox"/> Inst. Works &             |
| <input type="checkbox"/> Management                            | <input type="checkbox"/> Highway Sup.              |
| <input type="checkbox"/> Metrication                           | <input type="checkbox"/> Painting & Dec.           |
| <input type="checkbox"/> Motor Trade Man.                      | <input type="checkbox"/> Public Hygiene            |
| <input type="checkbox"/> Network Plan.                         | <input type="checkbox"/> Road Engineer.            |
| <input type="checkbox"/> Numerical Cont.                       | <input type="checkbox"/> Structural Eng.           |
| <input type="checkbox"/> Operational                           | <input type="checkbox"/> Surveying                 |
| <input type="checkbox"/> Research                              | <input type="checkbox"/> <b>GENERAL</b>            |
| <input type="checkbox"/> Personnel Man.                        | <input type="checkbox"/> Council of Eng.           |
| <input type="checkbox"/> Planning Eng.                         | <input type="checkbox"/> Inst.                     |
| <input type="checkbox"/> Production Eng.                       | <input type="checkbox"/> Farm Science              |
| <input type="checkbox"/> Quality Control                       | <input type="checkbox"/> General Educat.           |
| <input type="checkbox"/> Salesmanship                          | <input type="checkbox"/> Gen. Plastics             |
| <input type="checkbox"/> Storekeeping                          | <input type="checkbox"/> Pract. Maths              |
| <input type="checkbox"/> Work Study                            | <input type="checkbox"/> Pract. Slide Rule         |
| <input type="checkbox"/> Works                                 | <input type="checkbox"/> Pure & Applied            |
| <input type="checkbox"/> Management                            | <input type="checkbox"/> Maths                     |
| <input type="checkbox"/> <b>DRAUGHTSMANSHIP</b>                | <input type="checkbox"/> Refrigeration             |
| <input type="checkbox"/> A.M.I.E.D.                            | <input type="checkbox"/> Rubber Tech.              |
| <input type="checkbox"/> Design of Elec.                       | <input type="checkbox"/> Sales Engineers           |
| <input type="checkbox"/> Machines                              | <input type="checkbox"/> Tech. Report              |
| <input type="checkbox"/> Die & Press Tool                      | <input type="checkbox"/> Writing                   |
| <input type="checkbox"/> Design                                | <input type="checkbox"/> Timber Trade              |
| <input type="checkbox"/> Electrical                            | <input type="checkbox"/> University Ent.           |
| <input type="checkbox"/> Draughtsmanship                       |  |
| <input type="checkbox"/> Gen. Draughtsmanship                  |  |
| <input type="checkbox"/> Jig & Tool Des.                       |  |
| <input type="checkbox"/> Techn. Drawing                        |  |
| <input type="checkbox"/> <b>RADIO &amp; TELECOMMUNICATIONS</b> |  |
| <input type="checkbox"/> Colour TV                             |  |
| <input type="checkbox"/> C & G Radio/TV/                       |  |
| <input type="checkbox"/> Electronics                           |  |
| <input type="checkbox"/> C & G Telecomm.                       |  |
| <input type="checkbox"/> Tech.                                 |  |
| <input type="checkbox"/> Pract. Radio Elec.                    |  |
| <input type="checkbox"/> (with kit)                            |  |
| <input type="checkbox"/> Radio Amateurs                        |  |
| <input type="checkbox"/> Exam.                                 |  |

PLUS 58 'O' & 'A' LEVEL GCE SUBJECTS

tick here

IT PAYS TO BE QUALIFIED POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE20 Aldermaston Court, Reading RG7 4PF CE BPE20  
Please send full details and FREE 76-Page Book, without obligation.

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_

Accredited by C.A.C.C.

AGE \_\_\_\_\_



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

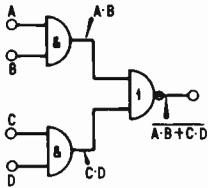


Fig. 6.3. Basic AND-OR-NOT configuration of circuit in Fig. 6.2 showing the economy effected by WIRED OR

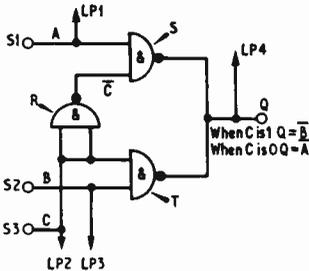


Fig. 6.4. Practical application of the AND-OR-NOT function for steering signals

an AND-OR-NOT gate—a frequently used function to enable two sources of digital waveforms to be selected alternately and fed (in an inverted form) into a common line.

Fig. 6.4 shows how you can demonstrate this on the Logic Tutor. The signal lines are A and B and digital waveforms can be simulated with switches S1 and S2; input C is the control line that selects the line we want to appear at the output Q. When C is 1 the output of gate S always wants to stay at 1 but the output of gate T wants to give an inverted form of input  $\bar{B}$ . AND the output of S with that of T and you get B. Waggle S2 and you will see the inverted signal appear at the output but signals from S1 (line A) will be inhibited. Make C go to 0 and the signal from A will pass while that from B will be inhibited.

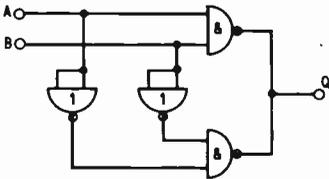


Fig. 6.5. The four gates plus the WIRED OR function in this circuit provide a well-known logic function. What is it?

Could you do this as economically without using the WIRED OR function? As an exercise try and sort out the logic of Fig. 6.5. The output of the gate configuration is quite well known; what is it?

by M. J. Hughes

Next month: The Half Adder.

## TO THE EXPERT CONSTRUCTOR

Do you know someone who would like to learn about electronics? EVERYDAY ELECTRONICS commences publication of a new series of electronic theory, allied to practical experiments, in the October issue.

### TEACH-IN '74

The series employs a special *Tutor Board* which has been designed to be easily constructed and yet provide a versatile, solderless basis for experimental work.

### PASS ON THE GOOD NEWS ALSO

**FREE INSIDE** a double sided Blue Print/Data Chart providing construction details of the *Tutor Board* plus information on component identification, colour codes, multipliers, abbreviations, etc. Designed to help both the beginner and the more experienced constructor.

OCTOBER ISSUE ON SALE  
FRIDAY, SEPTEMBER 21  
ORDER YOUR COPY NOW

#### THE GOOD COMPANIONS



Two magazines designed to complement each other in every way—together satisfying the needs of everyone involved in electronics.

# PE

# PERODO PART 2

# AUDIO AMPLIFIERS

BY R.A. COLE

## PRE-AMPLIFIERS

## POWER AMPLIFIERS

## TONE AND BALANCE CONTROLS

**I**n the first part of the RONDO series we described the subject of quadraphonics in general, its abilities, and the various systems available. In addition the construction of a CBS SQ quadraphonic decoder was explained in detail. Now we come to the power and pre-amplifiers and tone controls.

The Rondo system shown in block diagram Fig. 1.15 in Part 1 of the series uses integrated circuits extensively throughout. There are a total of 13 in the basic system, of which eight are in the power amplifier, tone control and pre-amplifier stages. The balance are two in the f.m. tuner, one in the a.m. tuner, one in the stereo multiplex decoder and one in the CBS SQ matrix decoder. An additional four are required for the full logic enhancement board.

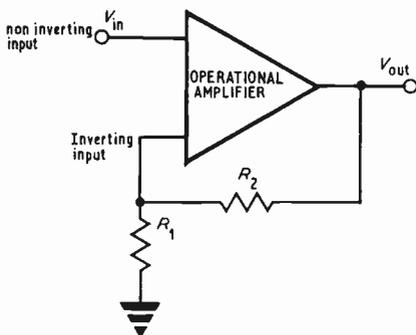


Fig. 2.1. Simplified schematic of an operational amplifier used in an audio application

Some of these integrated circuits perform specific complex functions, whilst others are used as "gain blocks". The eight used in the amplification stages fall in this latter category and are, in fact, operational amplifiers.

The Rondo power and pre-amplifiers use operational amplifiers of the 748 series which are available from many device manufacturers in a number of DIL and TO packages. The Rondo PC boards are drawn so as to accept either the 14 pin dual-in-line package or the 8 pin dual-in-line package.

Operational amplifiers have a number of points in their favour in amplifier design. For example, they replace quite complex discrete voltage gain circuits and require only a few external components and they can operate from a balanced supply which permits d.c. connection of some stages, thus reducing the use of electrolytic capacitors.

As they have a very high mid-band gain they can be very accurately equalised and yet have a good loop gain margin for reducing distortion. An inherently high ripple rejection allows them to work well on unregulated power supplies and reduces the chances of l.f. instability so often found in stereo systems due to large circulating earth currents.

High input and low output impedances simplify the design of feedback networks and a good common mode rejection, the ability to ignore spurious voltages which appear at both inputs rather than the differential signal inputs, is advantageous.

Fig. 2.1 is a simplified schematic of a typical operational amplifier, showing the two inputs and its application to audio amplification. The closed loop gain is determined as follows

$$\frac{V_{OUT}}{V_{IN}} = \frac{R_1 + R_2}{R_1}$$



## THE DISCERNING CONSTRUCTORS CHOICE :

- ★ *A Total Quadraphonic System*
- ★ *An advanced design AM/FM radio*
- ★ *Complete loudspeaker enclosure design*
- ★ *Flexible modular design allows individual to be incorporated in existing equipment*
- ★ *Switching facilities and modules for SQ, QS(RM) and CD4 systems*

### THE PRE-AMPLIFIERS

Two 748 operational amplifiers are used, one for each channel of the basic stereo system, one channel of which is shown in Fig. 2.3. The 748 (IC1) amplifies the incoming signal to around 100mV, whilst providing equalisations for the appropriate input signal.

There are four inputs selected by the selector switch bank.

The "Gram" input is compensated for RIAA disc characteristic, see Fig. 2.2, and requires an input of 3mV for full output. The compensation is carried out by the network R7, R9, C6, C7.

The other three inputs have a linear response, the gain of which is set by R8.

It will be noted that R7, which is in fact part of the RIAA network, is permanently in circuit. This is to reduce the switching transient caused by open-circuiting the feedback loop when using push-button switches. These switches are break-before-make types and if this precaution is not observed a momentary, but startling, screech will ensue. R7 and R8 are in parallel for all linear response inputs but as R7 is very large in comparison with R8 the resultant value is virtually the same as R8.

An output from the i.c. is taken via a 0.22 $\mu$ F capacitor from each channel to provide an isolated signal (prior to volume and tone controls) for tape recording.

### TONE CONTROL, VOLUME AND BALANCING

The tone controls, also shown in Fig. 2.3, are of the standard Baxandall type. The 748 integrated circuit IC2 provides the necessary loop gain requirements. There is only small interaction between the bass and treble controls and R12, R15 and R11, R14 provide the end stops for bass and treble controls respectively and limit their range (see Fig. 2.4).

A 10 $\mu$ F tantalum capacitor C11 is used at the output of the tone control stage before the master volume control. As the output voltage of the i.c. depends upon the input offset voltage, it can be of



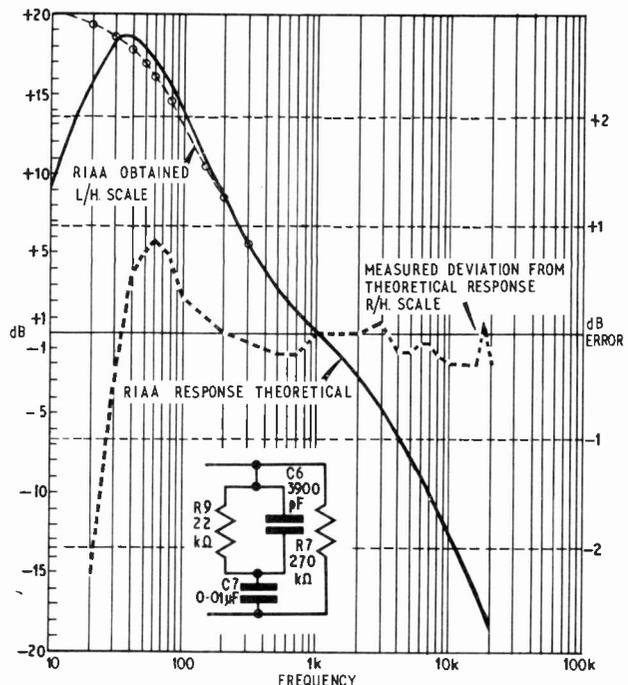


Fig. 2.2. Graphic representation of the playback response obtained for RIAA correction in disc playback and the filter network used

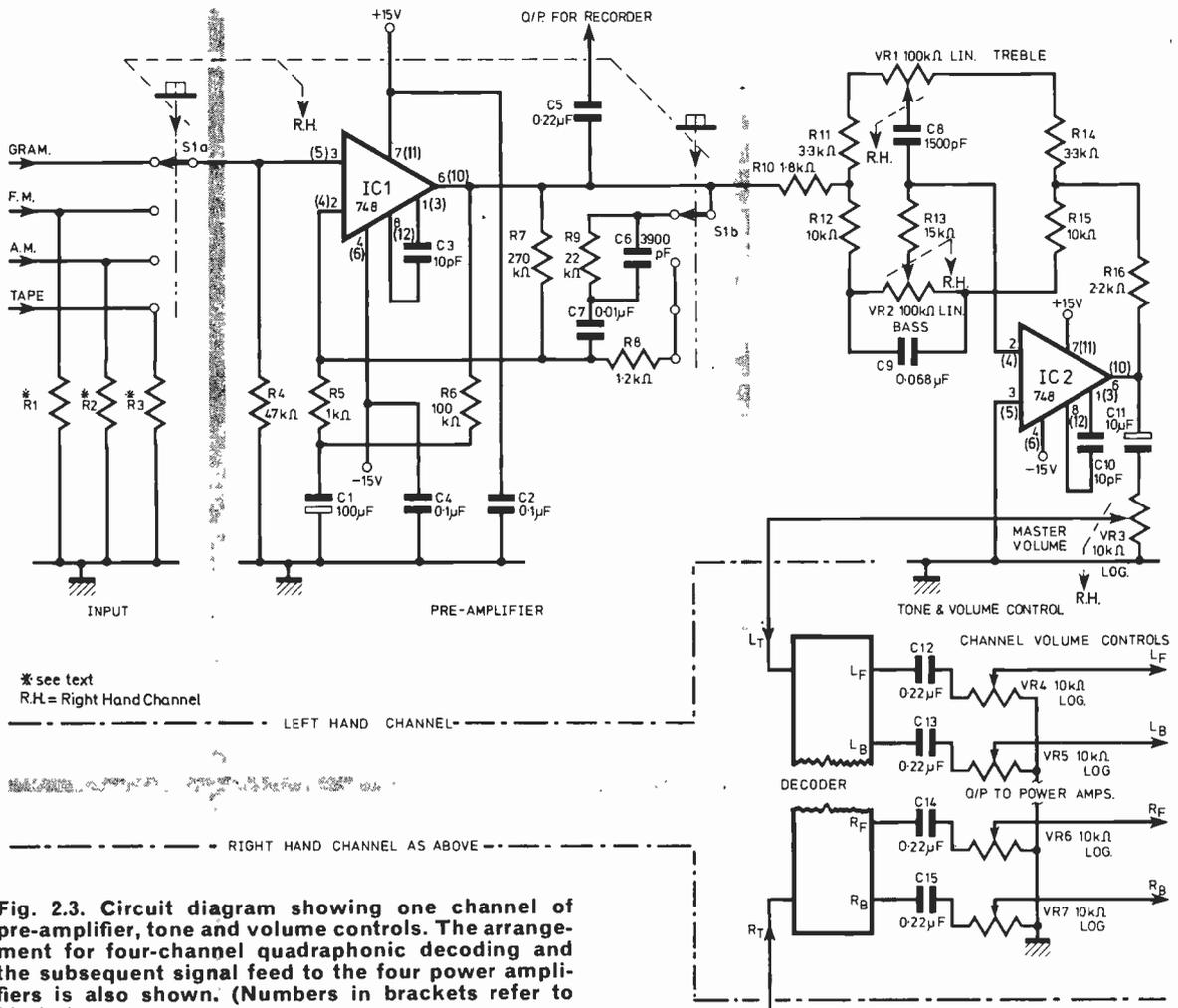

**Fig. 2.3.** Circuit diagram showing one channel of pre-amplifier, tone and volume controls. The arrangement for four-channel quadraphonic decoding and the subsequent signal feed to the four power amplifiers is also shown. (Numbers in brackets refer to 14-pin i.c.)

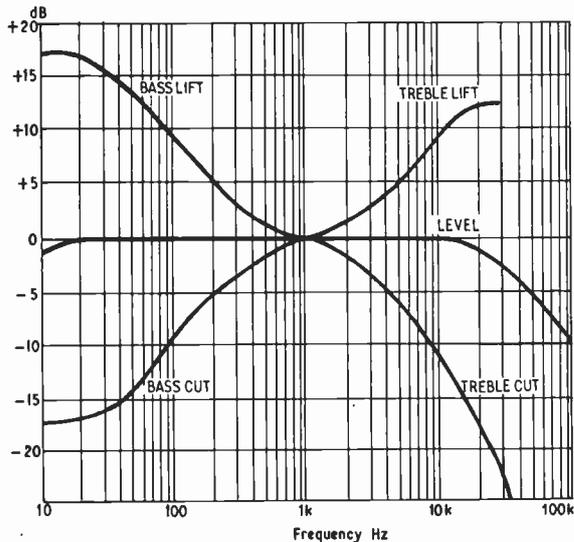


**Fig. 2.4.** Overall response of each tone control circuit

either polarity. The tantalum capacitor can withstand the maximum reverse polarity likely to be reached at any setting of the controls.


Fig. 2.5d shows a 1kHz square wave response of the pre-amplifier combined with the tone control stage with controls set level.

Signals have been processed as stereo signals up to the output from the master volume control. The signals are now passed through the quadraphonic decoder and are henceforth four channel signals; these pass, via 0.22μF capacitors C12 to C15, through the four balance controls VR4-VR7 to the power amplifiers.

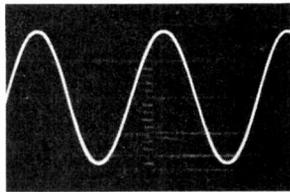
The balance controls provide total control over the level of each of the four channels and each can be faded to zero independently. This is considered to be superior to the normal left-right and front-back balance controls as fully independent control of each channel is far more flexible and fine control of low level listening can be obtained using the full swing of the master volume control VR3.



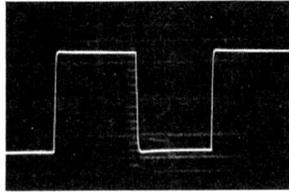
(a) 1kHz sine wave output at 21W, illustrating the onset of clipping



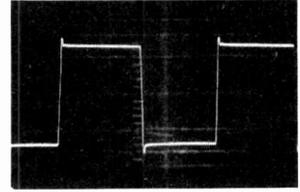
(b) A 1kHz square wave at 12W into an 8 ohm load



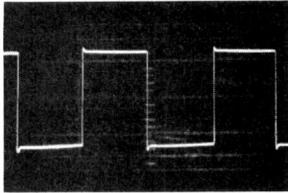
(c) As (b) but with 2µF in parallel with load



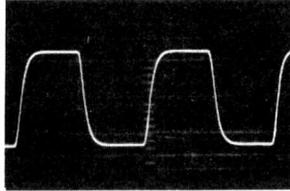(d) 1kHz square wave at output of pre-amplifier and tone controls at 100mV with tone controls in mechanically "level" position



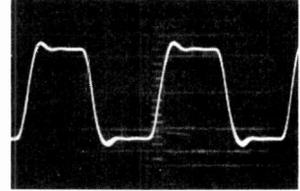(e) A 10kHz square wave at 12W into an 8 ohm load



(f) As (d) but with 2µF in parallel with load

Fig. 2.5. Oscilloscope photographs showing a variety of output responses for different operating conditions

## POWER AMPLIFIER

The overall voltage gain of the power amplifier, the circuit of which is shown in Fig. 2.6, is defined by the ratio of  $\frac{R17 + R20}{R17}$  and is about 40dB. The

reactance of C16 reduces the gain to unity at d.c. giving a final d.c. offset at the output of a few millivolts.

Normal loudspeakers, and those with inductive loads, e.g. crossover networks, can be coupled direct to the output stages without the use of output capacitors. Electrostatic loudspeakers can also be coupled direct.

Fig. 2.5b, c, e, and f show square wave responses at 1kHz and 10kHz with and without capacitive loads.

Fig. 2.5b, c, e, and f show square wave responses at 1kHz and 10kHz with and without capacitive loads.

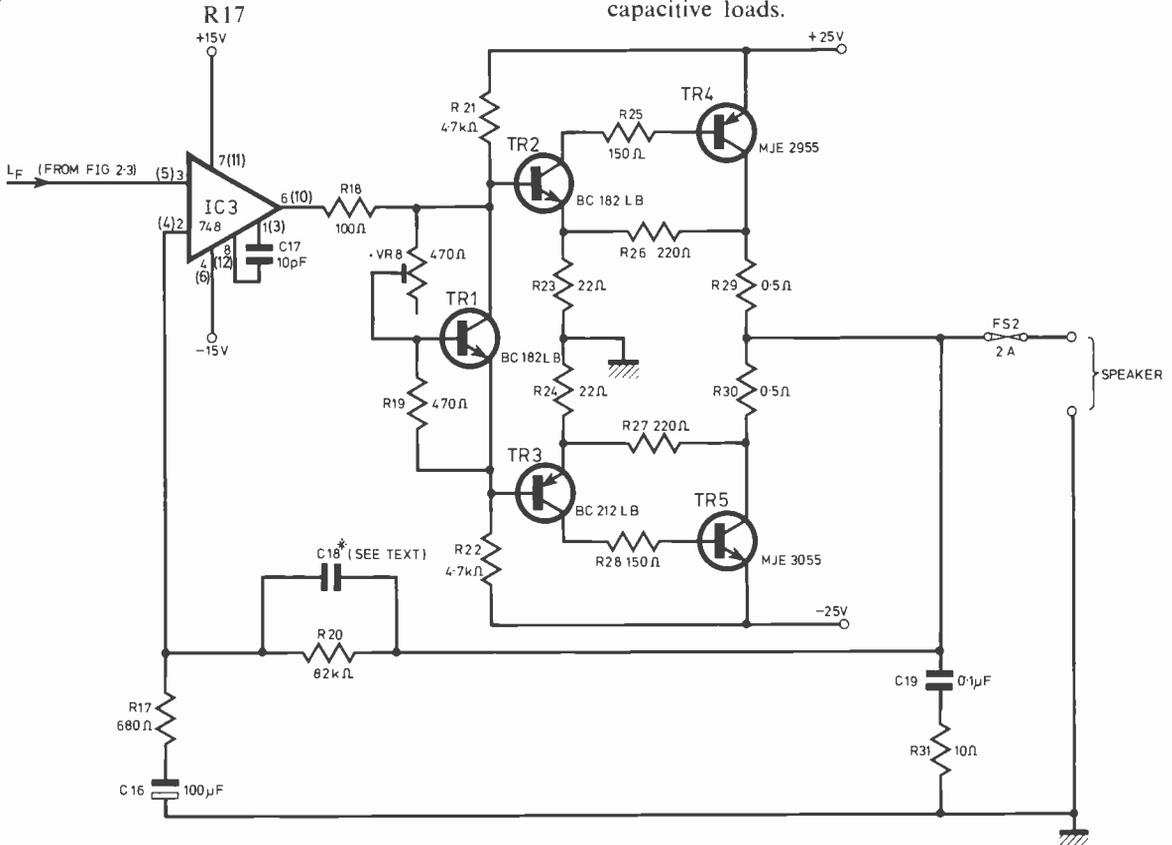


Fig. 2.6. Circuit diagram of the power amplifier (numbers in brackets refer to 14-pin device). Note that only one channel of a stereo pair is shown. There are four of these circuits mounted two to a board

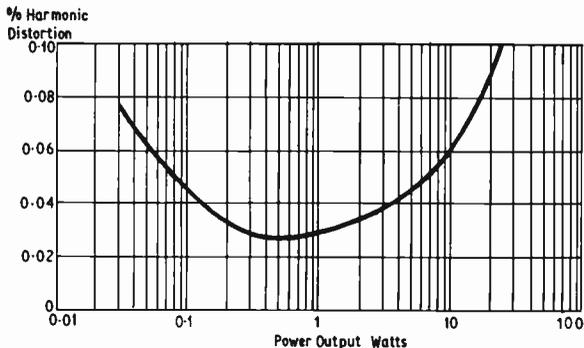


Fig. 2.7. Total harmonic distortion of power, tone, and pre-amplifier combination against power (log scale)

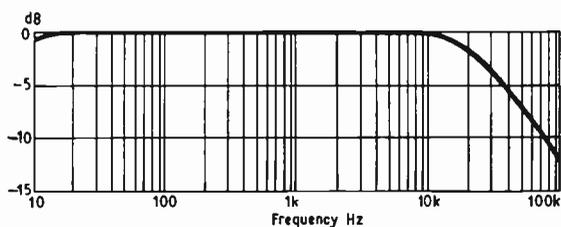


Fig. 2.8. Frequency response of the system at 1W into 8 ohms

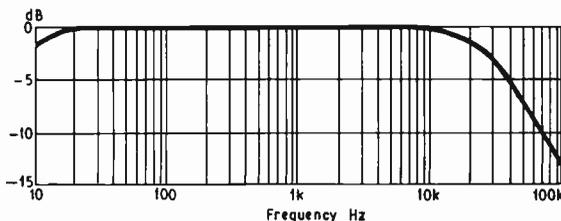


Fig. 2.9. The rated power bandwidth at 20W into 8 ohms

Although the open loop gain of the 748 i.c. op-amp is typically around 95dB, a stable closed-loop gain of some 20dB is utilised to give low harmonic distortion, see Fig. 2.7, and intermodulation products. It is therefore necessary to provide additional gain elsewhere.

This is achieved by use of a modified Darlington output stage in which resistors R26, R23 and R27, R24 apply attenuation of the feedback path in the Darlington pairs TR2, TR4 and TR3, TR5, giving a voltage gain of 20dB. The drivers TR2 and TR3 are fed by a phase splitter TR1 which also controls the bias conditions.

## QUIESCENT CURRENT

The quiescent current in the output stage, around 20mA, is controlled by the network R19 and VR8. VR8 is in the base-collector half and is preset for the correct quiescent current. Placing the preset in

this half of the network ensures that if the preset goes open circuit (the most common fault) the quiescent current in the output stages drops to a minimum and not, as so often happens, to a damaging maximum.

TR1 and TR2 are placed in contact with each other to provide a thermal path which enables the biasing to "track" easily so that, after prolonged full output, the quiescent current falls back to near normal in a much shorter time.

Two power amplifier channels are provided on each circuit board with a common heat sink. As much lower power is transmitted to the back channels from many quadraphonic recordings, one front and one back channel are routed to each board to balance the heat dissipation.

Fig. 2.8 shows the overall frequency response of the power amplifiers at 1W output into 8 ohms.

Fig. 2.9. The rated power bandwidth graph shows that, at full output, the frequency response is virtually the same as at lower outputs.

## DISTORTION

Reference back to Fig. 2.7 shows the small increase in harmonic distortion at low outputs. When drawn on a linear power scale (a very common way) this rise is masked and power outputs of 50mW or so are conveniently ignored.

Fig. 2.5a shows the sine waveform at 1kHz just at the onset of clipping (21W into 8 ohms), the condition being indicated by the bright-up at the crest of the waveform.

## CONSTRUCTION DETAILS

### Pre-amplifiers

Figs. 2.10a and b show the layout of the pre-amplifier board copper and components. Assembly follows normal practice. A space of  $\frac{1}{16}$ in is left between the plastic switch bodies and the board to prevent capillary action drawing the solder up into the switch mechanism.

### Tone, Volume and Balance Controls

Figs. 2.11a and b show the layout of this board. The slider controls should be soldered into the board after all other components have been assembled and soldered.

When the slider controls are mounted care should be taken to ensure that they are well seated onto the board surface so that the wiper levers are all parallel.

### Power Amplifiers

Figs. 2.12a and b show the layout of one of the stereo power amplifier boards. As mentioned earlier there is a common heat sink for the two amplifiers on each board.

The Motorola devices are supplied with a compression washer which should be tightened by the screw until the washer just deforms.

The Texas devices are supplied with a stepped insulating bush which should be inserted between the head of the screw and the fixing hole in the metal tab. The smaller mica insulating washer should have a thin smear of silicone grease applied to both sides to improve thermal conductivity between transistor and heat sink.

# PRE-AMPLIFIER MODULE

## COMPONENTS . . .

### PRE-AMPLIFIER

#### Resistors

R1, R101	Input matching resistors, to be discussed in future article	(2 off)
R2, R102		(2 off)
R3, R103		(2 off)
R4, R104	47k $\Omega$	(2 off)
R5, R105	1k $\Omega$	(2 off)
R6, R106	100k $\Omega$	(2 off)
R7, R107	270k $\Omega$	(2 off)
R8, R108	1.2k $\Omega$	(2 off)
R9, R109	22k $\Omega$	(2 off)

All  $\pm 5\% \frac{1}{4}W$  Hi-Stab carbon film

#### Capacitors

C1, C101	100 $\mu F$ 3V tantalum	(2 off)
C2	0.1 $\mu F$ polyester	(1 off)
C3, C103	10pF 30V polystyrene	(2 off)
C4	0.1 $\mu F$ polyester	(1 off)
C5, C105	0.22 $\mu F$ polyester	(2 off)
C6, C106	3900pF 30V polystyrene	(2 off)
C7, C107	0.01 $\mu F$ polyester	(2 off)

#### Integrated Circuits

IC1, IC101	ML748, $\mu 748$ or SN72748P	(2 off)
------------	------------------------------	---------

#### Switch

S1	4-pole 4-way Special (Lipar Isostat) selector switch—Sonax Electronics
----	--

#### Miscellaneous

Printed circuit board, link wire and connecting wires


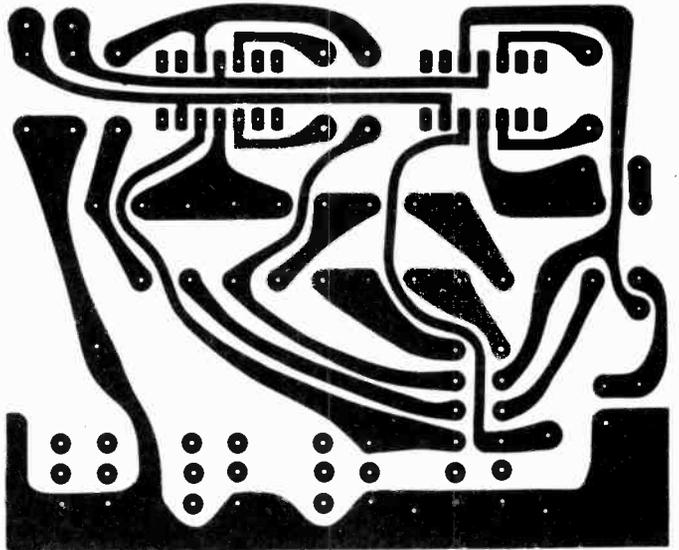
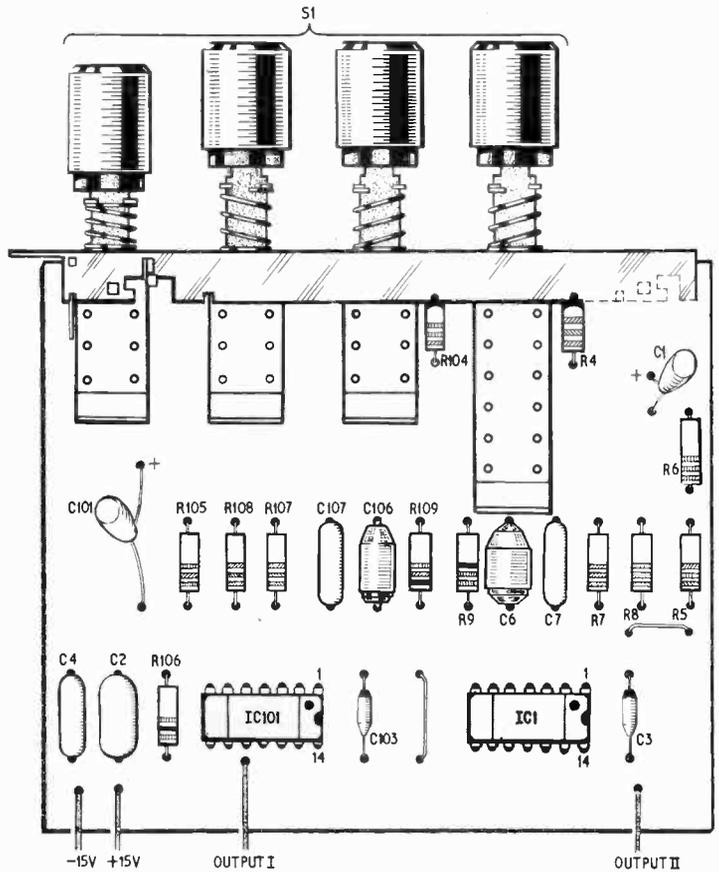
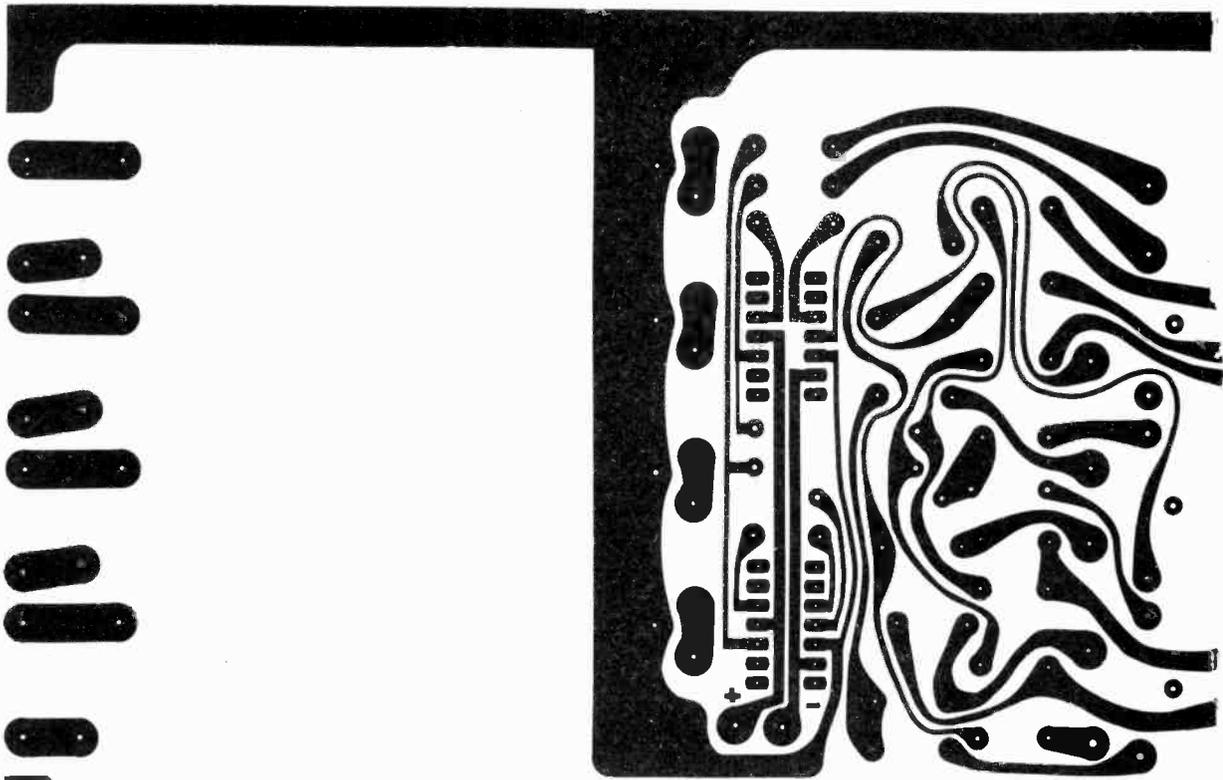


Fig. 2.10. Component layout and printed circuit master (full size) for the pre-amplifier board
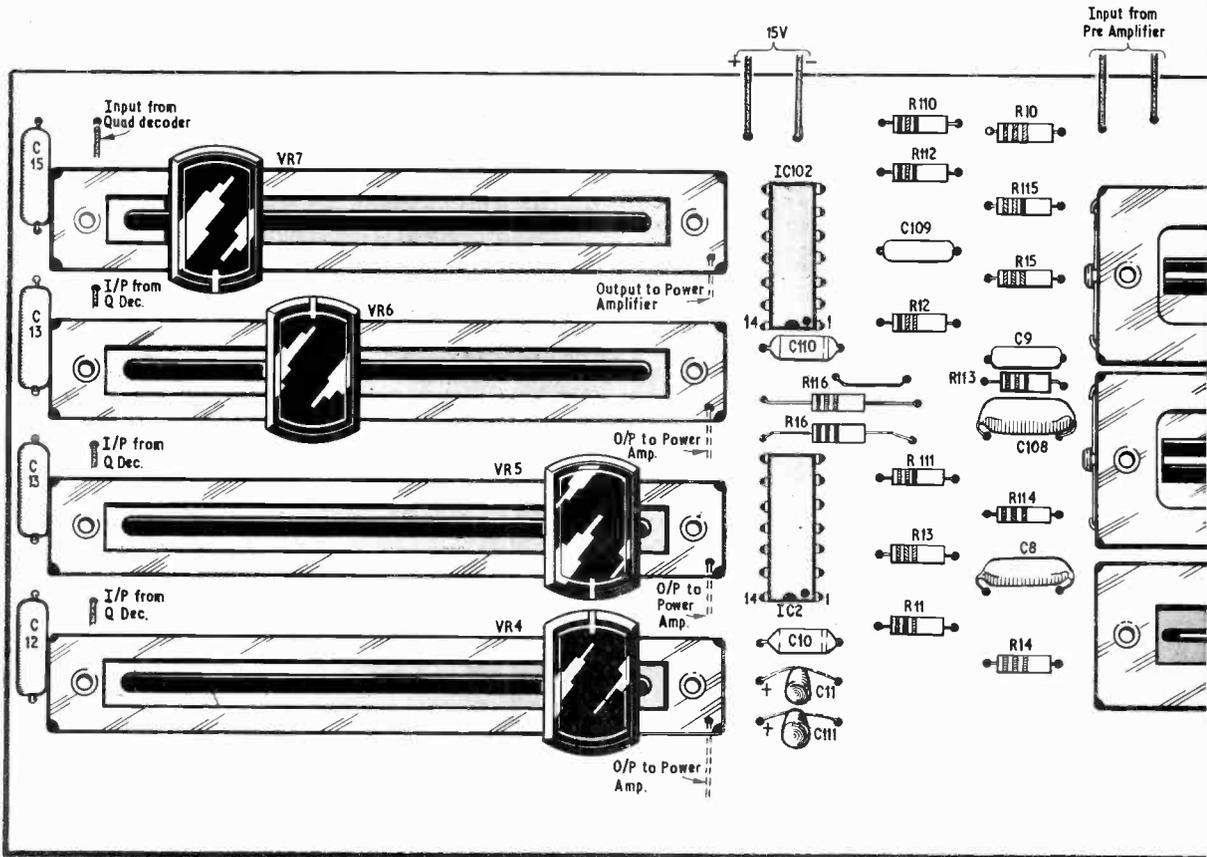
# TONE, BALANCE AND VOLUME CONTROL MODULE



## COMPONENTS . . .

### STONE AND VOLUME CONTROLS

#### Resistors

R10, R110	1.8k $\Omega$	R14, R114	3.3k $\Omega$
R11, R111	3.3k $\Omega$	R15, R115	10k $\Omega$
R12, R112	10k $\Omega$	R16, R116	2.2k $\Omega$
R13, R113	15k $\Omega$		

All 5%  $\frac{1}{4}$ W Hi-Stab carbon film (2 off each required)

#### Capacitors

C8, C108	1500pF 30V polystyrene	(2 off)
C9, C109	0.068 $\mu$ F polyester	(2 off)
C10, C110	10pF 30V polystyrene	(2 off)
C11, C111	10 $\mu$ F 16V bead tantalum	(2 off)
C12-C15	0.22 $\mu$ F polyester	(4 off)

#### Potentiometers

VR1/101	100k $\Omega$ lin.	} 2-gang (Alps) Sonax Electronics	(1 off)
VR2/102	100k $\Omega$ lin.		(1 off)
VR3/103	10k $\Omega$ log.		(1 off)
VR4-VR7	10k $\Omega$ log. (Alps)		(4 off)

#### Integrated Circuits

IC2, IC102	ML748, $\mu$ 748 or SN2748P	(2 off)
------------	-----------------------------	---------

#### Miscellaneous

Printed circuit board, connecting wires

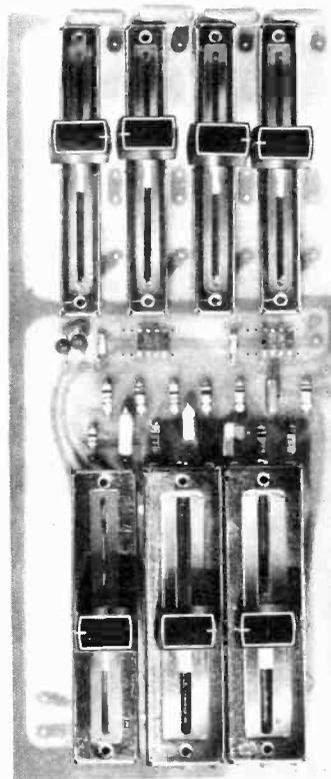
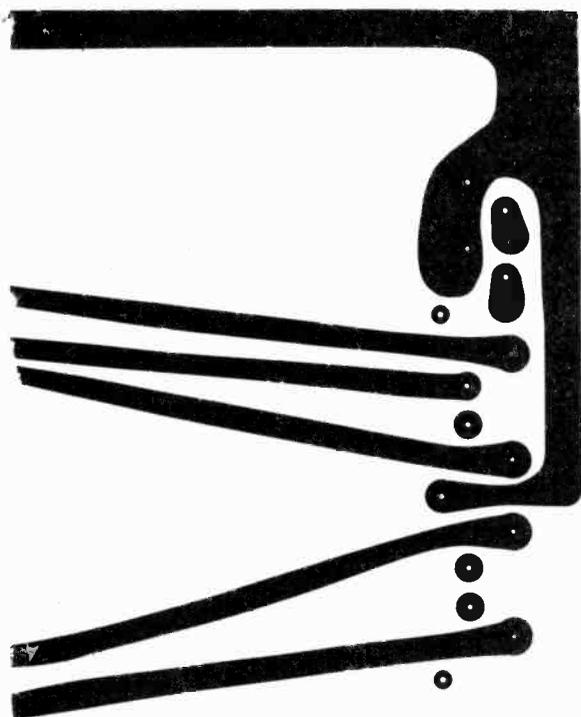
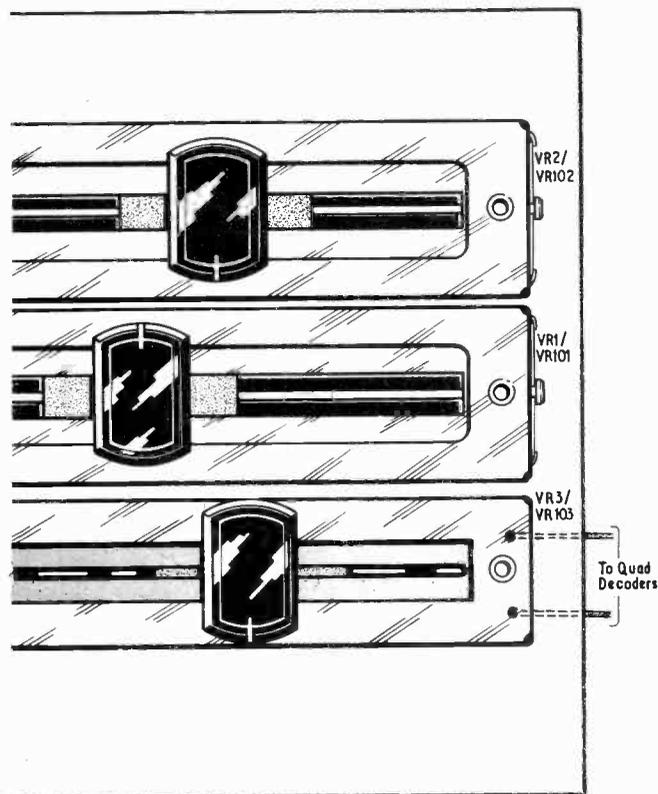


Fig. 2.11. Component layout and printed circuit master (full size) for the tone control and balance board. A photograph of a prototype board is also shown


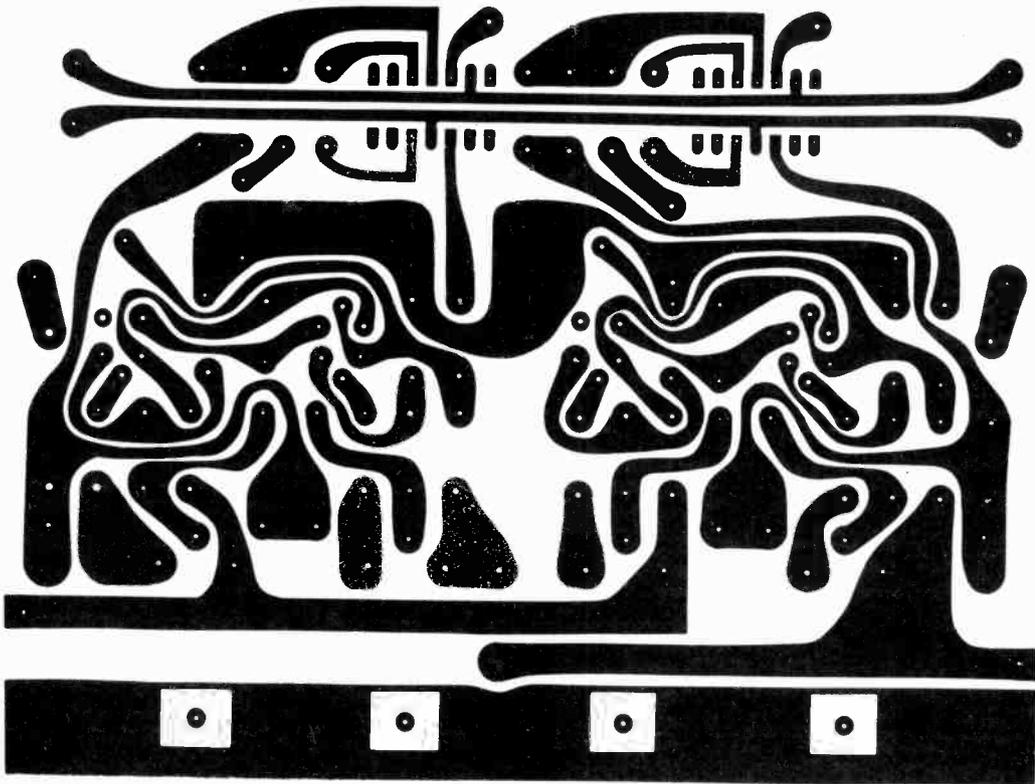


Fig. 2.12. Component layout and printed circuit master (full size) of one of the two power amplifier boards. Components on the right are similar to the left channel

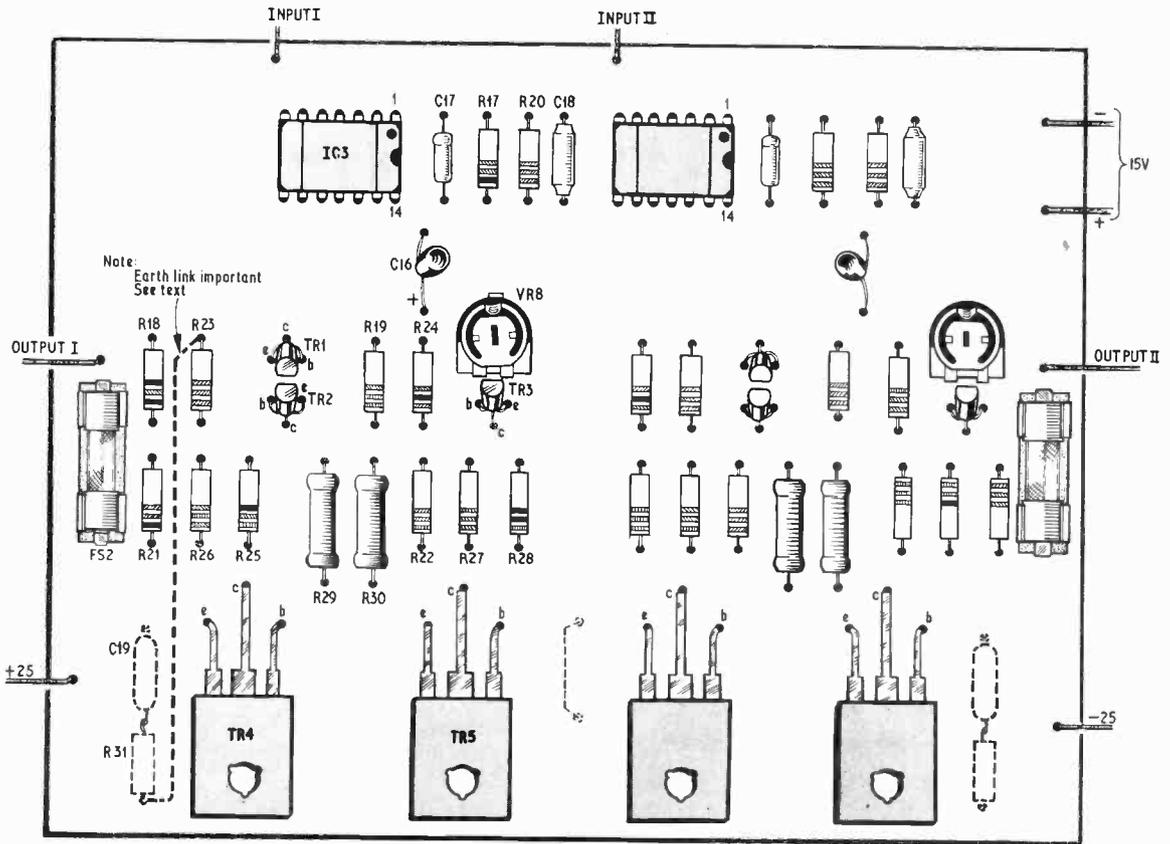

# PHASE LOCKED LOOPS

BY J.B. DANCE M.Sc.

**D**URING the past two or three years a type of circuit known as the phase locked loop has aroused enormous interest in a number of fields, especially in that of radio receiver design. These articles will provide readers with a simple explanation of the operation of phase locked loops, their advantages and limitations, together with some of their practical applications.

The phase locked loop offers certain advantages over the other types of detector used in radio receivers. It can also be employed in a wide variety of other applications such as in frequency synthesisers, in frequency shift keying demodulators, in f.m. generators, in tape recorder flutter meters, for electric motor speed control, etc.

## SINGLE INTEGRATED CIRCUITS

The principles of the phase locked loop have been known for many years (an account of the synchronous reception of radio signals was published as long ago as 1932). However, the circuits are so complex that it has not been very economical to construct them with discrete components. In the past three years, however, complete phase locked loops have become available as single integrated circuits. Their potential possibilities have stimulated great interest especially in radio receiver circuitry.

Currently available phase locked loops can replace nearly all of a receiver intermediate frequency strip (including the detector) with a single integrated circuit. The frequency of operation is set by a single component connected to the integrated circuit, whilst another component can be used to control the selectivity.

## THE PHASE LOCKED LOOP

The phase locked loop contains an electronically controlled oscillator which can be synchronised with an incoming signal.

The basic operation of the phase locked loop may be illustrated by the block diagram of Fig. 1.1.

In subsequent parts we shall see that this basic system can be employed as a demodulator for f.m. signals, and with some additional stages, it can be employed to demodulate a.m. signals.

## FREE-RUNNING FREQUENCY

If no input signal is fed to the phase locked loop of Fig. 1.1, the voltage controlled oscillator operates at a frequency known as the "free-running" or "centre" frequency. This frequency can be controlled by changing the value of certain components external to the integrated circuit phase locked loop.

In the free-running condition, the phase detector provides no output signal (or error signal). There is therefore no control voltage fed to the voltage controlled oscillator.

If an input signal is now applied to the system of Fig. 1.1, the phase detector will compare the phase of the input signal with that of the signal generated by the voltage controlled oscillator. The error voltage at the output of the phase detector is dependent on the phase difference between the two signals. It may be either positive or negative, according to which of the signals is leading or lagging the other in phase.

The error signal is passed through a low-pass filter, after which it is amplified to produce the signal which is used to control the frequency of the oscillator. The control voltage alters the frequency of the voltage controlled oscillator and can make it approach the frequency of the input signal. If the input frequency is close enough to the free-running frequency of the voltage controlled oscillator, the latter will become locked to the input frequency.

## PHASE DIFFERENCE

When the phase locked loop is "in lock", the voltage controlled oscillator frequency is identical with that of the input signal, but in general there is a

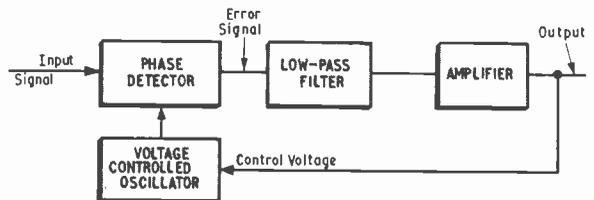


Fig. 1.1. Basic block diagram of a phase locked loop

certain finite phase difference between the signals. This phase difference must be present in order to generate the error voltage which is required to change the voltage controlled oscillator frequency from its free-running value to the input signal frequency.

## FEEDBACK SYSTEM

The feedback system employed in a phase locked loop enables the frequency of the voltage controlled oscillator to change automatically as the input frequency changes. A slight change in the input frequency will result in a phase change between the input signal and the signal from the voltage controlled oscillator. The error signal produced by the phase detector will automatically adjust itself so that the voltage controlled oscillator frequency is kept the same as the input frequency.

## PHASE COMPARATOR

It is instructive to note that the phase comparator is essentially a multiplier circuit which acts like a frequency changer. It operates on the input and voltage controlled oscillator signals so as to generate the sum and difference of these frequencies.

The sum frequency is unable to pass through the low-pass filter of Fig. 1.1. However, when the loop is locked the difference frequency is zero (since the two frequencies being fed to the phase comparator are the same) and a d.c. voltage is produced which can pass through the low-pass filter and keeps the loop locked.

If the input frequency is changing with time (as in an f.m. signal), the error signal will contain some frequencies which are much lower than the input frequency. The low-pass filter may transmit these frequencies almost unattenuated, in which case the voltage controlled oscillator will track the input frequency and the loop will remain locked.

Most phase detectors are also sensitive to the amplitude of the signals.

## LOCK RANGE

The lock range of a phase locked loop is the range of input frequencies over which the loop remains locked to the input signal. The lock range is also known as the tracking range.

The term "hold-in" range is sometimes used to denote the maximum allowable difference between the centre frequency and the signal frequency at which the loop just remains locked. It is one half of the lock range, since the latter extends on each side of the centre frequency.

In a loop which is locked to the input frequency, the error voltage is of zero frequency and will therefore always be transmitted by the low-pass filter. The lock range is therefore not affected by the characteristics of this filter.

The lock range is limited by the maximum value of the control voltage which can be generated in the loop and thus the corresponding frequency of the voltage controlled oscillator.

The lock range can be many times the bandwidth of the signals accepted by the loop. This means that if the frequency of the input signal varies somewhat, the voltage controlled oscillator frequency will follow it, but at all times the bandwidth will be narrow so that the amount of noise is small. Effectively this means that the tuning of the receiver is automatically corrected as the input frequency changes.

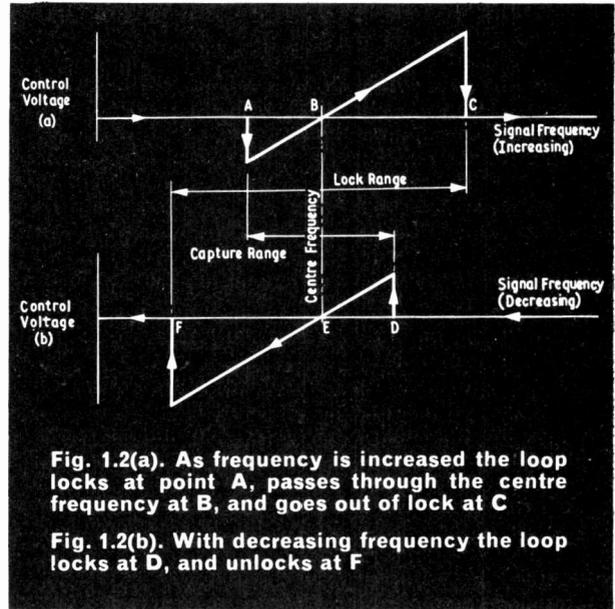


Fig. 1.2(a). As frequency is increased the loop locks at point A, passes through the centre frequency at B, and goes out of lock at C

Fig. 1.2(b). With decreasing frequency the loop locks at D, and unlocks at F

## CAPTURE RANGE

The capture range is the range of input signal frequencies which can cause the loop to become locked. The capture range is generally smaller than the lock range. In other words, if a signal near to one of the ends of the lock range is applied to an unlocked loop, it will not bring the loop into lock. However, a loop to which this signal is being fed will remain in lock.

The capture range never exceeds the lock range. It is a measure of how close the input signal frequency must be to the centre frequency of the loop for locking to take place.

If the signal frequency in Fig. 1.2(a) is slowly increased, the loop will suddenly become locked at point A which is the edge of the capture range. As the frequency is increased further, the control voltage applied to the voltage controlled oscillator decreases linearly with frequency and passes through a value of zero at the free-running frequency, B. The loop remains in lock until the frequency reaches point C, the edge of the lock range. The control voltage returns to zero when the system comes out of lock.

If the frequency is now reduced, one obtains the characteristic illustrated by Fig. 2(b). The loop does not come into lock until point D is reached, the edge of the capture range. The centre frequency, point E, is reached when the control voltage is zero and the loop finally comes out of lock at point F.

## THE CAPTURE PROCESS

The mechanism of the capture process may be examined by first considering a loop which is not yet locked to the input frequency. The phase detector produces sum and difference frequencies of the two signals being fed to it, but both of these frequencies are so high that they cannot pass through the low-pass filter. The voltage controlled oscillator therefore continues to operate at its free-running frequency.

If the signal frequency now approaches the free-running frequency, the difference frequency decreases until it falls within the pass band of the

low-pass filter. The part of the difference frequency voltage which passes through the low-pass filter causes the voltage controlled oscillator frequency to move towards the input signal frequency. This reduces the difference frequency further so that it is transmitted more easily through the low-pass filter and exercises a greater effect on the oscillator.

The mechanism is essentially one of positive feedback. It has the effect of causing the voltage controlled oscillator frequency to suddenly become the same as that of the input signal.

Capture occurs when the difference frequency between the input and the voltage controlled oscillator signals can pass through the low-pass filter without being attenuated so much that it cannot produce an adequate control voltage. The capture range is therefore determined mainly by the maximum frequency which can pass through the low-pass filter.

The capture effect determines the selectivity of the phase locked loop circuit. Thus selectivity is determined by the characteristic of the low-pass filter.

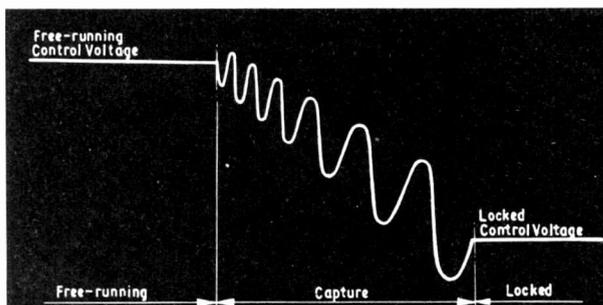


Fig. 1.3. Diagram showing transient locking characteristic

### THE LOCKING TRANSIENT

When the voltage controlled oscillator is free-running and as the loop approaches lock, the output from the phase detector contains a sinusoidal frequency equal to the difference frequency between the two signals. When the input frequency moves to a point within the capture range of the loop, the difference frequency is fed through the low-pass filter to the voltage controlled oscillator.

This oscillator frequency is modulated for a moment by the difference frequency and the latter will therefore vary with time. Once locking has occurred, the output from the phase comparator is of zero frequency.

The control voltage thus changes from the constant zero voltage in the unlocked state through an oscillating signal containing the difference frequency to a non-zero constant voltage when the loop is locked to the input frequency.

In the intermediate state during the capture process, the control voltages consists of a non-sinusoidal asymmetrical waveform containing a steady (or d.c.) component, as shown in Fig. 1.3.

The steady component causes the voltage controlled oscillator frequency to move towards the signal frequency. The difference frequency component in the control voltage gradually increases during the capture transient, as shown by the increasing width of the peaks in Fig. 1.3.

### PULL-IN TIME

The pull-in time of a phase locked loop is the time taken for the loop to become locked to the input frequency. In some systems the pull-in time can be very short—even less than the time for one oscillation of the difference frequency; in this case lock can be established without any oscillations in the frequency of the voltage controlled oscillator occurring.

The pull-in time depends on the difference between the initial free-running frequency and the signal frequency, the bandwidth of the low-pass filter and the overall gain around the loop. In general locking will take place more rapidly when the frequency of operation is relatively high, since a given number of cycles of the waveforms occur in a shorter time.

One might expect that locking would be instantaneous when the input frequency is exactly equal to the free-running frequency. This is not necessarily true, however, since although the frequencies are the same, the phases of the waveforms may be different and it is the phase differences which are detected.

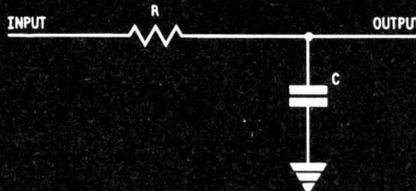


Fig. 1.4. The simplest low-pass filter circuit

### THE LOW-PASS FILTER

The low-pass filter is often extremely simple — merely a resistor and capacitor, as shown in Fig. 1.4, however, it has a very profound effect on the performance of the phase locked loop.

We have already seen how the characteristics of the low-pass filter can control the capture range. This filter also increases the pull-in time, since a rapid change of the output voltage from the phase comparator will produce a slower change in the output from the filter.

The use of the low-pass filter improves the noise rejection characteristics of the phase locked loop. If an interfering noise signal reaches the input of the phase comparator, the output will change almost instantaneously. However, the low-pass filter will delay any change in the oscillator frequency. The filter therefore acts as a short term memory which keeps the voltage controlled oscillator locked to the input frequency during a short noise pulse. Similarly, the loop remains locked during a short period when fading of the signal occurs.

### SELECTIVITY

The selectivity of the whole phase locked loop is controlled by the characteristics of the low-pass filter. Although the low-pass filter operates at a

relatively low frequency, its characteristics are effectively imposed on the high frequency response of the phase locked loop. A simple low-pass filter can provide selectivity which is equivalent to that of a conventional superheterodyne receiver containing six tuned circuits at the intermediate frequency.

Phase locked loops are especially useful for receiving radio signals which are "buried" in noise. Their pass band can be made almost ideal for this purpose.

If the bandwidth of the low-pass filter is sufficiently narrow, the signal-to-noise ratio at the output of the voltage controlled oscillator can be considerably better than that at the input. The use of a low-pass filter with a large time constant will provide greater noise rejection and immunity to a momentary loss of the input signal, but it does result in a lower tracking rate, a reduced capture range and a longer pull-in time.

The low-pass filter limits the rate at which the voltage controlled oscillator can track the input signal. If the frequency of the latter changes at a greater rate than the maximum rate for the loop used, the loop will not remain locked. Capture will not occur at the new input frequency if this is outside the capture range. A low-pass filter with a relatively high cut off frequency will produce a higher tracking rate, but the ability of the loop to reject short term noise will be reduced.

## THE INPUT LEVEL

If the input signal is relatively large, its amplitude will be limited either in the phase locked loop or in the preceding circuits. The capture range and the lock range are then independent of the signal amplitude.

Although a phase locked loop can act as its own limiter, greater freedom from noise and from spurious signals can be obtained when the input level is below the threshold at which limiting occurs. When the amplitude is high enough to drive the system outside the limit for linear operation, there are more cross modulation signals formed. However, higher input levels do result on a reduced pull-in time.

**Next month: f.m. and a.m. demodulation techniques will be described.**

## PRACTICAL ELECTRONICS

### ● INDEX

An index for volume 8 (January 1972 to December 1972) is now available price 11p inclusive of postage.

### ● BINDERS

Easi-binders with a special pocket for storing blueprints and data sheets, etc., are available price £1.10p inclusive of postage. State required volume, e.g., Vol. 1, 2, 6.

Orders for Binders and Indexes should be addressed to the Post Sales Department, IPC Magazines Ltd., Carlton House, 66 Gt. Queen Street, London, W.C.2.

# POINTS ARISING

## WIDE RANGE PULSE GENERATOR (June 1973)

Capacitor C1 should be positioned in the circuit adjacent the contact of S1 and not, as shown in Fig. 2, in the direct connection from pins 2 and 3 to C2. It is shown correctly in the wiring diagram of Fig. 3.

## THE 555 TIMER IC (June 1973)

It has been pointed out by a reader that any constructor attempting to use this chip to construct a 1:1 mark-space ratio monostable as described on pages 486 and 515 may run the risk of damaging TR1 because of a reduction of RA below a suggested value of 1 kilohm. The manufacturers have, in fact, not considered taking the resistance value below 1 kilohm.

## AUDIO COMPRESSOR (August 1973)

In the base diagram of the 2N3708 transistor in Fig. 2 the base and emitter leads are shown transposed. Copper strip should be broken at F12. Resistor R13 should go to K29 not J29.

## LIGHTING CONTROL UNIT (July 1973)

Page 612, the end of the fourth paragraph under the side heading "THE THYRISTOR" should read "so that the voltage applied to the load looks like Fig. 2 (c) not 3 (c)." Also, at the end of the section headed "TESTING" Fig. 4 should read Fig. 3.

## PHASING UNIT (September 1973)

Changing the 10kΩ linear dual-gang potentiometer VR2 for a logarithmic type will enhance the performance of the unit.

## P.E. SOUND SYNTHESISER (March 1973)

### POWER SUPPLY REGULATORS

It should be noted that the maximum input voltage for the voltage regulator  $\mu$ A7815 should not exceed 36V. Thus if the 30V Rec. Transformer by R. S. Components is being used in the power supply it is necessary to connect the 25V windings instead of the 30V windings given in March P.E.

Constructors using alternative 30V transformers should protect the regulator by means of an 8.2V 10W Zener diode connected between the bridge and C1 positive (cathode to the diode bridge). The Zener should be mounted on a heatsink, (2in x 2in 14 s.w.g. aluminium would suffice), which can be bolted to the power supply subframe lip above the transformer.

It will be necessary to insulate the heatsink from the subframe and separate heatsinks should be used for each Zener. The Z3B series of Zeners by Semitron would be suitable for use in the suggested circuit.

## 550 VOLT MEGOHMMETER (August 1973)

The function of VR2 was omitted. It should be adjusted so that the meter reads full scale with the leads shorted.

## SOUND SYNTHESISER LECTURE

Our author Mr. G. D. Shaw will present a lecture-demonstration at the coming International Audio Festival and Fair, Olympia, London. The lecture will be given at 2 p.m. on Tuesday, October 23, 1973.

# The Sinclair Cambridge... no other calculator is so powerful and so compact.

## Complete kit - £24.95! (PLUS VAT)

### The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

### Truly pocket-sized

With all its calculating capability, the Cambridge still measures just  $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$ . That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

### Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

### The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.



### Features of the Sinclair Cambridge


- \* Uniquely handy package.  $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$ , weight  $3\frac{1}{2}$  oz.
- \* Standard keyboard. All you need for complex calculations.
- \* Clear-last-entry feature.
- \* Fully-floating decimal point.
- \* Algebraic logic.
- \* Four operators (+, -, x, ÷), with constant on all four.
- \* Constant acts as last entry in a calculation.
- \* Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- \* Calculates to 8 significant digits, with exponent range from  $10^{-20}$  to  $10^{79}$ .
- \* Clear, bright 8-digit display.
- \* Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

# A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

## Contents:

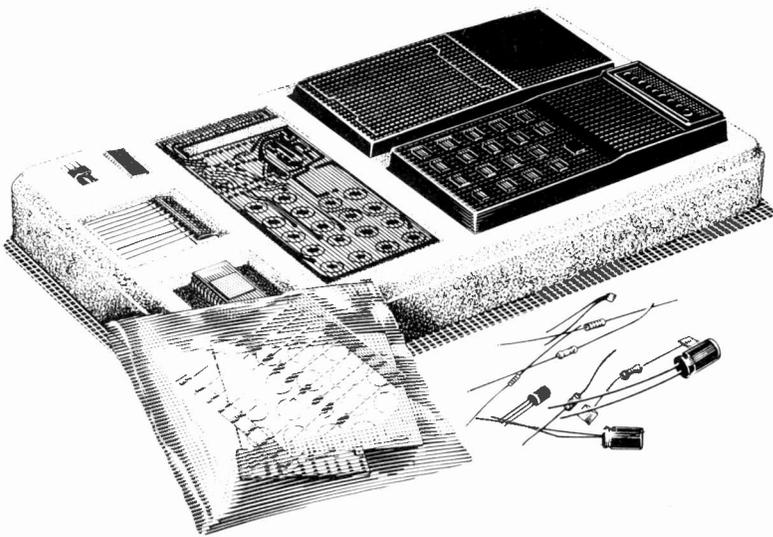
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.


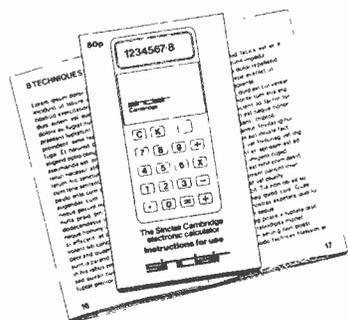
## This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines  
Tangents Reciprocals nth roots  
Currency Compound  
conversion interest  
and many others...

# sinclair

Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire  
Reg. no: 699483 England  
VAT Reg. no: 213 8170 88

## Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

## Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

**Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)**

**Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)**

PE1073	
To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdonshire, PE17 4HJ	
Please send me	Name _____
<input type="checkbox"/> a Sinclair Cambridge calculator kit at £24.95 + £2.50 VAT (Total: £27.45)	_____
<input type="checkbox"/> a Sinclair Cambridge calculator ready built at £29.95 + £3.00 VAT (Total: £32.95)	Address _____
*I enclose cheque for £ _____, made out to Sinclair Radionics Ltd, and crossed.	_____
*Please debit my *Barclaycard/Access account. Account number _____	_____
*Delete as required.	PLEASE PRINT

# PE Sound Synthesiser 9

## VOLTAGE CONTROLLED & DIFFERENTIAL AMPLIFIERS

By G.D. SHAW

THIS part describes the construction and operation of the Voltage Controlled Amplifiers, the Differential Amplifier and finalises the interconnection details outlined in Part 1 of the series.

### OUTPUT AMPLIFIERS

The heart of each of the Voltage Controlled Amplifiers is the Motorola MFC6040 electronic attenuator which was described in Part 7 of the series and which, by means of an externally derived voltage, enables the input signal to be attenuated by 77dB or amplified by 13dB.


Two Output Amplifiers are employed, each having two stages, and arranged to be operated in parallel with cross-coupling between the final stages by means of panning controls. The general arrangement is shown in block form in Fig. 9.1. The first stage consists of a two input resistive mixer at the front end of the MFC6040 which has, for each channel, a separate control amplifier. Output from the first stage is led to a pan-pot which can route the signal to either of the output stages direct or to both channels at a range of intermediate levels.

Fig. 9.2 shows the theoretical circuit of the left channel Output Amplifier in which IC1 provides the variable gain input mixer, IC2/TR1 the control amplifier and IC3 the final output stage. The right channel is identical in design except that the 'a' side of the pan-pot is coupled to IC3 of the left channel instead of direct to the right channel output stage. This is so that clockwise rotation of the pan-pots will route signals to the right channel and anticlockwise rotation to the left.
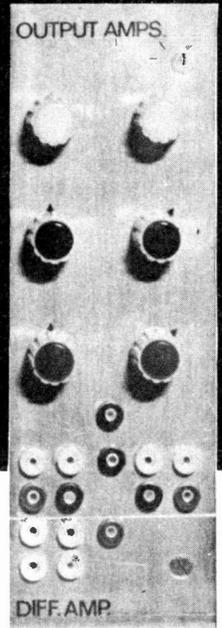
### PAN-POTS

The pan-pots themselves are designed to allow the smoothest possible transition when swinging the signal from one channel to the other and in such a way that equal increments of rotation of the pot give approximately equal incremental changes in the level of the signal.

The pots consist of two tracks ganged together and wired back-to-back so that as the output of one track increases the output of the other decreases by a similar amount. The ideal arrangement is when one of the tracks follows a logarithmic law with the other being anti-logarithmic. Unfortunately the manufacture of accurately matched tracks of this type is difficult and purpose built pots having the desired characteristics are not easily available and generally expensive.



The pan-pots in the Synthesiser represent a compromise in that they utilise linear tracks which, for most practical purposes, are made logarithmic in action by the addition of a relatively low value load resistor (R11 and R12 in Fig. 9.2).

### PRACTICAL PROBLEMS

On completion of the module and having checked that each channel's performance characteristics are similar for a given input signal the following procedure should be adopted for determining the electrical centre of rotation of the pan-pots. Set both pots to approximately the mid-point of rotation and apply a signal of about 250mV to the input of one channel only. The remaining inputs should be grounded.

With the gain on the appropriate channel turned full up monitor the output stages of both amplifiers and adjust the appropriate pan-pot until the output signals are exactly equal. With a well matched pot the electrical centre should be quite close to the


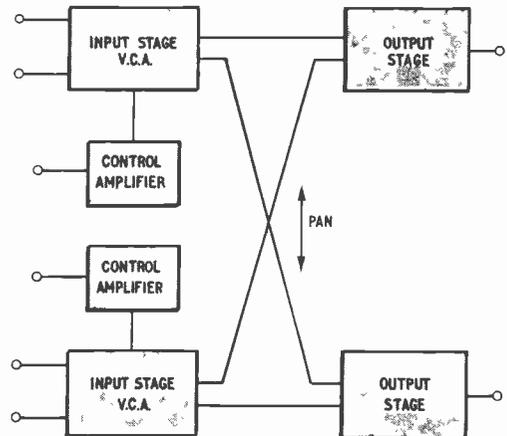


Fig. 9.1. General arrangement of voltage controlled Output Amplifiers

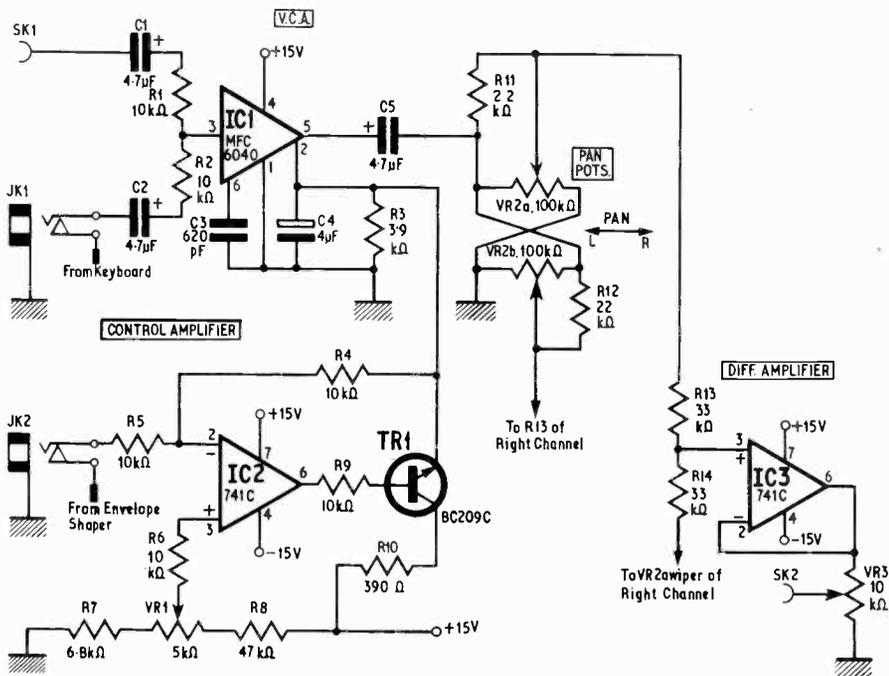

**Fig. 9.2. Output Amplifier for left channel, right channel is identical. Note that if the Envelope Shaper is not connected by prewired link or if auto-programming of gain is not required JK2 must carry a grounded jack plug in order that full range of attenuation gain is achieved**

## COMPONENTS . . .

### OUTPUT AMPLIFIERS (Left and right channels)

#### Resistors

- R1-R2 10k  $\Omega$  (4 off)
- R3 3.9k  $\Omega$  (2 off)
- R4-R6 10k  $\Omega$  (6 off)
- R7 6.8k  $\Omega$  (2 off)
- R8 47k  $\Omega$  (2 off)
- R9 10k  $\Omega$  (2 off)
- R10 390  $\Omega$  (2 off)
- R11-R12 22k  $\Omega$  (4 off)
- R13-R14 33k  $\Omega$  (4 off)
- All 5%  $\frac{1}{2}$  watt carbon

#### Capacitors

- C1-C2 4.7 $\mu$ F tantalum 35V (4 off)
- C3 620pF (2 off)
- C4 4 $\mu$ F elect. 18V (2 off)
- C5 4.7 $\mu$ F tantalum 35V (2 off)

#### Potentiometers

- VR1 5k  $\Omega$  midget linear carbon (2 off)
- VR2 100k  $\Omega$  ganged midget linear carbon (2 off)
- VR3 10k  $\Omega$  midget linear carbon (2 off)

#### Integrated Circuits


- IC1 MFC 6040 (2 off)
- IC2-IC3 741C (4 off)

#### Transistors

- TR1 BC209C (2 off)

#### Sockets

- SK1-SK2 2mm miniature sockets (4 off)
- JK1, JK2 3.5mm jack sockets (4 off)

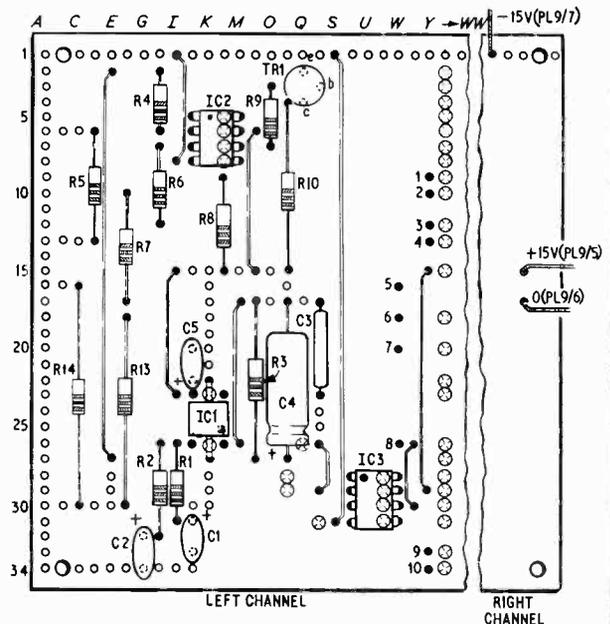

**Fig. 9.3. Component layout for Output Amplifiers. As both channels are identical only the left hand is shown**

mechanical centre. If there is more than say 10 to 15 per cent rotation between the two points it may be worth considering the empirical adjustment of one of the loading resistors in order to obtain a better balance or, alternatively, replacing the pot.

Both channels should be checked out in a similar manner and the electrical centres, when satisfactorily determined, marked on the front panel for reference.

### CONTROL AMPLIFIER

In Part 7 of this series the action of the MFC6040 was described and it was shown that the full range of attenuation/gain could be obtained by varying the control voltage applied to pin 2 of the device. Maximum attenuation is associated with a control of +6V whilst maximum gain is obtained when the control falls to +3.5V.

As in the Reverberation Amplifier the control voltages are supplied by a separate amplifier, IC2 in this case, which is operating in the differential mode. Signals normally arrive at the control amplifier, via R5, from the envelope shaper to which it is permanently linked by means of a pre-wired interconnection. This means that R5 is effectively grounded since it is looking into a low impedance whatever the setting of the envelope shaper level control.

The non-inverting input of IC2 is provided with a reference voltage supplied via the divider R8, VR1, R7, which is variable between +1.75V and +3V and which, since the feedback around IC2 is halved due to the coupling on R5, results in the amplifier having an output swing ranging between +3.5V and +6V.

TR1 acts as a follower/current amplifier to ensure that the current sink at the MFC6040 control input has no effect on the output voltage of IC2.

Fig. 9.3 shows the recommended board layout of the output amplifiers.

If the output amplifiers are tested out before making the necessary pre-wired interconnections it is essential to insert a grounded jack plug into the control socket, or otherwise ground the input end of R5, in order to ensure the correct functioning of the circuit.

### ENVELOPE COMPARISON

The rapidity with which the MFC6040 responds to changes in control voltage depends very largely on the value of C4 which has been chosen to present a time constant as close as possible to the fastest rate of attack/decay set by the envelope shaper. However it is prudent to compare the signal envelope at the output of the v.c.a. with the control envelope produced by the envelope shaper.

Fig. 9.4 gives a typical example of such a comparison. The slight rounding off at the corners of the signal envelope is due to the buffering action of C4

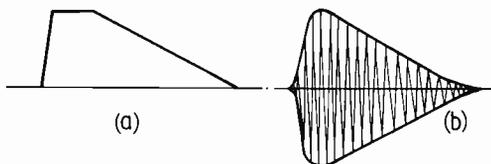


Fig. 9.4. (a) Control envelope—positive going (b) audio signal envelope with rounded edges

and is perfectly acceptable. If the rounding off is too pronounced there is a case for reducing the value of C4 to the next lowest preferred value but it is not recommended that the capacitor be removed entirely.

### DIFFERENTIAL AMPLIFIER

In common with the voltage inverter appearing in Part 3 there is little which need be said concerning the Differential Amplifier which is of the simplest kind. Despite its simplicity however the Differential Amplifier can be made to perform many useful functions in the Synthesiser particularly in connection with the mixing of complex programming waveforms.

Fig. 9.5 gives the circuit diagram of the differential amplifier, while Fig. 9.6 shows the recommended board layout. The front panel component layout and wiring is shown in Fig. 9.7.

### MODULE CONSTRUCTION

Construction of the module should generally follow the pattern already established in the series, that is, with the assembly and wiring of the components to the front panel before the panel itself is mounted to the circuit board support plate.

Wiring from the front panel components should be formed into two harnesses, one containing all leads to the output amplifiers passing out at the top of the front panel to the circuit board which is mounted in the position adjacent to the McMurdo plug. Leads to the differential amplifier should pass direct to the circuit board which is mounted in the lower position adjacent to the front panel.

The board size for this latter circuit should not exceed 17 ways in depth otherwise there may be some difficulty in clearing the ganged pan-pots.

### USING THE MODULE

As was explained last month the Voltage Controlled Amplifiers are principally intended for use with the Envelope Shaper in order that signals passing through them can be amplitude modulated in a variety of ways. However, only the left channel v.c.a. is permanently linked to the Envelope Shaper while the right channel control input is open circuit, that is, it requires a grounded jack plug inserted if control over signal amplitude is to be exercised.

With a jack plug in position the input level control may be operated in a similar fashion to a normal volume control, the characteristics of which were illustrated in graphical form in Part 7.

It is worth bearing in mind that the input level potentiometer is linear and thus the greatest degree of change in volume of the audio signal will occur within the last 30 degrees or so of rotation of the control. Alternatively, the control socket of the right channel may be linked by means of a patch-cord with the positive going envelope socket in order that both channels may be programmed by the envelope shaper. This latter procedure in no way compromises the audio signal and, in fact, with the pan-pots in the full left and right positions respectively the separation between channels is almost perfect.

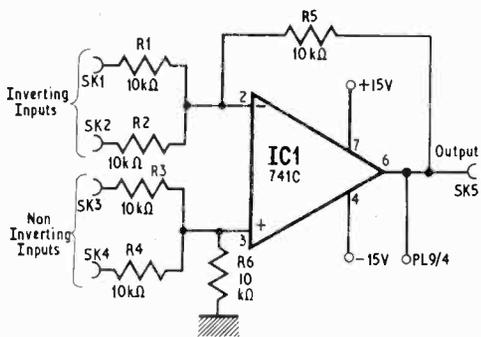


Fig. 9.5. Differential Amplifier circuit

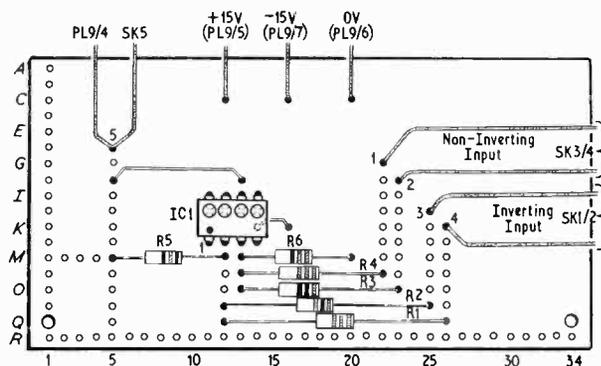


Fig. 9.6. Board layout for Differential Amplifier components

## COMPONENTS . . .

### DIFFERENTIAL AMPLIFIER

#### Resistors

R1-R6 10kΩ (6 off)

#### Integrated Circuit

IC1 741C

#### Sockets

SK1-SK5 2mm miniature sockets (5 off)

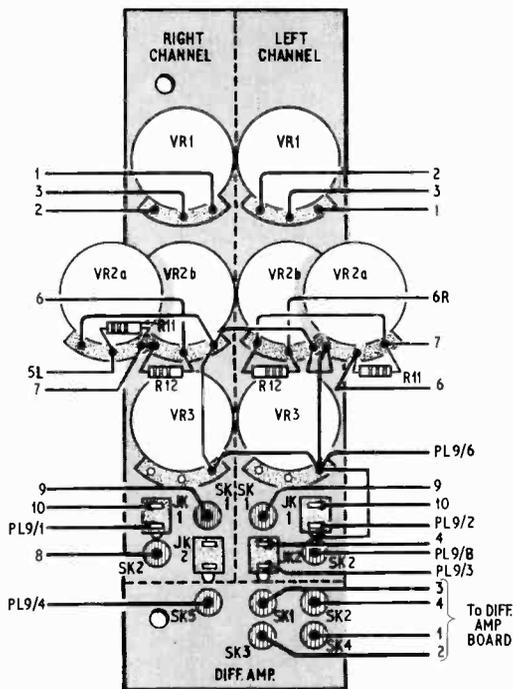
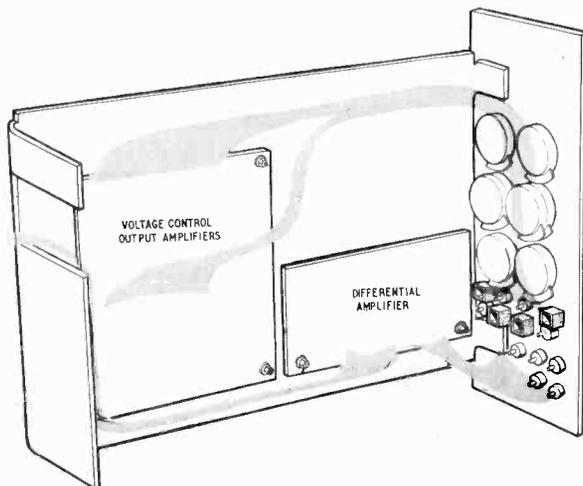
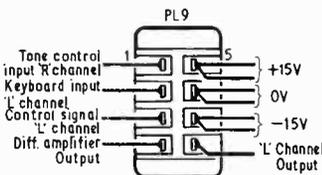


Fig. 9.7. Front panel wiring and inter-board connections. Note: Leads from VR3 as follows: wipers to SK2, unconnected tags to pin 8 on output amplifier board. Board positioning on the module is shown on the left with the McMurdo plug connections above

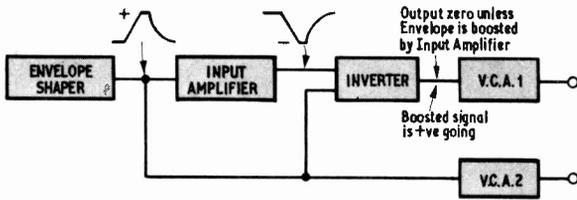


Fig. 9.8. Showing a method of obtaining a differential in envelope level

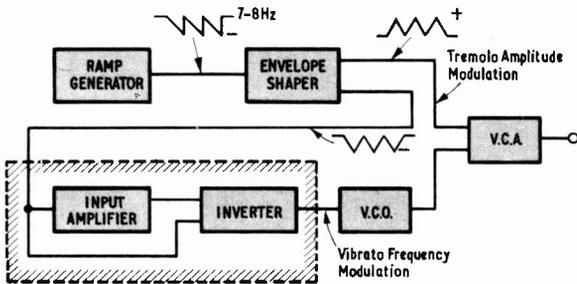


Fig. 9.9. Arrangement for combining tremolo and vibrato modulation

## INPUT LEVEL

The total audio input signal level to the MFC6040 should not exceed 500mV and it is worthwhile ensuring that, if two signals are to be mixed in the v.c.a., each signal does not exceed 250mV peak. The penalty for neglecting this precaution lies in the possibility of damage to the device. The mean output level of the final stages will depend very much on the settings of the pan-pots. However, with 500mV input to the v.c.a. and with the pan-pots in mid-position, the maximum output is unlikely to exceed 2.2V. Output level controls are provided so that the output may be tailored to suit a range of input levels required by external apparatus such as tape recorders, power amplifiers and so on.

When the Envelope Shaper is programming the amplitude of the audio signal it is normal to set the input level control to zero if the full 90dB range of the v.c.a. is to be used. An alternative method is to adjust the input level so that, with a zero level envelope, the signal is just audible. The provision of an envelope under these conditions will serve to emphasise parts of the continuing signal. This technique is useful when one channel is carrying a repetitive rhythm which is to be mixed with another signal derived from, say, the keyboard. In these circumstances it is sometimes possible for the rhythm to be swamped by the keyboard signal unless the former signal is boosted.

If it is required to provide a differential level of positive going envelope for the latter purpose a suitable method is illustrated in Fig. 9.8. Set the envelope shaper signal level to provide the lowest amplitude response required between the two channels. Route the positive-going envelope to an input amplifier set to unity gain and also to the inverter. The output of the input amplifier should similarly be routed to the inverter. Since the inputs to the inverter are now of equal level and opposite polarity, the net output will be zero. Advancing the

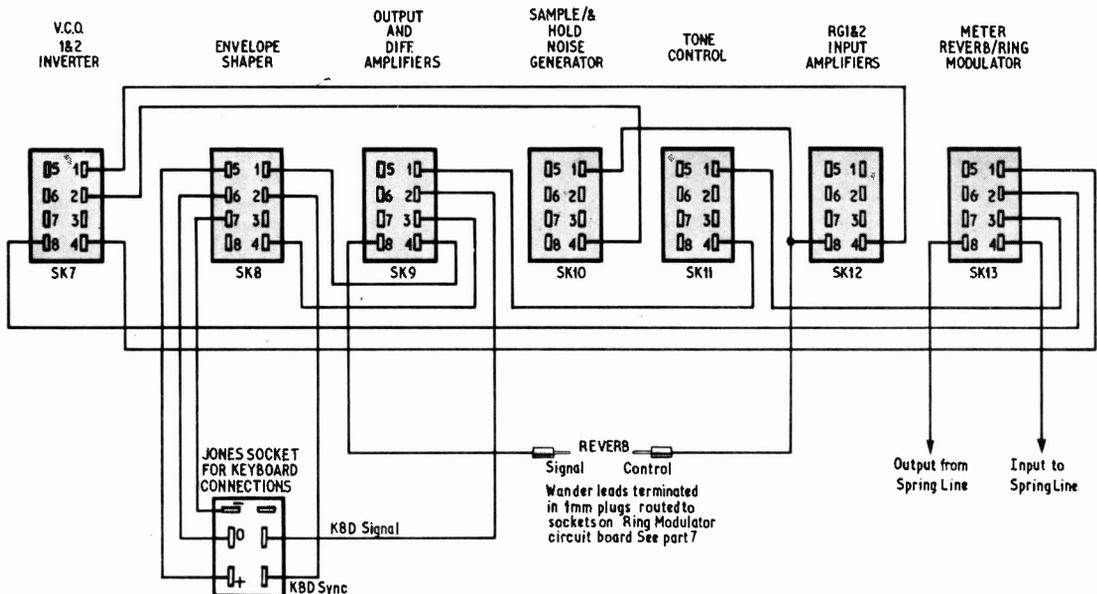


Fig. 9.10. Socket arrangement and wiring on connector mounting rails. Prewired interconnections are shown only

**Table 1: Prewired Connections**

Terminal Number	SK7 V.C.O. 1 & 2 Inverter	SK8 Envelope Shaper	SK9 Output Amplifiers Diff. Amp.	SK10 Sample/ Hold Noise Gen.	SK11 Tone Control	SK12 Ramp Gens. 1 & 2 Input Amps.	SK13 Meter Reverb. Ring Mod.
	Connect to	Connect to	Connect to	Connect to	Connect to	Connect to	Connect to
1	SK12 (4)	SK9 (4)	SK11 (4)	SK12 (8)	SK13 (3)	NC	SK7 (4)
2	SK10 (4)	Jones Skt. kbd. conn. sync.	Jones Skt. kbd. conn. signal	NC	NC	NC	SK7 (8)
3	NC	NC	SK8 (4)	NC	NC	NC	SK11 (1)
4	SK13 (1)	SK9 (3)	SK8 (1)	SK7 (2)	SK 9 (1)	SK7 (1)	Input to Spring Line
5	V+	V+	V+	V+	V+	V+	V+
6	O	O	O	O	O	O	O
7	V-	V-	V-	V-	V-	V-	V-
8	SK13 (2)	NC	Wandering lead	NC	NC	SK10 (1) Wandering lead	Output from Spring Line

gain control of the input amplifier will have the effect of providing a positive going envelope which may be adjusted to suit the requirements of the so-far unprogrammed output channel.

**TREMOLO EFFECTS**

An interesting experiment lies in the investigation of tremolo effects. Set a ramp generator to about 7-8Hz programming the envelope shaper direct. Adjust the attack and decay controls so that the resultant envelope is triangular in form and adjust the envelope level so that it provides peak modulation to a v.c.a. Couple a v.c.o. running at about 300Hz to the audio signal input of the same v.c.a. and adjust the input level control so that the sound does not die away completely at zero envelope level. The resultant pulsating sound is known as tremelo modulation.

The next stage is to take the negative going envelope and couple it to the same series of modules described in the previous example. The output of the inverter should be led to the v.c.o. providing the 300Hz signal. If the input level control to the v.c.a. is now turned to maximum and the input amplifier gain carefully increased the resultant sound is known as vibrato or, perhaps more suitably, frequency modulation. Variation of input amplifier gain, in conjunction with v.c.a. input level, can provide an interesting range of sounds in which tremelo and vibrato modulations are mixed. The schematic arrangement of modules for the above experiment is shown in Fig. 9.9.

Further interest may be provided by variation in the triggering rate of the envelope shaper and variation in the mark-space ratio of the envelope by careful adjustment of the ratio control.

**PRE-WIRED INTERCONNECTIONS**

This article concludes with some notes on interconnections which was outlined in Part 1.

Permanently connected interwiring is advocated to reduce the problems associated with external patch cords which, besides being possible sources of hum-pick-up, can often render the front panel controls difficult to operate particularly if a complicated patch is in use.

Table 1 gives the scheme of interconnection, whilst Fig. 9.10 gives a wiring layout based on the original illustration shown in Part 2 of the series. The socket numbers shown correspond to the socket numbers on that illustration which is a view from behind, as it were, of the front panel also depicted in that issue. Those constructors who have changed the arrangement of modules from that shown in Part 2 should note that the wiring on the McMurdo sockets will have been re-routed accordingly and would, perhaps, be well advised to use the table of connections as a guide.

There are two minor changes in the interwiring differing from the block diagram depicted in Part 1. These are:

- (a) V.c.o. 1 is no longer programmed direct from the envelope shaper since the range of sounds which could be produced was not considered wide enough to merit a permanent connection.
- (b) The Envelope Shaper programming of reverberation depth has been replaced by R.G.2 to gain the benefit of the wholly opposite type of effect resulting from the use of negative-going programming signals. At the same time the R.G.2 connection to the envelope shaper has been replaced by a connection from the differential amplifier since it has been found, in practice, to be the more useful of the two.

*Note: See Points Arising this month.*

**Next Month: Commencement of the Keyboard Unit. This is an independent instrument that can be used for live performance apart from the main Synthesiser.**

# WIND and RAIN EFFECTS

By P. J. TYRRELL

**T**HIS project describes the construction of a simple unit whose output when fed into an audio amplifier produces a sound resembling howling wind or falling rain. The circuit uses an operational amplifier in a dual-in-line package, which simplifies construction and aids stability in the high gain arrangement used. This also means that the circuit layout is less critical than if discrete components were used.

## PRINCIPLE OF OPERATION

The circuit consists basically of an active tuned filter fed from a white noise source. The sound of howling wind is produced by varying the resonant frequency of the filter. By removing one of the capacitors in the filter, the circuit behaves as a broad band amplifier, producing the sound of rain.

Fig. 1 shows the basic filter circuit used. The resonant frequency is determined by the values of  $C_1$ ,  $C_2$  and  $R_1$ ,  $R_2$  determining the gain of the system. Removing  $C_2$  widens the bandwidth of the filter. In the final circuit this function is performed by placing a variable resistor in series with  $C_2$ , permitting the rain to be gradually introduced.

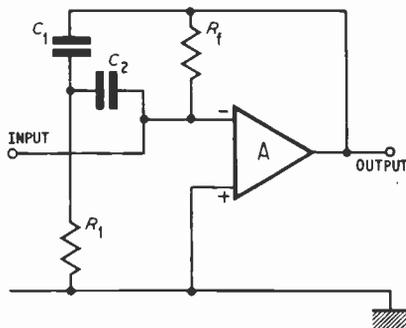


Fig. 1. Basic filter circuit.  $C_1$  and  $C_2$  determine the resonant frequency and  $R_1$  and  $R_2$  determine the gain

## FINAL CIRCUIT

The complete circuit of the unit is shown in Fig. 2. The white noise is generated in TR1 by giving it a reverse bias, then passed via  $R_2$  and  $C_3$  to the input of the filter. VR1 controls the resonant frequency of the filter, and is therefore, the wind control. VR2, in series with  $C_2$ , is the rain control.

The output from the filter passes through  $R_4$  to VR3, the output level control and then to the output socket SK1 via  $C_4$ . VR3 was wired as shown, not with the wiper connected to the output as it was envisaged that other equipment may be connected to the same input of the main amplifier.

The operational amplifier chosen for this circuit is the 741. It was chosen in preference to the 709 as the former requires no external frequency compensation and the greater bandwidth offered by the latter is not necessary in this application. The 741 will work satisfactorily from supply voltages of  $\pm 4$  to  $\pm 15$  volts, making it most suitable for operation from a pair of 9 volt batteries, as is done here. At this supply voltage the open loop voltage gain is over 90dB.

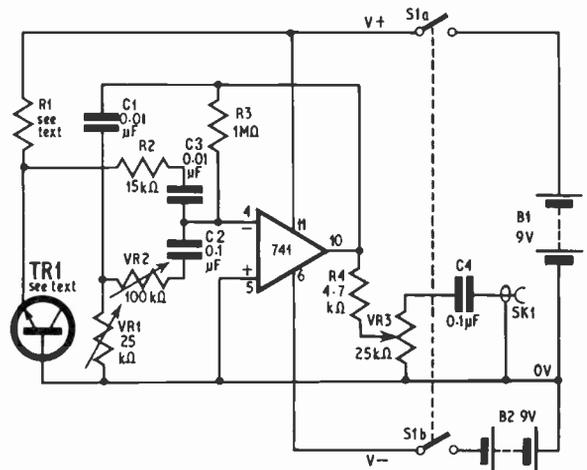


Fig. 2. Complete circuit diagram of the Wind and Rain Effects Unit

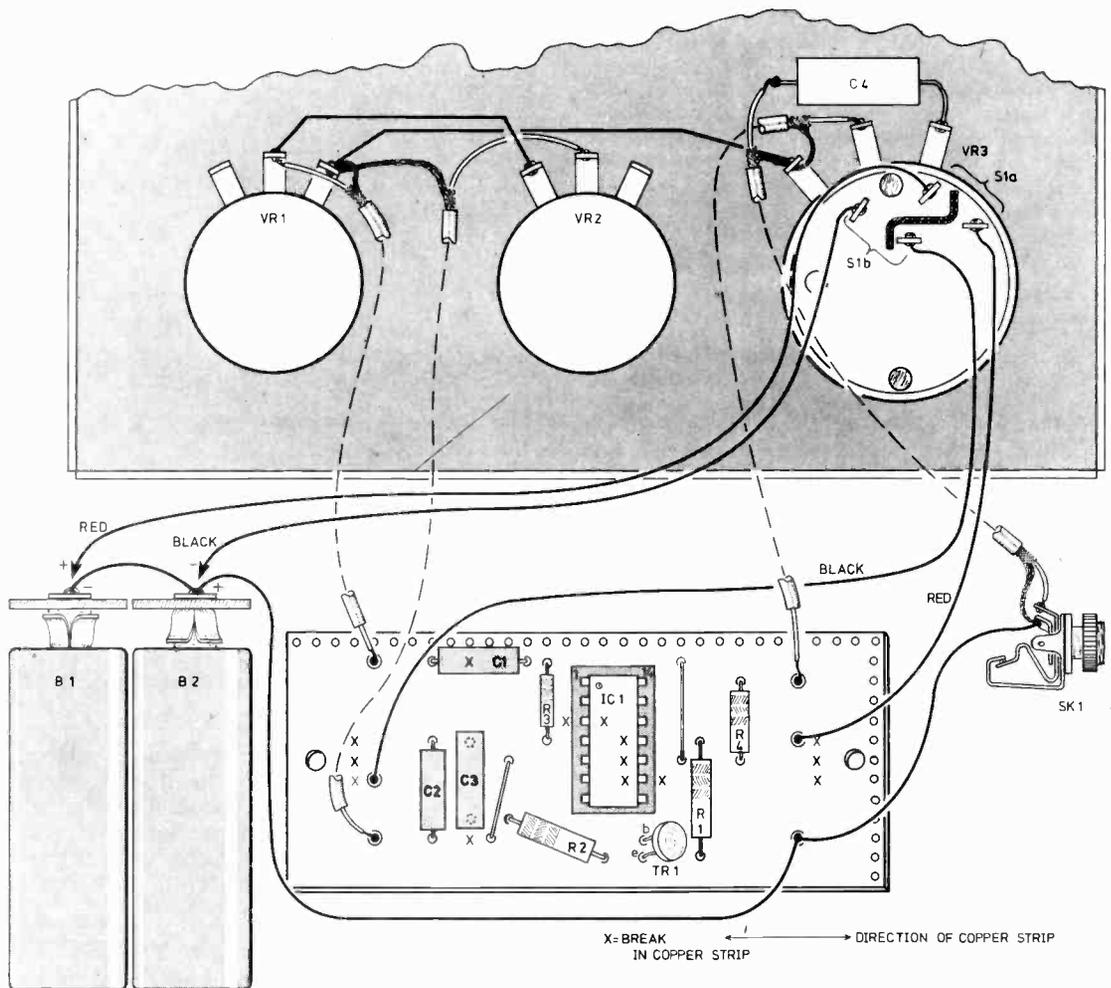


Fig. 3. Construction and interwiring details. All but battery leads should be screened leads

## COMPONENTS . . .

### Resistors

- R1 100k  $\Omega$  nominal (see text)
- R2 15k  $\Omega$
- R3 1M  $\Omega$
- R4 4.7k  $\Omega$
- All  $\frac{1}{4}$  or  $\frac{1}{8}$ W  $\pm 10\%$  carbon

### Potentiometers

- VR1 25k  $\Omega$  linear
- VR2 100k  $\Omega$  linear
- VR3 25k  $\Omega$  linear with double pole switch

### Capacitors

- C1 0.01 $\mu$ F      C3 0.01 $\mu$ F
- C2 0.1 $\mu$ F        C4 0.1 $\mu$ F
- All 160V polyester or polycarbonate

### Semiconductors

- TR1 Any *npn* transistor (see text)
- IC1 SN72741 or equivalent

### Miscellaneous

- Aluminium box 5 $\frac{1}{4}$ in x 4in x 1 $\frac{1}{2}$ in
- B1, B2 9V PP3 batteries (2 off)
- SK1 3.5mm jack socket
- Veroboard 0.1in matrix, 31 holes x 13 strips
- Veropins (6 off)
- Knobs, nuts, bolts, screened wire, aluminium for battery holder

## CONSTRUCTION

The circuit was constructed on a piece of 0.1 inch matrix Veroboard, using a socket for the 741.

Start by cutting the Veroboard to size (31 holes long by 13 strips wide). Next cut the copper strips according to Fig. 3, and then fix the Veropins for attachment of flying leads. All the components except TR1 and R1 should then be soldered in. The integrated circuit socket should be soldered before inserting the i.c. C4 is mounted directly onto VR3 to simplify wiring.

## SELECTING TR1 AND R1

In order to select suitable components for TR1 and R1, flying leads should be temporarily connected to V+, 0V and R2. The 9 volt batteries should be connected up and the output from R4 fed into an audio amplifier. VR2 can be left out of circuit, but VR1 should be temporarily wired in. It facilitates the selection process if a number of leads with insulated crocodile clips on both ends are available.

It is best to have a number of transistors at hand and select a suitably noisy specimen for TR1. Varying R1 alters the noise output from the transistor, but it should not be reduced below about two kilohms. In the prototype R1 was 100k $\Omega$  and TR1 was a silicon *nnp* device obtained from a computer board.

A *pnp* transistor can be used instead, by reversing the base and emitter connections. Alternatively, a noisy Zener diode, reverse biased, may be used. A number of advertisers in this magazine offer untested transistors for sale, cheaply in bulk, and it is worth investing in some of these.

Having chosen R1 and TR1, these should be soldered in place on the Veroboard.

## CASE CONSTRUCTION


The prototype was constructed in a ready-made aluminium box. Construction and interwiring details for the box and its lid are shown in Fig. 3. A battery retaining clip can be made from a piece of aluminium. The end of this should be wrapped with insulating tape to prevent the battery clips from shorting out.

If it is thought that the batteries may be inadvertently inserted the wrong way round then the inside of the box, next to the Veroboard, can be insulated as well. The Veroboard is mounted with two 6BA bolts and  $\frac{1}{4}$ in spacers. One of the bolts serves to hold the battery retaining clip in position as well.

The prototype box was covered with woodgrain pattern, plastic self-adhesive, and the lid brushed with steel wool. A piece of foam plastic was glued to the inside of the lid, to prevent the batteries from rattling, and Letraset legends applied above the three controls. The front panel was then given a coat of polyurethane varnish, to protect the surface and the lettering. Cellulose varnish should not be used as this dissolves Letraset.
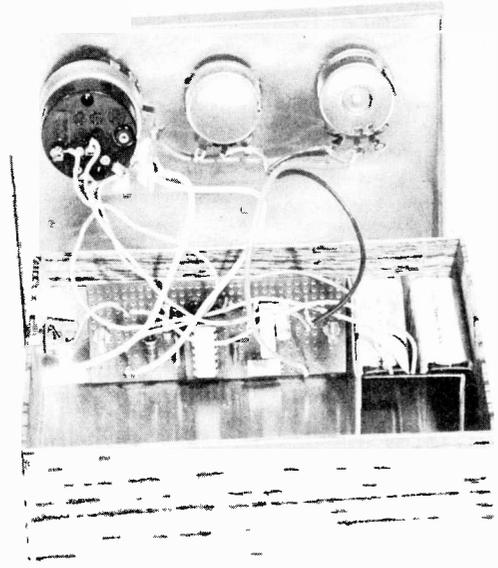
## FINAL WIRING UP

The circuit should be wired up using screened wire, apart from the battery leads, due to the possibility of instability in the high gain arrangement. Do not forget to connect C4, which is mounted on VR3.



Photograph of the internal layout

## TESTING AND OPERATION

With the circuit fully assembled, the current drawn from each battery should be about 1.6mA. With the unit connected to an audio amplifier, VR3 fully clockwise, VR2 and VR1 fully anticlockwise, a low moan should be audible. By advancing VR1 the frequency of the wind should rise up to a scream. With VR1 again fully anticlockwise, as VR2 is advanced, the sound of falling rain is heard, increasing in intensity with rotation of VR1 and VR2.

No detailed description of application is included here, as this is best left to the constructor's imagination. ★




Photograph of the completed Wind and Rain Effects unit
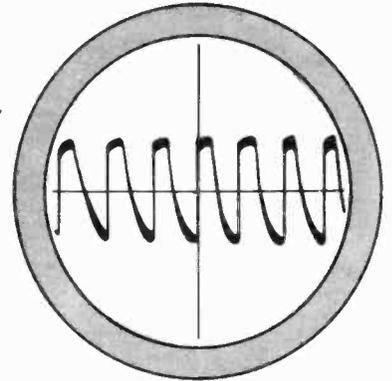
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
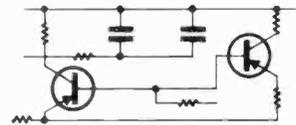
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME


BLOCK CAPS

ADDRESS

PLEASE EL103

**special free gift also to all our students**

# BIG Discounts

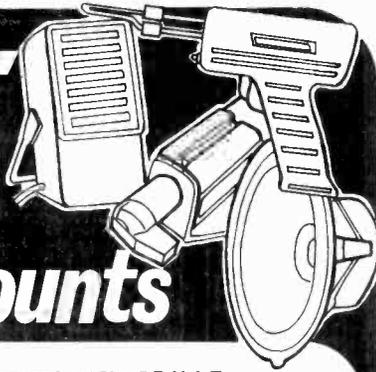

## ALL PRICES INCLUDE V.A.T.

<b>SPEAKER BARGAINS</b>					
EMI 13in x 8in 3, 8 or 15 ohm		FANE, 7in x 4in, 3 or 8 ohm	1-00	8in Dual cone 8 ohm	2-40
Plain	2-10	CELESTION 8in, 15 ohm	1-55		
With Co-Axial Tweeter	2-20	ADASTRA 10in, 8 or 15 ohm,			
Twin Tweeter	3-55	10W	2-75		
Type 350, 8 ohm, 20W	8-00	BAKER GROUP 25 12in, 8 or			
6in, 8 ohm, 10W	2-50	15 ohm, 25W	6-45		
8in, 8 ohm, 10W	3-75		P. & P.	0-25	
12in, 8 ohm, 20W	5-50	5in, 8 ohm, 5W C/Mag.	0-85		
8in x 5in C/Mag. 3W	1-20	2 1/2in, 8 ohm or 64 ohm	0-50		
8in x 5in, Dual cone 8 ohm,			P. & P.	0-10	
10W	2-50				
<b>TWEETER AND CROSSOVER</b>		Dome Tweeter 8 ohm, 30W	4-00		
EMI 3 1/2in, 3 or 8 ohm C/Mag.	1-00	Crossovers CN23 (3 ohm), CN28			
Cone Tweeter 8 or 15 ohm, 10W	1-90	(8 ohm), CN216 (16 ohm)	1-00		
Cone Tweeter 8 ohm, 3W	1-00		P. & P.	0-10	
Horn Tweeter 8 ohm, 20W	5-50				
<b>KIT FORM CABINETS, TEAK</b>		13in x 8in cutout	3-25		
EMI 3 1/2in, 3 or 8 ohm C/Mag.	1-00	18in x 11in x 9in with 13in x			
Cone Tweeter 8 or 15 ohm, 10W	1-90	8in cutout for EMI 350	4-85		
Cone Tweeter 8 ohm, 3W	1-00		P. & P. each	0-35	
Horn Tweeter 8 ohm, 20W	5-50				
17in x 10in x 6in with 8in or	2-45				
<b>MICROPHONES</b>		TW206	5-75		
CM20 Crystal Hand	0-50	CONDENSER MIKE 600 ohm,			
CM70 Planet stick metal,		uni-dir.	7-90		
switch crystal	1-55	Cassette Stick Mike with R.			
DM150 Dynamic uni-dir, ball		Control on/off switch (2 1/2			
metal	3-95	and 3-5mm J/Ply)	1-85		
UD130 50K/600 ohm, uni-dir,		Lapel, type, crystal	0-40		
ball metal	4-50		P. & P.	0-15	
<b>SOLDERING IRONS</b>		spare 1 1/2in, etc.)	2-85		
ANTEX CN240 15W	1-60	X25 25W (low leakage)	1-60		
SKI Kit (15 watt iron, 2			P. & P.	0-10	
<b>CARTRIDGES</b>		9THAC/G Slim fit, stereo cer.	1-80		
ACOS GP91/28C or GP91/38C		diam.	0-80		
Stereo comp.	1-00	19-TI Stereo crystal	2-25		
GP93/1 Stereo crystal	1-35	BSR SC5M Stereo ceramic	2-25		
GP94/1 Stereo crystal	1-75	SK5H Stereo crystal	1-60		
GP99/1	1-35	SK5M Stereo crystal	1-60		
(P99/1)	1-75	X6H Mono/stereo	1-25		
GP104	0-75	X6M Mono/stereo	1-25		
SONOTONE 9THAC Stereo		GOLDRING G800	3-85		
ceramic, diam.	1-80	G850	3-85		
			P. & P.	0-05	
<b>STYLI</b>			P. & P.	0-03	
<b>FOR ABOVE CARTRIDGES—</b>		GOLDRING G800	1-95		
Sapphire	0-35	G850	1-95		
D. Diamond	1-25		P. & P.	0-03	
<b>BATTERY ELIMINATORS</b>		socket) 6, 7.5 or 9 d.c. output			
240V input 6, 7.5 or 9 300mA	2-20	at 300mA	2-20		
12V d.c. input (fits in car lighter)			P. & P.	0-10	
<b>TAPES</b>		7in	85p	95p	110p
5in	Std.	LP	DP		
5 1/2in	45p	55p	70p	P. & P. 1-3 each	0-09
	55p	85p	95p	4 or more lot	0-30
<b>LOW NOISE CASSETTES</b>		Cassette Head Cleaner	0-35		
C60	35p	33p	30p	6-10 lot	0-15
C90	45p	43p	40p	11-20 post free	
C120	55p	52p	50p		
<b>PLASTIC LIBRARY CASES for</b>		7in Reels	0-25		
5in Reels	1-5	6-10	P. & P. 1-3 each	0-05	
5 1/2in Reels	0-22	4 or more		0-20	
<b>CASSETTE CASES</b>			0-10		
<b>BIB ACCESSORIES</b>		Book, Ref. 56	0-25		
Compact Tape Head Cleaning		Stylus Balance, Ref. 32A	1-15		
Kit, Ref. J	0-45	Spillet Lever, Ref. 46	0-50		
Tape Editing Kit, Ref. 23	1-30	Cassette Case (holds 12			
Recording Tape Splicer, Ref. 20	1-15	cassettes) Ref. 34	1-00		
Cassette Tape, Editing, Ref. 24	1-40	Hi-Fi Stereo Test Cassette	1-90		
Cassette Salvage Kit, Ref. 25	0-40	Groove-Kleen Record Cleaner	1-90		
Hi-Fi Stereo Hints and Tip			P. & P.	0-10	

Send 25p for COMPLETE CATALOGUE, refundable upon first order.  
ALL OUR MERCHANDISE IS FULLY GUARANTEED

**Riversdale Electronics**  
Mail Order Department PE/10  
P.O. Box 470, Manchester M60 4BU.

# FERRANTI

## ZN414 Radio i.c.

only £1.32 WITH DATA

### WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p			ZS271	16p
ZTX109	11p	ZTX382	13p	<b>* DIODES *</b>		ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	16p		
ZTX301	13p	ZTX500	12p	ZS124	18p		
ZTX302	17p	ZTX501	13p	ZS140	25p		
ZTX303	14p	ZTX502	17p	ZS141	43p		
ZTX304	21p	ZTX503	14p	ZS142	33p		

ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED

WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation  
PRICES SLASHED! RCA CA3090Q £2.25; CA3075 99p. Limited quantity only.

P. E. Triffid. ZT1711 24p; 2N1132 25p.  
POSTAGE AND PACKING 10p—Free over £2. Send S.A.E. for our full price list and data sheet.

ALL PRICES INCLUDE V.A.T.  
**DAVIAN ELECTRONICS**  
PO BOX 38, OLDHAM, LANCS. OL2 6XJ

### SPECIAL 40 MHZ SCOPE—

**SOLARTRON CD1212 ONLY**

450. Has to be a snag. There are no plug-in V amps available.

TB—100 nanoseconds per cm to 5 secs per cm in 24 calibrated ranges. 20 nanoseconds per cm with times 5 expansion. 5in flat faced tube.

Trace locator. 0.2 microsec signal delay. Built-in calibrator. 1kHz square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3 V/cm.

**MAIN FRAME Y AMP** boosts this to better than 200 Vm per cm at 40 MHz. 240V 50 Hz input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1.50.

**MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE**

**WITH OUR NEW LOW PRICED SOLID STATE SWITCH.** 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50. P. & P. 25p. (Not cased, not calibrated.)

**NEW WIDE RANGE WOBBLATOR**

5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 107 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied.

Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75p. P. & P. 25p. (Not cased, not calibrated.)

**20 Hz to 200 kHz WB.**

**SINE and SQUARE GENERATOR.** Four ranges. Independent amplitude controls. thermistor stabilised. Ready to use, 9V supply required. £7.85 each. P. & P. 25p (Not cased, not calibrated.)

**GRATICULES.** 12cm x 14cm high quality plastic 15p each. P. & P. 5p.

### COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors 1/2 and 1 watt, many high stabs, etc. Fine value at 50p.

P. & P. 17p.

**P.C.B. PACKS S & D.** Quantity 2sqft—no tiny pieces. 50p plus P. & P. 20p.

**FIBRE GLASS** as above £1 plus P. & P. 20p.

**5 CRYSTALS** 70 to 90kHz. Our choice 25p. P. & P. 15p.

**5 MOVING COIL METERS** various £2. P. & P. 37p.

**CAPACITOR PACK—50** Brand new components only 50p. P. & P. 17p.

**POTS—10** different values. Brand new—50p. P. & P. 17p.

**TRIMMER PACK—2** Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

**ELECTRONIC TIMER UNITS**—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2.50 incl. carriage.

**LIGHT EMITTING DIODES** (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

**PHOTOCELL** eq. OCP71, 13p each.

**PHOTO-RESIST** type Clare 703. Two for 50p.

**MODERN TELEPHONES** type 706. Two-tone grey, £2.75 each. The same but black, £3.75 each. P. & P. 25p each. Also TOPAZ YELLOW £4.50 each. P. & P. 25p.

**DELIVERED TO YOUR DOOR**—1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.


PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY  
**CHILMEAD LTD**

7/9 ARTHUR ROAD, READING, BERKS.  
(rear Tech. College) Tel.: Reading 582603/65916

# NEXT MONTH

# 4 IN HAND

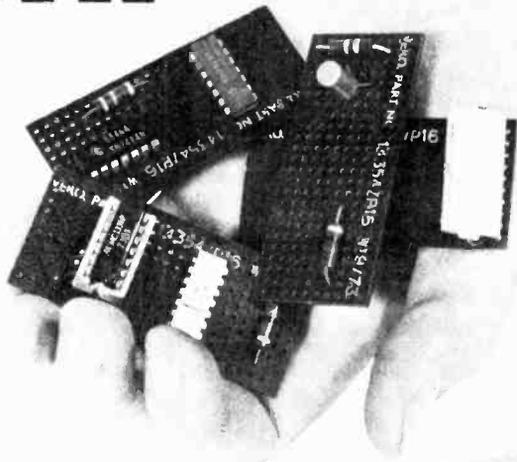

FOUR MINI PROJECTS FOR THE  
CONSTRUCTOR DESCRIBED IN A  
**SPECIAL 8-PAGE SUPPLEMENT**  
EACH BASED ON THE . . .


# FREE VEROBOARD SAMPLE

Suitable for I.C. and discrete projects with 0.1 in. hole spacing

INSIDE EACH ISSUE
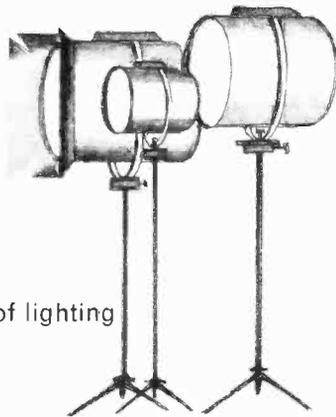
## STAGE LIGHT DIMMER

Four independent channels, each capable of controlling  $3\frac{1}{2}$  kW of lighting



**ALSO**

## SYNTHESISER LOG LAW OSCILLATORS

AS USED IN THE KEYBOARD UNIT—A COMPLETE "LIVE PERFORMANCE INSTRUMENT"

PRACTICAL

# ELECTRONICS

NOVEMBER ISSUE ON SALE OCTOBER 12, 1973

# PATENTS REVIEW...

## FOUR CHANNEL VOLUME AND BALANCING CONTROL

In BP1 317 530 Motorola Inc. of Illinois, USA, describe a simple but useful system for balancing 4-channel sound. The patent is concerned mostly with cartridge players for cars.

The basic system diagram is shown in Fig. 1. Four channels drive four speakers i.e., left rear, left front, right rear, right front.

Each of the four speaker driver amplifiers uses a transistor to act as a variable impedance device to control the gain of the audio signal, see Fig. 1. Usually the transistors used are of the *npn* type with the collector connected to the drive for the speakers and the emitter connected to earth. For *pnp* types the emitter and collector connections are reversed.

Potentiometer VR2 acts as a side balance (left to right) control and has one end connected to the left channels and the other end connected to the right channels. As VR2 slider is moved it thus provides a variable voltage divider network between the respective pairs of channels.

Adjustment of VR2 varies the amount of d.c. voltage delivered to the respective pairs of channels at the bases of their associated transistors. But the total sum of the d.c. applied remains the same; so it follows that although the respective pairs of channels are balanced, a constant volume is maintained with respect to the total output of the pairs of channels. This is because there is no shunting or limiting effect.

Potentiometer VR3 acts as a control for balancing the front and rear sets of speakers. One end is connected to the rear channels and the other to the front channels. VR3 functions in exactly the same manner as VR2 dividing a fixed amount of d.c. voltage between the front and rear channel pairs.

In the circuit shown fixed value resistors are connected in series with the base of each transistor to serve as a bias current limiting device.

The overall gain or volume of the system is controlled by VR1, the slider being connected directly to the sliders of VR2 and VR3 respectively. Once control VR1 has been set to achieve the required overall volume level, this will be maintained whatever balancing

BP1 317 530

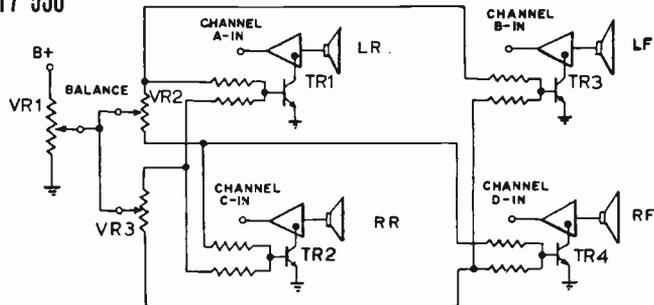


Fig. 1

positions are set on the other controls. Also, the set balance will remain the same as the overall volume level is raised or lowered.

## STEREO AMPLIFIER AVC

Blaupunkt-Werke of Germany in BP 1 307 074 describe an automatic volume control for a stereo amplifier. The idea is to provide a.v.c. with no cross-talk between channels, but without buffer amplifiers.

The output of the first channel amplifier is fed to one end of a potential divider network, the other end of the divider is connected to the positive line. Capacitor C3 connects the junction of resistors R3, R4 to one side of a bridge. The anodes of D2 and D4 connect via VR1 to the base of amplifier transistor TR1 and the cathodes of D3 and D4 are connected to the emitter of TR1. The second channel is connected in exact mirror fashion.

The collector of TR1 is connected through D5 and filter network C7, R12 to the base of TR2.

Its emitter is connected through VR2 to a pair of voltage dividers and transistors TR3 and TR4.

When one of the two channels produces a signal which is too large, the negative going half wave passes through the respective capacitors C3, C4, charged by the positive half wave and action of diodes D1, D3, via either D2 or D4 and VR1 to the base of TR1. The resultant control signal from the collector of TR1 is fed to the base of TR2 and is applied to the variable control VR2 which allows compensation for tolerances of TR3 and TR4.

With correct adjustment of VR2, the voltages on the bases of both TR3 and TR4 will be altered by equal amounts so that the collector/emitter junctions of the transistors are more or less conductive. This will achieve ganged automatic volume control because there will be an alteration in the ratio of the potentiometer in each channel formed by the input resistors R1, R2 and its respective transistors TR3 and TR4, with a resultant change in the fraction of the signal applied to the channel amplifiers.

BP1 307 074

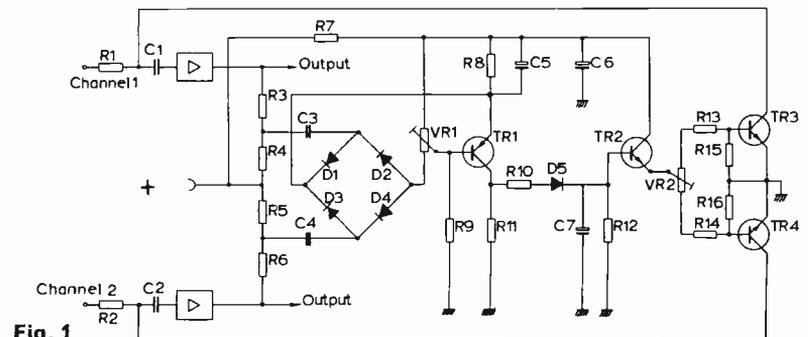


Fig. 1

# YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

ALL PRICES SUBJECT TO V.A.T.

## RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction.  
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.  
1/4W 2% ELECTROSIL TRS

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7Ω-2.2MΩ	E24	100+
1/4	10%	3.3MΩ-10MΩ	E12	1p 0.8p
1/4	2%	10Ω-1MΩ	E24	3p 0.8p
1/4	10%	1Ω-3.9Ω	E12	1p 0.8p
1/4	5%	4.7Ω-1MΩ	E12	1p 0.8p
1/4	10%	1Ω-10Ω	E12	6p 5.5p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/4W, lin 1/2W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 matrix).  
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

## TRANSISTORS

AC107 15p	AF125 20p	BD132 75p	OC28 50p	2N3702 12p
AC126 12p	AF126 20p	BD133 75p	OC35 50p	2N3703 12p
AC127 12p	AF127 20p	BF115 25p	OC42 12p	2N3704 12p
AC128 12p	AF139 32p	BF173 20p	OC44 12p	2N3705 12p
AC131 12p	AF178 32p	BF177 28p	OC45 12p	2N3706 12p
AC132 12p	AF180 40p	BF178 32p	OC70 12p	2N3707 12p
AC176 12p	AF181 40p	BF179 32p	OC71 12p	2N3708 10p
AC187 22p	BC107 9p	BF180 32p	OC72 12p	2N3709 11p
AC188 22p	BC108 9p	BF181 32p	OC81 12p	2N3710 11p
AD140 50p	BC109 9p	BF194 15p	OC82 12p	2N3711 11p
AD149 45p	BC147 13p	BF195 15p	2N2904 20p	2N4062 12p
AD161 33p	BC148 13p	BF197 15p	2N2926R 9p	40360 35p
AD162 36p	BC149 13p	BF200 32p	2N2926G 9p	40361 35p
AF114 20p	BC157 14p	BFY50 20p	2N2926Y 9p	40362 40p
AF115 20p	BC158 14p	BFY51 20p	2N2926G 9p	40408 40p
AF116 20p	BC159 14p	BFY52 20p	IN4148 10p	ZTX302 15p
AF117 20p	BC187 22p	BU105 225p	2N3054 58p	ZTX500 15p
AF124 22p	BD131 75p	OC26 45p	2N3055 60p	ZTX502 20p

## ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

## DIODES

DIODES	RECTIFIER	SIGNAL
BY127 1250V 1A 12p	OA85 7p	OA85 7p
BZ10 800V 6A 25p	OA90 5p	OA90 5p
BZ13 200V 6A 20p	OA91 5p	OA91 5p
IN4001 50V 1A 7p	OA202 7p	OA202 7p
IN4004 40V 1A 8p	IN4148 5p	IN4148 5p
IN4007 1000V 1A 10p	BA114 8p	BA114 8p

## BRUSHED ALUMINIUM PANELS

12in x 6in = 25p, 12in x 2 1/2in = 10p, 9in x 2in = 7p

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE GANG, 10K, 25K, 100K log. or lin. 40p.

DUAL GANG, 10K + 10K etc. log. or lin. 60p.

KNOB FOR ABOVE E12p.

FRONT PANEL 65p.

18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

## THERMISTORS

VA10555 15p
VA10665 15p
VA1077 15p
RS3 £1.35

## THYRISTORS

2N5060 50V 0.8A 30p.
2N5064 200V 0.8A 47p.
CRS1/40 400V 1A 25p.
106F 50V 4A 40p, 106D 400V 4A 55p.

## MULLARD POLYESTER CAPACITORS C196 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7 1/2p, 0.33μF, 11p, 0.47μF, 13p.

160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3 1/2p, 0.15μF 4 1/2p, 0.22μF 5p, 0.33μF 6p, 0.47μF 7 1/2p, 0.68μF 11p, 1.0μF 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 3 1/2p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6 1/2p, 0.47μF, 8 1/2p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

## ELECTROLYTIC CAPACITORS—MULLARD O15/6/7 RANGE REPLACES C426, C457 RANGES.

(μF/V) 1/0/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/40, 47/4.0, 47/10, 47/25, 47/40, 47/63, 68/6.3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6.3, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/6.3, 5p each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6.3, 1,000/4, 9p, 100/63, 150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/6.3, 12p, 220/63, 470/40, 680/25, 1,000/10, 1,500/10, 2,200/6.3, 15p, 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6.3, 4,700/4, 18p.

## SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V	12p
0.22μF 35V	4.7μF 35V	33μF 10V	
0.47μF 35V	6.8μF 25V	47μF 6.3V	
1.0μF 35V	10μF 25V	100μF 3V	

## VEROBOARD

2 1/2 x 3 1/2	0.1	0.15
2 1/2 x 5	22p	16p
3 1/2 x 5	24p	24p
3 1/2 x 3 1/2	24p	24p
3 1/2 x 5	25p	27p
17 x 2 1/2	75p	57 1/2p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	11p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

## JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 15p/metre.  
6 way screened cable 22p/metre.

## BATTERY ELIMINATOR

£1.50  
9V mains power supply. Same size as PP9 battery.

## LARGE (CAN) ELECTROLYTICS

1600μF 64V 74p	2500μF 64V 80p	4500μF 16V 50p
2500μF 40V 74p	2800μF 100V £2.60	4500μF 25V £1.68
2500μF 50V 58p	3200μF 16V 50p	5000μF 50V £1.10

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

## POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.  
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £5.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

## PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminated board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief. 97p

# LARGE RANGE ITT/TEXAS IC's NOW IN STOCK


PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400 18	16	14	13	7450 18	16	14	13	74121 43	40	38	36	36	
7401 18	16	14	13	7451 18	16	14	13	74141 100	95	90	85	85	
7402 18	16	14	13	7453 18	16	14	13	74145 140	130	130	130	130	
7403 18	16	14	13	7454 18	16	14	13	74150 330	280	250	220	220	
7404 20	18	16	14	7460 18	16	14	13	74151 110	100	95	89	89	
7405 20	18	16	14	7470 30	28	25	24	74153 120	110	105	95	95	
7406 50	45	40	35	7472 30	28	27	23	74154 200	180	170	160	160	
7407 50	45	40	35	7473 40	38	36	30	74155 150	120	100	86	86	
7408 36	30	27	23	7474 40	38	32	28	74156 130	120	100	96	96	
7409 36	30	27	23	7475 55	52	50	49	74180 155	136	112	105	105	
7410 18	16	14	13	7476 40	36	32	30	74190 195	190	185	180	180	
7411 23	21	20	18	7480 100	95	90	85	74191 195	190	185	180	180	
7412 36	30	27	23	7481 125	115	110	105	74192 200	190	180	164	164	
7413 34	28	26	22	7482 100	96	90	85	74193 200	180	170	150	150	
7414 45	43	39	34	7483 100	97	95	92	74196 200	190	180	170	170	
7420 18	16	14	13	7484 120	115	110	105	74197 200	195	180	170	170	
7421 36	30	27	23	7485 250	245	240	230						
7426 32	29	23	20	7486 45	42	37	33						
7430 20	18	16	14	7490 75	67	60	52						
7432 40	36	32	28	7491A 100	92	85	79	709	14 pin DIL			32p	
7440 20	16	14	13	7492 75	70	65	60	741	8 pin DIL			34p	
7441 80	75	70	65	7493 75	68	60	52	741	14 pin DIL			28p	
7442 80	75	70	65	7494 95	90	85	80	723	8 pin DIL			95p	
7443 125	120	115	115	7495 105	100	95	90	747	14 pin DIL			85p	
7447 175	165	150	120	7496 100	95	90	85	748	8 pin DIL			35p	
				74100 250	240	235	230	74197 200	195	180	170	170	

## LINEAR IC's

14 pin DIL	32p
8 pin DIL	34p
14 pin DIL	28p
8 pin DIL	95p
14 pin DIL	85p
8 pin DIL	35p
DIL socket, 14 pin and 16 pin	16p



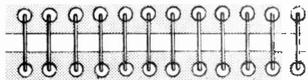

# INDUSTRY NOTEBOOK

By NEXUS



## CMOS CATCHES ON

Last year European manufacturers bought £1 million worth of CMOS devices. This year the figure will be £3 million and 1974 will see European sales topping £7 million. If these figures are correct, and top Motorola marketing men believe they are, then the faith of the pioneers led by RCA will be fully justified.

Watch out for Motorola grabbing a big share of the CMOS market. Their UK marketing manager is talking of "dedication" to the technique and is backing his words with a costly promotional campaign centred on a big applications seminar to be staged in London in early October. The seminar will also be going on tour to other European capitals.

Motorola latched on to the CMOS bandwagon by second-sourcing established RCA devices. But the pattern is now changing. Of 48 device types brought to the market last year by Motorola, 23 types were second-sourced RCA but 25 were Motorola originals. This year's developments bring the score up to 30 types second-sourcing RCA plus 50 Motorola originals.

While Motorola's newest European plant was in construction at East Kilbride there was indecision on its final function. But now the CMOS market is firming up I can reveal that East Kilbride is to be the major European centre for CMOS production.

At present, wafer diffusion is based on Phoenix, Arizona, assembly and packaging in plants in Mexico, Korea and Malaysia and with European testing in Scotland.

But East Kilbride is scheduled to start diffusion of 3-inch wafers in October and will thus have complete capability to serve Europe and will be totally committed to this task.

Manufacturers of CMOS see a world market worth more than £80 million annually in two years time. CMOS, they say, will bite savagely into the present TTL and DTL dominated markets at frequencies up to 25MHz. But more important is the opening up of completely new markets for which other forms of logic are not suitable. Cited are watches and clocks, car electronics, domestic appliances, and even toys.

## DRIVE-IN

The car market is not only opening up for electronic component manufacturers. The automatic test equipment (ATE) brigade are also moving in.

Historically, ATE found its feet in testing complex avionic systems and has slowly found its way down to more mundane tasks such as checking out PCB boards and other assemblies in manufacturing plants where it is used to speed up production and cut costs because automatic diagnosis of faults dispenses with skilled labour.

Car manufacturers are being invited to attend Automatic Test '73 Exhibition and Conference in Brighton in November where the programme includes papers on automated engine test beds. More than 30 ATE equipment manufacturers will be showing their skills in hardware and novel applications in the exhibition halls. But potential users of ATE still need a lot of education on the subject. I note from the provisional list of papers to be presented that D. B. Gemmell of Membrain Ltd. has submitted one with the intriguing title "Some Fancies and Fantasies in ATE Architecture" that could be amusing as well as instructional.

## TECHNICIAN TRAINING

A discussion document on technician training has been produced by a working party of the Institution of Electrical and Electronics Technician Engineers under the chairmanship of Robert Winton of Mullard Ltd. Entitled "The Future Development of Further Education Courses for Technician Engineers and Technicians" it proposes a modular course structure which will bring students forward to the educational standards stipulated by the Engineers' Registration Board.

An "open house" meeting will take place at 2.30 p.m., October 16, at the IEE H.Q., Savoy Place, for those interested in discussing the document with the working party. The document can be obtained free on request from the IEETE, 2 Savoy Hill, London, WC2R 0BS.

## CUT-PRICE COMPUTERS

While world meat prices soar, the cost of computing comes tumbling down. Computer Automation is now offering the latest Naked Mini/LSI for less than £500 in quantities of 200 or more. This is a computer-on-a-card, a single PCB of 15 x 17 x 1in dimensions weighing only 4lbs and designed for OEM use.

If you want the same thing boxed as a stand-alone unit with control console, data input keyboard and power supply the cost is £995 for one-off but still, say Computer Automation, less than half the listed price of the PDP-11-05 or Nova 1210 of comparable specification. Secret of the new low price is a central processor that uses only seven MOS LSI chips custom-built for the company.

## AUTUMN BOOM

After the August holiday season expect plenty of product and business announcements in September. FR Electronics is concluding marketing deals with more overseas companies. Dymar Electronics will be launching a complete new range of land mobile communications equipment in London on September 12 which could well be countered by a surprise announcement from market leader Pye. But Dymar, one of the liveliest companies in mobile radio, has a fine reputation and should continue to prosper in this highly competitive but fast-expanding field.

Expect, too, some new products from Racal Group whose 5th biennial Racalex exhibition and conference opens on September 25

## RAIDING PARTY

While British TV manufacturers are worried about the invasion of Japanese sets in the UK market, a group of British components and equipment manufacturers will be probing the Japanese market at the great Japan Electronics Show in Osaka in October.

Fifteen companies are taking the long trip East with the backing of the Department of Trade and Industry and the Electronic Engineering Association. Trade prospects in Japan, say the DTI, are good for companies that have the right products.

# Readout —

## A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

### PLUGGING THE LEAK

Sir—With regard to your present series of articles "P.E. Sound Synthesiser". First, may I point out, that my comments are in no way intended to "have a go" at Mr Shaw's circuits, which show considerable technical ability and have no doubt required considerable effort on his behalf.

I have found, however, during evaluation of the Ramp Generator circuit a possible snag and therefore supply my findings as other readers may find my conclusions useful.

In Mr Shaw's circuit, an OC140 transistor is employed to switch the direction of integration. It would appear that the two main factors governing the choice of transistor type are: low leakage—since the transistor is in a high current amplifying loop—and high base/emitter reverse bias capability—since the emitter is fixed at  $-3.5V$  during main ramp, with the base held at approximately  $-14V$  by the comparator output.

On testing my constructed generator, it was found that upon switching on the integrator output ramped positive to its positive

saturation level, although zero volts was applied to the input and the 10 megohm shunt in circuit. Adjustment of the offset null pot proved useless.

The problem, it was found, was due to leakage in TR1, being sufficient to drive the integrator, which once started, naturally continued to ramp until hitting the rail; the leakage being too large to be offset by the null control.

I believe Mr Shaw's choice of transistor was due to the OC140's base/emitter reverse bias capability, which is in the order of  $20V$ ; however, the leakage current of the device, being of germanium junction construction, can be as high as 3 microamps, more than adequate to cause IC1 to integrate. Further, since the direction of integration produced is positive, the comparator cannot switch and a steady state is produced with IC1 output "stuck" at the positive rail.

My suggested solution to the problem, should it arise, is as follows:

The OC140 may be replaced by a silicon transistor such as a BC109; this will reduce the maximum possible leakage current to nA. However, since the BC109 cannot withstand the high reverse bias, the

base/emitter junction will. Zener. This will not affect the circuit operation, but if it is considered "not nice" to Zener the junction, a small signal diode—such as an 1N914—can be inserted in series with the base to protect the transistor.

Finally, since a silicon transistor has a higher "on" resistance than a germanium device the 82 ohm resistor should be reduced in value until the ramp starts at zero volts. Without modification of this value the ramp will be approximately 200mV negative of earth.

Alan A. Thomas,  
Engineering Dept.,  
Dolby Laboratories Inc.

I am indebted to Mr Thomas who, with his lucid explanation of an apparent fault in the Ramp Generator, has highlighted an omission in the setting-up procedure for which I humbly apologise.

In order to avoid the problems associated with current leakage through TR1 it is necessary to temporarily disconnect R6 from the summing junction of IC1 during the balancing of the offset. With the setting-up procedure as outlined in the original text IC1 can be prevented from going into positive saturation by adjustment of VRI to counteract the leakage through TR1 but this is a rather unsatisfactory method since it is not possible to be absolutely sure of the input conditions at IC1 and thus there is little point in nulling the offset.

Mr Thomas's suggestion of replacing the OC140 with a diode protected BC109 is particularly valid since it has been learned that, although the OC140 is still available from a number of sources, it is now considered to be an obsolete device.

G. D. Shaw

### BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

#### November 1972

Mr. J. M. Cathrine, 53 Boosbeck Road, Skelton-in-Cleveland, Saltburn-by-the-Sea, Yorkshire, TS12 2DQ.

#### May 1971

Mr. D. J. Broad, 34 Rowan Crescent, Dartford, Kent, DA1 2QX.

#### January to October 1968

Mr. N. Lee, Cheadle Hulme School, Cheadle Hulme, Cheshire, SK8 6EF.

#### July to October 1972

Mr. S. T. Saw, 19 Malvern Road, Southsea, Hants., PO5 2LZ.

#### September 1971, February 1972, May 1972

Mr. S. E. Berry, Old Rectory, Tunworth, Basingstoke, Hants.

#### April to August 1971

Mr. R. J. Patterson, Laburnum Cottage, Poplar Road, Hargham Road, Attleborough, Norfolk.

#### September and October 1972

Mr. J. Williams, 31 Peel Crescent, Westfield, Lancaster, Lancs.

#### December 1972

Mr. J. I. Lewis, 89 The Grove, Isleworth Middlesex, TW7 4JD.

#### June 1971

Mr. A. J. Holmes, 4 Castle Avenue, Datchet, Bucks.

#### July to October 1972

Mr. J. Y. T. Lee, 20 Wong Chuk Hand Road, 2nd Floor, Aberdeen, Hong Kong.

#### December 1972

Mr. A. G. Morgan, 123 Queen Road, Eastwood, Nottingham, NG16 3NG.

#### July 1971

Mr. E. S. Eaves, Winthorpe, Holmfield Avenue, Blackpool, Cleveleys, Lancs., FY5 2QT.

#### August 1972

Mr. S. A. Hook, 21 Peak Veiv Road, Chesterfield, Derbyshire, S40 4NW.

#### June 1969 to March 1970

Mr. D. Quarterman, 49 Baddesley Road, Olton, Solihull.

#### April 1973

Mr. D. Weightman, 21 Glenroy Street, Roath, Cardiff.

#### July 1972 to March 1973

Mr D. Couser, Winnipeg, Manitoba, Canada.

#### March 1973

Mr H. Brede, 24 Branet Road, Scunthorpe, Lincs.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

#### August 1972 and February 1973

Mr Hans Gram, Civilingenior Tarphagevej 253-6800 Varde, Scandinavia.

#### October 1972

Mr G. Hibbert, 12 Moray Street, Richmond, NSW, Australia.

#### October and November 1972

Mr R. Thomas, 8440 18th Ave. S.W. Seattle, Washington, 98106, USA.

#### November and December 1968

Mr P. Ghose, Wireless inspector, 310-8, Hill Colony, P.O.—Bihar, India.

#### February to April 1973

Mr R. Shaul, 23 Southlea Avenue, Southbourne, Bournemouth.

#### February 1972

Mr C. Kelly, 59 Glentow Road, Whitehall, Dublin 9.

#### September 1968, April, June and September 1970

Mr D. Hill, The Jacarandas, Bois Lane, Chesham Bois, Bucks.

#### January and February 1973

Mr T. Robinson, Wayford, Bolney Road, Shiplake, Henley-on-Thames.

#### May 1969 to March 1970

Mr D. Yuill, 14 Belston, By Ayr, Scotland.

#### January to October 1968

Mr D. G. Haslam, 35 Berrigan Crescent, O'Connor, A.C.T. 2601, Australia.

# TRANSFORMERS

**MAINS ISOLATING SERIES**  
Primary 120/240 Volts. Secondary 120/240 Volts Centre  
Tapped and Earth Shielded  
**ALSO AVAILABLE WITH 115/120V SEC. WINDING**

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	1.94 30
149	60	3 12	9.9 x 7.7 x 8.6	2.88 36
150	100	5 8	9.9 x 8.9 x 8.6	3.16 52
151	200	8 0	12.1 x 9.3 x 10.2	5.31 52
152	250	13 12	12.1 x 11.8 x 10.2	7.01 67
153	350	15 0	14.0 x 10.8 x 11.8	9.40 82
154	500	19 8	14.0 x 13.4 x 11.8	13.55 * *
155	750	29 0	17.2 x 14.0 x 14.0	19.26 * *
156	1000	38 0	17.2 x 16.6 x 14.0	24.97 * *
158	2000	60 0	21.6 x 15.3 x 18.1	41.25 * *

**PLEASE NOTE  
NEW ADDRESS  
AS BELOW**

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.02 22
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.00 30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.42 36
66	300	6 4	9.9 x 9.6 x 8.6	..	4.70 52
67	500	12 8	12.1 x 11.2 x 10.2	..	6.98 67
84	1000	19 8	14.0 x 13.4 x 14.3	..	12.69 82
93	1500	30 4	14.0 x 15.9 x 14.3	..	18.39 * *
95	2000	32 0	17.2 x 16.6 x 14.0	..	24.00 * *
73	3000	40 0	21.6 x 13.4 x 18.1	..	32.67 * *

**TOTALLY ENCLOSED 115V AUTO TRANSFORMERS**  
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets. £9.49. P & P 67p.  
Also available a 20 Watt version, £2.03. P & P 22p.

**LOW VOLTAGE SERIES (ISOLATED)**  
**PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0 25	8 4	8 x 2.9 x 3.5 0-12V at 0-25A x 2	1.02 22
213	1.0	0 5	1 4	6.1 x 5.8 x 4.8 0-12V at 0-5A x 2	1.22 22
71	2	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	1.60 22
18	4	2 2	8.9 x 7.7 x 7.7	0-12V at 2A x 2	2.24 36
70	6	3 3	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.55 52
108	8	4 5	8.9 x 8.9 x 8.6	0-12V at 4A x 2	3.00 52
72	10	5 6	4 9	9.6 x 8.6 0-12V at 5A x 2	3.55 52
17	16	8 8	12 1	9.9 x 10.2 0-12V at 8A x 2	5.48 52
115	20	10 11	8	14.0 x 9.6 x 11.8 0-12V at 10A x 2	6.98 67
187	30	15 15	8	14.0 x 12.1 x 11.8 0-12V at 15A x 2	12.90 82
226	60	30 32	0	17.2 x 15.3 x 14.0 0-12V at 30A x 2	23.72 * *

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6 1	5.8 x 4.8 0-12-15-20-24-30V	1.22 22
79	1.0	2 4	7 0	6.7 x 6.1	1.62 36
3	2.0	3 4	8 9	7.7 x 7.7	2.43 36
20	3.0	4 8	9 0	8.3 x 8.6	2.99 42
21	4.0	6 4	9 9	9.6 x 8.6	3.55 52
51	5.0	6 12	12 1	8.6 x 10.2	4.42 52
117	6.0	8 0	12 1	9.3 x 10.2	5.28 52
88	8.0	12 0	12 1	11.8 x 10.2	6.82 67
89	10.0	13 12	14 0	10.2 x 11.8	8.36 67

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7 0	6.4 x 6.1 0-19-25-33-40-50V	1.60 30
103	1.0	2 12	8 3	7.4 x 7.0	2.34 36
104	2.0	5 8	7 9	8.9 x 8.6	3.25 42
105	3.0	6 12	9 9	10.2 x 8.6	4.41 52
106	4.0	10 0	12 1	10.5 x 10.2	5.84 52
107	6.0	12 0	14 0	10.2 x 11.8	8.63 67
118	8.0	18 0	14 0	12.7 x 11.8	11.27 97
119	10.0	25 0	17 2	12.7 x 14.0	14.13 * *

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	1 4	7 0	6.7 x 6.1 0-24-30-40-48-60V	1.62 36
126	1.0	3 4	8 9	7.7 x 7.7	2.26 36
127	2.0	6 4	9 9	9.6 x 8.6	3.55 42
125	3.0	8 12	12 1	9.9 x 10.2	5.41 52
123	4.0	13 12	12 1	11.8 x 10.2	6.98 67
120	6.0	15 8	14 0	12.1 x 11.8	10.12 82
122	10.0	25 0	17 2	12.7 x 14.0	16.75 * *

**EQUIPMENT TRANSFORMER**  
Ref. 238 PRI 0240 Screen Sec. 3.0 3V. RMS at 200mA. Size cm. 2.8 x 2.6 x 2.0. Weight 2oz. £1.18. P & P. 10p.

Ref. No.	Amps.	Weight lb oz	Size cm.	P & P £ p
45	1.5	1 8	7 0 x 6.1 x 6.1	1.61 30
5	4.0	3 4	8 9 x 7.7 x 7.7	2.45 42
86	6.0	6 4	9 9 x 9.6 x 8.6	3.70 52
146	6.0	6 12	9 9 x 10.2 x 8.6	4.22 52
50	12.5	12 0	14 0 x 10.2 x 11.8	6.29 67

All ratings are continuous. Standard construction: open with folder tags and vacuum impregnation. \*Carriage via B.R.S.

**FULL SPEC. TRANSISTORS**  
BC107/108/109 12p each. | 2N3055 60p each | AD161/162 60p pair  
+ mica and bushes | + mica and bushes

**ELECTROSIL RESISTORS • AVOMETERS**  
**PLEASE ADD 10% FOR V.A.T. INCLUDING P. & P.**

**BARRIE electronics**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/8  
NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

# TO SPARK YOUR IMAGINATION!

Kit comprises **EVERYTHING:**  
Case, cables,  
coil connectors,  
Silicon grease,  
8-page  
instruction  
leaflet.



the  
**SPARKRITE**  
Electronic Ignition Kit  
only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £9.35 inc. V.A.T. and postage (12 volt only. State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage. GUARANTEED 5 YEARS.

**ORDER NOW** To: ELECTRONICS DESIGN ASSOCIATES,  
82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing.)

PE10

TRANSISTORS	
Output Transistors	
BD 112	25p
OC 36	50p
BD 145	25p
Small Signal N.P.N.	
BC 108	10p
BC 109	10p
BF 194	10p
Transmitting Types	
BFR 64	£1
BKY 89A	£5
BLY 93A	£9
Microwave Varactor Diodes	
BXY 27/28/32/35/36/37/38/39/40/41	£1
Microwave Detector	
CAY 10	£5
Microwave Mixer	
CL 7331	£20
Microwave Gunn Effect Oscillator	
CL 8370	£10
CL 8380	£10
CL 8390	£10
CL 8470	£40
Microwave Tunnel Diodes	
AEY 13	£5
AEY 16	£10
R.F. Transistors	
BF 180	20p
BF 194	10p
AF 124	20p

Field Effect Transistors	25p
BFW 12/13/14	25p
Micro-miniature N.P.N.	
BFS 18R	10p
LDA 400/403/450/452	10p
Infrared Transmitters	
COY 11A	£4
COY 12A	£10
Light-sensitive Trans	
OCF 70	20p
Complementary Drivers, 2 watts (per matched pair)	30p

**NEW! NEW! NEW! NEW!**  
An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.  
Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.  
Light sensitive aerosol spray ... .. £1-00 plus Developer and Etchant ... .. 50p postage

**NEWER THAN NEW!**  
Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.  
75mm x 100mm ... .. 33p  
150mm x 100mm ... .. 66p  
150mm x 200mm ... .. £1-32  
Epoxy-Resin  
75mm x 100mm ... .. 22p  
100mm x 150mm ... .. 44p  
150mm x 200mm ... .. 88p  
Copper-clad Fibre Board  
12in x 6in ... .. 45p  
Copper-clad Epoxy Resin Board  
12in x 6in ... .. 25p

VEROBOARD	
2 1/2in x 1in x 0.15in	6p
3 1/2in x 2 1/2in x 0.15in	16p
3 1/2in x 3 1/2in x 0.15in	20p
5in x 2 1/2in x 0.15in	20p
5in x 3 1/2in x 0.15in	28p
17in x 2 1/2in x 0.15in	55p
17in x 3 1/2in x 0.15in	74p
3 1/2in x 2 1/2in x 0.1in	21p
3 1/2in x 3 1/2in x 0.1in	24p
5in x 2 1/2in x 0.1in	23p
5in x 3 1/2in x 0.1in	28p

Spot Face Cutter 38p. Pin Insert Tool 48p.  
Terminal Pins (0.1 or 0.15) 36 for 18p.  
Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p.  
\*\*ODDS & ENDS —1p sq in

MULLARD POLYESTER CAPACITORS			
500,000 in STOCK!!!			
0.001µF	0.0018µF	0.0056µF	0.015µF
0.0012µF	0.0022µF	0.01µF	0.033µF
0.0015µF	0.0027µF	0.012µF	0.082µF
20p dozen, 75p—100, £5—1,000, £40—10,000			
0.15µF	0.18µF	0.22µF	0.39µF
0.68µF			
20p dozen; £1—100; £6—50—1,000; £50—10,000			

ERIE MONOLITHIC CERAMIC CAPACITORS	
3p each, 20p dozen, £1-75 per 100	
10pF	68pF
15pF	100pF
22pF	150pF
33pF	220pF
39pF	330pF
47pF	470pF
560pF	620pF
680pF	1,000pF

**SPECIAL OFFER**  
**UNI-JUNCTION TRANSISTOR SIMILAR TO 2N2646**  
**25p**

**£1** 100 1/2 WATT RESISTORS  
100 CERAMIC CAPACITORS  
100 DIODES

**£1** 1 VEROBOARD CUTTER  
5 2 1/2in x 0.15 BOARDS  
50 SQ. IN "ODD PIECES"  
VERO

**£1** 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS  
BC108, ETC.

**£1** 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS

POSTAGE 15p PACK No. 1

POSTAGE 15p PACK No. 3

POSTAGE 15p PACK No. 5

POSTAGE 25p PACK No. 7

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
100 POLYSTYRENE CAPACITORS

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
50 MULLARD POLYESTER CAPACITORS

**£1** 1 TRANSISTORISED SIGNAL TRACER KIT  
1 TRANSISTORISED SIGNAL INJECTOR KIT

**£1** 100 RESISTORS  
100 CAPACITORS (ASSORTED TYPES)

POSTAGE 15p PACK No. 2

POSTAGE 15p PACK No. 4

POSTAGE 15p PACK No. 6


POSTAGE 15p PACK No. 8

**POSTAGE (MINIMUM) 15P PER ORDER ALL GOODS PLUS 10% V.A.T.**

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

NEAT!  
HANDY!  
TIDY!

**DISCOUNT PRICES**

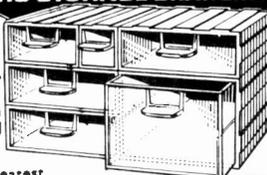

Newest, nearest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/1D and 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

**5 SIZES ALL INTERLOCK**

**BUY AT TRADE PRICES!**  
SINGLE UNITS (1D) (5ins x 2 1/2ins x 2 1/2ins). £1-25 DOZEN.  
DOUBLE UNITS (2D) (5ins x 4 1/2ins x 2 1/2ins). £2-10 DOZEN.  
TREBLE (3D) £2-20 for 8.  
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £3-25 for 8, EXTRA LARGE SIZE (6D1) £3-10 for 8.


**PLUS QUANTITY DISCOUNTS!**  
Orders £6 and over DEDUCT 5% in the £  
Orders £10 and over DEDUCT 7 1/2% in the £  
Orders £20 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES  
Please add 10% V.A.T. to total remittance

**IVORYET LIMITED** (Dept. PE10) 124 Cricklewood Broadway, London, N.V.2  
Tel. 01-450 4844

**QUADROPHONIC PAN POT**

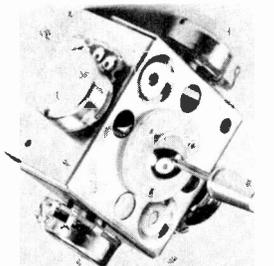

**A THIRD DIMENSION IN CONTROL TECHNOLOGY**

SEND **£6-75**  
(INC. V.A.T. AND POSTAGE)  
FOR SAMPLE

For full details and application notes write to:

**ALLEN & HEATH LTD.**  
PEMBROKE HOUSE • CAMPSBOURNE ROAD • HORNSEY • LONDON, N.8  
Telephone 01-340 3291

**A DEXTER DIMMASWITCH**

**ALLOWS COMPLETE LIGHTING CONTROL**




The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.  
600 watt £3.52 Kit form £2.97  
300 watt £2.97 Kit form £2.42  
All plus 12p post and packing  
Prices include VAT. Please send c.w.o. to:

**DEXTER & COMPANY**  
1 ULVER HOUSE  
19 KING STREET  
CHESTER CH1 2AH  
Tel: 0244-25883

AS SUPPLIED TO H.M. GOVERNMENT DEPARTMENTS, HOSPITALS, LOCAL AUTHORITIES, ETC.

# ALL OUR PRICES INCLUDE V.A.T.

## BSR LATEST SUPERSLIM STEREO & MONO

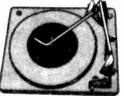

Plays 18", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V Size 13 1/2 x 11 1/2 in.

Above motor board 3 1/2 in. below motor board 2 1/2 in.

with STEREO and MONO XTAL £8.25 Post 25p.

### PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Chrome fittings.

Motor board cut for BSR deck £4.50 Post 25p

## E.M.I. WOOFER AND TWEETER KIT £5.75

Available separately Post 25p.

Woofer £4.25 Tweeter £1.50

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms

Maximum Power 12 watts

Useful Response 35 to 18,000 c/s

Base Resonance 45 c/s

SUITABLE ENCLOSURE 20 x 13 x 9 in. MODERN GROOVED FRONT DESIGN, TEAK FINISH



£9.90 Post 25p

## SPECIAL OFFER!

### SMITH CLOCKWORK 15 AMP TIME SWITCH



Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 80 minutes Type A or 0 to 6 hours Type B. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated.

OUR PRICE £1.65. or 23 pair. Post 25p

(PLEASE STATE TYPE A OR B WHEN ORDERING)

## WEYRAD P50 — TRANSISTOR COILS

RASW Ferrite Aerial 72p

Osc. P50/LAC 33p

I.F. P50/2CC 470 kc/s 38p

3rd I.F. P50/3CC 38p

Spare Cores 3p

Mullard Ferrite Rod 8 x 1/2 in, 20p. 6 x 1/2 in, 20p.

Driver Trans. LFDT4 58p

Printed Circuit, PCAL 58p

J.S. Tuning Gang 85p

Weyrad Booklet 10p

OPTI 58p

## VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.

STEREO L/S 5p. D.P. 75p.

Edge 5K.S.P. Transistor 25p.

80 Ohm Coax 4p yd.

BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40-£0.80 yd. £2.

FRINGE LOW LOSS 10p yd.

Ideal 625 and colour

## 8in. or 10in. ELAC HI-FI SPEAKER



Dual cone plasticised roll surround. Large ceramic magnet. 55-18,000 c/s. Bass resonance 50 c/s. 8 ohm impedance. 8in 10 watts, 10in 12 watts music power.

£3.75 Post 25p

## E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters. And crossover. £4.50

wait. State 3 or 8 or 15 ohm. As illustrated. Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. 8 ohm. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p

£2.75



## Bookshelf Cabinet 16 x 10 x 9in. £5.50

Teak finish Post 25p

## BRITISH MADE STEREO MULTIPLEX DECODER £6.95

Post 25p

Brand New. 7 transistors Plus integrated circuit. Fibre-Glass printed circuit board. Size 21 x 6 1/2 x 1 1/2 in. Pre-Aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100mV input. Full instructions for use with any FM Tuner. Some technical experience essential.

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 1/2 in sides 6 x 4 in 45p; 6 x 6 in 55p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 9 in 95p; 16 x 6 in 90p; 12 x 3 in 60p; 16 x 10 in £1.

ALUMINIUM BOX 6 x 4 x 4 in 80p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 9p; 8 x 6 in 15p; 14 x 9 in 18p; 10 x 7 in 19p; 12 x 8 in 20p; 12 x 8 in 25p; 16 x 6 in 28p; 14 x 9 in 29p; 12 x 12 in 40p; 16 x 10 in 50p.

PAXOLIN PANEL 10 x 8 in 15p.

# RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON

Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)

Buses 50, 68, 159. Rail Selhurst. Tel. 01-684-1665

## ANOTHER R.C.S. BARGAIN!

### 4 TRANSISTOR MONO AMPLIFIER

Powerful 8 watt output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. Post 25p

Size 6in wide x 4in deep x 3in high. £5.95

Suitable 7" x 4" speaker, £1.

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2.20 Post 25p

Details S.A.E. Size 3 1/2 x 1 1/2 in.

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 x 1 in. Response 25 c/s to 25 kc/s, 26 dB gain. Post 25p

For use with valve or transistor equipment. £9.9p

Full instructions supplied. Details S.A.E.

## COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 8 1/2 in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 240V A.C. mains. Attractive £25 Plus 25p carriage.

## BRITISH FM/VHF TUNING HEART

88 to 108 M/CS British made. 2 Transistors ready aligned requires 10-7 M/CS I.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price £3.95 Post 20p

## MAINS TRANSFORMERS

All post 25p each

Eagle MT12 12-0-12V 50mA 90p

250-0-250 90MA 6-3V 3-5A, 6-3V 1A, or 5V 2A £2.50

350-0-350 90MA 6-3V 3-5A, 6-3V 1A, or 5V 2A £3

300-0-300 120MA 6-3V 4A C.T.; 6-3V 2A £3.25

MINIATURE 200V, 20MA, 6-3V 1A, 2 1/2 x 2 1/2 in 75p

MIDGET 220V 45MA, 6-3V 2A, 2 1/2 x 2 1/2 in 90p

HEATER TRANS. 6-3V 3A 60p

GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A, 3A, 4A, 5A, 6A, 8A, 10A, 12A, 15A, 18A, 24A and 30V £2.80

1A, 6A, 8A, 10A, 12A, 15A, 18A, 24A, 30A, 36A, 40A, 48A, 60V £2.80

2A, 6A, 8A, 10A, 12A, 15A, 18A, 24A, 30A, 36A, 40A, 48A, 60V £2.80

5A, 6A, 8A, 10A, 12A, 15A, 18A, 24A, 30A, 36A, 40A, 48A, 60V £2.75

3A, 5A, 8A, 13V £1.00, Ditto 5A £1.20

3A, 5A, 8A, 10A, 13V, 5-0-5V £1.30, Ditto 5A £1.50

6-0-6 500 mA 90p

9V 1 amp 95p

12V 300 mA 75p

12V 500 mA 85p

12V 750 mA 95p

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V. 150W £2.80; 500W £6.25; 750W £10; 1000W £15.

CHARGER TRANSFORMERS. Inpnt 200/250V. for 6 or 12V, 1 1/2 A, £1.50; 2A, £1.80; 4A, £2.50.

BATTERY CHARGERS. 1 1/2 A £2; 3A £3; 4A £4; 5A £4.50.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Variolin impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 Carr. 50p

Famous make. (Value £10)

Can be used as 800W auto transformers 240-110V.

IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

## NEW ELECTROLYTIC CONDENSERS

2/350V	14p	250/25V	14p	50+50/350V	50p
4/350V	14p	500/25V	20p	60+100/350V	85p
8/450V	18p	1000/25V	35p	32+32/250V	20p
16/450V	22p	1000/50V	47p	32+32/450V	45p
32/450V	35p	8+8/450V	22p	350+50/325V	55p
25/25V	10p	8+18/450V	25p		
50/50V	10p	18+16/450V	40p	32+32+32/350V	55p
100/25V	10p	32+32/350V	40p	100+50+50/350V	55p

## LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.

500mF 12V 15p; 25V 20p; 50V 30p.

1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.

200mF 8V 25p; 25V 42p; 50V 57p.

2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.

5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF, 4p.

PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p.

500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p.

SILVER MICA. Close tolerance 1%. 2.2-500pF 8p; 680-2200pF 10p; 7.0-5.800pF 20p; 6.800pF-0.01, mid 30p each.

TWIN GANG. 2"00-280pF+176pF, 85p; 500pF standard 45p.

365pF+365pF with 25pF+25pF. Slow motion drive 50p;

SHORT WAVE SINGLE. 10pF, 30p, 25pF, 55p, 50pF, 85p.

NEON PANEL INDICATORS 250V AC/DC. Amber 20p.

RESISTORS. 1W, 1/2W, 1W, 20%, 1p; 2W, 5p. 10 to 10M. HIGH STABILITY. 1W 2%, 10 ohms to 6 meg., 10p.

Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p; each 0.5 ohm to 8 ohms 10p.

TAPE OSCILLATOR COIL. Valve type 35p.

ALL MODELS "BAKER SPEAKERS" IN STOCK  
Hi Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. £2p Post 1 free

## BAKER MAJOR 12" £9.90



Post 25p

30-14,500 c/s, 12in. Double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 6 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50

Please state 3 or 8 or 15 ohms. Post 25p

## BAKER "BIG-SOUND" SPEAKERS Ret 25p

'Group 25'	'Group 35'	'Group 50'
12in. £8.80	12in. £9.90	15in. £12
25W	35W	50W
3 or 6 or 15 ohm	3 or 6 or 15 ohm	3 or 15 ohm

TEAK VENEERED HI-FI SPEAKER & CABINETS.

For 12in or 10in dia. speaker 20 x 13 x 9in. £29.90. Post 25p.

For 12 x 8in or 8in speaker 16 x 10 x 8in. £25.50. Post 25p.

For 8 x 5in speaker 16 x 8 x 8in. £24.40. Post 25p.

For 6in and Tweeter 12 x 8 x 6in. £24.00. Post 25p.

LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

## GOODMANS 6 1/2in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12 x 6 x 2 1/2 Suitable Tweeter £2

£4



## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in deep. Rating 10W, 3 ohm or 15 ohm mod. Crossover 85p

£1.90 Post 20p.



## SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-18kc/s, 10W 8 ohm or 15 ohm £1.95.

De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £3.

CROSSOVERS. TWO-WAY 3,000 c/s 3 or 8 or 15 ohm 95p.

LOUDSPEAKERS P.M. 3 OHMS. 7x4in. £1.25; 6 1/2in. £1.50; 8 x 5in. £1.60; 10in. £2.00; 8in. £1.75; 10 x 6in. £1.80.

SPECIAL OFFER! 8 ohm, 2 1/2in, 2 1/2in; 35 ohm, 2in, 3in. 25 ohm, 2 1/2in dia., 3in dia., 5in dia.

25 ohm, 3 1/2in dia., 6 x 4in, 7 x 4in, 8 x 5in. £1 TYPE 3 ohm, 2 1/2in, 3 1/2in, 5in dia. (8 x 4in 8 ohms £1.50).

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4W £2.50, 10in diameter 5W £2.50; 12in diameter, 8W, £2.95.

VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.

MIKE trans. mn metal 100:1 £1.25.

## MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER



All purpose transistorised. Ideal for Groups, Disco and P.A. 4 input speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE.

£49 Carr. £100

## BARGAIN AM TUNER. Medium Wave. Transistor Superhet, Ferrite aerial. 9 volt. £4.95

## BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. STEREO VERSION OF ABOVE

£3.95

£5.95

## BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, 18 volt. D.C. Treble and bass controls. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES. SURFACE OR FLUSH 25p.

BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd.

JACK SOCKET Std. open-circuit 14p, closed circuit 25p;

Chrome Lead-Socket 45p. Phono Plugs 5p. Phono Socket 6p.

JACK PLUGS Std. Chrome 15p; 3.5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.

VALVE HOLDERS, 9p; CERAMICS 9p; CANS 5p.

## DE LUXE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt, spindle 1 1/2 x 3/8, size 3 1/2 x 3 1/2 in. As illustrated. With Cooling Fan. a.c. 240 V. Post 25p

£1.95

## TWO RPM GEARED MOTORS 95p

240V A.C. mains. Ideal for displays/disco light wheels. Post 25p.

## E.M.I. GRAM MOTOR. 120V or 240V a.c. 2,400 r.p.m. 2 pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p.

£1



# -the lowest prices!

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed  
Pak No. EQVT  
T1 8 2G3713 OC71  
T2 8 D1374 OC75  
T3 8 D1216 OC81D  
T4 8 2G381T OC81  
T5 8 2G382T OC82  
T6 8 2G344B OC44  
T7 8 2G343B OC45  
T8 8 2G378 OC78  
T9 8 2G399A 2N1302  
T10 8 2G417 AF117  
All 55p each pak

**ND120 NIXIE DRIVER TRANSISTOR.**  
Suitable replacement for BSX21, C407, 2N1893  
120eV  
1 25 100+  
0.19 0.17 0.18

Sil. trans. suitable for P.E. Organ. Metal TO-18  
Epyt. ZTX300 6p each.  
Any Quantity.

**GP100 TO3 METAL CASE SILICON**  
Vebo=80V. Vcco=50V.  
I.C.=10 amps. Ptot.=30W. hfe=30-170.  
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.  
1 25 100+  
0.48 0.44 0.40

**GP300 TO3 METAL CASE SILICON**  
Vebo=100V. Vcco=60V.  
I.C.=15 amps. Ptot.=115W. hfe=20. 100Tf.=1MHz. Suitable replacement for 2N3065, BDY11 or BDY20.  
1 25 100+  
0.55 0.58 0.51

**NEW 7th EDITION TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. 90p each.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.**

**UT46 UNIJUNCTION TRANSISTORS**  
Direct replacement for T1N 43rand BEN 3000 also electrically equivalent to 2N2846  
1 25 100+  
0.30 0.28 0.22

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY-27/28/95A.** All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2996, BCY70. When ordering please state preference NPN or PNP.  
20 For 0.55  
50 For 1.10  
100 For 1.92  
500 For 8.25  
1000 For 14.30

**SIL. G.P. DIODES 2p**  
300mA 30 0.55  
40FV (Min.) 100 1.65  
Sub-Min. 500 5.50  
Full Tested 1,000 9.90  
Ideal for Organ Builders.

**R2400 TO3 NPN SILICON HIGH VOLTAGE**  
Vebo=250V. Vcco=100V. I.C.=6 amps. Ptot.=30W. hfe=typ. 20  
1T=5MHz  
1 25 100+  
0.55 0.50 0.44

**AD161/162**  
M/P COMP. GERM. TRANS. OUR LOWEST PRICE OF 61p PER PAIR

**LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS**

**SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BPX25 and P21. BRAND NEW Full data available. Fully guaranteed.**  
Qty. 1-24 25-99 100up  
Price each 60p 44p 38p

## INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0.55	UIC46	= 5 x 7446	0.55	UIC86	= 5 x 7486	0.55
UIC01	= 12 x 7401	0.55	UIC48	= 5 x 7448	0.55	UIC90	= 5 x 7490	0.55
UIC02	= 12 x 7402	0.55	UIC50	= 12 x 7450	0.55	UIC91	= 5 x 7491	0.55
UIC03	= 12 x 7403	0.55	UIC51	= 12 x 7451	0.55	UIC92	= 5 x 7492	0.55
UIC04	= 12 x 7404	0.55	UIC53	= 12 x 7453	0.55	UIC93	= 5 x 7493	0.55
UIC05	= 12 x 7405	0.55	UIC54	= 12 x 7454	0.55	UIC94	= 5 x 7494	0.55
UIC06	= 8 x 7406	0.55	UIC60	= 12 x 7460	0.55	UIC96	= 5 x 7496	0.55
UIC07	= 8 x 7407	0.55	UIC70	= 8 x 7470	0.55	UIC00	= 5 x 74100	0.55
UIC08	= 12 x 7410	0.55	UIC72	= 8 x 7472	0.55	UIC121	= 5 x 74121	0.55
UIC20	= 12 x 7420	0.55	UIC73	= 8 x 7473	0.55	UIC141	= 5 x 74141	0.55
UIC30	= 12 x 7430	0.55	UIC74	= 8 x 7474	0.55	UIC151	= 5 x 74151	0.55
UIC40	= 12 x 7440	0.55	UIC76	= 8 x 7476	0.55	UIC154	= 5 x 74154	0.55
UIC41	= 5 x 7441	0.55	UIC80	= 5 x 7480	0.55	UIC193	= 5 x 74193	0.55
UIC42	= 5 x 7442	0.55	UIC81	= 5 x 7481	0.55	UIC199	= 5 x 74199	0.55
UIC43	= 5 x 7443	0.55	UIC82	= 5 x 7482	0.55			
UIC44	= 5 x 7444	0.55	UIC83	= 5 x 7483	0.55			
UIC45	= 5 x 7445	0.55						

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UICX1.

**2 Amp. BRIDGE RECTS.**  
50 v RMS 35p each  
100 v RMS 40p ..  
400 v RMS 50p ..  
Size 16 mm x 16 mm.

**D1699 NPN SILICON DUAL TRANSISTOR**  
(Similar to 2N2060)  
1 25 100+  
0.28 0.28 0.23

**BIP 19/20 TO3 NPN PLASTIC SILICON**  
Vebo=100V. Vcco=50V. I.C.=10 amps. Ptot. 50W hfe=typ. 100 fT=3MHz.  
1 25 100+  
0.38 0.35 0.32 0.68 0.61 0.55

**QUALITY TESTED SEMICONDUCTORS**

Pak No.	Description	Price 2p
Q 1	20 Red spot transistors pnp	0.55
Q 2	16 White spot R.F. transistors pnp	0.55
Q 3	4 OC77 type transistors	0.55
Q 4	6 Matched transistors OC44/45/81/81D	0.55
Q 5	4 OC75 transistors	0.55
Q 6	5 OC72 transistors	0.55
Q 7	4 AC128 transistors pnp high gain	0.55
Q 8	4 AC126 transistors pnp	0.55
Q 9	7 OC81 type transistors	0.55
Q 10	7 OC71 type transistors	0.55
Q11	2 AC127/128 Complementary pairs pnp/npn	0.55
Q12	3 AF116 type transistors	0.55
Q13	3 AF117 type transistors	0.55
Q14	3 OC171 H.F. type transistors	0.55
Q16	7 2N2926 Sil. Epoxy transistors mixed colours	0.55
Q17	2 GET880 low noise Germanium transistors	0.55
Q18	5 nps 2 x ST.141 & 3 x ST.140	0.55
Q19	4 MADDT'S 2 x MAT100 & 2 x MAT121	0.55
Q20	4 OC44 Germanium transistors A.F.	0.55
Q21	4 AC127 npn Germanium transistors	0.55
Q22	20 NKT transistors A.F. R.F. coded	0.55
Q23	10 OA202 Silicon diodes sub-min.	0.55
Q24	8 OA81 diodes	0.55
Q25	15 IN914 Silicon diodes 75P1V 75mA	0.55
Q26	8 OA95 Germanium diodes sub-min	0.55
Q27	2 10A 600 PIV Silicon rectifiers 18425R	0.55
Q29	2 Silicon power rectifiers BYZ13	0.55
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.55
Q30	7 Silicon switch transistors 2N706 npn	0.55
Q31	6 Silicon switch transistors 2N708, npn	0.55
Q32	3 pnp Silicon transistors 2 x 2N1131, npn	0.55
Q33	3 Silicon npn transistors 2N1711	0.55
Q34	7 Silicon npn transistors 2N2869, 300MHz (code P397)	0.55
Q35	3 Silicon pnp TO-5, 2 x 2N2904 & 1 x 2N2905	0.55
Q36	7 2N3646 TO-18 plastic 300MHz npn	0.55
Q37	3 2N3053 npn Silicon transistors	0.55
Q38	7 pnp transistors 4 x 2N3703, 3 x 2N3702	0.55

**ELECTRONIC SLIDE-RULE**  
The MK Slide Rule, designed to simplify Electronic calculations features the following scales:-  
Conversion of Frequency and Wavelength.  
Calculation of L, C and f of Tuned Circuits.  
Reactance and Self Inductance. Area of Circles.  
Volume of Cylinders. Resistance of Conductors.  
Weight of Conductors. Decibel Calculations.  
Angle Functions. Natural Logs and "e" Functions.  
Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and hp.  
A must for every electronic engineer and enthusiast. Size: 2cm x 4cm. Complete with case and instructions. Price each: 23.69

**FULL RANGE OF ZENER DIODES**

Voltage	Range	Price
2-33V	400mA (DO-7 Case)	15p ea. 11W (Top Hat) 20p ea. 10W (SO-10 Stud) 33p ea.

## KING OF THE PAKS Unequalled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	60 Mixed Germanium Transistors AF/RF	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.55
U 4	40 Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0.55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0.55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U10	20 BA Y50 charge storage Diodes DO-7 Glass	0.55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0.55
U13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0.55
U14	150 Mixed Silicon and Germanium Diodes	0.55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000 PIV	0.55
U17	30 Germanium PNP AF Transistors TO-5 like AC17-22	0.55
U18	8 6 Amp Silicon Rectifiers RYZ13 Type up to 600 PIV	0.55
U19	25 Silicon NPN Transistors like BC108	0.55
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0.55
U23	20 MADDT's like Milz Series PNP Transistors	0.55
U24	20 Germanium 1 Amp Transistors GJM Series up to 300 PIV	0.55
U25	25 300MHz NPN Silicon Transistors 2N708, BSY27	0.55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0.50
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR31/25-600	1.15
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0.55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0.55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 283042	0.55
U35	25 Silicon Planar Transistors PNP TO-18 2N2905	0.55
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.55
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0.55
U38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0.55
U39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0.55
U41	25 RF Germanium transistors TO-5, OC45, NKT72	0.55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0.55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.55
U44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0.55
U45	7 3A SCR. TO-68 up to 600PIV	1.10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

## NEW LOW PRICED TESTED S.C.R.'S

PIV	50	100	200	400	600	800
	2p	2p	2p	2p	2p	2p
1A TO5	0.22	0.27	0.27	0.32	0.42	0.63
3A TO66	0.27	0.27	0.32	0.42	0.52	0.70
5A TO66	0.39	0.52	0.54	0.59	0.75	0.88
5A TO64	0.36	0.52	0.54	0.62	0.76	0.88
7A TO48	0.52	0.55	0.62	0.67	0.84	0.99
10A TO48	0.55	0.63	0.67	0.83	1.07	1.32
16A TO48	0.58	0.62	0.67	0.77	0.97	1.50
30A TO48	1.27	1.54	1.78	1.93	—	4.40

POST OFFICE TELEPHONE		F.E.T.'S		DIACS		TRIACS	
DIALS 60p each.		2N3819 31p	2N5458 86p	FOR USE WITH TRIACS.		VROM 2A 6A 10A	
		2N3820 55p	2N5459 44p	BR100 (D32) 41p each		TO-5 TO-66 TO-18	
		2N3821 30p	2N5460 69p			2p	2p
		2N3823 31p	MPF105 41p	10 amp POTTED BRIDGE RECTIFIER on heat sink.		100V 35 55 88	
				100PIV. 99p each		200V 55 68 99	
						400V 77 83 1.21	

All prices quoted in new price. Giro No. 388-7006  
Please send all orders direct to warehouse and despatch department

**2N3055**  
115 WATT SIL POWER NPN 55p EACH

**BI-PAK**  
P.O. BOX 6, WARE - HERTS

Postage and packing add 11p. Overseas add extra for airmail.  
Minimum order 55p. Cash with order please.  
Guaranteed Satisfaction or Money Back

# P.E. RONDO

FULL SPECIFICATION KITS

Complete in every detail. Top Grade Glass Fibre PCBS. Full data and even solder included.

**CBS-SQ\* Matrix Decoder**  
£8.00 + VAT 80p

**PRE-AMP Board**  
£3.00 + VAT 30p

**MASTER VOLUME/TONE CONTROL**

**4 CHANNEL BALANCE CONTROL BOARD**

£8.50 + VAT 85p

**POWER AMP BOARD & HEAT SINK** (each board contains a stereo pair)  
£7.50 + VAT 75p

\*Regd. CBS INC.

Kits for all other units in the P.E. RONDO will be available as published.

## PHASE LOCKED LOOP STEREO DECODER

EASY TO BUILD!

(Approximately 30 mins.)

- EMPLOYS MC1301C
- REQUIRES 10-15v d.c.
- NO INSTRUMENTS NEEDED TO SET UP
- SIMPLE INSTRUCTIONS SUPPLIED

**COMPLETE KIT £3.40**

Plus 34p VAT

**AUTOMATIC BEACON FITTING**  
34p + 3p VAT Extra

## STUDIO ELECTRONICS

P.O. BOX No. 18, HARLOW, ESSEX CM18 6SH

Telephone: Harlow (02796) 25457

### ORDER FORM

ALL PRICES POST FREE!

Please Supply

CBS-SQ\* DECODERS

PRE-AMPS

POWER AMPS

MASTER VOL.

STEREO DECODER

Money Enclosed £


NAME

ADDRESS

BLOCK CAPITALS PLEASE

PE10

# VEROBOARD

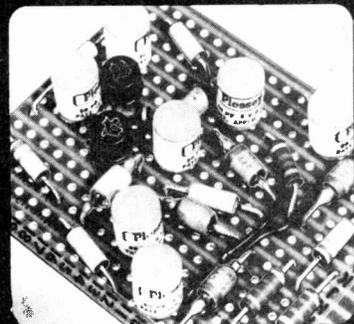

**VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK**

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER.

TRADE DISTRIBUTOR: N. Rose (Electrical) Ltd., London, W.C.1.



VERO ELECTRONICS LTD.  
Industrial Estate, Chandler's Ford,  
S05 3ZB Tel: Chandler's Ford 2952

## RADIO AMATEUR'S HANDBOOK 1973

APRIL

Price £2.95

**HANDBOOK OF PRACTICAL ELECTRONIC MUSICAL NOVELTIES** by Babani. Price 55p.

**GUIDE TO BROADCASTING STATIONS** by Wireless World. Price 80p.

**110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR** by R. M. Marston. Price £1.30.

**HOW TO USE INTEGRATED CIRCUIT LOGIC ELEMENTS** by J. W. Streater. Price £1.50.

**CONSTRUCTORS MANUAL OF ELECTRONIC CIRCUITS FOR THE HOME** by Babani. Price 55p.

**HI FI IN THE HOME** by John Crabbe. Price £2.15.

**TELEVISION ENGINEERS' POCKET BOOK** by P. J. McGoldrick. Price £2.65.

**COLOUR TV WITH PARTICULAR REF. TO THE PAL SYSTEM** by G. N. Patchett. Price £3.15.

**FOUNDATIONS OF WIRELESS AND ELECTRONICS** by M. G. Scroggie. Price £2.00.

**TRANSISTORIZED RADIO CONTROL FOR MODELS** by D. W. Aldridge. Price £2.65.

**VIDEO RECORDING RECORD AND REPLAY SYSTEMS** by G. White. Price £3.40.

\*ALL PRICES INCLUDE POSTAGE\*


## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185  
Closed Saturday 1 p.m.


## SINCLAIR EQUIPMENT

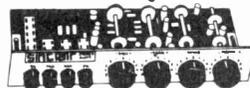

Project 60 FM Tuner	£15	(£1.70)
2 Z30/Stereo 60/PZ5	£16.75	(£2.05)
2 Z30/Stereo 60/PZ6	£18.85	(£2.25)
2 Z50/Stereo 60/PZ8/Trans	£23.20	(£2.70)
Z30 £3.50 (55p)	Stereo 60	£7.80 (98p)
Z50 £4.30 (63p)	Trans for PZ8	£2.95 (50p)
PZ5 £3.47 (57p)	2000 Amp	£22
PZ6 £6.30 (83p)	3000 Amp	£31.50 (£3.35)
AFU £4.40 (64p)	2000 Tuner	£27 (£2.90)
PZ8 £6.40 (84p)	3000 Tuner	£27 (£2.90)
Q16 £5.90 (79p)	Project 605	£20.98 (£2.40)

**PROJECT 60 KIT** £2.50 (36p)  
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuse-holder needed to complete Project 60.

**BATTERY ELIMINATOR BARGAIN**  
Introducing the most versatile battery eliminator ever offered, with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240V. Output voltage selected by front panel switch may be set to 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500 mA. Housed in a very strong, attractive, plastic case and fully guaranteed for 12 months.

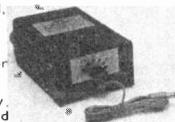

**IC RADIO CHIP TBA651** £2.10 (32p)  
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1.75 (29p).


**S-DECS AND T-DECS**

S-DECS £1.44 (25p)

T-DECS £2.88 (40p)


µ-DEC A £3 (41p)

16 di IC carriers £1.20 (17p)

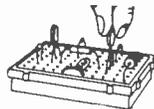

**SINCLAIR SUPER IC12** £2.10 (43p)

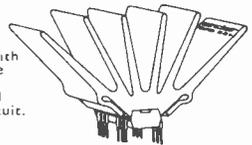Supplied complete with free 44-page instruction booklet and printed circuit.



**DELUXE KIT FOR THE IC12**  
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.45 (25p). Stereo model with balance control £3.30 (44p).

**BASIC KITS FOR THE IC12**  
Contains components for P.C. board and volume and simple tone controls. Mono version £1.25 (24p). Stereo model with balance control £2.90 (40p).


**IC12 POWER KIT**  
A set of components to construct a 28V 0.5A power supply £2.27 (45p).

**LOUDSPEAKERS FOR THE IC12**  
5in 8 ohm £1 (26p). 5in x 8in 8 ohm £1.45 (31p). 10in x 6in 15 ohm £2.20 (44p).

**PREAMPLIFIER KITS FOR THE IC12**  
Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1.20 (23p).

SEND S.A.E. FOR FREE LEAFLET ON KITS

**SINCLAIR EXECUTIVE CALCULATOR**

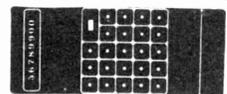

Now only £41 (£4.60)

## SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Mail order only. No callers, please.

## RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:—  
2 track record playback heads 50p each.  
2 track record playback heads 72p each.  
Erase heads are also available separately—2 track 35p—4 track 55p.  
MV metal mounting shields 39p each.  
2 track-heads already fixed on heavy mounting plate with shield £1-22.




## DRILL CONTROLLER NEW IKW MODEL

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-95. 13p post and p. Made up model also available. £2-95.
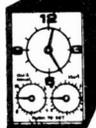
## MIGHTY MIDGET

Probably the finest possible radio, as described in *Practical Wireless*, January 73. All electronic parts £2-20 post paid.



## TIME SWITCH

Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bills, etc. £1-95.

## I CHIP RADIO

Ferranti's latest device ZN414 gives results better than superhet. Supplied complete with technical notes and circuits. £1-38 each. 10 for £11-11.

## HI-Q TUNER COMPONENTS

For experimenting with the ZN414.  
KIT No. 1. Plessey Miniature Tuning Condenser with built-in LW switch and 3in Ferrite slab and 1/2 inch wound MW coil, 72p.  
KIT No. 2. Air spaced tuning condenser 5in ferrite rod litz wound MW and LW coils, 94p.  
KIT No. 3. Air spaced TC with slow motion drive 8in ferrite rod, with litz wound LW and MW coils, £1-10.  
KIT No. 4. Permeability tuner with fast and slow motion drive and LW loading coils, 50p.

## ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1/2" 8p each, 10 for 82p.



## SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 1/2in rated 250V lamp. 8p each. 10 for 73p. Ditto as above but for printed circuit 6p each 10 for 63p.  
Sub Miniature Slide Switch, DPDT 10mm (1/4in approx.) between fixing centres. 20p each or 10 for £1-80. SP Change over spring return 250V 1 amp. 11p.

## MICRO SWITCH

5 amp changeover contacts, 11p each. 10 for 99p. 16 amp on/off. Model 15p each. Changeover 18p each.



## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5in casing with 5 1/2in fan blades. Kit comprises: motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2-75 + 20p P. & P.

## MAINS OPERATED SOLENOIDS



Model 772 — small but powerful 1in pull—approx. size 1 1/2 x 1 1/2 x 1 1/2in. 68p.  
Model 4001—1in. pull. Size 2 1/2 x 2 x 1 1/2in. 32p.  
Model 771—1 1/2in. pull. Size 3 x 2 1/2 x 2in. £1-98 plus 20p post and insurance.

## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable 6V, 9V, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1-10. Plus 20p postage.


## DESK TELEPHONES

Ex G.P.O. Black standard model with dialing dial but no internal bell. Supplied with connection diagram £1 each. Ditto, with bell but without dialing dial £1-25. Model as illustrated with bell and dial £1-50 each plus 50p post for single then 65p per pair.


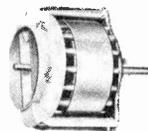
## PAPT MOTORS

Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. £1-65 each. Postage one 23p, two 33p, 23V model £3-30.



## 10 AMP DIMMER CONTROL

For the control of lighting on stage or in a studio or for control of portable equipment in workshops, etc. This has two 13 amp socket outlets each is controlled by a 5 amp solid state regulator. The overall length is 17in, width 3 1/2in and depth 1 1/2in. In the end is fitted a master On/Off switch indicator, lamp and fuse. Price £3-25.

## STANDARD WAFER SWITCHES

Standard size 1 1/2in wafer—silver-plated 5 amp contact, standard 1/2in spindle 2in long—with locking washer and nut.

No. of Poles	2way	3way	4way	5way	6way	8way	9way	10way	12way
1 pole	44p	44p	44p	44p	44p	44p	44p	44p	44p
2 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
3 poles	44p	44p	44p	44p	77p	77p	77p	£1-04	£1-04
4 poles	44p	44p	44p	77p	77p	77p	77p	£1-32	£1-32
5 poles	44p	44p	77p	77p	£1-04	£1-04	£1-04	£1-60	£1-60
6 poles	44p	77p	77p	£1-04	£1-04	£1-04	£1-04	£1-87	£1-87
7 poles	77p	77p	77p	£1-04	£1-32	£1-32	£1-32	£2-15	£2-15
8 poles	77p	77p	77p	£1-04	£1-32	£1-32	£1-32	£2-42	£2-42
9 poles	77p	77p	£1-04	£1-04	£1-60	£1-60	£1-60	£2-70	£2-70
10 poles	77p	77p	£1-04	£1-32	£1-60	£1-60	£1-60	£3-00	£3-00
11 poles	77p	£1-04	£1-04	£1-32	£1-87	£1-87	£1-87	£3-25	£3-25
12 poles	77p	£1-04	£1-04	£1-32	£1-87	£1-87	£1-87	£3-52	£3-52

## THE TWENTYLITE

Fluorescent lighting units with polycrystal choke and finished white enamel. 2ft. model, ideal kitchen, bedroom, hallway, porch, lift, etc., with tube. Assembled ready to install. Price £2-20 + 40p P. & P.



## MULLARD UNILEX

This D.I.Y. Stereo Amplifier is still available complete at £7-00 for the four Mullard Modules, or Modules can be bought separately as follows:—  
4 watt amplifier module (2 required) Mullard Ref. No. E.P.9000—£1-60. Pre amp module Mullard Ref. No. E.P.9001—£1-98 each.  
Power Module—Mullard Ref. No. E.P.9002—£2-53 each.  
In addition and made to Mullard specification we offer:—  
Standard Control Unit with escutcheon and knobs—£3-30.  
Knobs—Set of 4—50p.  
Special offer the complete Unilex with control panel at Pre VAT price £10-00 post paid.

## TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £2-85. 2kW Model as above except 2kW £2-75. Don't miss this. Control Switch 35p. P. & P. 40p.



## THIS MONTH'S SNIP

Room Thermostat made by the famous Smiths company. 15 amp at 250V. Elegant white and beige case, size 4 1/2in long by 1 1/2 square approx. Adjustment is by slider (lockable), adjusts through range 30°-90°F. Special Snip price £1-85.

## CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flows but virtually no noise. Approx. dimensions 10 1/2in wide x 1 1/2in dia. outlet into trunking 10 1/2 x 1 1/2in. £2-55 plus £1 post and insurance.



## TAPE PLAYBACK UNITS

Mains operated. Made by Redtune the famous "music in background people". These are complete units ready to work and we understand that they are in good going order. We have not tested them but would exchange any that do not work properly. These have a superior motor driven fly wheel to control the tape through the capstan and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Two models offered, good as new £2-50 and somewhat used at £2-50. 75p carriage up to 200 miles then 50p per 100 miles extra.



## 24-HOUR TIME SWITCH

Made by Smiths, these are A.C. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2-75 post and ins. 25p. Additional time contacts 55p pair.



## MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied.  
Model 1153 500mW power output 72p.  
Model 1172 750mW power output 94p.  
Model EP9000 4 watt power output £1-60.  
EP9001 twin channel or stereo per amp. £1-99.  
10% discount if 10 or more ordered.



TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6-00, otherwise add 20p.

## NEW ITEMS THIS MONTH

### MINIATURE SEALED RELAY

American made. Our Ref.: REL A1. Measures only 1/2in wide x 1/2in thick and 1/2in high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 28p including base.

### SUB-MINIATURE MICROSWITCH

Made by Burgess, their ref. V476 our ref. MS A1. These measure only 1/2in x 1/2in x 1/2in thick—have change over contacts and tag connection. Price 16p each or 10 for £1-44.

### 3 CORE MAINS FLEX

Metric size 0.5mm which is approx. equivalent to the old 14/36 rating. Suitable therefore for mower or similar portable tools. Cores are colour coded to the new European standard. Brown—live; Blue—neutral; Yellow/Green—earth. Grey P.V.C. covered overall. 100m coils £5. 50m coils £3 and 25m coils £1-75. Post 40p on 100m. 25p for 50m coils and 20p for 25m coils.

### PANIC SWITCHES

Tough enough to be foot switches and elegant enough to be panel switches. Bakelite construction with white push rod. Price 40p less quantity discounts. Switch is rated 250V-2 amp.



### 12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 µF smoothing. Price £2-20, plus 20p post and packing.

### 6 MAINS TRANSFORMERS

Our Ref.: MTM1 27 volt at 8 amp. Upright mounting fully shrouded—flying leads—fully tapped primary. Price £3-30.  
Our Ref.: MTM2 12v at 1 amp. Upright mounting with fixing lugs, tag connection. 240v primary—12v 1 amp secondary. Price 82p.  
Our Ref.: MTM3 6-3v 2 amp upright mounting with fixing lugs, tag connections. 240v primary 6-3v 2 amp secondary. Price 77p.  
Our Ref.: MTM4 18v-4 amp with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240v—secondary 18v at 4 amp. Price 88p.  
Mains Isolation MTM5 350 watts earth shielded—flex leads—upright mounting lugs for fixing. Price £4-40 each.

### 6 VOLT RELAYS


Our ref.: REL M1. Removable clear plastic enclosed two screw fixing. Have a 6 volt D.C. operated coil but two change-over contacts, each rated to make and break 240V A.C. at 15 amps. Price 66p each.

### P.O. TYPE 3000 RELAY

Our ref.: REL M2—100 ohms coil and 2 pair normally open heavy duty contacts. Price 75p each.
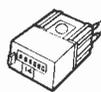
### 6 DIGIT COUNTER

Resettable. 440 ohm coil up to 25 impulses per second. Ex-equipment but guaranteed perfect. £2-20 each.



### COMBINATION SWITCH

This comprises of 12 miniature change-over micro switches. Joined in banks of 3 and mounted on frame with four digital numbered thumb wheels and a removable lever for locking the thumb wheel—the thumb wheel operates 3 banks. Over 4,000 combinations are possible but by re-wiring the switch connections underneath then thousands more variations are possible. If you are making equipment which you don't want switched on accidentally or without authority then this is a switch to consider—this can also be used as a coding switch for many other operations. Very neat and compact and measuring approx. 4in x 1 1/2in deep. Priced at £3-03.

### PUSH BUTTON SWITCH

Type 14 D.M.G. A very fine switch made by Honeywell. The switch is intended for mounting on panel through oblong hole. No screws required for fixing its sprung clips secure it quite firmly. The operating button is approx. 1in dia. round and disheal for ease of operation. Has 2 sets of 10 amp change-over contacts. Spring loaded, returns to normal when pressure is released. Ideal for instrument or quality gear. Price 50p each. 10 for £4-50, 100 for £40.

### PHOTO-MULTIPLIER TUBE

American R.C.A. type No. 4555. These tubes have a gain of a million or more. Regular Price—over £15. We have a limited quantity and offer these at £4-50.

## J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD  
Callers to 102/3 Tamworth Road, Croydon



## VARIABLE VOLTAGE TRANSFORMERS

**INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V**

All Types from 3 to 50 amp from stock.

### SHROUDED TYPE

1A £7. Post 50p 10A £22.50  
2.5A £8.05. Post 15A £25  
60p 20A £49  
5A £11.75. Post 37.5A £82  
75p 50A £98

CARRIAGE AND PACKING EXTRA unless shown (Panel Mounting)  
1 amp £7. Post 50p. 2½ amp £8.05. Post 60p.



2.5 amp OPEN TYPE


## L.T. TRANSFORMERS

All priorities 220-240V

Type No.	Sec. Taps	Price Post
1 30, 32, 34, 36V at 5A		£4.70 + 45p
2 30, 40, 50V at 5A		£6.90 + 60p
3 10, 17, 18V at 10A		£5.00 + 50p
4 6, 12V at 20A		£6.50 + 60p
5 17, 18, 20V at 20A		£7.30 + 60p
6 6, 12, 20V at 20A		£6.90 + 60p
7 24V at 10A		£5.30 + 50p
8 6, 6, 24 32V at 12A		£7.20 + 60p
9 6 and 12V at 10A		£3.80 + 40p

PARVALUX Type: SD1.

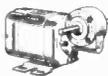5/86896/OJ  
230/250V A.C. 50 r.p.m. 7 lb/in.  
Continuously rated. Less base.  
£6. Post 30p incl. base.



PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of makers' price. £6.30. Post 70p.



PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £1.75. Post 35p.



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.



240V A.C. SOLENOID FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. In b.s.p. inlet/outlet. Precision made, British mfg. PRICE: £1.75. Post 25p. Special quotation for quantity. (New in makers' carton)



UNISELECTOR SWITCHES

NEW 4 Bank 25 Way, 24V d.c. operation. £6.90. Post 30p. 6 Bank 25 Way, 24V d.c. £7.90. Post 30p. 8 Bank 25 Way, 24V d.c. operation. £9.50. Post 40p.



GENERAL ELECTRIC POWER-GLAS TRIACS

10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV. £1. Post 5p. Type SC146E 10 amp, 500 PIV. £1.30. Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.

VOLTAGE CHANGING TRANSFORMER

M.f.g. to highest W.D. spec. Auto wound, and tapped 0-130-160-200-250 at least 2kVA. Can also be used as 230-240V input, 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30-40-50-70-90V at 10 amps. Weight 40lb, length, 260mm, height 190mm, width 230mm. In original maker's wooden case, £8. Carr. £1.

4 BANK 3c/o PUSH BUTTON ASSEMBLY

Black rectangular buttons. 5 units (min. order) 85p. Post 15p.



FOOT SWITCH

Suitable for Motors, Drills, etc. etc. 5 amp. 250 volt. Price 75p. Post 15p.



STROBE STROBE STROBE

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT

Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30. Post 30p.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. 1 output of Hy-Light. Price £10.50. Post 50p.

HY-LIGHT STROBE MK III

For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0.20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12. Post 50p.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

- Variable speed from 1-3 flash per sec.
- Reactor control circuit producing an intense white light. ONLY £20. Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Light Kit including reflector £4.75. Post 25p.

Super Hy-Light Kit including reflector £7. Post 60p.

7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 55p. Post 15p.

1 R.P.M. MOTOR


220/240 volt a.c., 1 r.p.m. synchronous motor. 2 watt. A/clock. Spindle 10mm long, 3mm dia. Motor only 20mm deep. Fixing centres 44mm. Price £1.10. Post 5p.

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Light or Super Hy-Light Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18. Post 50p. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

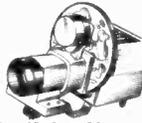Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p. 6 INCH COLOUR WHEEL As used for Disco lighting effects, etc. Price £5. Post 30p.



BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16. Post £1. Spare bulb £7. Post 40p.



BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt. Price £5.50. Post 30p. 2ft 20 watt, £4.25. Post 25p. (For use in stan. bi-pin fittings.) MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube, £1.70. Post 25p. (9in and 12in measures approx.)



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.25. Post 35p.

All prices are subject to 10% VAT. (10p in the £)

To all orders add 10% VAT to total value of goods including carriage/packaging.

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/2.5k ohm 95p. Post 10p.  
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm £1.35. Post 10p.  
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £1.95. Post 15p.  
Black Silver, Skirted knob calibrated in Nos. 1-9. 1½ in. dia. brass bush. Ideal for above Rheostats. 20p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1)	1	2	3	4
Coil ohms				
Col. (2)	52	4-6	6M	60p*
Working d.c. volts	150	6-12	4 c/o	80p*
	185	8-12	6M	60p*
	280	8-16	2 c/o	60p*
Col. 3	410	10-18	4 c/o	70p*
Contracts	600	9-18	2 c/o	60p*
	700	16-24	4M 2B	60p*
Col. (4)	700	16-24	4 c/o	80p*
Price	700	15-35	2 c/o HD	70p*
	700	16-24	6M	60p*
HD =	700	6-12	4 c/o HD	50p*
Heavy duty	700	20-30	6 c/o	80p*
	1,250	24-36	4 c/o	60p*
*Incl. Base	2,500	36-45	6M	60p*
All prices	2,400	30-48	4 c/o	50p*
incl. P. & P.	9,000	40-70	2 c/o	50p*
	15k	85-110	6M	50p*

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 5p.

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. Price: 55p. Post 5p. (100 lots) £40. 24 volt A.C. 3 c/o 55p. Post 5p.



MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 1½ high, 1½ wide, 1½ thick. Complete with 3in. leads. New 65p. Post 5p.



BLOWER UNIT

200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm. dia. x 60 mm. deep. Price £3. Post 30p.




230V FAN ASSEMBLY

Continuously rated, special sealed bearing, removable aluminium blades. Price 80p. Post 20p.



'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

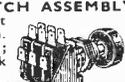Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob in. Fixing hole ½ in. ONE bank 30p; TWO bank 40p; THREE bank 50p. Quote for quantity.



VERY SPECIAL OFFER

Micro Switch. 5 amp c/o contacts. M.f.g. by Honeywell. NEW. Twenty for £1.50. Post 10p (min. 20).



'HONEYWELL' LEVER OPERATED MICROSWITCH

15 amps 250 volt A.C. c/o contacts. In maker's carton. PRICE: 10 for £1.90. Post 15p.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. Bin. W. 4in. H. 6in, weight 6lb. 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.



BALANCE/LEVEL METERS

100-0-100 Micro Amp. Size 1½ in + 1½ in. Price only 70p. Post 5p.



AMMETERS NEW! 2½ in. Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 5, 10, 20, both types \*£1.85. Post 15p. 0-300V A.C. £2. Post 15p.




All Mail Orders—Callers—Ample Parking  
Dept. PE10, 57 BRIDGMAN ROAD  
CHISWICK, LONDON W4 5BB  
Phone 01-995 1560  
Showroom open Mon.-Fri.

**SERVICE TRADING CO**

Personal callers only. Open Sat.  
9 LITTLE NEWPORT STREET  
LONDON WC2H 7JJ  
Phone 01-437 0576

# BI-PRE-PAK

## AUDIO BARGAINS

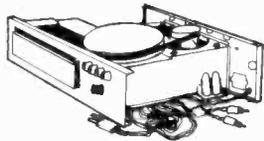

### 8 TRACK ONLY £11


incl. P. & P. and VAT

The latest **B.S.R. 8 Track** cartridge **Replay Deck**. Ready to install in your **Hi-Fi Stereo System**. This unit comes complete with **Hi Gain Stereo Pre-Amplifier**, **4-Programme Indicator Lamps**, **Track Selector Switch**, all leads and plugs, etc. for **230 volt A.C. mains** operation.

## 5W & 10W AMPS

**5W ONLY £1.98**  
**10W ONLY £2.49**

incl. P. & P. and VAT

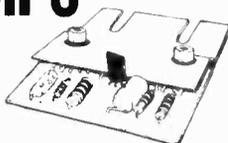

Specification:—

	5 Watt	10 Watt
Nominal Volts	12-14V	25-30V
In to 8 Ohms	5W	10W
In to 10 Ohms	2W	10W
In to 15 Ohms	1W	5W
Typical Distortion	0.5%	0.5%
Freq. response at 3dB	10Hz to 30KHZ	10Hz to 30KHZ
Sensitivity (Typically)	20mV	20mV
Full power consumption (30 Ohms)	650mA	580mA
Size	2 1/2 in x 1 1/2 in	2 1/2 in x 1 1/2 in

The **5W matchbox sized amplifier** will run satisfactorily from a **12V car battery**. Can also be used for portable voice reinforcement such as public functions where mains supply is not accessible. A small mains unit kit is available.

Two amplifiers are ideal for Stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit.

Discounts are available for quantity orders.

**Cheapest in the U.K. Built and tested**

## STEREO DECODER

### £4.95



incl. P. & P. and VAT

A ready built unit, ready for connection to the **I.F. stages** of your existing **FM Radio** or **Tuner**. A **tail-tale light** can be connected to show the presence of a **Stereo transmission** and correct operation.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a **L.E.D.** is used as the indicating light and a suitable device is available from us at **36p**. Supplied with all necessary instructions.

I enclose £..... for..... 8 Tracks/..... 5W Amps./..... 10W Amps./..... Decoders (Please insert quantities and delete those not applicable.)

Name .....


Address .....

**BI-PRE-PAK**  
Co. Regn. No. 820919

Dept. A, 222 224 West Road  
Westcliff-on-Sea, Essex SS0 9DF  
Tel.: Southend (0702) 46344
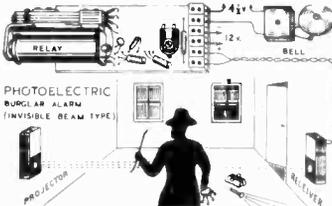
## PHOTOELECTRIC KIT

CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



**PHOTOELECTRIC KIT**  
**£2-85**

Postage and Pack. 16p (U.K.)

Commonwealth

**SURFACE MAIL 25p**

**AIR MAIL £1-40**

Australia, New Zealand,

S. Africa, Canada and U.S.A.

Also Essential Data Circuits

and Plans for Building

10 Advanced Designs

### INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price **£1-45**. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p

### LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price **£2-10**. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1-15

### BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.

CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C.s, Electrodes, Leads, Chassis Case, Batteries, Plans and Instructions. Price **£4-75** postage and pack. 25p (U.K.). Commonwealth: Surface 30p, Air Mail £1.

### ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT

Tunable Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.

CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis Case, Earphone, Battery, Plans and Instructions. Price **£3-25**, postage and pack. 15p (U.K.). Commonwealth: Surface 25p, Air Mail 75p.

**YORK ELECTRICS** Mail Order Dept.

**335 BATTERSEA PARK ROAD, LONDON, S.W.11**

Send S.A.E. for full details, a brief description of all Kits and Projects



## become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RAPY

**free!**

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**  
P.O. BOX 156, JERSEY

NAME: .....

ADDRESS: ..... EB103

BLOCK CAPS please

# TRANNIES

1 DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX  
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

ALL PRICES INCLUDE VAT

## £22.50 ELECTRONIC DIGITAL CLOCK

(For complete kit of parts including case.)



This 4 digit 24 hour clock is available to readers at this special price. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case. P.C. Board.

## Integrated Circuits

74 series T.T.L. I.C.'s (Prices inclusive of VAT)

1-24 25-99			100 plus				
SN7400	17p	16p	14p	SN7450	17p	16p	14p
SN7401	17p	16p	14p	SN7451	17p	16p	14p
SN7402	17p	16p	14p	SN7453	17p	16p	14p
SN7403	17p	16p	14p	SN7454	17p	16p	14p
SN7404	17p	16p	14p	SN7460	17p	16p	14p
SN7405	17p	16p	14p	SN7470	33p	29p	28p
SN7406	39p	35p	31p	SN7472	39p	35p	28p
SN7407	39p	35p	31p	SN7473	41p	40p	35p
SN7408	20p	19p	16p	SN7474	41p	40p	35p
SN7409	20p	19p	16p	SN7475	50p	43p	43p
SN7410	17p	16p	14p	SN7476	44p	44p	39p
SN7411	20p	19p	16p	SN7480	73p	72p	64p
SN7412	39p	34p	31p	SN7481	£1.32	£1.27	£1.17
SN7413	32p	29p	24p	SN7482	96p	94p	88p
SN7416	48p	44p	40p	SN7483	£1.21	£1.17	£1.07
SN7417	48p	44p	40p	SN7484	£1.10	£1.05	88p
SN7420	17p	16p	14p	SN7485	£3.96	£3.85	£3.65
SN7422	55p	53p	48p	SN7486	36p	34p	30p
SN7423	55p	53p	48p	SN7489	£5.50	£5.00	£4.75
SN7425	48p	45p	42p	SN7490	41p	37p	48p
SN7427	51p	48p	42p	SN7491	£1.10	£1.05	£1.00
SN7428	77p	72p	65p	SN7492	74p	70p	64p
SN7430	17p	16p	14p	SN7493	74p	70p	64p
SN7432	40p	35p	30p	SN7494	85p	82p	75p
SN7433	94p	83p	75p	SN7495	85p	82p	75p
SN7437	70p	62p	58p	SN7496	96p	93p	98p
SN7438	71p	68p	62p	SN74100	£1.57	£1.78	£1.66
SN7440	17p	16p	14p	SN74104	£1.07	£1.04	94p
SN7441	73p	71p	65p	SN74105	£1.07	£1.04	94p
SN7442	73p	71p	65p	SN74107	44p	42p	38p
SN7443	£1.33	£1.37	£1.27	SN74110	61p	58p	51p
SN7444	£1.43	£1.37	£1.27	SN74111	£1.37	£1.27	£1.15
SN7445	£1.98	£1.97	£1.84	SN74118	£1.10	£1.05	85p
SN7446	£1.10	£1.03	84p	SN74119	£1.48	£1.37	£1.37
SN7447	£1.10	96p	85p	SN74121	44p	41p	35p
SN7448	£1.10	£1.07	97p	SN74122	£1.54	£1.43	£1.23



## Electrolytic Capacitors

general purpose

4 VOLT		2,200µF		25p	
7µF	7p	4,700µF	39p	40 VOLT	7p
100µF	7p	10,000µF	34p	6.8µF	7p
220µF	7p	16 VOLT		15µF	7p
330µF	7p	15µF	7p	33µF	7p
1,000µF	15p	33µF	7p	100µF	7p
4,700µF	29p	68µF	7p	150µF	10p
6.8 VOLT		150µF	8p	200µF	11p
33µF	7p	220µF	8p	470µF	19p
68µF	7p	680µF	17p	680µF	26p
150µF	7p	1,000µF	19p	1,000µF	26p
470µF	11p	1,500µF	28p	2,200µF	44p
1,000µF	15p	2,200µF	35p	3,300µF	63p
1,500µF	20p	3,300µF	38p	63 VOLT	
2,200µF	22p	6,800µF	63p	1µF	7p
25 VOLT		25 VOLT		2.2µF	7p
10µF	7p	10µF	7p	4.7µF	7p
22µF	7p	22µF	7p	6.8µF	7p
33µF	7p	33µF	7p	10µF	7p
47µF	7p	47µF	7p	22µF	7p
68µF	7p	68µF	7p	33µF	7p
100µF	7p	100µF	7p	47µF	7p
220µF	8p	1,000µF	22p	68µF	7p
330µF	8p	2,200µF	40p	100µF	10p
470µF	10p	3,300µF	48p	150µF	14p
1,000µF	14p	4,700µF	68p	200µF	19p
1,500µF	20p			330µF	22p
				470µF	27p
				1,000µF	44p
				1,500µF	63p

## MISC.

- Crocodile Clips 5p
- Battery Clips 6p
- PP3 8p
- PP9 8p
- Fuse Holders
- Chassis mounting
- 20mm No. 5210 7p
- 1.25in Single 7p
- 1.25in Double 9p
- Connecting Wire Packet 5 x 5yd colls. 20p
- Mixed 20p
- Heat Sinks
- TO5 6p
- TO18 6p
- TO66 15p
- TO65 15p
- Pointer Knobs 12p
- DIN Connectors
- 2-way Loudspeaker type
- Plug 13p
- 3-way plug 11p
- 3-way socket 11p
- 4-way plug 15p
- 4-way socket 13p
- 5-way plug 16p
- 5-way socket 13p

## Linear Integrated Circuits

301 DIL	50p	307 8 PIN DIL	66p	741c 14 PIN DIL	89p
301 TO99	55p	308 TO99	£6.45	741c DIL	46p
301 8 PIN DIL	46p	308A TO99	£6.40	748c DIL	39p
301A DIL	69p	709c DIL	35p	748c TO99	41p
301A TO99	69p	709 TO99	148c	DIL	£1.27
301A 8 PIN DIL	66p	723c DIL	99p	TO99	£1.27
307 DIL	69p	723c TO99	95p	84p	84p
307 TO99	69p	741c 8 PIN DIL	38p	7303 DIL	£1.27



## Transistors Diodes

AC107	18p	OC35	45p
AC126	14p	OC36	45p
AC127	14p	OC44	10p
AC128	14p	OC45	10p
AC176	15p	OC71	9p
AC187	14p	OC83	14p
AC188	14p	TIP41A	85p
AD149	45p	TIP42A	96p
AD161	31p	2N2926	10p
AD162	31p	2N3053	26p
AF116	14p	2N3054	58p
AF117	14p	2N3055	52p
AL102	66p	2N3702	12p
BC107	9p	2N3704	12p
BC108	9p	2N3819	28p
BC109	10p	40636	75p
BC169	11p	Diodes	
BC182	12p	IN914	8p
BC183	12p	IN341A	8p
BC184	12p	OA90	8p
BC212	12p	OA91	8p
BC214	12p		
BD131	88p	This is only a	
BD132	90p	small selection,	
MP811	35p	many other	
MP812	40p	types stocked	
MP813	42p	at competitive	
OC28	45p	prices.	

## Transformers

Primary 210-240 volt	Price
Sec. Amps	Type inclusive
No.	P. & P.
12V 500mA	MT111 £1.12
12V 1A	MT123 £1.25
24V 250mA	MT111CS £1.12
24V 500mA	MT219CT £1.25
12V 2A	MT11AT £1.89
24V 1A	MT79 £2.01
30V 1A	MT9 £2.01
30V 2A	MT3 £3.28
50V 1A	MT103 £2.54
50V 2A	MT104 £3.75
50V 4A	MT106AT £6.00
60V 1A	MT126 £2.81
60V 2A	MT127 £3.98

Many other types stocked in our latest price list.

## Low Cost Panel Meters (1/4" scale)

M34	0-500 Ma	£1.90
M35	0 to 10 Ma	£1.90
M36	0 to 10 Ma	£1.90
M36	0 to 100 Ma	£1.90

## MULLARD POLYESTERS

**MULLARD POLYESTER CAPACITORS C330 SERIES**  
250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1,000µF, 1,500µF, 2,200µF, 3,300µF, 4,700µF, 6,800µF, 10,000µF.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1,000µF, 1,500µF, 2,200µF, 3,300µF, 4,700µF, 6,800µF, 10,000µF.

## VOLUME CONTROLS

Potentiometers  
Carbon track 500 Ω to 2.2M Ω  
Log or Linear  
Single 13p. Dual gang (stereo) 44p  
Single type with D.P. switch 13p extra.

- LOW SWITCHES
- Slide Switches 6p
- SPST 10p
- DPDT 10p
- Toggle Switches 16p
- SPST 22p
- DPDT 22p

## CARBON SKELETON PRESETS

Small high quality type (linear only).  
All valves 100-5 meg ohms.  
0.1 watt 5p each  
2.5 watt 6p each

## MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals (Data Sheet on request)  
ONLY £1.80  
15 D.I.L. Socket 33p  
Driven by 7447 98p

## RECTIFIERS

P.I.V.	1 AMP	1.5 AMP
50	IN4001 44p	PL4001 8p
100	IN4002 44p	PL4002 8p
200	IN4003 51p	PL4003 10p
400	IN4004 61p	PL4004 10p
600	IN4005 8p	PL4005 13p
800	IN4006 9p	PL4006 15p
1,000	IN4007 10p	PL4007 20p

## ZENER DIODES

400mW BZ788 range  
3.33-33V  
1 watt 6.8-200V 10p each  
19p each

## THYRISTORS

FLY	50	100	200	300	400
1 Amp	28	25	41	44	58
3 Amps	41	50	60	—	66
7 Amps	—	96	1.01	—	1.24

## RESISTORS

1 watt 5%, carbon 1p each  
1 watt 10%, carbon 1p each  
1 watt 10%, carbon 2p each  
Range 10 ohms to 4.7 meg.  
1/2 watt m/o 2% 3p each  
Range 10-1 meg ohms

## AMTRON KITS

We are now stockists of Amtron High Quality Kits.

- UK45 Intermittent Warning Lights £5.00
  - UK220 Signal Injector £2.57
  - UH515 MW Radio Receiver £7.86
  - UK525 VHF Tuner 120/160 MHz £12.40
  - UK875 Capacitive Discharge Electronic Ignition for Internal Combustion Engine £14.51
- Post and Packing 25p

# Sinclair Project 60

## New performance standards ... new safety margins

Such are the results of using a PZ8 Mk 3 to drive two Z.50 Mk 2 power amplifiers. Developed from the original Z 50, the Mk 2 has improved thermal stability, better regulated D.C. limiting to ensure more symmetrical output voltage swing with still less distortion at lower outputs and automatic transient overload protection. The PZ.8 Mk.3 is the most advanced power supply unit ever to be made at a reasonable price. It cannot be damaged by direct shorting, nor will it fail through overloading, because of an ingenious re-entrant current limiting principle used usually only in expensive laboratory equipment. Because output voltage is variable, the PZ8 Mk 3 makes a worthwhile alternative where PZ.5 and PZ.6 are recommended for Project 60 applications, particularly since this most powerful of all Sinclair supply units can be operated from a smaller mains transformer. Together, the Z 50 Mk 2 and PZ8 Mk 3 provide new standards of performance and reliability and these modules are compatible with earlier types in the Project 60 range.

### Z.50 Mk.2 SPECIFICATIONS

Input impedance 100 K $\Omega$   
 Input (for 30W into 8 $\Omega$ ) 400mV  
 Signal to noise ratio, referred to full o/p at 30V HT 80dB or better  
 Distortion 0.02% up to 20W at 8 $\Omega$   
 See published curve  
 Frequency response 10Hz to more than 200 KHz - 1dB  
 Max. supply voltage 45v (4 $\Omega$  to 8 $\Omega$  speakers) (50v 15 $\Omega$  speakers only)

Min. supply voltage 9v  
 Load impedance - minimum: 4 $\Omega$  at 45v HT  
 Load impedance - maximum: safe on open circuit

£5.48 + V.A.T.  
 54p

PZ.8 Mk.3 SPECIFICATIONS  
 Nominal working output 45V.  
 Adjustable between 20 & 50V

£7.98 + V.A.T.  
 79p

Mains Transformer £5.98 + V.A.T. 59p

### Other power supplies

In addition to the remarkable Sinclair PZ 8 Mk.III as described, there are two other power units available, which should be chosen according to their types in order to buy to best advantage. All are for operation from A.C. mains 240V.

PZ.5 30 volt, un stabilised  
 £4.98 + V.A.T. 49p

PZ.6 35 volt, stabilised (Not suitable for Super IC 12).  
 £7.98 + V.A.T. 79p


### Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.


Each Project 60 module is tested before leaving our factory and guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you. A small charge may be made in those cases where damage arises through mis-use. No charge is made for postage by surface mail. Air Mail charged at cost.
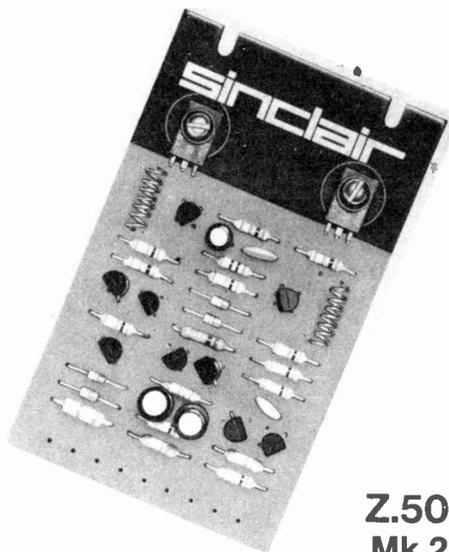
# sinclair

SINCLAIR RADIONICS LTD., LONDON RD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ Telephone: St. Ives (0480) 64311 Telex: 32250 Reg. No. 699483 England



Z.50  
Mk 2

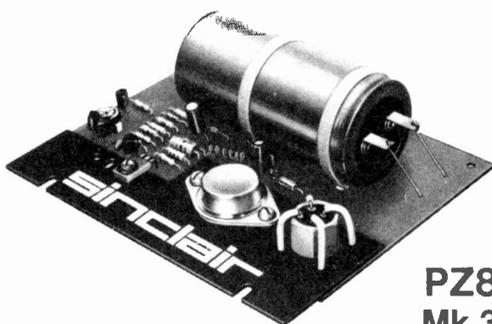

PZ8  
Mk 3

## Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.50	Crystal P.U., 12V battery volume control, etc.	£5.48 + V.A.T. 54p
Mains powered record player	Z.50, PZ.5	Crystal or ceramic P.U. volume control, etc.	£10.46 + V.A.T. £1.04
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.50, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£25.92 + V.A.T. £2.59
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.50, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£28.92 + V.A.T. £2.89
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50 Mk.2, Stereo 60; PZ.8 Mk.3 transformer	As above	£34.90 + V.A.T. £3.49
Indoor P.A.	Z.50 Mk.2, PZ.8 Mk.3 transformer	Mic., guitar, speakers, etc., controls	£19.44 + V.A.T. £1.94

A.F.U. (£5.98 + V.A.T. 59p) may be added as required.

# the world's most advanced high fidelity modules

## Q.16 high fidelity loudspeaker

The Q 16 employs original and by now well proven acoustic principles in which a special driver assembly is meticulously matched to a uniquely designed cabinet. In performance it comfortably stands comparison with very much more expensive loudspeakers. A solid teak surround is used with a special all-over cellular black foam front chosen both for its appearance and ability to pass all audio frequencies without masking.


### Specifications

**Construction:** A sealed seamless sound or pressure chamber is used with internal baffle, and special high flux driver

**Loading:** Up to 14 watts RMS, into 8 ohms

**Frequency response:** From 60 to 16,000 Hz

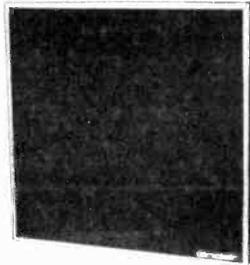**Size and styling:** 248 mm square x 120 mm deep (9 $\frac{7}{8}$  x 4 $\frac{3}{4}$ ) with neat pedestal base.



£7.70 + V.A.T.  
77p



## Stereo 60 pre-amp/control unit

Designed specifically for Project 60 systems, the Stereo 60 is equally suitable with any high quality power amplifier. Silicon epitaxial planar transistors used throughout ensure high signal-to-noise ratio and excellent tracking between channels. Input selection is by press buttons, with accurate equalisation on all input channels. The unit is easy to mount.

**SPECIFICATIONS—Input sensitivities:** Radio — up to 3mV, Mag. p.u. 3mV, correct to R.I.A.A. curve  $\pm 1$ dB. 20 to 25,000Hz. Ceramic p.u., — up to 3mV. Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz; BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed.

£9.98 + V.A.T.  
99p

## AFU filter unit

For use between Stereo 60 and two Z 30's or Z 50's in stereo formation. Cut-off frequencies are continuously variable, with 12dB/octave cut in the rejection band. Two stages of filtering — rumble (high pass) and scratch (low pass). Amplitude and phase distortion are negligible. Supply voltage needed — 15–35V. H.F. cut-off (-3dB) 28KHz to 5KHz; L.F. (-3dB) 25Hz to 100Hz. For Project 60 or any good stereo system.


Built, tested and guaranteed

£5.98

+ V.A.T. 59p


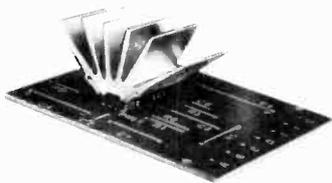
## Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, which was the first time an IC had ever been made available for such purposes, we followed it with an even more efficient version, the Super IC.12. This needs very few external resistors and capacitors to make an exceedingly efficient high fidelity amplifier for pick-up, F.M. radio or small P.A. set up etc. The free 40 page manual supplied details many other applications which this remarkable IC make possible. The Super IC.12 is the equivalent of a 22 transistor circuit

contained within a 16 lead DIL package, and the finned heat sink is sufficient for all likely requirements. The Super IC.12 is also compatible with those Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

### SPECIFICATIONS

**Output power:** 6 watts RMS continuous (12 watts peak) into 6–8  $\Omega$ . **Frequency Response:** 5Hz to 100KHz  $\pm 1$ dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free

With FREE printed circuit board and 40 page manual.

£2.98 + V.A.T. 29p  
Post free

## Project 605



## the simple way to build a Project 60 system without soldering

For the many audio enthusiasts anxious to build to high standards without too many involvements, there could be nothing better or simpler than Project 605. It offers the advantages of Project 60 and is absolutely complete down to the last piece of wire cut to length. Whilst not as powerful as assemblies using Z.50 power amplifiers, we know from experience that there are many for whom the specifications of Project 605 are ideal, particularly in relation to the environment in which it is required to be used. In Project 605 you have everything necessary to build a versatile Project 60 thirty watt high fidelity amplifier system suitable for all domestic requirements. The convenient pack includes two Z.30 power amplifiers, a Stereo 60 pre-amp control unit and the special Masterlink unit to and from which all input and output connections are made. For power a PZ.5 is provided. Building is particularly easy since all necessary leads are supplied colour coded, cut to length and terminated by contact clips which connect firmly to the modules. There is absolutely no soldering to be done. Complete with comprehensive, easy to follow instructions manual.

£29.95 + V.A.T. £2.99  
Post free

## Send coupon for leaflet

Please send leaflet and name and address of my nearest Sinclair stockist

Name \_\_\_\_\_

Address \_\_\_\_\_

SINCLAIR RADIONICS LTD., LONDON ROAD,  
ST. IVES, HUNTINGDON PE17 4HJ

PE1

# sinclair

ALL PRICES QUOTED IN THIS ADVERTISEMENT ARE THE RECOMMENDED RETAIL PRICES.

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

## COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY  
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY  
(WE CLOSE ALL DAY THURSDAY)  
13 SOUTH MALL, EDMONTON N.9 803 1685

### "CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses.

This budget system compares very favourably with the more sophisticated and much higher priced models. Specification: Projector 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel, 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15; 6in Liquid Wheel, £5—£20 + 75p carr.



### TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7.5 or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips cassette £3 plus 10p P. & P.



### DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £22.50 + 50p P. & P. Please send S.A.E. if you require more information.

### "CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD.IT

We supply the three modules for you to build this Disco Group-P.A. amplifier into the cabinet of your choice.

- ★ THE POWER AMP MODULE TP100W 170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). £14.28, carr. 45p.
- ★ THE PRE-AMP MODULE Four control pre-amp, Vol., Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £3.96, carr. 25p.
- ★ THE POWER SUPPLY MODULE PS100

V.A.T. From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

200/250V MAINS RELAY Heavy duty contacts. 2,500 coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.



### TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3 1/2in. x 1 1/2in. This converter supplies 6, 7.5 or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.


### STEREO/MONO HEADPHONE VOLUME CONTROL BOX

Plug stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/mono switch. Complete with stereo jack plug and 2m cable. A bargain at £1. P. & P. 10p.


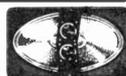
### TWO WAY STEREO ADAPTOR

Stereo Jack plug to two stereo free sockets, complete with 110mm cable. For connecting two stereo inputs into one. A bargain at 65p, plus 5p P. & P.



### MINI LOUDSPEAKERS

2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P. & P. on each L.S.



### CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 28p, C90 38p, C120 48p plus 5p P. & P.



### PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 600W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P.



If you require more information please send S.A.E.



### "CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

### LOW VOLTAGE AMPLIFIER


5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high I.M.P. input this amplifier will work as a record player, baby alarm, etc., amplifier.



£1.75 plus 13p P. & P.
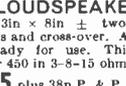
### EMI LOUDSPEAKER 450

10W 13in x 8in ± two 2-2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. £3.75 plus 38p P. & P. each.



### 7in x 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.



# KEEP WARM AT A COOL PRICE.

## Slash central heating costs with AMKIT.

If you can put in electric wiring, you can install Amkit. The unique nylon pipe hot water central heating system, that you install yourself in hours.

Look at these advantages:

- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To Autocon Manufacturing Co.

Spring House, 10, Spring Place, London, NW5, 3BH  
Please send your brochure telling me all about Amkit.

Name .....

Address .....



or see for yourself at: THE AMKIT D.I.Y. CENTRE,  
15, Procter St., London, W.C.1. (opp Holborn Underground).  
Open Mon-Fri 9.30 am-5.30 pm. Sat 9 am-1 p.m.

## FIBRE OPTIC

High quality glass Fibre Optic cable manufactured by a World famous W. German optical group. Ideal for all light transmission applications and experiments (450-1,300 nm) light monitoring - opto-electronic system - short distance communication systems etc.

**Type LKF 450.** 450 glass fibres, 40 micron diameter held within a tough, highly flexible P.V.C. sheathing. O.d. 2.3 mm. 17p per metre (39") plus P & P 5p.

**Type LKF 800.** 800 glass fibres, 70 micron diameter held within a tough, flexible P.V.C. sheathing. O.d. 4.0 mm. £1.75 per metre (39") plus P & P 10p.

**End Ferrules.** Specially produced brass ferrules for these cables. LKF 450 10p for 10 LKF 800 20p for 10. No P & P when purchased with either type of Fibre Optic cable.

Cheques or Postal Orders to:

H.V. SKAN LIMITED,  
425/433 Stratford Road, Shirley,  
Solithull, Warwickshire, B90 4AE.  
Tel. 021-744 6791.

# BRAND NEW SEMICONDUCTORS AND COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

## TRANSISTORS

2G301	0-15	2N3414	0-10	40360	0-46	BC125	0-15	BDV20	1-05	BSV26	0-20
2G302	0-15	2N3415	0-10	40361	0-43	BC126	0-20	BDV38	0-65	BSV27	0-15
2G303	0-25	2N3416	0-15	40362	0-45	BC127	0-30	BDY60	0-90	BSV28	0-15
2G306	0-30	2N3417	0-21	40363	0-61	BC128	0-11	BDY61	1-25	BSV29	0-20
2G309	0-25	2N3370	1-25	40389	0-46	BC137	0-15	BF117	0-43	BSV30	0-25
2G345B	0-25	2N3371	1-12	40394	0-38	BC138	0-15	BF119	0-25	BSV35	0-25
2G371	0-15	2N3572	0-97	40395	0-65	BC140	0-84	BF121	0-25	BSV54	0-20
2G374	0-15	2N3702	0-11	40406	0-44	BC141	0-39	BF123	0-27	BSV56	0-15
2N174	1-40	2N3703	0-10	40407	0-83	BC142	0-24	BF125	0-25	BSV65	0-20
2N404	0-43	2N3704	0-14	40408	0-50	BC143	0-21	BF152	0-20	BSV78	0-40
2N456	0-75	2N3705	0-10	40409	0-52	BC144	0-24	BF153	0-29	BSV79	0-40
2N456A	0-75	2N3706	0-09	40419	0-55	BC145	0-21	BF154	0-16	BSV95A	0-09
2N457A	0-80	2N3707	0-13	40411	0-25	BC147	0-12	BF158	0-28	C111	0-53
2N481	3-25	2N3708	0-07	40414	3-55	BC149	0-12	BF159	0-27	D40N3	0-55
2N696	1-18	2N3709	0-09	40474A	0-69	BC149	0-12	BF160	0-23	GET111	0-45
2N697	1-21	2N3710	0-12	40468A	0-44	BC165	0-18	BF161	0-42	GET114	0-20
2N698	0-25	2N3711	0-09	40600	0-69	BC154	0-18	BF163	0-20	GET115	0-60
2N699	0-52	2N3712	0-08	40601	0-67	BC157	0-14	BF166	0-35	GET119	0-35
2N706	0-18	2N3713	1-05	40602	0-46	BC158	0-14	BF167	0-21	GET255	0-20
2N708	0-18	2N3714	2-29	40603	0-58	BC169	0-18	BF173	0-24	GET286	0-20
2N709	0-38	2N3715	1-23	40604	0-52	BC170	0-17	BF177	0-29	GET288	0-20
2N711	0-30	2N3716	3-00	40636	1-10	BC187B	0-11	BF178	0-35	GET289	0-20
2N718	0-21	2N3773	3-96	40673	0-70	BC188B	0-13	BF179	0-43	GET287	0-20
2N720	0-50	2N3779	3-15	AC107	0-35	BC188C	0-11	BF180	0-35	TIP29A	0-49
2N721	0-55	2N3790	4-01	AC113	0-18	BC189B	0-13	BF181	0-35	TIP30A	0-58
2N914	0-22	2N3794	2-28	AC115	0-20	BC190C	0-11	BF182	0-40	TIP31A	0-62
2N916	0-41	2N3791	2-06	AC121	0-13	BC171	0-15	BF183	0-17	TIP32A	0-74
2N918	1-50	2N3794	0-10	AC126	0-25	BC172	0-11	BF185	0-17	TIP33A	1-01
2N929	2-14	2N3819	0-32	AC127	0-20	BC182	0-10	BF194	0-14	TIP35A	2-90
2N930	0-48	2N3820	0-47	AC128	0-30	BC182L	0-12	BF195	0-17	TIP36A	3-70
2N1090	0-25	2N3820	0-47	AC141K	0-20	BC183	0-09	BF196	0-15	TIP41A	4-70
2N1091	0-24	2N3823	1-42	AC142K	0-25	BC183L	0-09	BF197	0-15	TIP42A	0-90
2N1131	2-82	2N3824	1-33	AC151V	0-14	BC184	0-11	BF198	0-15	TIP2955	0-88
2N1132	0-83	2N3826	0-23	AC152V	0-17	BC184L	0-11	BF199	0-18	TIP3055	0-60
2N1302	0-16	2N3854	0-18	AC153	0-22	BC186	0-25	BF200	0-40	ME0402	0-20
2N1303	0-16	2N3854A	0-19	AC153K	0-25	BC207	0-12	BF225J	0-19	ME0404	0-13
2N1304	0-20	2N3855	0-19	AC154	0-34	BC208	0-11	BF237	0-22	ME0411	0-17
2N1305	0-20	2N3856	0-20	AC176	0-18	BC208	0-11	BF237	0-22	ME0412	0-18
2N1306	0-22	2N3856	0-19	AC187K	0-20	BC212K	0-10	BF238	0-22	ME0413	0-14
2N1307	0-22	2N3856A	0-20	AC188K	0-28	BC212L	0-18	BF244	0-16	ME1013	0-18
2N1308	0-25	2N3858	0-17	AC188K	0-28	BC214L	0-23	BF245	0-16	ME1200	0-25
2N1309	0-25	2N3858A	0-19	ACY17	0-35	BC247	0-09	BF246	0-43	ME1201	0-25
2N1483	0-24	2N3859	0-16	ACY18	0-24	BC238	0-06	BF247	0-49	ME4002	0-11
2N1507	0-20	2N3859A	0-18	ACY19	0-27	BC239	0-09	BF248	0-16	ME4003	0-14
2N1613	0-35	2N3860	0-20	ACY20	0-22	BC251	0-20	BF255	0-17	ME4101	0-10
2N1631	0-35	2N3866	1-69	ACY21	0-28	BC253	0-23	BF257	0-47	ME4102	0-11
2N1637	0-36	2N3877	0-25	ACY22	0-18	BC257	0-09	BF258	0-58	ME4103	0-10
2N1638	0-32	2N3877A	0-26	ACY28	0-20	BC258	0-09	BF259	0-45	ME4104	0-11
2N1701	1-10	2N3900	0-20	ACY30	0-42	BC259	0-13	BF272	0-43	ME6102	0-18
2N1702	2-15	2N3900A	0-21	ACY30	0-45	BC261	0-20	BF273	0-25	ME8002	0-17
2N1711	0-45	2N3901	0-32	ACY39	0-17	BC262	0-18	BF274	0-23	ME8003	0-16
2N1893	0-81	2N3903	0-24	ACY41	0-17	BC263	0-28	BF457	0-63	MJ400	0-78
2N2102	0-30	2N3904	0-27	ACY44	0-31	BC300	0-42	BF458	0-65	MJ420	0-88
2N2147	0-70	2N3905	0-24	AD136V	0-96	BC301	0-34	BF821A	0-27	MJ421	0-88
2N2148	0-94	2N3906	0-27	AD140	0-55	BC302	0-34	BF822	0-27	MJ429	0-76
2N2192	0-40	2N4036	0-46	AD142	0-50	BC307	0-54	BF898	0-28	MJ480	0-75
2N2192A	1-21	2N4037	0-40	AD143	0-45	BC303	0-54	BF910	0-61	MJ481	0-85
2N2193	0-40	2N4058	0-18	AD149V	0-86	BC308	0-09	BF911	0-61	MJ490	0-94
2N2193A	0-61	2N4059	0-21	AD144K	0-81	BC308	0-09	BF912	0-61	MJ491	1-10
2N2194	0-73	2N4060	0-11	AD181	0-45	BC307A	0-10	BF913	0-61	MJ492	1-12
2N2194A	0-30	2N4061	0-11	AD182	0-45	BC308A	0-09	BF914	0-61	MJ493	1-12
2N2195	0-37	2N4062	0-11	AD161	1-05	BC309B	0-10	BF915	0-61	MJ494	1-12
2N2195A	0-18	2N4302	0-25	AD162	1-05	BC309A	0-10	BF916	0-61	MJ495	1-12
2N2218A	0-86	2N4303	0-27	AF109R	0-40	BC309B	0-10	BF917	0-61	MJ496	1-12
2N2219	0-57	2N4304	0-47	AF110	0-25	BC309B	0-10	BF918	0-61	MJ497	1-12
2N2219A	0-86	2N4305	0-47	AF111	0-25	BC309B	0-10	BF919	0-61	MJ498	1-12
2N2220	0-45	2N4306	0-47	AF112	0-25	BC309B	0-10	BF920	0-61	MJ499	1-12
2N2221	0-41	2N4307	0-18	AF113	0-20	BC309B	0-10	BF921	0-61	MJ500	2-92
2N2221A	0-83	2N4308	0-18	AF114	0-20	BC309B	0-10	BF922	0-61	MJ501	2-92
2N2222	0-60	2N4309	0-99	AF115	0-50	BC309B	0-10	BF923	0-61	MJ502	2-92
2N2222A	0-81	2N4310	0-73	AF116	0-25	BC309B	0-10	BF924	0-61	MJ503	2-92
2N2268	0-21	2N4322	0-84	AF117	0-25	BC309B	0-10	BF925	0-61	MJ504	2-92
2N2299A	0-37	2N4323	0-83	AF118	0-25	BC309B	0-10	BF926	0-61	MJ505	2-92
2N2369A	0-41	2N4324	0-84	AF119	0-25	BC309B	0-10	BF927	0-61	MJ506	2-92
2N2466	0-77	2N4325	0-84	AF120	0-25	BC309B	0-10	BF928	0-61	MJ507	2-92
2N2647	1-20	2N4326	0-12	AF121	0-20	BC309B	0-10	BF929	0-61	MJ508	2-92
2N2711	0-30	2N4327	0-12	AF122	0-20	BC309B	0-10	BF930	0-61	MJ509	2-92
2N2712	0-12	2N4328	0-12	AF123	0-20	BC309B	0-10	BF931	0-61	MJ510	2-92
2N2713	0-17	2N4329	0-12	AF124	0-20	BC309B	0-10	BF932	0-61	MJ511	2-92
2N2714	0-18	2N4330	0-12	AF125	0-20	BC309B	0-10	BF933	0-61	MJ512	2-92
2N2904	0-56	2N4331	1-01	AF126	0-20	BC309B	0-10	BF934	0-61	MJ513	2-92
2N2904A	0-70	2N4332	1-10	AF127	0-20	BC309B	0-10	BF935	0-61	MJ514	2-92
2N2905	0-71	2N4333	1-10	AF128	0-20	BC309B	0-10	BF936	0-61	MJ515	2-92
2N2905A	0-88	2N4334	1-10	AF129	0-20	BC309B	0-10	BF937	0-61	MJ516	2-92
2N2906	0-56	2N4335	1-10	AF130	0-20	BC309B	0-10	BF938	0-61	MJ517	2-92
2N2906A	0-70	2N4336	1-10	AF131	0-20	BC309B	0-10	BF939	0-61	MJ518	2-92
2N2907	0-75	2N4337	1-10	AF132	0-20	BC309B	0-10	BF940	0-61	MJ519	2-92
2N2907A	0-88	2N4338	1-10	AF133	0-20	BC309B	0-10	BF941	0-61	MJ520	2-92
2N2923	0-12	2N4339	1-05	AF134	0-20	BC309B	0-10	BF942	0-61	MJ521	2-92
2N2924	0-14	2N4340	0-92	AF135	0-20	BC309B	0-10	BF943	0-61	MJ522	2-92
2N2925	0-17	2N4341	0-81	AF136	0-20	BC309B	0-10	BF944	0-61	MJ523	2-92
2N2926	0-12	2N4342	0-68	AF137	0-20	BC309B	0-10	BF945	0-61	MJ524	2-92
Green	0-12	2N4343	0-75	AF138	0-20	BC309B	0-10	BF946	0-61	MJ525	2-92
Yellow	0-10	2N4344	0-82	AF139	0-20	BC309B	0-10	BF947	0-61	MJ526	2-92
Orange	0-10	2N4345	0-81	AF140	0-20	BC309B	0-10	BF948	0-61	MJ527	2-92
2N3053	0-32	2N4346	0-81	AF141	0-20	BC309B	0-10	BF949	0-61	MJ528	2-92
2N3054	0-32	2N4347	0-81	AF142	0-20	BC309B	0-10	BF950	0-61	MJ529	2-92
2N3055	0-32	2N4348	0-81	AF143	0-20	BC309B	0-10	BF951	0-61	MJ530	2-92
2N3390	0-28	2N3200	2-49	BC109	0-10	BD136	0-50	BSX26	0-49	MPSA65	0-25
2N3391	0-28	2N3201	1-05	BC113	0-13	BD137	0-55	BSX27	0-84	MPSA66	0-28
2N3391A	0-29	2N3202	1-05	BC114	0-30	BD138	0-55	BSX28	0-47	MPSA67	0-28

# Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

## SITUATIONS VACANT

A responsible position is available within the Company for a person to take charge and supervise a small but expanding group of technicians engaged in the servicing and maintenance of a wide range of modern electronic equipment including portable radio, TV, cassette recorders, digital calculators, etc.

A working knowledge of the principles of transistor and integrated circuits pertinent to the above apparatus is required and qualifications to HNC, HND, T.Eng, Final C & G or equivalent is desirable. However, academic qualifications are not essential and proven practical ability is regarded as more important for this position where an active participation in the work is necessary.

A salary in the region of £2,500 is envisaged for this position coupled with excellent conditions and benefits of the Company situated at Audenshaw, near Manchester.

Write or telephone for application form from the Personnel Dept.:

**JONES SEWING MACHINE CO. LTD.**  
SHEPLEY STREET, AUDENSHAW, Nr. MANCHESTER

**MEN!**  
**£50 p.w.**  
**can be yours**

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators  
Training Centre  
M90, Oxford House  
9-15 Oxford Street, W.1  
Telephone 01-734 2874

**KA Solid State Switching**

We have a vacancy for a responsible person capable of furthering the development of this side of our activities. The responsibilities include design, production, testing, quality control, etc. for Solid State Switching Systems in a specialised field of industry. An interesting opportunity for the right person.

Apply to:

**KIMBER-ALLEN LTD.**  
London Road, Swanley, Kent  
Telephone: Swanley 63234

**MECHANICAL ENGINEER REQUIRED.**  
Electronics Engineer Required. Interesting work in Audio Industry. Salary negotiable. For further details please telephone 01-739 9672 (Ext. 8) between 9 a.m. and 5 p.m.

## EDUCATIONAL

### A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams **FIRST TIME!** Free books. Low cost. Personal tuition. Send **TODAY** for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name \_\_\_\_\_

Address \_\_\_\_\_

**ICS** Dept. 730U  
Stewarts Road,  
London SW8 4UJ

## WANTED

**TOP PRICES PAID**  
**NEW VALVES AND TRANSISTORS**  
Popular T.V. and Radio types  
**KENSINGTON SUPPLIES (B)**  
367 Kensington Street  
Bradford 8, Yorks.

**NEWNES RADIO** and T.V. Servicing 1964-1965 urgently required. Good price paid. Tel. Harrogate 86844

## FOR SALE

### FIBRE OPTICS

**Flexible Light Pipe** for conveying light to inaccessible positions. Fibroflex Type 1, Glass 1-14mm effective dia, PVC sheathed, 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

**Polariser Sheet** up to 1 sq. ft. max. size. 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those nixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

**Circuit Board Etching Kits.** Full instructions. £1.371 (VAT inc.), P. & P. 14p

**Photographic CDS Light Cells**—used (with part of original circuit free), 33p (VAT inc.), Post free.

All items are strictly C.W.O.

From: **ARVIN SERVICE COMPANY**  
12 CAMBRIDGE ROAD  
ST. ALBANS

**MORSE MADE EASY!!**  
**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.  
Beginner's Section only £2-30, complete course £4-50 (Overseas £1 extra) details only, 4p stamp, 01-860 2898  
**G8HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY**

**TV LINE OUT-PUT TRANSFORMERS**  
Tidman Mail Order Ltd., 236 Sandycroft  
Road, Richmond, Surrey TW9 2EQ  
01-948 3702

**CATALOGUE NO. 18,** Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.,** 28 Gardner Street, Brighton, Sussex.

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

**PRACTICAL ELECTRONICS.** Volumes 2-8 complete. Good Condition. Offers. Box No. 52.

## RECEIVERS AND COMPONENTS

### 5-N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.  
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

**REDHAWK SALES LTD.**  
45 Station Road, Gerrards Cross, Bucks.  
MAIL ORDER ONLY

**BRAND NEW COMPONENTS** by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10 mF, 7p, 22, 47, 47p (50V, 5p); 100, 51p (50V, 7p); 220, 6p (50V, 8p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02, 2p; 0.04, 0.05, 3p; 0.068, 0.1, 31p. Polystyrene 63V E12 series 10-1,000pF, 2p; 1,200-10,000pF, 3p. Miniature highstab resistors, 5%, E12 series—Carbon Film 1/4W, 1Ω-10MΩ (10% over 1 MΩ). Metal Film 1/4W, 10Ω-2.2MΩ and 1W, 27Ω-10MΩ all 3p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

## Trampus electronics

Add 10% VAT (h) to all prices. All brand new, no rejects. Money Back Warranty.  
**5V DIGITAL INDICATOR:** 0-9DP socket and filter £1.45.  
**LED TYPE 4** 0-9DP DIL £2.25 each; 6x £2.19 each; 4 digit type £1.  
**LIGHT EMITTING DIODES:** All with data and panel clip. TTL 209 1" dia. 26p. Red 1" dia. type 33p. Green 75p. INFRARED BEAM LED £1.10.  
**GA8 detector** £1.80. Ultrasonic transducer £2.  
**DALO PCB resist marking pen** 60p. Copper board 12" x 6" SRBP 40p. PCB etch PAK 19p.  
**INTEGRATED CIRCUITS:** with data if required.  
**IC LITE SWITCH:** Photo any trigger 40mA/11-20V relay or TTL 87p. Dill relay £1.10.

## IC digital clock

MOS/LSI type. 28 pin, 4 or 6 digit, 12/24hr. Chip with socket £13; PCB £1.69; KIT £21.49. DVM voltmeter £12. Data 39p. 3W AF amp £1.24.

741 D118 pin 28p; 709 19p. D11 29p; 748 29p; mono 710 33p. 555 TIMER/mono/astable osc. clock 99p. REGULATORS: 1A 5 to 20V £1.49; 723 57p. RECEIVER 2N15 £1.19. Mini Rx Kit £1.99. 1310 stereo decoder for tuner £2.69. KIT £3.45.

## NEW LOW PRICES

GATES 7400/1/2/3/4/5/10/20/30/40/50, etc., 14p each. 7413 27p; 7441 78p; 7447 £1.09; 7470, 7472 28p; 7473, 7474 30p; 7475 60p; 7476 32p; 7490 59p; 7492 87p; 7480 69p; 7483 £1.10; 7486 37p; 7493 73p; 7494 83p; 7495 83p; 7496 89p; 74121 46p; 74141 89p; 74190/91/92/93/96 £2.39. DIL Plug/IC case 10mm high 16 pin 35p.  
**DIL SOCKETS:** low or high profile 8/14/16 pin 13p.  
**SEMICONDUCTORS:**  
 BC107 8p; BC108 7p; BC109 8p; BC110 9p; BC117/8/9 13p; BC122/3/4 11p; BCY70/72 13p; B1013/12 55p; BP505/51/52 15p; T1843 UJT 24p; 2N706 11p; 2N3369 12p; 2N2926/9 8p; 2N2646 49p; 2N3053 17p; 2N3055 40p; 2N3614 55p; 2N3702/3/4/5/6/7/8/9/10/11 All 8p each.  
**FETS:** 2N3819 27p; 2N3823 29p; SCR 400V: 1A 23p; 4A 55p. TRANSFORMER: 1A 6 and 12V £1.  
**CAPACITORS:** Disc 22p to 0.1µF 4p. 25V electrolytic 10, 50, 100µF 5p; 1,000µF 15p. PRE-SETS 5p each. RESISTORS 4W 5% 11p each. CARBON POTS 12p each. Dual 40p. Switch +12p. All Din Pins 13p; sockets 9p; Vero RRP.

## FLUORESCENT LIGHTS 12VOLT £2.79

13" watt fully built with diffuser.  
**TBIO and CODAR** communications and Hi-Fi retailer. ELECTRONIC ORGANS from £67.  
**PW ELECTRONIC CAR IGNITION KIT** £6.67.  
**VAT: YOU MUST ADD 10% (h) to all prices.**  
**FREE CAT. S.A.E.** Data sheets 8p each. P. & P. 5p. C.W.O. P.O. BOX 29, BRACKNELL, BERKS.

## M. & M. ELECTRONIC SUPPLIES

**ALL ELECTRONIC COMPONENTS SUPPLIED BY RETURN OF POST**  
**ALL BRAND NEW AND GUARANTEED**  
 ★ MOTOROLA  
 ★ FAIRCHILD  
 ★ TEXAS  
 ★ SIEMENS  
 ★ GENERAL ELECTRIC  
 ★ MULLARD  
 ★ FERRANTI  
 ★ R.S. COMPONENTS

S.A.E. QUOTATIONS BY RETURN OF POST. MAIL ORDER ONLY.

ALL MAIL TO:

11 ANDREW STREET, WALTON

LIVERPOOL L4 4DS

RADIO & TELEVISION AERIAL BOOSTERS

£2.95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50. Carr. £1.50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

Practical Electronics October 1973

## PRECISION

### POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.  
 0.47µF: ±5% 30p; ±2% 40p; ±1% 50p  
 1.0µF: ±5% 40p; ±2% 50p; ±1% 60p  
 2.2µF: ±5% 50p; ±2% 60p; ±1% 70p  
 4.7µF: ±5% 70p; ±2% 80p; ±1% £1.15  
 6.8µF: ±5% 80p; ±2% £1.15; ±1% £1.50  
 10µF: ±5% £1.10; ±2% £1.40; ±1% £1.80  
 15µF: ±5% £1.60; ±2% £2.10; ±1% £2.70

**TANTALUM BEAD CAPACITORS.** Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) 45p.

**NEW 1-TRANSISTORS.** BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178 at 35p each or 3 for 95p.

**POPULAR DIODES.** IN914, 7p each; 8 for 50p; 18 for £1. IN916, 9p each; 6 for 50p; 14 for £1. IN944, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

**NEW LOW PRICE—400 mW Zeners.** Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 9p each; 6 for 50p; 14 for £1. Special offer 6 off each voltage (66 zeners) £4.25.

**RESISTORS.** Carbon film 5%, 1/4W at 40°C, 1/2W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 100 of any one value; 70p for 100 of any one value. Special pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) 45p.

**400V A.C. CAPACITORS.** 0.1µF, size 1 1/2" x 1/2" x 1/2"; 0.25µF, size 1 1/2" x 1/2" x 1/2"; 0.5µF, size 1 1/2" x 1/2" x 1/2"; 1.0µF, size 2 1/2" x 1/2" x 1/2"; 2.0µF, size 2 1/2" x 1/2" x 1/2".

**SILICON PLASTIC RECTIFIERS 1-5A—** Brand new wire-ended DO27, 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5. Please add 10% VAT to all orders

**MARCO TRADING**  
 Dept. E10, The Maltings, Station Road  
 Wern, Shropshire

## BRAND NEW FULL SPEC. DEVICES SATISFACTION OR YOUR MONEY BACK

**U.K. ORDERS—Add 10% VAT to total MICROCIRCUITS:** 709 24p; 710 36p; 723 51p; 741 (14 pin) 27p; 748 37p; PA230 60p; FET Op. Amp. £1.62. SOLDERCON IC Pin Sockets 8.5p per pin. SOCKETS: 14 pin DIL HI or LO 12p each. RECTIFIERS: 1A: 50V 31p; 100V 4p; 200V 41p; 400V 5p; 800V 6p; 1000V 7p. ZENERS: BZ788C 2V7 to 33V 10p each. DIODES: IN916 4p; OA90 6p; IN4148 4p; LED PANEL LAMP with Bush and Data 24p. DALO PC RESIST PEN 69p. TRANSISTORS: 2N2926 BROWN 5p; 2N3053 15p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 26p; 2N4058 12p; BC107A 8p; BC108B 8p; BC109B 8p; BC109C 8p; BCY70 15p; BFY50/51/52 15p; OC44/45/71/72 12p; AF114/5/6/7 12p; AC126/7/8 12p.

Above prices on 25th July—check our list.

## JEF ELECTRONICS (P.E.10)

York House, 12 York Drive, Grappenhall Warrington WA4 2EJ. Mail Order Only. C.W.O.P. & P. at cost. 10p min. LIST free.

**TUNBRIDGE WELLS.** Components from Teleservice. S.A.E. or call in for list. Special offers, limited quantity; Matched AD161/2, 68p; 10 transistors similar 2N3702/3 unmarked, 32p; 12 IN914/6, 20p unmarked; air spaced twin gang receiver tuning capacitors, unused, 50p; thin grey connecting flex, 1p yd. Minimum order 40p, post free, but add 10% VAT. 108 Camden Road, Tunbridge Wells, Kent. Tel. 31803.

**74 TTL lowest prices.** First grade ceramic packaged devices not to be confused with seconds or rejects. 7400, 10p. 7473, 27p. 7474, 27p. 7490, 50p. 7493, 65p. 74141, 65p. Data booklet 10p. Postage on all orders 10p. A. TOOTELL, 9 Mendip Close, St. Albans, Herts

## DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen: £4.12 per 100; £3.25 per 1,000; £275 per 10,000. VAT and post paid.

**G.W.M. RADIO LTD.**  
 40/42 Portland Road, Worthing, Sussex BN9 0QB 34897

## R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Verobond 6x5 0.1 Matrix, 2 for £1. 4x4 0.1 Matrix, 4 for £1. 12x3 0.15 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LPI166, £1.10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 1/2 in with circuit, £1.37 1/2 inc. P.P.

Crouzet Geared Motors, 30-60 r.p.m. New, £1.54 inc. P.P.

UHF TV Tuners. Transistorised, £1.65 inc. P.P.

VCR138 CRT. New, boxed, £3.30 inc. P.P. Brand New Panel VU Meters, 4 1/2 x 3 1/2 in calibrated, £3.30 inc. P.P.

Transformers. 7.5V + 7.5V 1/4A, 66p inc. P.P. 18-0-18V, 200mA + 24V, 77p inc. P.P. 9-0-9V, 100mA, 69p inc. P.P. 12-0-12V, 100mA 69p P.P. 20V, 1A 88p inc. P.P.

Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, £2.20 inc. P.P.

P.C. Board. 5/5, 5 1/2 x 5 1/2 in, 10 for 70p inc. P.P.

Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components 70p inc. P.P.

2,500 mfd 100V/V capacitor 4 1/2" x 1 1/2". New, 85p inc. P.P.

Panel Meter 50µA. Brand new, 4 1/2" x 3 1/2". £3.30.

Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, £2.20 inc. P.P.

Panel with 2 min. nixie tubes to slot in, £2 inc. P.P.

## COMPUTER PANELS 6 assorted. No rubbish. £1 (25p). M.C. METERS 3 assorted 2in-3in, £1.15 (25p). 6 Fig. RESETTABLE COUNTER 16/22V.

Works on 12V, £2.20 (15p). SILICON DIODES 650V 1A. 10 on tagboard 35p (5p). New 800V 1A. 6-26p (5p). UNIT WITH 4 x BFY61, 4 Silicon Diodes, 4 Zeners, caps and resistors 45p (8p).

COPPER CLAD PAK. PANELS 5 1/2 in x 5 1/2 in 6 for 85p (10p). WIRE ENDED WELONS 10-50p (8p). Bank of 5 with 6-C407 driver trans. 50p (5p). UNIT WITH 25V D.C. MOTOR 2 relays, 2 motorised switches, mass of gears, etc. £2 (30p). THREE BANK 12 WAY MIDGET UNISELECTOR 250 ohm coil £2.25 (15p). POLYSTYRENE CAPACITORS 125V. 100, 160, 330, 500, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 0-01, 0-012, 22p dozen (8p). Mixed with s/nics 100-60p c.p.

7LB ASSORTED COMPONENTS £1.60 c.p.

2LB ASSORTED COMPUTER PANELS £1.80 c.p.

Liste computer panels, etc. 10p stamps refunded on purchase.

## J.W.B. RADIO

75 HAYFIELD RD., SALFORD 6, LANCS.  
 Postage in Brackets Mail Order Only

## DIGITAL CLOCK COMPONENTS

4/6 Digit Clock Chip £9.00; 6 Minित्रon Displays £6.00; 1 Digit Driver £1.50; 1 Segment Driver £1.50; Minित्रon Sockets 25p each. 2N 7447 drivers £1.20 each.

## LOW COST LED LAMPS

Red 3mm dia. 25p each; Red 4.45mm dia. 35p each; Green 3mm dia. 68p each; Green 4.45mm dia. 68p each.

## CALCULATOR DISPLAY

0-12 inches Character Height Flatpack £2.00 each.

## SLIDER SWITCHES

1 pole 2 position—Miniature 14p each; 2 pole 2 position 14p each; 2 pole 3 position 21p each; 1 pole 4 position 23p each. U.K. Postage and packing 10p. Overseas 25p.

## PERDIX COMPONENTS LTD.

Dept. PE73, 31 Green Lane, Chislehurst, Kent.

## COMPONENTS GALORE.

Pack of 500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send £1 + 10p P. & P. C.W.O. to: CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

## CERAMIC SPACERS

250 PCB stand-off. 270 high 0-700 bore 30p. GOODHART, 8 Beltinge Road, Herne Bay, Kent, CT6 6DH.

555 TIMER I.C. only 90p each inc. VAT. P. & P. 5p. 2 or more post free. C.W.O. to: CHARNWOOD (D.P.E. 3), Castle Hill, Holmesfield, Sheffield, S18 5WQ. Mail order only.

**GUARANTEED SEMICONDUCTORS FAST SERVICE - LOW PRICES**

AC107	18p	2N706	10p	ZENER DIODES
AC126	18p	2N930	80p	400mW 5%
AC127	18p	2N1131	22p	6.3 to 33 volts
AC128	18p	2N1132	22p	10p each
BC107	9p	2N1711	80p	1 watt 6%
BC108	9p	2N2904	18p	6.8 to 200 volts
AF114	14p	2N2904A	28p	15p each
AF115	14p	2N2905	28p	
AF116	14p	2N3053	18p	
AF117	14p	2N3054	50p	
BCY70	18p	2N3053	38p	RECTIFIERS
BCY71	80p	2N3702	9p	P.I.V. 1 AMP
BCY72	18p	2N3703	9p	60 IN4001 41p
BFX84	24p	2N3704	9p	100 IN4002 41p
BFX85	26p	2N3705	9p	200 IN4003 5p
BFX86	21p	2N3706	9p	400 IN4004 6p
BFX87	24p	2N3707	9p	600 IN4005 7p
BFX88	20p	2N3708	8p	800 IN4006 8p
BSX20	18p	2N3709	9p	1000 IN4007 9p

CASH W.O. PLUS P.P. 10p TO ROSSLESS SERVICES PARNDON HALL - HAMSTEL ROAD HARLOW - ESSEX

**MISCELLANEOUS**

**LOW COST LEDs**

MLED 500 in standard TO92 package for P.C. mounting. MV54 is T3 size, 2 mm, miniature. Both provide visible red light from 1.65V, 20mA. 150Ω resistors available for 5V d.c. (TTL) operation.

MLED 500	£1-10	£2-20	£3-74	£6-60	£2-65
MV54	£1-10	£2-09	£3-52	£6-05	£2-10

MADE'S TAILS: Spray of several thousand glass fibres, ready to use as part of decorative displays. £11 each including P. & P. and VAT.

POLARISERS for light control, glare reduction, modulators, stress analysis, 5/N enhancement for displays.

HN32 Linear Polariser, for Kerr cells, etc. HRCPT Red Circular Polariser, for LED displays. HNCPT3 Neutral Circular Polariser, for c.r.t.s, meters, etc. Send 9 x 6in S.A.E. for full details of the above plus our full range of Fibre Optics.

**FIBRE OPTIC SUPPLIERS**

P.O. Box 702 LONDON W10 6SL

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec, or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

**Build the Mullard C.C.T.V. Camera**

Kits are now available with comprehensive construction manual (also available separately at 76p)

SEND 5" 7" S.A.E. FOR DETAILS TO: CROFTON ELECTRONICS 15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

**PROFESSIONAL CASES**

FOR THE PRICE OF A PLAIN ALUMINIUM OR DIECAST BOX

Attractive Black Anodised Alloy case. Polished Mahogany-veneer Wood Block ends. Complete with front panel, ventilated rear panel, Chrome screws and rubber feet. Assembled in seconds with 4 screws. Size 6 1/2" x 4" x 5" depth. Price £1-30. P. & P. 9p. Trade enquiries welcome. Other sizes available.

ADFONIC (PE), 18 Yew Lane, Ashley, New Milton, Hants BH25 5BA. C.W.O. Mail Order Only. Components Lists Free.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

**NEW FROM ELBON**

L.E.D.'s (Red Emitting) Ideally suited for panel indicators Price only: 33p each or £2-50 for 10

**Light SENSITIVE SWITCHES**

Two types available giving wide operating voltages LITE-IC2 11V-20V working - £1 each - £8-50 for 10 LITE-IC3 20V-30V working - £1 each - £8-50 for 10

Applications include. Relay, Triac or Logic Drive automatic light switching and door control, beam break detection - burglar alarm, batch counting and code reading.

**BARGAIN PACK!**

2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for £5-00

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE

Please send C.W.O. to:

LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX

GLASS FIBRE P.C. BOARD—large supplies available. 1/4 in single sided one ounce copper, 2p per 3 sq in (under 1ft); 75p per sq ft (over 1ft). 1/4 in double sided one ounce copper, 1p per sq in (under 1ft); £1 per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. SOLID STATE LIGHTING, The Fira, Smallworth Lane, Garboldisham, Diss, Norfolk.

**ENAMELLED COPPER WIRE**

S.W.G.	1lb Reel	1/2lb Reel
10-14	£1-27	72p
15-19	£1-27	72p
20-24	£1-30	75p
25-29	£1-38	83p
30-34	£1-43	88p
35-40	£1-54	91p

Please add 10% to all above prices to cover VAT

The above prices cover P. & P. in U.K. Supplied by **INDUSTRIAL SUPPLIES**

102 Parrwood Rd., Withington, Manchester 20 Telephone No. 061-224 3553

METER REPAIRS. Ammeters. Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesholm Rd., London N16 0DS.

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. nullpotentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

**SOLID STATE LAMPS**

Try out the latest light emitting diodes

Experimenters' pack of four Motorola light emitting diodes (LEDs) complete with circuits, data and full instructions.

£1-10 per pack plus 5p postage C.W.O.

Trium Company Ltd., 12 Mount Ephraim, Tunbridge Wells, Kent

**BUILD THE TREASURE TRACER MK III Metal Locator**



- Varicap tuning
- Excellent sensitivity and stability
- Weights only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- Completely new design
- Send s.a.e. for leaflet

Complete kit Post 35p **£9-80**

Built, tested and guaranteed Post 35p **£13-75**

MINIKITS ELECTRONICS, 35 LANGLEY DRIVE, WANSTEAD LONDON E11 2LN (Mail order only)

SPECIAL resistor kit. 1/4W 5 per cent carbon film. 10 each E12 value. 22Ω to 2.2M. Total 610 for £3. P. & P. 10p. NEK ELECTRONICS (P2), 28 Carnegie Road, St. Albans, Herts.

**OMNI-DETECTORS**

(Featured ★ TV ★ Radio ★ Nat. Press) Ancient art of Dowsing in Modern Guise. Thrill to new discovery in this overlooked aspect of the Electro-Magnetic Spectrum. A LABORATORY IN A SINGLE PACK. Treasure Hunters! Use Omni-Detectors to: ★ Locate ANY buried substance, ANY depth. ★ Save hours of fruitless searching — MAP-DOWSING pinpoint search area before you leave home. ★ Limitless other uses. Dowsing used in World War 2 and by U.S.A. troops in Vietnam to locate underground springs, tunnels, mines. Send only £2-80 + 15p p. & p. for unique pack of 4 dowsing instruments (non-electronic) and explicit 40-page manual to sole suppliers: Omni-Detector Co. (Dept. P.E.), 27 Latham Road, Twickenham, Middx. TW1 1BN.

**4-STATION INTERCOM**



Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in deluxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft and other accessories. P. & P. 40p. **£8-75**

MAINS INTERCOM (new model) No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £17-95. P. & P. 60p extra.

**INTERCOM/BABY ALARM**



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 60ft connecting wire. Complete with battery. P. & P. 30p. **£4-85**



Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 25p. Full price refunded if not satisfied in 7 days. **£3-99**

WEST LONDON DIRECT SUPPLIES (PE/10) 160 KENSINGTON HIGH STREET, LONDON, W.8

**BAIRD-TYPE T.V. REVIVAL.** Interested? Write: L.D.T.V. 1 Burnwood Drive, Wollaton, Nottingham.

**LOW COST I.C. MOUNTING.** I.C. socket pins in lengths of 100 pins for 60p. (P. & P. 5p). S.A.E. Details and sample. GASKELL, Oak Lodge, Tansley, Derbyshire.

**LADDERS**

**LADDERS** 24ft £12.39, carr. £1.10. Leaflet. HOME SALES LADDER CENTRE (PREE2), Haldane (North), Halesfield (1) Telford, Shropshire. Tel. 0952 586644.

**OSMABET LTD.**

We make transformers amongst other things.

**AUTO-TRANSFORMERS, 110/200/240V.**  
50V, £9-30; 750V, £12-75; 1000V, £15-75; 2000W, £28-50; 3000W, £39-00; 4000W, £60-00, etc.

**LOW VOLTAGE TRANSFORMERS**  
Prim. 200/240V a.c. 6.3V 6A CT. £2-10; 12V 1.5A, £1-35; 3A £2-15; 6A CT. £2-80; 18V 1.5A CT. £2-15; 24V 1.5A CT. £2-15; 3A CT. £2-85; 5A, £4-30; 8A, £6-75; 12A £9-40; 40V 3A CT. £3-75; 50V 6A CT. £1-125; 25V 2A + 25V 2A, £4-15.

**LT TRANSFORMERS TAPPED SEC.** Prim. 200/240V  
0-10-12-14-16-18V 2A, £2-25; 4A, £3-40;  
0-12-15-20-24-30V 2A, £3-00; 4A, £4-05;  
0-5-20-30-40-60V 1A, £3-00; 2A, £4-20;  
0-40-50-60-80-90-100-110V 1A, £4-20.

**MIDGET RECTIFIER TRANSFORMERS**  
For F.W. rect., 200V a.c. 0-9V 1A, 12-0-12V  
0.25A or 20-0-20V 0.15A, £1-45 each; 9-0-9V 1A,  
£1-20; 12-0-12V 1A or 20-0-20V 0.75A, £1-35 each.

**MAINS TRANSFORMERS FOR POWER AMPLIFIERS**

Prim. 200/240V a.c. TX6 sec. 425-0-425 500 Ma.  
6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A, £15-00;  
TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT  
4A, 0-5-6.3V 3A, £9-40; MT2A 250V 100Ma,  
6.3V 2A, £1-50.

**O/P TRANSFORMERS FOR POWER AMPLIFIERS**  
P.P. sec. tapped 3 8-15ohms. A-A 6.6kΩ 30W,  
£4-80; A-A 3kΩ 50W, £8-00; 100W (EL34 RTFR,  
etc.), £13-50; tapped Multi O/P 10W, £2-25.

**G.E.C. MANUAL O/P POWER AMPLIFIERS**  
Covering valve amplifiers of 30 to 300W, 30p.

**LOUDSPEAKERS FOR POWER AMPLIFIERS**  
BAKER 25W, £6-40; 35W, £7-20; HI-FI, Major  
Module 20W w/tweeter Xover, £9-20; Baker speaker  
lists: FANE 50W, £10-50; 60W, £13-50; EMI  
13 x 8in 3 or 15Ω, £1-60; speakers for HI-FI 5in  
8Ω, £1-18; 8 x 5in 3, 8 or 15Ω £1-75.

**LOUDSPEAKERS**  
2 1/2in, 8, 16 or 25Ω, 2 1/2in 25Ω, 3in, 3, 8 or 25Ω, 3 1/2in  
8, 15 or 80Ω, 80p; 3in 3, 8, 15 or 25Ω, 5 x 3in  
3, 8 or 25Ω £1-05; 6 1/2in 3Ω, 6 x 4in 25Ω, 7 x 4in  
3, 15 or 25Ω, 8 x 2 1/2in 3Ω £1-28; 8 x 5in 15 or  
25Ω £1-50; 10 x 6in 3Ω £1-50.

**SPEAKER MATCHING TRANSFORMERS**  
12W 3 to 8 or 15Ω, £2 or down, £1-15.

**BULK TAPE ERASERS**  
Instant erasure, tape spools, cassettes, demagnetises  
tape heads a.c. 200/240V a.c. £2-50 plus P. & P.

**CONDENSERS**  
Paper, tubular W/E 2 1/2mf 250V Xovers, etc. 15p,  
£6 per 100; Block 4mf 800V, 75p; 8mf 750V, 75p;  
Electrolytic, 900mf 350V, 50p; 0-01/2KV, 12 1/2p.

V.A.T. extra on all orders.  
Carriage extra on all orders.

**S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY**  
46 Kenilworth Road, Edgware, Middx. HA8 8YQ  
Tel. 01-958 9314

**SERVICE SHEETS**

**SERVICE SHEETS, Radio, TV, etc.** 8,000 models. Catalogue 15p, S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

**P.C.B.: For Mullard Transistor Audio and Radio Circuits Handbook**

The following boards are now available: 1st Edition: paper base laminate. 10W H.Q. audio amp, p. 102, 66p. 25W H.Q. audio amp, p. 106, 70p. 10/25W H.Q. audio pre-amp, p. 108, 73p.

2nd Edition: fibreglass laminate. 10W Audio Amp, p. 122, 69p. 15/20W Audio Amp, p. 126, 73p. 25W Audio Amp, p. 128, 73p (incorporates protection circuit, p. 130).

Universal pre-amp, mono, p. 148, 78p. Universal pre-amp, stereo, p. 148, £1-48.

No other circuits are available.

Price includes P. & P. but add VAT. Remittance (not cash or stamps) with order. Allow 14 days for cheque clearance otherwise prompt despatch subject to stocks.

All boards are roller tinned, drilled and have component idents. printed on reverse.

**BRIBOND PRINTED CIRCUITS LIMITED**

Regd. in England 593908

Terminus Road, Chichester Sussex

**SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER**



WITH LIGHT DIMMER  
Max. Load 2kW at 250V a.c.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7-80 inc. VAT + 25p P. & P. EXTRA FACILITIES. Push-button for Manual Pulsing. 25p extra. Photocell for turning on the lights as the ambient light decreases, 75p extra.

**THREE CHANNEL FILTER UNIT**

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested.

Price £3-40 inc. VAT + 15p P. & P.

**OIL WHEEL PROJECTOR**



Build your own using our MULTI-COLOURED OIL WHEEL AND MOTOR KIT Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- ★ 6in dia. or 4in dia. OIL WHEEL (please state size required when ordering).
- ★ Suitable Miniature mains motor.
- ★ Full instructions.

For Professional Discotheque use or home enjoyment. Price £7-15 inc. VAT + P. & P.

**ELECTRONIC COMPONENTS BAGGAIN COMPONENT PACKS**


- Pack No.
- 1 500 Carbon resistors, 1, 1, 1, 2W.
  - 2 100 Electrolytic Condensers.
  - 3 250 Ceramic, Polystyrene, Silver Mica, etc. Condensers.
  - 4 250 Polyester, Polycarbonate, Paper, etc. Condensers.
  - 5 25 Potentiometers, assorted.
  - 6 250 High-stab. 1%, 2%, 5% resistors.
  - 7 50 Assorted Tagstrips.
  - 8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
  - 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
  - 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED  
£1 + 25p P. & P. per pack £5 for 5 packs post free.

**G.T. ELECTRONICS**

267 Acton Lane, London W4 5DG  
01-994 6275

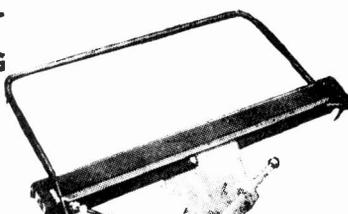**PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS**




With Bevelled Former Bars

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £17 carr. 50p
- No. 2. Capacity 18 gauge mild steel x 24in. wide ... £12 carr. 38p
- No. 3. Capacity 16 gauge mild steel x 18in. wide ... £12 carr. 38p

Also new bench models. Capacities 36in. x 18 gauge £35, 24in. x 16 gauge £32. Carriage 75p. Add 10% VAT to total price of machine and carriage. End folding attachments for radio chassis. Tray and Box making for 36in. model, 27 1/2p per ft. Other models 17p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

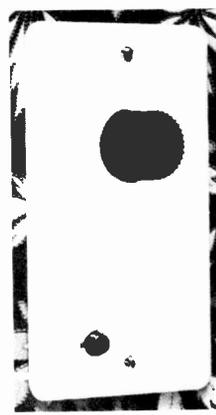A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997



**GAS & SMOKE DETECTOR**

COMPLETE parts kit  
MAINS OPERATED with flush or surface box £8-45 plus 20p P. & P.

Parts below available separately:

- TGS Sensor £1-80 plus 10p P. & P.
- Transformer £1-50 plus 15p P. & P.
- Speaker 50p plus 10p P. & P.

Please add 10% VAT to the above

**ELECTROMECH COUNTERS**  
Ruckinge, Ashford, Kent TN26 2EF

**PARTRIDGE MAINS ISOLATION TRANSFORMER.** Pri: 100-250V, 5V steps, Sec: 240V, 13 amps. £15, carr. pack. £1.

**PARMEKO MAINS TRANSFORMER** isolated windings. Pri: 200-250V. Sec: 90-120V at 4-5 amp. £4, carr. pack. 50p.

**GARDNER'S POTTED TRANSFORMER.** 0-250V. Pri: 200-250V. Sec. Input: 18V 500mA, 50V 150mA, 6V 250mA output. Size: 3in x 2 1/2in x 2 1/2in. £1, p.p. 20p. Ex equip. tested.

**RIPLEY MAINS TRANSFORMER.** Pri: 110V-240V. Sec: 12-5V: 0:12-5V 750mA 7V:0:7 V1A. £1, p.p. 20p.

**MAINS TRANSFORMER.** Pri: 100-250V. Sec: 22:0:22 200mA. 22:0:22 100mA 0:24V 20mA. 80p, p.p. 20p.

**TRANSISTOR OUTPUT TRANSFORMER.** Ratio 8:1, 120mH. Centre tap 2 watts. output, 20p, p.p. 3p.

**SMOOTHING CHOKE, 11MH, 1 1/2in x 1 1/2in x 1 1/2in.** 20p, p.p. 7p.

**BELLING LEE INSULATED TERMINALS.** Red or Black, 5 amp max. 10p pair, p.p. 4p.

**FINNED ALUMINIUM HEATSINK.** 9in x 1 1/2in. Ready drilled. 20p, p.p. 7p.

**FINNED ALUMINIUM HEATSINK.** 9in x 8in x 1 1/2in. in C: 4 x 2N3055, £2, p.p. 20p.

**SUB-MIN. CROC. CLIPS.** Red or Black, insulated 4p. Min. quantity, 6, p.p. 4p.

**GARRARD MAG. TAPE DECKS:** 1 1/2 i.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors £7-50 each, p.p. 60p.

**MOTEK 3 speed tape deck (1 1/2in x 3 1/2in x 7 1/2in)** reel to reel 7in mains operated, £7-50, p.p. 60p.

**10 REED SWITCHES** operated by push buttons and magnets, 50p, p.p. 25p.

**COMPONENT PANEL 6 s'ecs (200V 4 amps), 6 condensers, 12 resistors, 30p, p.p. 8p.**

**COMPONENT PANEL (9 1Cs FJH131) (1CA300), 1 crystal 7-68kHz + various other components, £1, p.p. 8p.**

**COMPONENT PANEL, 4 x 500 mfd, 50V d.c. cap. 1 x 2N1218, 1 x 2N11468, 2 x 2N598, plus various other components, 10p, p.p. 9p.**

**NEON PANEL, 24 neon's, wire ended, 90-240V, 20p p.p. 4p.**

**MAINS NEONS** Red or Green. Size: 1/2in x 1/2in x 1 1/2in. 15p, p.p. 4p.

**LEVER ACTION P.O. 1000 TYPE SWITCHES** Lock 4-pole changeover, 15p, p.p. 4p. Ex equip. Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

**MULLARD & MALLORY SCREW TERMINAL CAPACITORS** 4,500pF 64V, 7,100pF 40V, 50p each. 29,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 10p.

**MULLARD FULLWAVE RECTIFIERS** 6-48V, 15 amp, 75p, p.p. 9p.

**BELLING LEE 1.5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.**

**RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.**

**SOLENOIDS 12 VOLT PULL ACTION** 2in x 1in x 1/2in, 40p, p.p. 8p.

**SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 5p.**

**SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 1 1/2in, 50p, p.p. 9p.**

**BANGMO WESTON TIME LAPPED METER** Mains operated. 1 1/2in x 1 1/2in x 2in, £1-50 p.p. 7p.

**ARROW RELAY, 240V a.c. coil, double pole change over, make contact's 10A, 240V a.c., 25p, p.p. 8p.**

**OMRON MK2 MIDGET POWER RELAY, 12V d.c.** Double pole changeover. New, 70p, p.p. 5p.

**STC MINIATURE RELAY 280Ω, perspex cover, double pole changeover, 6-15V new, 35p, p.p. 5p.**

**STC VARLEY, miniature relays 700Ω, perspex cover, 4 pole changeover, 40p, p.p. 5p.**

**POTTER BRUMFIELD 12V d.c. 3 pole changeover** with base, contacts rated 7A d.c., £1, p.p. 10p.

**TELESCOPIC AERIALS** Chromed 7in closed, 28in extended, 6 section ball jointed base, 23p, p.p. 3p new.

**MULLARD 4 DM 160 INDICATORS** in plastic holder/cover, ex equip., size approx. 1 1/2in x 1 1/2in x 1/2in, 30p, p.p. 5p.

**PRINTED CIRCUIT BOARD/19 ACY 19\* 10 OA200** Diodes: 1 reel relay: 1 AZ 229 zener ass. capacitor/resistors. Power supply 22V, 250 mA d.c. Output 240V a.c., £1, p.p. 20p. Ex equip.

**WIRING CABLE** Size-1-020. Various colours. 350yds, 60p, p.p. 23p.

**TAPE POSITION INDICATOR** Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

**FIELD ELECTRIC LIMITED**

3 Shenley Road  
Borehamwood, Herts.  
Tel.: 01-953 6009



# WILMSLOW AUDIO

**THE Firm for speakers!**

## SPEAKERS


- EMI 13 x 8, 3, 8 or 15 ohm £2-83
- EMI 13 x 8, 150 d/c 3, 8 or 15 ohm £2-25
- EMI 13 x 8, 450 t/w 3, 8 or 15 ohm £3-60
- EMI 13 x 8 type 350 8 ohm £3-25
- EMI 6 1/2in 93650 4 or 8 ohm £2-60
- EMI 8 x 5 d/c cone roll/s 8 ohm £2-50
- Baker Group 25 3, 8 or 15 ohm £6-60
- Baker Group 35 3, 8 or 15 ohm £7-50
- Baker De Luxe 12in d/c cone £9-62
- Baker Major 12in £7-50
- Kef T27 £4-67
- Kef T15 £5-50
- Kef B110 £6-16
- Kef B200 £7-42
- Kef B139 £10-72
- Kef DN8 £1-92
- Kef DN9 £1-37
- Kef DN12 £2-12
- Kef DN13 £2-75
- Fane Pop 100W 8/15 ohm £21-45
- Fane Pop 60W 8/15 ohm £12-26
- Fane Pop 50W 8/15 ohm £10-17
- Fane Pop 25/2 25W 8/15 ohm £5-94
- Fane Pop 15W 8/15 ohm £4-40
- Fane Crescendo 15in 8 or 15 ohm £27-50
- Fane Crescendo 12A 100W 8 or 15 ohm £24-20
- Fane Crescendo 12B 75W bass 8 or 15 ohm £24-20
- Fane 80T7 8in d/c roll/s 8 or 15 ohm £3-16
- Fane 80B7 8in d/c cone 8 or 15 ohm £2-64
- Goodmans Axent 100 tweeter £6-60
- Goodmans 8P 8 or 15 ohm £3-60
- Goodmans 10P 8 or 15 ohm £4-49
- Goodmans 12P 8 or 15 ohm £11-55
- Goodmans 15P 8 or 15 ohm £17-05
- Goodmans 18P 8 or 15 ohm £29-78
- Goodmans Twinxiom 8 £6-79
- Goodmans Twinxiom 10 £7-61
- Eiac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm £2-53
- Eiac 6 1/2in d/c roll/s 8 ohm £3-22
- Eiac 6 1/2in d/c cone 8 ohm £2-59
- Eiac 4in tweeter TW4 £1-21
- Wharfedale Bronze 8 RS/DD £3-11
- Wharfedale Super 8 RS/DD £3-60
- Wharfedale Super 10 RS/DD £9-80
- Coral 6 1/2in d/c cone roll/s 8 ohm £1-44
- Siran 6 1/2in 3 or 8 ohm £2-20
- Richard Allan 12in d/c 3 or 15 ohm 10in x 6in 3, 8 or 15 ohm £1-92
- 8in x 5in 3 or 8 ohm £1-38
- 7in x 4in 3 or 8 ohm £1-38
- 2 1/2in 64 ohm or 70mm 80 ohm £5p
- Adestra Hiten, 10in 10W 8 or 15 ohm £2-80
- Eagle DT33 dome tweeter £5-45
- Eagle HT15 tweeter £3-66
- Eagle CT5 tweeter £1-25
- Eagle CT10 tweeter £2-54
- Eagle MHT10 tweeter £3-74
- Eagle FR4 £4-45
- Eagle xover CN23, 28, 216 £1-15
- Sp matching transformer 3-15 ohm £1-10
- Celestion MF1000 25W horn 8 or 15 ohm £16-45
- Celestion PS3 (for 10in) £2-16
- Celestion G12M 8 or 15 ohm £12-00
- Celestion G12H 8 or 15 ohm £15-00
- Celestion G15C 8 or 15 ohm £24-00
- Celestion G18C 8 or 15 ohm £33-00

Car Stereo speakers—ask for leaflet
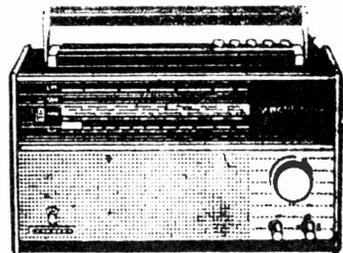
## SPEAKER KITS

- Wharfedale Unit 3 £8-25
- Wharfedale Unit 4 £14-50
- Wharfedale Unit 5 £21-00
- Richard Allan Twinkit £7-33
- Richard Allan Triple 8 £10-76
- Richard Allan Triple Assom £16-20
- Richard Allan Super Triple £19-36
- Goodmans DIN 20 £6-58
- Fane Mode One £9-00

- Kefkit 2 £24-75
  - Kefkit 3 £35-50
  - Peerless 2-8 £5-50
  - Peerless 3-15 £10-45
  - Peerless 3-25 £16-00
  - Peerless 10-2 £8-47
  - Peerless 20-2 £10-41
- Stephen speaker kits and cabinets—send for free booklet Choosing a Speaker.  
PRICES INCLUDE VAT.  
Carriage and insurance 50p per kit.



## RADIOS/CASSETTES/AMPS

- Grundig Mariner TR865 £32-00
  - Grundig Party Boy 210 £20-00
  - Grundig Elite Boy 500 £27-00
  - Grundig Melody Boy 500 £27-00
  - Grundig Melody Boy 1000 £36-75
  - Grundig Yacht Boy 210 £34-25
  - Grundig RF430 mains £27-00
  - Grundig RF310 mains £22-75
  - Grundig Top Boy £16-75
  - Grundig Satellite 1000 £121-00
  - Grundig C402 cassette £27-00
  - Tandberg TP41 £37-75
  - Nordmende 7000 £87-00
  - BASF 9301 radio/cassette £58-00
  - Bush RTP100 radio/cassette £30-50
  - Trio KA2000A £33-00
  - Trio KA2002 £41-00
  - Hitachi TRQ232S stereo cassette £48-50
  - Hitachi TRQ257 cassette £20-00
  - Hitachi KCT1210L radio/cassette £37-50
  - Hitachi KH966 £18-70
  - ITT/KB Golf Preset £21-25
  - ITT/KB Weekend Auto £16-00
  - ITT/KB Europa £18-00
  - ITT/KB SL53 cassette £22-62
  - ITT/KB Studio 60M cassette £29-32
  - ITT/KB Studio 73 stereo cassette £44-00
  - Koyo KTR1664 8 waveband £40-00
  - Koyo KTR 1770 11 waveband £56-50
- Prices include VAT.  
Carriage and insurance 50p. FREE with each radio—world radio stations book.

## PA/DISCO AMPLIFIERS

(carr. and ins. £1)


- Baker 100W £46-00
- Linear 30/40 £25-00
- Linear 40/60 £30-00
- Linear 80/100 £55-00

**FREE with speaker orders over £7**

"Hi Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.  
Carriage and insurance 25p per speaker (tweeters and crossovers 15p). ALL PRICES QUOTED INCLUDE VAT.
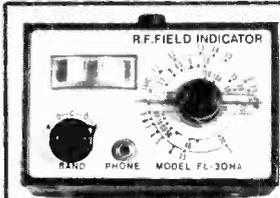
## WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Radios, etc.: 10 Swan Street, Wilmslow, Cheshire, SK9 1HF. Telephone: Wilmslow 29599.



**R.F. FIELD INDICATOR**  
Model FL-30HA. Frequency Range: 5 ranges 1Mc/s to 250Mc/s. £3.40.

**TAPE RECORDER LEVEL METER**  
500µA, 55p



**CARDIOID DYNAMIC MICROPHONE**

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £4.95.



**4 1/4 x 3 1/4 in METER.** 30µA, 50µA or 100µA, £2.86.

**MULTI-METER**

Model 200H  
20,000 ohm/volt, £5.28.




**3 WATT STEREO AMPLIFIER**  
£4.30



All items advertised in previous numbers of this magazine still available. All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 5. Special prices for quantity quoted on request.

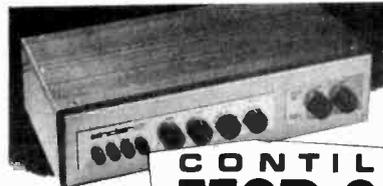**M. DZIUBAS**

158 Bradshawgate • Bolton • Lancs. BL2 1BA




**CONTIL MOD-2**

48 sizes of low cost cases in blue PVC coated steel with PVC coated aluminium front and rear panels. The design of these cases permits the instrument to be built up or serviced without the external panels. Price includes all stainless steel assembly screws, rubber feet and one or two chassis according to size, and also VAT and P. & P. Delivery ex stock. Special punching to take Sinclair Hi-Fi modules available.

Wood grain  
D. £4.34  
E.G. £5.00  
H. £5.50

Quantity Discounts

	X	Y	Z	I off
A	4.5	3	6.5	£2.89
B	4.5	7	6.5	£3.24
C	4.5	10	6.5	£3.90
D	9	3	6.5	£3.90
E	9	7	6.5	£4.34
F	9	10	6.5	£5.00
G	13	3	6.5	£4.34
H	13	7	6.5	£5.00
I	13	10	6.5	£5.50
J	18	3	6.5	£5.00
K	18	7	6.5	£6.71
L	18	10	6.5	£8.14
M	4.5	3	13	£3.24
N	4.5	7	13	£4.34
O	4.5	10	13	£5.50
P	9	3	13	£4.34
Q	9	7	13	£5.50
R	9	10	13	£6.71
S	13	3	13	£5.50
T	13	7	13	£6.71
U	13	10	13	£8.14
V	18	3	13	£6.71
W	18	7	13	£8.14
X	18	10	13	£9.73

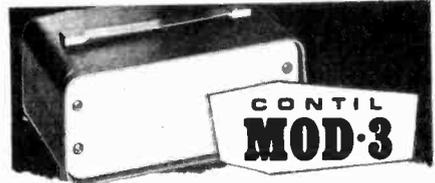

**CONTIL MOD-3**

Contil Mod 3 cases come in six sizes and offer the manufacturer of small instruments an attractive low cost case available ex stock. Made in blue PVC coated steel, these cases offer strength and rigidity and come complete with front and rear panels. PCB and PSU mounting systems are also available.

Dim. in ins.  
Mod-301 7 x 3 x 5 1/2  
Mod-302 7 x 4 x 5 1/2  
Mod-303 7 x 6 x 5 1/2  
Mod-304 11 x 3 x 5 1/2  
Mod-305 11 x 4 x 5 1/2  
Mod-306 11 x 6 x 5 1/2

One off (less for quantities)  
£3.25  
£3.41  
£3.85  
£3.85  
£4.56  
£5.28

Prices include case, chassis, feet, stainless screws, P. & P. and V.A.T.

**WEST HYDE**



WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRESCENT, NORTHWOOD HILLS, MIDDX. HA8 1NN  
Telephone: Northwood 24941/26732  
Telex 923231 Code: West Hyde Mthwd.

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

C.W.O. Please. P. & P. please add 10p to orders under £2  
MAIL ORDER. CALLERS SATURDAYS ONLY

## SEMICONDUCTORS

TRANSISTORS		DIODES		LINEAR IC's	
AC125	12p	BC147	12p	OC70	10p
AC126	12p	BC148	12p	OC71	10p
AC127	12p	BC149	12p	OC72	10p
AC128	12p	BD131	49p	2N2218A	13p
AC187	12p	BD132	49p	2N2220	10p
AC188	12p	BF194	15p	2N2221	10p
AD161	30p	BF195	15p	2N2483	10p
AD162	30p	BFY50	22p	2N2484	10p
AF114	12p	BFY51	22p	2N2926R	9p
AF115	12p	OC26	40p	2N2926V	9p
AF116	12p	OC28	40p	2N2926V	9p
AF117	12p	OC35	40p	2N2926G	10p
BC107	9p	OC42	10p	2N3014	10p
BC108	9p	OC44	10p	2N3055	55p
BC109	9p	OC45	10p	OA85	7p
				OA90	5p
				OA91	5p
				OA200	8p
				OA202	8p
				723C	14 pin 80p
				IN914	4p
				IN4001	6p
				IN4002	6p
				IN4003	7p
				IN4004	7p
				IN4005	7p
				IN4006	8p
				BYZ 88 series	8p
				400mV 3.3V-30V.	30p
				Price 12p each	

THYRISTOR	JACK PLUGS (CHROME)	SWITCHES
200V 4A	Standard Screened 12p. Stereo Screened 30p. 2.5mm Screened 8p. 3.5mm Screened 10p.	TOGGLE SPST 18p DPDT 22p SLIDE DP 1A 10p ROTARY Wafer 1-12 way 25p
VEROBOARD	SOCKETS	DIN PLUGS, SOCKETS AND COUPLERS
24 x 3 1/2 in 0.1 0.15	Standard 12p. Stereo 15p. 2.5mm 7p. 3.5 mm 7p.	Pin: 2, 3, 4, 5 (180, 240), 6, 7. Plugs 12p. Sockets 9p. Couplers 10p.
24 x 5 in 20p 18p		PHONO PLUGS, SOCKETS AND COUPLERS
24 x 5 in 24p 22p		Plugs 5p. Couplers 6p
24 x 5 in 24p 22p		SOCKETS: Single 5p. Double 7p. Triple 10p
24 x 5 in 27p 30p		COAXIAL
24 x 17 in 75p 60p		Plugs 10p
24 x 17 in 97p 84p		Sockets 8p
5 x 17 in 128p		
24 x 17 in (plain) 40p		
24 x 17 in (plain) 60p		
5 x 17 in (plain) 80p		
Pkt. 50 pins 20p		
Spot face cutter 42p		
Pin insertion tool 52p		

**TGS GAS SENSOR HEAD (ELECTRONIC NOSE)** for detection of combustible gases, with a proven record for an extremely reliable Fire Detection. TGS Head can detect extremely low gas concentration levels without amplification. (PE July '73, "ELECTRONIC NOSE" illustrates amplified alarm system. TGS HEAD AND CIRCUIT APPLICATION DATA. PRICE £1.85.

## RESISTORS

Power Watts	Tol.	Range	Miniature wire wound. Values Available	1-9	10-99	100+
1/2	5%	2.2-2.2M	E12	1p	0.8p	0.7p
1	5%	2.2-4.7M	E12	1p	0.8p	0.7p
1	5%	2.2-10M	E12	2p	1.6p	1.4p
4	10%	1-10 ohm	E12	6p	5p	—

Do not mix ohmic values to obtain quantity prices. Ignore fraction

## POLYESTER CAPACITORS.

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2µF, 0.01µF, 0.015µF, 0.022µF, 0.047µF, 3p; 0.068µF, 0.1µF, 0.15µF, 4p; 0.22µF, 7p; 0.33µF, 10p; 0.47µF, 13p.  
160V: 0.1µF, 0.15µF, 4p; 0.22µF, 5p; 0.33, 6p; 0.47µF, 7p; 0.68µF, 10p; 1µF, 13p.  
Radial lead P.C. type:  
250V: 0.01µF, 0.015µF, 0.022µF, 3p; 0.033µF, 0.047µF, 0.068µF, 3p; 0.1µF, 4p; 0.15µF, 4p; 0.22µF, 0.33µF, 5p; 0.47µF, 7p; 0.68µF, 10p; 1.0µF, 11p.

## ELECTROLYTIC CAPACITORS.

Miniature axial lead type.  
63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 47µF, 68µF, 6p each.  
40V: 100µF, 6p; 150µF 25V, 6p; 25V: 220µF, 11p; 470µF, 13p; 680µF, 20p; 1,000µF, 25p.

## CERAMIC CAPACITORS:

50V d.c. Plaquette body 25mm leads. Range: 22pF-10,000pF. Price 2p each.

## POTENTIOMETERS:

Carbon Track 0-25W, log and linear values.  
1kΩ-2MΩ Single gang 12p  
5kΩ-2MΩ/gang w/switch 24p  
5kΩ-2MΩ Dual gang 37p

## PRESET POTENTIOMETERS

0-25W 1kΩ-1MΩ Hor. and Vert. 6p  
0-1W 100Ω-220kΩ Vert. only 3p

## KNOB

To fit 1/4 in shaft unless specified.  
Black Pointer type 8p  
Slim Silvered 10p  
Black lin W/chrome Rim 15p  
Slider Pot knob 10p

## SLIDER POTENTIOMETERS

0-25W log and linear values  
10kΩ-100kΩ Single gang 35p  
10kΩ-100kΩ Dual gang 50p

## WATFORD ELECTRONICS

35 CARDIFF RD., WATFORD, HERTS, ENGLAND.

Enclose 10p stamps for our comprehensive catalogue.

Name

Address

# BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

**VCO-2 STABLE, PRECISION V/C OSCILLATOR** gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. OFT-1 chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Approved by a Musical Association. Send 15p for full catalogue of our famous musical effects.

## D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

## Dewtron

using (Regd. Trademark)

PROFESSIONAL MODULES  
CASH SAVINGS

by buying modules and parts in bulk!

All modules are available separately:

Ring Modulator RM2, £8. Voltage-controlled Oscillator VC01, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5.50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

## Dimmit


range of light dimmers

Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression, 60mm slider range; size 12 x 5 x 4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £5.50 inc. VAT, add 10p P. & P. Also available in 2kW, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 400W, 1,000W, 2,000W.

NEW addition to Dimmit range—Model 5L800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Black A1 case—size 12 x 4 x 7cm. Full instructions, £6.50 inc. VAT, add 10p P. & P. Send for complete illustrated catalogue and price list.

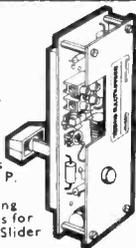**YOUNG ELECTRONICS** Mail Order Dept.  
54 Lawford Road, London NWS 2LN. Telephone 01-267 0201



## BAKER 12" MAJOR £9-90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

## MAJOR MODULE KIT £12-50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

### BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8.80	Superb 12 in. 20W	£16.50	ALL PRICES INCLUDE V.A.T.
Major 12 in. 20W	£9.90	Group 25 12 in. 25W	£8.80	
Deluxe 12 in. 15W	£11.00	Group 35 12 in. 35W	£9.90	

**BAKER LOUSPEAKER CO., BENSAM MANOR PASSAGE**


THORNTON HEATH, SURREY Tel. 01-684 1665

LOUSPEAKERS CATALOGUE AND ENCLOSURE PLAN 5p



# RAYMER MICROCHIP

# RE500

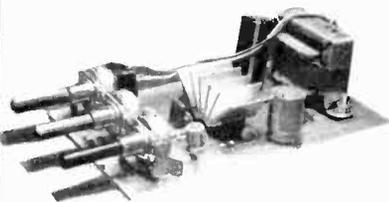

### SPECIFICATIONS

OUTPUT 5W RMS (10W peak)  
FREQUENCY RESPONSE 10Hz to 50kHz ± 3dB  
TOTAL HARMONIC DISTORTION less than 1%

LOAD IMPEDANCE 4 to 16 ohms  
INPUT IMPEDANCE 100kΩ nominal  
POWER GAIN 40dB typical  
SIZE 140mm x 80mm x 45mm  
With free instruction sheet  
PRICE £6-93 (inc. VAT) + 25p P. & P.

Guaranteed 12 months against failure in normal use. This advanced high-fidelity integrated amplifier is completely self-contained and only requires connecting to mains, speaker and input.

Ideally suited for:  
MONO RECORD PLAYERS  
MONO CONVERSION TO STEREO  
STEREO CONVERSION TO QUADRAPHONIC  
(x 2 Microchip + Decoder)  
TV AMPLIFIER  
TAPE AMPLIFIER

PA INSTALLATIONS  
AUDIO ALARM, ETC.

TRADE ENQUIRIES WELCOMED

NAME.....

ADDRESS.....

PLEASE SEND.....

I enclose P.O./Cheque/Money Order

**RAYMER ELECTRONICS LTD., STANLEY ROAD  
CAMBRIDGE CB5 8LB**

Reg. Bus. 1031205

# FREE!

## Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.L.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O., Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE09, Aldermaston Court, Reading RG7 4PF.**

Published approximately on the 10th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd. Publishers' Subscription Rate (including postage): For one year to any part of the world £2.65.

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not, be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



#### CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL	<input type="checkbox"/> Man. Prod.—cont.	<input type="checkbox"/> Constructional-cont.
<input type="checkbox"/> A.M.S.E. (Mech.)	<input type="checkbox"/> Quality Control	<input type="checkbox"/> Building
<input type="checkbox"/> Boiler Inspect. & Operation	<input type="checkbox"/> Salesmanship	<input type="checkbox"/> Building Drawing
<input type="checkbox"/> C & G Eng. Crafts	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> Build. Foreman
<input type="checkbox"/> C & G Fabricat.	<input type="checkbox"/> Work Study	<input type="checkbox"/> Carpentry & Join.
<input type="checkbox"/> Diesel Eng.	<input type="checkbox"/> Works	<input type="checkbox"/> Civil & Municipal
<input type="checkbox"/> Eng. Inspection	<input type="checkbox"/> Management	<input type="checkbox"/> Engineering
<input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP	<input type="checkbox"/> Constructional
<input type="checkbox"/> Inst. Eng. & Tech.	<input type="checkbox"/> A.M.I.E.D.	<input type="checkbox"/> Construction
<input type="checkbox"/> Inst. Motor Ind.	<input type="checkbox"/> Design of Elec.	<input type="checkbox"/> Surveyors
<input type="checkbox"/> Mainten. Eng.	<input type="checkbox"/> Machines	<input type="checkbox"/> Institute
<input type="checkbox"/> Mechanical Eng.	<input type="checkbox"/> Die & Press Tool	<input type="checkbox"/> Clerk of Works
<input type="checkbox"/> Sheet Metal Work	<input type="checkbox"/> Design	<input type="checkbox"/> Council Eng.
<input type="checkbox"/> Welding	<input type="checkbox"/> Electrical	<input type="checkbox"/> Geology
<input type="checkbox"/> ELECTRICAL & ELECTRONIC	<input type="checkbox"/> Draughtsman-ship	<input type="checkbox"/> Health Eng.
<input type="checkbox"/> A.M.S.E. (Elec.)	<input type="checkbox"/> Gen. Draughts-ship	<input type="checkbox"/> Hydraulics
<input type="checkbox"/> C & G Elec. Eng.	<input type="checkbox"/> Jig & Tool Des.	<input type="checkbox"/> Inst. Builders
<input type="checkbox"/> C & G Elec. Inst.	<input type="checkbox"/> Tech. Drawing	<input type="checkbox"/> Inst. Works & Highway Sup.
<input type="checkbox"/> C & G Elec. Tech.	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS	<input type="checkbox"/> Painting & Dec.
<input type="checkbox"/> Computer Elect.	<input type="checkbox"/> Colour TV	<input type="checkbox"/> Public Hygiene
<input type="checkbox"/> Elec. Maths	<input type="checkbox"/> C & G Radio/TV	<input type="checkbox"/> Road Engineer.
<input type="checkbox"/> Elec. Science	<input type="checkbox"/> Electronics	<input type="checkbox"/> Structural Eng.
<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> C & G Telecomm.	<input type="checkbox"/> Surveying
<input type="checkbox"/> Electrical Eng.	<input type="checkbox"/> Tech.	<input type="checkbox"/> GENERAL
<input type="checkbox"/> Install. & Wiring	<input type="checkbox"/> Prac. Rad. Elec. (with kit)	<input type="checkbox"/> Agricultural Eng.
<input type="checkbox"/> Meters	<input type="checkbox"/> Radio Amateurs	<input type="checkbox"/> Council of Eng. Inst.
<input type="checkbox"/> & Measuring Instruments	<input type="checkbox"/> Exam	<input type="checkbox"/> Farm Science
<input type="checkbox"/> MANAGEMENT & PRODUCTION	<input type="checkbox"/> Radio Servicing & Repairs	<input type="checkbox"/> General Educat.
<input type="checkbox"/> Auto. Control	<input type="checkbox"/> Radio & TV Eng.	<input type="checkbox"/> Gen. Plastics
<input type="checkbox"/> Computer Prog.	<input type="checkbox"/> Trans. Course	<input type="checkbox"/> Pract. Maths
<input type="checkbox"/> Electronic Data	<input type="checkbox"/> TV Main. & Serv.	<input type="checkbox"/> Pract. Slide Rule
<input type="checkbox"/> Processing	<input type="checkbox"/> AUTO & AERO	<input type="checkbox"/> Pure & Applied Maths
<input type="checkbox"/> Estimating	<input type="checkbox"/> Aero Eng.	<input type="checkbox"/> Refrigeration
<input type="checkbox"/> Foremanship	<input type="checkbox"/> A.M.I.M.I.	<input type="checkbox"/> Rubber Tech.
<input type="checkbox"/> Inst. Cost & Man. Accountants	<input type="checkbox"/> A.E.C. Cert.	<input type="checkbox"/> Sales Engineers
<input type="checkbox"/> Inst. Marketing Management	<input type="checkbox"/> Auto Engineer.	<input type="checkbox"/> Tech. Report
<input type="checkbox"/> Meritication	<input type="checkbox"/> Auto Repair	<input type="checkbox"/> Writing
<input type="checkbox"/> Motor Trade Man.	<input type="checkbox"/> C & G Auto. Eng. Garage	<input type="checkbox"/> Timber Trade
<input type="checkbox"/> Network Plan.	<input type="checkbox"/> Management	<input type="checkbox"/> University Ent.
<input type="checkbox"/> Numerical Cont.	<input type="checkbox"/> M.A./I.MI Dipl.	<input type="checkbox"/>
<input type="checkbox"/> Operational	<input type="checkbox"/> Motor Vehicle Mechanics	<input type="checkbox"/>
<input type="checkbox"/> Research	<input type="checkbox"/> CONSTRUCTIONAL	<input type="checkbox"/>
<input type="checkbox"/> Personnel Man.	<input type="checkbox"/> A.M.S.E. (Civil)	<input type="checkbox"/>
<input type="checkbox"/> Planning Eng.	<input type="checkbox"/> Architecture	<input type="checkbox"/>
<input type="checkbox"/> Production Eng.	<input type="checkbox"/>	<input type="checkbox"/>

*Coaching for many major exams, including C & G and assistance in O.N.C./H.N.C.*

**G.C.E.**  
**58 'O' & 'A'**  
**LEVELS SUBJECTS**  
**Over 10,000**  
**group passes**

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE09 Aldermaston Court, Reading RG7 4PF BPE09

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by C.A.C.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# Henry's

**DON'T RELY ON YOUR MEMORY**  
**BUY NOW AT BARGAIN PRICES**  
 Order your latest Henry's Catalogue Price 55p post paid  
 complete with Discount Vouchers



You pay less  
 VAT with Henry's  
 Low Prices

Now built and used by thousands of satisfied customers.

**FEATURES:** slim design, overall size in cabinet 15 1/2 in x 2 1/2 in x 6 1/2 in  
 6-IC's, 10 transistors, stabilisers, Gardners low field transformer, Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form.


**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED TEXAS ENGINEERS FOR PERFORMANCE, BY RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES.** On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc. Constructional details Ref. No. 21, 30p. Distributed by Henry's throughout UK.

**FREE** Teak cabinet with complete kit. Kit price **£28.50** (+ VAT + 50p carr/packing) or built and tested **£35** (+ VAT + 50p carr/packing) as illustrated.

## BUILD THE TEXAN

**20 + 20 WATT IC STEREO AMPLIFIER**

As featured by Practical Wireless 1972

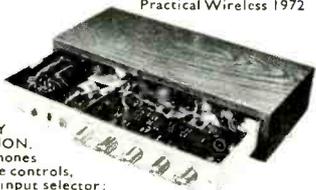

## TEXAN STEREO SYSTEM

PLUS Price Savings



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems, size 12 1/2 10in and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

**SYSTEM 25** (list approx. £109) **£79.50**  
**SYSTEM 76** (list approx. £117) **£89.50**  
 (plus 10% VAT and plus £1.45 carr/packing).

### BARCLAYCARD/ACCESS

Call, write or phone your order  
 01-402 4736  
 EASY TERMS FOR CALLERS

**KITS - TEST GEAR - AMPLIFIERS - SPEAKERS - DECKS - POWER SUPPLIES - TRANSISTORS - IC's**

See pages 847, 848 and 849 of this magazine

## BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise, IF stages, LED indicators, Tuning meter, AFC. Easy to construct and use. Mains operated. Slim modern design with fibre glass PC teak cabinet, etc. Available as a kit to build or ready built. Overall size: 8in x 2 1/2 in x 6 1/2 in. Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5, 30p.) Henry's are sole distributors UK and Europe.



Kit price **£21** (+ VAT)  
 or built and tested **£24.95** (+ VAT)

**LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN REC. PRICES.**

	3 for	6 for	10 for	25 for
C60	£1.00	£1.80	£2.80	£6.75
C90	£1.33	£2.57	£4.20	£10.25
CI20	£1.62	£3.15	£5.00	£12.25



Quantity and trade enquiries invited.

**LEARN A LANGUAGE**—complete with phrase book. German, French, Spanish, Italian. £1.36 per course. £5 for any 4.

## LOW COST HI-FI SPEAKERS SPECIAL OFFERS

EMI 13in x 8in—full range speakers (post 20p each or 30p pair); \*150TC—8 ohms Twin Cone 10 watt, £2.20 each or £4 pair; \*450 10 watt c/o Twin Tweeters 3, 8 or 15 ohms, £3.50 each or £6.90 pair; EW 15 watt 8 ohms c/o Tweeters, £4.30 each or £7.90 pair; 350 20 watt c/o Tweeters 8 or 15 ohms, £7.50 each or £14.20 pair.



\* Polished wood cabinet £4.60, post 35p.  
**8 ohms full range (post 20p)**  
 FR4 4in 5 watt, £4; FR65 6 1/2in 10 watt, £5.50;  
 FR8 8in 15 watt, £7.60; FR23 9 x 6in 15 watt, £6.00.

**BASS AND MID RANGE**—8 ohms (post 20p)  
 AA12 5in 15 watt, £3.20; B10 5 1/2in 15 watt, £5.60; B200 8in 15 watt, £6.45; B139/2 13in x 8in 30 watt LF, £10.25.

**TWEETERS AND CROSSOVERS** (post 20p)  
 K2006 10 watt 8 or 5 ohms, £1.90; FH76 15 watt 8 ohms, £3.20; K2011 30 watt 8 ohms, £3.75; T27 KEF, £4.25; Accent 100 30 watt 8 ohms, £4.90; K4009 1kHz/5kHz c/o, £2; SN75 3kHz var. c/o, £1.75.

**SPEAKER KITS** (carr. etc. 35p)  
 20-2 8in 30 watt, £10 each; 20-3 8in 40 watt, £15 each; LINTON 2 20 watt, £15.95 pair; GLENDALE 3 30 watt, £28.95 pair; DOVEDALE 3 50 watt, £42 pair; KEF KK2, £20.40 each; KEF KK3, £32 each.

## BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size: 4 1/2 in long x 2 1/2 in wide x 1 1/2 in deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines, etc.




Price **£24.95** + VAT  
 Also available assembled ready to use **£29.95** + VAT
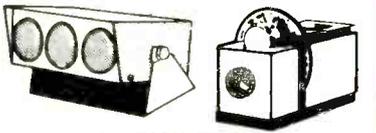
## EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



- DISCO MINI:** A complete portable disco, fitted mixer/preamp, 2 decks all facilities. 100 watt amplifier for above **£98.50**
- SL100:** 100 watt mixer/amplifier with slider controls **£38.75**
- RS0:** 50 watt mixer/amplifier **£69.00**
- DISCO AMP:** 100 watt mixer/amplifier chassis unit **£49.50**
- DISCO MIXER/PREAMPLIFIERS (O/P for up to 6-100 watt amplifiers):**
- SDL1** (rotary controls) **£65.85**
- SDL11** (slider controls) **£49.50**
- DISCO VOX** (slider controls): The complete disco unit **£58.50**
- DJ100:** 100 watt power amplifier for above **£69.50**
- DJ30L:** 3 channel 3kW sound to light **£38.75**
- DJ40L:** as 30L plus built-in microphone **£29.50**
- DJ40L:** as 30L plus built-in microphone **£38.75**
- DIMANATIC:** 1kW adjustable speed auto dimmer **£25.00**
- SCENESTROBE** **£19.00**
- ROAD STROBE** **£25.00**
- Disco anti-feedback microphone **£11.95**
- Coit 150 watt liquid wheel projector **£22.50**
- 150 watt QI liquid wheel projector **£50.00**
- 150 watt QI cassette wheel projector **£50.00**
- Spare Effects cassettes, large range of patterns **£8.00**
- Mini spot bank fitted 3 lamps **£11.00**
- Auto Trilite (mini with flashers) **£17.00**
- Mixer/Mics/Speakers/Lighting, UK's largest range



All prices carr. paid (UK) (VAT EXTRA). Barclaycard/Access call, write or phone your order 01-723 6963—easy terms for callers.

**10% VAT TO BE ADDED TO ALL ORDERS.** Prices and descriptions correct at time of press E & OE.

# Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-4028381  
 354-356 High Fidelity and Tape Equipment 01-4025854/4736  
 309 PA-Disco-Lighting High Power Sound 01-723 6963  
 303 Special offers and bargains store  
 All mail to 303 Edgware Road, London W2 1BW

Open:-  
 9 am-6 pm  
 6 days a week  
 All stores open all day Saturday

# **Audio IC Identichart**

## CIRCUIT IDEAS

### SINGLE PREAMPLIFIERS

Type	Man	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	V <sub>out</sub>	BW	Dis	Noise
PA230	Ge	12	76	35	100	10	0.5	1	2
MFC8040	Mo	30	80	75	100	7		0.1	1
LD3050	Sy	7.5	24	6.8		0.8		0.3	
(includes driver)									
LD3100	Sy	5.5	50	70		0.8		0.3	45+
LD3110	Sy	15	75	50		2		0.2	4.5mV+
LD3115	Sy	15	65	110		3.3			1.2
LD3120	Sy	20	65	110		4.5		0.1	1
LD3130	Sy	30	64	110		6		0.1	1
LD3141	Sy	20	66	65		4.2		0.1	700+
LD3150	Sy	9	66	90		1.6			1

### DUAL (STEREO) PREAMPLIFIERS


Type	Man	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	V <sub>out</sub>	BW	Dis	Noise	CS
PA239	Ge	12	68	250	100	1.5		0.5	0.7	90
MC1303	Mo	±15	80			5.5		0.1	100+	60
LM1303	Na									
MC1339P	Mo	12	66	250	100	1		1.2	0.7	70
LM381	Na	9 to 40	55	100	150	V <sub>s</sub> -2	75k	0.1	0.5	60
LM382	Na	9 to 40	50	100	150	V <sub>s</sub> -2	75k	0.1	0.8	60
CA3048	Rc	12	58	90	1k	2.4	0.3	0.65	300+	45
LA314B	Sy									
CA3052	Rc									
LA3100	Sy	6	61	90	1k	1.5	0.4	0.4	1	40
(includes driver)										
LA3101	Sy	6	60	90	1k	1.5	0.4	0.4	1	40
SN76131N	Te	±15	86	150	5k	22			1	140
TH9014P	To	30	75			6.5		0.1	100+	

### 1 TO 1W AMPLIFIERS


Type	Man	P <sub>o</sub>	R <sub>L</sub>	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	Dis	
MFC4000	Mo	1/4	16	9	36			4	
MFC6000	Mo	1/4	16	9	44			4	
MC1306P	Mo	1/2	8	9	50		0.5	0.5	
TAA611A	Sg	0.65	4	6	68				
MC1454G	Mo	1	16	16	20	10	0.4	0.4	
(3 gain options)									
					25				
					31				
MFC6070	Mo	1	16	16	32			1	
MFC8010	Mo	1	16	16	52			1	
PA222	Ge	1	22	22	72*	55	1	1	
PA234	Ge	1	22	22	18	100	2	3	
ULX2275	Sp	1	8	14	72	20M		0.75	
(Dual Audio Amplifier)									
LA4030	Sy	1	8	11	30	8	0.45	0.5	
SN76001	Te	1	8	9	68	750		4	

### 1 TO 3W AMPLIFIERS


Type	Man	P <sub>o</sub>	R <sub>L</sub>	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	Dis	
TAA611E	Sg	1.1	8	9	68				
PA266	Ge	1.5	16	22	55	40	1.5	1	
PA237	Ge	2	16	9 to 27				1	
LM380	Na	2	8	18	34	150		0.2	
MFC9010	Mo	2	16	19	50			2	
SL402D	PI	2	7.5	14 (P)	24	20M		0.1	
(Main amp + preamp)									
					(M) 26	100M	0.2	0.3	
TBA820	Sg	2	8	12	75				
ULX2277	Sp	2	8	18	72	20M		0.75	
(Dual Audio Amplifier)									
LA4031	Sy	2	4	13.2	30	8	0.45	0.5	
TAA611B	Sg	2.1	8	9	70	750		1	
TAA621	Sg	2.2	16	18	72	150		10	
TBA641A	Sg	2.2	4	9	46	3M		0.6	
SL403D	PI	3	7.5	18 (P)	24	20M		0.1	
(Main amp + preamp)									
					(M) 26	100M	0.2	0.3	
SL414A	PI	3	7.5	18 (P)	24	20M		0.1	
(Main amp + preamp)									
					(M) 26	100M	0.2	0.3	
LA4032	Sy	3	8	18	34	10	0.35	0.5	

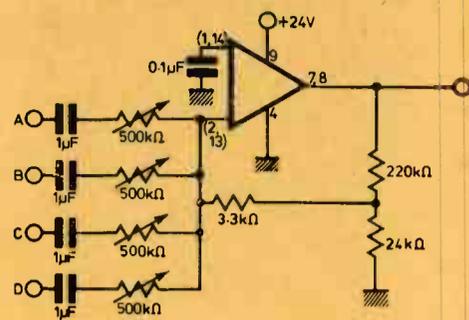

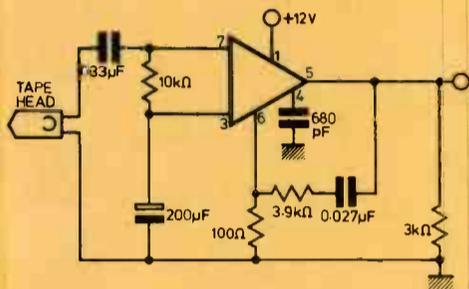
A four channel audio mixer using the LM381 (National Semiconductor)



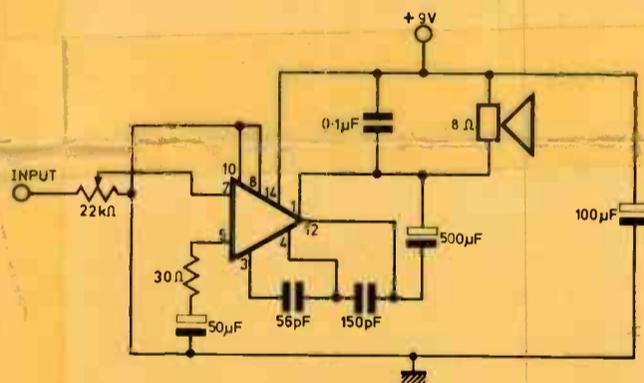
A tape playback preamplifier with NAB equalisation using the MC1339P (Motorola)




A 1W amplifier using the SN76001 (Texas)

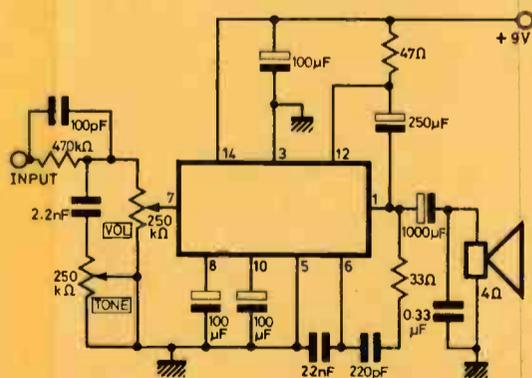


A 4.5W amplifier using the TBA641 (SGS)

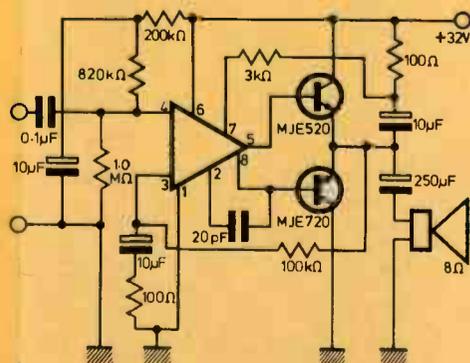

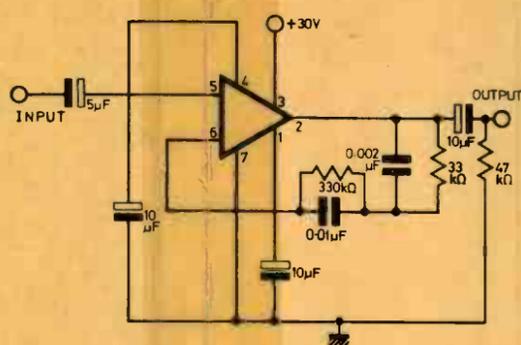
A 10W amplifier using the MFC8020 Class B driver (Motorola)



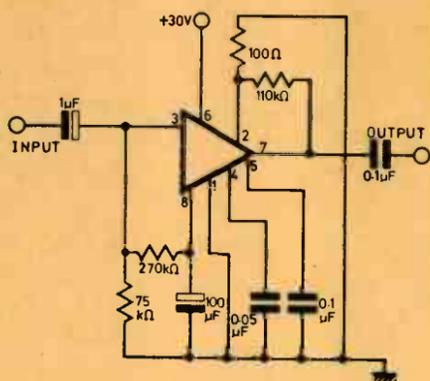
A magnetic pickup preamplifier circuit with RIAA equalisation (Toshiba TH9014P)



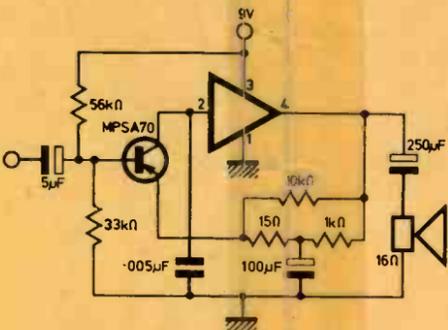
A wideband amplifier using the MFC8040 (Motorola)



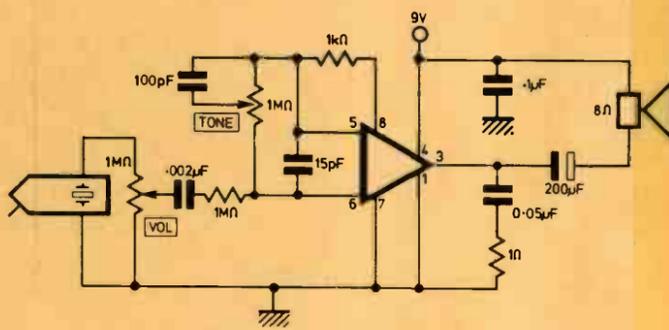
A sensitive 1/4W amplifier using the MFC4000 (Motorola)



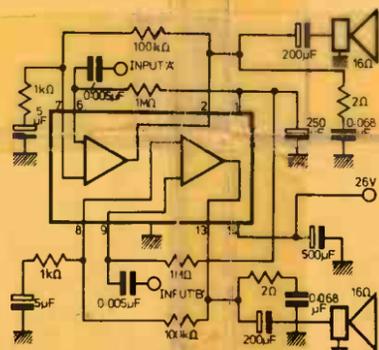
A 1/2W amplifier for use with a record player using a ceramic pickup (Motorola MC1306P)



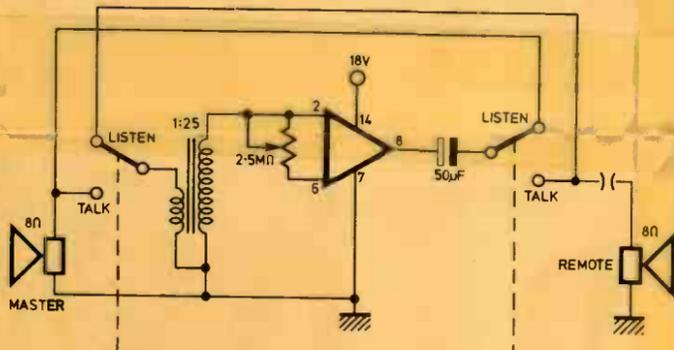
A stereo 4 + 4W amplifier using a single ULX2276 integrated circuit (Sprague)



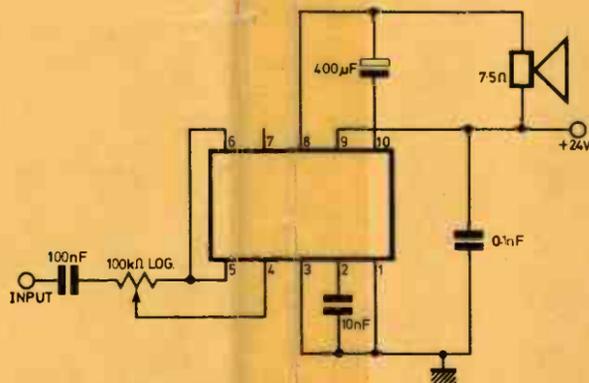
A simple intercom using the LM380 integrated circuit (National Semiconductor)



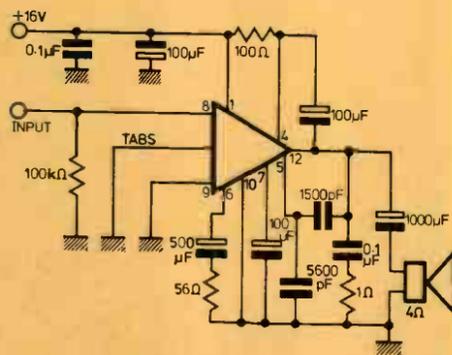
A basic 5W amplifier using the SL415A (Plessey)



A 7W amplifier using the TBA810S (SGS)

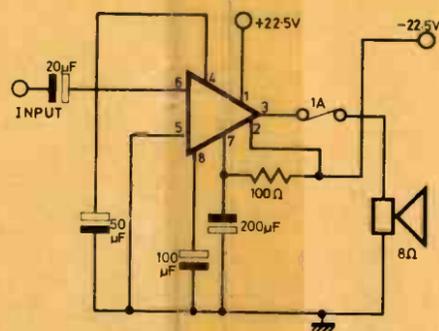

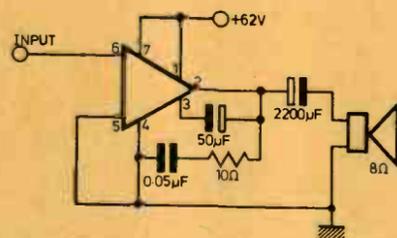A 20W amplifier using the TH9013P (Toshiba)



A 50W amplifier using the SI1050A (Sanken)

## 3 TO 10W AMPLIFIERS

Type	Man	P <sub>o</sub>	R <sub>L</sub>	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	Dis
TAA611C	Sg	3.3	8	15	72	750		1
PA263	Ge	3.5	16	30	58			5
LA4000	Sy	3.5	4	13.2	65	8		0.5
STK405	Sy	3.5	4	13.2	40	27		1.5
MFC9000	Mo	4	16	21	50	500		2.8
ULX2276	Sp	4	16	26	72	20M		2
<b>(Dual Audio Amplifier)</b>								
LA4033	Sy	4	8	22	34	10	0.4	0.5
TBA641B	Sg	4.5	4	14	46			
STK401	Sy	4.5	4	13.2	40	27		1.5
PA246	Ge	5	16	34	56		0.6	0.7
SL415A	PI	5	7.5	24	(P) 24	20M		0.1
<b>(Main amp + preamp)</b>								
SN76006	Te	6	8	26	34			0.3
SN76013	Te	6	8	24	48	200		1
SN76023	Te	5	8	24	48	200		1
TBA810S/AS	Sg	7	4	16	80	5M		0.3
STK011	Sy	8	8	25	35	40		
TCA940	Sq	10	4	18				

## 10W AND ABOVE AMPLIFIERS

Type	Man	P <sub>o</sub>	R <sub>L</sub>	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	Dis
STK015	Sy	13	8	32	33	40		1
STK020	Sy	13	8	±16	33	40		1
STK016	Sy	15	8	38	33	40	0.2	1
STK023	Sy	20	8	44	30	27		0.5
STK025	Sy	20	8	±22	30	27		0.5
TH9013P	To	20	8	45	32	22		1
STK029	Sy	25	8	48	30	27		0.5
STK030	Sy	25	8	±24	30	27		0.5
STK032	Sy	25	8	±24	30	27		0.5
SI1020A	Sa	25	8	48	30	70	0.2	0.5
SI1025A	Sa	25	8	48	30	70	0.2	0.5
SI1050A	Sa	50	8	62	30	70	0.2	0.5

## TRANSISTOR DRIVERS

Type	Man	V <sub>s</sub>	G <sub>v</sub>	R <sub>in</sub>	R <sub>out</sub>	Dis	Description
CA3007	Rc	±6	22*	4	60	0.28	Class B driver
MFC8020	Mo	32	58	1M		1	Class B, driving up to 10W output
MFC8021A	Mo	14	87	500		1	Class B driver
MFC8022A	Mo	40	99	500		1.5	Class B driver
MFC4050	Mo	12	21				Class A driver

## ABBREVIATIONS

- V<sub>s</sub> Recommended supply voltages (volts). The sign "±" before a voltage indicates that two power supplies are needed
- G<sub>v</sub> Voltage gain of the i.c. (\* indicates power gain)
- R<sub>in</sub> Input impedance (kiloohms)
- R<sub>out</sub> Output impedance (ohms)
- V<sub>out</sub> Typical peak-to-peak output voltage capability (volts)
- BW 3dB down high frequency point (megahertz)
- Dis Typical distortion at rated output power (per cent)
- Noise Typical noise voltage referred to the input (µV) (+ indicates referred to output)
- CS Typical channel separation figure (dB)
- R<sub>L</sub> Recommended load (speaker) impedance (ohms)
- P<sub>o</sub> Typical power output into R<sub>L</sub> at given V<sub>s</sub> (watts)
- Man Manufacturer. See accompanying list for addresses (below)

Manu- facturer	Code	Address	Sanken	Sa	Photain Controls, Randalls Road, Leatherhead, Surrey.
General Electric	Ge	International General Electric Co., 296 High Holborn, London, W.C.1.	Sanyo	Sy	Guest International Ltd., Nicholas House, Brigstock Road, Thornton Heath, Surrey.
Motorola	Mo	Motorola Semiconductors, York House, Empire Way, Wembley, Middlesex.	SGS	Sg	SGS-ATES, Planar House, Walton Street, Aylesbury, Bucks.
National Semi- conductors	Na	National Semiconductor (UK) Ltd., The Precinct, Broxbourne, Hertfordshire.	Sprague	Sp	Sprague Electric (UK) Ltd., 159 High Street, Yiewsley,
Plessey	Pl	Plessey Semiconductors, Cheney Manor, Swindon, Wiltshire.	Texas	Te	West Drayton, Middx. Texas Instruments Ltd., Manton Lane, Bedford.
RCA	Rc	RCA Ltd., Sunbury-on-Thames, Middlesex.	Toshiba	To	Erie Distributor Division, Erie Electronics Ltd., Gt. Yarmouth, Norfolk.