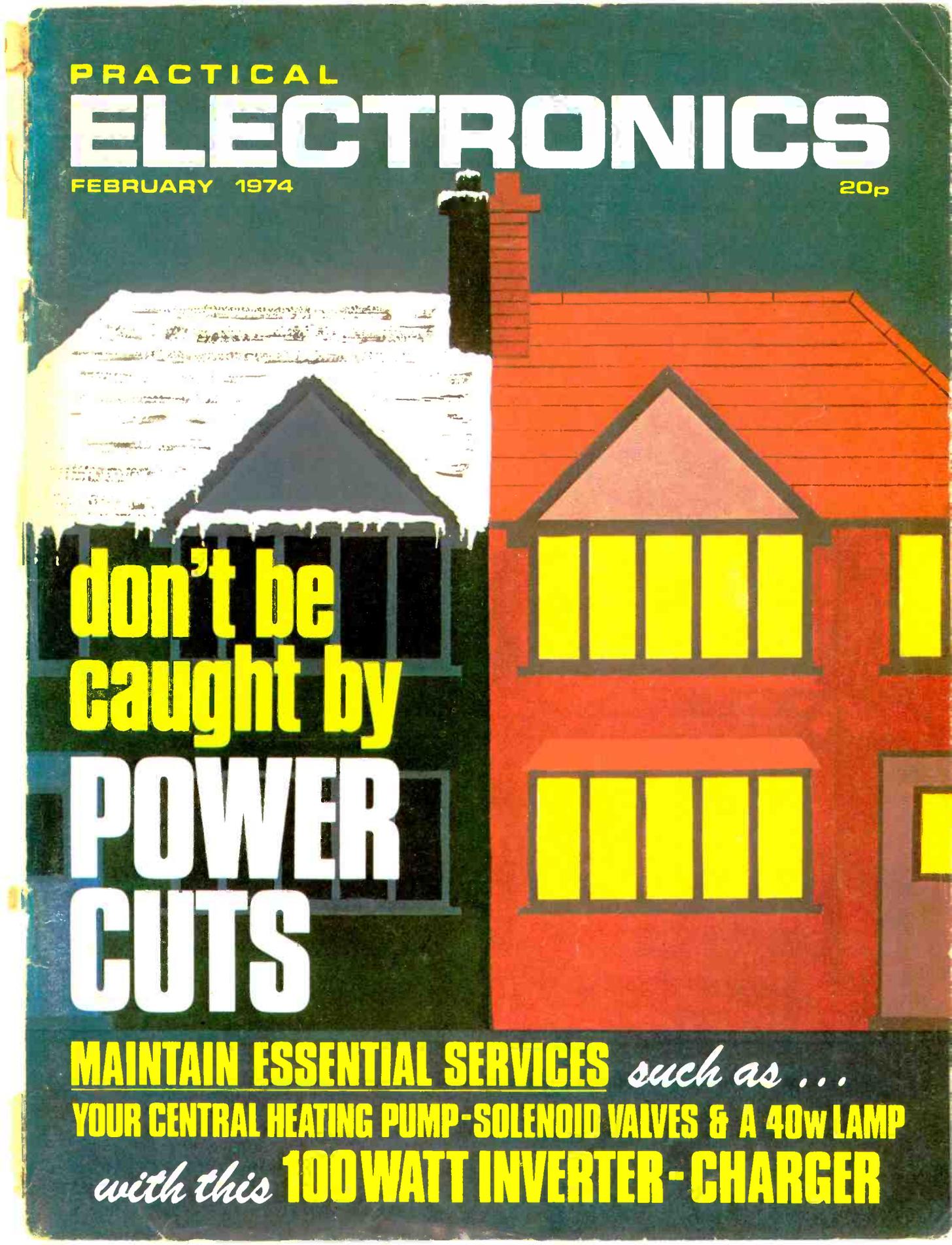


PRACTICAL

ELECTRONICS

FEBRUARY 1974

20p

An illustration of a house with a snow-covered roof and a red house next to it. The snow-covered house has a dark roof and a chimney. The red house has a red roof and several windows that are lit up with a yellow glow. The background is a dark green color.

**don't be
caught by
POWER
CUTS**

MAINTAIN ESSENTIAL SERVICES *such as ...*
YOUR CENTRAL HEATING PUMP-SOLENOID VALVES & A 40W LAMP
with this **100WATT INVERTER-CHARGER**

Write the Specification of your perfect iron

and compare it with an Antex

*low leakage and
Precision for delicate
equipment
Interchangeable Bit
Iron-coated
large*



MODEL X25 Soldering Iron 220-240 or 100-120 Volts. The leakage current of the NEW X25 is only a few micro amps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element. Ceramic and steel shaft. Bits do not "freeze" and can easily be removed. **PRICE £2-05** (rec. retail) P & P 10p Suitable for production work and as a general purpose iron.

MODEL CCN 220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16" 1/4" and 3/64" including Heat Shield. **PRICE £2-48** (rec. retail) P & P 10p.



MODEL C Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE £2-05** (rec. retail) P & P 10p.

MODEL MLX KIT
Battery operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet and with booklet "How to Solder". **PRICE £2-54** (rec. retail) P & P 12p.

ST3 Stand - This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration. **PRICE: £1-00** (rec. retail) P & P 10p.

MODEL G 18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. **PRICE £2-26** (rec. retail) P & P 10p.

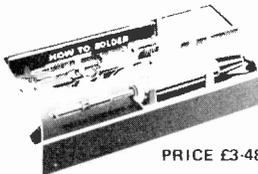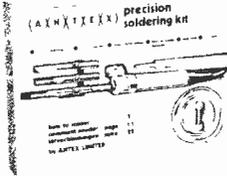MODEL SK.2 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink solder and "How to Solder" booklet. **PRICE £3-25** (rec. retail) P & P 10p.



MODEL SK.1 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. **PRICE £3-48** (rec. retail) P & P 12p.



ALL PRICES include VAT at 10%

Please send the following:

Please send the ANTEX colour catalogue

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:
ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR
(no stamp required) Tel 0752 67377.

I enclose cheque/P.O./Cash (Giro No. 258 1000)

NAME _____

ADDRESS _____

PE2

PRACTICAL ELECTRONICS

VOLUME 10 No. 2 FEBRUARY 1974

CONSTRUCTIONAL PROJECTS

- 100W INVERTER/CHARGER** *by R. Verrill* 132
Maintains essential services in the home
- STAGE LIGHTING DIMMER** *by R. Liffen* 142
The author replies to points raised by readers
- P.E. SOUND SYNTHESISER—13** *by G. D. Shaw* 151
This concluding article deals with the keyboard frame and final tuning
- AUTO CHARGER-REGULATOR** *by J. R. Watkinson* 156
Convert your vehicle to solid state charging control and improve efficiency
- AUDIO/VISUAL THERMOMETER** *by M. Plant* 164
A preset temperature sensing device that has many applications
- AUDIO MILLIVOLTMETER** *by J. N. Watt* 168
Measures alternating voltages down to 1mV at frequencies from 30Hz to 50kHz

GENERAL FEATURES

- INGENUITY UNLIMITED** 141, 166
Touch Volume Control—Electronic Doorbell
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—6** *by R. A. Cole* 146
Pick-ups and turntables for quadrasonics


NEWS AND COMMENT

- EDITORIAL—Conservation** 131
- SPACEWATCH** *by Frank W. Hyde* 145
The French Approach—The Japanese Approach
- MARKET PLACE** 150
A look at a cassette tape library, electronic organ kit, and a new i.c. audio amplifier
- INDUSTRY NOTEBOOK** *by Nexus* 167
What's happening inside industry
- READOUT** 178
Quadrasonics sound controversy

Our March issue will be published on Friday, February 8, 1974

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, to any part of the world, £2-65. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

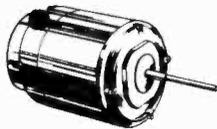"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



MOTOR

Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can

be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC. (synchronous) operation at 120r., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 3/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price **OUR PRICE ONLY £15**

MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/2" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 3/8" bore, plunger non-captive. NEW in original maker's boxes. £1.20. P. & P. 20p. Large number available, special price for quantity.



SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/8"; (80 DB) 3/4" x 5/32" x 1/8". Equipment, all tested. £1.20 each. P. & P. FREE.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged 1" x 1" x 1" bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 1/2" x 1 1/2" x 1 1/2". Travel 1". 90p. each. P. & P. 10p.
240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case)
240 A.C. 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p.
110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant. Ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.


SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 5amp at 120v. 1 1/2amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8; 100 for £16.50. FREE P. & P. over 10.



AMPEX 7.5v. D.C. MOTOR

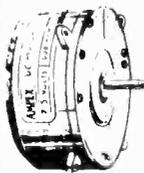


This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available 75p each. FREE P. & P.

ALL PRICES NOW INCLUDE V.A.T. UNLESS OTHERWISE STATED

All items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50 C.W.O., please. Company orders under £2.50, surcharge 60p unless C.W.O.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580

ELECTRO-TECH COMPONENTS LTD.

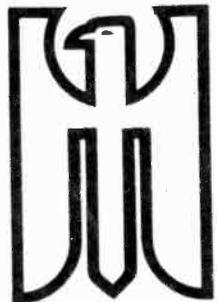

Phoenix Electronics (Portsmouth) Ltd.

139 - 141 Havant Road,
Drayton, Portsmouth, Hants.

afdec


Full member of AFDEC—the industry's association of franchised electronic component distributors. NOW—you can get the same service and range of products normally available to industrial customers. Brand new devices from the industry leaders in component manufacture—large stocks on our shelves. Our prices include VAT at the current rate—and carriage on all goods is free. Send for our catalogue and price list—we'll mail that to you free, too.

Please send your catalogue — free!

Name

Address

.....
.....

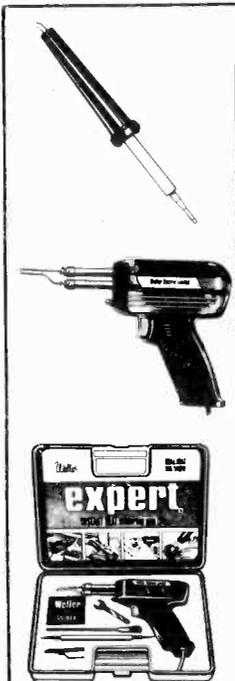

PROFESSIONAL QUALITY SOLDERING FOR EVERYONE!

We are official distributors for Adcola and Weller soldering equipment.

Weller Marksman mains pencils:

SP25D 25W iron £2.00

SP25DK Iron kit, boxed with tips, solder, etc. £2.55

Adcola Invader mains pencils:

L646 23W iron £2.00

Weller Expert soldering guns:

8200D Instant dual-heat gun, mains voltage £5.40

8200DPK Soldering gun kit, with gun, spare tips, spanner, brush, solder, etc. in a smart carrying case £6.50

Adcola solder and braid:

60/40 Solder, BS441, resin-cored, 22 s w g, 30ft approx. £0.12

Type AB Desoldering braid £0.80

We also carry extended ranges of soldering and desoldering equipment, spares, tips, etc. For the real professional, ask for our industrial ranges of temperature-controlled irons, low-voltage equipment, etc.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES
NORMAL HOUSEHOLD
TYPE

EX G.P.O. Only **£1-05_p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.
Only **27 1/2_p** POST & PACKING 16_p

Tested and Guaranteed Paks



- B79 4 IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic 55p
- B81 10 Reed Switches, 1" long 1/2" dia. Highspeed P.O. type 55p
- B99 200 Mixed Capacitors. Approx. quantity, counted by weight Post & packing 15p.
- H4 250 Mixed Resistors. Approx. quantity counted by weight Post & packing 15p.
- H35 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked 55p
- H38 30 Short lead Transistors, NPN Silicon Planar types 55p
- H39 6 Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945 55p
- H41 2 BD131/BD132 Complementary Plastic Transistors 55p



Unmarked Untested Paks

- B1 50 Germanium Transistors PNP, AF and RF 55p
- B66 150 Germanium Diodes Min. glass type 55p
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 55p
- B86 100 Sil. Diodes sub. min. IN914 and IN916 types 55p
- H16 15 Experimenters' Pak of Integrated Circuits. Data supplied 55p
- H20 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts 55p
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can 55p

Make a rev counter for your car

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system. **£1-10_p** each

A Cross Hatch Generator £3-85 post paid

A complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sep. '72 edition of Television.

Electronic Transistor Ignition

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility. This project was a "star" feature in the September 1973 edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

£6-60_p Complete kit incl. V.A.T., P. & P. 11p.
Ready built & tested unit £9-90 inc. V.A.T.

New Paks

Tested & Guaranteed

- H63 4 2N3055 Type NPN Sil. power transistors. Below spec. devices 55p
- H65 4 40361 Type NPN Sil. 55p TO-5 can comp.
- H66 4 40362. Type PNP Sil. transistors TO-5 can comp. to H65 55p
- Untested, Unmarked
- H67 10 3819N Channel FET's plastic 55p case type.

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Silicon Planar Plastic Transistors

Unmarked, untested factory clearance. A random sampling showed these to be of remarkably high quality. Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc. Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9, etc. ALL AT 500 for £3-30, 1,000 for £5-50, 10,000 for £44. P. & P. 11p per 1,000. Please state Audio NPN or Audio PNP when ordering.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" PNP Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR £1-10_p PNP 27_p.

Plastic Power Transistors

NOW IN TWO RANGES



These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min. 15	HFE Min. 15	
	1-12	13-25	26-50
40 watt	22p	20p	18p
90 watt	26 _p	24 _p	22 _p
Range 2	VCE Min. 40	HFE Min. 40	
	1-12	13-25	26-50
40 watt	33p	31p	29p
90 watt	38 _p	36 _p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 AUDIO I.C. as featured in Practical Wireless December issue. Complete with application data, £1-10.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size. 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16_p each } Now new low
16 pin type at 18_p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P. & P. on this Pak.
Please ask for Pak P.1. only 55_p

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....
ADDRESS.....

ALL PRICES INCLUDE 10% V.A.T.
MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg. No B20919

Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344.

RST

VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

	sp	sp	sp	sp	sp				
1N21	0-37	AFZ12	1-50	BYZ10	0-45	OAZ2209	0-40	ZS170	0-10
1N23	0-35	ASY26	0-25	BYZ11	0-40	OAZ2210	0-40	ZS271	0-18
1N85	0-88	ASY27	0-30	BYZ12	0-40	OAZ2211	0-40	ZT21	0-25
1N253	0-50	ASY28	0-25	BYZ13	0-35	OAZ2222	0-45	ZT43	0-25
1N266	0-50	ASY29	0-30	BYZ15	1-25	OAZ2223	0-45	ZTX107	0-18
1N645	0-25	ASY36	0-25	BYZ16	0-30	OAZ2224	0-45	ZTX108	0-10
1N725A	0-20	ASY50	0-20	BYZ88C3V3	0-10	OAZ2241	0-22	ZTX300	0-14
1N914	0-05	ASY51	0-40			OAZ2242	0-22	ZTX304	0-24
1N407	0-20	ASY63	0-20	BZY88C3V3	0-10	OAZ2244	0-22	ZTX500	0-15
18113	0-15	ASY65	0-20			OAZ2246	0-22	ZTX503	0-18
18131	0-18	ASY62	0-25	C111	0-55	OAZ2290	0-22	ZTX531	0-25
18202	0-23	ASY66	0-23	CRS1/05	0-30	OC16	0-25		
2G371	0-40	ASZ21	1-00	CRS1/40	0-45	OC18T	0-33		
2G381	0-25	ARZ23	0-75	CS4B	2-50	OC19	0-50		
2G414	0-30	AU101	1-50	CS10B	3-13	OC20	1-25	7400	0-20
2N404	0-22	AU10	1-00	DD000	1-15	OC22	1-00	7401	0-20
2N697	0-15	AC108	0-12	DD006	0-15	OC23	1-25	7402	0-20
2N698	0-30	AC109	0-12	DD007	0-40	OC24	1-10	7403	0-20
2N706	0-10	BC113	0-15	DD008	0-30	OC25	0-50	7404	0-20
2N706A	0-12	BC115	0-20	GD3	0-33	OC28	0-35	7405	0-20
2N708	0-15	BC116	0-20	GD4	0-10	OC29	0-65	7406	0-40
2N709	0-40	BC116A	0-23	GD5	0-33	OC30	0-50	7407	0-40
2N1091	0-55	BC118	0-15	GD8	0-25	OC35	0-55	7408	0-25
2N1131	0-25	BC121	0-20	GD12	0-10	OC36	0-65	7409	0-20
2N1132	0-25	BC122	0-20	GE1102	0-50	OC41	0-50	7410	0-20
2N1302	0-18	BC125	0-68	GE1103	0-40	OC42	0-40	7411	0-22
2N1303	0-15	BC125	0-68	GE1113	0-35	OC43	0-70	7412	0-22
2N1305	0-22	BC140	0-55	GE1114	0-30	OC44	0-18	7413	0-20
2N1306	0-22	BC147	0-12	GE1115	0-75	OC44M	0-17	7416	0-30
2N1307	0-28	BC148	0-10	GE1116	0-85	OC45	0-18	7417	0-20
2N1308	0-28	BC149	0-12	GE1120	0-60	OC45M	0-18	7420	0-20
2N148	0-75	BC167	0-15	GE1122	0-30	OC46	0-27	7422	0-22
2N1610	0-61	BC169	0-12	GE1125	0-40	OC57	0-60	7423	0-40
2N2128	0-23	BCY31	0-45	GET880	0-55	OC58	0-60	7425	0-37
2N2219	0-25	BCY32	0-55	GET881	0-25	OC59	0-60	7427	0-27
2N2369A	0-16	BCY33	0-35	GET882	0-35	OC66	0-50	7428	0-20
2N2444	1-89	BCY34	0-25	GET885	0-35	OC70	0-18	7432	0-37
2N2446	0-25	BCY38	0-55	GET886	0-35	OC71	0-15	7433	0-48
2N2494	0-50	BCY39	1-00	GEX44	0-08	OC72	0-25	7437	0-43
2N2904	0-20	BCY40	0-80	GEX45	0-45	OC73	0-50	7438	0-48
2N2904A	0-25	BCY42	0-30	GEX941	0-45	OC74	0-30	7440	0-20
2N2906	0-20	BCY70	0-15	GEX941	0-45	OC75	0-30	7441A	0-25
2N2924	0-22	BCZ10	0-60	GJ3M	0-38	OC76	0-30	7442	0-85
2N2925	0-15	BCZ11	0-65	H8100A	0-20	OC79	0-80	7450	0-20
2N2926	0-10	BD121	1-00	MAT100	0-20	OC81	0-28	7453	0-20
2N3054	0-45	BD123	1-00	MAT101	0-25	OC81D	0-28	7454	0-20
2N3055	0-45	BD124	0-80	MAT120	0-20	OC81M	0-20	7459	0-20
2N3702	0-11	BDY11	1-45	MAT121	0-25	OC81DM	0-18	7472	0-38
2N3706	0-11	BF171	0-22	MJE520	0-65	OC82	0-28	7473	0-44
2N3707	0-13	BF172	0-22	MJE2953	1-10	OC82	0-28	7474	0-48
2N3709	0-10	BF173	0-25	NKT3055	0-75	OC82D	0-25	7475	0-59
2N3710	0-11	BF181	0-33	NKT128	0-45	OC83	0-25	7476	0-59
2N3711	0-11	BF184	0-22	NKT129	0-30	OC84	0-25	7477	0-45
2N3819	0-35	BF188	0-22	NKT211	0-25	OC114	0-38	7482	0-87
2N5027	0-55	BF192	0-20	NKT213	0-25	OC122	0-22	7483	1-20
2N5088	0-23	BF193	0-13	NKT214	0-24	OC123	1-10	7484	1-00
2S301	0-50	BF196	0-15	NKT216	0-40	OC139	0-40	7486	0-50
2S304	1-15	BF197	0-15	NKT217	0-20	OC140	0-65	7488	0-50
2S501	0-37	BF881	0-25	NKT218	1-13	OC141	0-80	7489	0-75
AA129	0-20	BF598	0-25	NKT219	0-33	OC169	0-20	7492	0-75
AAZ13	0-10	BFX13	0-25	NKT220	0-30	OC170	0-25	7493	0-75
AC107	0-25	BFX29	0-28	NKT224	0-35	OC171	0-30	7494	0-85
AC126	0-25	BFX30	0-28	NKT227	0-20	OC200	0-55	7495	0-85
AC127	0-25	BFX33	0-28	NKT271	0-20	OC201	0-80	7495	1-00
AC128	0-25	BFX35	0-28	NKT272	0-20	OC202	0-80	7496	1-00
AC187	0-25	BFX63	0-50	NKT273	0-20	OC203	0-55	7497	4-32
AC188	0-20	BFX87	0-28	NKT274	0-20	OC204	0-65	74107	0-61
ACX17	0-25	BFX87	0-25	NKT275	0-25	OC205	1-00	74110	0-57
ACX18	0-27	BFX88	0-22	NKT277	0-20	OC206	1-00	74111	0-86
ACX19	0-27	BFY10	1-00	NKT278	0-25	OC207	1-00	74111	0-87
ACX20	0-22	BFY11	1-25	NKT403	0-70	OC208	0-20	74118	1-92
ACX21	0-22	BFY12	0-20	NKT404	0-60	OC209	0-80	74121	1-00
ACX22	0-15	BFY18	0-45	NKT407	0-80	ORP11	0-65	74122	1-44
ACX27	0-25	BFY19	0-55	ORP12	0-65	ORP60	0-45	74123	1-44
ACX28	0-25	BFY24	0-45	ORP61	0-48	ORP61	0-48	74141	1-00
ACX39	0-65	BFY44	1-00	S19T	0-30	S19T	0-30	74143	1-44
ACY40	0-22	BFY50	0-20	SAC40	0-25	SAC40	0-25	74150	2-30
ACY41	0-22	BFY51	0-20	SFT308	0-38	SFT308	0-38	74151	1-15
AD140	0-50	BFY53	0-17	ST72	0-38	ST72	0-38	74155	1-15
AD149	0-50	BFY60	0-45	ST7231	0-68	ST7231	0-68	74156	1-15
AD161	0-39	BFY90	0-75	OX58	0-20	OX58	0-20	74157	1-09
AD162	0-39	B8X27	0-60	OX631	0-45	OX631	0-45	74157	1-09
AD166	0-30	B8X60	0-88	OX641	0-75	OX641	0-75	74174	1-80
AD114	0-25	B8X76	0-18	OX642	0-60	OX642	0-60	74176	1-44
AD116	0-25	B8Y26	0-18	OX645	0-85	OX645	0-85	74190	2-30
AD118	0-25	B8Y27	0-18	OX646	0-75	OX646	0-75	74191	2-30
AD119	0-25	B8Y28	0-18	OX647	0-75	OX647	0-75	74192	2-30
AD117	0-20	B8Y31	0-50	OX648	0-75	OX648	0-75	74193	2-30
AD118	0-50	B8Y50A	0-12	OX649	0-75	OX649	0-75	74194	1-72
AD119	0-20	B8Y95	0-12	OX650	0-75	OX650	0-75	74195	1-44
AD124	0-30	BT102/5000	0-75	OX651	0-75	OX651	0-75	74195	1-44
AD126	0-30	BT102/5000	0-75	OX652	0-75	OX652	0-75	74196	1-68
AD126	0-30	BT102/5000	0-75	OX653	0-75	OX653	0-75	74197	1-58
AD126	0-30	BT102/5000	0-75	OX654	0-75	OX654	0-75	74198	3-16
AD126	0-30	BT102/5000	0-75	OX655	0-75	OX655	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX656	0-75	OX656	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX657	0-75	OX657	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX658	0-75	OX658	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX659	0-75	OX659	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX660	0-75	OX660	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX661	0-75	OX661	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX662	0-75	OX662	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX663	0-75	OX663	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX664	0-75	OX664	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX665	0-75	OX665	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX666	0-75	OX666	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX667	0-75	OX667	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX668	0-75	OX668	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX669	0-75	OX669	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX670	0-75	OX670	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX671	0-75	OX671	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX672	0-75	OX672	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX673	0-75	OX673	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX674	0-75	OX674	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX675	0-75	OX675	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX676	0-75	OX676	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX677	0-75	OX677	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX678	0-75	OX678	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX679	0-75	OX679	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX680	0-75	OX680	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX681	0-75	OX681	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX682	0-75	OX682	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX683	0-75	OX683	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX684	0-75	OX684	0-75	74199	2-88
AD126	0-30	BT102/5000	0-75	OX685	0-75	OX685	0-75	74199	2-88
AD126	0-30	BT102/5000							

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! THIS ONE is **SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! Send quickly, test on mail order 7 day approval from receipt of goods! THIS ONE is **UNBEATABLE!** Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread for absolute "pinpoint" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space-ship and satellite communications. Yes, EVERY WAVE-BAND instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF: FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39" in approx. It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 13in x 10in x 4 1/2in overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!) With WRITTEN GUARANTEE, manual with simple operating instructions & circuit diagram. PLUS ultra sensitive earphone for personal listening. ONLY £18.50 (with mains/battery eliminator £22.25 extra) BOX, POST, ETC. 45p. **NO MORE TO PAY!** *BUT WAIT, for only 75p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE (it enables you to zone and time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. NO GUESSING! NO MESSING!) PLUS Standard "longlife" batteries and Converter Plug. (Sorry—We cannot change these new radios for any earlier model already purchased.) Send quickly to Uxbridge Road address, or call at either Store. **HURRY!** SHOPERTUNITIES SAVE YOU £££'s & £££'s!

THOUSANDS OF MILES REDUCED TO INCHES? LATEST RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?



THIS FANTASTIC EARTH SHRINKER

YES, 24,901 miles
SHRUNK TO ONLY 13" x 10" x 4 1/2"
inches approx?

28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BRAND NEW FABULOUS ASTRAD 17 PORTABLE RADIO & COMMUNICATIONS RECEIVER



***MUST YOU PAY UP TO £80?**

FIRST TIME EVER!
*NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!
NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to ZONE & TIME IN A FLASH for transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £23.03 NOW!**

Fabulous BRAND NEW **SOLID STATE** This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

OUR PRICE £20.97 CARR. ETC. 50p

RECOMMENDED RETAIL PRICE

Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord). Record and play back anything, anywhere! IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE! Wonderful features: * Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL! * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or 'monitoring') and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££ more for a Car Radio or Car Cassette player ALONE! £20.97, carr. etc., 50p—NO MORE TO PAY! Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE. Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required. Callers ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES

FIRST TIME EVER! *SAVE £16.02!

BRAND NEW AC/DC BATTERY/MAINS **Cassette TAPE RECORDER & PLAYER**

WITH remote control microphone.

FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!

OUR PRICE £10.95 POST ETC. 50p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de-luxe portable BATTERY/MAINS tape recorder and player—and incredible Shopertunities bring it to you for ONLY £10.95. Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes, obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2in x 5 1/2in x 2 1/2in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. (Importers recommended selling price £26.97!) **OUR PRICE ONLY £10.95**, post, etc. 50p. **NO MORE TO PAY!** Send and Test, on mail order 7 day approval from receipt of goods—refund if not delighted. Or call at either of our stores. **BONUS OFFER** (Rationed one per customer)—Cassette tape, Standard batteries AND microphone stand 55p extra if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores.—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn Store.)

SHOPERTUNITIES LTD.

Dept. PE/NC/35, 164 UXBIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AG. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's
**LARGEST RANGE
 OF KITS &
 GADGETS**



TEST EQUIPMENT MULTIMETERS

- (Carr., etc. 30p)
 M210 20k/V Spline, £6.75
 T4133D 2k/V Robust, £7.50
 U437 10k/V Steel case, A.C. up to 40kHz, £4.95
 U4324 20k/V with A.C. current ranges, £8.00
 AF105 50k/V, £11.95
 U4313 20k/V A.C. current. Steel case, £10.50
 U4341 Plus built in transistor tester, £10.50
Model 500 30k/V, £9.95
- OTHER EQUIPMENT**
 SE250B Pocket Signal Injector, £2.10, Carr. 15p
 SE500 Pocket Signal Tracer, £1.70, Carr. 15p
 TE15 Grid Dip Meter 440kHz-280MHz, £15.00, Carr. 30p
 TE40 A.C. Millivoltmeter 1-2MHz, £18.95, Carr. 35p
 TE65 28 Range Valve Voltmeter, £19.95, Carr. 40p
 TE20D 120kHz-500MHz RF Generator, £17.95, Carr. 40p
 TE22D 20Hz-200kHz Audio Generator, £18.95, Carr. 40p
 SE350A Deluxe Signal Tracer, £12.50, Carr. 20p
 SE400 Volts/ohms/R.C. sub./RF field/RF gen., £14.75, Carr. 20p


New Revolutionary Superstret 680R

- 680R Multi-tester, £18.50
- | Accessories | £11.00 |
|----------------------|--------|
| Transistor tester | £18.00 |
| Electronic voltmeter | £11.95 |
| Amplamp | £11.95 |
| Temperature probe | £11.95 |
| Gauss meter | £5.95 |
| Signal injector | £5.95 |
| Phase sequence | £5.95 |
| EHT Probe | £4.50 |
| Shunts | £4.50 |
| 25.50/100A | each |

- A SELECTION OF INTERESTING ITEMS**
 C3025 Compact transistor tester, £6.30, P. & P. 15p
 E1300 Mono mag cart preamp, £2.75, P. & P. 15p
 E1310 Stereo mag cart preamp, £4.62, P. & P. 25p
 Esiphone telephone amplifier, £7.95, P. & P. 25p
 D1203 Teleamp with PU coil, £4.40, P. & P. 20p
 LL1 Door Intercomm. and chime, £7.95, P. & P. 25p
 Chatalite (lights as you talk), £13.90, P. & P. 20p
 1kV Dimmer-controller, £3.00, P. & P. 10p
 9in Twin spring unit, for Reverbs, £3.30, P. & P. 15p
 16in Twin spring unit, for Reverbs, £6.85, P. & P. 25p
 Car Tachometer electronic, £8.95, P. & P. 15p
 VHF Aircraft band corrector, £4.50, P. & P. 15p
 B2005 4 Ch. mic. mixer, £3.75, P. & P. 15p
 B2004 2 Ch. stereo mixer, £5.95, P. & P. 15p
 BK3 Kit. Etch your own printed circuits, £1.50, P. & P. 20p

BUILD THIS RADIO

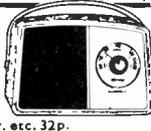PORTABLE MW/LW RADIO KIT using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600mW output. All parts £7.98 (battery 22p). Carr. etc. 32p.



EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO + or - earth with speaker and fixings. £6.50 carr/pack. 30p
- 8 TRACK CAR STEREO** (- earth) with speakers, in pods and fixings. £12.50 carr/pack. 40p
- HANIMAX HC1000 battery cassette recorder, £10.50 carr/pack. 25p
- HANIMAX HC2000 battery/mains cassette recorder, £13.50 carr/pack. 30p
- AKAI GCX40 stereo cassette recorder, £59.95 carr/pack. 50p
- Pair Akai ADM microphones, £6.95 carr/pack. 20p
- WAVEBAND PORTABLE TWIN SPEAKER RADIO** FM/MW/SW/ AIR-CRAFT — PUBLIC SERVICES. £10.45 carr/pack. 30p.
- P O R T A B L E CASSETTE TAPE PLAYER** — for car or carry around. £7.25 carr/pack. 20p.
- HANIMAX BC808 POCKET CALCULATOR with % key. £28.95.

SPECIAL PURCHASES

- AVOMETER MOVEMENTS**
 AVO 8 or 9 50mA MOVEMENTS. Ex Brand New AVO's. £3.50, Post 20p.
- UHF TV TUNERS CHANNELS 21 to 64**
 Brand new transistorised geared tuners for 625 Line Receiver IF output. £2.50, Post 20p.



EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

- | Model No. | £ |
|--|-------|
| 310 Radio control receiver | 2.98 |
| 300 4-channel R/C transmitter | 5.95 |
| 345 Superhet R/C receiver | 5.95 |
| 455 AM signal generator | 12.33 |
| 65 Simple transistor tester | 1.40 |
| 115 8W amplifier | 3.90 |
| 120 12W amplifier | 4.70 |
| 125 Stereo control unit | 5.70 |
| 130 Mono control unit | 4.50 |
| 605 Power supply for 115 | 6.05 |
| 610 Power supply for 120 | 4.55 |
| 615 Power supply for 2 x 120 | 5.73 |
| 230 AM/FM aerial amplifier | 2.93 |
| 240 Auto packing light | 5.90 |
| 275 Mic. preamplifier | 6.08 |
| 570 LF generator 10Hz-1mHz | 15.80 |
| 575 Sq. wave generator 20Hz-20kHz | 14.60 |
| 590 SWR meter | 12.85 |
| 620 Ni-CAD Charger 1.2-12V (-Ve Earth) | 8.00 |
| 630 STAB. Power supply 6-12V 0.25-0.1A | 8.15 |
| 690 D.C. motor speed Gov. | 2.87 |
| 700 Electronic Chaffinch | 7.00 |
| 705 Windscreen wiper timer | 6.80 |
| 760 Acoustic switch | 10.75 |
| 780 Metal Detector (electronics only) | 9.65 |
| 790 Capacitive burglar alarm | 6.85 |
| 835 Guitar preamp | 4.25 |
| 840 Delay car alarm | 6.15 |
| 875 CAP. Discharge ignition for car engine | 13.15 |
| 80 Scope calibrator | 2.25 |
| 255 Level indicator | 6.15 |
| 525 120-160MHz VHF timer | 11.30 |
| 715 Photo cell switch | 7.70 |
| 795 Electronic continuity tester | 4.30 |
| 860 Photo timer | 13.25 |
| 871 Slide projector auto feed control | 7.15 |
| 235 Acoustic alarm for driver | 7.60 |
| 465 Quartz XTAL checker | 8.75 |
| 220 Signal Injector | 2.30 |
| 390 VOX | 15.50 |
| 432 Testkit | 19.30 |
| 670 Buffer Battery Charger | 6.55 |
| 885 Capacitive Contact Alarm | 6.25 |
| 850 Electronic Keyer | 18.75 |
| 820 Electronic Digital Clock | 58.50 |

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY
 Prices correct at time of preparation, subject to change without notice.


BUILD THIS TUNER

MW/LW Radio tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built-in battery. Excellent results. Size: 7in x 2½in x 3½in. All parts £4.85, Carr. 15p.

MULTI-USE AND RADIONIC KITS

- | | £ |
|-----------------------------------|-------|
| 10-1 10 Projects | 3.60 |
| 50-1 50 Projects | 8.00 |
| 150-1 150 Projects | 13.20 |
| Telephone Communicator X20 (Elec) | 7.20 |
| X40 (radio) Projects | 4.95 |
| (Carr./Packing 40p) | 9.45 |
- ALL TRANSISTOR CIRCUITS WITH HANDBOOKS**

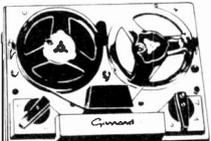All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT to be ADDED TO ALL ORDERS. UK post, etc. 15p per order unless stated.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted recorder/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4in spools. Brand new complete with head circuits. £9.50, Carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).
 Singles Log and Lin
 E1210 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1 Meg. 45p each.
 Ganged Log and Lin
 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 65p each.
 (Quantity discounts available). Complete with knobs.

MARRIOT TAPE HEADS


4 TRACK MONO or 2 TRACK STEREO
 '17' High Impedance, £2.00; Erase Heads for '17' and '18'. 75p; '63' 2 track mono. Hi Imp., £1.75; '43' Erase Head for '63'. 75p. (Post, etc. 15p any quantity).
 R730/E73 2 Track Mono Record Erase Low Imp., 75p pair.

SINCLAIR, MINIATURE AMPLIFIERS AND TUNER/DECODER

- AMPLIFIERS** (Carr. etc. 20p).
- | | |
|--|-------|
| 4-300 0.3 watt 9 volt | 1.75 |
| 104 1 watt 9 volt | 2.80 |
| 304 3 watt 9 volt | 2.95 |
| 555 3 watt 12 volt | 3.10 |
| E1208 5 watt 12 volt | 5.10 |
| 608 10 watt 24 volt | 4.10 |
| 410 10 watt 28 volt | 4.95 |
| E1206 30 watt 45 volt | 9.95 |
| E1210 24+24 watts 12 volt | 6.25 |
| RE500 5 watt IC mains operated Amplifier with controls | 6.30 |
| SAC14 7 + 7 watt Stereo with controls | 8.70 |
| SAC30 15 + 15 watt Stereo with controls | 11.75 |
- SINCLAIR PROJECT 60** (Carr. 20p)
- | | | |
|------------------------|-----|------|
| Z30 3-57 | Z50 | 4.37 |
| Stereo 60 Preamplifier | | 7.97 |
| PZ5 | | 3.97 |
| PZ6 | | 6.37 |
| PZ8 (for Z50) | | 4.77 |
| TRANS. | | 2.95 |
| AFU | | 4.45 |

NEW SINCLAIR PROJECT 80

- | | |
|--------------------------------|--------|
| Stereo Preamplifier | £11.95 |
| Audio Filter Unit | 6.95 |
| Z40 15 Watt Amplifier | 5.45 |
| Z60 25 Watt Amplifier | 6.95 |
| PZ5 Model for 1 on 2 Z40 | 4.98 |
| PZ6 Model (S. Tab.) 1 on 2 Z40 | 7.98 |
| PZ8 Model (S. Tab.) 1 on 2 Z60 | 7.98 |
| TRANSFORMER FOR PZ8 | 2.95 |
| Project 605 Kit | 19.95 |

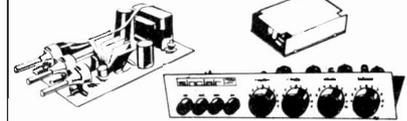

POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 67½/9V 300mA. (Includes Multi-Adaptor for Tape Recorders, etc.). £2.15, Post 20p
- Car Lighter Voltage Adaptors 300mA (State Voltage 6V, 7½V, 9V). £1.95 each. Post 25p
- SC202 3/67½/9V 400mA, £3.35, Carr. 30p
- HC24R Stabilised version, £4.35, Carr. 30p
- P500 9V 500mA, £2.90, Post 20p
- P11 24V 500mA (chassis), £2.90, Post 20p
- P15 26/28V 1 amp (chassis), £2.90, Post 20p
- P180 12V 1 amp (chassis), £4.25, Post 20p
- P1081 45V 0.9 amp (chassis), £7.50, Post 20p
- P12 44-12V 0.4-1 amp, £7.15, Post 30p
- SE101A 3/67½/12V 1 amp (Stab.), £10.30, Post 25p
- RP164 67½/9/12 1 amp (Stab.), £10.20, Post 30p



FIBRE OPTICS

- 0.01 dia. Mono Filament, £1.50 per 25 metre reel.
 0.13 dia. 64 Fibres Sheathed, £1.00 per metre.
 SPRAYS 15mm dia. Mares Tail, £9.50.



Henry's RADIO LIMITED

SEE FACING PAGE FOR ADDRESSES

EDGWARE ROAD, W2


Henry's

UK'S LARGEST RANGE OF TRANSISTORS, IC'S RECTIFIERS, ALL SEMICONDUCTOR DEVICES
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL



FREE BOOKLET

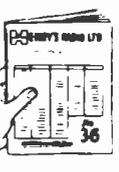All types of TRANSISTORS · RECTIFIERS BRIDGES · SCR'S · TRIACS INTEGRATED CIRCUITS F.E.T. · LIGHT DEVICES OVER 1500 DIFFERENT DEVICES ENTIRELY NEW 1973 EDITION **SEND FOR YOUR FREE COPY TODAY!**



MORE DEVICES NEW PRICES NEW RANGES THIS IS A MUST FOR ALL SEMI-CONDUCTOR USERS!

(ask for Booklet No. 36)

INTEGRATED CIRCUITS, VERY IMPORTANT—ONLY BRANDED IC'S ARE TO THE FULL MANUFACTURERS' SPECIFICATIONS. ALL OTHERS ARE NOT. HENRY'S SELL ONLY BRANDED INTEGRATED CIRCUITS FROM TEXAS... I.T.T. ... FAIRCHILD ... SIGNETICS ... SO WHY BUY ALTERNATIVES OR UNDER SPEC. DEVICES WHEN YOU CAN PURCHASE THE GENUINE ARTICLE FROM US EX STOCK ... NEED WE SAY MORE!

Type	1-	12-	30-	Type	1-	12-	30-
8N7400N	20	18	16	8N7446N	2-16	2-18	1-89
8N7401N	20	18	16	8N7447AN	1-80	1-80	1-67
8N7401AN	38	38	38	8N7448N	1-50	1-27	1-18
8N7402N	20	18	16	8N7450N	20	18	16
8N7403N	20	18	16	8N7451N	20	18	16
8N7403AN	38	38	38	8N7453N	20	18	16
8N7404N	24	21	18	8N7454AN	20	18	16
8N7405N	20	18	16	8N7456N	20	18	16
8N7406AN	44	44	38	8N7470N	33	30	27
8N7408N	40	38	35	8N7472N	38	37	34
8N7407N	40	38	35	8N7473N	44	41	37
8N7408N	25	22	19	8N7474AN	48	48	42
8N7409N	38	38	28	8N7475N	59	55	51
8N7409AN	44	44	38	8N7476N	45	36	32
8N7410N	20	18	16	8N7480N	80	70	50
8N7411N	25	23	21	8N7481N	1-25	1-10	95
8N7412N	28	28	25	8N7482N	87	80	72
8N7412AN	38	38	33	8N7483N	1-20	1-10	1-00
8N7413N	30	27	25	8N7485N	1-87	1-87	1-63
8N7414N	72	72	68	8N7486N	50	50	44
8N7416N	30	27	25	8N7489N	4-32	4-32	3-78
8N7417N	30	27	25	8N7490N	75	70	63
8N7420N	28	28	25	8N7491AN	1-10	1-10	95
8N7422N	28	28	25	8N7492N	75	70	63
8N7422AN	38	38	33	8N7493N	75	70	63
8N7423N	37	34	32	8N7494AN	85	80	75
8N7426N	37	37	32	8N7495N	85	80	75
8N7427N	37	37	32	8N7496N	1-00	90	88
8N7428N	48	48	37	8N74100N	2-16	1-89	1-89
8N7430N	20	18	16	8N74101AN	60	60	53
8N7432N	37	37	32	8N74105N	60	53	45
8N7433N	48	48	38	8N74107N	51	51	45
8N7433AN	47	47	50	8N74110N	57	57	50
8N7437N	53	53	57	8N74111N	86	86	76
8N7438N	48	48	37	8N74116N	2-16	2-18	1-89
8N7438AN	57	57	50	8N74118N	1-00	90	89
8N7440N	20	18	16	8N74119N	1-92	1-92	1-88
8N7441AN	85	79	73	8N74120N	1-05	1-05	92
8N7442N	85	79	73	8N74121N	57	57	50
8N7443N	1-50	1-27	1-13	8N74122N	80	80	70
8N7444N	1-50	1-27	1-13	8N74123N	1-44	1-44	1-28
8N7446N	2-16	2-16	1-89	8N74125N	69	69	60

PRICING OF 8N7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
 SN74 (HIGH POWER), SN74 (LOW POWER) series in stock. Send for List 36 free on request. Low Profile Sockets. 14 pin, 15p, 16 pin, 17p, 8 pin, 14p.

TRANSISTORS—A selection

For full list send for booklet 36 today

£ p	14	14	14	14	14	14	14
AAZ13	10	BC169C	14	BY100	15	OC36	65
AC107	35	BC182	12	BY127	15	OC44	18
AC128	20	BCY32	85	BYZ13	35	OC45	18
AC187	20	BCY39	1-00	CI06D	55	OC71	15
ACY17	35	BCY55	2-50	GET111	55	OC72	25
ACY39	65	BCY70	1-50	GET115	75	OC77	25
AD149	50	BCY71	20	GET880	55	OC81	28
AD161	39	BCY72	13	LN309K1	87	OC83	25
AD162	39	BD124	80	MAT121	25	OC140	65
AF117	20	BF159	45	MIE340	50	TIL209	25
AF118	50	BF115	22	MJE520	65	OC200	55
AF139	33	BF180	33	MJE3055	75	OC202	90
AF186	40	BF194	13	MPF105	45	OC271	1-00
AF239	44	BFX13	25	NKT217	45	ORP12	55
ASV27	30	BFX34	25	NKT404	60	ORP60	45
BA115	10	BFX88	22	OA5	60	PF346	70
BA113	20	BFY59	45	OA200	80	TIP29A	49
BC107	15	BFY51	20	OA200	80	TIP29A	49
BC108	15	BFY64	45	OA202	10	TIP30A	58
BC109	15	BFY90	75	OC16	85	TIP31A	61
BC109C	14	BLY36	6-25	OC20	1-25	TIP41A	74
BC113	16	BSX20	15	OC28	65	TIP42A	90
BC147	12	BU105	2-20	OC35	55	TIS43	26

All types offered subject to availability. Prices correct at time of press. E. & O.E.

TBA 800 5 WATT I.C.
 Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output.
 With circuits and data £1-50.



SINCLAIR IC12
 With circuits and data. 6 W IC with printed circuit board 28V operated, £1-80.




ZN414 IC
 Integrated circuit radio as featured by many magazines. (PW Jan. 73 Reprint Ref. No. 19 for 10p), £1-20.



STROBE TUBE ZFT4A/XTF5
 Suitable for Dec. 73 Pract. Electronics. £2-50
ST2 (D32) DIAC 25p
CRS1/40 SCR 45p



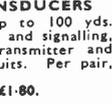ULTRASONIC TRANSDUCERS
 Operate at 40KHz up to 100 yds. Ideal remote switching and signalling, complete with data transmitter and receiver, new I.C. circuits. Per pair, £5-90
TA 960 I.C. with socket £1-80.



3015F 7 SEC.
 IC size complete with data price £1-70 each. (Digital clock circuits Ref. No. 31, 15p).



TRANSISTORS—SPECIAL OFFERS

2N3055	BY127
25 47p each	25 12p each
100 42p each	100 10p each
500 39p each	500 9p each
1000 34p each	1000 8p each

ZENER DIODES

400m/w BZY88/BZX83.	1-3V 5% Miniature tubulars	IN4700 series.	From 3-3V—33V, 18p each.	10W. Std. Mounting ZS series 6-8V—100V 5%, 40p each.
702C (T05) 75	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	747C (T09) 1-00
709C (T05) 39	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	747C (DIL) 1-00
709C (DIL) 39	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	748C (DIL) 61
723C (T09) 90	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	
723C (DIL) 90	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	
723C (DIL) 90	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	
723C (DIL) 90	728C (DIL) 90	741C (T05) 50	741C (DIL) 50	

SILICON RECTIFIERS
 IN4001 to IN4007. From 6p each.
 1-5 amp. PL4001 to PL4007. From 8p each.
 3 amp. PL7001/IN5400. From 14p each.
 Send for full list 36.

SEMI-QUANTITY DISCOUNTS
 10% 12+, 15%, 25+, 20% 100+
 All one type except where quantity discounts shown.
 Min. order £1-00 please.

MORE OF EVERYTHING AT HENRY'S
 See pages 110, 111 and Back Cover of this magazine.
BEST VALUE

100% VAT TO BE ADDED TO ALL ORDERS

TRIACS—Stud Mounting with accessories
3 AMP RANGE 1-11
 Type P.I.V. Price ea.
 SC35A 100V 80p
 SC35B 200V 85p
 SC35D 400V 90p
 SC35E 500V £1-20

6 AMP RANGE 90p
 SC40A 100V 90p
 SC40B 200V 95p
 SC40D 400V £1-20
 SC40E 500V £1-50

10 AMP RANGE £1-05
 SC45A 100V £1-05
 SC45B 200V £1-15
 SC45D 400V £1-45
 SC45E 500V £1-85

15 AMP RANGE £1-45
 SC50A 100V £1-45
 SC50B 200V £1-65
 SC50D 400V £1-95
 SC50E 500V £2-25

TRIACS—Additional Types
 40430 TRIAC (T066) 85p
 40669 TRIAC (Plastic) 90p
 40486 TRIAC (T05) 75p

NEW RANGES BRIDGE RECTIFIERS FEATURES SMALL SIZE & LOW COST
 250 mA / 4 AMP P.I.V.
 B05/05 50V 16p
 B05/10 100V 18p
 B05/20 200V 23p
 B05/40 400V 25p
 B05/60 600V 27p

1 AMP P.I.V. Price ea.
 B05/05 50V 25p
 B1/10 100V 25p
 B1/20 200V 28p
 B1/60 600V 30p

1 AMP P.I.V. Price ea.
 W005 50V 29p
 W01 100V 30p
 W02 200V 32p
 W06 600V 35p

1 AMP P.I.V. Price ea.
 B2/05 50V 35p
 B2/10 100V 40p
 B2/20 200V 45p
 B2/60 600V 55p
 B2/100 1000V 55p

4 AMPS P.I.V. Price ea.
 B4/100 100V 55p
 B4/200 200V 59p
 B4/400 400V 65p
 B4/600 600V 75p
 B4/800 800V £1-00

6 AMPS P.I.V. Price ea.
 B6/05 50V 65p
 B6/10 100V 70p
 B6/20 200V 80p
 B6/40 400V 90p
 B6/60 600V £1-00

SILICON CONTROLLED RECTIFIERS
Type 1 AMP (T05) P.I.V.
 CRS 1/05AF 50V 30p
 CRS 1/10AF 100V 30p
 CRS 1/20AF 200V 35p
 CRS 1/40AF 400V 55p
 CRS 1/60AF 600V 55p

3 AMP (T048) P.I.V.
 CRS 3/05AF 50V 40p
 CRS 3/10AF 100V 40p
 CRS 3/20AF 200V 45p
 CRS 3/40AF 400V 55p
 CRS 3/60AF 600V 65p
5 AMP CRS 4/00V 60p
5/400V 60p

7 AMP (T048) P.I.V.
 CRS 7/100 100V 60p
 CRS 7/200 200V 67p
 CRS 7/400 400V 85p
 CRS 7/600 600V 95p

Henry's RADIO LIMITED
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 203 Edgware Road, London W2 1BW

Open:-
 9 am-6 pm
 6 days a week
 All stores open all day Saturday

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses. This budget system compares very favourably with the more sophisticated and much higher priced models. Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15; 6in Liquid Wheel, £5 = £20 + 75p carr.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2½in. x 3½in. x 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.

MINI LOUDSPEAKERS

2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £29.50 + 50p P. & P. Please send S.A.E. if you require more information.

VAT

Please include 10% VAT on goods plus carriage.

200/250V MAINS RELAY
Heavy duty contacts, 2,500 Ω coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.

CRESCENT "C.300" DISCO CONTROL PACK

A control unit which when connected to twin decks makes a disco of professional quality. We supply a smart front panel which incorporates controls, switch and input sockets. The control module, I.C. construction incorporating mixing, pre-amp and headphone listening amplifier. The power pack enables this unit to work from the standard mains. * Inputs include Mic., Tape/Cassette and Twin Decks. * Controls include Mic., Tape, Each Deck,

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.B.U.I.D.17

We supply the three modules for you to build this Disco Group-P.A. amplifier into the cabinet of your choice. ★ THE POWER AMP MODULE TP100W 170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). £14.28, carr. 45p. ★ THE PRE-AMP MODULE Four control pre-amp, Vol., Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £3.96, carr. 25p. ★ THE POWER SUPPLY MODULE PS100 is supplied complete with the mains transformer. £2-86, carr. 50p. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules. £25, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

CRESCENT CATALOGUE

If you construct you should own one
Send 20p, inc. carriage

EMI LOUDSPEAKER 450
10W 13in x 8in ± two 2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp.
£3.75 plus 38p P. & P. each.

7in x 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38 000. Max. Freq. range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.



CRESCENT CASSETTES
Top quality cassettes at unbeatable prices (complete with standard storage case): C60 25p, C90 38p, C120 48p plus 5p P. & P.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 260V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed)
£18.50 plus 38p P. & P.

If you require more information please send S.A.E.



"CRESCENT BEAT BRITTE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4" x 3" x 2½" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a recorder player, baby alarm, etc., amplifier.



£1.75 plus 13p P. & P.

KEEP WARM AT A COOL PRICE.

Slash central heating costs with AMKIT.

If you can put in electric wiring, you can install Amkit. The unique nylon pipe hot water central heating system, that you install yourself in hours.

Look at these advantages:

- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To Autocon Manufacturing Co.
Spring House, 10, Spring Place, London, NW5, 3BH
Please send your brochure telling me all about Amkit.


Name
Address



or see for yourself at: THE AMKIT D.I.Y. CENTRE,
15, Procter St., London, W.C.1. (opp Holborn Undgnd).
Open. Mon-Fri 9.30 am-5.30 pm. Sat 9 am-1 pm.

PHOTOELECTRIC KIT

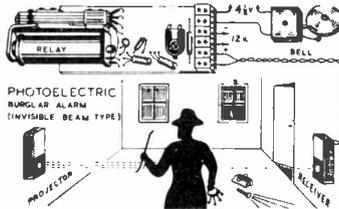CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



PHOTOELECTRIC KIT £2-85

Postage and Pack. 15p (U.K.)
Commonwealth
SURFACE MAIL 25p
AIR MAIL £1.40
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photoelectric Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1.15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.

CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4-75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p. Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT

Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.


CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3-25, postage and pack. 15p (U.K.). Commonwealth: Surface 25p. Air Mail 75p.

YORK ELECTRICS Mail Order Dept.
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

NEW EDU-KIT MAJOR

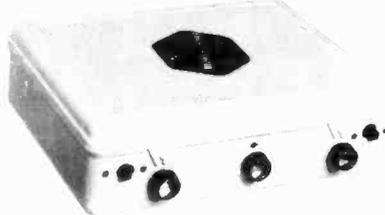COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



TOTAL BUILDING COSTS

£7-23 P.P. & INS. 44p
(Overseas P.P. £1-85p)
(+10% VAT 72p)

Components include:

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN —PNP
- 4 Transistor Push Pull Amplifier
- 6 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio.
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 31 Loudspeaker
- Earpiece
- Mica Baseboard
- 3 12-way Connectors
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 6j yards of wire
- 1 yard of sleeving, etc.
- Parts price list and plans 50p (free with parts)

NEW ROAMER NINE


WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and 8W. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2in x 7in x 2 1/2in approx. Parts price list and plans 80p (FREE with parts).

TOTAL BUILDING COSTS

£6-95
(+10% VAT 89p)

P.P. & INS. 44p
(OVERSEAS P. & P. £1-85)

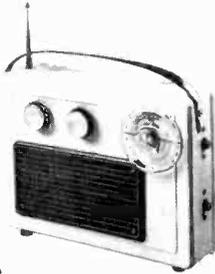

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4j volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9in x 6 1/2in x 2 1/2in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS

£2-73
(+10% VAT 27p)

P.P. & INS. 30p
(OVERSEAS P. & P. £1-25)



EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS

£3-60
(+10% VAT 36p)

P.P. & INS. 30p
(OVERSEAS P. & P. £1-25)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW. Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and easy build plans 20p. Free with parts.

TOTAL BUILDING COSTS

£4-08
(+10% VAT 40p)

P.P. & INS. 31p
(OVERSEAS P. & P. £1-85p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS:

MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

£6-98
(+10% VAT 69p)

P.P. & INS. 47p
(OVERSEAS P. & P. £1-85)




POCKET FIVE

3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5 1/2in x 1 1/2in x 3 1/2in approx. Plans and parts price list 15p (FREE with parts).



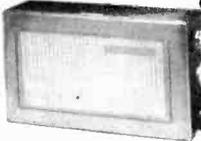Total Building Costs **£2-50** P.P. & Ins. 26p
(+10% VAT 26p)
(Overseas P. & P. £1-25)



Total Building Costs **£2-28**
(+10% VAT 22p)
P.P. & Ins. 26p
(Overseas P. & P. £1-25)

TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).


TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

£4-48
(+10% VAT 44p)

P.P. & INS. 33p
(OVERSEAS P. & P. £1-25)

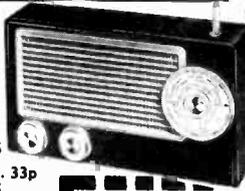

ROAMER SIX CASE AND LOOKS AS TRANS EIGHT

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS

£3-98
(+10% VAT 39p)

P.P. & IN. 31p
(OVERSEAS P. & P. £1-85)


ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS

£8-50
(+10% VAT 80p)

P.P. & INS. 52p
(OVERSEAS P. & P. £1-85)

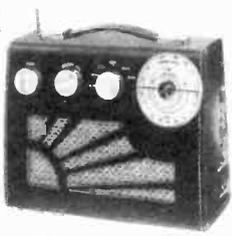

EDU-KIT

Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plug and Sockets: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

£5-50
(+10% VAT 50p)

P.P. & INS. 33p
(OVERSEAS P. & P. £1-85)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 62867 Reg. No. 788372

I enclose £..... for.....

Name.....

Address.....

P.E.60

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

Better built
Better performance
Better value

**SAXON HI-FI POWER AMPS
IN THREE USEFUL SIZES
FOR DOMESTIC
& COMMERCIAL
APPLICATIONS**

New versions using 3A
"Plastic Power" Driver
Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

SA50 50 watt RMS
7 transistors, 7 diodes
Carr. paid **£5.65**

SA100 makes an ideal
unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10.90**

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0.2% at 1kHz	
Load	4 to 16 ohms	
Quietest current	15mA	
Noise	Better than -75dB	
Supply voltage	SA35-45V SA50 45/65V SA100 40-70V	
Size	4 1/2in x 4in x 1in (SA100) 4in x 3in x 1in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

**POWER SUPPLIES
FOR THE SA35, SA50 AND SA100 POWER AMPS.
ABOVE**


PU45	Unstabilised supply for 2 SA35's	£4.90
PU70	Unstabilised supply for one or two SA50 or SA100	£7.75 carr. 40p
PS45	Stabilised module for two SA35's or one SA50	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

SAXON PA MIXER-CONTROL UNITS

In extra slimline easy-fit case.

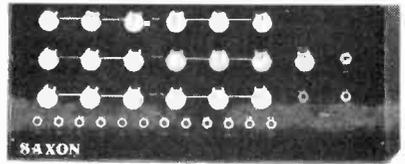Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master control on output of M6HL. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.



- **HIGH AND LOW IMPEDANCE INPUTS**
- **BASS/TREBLE/VOLUME ON EACH PAIR**
- **MASTER CONTROL ON OUTPUT**

M4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" and only 2 1/2in deep. Carr. paid. **£18.50 + V.A.T.**

M6HL


12 inputs (6 high Z, 6 low Z) 18" x 8" x 2 1/2". Carr. paid **£27.50 + V.A.T.**

Channel section modules, for building your own: gain—16 x (24dB). Tone controls—18dB swing. Carr. paid. **£3.50 + V.A.T.**

CONTROL UNITS UNBEATABLE FOR QUALITY AND VALUE

Stereo Version **£15.80**
Carr. 30p.

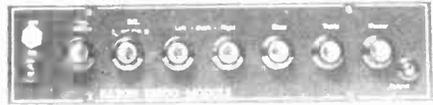Mono (illustration) **£6.50**
For 9v. battery operation. As stereo model, less mic. input. Carr. 20p.



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2in x 3in x 4in deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off. Comparable to units at over twice the price.

AKG HEADPHONES

World famous D.190C—the one the professionals use—at special bargain price **£19.50** Plus V.A.T.

120 W HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.
SPECIFICATION:
Power output, 120W into 8 ohms
Freq. response, 20-20,000Hz ± 2dB
Input sensitivity, 200mV into 10K
Construction, Fibreglass board
Size, 8in x 4in x 4in (5in with supply)
Low distortion parallel push-pull output stage.

Module and power supply (Carr. 40p) **£18.95**
● 160 watts version with power supply (Carr. 50p) **£27.90**



SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. **£19.75**
Carr. 30p.

SINGLE CHANNEL UNIT

Operates from 5-100W amplifiers. Supplied for bass tone operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£7.50**

COMPLETE AMPLIFIERS CSE 100

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.



£34.90 carr. free



SAXON 100 £48.50 carr. free

With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!
12in 25W 8/15 ohms **£6.95** carr. 30p. 15in 50W 8/15 ohm **£14.50** carr. 50p. 12in 40W 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p.

Please include S.A.E. with written enquiries

V.A.T. Please add 10% to total value of order (including carr.) for Value Added Tax.

Prices subject to alteration without notice. E. & O.E.

Order and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS

Telephone 01-684 6385

From 9.30 a.m.-5.30 p.m.

TRADE AND EXPORT ENQUIRIES INVITED

Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T.

TERMS OF BUSINESS

Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.

SPECIAL OFFER !!!

SMALL ELECTROLYTICS

Ref No	Capacity	Voltage	Price	Ref No	Capacity	Voltage	Price
H8/1	1µF	150V	4p	H7/4	64µF	35V	5p
H8/1A	2µF	150V	2p	H7/5	80µF	16V	4p
H8/2	2-2µF	25V	4p	H7/6	100µF	25V	5p
H8/2A	3-3µF	25V	4p	H7/6A	100µF	15V	4p
H8/3	3µF	50V	4p	H7/7	100µF	25V	4p
H8/3A	4µF	50V	4p	H7/8	125µF	16V	5p
H8/4	4.7µF	25V	4p	H7/8A	100µF	35V	6p
H8/4A	5µF	64V	4p	H7/9	100µF	63V	6p
H8/5	5µF	10V	4p	H7/9A	125µF	4V	4p
H8/5A	5µF	150V	4p	H7/10	125µF	25V	6p
H8/6A	10µF	10V	4p	H7/10A	160µF	2.5V	3p
H8/7	10µF	70V	4p	H7/11	160µF	25V	6p
H8/8	16µF	35V	4p	H7/11A	150µF	16V	5p
H8/8A	16µF	16V	4p	H7/13A	200µF	25V	6p
H8/9	20µF	6V	2p	H7/14	220µF	50V	10p
H8/9A	20µF	70V	4p	H7/14A	220µF	16V	6p
H8/10	22µF	50V	4p	H7/15	220µF	25V	5p
H8/10A	22µF	100V	4p	H7/15A	220µF	35V	10p
H8/11	25µF	12V	4p	H8/1A	250µF	4V	3p
H8/11A	24µF	275V	4p	H6/2	250µF	25V	3p
H8/12	32µF	15V	4p	H6/3A	320µF	2-5V	3p
H8/12A	30µF	10V	4p	H6/4	320µF	10V	4p
H8/13A	32µF	50V	4p	H6/4A	330µF	16V	5p
H8/14	40µF	25V	5p	H6/5	330µF	25V	10p
H8/14A	40µF	16V	4p	H6/5A	330µF	35V	15p
H8/15	47µF	50V	4p	H6/8	470µF	25V	10p
H8/15A	40µF	35V	4p	H6/8A	470µF	35V	20p
H7/1	50µF	6V	3p	H6/9	500µF	15V	4p
H7/1A	50µF	10V	4p	H6/9A	400µF	40V	20p
H7/2A	64µF	2.5V	2p	H6/10	750µF	12V	5p
H7/3A	64µF	25V	4p	H6/13A	1000µF	25V	16p
H7/4	15V	4p					

POSTAGE: 15p PER ORDER

ALL GOODS PLUS 10% V.A.T.

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series		Working Voltage Vdc	Capacitance µF	Max. Ripple Current at 50° C	Weight	Price
Type No	15332	16	3300	2.4 amps	1oz	15p
071	15472	16	4700	3.9 amps	1oz	17p
071	15682	16	6800	5.8 amps	1½oz	22p
071	18222	63	2200	5.8 amps	3oz	30p
072	15752	16	7500 + 7500	10.5 amps	3oz	37p
072	15113	16	11000 + 11000	13.8 amps	4½oz	49p
071	16472	25	4700	5.4 amps	1½oz	22p
072	16502	25	5000 + 5000	9.6 amps	3½oz	37p
072	16752	25	7500 + 7500	12.6 amps	4½oz	49p
072	17342	40	3400 + 3400	9.1 amps	3½oz	37p
071	18681	63	680	2.1 amps	1oz	15p

106 and 107 Series		Working Voltage Vdc	Capacitance µF	Max. Ripple Current at 50° C	Weight	Price
106	16223	25	22000	17 amps	10oz	£1-12

UNIJUNCTION TRANSISTORS similar to 2N2646		Working Voltage Vdc	Capacitance µF	Max. Ripple Current at 50° C	Weight	Price
106	17103	40	10000	12 amps	7½oz	94p
107	10222	100	2200	10 amps	5½oz	74p

Type No	Working Voltage Vdc	Capacitance µF	Max. Ripple Current at 50° C	Weight	Price
102	15163	16	16000	8oz	20p
104	90003	20	39000	16oz	30p
102	16802	25	8000	7oz	25p
104	17562	40	5600	5oz	25p
104	90001	45	20000	16oz	50p
104	18332	63	3300	5oz	25p

A further 10% discount on lots of 100 of any one type

Please calculate the weight of your order and include appropriate postage

Not over	Ordinary Parcels	Not over	Ordinary Parcels
1½lb	16p	10lb	37p
2lb	21p	14lb	47p
4lb	25p	18lb	57p
6lb	29p	22lb	67p

£1 100 1/2 WATT RESISTORS 100 CERAMIC CAPACITORS 100 DIODES	£1 1 VERO-BOARD CUTTER 5 2 1/4 x 1 1/4 x 6-13 BOARDS 50 80 IN "ODD PIECES" VERO	£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC.	£1 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS
POSTAGE 15p	POSTAGE 15p	POSTAGE 15p	POSTAGE 25p
PACK No. 1	PACK No. 3	PACK No. 5	PACK No. 7

£1 100 RESISTORS 100 CERAMIC CAPACITORS 100 POLYSTYRENE CAPACITORS	£1 100 RESISTORS 100 CERAMIC CAPACITORS 50 MULLARD POLYESTER CAPACITORS	£1 1 TRANSISTORISED SIGNAL TRACER KIT 1 TRANSISTORISED SIGNAL INJECTOR KIT	£1 100 RESISTORS 100 CAPACITORS (ASSORTED TYPES)
POSTAGE 15p	POSTAGE 15p	POSTAGE 15p	POSTAGE 15p
PACK No. 2	PACK No. 4	PACK No. 6	PACK No. 8

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME: _____

ADDRESS: _____ EB 24

BLOCK CAPS please

TRAMPUS

MONEY BACK IF NOT SATISFIED
all brand new, full spec. Top grade.
Free fabulous NEW catalogue. Send SAE.

red+ 1/8" pin source **LED's 17p!** **Til209** & clip 22p
BIG 1/4 panel clip & RED LED 28p. GREEN & clip 59p
INFRA RED LED EL. IC photo amp 44p. & amp/switch 85p

Digital Display LED 1/3 0-9DP.DIL. £1-69
Minitron type 0-9dpDIL. £1-19. SOCKETS 13p.

IC DIGITAL CLOCK CHIPS.
Texas etc with 4 displays £12. 6 displays & chip £14. pcb £1-49
Mostek date & alarm chips with 6 displays £19. pcb £1-49

hit! All parts & case. National chip. 4 digit £20. 6x £23

with data **integrated circuits**
741: 8pin 29p, to99 & 14pin 27p 748 33p 709 21p
710 35p 723 59p. 555 timer 79p. ZN414 rx. £1-10
703 rf if 28p mc 1310 & led £2-76 mc 1339 £1-20 TAD100 & if £2

1AMP+ REGULATOR 7805, 5 (& 7-20)V. also 12 & 15V £1-49
AUDIO AMPS: mfc4000 50p; 1 & 2W £1-19; 3W £1-29; 6W...

gates 7400 etc 16P 7413 32P 7447 £1-25
7470/72 32P 7474/76 39P 7490 63P
7492 69P 74121 49P & all others in cat. **low prices.**

NEW 16pin counter/driver 90/47 £2-25 DALO pcb. PEN 69p.
DIL. SOCKETS: Professional / gold P.Pins hi or lo Prof file 8, 14, 16 Pin 13P

2N3055 33p. four £1. BC107, BC108, BC109 all 7p ea
IN914 3p ZENERS BZY88 8p. 1A RECTS 50v 3 1/2p 400v 5p. BRIDGE 20p
FETS: 2N3819 19p 2N3823E 20p 4410E 25p BC182/3/4 10p
BC212/3/4 11p BCY70 13p BD131/2 35p ea. BFY523 15p TIS43 25p
2N2926 0y 7p 2N3053 15p 2N3702/3/4/5/6/7/8/9/10/11 all 9p ea
2N3904/6 14p HEATSINKS 5F/T05 18F/T018 5p. T03: 4YL 29p TV3 14p
CAPACITORS 25V10, 50, 100µF 5p. DISCS 4p. PRESETS 5p. CARBON -
POTS 11P. Switch 11P. Dual 5.5p. ULTRASONIC TRANSDUCERS £2.9a
FLUORESCENT LIGHTS, 8W, 13" 12VOLT £2-59

Trampus electronics ADD 10% VAT TO PRICES. P&P 10P CWO.
P.O. BOX 29, BRACKNELL, BERKS.

C. T. ELECTRONICS 267 Acton Lane, London W4 5DG

Tel. 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

semiconductors

AC107	35p	BCY30	30p	MJ2901	£2-20	OC42	30p	TIP36C	£4-10	2N2904	20p
AC125	25p	BCY33	30p	MJE340	50p	OC44	30p	TIP41C	95p	2N2905	25p
AC126	25p	BCY34	30p	MJE370	73p	OC45	20p	TIP42C	£1-10	2N2906	22p
AC127	25p	BCY55	60p	MJE371	66p	OC70	15p	TIS50	40p	2N2907	25p
AC128	25p	BCY70	20p	MJE520	58p	OC71	17p	ZTX107	15p	2N2962	10p
AC176	25p	BCY71	20p	MJE521	73p	OC72	20p	ZTX300	15p	2N3053	30p
AC177	25p	BCY72	20p	MJE2955	£1-95	OC75	25p	ZTX500	15p	2N3054	40p
AC178	25p	BD121	75p	MJE3055	85p	OC76	40p	ZT X531	27p	2N3055	50p
AC199	25p	BD123	75p	MM1613	43p	OC77	25p	IN659	7p	2N3232	64p
ACY20	25p	BD124	60p	MK1712	60p	OC81	25p	IN614	8p	2N3702	10p
ACY39	50p	BD131	75p	MPF102	45p	OC82	25p	IN616	8p	2N3703	10p
ACY21	25p	BD153	75p	MPF103	35p	OC83	25p	IN4001	8p	2N3704	10p
AD140	55p	BD156	75p	(2N5457)	35p	OC84	25p	IN4002	8p	2N3705	10p
AD149	85p	BDY11	£1-40	MPF104	40p	OC139	30p	IN4003	9p	2N3706	10p
AD161	37p	BDY17	£1-50	(2N5458)	35p	OC140	30p	IN4004	10p	2N3707	10p
AD162	37p	BDY19	£1-50	MPF105	40p	OC170	25p	IN4005	12p	2N3708	10p
ADZ11	£1-90	BF151	20p	(2N5459)	40p	OC171	25p	IN4006	12p	2N3709	10p
AF114	25p	BF194	14p	MPSA06	35p	OC200	50p	IN4007	18p	2N3771	£2-70
AF115	25p	BF195	15p	MPSA16	30p	OC201	60p	IN4148	7p	2N3772	£2-75
AF116	25p	BFX29	30p	MPSA56	35p	OC202	65p	2N696	25p	2N3773	£2-90
AF117	25p	BFX84	25p	MPSU06	75p	TIP29A	40p	2N697	20p	2N3819	35p
AF118	50p	BFX85	30p	MPSU56	70p	TIP30A	50p	2N698	25p	2N3820	55p
AF172	25p	BFX86	25p	NKT135	35p	TIP31A	62p	2N706	12p	2N3866	85p
BFX88	25p	BFX88	25p	NKT222	25p	TIP32A	74p	2N706A	12p	2N3926	22p
ASZ21	55p	BFY10	35p	NKT401	85p	TIP33A	£1-05	2N708	15p	2N3905	25p
BA102	30p	BFY44	50p	NKT404	60p	TIP34A	£1-55	2N930	20p	2N4058	12p
BA112	60p	BFY50	25p	NKT773	25p	TIP35A	£2-65	2N1132	25p	2N4059	12p
BA114	18p	BFY51	20p	NKT774	25p	TIP36A	£3-35	2N1302	18p	2N4060	12p
BA156	15p	BFY52	22p	OA5	20p	TIP41A	75p	2N1303	18p	2N4061	12p
BC107	10p	BFY53	19p	OA10	20p	TIP42A	90p	2N1304	20p	2N4062	12p
BC108	10p	BFY54	20p	OA47	60p	TIP29B	60p	2N1305	20p	2N4063	17p
BC109	10p	BLY10	£3-00	OA70	12p	TIP30B	66p	2N1306	25p	2N4286	15p
BC147	12p	BSW6	60p	OA79	12p	TIP31B	70p	2N1307	25p	2N4287	15p
BC148	12p	BSW6	75p	OA81	10p	TIP32B	82p	2N1308	25p	2N4288	15p
BC149	12p	BSY95A	12p	OA90	10p	TIP33B	£1-12	2N1309	25p	2N4289	15p
BC157	13p	C111	40p	OA91	10p	TIP34B	£1-68	2N1613	20p	2N4290	15p
BC158	13p	C426	30p	OA200	10p	TIP35B	£2-81	2N1711	25p	2N4444	£1-90
BC159	13p	BY100	15p	OA202	10p	TIP36B	£3-64	2N2147	70p	2N4871	35p
BC169C	13p	BY122	85p	OA210	35p	TIP41B	83p	2N2160	55p	2N4920	86p
BC182	10p	BY126	20p	OA211	35p	TIP42B	98p	2N2217	18p	2N5191	96p
BC183	10p	BY127	20p	OC19	85p	TIP29C	71p	2N2218	18p	2N5194	£1-10
BC184	10p	BY184	85p	OC22	50p	TIP30C	78p	2N2219	25p	2N5457	35p
BC212	14p	IS100	15p	OC25	50p	TIP31C	85p	2N2222	20p	2N5458	33p
BC213	14p	IS103	20p	OC28	85p	TIP32C	£1-05	2N222A	34p	2N5459	40p
BC214	14p	MJ340	50p	OC28	55p	TIP33C	£1-30	2N2398	40p	40361	50p
BC238	12p	MJ481	85p	OC35	50p	TIP34C	£1-90	2N2646	50p	40362	55p
BC239	12p	MJ2801	£1-20	OC36	80p	TIP35C	£3-20	2N2846	£1-50	40250	70p

DIGITAL INTEGRAL CIRCUITS

SN7400	20p	SN7427	42p	SN7470	30p	SN74100	£2-50	SN74165	£4-00
SN7401	20p	SN7428	50p	SN7472	30p	SN74104	£1-45	SN74166	£4-00
SN7402	20p	SN7430	20p	SN7473	40p	SN74105	£1-45	SN74167	£8-25
SN7403	20p	SN7432	42p	SN7474	40p	SN74107	50p	SN74170	£4-10
SN7404	20p	SN7433	70p	SN7475	55p	SN74118	£1-00	SN74175	£1-35
SN7405	20p	SN7437	65p	SN7476	45p	SN74119	£1-90	SN74176	£1-60
SN7406	30p	SN7438	65p	SN7480	80p	SN74122	£1-35	SN74177	£1-60
SN7407	30p	SN7443	20p	SN7481	£1-25	SN74123	£2-70	SN74178	£1-55
SN7408	20p	SN7444	20p	SN7482	85p	SN74124	£1-00	SN74180	£7-00
SN7409	45p	SN7442	75p	SN7483	£1-00	SN74125	£1-00	SN74182	£2-40
SN7410	20p	SN7443	£1-00	SN7484	90p	SN74126	£1-35	SN74185A	£2-40
SN7411	23p	SN7445	£2-00	SN7486	45p	SN74127	£1-35	SN74190	£1-95
SN7412	42p	SN7446	£2-00	SN7490	75p	SN74128	£1-55	SN74191	£1-95
SN7413	30p	SN7447	£1-75	SN7491A	£1-00	SN74129	£1-55	SN74192	£2-00
SN7414	30p	SN7448	£1-75	SN7492	75p	SN74130	£1-60	SN74193	£2-50
SN7415	30p	SN7450	20p	SN7493	75p	SN74131	£1-60	SN74195	£1-85
SN7420	20p	SN7451	20p	SN7494	80p	SN74132	£2-60	SN74196	£1-50
SN7422	48p	SN7453	20p	SN7495	80p	SN74133	£3-40	SN74197	£1-50
SN7423	48p	SN7454	20p	SN7496	£1-00	SN74134	£3-40	SN74198	£4-60
SN7425	48p	SN7460	20p	SN7497	£8-25	SN74164	£2-75	SN74199	£4-60

TRIACS

SC40D 6A 400V	£1-00
SC40E 6A 500V	£1-20
SC45D 10A 400V	£1-25
SC45E 10A 500V	£1-45
SC50D 15A 500V	£1-85
40330 6A 400V	85p
DIAC	25p

S.C.R.

BTY 79/400R	75p
CRS 1/05	25p
CRS 1/10	30p
CRS 1/20	30p
CRS 1/40	35p
CRS 3/035	30p
CRS 3/10	30p
CRS 3/40	30p
CRS 3/60	60p
CRS 7/400	70p
CRS 7/600	98p
CRS 16/100	65p
CRS 16/200	72p
CRS 16/600	£1-95
C 106D	15p
TIC 44	35p
16RC/20	70p
2N3525	£1-05

LINEAR OP. AMPS

709C TO99 DIL	35p
723C TO99 DIL	£1-05
741C DIL	45p
747C TO99 DIL	£1-10
72749P DIL	85p
723C TO99	£1-05
CA3014	£1-55
CA3018	£1-00
CA3048	£2-34
MC1303L	£1-85
MFC4000	55p
MFC4000B	60p
SL403D	£1-50
ZN414	£1-25
LM309K	£1-90

BRIDGE RECTIFIERS

BY122 1.5A 40V	40p
BY164 1.4A 200V	57p
CIC2-100 2A 100V	39p
6A 100V	85p

ZENER DIODES

BZY88 series 400mW	15p
1.5 Watt range	25p
10 Watt range	45p
TIL 209 H P	28p
ORP 12	50p

LOW COST OSCILLOSCOPES

Cosmor—1035 D.B. 1049 Mk 3A
D.B. 1049 Mk 4, D.B.
EM1—WM2, WM3B WM7 WM8
WM16 WM18 WM26
Selatron—AD557 CD513 2, CD523
S 2, CD643, CD6431 1, CD711 S 2.
All prices and details on application,
phone 01-994 6275. Inspection wel-
come—call at warehouse

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE of V.A.T.
Please add 10% to all orders. Carriage orders under £5 + 20p
Over £5 post free

WAREHOUSE

20-24 BEAUMONT ROAD, W.4

SURPLUS COMPONENTS TEST EQUIPMENT etc etc

THOUSANDS OF BARGAINS

Test Equipment * Oscilloscopes * Signal Generators * Counters
Cabinets * Bridges * Meters * Transmitters * Receivers * Power Supplies
Laboratory Equipment * Galvanometers * Audio Equipment * Video
Equipment * Meters * Battery Chargers * Motors * Etc * Etc

20 TONS OF ELECTRONIC EQUIPMENT

Resistors * Relays * Capacitors * Switches * Transformers * Meters
Potentiometers * Component Panels * Semiconductors * Cable * Valves
Etc * Etc * Etc

Regret no lists available. Personal callers only. Cash and Carry only

AUDIO ACCESSORY SHOP

17 TURNHAM GREEN TERRACE, CHISWICK, W.4

VALVE AMPLIFIERS

5 Watt	£12-50
15 Watt	£24-50
30 Watt	£29-50
50 Watt	£36-25
150 Watt	£75-90
500 Watt	£124-50

TRANSISTOR AMPLIFIERS

FAL Phase 50W	£39-93
FAL Phase 100W	£89-95

DISCO CONSOLES

FAL Disco Mk 2	£82-99
FAL Power Disco (with 70W rms Amp)	£123-75

HEAVY DUTY LOUDSPEAKERS

* SPECIAL OFFER PRICE +
15 in 70W E.M.I. 8 ohm **£19-50**
Decca Bin, 10 watt Hi-Fi. Speaker
plus matching tweeter **£7-50** com-
plete Suitable 2-way cross-
over **£1-21**

SPEAKER CABINETS

Suitable for any 12 in speaker
covered in Rexine and Vynair Size
18 in x 18 in x 8 in approx **£9-90**

DISCO LIGHTING

Sound-Light Module	£7-90
3 Channel Sound-Light	£22-50
Oil Wheel 6 in dia	£5-25
Suitable 1 rpm Motor	£1-00
Strobe 4 Joule	£25-00
Single Flash Box	£7-50
(100W Red Blue Gn Yel)	
Triple Flash Box	£16-25

TEAK VENEERED SPEAKER CABINETS

For 8 x 5 in speaker **£3-50** each
For 8 in + Tweeter **£5-00** each
For 13 x 8 in. **£8-50** each
For 12 in. + Tweeter **£9-90** each
ALSO Audio Connecting Leads Tape Cassettes Stereo Systems, Mixers
Mic. Stands Speaker Cloth, Turntables, Plinths Covers etc etc

SGS EA1000

3W
AMPLIFIER
MODULE
£2-45
HANDBOOK
10p
SolidDev 15W.
Class B Audio
Circuit, £3-65;
Handbook, 15p.
TBA800 5W Audio
I.C. £1-50; Data
10p.
UA041 5W Amplifier
Module, £3-75

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

Pack No	
1	500 Carbon resistors, 1/2, 1/4, 1/2 watt
2	100 Electrolytic Condensers
3	250 Ceramic, Polystyrene, Silver Mica etc Condensers
4	2



WILMSLOW AUDIO

THE Firm for speakers!


SPEAKERS

EMI 13 x 8 3 8 or 15 ohm	£2-03
EMI 13 x 8 150 d c 3 8 or 15 ohm	£2-25
EMI 13 x 8 450 11w 3 8 or 15 ohm	£3-60
EMI 13 x 8 type 350 8 ohm	£8-25
EMI 6 in 93850 4 or 8 ohm	£2-80
EMI 8 x 5 d cone roll s 8 ohm	£2-50
Baker Group 25 3 8 or 15 ohm	£6-60
Baker Group 35 3 8 or 15 ohm	£7-50
Baker De Luxe 12 in d cone	£9-62
Baker Major 12 in	£7-50
Kef T27	£4-67
Kef T15	£5-50
Kef B110	£6-16
Kef B200	£7-42
Kef B139	£10-72
Kef DN8	£1-92
Kef DN9	£1-37
Kef DN12	£4-12
Kef DN13	£2-75
Fane Pop 100W 8 15 ohm	£21-45
Fane Pop 60W 8 15 ohm	£12-26
Fane Pop 50W 8 15 ohm	£10-17
Fane Pop 25 2 25W 8 15 ohm	£5-94
Fane Pop 15W 8 15 ohm	£4-40
Fane Crescendo 15 in 8 or 15 ohm	£27-50
Fane Crescendo 12A 100W 8 or 15 ohm	£24-20
Fane Crescendo 12B bass	£24-20
Fane 8077 8 in d c roll s 8 or 15 ohm	£3-85
Fane 8087 8 in d cone 8 or 15 ohm	£2-64
Goodmans Axent 100 tweeter	£2-60
Goodmans 8P 8 or 15 ohm	£3-80
Goodmans 10P 8 or 15 ohm	£4-49
Goodmans 12P 8 or 15 ohm	£11-55
Goodmans 15P 8 or 15 ohm	£17-05
Goodmans 18P 8 or 15 ohm	£29-70
Goodmans Twinaxiom 8	£6-79
Goodmans Twinaxiom 10	£7-61
Elac 9 x 5 59RM109 15 ohm 59RM114 8 ohm	£2-53
Elac 6 in d c roll s 8 ohm	£3-22
Elac 6 in d cone 8 ohm	£2-59
Elac 4 in tweeter TW4	£1-21
Wharfedale Super 10 RS DD	£9-80
Coral 6 in d cone roll s 8 ohm	£2-42
Siran 6 in 3 or 8 ohm	£1-44
Richard Allan 12 in d c 3 or 15 ohm	£2-20
10 in x 6 in 3 8 or 15 ohm	£1-92
8 in x 5 in 3 or 8 ohm	£1-38
7 in x 4 in 3 or 8 ohm	£1-38
2 in 64 ohm or 70 mm 80 ohm	65p
Adastral Hiten 10 in 10W 8 or 15 ohm	£2-80
Eagle DT33 dome tweeter	£5-45
Eagle HT15 tweeter	£3-66
Eagle CT5 tweeter	£1-25
Eagle CT10 tweeter	£2-54
Eagle MHT10 tweeter	£3-74
Eagle FR4	£4-45
Eagle xover CN23 2B, 216	£1-15
SP matching transformer 3-15 ohm	£1-10
Celestion MF1000 25W horn 8 or 15 ohm	£10-45
Celestion PS8 (for Unilex)	£2-16
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00

SPEAKER KITS

Wharfedale Linton 2	£8-75
Wharfedale Glendale 3	£15-75
Wharfedale Doveedale 3	£24-25
Richard Allan Trunkit	£7-95
Richard Allan Triple 8	£11-75
Richard Allan Triple Assem	£17-50
Richard Allan Super Triple	£20-75
Goodmans DN 20	£8-58
Fane Mode One	£9-00

Kefkit 2	£24-75
Kefkit 3	£35-50
Peerless 2-8	£5-50
Peerless 10-2	£8-47
Peerless 20-2	£10-41
Heime XLK 25 (pair)	£18-17
Heime XLK 50 (pair)	£37-18
Stephen speaker kits and cabinets—send for free booklet Choosing a Speaker	
PRICES INCLUDE VAT.	
Free with orders over £7— Hi-fi Loudspeaker Enclosure book. All units guaranteed new and perfect.	
Prompt despatch. Carriage and insurance speakers 35p each, speaker kits 75p each, tweeters and crossovers 20p each.	
Carriage and insurance 50p per kit.	

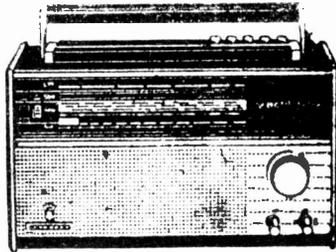

RADIOS/CASSETTES/AMPS

Grundig RF310	£21-25
Grundig Signal 500	£27-00
Grundig Manner TR865	£32-00
Grundig Elite Boy 500	£27-00
Grundig Melody Boy 500	£27-00
Grundig Melody Boy 1000	£38-75
Grundig Yacht Boy 210	£34-25
Grundig RF430 mains	£27-00
Grundig RF310 mains	£22-75
Grundig Top Boy	£16-75
Grundig Satellit 1000	£121-00
Grundig C230 cassette	£28-00
Grundig C402 cassette	£27-00
Tandberg TP41	£37-75
BASF 9301 radio cassette	£64-00
Bush VTR178 5 band (inc AIR)	£29-00
Trio KA200A	£33-00
Trio KA2002	£41-00
ITT/KB Colt	£9-95
ITT/KB Golf Preset	£21-25
ITT/KB Weekend Auto	£16-00
ITT/KB Europa	£18-00
ITT/KB SL53 cassette	£22-82
ITT/KB Studio 60M cassette	£29-32
ITT/KB Studio 73 stereo cassette	£44-00
Koyo KTR1664 8 waveband	£40-00
Koyo KTR1770 11 waveband	£56-50
Koyo KTR1883 5 band (inc AIR)	£23-50
GEC 200 Radio/Cassette	£31-00
Prices include VAT	
Carriage and insurance 75p FREE with each radio—mono radio stations book	

PA/DISCO AMPLIFIERS

(carr. and Ins. £1)	
Baker 100W	£46-00
Linear 30 40	£25-00
Linear 40 60	£30-00
Linear 80 100	£55-00

FREE with speaker orders over £7

"Hi Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and insurance 25p per speaker (tweeters and crossovers 15p). ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Radios, etc.: 10 Swan Street, Wilmslow, Cheshire, SK9 1HF. Telephone: Wilmslow 29599.

SINCLAIR CAMBRIDGE CALCULATOR
Fully assembled only £26-45 (£3)
Also available Sinclair Executive Calc £34 (£3-70)

JOSTY KITS—AN APOLOGY
We regret that we will not now be stocking these kits and apologize both to the Josty Company and to customers inconvenienced by our earlier advertisements

SINCLAIR EQUIPMENT

Z40 £4-25 (63p) Project 605 £19-90 (£2 30)
Z60 £5-38 (74p) Stereo 80 Pre-amp £9-53 (£1 05)
O16 £5-90 (79p) Project 80 Tuner £8-95 (£1 10)
P25 £3-47 (57p) Project 80 Decoder £5-69 (77p)
P29 £5-95 (99p) Project 80 AFU £5-38 (74p)
P28 £8-40 (84p) Trans for P28 £2-95 (50p)

SINCLAIR SUPER IC12
6W rms power with 44 page booklet and printed circuit £2-10 (43p)

SWANLEY IC TOMORROW £2-60 (47p)
The world's most powerful IC amplifier. Similar appearance to IC12 but rated at 10W rms power

FERRANTI ZN414 £1-20 (23p)
Fabulous TRF integrated circuit radio chip

BATTERY ELIMINATOR BARGAIN
The most versatile battery eliminator ever offered. Switched output of 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500mA.
Other eliminators stocked: 50mA unswitched 4½V £1-50 (30p), 6V £1-50 (30p), 9V £1-50 (30p), 7½V cassette type £2-25 (30p). Double 4½V + 4½V £2-50 (35p), Double 6V + 6V £2-50 (35p), Double 9V + 9V £2-50 (35p), Switched model giving 6V 7½V and 9V at 400mA £4 (50p).

£3-60 (58p)

IC RADIO CHIP TBA851 £2-10 (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2-10 (32p). Send SAE for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1 75 (29p)

S-DECS AND T-DECS

S-DECS £1-44 (25p)
T-DECS £2-88 (40p)
µ-DEC A £3-14 (43p)
µ-DEC B £5-94 (71p)
16 di IC carriers £1-20 (17p)

DE LUXE KIT FOR THE IC12
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-55 (26p). Stereo model with balance control £3-50 (46p)

IC12 POWER KIT
Supplies 28V 0-5A £2-47 (50p)

LOUDSPEAKERS FOR THE IC12
5 in 8 ohm £1-10 (27p), 5 in x 8 in 8 ohm £1-55 (37p)

PREAMPLIFIER KITS FOR THE IC12
Type 1 for magnetic pickups, mics and tuners Mono model £1-30 (24p). Stereo model £2-30 (34p). Type 2 for ceramic or crystal pickups Mono 80p (17p), Stereo £1-20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

ECONOMICAL QUADRAPHONICS £11-95 (£1-50)
Eagle AA10 Quadrasonic Synthesizer. Complete, self-contained matrix system in attractive cabinet. Just feed ordinary 2 channel stereo into it and connect outputs to 4 loudspeakers to obtain the latest experience in sound 35 watts rms/channel.

SWANLEY ELECTRONICS
32 Goldsai Road, Swanley, Kent
Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools, etc. welcome. Mail order only. No callers, please.

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way.*

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


You LEARN—but it’s as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

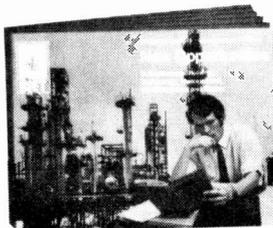If you wish to make a career in Electronics, send for your **FREE** copy of “**NEW OPPORTUNITIES**”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE 46 ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

CL BPE 46

NAME (BLOCK CAPITALS)

AGE

ADDRESS

SUBJECT OF INTEREST

P.C. BORED?

— not with the

decon-dalo 33PC



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

NO MESS — NO MASKING

A perfect circuit every time!

The Decon-Dalo 33 PC marker is now available in France, Germany, Italy, Switzerland, Austria and all Scandinavian countries. Send for details of local supplier.

Please send me further details on the 33PC:

Name

Address

PE1

Post to: **DECON LABORATORIES LTD.**
FREEPOST
PORTSLADE, BRIGHTON, ENGLAND
 (No Stamp Needed) Phone 0273 414371

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed

Pak No.	EQVT
T1 8	2G3713 OC71
T2 8	D1374 OC75
T3 8	D1216 OC81D
T4 8	2G381T OC81
T5 8	2G382T OC82
T6 8	2G344B OC44
T7 8	2G345B OC45
T8 8	2G378 OC78
T9 8	2G399A 2N1392
T10 8	2G417 AF117

All 55p each pak

ND120 NIXIE DRIVER TRANSISTOR.
Suitable replacement for BSX21, C407, 2N1893 120voh.

1	25	100+
0-19	0-16	0-16

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqty. ZTX300 6p each. Any Quantity.

GP1000 TO3 METAL CASE GERMANIUM
V_{beo}=80V. V_{ceo}=50V. I.C.=10 amps. Ptot=30W. h_{fe}=30-170.
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-48	0-44	0-40

GP300 TO3 METAL CASE SILICON
V_{beo}=100V. V_{ceo}=60V. I.C.=10 amps. Ptot=115W. h_{fe}=20, 100T=1MHz. Suitable replacement for 2N3055, BDY11 or BDY20.

1	25	100+
0-55	0-58	0-51

NEW 8th EDITION
260 pages

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK, £1.95 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

UT46 UNIJUNCTION TRANSISTORS
Direct replacement for TIS 43rand BEN 3000 also electrically equivalent to 2N2945

1	25	100+
0-80	0-28	0-22

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706. BSY-87/28/85A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	0-55
50	For	1-10
100	For	1-92
500	For	8-25
1000	For	14-30

SIL. G.P. DIODES 2p
300mW. I_{SM} 30 0-55
40PIV(Min.) 100 1-65
Sub-Min. 500 5-50
Full Tested 1,000 9-90
Ideal for Organ Builders.

R2400 TO3 NPN SILICON HIGH VOLTAGE
V_{beo}=250V. V_{ceo}=100V. I.C.=6 amps. Ptot=30W. h_{fe}=typ. 20
f_T=5MHz.

1	25	100+
0-55	0-50	0-44

ADI61/162 PNP M/P COMP. GERM. TRANS. OUR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

SILICON PHOTO TRANSISTOR. 15 Lens and NPN Sim. to BPX25 and P21. BRAND NEW. Full data available. Fully guaranteed.
Qty. 1-24 25-99 100up
Price each 44p 40p 88p

INTEGRATED CIRCUIT PAKS
Manufacturers' "Full Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
UIC00=12 x 7400	0-55	
UIC01=12 x 7401	0-55	
UIC02=12 x 7402	0-55	
UIC03=12 x 7403	0-55	
UIC04=12 x 7404	0-55	
UIC05=12 x 7405	0-55	
UIC06=8 x 7406	0-55	
UIC07=8 x 7407	0-55	
UIC10=12 x 7410	0-55	
UIC20=12 x 7420	0-55	
UIC30=12 x 7430	0-55	
UIC40=12 x 7440	0-55	
UIC41=5 x 7441	0-55	
UIC42=5 x 7442	0-55	
UIC43=5 x 7443	0-55	
UIC44=5 x 7444	0-55	
UIC45=5 x 7445	0-55	

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

Pak No.	Contents	Price
UIC46=5 x 7446	0-55	
UIC48=5 x 7448	0-55	
UIC50=12 x 7450	0-55	
UIC51=12 x 7451	0-55	
UIC53=12 x 7453	0-55	
UIC54=12 x 7454	0-55	
UIC60=12 x 7460	0-55	
UIC70=8 x 7470	0-55	
UIC72=8 x 7472	0-55	
UIC73=8 x 7473	0-55	
UIC74=8 x 7474	0-55	
UIC76=8 x 7476	0-55	
UIC80=5 x 7480	0-55	
UIC81=5 x 7481	0-55	
UIC82=5 x 7482	0-55	
UIC83=5 x 7483	0-55	

QUALITY TESTED SEMICONDUCTORS Pak No.

Q 1 20	Red spot transistors pnp	0-55
Q 2 16	White spot R.F. transistors pnp	0-55
Q 3 4	OC77 type transistors	0-55
Q 4 6	Matched transistors OC44/45/81/81D	0-55
Q 5 4	OC75 transistors	0-55
Q 6 5	OC72 transistors	0-55
Q 7 4	AC128 transistors pnp high gain	0-55
Q 8 4	AC126 transistors pnp	0-55
Q 9 7	OC81 type transistors	0-55
Q 10 7	OC71 type transistors	0-55
Q11 2	AC127/128 Complementary pairs pnp/npn	0-55
Q12 3	AF116 type transistors	0-55
Q13 3	AF117 type transistors	0-55
Q14 3	OC171 H.F. type transistors	0-85
Q15 7	2N2926 Sil. Epoxy transistors mixed colours	0-55
Q16 2	GET880 low noise Germanium transistors	0-55
Q17 5	npn 2 x ST.141 & 3 x ST.140	0-65
Q18 4	MADT*8 2 x MAT100 & 2 x MAT120	0-55
Q19 3	MADT*8 2 x MAT101 & 1 x MAT120	0-55
Q20 4	OC44 Germanium transistors A.F.	0-55
Q21 4	AC127 npn Germanium transistors	0-55
Q22 20	NKT transistors A.F. R.F. coded.	0-55
Q23 10	OA202 Silicon diodes sub-min.	0-55
Q24 8	OA81 diodes	0-55
Q25 15	IN914 Silicon diodes 75PIV 75mA	0-55
Q26 8	OA85 Germanium diodes sub-min IN69	0-55
Q27 2	10A 600 PIV Silicon rectifiers IS425K	0-55
Q28 2	Silicon power rectifiers BYZ13	0-55
Q29 4	Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-55
Q30 7	Silicon switch transistors 2N706	0-55
Q31 6	Silicon switch transistors 2N708, npn	0-55
Q32 3	pnp Silicon transistors 2 x 2N1131, 1 x 2N1132	0-65
Q33 3	Silicon npn transistors 2N1711	0-55
Q34 7	Silicon npn transistors 2N2369, 400MHz (code P397)	0-55
Q35 3	Silicon pnp TO-18, 2 x 2N2904 & 1 x 2N2905	0-55
Q36 7	2N3646 TO-18 plastic 300MHz npn	0-55
Q37 3	2N3053 npn Silicon transistors	0-55
Q38 7	pnp transistors 4 x 2N3703, 3 x 2N3702	0-55

ELECTRONIC SLIDE-RULE
The MK Slide Rule, designed to simplify Electronic calculations features the following scales:
Conversion of Frequency and Wavelength.
Calculation of L, C and f of Tuned Circuits.
Reactance and Self Inductance. Area of Circles.
Volume of Cylinders. Resistance of Conductors.
Weight of Conductors. Decibel Calculations.
Angle Functions. Natural Logs and "e" Functions.
Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp.
A must for every electronic engineer and enthusiast. Size: 22cm x 4cm. Complete with case and instructions. Price each: £3-69

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-33V. 400mW (DO-7 Case) 12p ea. 11W (Top-Hat) 18p ea. 10W (SO-10 Stud) 32p ea.

NEW LOW PRICED TESTED S.C.R.'S

PIV	50	100	200	400	600	800
1A	TO5	0-22	0-27	0-32	0-42	0-63
3A	TO66	0-27	0-27	0-32	0-42	0-52
5A	TO66	0-39	0-52	0-54	0-59	0-75
5A	TO64	0-39	0-52	0-54	0-62	0-75
7A	TO48	0-52	0-55	0-62	0-87	0-84
10A	TO48	0-55	0-63	0-67	0-88	1-07
16A	TO48	0-58	0-82	0-87	0-87	1-50
30A	TO48	1-27	1-54	1-76	1-93	4-40

BIP 19/20 TO3 NPN PLASTIC SILICON
V_{beo}=100V. V_{ceo}=50V. I.C.=10 amps. Ptot 50W. h_{fe}=typ. 100 f_T=3MHz.
BIP 19/20 Matched Pair.
1 25 100+ 0-66 0-85 0-82

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	60 Mixed Germanium Transistors AF/RF	0-55
U 3	73 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-55
U 4	40 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil Planar Trans. NPN like BSY95A, 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 65	0-55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA260/292	0-55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-55
U10	20 BAY30 charge storage Diodes DO-7 Glass	0-55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U19	25 Silicon NPN Transistors like BC108	0-55
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0-55
U23	30 MADT's like M1Z Series PNP Transistors	0-55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U25	25 300MHz NPN Silicon Transistors 2N708, BSY27	0-55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0-50
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1-15
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0-55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise AMP 2N3707	0-55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26/30/4	0-55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-55
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0-55
U38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0-55
U39	30 RF Germ. PNP Transistors 2N1303/3 TO-5	0-55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0-55
U41	25 RF Germanium Transistors TO-5, OC45, NKT72	0-55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0-55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-55
U44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-55
U45	7 3A SCR. TO66 up to 600PIV	1-10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

POST OFFICE TELEPHONE
DIALS 60p each.

F.E.T.'S
2N3819 31p 2N5468 35p
2N3820 55p 2N5459 44p
2N3821 30p 2N5410 66p
2N3823 81p MPP105 41p

CADMIUM CELLS
ORP12 48p

FREE
One 55p Pak of your own choice free with orders valued £4 or over

2N3055
115 WATT SIL POWER NPN 55p EACH

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
DO-7	3016	3016	3016	3016	8010	8010	TO48
50	0-05	0-06	0-05	0-08	0-15	0-21	0-60
100	0-05	0-07	0-06	0-10	0-17	0-23	0-75
200	0-06	0-10	0-07	0-12	0-22	0-28	1-00
400	0-08	0-15	0-08	0-15	0-30	0-38	1-85
600	0-09	0-17	0-10	0-18	0-36	0-45	1-90
800	0-12	0-19	0-11	0-20	0-38	0-55	2-10
1000	0-14	0-20	0-12	0-25	0-48	0-65	2-40
1200	—	0-35	—	0-30	0-58	0-75	3-00

DIACS
FOR USE WITH TRIACS.
BR100 (D32) 41p each

10 amp POTTED BRIDGE RECTIFIER on heat sink.
100PIV. 99p each

TRIACS
VBOM 2A 6A 10A
TO-6 TO-66 TO-48

2p	5p	8p
100V	33	55
200V	55	66
400V	77	88
	1-21	

BI-PAK
P.O. BOX 6, WARE, HERTS
Postage and packing add 11p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.
Guaranteed Satisfaction or Money Back

POWER SUPPLY UNITS

AC-DC & DC-DC

Different Voltages
All English make
Fully Guaranteed
for parts and labour

AC.601 240V a.c. INPUT
OUTPUTS 3V, 4.5V, 6V, 7.5V, 9V and 12V d.c.
MAX. CURRENT 500mA

AC.301 INPUT 240V a.c.
OUTPUT 6V, 7.5V, 9V d.c.
MAX. CURRENT 500mA

AC.201 INPUT 240V a.c.
OUTPUT 9V and 12V d.c.
MAX. CURRENT 1 Amp

AC.105 INPUT 240V a.c.
OUTPUT 12V d.c.
MAX. CURRENT 6 Amp

AC.101 INPUT: 240V a.c.
OUTPUT 6V or 7.5V or 9V d.c.
MAX. CURRENT 500mA

DC.301 FULLY STABILIZED
INPUT: 12V d.c.
OUTPUT 6V, 7.5V and 9V d.c.
MAX. CURRENT 500mA

DC.101 Suitable to use from Car cig. lighter.
INPUT: 12V d.c.
OUTPUT 7.5V or 9V d.c.
MAX. CURRENT 500mA

NORMAN ROSE

(ELECTRICAL) LTD.

Head Office:
"Norman House"
8 St. Chad's Place
London WC1X 9HJ
Telephone: 01-837 9111/3

Birmingham Branch:
29 Constitution Hill
Birmingham 19
Telephone: 021-236 4710

Manchester Branch:
25/27 Harkness St. Ardwick
Manchester M12 6DS
Telephone: 061-273 1498

Bradford Branch:
10 Sackville Street
Bradford, Yorkshire
Telephone: 0274 26104

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened

ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	2.32 30
149	60	3 12	9.9 x 7.7 x 8.6	3.45 36
150	100	5 8	9.9 x 8.9 x 8.6	3.79 52
151	200	8 0	12.1 x 9.3 x 10.2	6.45 52
152	250	13 12	12.1 x 11.8 x 10.2	8.41 67
153	350	15 0	14.0 x 10.8 x 11.8	11.20 82
154	500	19 8	14.0 x 13.4 x 11.8	16.25 *
155	750	29 0	17.2 x 14.0 x 14.0	22.10 *
156	1000	38 0	17.2 x 16.6 x 14.0	29.87 *
158	2000	60 0	21.6 x 15.3 x 18.1	49.25 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.22 22
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.40 30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.89 36
66	300	6 4	9.9 x 9.6 x 8.6	...	5.63 52
67	500	12 8	12.1 x 11.2 x 10.2	...	8.36 67
84	1000	19 8	14.0 x 13.4 x 14.3	...	15.19 82
93	1500	30 4	14.0 x 15.9 x 14.3	...	21.99 *
95	2000	32 0	17.2 x 16.6 x 14.0	...	28.70 *
73	3000	40 0	21.6 x 13.4 x 18.1	...	39.17 *

CASED AUTO TRANSFORMERS

115 500W enclosed transformer, with mains lead and two 115V outlet sockets, £9.49, P & P 67p. 20W version, £2.02, P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0.25	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.22 22
213	1.0	0.5	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.44 22
71	2	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	1.90 22
18	4	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.68 36
70	6	3 3	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.20 42
108	8	4 5	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.60 52
72	10	5 6	9.9 x 8.9 x 8.6	0-12V at 5A x 2	4.25 52
116	12	6 12	9.9 x 10.2 x 8.6	0-12V at 5A x 2	5.10 52
17	16	8 8	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.56 52
115	20	10 11	14.0 x 9.6 x 11.8	0-12V at 10A x 2	8.36 67
187	30	15 15	14.0 x 12.1 x 11.8	0-12V at 15A x 2	15.40 82 *
226	60	30 32	17.2 x 15.3 x 14.0	0-12V at 30A x 2	28.44 *

30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.42 22
79	1.0	2 4	7.0 x 6.7 x 6.1	...	1.92 36
3	2.0	3 4	8.9 x 7.7 x 7.7	...	2.90 36
20	3.0	4 8	9.9 x 8.3 x 8.6	...	3.58 42
21	4.0	6 4	9.9 x 9.6 x 8.6	...	4.25 52
51	5.0	6 12	12.1 x 8.6 x 10.2	...	5.30 52
117	6.0	8 0	12.1 x 9.6 x 10.2	...	6.31 52
88	8.0	12 0	12.1 x 11.8 x 10.2	...	8.18 67
89	10.0	13 12	14.0 x 10.2 x 11.8	...	10.33 67

50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	1.90 30
103	1.0	2 12	8.3 x 7.4 x 7.0	...	2.80 36
104	2.0	5 8	7.9 x 8.9 x 8.6	...	3.87 42
105	3.0	6 12	9.7 x 10.2 x 8.6	...	5.26 52
106	4.0	10 0	12.1 x 10.5 x 10.2	...	6.99 52
107	6.0	12 0	14.0 x 10.2 x 11.8	...	10.35 67
118	8.0	18 0	14.0 x 12.7 x 11.8	...	13.51 97
119	10.0	25 0	17.2 x 12.7 x 14.0	...	16.95 *

60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60V	1.93 36
126	1.0	3 4	8.9 x 7.7 x 7.7	...	2.70 36
127	2.0	6 4	9.9 x 9.6 x 8.6	...	4.25 42
125	3.0	8 12	12.1 x 9.9 x 10.2	...	6.46 52
123	4.0	13 12	12.1 x 11.8 x 10.2	...	8.36 67
40	5.0	12.00	14.0 x 10.2 x 11.8	...	9.85 67
120	6.0	15 8	14.0 x 12.1 x 11.8	...	12.14 82
121	8.0	25.00	14.0 x 14.7 x 11.8	...	13.65 *
122	10.0	25 0	17.2 x 12.7 x 14.0	...	20.09 *
189	12.0	29.00	17.2 x 14.0 x 14.0	...	22.49 *

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P £ p
238	200	2	2.8 x 2.6 x 2.0	3-0-3	1.31 10
212	1A, 1A	1 4	6.1 x 5.8 x 4.8	0-5-0-6	1.52 22
13	100	4	3.9 x 2.6 x 2.9	9-0-9	1.12 10
235	330, 330	4	4.8 x 2.9 x 3.5	0-9-0-9	1.52 10
207	500, 500	1 00	6.1 x 5.4 x 4.8	0-8-9-0-8-9	2.03 22
208	1A, 1A	1 12	7.0 x 6.4 x 6.1	0-8-9-0-8-9	2.73 30
236	200, 200	1 4	4.8 x 2.9 x 3.5	0-15-0-15	1.52 10
214	300, 300	1 4	6.1 x 5.8 x 4.8	0-20-0-20	1.60 22
221	700 (d.c.)	1 8	7.0 x 6.1 x 6.1	20-12-0-12-20	1.41 30
206	1A, 1A	1 2	8.3 x 7.7 x 7.9	0-15-20-0-15-20	3.08 38
203	500, 500	2 4	8.3 x 7.0 x 7.0	0-15-27-0-15-27	2.82 38
204	1A, 1A	3 4	8.9 x 7.7 x 7.7	0-15-27-0-15-27	2.86 38

*Carriage via B.R.S.

PLEASE ADD 10% FOR V.A.T.
INCLUDING P. & P.


BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & ALDGATE EAST

parts for PRACTICAL ELECTRONICS projects. "One Source" buying makes sense—saves you time, money and postage.

After many requests, *Electro Spares* are now supplying lists of components for ALL the projects featured in "Practical Electronics" commencing July 1973 issue. Just forward a S.A.E. (preferably 9" x 4" minimum) stating which project is of interest to you—we will forward an individually priced list of components required. No need to buy a full kit—you need only purchase the parts you require at any one time. All *Electro Spares* supplied components are new, branded products of reputable manufacturers and carry full makers' guarantee. We regret we cannot supply lists for projects published before July 1973 issue.

"P.E. RONDO" QUADRAPHONIC SOUND SYSTEM

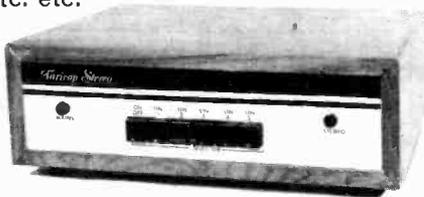Complete kits for the entire P.E. Rondo Project will be available as this appears in the magazine. These contain top quality components with fibre glass p.c. board, etc. etc.



"P.E." F.M. VARICAP STEREO TUNER

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973.

Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "no problem" construction requiring only a few simple setting up adjustments with a d.c. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator. Fibre Glass P.C. Board, neat slim-line cabinet, with brushed aluminium front panel, pushbuttons, etc. etc.

IDEAL FOR USE WITH THE "TEXAN",
"P.E. GEMINI" AND ANY GOOD
QUALITY STEREO AMPLIFIER.

ALL PARTS for Varicap tuner and Gemini amplifier supplied separately.

Please send S.A.E. for full details of any of the above or call yourself. Visitors welcome—easy parking.

"P.E. GEMINI" STEREO AMPLIFIER

QUALITY HI-FI FOR THE
HOME CONSTRUCTOR. 30 Watts (R.M.S.)
per Channel into 8 ohms!
Total Harmonic Distortion 0.02%!
Frequency Response (—3 dB) 20 Hz—
100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc. etc., price 55p plus 4p postage.

Our new, low comprehensive price list is supplied with each booklet, or prices for components supplied separately on receipt of large S.A.E.

FOR PEOPLE WHO REQUIRE THE
BEST—IT HAS TO BE THE "p.e. gemini"

ELECTRO SPARES

The Component Centre of the North.

288 Ecclesall Road
Sheffield S11 8PE
Tel.: Sheffield (0742)
668888

es

NEW QUICK and EFFICIENT MAIL ORDER DEPARTMENT


Introducing the new

LASKYS

INCORPORATING LASKYS RADIO LTD. & G. W. SMITH & CO. (RADIO) LTD.

Following the successful merger in 1972 of **LASKYS RADIO LTD. & G. W. SMITH & CO. (RADIO) LTD.**

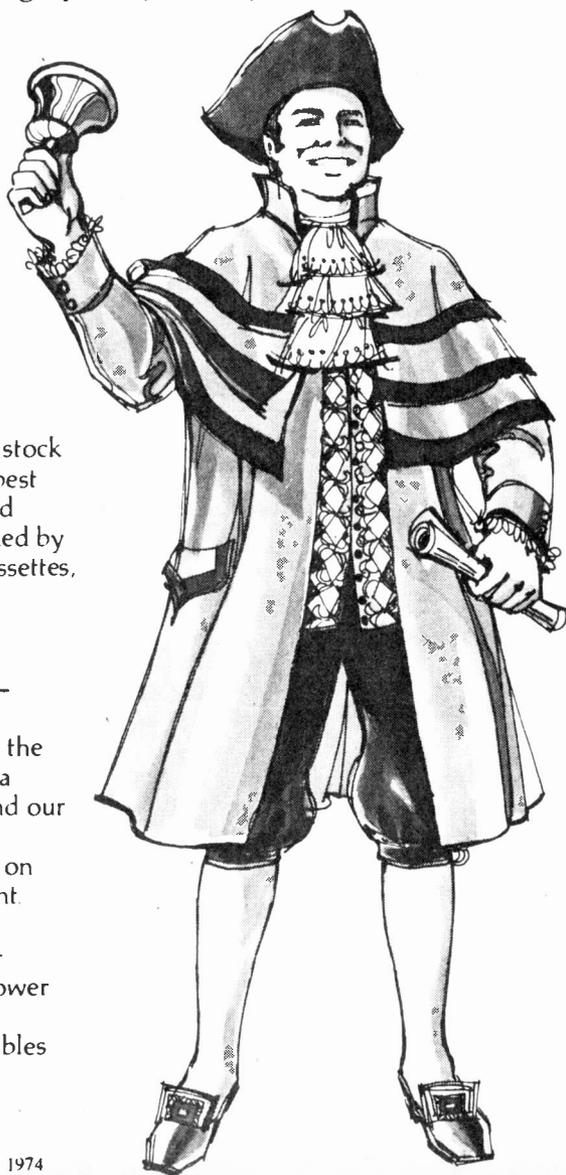the U.K.'s two leading audio retailers through Audiotronic Holdings Ltd. the final phase of the integration has now been completed. One retail company trading under the name of "Laskys" has been formed to bring you a wider choice of equipment, highly competitive prices and a better than ever service.



LASKYS RANGE—We stock the widest range of the best equipment in the U.K. and probably the world, backed by accessories, tapes and cassettes, components and other electronic equipment.

LASKYS BRANCHES—We have 24 branches throughout London and the provinces each holding a comprehensive range and our staff will be pleased to demonstrate and advise on your choice of equipment.

LASKYS PRICES—Our enormous purchasing power together with reduced administration costs enables us to offer you the most competitive prices to be found in the U.K.

LASKYS GUARANTEE—All equipment purchased from us is offered with a full 12 months guarantee including parts and labour.

LASKYS SERVICE—At head office we have a fully equipped service department and extensive stocks of spares.

LASKYS MAIL ORDER—We offer a speedy and efficient service. Immediate attention given to all orders.

LASKYS EXPORT—Personal exports arranged for overseas visitors. Goods despatched to all parts of the world through our Export Mail Order Department.

LASKYS

INCORPORATING LASKYS RADIO LTD & G W SMITH & CO (RADIO) LTD

ALL PRICES EXCLUDE VAT



WALKIE TALKIES

SKYFON 100mW
OUR PRICE £24.95 per pair
 P302 Two Channel 300mW
OUR PRICE £52.50 per pair
 P1003 Three Channel 1 Watt
OUR PRICE £71.25 per pair
 P&P 50p per pair

LB3 TRANSISTOR TESTER

Tests ICO and BPNP/NPN. Operates from 9V battery. Complete with all instructions etc.
OUR PRICE £3.95 P&P 20p



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.
OUR PRICE £4.50 P&P 20p



BELCO Sine Square Wave CR OSCILLATOR

Sine 18 x 200,000Hz Square 18 x 20,000Hz. Maximum output +10dB (10k ohms) Operates from internal batteries. Attractive two tone case. Size: 196 x 127 x 50mm.
OUR PRICE £17.50 P&P 17p



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 1/4" diameter shafts. Bulk quantities available.
 25 WATT 10/25/50/100/250/500/1000 Ohms. £1.15 P&P 10p
 50 WATT 10/25/50/100/250/500/1000/2500/5000 Ohms. £1.62 P&P 10p
 100 WATT 1/5/10/25/50/100/250/500/1000/2500 Ohms. £2.34 P&P 15p



YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V 50/60Hz. Variable output 0-250V
MODEL S280 GENERAL PURPOSE BENCH MOUNTING
 P&P
 1A £8.75 30p
 2.5A £10.00 35p
 5A £14.70 37p
 8A £25.50 50p
 10A £28.10 75p
 12A £29.50 100p
 20A £72.50 125p
 25A £72.50 130p
 40A £103.10 150p
MODEL S260B
 2.5A £8.75 30p
 1A £10.00 35p



AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.
 80W £2.75 P&P 18p
 150W £3.50 P&P 18p
 300W £4.50 P&P 23p
 500W £6.95 P&P 33p
 1000W £9.50 P&P 38p
 1500W £12.50 P&P 43p
 2250W £20.95 P&P 50p
 5000W £44.95 P&P £1

SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52 Ohm Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.
OUR PRICE £4.25 P&P 25p



240° Wide Angle 1mA METERS

MW 1-6 60x60mm
£3.97 P&P 15p
 MW 1-8 80x80mm
£4.97 P&P 15p



CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS AND EDUCATIONAL AUTHORITIES.

Over 2,000 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.




Clear Plastic Model SD830



Enlarged Window Model S80



Bakelite Model 65

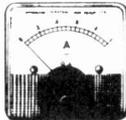

Clear Plastic Model 45P



Model ED107

RANGE	MR 38P	MR 45P	MR 52P	MR 65P	MR 85P	MR 65	S 80	SW 100	SD 460	SD 640	SD 830	PE 70	ED 107
25uA	—	—	—	—	—	£4.60	—	—	—	—	—	—	—
50uA	£2.55	£2.70	£3.50	£3.70	£4.40	£3.55	£3.50	£4.15	£2.80	£3.05	£3.40	£3.75	£6.90
100uA	£2.45	£2.60	£3.00	£3.15	£4.25	£3.00	£3.40	£3.95	£2.75	£3.00	£3.35	£3.60	£6.40
200uA	£2.40	£2.50	—	£3.05	£4.05	—	—	—	£2.70	£3.00	£3.30	£3.40	—
500uA	£2.25	£2.45	£2.65	£2.75	£3.90	£2.70	£3.05	£3.70	£2.55	£2.95	£3.15	£3.20	—
50-0-50uA	£2.50	£2.85	£3.05	£3.15	£4.25	£3.05	£3.40	£3.95	£2.80	£3.05	£3.40	£3.60	£6.40
100-0-100uA	£2.40	£2.50	£2.95	£3.10	£4.05	£3.00	£3.30	£3.90	£2.75	£3.00	£3.35	£3.50	—
500-0-500uA	£2.25	£2.40	—	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
1mA	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	£3.00	£3.60	£2.60	£2.90	£3.10	£3.20	—
1-0-1mA	£2.25	—	—	—	£3.90	£2.60	—	—	—	—	—	—	—
2mA	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
5mA	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	£2.60	£2.90	£3.10	—	—
10mA	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	£2.60	£2.90	£3.10	—	—
20mA	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
50mA	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	£2.60	£2.90	£3.10	—	—
100mA	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	£2.60	£2.90	£3.10	—	—
150mA	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
200mA	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
300mA	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
500mA	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	£2.60	£2.90	£3.10	—	—
750mA	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
1A DC	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	£3.00	£3.60	£2.60	£2.90	£3.10	—	£5.95
2A DC	£2.25	—	—	—	—	£2.60	—	—	—	—	—	—	—
5A DC	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	£3.00	£3.60	£2.60	£2.90	£3.10	—	£5.95
10A DC	£2.25	—	—	£2.60	—	—	—	—	£2.60	£2.90	£3.10	—	—
15A DC	£2.25	—	—	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
20A DC	£2.25	—	—	£2.60	—	—	—	—	—	—	—	—	—
30A DC	—	—	—	£2.80	£3.95	£2.60	—	—	—	—	—	—	—
50A DC	—	—	—	£2.90	—	£2.60	—	—	—	—	—	—	—
3V DC	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
5V DC	—	—	—	£2.60	—	£2.60	—	—	£2.60	£2.90	£3.10	—	£5.95
10V DC	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	£2.60	—	£3.10	—	£5.95
15V DC	£2.25	—	—	—	—	—	—	—	—	—	—	—	£5.95
20V DC	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	£3.00	£3.60	—	£2.90	£3.10	—	£5.95
50V DC	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	£3.00	£3.60	£2.60	£2.90	£3.10	—	£5.95
100V DC	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
150V DC	£2.25	—	—	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
300V DC	£2.25	£2.40	£2.50	£2.60	£3.90	£2.60	£3.00	£3.60	£2.60	£2.90	£3.10	—	£5.95
500V DC	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
750V DC	£2.25	—	—	—	—	—	—	—	—	—	—	—	—
15V AC	£2.30	£2.45	£2.60	£2.80	£3.95	—	—	—	£2.70	£3.00	£3.30	—	—
30V AC	—	—	—	—	—	£2.65	—	—	—	—	—	—	—
50V AC	£2.30	—	—	£2.80	—	£2.65	—	—	—	—	—	—	—
150V AC	£2.30	—	—	£2.80	—	£2.65	—	—	—	—	—	—	—
300V AC	£2.30	£2.45	£2.60	£2.80	£3.95	£2.65	£3.00	£3.70	£2.70	£3.00	£3.30	£3.25	—
500V AC	£2.30	—	—	£2.80	—	£2.65	—	—	—	—	—	—	—
S Meter 1mA	£2.30	£2.50	£2.60	£2.85	£3.90	—	—	—	—	—	—	—	—
VU Meter	£2.65	£2.70	£3.60	£3.70	£4.55	£3.65	£3.70	£4.30	£2.90	£3.15	£3.50	£3.85	—
1A AC	—	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
5A AC	—	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
10A AC	—	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
20A AC	—	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
30A AC	—	£2.40	£2.50	£2.60	£3.90	£2.60	—	—	—	—	—	—	—
50A AC	—	—	—	—	—	£2.60	—	—	—	—	—	—	—
50mA AC	—	—	—	—	£2.60	—	—	—	—	—	—	—	—
100mA AC	—	—	—	—	£2.60	—	—	—	—	—	—	—	—
200mA AC	—	—	—	—	£2.60	—	—	—	—	—	—	—	—
500mA AC	—	—	—	—	£2.60	—	—	—	£2.60	—	—	—	—
50mV DC	—	—	—	—	—	—	—	—	£2.90	—	—	—	—
100mV DC	—	—	—	—	—	—	—	—	£2.90	—	—	—	—
500mA/5A DC	—	—	—	—	—	—	—	—	—	—	—	—	£7.00
1/15A DC	—	—	—	—	—	—	—	—	—	—	—	—	£7.00
5/15V DC	—	—	—	—	—	—	—	—	—	—	—	—	£7.00
5/50V DC	—	—	—	—	—	—	—	—	—	—	—	—	£7.00

SEW PANEL METERS—SIZES AND FIXING INFORMATION

	Front	Panel Hole	Fixing		Front	Panel Hole	Fixing
Model 38P	42 x 42mm	32mm dia.	4 studs	Model SW100	100 x 80mm	65mm dia.	4 studs
Model 45P	50 x 50mm	38mm dia.	4 studs	Model SD460	59 x 46mm	38mm dia.	4 studs
Model 52P	60 x 60mm	48mm dia.	4 studs	Model SD640	85 x 64mm	45mm dia.	4 studs
Model 65P	86 x 78mm	57mm dia.	4 studs	Model SD830	110 x 83mm	58mm dia.	4 studs
Model 85P	120 x 110mm	98mm dia.	4 studs	Model PE70	60 x 34mm	70 x 31mm	2 holes
Model 65	80 x 80mm	64mm dia.	4 studs	Model ED107	Size: 100 x 90 x 150mm high	including terminals.	
Model S80	80 x 80mm	65mm dia.	4 studs				



ALL PRICES EXCLUDE VAT

PS200 Regulated POWER SUPPLY UNIT
Solid state, Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.
OUR PRICE £19.95 P&P 25p




PS100B Regulated POWER SUPPLY UNIT
Solid state, Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 159mm.
OUR PRICE £11.97 P&P 25p



MCA220 Automatic Voltage Stabiliser
Input 88-125V AC or 176-250 V AC. Output 220/240V AC. 200V A rating.
OUR PRICE £11.97 P&P 50p



TO3 Portable OSCILLOSCOPE
3" tube. Y amp sensitivity 0.1Vp/p/CM. Bandwidth: 1.5Hz-1.5MHz. Input Impedance 2Mohms, 25pF. X amp sensitivity 0.9Vp/p/CM. Bandwidth 1.5Hz-800kHz. Input impedance 2 Meg Ohms, 20pF. Time base, five ranges 10Hz to 300kHz. Synchronisation. Internal or external. Illuminated scale 140 x 215 x 330mm. Weight 15½lbs. 220/240V AC. Supplied brand new with handbook.
OUR PRICE £52.50 P&P 50p

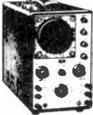


RUSSIAN C116 Double Beam OSCILLOSCOPE
5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular ultra 5" x 4" CRT. Calibrated triggered sweep from 0.2µsec to 100 milli-sec/cm. Free running time base 50Hz-1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.
OUR PRICE £87.00 Carr. paid



C15 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mms: 0.1-25 HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mms: 0.3-25 Preset triggered sweep 1-300µsec. Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V AC.
OUR PRICE £39.00 Carr. paid



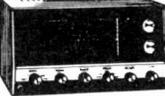LAFAYETTE HA600 Receiver
General coverage 150-400kHz, 550 kHz-30MHz. FET front end 2 mechanical filters, product detector. Noise limiter, variable BFO, S Meter. Bandspread and RF gain. 220/240V AC or 12V DC. Brand new with instructions.
OUR PRICE £50.00 P&P 50p




SUPER VALUE TOP QUALITY TRIO communications equipment

TRIO JR599 RECEIVER
Nine wave bands covering 1.8-29.7 MHz, 144-146MHz and 10MHz VVVV SSB, CW, AM and Phono. AF output is more than 1 watt. S Meter. Squelch control. BFO. Variable AF and RF controls. 4-16 ohm output and jack for phono. Power requirement 100/240V AC, 12/14V DC. Size: 270 x 140 x 310mm.
OUR PRICE £132.50 Carr. paid



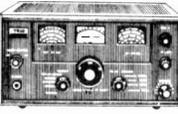TRIO 9R590S RECEIVER
Four bands covering 550kHz to 30 MHz continuous and electrical bandspread on 10, 15, 20, 40, and 80 mtrs. 8 wave plus 7 diode circuit. 4 to 8 ohm output and phono jack. SSB, CW, ANL, variable BFO. S Meter and separate band spread dial. IF frequency 445kHz, audio output 1½ watt. Variable RF and AF gain controls. 115/250V AC, with instructions.
OUR PRICE £42.50 Carr. paid




TRIO JR310 SSB RECEIVER
Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1MHz bands and VVVV 15MHz SSB, AM and CW. AF output more than 1W. Crystal controlled BFO for SSB. S Meter, ANL, etc. AC 110/120-220/240V. Size: 330 x 175 x 310mm.
OUR PRICE £75.00 Carr. paid



TRIO TR2200 RECEIVER
Fully transistorised portable VHF receiver. Will transmit and receive on six channels between 144-146MHz. 1 watt transmitter. 12V DC internal or external supply. Built-in charger for Ni-Cad cells. Power/volume switch, squelch control, channel selector, mic. socket, earphone/external speaker socket. Complete with microphone and 144.48, 144.72 & 145.32 crystals. Size: 179 x 58 x 180mm.
OUR PRICE £79.50 Carr. paid



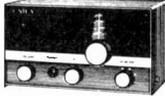UNR30 RECEIVER
Four bands covering 550 KHz-30MHz BFO. Built-in charger. Operates from 220/240V AC. Brand new with instructions.
OUR PRICE £15.75 P&P 37p



BELTEK W5400 CAR TRANSCIVER
Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off/volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. PTT switch, three headset w/soft ear pads. 144.48, 144.6 and 145MHz, mounting bracket and instructions. Size: 150 x 70 x 220mm.
OUR PRICE £75.00 P&P 50p



RUH6 Reflex Horn Speaker
Built-in driver unit. Impedance 16 ohms. Power rating 10W. Response 380-7000Hz. Size app. 6" x 6". Weather and shock protected.
OUR PRICE £4.97 P&P 30p



TE1018 Deluxe Mono High Impedance Headset.
Sensitive magnetic headset with soft ear pads. Impedance 2,600 ohms (600 ohms DC). Frequency response: 200-4,000Hz.
OUR PRICE £2.25 P&P 30p



DH02S STEREO HEADPHONES
Wonderful value and excellent performance combined. Adjustable head band. Impedance 8 ohms 20-12,000Hz. Complete with lead and plug.
OUR PRICE £2.25 P&P 30p



LH02S STEREO HEADPHONES
Light weight headphones with padded ear pieces. 4/16 ohms 20-20,000Hz. Complete with 5' lead and plug.
OUR PRICE £1.97 P&P 30p



BH001 HEADSET and Bnm Microphone
Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.
OUR PRICE £5.95 P&P 30p



SH62S STEREO HEADPHONES
Outstanding value. With soft ear pads and adjustable headband. Impedance 8 ohms, 20-20,000Hz. Complete with lead and stereo plug.
OUR PRICE £1.87 P&P 30p



SPECIAL PURCHASE!! BSR 8 Track Player Chassis
Famous BSR 8 track chassis as used in model TDBS complete with silver and black escutcheon, ready to fit into cabinet. Output 125mV, 240V AC. Overall size app. 185 x 215 x 80mm.
OUR PRICE £8.95 P&P 50p



HIGH QUALITY CONSTRUCTION KITS
WE ARE APPOINTED STOCKISTS AT ALL BRANCHES



All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing 15p per kit.

AF20 Mono amplifier.....	£4.80
AF30 Mono pre-amplifier.....	£2.61
AF310 Mono amplifier.....	£5.91
AT5 Auto light control.....	£2.58
AT30 Photo cell switch unit	£5.70
AT50 400W Light dimmer/speed control.....	£4.80
AT55 1,300W Light control/speed control.....	£5.70
AT56 2,200W Light dimmer/speed control.....	£6.90
AT60 1 channel light control	£7.80
AT65 3 channel light control	£14.55
HF61 MW transistor radio.....	£3.33
HF75 FM transistor radio.....	£2.88
HF310 FM tuner unit.....	£15.81
HF326 Deluxe FM tuner unit	£24.12
HF330 FM stereo decoder.....	£9.96
HF395 Aerial amplifier for AM/FM bands II, III, III.....	£1.77
GP310 PSU 200V pre-amplifier.....	£21.27
GU330 Tremolo unit.....	£7.50
NT10 PSU 100mA/9-12V.....	£6.15
NT300 Professional stabilised PSU, 2 x 30V, 2.2A.....	£12.51
NT305 Transistor converter 12/15V AC/DC to 6V, 7.5V or 9V DC.....	£4.50
NT310 PSU 240V AC to 2 x 18V DC at 2A.....	£4.80
NT315 PSU 240V AC to 4.5-15V DC at 500mA.....	£9.57
A1 100mV output stage.....	£1.65
A2 Pre-amplifier.....	£1.26
A3 Diode receiver.....	£2.00
A4 Flasher.....	£1.09
A5 Treble filter.....	£1.05
A6 Monostable multivibrator	£1.02
A7 RC generator.....	£1.06
A8 Bass filter.....	99
A9 Treble filter.....	99
A10 CCR filter.....	99

NEW FROM JOSTY-KIT 'Amateur Electronics'
The professional book for the amateur covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for making ten of the kits listed above.
OUR PRICE £3.30 (No VAT)
P & P 25p plus VAT

FRUSTRATED EXPORT ORDER!!
Philco Ford 5245 Mains Tape Recorder.
2 track BSR deck with push button controls for easy operation. Tape counter and volume control. Complete with hand microphone, direct recording lead, 1,200' reel of tape and spare reel. 200/250V AC. Fully guaranteed.
OUR PRICE £17.50 P&P 75p



Philco Ford 5248 Mains Tape Recorder.
Four track, two speed, two track. Piano key type controls, tape counter, recording level meter, volume and tone controls etc. Complete with hand, microphone lead for direct recording 1,800' of tape and spare reel. 200/250V AC. Fully guaranteed.
OUR PRICE £27.50 P&P 75p



BVD5 Vernier TUNING DIAL
App: 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. Deep including knob and coupling. 1/2" diam. shaft.
OUR PRICE £1.62 P&P 15p



SINCLAIR CAMBRIDGE CALCULATOR
To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.
OUR PRICE £24.95 P&P free



ALSO AVAILABLE READY BUILT
Recommended Price £29.95
OUR PRICE £27.20 P&P 25p

MINUTEMAN MM3 POCKET CALCULATOR
Size only 103 x 77 x 25mm. 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.
OUR PRICE £23.95 P&P 25p



Also available—SINCLAIR EXECUTIVE
Recommended Price £39.00
OUR PRICE £35.45
SINCLAIR EXECUTIVE WITH MEMORY
Recommended Price £49.00
OUR PRICE £40.75

EMI LOUSPEAKERS
Model 350 13 x 8" with twin tweeter/crossover 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.
OUR PRICE £7.25 each P&P 37p
Model 450 13 x 8" with twin tweeter/crossover 35-13,000Hz. 8 watts RMS. Available 8 or 15 ohms.
OUR PRICE £3.62 each P&P 25p



MP7 MIXER-PREAMPLIFIER
5 Microphone inputs each with individual gain control. Enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics, 3 x 3mV 30k-200k; Phono, 500 ohms, Phono, Mag. 40k 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.
OUR PRICE £8.97 P&P 20p



KE630 3 Station INTERCOM
Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries.
OUR PRICE £5.25 P&P 50p



1021 Stereo Listening Station
For balancing and gain selection of left and right channels with additional facility for stereo headphone switching. Two gain controls, speakers on-off side switch, stereo headphone socket.
OUR PRICE £2.25 P&P 15p



FM TUNER CHASSIS
6 transistor high quality tuner. Size only 153 x 101 x 63mm 31.15 standard. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.
OUR PRICE £5.95 P&P 20p



A1018 FM TUNER
Specification as above FM chassis but complete in cabinet with on/off switch. Size: 184 x 86 x 127mm.
OUR PRICE £9.65 P&P 30p
Stereo multiplex adaptor £4.97





ALL PRICES EXCLUDE VAT

INCORPORATING LASKYS RADIO LTD & G W SMITH & CO (RADIO) LTD

OT55B DIGITAL CLOCK MECHANISM

Features
24 hour alarm setting with built in buzzer On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switching rating 250V, 3 Amp.
OUR PRICE £5.95 P&P 30p



AUDIOTRONIC AR3000 AM/FM Portable Radio

4 wave-bands covering FM 87-105MHz MW: 510-1605kHz LW: 145-285 kHz, SW: 5.8-12.5MHz. Push button wave change plus AFC and on/off. Thumbwheel tuning. Slider volume and tone controls. Earphone socket. Built-in and telescopic aerials. Car aerial socket. Battery and mains operation.
OUR PRICE £14.95 P&P 50p




AUDIOTRONIC ACD660 Stereo Cassette Deck

A beautifully styled four track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm microphone input sockets etc, etc. Frequency response: 40-12kHz (40-16kHz CrO2), S/N: -45dB, Crosstalk 45dB, Separation: -35dB, Noise limiter -6dB at 10kHz. Complete with connecting leads.
OUR PRICE £39.50 P&P 50p



BINATONE DS100 Digital Clock

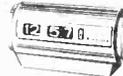240V mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Size 159 x 76 x 82mm.
OUR PRICE £4.50 P&P 30p



SPECIAL BARGAIN!! PHONIC 10 Two Way Speakers

Matched pair of compact book-shelf speakers of unique design. Incorporating a 2" high frequency unit & 8" woofer. 8 ohms impedance. Size: 348 x 228 x 110mm.
OUR PRICE £8.85 Pair P&P 50p



AUDIOTRONIC DOLBY B Noise Reduction Units

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size: 460 x 228 x 79mm. AC 220/240V



AUDIOTRONIC AMR900 Global AM/FM Portable Radio

10 wave-bands covering AM: 535-1605kHz LW: 150-380 kHz, MB 1.6-4MHz, SW1: 4-9MHz, SW2: 8-1.6 MHz, SW3: 16-24MHz, PSB1: 30-50 MHz, PSB2: 148-174MHz, FM 88-108MHz, Air: 108-136MHz. Feature time zone trap and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC on FM, 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm.
OUR PRICE £36.00 P&P 50p



AUDIOTRONIC LOW NOISE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C60	£1.37	£2.61	£6.16
C90	£1.95	£3.70	£8.71
C120	£2.38	£4.50	£10.65

Postage and Packing 15p

RECORD DECKS P&P 50p

BSR McDONALD

C114 Mini.....	£3.95
C129 Mono.....	£5.50
C137 Stereo.....	£7.00
510/TPD1.....	£12.55
610.....	£10.55
610/TPD1.....	£13.90
715.....	£21.15
810.....	£26.30
MP60.....	£8.25
MP60/ADC K8.....	£10.90
MP60/TPD1.....	£13.20
HT70.....	£11.60
HT70/ADC K7E.....	£14.25
HT70/TPD1.....	£16.55

CONNOISSEUR

BD1 Kit.....	£10.20
BD1 Chassis.....	£12.50
BD2/SAU2/Chassis.....	£25.50
BD2/SAU2/Plinth/Cover.....	£32.25

GARRARD

1025T Stereo.....	£4.95
2025T Less Cartridge.....	£6.35
SP25 Mk3/M44A.....	£6.95
SP25 Mk3.....	£9.25
SP25 Mk3/G800.....	£9.95
SP25 Mk3/M75-6.....	£13.90
SP25 Mk4.....	£10.90

RECORD DECK PACKAGES

BSR McDONALD

210/SC7M.....	£7.40
C129.....	£9.50
MP60/G800.....	£16.50
MP60/TPD1/ADC K8.....	£15.80
MP60/M44-7.....	£17.50
HT70/TPD1/G800.....	£19.20
610/TPD1/ADC K8.....	£18.10

GARRARD

2025TC/9TA-HCD.....	£11.35
SP25 Mk3/G800.....	£17.10
SP25 Mk3/M44E.....	£18.25
SP25 Mk3/M44-7.....	£27.50
SP25 Mk3/M55E.....	£18.80
SP25 Mk3 Module/M75-6.....	£19.45
AP76/G800.....	£26.75
AP76/G800E.....	£28.95
AP76/M44-7.....	£27.50
AP76/M44E.....	£28.00
AP76/M55E.....	£28.60
AP76/M75E.....	£29.20
AP76/M75EJ.....	£31.20

GOLDRING

G101/PC/G800.....	£23.70
GL72/G800.....	£34.20
GL75/G800.....	£39.10

PHILIPS

GA105/GP200.....	£12.40
GA160/GP200 Teak.....	£19.50
GA160/GP200 Walnut.....	£25.45
GA205.....	£17.40
GA207.....	£20.90

RANK DOMUS

BD20000.....	£43.60
BA4000.....	£53.95
BD6000.....	£57.50

WHARFEDALE

Linton W30 Teak.....	£23.90
Linton W30 White.....	£25.10

PROCESS 4

For use with semi-professional tape recorders. Frequency response 30Hz-20kHz ± 2 dB. S/N better than 70dB. Full source/tape monitoring. Switchable multiplex filter. Supplied with test tape.
OUR PRICE £50.00 P&P 50p

PROCESS 2

For use with cassette and tape recorders. Frequency response 30Hz-20kHz. Switchable multiplex filter. 2 Dolby calibration meters. Off tape monitoring. S/N better than 70dB. Supplied complete with test tape or cassette.
OUR PRICE £34.50 P&P 50p



CT5050 Cassette Recorder

Instant recording and playing. Piano key controls. Automatic level control. Built-in speaker. Complete with remote control microphone, carrying case and shoulder strap.
OUR PRICE £8.50 P&P 50p



AUDIOTRONIC AHP8-D 8 Track Stereo Tape Deck

Can be used with most hi-fi amplifiers. Push button track select & illuminated track indicator. Attractive cabinet with black and silver trim. Output level 750mV. 220/240V AC.
OUR PRICE £11.95 P&P 50p



SPECIAL BARGAIN!! STEREOSOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 368 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with Din lead.
OUR PRICE £12.95 P&P 50p



AUDIOTRONIC STEREO HEADPHONES

LSH20 Individual volume controls. Stereo/mono switch. 8 ohms. 19,000Hz.
£3.75 P&P 30p



LSH30 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000Hz.
OUR PRICE £5.95 P&P 30p



LSH40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000Hz.
OUR PRICE £7.50 P&P 30p



LSH60 3" speaker units. 8 ohms. Complete with zippered carrying case. 20-20,000Hz.
OUR PRICE £8.95 P&P 30p



LSH50 Electrostatic with self powered energiser. and control unit, with headphone speaker selector. 4-32 ohms. 20-24,000Hz.
OUR PRICE £16.95 P&P 30p



LQH400 4 channel dynamic head phones. Each earpiece has four drive units. 4-32 ohms. 20-20,000Hz.
OUR PRICE £9.95 P&P 30p



CENTRAL LONDON

10 Tottenham Court Road, W.1. Tel. 01-637 2232
27 Tottenham Court Road, W.1. Tel. 01-637 3715
33 Tottenham Court Road, W.1. Tel. 01-636 2605
42/45 Tottenham Court Road, W.1. Tel. 01-636 0845
87 Tottenham Court Road, W.1. Tel. 01-580 3739
257/8 Tottenham Court Road, W.1. Tel. 01-580 0670
21 Old Compton Street, W.1. Tel. 01-437 9369
3 Lisle Street, W.C.2. Tel. 01-437 8204
34 Lisle Street, W.C.2. Tel. 01-437 9155
118 Edgware Road, W.2. Tel. 01-723 9789
193 Edgware Road, W.2. Tel. 01-723 6211
207 Edgware Road, W.2. Tel. 01-723 3271
311 Edgware Road, W.2. Tel. 01-262 0387
346 Edgware Road, W.2. Tel. 01-723 4453
382 Edgware Road, W.2. Tel. 01-723 4194
109 Fleet Street, E.C.4. Tel. 01-353 5812
152/3 Fleet Street, E.C.4. Tel. 01-353 2833
378 Harrow Road, W.9. Tel. 01-286 9530

ESSEX

86 South Street, Romford Tel. 70-20218

SURREY

1046 Whitgift Centre, Croydon Tel. 01-681 3027
27 Eden Street, Kingston Tel. 01-546 7845
32 Hill Street, Richmond Tel. 01-948 1441

KENT

53/57 Camden Road, Tunbridge Wells Tel. 0892-30272

LEICESTERSHIRE

45 Market Place, Leicester Opening mid January

HEAD OFFICE & MAIL ORDER DEPARTMENT - Unit 4, The Hyde Industrial Estate, The Hyde, London NW9 6JJ Telephone 01-205 3735

Many special clearance offers and end of stock lines for personal shoppers at our **BARGAIN CENTRE!** 87 TOTTENHAM COURT ROAD, LONDON W.1.

HUGE STOCKS OF WORLD FAMOUS HI-FI AND AUDIO MAKES INCLUDING-
ACOS - AKG - AKAI - ALPHA - ALBANY HOUSE - AMSTRAD - ARMSTRONG - AUDIOTRONIC - AUDIO DEVELOPMENT - AUDIO TECHNICA - BAKER - BASF - BSR - CAMBRIDGE - CELESTION - CONNOISSEUR - DECCA - EAGLE - ELIZABETHAN - ELPICO - EMI - EMPIRE - FANE - FERGUSON - FERROGRAPH - FIDELITY - GARRARD - GOLDRING - GOODMANS - GRADO - HACKER - HITACHI - HOWLAND WEST - IMF - JBL - JORDAN WATTS - JOSTY KIT - JVC - NIKON - KEF - KELETRON - KELLAR - KOSS - LEAK - LEAR - JET - MEDWAY - METROSOND - MOTOROLA - NATIONAL - NEAT - NIKKO - ORTOFON - PHILIPS - PICKERING - PIONEER - PYE - QUAD - RADIOMOBILE - R ALLAN - ROGERS - ROTEL - SANSUI - SANYO - SANNHEISER - SHARP - SHURE - SIEMENS - SINCLAIR - SME - SONAB - SONY - TANDBERG - TANNOR - TEAC - TECHNICS - TELETON - THORENS - TRIO - ULTRA - WHARFEDALE - YAMAHA
Send S.A.E. for latest comprehensive Price List!

MAIL ORDER SPECIALISTS
We offer a speedy and efficient service by Mail Order. Remember to add 10% VAT to total value of goods including Carriage and Packing, and send cash with order to Head Office.

TO AVOID DELAYS PLEASE PRINT NAME AND ADDRESS CLEARLY IN CAPITALS.

PERSONAL EXPORT
Personal exports can be arranged for overseas visitors at all our branches. Goods despatched to most parts of the World through our Export Mail Order Department. Immediate attention given to all orders.




BARCLAYCARD & ACCESS HOLDERS WELCOME call into any branch or telephone your order to head office!

CREDIT TERMS for personal shoppers on sales of £50 and over, and Mail Orders of £80 and over. CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH A BANKERS CARD.

Prices correct at 14.12.73 but subject to change without notice E&OE

The Catalogue you MUST have!

HOME RADIO COMPONENTS

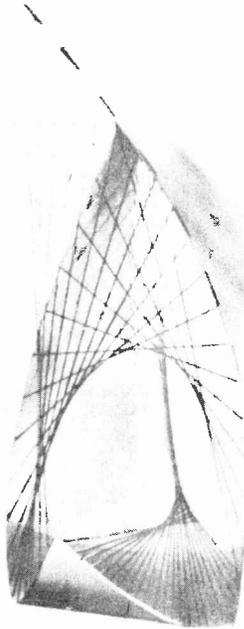

250 pages 11 3/4" x 8 1/4"

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p. plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

Please write Name and Address in block capitals

Name _____

Address _____



The price of 77p applies only to customers in the U.K. and to BFPO addresses

HOME RADIO (Components) LTD. Regd No 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

CONSERVATION

SUDDENLY, we are all conservationists. Not by any means as voluntary converts, but rather because we are victims of our own materialistic expansion. Circumstances now force us all to look twice at any proposed expenditure: the cost factor, if not an actual shortage of particular commodities, being a very effective brake to indiscriminate spending.

The old question, how to escape from the rat race must be in many minds. Complete self-sufficiency is an idle dream for members of modern industrialised and over-organised societies. But the man who is capable of applying his own skills to satisfy part—even a minor part—of his needs is obviously at an advantage compared with his less endowed fellows. Make-do-and-mend is a good, sensible philosophy, and never was more pertinent than at this present time of economic crisis.

The individual craftsman—in all senses of the word—is a true asset to the community. Most of us will have had cause at one time or another to regret the demise of certain professional craftsmen—in various trades—when we have required some special service to be performed. In place of that vanishing breed, the amateur “do-it-yourselfer” looks like becoming the torch bearer for traditional craftsmanship.

Social and cultural considerations apart, there is now a greater economic incentive for private individuals to acquire new skills, or to re-exercise dormant skills, through practical activities in their spare time. Those who have adopted electronics as a hobby are particularly fortunate, in that electronic circuits can be applied to help overcome many of the problems associated with fuel and power shortages.

Unlike many other industries, electronics cannot be accused of squandering vast amounts of raw materials. Yet it would be true and honest to admit that this rapidly expanding technology has been rapacious in its consumption of ideas and especially of circuit devices. Too often an interesting device has hardly seen the light of day before being made obsolescent by a “new generation”. Progress is fine, but perhaps quite a lot has been lost on the way.

Shortages in certain types of resistors, capacitors and solid state devices have already been experienced throughout the industry. This reflects the continuing healthy expansion of electronics, and is not primarily attributable to shortages in raw materials. If shortages in certain components do become really acute—and this is a possibility that must always be kept in mind—some of these neglected “obsolete” devices may be given proper attention and a new lease of life.

So as good conservationists we should on occasion take a look inside the Junk Box; check up on alternatives and substitutes, and if necessary devise modified circuits to permit the resuscitation of these victims of rapid technological advancement.

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*


Phone: 01-634 4301

Editorial & Advertising Offices:

Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452

Advertisements 01-634 4202

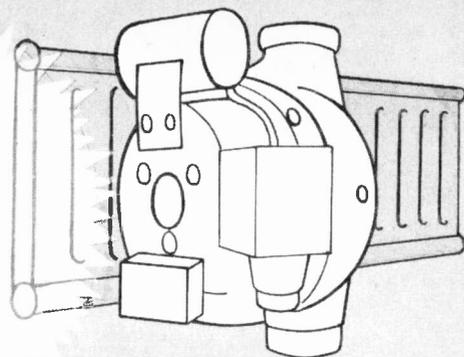MAINTAIN THE ESSENTIALS... WITH THIS 100W INVERTER - CHARGER



By R. VERRILL B.Sc.

THE present unit was developed by the author during the coal miners' strike of 1971. A home-made car battery charger was modified to work in reverse thus producing a 240V 50Hz supply.

During the four-hour power cuts the mains supply to the house was isolated at the main switch and the output of the inverter was plugged into a wall socket. It was then possible to operate such combinations as a 100W lamp, two 40W lamps and the stereo hi-fi system, or one 40W lamp and the central heating pump and solenoid valves of the gas-fired central heating system.

A 50 ampere-hour battery supplied adequate power for the duration of the four-hour cuts and a switch on the unit converted it back to the battery charger function, where up to about 10A could be obtained. This was sufficient to recharge the battery between cuts.

Such a unit can of course be used anywhere where a small portable supply is required for normally mains operated equipment.

CIRCUIT DESCRIPTION

The basic circuit diagram of the inverter/charger is shown in Fig. 2. The two-pole switch S1 is shown in the inverter position.

The output of a 100Hz multivibrator TR1, TR2 is fed to a flip-flop TR3, TR4 where the frequency is divided by two. The output from transistors TR3 and TR4 are two 50Hz square waves in antiphase with exactly one-to-one mark space ratio, although the multivibrator mark space ratio may differ widely from one to one as only one of its two timed periods is adjusted to obtain the required frequency.

The TR3/TR4 outputs are fed to power transistors TR5 and TR8 via drivers TR6 and TR7, so that a square wave of current flows alternately through the two halves of the transformer winding.

TUNED CIRCUIT

The capacitor C7 forms a tuned circuit with the transformer secondary inductance. C7 is selected to tune to 50Hz. The circuit is efficient since the transistors TR5 and TR8 operate in the saturated mode, i.e. only their low saturation voltage appears

COMPONENTS . . .

Resistors

R1	10k Ω	R10	10k Ω
R2	150k Ω	R11	220 Ω
R3	100k Ω	R12	560 Ω
R4	10k Ω	R13	47k Ω
R5	100k Ω	R14	100k Ω
R6	47k Ω	R15	10 Ω 7W wirewound
R7	220 Ω	R16	150 Ω
R8	560 Ω	R17	10 Ω 7W wirewound
R9	10k Ω	R18	150 Ω

All 5% tolerance, $\frac{1}{4}$ W except where noted

NOTE: R15 and R17 should be mounted $\frac{3}{8}$ in from board.

Capacitors

C1	0.05 μ F
C2	0.05 μ F
C3	250 μ F 16V
C4	0.01 μ F
C5	0.01 μ F
C6	1 μ F 45V RMS (63V d.c.)
C7	Select in test. Must be capable of withstanding mains a.c. conditions. 2 μ F, 600 V.W. available from Home Radio.

Potentiometers

VR1	100k Ω $\frac{1}{4}$ W preset	Plessey MPD
VR2	3 Ω 10A	Rheostat.

Transistors

TR1 to TR4	ZTX502 or BC212 (4 off) (see text)
TR5	2N3055
TR6 and TR7	BFS59 (2 off) or BFS60 or 61 (see text)
TR8	2N3055

- ✱ Capable of providing 80 to 100W output
- ✱ Battery charger up to 10A 12V d.c.
- ✱ Drive your central heating pump/solenoids
- ✱ Run 80W of filament lighting


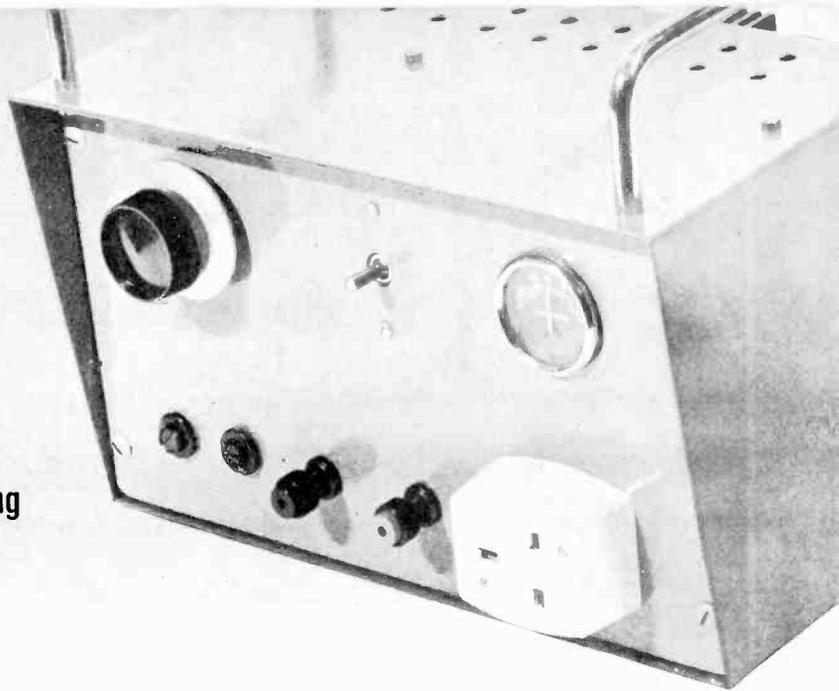


Fig. 1. Inverter output voltage waveforms showing the effect of tuning the transformer T1 by adjusting C7

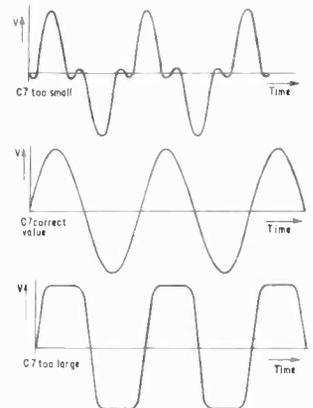

Diodes

- D1 to D4 IN914 or IN4148 or ZS120, etc. (4 off)
- D5 to D8 50V 5A silicon rectifier (4 off) or one potted 10A bridge rectifier Bi-Pak, AEI, Motorola, etc.

Miscellaneous

- Switch S1 Double pole change-over toggle switch with at least one pole rated for 10A d.c.
- Transformer T1 Primary, 240V 50Hz
Secondary 12.0-12V, 10A*
- Inductor L1 8mH 10A*
- Fuses FS1 10A
FS2 1A
- Glass fibre printed circuit board or Veroboard
- Tagstrip for mounting capacitors C6 and C78.
- Suitable chassis, terminals for battery, battery terminal clips, mains lead, centre zero 10A meter

* A variety of suitable transformers are available from several sources. The first prototype used an unidentified item with extra windings added to provide the required voltages. The second utilised a shrouded Douglas MT 89 EC. PCB, LI, TI—Veritronics, 23 Roper Close, Rugby.

The inductor L1 is available from Zeta Windings, 26 All Saints Road, London, W.11, as No. 1028 at £5.20 incl. VAT to callers and £6.30 including P. & P. and VAT.


between collector and emitter during the time the transistor is conducting.

The waveforms shown in Fig. 1 should help to clarify the above description.

An earlier version of the unit which did not include the inductor L1 and the capacitor C7 gave a square wave output. This circuit was rejected however because it proved unable to power the writer's central heating pump or electric clocks which just made a rather disturbing rattling noise, nor a 40W fluorescent tube which caused the inverter to fail altogether. When the circuit was modified by including L1 to give a sine wave output these devices all operated although the sine wave shape showed some distortion at full output.

The capacitor C6 was included to suppress high voltage spikes which occurred at the collectors of TR5 and TR8 just after switching off and before the current was established in the other transistor. The effect was probably due to transformer leakage inductance limiting the rate of rise and fall of current in the two halves of the winding. The value of C6 is not critical; about 1 μ F was found to be sufficient to reduce the amplitude well below the breakdown voltage of the transistors used.

Fig. 2. General circuit diagram of the inverter. Note the modification (below) to S1 allowing switching of both battery and a.c. circuits. This alternative obviates the danger of mixing mains and inverted output voltages but requires a 4-pole 10A centre-off switch or two strapped 2-pole switches

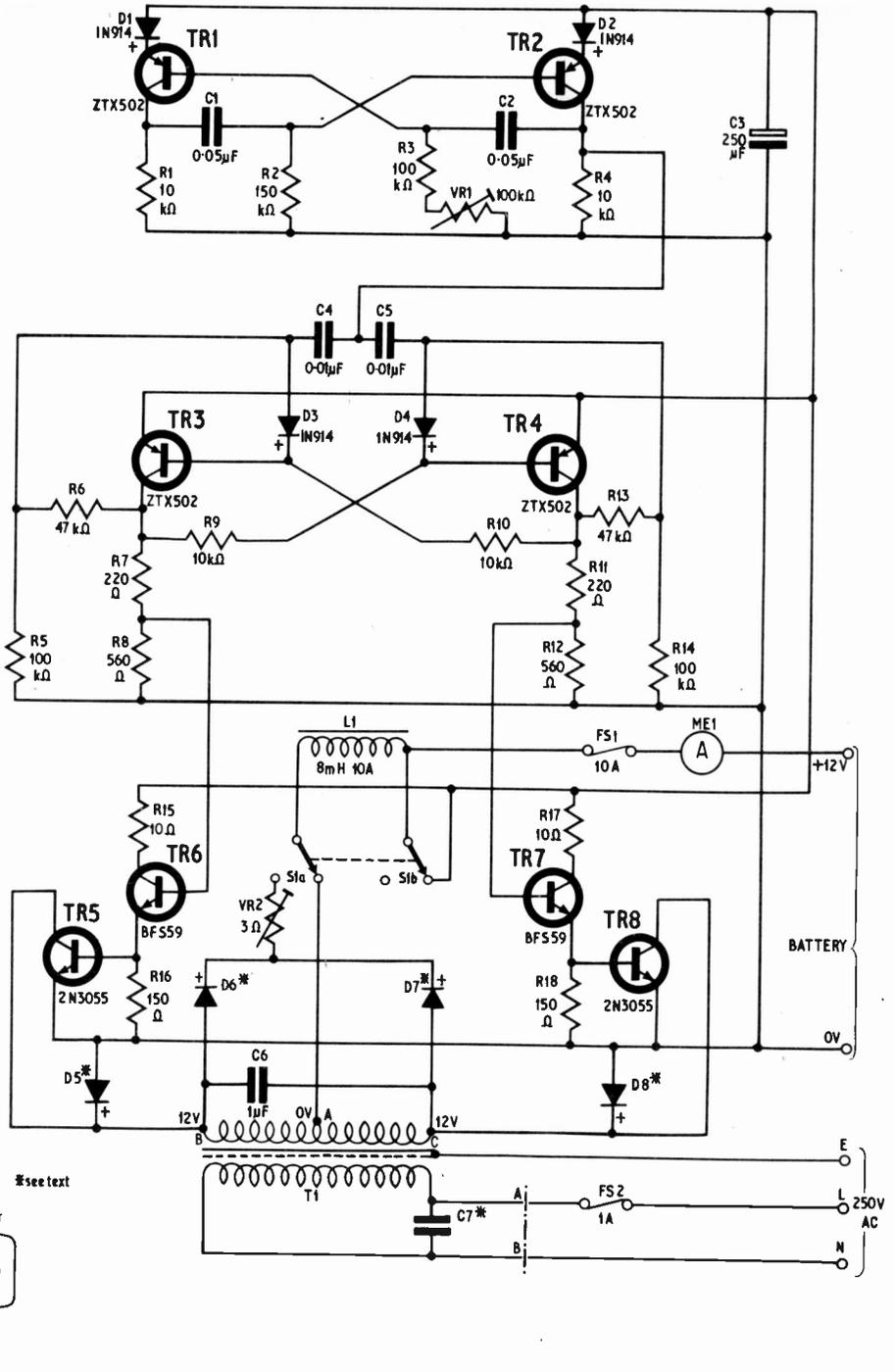

FREQUENCY CONTROL

The multivibrator frequency is determined by two separately timed periods during which TR1 is on while TR2 is off, or TR2 is on and TR1 is off. During the time transistor TR1 is off its base is held positive by the capacitor C2. This capacitor is being discharged via the resistors R3 and VR1. When the voltage on the base of TR1 has fallen sufficiently to make it conduct, its collector voltage starts to rise. Because an instantaneous voltage charge cannot occur across a capacitor the

voltage on the base of TR2 must also rise. TR2 starts to turn off and its collector voltage falls.

The current in R5 which was flowing through TR2 now flows through C2 from the base of TR1, charging C3 and turning TR1 harder on. Regeneration occurs finishing with TR1 fully on and TR2 fully off with its base held positive. This cycle is repeated with the two transistors changing roles. The diodes D1 and D2 are included to prevent the base emitter junctions of transistors TR1, TR2 from breaking down when the other transistor turns on.

STEERING CIRCUIT

The flip-flop has two stable states in which either TR3 is on and TR4 is off, or TR4 is on and TR3 is off. If TR3 is off current will flow from the base of TR4, through resistors R7, R8 and R9 holding TR4 on. Since TR4 is on, no base current can flow in TR3 through resistor R10. Without any input from the multivibrator, the flip-flop would remain in this condition indefinitely.

The components C4, R6, R5, and D3 and components C5, R14, R13 and D4 form two halves of what is known as a steering circuit. The function of this circuit is to direct the positive-going edges of the multivibrator waveform at TR2 to the base of either TR3 or TR4 depending on which of these two transistors is conducting.

The circuit is best understood if resistors R5 and R14 are assumed to be removed. If TR3 is on, the anode of D3 will be at a voltage close to the 12V power rail since R6 will have charged C4 up to the same voltage as the collector of TR3. The voltage across D3 will be very nearly equal to the base-emitter voltage of TR3 so D3 will be on the point of conducting. The voltage on the anode of D4, however, will be nearly zero because TR4 is off. Thus D4 will have a reverse voltage nearly equal to the supply. If a positive-going pulse now occurs at the junction of C4 and C5, D3 will conduct immediately causing TR3 to turn off and driving the flip-flop into its other state.

Since D4 had a large reverse voltage before the pulse occurred this reverse voltage will only be reduced towards zero so that TR4 is free to turn on as soon as TR3 goes off. The resistors R5 and R14 merely give the circuit some noise immunity by giving a small reverse bias across the two diodes so that an input pulse of finite magnitude is required to trigger the change of state. Without this the circuit would be likely to switch erratically due to any small amount of noise fed back from the power output stage.

DESIGN CALCULATIONS

The two timed periods of the multivibrator are approximately

$$t_1 = 0.7 C1.R2 \text{ and} \\ t_2 = 0.7 C2.(R3 + VR1)$$

Where time is measured in seconds, capacitance in farads, and resistance in ohms. The frequency required is 100Hz, so $t_1 + t_2 = 10\text{ms}$ and we can make $t_1 = t_2 = 5\text{ms}$.

R2 is chosen as 150k Ω since this will ensure adequate current to saturate TR2. R1 and R4 are chosen as 10k Ω . Adjustment of VR1 will vary t_2 by ± 33 per cent giving a variation of about ± 13 per cent in the multivibrator frequency. This should be sufficient to obtain exactly 100Hz if 10 per cent tolerance capacitors and 5 per cent tolerance resistors are used.

The required values for C1 and C2 are:—

$$C = \frac{t}{0.7R} = \frac{5 \times 10^{-3}}{0.7 \times 1.5 \times 10^5} = 4.76 \times 10^{-8}$$

The nearest available values are 0.047 μF or 0.5 μF .

The resistors R1 and R4 are chosen as 10k Ω which is sufficiently low to allow C1 and C2 to be completely recharged between half cycles.

The value of C4 and C5 is not critical except that they must be small enough to be recharged in

the 5ms half cycle of the multivibrator. This will be achieved if the time constant C4 (R6/R5) is less than 1ms. This time constant must also be longer than the rise time of the multivibrator. With R5 and R6 equal to 100k Ω and 47k Ω respectively and C4 at 0.01 μF this time constant is about 30 μs . The rise time of the multivibrator is less than 1 μs , so both conditions are satisfied.

The flip-flop has a low output impedance so that adequate power is delivered to the output stage. R15 and R17 are 10 Ω resistors giving approximately 1A of base drive to the output transistors which are required to switch approximately 10A into the transformer for full load.

TRANSFORMER CALCULATIONS

The waveform at the centre tap of the 12-0-12V winding is 12V because of the equal number of the d.c. voltage dropped across L1 is small, the average d.c. level at this point is approximately equal to the 12V power supply. The average d.c. level of a rectified sine wave of peak value V_m is:

$$\frac{V_m}{\pi} \int_0^\pi \sin \omega t \, d(\omega t) = \frac{2V_m}{\pi}$$

$$\therefore V_m = \frac{\pi}{2} \cdot V \text{ supply}$$


The maximum voltage at the ends of the tapped winding is 12V because of the equal number of turns on the two halves of the winding. The maximum collector voltage of TR5 and TR8 is therefore $12\pi \approx 37.7V$.

So transistors capable of withstanding at least this voltage must be used here. The total voltage swing across the primary of the transformer is 37.7V peak-to-peak assuming negligible resistance in L1 and negligible saturation voltage for the power transistors. The r.m.s. value is

$$\frac{37.7}{\sqrt{2}} = 26.6V$$

Thus if a mains transformer with a 12V-0-12V winding is used this will give some allowance for voltage drop in L1 and the power transistors.

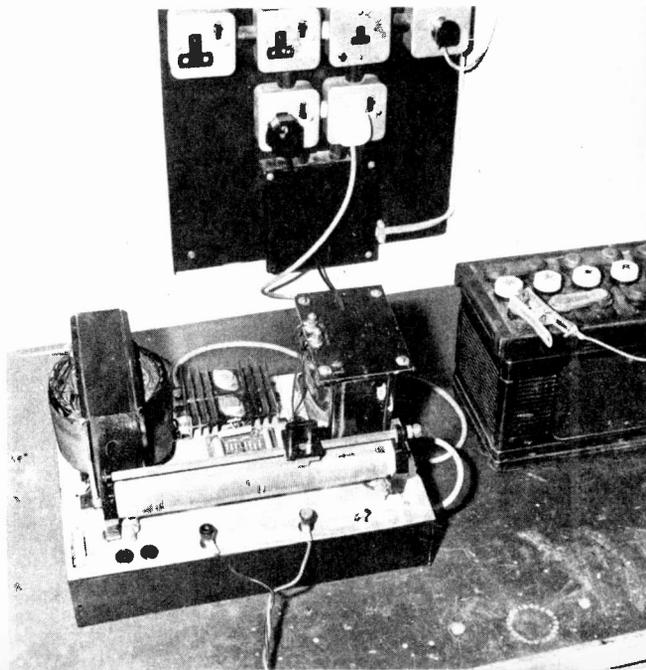Prototype of the inverter/charger acting as a charger





The second prototype equipment boxed in a case and using a circular potentiometer and centre-off control switch

To give a reasonably constant excitation current at full load the inductor L1 should have an impedance of about four or more times the load impedance reflected back to the transformer primary. Since this current is effectively fed into a 12V winding on a 240V output transformer the turns ratio is 20:1. If the load is 100W at 240V, then the load resistance is

$$\frac{240^2}{100} = 576 \text{ ohms}$$

This appears on the 12V primary as a resistance of

$$\frac{576}{20^2} = 1.44 \text{ ohms}$$

Thus the required impedance of the inductor L1 is $4 \times 1.44 = 5.76 \text{ ohms}$.

Since the voltage waveform which appears across L1 is a full wave rectified sine wave, its fundamental frequency is twice the output frequency, i.e. 100Hz and thus the value of reactance is given by

$$X_L = L \times 2\pi \times 100 = 5.76\Omega$$

$$\therefore L = \frac{5.76}{100 \times 2\pi} = 9.2\text{mH}$$

The value of L1 used in the prototype was 8mH. With this condition satisfied the excitation current will be a good square wave and will contain the maximum possible content of the 50Hz fundamental.

In order to get a reasonable sine wave at the transformer output it is also necessary to have reasonable value of Q for the tuned circuit. If this is not so no amount of increase in the inductance L1 will give any improvement. However, experience has shown that for most applications it is sufficient if the corners of a square wave are merely rounded off but, if necessary, extra inductance and capacitance can be added in parallel with the transformer output in order to give a higher Q and hence a better sine wave.

The value of the capacitor C7 required in the prototype to tune the transformer inductance to 50Hz was 2μF. The impedance of a 2μF capacitor at 50Hz is:

$$\frac{1}{2\pi \times 50 \times 2 \times 10^{-6}} = 1,600 \text{ ohms}$$

With a load resistance of 576 ohms this gives a Q of only:

$$\frac{576}{1600} = 0.36$$

This was found to be quite adequate to drive the equipment mentioned at the beginning of this article. As an experiment an extra 4μF capacitor was added to C7 and sufficient inductance in parallel to retune to 50Hz. This made a marked improvement to the output sine wave at full load.

TRANSISTORS USED

The transistors used for the two low power stages were Ferranti ZTX502. The requirements are a V_{ce} rating of greater than 24V and an h_{te} gain of greater than 50 over a range of collector currents from 1mA to 60mA. Another cheap alternative is the BC212 series of transistors.

Driver transistors TR6 and TR7 must be capable of switching 1A and the current is limited to this value by the 10 ohm collector resistors R15 and R17. The type used in the prototype was the Ferranti BFS61 but either the BFS59 or BFS60 would be equally suitable or equivalents such as BFY50, BFY51, BFX84 or BFX85.

The two resistors R15 and R17 dissipate a total of about 12W. This limitation to the efficiency of the inverter could be reduced if these resistors were omitted and the collectors of TR6 and TR7 taken to the collectors of TR5 and TR8 respectively.

It would then also be necessary to use larger transistors for the drivers TR6 and TR7 because under excess load conditions TR5 and TR8 would not bottom properly thus increasing the dissipation in all four transistors. Even under normal operating conditions the improvement to efficiency would be only marginal since TR5 and TR8 would never be able to saturate below their base emitter voltage of 0.7V plus the saturation voltage of TR6 and TR7.

The 2N3055 transistors used for TR5 and TR8 may be chassis mounted using TO3 mica washer insulators. These transistors will only dissipate a few watts if the circuit is operating correctly since they operate in the saturated switching mode.

THE BATTERY CHARGER

In order to obtain a good charging characteristic a voltage well in excess of the 12V battery voltage is needed so the full 24V winding is used to drive a bridge rectifier. This winding now becomes the secondary of the transformer with the 240V primary connected across the normal mains supply. It is essential to use a full wave rectifier if currents approaching the full rating of the transformer are required.

This is because a half-wave rectifier causes a net d.c. current to flow thus magnetising the core into saturation and causing a larger a.c. magnetising current to maintain the required rate of change of magnetic flux, with consequent overheating of the transformer.

The diodes D5, D6, D7 and D8 form the bridge rectifier. If separate rectifiers are used these should be rated for at least 50V 5A or half the required charging current and they should be mounted on separately insulated heat sinks of approximately 2in square 16 s.w.g. aluminium.

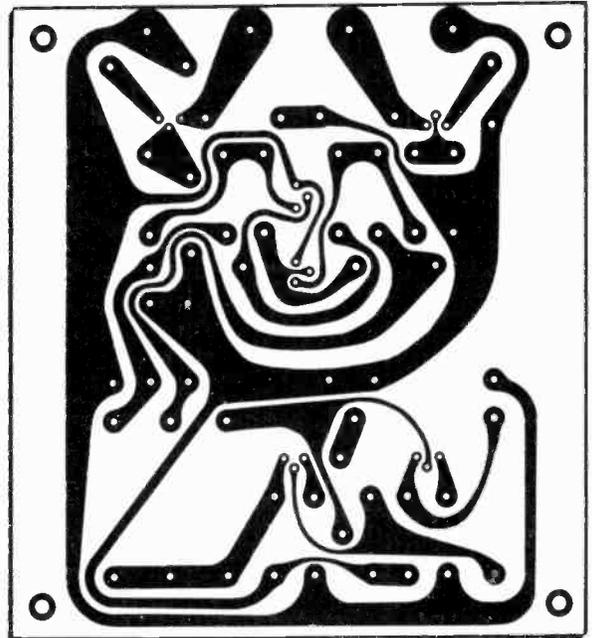
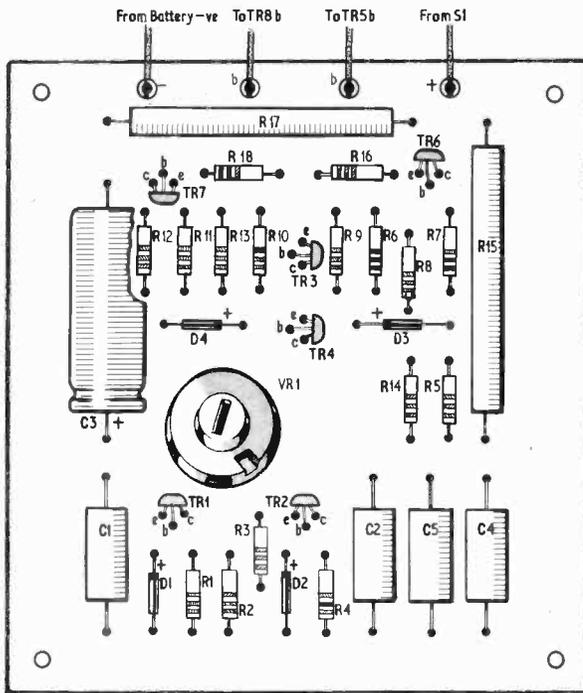


Fig. 3. Component layout and printed circuit master (full size) for the inverter

VARIABLE RESISTORS

The 3 ohm 10A variable resistor VR2 used in the prototype was of the heavy duty sliding type of rheostat. Rotary types suitable for panel mounting are also available but if desired a fixed resistor of from 1 to 3 ohms rated at 100W may be used, preferably with tapping band so that the required current can be preset.

When operating as a battery charger the inductor L1 is left in circuit. This has the advantage that a nearly constant current is obtained with very little ripple instead of the high peaks of current which are obtained with most conventional battery chargers.

AMMETER

The ammeter used in the first prototype was an edgewise 1mA meter which was adjusted and re-scaled to produce a centre reading $500\mu\text{A}$ - 0 - $500\mu\text{A}$. A 10A shunt was made from a few inches of 16 s.w.g. tinned copper wire. If this method is used it is important to make up a four terminal shunt by tapping two points along the wire to give the leads to the meter. In this way any danger of overloading the meter due to contact resistance is avoided. Alternatively, a conventional car dashboard type of centre reading ammeter can be used as in the second model.

PRINTED CIRCUIT


All the smaller components are mounted on a printed circuit board, see Fig. 3. The terminals marked "b" should be wired to the bases of the power transistors + to S1b and - to the battery negative (Fig. 2).

OPERATION AND SETTING UP

It is important when operating the device as a charger to ensure that the switch S1 is in the charge position before plugging into the mains, as otherwise the fuses will blow and there will be danger of damage to the output transistors. When operating as an inverter it is important to ensure that the normal mains supply has been isolated and that not more than 100W of load is connected.

The only setting up requirements are the adjustment of the frequency to 50Hz and the selection of the capacitor C7. If an oscilloscope is available the procedure is simplified though this is not essential.

The second equipment opened to show the somewhat cramped interior arrangement which requires careful ventilating

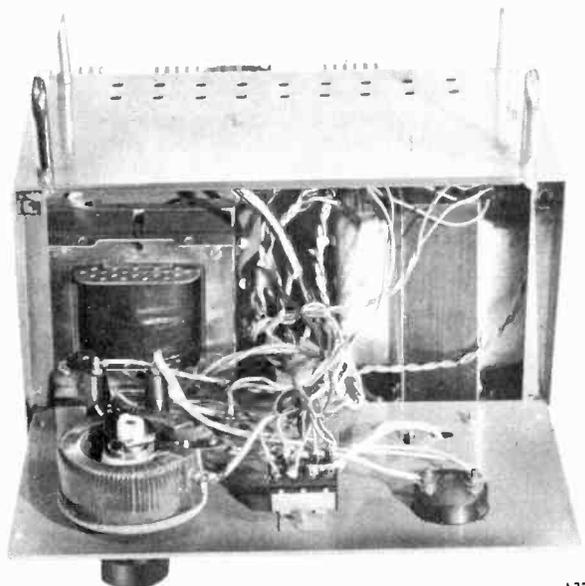

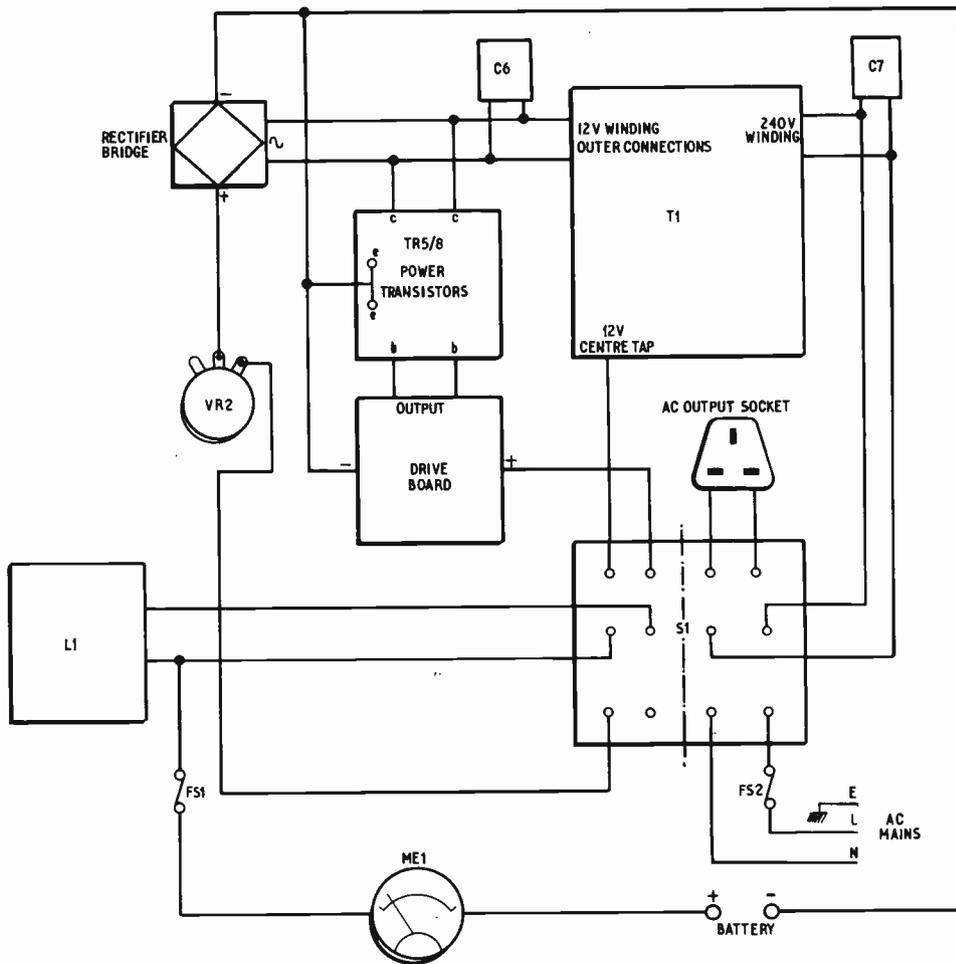


Fig. 4. Block wiring diagram of the inverter with a 4-pole changeover switch as in the second prototype

TUNING PROCEDURE

First switch S1 to 'Invert'. Connect up the 12V car battery taking care of polarity. Do not connect an output load yet. Monitor the waveform at the collector of TR4. This will be a square wave of 12V amplitude. Adjust the frequency by means of VR1 to obtain 50Hz, i.e. square pulses of 10mS width and total period 20mS. If this frequency is required accurately so that clocks will keep time, this is best done by triggering the oscilloscope with 50Hz mains and adjusting VR1 for minimum horizontal drift of the trace.

Obtain several capacitors in the range of 0.5 μ F to about 4 μ F rated at 240V r.m.s. If the values 0.5, 1, 2 and 4 μ F are obtained it will be possible to obtain by parallel combination any value between 0.5 and 7.5 μ F.

Monitor the 240V output waveform on an oscilloscope with no load connected and select the value of capacitance which gives the best sine wave.

A 100W lamp may now be connected as a load. The waveform will probably now show some distortion towards a square wave shape. If desired extra capacitance and inductance may be added as

already described and the system retuned with the load disconnected. Do not attempt circuit alterations with the unit switched on.

WITHOUT OSCILLOSCOPE

If no oscilloscope is available the following procedure should be carried out. Set VR1 approximately to the mid point. Switch S1 to 'Invert' and connect up the 12V car battery. With no load connected listen to the transformer hum. Connect values of capacitance to the transformer output as above and adjust VR1.

If reducing VR1 causes the hum level to diminish, this indicates that more capacitance should be added. When a value of capacitance is obtained such that the hum disappears with VR1 in its central position, the frequency can be finally adjusted, using VR1, such that an electric clock driven by the inverter keeps accurate time.





CAUTION

The same precaution as with any live equipment must be taken with this device as the output of the inverter is just as lethal as the 240V mains supply.

FREE

HEATHKIT Electronics Catalogue

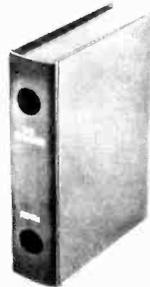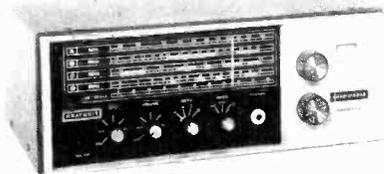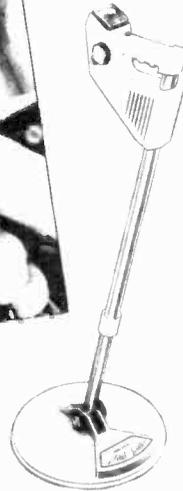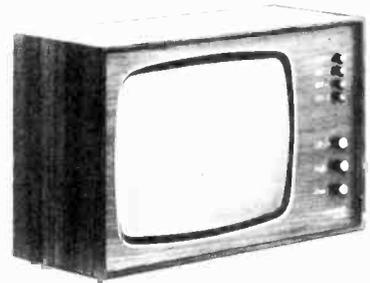There's something for everyone
in the latest FREE Heathkit
catalogue



Choose cash or Heath Monthly Budget Plan

HEATHKIT for Television, Calculators,
Metal Detectors, SW Receivers, Car
Radios, Digital Clock, Burglar Alarm and
Car Test Equipment kits.

VISIT THE HEATHKIT CENTRES

LONDON

233 Tottenham Court Road.

GLOUCESTER (Factory & Showroom)
Bristol Road, Gloucester.


Please send me a FREE Heathkit catalogue

Name _____


Address _____

Heath (Gloucester) Limited, Department: PE/2/74
Gloucester GL2 6EE. Telephone 0452 29451

HEATH
Schlumberger

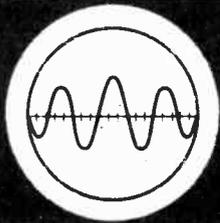

TUAC

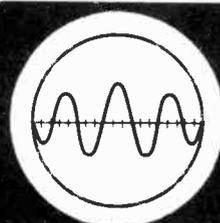

NEW TUAC POWER MODULES. Now in their second successful year offering more power and quality than ever before.



TP100 ★ 125 Watts RMS continuous sine wave output
Illustrated ★ 4 RCA 150 Watt 15 Amp output transistors
£15.25 ★ Special layer wound driver transformer
★ Short, open, and thermal overload protection
★ Compact size: 7 x 6½ x 3 in.



TL100 ★ 100 Watts RMS sine wave
Illustrated ★ 2 RCA 15 Amp output transistors
£11.50 ★ Rugged transformer driver
★ Full thermal overload protection
★ Compact size: 5 x 5 x 3 in.


TL60 ★ 60 Watts RMS sine wave
£9.75 ★ RCA 115 Watt output transistors
★ Only six connections to make
★ Same size as TL100

Specification on all three power modules :

All output power ratings ±1dB. Output impedance 8-15 Ohms. THD at full power 1% typically 0.5%. Input sensitivity 60mV into 10kΩ. Frequency response 10Hz-25kHz ±2dB. Hum and noise better than -75dB.

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 ±50 volts for one TP100	£8.75
PS 100 ±45 volts for one TL100	£8.00
PS 60 ±40 volts for one TL60	£6.75
PSU 2 For supplying Disco Mixer	£4.00

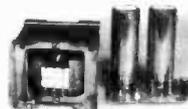

PRE AMPLIFIERS

All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits, producing superb sound quality from any signal. Previous range still available. 40V d.c.: 60mV o/p.

- VA08** Vol. Treb. Mid and Bass Controls. HI IMP. FET I/P. Suitable Mic, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treb +35dB at 16kHz, Mid +20-15dB at 1kHz, Bass +20-10dB at 40Hz. **£4.22**
- VA06** Vol. Treb and Bass Controls. 8mV sensitivity. Treb +28-15dB at 12kHz, Bass ±18dB at 40Hz. **£3.72**
- AMF01** Tuac Auto Fade Unit fades music when you speak. Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade O/P to main Amp. 30mV operating level. Depth and Vol. Controls. **£4.40**

VA08 ILLUSTRATED



SIZE 6½" x 2" x 1"

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS.




TUAC DISCOTHEQUE MIXER WITH AUTO FADE

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions.

£25.50

Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw. Tape Vol, L & R Deck Faders, Deck Volume. Treb. & Bass. H. Phon Vol, Selector. Master Vol, on/off sw. Max. output 1V RMS. Specification as VA06. **PANEL SIZE 18" x 4½" DEPTH 3"**

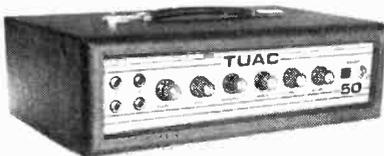TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last




50 WATT RMS SINE WAVE ALL PURPOSE AMPLIFIER

Suitable for Disco, PA, Guitar. 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leather-cloth covered case, short and open circuit protection. Tone control specification as VA08 pre-amp. FULLY FUSED.

50 WATT £44.00

100 WATT £66.00

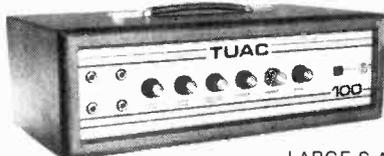

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE

TUAC LIGHT MODULATORS

Constructed on glass fibre P.C. board, individually tested.

Three channel light modulator will control three separate sets of lights up to 1000 Watts each set. One channel responds to the bass, one to the middle, and one to the high frequencies. Input sensitivity only 0.5 Watt! Three individual controls allow for adjustment of the three channels, and a master sensitivity control allows for input levels up to 100 Watts to be safely accommodated. Full interference suppression. Full SILMB 3 Channel wave control. Isolating input transformer does not affect Amplifier operation. Fully Fused.




3 Channel SILMB illus.

£17.45

SINGLE CHANNEL VERSION S2LMB
Increased capacity of 1800 Watts. S2LMB 1 Channel Sensitivity control. Isolating input transformer does not affect amplifier operation. **£6.47**

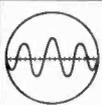MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD. (DEPT. E) 163 MITCHAM ROAD LONDON SW17 9PG 01-672 3137/9080

Do not attempt any circuit adjustment, other than the trimming of VR1 with an insulated screwdriver, while the battery is connected.

IMPORTANT APPLICATION NOTES

As will be seen from the parts list, both the transformer and the choke are fairly heavy in terms of current and in fact it is possible to use a somewhat lower capacity transformer than 10 amp if it is to be used only as an inverter since each half winding carries current alternately. However, as the reduction is only marginal, say, a couple of amps drop in rating, it hardly seems worth while in the face of the availability of the full rating item.

As to the choke, there are in fact many applications where both this and C7 are just not needed. For example, if it is only required to drive incandescent lamps or some forms of induction motor then this can usually be achieved without the choke and C7 and thus with quite a saving in component costs.

It should be remembered that some synchronous motors just will not work on a square wave and thus care should be taken in deciding on the presence or absence of the choke. For example, the normal electric clock only buzzes and jerks when a square wave is applied. In addition, some central heating systems use an electric clock mechanism to effect switching control and it is possible that not only will these not work with a square wave but they might also be damaged by continued application.

If the unit is to be used to drive an audio system including a deck then sine wave operation is a must for the deck motor. In the same area, this equipment is not sufficiently powerful or suitable to drive a T.V. but will probably cope with most radios.

NATURE OF THE LOAD

In fact, the ability of the inverter to cope with various loads depends to a great degree on the nature of the load. A fluorescent fitting containing as it does both a large capacitance and a choke, can prove difficult to handle even with a load as low as 40W. Also, whilst one might wish to drive a motor which has a running rating of say 60W, the starting current demanded might well be considerably above this figure and could prove to be too much for the unit.

In this latter application there is risk of damage to both motor and inverter if such a load is simply left on since it could draw starting current with the result that it burns out and damages the inverter in the process.

Finally, it must always be remembered that whilst in fact the initial rating of the equipment is 120VA (12V at 10A), losses in the system, the individual characteristics of each inductor and the state of both load and, most important, the battery, all contribute to give a greater or lesser output. In any event, overall efficiency will not normally be greater than about 80 per cent.

The original prototype has been used to drive a variety of loads including those mentioned at the beginning of this article.

It has also proved possible to drive such items as a Cadet "S" Circulator central heating pump, a synchronous motor fan and a wide variety of filament bulb loads. ★



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

TOUCH VOLUME CONTROL

I HAVE recently been experimenting with a circuit which may be of interest to other readers. It is a touch volume control, a solid state substitute for the common-or-garden type potentiometer volume control.

The circuit diagram is shown in Fig. 1. The channel of a field effect transistor TR2 may be regarded as a pure resistance, provided that the drain-source voltage is fairly low (less than 3V). The value of this resistance is controlled by the gate-source voltage, and hence by the charge on C3, see Fig. 1.

Capacitor C2 and the resistance of the f.e.t. decouple the resistance in the emitter line of TR1. Thus, the gain of the stage is varied by the charge on C3. The stage gain can be increased by touching plates B and C, or decreased by touching plates A and B simultaneously.

The volume can be varied over a fairly wide range and little drift of volume was experienced. Capacitor C3 should be a polycarbonate or a tantalum type, for low leakage. Almost any n-channel f.e.t. will do for TR2.

If it is desired to use a positive supply line, the polarities of the transistors and the electrolytic capacitors should be reversed.

Provided that the input signal level is kept within reasonable limits, harmonic distortion should be low enough for most applications.

C. Budd,
Petersfield,
Hants.

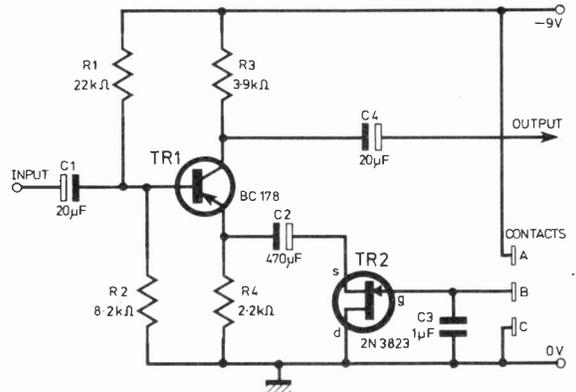


Fig. 1. Touch volume control circuit diagram

STAGE LIGHTING DIMMER

Our author R. Liffen replies to some of the points raised from the article published in our November 1973 issue

TRIAC RATING

Many readers have expressed concern that the surge current through incandescent lamps is greater than the surge current rating of the SC50D.

The peak surge current of the SC50D is 100 amp and the dimmers have been functioning for three years with no triac failures. In any case, the normal mode of operation is to fade the lamps to full brightness and not to simply switch them on with the fader up.

NEON MIMIC LAMPS

The use of mimic lamps with filament lamps and voltage dropper resistors consumes a great deal of power. Cannot neon lamps be used?

Neon tubes were rejected as mimics because they are not analogue devices at low voltage levels.

SUPPRESSION

It is normal to include inductive electromagnetic or radio frequency interference suppression as high power dimmers tend to produce enough interference to affect other people's equipment. Why was this omitted?

I would have preferred to include inductive as well as capacitive interference suppression. My enquiries indicated, however, that 13A chokes of suitable inductance were unobtainable "off the shelf" and would cost £10 to £15 each if specially made. This would have doubled or even trebled the cost of the unit. The capacitive suppression has proved adequate during tests, one of these being the effect (nil) on a nearby digital computer.

WIRING

Is there not a danger that if the electronics are wired using a wire size of, say, 14/0076 that this wire will "blow" before the supply fuse?

Certainly there would be an element of danger if an inexperienced constructor used 1A cable throughout, but he would then have ignored the last sentence of the explanation attached to Fig. 4 in the article.

For the sake of completeness may I suggest the following cables be used? (Modern metric standard)

Cables carrying lighting load to be 50/0.25mm T.C.W. Nominal C.S.A. 2.5sq mm 15A/Triac gate control electronics 16/0.2mm T.C.W. Nominal C.S.A. 0.50sq mm 3A.

SAFETY

In order to connect to an existing supply should not a connection box be used, for instance a GEC Henley 43802, and, since a connection has to be made into a live cable, assistance from the electricity board be sought?

If adaptors are used then more than one 13A fuse would be connected to the output exceeding the rating of the triacs and decreasing the safety factor. Would it not be better to put a 15A fuse inside the unit, thus allowing adaptors to be used whilst maintaining safety?

Should not the equipment be tested before being put into service, not only for insulation, etc. but for earth loop impedance as well. Since this requires equipment not normally used by the amateur would it not be wise for the assistance of a competent electrical engineer to be sought?

Is the heat sink of sufficient size to dissipate the heat generated by the triacs?

The unit was originally fitted with a Henley connector but this was removed by an electrical supervisor from the Department of the Environment and the input cables were plumbed straight into the MEM switched fuse.

"No adaptors" is, of course, the rule. It is assumed that in the case of multiple lamps (e.g. footlights) that the lighting electrician will calculate the loading for each dimmer and keep it within the safety limit.

The Stage Lighting Dimmer was designed to be used with existing lamp installations which should have been fully electrically checked. If a brand new hall or theatre is being built then the local bylaws and electricity supply regulations will normally ensure the full electrical safety of the installation.

To answer the point about the heat-sink: no triac failure has occurred from surge currents or overheating. It would do no harm, however, if constructors chose to limit the current capacity of their own dimmer units to, say, 10A per channel. They should then only use lamps up to a value of 2½kW. Alternatively there is now available an even larger triac, the SC60D, which has a steady current rating of 25A and will stand peak surge currents of 250A.

The unit was checked after installation by an electrical supervisor from the Department of the Environment.

FUSING

As short circuits are quite common in stage lighting work, should not a fuse be connected in series with each lamp circuit?

Some readers seem to have overlooked the fact that since 13A sockets are fitted to each dimmer channel, then the corresponding plug will have a 13A fuse fitted and this will protect against lamp failure.

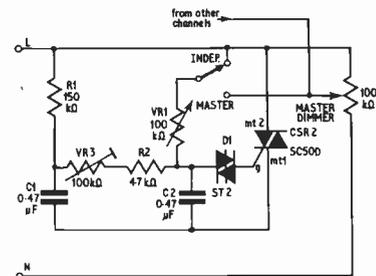


Fig. 1. A modification to the master dimmer control.

MODIFICATIONS

It is a pity that Mr Liffen has adopted the American system of master dimming rather than the British, which is superior.

The American system works as follows. Suppose that Lamp 1 is at 100 per cent brilliance, lamp 2 is at 50 per cent and lamp 3 is at 30 per cent. As the master dimmer is brought from 100 per cent down to zero, the relative brilliances of the lamps vary enormously.

With the master at 100 per cent, the relative intensities are 100:50:30, with the master at 50, the relative intensities have changed to 50:0:0. This completely upsets the balance.

Fortunately, a simple modification to Mr Liffen's design will convert the circuit to the British method. The correct balance is maintained for all master dimmer settings. The circuit to achieve this is shown in Fig. 1. Notice that only one (single-gang) master control is needed.


A. J. Fisher,
Hereford.

The master control circuit suggested by Mr Fisher may perhaps give a better balance between lamps at intermediate master fader settings, but the presence of a 100k Ω fader directly across the mains with no fuse protection seems dangerous.

look! electronics really mastered

...practical
...visual
...exciting!

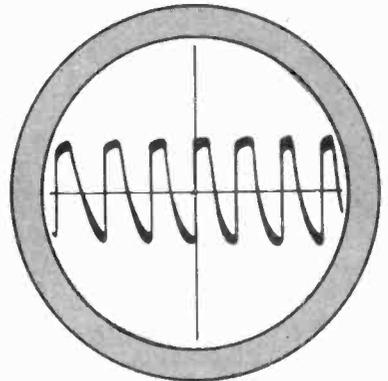no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

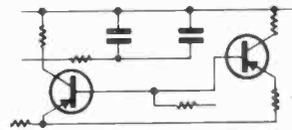2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL 24

special free gift also to all our students

RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:
 2 track record playback heads 50p each.
 4 track record playback heads 72p each.
 Erase heads are also available separately—2 track 33p—4 track 55p.
 MV metal mounting shields 30p each.
 2 track-heads already fixed on heavy mounting plate with shield £1.22.


CONTROL DRILL SPEEDS

DRILL CONTROLLER

NEW IKW MODEL
 Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.95. 13p post and p. Made up model also available. £2.95.

MIGHTY MIDGET

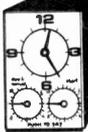Probably the finest possible radio, as described in *Practical Wireless*, January 73. All electronic parts £2.20 post paid.



TIME SWITCH

Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bills, etc. £1.95.

I CHIP RADIO

Ferranti's latest device ZN414 gives results better than superhet. Supplied complete with technical notes and circuits. £1.38 each. 10 for £11.11.

HI-Q TUNER COMPONENTS

For experimenting with the ZN414.
 KIT NO. 1. Plesey Miniature Tuning Condenser with built-in LW switch and 3in ferrite slab and litz wound MW coil, 72p.
 KIT NO. 2. Air spaced tuning condenser 6in ferrite rod litz wound MW and LW coils, 84p.
 KIT NO. 3. Air spaced TC with slow motion drive 8in ferrite rod, with litz wound LW and MW coils, £1.10.
 KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils, 50p.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete when fitting instructions and ready wired dashboard switch. £6.85 plus 25p post and insurance.



TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 42p. KNUCKLED MODEL FOR F.M. 55p.



EXTRACTOR FAN

Cleanse the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2in casing with 5 1/2in fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2.75 + 20p P. & P.

MAINS OPERATED SOLENOIDS

Model 772 — small but powerful 1in pull—approx. size 1 1/2 x 1 1/2 x 1 1/2in. 68p.
 Model 4001—1in. pull. size 2 1/2 x 2 x 1 1/2in. 83p.
 Model TT1—1 1/2in pull. size 3 x 2 1/2 x 2in. £1.95 plus 20p post and insurance.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10. Plus 20p postage.

DESK TELEPHONES

Ex G.P.O. Black standard model with dialing dial but no internal bell. Supplied with connection diagram £1 each. Ditto with bell but without dialing dial £1.25. Model as illustrated with bell and dial £1.50 each plus 60p post for single then 65p per pair.



SMOKE WILL KILL—GAS WILL KILL—FIRE WILL KILL

But, if you install SAGA (our smoke and gas alarm) your family will have the latest electronic protection, against these killers. SAGA uses a fantastic electronic sensor which "smells" smoke and gas and sounds the alarm immediately, in a neat case measuring approx. 5in x 3 1/2in x 2 1/2in. It has its own internal alarm, also a connector for additional bells. You just plug it in to the mains and hang it near the ceiling. SAGA uses so little electricity that it will hardly move the meter, leave it on always to give night and day protection. One year's guarantee, also 7-day cash return offer, (or kit of parts £5.99. Battery model kit only £4.99), £6.99 plus 30p post and service. Sensor (SD) only £2.20.



ULTRA-SONIC REMOTE CONTROLLER

As featured in this issue! Our 1974 catalogue lists hundreds of bargains and probably many of the parts needed for this project. 68p brings the catalogue and the next 6 monthly supplements.

STANDARD WAFER SWITCHES

Standard size 1 1/2in wafer—silver-plated 5 amp contact, standard 1/2in spindle 2in long—with locking washer and nut.

No. of Poles	2way	3way	4way	5way	6way	8way	9way	10way	12way
1 pole	44p	44p	44p	44p	44p	44p	44p	44p	44p
2 poles	44p	44p	44p	44p	44p	44p	44p	44p	77p
3 poles	44p	44p	44p	44p	44p	77p	77p	77p	£1.04
4 poles	44p	44p	44p	77p	77p	77p	77p	£1.32	£1.32
5 poles	44p	77p	77p	77p	£1.04	£1.04	£1.04	£1.60	£1.60
6 poles	44p	77p	77p	77p	£1.04	£1.04	£1.04	£1.87	£1.87
7 poles	77p	77p	77p	£1.04	£1.32	£1.32	£1.32	£2.15	£2.15
8 poles	77p	77p	77p	£1.04	£1.32	£1.32	£1.32	£2.42	£2.42
9 poles	77p	77p	£1.04	£1.04	£1.60	£1.60	£1.60	£2.70	£2.70
10 poles	77p	77p	£1.04	£1.32	£1.60	£1.60	£1.60	£3.00	£3.00
11 poles	77p	£1.04	£1.04	£1.32	£1.87	£1.87	£1.87	£3.25	£3.25
12 poles	77p	£1.04	£1.04	£1.32	£1.87	£1.87	£1.87	£3.52	£3.52

THE TWENTYLITE

Fluorescent lighting units with polyester choke and finished white enamel. 2ft. model, ideal kitchen, bedroom, hallway, porch, lift, etc. with tube. Assembled ready to install. Price £2.20 + 40p P. & P.



RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.20—twin stethoscopes instead of earpiece 83p extra—post and ins. 20p.



TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, impeller, 2kW element allowing switching 1, 2kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £2.75. Don't miss this. Control Switch 44p. P. & P. 40p.

CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flows but virtually no noise. Approx. dimensions 10 1/2in wide x 12in dia. outlet into trunking 10 1/2 x 4 1/2in. £2.55 plus £1 post and insurance.



CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price £6.55 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. £7.95.

SWITCH TRIGGER MATS

So thin is undetectable under carpet, but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in £1.60; 13in x 10in £1.21.

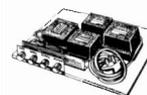


PHOTO ELECTRIC KIT

Contains photo cell, relay, transistor and all parts to make light operated switch. £1.75 plus 20p post and ins.

MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this:—
 1 Unilex Amplifier Ref. EP.9000 £1.60. 1 Unilex Amplifier Ref. EP.9001 £1.60. 1 Unilex Pre-Amp. Ref. EP.9002 £2.53. 1 Control panel kit with spun aluminium faced knobs £2.30. Or the complete outfit—£11.30 post paid. Pair of 15 ohm speakers made by E.M.I. are also available if required. Price £3.30 the pair. No extra postage if ordered with the above, otherwise add 25p.



TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 20p.

SIX MULTI-SPEED MOTOR

Multi speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 & 15,500 r.p.m. Shaft is 1/2in diameter and approximately 1 in. long. 230V/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor, size approx. 2in dia. x 5in long. Price 97p plus 23p postage and insurance.



SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 3in rated 250V lamp. 8p each, 10 for 73p. Ditto as above but for printed circuit 8p each, 10 for 68p. Sub-Miniature Slide Switch, DPDT 19mm (1in approx.) between fixing centres. 20p each or 10 for £1.90. SP Changeover spring return 250V 1 amp. 11p.



TREASURE TRACER

Complete Kit (except wooden battery) to make the metal detector as the circuit in *Practical Wireless*, August issue. £8.30 plus 20p post and insurance.

IMMERSION HEATERS BY REMPLOY

Standard fitting for domestic water tanks, made by the famous Remploy Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 1 1/2in. 2kW or 3 kW £1.65 plus 20p each post and insurance.



GOOD COMPANION I.C. VERSION

We can now offer these again in I.C. version using Ferranti ZN414 and Mullard AF Module 1172. Cabinet size approx. 1 1/2in wide x 8in high x 3in deep. Complete assembly instruction—Excellent tone wood cabinet £5.75 plus 25p post and insurance.



MOTORS FOR £1.30

Post included. As used in racing cars and power models. All battery operated and reversible.



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 75p. Postage 20p for first one then 10p for each one ordered.



PC BOARD MARKER

Valve action fibre tipped marking pen filled with black etch resist—it's easy with this to make a perfect PC board, just draw straight on to the copper—allow 15 minutes to dry, then immerse in ferric chloride or other etchant on removal the circuit stand in high relief, 99p.

EDUCATIONAL KITS—all with pictorial instructions

3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 44p each post paid. Special price for all 7 kits £3.00 with free balance kit.



- KA2 Lens Kit. Eleven parts, concave lens, one convex lens, stage and slit frame, etc.
- KA3 Water Pump Kit. Thirteen parts. Transparent so that operating parts may be observed. You can make Lift pump, Force pump and Force pump with reservoir and nozzle.
- KA4 Buzzer Kit. Eleven parts. Operation of buzzer seen.
- KA7 Electro-Magnet Kit. Fifteen parts, includes compass, showing how magnetism works.
- KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. "OHMS LAW" etc.
- KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell.
- KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate.

J. BULL (ELECTRICAL) LTD.
 (Dept. P.E.), 7 Park Street, Croydon CRO 1YD
 Callers to 102/3 Tamworth Road, Croydon



BY FRANK W. HYDE

THE FRENCH APPROACH

Inner space is emphasised as part of the French space programme of research in a number of projects.

The development of using high level balloons tethered and free and what they call space platforms, extends into many scientific fields and offers this rather intermediate technique as a supplement and in some cases an alternative to satellites. Education in emerging countries by using high captive balloons for television distribution is another specific area under intensive study.

All this emerged in a colloquium organised by the AERALL. This stands for Association d'Etude et de Recherche sur les Aeronefs Alleges.

The colloquium which was attended by many delegates from Europe, was held in Paris. Among the more ambitious of the projects was one for a gigantic flying saucer. This experiment, known as the *Pagase* platform, is some 420 metres in diameter and 66 metres in height. It takes the form of a double convex shape or lenticular as it is described in the paper given by J. Roux of "Aeroconsult France" who operate from Lyon.

The device which is intended to fly at great height, will be maintained geostationary by a proposed ion motor. The special fabric which will be used as the outer skin was developed in France and is the same material which was used for large captive balloons from which the recent French atomic test device was dropped.

The operating height that is expected to be chosen for the flying saucer is some 21,000 metres and each operational period of the order of one year. It is to be expected that the advent of this enormous object would set up a new wave of UFO sightings.

As the immediate propulsion systems are likely to be propellers driven by electric motors powered by batteries or fuel cells with a turbo system using liquid hydrogen, the amount of gas required to fill the hull would be of the order of 700,000 cubic metres.

It is claimed that such a device would in the long run be cheaper than satellites for educational television. This claim was also put forward for smaller balloons and dirigibles both captive and free.

The French scientific programme involving these devices has ranged from meteorological studies to infra-red and detailed studies of the Sun. So great is the interest in these matters that the various authorised research departments of the government and the various independent centres have been funded to a level of 90 billion francs.

One thing particularly noticeable about the French attitude is that meticulous attention to detail is the primary requirement and every project is one in which nothing in the way of testing is left to chance. Indeed this is carried so far that nothing is allowed to operate in full scale until every aspect of possible failure has been examined.

There is a definite end product commercially in spite of the emphasis on the pure research for research sake. It is planned that when the projects are proved they will be offered to emerging countries as a means to improve education, communication and transport. The French Ministry of the Environment keeps a very close watch on all the projects and were in attendance at the colloquium.

In a strictly down to earth way the British contribution was for the design of an airship to carry heavy individual loads. This airship was some 1,300 feet long and capable of carrying loads of the order of 400 tons. It was also suited to use as a scientific platform for meteorology, geodesy, oceanography to mention a few of the inner space uses. The detailed design was given in a paper by Dr. E. Mowforth of Airfloat Transport Ltd.

THE JAPANESE APPROACH

The Japanese decided to take an independent approach to space matters. Clearly, they wished to be able to control their own launchings and not to depend upon other countries. This is perhaps the reason behind their decision not to use Woomera but to develop their own sites for launchings.

All the proposed projects are peaceful ones and one of the requirements for the consent of the people as a whole to the building of launching sites was that these bases would never be used for military purposes. The World Weather

Watch which is to be undertaken is in accordance with the peaceful policy line.

The preparation of launch vehicles was undertaken in the country even though they could have been purchased more cheaply from abroad. There has been a slight departure from the original rather austere attitude to the extent that some foreign components have been used. Some still important projects such as the *ISS*, Ionospheric Sounding Satellite, are almost wholly Japanese. However, there has been some discussion as to whether Japan should purchase some of the elements of the Geostationary Meteorological satellite to be launched in 1976.

Already Japan's tracking stations have been used in the past space-flights of the *Apollo* series. This is in accordance with the Japanese declared intent of world cooperation. It is not likely that they will take part in the space shuttle programme because decisions for this were made final before Japan was ready. There is, however, a distinct air of national prestige in the general attitude to space projects.

FUTURE PROGRAMMES

The Japanese space programme for the future include a geostationary communications satellite which is regarded as vital to TV coverage in a country where mountains present a problem for surface transmission ranges and where the educational requirement demands coverage of rural areas. Also a navigational satellite for the benefit of the maritime activities of the country and for the fishery industry vital to food supplies. The third important project is the geodesic survey satellite. This will take the form of a balloon with a circular orbit of about 620 miles. It will carry laser reflectors.

The launchers to be used for the applications satellites will be by a three stage vehicle. This employs liquid fuel for the first and second stages and solid fuel for the injection motor. These cannot be regarded as strictly Japanese for they are built under licence by Mitsubishi from McDonnell Astronautics and Rockwell International.

There are a number of government establishments engaged in supporting activities. One of the larger facilities is the National Aerospace Laboratory founded in 1965. The Science and Technology Agency now operate it. Much of its efforts are directed to system studies of launch vehicles and engine research. Guidance and control and instrumentation is also undertaken together with work on the structural dynamics of rocket launchers.

PERIODO PART 6

PICK-UPS & TURNTABLES FOR QUADRAPHONICS

BY R.A. COLE

THE weakest links in a sound reproducing system are always the first and last, the pick-up and the loudspeaker. The "state of the art" in amplifier design is so advanced that distortion figures of less than 0.1 per cent are obtainable from all but the most modest amplifiers.

It is surprising to hear of the elaborate designs currently appearing for amplifiers of even better performance, when the pick-up cartridge, turntable, tape mechanism or tuner feeding signals to the amplifier themselves have distortion figures that can only be described as mediocre.

At the other end of the reproducing chain, the loudspeaker is even worse in its ability to reproduce sounds accurately. This article deals with the problems of quadrasonic reproduction.

BASIC REQUIREMENT

To play a gramophone record, one needs a mechanism to rotate the record at a constant and accurate speed. This basic requirement would appear to be a simple engineering problem and yet good turntables have far from good performance, when compared with the amplifier. Any production of mechanical noise or variation in speed will distort the accurate transfer of the original waveform from the record to the amplifier.

There are of course similar distortions of the original recorded sound up to the record itself, which we have to ignore and live with. These distortions are of a lower magnitude than in disc reproduction, due to the fine engineering quality of recording equipment.

MECHANICAL NOISE

The principal sources of mechanical noise in turntables are in the bearing on which the turntable rotates and the mechanical drive link between the motor and turntable. These give rise to a phenomenon called "rumble".

In addition to mechanical noise there are substantial fluctuations in speed. The first fluctuation is called "wow" and is a low speed variation caused by inaccuracies in the drive mechanism and turntable itself. The second source of speed fluctuation, caused primarily by inaccurate drive linkages, is of a higher frequency and is aptly called "flutter".

All of these deficiencies are reduced to lower proportions if great care is taken in design and manu-

facturing. This inevitably leads to higher costs. Turntable mechanisms vary in cost from a few pounds to a hundred or more pounds, and the listener should choose the best he can afford.

DRIVE SYSTEMS

There are three principal methods of driving a turntable. The first and most common, uses a horizontal intermediate rubber idler wheel between the motor and the turntable.

The rubber idler wheel is driven by the motor capstan and in turn drives the turntable. It is held in contact with both capstan and turntable by a spring. The idler wheel is disengaged when the turntable is switched off mechanically. If it does not disengage, a depression or flat will occur on the periphery of the idler wheel which causes a "bumping" noise. The more these flats occur, the more frequent the "bumping" noise. In extreme cases where numerous flats occur, the bumping noise becomes a form of rumble.

To guard against this, never turn the turntable off *electrically*. Always use the mechanical system which switches the motor off electrically *and* disengages the idler wheel.

The second method works on a similar principle to the horizontal idler wheel method, but uses a vertical idler wheel running off a horizontal tapered or stepped capstan. In this case rumble is imparted to the turntable in a vertical sense and gives slightly better performance.

The same precautions regarding idler disengagement are needed. One advantage of this system is the ability to vary the speed over a wide range with the elongated tapered capstan and the subsequent wide range of drive ratios available.

The third and most effective method is the "belt drive" method which transfers the rotation of the capstan to the turntable by means of a "rubber" belt drive. The flexibility of the thin rubber belt provides effective decoupling between the motor and turntable.

Various types of material are used for manufacturing the belt drive. Different cross-sections are used by various manufacturers. The main disadvantage is the relatively low degree of energy transfer obtainable when compared with the previous methods. The belt must be scrupulously clean and free from oil or grease or belt slip may occur.

MOTORS

Some cheap turntables use motors with two poles which tend to have high hum fields. Four-pole motors are most common in medium price units. The better turntables, including belt drive turntables, tend to use multi-pole motors, sixteen-pole principally. These motors are small and have virtually no hum field.

TURNTABLE BEARINGS

There are a number of views regarding turntables and their bearings. The cheaper turntables tend to use a thrust plate and ball race bearing. These bearings are to be avoided like the plague as they can impart serious rumble. There is no better bearing than the shaft and bush bearing. These appear in various forms, sometimes with a tapered shaft and sometimes with a single ball bearing in the bottom of the bush.

The more expensive turntables use precision machined heavy diecast non-ferrous turntables with the weight distributed mainly around the periphery. However, since the use of multi-pole motor has become common, much lighter turntables tend to be used because of the accuracy and speed constancy of these motors.

Rumble figures of 50dB to 65dB (weighted) are now common in belt drive turntables. The cheaper turntables tend to have such poor rumble figures and vary from one sample to another to such a degree that the buyer can never be sure how reliable his particular sample will be.

There are new types of turntable appearing recently; the "linear motor" turntable to mention one. These overcome many of the shortcomings mentioned above, but they are all at this time in the very high price bracket.

PICK-UP ARMS

Most turntables use a pick-up arm which carries the cartridge across the record attempting, ideally, to present the cartridge axis at a tangent to the groove. However, the errors introduced can be quite

staggering. The better arms have tangential errors as little as a half degree, but needless to say they are very expensive. True parallel tracking arms which move across the record in a straight line are available, but their prices are high.

Other factors which are significant in pick-up arm design, are the bearings, which have to be virtually frictionless; arm resonance, damping, and general design geometry. All these factors are dealt with by various manufacturers to a degree which is usually related to price.

The minimum requirement for hi-fi reproduction should include an adjustable counter weight, removable head shell and a reliable arm lifting mechanism. Additionally a device to overcome the natural tendency for the arm to move into the centre of a rotating record is desirable. This is called a bias compensator or anti-skating device. As the degree of bias depends upon the weight of the pick-up upon the record, this compensator should be adjustable as well.

A word about pick-up lifts. Although a precise lift can be made using a simple type mechanism, it is useful if the lowering action is damped. Some of the viscous damped, or hydraulic mechanisms permit a precise and gentle lowering action.

PICK-UP CARTRIDGES

There are two main types of pick-up cartridge. One uses the piezo-electric effect in which certain types of crystal when flexed generate small voltages across an axis of the crystal.

The cheapest of these cartridges are made from Rochelle salt. The more modern cartridge has a man-made crystal which gives a more uniform response and is less temperature and humidity sensitive. A good ceramic cartridge can give adequate hi-fi performance and falls in the medium price bracket. The output is around 25mV to 100mV and must be fed into a high impedance, usually around 2 megohms.

Perfectly adequate reproduction of SQ and QS Quadraphonic records can be obtained using a normal stereo ceramic cartridge.

Magnetic cartridges cover the widest spectrum of price and quality in hi-fi reproduction. At the lower price end of the spectrum there appear to be some "shockers" and better performance can often be obtained from a ceramic cartridge in the same price range. However, there are a number of quite low price magnetic cartridges which can be used for SQ and QS recordings to great advantage.

Do not be tempted to buy a cartridge which does not have stylus replacements available on a nation-wide basis.

MAGNETIC TYPES

Magnetic cartridges fall into three main types. The most common is the moving magnet cartridge which generates its output by movement of a small magnet within a coil of wire.

The second method, which has fallen somewhat into disfavour in recent years, is the moving iron method in which a soft iron strip moves within a coil of wire, the iron being magnetised by an external fixed magnet.

The third method utilises a coil which moves within a magnetic field. The dimensions and mass of the coil are amazingly minute and moving coil cartridges are usually in the higher priced bracket.



The Goldring G101, typical of equipments suited to Quadraphony

All the movements in each of these cases are damped.

There are other methods used in cartridge manufacturing: photo-electric, condenser and ribbon types for example. As these cartridges are rather rare and expensive, they will not be described.

PLAYING WEIGHTS

In all the cases mentioned above, the stereo or quadrasonic waveform on the record is traced by a stylus which is attached to a cantilever arm. This arm is coupled to a "bridge" which has two limbs at right angles to each other and at 45 degrees with respect to the record plane. This bridge transfers the energy along each axis to one of two transducers.

The lower price cartridges tend to require higher playing weights and the stylus suspension or compliance is rather stiff. Such cartridges are more suited to simple low quality arms. More expensive cartridges are used at considerably lower playing weights and due to their more delicate compliances require better quality arms to avoid mistracking.

Never play records at a higher or lower playing weight than recommended, as distortion and record wear will occur.

PICK-UP STYLI

The use of a diamond or a diamond-tipped stylus is a "must" for hi-fi due to the long life of diamond. The use of a sapphire stylus is to be avoided.

A diamond stylus should be inspected under a stylus microscope every 1,500 to 2,000 playings. One can expect 2,000 to 3,000 playings before a "flat" becomes noticeable on the tip. In the case of sapphire a life of 20 to 30 playings is probably the maximum safe life. No stylus should be used after a flat is visible under a stylus microscope, otherwise serious record wear may occur.

A simple comparison of the cost of a new stylus against the value of the records played, should leave no doubts on this matter. Styli are usually ground and polished to a cone with the tip radiused. This radius can vary from around 0.0003in to 0.0007in for L.P. records.

ELLIPTICAL STYLI

In order to improve the tracking of the stylus and to improve the upper frequency response elliptical styli are now quite common. The diamond is ground and polished to give a tip of elliptical cross-section usually 0.0003×0.0007 in.

switch. It would probably be of considerable help to the uninitiated in springs to know that one can attach the offending item quite easily with the switch mechanism in an apparently wrong position and then apply the tension by rotating the mechanism to the correct position.

This process is fairly simple for those used to dealing with reluctant springs but will probably give some trouble to the newcomer to the effects of a suddenly released tension spring which invariably flies to the darkest corner of the room.

THE CONNOISSEUR BD1

TURNTABLE KIT

AND SAU2 PICK-UP ARM

The kits for these two items are available off the shelf from A. R. Sugden & Co. (Engineers) Ltd., of Brighouse, Yorkshire at prices of £13.31 and £14.52 respectively. In combination and used with a suitable pick-up cartridge they form a unit suited for incorporation in the PE Rondo Quadrasonic system.

The two items are sent out to customers securely packaged, the first in a folded corrugated cardboard packing with individual kit parts or sets of parts carried in plastic bags. The pick-up arm is packaged in a suitably moulded expanded polystyrene box form suitably secured with a cardboard sleeve.


Taking the turntable unit first, this is supplied with three basic items of literature, the assembly instructions themselves, a layout sheet or template for cutting the mounting board, and some fairly comprehensive descriptive material which gives specification, installation and service details.

As with any kitting exercise, it is always advisable to first read through the instructions before starting on the mechanical assembly. This is no exception as there is always the risk that the supplier might call an item by one name whereas the builder might know the same item by a totally different name.

In the present case all appeared in order from the beginning and construction was commenced.

Each step is detailed in the instructions in fairly simple terminology and in an easy-to-follow order. Indeed if anything the instructions are perhaps more detailed than necessary for the greater majority of readers.

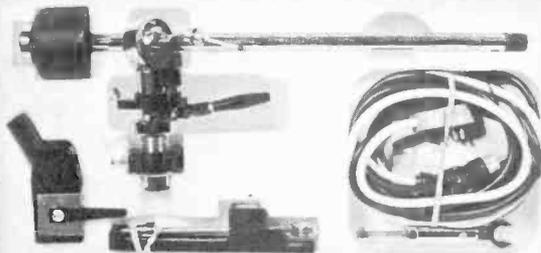The only error discovered, if error it can be called as it is more one of omission than fact, concerns the fixing of a small but strong spring to the on/off



The Connoisseur SAU2 pick-up arm kit



The Connoisseur BD1 turntable kit

Such a stylus presents its smaller dimension to the modulations on the groove walls, but will still be prevented from "bottoming" by its major dimension. The process of elliptical grinding and polishing is expensive and elliptical versions of cartridges normally fitted with a spherical stylus are more expensive.

The foregoing forms are used for a stereo and SQ-QS quadrasonic reproduction. The CD-4 system however requires a cartridge with a much higher frequency response.

For good CD-4 reproduction an upper frequency response of 45kHz to 50kHz is required and it is also necessary to utilise styli of special form, such as the Shibata stylus. This has four times the groove contact area of the conventional styli and a cross-section which is small enough to trace the high frequency modulations on the CD-4 disc.


RECORD AND STYLUS CLEANING

In order to preserve a record collection it is imperative that all records should be kept clean. It is only too easy to allow dust, finger marks and abrasions to accumulate and once they have accumulated the whole standard of reproduction of records falls.

In fact, assembly took only about 30 minutes and proved to be easy. One warning, do not be too liberal with the oil on the main spindle or you will only have to remove most of it afterwards since the fit between the shaft and the bearing is, of necessity, close and as the bearing is closed at the lower end air becomes trapped in the space below the spindle. Whilst it is very nice to run on an effective air bearing this is not the object of the exercise and in any case it makes the turntable ride far too high.

Newcomers to the type of drive used in the Connoisseur BD1 will probably note with some surprise that the on/off or start switch includes a small button which engages with the turntable as the switch is operated. This is intended to overcome the basic inertia of the mass of the turntable by giving it a small push in the direction of rotation.

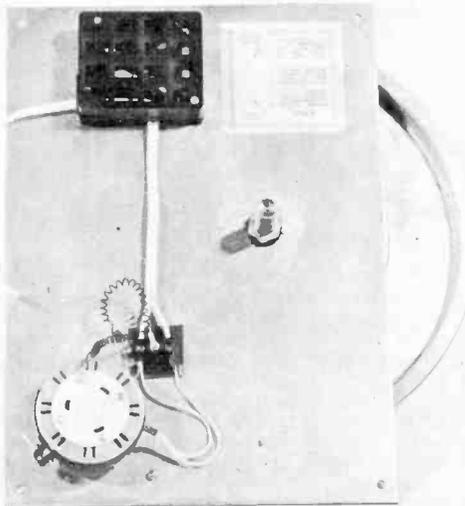Underside view of the assembled BD1 turntable



Equally so, the gramophile can be persuaded to use patent cleaners and fluids that tend to leave traces of fluff and oily deposits. The combination of fluff, greasy deposits and dust become gathered by the stylus into congealed lumps, that harden and are finally pushed round by the stylus, scoring the groove walls.

A series of cleaning aids, pioneered by Cecil Watts and now copied by numerous others, provide a safe, efficient and inexpensive means of preserving records. These consist of the Dust Bug, the Disc Preener and the stylus brush.

The only fluid that can be safely used on records is pure absolute ethyl alcohol or a mixture of the same with distilled water (not demineralised).

The expedient of using alcohol or alcohol diluted should only be used to clean excessively dirty records. Any claims for the use of fluids should be treated with reserve until the user is sure that no deposits are left.

The stylus brush may be used in conjunction with a little stylus cleaning fluid. The brush is used so that the bristles move backwards and forwards along the axis of the cantilever; never side to side. In the case of CD-4 records, it is advisable to clean the disc with a disc preener before and after playing.


This is done for two reasons. In the first place the belt used is light and fairly elastic. Secondly, the turntable is fairly heavy in order to give the mass needed to provide the very good rumble and flutter figures.

Thus the small hand-operated push. It allows the motor, belt and flywheel all to take up the drive without jerks, jumps or other unnecessary problems.

The SAU2 pick-up arm proved to be an even simpler job to assemble, taking only a matter of moments to work out which part goes where.

Whilst the whole assembly was not mounted on a plinth the procedure was rehearsed and is simple, particularly as it is assisted by the presence of a cutting template for drilling the arm mounting hole and an alignment protractor for adjusting the pick-up in the head.

Assembled BD1 and SAU2

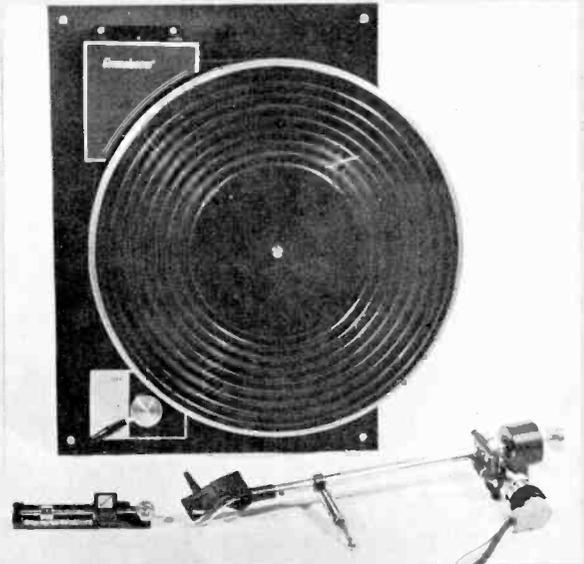

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

ORGAN KIT


For an American company (one of the largest) that is spending over £3 million on launching its UK operations, it seems ironical that the construction kit our Editor brought back from **Tandy Corporation's** official opening ceremony in Birmingham should be minus a component. (From a £3.95 kit!)

Dealing mainly in hi fi equipment, Tandy's Science Fair P-Box construction kits range from a "Goofy Lite" to an "Analogue Computer" and may interest some readers. The kit we constructed was the 28-101 Electronic Organ.

A feature of these kits is the use of the bottom of the boxes as a mounting base for components. A matrix of holes drilled in the base, annotated with a number for holes and a letter for rows, takes the components.

Included with each kit is a set of instructions and a booklet on construction hints. For readers who have not tackled much constructional work it is recommended that these hints be read first, particularly the hints on soldering.

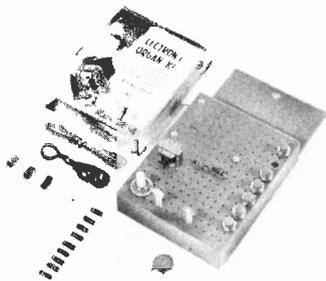The organ kit consists of 27 components plus P-box and took approximately two hours to construct following their instructions. But if one was to just follow their excellent wiring diagram it would probably only take one hour.



Science Fair Electronic Organ Kit from Tandy

Apart from the practice of inserting two component leads in one hole and the difficulty in soldering a strapping lead, without burning the case, across the key switches the kit is very well designed. However, for a unit that is called an "electronic organ" the sound reproduced from our kit is certainly not anything like an organ sound, in fact, it's more like that produced by a cat that's got its tail caught in a mouse trap.

All Tandy products are available from franchise shops which have been or are being set up throughout the Midlands. Eventually Tandy franchise shops will be nation-wide.

If you want to obtain a franchise it will cost you £2,000 and an additional outlay of approximately £12,000 for a shop and stock.

A catalogue of Tandy products is available from any dealer or direct from their head office at Bilton Road, Holyhead Road, Wednesbury, Staffordshire WS10 7JN.

CASSETTE LIBRARY KIT

After the success of their Record Library kit, **Bib** are now marketing a Tape Indexa system catering for tape cassettes, cartridges or reels.




Bib Cassette library system

claimed to be completely flexible. The recommended retail price is 66p, excluding vat.

NEW AUDIO I.C.

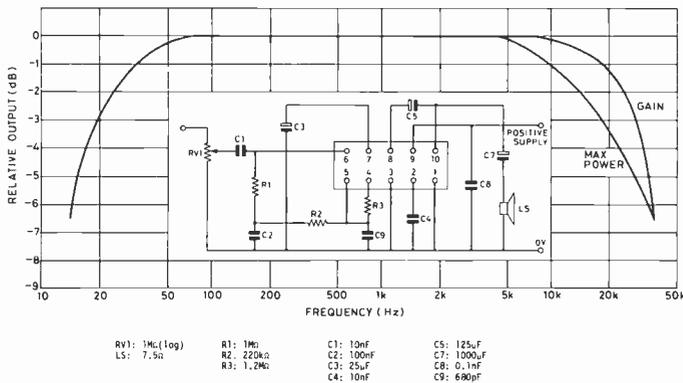Over the last few years we have published several audio circuits which have used the excellent Plessey SL402/3 integrated circuit because of its dependability. Now Plessey's announce the replacement



Typical external components required for the Plessey SL414 and SL415 audio amplifier integrated circuit

The system enables 1 to 100 cassettes, cartridges or reels to be referenced and with additional units it can be expanded to accommodate up to 999 cassettes. The kit comprises a cassette library case to hold 20 index cards and two summary cards, which are clipped together and swivelled to read entries. There are 300 self-adhesive labels, three of each numbers from 1 to 100, and 10 spare Indexa Cards.

One label of each number is stuck on each side of a cassette and the appropriate library case. Entries are made on the cards detailing any particular points the collector wants to record.

Full details of using the Bib Cassette Tape Indexa are included with the kit and the system is

of the 402/3 with two new audio amplifiers with the reference of SL414 and the SL415.

The amplifiers have an output of 3 and 5 watts r.m.s. respectively into a 7.5 ohms load. Designed for operation from a 20V (SL414) and 25V (SL415) supply, distortion is quoted as being 0.1 per cent r.m.s. and 0.3 per cent with a power output of 1W at a frequency of 400Hz.

The high input impedance of the new devices is obtained by using a built-in pre-amplifier consisting of a triple Darlington stage.

The SL414 and the SL415 should be available from most advertisers or can be obtained direct from **SDS Components Ltd., Hilslea Trading Estate, Portsmouth, Hants PO3 5JW.**

PE Sound Synthesiser 13

KEYBOARD

By G.D. SHAW



In this last part keyboard construction will be completed and final tuning described.

KEYBOARD HOUSING CONSTRUCTION

The design of the keyboard housing is based on the use of the four octave Kimber-Allen keyboard. Constructors using keyboards other than the one specified will have to modify some of the dimensional details accordingly. Fig. 13.1, is a composite illustration giving details of the various timber components required to construct the main housing. Since no interlocking joints are used it is recommended that all joints be secured with a powerful adhesive such as Araldite together with pins or woodscrews as necessary.

Firstly the end frames, cheek plates complete with battens and baseboard were made according to the figures and lightly tacked together dry, as a check on dimensional accuracy. The housing was then stripped and, with the exception of the faces to be glued and the underside of the baseboard, all parts were finished with two coats of dark grey undercoat and four sprayed coats of matt black paint.

A piece of upholsterer's heavy quality black figured vinyl was then cut to cover the underside and front lip of the baseboard. In cutting the vinyl an allowance of about 38mm should be made for overlapping each of the long edges of the baseboard and, similarly, allow about 50mm on the overall width. Do not attempt to cut out the rectangular opening at this stage.


With the vinyl spread out on a flat surface coat the underside with a thin layer of suitable adhesive leaving about 25mm clear all round. Dunlop

"Thixofix" was used in the prototype. The underside of the baseboard should be similarly prepared.


When the adhesive appears dry to the touch place the baseboard, glued side up, on a table and cover lightly with a sheet of greaseproof paper or similar. Place the vinyl over the baseboard, glued side down, and adjust its position to allow for the overlaps. When correctly positioned gradually slip the paper from between the two glued surfaces and roll the vinyl onto the baseboard. A wallpaper joint roller would be suitable for this purpose.

Ensure that the vinyl goes on without wrinkling but do not attempt to apply any degree of stretching otherwise shrinkage will occur at a later date. The vinyl may, however, be pulled tight over the batten on the front lip of the baseboard. When this stage has been reached reverse the position of the baseboard and apply a layer of adhesive to both long edges of the vinyl, baseboard, rear face of the batten and in a 38mm strip around the rectangular opening.

With a sharp knife, and following the contour of the opening, cut out a rectangle leaving an overlap of about 38mm all round. Make three or four cuts into the radiused corners of the opening as shown but leave a gap between each cut and the timber edge. Roll down each of the overlaps in turn pulling the vinyl tightly over the edges of the baseboard. In the case of the opening set down the corners first of all before attempting the long edges.

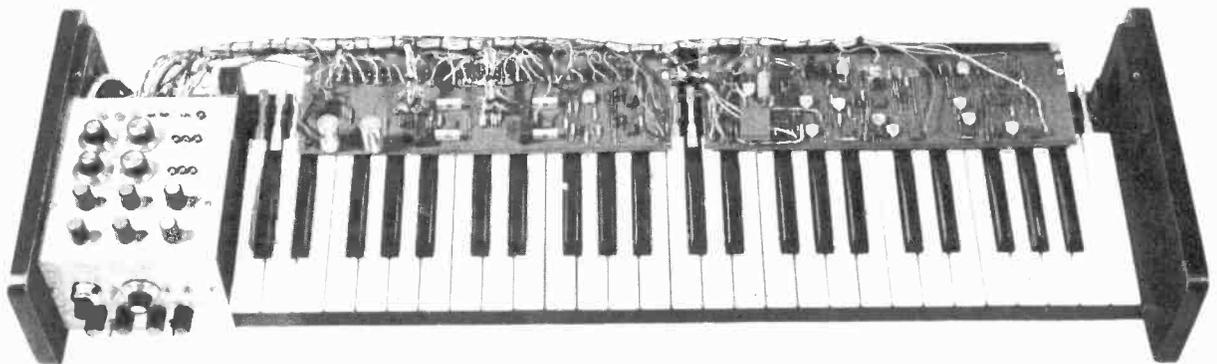

KEYBOARD FRAME

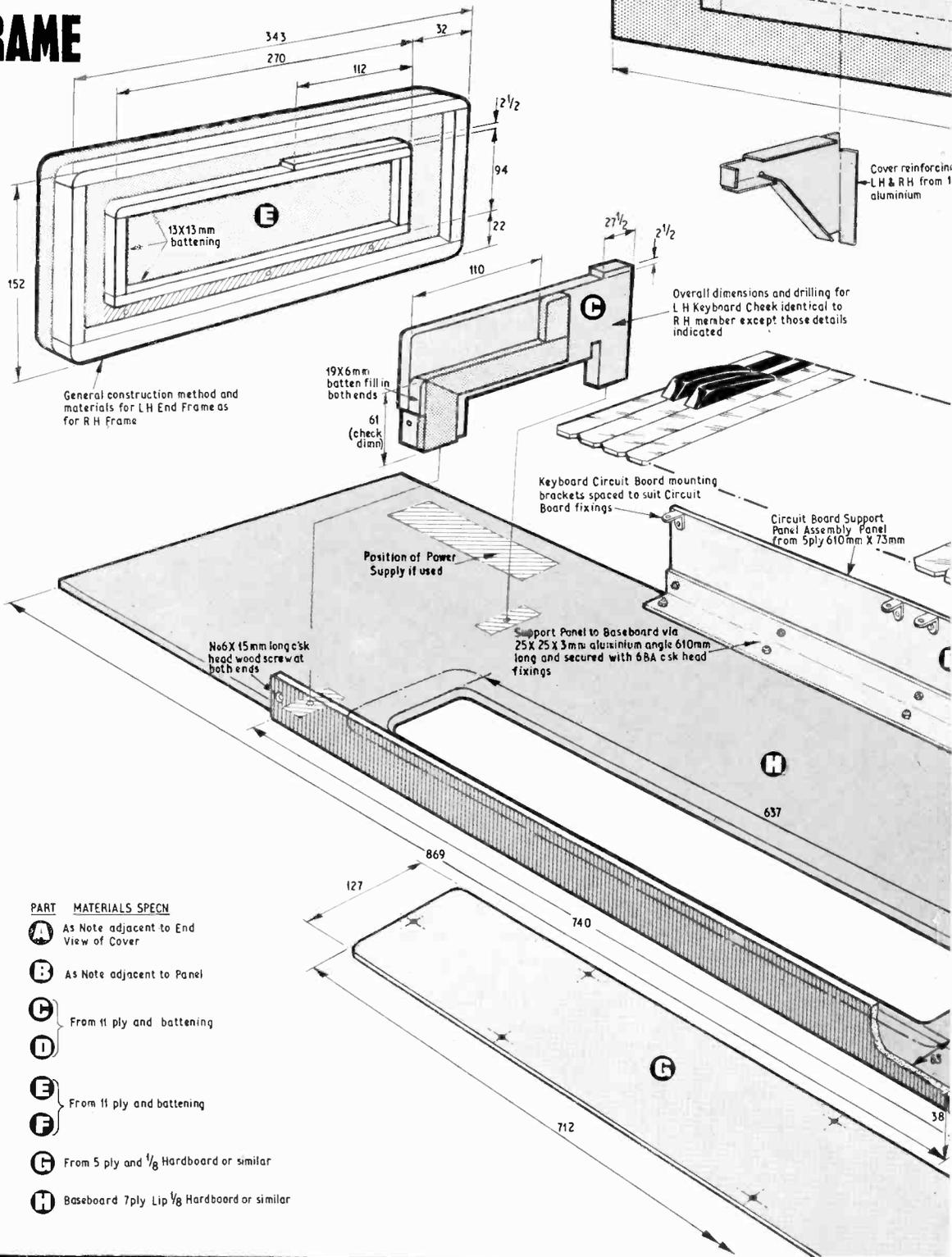

- | PART | MATERIALS SPECN |
|------|---|
| (A) | As Note adjacent to End View of Cover |
| (B) | As Note adjacent to Panel |
| (C) | From 11 ply and battening |
| (D) | |
| (E) | From 11 ply and battening |
| (F) | |
| (G) | From 5 ply and 1/8 Hardboard or similar |
| (H) | Baseboard 7ply Lip 1/8 Hardboard or similar |

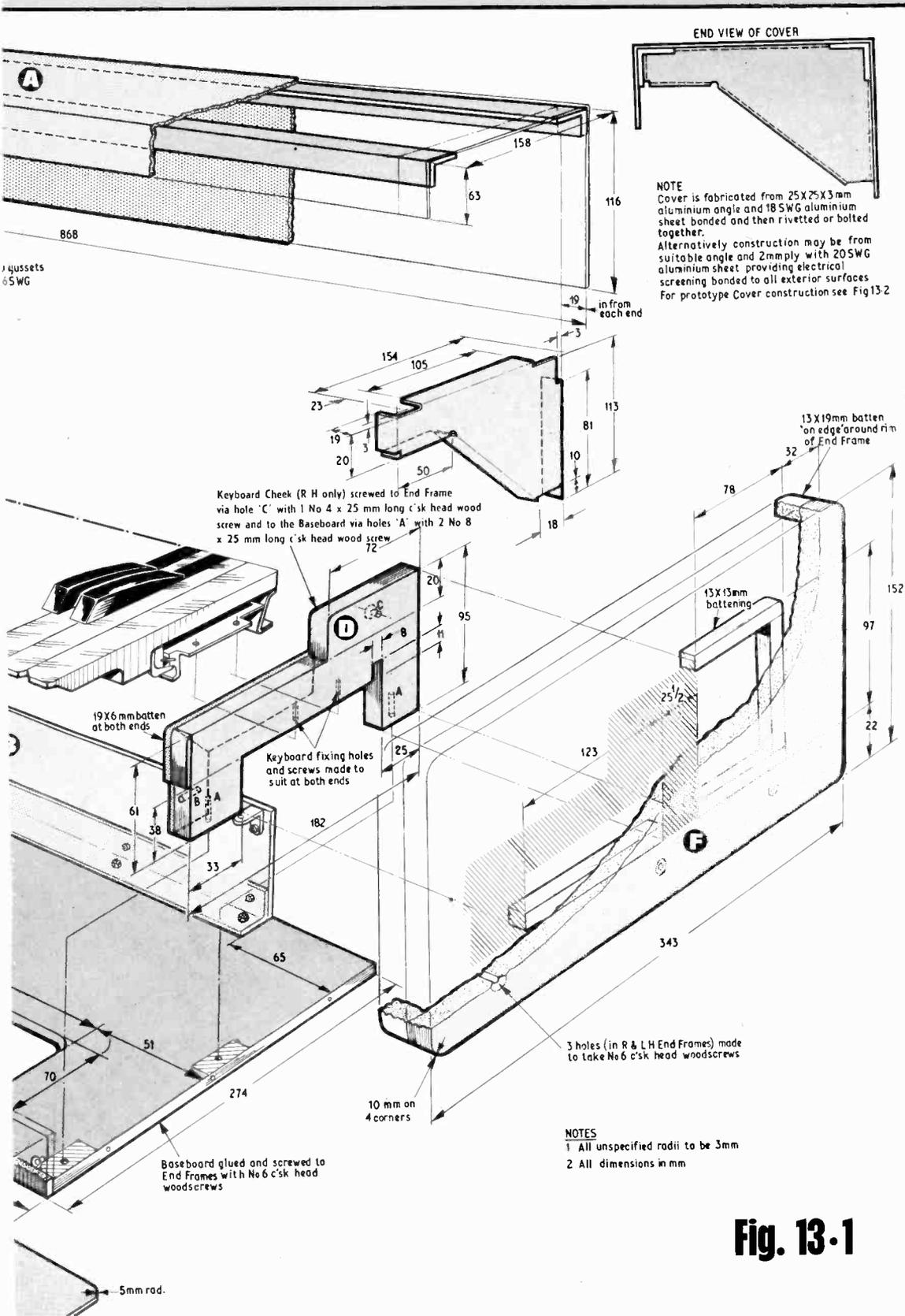


Fig. 13-1

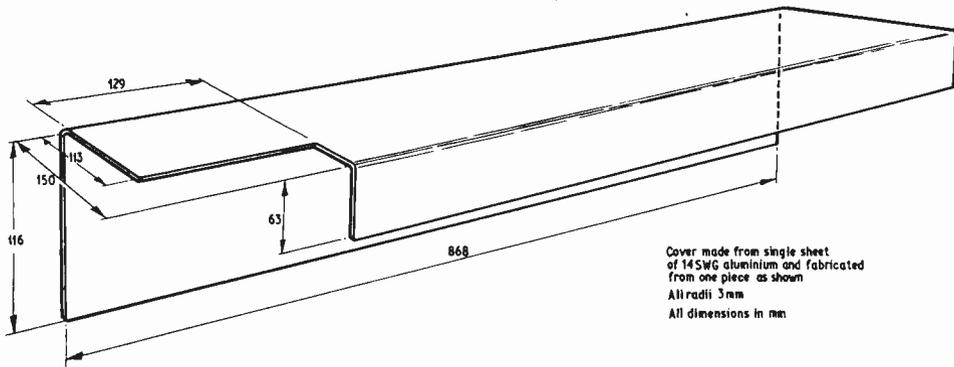


Fig. 13.2. Prototype bending and cutting detail of keyboard cover plate

After allowing the baseboard to settle overnight the excess lengths of vinyl may be trimmed off with a sharp knife.

The baseboard may now be glued and screwed to the endframes of the keyboard housing using round head screws, with washers, to prevent wrinkling of the vinyl. Set aside for the glue to set, ensuring the endframes are square with the baseboard.

ASSEMBLING THE KEYBOARD

Attention may now be given to the keyboard itself. Drill two holes 10mm in from each end of the aluminium extrusion which forms the main frame of the keyboard together with coincident sighting holes in each of the cheekplates. Secure the cheeks to the frame with No. 8 round-head woodscrews. Make sure that the aluminium frame is barely flush with but does not protrude beyond the cheeks. The keyboard may now be turned upside down resting on the left cheek and with a suitable block of wood placed beneath the right cheek. Trim the length of the contact strip so that it fits easily into the space to the rear of the actuators.

Place a contact assembly at each end of the strip such that the front of the assembly is flush with the leading edge of the strip, and then manoeuvre the strip so that the plain wires on the contact assemblies slightly protrude above and beyond the actuators. When satisfied with the positioning carefully remove the contact assemblies and mark the position of the strip relative to the actuators. The contact strip

may now be removed and prepared for permanent fixing.

The contact assemblies themselves will be secured to the strip by means of adhesive and thus the upper surface of the strip has to be prepared by thoroughly roughening the surface by means of coarse grade emery or glass paper.

The contact strip may be secured to the keyboard frame by means of adhesive or by means of screws. In the former case the lower surface of the strip must also be thoroughly roughened together with its mating face on the mainframe of the keyboard. In the latter case a minimum of three screws will be required (each end and centre) and the appropriate drillings made through the contact strip and frame. Note that if the latter method is employed keys will have to be removed in line with each drilling. The contact actuators can be removed by a straight upwards pull after which the key spring will have to be disconnected before the key can be removed.


The contact assemblies may now be fixed into position with the front face of the assembly flush with the edge of the strip and with the long, plain wires centred squarely over their respective actuators.

WIRING THE KEYBOARD

The first stage in wiring up the contact assemblies is to fan out, in a vertical plane, the lead out wires common to each unit. With the keyboard inverted and, facing the rear of the assembly, key 1 at the left end is the lowest C while key 49 at the extreme right is the highest C. Starting with the lead-out wire nearest to the contact strip wire all these together from key 1 to 49 inclusive. 24 s.w.g. tinned copper wire is suitable for this purpose. This row will form the -15V busbar and an insulated wire should be connected to row 1 key 1 for subsequent coupling to the -15V rail. Although not absolutely essential it is a good idea to use short lengths of insulated sleeving on the bare sections of connecting wire between contact assemblies.

Row No. 2 forms the envelope shaper triggering busbars. Link together all No. 2 wires from key 1 to key 18 inclusive and attach an insulated wire to key 1 row 2 for subsequent attachment to the link switch (S2b). A similar procedure is adopted for key 19 to 49 inclusive with an insulated wire attached to key 19 row 2.

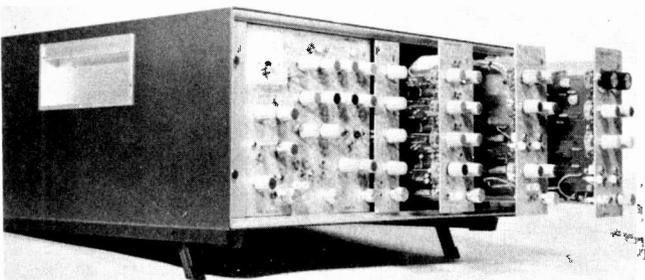Row No. 3 is wired in an identical manner to Row No. 2 except that the busbars so formed will be carrying V.C.O. control voltages and the insulated lead-out wires will be connected to S2a.



CODED KEY WIRES

The contact assembly wires in row No. 4 are individually hard wired direct to the keyboard divider circuit board. It is best to ensure that each key in any octave has its own distinctive wire colour.

Loosely bunch tie the octave wire groups together so that there is less likelihood of confusion when wiring into the divider board.

When the contact wiring has been completed the keyboard assembly may be mounted into the main housing and secured. Fit the circuit board supporting panel and mount the two large circuit boards into the positions shown in the sketch. In the prototype Vero brackets were used for this purpose and secured to the circuit boards by means of nylon screws and nuts. The wiring to the divider should be led through the gap between the panel and circuit board, trimmed to length and soldered to their respective pins.

Place the control panel temporarily in place on the keyboard housing and slide the envelope shaper sub-chassis into position making sure that the control shafts protrude through their respective holes in the control panel. Secure the sub-chassis to the baseboard by means of suitable woodscrews.

FINAL TUNING

With the installation of the power supply unit or connection of the umbilical cable the final tuning of the keyboard unit may be accomplished.

Having already matched the performance of the v.c.o.s the final tuning consists quite simply of matching the setting of the fixed span control (VR3) to suit the requirements of the oscillators. Constructor/musicians will find this to be a relatively easy matter since it is only necessary to play, consecutively, two notes an octave apart and adjust VR3 until the required pitch difference is achieved. For those constructors who do not possess the keen "pitch ear" of the practised musician it will be necessary to revert to the use of the oscilloscope.

Using one oscillator only and monitoring the output signal, adjust the tune control so that, with middle C depressed, the frequency is exactly 250Hz. Next depress the C above middle C and note the frequency, adjusting VR3 until it stabilises at 500Hz. The adjustment to VR3 will have caused the lower frequency to move so it will now be necessary to go back to middle C again and re-adjust the tune control so that it is once again 250Hz. Further adjustment to VR3 and the tune control are made until such time as the frequency ratio between middle C and its octave is exactly 1:2.

Very close octave spans may be achieved by taking the lowest and highest C's on the keyboard for the purpose of tuning. If the lowest C is set at 50Hz by means of the tune control then the upper C will require to be set to 800Hz corresponding to a frequency ratio of 1:16.

Once VR3 has been set, the tune control may be adjusted over quite a wide range without disturbing the octave frequency span. This feature presents a number of advantages because it allows the four octave register of the keyboard to be positioned almost anywhere within the audio frequency spectrum without the necessity of retuning. Similarly it allows the natural notes, normally the key of C, to play in any other key designation.

The variable span control may be switched in as required in order that the keyboard may be matched with acoustic instruments which may be slightly out of tune. At extreme settings the variable span control can reduce the frequency span of the keyboard to a semitone or less or extend the frequency such that one octave on the keyboard covers about three octaves of frequency. These latter possibilities will perhaps be of greatest interest to those musicians wishing to explore the realms of micro and macro tone compositions.


MODULATION AMPLIFIERS


Modulation amplifiers are provided to enable the setting up of relatively complex relationships between oscillators without the necessity for complex circuitry. The simplest use for the modulation amplifiers lies in the provision of vibrato modulation. In this case V.C.O.2 is switched off and its frequency adjusted to about 7Hz by means of its manual control. S6(1) is then closed and the depth control VR7(1) adjusted until the desired degree of vibrato is achieved. The characteristics of sine, triangular and square wave induced vibrato are quite different and many interesting effects are possible by simply varying waveform and modulation depth.

Some of the most interesting effects however occur when both the v.c.o.s are cross modulating one another, and it is possible to simulate a number of conventional acoustic instruments even to providing very realistic bell tones when the appropriate envelope characteristics are combined with a degree of reverberation. In this latter mode of operation extreme settings of the depth controls can provide a series of very bizarre effects in which key positions appear to be juxtaposed and with a number of keys providing grunting, warbling or twittering sounds.

The synthesiser is still a relatively young instrument, having been available to the public for about five or six years. As a creative tool it is without equal but there is still a great deal of development to be done and constructors who have followed the project so far will not only be amongst the first synthesiser owners but will find themselves in the unique and exciting position of perhaps being able to make some contribution towards the further growth of the instrument. ★

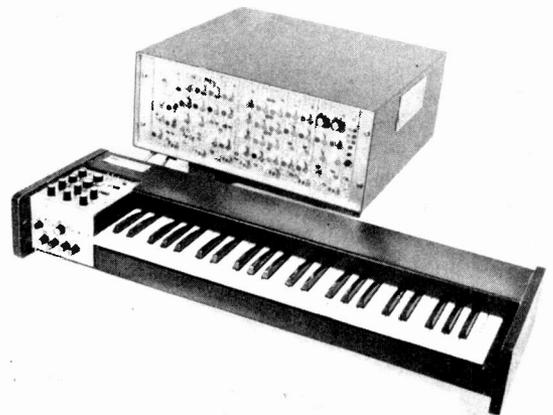An Invitation to a Lecture . . . see page 178



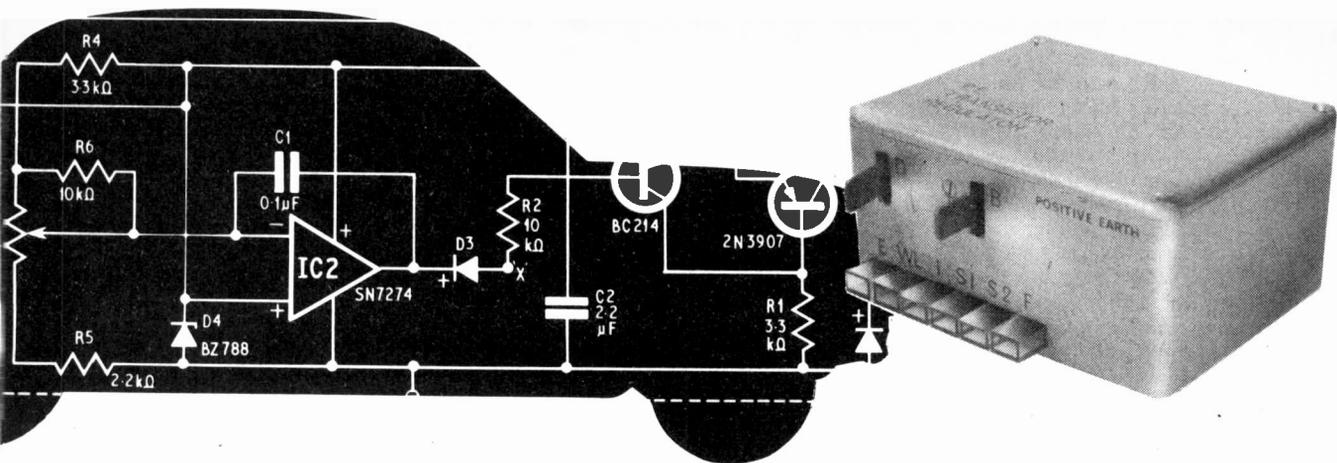

AUTO-CHARGER REGULATOR

By J.R. WATKINSON B.Sc.

IN COMMON with many other vehicle components, the voltage regulator which controls the car d.c. generator or dynamo appears to have been passed by as far as electronics is concerned. Thus regulators fitted to new vehicles today retain the same electromechanical form as when they were first devised.

VEHICLE POWER SYSTEM

The electrical devices in a vehicle which is moving are driven by power from the dynamo which in turn is driven by the engine. When the engine is not running power is still needed to operate the starter motor and ignition as well as parking lights, etc. and thus the battery is required.

Basically, when the engine is not running, the battery provides power, and when the engine is started the dynamo takes over, and recharges the battery.

REGULATOR FUNCTION

In order to charge the battery, current must be passed through it in the opposite direction to that in which it flows with the battery in use. Also in the case of a 12V battery the voltage applied must be more than 12V.

Referring to Fig. 1a, assume that the dynamo is producing a charging voltage then a current I_1 will flow, and the battery will charge.

If the generator stops the battery voltage can cause a heavy reverse current I_2 to flow as in Fig. 1b. The presence of the diode in Fig. 1c prevents this current flowing.

One of the jobs performed by the regulator is to prevent this reverse current, using a cut-out.

As the dynamo is directly coupled to the engine its speed will vary from a few hundred to several thousand rev/min, so that its output will vary accordingly. Again, the regulator must control the dynamo voltage so it does not rise too much at high speeds and cause damage.

SOLID STATE REGULATOR

The present solid state regulator has no moving parts. The circuit is shown in Fig. 2 with a table of negative earth changes in Table 1.

Operation is as follows. Diode D1 replaces the cut-out as it will only allow current to flow one way from the generator. The ignition light is connected across the diode *via* the ignition switch so that when the engine is not running it will light and when the generator voltage rises it will go out as is normal.

Transistors TR1 and TR2 switch the field current to the generator, and diode D2 suppresses the inductive spike which would otherwise occur when TR1 switches off.

The Zener diode D4 is a 5.1V device selected for low temperature coefficient. In conjunction with R3 it forms a reference voltage. R4, VR1 and R5 form a potential divider across the battery, and the integrated circuit operational amplifier IC1 compares the potential at the wiper of the preset with that across the Zener diode.

Should the voltage at the wiper of VR1 exceed 5.1V, caused by the battery voltage being driven high by the generator, then the output of IC1 will

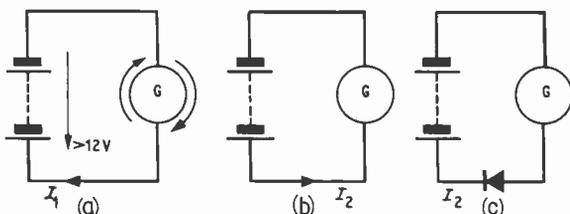


Fig. 1. Car dynamo current conditions for charge (a), incorrect discharge (b) and prevention of the latter (c)

swing towards earth, causing current to pass through D3 and R2, turning on TR3, and reducing the base current to TR2 and hence TR1.

Should the supply voltage fall below the correct amount, the output of IC1 swings away from earth, reducing the current through TR3, and allowing more base current into TR2, hence increasing the field current.

OPERATION

Operation is very similar to that of a stabilised power supply and since the battery acts as a very large capacitor and the gain of the circuit is high, regulation is very good. In practice, the needle of a voltmeter connected to the battery cannot be seen to move when the engine is rapidly speeded up from about 500 to 4,000 r.p.m.

The remaining components are C1, which limits the slewing rate of IC1 and prevents instability, C2, which shorts out any r.f. interference or spikes from the ignition and R6, which switches off the field

vibrating regulators fatigue and require readjustment periodically for optimum performance.

The generator voltage must rise appreciably above battery voltage before a mechanical cut-out will pull in, whereas the cut-out diode conducts as soon as its forward bias voltage is exceeded. Thus in traffic, the generator can operate for a slightly larger percentage of the time, easing the load on the battery.

With a little shopping around, the unit can be built for less than a new conventional regulator.

TABLE 1
For **NEGATIVE** Earth vehicles alterations to Fig. 2 are

ITEM	ACTION
Battery	Reversed
D1 to D4	"
IC1	Reverse Pins 4 and 7
TR1	Substitute OC28 or pnp 2N3055
TR2	" 2N2907
TR3	" BC214

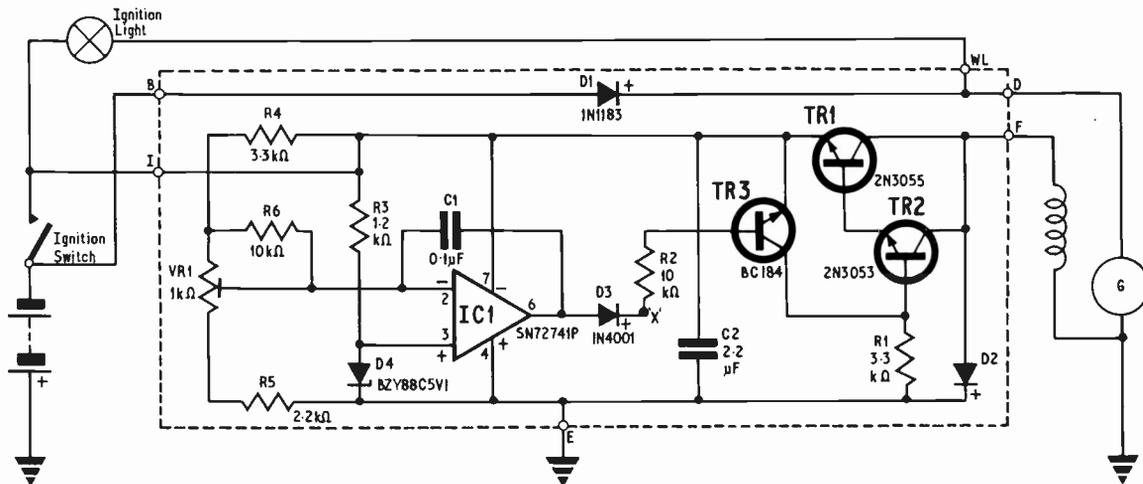


Fig. 2. Solid state voltage regulator for positive earth vehicles

Fig. 3. (Right) Added circuit to give current regulation as well as voltage regulation

current, should the wiper of VR1 go open circuit for any reason causing charging to cease, and the ignition light to come on).

To convert the regulator to combined current/voltage regulation, the circuit of Fig 3 is added. The generator current is monitored by detecting the voltage drop across the wire from the generator to the cut-out diode, and when it exceeds an amount pre-set by VR2, the output of IC2 will swing towards earth, cutting off the field current as before.

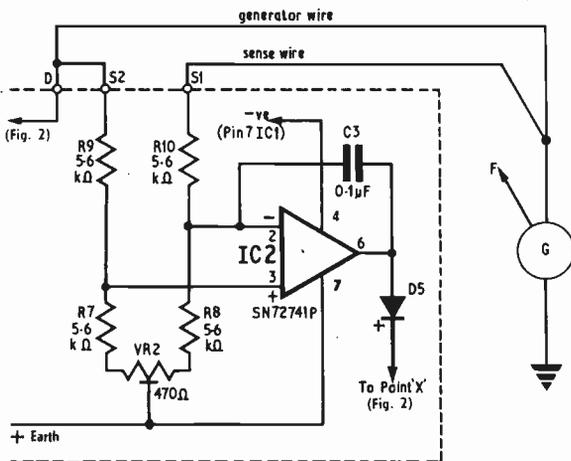


TABLE 2
For **NEGATIVE** Earth vehicles the following alterations apply

ITEM	ACTION
IC1	Reverse pins 4 and 7
Earth	Becomes -Ve
-Ve	Becomes +Ve
D5	Reverse




ADVANTAGES

As all of the active components are semiconductors, the regulator should last indefinitely, and can easily be transferred from car to car.

The precise voltage regulation obtained means that the vehicle's headlamp, and other bulbs should last longer, as filaments are very sensitive to even marginal overvoltage which can occur with conventional regulators. The unit, once adjusted, need never be touched, whereas the relay springs in

Fig. 4. Mechanical assembly of a positive earth version current/voltage regulator showing component, Veroboard and cutting details below.

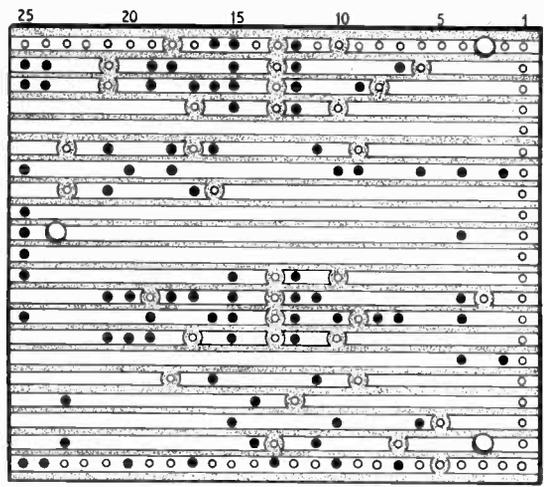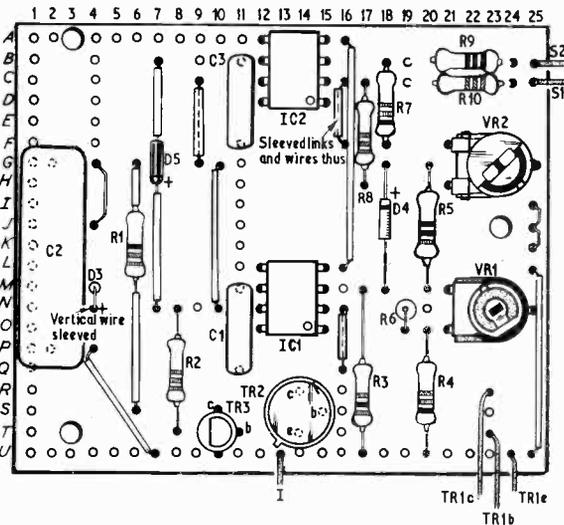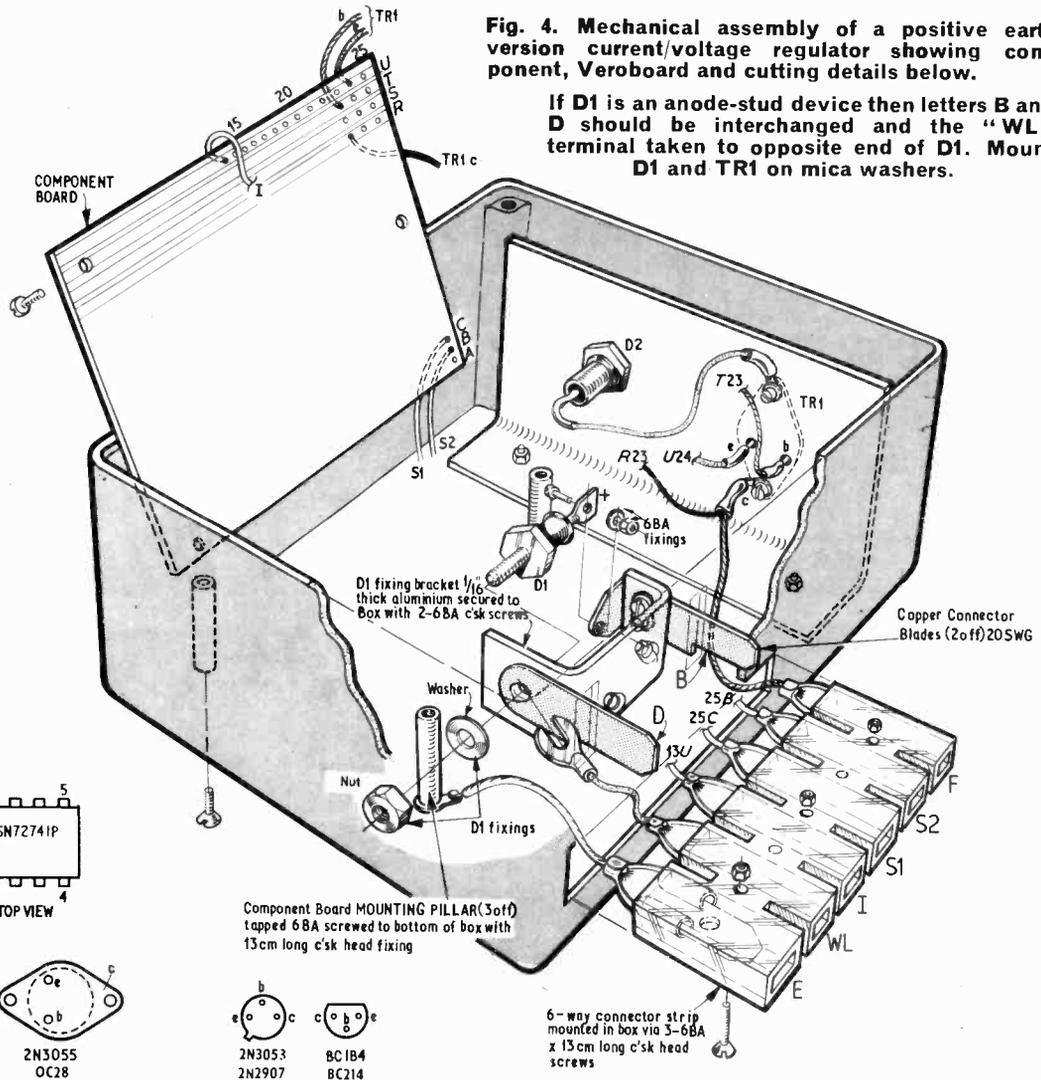If D1 is an anode-stud device then letters B and D should be interchanged and the "WL" terminal taken to opposite end of D1. Mount D1 and TR1 on mica washers.



CONSTRUCTION

The unit is housed in a die-cast box, as it is important to prevent ingress of moisture or oil.

The positive earth version is slightly easier to build as the generator flywheel diode D2 can be fitted direct to chassis.

Almost any car can be instantly converted from one polarity to the other, simply by removing the existing regulator, turning round the battery, and fitting the appropriate solid state regulator. Any car radio or other devices must also be adjusted for the correct polarity to prevent damage.

To make the unit physically compatible with a vehicle wiring system, it is fitted with blade connectors, $\frac{3}{8}$ in wide for the high current connections to the diode D1 and $\frac{1}{4}$ in wide for the rest. The $\frac{1}{4}$ in blade connectors are available in strips of 12 blades from auto electric dealers and resemble barrier strips.

The voltage regulator unit requires a four blade block to be cut from a strip, and the current/voltage regulator requires six blades. This connector block is mounted in the base of the box so as to project through a slot drilled and filed in the side.

The diode D1 should be fitted next, and as it passes a heavy current, should be well coupled thermally to the box. It must, however, be very carefully insulated from the box, as any short circuit between the two could cause severe damage to the wiring of the car.

Thus the diode is bolted directly to a 16 s.w.g. aluminium bracket, and the nut also holds the copper connector blade for the cathode (+ earth only and a tag washer). The $\frac{3}{8}$ in connector blades are made from $\frac{1}{4}$ in wide copper conduit clips, available from an electrical dealer. These clips can easily be straightened, cut and filed to size. See Fig. 4.

INSULATION

The anode connection to the diode is similarly made, and should be fastened to the diode bracket with nylon screws, and with a piece of mica for insulation. A 6BA tag washer should be included on the screw connecting the anode terminal to the blade (negative earth only).

The diode assembly should now be used to mark out two slots for the blades, and the mounting holes. Remember that the lid of the box has a flange which comes below the top of the box sides. This must not be allowed to touch the diode bracket.

The diode bracket should be fitted with nylon screws and a thin mica sheet between it and the box. Silicone grease must be used on both sides of the mica. If mica is not available, the diode bracket can be spaced off with TO3 transistor bushes, and the gap filled with silicone grease.

The assembly should be thoroughly tested, preferably with a battery and light bulb, to show that the diode is functioning, and that both its terminals are insulated from the box side.

If an ohmmeter is available, the insulation between the body of the diode and the box should be at least 1M Ω .

When tested, the space around the blades can be filled with silicone rubber to make the box water-tight again.

Next, the heat sink for D2 and TR1 should be made, and these components fitted. TR1 should be fitted with a mica washer and a tag washer under both collector bolts. Check the insulation. D2 may

be bolted direct to the heat sink for the positive earth version, but for the negative earth version it must be insulated, and a tag washer fitted for connection purposes, or an anode stud diode must be used.

CIRCUITRY

Having tested the insulation if necessary of the diode the appropriate end should be connected to the adjacent collector tag of the power transistor. The heat sink should now be fitted to the box.

The rest of the circuitry may be built on a small piece of 0.1in matrix Veroboard and mounted in the box with 6BA standoff screws and nuts. Because of the vibration environment, the transistors should be fitted with mounting pads. Do not use i.c. sockets.

The wiring should be completed as per the diagram and checked. The connections to the rear of the blade connector block are made with $\frac{1}{4}$ in push connectors crimped or soldered to the wires.

In the positive earth version, the ignition warning light terminal WL is connected to the cathode tag washer of D1, and in the negative earth version, to the anode tag.

TESTING AND ADJUSTMENT

Only the voltage regulator can be tested out of the vehicle. If the current regulator is to be added, leave out the diode D5 until the voltage regulator has been tested.

COMPONENTS . . .

Resistors

R1	3.3k Ω	$\frac{1}{2}$ W	5%	R4	3.3k Ω	$\frac{1}{2}$ W	5%
R2	10k Ω	$\frac{1}{2}$ W	5%	R5	2.2k Ω	$\frac{1}{2}$ W	5%
R3	1.2k Ω	$\frac{1}{2}$ W	5%	R6	10k Ω	$\frac{1}{2}$ W	5%
R7-R10	5.6k Ω	$\frac{1}{2}$ W	2% (4 off)				

Potentiometers

VR1	1k Ω miniature preset
VR2	470 Ω miniature preset

Capacitors

C1	0.1 μ F	250V
C2	2.2 μ F	50V (NOT electrolytic)
C3	0.1 μ F	250V Polyester

Integrated Circuits

IC1	SN72741 P.	8-pin DIL version
IC2	SN72741 P.	8-pin DIL version
Both IC1 and 2 may be replaced with one unit, the SN72747 N which is a dual 741 but cost will increase.		

Transistors

TR1	2N3055 (pos earth).	2N3614 (neg earth)
TR2	2N3053 (pos earth).	2N2907 (neg earth)
TR3	BC184 (pos earth).	BC214 (neg earth)

Diodes

D1	35A, 50V p.i.v. silicon diode
D2	10A, 50V p.i.v. silicon diode
D3	General purpose silicon diode
D4	BZY88, C5V1. 5.1V 400mW Zener
D5	General purpose silicon diode

Miscellaneous

Case, Eddystone diecast box $3\frac{1}{2}$ in \times $4\frac{1}{2}$ in \times 2in. Veroboard, 0.1in Matrix, $2\frac{1}{2}$ in \times $1\frac{1}{2}$ in. 1 \times 12 way, $\frac{1}{4}$ in blade connector strip and connectors. Assorted aluminium sheet, washers, mica, nuts and screws to suit

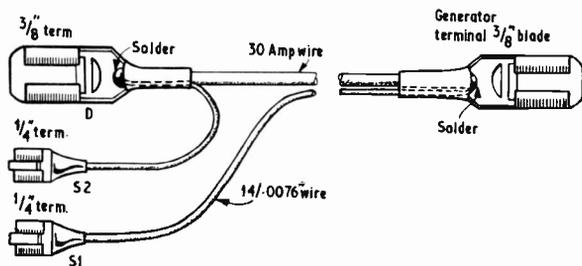


Fig. 5. Current sensing generator cable

Connect a 24W (or similar) bulb (12V) from terminal F to earth and earth the box. Turn VR1 until the wiper is at the R6 and R4 end of the track. Connect the live battery wire, in series with a 5A fuse to the I terminal. (The fuse is to protect you and the car if a short exists.) The bulb should not light.

If the wiper of VR1 is now advanced along the track, the bulb should light about 1/4-way along. This simulates a fall in battery voltage turning on the field current. Now take an ordinary 1.5V U2 battery, and connect it in series with the car battery lead to I so that the voltages add. Turn the wiper so that the bulb is *just* extinguished with the two batteries in series. If the U2 is removed and the car battery reconnected the bulb should now light again. If this procedure has been followed correctly the preset VR1 should be approximately adjusted.

The box should now be temporarily installed. Locate the old regulator and record the positions of the wires connected to it. Disconnect the live end of the car battery, and remove the wires from the old regulator, and re-connect them, terminal by terminal, to the blades on the box. Take a new wire from terminal I to any point which is switched by the ignition switch, e.g. the live side of the ignition coil, or the wiper switch.

Reconnect the battery. If there are any large sparks when attempting this, recheck the insulation of D1, and ensure it is reverse biased when the engine is stationary! If all is well, connect an accurate voltmeter across the battery and start the engine. The red ignition light should go out, and as revs increase, the voltage should rise to a little over 13V and stay there for any higher revs. The ammeter should show a charging current, which will reduce as the battery recharges after starting.

VR1 should now be accurately adjusted, with the engine revving, to set the voltage to the makers' recommended value. This can be found from a workshop manual, or from your garage, but will not be far from 15V.

CURRENT REGULATOR

If the voltage regulator only has been built, it is now complete. Disconnect the battery, remove the box, make sure all the screws are tight, then re-fit it permanently and fit the lid. After another quick check, the unit can be virtually forgotten if it has been built correctly.

For the current regulator version, now fit D5 (make sure you refer to the correct diagram, and get the polarity right), and make up a special current sensing generator cable Fig. 5.

The generator cable in most cars has a connector block in it and the contact resistance of this

will spoil the accuracy of the current regulator or could prevent any charging!

The new cable must be in one piece and of adequate rating (30A). At the generator end, the sense wire and the current carrying wire should be soldered together into the same 3/8 in blade connector, and pushed on to the generator in place of the old cable which should be tied back and insulated, for re-use, should you wish to dispose of the car and retain the regulator.

Both wires should be taken to the regulator, where a separate wire should be taken from the end of the current cable to blade S2. This again is to eliminate the contact resistance of the 3/8 in generator blade connection. The sense wire from the generator end of the cable should go to blade S1. The sense wire need not be very thick, as it is in series with 5.6kΩ resistors, which serve to swamp the contact resistance of S1 and S2 connections, and little current flows. Use 14/0076 wire or equivalent for robustness.

The next step is to measure the resistance of the current carrying conductor. As a guide, 6ft of 30A cable has approximately one hundredth (0.01Ω) of an ohm resistance.

Measure the current taken by, say, a headlamp, and call it *I*. Now connect the generator cable firmly in the same current path, and with a voltmeter on a range of approximately 0.25V f.s.d. measure the voltage across the S1 and S2 connections, and call it *V*.

The maximum safe current for the average generator is 20A and the object of this exercise is to find out what potential will exist across the sensing cable when 20A is flowing. This voltage will be given by

$$V_{20A} = 20 \times \frac{V}{I}$$

where $\frac{V}{I}$ is the resistance of the wire calculated from the noted values.

INSTALLATION

Now install the regulator as before, and fit the current sensing leads. The regulator should now have no blade without a connection to the car.

Set the wiper of VR2 to the R7 end of the track, reconnect the battery and start up. The ignition light should stay on, even when revving up. Now connect the voltmeter across S1 and S2 and slowly advance VR2 until a reading is obtained, again with the engine revving. If the full headlights and wind-screen wipers are switched on, to load the generator, then VR2 can be advanced, so that the voltage across S1 and S2 is the value V_{20A} that you calculated beforehand but not more. VR2 is now adjusted, and final installation can take place as before.

Finally, a word of warning. A car battery has a very low output resistance, and if it is shorted out, several hundred amps may flow. If a spanner is dropped across the terminals, it may be melted, or if you short out a wire you are holding, you could be burned. Before making any modification to a car's wiring, if you are inexperienced, disconnect the battery first. The battery should also be disconnected if you use a charger, with this regulator, to protect the semiconductors from transients. ★

FREE!

INSIDE OUR NEXT ISSUE

DOUBLE SIDED

BLUEPRINT

TO HELP YOU BEAT THE FUEL/POWER CRISIS....
IN YOUR CAR AND IN YOUR HOME

SCORPIO Mk 2 CAR IGNITION SYSTEM

FLUORESCENT LAMP INVERTER

Suitable for 12V and 6V vehicles the Mk 2 still gives you more miles per gallon, all weather starting, longer spark plug life, improved battery life and elimination of contact breaker bounce and burn. Also, the improved design overcomes radio interference and tachometer (rev. counter) compatibility problems.

Lighting failures needn't be a problem with this useful unit. Details are given for building an 8W, 13W or 20W version—all powered from a 12V d.c. source.

ALSO

RHYTHM GENERATOR



For the first time, a compact Rhythm Generator that allows you to select an infinite variety of rhythmic patterns using any of eight percussion instruments programmed at 16th note intervals. Tempo and dance measures are variable.



PRACTICAL

ELECTRONICS

MARCH ISSUE ON SALE FEBRUARY 8, 1974

Subject to the current National industrial situation at the time of going to press

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit - £24.95! (PLUS VAT)

The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.



- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$, weight $3\frac{1}{2}$ oz. Smart black and tan styling.
- * Standard keyboard. All you need for complex calculations.
- * Keys react with positive click when pressed.
- * Clear-last-entry feature.
- * Automatic ('implied') constant - no need for separate operating button.
- * Common-sense ('algebraic') logic - enter calculations just as you write them.
- * Calculates to 8 significant digits; fully floating decimal point positions itself automatically.
- * Clear, bright 8-digit display.
- * Unwanted zeros are suppressed.
- * Display flashes to indicate overflow.
- * Operates for weeks on four U16-type batteries.

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:


1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

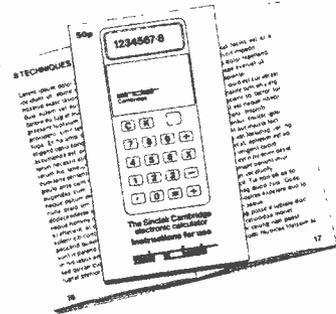But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)

Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

PE 274

Please send me

a Sinclair Cambridge calculator kit at
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready
built at £29.95 + £3.00 VAT
(Total: £32.95)

Name _____

Address _____

*I enclose cheque for £ _____, made
out to Sinclair Radionics Ltd, and
crossed.

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required.

PLEASE PRINT



Audio/Visual

THERMOMETER

By M. PLANT

ONE of the great advantages of using a thermistor sensor in an electronic thermometer is the rapidity with which temperature measurements can be made. If you combine this facet with audio and visual indication when a preset temperature is reached, one can see the versatility of the unit to be described.

The unit can be calibrated for 0°C if it is intended for use as a frost alarm for an orchard, hatchery or greenhouse. At this setting it is a useful car accessory, warning of icy roads.

CIRCUIT OPERATION

It is best to regard the circuit of Fig. 1 as consisting of two parts divided by the dotted line. The part to the left of the line is a sensitive electronic switch producing a positive voltage at the collector of TR3 when the thermistor temperature has fallen to

a value which is predetermined by the setting of the potentiometer VR3. That part to the right is a two transistor (complementary pair) astable oscillator by R9 and is switched on by the rising voltage across R8 when TR3 begins to conduct. The oscillator produces a note, the frequency of which is to some extent determined by the value of C1.

A light emitting diode provides the load in the emitter of TR4 and lights up, actually pulsing at the frequency of the note which is heard from the loudspeaker.

TR1 and TR2 are connected as a long-tailed pair since they share a common emitter resistor R3. The base of TR1 is connected to the voltage divider made up of the temperature sensitive combination TH1, VR1 and VR2. The base of TR2 is connected to the voltage divider consisting of the series combination VR3, R4, R5 and R6.

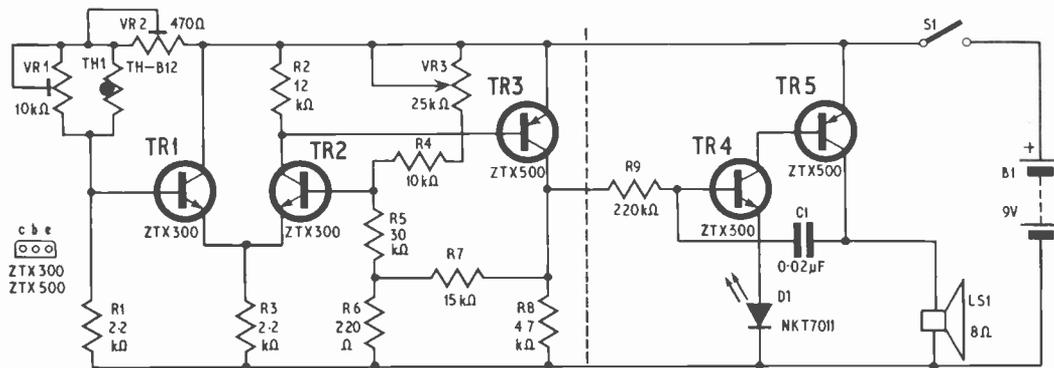


Fig. 1. Circuit diagram of thermometer

TEMPERATURE SETTING

Suppose that the base of TR2 is arranged at 3V by the temperature setting control VR3 and TR1 is at 2V. Since the emitters of these two transistors will take up the higher of these two voltages, the base/emitter junction of TR1 will be reverse-biased and that of TR2 will be forward biased. Hence TR3 will be switched on in turn switching on the oscillator due to the voltage drop across R8.

As the temperature of the thermistor increases its resistance falls since it is a negative temperature coefficient type. Thus the voltage drop across TH1 falls and the base voltage of TR1 rises. As it reaches 3V, the base voltage of TR2, both transistors are on and the speaker remains sounding a note. But as the base voltage of TR1 rises the base/emitter of TR2 become reverse biased, so that TR3 switches off hence switching off the oscillator.

TR1 and TR2 actually form a differential amplifier the on/off states of which are immune to changes of battery voltage and circuit temperature. It is both sensitive and stable giving reliable readings during the life of the battery and under different environmental temperatures.

FEEDBACK

In order that the switching on and off of TR3 is precise, positive feedback is provided by R7 between the collector of TR3 and the base of TR2.

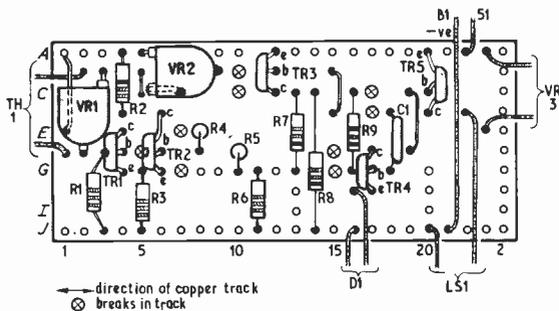


Fig. 2. Component layout and wiring

A fraction of the rising voltage across R8, as TR3 begins to switch on, is fed back to the junction of R5 and R6 which enhances the rising base voltage of TR2 so encouraging this transistor to switch hard on and hence TR3.

ASSEMBLY DETAILS

A $2\frac{1}{2} \times 1$ in, 0.1 in matrix Veroboard is used for mounting the majority of small components as in Fig. 2. The cuts to be made in the copper tracks are marked with an X.

The housing for the prototype unit was a Kodachrome transparency box which provided enough space for the board assembly, speaker, switch, temperature potentiometer and battery and kept the whole unit to pocket sized proportions.

Two types of thermistor are recommended for the thermometer. The cheaper one, VA1098, has a resistance of about 4.7 kilohms at 25°C and although its disc like structure enables connecting leads to

COMPONENTS . . .

Resistors

R1	2.2k Ω	R6	220 Ω
R2	12k Ω	R7	15k Ω
R3	2.2k Ω	R8	4.7k Ω
R4	10k Ω	R9	220k Ω
R5	30k Ω		
All $\frac{1}{4}$ W 5% carbon			

Capacitor

C1 0.02 μ F

Transistors

TR1, TR2, TR4 ZTX300 (3 off)
TR3, TR5 ZTX500 (2 off)

Diode

D1 NKT 7011 i.e.d.

Thermistor

TH1 TH-B12 or VA1098 (see text)

Potentiometers


VR1 10k Ω cermet preset
VR2 470 Ω cermet preset
VR3 25k Ω min. carbon, linear

Miscellaneous

B1—9V PP3, S1—on/off switch, LS1—2in, 8 Ω miniature loudspeaker

be attached to it easily, there is the problem of insulating the semiconducting disc against the action of conducting liquids in which it might be immersed. For this reason the glass encapsulated bead type TH-B12 is to be preferred.

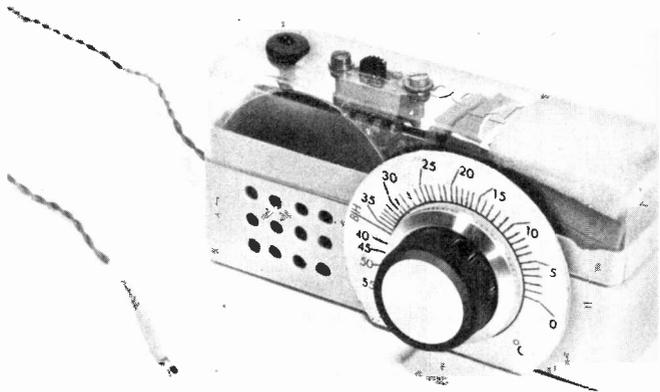In order that the leads can be insulated from contact with liquids, heat-shrinkable sleeving of 3mm diameter was used extending half way up the stem of the glass encapsulation.



The finished thermometer. Note the clearly delineated temperature scale

CALIBRATION

To calibrate the thermometer a cardboard disc of about 2in diameter should be arranged to go under the fixing nut of VR3. A pointer knob is next attached to the spindle. First crush a few cubes of ice and place them in a container with some cold water. Strap the thermistor to the bulb of a 0–100°C thermometer and use the whole to stir the ice/water admixture.


When the temperature has reached 0°C rotate the knob of VR3 until the l.e.d. comes on and the speaker sounds. Use the marker on the knob to pencil a line on the cardboard disc indicating 0°C.

Heat the ice-water gently until the ice has melted and at degree intervals mark the cardboard disc with the appropriate temperature. When the dial has been calibrated in this way, remove it and ink in the marks and the temperatures. When replacing the disc behind the nut ensure that it is placed in the original position and check by using the melting ice again that the disc, in relation to the angular position of the potentiometer, has not changed.

RESOLUTION

To ensure a resolution of 1°C between 0 and 65°C and of 3°C between 65 and 80°C the presets VR1 and VR2 are included in the circuit. Prior to the calibration process these should be adjusted to about 7 kilohms and 400 ohms respectively to achieve this. ★

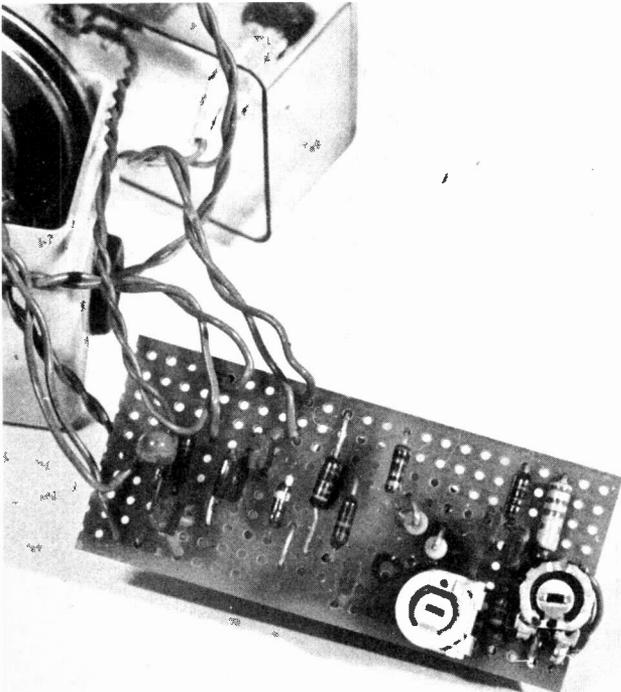Layout of components on the small piece of Vero-board



INGENUITY UNLIMITED

ELECTRONIC DOORBELL

THE circuit is basically one multivibrator running at a chosen audio frequency and switched on and off by another running at a few hertz. The pulsed signal is then amplified and fed to a loud-speaker.

The circuit diagram is shown in Fig. 1, and it operates in a similar manner to the conventional multivibrator. When power is applied circuit imbalances will favour one gate, assuming that they operate such that pin 6 goes towards the positive supply rail then C1 will charge up through R1. At first the voltage across R1 will be large but as C1 charges the voltage will fall until logic state 0 is reached at about 1.5V.

Since an unused input to a gate is at logic state 1 the output of the gate connected to R1 will be controlled by the input on pin 2, and will be in the opposite state.

Therefore when pin 2 falls to a 0 pin 3 will go to 1, causing C2 to charge up through R2 in a similar manner to C1/R1. When the voltage on pin 4 falls to logic state 0 the output on pin 6 will go to 1 and the cycle will begin again with C1 charging.

C1 will have discharged during the time when C2 was charging as at that time pin 6 will have been at 0 due to the 1 on pin 4. Similarly C2 discharges while C1 is charging.

The abrupt change of state as the logic thresholds are reached produces a square wave output. The output of the low frequency (switching) multivibrator is applied to an input of one of the gates in the tone multivibrator, and since the output of a gate will not change if an input is held at 0 the tone oscillator only runs when the output of the low frequency oscillator puts a 1 on pin 1.

A. Piper,
Teddington, Middx.


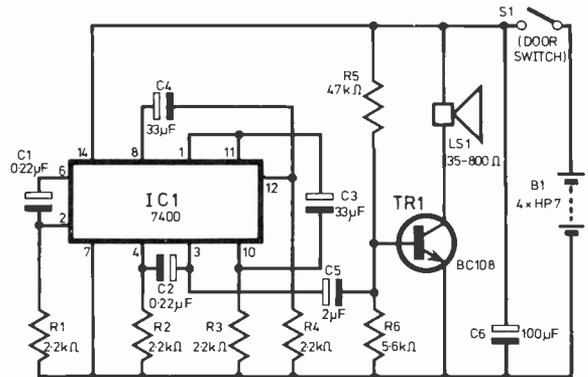


Fig. 1. Circuit diagram of the doorbell

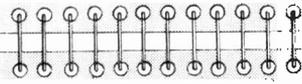

INDUSTRY NOTEBOOK

By NEXUS



TEST GEAR PERKS UP

After four dreary years of stagnation the UK instrument industry has come into a long-awaited growth phase in 1973, and 1974 looks even better with more investment capital about.

Britain's largest and strongest indigenous instrument specialist, Marconi Instruments, is expecting to top £10 million turnover in 1974. The USA is still MI's best individual country but in total volume Europe is the biggest market and getting better all the time. But they are also strong in Eastern Europe, including the Soviet Union, and have healthy and improving business in Australasia and the Middle and Near East. The Far East market is patchy although 1973 showed a lot of improvement following participation in the British exhibition in Peking.

With an engineering department of 230 people, 90 of them design engineers, the level of innovation is high and with three BCS-approved calibration laboratories MI's technical capability is beyond question. Large investment in development is now beginning to surface and no less than 14 new products are in process of being brought to the market.

Some equipment I have seen in their labs are more systems than instruments, for example the fully automated TV test equipment which monitors picture quality, provides a printout of performance at pre-arranged intervals and sounds the alarm for deterioration of quality before the viewer would even notice it.

Scheduled for early 1974 is a new spectrum analyser which is definitely in the world class, and a white noise equipment with a number of technical advances.

MI's Autotest automatic testing systems are now doing well.

The upturn in instrument business was confirmed by Peter Finch, managing director of Labhire, the rental company. Having got the company well established in the UK, Finch is now branching out in Europe. His French operation, based in Paris, is headed by Guy Goulet, formerly head of Schlumberger's sales network in France. A Dusseldorf office has been opened under Rainer Mader and a second base in Germany is soon to be set up in Munich under Kuno Vinbruck, formerly Schlumberger's sales co-ordinator in Germany.

Nothing if not ambitious, Finch is busily planning expansion of the Labhire service into Scandinavia, Italy and Spain. Europe, he believes, has fantastic potential for instrument hire. The belief is clearly shared by the top Schlumberger executives who have joined him in the enterprise.

NEW ARRIVAL

A market revival always attracts new entrants. Look out for a miniature oscilloscope from Lawtronics, better known as a semiconductor distributor in Kent. Bernard Lawson has one on the stocks, battery-operated and weighing but 3lbs. Specification is said to include 10MHz bandwidth and 10mV sensitivity at 1MHz and 500mV at 10MHz. Price not yet fixed but I understand it will be less than £100.

Initially Lawson plans to put manufacture out to sub-contract but hopes to set up his own plant, in which case the Pocket Scope will be supplemented by a whole range of tiny instruments.

COMPONENT HEADACHES

Component supply is still a headache. Because big users have been ordering here, there and everywhere in the hope of getting what they can, the manufacturers have only the slightest idea of what the demand really is. All they know with certainty is that business has never been better.

Harlow-based B & R Relays tell me that their problem as a manufacturer is now materials supply. Some types of plastics as well as steel are getting difficult. And a sign of the times is that Siemens' flat-pack relays which B & R import as a factored line are selling better than ever despite a price rise (from devaluation of the Pound in relation to the DM) of what at one time would have been a crippling 30 per cent in a single year. Price, says B & R managing director Brian Austin, is no barrier if the product is really needed.

A change in marketing policy for 1974 is also announced by B & R. A decision has been made to sell small quantities (typically 200-off or less) through distributor stockists while the big orders, such as one for 20,000-off recently won, will be handled direct.

HUGE MLS MARKET

A £1,000 million market is not to be sneezed at. This is the estimate for Microwave Landing Systems (MLS) to replace the present Instrument Landing Systems (ILS) at the world's airports. ILS is at the limit of technical "stretch", the best examples being seen at London Airport, Heathrow, and at Dulles, USA, and Orly, France, all of which have Category III installations for fully automatic landing.

There are several problems with ILS, the most important being siting constraints which introduce difficulty at many airports, and the heavy operational constraints because aircraft have to follow a precisely defined centre-line and glide-slope approach.

With MLS, which will operate at 5GHz, it is much simpler to install and aircraft can make their approaches on a curved path and at what angle of descent is most appropriate — a big plus-feature with new generations of STOL and VTOL aircraft on the drawing board.

Technical proposals for MLS are currently being submitted to a Working Group of the International Civil Aviation Organisation (ICAO) All Weather Operations Panel. The two basic proposals under consideration are a microwave scanning beam system and a commutated Doppler technique. The British proposal is for the latter and Plessey Radar is involved in a £1 million development programme in co-operation with the Ministry of Defence Procurement Executive and the Department of Trade and Industry.


The commutated Doppler principle is due to the British navais pioneer Charles Earp who is a consultant to Plessey Radar. First hardware for the proposed system will be delivered to the Royal Aircraft Establishment for evaluation trials by mid-74.

Meantime, it will be up to ICAO to decide on the best system from technical proposals put forward by the UK, USA, Germany, France and Australia. Decision will be purely on technical merit and whatever the system finally decided upon there will be plenty of work for all the "contestants".

Safety of passengers is an essential so MLS will have a long evaluation period and first operational systems are not expected to be in service before 1980.

AUDIO MILLIVOLTMETER

By J. N. WATT

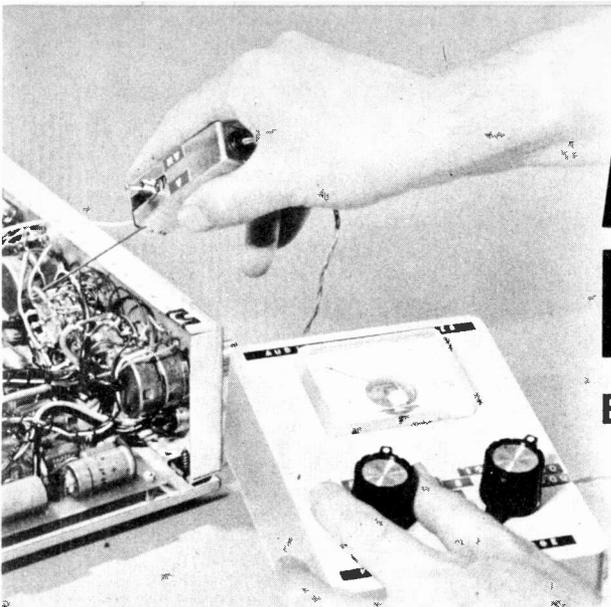

SPECIFICATION

Ranges	1mV to 100V r.m.s. f.s.d. in 11 ranges
Frequency response	30Hz to >50kHz
Input impedance	1M Ω
Accuracy	3% f.s.d.
Amplifier output	0.5V r.m.s.
Power supply	Two nine volt batteries

MOST of the multi-range testmeters used by home experimenters have a.c. ranges that do not extend down to as low levels as the d.c. ranges. This is a pity, for such testmeters often have a frequency response up to at least a few kilohertz, and meaningful measurements on audio amplifiers would frequently be useful if they could be made at the lower levels commonly encountered.

This lack of sensitivity makes it impossible to trace signals through a multi-stage amplifier or through a filter, for example. The measurement of hum levels on supply lines, via a d.c. blocking capacitor, is another field where a highly sensitive meter would be an advantage.

It was with these factors in mind that the unit described here was put together. It has a full scale deflection, on the most sensitive range, of 1mV, a frequency range of 30Hz to at least 50kHz, and an input impedance of 1M Ω .

An additional feature is the capability of the unit being used as an amplifier with a voltage gain of up to 500, and for this purpose an output socket is provided, with the internal meter switched out.

Thus a useful pre-amplifier stage for oscilloscopes and amplifiers is available.

SEPARATE PROBE

The instrument described here consists of two principal parts, namely the main unit, containing the meter, fine range and function switching and the meter amplifier, and a small probe, which contains an f.e.t. pre-amplifier and a divide-by-1,000 switch for coarse range switching.

Why is it necessary to have this separate probe? Consider the situation where a pair of test leads, say 1ft long, are used to connect a test instrument to an amplifier or other equipment under test. It is

quite likely that the capacity existing between this pair of leads could be 30pF or so, which corresponds to a reactance of 1M Ω at only 4kHz.

Since this millivoltmeter has been arranged to have an input impedance of 1M Ω (so that no undue loading of the circuit under test should occur), it follows that at a frequency of 4kHz an error in measurement by a factor of about two would be present; at higher frequencies these errors would become worse, so that at 20kHz the reading registered on the millivoltmeter would be about 17 per cent of the correct value.

An external probe improves matters in the following manner. Connections from the small, readily handled probe to the test circuit are easily kept very short and can in fact be no more than an inch or two if required.

The circuit contained in the probe has a high input impedance and a low output impedance, and thus the impedance level at which signals are conveyed to the main unit is very much lower than 1M Ω (in point of fact it is of the order of 1k Ω), so that although the probe is used on a lead of about one foot in length and of perhaps 30pF self capacitance, no error due to that capacitance arises.

FREQUENCY RESPONSE

Theoretically, this particular layout would introduce no error until a frequency of about 6MHz is reached—a frequency well beyond the upper limit of the main instrument.

This raises the question of frequency response. The lower limit of 30Hz should cover most audio requirements and ensure that measurements can be made of 50Hz mains ripple on supply lines, etc.

The upper limit is quoted at 50kHz simply because it was found that the unit was linear up to that

point and 50kHz was the upper limit of the author's audio test gear! Investigation with an r.f. generator was unfruitful, since the millivoltmeter had been designed to have an upper limit of about 100kHz.

The upper limit was set at this point for two reasons. Firstly, with the readily available integrated circuit employed, attempts to obtain reliable amplification at much higher frequencies would most likely lead to instability problems, unless stringent precautions in respect of layout were taken. This could have created difficulties in a home construction design.

Secondly, with such an upper limit, spurious pick-up of high power broadcasting stations such as Radio 2 on 200kHz will not cause difficulties.

At the same time, the quoted upper limit of 50kHz is so far above the audio spectrum that no doubt about the instrument's fidelity could be levelled at it on that score.

CIRCUIT OPERATION

Consider now the overall circuit diagram of Fig. 1. Input to the probe is via S1 (used to select either volts or millivolts range) which, in the "mV" position passes the signal, via C3 and R4, to TR1. Capacitor C3 is a d.c. blocking capacitor, R3 is the gate resistor of TR1 and sets the input impedance on the "mV" setting of S1, while R4 limits any gate current to a safe value. Excessive gate current could otherwise flow, due, for instance, to charging and dis-

charging of C3 whenever the probe input was connected to a point at a high d.c. potential.

With S1 in the "V" position, division of the input voltage by a factor of 1,000 takes place by means of R1 and R2, with C1 and C2 providing frequency compensation.

Without these two capacitors, stray capacitance across R1, R2 and S1 would give unequal voltage division at different frequencies. Details of how C1 is adjusted for best performance are given later.

The transistors TR1 and TR2 are used in a very stable configuration in which a voltage gain of about six times is obtained. Only TR1 however is in the probe itself, TR2 and its associated collector load resistors being housed in the main unit, thus allowing the probe to be built in as small a volume as possible.

The signal paths from the probe to the main unit are in fact the source lead of TR1 which is at low impedance, and the connection to the base of TR2, similarly at low impedance.

Variable resistor VR1, decoupled by C4, is required so that the correct d.c. working voltage can be set at TR2 collector, thus allowing for the rather wide spread of characteristics usually found in the low cost f.e.t. used for TR1.

The amplified signal appearing at TR2 collector is passed to the high accuracy attenuator R8 to R13, the appropriate range then being selected by S2 for further signal amplification by IC1.

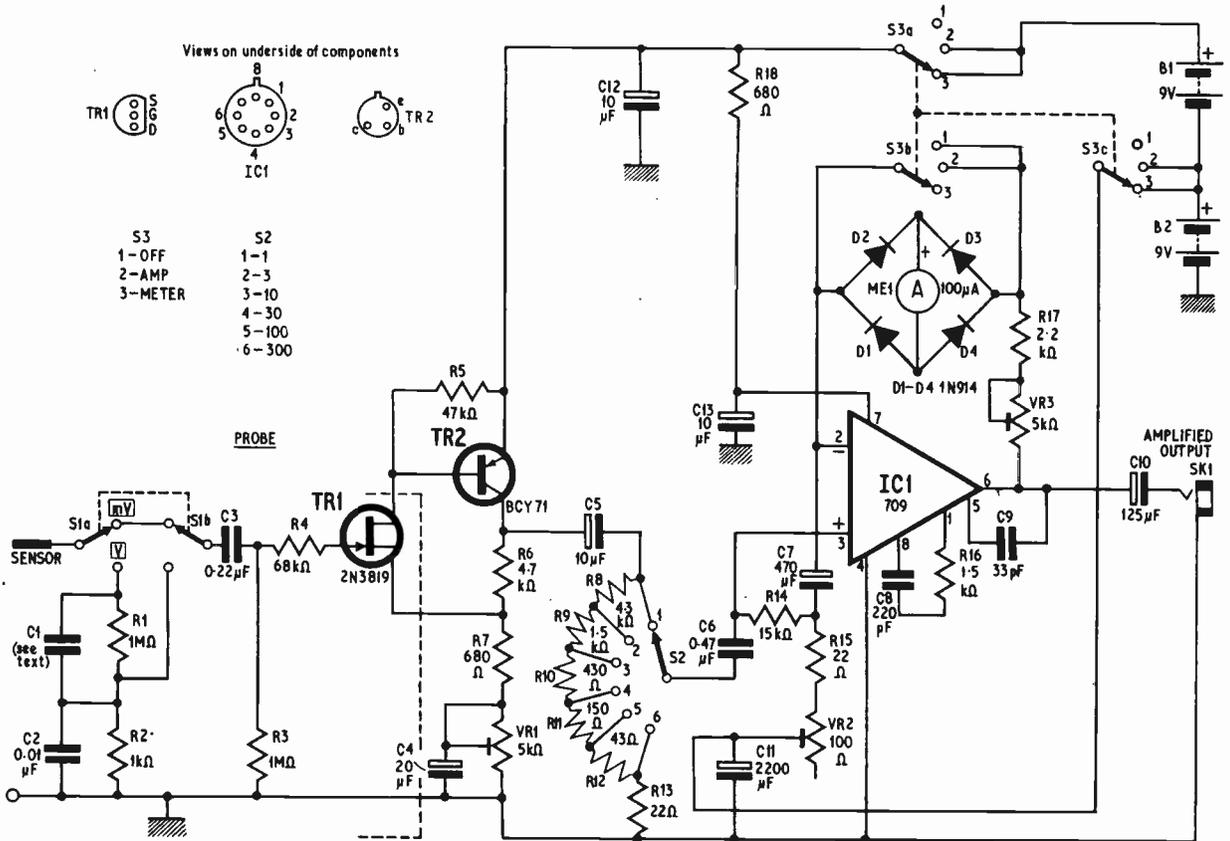


Fig. 1. Circuit diagram of the Audio Millivoltmeter. The circuit to the left of the dotted line is that contained within the separate probe

This particular integrated circuit is probably the most readily available linear i.c. on the market and is advertised under various type numbers, all of which include the figures "709". We require the TO99 (similar to TO5) version.

INTEGRATED CIRCUIT AMPLIFIER

Integrated circuit IC1 is arranged as a non-inverting amplifier, i.e. the output is in phase with the input. The output is fed back, via the bridge rectifier D1 to D4 and the meter, to the inverting input, and, due to the very high gain available in IC1, the signal at the inverting input terminal closely follows that at the non-inverting input.

Since C7 has a negligible reactance, current through R15 and VR2, and hence through the meter, depends only on the input voltage. This is the case even with the diodes included in the circuit and hence linearity is assured even at small signal levels.

It is this effect that enables the instrument to respond accurately to signals as small as 1mV.

Signals fed back from the output of IC1 appear in phase with the input signal at the lower end of R14, thus R14 has signals of almost equal amplitude and of the same phase at each end, so that its apparent value is thereby very much greater than its actual value, so increasing the input impedance of the i.c. stage. This effect is known as "bootstrapping".

This bootstrapping method of increasing input impedance prevents loading of the attenuator R8 to R13, while at the same time it allows the use of a resistor of fairly low value for R14.

A greater value resistor in this position could cause d.c. offset at the input to IC1 due to the unavoidable current flowing in R14 from the i.c. non-inverting input terminal, caused by base current in the i.c.'s input stage.

Keeping R14 down to the value employed here ensures that this effect gives rise to no inaccuracy in meter deflection.

The capacitor C7 has been chosen to be 470 μ F to ensure that little phase shift occurs in the signal fed back to the lower end of R14 even at low frequencies, so preserving the bootstrap effect.

VOLTAGE LINES

The sensitivity of the millivoltmeter is set by adjustment of VR2 by a method to be described later. This resistor is returned to the +9V line, so ensuring that the non-inverting input of the i.c. (and hence, by the negative feedback action already described, the inverting input also) is maintained at about half way between the positive supply rail (in this case +18V) and the negative supply rail (in this case ground).

Often, it is arranged that these supply rails lie either side of zero potential, e.g. +15V and -15V, but in this case it was thought best to earth one side of the supply and use a centre-tapped battery to produce the same effect in the manner described.

The very large value of capacitor employed for C11 ensures that the source impedance of the +9V rail is maintained at a sufficiently low value even at the lowest frequency at which the millivoltmeter is to be used. Unwanted impedance here would have the effect of increasing the apparent value of R15 plus VR2; this unwanted increase would have led to incorrect meter deflection at the lower frequencies.

DECOUPLING AND FREQUENCY COMPENSATION

Since both the pre-amplifier stage (TR1 and TR2) and the main amplifier (IC1) are both arranged as non-inverting amplifiers, there is a danger that via the +18V supply rail, thereby leading to errors. Coupling could take place between the two stages. Accordingly, R18 and C13 are incorporated to decouple the supply to IC1.

Components C8, R16 and C9 have the values recommended by the i.c. manufacturer for stable operation under the gain/frequency conditions used here, and serve to limit the frequency response to the desired value, as mentioned earlier.

Variable resistor VR3 and fixed resistor R17 set the overall gain of the main amplifier stage to give a convenient level at the output when the instrument is used in the "amplifier" mode. In that condition, the diode bridge D1 to D4 is shorted out by the pole of S3b; if these diodes were to remain in circuit, distortion of the output waveform would result, due to their almost constant voltage drop.

Before going on to constructional details, it is worth noting that the gain of the pre-amplifier is determined by the ratio of the value of two resistors, namely R6 and R7, while in the main amplifier, meter deflection is set by the value of the combination of R15 and VR2.

These methods of stabilising gain mean that any alterations in transistor or i.c. parameters have no deleterious effect on the meter reading. Further, the additional complexity of a stabilised power supply, together with the resultant power consumption, is thereby rendered unnecessary.

CONSTRUCTION

Practical construction can be arranged to suit individual requirements, but that shown in Figs. 2 and 3 is recommended.

A robust die-cast box gives both excellent mechanical protection and electrical screening and the size chosen is small enough to make the instrument light and readily handled.

Construction of the probe (Fig. 2) will depend to some extent on what is available to the particular constructor. In the author's case, a screening can from a valve type i.f. transformer was employed (an old TV set is one good source of supply), but provided the general layout is followed, almost any metal container of the appropriate size can be used.

The switch S1 is held down to the strip of 0.1in Veroboard by thin tinned copper wires threaded through its terminals. A slot cut in the can side takes the switch bush and this is retained by the fixing nut.

The coil former was cut away from its base and then discarded, and the Veroboard joined to the base by means of wire soldered into three of the six terminal holes; one of these wires is continued through on the outside as an earth connector to the equipment under test, while the centre one is brought out using 18 s.w.g. tinned copper wire to form a probe, for signal input.

Three wires are passed through the centre hole at the top of the can to connect the probe to the main unit, while the Veroboard holding the components is wrapped in a piece of polythene sheet to guard against inadvertent contact with the case.

COMPREHENSIVE HOME CONSTRUCTOR KITS

AS SPECIFIED IN THE P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ* MATRIX DECODER *TM CBS Complete kit. Post Free. Inc. CBS Licence Fee + VAT 80p	£8.00	RONDO CASE Post Free. + VAT 17p	£1.75
PREAMPLIFIER BOARD Complete kit. Post Free. + VAT 30p	£3.00	HARDWARE PACK Post Free. + VAT 20p	£2.00
MASTER VOL./TONE/BALANCE BOARD Complete kit. Post Free. + VAT 85p	£8.50	CONTROL SECTION FASCIA Post Free. + VAT 35p	£3.50
POWER AMP BOARD AND HEATSINK (Stereo Pair) Complete kit. Per Board. Post Free + VAT 75p	£7.50	STEREO DECODER KIT Post Free. + VAT 39p	£3.98
POWER SUPPLY BOARD COMPLETE Post Free. + VAT 50p	£5.00	STEREO DECODER READY BUILT AND TESTED Post Free. + VAT 49p	£4.98
MAIN SMOOTHING CAPACITORS (TWO reqd.) Post Free. + VAT 15p Per Pair	£1.50	GOLDRING G101/2 TURNTABLE Less Cartridge Post Free. + VAT £2.29	£22.90
MAINS TRANSFORMER Post Free. + VAT 62p	£6.25	DEUTSCHE ELAC STS 144/17 CARTRIDGE Post Free. + VAT 69p	£6.90
CHASSIS-PUNCHED AND DRILLED WITH SCREENS Post Free. + VAT 32p	£3.25		

**L
S
O
U
B
S
P
Y
S
T
E
M
S**

READY BUILT LOUDSPEAKERS (Teak or White Veneer) Post £2.00. + VAT £4.40	£42.00 Per Pair	BASS DRIVE UNITS (2 per cabinet) Post Free. + VAT 39p	£3.95 EACH
COMPLETE SPEAKER KIT WITH 4 DRIVE UNITS, CROSS-OVER WADDING, ETC. (Four kits reqd. for Rondo) Post 50p. + VAT £1.90	£18.50 EACH	TWEETERS (2 per cabinet) Post Free. + VAT 12p	£1.20 EACH
DITTO Per Pair Post £1.00. + VAT £3.55	£34.50	CROSSOVER KIT (1 per cabinet) Post Free. + VAT 25p	£2.50 EACH
DITTO Per Four Post £2.00. + VAT £6.40	£62.00	WRAPROUND CABINET (Teak or White Veneer) Post 50p. + VAT £1.00	£9.50 EACH

SONAX
ELECTRONICS
SPENCER HOUSE
BRETENHAM ROAD
EDMONTON
LONDON, N.18

TRADE ENQUIRIES WELCOME

PLEASE SEND ME

- CBS SQ DECODER BASS DRIVE UNITS ()
- PREAMPLIFIER BOARD TWEETERS ()
- MASTER VOLUME BOARD CROSSOVER KIT ()
- POWER AMP BOARDS CABINET KIT WHITE ()
- POWER SUPPLY BOARDS CABINET KIT TEAK ()
- SMOOTHING CAPACITORS COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSSOVER WADDING, ETC. WITH WHITE CABINET ()
- MAINS TRANSFORMER DITTO WITH TEAK CABINET ()
- CHASSIS
- STEREO DECODER KIT
- STEREO DECODER BUILT
- READY BUILT LOUDSPEAKER TEAK CABINET ()
- READY BUILT LOUD-SPEAKERS WHITE CABINET ()
- GOLDRING G101 TURN-TABLE LESS CARTRIDGE
- ELAC 144 CARTRIDGE

Please insert quantity in open brackets

BLOCK CAPITALS PLEASE DETAILS OF ANCILLARY KITS

NAME

ADDRESS

PLEASE TICK BOX

- RONDO CASE
- HARDWARE PACK
- CONTROL SECTION FASCIA

MONEY ENCLOSED

£


CHEQUE

P.O.

MONEY ORDER

P.E.2/4

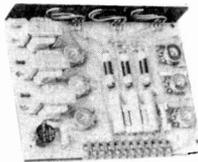Mk III Sound to Light Unit Chassis Version




The audio drive voltage is derived directly from the amplifier output or across the speaker load. The unit converts the audio-frequency signals into a three-coloured light display when used with coloured flood lamps or similar; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size: 9in x 7in x 3in. Price £27.50.



MN3 3 Channel I.C. Mixer Kit.

Three channel I.C. audio mixer kit MN3 is specially designed for the home constructor or educational project. Suitable for use in domestic audio, discotheque and, simple p.a. applications. The MN3 mixer kit has the following features: Advanced design using 5 ICs; Slider fader level controls mounted directly to p.c. board; Full range Bass and Treble controls; Uses top grade components with fibreglass ready-drilled and tinned printed circuit board and the unit may be operated from twin 9V batteries (PP3) if required.

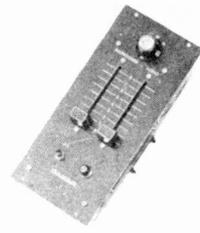As optional extras, an attractive ready-punched fascia panel and control knobs are available. The unit is available as a ready built mixer with fascia. Size: 9.5in x 4.8in x 1.5in (with fascia). Construction manual available separately at 25p. Kit Price £11.



STL/1 Single Channel Sound to Light Unit


Single channel "Sound to Light" unit with 60mm slider fader controls for audio trigger level and background load dimmer. This unit is switchable for response to High, Mid, and Low frequency audio signals, selected by fascia control. A D.J. "pulse-flash" push button is fitted for manual flashing of the lamp load together with neon load indicator. Maximum Load: 1kW at 240V a.c. Size: 8in x 3.6in x 3in. Price £14.30.

Practical Electronics "Scorpio" Electronic Ignition System Kit



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc. Case size: 7.25in x 4.5in x 2in approx. Complete assembly and wiring manual 25p. Price £12.10.

STL/3 Sound to Light Unit

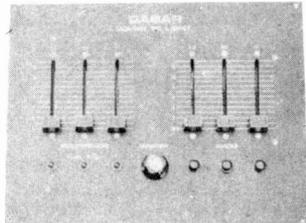

The performance of this unit is similar to the Mk III chassis version above, but is provided with an attractive black anodised fascia panel and designed to mount directly into equipment desks or cabinets. High, Mid, and Low frequency channel sensitivity controls employ 60mm slider faders for present-day attractive appearance and ease of use. Size: 11in x 8.5in x 4in. Price £42.35.


AUDIO EFFECTS

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES, ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9V BATTERY (not supplied). COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD AND FULL INSTRUCTIONS. KIT PRICE £2.86.

All prices quoted include postage and VAT. S.A.E. for further details.

DABAR ELECTRONIC PRODUCTS
98 LICHFIELD STREET, WALSALL
STAFFS WS1 1UZ

INTER-LOCKING PLASTIC STORAGE DRAWERS

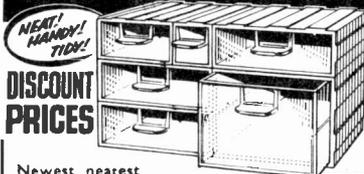

NEAT!
HANDY!
TIDY!

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/ID and 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES
ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £1.40 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). £2.30 DOZEN.

TREBLE (3D) £2.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £3.60 for 8, **EXTRA LARGE SIZE (6D1)** £3.40 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £10 and over DEDUCT 5% in the £ Orders £20 and over DEDUCT 7½% in the £ Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES Please add 10% V.A.T. to total remittance

FLAIR (Dept. PE2) 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4844

4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 17p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £18.85. P. & P. 60p extra.

INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 35p.



Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/2)
169 KENSINGTON HIGH STREET, LONDON, W 8

OSMABET LTD.

We make transformers amongst other things.
AUTO-TRANSFORMERS, 110/200/220/240V.
500W, £9.30; 750W, £12.75; 1000W, £15.75; 2000W, £28.50; 3000W, £39.00; £60.00, etc.
LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 6A CT, £2.10; 12V 1.5A, £1.85; 3A £2.15; 6A CT, £2.80; 18V 1.5A CT, £2.15; 24V 1.5A CT, £2.15; 3A CT, £2.85; 5A, £4.30; 6A, £5.75; 12A £9.40; 40V 3A CT, £3.75; 50V 6A CT, £11.25; 25V 2A + 25V 2A, £4.15.
LT TRANSFORMERS TAPPED SEC. Prim. 200/240V
0-10-12-14-16-18V 2A, £2.25; 4A, £3.40;
0-12-15-20-24-30V 2A, £3.00; 4A, £4.05;
0-5-20-30-40-60V 1A, £3.00; 2A, £4.20;
0-40-60-80-80-90-100-110V 1A, £4.20.
MIDGET RECTIFIER TRANSFORMERS
For FW rect.: 200/240V a.c. 0-9-9V 0-3A, 12-0-12V 0-25A or 20-0-20V 0-15A, £1.45 each; 9-0-9V 1A, £1.20; 12-0-12V 1A or 20-0-20V 0-75A, £1.85 each.
MAINS TRANSFORMERS FOR POWER AMPLIFIERS
AMPLIFIERS
Prim. 200/240V a.c. TX6 sec., 425-0-425 500 Ma, 6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A, £15.00;
TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £9.40; MT3 Prim. 0-110-240V, Fec. 260V, 100 Min Amp, 6.3V 2A E-F £1.50.
O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3-8-15ohms, A-A 6-6kΩ 30W, 44-80; A-A 3kΩ 50W, £2.00; 100W (E134 KT88, etc.), £18.60; tapped Multi O/P 10W, £2.25.
G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30 to 400W, 30p.
LOUDSPEAKERS FOR POWER AMPLIFIERS
BAKER 25W, £6.40; 35W, £7.20; HI-FI, Major Module 20W w/tweeter Xover, £9.20; Baker speaker Hets; FANE 50W, £10.50; 60W, £13.60; EMI 13 x 8in 3 or 15Ω, £1.60; speakers for HI-FI 5in 8Ω, £1.15; 8 x 5 in 3, 8 or 15 Ω £1.75.
LOUDSPEAKERS
2½in 8, 16 or 75Ω, 2½in 8 or 25Ω, 3in 8, 15 or 35Ω, 3½in 8, 15 or 80Ω, 80p; 5in 3, 8, 15, 25 or 35Ω, 5 x 3in 3, 8 or 25Ω, £1.05; 6in 3Ω, 7 x 4in 3, 15 or 25Ω, 8 x 2½in 3Ω, £1.28; 8 x 5in 3, 15 or 25Ω, £1.50; 10 x 6in 3Ω, £1.50.
SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15Ω up or down, £1.15.
BULK TAPE ERASERS
Instant erasure, tape spools, cassettes, demagnetises tape heads a.c. 200/240V a.c. £3.25 plus P. & P.
CONDENSERS
Block 4mfid 800V, 75p; Electrolytic, 900mfid 350V, 50p; 200 + 100 + 100/350V, 50p.
TAPE RECORDER MOTOR
Blowers, Fans, etc., New 110V a.c. 60p each. V.A.T. extra on all orders.
Carriage extra on all orders.
S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 9JY
Tel. 01-958 9314

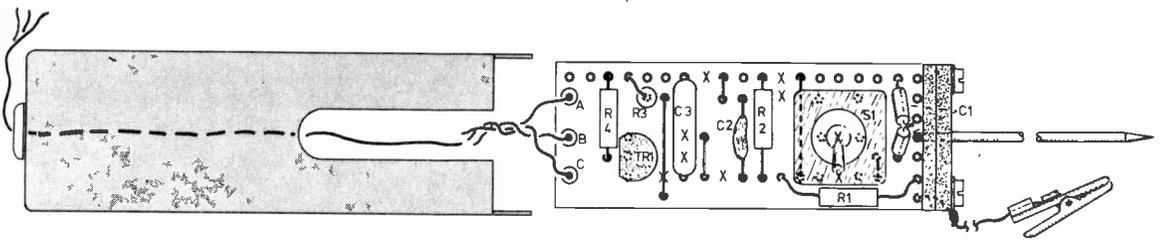


Fig. 2. Construction of the probe which forms a separate hand-held unit. The circuit on the Veroboard must be screened; an old coil screening can was used in the prototype

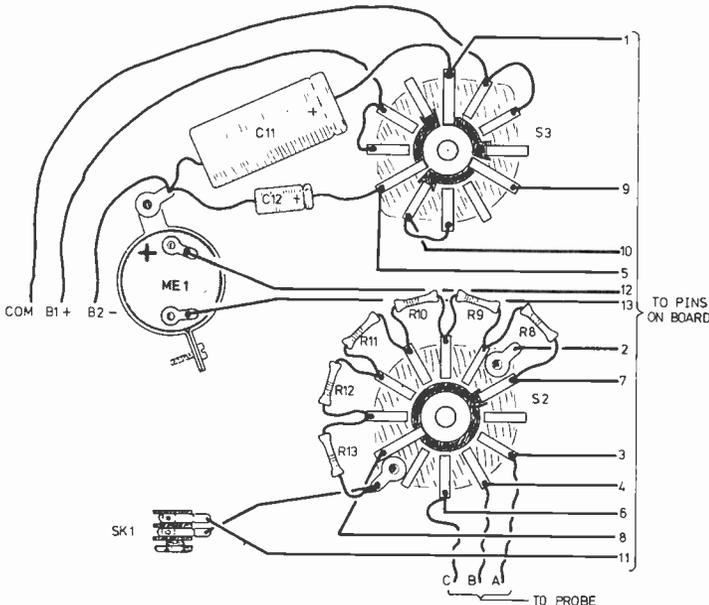
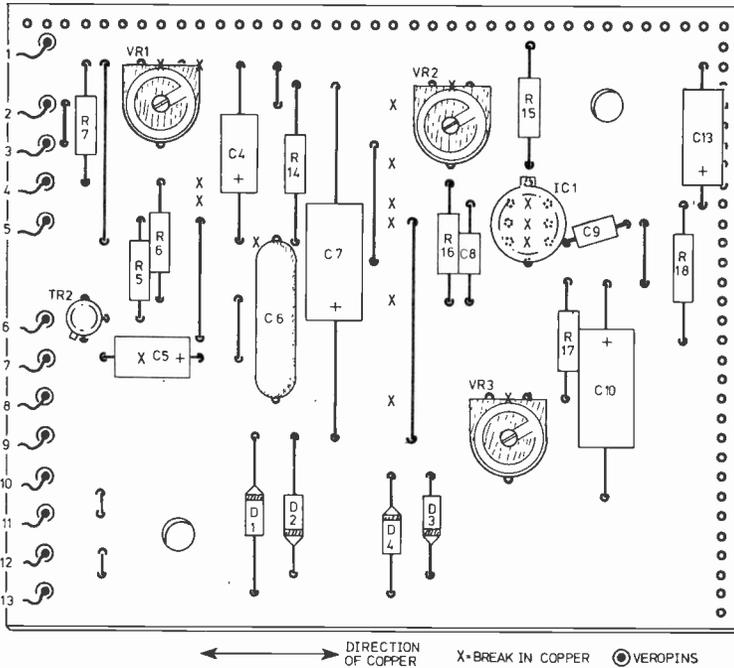


Fig. 3. Construction of the main unit of the Audio Millivoltmeter. The Veroboard is mounted in the lid of the box and the other components in the base (see photograph)

COMPONENTS . . .

Resistors

R1	1M Ω 2%	R10	430 Ω 2%
R2	1k Ω 2%	R11	150 Ω 2%
R3	1M Ω	R12	43 Ω 2%
R4	68k Ω	R13	22 Ω 2%
R5	47k Ω	R14	15k Ω
R6	4.7k Ω	R15	22 Ω
R7	680 Ω	R16	1.5k Ω
R8	4.3k Ω 2%	R17	2.2k Ω
R9	1.5k Ω 2%	R18	680 Ω
All $\pm 5\%$ $\frac{1}{4}$ W carbon unless otherwise stated			

Potentiometers

VR1	5k Ω	} horizontal skeleton presets
VR2	100 Ω	
VR3	5k Ω	

Capacitors

C1	see text
C2	0.01 μ F ceramic
C3	0.22 μ F polyester
C4	20 μ F 10V elect.
C5	10 μ F 16V elect.
C6	0.47 μ F polyester
C7	470 μ F 3V elect.
C8	220pF
C9	33pF
C10	125 μ F 10V elect.
C11	2,200 μ F 16V elect.
C12	10 μ F 25V elect.
C13	10 μ F 25V elect.

Semiconductors


D1-D4	1N914 or similar small signal silicon (4 off)
TR1	2N3819
TR2	BCY71
IC1	709 TO5 can

Switches

S1	Miniature d.p.d.t. toggle
S2	2-pole 6-way make-before-break wafer (only 1 pole used)
S3	4-pole 3-way make-before-break wafer (only 3 poles used)

Miscellaneous

ME1	100 μ A f.s.d.
SK1	3.5mm jack socket
Diecast box 6 $\frac{1}{2}$ in \times 4 $\frac{1}{2}$ in \times 2in	
0.1in matrix Veroboard	
3 $\frac{1}{2}$ in \times 3 $\frac{1}{2}$ in and 2in \times $\frac{1}{2}$ in	
Screening can for probe, knobs, nuts and bolts, grommets, etc.	

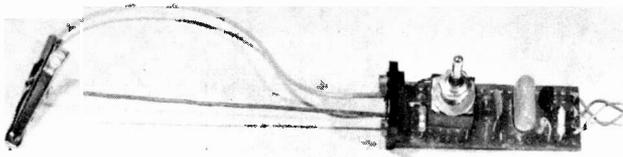

Photograph showing the internal construction of the hand-held probe. The screening consists of a coil screening can. It is bolted to the tag holding the lead to the earth clip

MAIN UNIT CONSTRUCTION


The construction of the main unit (Fig. 3) follows a conventional pattern, with the two switches and meter on the front panel, and the 0.1in pitch Vero-board mounted on the rear (or lid) of the box. For insulation, two thicknesses of 2mm polystyrene wall insulation are interposed between board and box lid, with the board held in place by means of two 6BA screws and nuts.

Two PP3 batteries are used. Held together with rubber bands, they are clamped in place, when the box lid is tightened down, by a piece of foam plastic glued to the lid, and prevented from sideways movement by means of a scrap of ¼in hardwood, glued to the box itself.

Resistors R8 to R13 are best mounted on the wafer of switch S2, which must be of make-before-break action. Should a break-before-make switch be employed, when S2 is operated, the i.c. will have only R14 at its non-inverting input between positions, and since this latter resistor appears to the i.c. to be very much larger than its actual value due to the bootstrap action described earlier, sufficient random noise would be generated to give a large unwanted meter deflection.

Switch S3 should also be of make-before-break action, to preserve continuity of battery supply when switching.

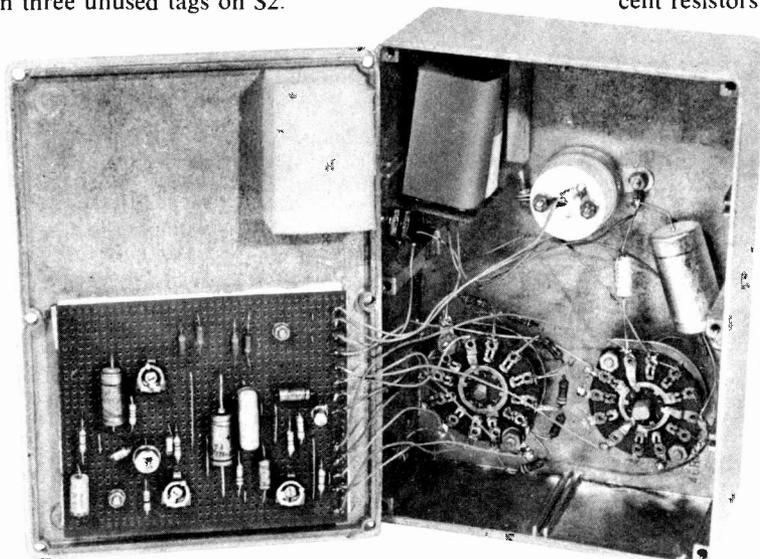The three leads from the probe enter through a hole close to S2 and, for convenience, are terminated on three unused tags on S2.



Photograph of the internal layout of the components within the die-cast box

SETTING UP

After careful checking of the wiring—it is often a good idea to get somebody else to give a final check—move switch S3 to “amplifier”. Monitor the potential at IC1 output, i.e. its connection to C10; it should lie close to +9V.

Next, transfer the meter to TR2 collector (the metal can makes a convenient anchor point for a clip) and adjust VR1 to give a reading of about 10V. This setting of the quiescent voltage at this point has been found to give the best dynamic range, so allowing stable amplification without clipping.

Now provide a signal of suitable frequency (say 400Hz) and amplitude. If no audio generator with accurate output level indication is to hand, then a mains transformer with a secondary of around 10V will suffice (see Fig. 4).

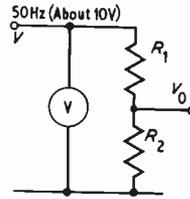


Fig. 4. Set-up for generation of 50Hz test signal

$$V_0 = \frac{R_2}{R_1 + R_2} \times V$$

$$R_1 + R_2 = 10 \text{ to } 15\text{k}\Omega$$

$$V_0 = 300\text{mV or less}$$


Measure the actual voltage available with an a.c. meter of known accuracy, and then arrange resistors to give a voltage of 300mV or slightly less; use resistors of 2 per cent tolerance or better, if possible, and of total value of about 10kΩ to 15kΩ.

Set the millivoltmeter to “300” and “mV”. Inject the test signal and adjust VR2 to give the required meter deflection, i.e. that corresponding to the level decided upon.

Now change the test signal to 1V or slightly less, and, switching the millivoltmeter to “1” and “V”, check the reading. All should be well if R1 and R2 and R8 to R13 are correct.

This method of setting up makes use of an external a.c. meter used on a range where its accuracy can be expected to be at its best. Subsequently, the millivoltmeter will be able to read 1mV f.s.d. with the same accuracy, provided that 2 per cent resistors have been used where suggested.

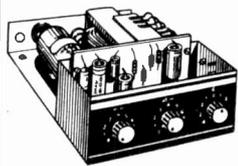
PRICES INCLUDE VAT SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 3 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. A.C. 200/250V.

PRICE £11.60 P. & P. 40p.

DE LUXE STEREO AMPLIFIER

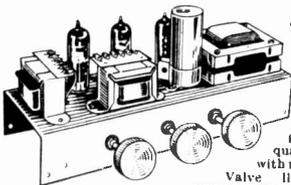

A.C. mains 200-240 volts. Using heavy duty fully insulated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:-2x

6CL8L Triode Pentodes. ECL82. Fitted with 1x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit. Allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. x 4in. x 5in. Overall height including valves 5in. Ready built and tested to a high standard. **Price £9.90**, P. & P. 60p.

NEW! POWER SUPPLY UNIT

200/240V A.C. Input. Four switched fully smoothed D.C. outputs giving 6V and 7.5V and 9V and 12V at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £5 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2in x 3in approx. 28p pair. P. & P. 6p.

HIGH GRADE COPPER LAMINATE BOARDS. 8" x 6", 5 for 55p. P. & P. 25p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V. Half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V at 2 amp full wave. Size 3inL x 3 1/2inW x 3inD. Price £2.31, P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V Sec. 0-9 at 500mA. £1.10 P. & P. 25p. Pri. 200/240V Sec. 12-0-12 at 1 amp. £1.21 P. & P. 25p. Pri. 200/240V Sec. 10-0-10 at 2 amp. £1.82 P. & P. 35p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or on H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/2 in. Brand new — complete with instructions. Price £1. P. & P. 16p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS. Covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed. Diode Equivalents 80p. Transistor Equivalents 90p. Transistor Characteristics £1.20. All three together £2.60 POST FREE

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistor equivalents. ONLY 40p. Post 5p. * pole 3 way 2 bank low loss Yaxley type switches 14" sections. Standard spindle. 2 switches 66p + 10p P. & P. **NEW ISSUE**—Thyristor, Triac, Diac, etc. encyclopedias 95p Fmt Free.

Open 9-5.30 Mon. to Fri.
9-5 Sat. Early closing Wed.

A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W. 19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

CENTRE ZERO MINIMATURE MOVING COIL METER. 100µA for balance or tuning. Approx. size 1in x 1in $\frac{1}{2}$ in. Limited number 88p. P. & P. 12p.

RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **LATEST B.S.R. C100/C129 AUTOCHANGER UNITS.** With latest stereo/mono compatible cartridge £7.60 plus 50p P. & P. **Garrard SP25 Mk. III** with heavy precision machined die cast turntable. £10.58. Carr. 55p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, S100, SP25 II and III, SL66B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in x 14 1/2in x 3 1/2in high (approx. 7 1/2in high, including rigid smoked acrylic cover). P. & P. 70p. **Now only £4.95**

LATEST ACOS GP91/150 Mono Compatible Cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50, P. & P. 15p.

SONOTONE STAC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.30. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.90. P. & P. 15p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1.63. P. & P. 15p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment £1.50. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6 h. Ready built and tested. **PRICE £4.40**. P. & P. 50p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £5.85**. P. & P. 60p.

SPECIAL OFFER!! HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tegan-Vynair front. Size 16in high x 10 1/2in wide x 6in deep. Fitted with E.M.I. Ceramic Magnet 13in in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9.25 Carr. 75p.

CABINET AVAIL. SEPARATELY £4.95. Carr. 65p. Also available in 8 ohm with EM1 13in x 8in. bass speaker with parasitic tweeter. £7.15. Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE £3.30 P. & P. 40p

LOUDSPEAKER BARGAINS

5in 3 ohm £1.05, P. & P. 15p. 7 x 4in 3 ohm £1.15, P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1.82, P. & P. 20p. E.M.I. 13 1/2 x 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm £3.50, P. & P. 30p. E.M.I. 13 x 8in. 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.85, P. & P. 30p. **EMI CERAMIC MAGNET HEAVY DUTY TWEETER.** Approx. 3in. Av. 3 or 8 or 15 ohms. £1.25 plus 20p P. & P. **BRAND NEW.** 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiFi ceramic ferrobar magnet assembly £7.50. Guitar models: 25w £7.00, 35w £9.35. P. & P. 45p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2.70. P. & P. 35p.

Also available specification as above but size 10" x 6" £2.70 and size 8" round £2.60 P. & P. 35p.

LIMITED NUMBER EM1 2 1/2" 8 ohm Tweeters. Mounted on flat bracket, size 2 1/2" wide x 7 1/2" long. 70p per pair plus 15p P. & P. Exe equipment but new and tested. 70p per pair plus 15p P. & P.


12in "RA" TWIN CONE LOUSPEAKER 10 watts peak handling, 3 or 15 ohm. £2.45 P. & P. 35p. **35 ohm SPEAKERS 3".** ONLY 70p. P. & P. 25p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER Size 1 1/2in x 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6.55 each. P. & P. 34p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 1/4 jack plug. Frequency response 30-16,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £3.30**, P. & P. 25p.

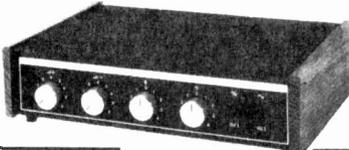HAVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION


A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon. Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 16 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. 5 channels into 5 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 16 Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35W at 10 amp. Overall size—12" wide x 8" deep x 2 1/2" high.

Fully detailed 7-page construction manual and parts list free with kit or send 15p plus large S.A.E. **PRICES** AMPLIFIER KIT, £11.55 P. & P. 25p. (Magnetic input components 33p extra) POWER PACK KIT, £3.30 P. & P. 35p. CABINET, £3.30 P. & P. 35p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £23-10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Diatoneque use, etc.

3-VALVE AUDIO AMP. HA34 MK II

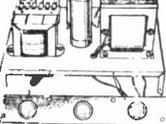


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker.

Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.50. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

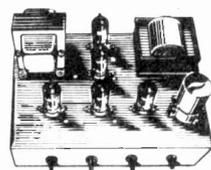A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.



Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF85 and E280 rectifier. Simple instruction booklet 15p plus S.A.E. (Free with parts). All parts sold separately. ONLY £2.80. P. & P. 60p. Also available ready built and tested £12-10. P. & P. 70p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £39 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

WINDSCREEN WIPER DELAY KIT

Complete kit of parts including drilled and tinned fibreglass printed circuit board.

The unit provides intermittent wiper operations with a delay up to approximately 60 seconds which can be varied to optimise visibility in conditions of light rain, spray, etc. The original wiper switch overrides when normal operation is required.

£3.60 including V.A.T. & P. & P. Cash with order.

Additional relay available for foreign cars £1.10 including V.A.T.

ESSEX X-RAY CO. LTD.

57 THEYDON PARK ROAD, THEYDON BOIS
EPPING, ESSEX CM16 7LR

ELECTRONIC DETECTOR for GAS & SMOKE

COMPLETE MAINS OPERATED parts kit & flush or surface mounting box £8.45 P&P 20p. parts available separately;


TGS 105 sensor £1.80 P&P 10p.

Transformer £1.50 P&P 20p.

PCB and circuit diagram £0.55 P&P 10p.

PLEASE ADD 10% VAT TO THE ABOVE

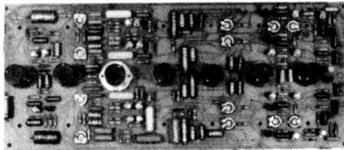ELECTROMECH Ltd, Ruckinge, Ashford, Kent TN26 2EF



AURORA

Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCR's), Rs, Cs, Pots, Cores—8 ch. £17.50; 4 ch. £9.95. Reg. PSU £3.65. PCB—4 ch. control (4 1/2in x 10 1/2in) Mk. 2—also holds rotary or slider pots £2.20. PCB (4 1/2in x 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCR's, £1.10. SCR's—1A, 50p.

A. F. SIGNAL GENERATOR

(PE Nov. 72). S/c's, Rs, Cs, Pots, Sw's, PCB (2 1/2in x 4in) also holds Sw's, £3.15. White stocks last.

LOUD-HAILER AND SIREN

(Pre-amp and Siren Generator) (PW Dec. 72). S/c's, Rs, Cs, Pot, PCB (2 1/2in x 2 1/2in). £2.20 (White stocks last). Main Amp Module PC5+ obtainable to special order. £6.25.

GEMINI STEREO AMPLIFIER

(PE Nov. 70/Mar. 71) Stereo Sets & PCB's. Pre-amp—S/c's. £1.80. Rs, Cs, Pots, Maka-Sw's—with 1W MO Rs, £10.90—with 1/2W or 1/4W CF Rs, £8.90. PCB (3 1/2in x 10 1/2in) for sets with MO and 1/2W Rs, also holds rotary or slider pots and Maka-Sw's. £1.90. Main Amp—Rs, Cs, Pots, £5.20. PCB (3 1/2in x 5in), £1.15. PSU—Rs, Cs, Pot, £3.70. PCB (2in x 4in), 65p.

GEMINI STEREO TUNER

(PE Apr./Jun. 72). PCB as publ., £1.50.

MICROPHONE MIXER

(PE Apr. 69). S/c's, Rs, Cs, Pots, PCB (3 1/2in x 4 1/2in) also holds 6 rotary or 4 slider pots, £3.70.

LOGICAL RADIO CONTROL AND MODEL SERVO CONTROL
(PE Feb./Jun. 72)—Still some PCB's left.

BIOLOGICAL AMPLIFIER

(PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1 1/2in x 3 1/2in), £3.20. O/P Stages (S/c's, Rs, Cs, Pots and Sw's as req'd.). Alphaphone 53p. Cardiophone 66p. Freq. Meter £1.60. Vis-Feedback 55p. Audio Amp PC7 avail. to order £5.20.


ELECTRONIC PIANO

(PE Sep. 72/Jan. 73). Details in lists.

8 WATT AMPLIFIER

(PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, £2.50. Stereo, £5.20. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots and Sw, £1.50. Main Amp—S/c's, Rs, Cs, Pot—Mono, £3.65; Stereo, £7.30. PCB (2 1/2in x 3in) Mono, 60p.

PHONOSONICS PCB'S AND KITS AT LOW PRICES

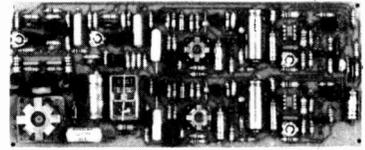

HI-FI TAPE LINK

(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, £11.80; Stereo, £18.70. PSU, £3.58. PCB—Main Circuit (3 1/2in x 9in) (Stereo) also £3.58. PCB—Sub-Assembly. (2 1/2in x 6 1/2in) (Stereo) Mk. 2 holds relay and cores, £1.85. PCB—Sub-Assembly and mounts on Sw's, 80p.

REVERBERATION UNIT

(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, £6.80. PCB (2in x 1 1/2in) also holds sliders, £1.20. 9in Spring Unit, £3.75.

VIBRASONIC GUITAR

(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, £6.65. PSU, £3.32. PCB (3 1/2in x 10 1/2in) Mk. 2, also holds 7 rotary or slider pots, £1.75.

ULTRASONIC TRANSMITTER-RECEIVER

(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in x 5 1/2in), £3.90. T/ducers excluded.

ALSO

PCBs as published (white stocks last) for:

DIGITAL PSU (PE Aug. 72), 50p
OSCILLOSCOPE P/A (PE Aug. 72), 33p
SCORPIO (PE Nov./Dec. 71), 60p
TRIFFID (PE Feb. 73), 60p

AND

DIGITRONIC (PW Mar. 73). Read-out PCB (1 1/2in x 3 1/2in), 60p.

SEMICONDUCTORS

AC128	20p	ZTX107	9p
AC176	20p	ZTX503	14p
AD161	40p	ZTX531	22p
BD107	9p	2N697	18p
BC108	9p	2N706	13p
BC109	9p	2N114	22p
BC147	11p	2N1304	20p
BC148	11p	2N1711	18p
BC149	11p	2N2219	25p
BC157	12p	2N2905	23p
BC158	12p	2N2907	22p
BC159	12p	2N3702	10p
BC182L	11p	2N3703	10p
BC204	14p	2N3704	10p
BC209c	14p	2N3819	27p
BC212L	13p	2N3823E	31p
BC214L	13p	2N5777	40p
BCY71	22p	IN914	4p
BFY50	20p	IN4001	6p
BSY95A	12p	IN4002	7p
MJE2955	165p	IN4004	8p
MJE3055	83p	IN4005	10p
OC28	45p	BA145	17p
OC71	12p	OA91	7p
OC84	24p	OA200	7p
ORP12	48p	Z11	50p
TIS43	24p		

CAPACITORS

ELECTROLYTIC		(µF/V)		TANTALUM BEAD		(µF/V)		POLYESTER C280AE		250V(µF)	
1.0/63	6p	220/10	6p	0.1/35	12p	0.01	3p	0.01	3p	0.015	3p
2.2/63	18p	220/25	10p	0.22/25	12p	0.015	3p	0.022	3p	0.022	3p
4.7/63	6p	220/40	12p	0.47/35	12p	0.033	3p	0.033	3p	0.033	3p
10/63	6p	220/50	10p	1.0/35	12p	0.047	3p	0.047	3p	0.047	3p
15/40	6p	220/63	18p	1.5/35	12p	0.068	3p	0.068	3p	0.068	3p
22/10	6p	220/75	12p	2.2/35	12p	0.1	3p	0.1	3p	0.1	3p
22/25	6p	220/100	10p	4.7/35	12p	0.15	3p	0.15	3p	0.15	3p
33/6.3	6p	220/125	10p	10/25	16p	0.22	3p	0.22	3p	0.22	3p
33/16	6p	220/150	10p	15/16.3	16p	0.33	3p	0.33	3p	0.33	3p
33/40	6p	220/175	10p	22/16	16p	0.47	3p	0.47	3p	0.47	3p
47/6.3	6p	220/200	10p	47/6.3	16p	0.68	3p	0.68	3p	0.68	3p
47/25	6p	220/225	10p	100/10	12p	1.0	3p	1.0	3p	1.0	3p
47/40	6p	220/250	10p	100/25	20p						
47/63	6p	220/300	10p	100/40	40p						
100/10	6p	220/350	10p	100/63	60p						
100/25	6p	220/400	10p	100/100	130p						
100/40	6p	220/450	10p	3300/63	130p						
100/63	6p	220/500	10p	3300/100	320p						
150/16	6p	220/550	10p	4700/16	60p						
150/33	6p	220/600	10p	4700/25	75p						
150/63	12p	220/630	10p	4700/40	93p						

SWITCHES

Makaswitch:	Shaft assembly	48p
	Wafers	33p
	Screens (per pk of 5)	12p
	Spacers (per pk of 10)	8p
	Rotary:	
	3P4W	28p
	Multipole Lever:	
	4CL/4CL	£1.30
	4CL/4CN	£1.30
	Knobs	6p
	Slide	9p
	DPDT	12p
	RELAYS	
	2PCO 12V	£1
	4PCO 12V	£1.30
	Relay base & Relay	20p
	Reed	Relay 85p
	6.9V	

SOUND SYNTHESISER (PE 1973)

Details of PCB's & Components in lists.

RONDO (PE current series)

PHASING UNIT (PE Sept. 73)

ENLARGER EXPOSURE METER AND THERMOMETER (PE SEPT. 73)

SEMICONDUCTOR TESTER (PE OCT. 73)

WIND AND RAIN EFFECTS (PE OCT. 73)

PROJECT Q4 (PW Quadrasonic System 1973)

DETAILS IN LISTS

VAT
ADD 10%


P. & P.
10p

S.A.E.
FOR
FREE LIST

GENERAL
All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published". PCBs are designed by Phonosonics. Pots are rotary unless stated as slider. Prices and deliveries of individual components subject to stock availability. Export: P. & P. extra, VAT: non-applicable.

PHONOSONICS, DEPT. PE22, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW

MAIL ORDER ONLY

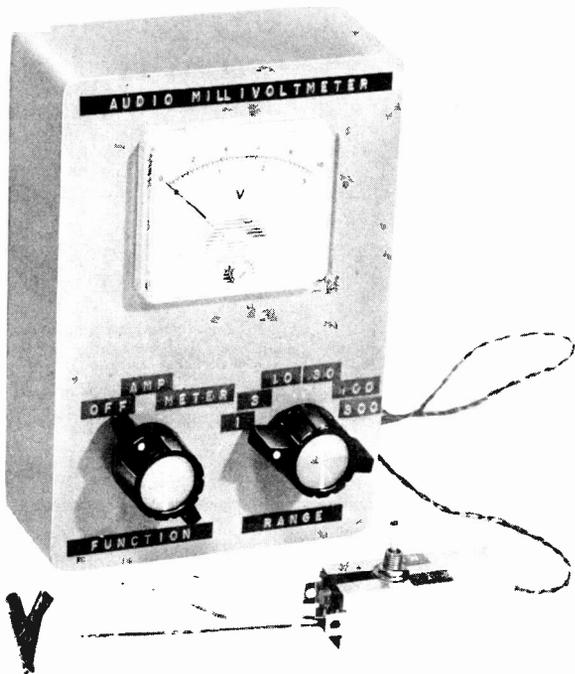

Photograph of the completed Audio Millivoltmeter showing disposition of controls on the front panel

ADJUSTMENT OF PROBE CAPACITOR

Adjustment of C1 comes next. Inject a 400Hz signal with the instrument on the 300mV range, and set the input level for full scale deflection on the meter. Switch to the 1V range; the meter should indicate 0.3 of f.s.d.

Now repeat with a signal in the range 20kHz to 50kHz. If C1 has the correct value, identical results will be obtained; if C1 is too small, then, on the 1V range the meter will read low.

As a guide, the author used a value of 6.7pF, obtained by means of a series combination of 10pF and a 22pF polystyrene capacitors.

The setting of VR3 can be done to suit individual requirements; in the author's instrument it was found convenient to have 0.5V r.m.s. output available, on the "amplifier" position of S3 when meter f.s.d. was indicated on the "meter" position.

THE INSTRUMENT IN USE

In use, put S3 to the "amplifier" position for a few seconds before switching to "meter", so that the large value electrolytic capacitors employed in various positions can charge up to their working voltages without causing damage to the meter movement.

Remember that C3 has a working voltage of 250V; should the millivoltmeter be used to measure the hum level on the h.t. line of a valve amplifier for example, then a suitable capacitor must be connected in series with the input to the probe. A 1μF 500V component should suffice.

Probe construction is such that the instrument should not really be used to measure a.c. voltages of greater than 100V (see specification), although the controls can be set to "300" and "V". An ordinary moving coil meter plus rectifiers combination (as

used in most multi-purpose testers) would be more appropriate for voltages of that level and above, the millivoltmeter being intended for use at much lower levels.

FREQUENCY RESPONSE CURVES

One typical application of the millivoltmeter is in the plotting of the response curves of audio amplifiers, and utilises the set-up shown in Fig. 5. The millivoltmeter is used firstly to check that as the audio generator output frequency is varied, its output level remains constant. If this is not so (and few audio generators have an output level that is constant in that way) then the level should be re-adjusted at each frequency as it is brought into use. With the millivoltmeter then placed across the amplifier output, the level of voltage present there is easily read. In this way a frequency response curve can be plotted.

The term "amplifier" can, of course, be any power amplifier or pre-amplifier and further curves can be plotted for different settings of the tone controls, etc.

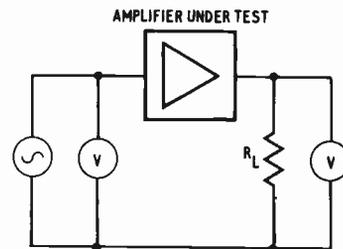


Fig. 5. A typical set up for using the Audio Millivoltmeter to measure frequency response curves of audio amplifiers or overload points

The load resistor RL must be included to simulate the actual load for the amplifier under test, although naturally it can be the load normally employed, e.g. a loudspeaker.

As a safety measure, it is a good rule to always set the audio millivoltmeter to a higher range than that expected. For example, if a level of 1V is thought to be present, set the instrument to the 10V range, subsequently reducing the setting when the actual level is confirmed.

This simple precaution (which applies to the use of all test instruments) will vastly reduce the chance of damage to expensive moving coil meters.

AMPLIFIER OVERLOAD

A further use for the audio millivoltmeter is in determining the overload point of an amplifier. This can be done with the set up of Fig. 5, as follows.

Increase the input to the amplifier in convenient steps, say by a doubling of the level from the audio oscillator, while monitoring the output of the test amplifier. The millivoltmeter will need to be changed from amplifier input to amplifier output alternately to do this. Eventually, an increase in input voltage will not be matched by a corresponding increase in output voltage, and this is the point at which overload begins at the frequency in use.

A plot of output against input voltage will readily enable the exact point of overload to be found. ★

Readout—

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Quad-wrangle

Sir—Regarding Mr. Wadsworth's letter (*Viewpoint*, December 1973) when he questions whether or not quadrasonic sound is a "con": of course it's a con! So for that matter is recorded music. But we seem to have adapted to eating food out of tin cans and deep freeze packets, why not listening to orchestral music out of loudspeakers? Only electronic music was designed specifically to be heard through loudspeakers.

On that basis, one might as well make one's canned music as palatable as possible and quadrasonic reproduction definitely enhances such music to no small degree. On the face of it, quadrasonics may seem an expensive luxury, but thanks to P.E. Rondo, this is not the case. The four 20W amplifiers, pre-amplifiers, SQ decoder, power supply unit, and all hardware have been built for just on £50. Could the system be obtained off-the-peg for this price? I doubt it.

Having now got the basic system operational, I can confirm the quality to be of a very high standard for the price.

So I've been conned and am thoroughly enjoying it: in this quarter quadrasonic sound has definitely caught on.

One plea, however: Two good "music system" projects in one year (P.E. Synthesiser and now P.E. Rondo) have proved expensive in total. Could you keep your hands off that super-con Octasonic for at least another year, please?

I. Stuart-Colwill,
London, S.W.16.

More lifelike

Sir—I read with interest E. Wadsworth's letter in P.E. November 1973, and I must disagree with what he says.

The whole point of a hi-fi system, be it mono, stereo or quadrasonic is that it tries to reproduce as faithfully as possible the sounds one would hear in a concert hall. As Mr. Wadsworth points out, a musical group has a definite width, and to members of the audience, different sounds will appear to come

from different directions. The great advantage of polyphonic as opposed to monophonic systems is that they reproduce, as far as is possible within the limits of the listening area, this effect can add therefore, to the realism of the music. How lifeless some music feels when it appears to come from only one source.

Stereo and quadrasonic systems are surely not a "con" therefore. They make the music sound more lifelike, and this is what hi-fi is all about.

I disagree with Mr. Wadsworth's comparison of colour television with amateur slides. I suggest he looks at a correctly adjusted television, which, as he will find, is capable of giving quality equal to the very best 35mm slides.

I would query on what authority Mr. Wadsworth makes such a brash statement. Also, he seems to be equating "amateur" with "incompetent" which is not true by any means, as the large number of excellent articles in P.E. proves.

M. Norton,
Hailsham.

You are not alone

Sir—In reply to Mr. E. Wadsworth of Huddersfield:—You are not alone. You are simply one of the 90 per cent of the population who does not appreciate good music correctly presented, and you have not got a colour T.V. or, if you have, dump it and get a good Japanese one and get someone who knows the job to set it up for you.

I reckon you will be just about line of sight to Holme Moss and Emley Moor transmitters so you have no excuse for poor reception.

You appear to believe that stereo just gives a wider sound picture. That can be achieved by putting a mono sound source into two loudspeakers set well apart but it won't be stereo. Correct stereo reproduction will bring the orchestra or artists, or whatever the sound source is, into your living room so you can close your eyes and feel the presentation is live.

Each artist or instrument will sound to left or right, or some place between just as they were

positioned at the time. That is no "con" trick. It actually takes place.

I've never thought the industry pushed stereo at all, it sells itself to those who know what sounds right. I think we are lucky that stereo and the transistor grew up together so we are able to have good quality sound at good power from the compact equipment at a reasonable price.

I should think that your group of musicians stood close together in order to get each one's sound into the single microphone which was practice before stereo, whereas now each artist has his own microphone. You have admitted that "a group of musicians constitutes a certain size" and that size is much larger than a single loudspeaker.

Concerning "quad." I am sure this adds even more realism to stereo, but I feel this requires a good sized room to be really effective but it is a step forward.

You must have listened to some rubbish stereo set-ups and watched some delapidated colour T.V.'s.

If you still think it's a con trick—come over and look and listen. My set-up didn't cost the earth and I'm not rich, but I use my eyes and ears. I've not been conned.

C. A. King,
Nr. Sheffield.

Good advert

Sir—I would like to commend (through your columns) the following advertisers for prompt and efficient postal service:

R.T.V.C. (Acton) Ltd.,
Unisound amplifier—6 days.

Henry's Radio Ltd.,
Sinclair amplifier—5 days.

Radio Component Specialists
(Croydon),

B.S.R. Autocharger—5 days.

All include day of posting, which is excellent service and also proves that our postal system is not always as bad as it is often claimed.

D. L. Baxter,
Newbury.

AN INVITATION

UNIVERSITY OF ESSEX


A lecture **THE P.E. SOUND SYNTHESISER** will be given by **Douglas Shaw** on **Wednesday, January 23, 1974, at 7 p.m.** Readers in the Colchester area who would like to attend will be most welcome. Write to **P. Noakes, Department of Electrical Engineering Science, University of Essex, Colchester.**

NOW AVAILABLE IN THE U.K!

CHINAGLIA



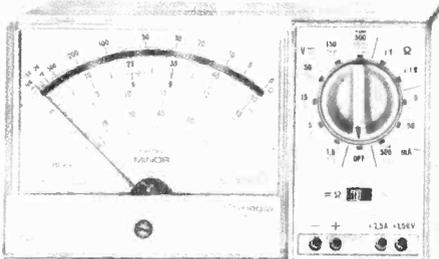ONE OF ITALY'S LEADING TEST EQUIPMENT MAKERS
PRESENT THE CORTINA MINOR



One of a range of professional quality instruments now available to U.K. users

● SENSITIVITY 20,000 Ω/VOLT (D.C.), 4,000 Ω/VOLT (A.C.) ● ROBUST DIODE PROTECTED PRECISION MOVEMENT ● 33 RANGES D.C. VOLTS 0-100mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1,500V D.C. CURRENT 0-50μA, 5mA, 50mA, 500mA, 2.5A. A.C. VOLTS, 0-7.5V, 25V, 75V, 250V, 750V, 1,500V. A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A. F.S.D. CAPACITANCE RANGES 100μF, 1F, 10F. A.C. VOLTAGE AND CURRENT 3.5% ● OHMS RANGES POWERED BY INTERNAL BATTERIES ● COMPACT SIZE: 150 x 85 x 40mm 350gr ● CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR ● PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT ● FULLY GUARANTEED FOR 12 MONTHS ● AFTER SALES SERVICE AND SPARES FACILITIES ● SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET ● SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.
PRICE £13 (p & p 80p) PROBE £7-50 inc. of VAT

For full details of the Chinaglia range contact:

CHINAGLIA (U.K.) LTD.

19 MULBERRY WALK, LONDON, S.W.3 Tel. 01-352 1897

ELECTRONIC AND AUDIO BARGAINS

HILLS HEADPHONE JUNCTION BOX MODEL JB3

For connecting headphones to amplifiers
OUR PRICE £1.37



CAR STEREO SPEAKERS MODEL CRB200

Designed for door and shelf mounting 5 watts
OUR PRICE £3.85
P/P 27p



VYNIAR SPEAKER CLOTH

Black or Black and Silver
SIZES 18in. x 25in £1.10
36in x 25in £1.10
36in x 50in £2.20

Send 10p stamp for our samples of Vyniar and Audio Components Catalogue.

SOLDERING IRONS

CCN240 15 Watt £1.76
X25 25 Watts £1.54
Replacement Elements £1.06
Replacement Bits 33p
ST3 Stand 88p

SWITCHES

Small Slide Switch 10p
Large Slide Switch 10p
SPST Toggle Switch 16p
DPDT Toggle Switch 20p
Small (Biased) Push to Test Switch 10p

VEROBOARD

	Plain	
	0.1	0.15
2.5in x 3.75in.	19p	16p
2.5in x 5in	23p	22p
3.75in x 3.75in.	24p	22p
3.75in x 5in	26p	26p
Spot Face Cutter	39p	39p
Pin Insertion Tool	50p	50p

HILLS DYNAMIC HEADPHONES MODEL H707VS DE LUXE

Extremely high quality with padded Headband & Earcups & Slider Volume Controls.
OUR PRICE £6.30
P/P 27p



HONNER INTERCOM

2 Station inc. Volume Control On-Off Switch Batteries & 60ft of Cable
OUR PRICE £3.50



CARTRIDGES

Acos GP91-3SC Mono Crystal Compatible 85p
GP93-1 Stereo Crystal £1.15
GP95-1 Stereo Ceramic £1.65
Sonotone 9TAMC Diam. £1.80

SPEAKER

6 x 4 Std. Magnet 8Ω £1.10
7 x 4 Std. Magnet 3Ω £1.10
8 x 5 Std. Magnet 8Ω & 3Ω £1.26

ALUMINIUM BOXES

HA1	5 1/2" x 2 1/2" x 1 1/2"	42p
HA2	4" x 4" x 1 1/2"	41p
HA3	4" x 2 1/2" x 1 1/2"	41p
HA4	5 1/2" x 4" x 1 1/2"	47p
HA5	4" x 2 1/2" x 2"	41p
HA6	3" x 2" x 1"	34p
HA7	7" x 5" x 2 1/2"	66p
HA8	8" x 6" x 3"	84p
HA9	6" x 4" x 2"	54p

CASSETTE TAPE RECORDER DYNAMIC MICROPHONE

with Remote Control On-Off Switch.
OUR PRICE £1.40

TELEPHONE PICKUP COIL

for Amplifiers or Tape Recorders
OUR PRICE 35p

VISIT OUR TRADE COUNTER

ALL CALLERS WELCOME
MON-SAT 9 a.m. till 5.30 p.m.

HILLS COMPONENTS LTD.

DEPT. (PW-2), UNIT NO. 6, MELINITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 27711

ALL PRICES INCLUDE V.A.T.
Please add 10% for P/P.
Min. Order £1.00

ADCOLA
meet the precision
'INVADER' SOLDERING INSTRUMENTS

Precision instruments supplied with standard detachable copper chisel face bits. Standard temp. 360°C at 19/23/27 watts. Special temps. from 250°C/410°C.

For perfection
in soldering

L1076

BIT SIZE 1/4"
6.34 mm Dia.
27 watts.
£2.48
inc. VAT

L646

BIT SIZE 3/16"
4.75 mm Dia.
23 watts
£2.42
inc. VAT

L706

BIT SIZE 1/8"
3.2 mm Dia.
19 watts
£2.23
inc. VAT



Don't take chances. We don't. All our ADCOLA Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this production tool. ADCOLA day after day.
Send for NEW catalogue today

ADCOLA PRODUCTS LTD., ADCOLA HOUSE, GAUDEN ROAD, LONDON SW4 6LH
Regd. No. 442762 ENGLAND

Please add 10p for postage and packing

Models required
Enclosing P/O or cheque for
Name
Address PE6

Exciting...the Stereo 21!

Can you really get sound quality like this FOR LESS THAN £19? YES, YOU CAN! WITH THE NEW

STEREO 21

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable £18.45, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21

the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . .

everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!

And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for £18.45 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money refund if not

satisfied if your pleasure in STEREO 21 is not complete!


Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Power Output 2.7 watts per channel and headphone socket with automatic cut-out. Provision for auxiliary inputs—radio tape etc. and output for taping discs. Overall dimensions: Speakers approx. 15½ × 8 × 4 in. Complete deck and cover enclose position approx. 15½ × 12 × 6 in.

Personal shoppers and mail order price
£18.45 INCLUDING VAT plus £1.60 p. & p.
 Diamond stylii, if required. £1.37 extra
 Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. £3.85.

EMI SPEAKERS AT UNBELIEVABLE PRICES

950 Kit. Five matched speakers and crossover unit for handling up to 45 watts, from 20 to 20,000 Hz. Huge—19in × 14in (approx.) high efficiency 16, 500-gauss bass unit built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3½in dia. approx., are fed by the crossover with a critically adjusted signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2in others 0.5in. Recommended list price £44.
OUR PRICE £25.00 + £1.50 p. & p.

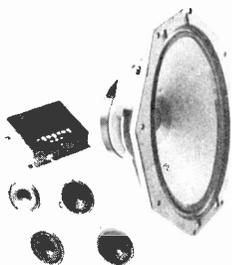

15in 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3in voice coil.
 Recommended retail price £40.80.

OUR PRICE £18.70 + £1.50 p. & p.

Just write your order giving your Credit Card Number. Do not send your card.



RADIO AND TV COMPONENTS (ACTON) LTD. 21D HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2

Edgware: 9 a.m. to 5.30 p.m., half day Thurs.
 Acton: 9.30 a.m. to 5 p.m. Closed all day Wed. also see opposite.
 Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope Goods not despatched outside U.K.



RTVC VISCOUNT III

a boost in the output.

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it . . . we make it . . . we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back. And the teak finish will harmonise and enhance virtually any style of interior decor!

The heart-stopping timbre of Tom Jones at his most virile . . . the last lingering harmonics of a solo performance by Heifetz or Menuhin . . . the pathos and the panache of Liza Minelli . . . the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have *never* experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx 17in x 10in x 6in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair. £2.20 p. & p. Duo Type III Size approx 23in x 11in x 9in. Drive unit 13in x 8in with HF speaker. Max. power 20 watts 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20 - £1 p. & p.
2 Duo Type II speakers	£14.00 + £2.20 p. & p.
Garrard SP25 Mk III with	
MAG cartridge plinth & cover	£18.00 - £1.75 p. & p.
total	£56.20


Available complete for only £49.00 - £3.50 p. & p.

PRICES: SYSTEM 2

Viscount III R 102 amplifier	£24.20 - £1 p. & p.
2 Duo Type III speakers	£32.00 - £3.30 p. & p.
Garrard SP25 Mk III with	
MAG cartridge plinth & cover	£18.00 - £1.75 p. & p.
total	£74.20

Available complete for £65.00 + £4 p. & p.

STILL ONLY **£49** COMPLETE

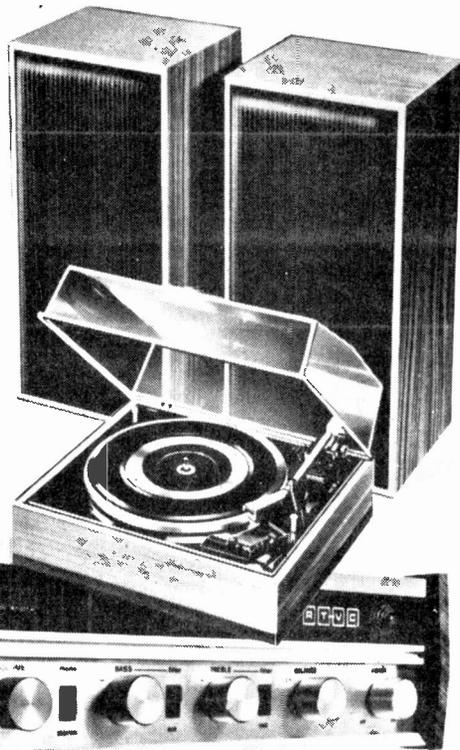

THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles it covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4in deep.


* Circuit diagram and comprehensive instructions 55p free with parts.

* Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. & p. 55p

Speaker with baffle and fixing strips £1.65. 23p p. & p., post free if bought with the kit. Send stamped addressed envelope for leaflet.

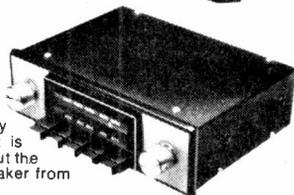If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.



RELIANT Mk IV £13.50 Mono Amplifier

*5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer

employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of


medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx.

12½ x 6 x 3½ ins. £13.50 p. & p. 60p.

UNISOUND MODULES

ONLY £7.64 + 55p p. & p.

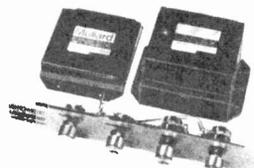For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.




The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit, £10.60 p. & p. 90p. simply connect up.

ALL PRICES INC. VAT


PE TAPE LINK CONSTRUCTORS

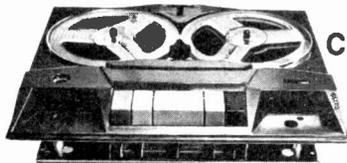Suitable 3 speed tape deck, less heads. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty. £1 p. & p. **£4.00**



SEE OPPOSITE PAGE FOR ADDRESS DETAILS

MM5314 - JUMBO EVALUATION KIT

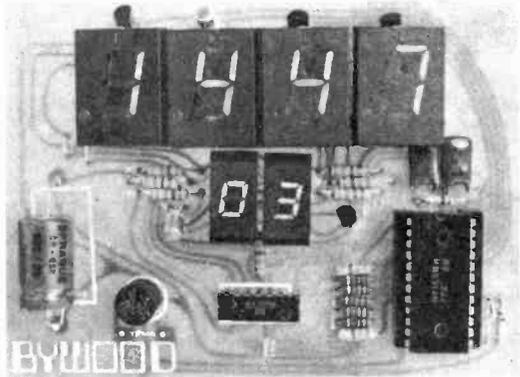

A NEW Digital Clock Kit from BYWOOD!

We supply - MM5314 Digital clock chip and 24 pin socket.
Four DL747 and two DL707 LED displays.
CA3081 driver, 5" x 4" fibreglass PCB.

You supply - 6 transistors, 3 capacitors, 2 diodes, transformer.
16 resistors, 4 way switch.

Kit price £26.80 + VAT. Cases - phone for details.
Alarm chips with liquid-crystal or phosphor-diode display
evaluation kits also available. All chips, displays, PCBs
are available separately. Catalogue 15p.

BYWOOD ELECTRONICS Tel 0442:62757.
181 Ebbens Road, Hemel Hempstead, HP3 9RDB.



MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/
volt High Sensitivity Meter
£12.37.

**TAPE
RECORDER
LEVEL
METER**
500µA, 55p



**CARDIOD
DYNAMIC
MICROPHONE**

Model UD-130. Fre-
quency response 50-
15,000c/s. Impedance
Dual 50K and 600 ohms,
£4.95.



4 1/2 in x 3 1/2 in **METER.** 30µA,
50µA or 100µA, £3.00.

**MULTI-
METER**

Model 200H
20,000 ohm/
volt, £5.28.




**3 WATT STEREO
AMPLIFIER**
£4.30

All above prices include 10% V.A.T. Please add 10p for P & P. on
orders under £5. LARGE S.A.E. for List No. 6. Special prices for
quantity quoted on request.

M. DZIUBAS

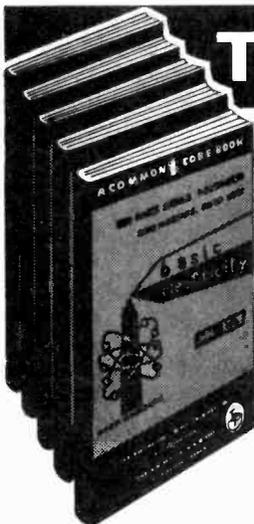158 Bradshawgate • Bolton • Lancs. BL2 1BA



The Pictorial Method

BASIC ELECTRICITY (5 vols) BASIC ELECTRONICS (6 vols) BASIC TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly
successful PICTORIAL METHOD. The essential facts
are explained in the simplest language, one at a time,
and each is illustrated by an accurate cartoon-type
drawing. These clear and concise illustrations make
study a real pleasure. The books are based on the latest
research into simplified learning techniques. This easy-
approach-to-learning method has proved beyond doubt
that acquiring knowledge can be an enjoyable ex-
perience.

The series
will be of ex-
ceptional value in
training mechanics and
technicians in Electricity,
Radio and Electronics.

WHAT READERS SAY

The manuals really open the door. *D.C. Newbury*

You can be assured that I will recommend your
manuals to my friends *P.L. Lowestoft*

These manuals are wonderful value for the prices
asked. *W.G. Bramhall*

I find the manuals most enlightening and I am very
grateful. *A.C. Stratford*

By far the easiest and simplest manuals I have ever
studied. *L.S. High Wycombe*

**YOUR
100%
GUARANTEE**

Should you be, in
any way dissatis-
fied with the
MANUALS your
money will be re-
funded by return
of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES,
BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £5.30

BASIC ELECTRONICS 6 parts £6.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to
return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS

FULL POSTAL.....

ADDRESS

POST NOW FOR THIS OFFER!

Marshall's

A. Marshall & Son (London) Limited
42 Cricklewood Broadway London NW2 3HD Telephone 01-452 0161
& 65 Bath Street Glasgow G2 2BX Telephone 041-332 4133

months best buy^{ex-stock}
All British made 'Calcatec' calculator
One of the first electronic calculators in the world
with no mechanical switches or moving parts. Touch
button operation using latest MOS integrated
circuitry. Complete with charger and case. 1 year
guarantee. 140mm x 80mm.
Our price £29.00 excluding VAT
Recommended price £42.50 P&P 30pence UK

Transistors

20301	0-15	2N3392	0-18	3N187	1-55	ASY29	0-38	BCY72	0-13	BFY11	0-45
20302	0-15	2N3393	0-18	3N200	2-49	ASY50	0-20	BCY87	3-54	BFY17	0-90
20303	0-25	2N3394	0-18	3N201	1-12	ASY55	0-16	BCY88	2-42	BFY18	0-35
20306	0-40	2N3402	0-18	40020	0-78	BC107	0-16	BCY89	0-97	BFY19	0-35
20309	0-30	2N3403	0-18	40231	0-81	BC108	0-15	BCZ10	0-59	BFY20	0-50
20345B	0-25	2N3404	0-24	40309	0-80	BC109	0-18	BCZ11	0-59	BFY21	0-40
20371	0-15	2N3406	0-27	40310	0-50	BC113	0-13	BD115	0-75	BFY37	0-20
20374	0-15	2N3414	0-10	40313	0-82	BC114	0-12	BD116	0-75	BFY41	0-43
2N174	1-40	2N3415	0-10	40316	0-50	BC115	0-15	BD121	0-75	BFY43	0-65
2N404	0-40	2N3416	0-16	40318	0-82	BC116	0-16	BD123	0-82	BFY60	0-22
2N450	0-75	2N3417	0-21	40360	0-46	BC116A	0-18	BD124	0-67	BFY61	0-18
2N456A	0-75	2N3370	1-25	40376	0-50	BC117	0-21	BD132	0-50	BFY62	0-20
2N467A	0-25	2N3571	1-12	40382	0-60	BC119	0-29	BD135	0-43	BFY63	0-16
2N491	3-58	2N3572	0-97	40383	0-61	BC121	0-23	BD136	0-49	BFY64	0-41
2N696	0-15	2N3702	0-11	40389	0-56	BC125	0-15	BD137	0-55	BFY76	0-40
2N697	0-15	2N3703	0-12	40394	0-56	BC126	0-20	BD138	0-63	BFY76	0-22
2N698	0-25	2N3704	0-14	40395	0-56	BC126	0-20	BD139	0-71	BFY77	0-24
2N699	0-29	2N3705	0-12	40400	0-44	BC132	0-30	BD140	0-87	BFY78	0-36
2N706	0-18	2N3707	0-13	40408	0-48	BC134	0-11	BD141	1-26	BFY90	0-80
2N708	0-14	2N3708	0-70	40409	0-52	BC136	0-15	BDY11	1-50	BFY93	0-20
2N709	0-38	2N3709	0-11	40410	0-52	BC137	0-15	BDY17	1-50	B8X19	0-13
2N711	0-30	2N3710	0-12	40411	2-25	BC138	0-24	BDY18	1-75	B8X20	0-20
2N718	0-29	2N3711	0-11	40414	3-55	BC140	0-39	BDY19	1-97	B8X21	0-20
2N718A	0-49	2N3712	0-96	40467	0-69	BC141	0-29	BDY20	1-05	B8X26	0-49
2N720	0-59	2N3713	1-20	40468A	0-40	BC142	0-23	BDY38	0-85	B8X27	0-34
2N721	0-25	2N3714	1-28	40469	0-30	BC143	0-12	BDY60	0-69	B8X28	0-25
2N914	0-22	2N3715	1-50	40601	0-67	BC144	0-24	BDY61	1-25	B8X29	0-20
2N916	0-41	2N3716	1-80	40602	0-46	BC145	0-21	BDY62	1-00	B8X60	0-54
2N918	0-47	2N3773	2-65	40603	0-58	BC147	0-12	BF115	0-25	B8X61	0-42
2N929	0-30	2N3779	3-15	40604	0-56	BC148	0-13	BF116	0-23	B8X76	0-15
2N930	0-48	2N3790	2-40	40636	1-10	BC149	0-12	BF117	0-43	B8X77	0-20
2N1090	0-30	2N3791	2-55	40673	0-70	BC153	0-18	BF119	0-58	B8X78	0-25
2N1091	0-32	2N3792	0-99	40497	0-25	BC154	0-11	BF120	0-27	B8Y70	0-28
2N1132	0-54	2N3794	0-40	AC113	0-18	BC157	0-14	BF123	0-27	B8Y93	0-20
2N1302	0-18	2N3819	0-37	AC117	0-20	BC158	0-13	BF125	0-25	B8Y93	0-20
2N1303	0-18	2N3820	0-38	AC121	0-13	BC159	0-14	BF152	0-20	B8Y26	0-20
2N1304	0-24	2N3823	0-42	AC126	0-25	BC160	0-17	BF153	0-21	B8Y27	0-15
2N1306	0-24	2N3824	0-23	AC127	0-25	BC167B	0-13	BF154	0-16	B8Y28	0-15
2N1306	0-31	2N3826	0-33	AC128	0-25	BC168B	0-13	BF158	0-23	B8Y38	0-19
2N1307	0-22	2N3825	0-49	AC141K	0-30	BC168C	0-12	BF159	0-20	B8Y39	0-19
2N1308	0-25	2N3834A	0-18	AC142K	0-15	BC169	0-13	BF160	0-23	B8Y40	0-19
2N1309	0-35	2N3850	0-19	AC151V	0-24	BC169C	0-13	BF161	0-41	B8Y52	0-25
2N1483	0-90	2N3850A	0-20	AC162V	0-17	BC170	0-11	BF163	0-31	B8Y53	0-25
2N1507	0-30	2N3856	0-19	AC153	0-25	BC171	0-13	BF166	0-31	B8Y54	0-30
2N1512	0-33	2N3856A	0-20	AC153K	0-25	BC172	0-11	BF167	0-21	B8Y56	0-79
2N1631	0-38	2N3858	0-16	AC154	0-20	BC182	0-12	BF173	0-21	B8Y65	0-16
2N1637	0-38	2N3859	0-19	AC176	0-19	BC182L	0-12	BF174	0-29	B8Y76	0-40
2N1638	0-32	2N3859	0-14	AC176K	0-25	BC182L	0-09	BF178	0-35	B8Y79	0-40
2N1701	1-19	2N3859A	0-19	AC187K	0-28	BC183	0-09	BF179	0-43	B8Y90	0-45
2N1702	2-15	2N3860	0-19	AC188K	0-34	BC184	0-11	BF180	0-35	B8Y95A	0-10
2N1711	0-45	2N3866	1-09	ACY17	0-35	BC184L	0-11	BF181	0-34	BU104	1-42
2N1853	0-81	2N3877	0-25	ACY18	0-24	BC186	0-25	BF182	0-40	BU105	2-26
2N1924	0-30	2N3877A	0-28	ACY19	0-27	BC187	0-27	BF183	0-40	CU111	0-53
2N2147	0-70	2N3902	0-29	ACY20	0-22	BC207	0-19	BF184	0-17	DA028	0-55
2N2148	0-94	2N3900A	0-21	ACY21	0-26	BC208	0-11	BF185	0-17	GET111	0-45
2N2192	0-40	2N3901	0-32	ACY22	0-12	BC212K	0-10	BF194	0-16	GET113	0-25
2N2192A	0-40	2N3903	0-24	ACY28	0-20	BC212L	0-18	BF195	0-17	GET114	0-20
2N2193	0-40	2N3904	0-27	ACY30	0-42	BC214L	0-21	BF196	0-15	GET115	0-50
2N2193A	0-40	2N3905	0-24	ACY39	0-65	BC237	0-09	BF197	0-15	GET119	0-35
2N2194	0-73	2N3906	0-27	ACY40	0-17	BC238	0-09	BF198	0-16	GET120	0-40
2N2194A	0-61	2N3907	0-28	ACY41	0-17	BC239	0-19	BF199	0-17	GET133	0-20
2N218A	0-68	2N4037	0-42	ACY44	0-31	BC251	0-20	BF200	0-40	GET358	0-20
2N2219	0-57	2N4058	0-16	AD136V	0-98	BC252	0-18	BF244J	0-14	GET358	0-20
2N2219A	0-88	2N4059	0-09	AD142	0-50	BC253	0-23	BF225J	0-19	GET873	0-12
2N2220	0-45	2N4060	0-11	AD143	0-45	BC257	0-09	BF237	0-22	GET875	0-15
2N2221	0-41	2N4061	0-11	AD149V	0-68	BC258	0-09	BF238	0-22	GET880	0-35
2N2221A	0-83	2N4062	0-11	AD160	0-63	BC259	0-13	BF244	0-16	GET883	0-20
2N2222	0-60	2N4063	0-11	AD161	0-45	BC261	0-20	BF245	0-33	GET887	0-20
2N2222A	0-31	2N4303	0-47	AD162	0-45	BC282	0-18	BF246	0-43	GET890	0-25
2N2368	0-31	2N4916	0-11	AD161	Pr.	BC293	0-23	BF247	0-49	GET895	0-25
2N2369	0-37	2N4917	0-17	AD162	1-05	BC300	2-12	BF254	0-16	TI295A	0-49
2N2369A	0-41	2N4918	0-73	AF109R	0-40	BC301	3-34	BF255	0-17	TI295A	0-68
2N2646	0-77	2N4919	0-84	AF111	0-25	BC302	0-29	BF257	0-47	TI295A	0-82
2N2647	1-12	2N4920	0-89	AF115	0-24	BC303	0-54	BF258	0-59	TI295A	0-74
2N2711	0-13	2N4921	0-85	AF118	0-40	BC304	1-15	BF260	0-25	TI295A	0-31
2N2712	0-12	2N4922	0-84	AF117	0-20	BC307A	1-10	BF270	0-21	TI295A	1-61
2N2713	0-17	2N4923	0-83	AF118	0-50	BC308	0-09	BF272	0-53	TI295A	2-90
2N2714	0-18	2N5172	0-12	AF121	0-22	BC308A	0-12	BF273	0-15	TI295A	3-70
2N2904	0-55	2N5174	0-22	AF124	0-24	BC308B	0-09	BF274	0-17	TI295A	0-79
2N2904A	0-70	2N5175	0-28	AF125	0-20	BC309	0-10	BF467	0-55	TI295A	0-80
2N2905	0-71	2N5176	0-32	AF126	0-19	BC309A	0-10	BF468	0-63	TI2955	0-98
2N2905A	0-87	2N5199	0-92	AF127	0-40	BC309	1-15	BF469	0-25	TI295A	0-31
2N2906	0-65	2N5191	0-95	AF139	0-38	BC327	0-21	BF828	0-22	ME400	0-18
2N2906A	0-70	2N5192	1-94	AF170	0-26	BC328	0-19	BF861	0-27	ME402	0-20
2N2907	0-38	2N5195	1-46	AF172	0-25	BC337	0-19	BF898	0-20	ME404	0-18
2N2907A	0-41	2N5245	0-43	AF178	0-55	BC338	0-19	BFW11	0-81	ME411	0-17
2N2925	0-12	2N5437	0-49	AF179	0-65	BCY30	0-43	BFX13	0-23	ME412	0-18
2N2924	0-14	2N5438	0-45	AF180	0-50	BCY31	0-51	BFX29	0-30	ME413	0-14
2N2925	0-17	2N5439	0-42	AF182	0-40	BCY32	1-15	BFX30	0-25	ME414	0-25
2N2926	0-13	2N5440	0-42	AF183	0-35	BCY33	0-31	BFX37	0-33	ME401	0-09
Green	0-12	3N138	1-65	AF239	0-55	BCY34	0-36	BFX44	0-33	ME4002	0-11
Yellow	0-11	3N139	1-42	AF240	0-72	BCY38	0-52	BFX63	0-28	ME4003	0-14
Orange	0-13	3N140	0-92	AF279	0-54	BFX39	1-05	BFX68	0-30	ME610	0-10
0-11	3N141	0-81	AF280	0-54	BCY40	0-87	BFX84	0-24	ME4102	0-11	
2N3053	0-32	3N142	0-58	AFY42	0-74	BCY42	0-15	BFX85	0-30	ME4103	0-10
2N3054	0-86	3N143	0-75	AF102	0-75	BCY43	0-15	BFX86	0-28	ME4104	0-11
2N3065	0-75	3N152	0-82	AL103	0-70	BCY58	0-21	BFX87	0-28	ME4101	0-14
2N3390	0-28	3N153	0-81	ASY26	0-30	BCY59	0-22	BFX88	0-25	ME6102	0-18
2N3391	0-28	3N154	0-84	ASY27	0-36	BCY70	0-17	BFX89	0-45	ME8002	0-16
2N3391A	0-29	3N159	1-17	ASY28	0-28	BCY71	0-22	BFY10	0-35	ME8003	0-17

Open
9.30 am - 5.30 pm
Mon to Sat
Return of post
service
Barclaycards
accepted

Litronix LEDs
RL-2 02 03 04 46p
RL54 13p
RL55 42p
RL209 33p
RL4850 31p
DL707 (Alphanumeric) 235

Litronix LEDs
Sesocem
semi-conductors.
Full range of
Cosmos
Capacitors -
Siemens Nitsuko
Ducati

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT PE, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

CALLERS WELCOME Mon.-Sat. 9 a.m.-5 p.m.
PLEASE ADD 10% VAT

RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.
1/4W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price 1-99	100+
1/4	5%	4.7Ω-2.2MΩ	E24	1p	0-8p
1/4	10%	3.3MΩ-10MΩ	E12	1p	0-8p
1/4	2%	10Ω-1MΩ	E24	3-5p	3p
1/4	10%	1Ω-3.9Ω	E12	1p	0-8p
1/4	5%	4.7Ω-1MΩ	E12	1p	0-8p
1/4	10%	1Ω-10Ω	E12	6p	5-5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40, E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/4W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	15p	AF139	32p	BF177	28p	OC45	12p	2N3710	11p
AC126	12p	AF178	32p	BF178	32p	OC70	12p	2N3711	11p
AC127	15p	AF180	40p	BF179	32p	OC71	12p	2N3819	32p
AC128	15p	AF181	40p	BF180	32p	OC72	12p	2N4062	12p
AC131	12p	BC107	12p	BF181	32p	OC81	12p	2N4286	20p
AC132	12p	BC108	12p	BF194	14p	OC82D	12p	2N4289	20p
AC176	15p	BC109	12p	BF195	14p	2N2646	60p	40360	35p
AC187	22p	BC147	12p	BF197	15p	2N2904	20p	40361	35p
AC188	22p	BC148	12p	BF200	32p	2N2926	10p	40362	40p
AD140	50p	BC149	12p	BFY50	20p	2N3054	58p	40408	40p
AD149	45p	BC157	14p	BFY51	20p	2N3055	60p	ZTX108	15p
AD161	33p	BC158	14p	BFY52	20p	2N3702	13p	ZTX300	15p
AD162	36p	BC159	14p	BUY105	22p	2N3703	12p	ZTX302	20p
AF114	20p	BC187	22p		£2.25	2N3704	13p	ZTX500	15p
AF115	20p	BD131	75p	OC26	45p	2N3705	12p	ZTX503	20p
AF116	20p	BD132	75p	OC28	50p	2N3706	11p		
AF117	20p	BD133	75p	OC35	50p	2N3707	12p		
AF118	38p	BF115	25p	OC42	12p	2N3708	10p		
AF126	20p	BF173	20p	OC44	12p	2N3709	11p		

ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS, 3W, 10, 25,
50Ω and decades to 100kΩ, 35p.

DIODES

DIODES RECTIFIER			SIGNAL	
BY127	1250V	1A	OA85	7p
IN4001	50V	1A	OA90	5p
IN4002	100V	1A	OA91	5p
IN4004	400V	1A	OA202	7p
IN4006	800V	1A	IN4148	5p
IN4007	1000V	1A	BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K, log, or lin, 40p.

DUAL GANG, 10K + 10K, ecc. log, or lin, 60p.

KNOB FOR ABOVE 12p.

FRONT PANEL 65p.

18 Gauge panel 12in x 4in with slots cut for use
with slider pots. Grey or matt black finish
complete with fixings for 4 pots.

THYRISTORS

2N5060 50V 0.8A 30p.

2N5064 200V 0.8A 47p.

CR51/40 400V 1A 25p.

106F 50V 4A 40p, 106D

400V 4A 65p.

ALUMINIUM BOXES

AB7	2 1/2 x 5 1/2 x 1 1/2in	50p	AB14	7 x 5 x 2 1/2in	84p
AB8	4 x 4 x 1 1/2in	30p	AB15	8 x 6 x 3in	£1.08
AB9	4 x 2 1/2 x 1 1/2in	50p	AB16	10 x 7 x 3in	£1.22
AB10	4 x 5 1/2 x 1 1/2in	50p	AB17	10 x 4 1/2 x 3in	£1.08
AB11	4 x 2 1/2 x 2in	60p	AB18	12 x 5 x 3in	£1.20
AB12	3 x 2 x 1in	44p	AB19	17 x 8 x 3in	£1.60

HEATSINKS

2W 24p	4W 45p	TO5 clip 5p	TO1 single 5p
3W 36p	6W 60p	TO18 clip 5p	TO1 double 8p

TRANSFORMERS

All have 240V primary			
MT30/2	0-12-15-20-24-30V	2A	£2.85
MT50/1	0-19-25-33-40-50V	1A	£1.90
MT50/1	0-19-25-33-40-50V	1A	£2.55
MT50/2	0-19-25-33-40-50V	2A	£3.50
MT60/1	0-24-30-40-48-60V	1A	£2.10
MT60/1	0-24-30-40-48-60V	1A	£2.80
MT60/2	0-24-30-40-48-60V	2A	£3.80

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 0.01μF,
0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 0.1μF, 4p, 0.22μF, 7 1/2p,
0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3 1/2p, 0.15μF 4 1/2p,
0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7 1/2p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF,
0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6 1/2p, 0.47μF, 8 1/2p, 0.68μF, 11p, 1.0μF, 13p,
1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,
3 1/2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7

(μF/V) 1/63, 1/5/63, 2/2/63, 3/3/63, 4/7/63, 6/8/40, 6/8/63, 10/25, 10/63, 15/16, 15/40,
15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16,
100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63, 100/40,
150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1,000/4, 10p, 470/10,
680/6.3, 11p, 100/63, 150/6.3, 220/6.3, 1,000/10, 12p, 470/25, 680/16, 1,500/6.3, 13p,
470/40, 680/25, 1,000/16, 1,500/10, 2,200/6.3, 18p, 330/63, 680/40, 1,000/25, 1,500/16,
2,200/10, 3,300/6.3, 4,700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF	35V	2.2μF	35V	22μF	16V	12p
0.22μF	35V	4.7μF	35V	33μF	10V	
0.47μF	35V	6.8μF	25V	47μF	6.3V	
1.0μF	35V	10μF	25V	100μF	3V	

VEROBOARD

2 1/2 x 3 1/2	0.1	0.15
2 1/2 x 5	22p	16p
3 1/2 x 5	24p	24p
3 1/2 x 5	24p	24p
3 1/2 x 5	27p	27p
17 x 2 1/2	75p	57 1/2p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p, Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable 22p/metre.

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	2500μF 64V	80p	4500μF 16V	50p
2500μF 40V	74p	2800μF 100V	£2.60	4500μF 25V	£1.68
2500μF 50V	58p	3200μF 16V	50p	5000μF 50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	10p	0.047μF	13p	0.22μF	20p
0.022μF	12p	0.1μF	13p	0.47μF	22p

POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas
or smoke into an electrical signal. The sensor decreases its electrical resistance when
it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide,
methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or
smoke. This decrease is usually large enough to be utilized without amplification.
Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but
excluding case. Mains operated detector £5.20. 12 or 24V battery operated audible
alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

9p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to
dry, and immerse the board in the etchant. On removal the circuit remains in high
relief.

METERS

£1.90
1 1/2in scale 500mA, 1mA, 10mA, 100mA.

BULGIN MAINS CONNECTORS

3 pin 1 1/2A chassis plug	10p	3 pin 1 1/2A chassis socket	18p
line socket	13p	line plug	13p
3 pin 3A chassis plug	10p	3 pin 3A chassis socket	21p
line socket	14p	line plug	23p
3 pin 5A chassis plug	16p	line socket	18p
line socket	18p	2 pin 5A line plug	20p

THERMISTORS

VA1005	15p
VA1026	15p
VA1033	15p
VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.35

WAVECHANGE SWITCH

23p
12W 1p, 4W 3p, 2W 2p, 6W 2p, 3W 4p.

LINEAR IC's

700	14 pin dil.	40p
741	8 pin dil.	30p
741	14 pin dil.	30p
743	14 pin dil.	45p
747	14 pin dil.	85p
748	8 pin dil.	85p
	Dil. sockets 14 pin and 16 pin	16p

DISCO, SHOP, SOUND TO LIGHT, STAGE PHOTO-FLOOD LIGHT FITTINGS

ALL STEEL, DARK BLUE HAMMER FINISH

TAKES STANDARD 100 WATT SPOT LAMPS, OBTAINABLE FROM MOST ELECTRICAL SHOPS

3 BANK UNITS (LESS LAMPS)

ONLY **£6.50** INCLUDING V.A.T.
Plus Post/Packing 35p


SINGLE SPOT FITTING (LESS LAMP)

ONLY **£1.50** INCLUDING V.A.T.
Plus Post/Packing 20p

LAMPS CAN BE SUPPLIED

RED, PINK, GREEN, YELLOW, BLUE, VIOLET, CLEAR
MINIMUM 3 LAMPS. (State second colour.)

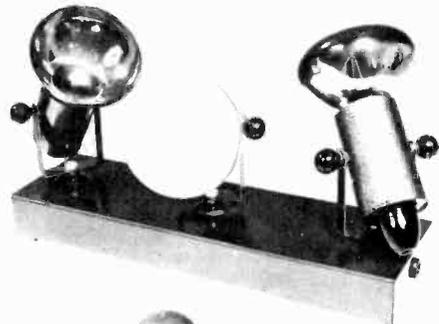ONLY **£2.25** INCLUDING V.A.T.
Plus Post/Packing 20p



TRAFALGAR SUPPLIES, Dept. H.T.

STANDISH STREET • BURNLEY • LANCs.

Digital Clock Kits

SPACE RESEARCH NOW BRINGS YOU A DIGITAL CLOCK - WITH NO MOVING PARTS - FOR YOU TO BUILD.



CHOOSE FROM TWO EASY TO BUILD KITS -

KIT O All components, including P.C.B. designed for easy home assembly - Bright and clear digits. Tough A.E.S. plastic case with contrasting front panel.

PRICE - £23.00 plus £2.30 V.A.T.
Total £25.30 inc. post and package

KIT M Smaller digits than in kit O. All components and steel case covered in blue and white plastic (as made up in illustration).

PRICE - £21.00 plus £2.10 V.A.T.
Total £23.10 inc. post and package

Only our advanced designed techniques make these low prices possible. Both kits are tested before they leave us and are covered by the P.E.A. money back guarantee.



P.E.A. Ltd.
35 High Street
WELWYN
Herts. AL6 9EE

Please send details of: Kit O Kit M

Please send me: Kit O Kit M

I enclose PO/Cheque to the value of £ _____

NAME _____

ADDRESS _____

TWO NEW SOLDER SIPPERS MAKE DE-SOLDERING QUICK & EASY

A SUPER PRESENT ANYTIME!

Longs

Longs Ltd.
Hanworth Lane
Trading Estate
Chertsey Surrey
KT16 9LZ.



Maxi-Super HT 1810 and Maxi-Mini HT 1800 Solder Sippers

Designed for use when working or re-working P.C. Boards. Permits removal of molten solder from Multi-leg components, enabling easy extraction. The solder is 'sipped' through the nozzle, and automatically ejected when the instrument is next used. A Swiss precision instrument manufactured to a high degree of accuracy.

The anti-corrosive outside casing has a knurled finish for more positive grip, and encases plated internal parts.

The Maxi-Super has been designed with a 3.5 kg. spring action recoilless plunger, whilst the Maxi-Mini with its conveniently shaped operating button, has a 2.5 kg. spring action plunger, protected by a channel guard.

Both models have been designed with an easy-to-replace 'dupont' teflon screw-in nozzle.

PLEASE FORWARD without obligation further details. <input type="checkbox"/>	PLEASE SUPPLY Maxi-Super HT 1810 at £6.60 <input type="checkbox"/>	PLEASE SUPPLY Maxi-Mini HT 1800 at £4.95 <input type="checkbox"/>
I enclose cheque value £ _____		
NAME _____		POSITION _____
COMPANY _____		
ADDRESS _____		
SIGNED _____		Reg. England 68496
Prices include VAT		

An electronic piano for only £60

You'll enjoy building – and playing – this really top quality musical instrument. And it will cost you pounds less than you would pay for a commercial electronic piano. Yet it boasts the kind of refinements you would find only on the most expensive. A significant feature of this design is that the instrument is touch-sensitive like a conventional piano: the harder you strike the keyboard the louder the sound. The keyboard provides a range of five octaves, and there is a 'sustain' pedal equivalent to the loud pedal on a piano.

Two new designs for Horn Loudspeakers

Many people consider that horn loudspeakers give better sound reproduction than any other type. We've got two highly adaptable designs whose specifications amount to a comprehensive design code for a wide range of horn loudspeakers.

Build it with Wireless World

FERRANTI



Buy from the experts!

- * ALL DEVICES
- * WE HAVE STOCKS OF ALL DEVICES FOR IMMEDIATE DELIVERY.
- * WE CAN SUPPLY ANY FERRANTI DEVICE TO ORDER. Send S.A.E. for quotation.
- * WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS, WITH A STAFF OF EXPERIENCED ENGINEERS.

ZN414 £1.32 WITH CIRCUITS AND DATA

BFS59	15p	ZTX310	8p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p			ZS271	16p
ZTX109	11p	ZTX382	15p			ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	16p		
ZTX301	13p	ZTX500	12p	ZS124	18p		
ZTX302	17p	ZTX501	13p	ZS140	25p		
ZTX303	14p	ZTX502	17p	ZS141	43p		
ZTX304	21p	ZTX503	14p	ZS142	33p		

* DIODES *

* ZENERS *
KS030A to
KS180A
all types 19p

MOTOROLA MJE2955 £1.17; MJE3055 72p each.
RCA PRICES SLASHED! CA3075 99p; CA3090Q £3.25 limited quantity only
P.E. TRIFFID ZT1711 24p; 2N1132 25p.
GEMINI AMPLIFIER P.C.B.s and Semiconductor kits still available.

FREE! Our comprehensive catalogue giving data and connection diagrams for a wide range of Ferranti semiconductors. Just send S.A.E.

POSTAGE AND PACKING 10p. FREE ON ORDERS OVER £2
ALL OUR PRICES INCLUDE V.A.T.

DAVIAN ELECTRONICS

PO BOX 38 OLDHAM, LANCS, OL2 6XJ

Dimmit

range of light dimmers


Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression, 60mm slider range, size 12x5x4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £5.50 inc. VAT, add 10p P. & P. Also available in 2kW, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800 watt. Full instructions. £7.50 inc. VAT, add 10p P. & P. Send 10p for complete illustrated catalogue and price list.

YOUNG ELECTRONICS Mail Order Dept.

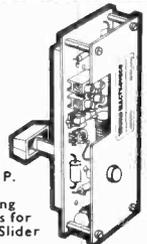54 Lawford Road, London NW5 2LN. Telephone 01-267 0201



AMAZING MINI-DRILL



FOR PRECISION
**MODEL
WORK**



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL Super Kit (extra power, interchangeable chuck) £6.35 p.p. 13p.
De Luxe Professional Kit with 17 tools £9.40 p.p. 23p. Prices include V.A.T.


Money ref. g'tee. **MERLIN SUPPLY CO.**

Dept. PE274, Nailsea, Bristol BS19 2LP

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

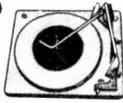Plays 12, 10 or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V Size 13" x 11 1/2". Above motor board 3 1/2". below motor board 2 1/2".



with STEREO and MONO XTAL £6.25 Post 25p.

PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Chrome fittings.

Motor board cut for BSR deck £4.50 Post 25p

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact, overall size only 13" x 10" x 8 1/2". 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains.



Attractive Teak finish. Weight 13 lb. Bargain Price £25 85p carriage

SPECIAL OFFER!

SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes Type A or 0 to 6 hours Type B. Makers' last list price £4.50. Brand new and fully guaranteed. Fully insulated. Post 25p (PLEASE STATE TYPE A OR B WHEN ORDERING)



WEYRAD P50 — TRANSISTOR COILS

RAZV Ferrite Aerial 85p
Osc. P50/1AC 40p
I.F. P50/2CC 40p
3rd I.F. P50/3CC 40p
Spare Cores 3p
Mullard Ferrite Rod 6 x 1/2". 20p. 6 x 1/2". 20p. 3 x 1/2". 10p.

Driver Trans. LFDT4 65p
Printed Circuit, PCA1 65p
J.B. Tuning Gang 65p
Wayrad Booklet 10p
OPT1 65p

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edges 5K.S.P. Transistor 25p.

80 ohm Coax 4p yd.
BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40 80 yd. £2.
FRINGE LOW LOSS Ideal 625 and colour 10p yd

8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticated roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance, 8in 10 watts, 10in 12 watt music power. £3.75 Post 25p



E.M.I. 13 1/2" x 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p £4.50



With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-80 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p £2.75

Bookshelf Cabinet 16 x 10 x 9in. £5.50 Teak finish Post 25p

SET OF 3 MOTORS FOR COLLARO STUDIO TAPE DECK £2.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in sides 6 x 4in 45p; 8 x 6in 53p; 10 x 7in 65p; 12 x 8in 85p; 14 x 9in 90p; 16 x 10in 90p; 12 x 3in 50p; 18 x 10in £1. ALUMINIUM BOXES, 3 x 3 x 3in 60p; 4 x 4 x 4in 70p; 6 x 4 x 4in 80p; 9 x 4 x 4in £1; 12 x 4 x 4in £1.30. ALUMINIUM PANELS 18 s.w.g. 6 x 4in 9p; 8 x 6in 15p; 14 x 3in 18p; 10 x 7in 19p; 12 x 5in 20p; 12 x 8in 24p; 16 x 6in 28p; 14 x 9in 34p; 12 x 12in 40p; 16 x 10in 50p. PAXOLIN PANEL 10 x 8in 15p.

ANOTHER R.C.S. BARGAIN! 4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watt output, 15 ohm. AC mains operated with transformer. 3 Controls, volume, treble, bass and On/Off switch with knobs. Reely made on printed circuit board. Fused inputs and outputs. Famous make, size 8in wide x 4in deep x 3in high. Suitable 7 x 4 speaker, £1. £5.95 Post 20p

R.C.S. STABILISED POWER PACK KITS

All parts and Instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2.20 Post 25p Details S.A.E. Size 3 1/2" x 1 1/2" x 1 1/2".

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2" x 1 1/2" x 1/2". Response 25 c/s to 25 Kc/s. 26 dB gain. For use with valve or transistor equipment. 99p Post Full Instructions supplied. Details S.A.E. 20p

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 100 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. 95p Post 20p

BRITISH FM/VHF TUNING HEART

88 to 108 M/C/S British made. 2 Transistors ready aligned requires 10-7 M/C/S I.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 Post 20p

MAINS TRANSFORMERS

	ALL POST 25p each
Eagle MT12 12-0-12V 50 mA	90p
250-0-250 80 mA, 6-3V 3-5A 6-3V 1A or 5V 2A	£2-50
350-0-350 80 mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£3-00
300-0-300 120 mA, 6-3V 4A C.T.; 6-3V 2A	£3-25
MINIATURE 200V 20 mA, 8-3V 1A 2 1/2" x 2 1/2" x 1 1/2"	75p
MIDGET 220V 45 mA, 6-3V 2A 2 1/2" x 2 1/2" x 1 1/2"	90p
HEATER TRANS. 6-3V 3A	60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £2-80	
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2-25	
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3-80	
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3-75	
5, 8 and 10V; 5 amp £1-20, 3 amp. 3, 5, 8, 10, 13 and 5-0-5V £1-30. Dims 5 1/2" x 5 1/2" x 1 1/2". 500mA 90p 9V 1 amp 95p, 12V 300mA 75p, 12V 500mA 85p, 12V 750mA 95p, 40V 1 amp £1-75.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £2-25; 500W £6-25; 750W £10; 1000W £15	
CHARGER TRANSFORMERS. Input 200/250V, for 6 or 12V, 1 1/2 amp £1-50; 2 amp £1-80; 4 amp £2-50	
BATTERY CHARGERS. Fully built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4-50.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1 amp 40p; 2 amp 55p; 4 amp 85p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 Carr. 50p Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS			
2/350V	14p	14p	50 - 50/350V 50p
4/350V	18p	500/25V	60 - 100/250V 85p
8/450V	18p	1000/25V	32 - 32/250V 20p
16/450V	22p	1000/50V	47p 32 - 32/450V 60p
32/500V	50p	8 - 8/450V	22p 350 - 50/325V 55p
25/25V	10p	8 - 16/450V	25p 32 - 32 - 32/350V 55p
50/50V	10p	16 - 16/450V	40p 100 - 50 - 50/350V 55p
100/25V	10p	32 - 32/350V	40p

LOW VOLTAGE ELECTROLYTICS. 1, 2, 4, 5, 8, 15, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 6V 25p; 25V 42p; 50V 57p. 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p. 5000mF 8V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC, 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 9p; 0.47 25p. SILVER MICA. Close tolerance 2, 2.2, 2.5, 500pF 8p; 560-2, 200pF 10p; 2, 200-10, 10p 20p; 8, 800pF -0.01, mid 30p each. TWIN GANG, "0-0" 200pF - 178pF, 65p; 500pF standard 45p. 365pF + 365pF with 25pF + 25pF. Slow motion drive 50p. SHORT WAVE SINGLE, 10pF, 30p, 25pF, 55p, 50pF, 55p. NEON PANEL INDICATORS 250V AC/DC. Amber 20p. RESISTORS. 1/4W, 1/2W, 1W, 20% 1p; 2W, 5p, 10p to 10M. HIGH STABILITY. 1/4W, 10 ohms to 100 ohms, 10p. DITO 5%. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 ohms, 10 watt, 15 watt, 15 ohms to 100K 10p each; 0.5 ohm to 8.2 ohms 10p. TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12IN 50 WATT. GROUP 50/12. 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. £17.60

BAKER MAJOR 12" £9.90

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated. Post free

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50

Please state 3 or 8 or 15 ohms. Post free

BAKER "BIG-SOUND" SPEAKERS Post free

Group 25'	Group 35'	Group 50'
12in. £8.80	12in. £9.90	15in. £22
25W 3 or 8 or 15 ohm	35W 3 or 8 or 15 ohm	50W 8 or 15 ohm

TEAK VENERED HI-FI SPEAKER & CABINETS
For 12in or 10in dia. speaker 20 x 13 x 8in. £9.90. Post 25p
For 13 x 8in or 8in speaker 16 x 8 x 6in. £5.50. Post 25p
For 8 x 5in speaker 16 x 8 x 6in. £4.40. Post 25p
For 6in and Tweeter 12 x 8 x 6in. £4.00. Post 25p
LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

GOODMANS 6 1/2in. HI-FI WOOFER

8 ohm, 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. De Luxe Hi-Fi Enclosure Systems, etc. Sutable Cabinet 12 x 8 x 6 1/2 Sutable Tweeter £2 £4

ELAC CONE TWEETER
The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 16,000 c/s. Size 3 1/2" x 2in deep. Rating 10W, 3 ohm. Crossover 95p £1.90 Post 20p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1-95. De Luxe Hi-Fi Enclosure Systems, etc. CROSSOVERS, TWO-WAY 3,000 c/s or 8 or 15 ohm 95p. LOUDSPEAKERS P.M. 3 OHMS. 7.4in. £1.25; 6.1in. £1-50; 5.8in. £1-80; 10in. £2-00; 8in. £1-75; 10" 6in. £1-90. SPECIAL OFFER! 80 ohm, 2in, 2 1/2in; 15 ohm, 2in, 3in, 25 ohm, 2 1/2in dia., 3in dia., 5in dia. £1 EACH TYPE 2 ohm, 2 1/2in, 3in, 5in dia. (6 x 4in 8 ohms £1-50.) RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. DIAMETER 4W £2-50. 10in diameter 5W £2-50. 12in diameter, 8W. £2-95. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 85p. Mike trans. mu metal 100:1 £1-25.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E. £49 Carr. £1-00 PROFESSIONAL VALVE MODEL, 100W, callers only. £69.



BARGAIN AM TUNER. Medium Wave. Transistor Superhet, Ferrite aerial. 9 volt. £4.95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass controls. 18 volt d.c. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE 25p. BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd. JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead-Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMICS 8p; CANS 5p.

REVERSIBLE 4 POLE MOTOR 1,400 r.p.m. Reversible 42 Watt £1.95

splide 1 1/2" x 1 1/2" size 3" x 3". As illustrated. With Cooling Fan. a.c. 240V. Post 25p

E.M.I. GRAM. MOTOR. £1

120V or 240V a.c. 2,400 r.p.m. 2 pole 70mA. Size 2 1/2" x 2 1/2" x 2 1/2". Post 25p

SPECIAL OFFER 100 ohm 20W Rheostat 2 1/2in dia. Ceramic Former, screw terminals, 1/2in diam. spindle. 95p, post 25p.

RADIO COMPONENT SPECIALISTS

Illustrated Colour Brochure, Radio Books and Component Lists 10p. (Minimum posting charge 20p.) 337 WHITEHORSE ROAD, CROYDON 9-6 Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

MAPLIN ELECTRONIC SUPPLIES

★ SAME DAY SERVICE

LARGE or SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel: blue hammer. Detachable aluminium front panel finished in white. Dimensions in inches.



Model	W	H	D	Price
120	8	2 1/2	3	£1.85
220	8	6	3 1/2	£2.65
221	8	6	6	£2.80
320	12	8	12	£5.00

Chassis for model 320 £1.75 extra. Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board including tremulant if required. ONLY 3 7/16" x 4 1/8". ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed. ★ DMO2T (with tremulant) ONLY £14.25. ★ DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 87 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

S.a.e. please for full technical details. Trade enquiries welcome.



MAPLIN: Projected site of London's third airport.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES! We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards. Send s.a.e. now for our detailed price lists.

YOU SIMPLY MUST SEE OUR PRICES!

Keyboard 49 note C-C	£14.35
UA 7815 (15V 1.5A) voltage regulator	£2.30
741C 8-pin DIL	36p
MFC 6640 electronic attenuator	£0.95
SG 3402N for Ring Modulator	£1.69
CA 3046	69p

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd	V	Price	Mfd	V	Price
1	63	6p	68	6.3	6p
1.5	63	6p	68	16	6p
2.2	63	6p	68	30	6p
3.3	63	6p	100	4	6p
4.7	63	6p	100	10	6p
6.8	40	6p	100	25	6p
6.8	63	6p	100	40	6p
10	25	6p	100	63	12p
10	63	6p	150	6.3	6p
15	16	6p	150	16	6p
15	40	6p	150	25	6p
15	63	6p	150	40	6p
22	10	6p	150	63	12p
22	25	6p	220	4	6p
22	63	6p	220	10	6p
33	6.3	6p	220	16	6p
33	16	6p	220	25	10p
33	40	6p	220	40	12p
47	4	6p	220	63	12p
47	10	6p	330	4	6p
47	25	6p	330	10	6p
47	40	6p	330	16	10p
47	63	6p	330	63	22p
47	63	6p	330	63	22p



PLUGS AND SOCKETS



DIN PLUGS	MAINS	RS8 8 way chassis socket	Std. 1/2" stereo plug Plastic 16p
2 pin (1 flat) 8p	P380 3 pin 1.5A chassis plug with 4 pin, 5 pin A line socket. Per pair (180°), 5 pin B chassis plug 17p	SA 2190 3 pin 5A chassis plug 17p	Screened 25p
3 pin 8p	SA 1862 Line socket for above 18p	SA 1862 Line socket for above 18p	Open mono socket 1/2" 10p; Moulded mono socket 1/2" with 2 break contacts 13p; Moulded stereo socket 1/2" with 3 break contacts 18p; 3.5mm. plug plastic 8p; screened 11p; open socket 8p
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p	McMURDO RP8 8 way chassis plug 36p	JACK	
DIN Sockets		Std. 1/2" mono plug Plastic 13p; Screened 17p	
2 pin 6p			
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 7p			

WE KNOW YOU NEED IT!

The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our HIGH VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue.



and leave the rest to us!

OMNIUM GATHERUM

PP3, 6 etc. battery clip dual min. 9p.
PPI-9 etc. battery clip separate per pair 6p.
Pair crocodile clips 1 red, 1 black insulated sleeve 7p.
Solder Multicore 22 s.w.g. 10 metres 20p.
Silicone grease in special dispenser 20ml 43p.
Red neon 240V panel mounting 25p.
Lacing Cord Strong rayon covered PVC 25m 43p.
Panel fuse holders 20mm 20p; 14m 30p.

Transformers
LF780 min. output transformer Pri. 1-2kΩ Sec. 5Ω 200mW 35p.

Sub-min. Mains Transformer
6-0-6V 100mA 95p, 12-0-12V 50mA 95p.
Size: Both approx. 30 x 27 x 25mm

Min. Mains Transformer
Size: 46 x 31 x 38mm.
0-12V 250mA, 0-12V 250mA £1.36.

Mains Transformer MT3AT
Pri. 200-220-240V. Sec. 12-15-20-24-30V 1A £2.48.

Mains Transformer MT206AT
Pri. 200-220-240V. Sec. 0-15-20V 1A, 0-15-20V 1A £3.10.

Hook-up wire, 7 strand 0.2mm. PVC covered tinned copper wire for light general connexions up to 1.4A. 11 colours: black, blue, brown, green, grey, orange, pink, red, violet, white, yellow. 10 metres of any one colour 17p. Pack of 11 (1 of each colour) 10m coils £1.75.

Single core screened 6p per metre.
Twin individually screened 9p per metre.
High quality single screened 50Ω 100pF per metre: ideal for high grade audio connexions 12p per metre.

Mains 3-core sub-miniature 1A black PVC covered 19 strand 0.1mm per conductor. 6p per metre.

POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle

Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p



Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p.

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 53p.

PRESETS

Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p

Wirewound 10% 1W 1/2" spindle 10, 50, 100R 34p; 250, 500, 1k, 5k 33p; 10k, 37p; 25k 40p; 50k 44p.

RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12	1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1.2M to 10M E12	1p
Carbon Film 1/4W 5% 1Ω to 910k E12 & E24	1p
Carbon Film 1W 5% 10Ω to 10M E12	3p
Metal Oxide 1/4W 2% 10Ω to 1M E12 & E24	4p
Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12	10p
Wirewound 2 1/2W 5% 1ohm to 270ohms E12	10p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades


TRANSISTORS, DIODES & I.C.'s.

AC127	25p	MPP102	36p	2N3053	18p
AC128	20p	OC25	49p	2N3054	55p
AC176	17p	OC28	49p	2N3055	49p
AD149	47p	OC35	49p	2N3819	24p
AD161/2	69p	OC44	20p	OC49	7p
BC107	10p	OC71	20p	OC91	6p
BC108	10p	T1843	28p	1N914	4p
BC109	10p	2N706	10p	1N4148	4p
BC147	10p	2N1304	30p	1N4001	6p
BC148	10p	2N1711	24p	1N4002	6p
BC149	10p	2N2219	25p	1N4002	7p
BC168	13p	2N2646	45p	1N4004	7p
BC169C	12p	2N2905	33p	1N4005	8p
BC182L	12p	2N2907	25p	1N4006	8p
BC204	14p	2N2909	10p	1N4007	9p
BC209L	14p	2N2934	10p	W005	3p
BD131	45p	2N2936	10p	W04	3p
BD132	54p	741C 8-pin DIL	38p		
BD131/2	£1.20	741C 14-pin DIL	45p		
BF194	15p	DIL Sockets 3-pin	20p		
BFY51	16p	14-pin	16p		

See our catalogue for our full range of transistors, 74 series I.C.'s bridges, etc.

SWITCHES

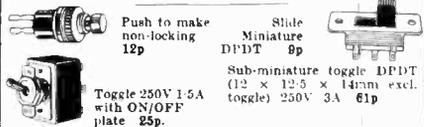Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p. Mains rotary DPDT 250V 2A 20p.



Push to make non-locking 12p
Slide Miniature DPDT 8p
Sub-miniature toggle DPDT (12 x 12.5 x 14mm) excl. W005 61p
Toggle 250V 1.5A with ON/OFF plate 25p.

VAT

Please add 10% to the final total.


Post and Packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea 0702 44101



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

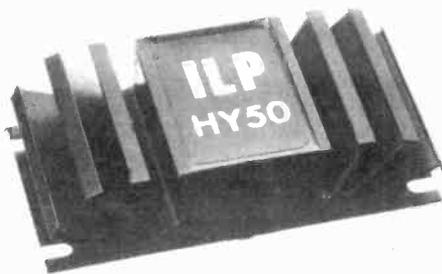

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular audio amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of "King-size" cigarettes. Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER: 25W RMS, 50W peak music power.
LOAD IMPEDANCE: 4-16Ω into 8Ω
INPUT SENSITIVITY: 0dB (0.775V RMS).
INPUT IMPEDANCE: 47kΩ.
TOTAL HARMONIC DISTORTION: Less than 0.1% at 25W typically 0.05.
SIGNAL/NOISE RATIO: better than 75dB.
FREQUENCY RESPONSE: 10Hz-50kHz ± 1dB.
SUPPLY VOLTAGE: ± 25V.
SIZE: 105 x 50 x 25mm.

SPEC.

Price £5.40 mono £10.80 stereo. Price inclusive of VAT & P. & P.

NEW HY5 PREAMPLIFIER


Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components and has been redesigned to run off a split power line with improvements in signal/noise, overload capability and reduced distortion. The output has been increased to match the power module (0dB), and share the same power supply.

Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 and power supply only potentiometers are required to complete a simple mono amplifier with input and output facilities expected to be found on Hi-Fi amplifiers.

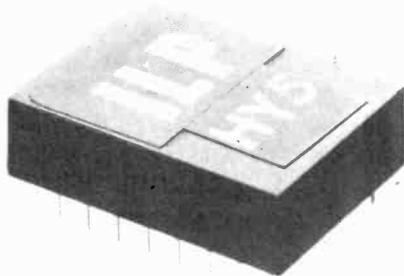The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.



INPUTS
 Magnetic Pick-up 3mV (within 1dB RIAA curve)
 Ceramic Pick-up up to 3mV.
 Microphone 10mV.
 Tuner 250mV.
 Auxiliary 3-100mV.
 Input impedance 47kΩ 1 kHz

OUTPUTS
 Tape 100mV.
 Main output: 0dB (0.775V).

SPEC.


ACTIVE TONE CONTROLS
 Treble ± 12dB at 10kHz
 Bass ± 12dB at 100Hz

OVERLOAD CAPABILITY
 (equalization stage) 40dB on most sensitive input.

OUTPUT NOISE LEVEL
 (below 10mV magnetic input) 68dB.

DISTORTION 0.05% at 1kHz.
SUPPLY VOLTAGE ± 16-25V.
SUPPLY CURRENT 15mA.

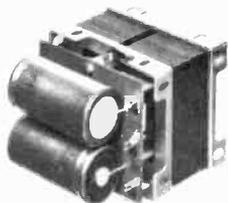Price £4.51 mono £9.02 stereo. Price inclusive of VAT & P. & P.



POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2¼in high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE ± 25V.
INPUT VOLTAGE 210-240V.
SIZE: L. 70 D. 90 H. 60mm.
 Price £5.23. Price inclusive of VAT & P. & P.


CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218


Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

Sinclair Project 80

exciting

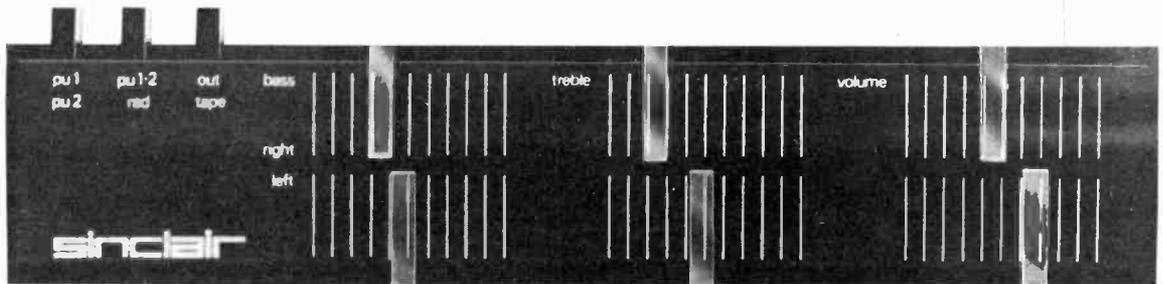

Stereo 80 pre-amplifier/control unit

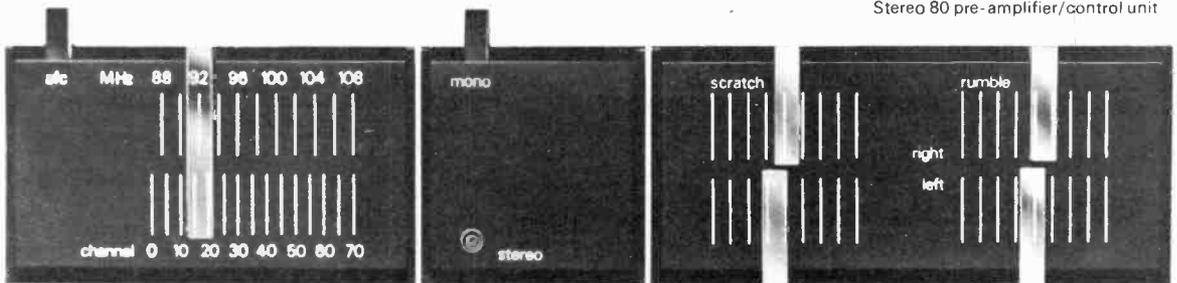

Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

only $\frac{3}{4}$ " deep x 2" high


Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

Typical Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5 45 +54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10 43 +£1.04 V.A.T.
30W, RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.6	£30 83 +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amp.	2 x Z.60s, Stereo 80; PZ.8	£33 83 +£3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14 93 +£1.49 V.A.T.

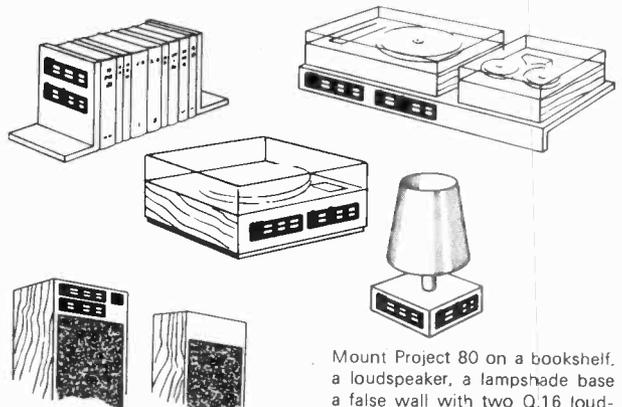
Project 80 FM tuner, decoder, and A.F.U. may be added as required



Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base a false wall with two Q.16 loudspeakers... almost anywhere.

new thinking in modular hi-fi

Stereo 80 pre-amplifier and control unit

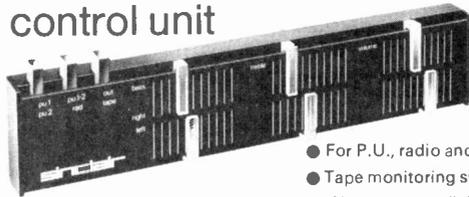

- For P.U., radio and tape
- Tape monitoring switch
- Simplest ever fixing


Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm (10 1/4 x 2 x 3/4 ins)
 Finish - Black with white indicators and transparent sliders
 Inputs - Magnetic pick-up 3mV RIAA corrected, Ceramic pick-up 300mV
 Radio 300mV; Tape 30mV
 Signal/noise ratio - 60dB
 Frequency range - 20Hz to 15KHz \pm 1dB; 10Hz to 25KHz \pm 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV + AB monitoring for tape
 Controls - Press button for tape radio and P.U. Sliders for volume, bass (-12dB to -14dB at 100Hz) treble (+11dB to -12dB at 10KHz)

R.R.P. **£11.95** +£1.19 V.A.T.

Project 80 FM tuner and stereo decoder

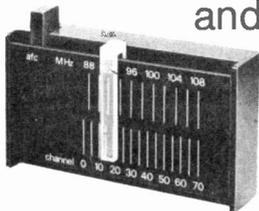

- Twin dual varicap tuning: 4 pole ceramic filter: switchable A.F.C.
- On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

TECHNICAL SPECIFICATIONS OF TUNER

Size - 85 x 50 x 20mm (3 1/2 x 2 x 3/4 ins)
 Tuning range - 87.5 to 108 MHz
 Detector - I.C. balanced coincidence for good A.M. rejection
 One I.C. equal to 26 transistors
 Distortion - 0.2% at 1KHz for 30% modulation
 4 pole ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Output - 300 mV for 30% modulation
 Power requirements - 23 to 33 volts

DECODER

Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/4 ins)
 One 19 transistor I.C.

R.R.P. **£11.95** +£1.19 V.A.T.

R.R.P. **£7.45** +0.74 V.A.T.


Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a charge (typically £1.00) will be made.


sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ
 Telephone St. Ives (0480) 64646
 Practical Electronics February 1974

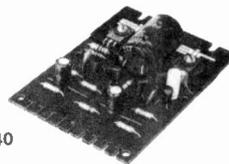Z.40 & Z.60 power amplifiers totally short-circuit proof



Z.40

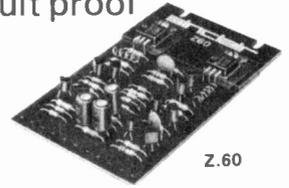

Z.60

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

Z.40 TECHNICAL SPECIFICATIONS

Size - 55 x 80 x 20mm (2 1/4 x 3 1/4 x 3/4 ins) 9 transistors
 Input sensitivity - 100mV
 Output - 15 watts RMS continuous into 8 Ω (35V)
 Frequency response - 10Hz - 100KHz \pm 1dB
 Signal/noise ratio - 64dB
 Distortion - at 10 watts into 8 Ω less than 0.1%
 Power requirements - 12 to 35 volts


Z.60 TECHNICAL SPECIFICATIONS

Size - 55 x 98 x 15mm (2 1/4 x 3 7/8 x 3/4 ins) 12 transistors
 Input sensitivity - 100-250mV
 Output - 25 watts RMS continuous into 8 Ω (45V)
 Distortion - typically 0.03%
 Frequency response - 10Hz to more than 200KHz \pm 1dB
 Signal/noise ratio - better than 70dB
 Built-in protection against transient overload and short circuiting
 Load impedance - 4 Ω min, max safe on open circuit

Z.40 R.R.P. **£5.45** +0.54 V.A.T., Z.60 R.R.P. **£6.95** +0.69 V.A.T.

Project 80 active filter unit

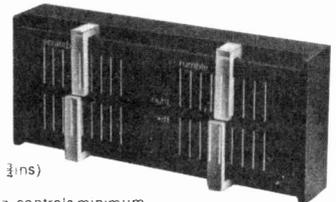Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.



TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/4 ins)
 Voltage gain - minus 0.2dB
 Frequency response - 36Hz to 22KHz controls minimum
 Distortion - at 1 KHz - 0.03% using 30V supply
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct slope
 L.F. cut off (rumble) - 28dB at 20Hz 9dB/oct slope


- For scratch and rumble control
- Transistorised active circuitry

R.R.P. **£6.95** +0.69 V.A.T.

Power supply units

PZ.8

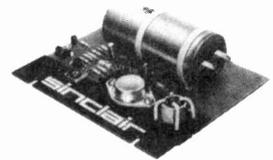Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.



R.R.P. **£7.98** +0.79p V.A.T.
 Without mains transformer

PZ.5 30V un stabilised
 R.R.P. **£4.98** +0.49p V.A.T.

PZ.6 35V stabilised
 R.R.P. **£7.98** +0.79p V.A.T.

To **SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ**


Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

ELECTROVALUE CATALOGUE 7

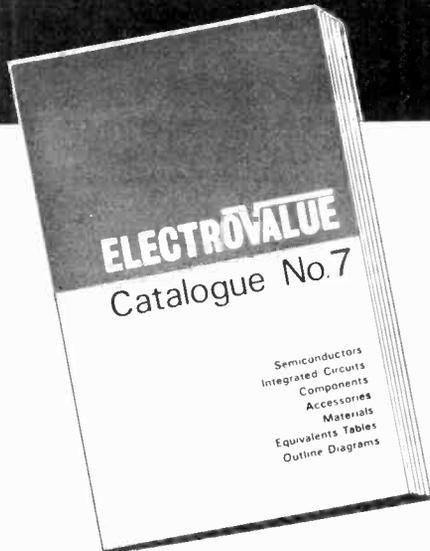

25p
POST FREE
(Including
25p REFUND
VOUCHER)

The best yet!

112 pages (plus covers) and our best yet! Almost all items in Catalogue 7 are there through information fed from our own computer, which enables us to control stock-buying to meet demand with remarkable accuracy. This means that orders, which we micro-film for record keeping are handled with utmost speed and efficiency. EV prices remain keenly competitive and in addition there are discounts as well, to give you further savings. The refund voucher for 25p which we give with the catalogue is allowable on orders for £5 or more list value and this saves you still more.

This is EV Service

1 DISCOUNTS

allowed on all items (except those shown NETT) as follows: 10% on orders from £5 to £14.99 (list), 15% on orders for £15 and over (list)

2 WE PAY POSTAGE

on orders within the U.K. For mail orders for £2 and under a handling charge of 10p is made.

3 GUARANTEE OF QUALITY

All goods are brand-new and sold as being to makers' full stated specifications and guaranteed accordingly.

GIRO ACCOUNT No. 38/671/4002

ELECTROVALUE

All mail orders and correspondence to head office
ELECTROVALUE LTD., 26 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603
Hours 9 a.m. - 5.30 p.m. daily. Saturdays 9 a.m. - 1 p.m. Telex 264475
NORTHERN BRANCH
Electrovalue Ltd., 680 Burnage Lane, Manchester M19 1NA
Hours 9 a.m. - 5.30 p.m. daily. Saturdays 9 a.m. - 1 p.m. Phone 061-432 4945

NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

HANDBOOK OF SEMI-CONDUCTOR CIRCUITS ...	£1-95	4-CHANNEL STEREO FROM SOURCE TO SOUND, by K. Sessions ...	£1-35
ALL-IN-ONE T.V. ALIGNMENT, by J. Shane ...	£1-75	JAPANESE RADIO, RECORD AND TAPE PLAYER SCHEMATIC / SERVICING MANUAL, by Homer L. Davidson ...	£1-90
BASIC ELECTRONIC CIRCUITS SIMPLIFIED, by N. Hibbs ...	£1-85	101 T.V. TROUBLES FROM SYMPTOM TO REPAIR, by A. Margolis ...	£1-40
BASIC ELECTRONIC COURSE, by N. Crowhurst	£1-85	STEREO/QUAD HI-FI PRINCIPLES AND PROJECTS, by K. Sessions	£1-35
FET APPLICATIONS HANDBOOK, by J. Eimbinder ...	£1-85	HOW TO REPAIR MUSICAL INSTRUMENT AMPLIFIERS, by B. Wels ...	£1-50
BASIC ELECTRONIC TEST PROCEDURES, by I. M. Gottlieb ...	£1-95	INSTALLING HI-FI SYSTEMS, by J. Markell and J. Stanton ...	£1-40
BASIC ELECTRICITY AND BEGINNING ELECTRONICS, by M. Clifford ...	£1-40	NEW WAYS TO DIAGNOSE ELECTRONIC TROUBLES, by Jack Darr ...	£1-50
HANDBOOK OF IC CIRCUIT PROJECTS, by J. Ashe ...	£1-40	SERVICING THE SOLID-STATE CHASSIS, by H. Davidson ...	£1-40
PICTORIAL GUIDE TO TAPE RECORDER REPAIRS, by F. H. Belt ...	£1-40	MODEL CAR RACING BY RADIO CONTROL, by G. Siposs ...	£1-40
SIMPLIFIED T.V. TROUBLE DIAGNOSIS, by Robert L. Goodman ...	£1-85		
MARINE ELECTRONIC HANDBOOK, by L. G. Sands	£1-35		
SELECTING AND IMPROVING YOUR HI-FI SYSTEM by H. Swearer ...	£1-40		



FOULSHAM-TAB LTD.
YEOVIL ROAD, SLOUGH, BUCKS.

SPARKRITE Mk II ELECTRONIC IGNITION KIT



COMPRISES Everything:

Ready Drilled Case and Metalwork, Cables, Coil Connectors, Silicon Grease, Printed Circuit Board, 5-year guaranteed components and a full 8-page instruction leaflet.

WHEN COMPLETE THE UNIT CAN BE FITTED TO YOUR CAR IN ONLY 15 MINUTES USING THE STANDARD COIL AND CONTACT BREAKER POINTS. TO GIVE YOU:

Instant all weather starting. Up to 20% fuel saving. Longer battery life. Higher top speed. Faster acceleration. Spark plugs last about five times longer. Misfire due to contact breaker, bounce electronically eliminated. Purer exhaust emission resulting in less air pollution. Contact breaker burn *eliminated*. Suitable for all petrol engines up to 8 cylinders.

PRICE ONLY £12.65

Ready Built Unit £14.85. Unit for Motor Cycles with twin coils and twin C. B. Points £19.80 (prices include VAT and post and packing). (Not available in kit form)

Please state whether positive or negative earth units are required when ordering.

SEND FOR YOUR UNIT OR FULL BROCHURE NOW

From

ICE ELECTRONIC SYSTEMS, Dept. PE
144 PARK FARM ROAD, BIRMINGHAM B43 7QH

VARIABLE VOLTAGE TRANSFORMERS

**INPUT 230/240V a.c. 50/60 OUTPUT
VARIABLE 0-260V**

All Types

SHROUDED TYPE

0.5 KVA (2 amp) £10.00
1 KVA (5 amp) £14.70
2 KVA (10 amp) £28.10
3 KVA (15 amp) £31.25
4 KVA (20 amp) £72.50
37.5 amp £102.50
50 amp £122.50



CARRIAGE AND PACKING
EXTRA

RING TRANSFORMERS

Functional Versatile Educational

These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g. using the RT.100 VA Model the output could be wound to give 8V @ 12A, 4V @ 25A or 2V @ 50A, etc.



Price:
RT.100VA 3-18 turns per V. £3.00, Post 35p.
RT.1KVA 1-82 turns per V. £8.60, Post 50p.
RT.2KVA 1-5 turns per V. £14.00, Post 75p.
RT.3KVA 1-5 turns per V. £19.00, Post £1.

VOLTAGE CHANGING TRANSFORMER

M.f.g. to highest W.D. spec. Auto wound, and tapped 0-130-160-200-250 at least 2kVA. Can also be used as 230-240V input, 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30-40-50-70-90V at 10 amps. Weight 40lb, length, 260mm, height 190mm, width 230mm. In original maker's wooden case, £8, Carr. £1.

BLOWER UNIT

200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm dia. x 60 mm deep. Price £3. Post 30p.




4 BANK 3c/o PUSH BUTTON ASSEMBLY

Black rectangular buttons.
5 units (min. order) 85p.
Post 15p.



PARVALUX Type: SD1

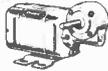5/86896/OJ
230/250V A.C. 50 p.p.m. 7 lb/in.
Continuously rated.
£6, Post 30p incl. base.



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.



2000 WATT POWER CONTROL

For Power tools, Heating, Sewing Machines, Lighting, etc. £8.00, Post 27p.

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted direct case. Tested and in perfect condition £4.75. Post 25p.



FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp. 250 volt.
Price 75p. Post 15p.



UNISELECTOR SWITCHES

NEW 4 Bank 25 Way,
24V d.c. operation. £6.90, Post 30p.
6 Bank 25 Way, 24V d.c.
£7.90, Post 30p.
8 Bank 25 Way, 24V d.c. operation.
£9.50, Post 40p.



TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS
10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV, £1. Post 5p. Type SC146E 10 amp, 500 PIV, £1.30, Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30, Post 30p.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. 1/2 output of Hy-Lyght. Price £10.50, Post 50p.

HY-LYGHY STROBE MK III

For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12, Post 50p.

THE 'SUPER' HY-LYGHY KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

● Variable speed from 1-3 flash per sec.
● Reactor control circuit producing an intense white light. ONLY £20, Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector £4.75, Post 25p.

Super Hy-Lyght Kit including reflector £7, Post 60p.

7-INCH POLISHED REFLECTOR


Ideally suited for above Strobe kits. Price 55p. Post 15p.

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18, Post 50p. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

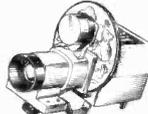Complete with oil-filled colour wheel.
100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50, Post 50p.



6 INCH COLOUR WHEEL

As used for Disco lighting effects, etc. Price £5, Post 30p.

1 R.P.M. MOTOR

220/240 volt a.c. 1 r.p.m. synchronous motor. 2 watt. A/clock. Spindle 10mm long. 3mm dia. Motor only 20mm deep. Fixing centres 44mm. Price £1.10, Post 5p. Suitable for above wheel.

BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp.

Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16, Post £1.

Spare bulb £7, Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt. Price £5.50, Post 30p. 2ft 20 watt, £4.25, Post 25p. (For use in-stan. bi-pin fittings.)

MINI. 12in 8 watt, £1.60, Post 15p. 9in 6 watt, £1.30, Post 15p. Complete ballast unit and holders for 9in and 12in tube, £1.70, Post 25p. (9in and 12in measures approx.)



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.25, Post 35p.

50 IN 1 ELECTRONIC PROJECT KIT
50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 25p.

All prices are subject to

10% VAT. (10p in the £)

To all orders add 10% VAT to total value of goods including carriage/packaging.

SERVICE TRADING CO

Superior Quality Precision Made

NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/ohm
£1.15, Post 10p.
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/ohm
£1.60, Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm
£2.35, Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9 1/4in. dia. brass bush. Ideal for above Rheostats, 22p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1)	1	2	3	4
Coil ohms				
Col. (2)	52	4-6	6M	60p
Working d.c. volts	58	5-9	6 c/o	80p
	185	8-12	6M	70p*
Col. 3	230	6-12	2 c/o	70p*
Contracts	280	8-16	2 c/o	60p*
	325	9-14	4 c/o	75p*
Col. (4)	410	10-18	4 c/o	70p*
Price	700	16-24	4M 2B	60p*
	700	16-24	4 c/o	80p*
HD =	700	15-35	2 c/o HD	70p*
Heavy duty	700	6-12	1 c/o HD	50p*
	700	20-30	6 c/o	80p
	2,500	38-45	6M	60p
	2,400	30-48	1 c/o	60p
	5,800	24-26	2 c/o	60p
	9,000	40-70	2 c/o	60p*
*Incl. Base				
All prices incl. P. & P.	15k	85-110	6M	60p

6 VOLT D.C. 1 make contacts 35p. Post 5p.

6 VOLT D.C. 2 make contacts 75p. Post 5p.

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 75p. Post 5p.

24 VOLT D.C. 3 c/o 75p. Post 5p.

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 55p. Post 5p.



100 VOLT A.C.

2 c/o seated type, octal base 11. Post 10p.

24 VOLT A.C. 3 c/o 55p. Post 5p.

CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.

HEAVY DUTY A.C. SEALED RELAYS

230/240 V. 2 c/o. 20 amp contacts. 110 Volt. 2 c/o 20 amp contacts. Either type £1.25, Post 10p.



DRY REED RELAYS

Mfg. by ERG, 12 volt d.c. encapsulated. Single c/o 65p, post paid. Two c/o 85p, post paid. STC 280 ohm coil 6/12V d.c. 3 make metal shrouded. 60p post paid. Large range of other types, details on request.


"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob 1in. Fixing hole 1/4in. ONE Bank 30p; TWO bank 40p; THREE bank 50p. Quote for quantity.



VERY SPECIAL OFFER

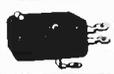Micro Switch, 5 amp c/o contacts. M.f.g. by Honeywell. NEW. Twenty for £1.50, Post 10p (min. 20).



'HONEYWELL' LEVER OPERATED MICROSWITCH

15 amps 250 volt A.C. c/o contacts. In maker's carton. PRICE: 10 for £1.90, Post 15p.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34, Post 60p. 500V, 500 megohms, £28, Post 60p.



BALANCE/LEVEL METERS

100-0-100 Micro Amp. Size 1 1/2in x 1 1/2in. Price only 70p. Post 5p.



METERS NEW! 2 1/2in. Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, both types £2.00, Post 15p. Voltmeter 0-300V A.C. £2, Post 15p.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET

LONDON WC2H 7JJ

Phone 01-437 0576

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 6p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

BOOKS AND PUBLICATIONS

DIRECT FROM MANUFACTURER—a comprehensive catalogue of U.H.F. and V.H.F./F.M. aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (P.E.), 261 Hardness Street, London, SE24.

SITUATIONS VACANT

**MEN!
£70p.w.
can be yours**

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators
Training Centre
S60, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

TECHNICIANS AND ENGINEERS FOR ST. ALBANS AND LUTON

QUALIFIED OR NOT!

OPPORTUNITIES for challenging work on testing and calibrating valve and solid-state electronic measuring equipments embracing all frequencies up to u.h.f. in Production, Service and Calibration departments.

APPLICATIONS are invited from people of all ages with experience or formal training in electronics and from Ex-Services technicians.

HIGHLY COMPETITIVE SALARIES, negotiable and backed by valuable fringe benefits. Overtime normally available.

GENEROUS RE-LOCATION EXPENSES available in most instances.

CONDITIONS excellent; free life assurance, pension schemes, canteen, social club.

37½ hour, 5-day, working week.

WRITE or phone for application forms quoting reference PE742.



MARCONI INSTRUMENTS LTD,
Longacres, St. Albans, Herts
Tel: St. Albans 59292
Luton Airport, Luton, Beds
Tel: Luton 33866

A GEC-Marconi Electronics Company



COMPUTER ENGINEERING

We require additional Electronic and Electro-Mechanical Engineers, to be involved in the maintenance of medium to large scale digital computing systems.

Training programmes will be arranged for successful applicants, 21 years of age and over, who have a good technical background to ONC/HNC level, City and Guilds or Radio/Radar experience in the Forces.

After training, and in appropriate circumstances, shift allowances will enhance the competitive basic salary, as will our twice yearly bonus. A contributory pension

plan includes generous life insurance.

Opportunities also exist for more junior trainees aged 18 and over who should have a good standard of education, an aptitude for, and an interest in, mechanics, electronics and computers.

Please write quoting Ref PE for an application form to: E. J. Young,
NCR, 1000 North Circular Road, London NW27TL

Plan your future with **NCR**

EDUCATIONAL

CITY AND GUILDS EXAMINATIONS

Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications Technicians and Radio Amateurs. Free details from: International Correspondence Schools, Dept. 730C, Intertext House, London, SW8 4UJ.

COLOUR TV SERVICING

Make the most of the current boom. Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from: International Correspondence Schools, Dept. 730C2, Intertext House, London, SW8 4UJ.

TECHNICAL TRAINING

Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self build radio kits. Free details: International Correspondence Schools, Dept. 730C3, Intertext House, London, SW8 4UJ.

FOR SALE

FIBRE OPTICS

Flexible Light Pipe for conveying lights to inaccessible positions. Fibroflex Type 1. Glass 1.14mm effective dia. PVC sheathed. 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size, 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those fixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. £1-37½ (VAT inc.), P. & P. 20p

Photographic CDS Light Cells—used (with part of original circuit free), 33p (VAT inc.), Post free.

All items are strictly C.W.O.

From: **ARVIN SERVICE COMPANY**
12 CAMBRIDGE ROAD
ST. ALBANS

MORSE MADE EASY!!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 13 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £3-30, complete course £4-50 (P.P., etc., plus 10%).

(Overseas £1 extra) details only, 4p stamp. 01-880 2898
G3HC (Box 19), 45 GREEN LANE, PURLEY, SURREY

TV LINE OUT-PUT TRANSFORMERS

Tidman Mail Order Ltd., 236 Sandycroft Road, Richmond, Surrey TW9 2EQ
01-948 3702

CATALOGUE NO. 18. Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. I. WHISTON, Dept. PB, New Mills, Stockport.

PRACTICAL ELECTRONICS. Complete from No. 1 to date (except November 1972). Offers: INGHAM, 19 Spring Lane, Sedgfield, Stockton-on-Tees, Teesside.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

RECEIVERS AND COMPONENTS

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. Extremely low leakage. All 50V d.c. Plus or minus 1% tolerance. 0.47µF. 56p; 1.0µF. 85p; 2.2µF. 80p; 4.7µF. £1-20; 6.8µF. £1-64; 10µF. £2; 15µF. £2-75. Also available ±2% and ±5%, ex. stock.

TANTALUM BEAD CAPACITORS: Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10µF at 16/20V or 25V; 15µF at 10/16V or 20V; 22µF at 6/10V or 16V; 33µF at 6V or 10V; 47µF at 3V or 6V; 100µF at 3V. All at 10p each, 10 for 95p; 50 for £4.

TRANSISTORS: BC107, BC108, BC109. All at 9p each, 6 for 51p; 12 for 96p. May be mixed for quantity price BC182 and BC212 at 10p each, AF178 at 30p each. All brand new and marked. Full spec. devices.

POPULAR DIODES: IN914, 6p each, 8 for 45p; 18 for 90p. 1N918, 8p each, 6 for 45p; 14 for 90p. 1S44, 5p each, 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 7p each, 6 for 39p; 14 for 84p. Special offer 6 of each voltage (66 zeners) £3-65.

RESISTORS: Carbon film 5%, ¼W at 40°C, ¼W at 70°C. Range from 2-2Ω to 2-2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each: 8p for 100 of any one value, 70p for 100 of any one value. Special pack—10 of each value 2-2Ω to 2-2MΩ (730 resistors) £5.

440V A.C. CAPACITORS: 0.1µF, size 1½in x ½in. 40p; 0.25µF (1½in x ½in). 55p; 0.47 and 0.5µF (1½in x ½in). 66p; 1.0µF (2in x ½in). 85p; 2.0µF (2in x ½in). £1-15.

SILICON PLASTIC RECTIFIERS 1-5A. Brand new wire-ended DO27. 100VIV at 7p each, 4 for 28p. 400VIV at 8p each; 4 for 30p; 800VIV at 11p each, 4 for 42p.

7p post and packing on all orders below £5.

Export orders—please add cost of air/sea mail.

PLEASE ADD 10% VAT TO ALL ORDERS

Send S.A.E. for lists of other ex-stock items. L.E.D.'s, disc capacitors, electrolytics, etc. Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. E2, The Maltings Station Road
Wem, Salop.
Tel. Nantwich (Cheshire) 63291

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen; £4-12 per 100; £30-25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex 0903 34897

KX2 GLASS FIBRE P.C. KIT

For transistor and integrated circuits (DIL, TO5, etc.). Track width and spacing capability down to 1mm. Full instructions and all materials supplied, including 3 pieces of 1 oz. copper board 3" x 4".

£1-65 plus 10p P. & P.

KELTRONIX LTD.

15 Barra Street, Glasgow G20 0AX

RADIO & TELEVISION AERIAL BOOSTERS £2-95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7-50. Carr. £1-50. S.A.E. for 3 leaflets. **VELCO ELECTRONICS**, Bridge St., Ramsbottom, Bury, Lancs.

TUNBRIDGE WELLS. Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6×5 0-1 Matrix, 2 for £1. 4×4½ 0-1 Matrix, 4 for £1. 12×3½ 0-15 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LP1166, £1-10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2½×2×1½ in with circuit, £1-37½ inc. P.P.

Crouzet Geared Motors, 30-60 r.p.m. New, £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

VCRI38 CRT. New, boxed, £3-30 inc. P.P.

Transformers. 7-5V + 7-5V ¼A, 66p inc. P.P. 18-0-18V, 200mA + 24V, 77p inc. P.P. 9-0-9V, 100mA, 69p inc. P.P. 20V, 1A, 88p inc. P.P.

Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, £2-20 inc. P.P.

P.C. Board. S/S, 5½×5½in, 10 for 70p inc. P.P.

Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, £2-20 inc. P.P.

Transistorised Timer. Variable delay. 110V or 250V A.C. input. With instructions. Brand new, £2 inc. P.P. Size 3"×2"×2".

10" Speaker in Cabinet, 3Ω with long lead and jack plug made by Pye. Ex-Govt., brand new £5-50 inc. P.P.

Electrolytic Capacitors, 4,000 MF, 50 WV, 4½×1½ 75p inc. PP.

Ampex Tape 7in. L.P. 1,800ft, £1-60 inc. P.P.

LARGE COMPUTER PANELS £42 18 trans, 44p. £12 44 trans, 38p. £46 18 trans, 44p (post 12p each).

M.C. METERS. THREE ASSORTED 2-3in. £1-15 (27p). 5 FIGURE RESETTABLE COUNTER 18/25V. WORKS on 12V, £2-20 (20p).

SILICON DIODES 650V ¼A, 10 on tagboard 35p (5p). NEW 800V ¼A, 6 for 25p (5p). **STABILISED MAINS POWER SUPPLY** variable output. 13-26V 4A, d.c. 10×7×7in. £8-50 (60p).

COPPER CLAD P.A.K. PANELS 6½×3½in 6 for 45p c.p. 7½×3in 25p c.p. 6 for £1-25 c.p. 8½×9in 30p c.p. 6 for £1-35 c.p. 10×9in 35p c.p. 6 for £1-45 c.p. **WIRE ENDED NEONS** 10 for 50p (8p). Bank of five with 5×C407 driver trans. 50p (8p).

COPPER CLAD FIBRE GLASS PANELS 15×3½in or 12×4½in 80p c.p. **FOUR WAY PLANO KEY SWITCH WITH INTERLOCK** 38p (7p).

SILVER MICA CAPACITORS 100 assorted 55p c.p. **POLYSTYRENE CAPACITORS** 100 assorted 75p c.p.

Your choice 2p each.

7b ASSORTED COMPONENTS £1-65 c.p.

21b ASSORTED COMPUTER PANELS £1-65 c.p.

List of computer panels, etc. 10p stamps, refunded on purchase.

J.W.B. RADIO

2 BARNFIELD CRESCENT

SALE, CHESHIRE M83 1NL

Postage in brackets. Mail order only

BRAND NEW COMPONENTS by return

Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7 10 mF, 4p; 22, 47, 82p (50V, 5p); 100, 51p (50V, 7p); 220, 60p (50V, 9p).

Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 8p.

Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02, 0.2p; 0.04, 0.05, 3p; 0.068, 0.1, 3½p.

Polystyrene 63V E12 series 10–1,000pF, 2p; 1,200–10,000pF, 3p.

Miniature highstab resistors, 5%, E12 series—Carbon Film ¼W, 1Ω–10MΩ (10% over 1 MΩ). Metal Film ¼W, 10Ω–2.2MΩ and 1W, 27Ω–10MΩ all 3p each.

Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

COMPONENTS GALORE.

500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send £1 + 10p P. & P. C.W.O. to: CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

100 RESISTORS (mixed), our choice, 40p; 50

Hi-stab resistors, our choice, 30p; 50 resistors 2W and above, our choice, 40p; 100 capacitors (mixed), our choice, 40p; 450 pF Triumper capacitors, 10p; 20 mixed valve bases, our choice, 35p; 10 B9A (Paxolin) valve bases, 40p;

10 mixed Pre-sets, our choice, 30p; 500K dual gang pots with DP switch, 20p; dual concentric pots 500K/10K log with DP switch, 25p; 10 mixed pots, our choice, 40p.

Postage and packing 15p per item. £3 or over post free. S.A.E. for list. G.R.C., 82 High Street, Winsford, Cheshire.

DESOLDERWICK

SOLDER-ABSORBING WICK

Approx. 1 cm. completely desolders a P.C.B. joints. Use with any 20-40W soldering iron. 30cm. Pack 26p inc. P. & P., etc. Multipack: Four lengths of wick in various widths: 80p inc. P. & P., etc.

ORIENTATION LIMITED
Coverack, Cornwall

MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v, 9v, £2.20
For two separate outputs, 6v + 6v., 9v + 9v, £2.75. P. & P. 20p per unit. (Please state outputs reqd.).



All units are completely isolated from mains by double wound transformer ensuring 100% safety. ALL PRICES INCLUDE VAT.
R.C.S. Products (Radio) Ltd. (Dept. P.E.)
36 Raymond Avenue, South Woodford, London E18 2HG.

5 N-CHANNEL FETS. Type 3819E (2N3819) for £1 (inc. VAT). Full spec. transistors complete with circuit details for building voltmeter, timer, ohmmeter, etc. For complete list of FETs and other transistors available send 10p P.O. **REDHAWK SALES LTD.**, 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

LADDERS

LADDERS, "Special Offer" Unvarnished Triples, 9ft 7in closed—24ft 7in extended. £18.70 delivered. **HOME SALES LADDER CENTRE (PE)2**, Haldane (North), Halesfield (1), Telford, Shropshire. Tel. 0952 586644.

MISCELLANEOUS

	BA NUTS BOLTS AND WASHERS Assorted length bolts shake-proof washers	Size	PER 100 Nuts Bolts	Wrs
		0	53p 75p	29p
		2	46p 53p	22p
		4	35p 46p	18p
		6	29p 35p	16p

	FASTENERS Box of 100 Assrt		PVC 100 GROMMETS in 1/4in or 3/16in hole. Slate size
	29p		44p

	5in PLIERS Insulated Handles
59p	59p

Post free over £2 Orders under £2 add P & P 15p All prices include VAT

SILHIL PRODUCTS

Dept PE3, 226 Mary Street, Birmingham B12 9RU
Tel. 021-440 3600

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ **POCKET-SIZED MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!) Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz (85g). Send £1.35 for your Maxi-volt now!

★ **UNIQUE TRANSMITTER/RECEIVER KIT.** No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!

★ **PSYCHEDELIC MINI-STROBE KIT.** Take a pocket-sized lightning storm to Disco's and Parties. "BRAIN-FREEZE" EM with vari-speed stop-motion flashes. Includes super case, too. Send £2.20 now!

(All prices include VAT, packing & postage)


Send remittance to:

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey (Mail order only)

Or for more details, send 15p for lists, plus free design project sheet

MORE RANGES FOR LESS MONEY!

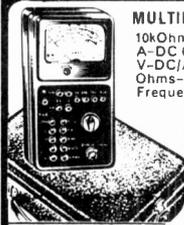

MULTIMETER AC-DC Type U-437

10kOhms/V 2.5% Precision
A-DC 0-1-1A - 5 Ranges
V-DC/AC 2.5 to 1000 V - 6 Ranges.
Ohms - 100 to 1 MegOhm - 4 Ranges.
Frequency: 45-40kHz - 2 Ranges.


TAUT SUSPENSIONS
MOVEMENT.
Complete with steel case.
Dimensions without case:
212 x 118 x 75mm

£4.95

AC/DC Multimeter type U4324

A-DC 0-0.06-3A - 6 Ranges.
A-AC 0-3-3A - 5 Ranges.
V-DC 0-6-1200 V - 9 Ranges.
V-AC 3-300 V - 8 Ranges.
Frequency: 45 to 20kHz-2 Ranges.
Resistance: 500 Ohm to 5 MOhm-5 Ranges. Decibel: -10 to +12dB - 2 Ranges. Accuracy: 2.5%.
Dimensions: 167 x 98 x 63mm.

Only £8.00

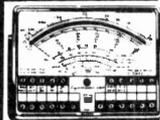

SUPRETESTER 680 RICE

10 Fields - 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC - Temperature -50C to +200C - Magnetic fields up to 15 KGauss - Phase indicator - EHT 25kV Electronic Volt Ohm-meter Transistor Diode Tester etc.
Dimensions: 128 x 95 x 32 mm - 300 grams 20kOhm/V Accuracy 1% DC Ask for free catalogue

£18.50

Add 10% VAT to all items +35p P&P
ELECTRONIC BROKERS LTD.
49-53 Pancras Road London NW1 2OB. Tel. 837 7781

fibres optic suppliers

LOW COST LED-MLED 500, MV 54
MLED 500 is in TO92 case, for PC board mounting. MV 54 is 1/4 size, 2mm, miniature. Both emit visible red light. Current requirement 20mA. 150Ω resistors available for 5V d.c. (TTL) operation.

2N5777-SILICON PHOTO DARLINGTON AMPLIFIER
Economical, high sensitivity, TO92, LIGHT DETECTOR.

	2	5	10	25
MLED500	22p	44p	£1.10	£2.20
MV54	22p	44p	£1.10	£2.09
150Ω				11p
2N5777	55p	£1.10	£2.53	£4.62

ULTRASONIC TRANSDUCERS-TRANSMITTER RECEIVER PAIR
40kHz for burglar alarm, remote control, novelties. Great value at £3.85 per trans/receiver pair.

HNCP 37-NEUTRAL CIRCULAR POLARISER

Reduce glare on CRT's, meters, displays, panels. 50mm x 50mm (2in), 66p; 75mm x 75mm, £1.21; 150mm x 150mm, £4.40.

CROFON 1610-64 FILAMENT LIGHT CONDUIT
1.8mm active dia., 3.3mm o/d. Simply cut to length and conduct light where required. For displays, internal illumination, multiple point lighting: 1 metre, £1.32; 2m, £2.64; 5m, £5.50; 10m, £10.45.

FP40-PLASTIC OPTICAL MONO-FIBRE, 1mm DIAMETER
Single strand unjacketed light guide, simple to use. 5 metres, £1.10; 10m, £1.98; 25m, £3.85. FP20 (0.5mm) and FP60 (1.5mm) also available.

MARE'S TAILS FOR DECORATIVE DISPLAYS
7,000 fibres, professionally finished, beautiful. Add lamp, stand, cover to make a Fibre Optic Lamp. Eye catching in boardroom, hall or foyer, £11.00 each.

All prices shown include P. & P., VAT. C.W.O. please. For full information on our complete range, send 9in x 6in S.A.E. to **FIBRE OPTIC SUPPLIERS (PE)**
P.O. Box 702 London W10 6SL

A
L
S

A.L.S. PRESENTS OUR

E.C. 100 Watt Hi-Fi Amplifier
ready drilled P.C.B. with full instructions only £2 plus 10p post.

We also supply:
Service Sheets, Manuals, Books, etc.
See our main advert in 'TELEVISION' or send S.A.E. for details.

10 DRYDEN CAMBERS, 119 OXFORD ST., LONDON W1R 1PA (B).

BUILD THE TREASURE TRACER

MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weights only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send s.a.e. for leaflet

Complete kit: 35p **£9.80** Built, tested and guaranteed: Post: 35p **£13.75**

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order only)

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76½p)

SEND 5" x 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	3/16 Reel
10-14	£1.27	72p
15-19	£1.27	72p
20-24	£1.30	75p
25-29	£1.38	83p
30-34	£1.43	88p
35-40	£1.54	91p

Please add 10% to all above prices to cover VAT
The above prices cover P. & P. in U.K. Supplied by **INDUSTRIAL SUPPLIES**
102 Farswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

GLASS FIBRE P.C. BOARD—large supplies available. 1/4 in single sided one ounce copper, 2p per 3 sq in (under 1ft); 75p per sq ft (over 1ft). 1/2 in double sided one ounce copper, 1p per sq in (under 1ft); £1 per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. **SOLID STATE LIGHTING**, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

HARDWARE SUPPLIES—Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers, etc., Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes, etc., 7p for list. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwks., CV37 9JP.

UFO's. Wave Prediction Chart, 49p. TV Notes for Detection, 2 Optical Circuits, 55p. UFO Map, 42p. Daily Flight Pattern, 42p. Transistor Optical Circuit, 66p. Optical/Radiation Detector Circuit, 44p. Microdetector Circuits, with Memory, LSI, 75p. R. & E., Highlands, Needham, Suffolk.

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.


METER REPAIRS. Ammeters, Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. **METER REPAIRS**, 39 Chesholm Rd., London N16 0DS.

HOLIDAY FOR BOYS. 14/16 years, August 1974. Tuition and practical work in electronics, radio production and tape recording, engineering (Karting) and photography. Eleven days in Norfolk, £17.50. Write for free brochure: **INTER-SCHOOL CHRISTIAN FELLOWSHIP**, c/o 1 Hubbard Road, London, SE27 9PJ.

RAYMER ELECTRONICS


RE 500

Advanced integrated Hi-Fi Amplifier only requires connection to mains speaker and input.
 Specifications load imp 4-16 ohm.
 Output: 5 watts.
 Frequency response 20 Hz to 35kHz ± 3 dB
 Total distortion less than 1%. I/P Imp 100k ohm Nom. £8.30. Post free.
 Size 140 x 80 x 45mm.

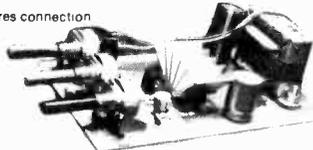

MICROCHIP I.C.

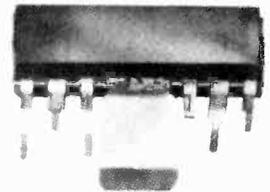5 watts RMS
 A general purpose Audio i.c. for the constructor capable of 5 watts RMS O/P at less than 1% total distortion, forms an ideal basis for an excellent Hi-Fi system.
 Free Data I.C. £1.50.
 Data. Printed Circuit Board. 75p.
 Post paid.



COMPLETE QUADRAPHONIC AMPLIFIER KIT: RE 4K

A Hi-Fi kit comprising CBS SQ decoder, preamplifier and four channel main amplifier. All modules built and tested.
 Specifications
 Similar to the Quadrix system (see below) but with four channel main amplifier giving 40 watts total peak power.
 This is an opportunity to experience quadraphonic sound at the very minimum of cost.

RE QUADRIX

This is a high quality CBS specification SQ decoder with Hi-Fi stereo amplifier. Designed to allow the conversion of any stereo system to full quadraphonic performance with minimum cost. Extraordinary new presence and reality of sound. More than 20 Watts total peak power.

Specifications

Decoder

I/P impedance 40k Ω
 O/P impedance <300 Ω
 Nominal I/P 100mV RMS
 Front separation <60dB
 Rear separation <20dB

Amplifier

Power O/P 5W RMS per channel (simultaneously)
 Distortion at full O/P less than 1%
 Sensitivity for full O/P 100mV
 Active tone control Bass ± 10 dB Treble ± 12 dB at 100Hz-10kHz
 Load impedance 8-16 ohms

Special Offer SQ records (full quadraphonic sound) available direct. Comprehensive list free on request.

GUARANTEE

ALL PRODUCTS ARE GUARANTEED AGAINST FAILURE FOR A PERIOD OF 12 MONTHS AND WILL BE SERVICED FREE OF CHARGE IF PURCHASED DIRECT AND REFUNDED TO US FOR REPAIR

NAME
 ADDRESS
 PLEASE SEND

(enclose P.O.cheque/M.O.)
RAYMER ELECTRONICS LTD.
 Stanley Road, Cambridge CB5 8LB, England.
 (0223) 54414. Reg. No. 1021205



(Power Amp only shown)

Power Supply Extra (RE 35 psu)

£30.00. Post free



£49.00. Post free

PLEASE ADD 10% FOR V.A.T.

Mullard Components

CARBON FILM RESISTORS

High stability, very low noise. E12 series 4R7-1M. Prices are per ohmic value. Ignore fractions.

+	100+	1,000+
0.33W 5%	0.7p	0.7p
		0.6p

POLYESTER CAPACITORS

C280 series. 250V PC mounting: 0.01, 0.015, 0.022, 2p; 0.033, 0.047, 0.068, 0.1, 3p; 0.15, 0.22, 4p; 0.33, 5p; 0.47, 6p; 0.68, 8p; 1.0, 10p; 1.5, 14p; 2.2, 16p.

All prices include VAT. Please add 8p postage and packing on orders below £2. Fast service. Cash with order only. Send 5p stamp for our comprehensive catalogue.

C. N. STEVENSON
 304 Avery Hill Road
 London SE9 2JN

Please mention

PRACTICAL ELECTRONICS
 when replying to
ADVERTISEMENTS

P.E. SOUND SYNTHESISER

Complete kits or individual components. Full building instructions, circuits, etc. for this exciting project. £2.50.

741C mini DIL 37p; 748CS mini DIL 48p.
4-Quadrant Multipliers
 SG3402N £1.74; SG3402T £1.74; SG1495D £2.90.
Electronic Attenuator
 MFC6040 £1.
Noise Diodes
 Z1J 50p; Z1M Wideband £1.20.
Zener Diodes BZY88 series
 3.3V; 3.6V; 3.9V; 5.1V; 6.8V; 7.5V; 11V; 12V.
 All at 22p each.
Voltage Regulators
 MVR15-15V 450mA—TO3 £1.80.
 μ A723 (Equiv.) adjustable 8-37V—TO5 outline £1.80. μ A7815-15V—TO66 outline £2.20.
Bridge Rectifiers
 Rec. 41a, 100 PIV 2.2A £1.20.
 Rec. 70, 400 PIV 800 mA 40p. ML3046P 75p.
Transistors/Diodes
 BC184; BC182; BC213 all at 9p each.
 BC209C npn 150mW 9p; BC204 pnp 150mW 9p;
 AC176 npn Ger 24p; 2N2219 npn 800mW 22p;
 2N2905 pnp 800mW 27p; 2N3819 f.e.t. 46p;
 1N914 5p; 1SJ50 12p; 1GP7 10p.
Hook-up Wire
 1m each, 20 diff. colours 60p.
 1m each, 36 diff. colours £1.07.
 Supplied in longer lengths by request.
Screened Cable. Low noise 7/02 Cap.92pF/m.
 Nom. imp. 50 ohm. 15p/metre.
Lacing Cord
 Rayon cored black p.v.c. 2p/m.
McMurdo's. New stocks—Low prices
 8 pole plug RP8 30p; 8 pole skt. RS8 48p.
 2mm plugs/skts. 7.5p/35p for 5.
 Black, blue, red, green, yellow, white.
Mains Transformers
Miniature Type
 Secs. 0-12V, 0-12V @ 3VA each £1.38.
 Secs. 0-20V, 0-20V @ 3VA sct. £1.38.
Regulator Type 634
 Sec. 17.5V @ 1.6A £2.15.
MT102 AT (Douglas)
 Sec. 0-19, 25, 33, 40, 50 @ 500mA £2.35.

Potentiometers

Min. Moulded Carbon. Lin. Tracks:
 5k Ω ; 10k Ω ; 25k Ω ; 50k Ω ; 100k Ω ; 1M Ω 18p;
 Log. Tracks. 10k Ω 18p.

Ganged

5k Ω log; 10k Ω ; 100k Ω lin. 64p.
Carbon Presets. Horiz. Type.
 10k Ω ; 47k Ω ; 100k Ω ; 470k Ω 10p.
Cermet Presets. Horiz. Type
 100; 500; 1k Ω ; 10k Ω ; 50k Ω ; 100k Ω 35p.
15 Turn Cermet Trimmers
 10k Ω £1.20.

Semi-precision Wirewound Pot.
 1k Ω 52p.

Precision 10 Turn Miniature
 10k Ω (Spectrol) 23mm dia. \times 19mm £3; 1k Ω
 (R.5) 13mm dia. \times 40mm £3.

10 Turn Counting Dial (Amphenol) £2.

Rotary Switches

2P 6W; 3P 4W; 4P 3W; 6P 2W 37p.

Min. push to make buttons 30p.

Sub-miniature toggles

S.P.S.T. 75p; D.P.D.T. £1.

Stripboards. Cu. strips drilled 0.1" crs. 115 \times 34

ways. 95p.

Hutchinson Tone Control. 3" epoxy glass,

roller rinsed PCB. 95p.

Resistors

2% metal oxide Mullard/Electrosil 16p for 5.

5% carbon film Mullard/Erie 9p for 5.

Capacitors

Tantalum bead, Silver Mica, Polyester, Polystyrene, Ceramic, Electrolytic.

4ip stamp brings latest lists.



Simply send exact details of name and number copied from the face of your Access Card and leave the rest to us.

EATON AUDIO P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.V.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2.
 Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.

P.E. RONDO

FULL SPECIFICATION KITS

- * EDGE CONNECTOR £1. Post Free + 10p VAT
 - * QUAD SEL. SWITCH £1-30. Post Free + 13p VAT
 - * CBS-SQ MATRIX DECODER £8. Post Free + 80p VAT.
 - READY BUILT £11. Post Free + £1 10 VAT
 - * PRE-AMP BOARD, COMPLETE £3. Post Free + 30p VAT
 - * MASTER VOLT/TONE/BAL. BD. £8-50. Post Free + 85p VAT
 - * POWER AMP BOARD HEATSINK. Two reqd for Rondo £7-50. Post Free + 75p VAT
 - * POWER SUPPLY BOARD £5. Post Free + 50p VAT
 - * MAIN SMOOTHING CAPS £1-50 per pair. Post Free + 15p VAT
 - * MAINS TRANSFORMER £8-25. Post Free + 62p VAT
 - * PUNCHED CHASSIS £3-25. Post Free + 32p VAT
 - * RONDO CASE £1-75. Post Free + 17p VAT
 - * HARDWARE PACK £2. Post Free + 20p VAT
 - * CONTROL SECTION FASCIA £3-50. Post Free + 35p VAT
 - * STEREO DECODER KIT £3-88. Post Free + 39p VAT
 - * STEREO DECODER BUILT AND TESTED £4-98. Post Free + 49p VAT
 - * GOLDRING G101/2 TURNABLE Less Cartridge £23-90. Post Free + £2 39 VAT
 - * DEUTSCHE ELAC CARTRIDGE STS 144/17 £8-90. Post Free + 69p VAT
 - * READY BUILT LOUDSPEAKERS (Teak or white veneer) per pair £42. Post £2 + £4 40 VAT
 - * COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSS OVER, WADDING, ETC. (Four reqd for Rondo) £18-50 each Post 50p + £1 90 VAT
 - * COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSS OVER, WADDING, ETC. per pair £35-50. Post £1 + £3 65 VAT
 - * COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSS OVER, WADDING, ETC. per four £82. Post £2 + £6 40 VAT
 - * BASS DRIVE UNITS (2 per cabinet) £3-95 each. Post Free + 39p VAT
 - * TWEETERS (2 per cabinet) £1-20 each. Post Free + 12p VAT
 - * CROSS OVER UNIT (1 per cabinet) £2-50 each. Post Free + 25p VAT
 - * WRAP ROUND CABINET (Teak or white veneer) £9-50 each. Post 50p + £1 VAT
- ANCILLARY KITS LIST NOW AVAILABLE

STUDIO ELECTRONICS

P.O. BOX No. 18. HARLOW. ESSEX CM18 6SH
Telephone: Harlow (0279) 25457

ORDER—PLEASE SEND

EDGE CONNECTOR
QUAD SEL SWITCH
CBS-SQ DEC BUILT
PRE-AMP
MASTER VOL
POWER AMPS
POWER SUPPLY
CAPACITORS
TRANSFORMER
CHASSIS
RONDO CASE
HARDWARE
CONTROL FASCIA
STEREO DECODER KIT
STEREO DECODER BUILT
BUILT SPEAKER Teak ()
BUILT SPEAKER White ()
BASS DRIVE UNITS ()
TWEETERS ()
CROSS OVER KIT ()
SPEAKER CABINET KIT White ()
SPEAKER CABINET KIT Teak ()
COMPLETE SPEAKER KIT White ()
COMPLETE SPEAKER KIT Teak ()
GOLDRING G101 TURNABLE Less cart
ELAC 144 CARTRIDGE

Please insert quantity in open brackets

ENCLOSED £ CHEQUE/P.O.
NAME
ADDRESS

PE/2/4

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression. 600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO H.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

HI-FI YEAR BOOK 1974

by Colin Sproxtton Price £1.75

R.S.G.B. AMATEUR RADIO CALL BOOK by R.S.G.B. Price 75p.

FET APPLICATIONS HANDBOOK by J. Eimbinder. Price £2.

IMPROVING YOUR HI-FI by John Earl. Price £3-20.

HOW TO SOLVE SOLID-STATE CIRCUIT TROUBLES by W. Lemons. Price £1-90.

SOLID STATE HOBBY CIRCUITS MANUAL by R.C.A. Price £1-20.

UNDERSTANDING SOLID STATE ELECTRONICS by Texas Instruments. Price £1-40.

THE HOUSEHOLDER'S ELECTRICAL GUIDE by G. Burdett. Price £1-10.

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price £1-95.

HOW TO BUILD SOLID STATE AUDIO CIRCUITS by M. Horowitz. Price £1-90.

THE RADIO AMATEUR'S VHF MANUAL by A.R.R.L. Price £1-75.

BASIC TELEVISION IN THREE PARTS by Common Core. Price £3-75.

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

- PARTRIDGE MAINS ISOLATION TRANSFORMER. Pri: 105-250V, 5V steps, Sec: 240V, 13 amps. 8½, carr. pack. £1-50.
- PARMEKO MAINS TRANSFORMER isolated windings. Pri: 200-250V, Sec: 90-120V at 4-5 amp. £4, carr. pack. 75p.
- GARDNER'S POTTED TRANSFORMER, 0-250V. Pri: 200-250V, Sec. Input: 18V 500m/n, 50V 150m/a, 6V 250m/a output. Size: 3in x 2½in x 2½in, £1, p.p. 28p. Ex equip. tested.
- RIPLEY MAINS TRANSFORMER, Pri: 110V-240V, Sec: 12-5V: 0:12-5V 750m/A 7V:0:7 V1A, £1, p.p. 26p.
- MAINS TRANSFORMER, Pri: 100-250V, Sec: 22:0:22 200m/A, 22:0:22 100m/A 0:24V 20m/A, 80p, p.p. 25p.
- MAINS TRANSFORMER, Pri: 230V, Sec: 14V, 120 amps. £15, p.p. £1-50.
- MAINS TRANSFORMER, Pri: 100-240V a.c. 36-5-0-36-5V, 27 m/A, 0-21-5, 260 m/A, 80p, p.p. 25p.
- TRANSISTOR OUTPUT TRANSFORMER, Ratio 8:1, 120mH. Centre tap 2 watts. output, 80p, p.p. 8p.
- SMOOTHING CHOKE, 11MH, 1½in x 1½in x 1½in, 80p, p.p. 8p.
- FINNED ALUMINIUM HEATSINK, 4½in x 6in x 1in, 2 x 2N3055, £1, p.p. 13p.
- GOODMANS 6in SPEAKERS 3 Ω £1-50, p.p. 28p.
- FINNED ALUMINIUM HEATSINK, 9in x 8in x 1½in. In C.: 4 x 2N3055, £2, p.p. 29p.
- GARRARD MAG. TAPE DECKS: 1½i.p.a., 50V, solenoid operated, brackets, etc. Mains voltage motors £7-50 each, p.p. 60p.
- MOTEK 3 speed tape deck (1½in x 3½in x 7½in) reel to reel 7in mains operated, £7-50, p.p. 63p.
- 10 REED SWITCHES operated by push buttons and magnets, 50p, p.p. 25p.
- COMPONENT PANEL, 6 scr's (300V, 1-6A) 6 cond., 12 resistors, 6 diodes, 45p, p.p. 8p.
- COMPONENT PANEL, 6 scr's (200V 4 amps), 6 condensers, 12 resistors, 30p, p.p. 8p.
- COMPONENT PANEL (9 ICs FJH131) (1-CA300), 1 crystal 7-68kHz + various other components, £1, p.p. 8p.
- COMPONENT PANEL, 2 x 500mF 50V, 3 x 100mF 25V, cap. 1 x 2N2612, 2 x 2N404, 3 diodes plus various other components, 10p, p.p. 9p.
- COMPONENT PANEL, 24 OA81 diodes, 10p, p.p. 8p.
- VEEDER ROOT ELECTRICAL IMPULSE COUNTER NON-RESETTING, A.C. 200-250V, £1-10, p.p. 13p.
- GEC MAINS CIRCUIT BREAKERS, 2 amp or 5 amp, £1 each, p.p. 14p.
- LEVER ACTION P.O. 1000 TYPE SWITCHES
Lock 4-pole changeover, 15p, p.p. 4p. Ex equip.
Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.
- MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500µF 64V, 7,100µF 40V, 50p each, 20,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 21p.
- MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, 76p, p.p. 10p.
- BELLING LEE 1-5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.
- RUBBER 3 PIN 6 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.
- SOLENOIDS 12 VOLT FULL ACTION
2in x 1in x ½in, 40p, p.p. 8p.
- SOLENOIDS 12-24V d.c. pull action 1½in x 1½in x 1½in, 40p, p.p. 8p.
- SOLENOIDS 240V a.c. pull action 2½in x 1½in x 1½in, 50p, p.p. 9p.
- SANGAMO WESTON TIME LAPPED METER
Mains operated, 1½in x 1½in x 2in, £1-50 p.p. 7p.
- SCR WITH HEAT SINK (600V 15 amp), 50p, p.p. 5p.
- OMRON MK2 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, 70p, p.p. 5p.
- STC VARLEY, miniature relays 700 Ω, 17-5-37V, perspex cover, 4 pole changeover, 40p, p.p. 5p.
- POTTER BRUMFIELD 12V d.c. 3 pole changeover with base, contacts rated 7A d.c., £1, p.p. 10p.
- I.T.T. LOW PROFILE RELAYS, 4 pole c/overs, 500 Ω 12-18V, 75p, p.p. 5p.
- MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts, 50p, p.p. 7p.
- TELESCOPIC AERIALS
Clamped 7in chord, 28in extended, 6 section ball jointed base, 23p, p.p. 5p new.
- PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 reed relay: 1 AZ 229 zener ass. capacitor/resistors. Power supply 22V, 250 m/A d.c. Output 240V a.c., £1, p.p. 25p. Ex equip.
- WIRING CABLE
Size-1-020. Various colours. 350yds, 60p, p.p. 28p.
- TAPE POSITION INDICATOR
Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED
3 Shenley Road
Borehamwood, Herts.
Tel. 01-953 6009



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5
Savbit alloy
18 swg. 20p
(illustrated).
Size 19A
60/40 alloy
18 swg. 22p
Size 15
60/40 alloy
22 swg. 25p

IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges. 30p



Size 12 REEL
for Service Engineers and Electricians.
18 swg
Savbit alloy 95p



BIB WIRE STRIPPER AND CUTTER

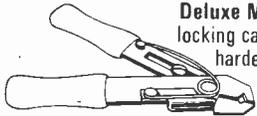

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjustable to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to: **Multicore Solders Ltd.**, Hemel Hempstead, Hertfordshire HP2 7EP

TRANSISTORS

AC126 14p	AF180 45p	BC158 14p	BF180 32p	BFY51 21p
AC127 16p	AF181 45p	BC159 14p	BF181 32p	2N3053 23p
AC128 14p	AF239 44p	BC177 20p	BF184 35p	2N3054 37p
AC141K 24p	BC107 12p	BC183L 14p	BF185 35p	2N3055 60p
AC142K 24p	BC108 10p	BC184L 12p	BF186 45p	TIP29 66p
AC176 20p	BC109 12p	BC187 22p	BF194 15p	TIP30 75p
AC187 18p	BC113 25p	BC294 16p	BF195 15p	TIS91 48p
AC187K 24p	BC114 30p	BC460 50p	BF196 15p	
AC188K 24p	BC115 20p	BC460 60p	BF197 15p	
AD142 45p	BC116 20p	BD124 80p	BF200 32p	
AD149 45p	BC117 15p	BD131 60p	BF258 40p	
AD161 34p	BC125 14p	BD132 60p	BF259 40p	
AD162 34p	BC142 25p	BD139 63p	BF337 23p	
AF115 21p	BC143 13p	BDX32 £2.00	BFT42 44p	
AF116 21p	BC147 15p	BF115 25p	BFT43 44p	OA91 7p
AF117 21p	BC148 13p	BF121 35p	CA202 9p	OA202 9p
AF118 49p	BC149 13p	BF158 19p	BFX84 30p	IN4148 4p
AF139 40p	BC154 20p	BF167 20p	BFX89 67p	BY127 11p
AF178 45p	BC157 14p	BF179 39p	BFY50 21p	IN4006 8p

RESISTORS METAL FILM

5% TOL.
1W, 1/2W, 1/4W, E12 values to 2.7M all 1p each.
1W to 10M E12 values 3p each.
2W to 10M E12 values 4p each.
5W wire wound, 10W wire wound 8p and 9p each. See Cat. for values.

POTENTIOMETERS-CARBON TRACK

5K, 10K, 25K, 50K, 100K, 250K, 500K 4M
Log or lin less switch 11p
Log or lin with switch 23p
Dual log less switch 250K, 500K, 1M, 2M, only 39p
Dual lin less switch 5K, 10K, 25K, 50K, 100K, only 39p
Dual log with switch 10K, 100K, 250K, 500K, 1M only 55p

JACK PLUGS AND SOCKETS

Standard insulated 11p; Standard screened 18p; Stereo insulated 22p; Stereo screened 30p; 3.5mm insulated 8p; 3.5mm screened 12p; Standard socket switched 17p; Stereo socket switched 21p; 3.5mm socket switched 6p; Standard line socket 15p; Stereo line socket 22p; 3.5mm line socket 10p.

PHONO-D.I.N. PLUGS AND SOCKETS

Phono plug insulated 7p; Phono plug screened 11p; Phono line socket screened 12p; Metal coax plug 8p; 2, 3, 5 pin 180°, 240°, D.I.N. plugs 12p; 4, 6, 7 pin plugs 15p; 2, 3, 5 pin 180° line sockets 13p; 2, 3, 5 pin 180° chassis sockets 7p.

CABLES AND SCREENED WIRES


Min. mike cable single 7p/metre; Min. twin mike cable 11p/metre; Pick up wire single 7p/metre; Pick up wire twin 11p/metre; Stereo screened twin 10p/metre; 4 core individually screened 14p/metre; Speaker wire twin coded 6p/metre.

E. A. HALL (ELECTRONICS)

The Manse, Little Brington, Northampton NN7 4HX
Mail Order Only. C.W.O. Postage and packing 10p per order. Detailed Catalogue 6p. Please add V.A.T. on total order incl. postage and packing. Many other items in our catalogue.

BI-PRE-PAK

STEREO DECODER £4.95

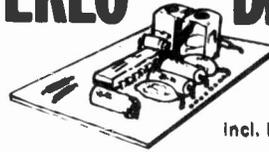


Incl. P. & P. and VAT

Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tell tale light can be connected. The unit is a small printed circuit, no further alignment necessary. L.E.D. is recommended as the indicating light, suitable device available from us at 36p. Instructions included.


3 W_{r.m.s.} I.C. AMP only £1.65

Incl. P. & P. and V.A.T. Order Code I.C.A.1.

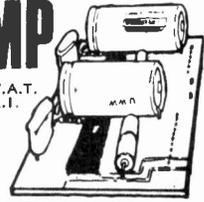On P.C. Board with all components or 2 on one board for £2.86. Order Code I.C.A.1/S. These amps are supplied with a free booklet on connecting up, specifications and easy-to-build projects using the I.C.A.1



5W & 10W AMPS

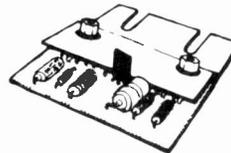

5W ONLY £1.98
10W ONLY £2.49

Incl. P. & P. and V.A.T.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/2 in x 1 1/2 in. The 5W Amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the U.K. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2in x 3in available in stereo only, will fit 0-15 edge connector.
Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain or ceramic pick-up cartridges. £1.21
Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. £1.69
Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. £1.21
Instruction leaflet supplied with all units. Post and packing and V.A.T. included in prices.

I enclose £.....for
.....8 Tracks/.....3W Amps/.....5W Amps
.....10W Amps/.....Stereo Pre-Amps 1
.....Stereo Pre-Amps 2.....Stereo Tone Controls
(Please insert quantities and delete those not applicable).

Name


Address

BI-PRE-PAK

Dept. A, 222/224 West Road, Westcliff-on-Sea, Essex SS0 9DF. Telephone: Southend (0702) 46344.

Co. Regn. No. 820919

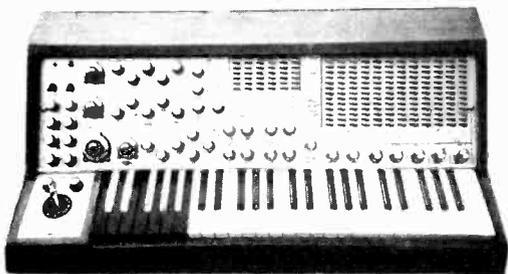BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. **OFT-1** chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.1. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

**PROFESSIONAL MODULES
CASH SAVINGS**

by buying modules and parts in bulk!
All modules are available separately:
Ring Modulator RM2, £8. Voltage-controlled Oscillator VC01, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5.50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

CASED AMPLIFIERS



Polished wooden cabinet 14 1/2 x 9in containing a sensitive (20uV) 4 valve amplifier with tone and volume controls. 3W output to 7 x 4in 3Ω speaker. Also included is a non-standard tape deck with solenoid operation. Supplied in good working condition complete with circuit diagram. Standard mains operation. Only £3 (£1 up to 200 miles, £1.25 over). Suitable cassette £1. Spare head 30p; Amplifier chassis only, complete and tested £1.65 (40p). 7 x 4in speaker 40p (12p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, crystals, pots, switches, computer panels with transistors and loads of odds and ends. Still only £1.65 (40p).

COMPUTER PANELS

31b assorted panels £1 (30p); 71b £2 (40p); 561b £13 (c/pd). 12 top quality panels containing power transistors, IC's, trim pots, etc. £2 (30p); 100 boards £12 (£1). Pack containing at least 500 components including at least 50 transistors 60p (20p).

ADD 10% TO TOTAL FOR VAT
Carr. in brackets; small parts 5p

GREENWELD (PE9)

24 Goodhart Way, West Wickham, Kent. SHOPS AT: 21 Depford Broadway SE8. (Tel. 01-692 2009) and 38 Lower Addiscombe Road, Croydon.

NEW COMPONENTS
SCR's: 200V 5A 40p; 400V 5A 60p; BYZ10 1200V 6A 40p; OC16 20p; OC45 8p; OC71 8p; OC140 25p; OC170 15p; OC171 15p; BFY18 12p; BCY72 8p; 2N3055 35p; XC121 5p; BC107 8p; 2N3708 8p; 741C TO99 or 8 pin DIL 32p; 100V 8A diodes 20p; 3.9V or 27V 400mW zeners 7p; 22V 1W 10p.

BULK COMPONENTS
500 assorted resistors £1 (20p); 300 capacitors, all types £1 (30p); 25 assorted 10X crystals 75p (30p); 40 assorted pots £1 (30p).

EX-COMPUTER EQUIPMENT
1200ft 1/2in tape on 7in NAB spool 68p (30p); 1800ft 1/2in tape on 10 1/2in NAB spool in case 68p (40p); Screw top electrolytic capacitors: 20,000uF 50V 60p (25p); 46,500uF 25V 60p (25p); 35,000uF 15V 40p (20p); 40,000uF 10V 40p (20p); 20,000uF 30V 40p (20p); 25,000uF 25V 40p (20p).

Fans: 230V 50Hz 6 1/2in dia. blades 2,800 r.p.m. complete with grill and mounting plate £2.50 (40p). Heavy duty heat sinks 6 x 5 x 3in with 2 power transistors 80p (30p). 1/2" tape deck, 16 track £30.

TEST GEAR
TF144G sig. gen. .85kHz to 25MHz, 1uV to 1V output £16. BFO No. 8 Audio oscillator, 50Hz to 20kHz 10 or 600 output, metered. £9. Oscilloscopes in stock, ring for details.

ODD UNITS
Useful module containing OC35, 2 OC44, GET103, R's, C's, etc. 40p (10p). Cat's whisker and crystal 15p; Unit with 2 modern c/o lever switches, 3 trim pots, etc. 60p (10p).

BAKER 12" MAJOR £9-90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £12.50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8.80	Superb 12 in. 20W	£16.50	New Group 50/12	
Major 12 in. 20W	£9.90	Group 25 12 in. 25W	£6.80	12 in. 50W	
Deluxe 12 in. 15W	£11.00	Group 35 12 in. 35W	£9.90	30-16000 cps.	£17-60

BAKER LOUSPEAKER CO., BENSAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684-1665
PRICES INCLUDE VAT. HI-FI ENCLOSURE PLANS 42p

F.M.Ø. VARICAP TUNER

LP1185/86	£9.00/pair
MC1310P	£3.15 each
MFC4060 (late deliveries)	78p
P.C. BOARDS	£1.87
READY BUILT BOARDS	£23.00
COMPLETE TUNERS IN CABINETS	£33.00

NEW! LP1400 DECODER MODULES
—LIMITED STOCKS £4.96

Prices include V.A.T. P. & P. 25p.

B. & B. ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK, NOTTS.
Telephone: NEWARK 6895

FREE!

Over 150 ways to engineer a better future



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course". - Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". - Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE 33, Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers— A.M.S.E. (Mech.) Institute of Engineers & Technicians (A.M.I.E.) CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineers— Designers (A.M.I.E.D.) General Draughtsmanship Elec. Draughtsmanship Architectural Draughtsmanship Technical Drawing	<input type="checkbox"/> A.R.T. Clerk of Works Construction Surveyors Institute— I.C.S.I. CITY & GUILDS General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities, Estimates Hydraulics Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers— A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS Radio, TV Electronics CITY & GUILDS Telecons. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Accnts. Computer Programming Works Mgmt. Work Study Gen. Production Eng. Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I.I. CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage Mgmt. ARB Aero Engineering Certs. Gen. Aero Eng.	<input type="checkbox"/> <i>Supplementary courses for Nat. Certificates.</i>
G.C.E. — choose from '58 'O' & 'A' level subjects.		
<i>Coaching for many exams, including C & G</i>		

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE 33 Aldermaston Court, Reading RG7 4PF QN BPE 33

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____
AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/Sia) Ltd.; South Africa—Central News Agency Ltd. Publishers' Subscription Rate (including postage): For one year to any part of the world £2.65. Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

DONT RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES
 Order your latest Henry's Catalogue Price 55p post paid
 complete with Discount Vouchers



You pay less
VAT with Henry's
 Low Prices

Now built and used by thousands of satisfied customers.
FEATURES: slim design, overall size in cabinet 15in x 23in x 6in
 6-IC's, 10 transistors, stabilisers, Gardners low field transformer, Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form.
HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES. On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc. Constructional details Ref. No. 21, 30p. Distributed by Henry's throughout UK.

BUILD THE TEXAN

20 + 20 WATT IC STEREO AMPLIFIER

As featured by Practical Wireless 1972



FREE Teak cabinet with complete kit.
KIT £28.50 (+ VAT + 50p carr/packing) or
PRICE £35.00 (+ VAT + 50p carr/packing) as illustrated

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



- DISCO MINI:** A complete portable disco, fitted mixer/preamp, 2 decks all facilities. As above but with Slider Controls £98.50
- 100 watt amplifier for above £118.50
- 100 watt amplifier for above £42.50
- SDLS100:** 100 watt mixer/amplifier with slider controls £69.00
- R50:** 50 watt mixer/amplifier £49.50
- R100:** 100 watt mixer/amplifier £57.50
- DISCO AMP:** 100 watt mixer/amplifier chassis unit £73.00
- DISCO MIXER/PREAMPLIFIERS (O/P for up to 6-100 watt amplifiers):**
- SDL1** (rotary controls): £49.50
- SDL11** (slider controls): £58.50
- DISCO VOX** (slider controls): The complete disco preamp £72.00
- DJ100:** 100 watt power amplifier for above £49.50
- DJ30L:** 3 channel 3kW sound to light £36.00
- DJ40L:** as 30L plus built-in microphone £47.50
- DIMAMATIC:** 1kW adjustable speed auto dimmer £25.00
- Carlsbro Reverberation Unit** £44.00
- SCENE STROBE** £19.00
- ROAD STROBE** £25.00
- SUPER STROBE** £45.00
- Disco anti-feedback microphone** £11.95
- Colt 150 watt liquid wheel projector** £22.50
- 150 watt QL liquid wheel projector** £50.00
- 150 watt QL cassette wheel projector** £50.00
- Spare Effects and Liquid cassettes, large range of patterns:** £6.00
- Mini spot bank fitted 3 lamps** £12.95
- Auto Trillite (mini with flashers)** £17.00
- Bubblemaster with 1 gal. liquid** £41.15
- MIXERS/MICS/SPEAKERS/LIGHTING**
- U.K.'s largest range of Disco lighting 6in liquid wheels £5.00
- FREE STOCK LIST Ref. No. 18 ON REQUEST**
- AKG/RESLO/DJ/CARLSBRO/EAGLE CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURNTABLES, PUBLIC ADDRESS COMPONENTS, MICS., STANDS, MIXERS, CABINETS**



All prices carr. paid (UK) (VAT EXTRA). Barclaycard/Access call, write or phone your order 01-723 6963—easy terms for callers.

TEXAN STEREO SYSTEM

PLUS Price Savings



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems, size 12x12x10in and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk.III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

- SYSTEM 25** (list approx. £109) £79.50
 - SYSTEM 76** (list approx. £117) £89.50
- (plus 10% VAT and plus £1.45 carr/packing).

BARCLAYCARD/ACCESS

- Call, write or phone your order 01-402 4736. EASY TERMS FOR CALLERS
- Stereo Preamplifier** £11.95
 - Audio Filter Unit** £6.95
 - Z40 15 watt Amplifier** £5.45
 - Z60 25 watt Amplifier** £6.95
 - PZ6 Mod. for 1 on 2 Z40** £4.98
 - PZ Mod. (S Tab) 1 on 2 Z40** £7.98
 - PZ8 Mod. (S Tab) 1 on 2 Z60** £7.98
 - TRANSFORMER FOR PZ8** £2.95
 - NEW FM TUNER** £11.95
 - STEREO DECODER** £7.45
- All items post paid—Best price on request.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise, IF stages, LED indicators, Tuning meter, AFC. Easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size: 8in x 23in x 6in. Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5, 30p.) Henry's are sole distributors UK and Europe.



Kit Price £21.00 (+ VAT)
 or built and tested £24.95 (+ VAT)

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN 1/2 REC. PRICES. COMPLETE WITH LIBRARY CASES.

	3 for	6 for	10 for	25 for
C60	£1.00	£1.80	£2.80	£6.75
C90	£1.33	£2.57	£4.20	£10.25
C120	£1.62	£3.15	£5.00	£12.25



Quantity and trade enquiries invited.
LEARN A LANGUAGE—complete with phrase book. German, French, Spanish, Italian. £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS SPECIAL OFFERS

EMI 13in x 8in—full range speakers (post 20p each or 30p pair): *150TC—8 ohms Twin Cone 10 watt, £2.20 each or £4 pair; *450 10 watt c/o Twin Tweeters 3, 8 or 15 ohms, £3.50 each or £6.90 pair; EW 15 watt 8 ohms c/o Tweeter, £4.30 each or £7.90 pair; 350 20 watt c/o Tweeters 8 or 15 ohms, £7.50 each or £14.20 pair.

* Polished wood cabinet £4.60, post 35p.
8 ohms full range (post 20p)
 FR4 4in 5 watt, £4; FR65 6in 10 watt, £5.50;
 FR8 8in 15 watt, £6.95; FR23 9 x 6in 15 watt, £6.00.
BASS AND MID RANGE—8 ohms (post 20p)
 AA12 5in 15 watt, £3.30; B110 5in 15 watt, £5.60; B200 8in 15 watt, £6.45; B139/2 13in x 8in 30 watt LF, £10.25.



TWEETERS AND CROSSOVERS (post 20p)
 K2006 10 watt 8 or 15 ohms, £2.10; FHT6 15 watt 8 ohms, £3.30; K2011 30 watt 8 ohms, £4.75; T27 KEF, £4.25; Axent 100 30 watt 8 ohms, £4.90; K4009 1kHz/5kHz c/o, £2.20; SN75 3kHz var. c/o, £2.

SPEAKER KITS (carr. etc. 35p)
 20-2 8in 30 watt, £10 each; 20-3 8in 40 watt, £15 each; LINTON 2 20 watt, £15.95 pair; GLENDALE 3 30 watt, £28.95 pair; DOVEDALE 3 50 watt, £42 pair; KEF KK2, £20.40 each; KEF KK3, £32 each.

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size: 4 1/2in long x 2in wide x 1 1/2in deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines, etc.



Price £24.95 (+ VAT)
 Also assembled £27.22 (+ VAT)
 ready to use

10% VAT TO BE ADDED TO ALL ORDERS. Prices and descriptions correct at time of press E & O E. See pages 110 and 111 of this magazine.

Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

Henry's LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736
 309 PA—Disco—Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road, London W2 1BW

Open—
 9 am—6 pm
 6 days a week
 All stores
 open all day
 Saturday