

PRACTICAL

ELECTRONICS

JULY 1974

25p

20+20


40+40

65+65

100+100

WATTS r.m.s

FOUR
TWIN-CHANNEL
AMPLIFIERS

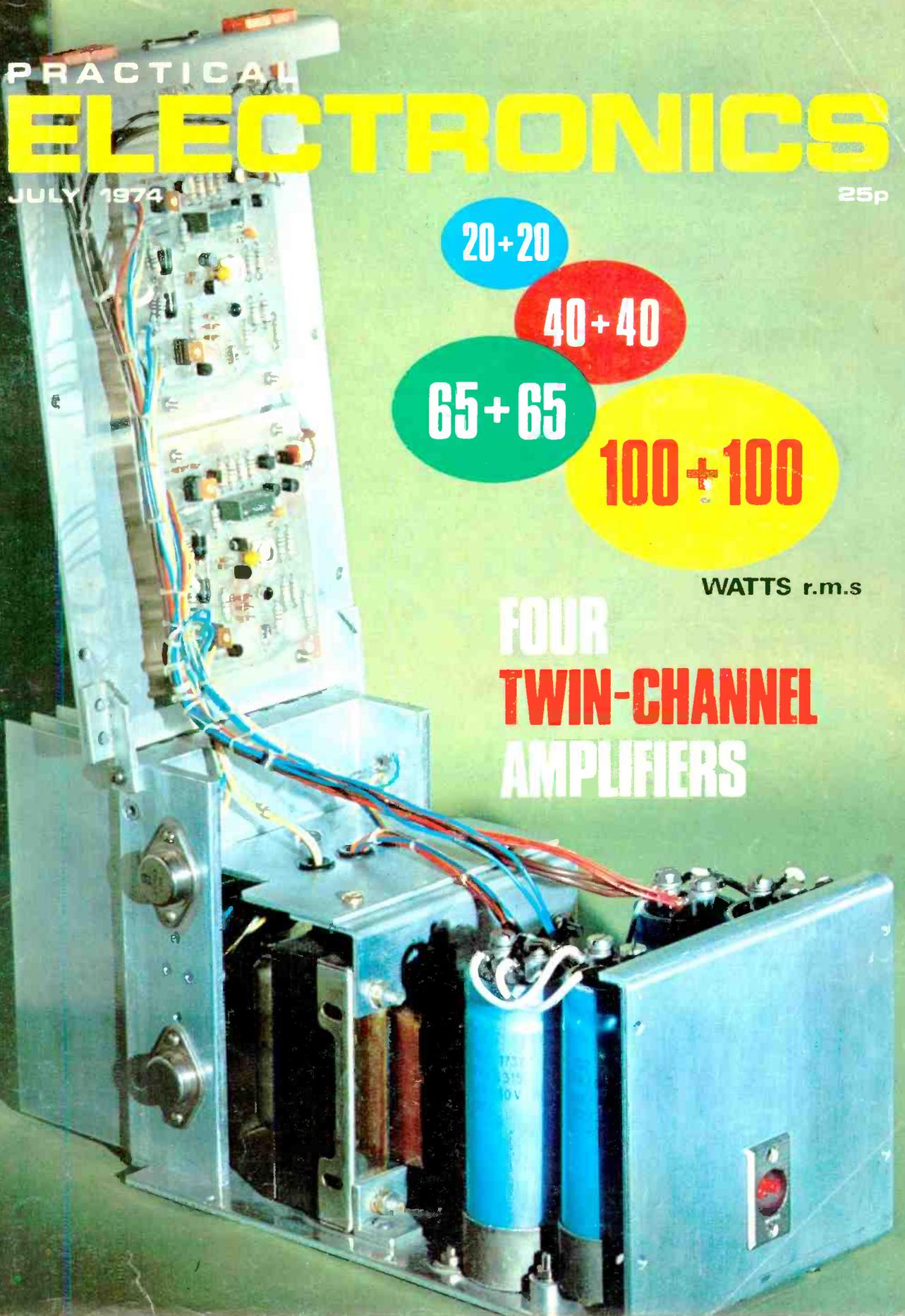

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



TOTAL BUILDING COSTS

£7-23 P.P. & INS. 44p
(Overseas P.P. £1-85p)
(+10% VAT 72p)

Components include:

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN -PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 3 1/2 Loudspeaker
- Earpiece
- Mica Baseboard
- 3 1/2-watt Connectors
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.
- Parts price list and plans 50p (free with parts)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands, as Roamer Ten.

Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes. Tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wave change controls. Attractive all white case with red grille and carrying strap. Size 9 1/2in x 7in x 2 1/2in approx. Parts price list and plans 30p (FREE with parts).

£6-95 P.P. & INS. 44p
(+10% VAT 69p) (OVERSEAS P. & P. £1-85)



NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9in x 5 1/2in x 2 1/2in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS £2-73
(+10% VAT 27p) P.P. & INS. 30p (OVERSEAS P. & P. £1-25)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS £3-60
(+10% VAT 36p) P.P. & INS. 30p (OVERSEAS P. & P. £1-25)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and easy built plans 20p. Free with parts.

TOTAL BUILDING COSTS £4-08
(+10% VAT 40p) P.P. & INS. 31p (OVERSEAS P. & P. £1-85p)




ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVE BANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS, ALSO AIRCRAFT BAND

Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

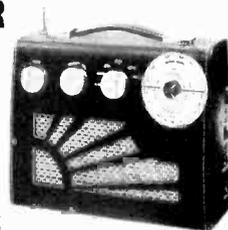TOTAL BUILDING COSTS £8-50
(+10% VAT 85p) P.P. & INS. 52p (OVERSEAS P. & P. £1-85)



POCKET FIVE

3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5 1/2in x 1 1/2in x 3 1/2in approx. Plans and parts price list 15p (FREE with parts).



Total Building Costs **£2-28**
(+10% VAT 22p) P.P. & Ins. 26p (Overseas P. P. £1-25)



Total Building Costs **£2-50** P.P. & Ins. 26p
(+10% VAT 25p) (Overseas P. & P. £1-25)

TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS:

MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone control. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS £6-98
(+10% VAT 69p) P.P. & INS. 47p (OVERSEAS P. & P. £1-85)



EDU-KIT

Build Radios Amplifiers, etc., from easy stage, diagrams.

Five units including master unit to construct.


Components include: Tuning Condensers: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS £5-50
(+10% VAT 55p) P.P. & INS. 33p (OVERSEAS P. & P. £1-85)

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW, and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

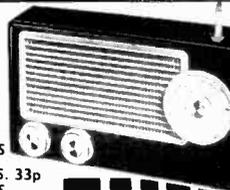TOTAL BUILDING COSTS £4-48
(+10% VAT 44p) P.P. & INS. 33p (OVERSEAS P. & P. £1-25)



ROAMER SIX CASE AND LOOKS AS TRANS EIGHT

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages 6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS £3-98
(+10% VAT 39p) P.P. & IN. 31p (OVERSEAS P. & P. £1-85)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1, 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52867 Reg. No. 788372

I enclose £ for

Name

Address

PRACTICAL ELECTRONICS

VOLUME 10 No. 7 JULY 1974

CONSTRUCTIONAL PROJECTS

- P.E. POWER SLAVES** *by B. Reeson*
A family of dual-channel high power audio amplifiers 590
- RANDOM LIGHT DISPLAY** *by K. L. Spence*
A simple lighting unit capable of producing an endlessly varying and unpredictable pattern of colours 607
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—8** *by R. A. Cole*
Introduction to the f.m. tuner and decoder with decoder construction details 610
- CAR SYSTEMS MONITOR** *by J. P. Perry*
Safeguard yourself against the silent faults; add audible indication to water, oil and charging circuits 614
- NIM MACHINE** *by R. D. Mount*
An unbeatable opponent for the old chinese stick game 627

GENERAL FEATURES

- FIRST STEPS IN CIRCUIT DESIGN—4** *by A. P. Stephenson*
Biasing gain and the emitter follower 596
- INGENUITY UNLIMITED**
Synthesiser patchboard 603
- SOLAR POWER AND ITS APPLICATIONS FOR TODAY** *by P. S. Woodcock*
A look at the utilisation of solar energy and its effects 618

NEWS AND COMMENT

- EDITORIAL—SOUND POWER** 589
- SPACEWATCH** *by Frank W. Hyde*
The Sun by Skylab 595
- ELECTROMUSE** *by Malcolm Pointon*
A musician discusses the application of electronic techniques to composition and performance 600
- BOOK REVIEWS** 604, 616
Selected new books we have received
- NEWS BRIEFS** 616, 625
Marconi Centenary Exhibition—Obituary
- TUNING IN TO ESP** *by Peter Verwig*
A report from a recent IEEE conference in America on parapsychology 617
- INDUSTRY NOTEBOOK** *by Nexus* 622
What's happening inside industry
- PATENTS REVIEW** 631
Reminders on general British Patent procedures
- READOUT** 634
A selection of readers' letters
- SOUND SYNTHESIS FOR THE AMATEUR** 635
A special offer to Clubs, Schools and Universities to hear the P.E. Lecture on "Sound Synthesis" using the P.E. Synthesiser

Our August issue will be published on Friday, July 12, 1974

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £3.50. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT. PE, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK, BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

CALLERS WELCOME Mon.-Sat. 9 a.m.-5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 1/4W 2%
ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7 Ω-2.2 MΩ	E24	1-99 100+
1/4	10%	3.3 MΩ-10M Ω	E12	1-3p 1-1p
1/4	2%	10 Ω-1M Ω	E24	1-3p 1-1p
1/4	10%	1 Ω-3.9 Ω	E12	1-3p 1-1p
1/4	5%	4.7 Ω-1M Ω	E12	1-3p 1-1p
1/4	10%	1 Ω-10 Ω	E12	1-3p 1-1p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7 Ω to 1M Ω.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5k Ω to 2M Ω, log or linear (log 1/4W, lin 1/4W).
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch 28p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5M Ω. Horizontal or vertical P.C. mounting
(0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector. Detector GDI1, £2. Kit of parts for mains operated detector including GDI1 but excluding case, £5.60. Suitable case, £1.50. Kit of parts for 12 or 24V battery operation, including GDI1 and P.C. board, £7.70. As above for PP9 battery, £6.90. Note: The battery operated kits incorporate our patented circuit to minimise battery drain—typically 90mA for 24V.

PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, the immerse the board in the etchant. On removal the circuit remains in high relief. 97p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 3p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 33p, 0.047μF, 0.068μF, 0.1μF, 5p, 0.15μF, 6p, 0.22μF, 7p, 0.33μF, 11p, 0.47μF, 13p.

160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 3p, 0.15μF, 4p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 4p, 0.15μF, 5p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V CERAMIC DISC CAPACITORS 100pF to 10,000μF, 2p

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 0.05μF, 0.1μF, 4p.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/63, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1,000/4, 10p, 470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1,000/10, 12p, 470/25, 680/16, 1,500/6.3, 13p, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6.3, 18p, 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6.3, 4,700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V	12p
0.22μF 35V	4.7μF 35V	33μF 10V	
0.47μF 35V	6.8μF 25V	47μF 6.3V	
1.0μF 35V	10μF 25V	100μF 3V	

VEROBOARD

2 1/2" x 3 1/2"	0.1	0.15
2 1/2" x 5"	24p	20p
3 1/2" x 3 1/2"	28p	28p
3 1/2" x 5"	28p	28p
3 1/2" x 5"	32p	32p
17" x 2 1/2"	85p	67p
17" x 3 1/2"	120p	108p
17" x 3 1/2" (plain)	76p	52p
17" x 3 1/2" (plain)	—	41p
2 1/2" x 5" (plain)	—	12p
2 1/2" x 3 1/2" (plain)	—	11p
Pin insertion tool	62p	62p
Spot face cutter	52p	52p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard insulated	28p	2.5mm insulated	12p
Standard screened	18p	3.5mm insulated	12p
Stereo screened	40p	3.5mm screened	18p
Standard socket	20p	2.5mm socket	10p
Stereo socket	30p	3.5mm socket	11p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin, 7 pin
Plug 12p. Socket 8p.
4 way screened cable, 25p/metre.
6 way screened cable 30p/metre.

BATTERY ELIMINATOR

£1.70
9V mains power supply. Same size as PP9 battery.

FERRIC CHLORIDE

Anhydrous to Mill-spec in 1lb sealed packs 1lb 55p (20p). 3lb £1 32 (30p). 10lb £3 85 (60p).

VERSATILE POWER UNIT

Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1.7-10.5V output with 2 extra capacitors. Brand new. Only 85p (20p). Also available in a toy garage with press switch lamp etc. (Used for 'Hot Wheels') Only £1.85 (30p).

AMPLIFIER UNIT

Intfully screened case 5 1/2" x 5 1/2" x 3 1/2" 2 GET116 on heat sink 2 zeners, 3 pot cores, 4 small transformers, 1% R.S. C.s. etc 70p (30p) with circuit.

3W CASED AMPLIFIER

Polished wooden cabinet 14in x 13in x 9in, containing a sensitive (20μV) 4 valve amplifier with tone and volume controls. Gives 3 watts output to the 7in x 4in 3Ω speaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation, £3.50 (£1). Suitable cassette £1.10 (30p). Spare head 33p. Tape (ex-computer) 75p (20p). Amplifier chassis only, complete and tested (2 x ECC83, EL84, EZ80) - speaker £2.50 (40p).

71B BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, pots, switches, + PC boards with transistors and diodes, also crystals and loads of odds and ends. Amazing value. £1.82 (40p)

Scopes in stock for callers, ring for details. S.A.E. List. All prices include VAT. Carriage in brackets, small parts 5p.

GREENWELD ELECTRONICS (PE4)

51 Shirley Park Road, Southampton

New wholesale/retail shop and mail order department. Other retail shop at 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.



Beginner's Guide To Electronics

3rd Edition

T.L. Squires and C.M. Deason

ELECTRONICS



This book describes as simply as possible the basic concepts in electronic engineering and the various components used in electronic equipment so that the reader gains an understanding of the terms used and the practical side of the subject. Prominence throughout has been given to the transistor and the integrated circuit.

- Provides a 'short cut' for those wishing to obtain a quick acquaintance with modern electronics
 - Completely revised and brought up-to-date
 - Each section is dealt with non-mathematically and explanatory diagrams are used throughout
- 240 pages 191 x 128mm. ISBN 0 408 00126 7
Cased £1.90

BUY NOW



Newnes-Butterworths

Borough Green, Sevenoaks, Kent

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors - Up to date
Brochures on request

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.



**UK's
LARGEST RANGE
OF KITS &
GADGETS**

TEST EQUIPMENT MULTIMETERS

(carr. etc. 30p)
PT12 20K/Volt Slimline £5.95
M210 (Case £1-25) 20K/Volt
Slimline deluxe £6.75
TLH33D 2K/Volt Robust £7.50
U437 10K/Volt Steel case. AC up to 40kHz 4.95
AF105 (Case £1-90) 50K/Volt 11.95
U4313 20K/Volt AC current. Steel case 10.50
U4341 Plus Built-in transistor tester 10.50
Model 500 (Case £1-95), 30K/Volt 9.95



OTHER EQUIPMENT

SE250B Pocket Signal Injector 2-10 carr. 15p
SE500 Pocket Signal Tracer 1-70 carr. 15p
TE15 Grid Dip meter 440kHz 280mHz 15.00 carr. 30p
TE40 AC Millivoltmeter 1.2mHz 19.75 carr. 35p
TE65 28 Range valve voltmeter 22.50 carr. 40p
TE20D 120kHz-500mHz RF Gen. 18.95 carr. 40p
TE22D 20Hz-200kHz Audio Gen. 19.95 carr. 40p
SE350A Deluxe Signal Subr. 12.50 carr. 20p
SE400 Volts/ohms/R-C tracer./RF field/RF gen. 14.75 carr. 20p

New Revolutionary Supertester 680R

680R Multi-tester £18.50
Accessories
Transistor tester 11.00
Electronic voltmeter 18.00
Amplclamp 11.95
Temperature probe 11.95
Guass meter 11.95
Signal injector 5.95
Phase Sequence 5.95
EHT Probe 5.95
Shunts 25/50/100A 4.50

A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester 6.95 p & p 15p
Q4002 Photoelectric System £13.70
E1310 Stereo mag. cart. preamp. 4.80 p & p 25p
Easiphone D1201 telephone amp 7.95 p & p 20p
D1203 Teleamp. with PU coil 4.95 p & p 20p
LL1 Door Intercom. and chime 8.40 p & p 25p
1kW Dimmer/controller 3.00 p & p 10p
9" Twin spring unit For 3.30 p & p 15p
16" Twin spring unit Reverbs 6.85 p & p 25p
LUS50 Ultrasonic Switch Trans/Rec £12.75
C3041 1-250mHz £4.25
C3043 5CH 1-300mHz £5.75
VHF 105 Aircraft Band Converter 4.50 p & p 15p
B2005 4 ch. mic. mixer 4.20 p & p 15p
B2004 2 ch. Stereo mixer 6.75 p & p 15p
PK3 Kit £1.95 p & p 20p

EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO
+ or - Earth with speaker
and fixings. £6.50 c/p 30p.
8 TRACK CAR STEREO
(- Earth) with speakers in
Pods and fixings £12.50
c/p 40p. Portable Batt/Cass
Tape Player £7.25.
Car Lighter Plug and
adaptor for all cassette and
radio 6/7/19 V output
(state width) £1.95 each
Rotel Stereophones RH630
£4.50. RH700 £6.75. RH430
£3.30. Rotel RA310 15+15
watt Stereo Amplifier
(List £52.00) £34.52. Wem
W500 Battery/Main Cassette
Recorder £12.75.
Plus free pair of stereo
phones.

BUILD THIS RADIO

Portable MW/LW radio kit
using Mullard RF/IF
module.
Features MW - bandspread for extra
selectivity. Slow motion tuning.
Fibre glass PVC cabinet. 600MW
output. All parts £7.98 (battery
22p), carr. etc. 32p.



FIBRE OPTICS

0.01 diam. Mono Filament £3.00 per 50 metre reel
0.11 diam. 64 Fibres Sheathed £1.00 per metre.
SPRAY5 15mm diam. (Mare's Tail Spray £10.50, 7mm
diam. £5.00).

SPECIAL PURCHASES

UHF TV TUNERS CHANNELS 21 TO 64
Brand new transistorised geared
tuners for 625 Line Receiver
IF output. £2.50. Post 20p.



EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

Model No.	£ p	Model No.	£ p
310 Radio control receiver	2.98	760 Acoustic switch (electronics only)	10.75
300 4-channel R/C transmitter	5.95	780 Metal Detector	9.65
345 Superhet R/C receiver	5.95	790 Capacitive Burglar alarm	6.85
455 AM signal generator	12.33	835 Guitar preamp.	4.25
65 Simple transistor tester	1.40	840 Delay car alarm	6.15
115 8 watt Amplifier	3.90	875 CAP Discharge ignition (for car engine (-Ve Earth))	13.15
120 12 watt amplifier	4.70	80 Scope Calibrator	2.25
125 Stereo control unit	5.70	255 Level Indicator	6.15
130 Mono control unit	3.60	525 120-160mHz VHF timer	11.30
605 Power supply for 115	4.55	715 Photo cell switch	7.70
610 Power supply for 120	4.55	795 Electronic continuity tester	4.30
615 Power supply for 2-120	5.73	860 Photo timer	13.25
230 AM/FM aerial amplifier	2.93	871 Slide projector auto feed control	7.15
240 Auto packing light	5.90	235 Acoustic Alarm for driver	7.60
275 Mic. preamplifier	6.08	465 Quartz XTAL checker	8.75
570 LF generator 10Hz-1mHz	15.80	220 Signal Injector	2.30
570 Sq. wave generator 20Hz-20kHz	14.60	390 VOX	15.50
590 SWR meter	12.85	432 Testakit	19.30
620 NI-CAD Charger 1-2-12V	8.00	670 Buffer Battery Charger	6.55
630 STAB Power supply 6-12V 0.25-0.1A	8.15	885 Capacitive Contact Alarm	6.25
690 DC motor speed Gov.	2.87	850 Electronic Keyer	18.75
700 Electronic Chaffinch	7.00	820 Electronic Digital Clock	58.50
705 Windscreen wiper timer	6.80		



ALL KITS OFFERED
SUBJECT TO STOCK
AVAILABILITY
Prices correct at time
of preparation.
Subject to change
without notice.

BUILD THIS TUNER

MW/LW Radio Tuner to use with any amplifier.
Features Mullard RF/IF module Ferrite aerial,
built in battery. Excellent results. Size 7" x
2 1/2" x 3 1/2". All parts £4.85, carr. 15p.

MULTI-USE & RADIONIC KITS

10-1	10 Projects	3.60
50-1	10 Projects	8.00
150-1	150 Projects	13.20
Telephone Communicator		7.20
X20	20 (Elec.)	4.95
X40	40 (radios)	9.45

(carr./packing 40p)
All transistor circuits with handbooks

TBA800 5 WATT I.C.
Suitable alternative to SL 403D.
5/30 volt operated. 8/16 ohm
5 watt output.
With circuits and data £1.50.



STROBE TUBE ST2 (D32) DIAC 25p
CRS1/40 SCR 45p
ZFT4 £3.00
ZFT8 £3.50
Electronics. £3.00

All types offered subject to availability.
Prices correct at time of press E & OE.
10% VAT TO BE ADDED TO ALL ORDERS.
UK post, etc. 15p per order unless stated.



U.K.'s LARGEST RANGE OF TRANSISTORS & DEVICES

JUST A SELECTION

*TBA800 5W IC £1.50
*Sinclair ICR 6W IC £1.80
*ZN4141C Radio IC £1.20
*Ultrasonic Transducers £5.90 pr.
*3015F 7SEG Indicator £1.70
TIL 209 LED 24p each
22p each per 10
*With circuits/data sheet.

OVER 1,500 DIFFERENT SEMI- CONDUCTOR DEVICES IN STOCK

Free stock list—latest edition (Ref. 36) on request.
Includes Radio valves, I.C.'s, rectifiers, triacs,
SCR's, LEDs, etc. More types—better prices—
discounts for quantity small or large.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt
tape decks. Fitted record/
play and oscillator/erase
heads. Wind and rewind
controls. Takes up to 4"
spools. Brand new com-
plete with head circuits. £9.50 carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high
quality controls com-
plete with knobs (post,
etc. 15p any quantity).
Singles Log and Lin
5K, 10K, 22K, 50K,
100K, 250K, 500K, 1
Meg. 45p each.
Ganged Log and Lin
10K, 22K, 50K, 100K,
250K, 65p each.
(Quantity discounts
available)
Complete with knobs.

MARRIOT TAPE HEADS

4 TRACK MONO or
2 TRACK STEREO
" 17 " High Impedance
£2.50
" 18 " Med. Impedance
£2.50
" 36 " Med. Impedance
£5.00
R730/E732 track mono
Record/Eraser low imp.
75p pair.
Erase Heads for " 17 "
" 18 " and " 36 " £1.00
" 63 " 2 track mono,
High Imp. £1.75
" 43 " Erase Head for
" 63 " 75p
(Post, etc. 15p any
quantity).

SINCLAIR MINIATURE AMPLIFIERS & TUNER/DECODER

AMPLIFIERS (carr. etc. 20p)
A-3000, 0.3w 9 volt 1.75
104, 1 watt 9 volt 3.00
304, 3 watt 9 volt 3.95
555, 3 watt 12 volt 4.10
E1208, 5w 12 volt 5.10
608, 10 w 24 volt 4.95
410, 10 w 28 volt 4.45
E1206, 30 w 45 volt 9.95
E1210, 2 1/2 + 2 1/2
watts 12 volt 7.75
RE500, 5 watt IC
mains operated
Amplifier with
controls 6.30
SAC14, 7 + 7 watt
Stereo with
controls 11.75
SAC13, 15 + 15 w
Stereo with
controls 14.95
SP40-5 2Z40/
Stereo 80/PZ5 25-00
SP40-6 2Z40/
Stereo 80/PZ6 27-75
SP60 2Z60/
Stereo 80/PZ8 30-45
Transformer PZ8 3.95

POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)
470C 6/7 1/2 volt 300 MA (includes Multi-Adaptor
for Tape Recorders, etc.) 2.15 post 20p
Car Lighter Voltage Adaptors 300mA (State
voltage 6V, 7.5V, 9V) 1.95 ea. post 25p
SC202 3/6 7 1/2 volt 400mA 3.65 carr. 30p
HC244R Stabilised version 4.90 carr. 30p
P500 9 volt 500mA 3.20 post 20p
P11 24 volt 500mA (chassis) 2.90 post 20p
P15 26/28 volt 1 amp (chassis) 2.90 post 20p
P108 12V 1 amp (chassis) 4.50 post 20p
P1081 45V 0.9 amp (chassis) 7.50 post 20p
P12 44-12 volt 0.4-1 amp 7.15 post 30p
SE101A 3/6/9/12 volt 1 amp (Stab.) 12.50 post 25p
RP164 6/7 1/2/9/12 1 amp (Stab.) 12.95 post 30p



**Henry's RADIO
LIMITED**
EDGWARE ROAD, LONDON W2


404-406 Electronic Components and Equipment 01-402 8381
309 PA—Disco—Lighting High Power Sound 01-723, 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 8554/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm - six days a week
Hi-Fi—Tape Equipment
Discount Stock List
Free at all stores



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

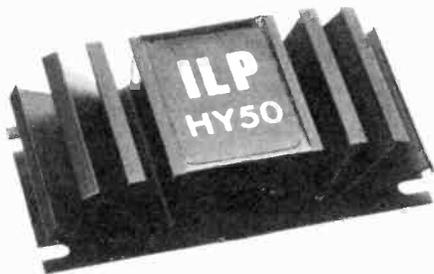

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular audio amplifier to a simple input/output device requiring only the addition of a basic unregulated (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of "King-size" cigarettes. Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER: 25W RMS, 50W peak music power.
LOAD IMPEDANCE: 4-16Ω into 8Ω
INPUT SENSITIVITY: 0dB (0-775V RMS).
INPUT IMPEDANCE: 47kΩ.
TOTAL HARMONIC DISTORTION: Less than 0.1% at 25W typically 0.05.
SIGNAL/NOISE RATIO: better than 75dB.
FREQUENCY RESPONSE: 10Hz-50kHz ± 1dB.
SUPPLY VOLTAGE: ±25V.
SIZE: 105 × 50 × 25mm.

Price £5.80 mono £11.60 stereo. Price inclusive of VAT & P. & P.


NEW HY5 PREAMPLIFIER

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components and has been redesigned to run off a split power line with improvements in signal/noise, overload capability and reduced distortion. The output has been increased to match the power module (0dB), and share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 and power supply only potentiometers are required to complete a simple mono amplifier with input and output facilities expected to be found on Hi-Fi amplifiers.

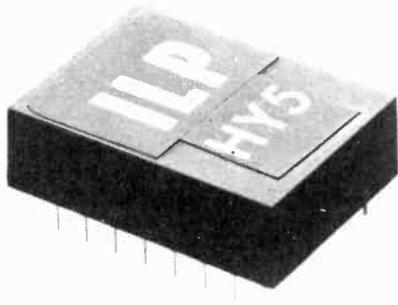The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.




INPUTS
Magnetic Pick-up 3mV (within 1dB RIAA curve)
Ceramic Pick-up up to 3mV.
Microphone 10mV.
Tuner 250mV.
Auxiliary 3-100mV.
Input impedance 47kΩ 1 kHz
OUTPUTS
Tape 100mV.
Main output. 0dB (0-775V).

SPEC.

ACTIVE TONE CONTROLS
Treble ± 12dB at 10kHz
Bass ± 12dB at 100Hz
OVERLOAD CAPABILITY
(equalization stage) 40dB on most sensitive input.
OUTPUT NOISE LEVEL
(below 10mV magnetic input) 68dB.
DISTORTION 0.05% at 1kHz.
SUPPLY VOLTAGE ± 16-25V.
SUPPLY CURRENT 15mA.

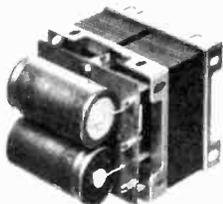Price £4.85 mono £9.70 stereo. Price inclusive of VAT and P. & P.



POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 24in high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE ± 25V.
INPUT VOLTAGE 210-240V.
SIZE: L. 70 D. 90 H. 60mm.
Price £5.23. Price inclusive of VAT & P. & P.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

NOW AVAILABLE IN THE U.K!

CHINAGLIA




PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

**CORTINA MINOR
33 RANGE POCKET MULTIMETER**

- SENSITIVITY 20,000Ω/VOLT (D.C.), 4,000Ω/VOLT (A.C.).
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0-100mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1,500V; D.C. CURRENT 0-50μA, 5mA, 50mA, 500mA, 2.5A; A.C. VOLTS, 0.75V, 25V, 75V, 250V, 750V, 1,500V; A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A; dB RANGES -10 to +69; AF VOLTS RANGES 0-1,500V; RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100μF IF F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, 2-5%; A.C. VOLTAGE AND CURRENT 3-5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 x 85 x 40mm, 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

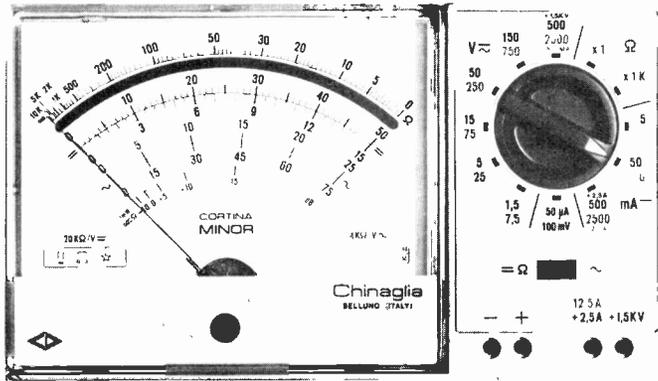

METER PRICE £13.75 (p & p 80p) PROBE £8.00 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone:—

CHINAGLIA (U.K.) LIMITED

19 Mulberry Walk, London S.W.3.

Telephone 01-352 1897

TRADE ENQUIRIES WELCOMED

***STILL AT £42.50**

Solartron CD 7115.2 Double Beam Oscilloscope D.C.—9 Mc/s; 3 MV/cm; trigger delay; crystal calibrator; 4in flat-faced tube. In good working condition. Carr. £1.50.

NEW WIDE RANGE WOBBLULATOR

5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75p. P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE AND SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each. P. & P. 25p (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each. P. & P. 5p. 12" Long Persistence CRT, full spec. Price £7.50 to include V.A.T. & carr. £1 WORTH OF "UPS". Six brand new capacitors all between 15V and 100V. Total capacitance not less than 7,000mF. P. & P. 45p.

Large quantity of good quality components — NO PASSING TRADE — so we offer 3 lb of **ELECTRONIC GOODIES** for £1.50 post paid.

ROTARY SWITCH PACK. Six brand new switches (1 ceramic, 1 off, 4 pole, 2 way, etc.), 50p. P. & P. 20p.

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt, many high stabs, etc. Fine value at 50p. P. & P. 17p.

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College)

Tel.: Reading 582605/65916

P.C.B. PACKS S & D. Quantity 250ft —no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

S CRYSTALS 70 to 90kHz. Our choice, 25p. P. & P. 15p.

SANGO 50 microamp meters. 21" diameter. Ex-new radiation equip. £1.25 each. P. & P. 17p.

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p.

POTS—10 different values. Brand new—50p. P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot. P. & P. 10p.

FLAT FACED 4" Twin Beam Tube, type Corsor 89D. Green trace. Brand new £4 each. P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each. Mullard OCP70, 10p each.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. Two-tone green, £3.75 each. Black, £3.75 each. P. & P. 25p each.

IDEAL EXTENSION Telephones with standard GPO type dial, bell and lead coding. £1.75 each. P. & P. 25p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.



for fast, easy reliable soldering.
Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS




Size 5
Savbit alloy
18 swg, 24p (illustrated).
Size 19A
60/40 alloy
18 swg, 25p
Size 15
60/40 alloy
22 swg, 28p

IDEAL FOR HOME CONSTRUCTORS



Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 36p
Size 12 REEL for Service Engineers and Electricians. 18 swg Savbit alloy. £1.16

BIB WIRE STRIPPER AND CUTTER

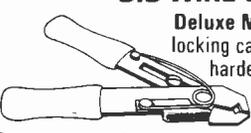

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops, if unobtainable, send 10p p&p direct to Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP

ELECTROVALUE

Present

THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

EVERYTHING BRAND NEW ★ ATTRACTIVE DISCOUNTS ★ FREE POSTAGE (U.K.)

TRANSISTORS

and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc., etc.

MINITRON DIGITAL INDICATORS

30154F Seven segment filament, compatible with standard logic modules, 0-9 and decimal point; 9mm characters in 16 lead DIL, £1.20. Now available in 8mA or 15mA per segment rating. Suitable BCD decoder driver 7447, £1.15. 3015G showing + or - and I and dec. pt, £1.20.

CAPACITORS

DALY ELECTROLYTIC

In cons. plastic sleeve
1,000mF/25V, 28p; 5,000mF/25V, 62p; 1,000mF/50V, 41p; 2,000mF/50V, 57p; 5,000mF/50V, £1.18; 5,000mF/100V, £2.91.

POLYESTER TYPE C280

Radial leads for P.C.B. mounting. Working voltage 240V d.c.
0-01, 0-015, 0-022, 0-033, 0-047, 3p each; 0-068, 0-1, 0-15, 4p each; 0-22, 5p; 0-33, 7p; 0-47, 8p; 0-68, 11p; 1-0, 14p; 1-5, 21p; 2-2, 24p.

SILVERED MICA

Working voltage 500V d.c.
Values in pF—2 to 820 in 32 stages, 6p each; 1,000, 1,500, 7p each; 1,800, 8p; 2,200, 10p; 2,700, 3,600, 12p each; 4,700, 5,000, 15p each; 6,800, 20p; 8,200, 10,000, 25p each.

TANTALUM BEAD

0-1, 0-22, 0-47, 1-0mF/35V, 13p each. 2-2/16V, 2-2/35V, 4-7/16V, 10/6-3V, 13p each. 4-7/35V, 10/16V, 22/6-3V, 16p each. 10/25V, 22/16V, 47/6-3V, 100/3V, 18p each.

POLYCARBONATE TYPE B32540

Working Voltage 250V.
Values in mF: 0-0047, 0-0068, 0-0082, 0-01, 0-012, 0-015, 3p each. 0-018, 0-022, 0-027, 0-033, 0-039, 0-047, 0-056, 0-068, 0-082, 0-1, 4p each.

CERAMIC PLATE CAPACITORS

Working voltage 50V d.c.
In 26 values from 22pF to 6,800pF, 2p each.

POTENTIOMETERS

ROTARY, CARBON TRACK.

Double wipers for good contact and long working life.
P20 SINGLE linear 100 ohms to 4.7M Ω , 14p each.
P20 SINGLE log, 4.7k Ω to 2.2M Ω , 14p each.
JP20 DUAL GANG linear 4.7k Ω to 2.2M Ω , 48p each.
JP20 DUAL GANG log, 4.7k Ω to 2.2M Ω , 48p each.
JP20 DUAL GANG log/antilog 10K, 22K, 47K, 1M Ω only, 48p each.
JP20 DUAL GANG antilog 10k only 48p.
2A DP mains switch with any of above 14p extra. Decades of 10, 22 and 47 only available in ranges above. SKELETON CARBON PRESETS 6p each.

SLIDER

Linear or log, 4.7k Ω to 1M Ω in all popular values. 30p each.
Escutcheon plates, black, white or light grey, 10p each.
Control knobs blk/wht/red/yel/grn/blu/dk. grey/lt grey, 7p each.

JACKS AND PLUGS

Sockets

2-circuit, unswitched, S1/S5 11p
2-circuit/2 break contacts, S1/BB 13p
3-circuit, unswitched (not GPO), S3-S55 15p
3-circuit with 3 break contacts, S3/BBB 20p
2 circuit with chrome nut and black/white/red/green or grey unswitched, S5/S5 14p
2 circuit with chrome nut and black/white/red/green with 2 break contacts, S5/BB 17p
Miniature, 3.5mm, 2-circuit (black), 2 br. cont., S6/BB 8p

EV CATALOGUE 7

2nd Printing

112 pages, thousands of items, illustrations, diagrams, much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p post free and includes a refund voucher for 25p for spending when ordering goods list value £5 or more.

Plugs

2-circ. screened, top entry, P.1 24p
2-circ. screened, side entry, SEP1 36p
Line socket, mono, 231 40p
Line socket, stereo, 244 40p
3-circuit, unscreened, bl/grey/wh, P.4 36p
2-circuit, unscreened, bl/wh/red/bl/grn/grey, P2 18p
3-circuit, screened, top entry, P3 53p
3-circuit, screened, side entry, SEP3 55p
Miniature, 3.5mm, 2-circ., screened, P5 13p
Miniature, 3.5mm, 2-circ., unscreened, various colours, P6 10p

INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, tag and nuts. 15A/250V. In blk/brwn/red/yel/grn/bl/grey/wh, Type TP.1, 14p each.

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4.7-470K	1.3	1.1	0.9 nett
C	1/2	4.7-10M	1.3	1.1	0.9 nett
C	3/4	4.7-10M	1.5	1.2	0.9 nett
C	1	4.7-10M	3.2	2.5	1.9 nett
MO	1/2	10-1M	4	3.3	2.3 nett
WW	1	0.22-3.9	9	9	8
WW	3	1-10K	7	7	6
WW	7	1-10K	9	9	8

(see note below)

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide, Electrofil TR5, ultra low noise.
WW = wire wound, Plessey.
Values: All E12 except C $\frac{1}{2}$ W, C $\frac{3}{4}$ W, and MO $\frac{1}{2}$ W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.
Tolerances: 5% except WW1 10%
 $\pm 0.05 \Omega$ below 10 Ω and MO $\frac{1}{2}$ W 2%

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90. The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2.30. Loudspeaker Unit 59RM109, £2.45. Cabinet Kit (to Baxandall design), £10.45. Cross-over choke included in full kit above, £1.30.

ELECTROLYTICS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	—	11p	8p
1.0	—	—	—	—	—	—	—	8p
2.2	—	—	—	—	11p	—	—	8p
4.7	—	—	—	11p	—	8p	8p	8p
10	—	—	—	—	8p	8p	8p	8p
22	—	—	—	—	8p	8p	8p	10p
47	8p	—	—	—	8p	8p	8p	10p
100	9p	8p	8p	8p	8p	8p	10p	12p
220	8p	8p	9p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

ZENER DIODES full range E24 values: 400mW; 2.7V to 36V, 14p each; 1W; 6.8V to 82V, 21p each; 1.5W; 4.7V to 75V, 48p each. Clip to increase 15W rating to 3 watts (type 266F) 5p.

VEROBORD

Copper clad 0.1 in. matrix—2.5 x 3.75 ins. 27p. 3.75 x 3.75 ins., 30p. 2.5 x 5 ins., 30p. 3.75 x 5 ins., 33p.
Copper clad 0.15 in. matrix—2.5 x 3.75 ins., 20p. 3.75 x 3.75 ins., 30p. 2.5 x 5 ins., 30p. 3.75 x 5 ins., 36p.
Vero spot face cutter (any matrix), 43p. 0.040 pins (for 0.1 matrix) per 100, 35p. 0.052 pins (for 0.15 matrix) per 100, 35p.

KNOBS

In a great variety of modern types, for $\frac{1}{2}$ in. shaft, from plastic to solid aluminium, from typically 63p per pack of two (Catalogue 7, page 62).

CONNECTORS

DIN from 2-way to 7-way plugs and sockets; phone types, mains connectors, etc. (Catalogue 7, page 88).

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14.99. 15% on orders £15 and over.

PACKING AND POSTAGE FREE

in U.K. for pre-paid mail orders. For orders £2 and under, there is an additional handling charge of 10p.

GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, "seconds" or sub-standard merchandise is offered for sale.

PRICES QUOTED DO NOT INCLUDE VAT, for which 10% must be added to total nett value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices are subject to alteration without notice. S.A.E. with written enquiries please.

GIRO ACCOUNT No. 38/671/4002

All postal communications, mail orders, etc., to Head Office at Egham address, Dept. PE6.

ELECTROVALUE LTD

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475 Shop hours—9-5.30 daily. Saturdays 9-1 p.m.

Northern Branch: 680 BURNAGE LANE, BURNAGE, MANCHESTER M19 1NA
Telephone 061-432 4945 Shop hours—Daily 9-1 and 2-5.30 p.m. Saturdays 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081

GENESIS



**ONLY
£22-95**

**TABLE TOP
HEIGHT 18"
DJA SPAN
22 INCHES**

At the head of our fibre optic kingdom stands the unique genesis. This fantastic model incorporates the largest mares tail you can buy. Now combined with the most sensational Kinetic light base ever designed in this field. This lamp is unique in the way that the base is opaquely translucent. The tinted upper section allows one to see a slowly rotating eight coloured sculptured wheel, that seems to be floating on a blue haze, that radiates a warm mystic glow.

Thousands of optical fibres energized with colour. Fibre tips flash like stars, bright with all the changing colours of the rainbow. Available in blue or green. M.M. Discount price £22.95 inc p.p. and VAT.



**Ready
to
use**

CASCADE Height 18"

Cascade, the fibre optic that's also a beautiful corner light, M.M. Discount price £16.65 inc p.p. and VAT.



**Ready
to
use**

LITTLE GEM

Little Gem, complete with the smaller mares tail, (8mm approx, 18" x 10" high, overall height from table approx 14"). With a single white light display, housed in a red translucent base, cowlled with a special moulded three dimensional filter that throws light in array. It's amazing, we have completely shattered the style of conventional optics with the fabulous little gem.

ONLY £10

inc post and VAT.


OILWHEEL PROJECTORS

Multi-coloured. For projecting psychedelic colours 6" or 4" diameter. Ideal for fibre optics. 6" oil wheel £5.00 + p.p. 15p. 4" (suitable for optics) £2.65 + p.p. 10p.

BUY WITH CONFIDENCE FROM A FIRM WITH A NATIONAL REPUTATION

MIDLAND MATERIALS

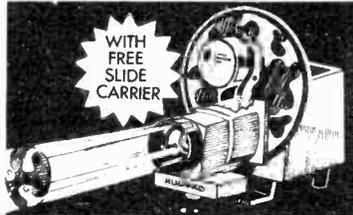OPTICS, 180 WELLINGBOROUGH ROAD, NORTHAMPTON TEL 33487



**WITH
FREE
SLIDE
CARRIER**

AQUARIUS 100

A star for home parties, this budget priced 100-watt projector will transform your room into a swirling image of continuously changing liquid colour of reds, blues, yellows and greens. This machine is supplied with one six inch liquid wheel and includes lamp and lead. Complete with free 2 x 2 slide projection carrier. M & M discount price £19.95 post free.

D.I.Y. SECTION

THE SENSATIONAL MARES TAIL

Three sizes to choose from:

18mm ferrule, 11" high x 22" dia.

7,500 fibres, £10.50 +20p p.p.

12mm ferrule, 10" high x 19" dia.

4,800 fibres £7.85 +12p p.p.

8mm ferrule, 10" high x 18" dia.

2,900 fibres £4.95 +10p p.p.

Complete instructions supplied.

Display bunching of various types of fibres at low cost. TYPE A 1320. Fibres contained in a tough flexible sheath. Makes delightful displays.

M.M. Discount Price 40p per ft.

£1.10 per yd. +5p p.p.

TYPE B. Light guides comprising of 64 fibres.

Each fibre .010 inch diameter in a flexible sheath

1/8 inch. 45p per ft. £1.28 per yd +5p p.p.

TYPE C. Monofilament .040 dia, single strand

flexible plastic that enables heat bending for

combined use with type A or type B.

22p per ft. min order 3ft 66p +5p p.p.

SLOW SPEED MAINS MOTOR

to rotate oil wheel and static wheel 70p inc p.p.



STATIC COLOUR DISC

M.M. Discount price £1.40 inc post.

Specially made for optics. Complete

with metal boss. To fit motor. 4" dia, seven

prominent colours contained in separate sections.

Bulb and baton kit plus 6ft of flex

75p inc post and VAT.




Terms: C.W.O. cheques/po's
C.O.D. please send 50 pence when ordering

P.C. BORED?

— not with the

decon- dalo 33PC

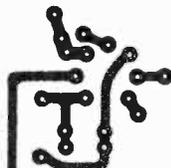

A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

NO MESS — NO MASKING

A perfect circuit every time!

£1.10 for one off

£4.40 for six

£8.80 for twelve

V.A.T. and Post included. Available now in every country in Europe.

Please send me further details on the 33PC:

Name

Address

Post to: **DECON LABORATORIES LTD.**

FREEPOST


PORTSLADE, BRIGHTON, ENGLAND

(No Stamp Needed) Phone 0273 414371

R T V C

FOR AUDIO ON A BUDGET

PUSH BUTTON^(*) CAR RADIO KIT

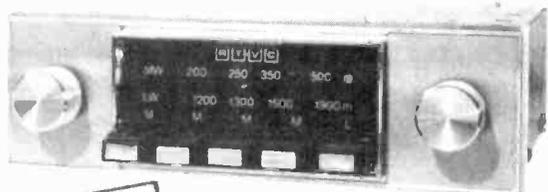

The first time Motor magazine have nominated a push button car radio for their Top Ten Accessory Awards



NOW BUILD YOUR OWN AWARD WINNING PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- 2.) Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.

Size Chassis 7 ins. wide, 2 ins. high and 4 1/8 ins. deep approx.

NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p. free with kit.

Car Radio Kit

£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips
£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.
£1.35 post paid.

STEREO 21



QUALITY SOUND^(*) FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes: -

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded: -

Specifications:

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout.

Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions**. Speakers approx.

15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6". Complete only **£18.95**

Extras if required. £1.37 + £1.60 p & p.

Optional Diamond Stylus

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs.

*Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.


INPUT SENSITIVITIES

- 1) Crystal Mic or Guitar 9mV.
- 2) Moving coil Mic or Guitar 8mV.
- 3), 4), 5) Medium output equipment (Gram. Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.

AC Mains 240V. operation. Size approx. 12 1/2 ins x 6 ins x 3 1/2 ins

£15.00 + 60p. postage & packing

DISCO 50

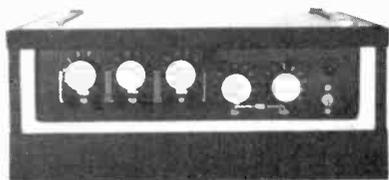

45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/4 x 10 1/2 x 8 ins. approx. Amplifier **£27.50 + £1.50 p. & p**

Special Offer: Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). **Complete £57.00 + £4.00 p&p.**

COMPLETE(*) STEREO SYSTEM



£51-00

40 Watt Amplifier.
Viscount III - R102 now 20 watts per channel.
System I includes,
Viscount III amplifier - volume, bass, treble
and balance controls, plus switches for mono/
stereo on/off function and bass and treble
filters. Plus headphone socket.

Specification
20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0.1%. *P.U.1* (for
ceramic cartridges) 150mV into 3 Meg. *P.U.2*
(for magnetic cartridges) 4mV @ 1kHz into 47K.
equalised within ± 1 dB R.I.A.A. *Radio* 150mV
into 220K. (Sensitivities given at full power).
Tape out facilities: headphone socket, power
out 250mW per channel. *Tone controls and filter
characteristics.* Bass: +12dB to -17dB @
60Hz. Bass filter: 6dB per octave cut. Treble
control: treble -12dB to -12dB @ 15kHz.
Treble filter: 12dB per octave. *Signal to noise
ratio:* (all controls at max.) -58dB.
Crosstalk better than 35dB on all inputs.
Overload characteristics better than 26dB on all
inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

**Garrard SP25 deck, with magnetic cartridge,
de luxe plinth and hinged cover.**

Two Duo Type II matched speakers -
Enclosure size approx. 17 $\frac{1}{2}$ " x 10 $\frac{3}{4}$ " x 6" in
simulated teak. Drive unit 13" x 8" with parasitic
tweeter
Complete System £51-00 Available complete for only **£69-00** + £4 p & p
10W handling.

£69-00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 (As System I)
Two Duo Type IIIA matched speakers -
Enclosure size approx. 31" x 13" x 11 $\frac{1}{2}$ ".
Finished in teak veneer. Drive units approx.
13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with 3 $\frac{1}{2}$ " HF speaker. Max. power
20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £69.00

PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24-20	+ £1 p & p
2 Duo Type II speakers	£14-00	+ £2-20 p & p
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover	£21-00	+ £1-75 p & p.

total £59-20

Available complete for only **£51-00** + £3-50 p & p.


PRICES: SYSTEM 2

Viscount R102 amplifier	£24-20	+ £1-00 p & p
2 Duo Type IIIA speakers	£39-00	+ £4-00 p & p
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover	£21-00	+ £1-75 p & p.

total £84-20

EMI SPEAKERS AT FANTASTIC REDUCTIONS

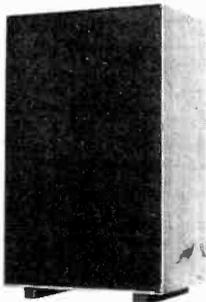THE ULTIMATE COMPLETE SPEAKER SYSTEM
EMI LE 315. List Price £86-00



A professional standard five way speaker
system with enclosure giving top quality
performance.

Enclosure Dimensions
approx. (3ft. x 2ft. x 1ft.).

Drive Units
Hand built - 15" diameter bass with 3"
voice coil, - two 5" diameter Mid Range
units, - two 3 $\frac{1}{2}$ " HF units, plus matching
crossover panel with two variable
potentiometers for mid and high frequency
adjustment.

Power Handling
Continuous rating 35 W rms., Peak power
rating 70 W.

Frequency Response
20 Hz 20,000 Hz. Imp. 8 ohms.

Our price £45-00 + £3-50 p. & p.



15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis.
Superior cone material handles up to 50
watts RMS, and is treated to give a smooth
frequency response. Resonance 30 Hz. Flux
density 360,000 Maxwells. Impedance at
1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40-80.

OUR PRICE £18-70 + £1-50 p & p + £1-50 p & p **Special Offer.**



**950
KIT**

Five matched speakers and crossover unit
for handling up to 45 watts, frequency
response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency
Bass-Speaker with 16,500-gauss magnet
built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 $\frac{1}{2}$ "
dia. approx., are fed by the crossover which
critically adjusts signal for maximum
fidelity. Impedance at 1 kHz is 8 ohms.
Bass coil 2", others 0-5". Recommended
list price £44-00

OUR PRICE £19.50



BUILD YOUR OWN STEREO AMPLIFIER(*)

For the man who wants to design his own stereo - here's your chance to start
with Unisound - pre-amp, power amplifier and control panel. No soldering -
just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV
(for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic
power chips which ensure very low distortion over the audio spectrum.
240V. AC only.

£7-64 + 55p. p & p



8TRACK CARTRIDGE PLAYER(*)

Elegant self selector push button player for use with your stereo system.
Compatible with Viscount III system, Unisound module and the Stereo 21.
Technical specification: Mains input, 240V. Output sensitivity 125mV
Comparable unit sold elsewhere at £24-00 approx.

Yours for only £10.95 + 90p. p & p



Just write your order giving
your credit card number

**DO NOT SEND
YOUR CARD**

- Mail orders to Acton. Terms C.W.O.
All enquires Stamped Addressed Envelope.
Goods not despatched outside U.K.
- Leaflets available for all items listed
thus(*)
Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG/d
323 Edgware Road, London W2

Personal Shoppers — Edgware Road: 9a.m.—5.30p.m. Half day Thurs.
Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES
NORMAL HOUSEHOLD
TYPE

EX G.P.O. Only **£1-05p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16p

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. **38 1/2p**

Cable can be sent by Parcel Post. Post and Packing per 50 yds.: 731p.
Extension Telephones 71p each, p.p. 271p.
£1-37 for 2, p.p. 55p. These phones are extensions and do not contain bells.

Electronic Transistor Ignition **£6-60**

Complete Kit incl. V.A.T. P. & P. 11p.
Ready built and tested unit **£9-90** incl. V.A.T.
Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Plastic Power Transistors

NOW IN TWO RANGES



These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	15	HFE Min.	15
		1-12		13-25
40 watt				26-50
90 watt				18p
				22p
Range 2	VCE Min.	40	HFE Min.	40
		1-12		13-25
40 watt				26-50
90 watt				29p
				33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 AUDIO I.C. as featured in Practical Wireless December issue. Complete with application data, £1.10.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS
14 pin type at 16p each } Now new low
16 pin type at 18p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Tested and Guaranteed Paks



H79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B01	10	Reed Switches, 1" long 1/4 dia. Highspeed P.O. type	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	55p
H66	4	40362. Type PNP Sil. transistors TO-5 can comp. to H65	55p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	55p
B64	150	Germanium Diodes Min. glass type	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p
H67	10	3B19N Channel FET's plastic case type.	55p

Make a rev counter for your car

The "TACHO BLOCK". This encapsulated block will turn any 0.1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available. Featuring plug-in ICs and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3in X 5 1/2in X 3in. We have already received a large order from a major TV Rental company.

Ready built **£10-92** Complete **£8-72**
unit only Kit
(includes V.A.T. & P. & P but no batteries)

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR £1-10p PNP 271p.

High Speed Magnetic Counter

4 digit (non-reset)
24V or 48V (state which)
4 X 1 X 1 in. 33p, p.p. 5p.



Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P. & P. on this Pak.
Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% V.A.T.
MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg. No 820913

Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344.

MAPLIN ELECTRONIC SUPPLIES

★ SAME DAY SERVICE

LARGE OR SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white. Dimensions in inches.



Model	W	H	D	Price
120	8	2 1/2	6	£2.52
220	8	6	3 1/2	£3.42
221	8	6	6	£3.71
320	12	8	12	£7.82

Chassis for model 320 £2.14 extra
Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the 8AJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3 7/16" x 4 5/16". ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY £14.25.
DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to sawtooth by the addition of a few components. 8AJ110: £2.83 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.



MAPLIN: Projected site of London's third airport.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES! We are stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Verobroads. Also parts for the "Electronics Today International" Synthesiser stocked. Send S.A.E. now for our detailed price lists.


YOU SIMPLY MUST SEE OUR PRICES!
Keyboard 49 note C/C £14.35
741C 8-pin DIL 36p
MFC 6040 electronic attenuator 95p
SG 3402N for Ring Modulator £1.69
CA 3046 69p

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1.83 6p	68 6.3 6p	100 4 6p	470 6.3 6p
1.5 63 6p	68 16 6p	100 10 6p	470 10 10p
2.2 63 6p	68 63 10p	100 25 6p	470 25 12p
3.3 63 6p	100 4 6p	100 40 6p	470 40 18p
4.7 63 6p	100 10 6p	100 63 12p	470 40 18p
6.8 63 6p	100 25 6p	100 100 10 12p	470 25 12p
6.8 63 6p	100 40 6p	100 150 6.3 10p	470 25 12p
10 25 6p	100 63 12p	150 16 6p	680 16 18p
10 63 6p	150 6.3 6p	150 25 6p	680 25 18p
15 40 6p	150 16 6p	150 40 6p	680 25 18p
15 40 6p	150 25 6p	150 63 12p	680 25 18p
15 63 6p	150 40 10p	150 100 10 12p	680 25 18p
22 10 6p	150 63 12p	150 150 6.3 10p	680 25 18p
22 25 6p	220 4 6p	150 220 6.3 10p	680 25 18p
22 63 6p	220 10 6p	150 220 16 6p	680 25 18p
33 6.3 6p	220 16 6p	150 220 25 10p	680 25 18p
33 16 6p	220 25 10p	150 220 40 12p	680 25 18p
33 40 6p	220 40 12p	150 220 63 18p	680 25 18p
47 4 6p	220 63 18p	150 220 100 10 12p	680 25 18p
47 10 6p	220 100 10 12p	150 220 150 6.3 10p	680 25 18p
47 25 6p	220 150 6.3 10p	150 220 150 16 6p	680 25 18p
47 40 6p	220 150 16 6p	150 220 150 25 10p	680 25 18p
47 63 6p	220 150 25 10p	150 220 150 40 12p	680 25 18p

PLUGS AND SOCKETS

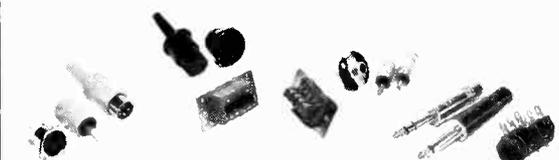

DIN PLUGS
2 pin (1 flat) 6p
3 pin 6p
4 pin, 5 pin A pair 10p
(180°), 6 pin 10p

MAINS
P360 3 pin 1.5A chassis plug with line socket 2p
SA 2190 3 pin 5A chassis plug 20p
SA 1862 Line socket for above 23p

DIN Sockets
2 pin 6p
3 pin, 4 pin, 5 pin 6p
A (180°), 5 pin B RPS 8 way chassis plug 47p

RSR 8 way chassis socket 62p

PHONO
Plug plastic 5p
Plug screened 12p
Chassis socket 4p

JACK
Std. 1/2" mono plug Plastic 13p
Screened 21p

Std. 1/2" stereo plug Plastic 18p
Screened 30p
Open mono socket 1/2" 10p; Moulded mono socket 1/2" with 2 break contacts 13p; Moulded stereo socket 1/2" with 3 break contacts 18p; 3.5mm plug plastic 7p; screened 15p; open socket 8p.

WE KNOW YOU NEED IT!

The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue.

and leave the rest to us!

OMNIVUM GATHERUM

PP3 6 etc., battery clip dual min 9p.
PPI 9 etc., battery clip separate per pair 6p.
Pair crocodile clips 1 red 1 black insulated sleeve 10p.
Soldier Multicore 22 s.w.g. 10 metres 20p
Silicone grease in special dispenser 20ml 43p.
Red neon 240V panel mounting 25p.
Lacing Cord. Strong rayon cord PVC 25m 51p.
Panel fuse holders 20mm 20p; 14in 35p.

Transformers
LT7000 main output transformer Pri. 1.2kΩ Sec. 5Ω 200mA 50p.

Sub-main. Mains Transformer
6-0-6V 100mA 95p, 12-0-12V 50mA 95p.
Size: Both approx. 30 x 27 x 25mm.

Mfin. Mains Transformer
Size: 46 x 31 x 38mm.
0-12V 250mA 0-12V 250mA £1.36.

Mains Transformer MT3AT
Pri. 200-220-240V. Sec. 12-15-20-24-30V 1A £3.31.

Mains Transformer MT206AT
Pri. 200-220-240V. Sec. 0-15-20V 1A. 0-15-20V 1A £3.98.

Hook-up wire, 7 strand 0.2mm. PVC covered tinned copper wire for light general connexions up to 1.4A 11 colours: black, blue, brown, green, grey, orange, pink, red, violet, white, yellow 10 metres of any one colour 20p. Pack of 11 (1 of each colour) 10m coils £2.05.

Single core screened 6p per metre.
Twin individually screened 10p per metre.
High quality single screened 50 (100p) per metre, ideal for high grade audio connexions 15p per metre.

Mains 3-core sub-miniature 1A black PVC covered 19 strand 0.1mm per conductor. 71p per metre.

POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle

Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 14p

Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 44p

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 28p

PRESETS
Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 25p

LINEARS

1.H0042C, TO99 (TO5), FET 1/2p Op Amp £4.25
LM301A, 8-pin DIL, Op Amp 50p
LM380 14-pin DIL, 2W Audio Amp £1.32
MC1303L 14-pin Stereo Pre-amplifier £1.39
MC1310P 14-pin DIL FM Stereo Decoder (no coils needed) £3.15
MFC4000B, 1W Audio Amp 38p
MFC8010, 8-pin case, 1W Audio Power Amp £1.20
MFC9020, 10-lead case, 2W Audio Power Amp £1.37
NE555V, 8-pin DIL, Precision Timer 79p
NE561B, 16-pin DIL, Phase Locked Loop £4.48
SG195D, 14-pin DIL, Four Quadrant Analogue Multiplier £2.70
uA723C, TO99 (TO5) 2 to 37V Voltage Regulator 80p
uA723C, 14-pin DIL, 2 to 37V Voltage Regulator 80p
uA741C, 8-pin DIL, Op Amp 36p
uA741C, 14-pin DIL, Op Amp 45p
uA747C, 16-pin DIL, Dual Op Amp £1.05
uA748C, 8-pin DIL, Op Amp 39p
ZN414, TO5, TRF Radio £1.20
More linears are listed in the "PE SOUND SYNTHESISER" box, above.
Full data, pin conversions, etc., on nearly all types above in our catalogue. Price 25p.

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each/82p
Mains rotary DPDT 250V 2A 20p.

Push to make non-locking 14p

Slide Sub-miniature DPDT 9p

Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl toggle) 77p

Toggle 250V 1.5A with ON/OFF plate 25p.

RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 11Ω to 910k E12 & E24 1p
Carbon Film 1W 5% 10Ω to 10M E12 34p
Metal Oxide 1/4W 9% 10Ω to 1M E12 & E24 4p
Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12 12p
Wirewound 2 1/2W 5% 1ohm to 27ohms E12 12p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

VAT Please add 10% to the final total.

Post and Packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex, Tel. Southend-on-Sea 0702 44101

NEW from A.S.P.


Also available 1 watt @ 70°C Carbon Film Resistors E12. Range: 10Ω to 2-1mΩ 5% tol., above 470kΩ 10% tol. Price 87p per 100.

CASED AUTO TRANSFORMERS

240 Volt Mains to 115 Volts, smart steel-cased units coated in tough resin, fitted with power lead, fuse and 115 Volt American type socket up to 500VA. above 500VA Cable entry.
VA (Watts) Price P. & P.
200 .. £5-56 £0-38
500 .. £9-50 £0-67
1000 .. £15-92 £0-92
2000 .. £29-70 £1-50
20VA version uncoated, no fuse £2-52 £0-30

MAINS KEYNECTOR

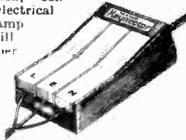The safe, quick, connector for electrical appliances, 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains, ideal for testing, demonstrating, window displays, etc. Warning Light, interlocked to prevent connecting when live.
Trade Price: £2-95. Post 25p.



ELECTRONIC MAINS TIMER

A reliable unit ideal for timing Bathroom/Toilet Ventilators, Stairway/Cloakroom Lighting, etc. Gives up to 30 mins. delay before switching off. Delay: 1-30 mins. adjustable. Max Load: 400VA or 1000 watts resistive. Ivory Case. 3 1/2" x 8 1/2" x 2". Fitting instructions included.
Trade Price: £5-80. Post 20p.



TRANSFORMERS

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen.		Price	Open	Post
VA	Ref.	£	£	£
(watts)	No.	Cased	£3-74	0-38
60	149	—	4-16	0-52
100	150	—	—	—
200	151	£9-48	7-48	0-52
250	152	12-05	9-57	0-65
350	153	14-00	11-44	0-80
500	154	15-80	13-20	1-00
1000	166	30-70	27-46	1-20
2000	168	60-95	55-44	—
3000	169	79-53	72-49	—

12 & 24 Volts

Amps	24V	Type	Price	Post
12V	No.	No.	£	£
0-3	0-15	242	1-34	0-22
0-5	0-25	111	1-34	0-22
1	0-5	213	1-59	0-22
2	1	71	2-09	0-22
4	2	18	2-75	0-38
6	3	70	3-56	0-42
8	4	108	3-98	0-52
10	5	72	4-87	0-52
12	6	116	5-87	0-52
16	8	17	6-84	0-52
20	10	115	10-23	0-69
30	15	187	13-75	0-97
40	20	232	18-26	1-00
60	30	325	22-52	1-10

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.		Price	Post
Amps	Type	£	£
0-5	112	£1-58	0-22
1	79	2-20	0-38
2	3	3-19	0-38
4	20	3-96	0-42
6	21	4-68	0-52
8	51	5-80	0-52
10	117	6-93	0-52
12	88	9-00	0-67
16	89	10-00	0-67

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.		Price	Post
Amps	Type	£	£
0-5	102	£2-11	£0-30
1	103	3-08	0-38
2	104	4-29	0-42
3	105	5-77	0-52
4	106	7-48	0-52
6	107	11-00	0-67
8	118	14-19	0-97
10	119	17-60	0-97

60 Volts

Prim. 200-240V. Sec. 24, 30, 40, 48, 60V.		Price	Post
Amps	Type	£	£
0-5	124	£2-10	£0-38
1	126	2-97	0-38
2	127	5-77	0-42
3	125	7-16	0-52
4	123	9-35	0-67
5	40	11-55	0-67
6	120	13-57	0-82
8	121	18-00	1-00
10	122	19-40	1-00
12	189	21-62	1-10

MINIATURE AND EQUIPMENT

Prim. 240V with screen.		Milliamps	Type	Price	Post
Sec. 1 Volts	Sec. 2	Sec. 1	Sec. 2	No.	£
3-0-3	—	200	—	238	1-23 0-10
0-6	0-6	500	500	234	1-80 0-10
0-6	0-5	1000	1000	212	1-88 0-22
9-0-9	—	100	—	13	1-23 0-10
0-9	0-9	330	330	235	1-48 0-10
0-8-9	0-8-9	500	500	207	2-28 0-22
0-8-9	0-8-9	1000	1000	208	3-03 0-30
15-0-15	—	40	—	240	1-23 0-10
0-15	0-15	200	200	236	1-30 0-10
20-0-20	—	30	—	241	1-23 0-10
0-20	0-20	150	150	237	1-80 0-10
0-15-20	0-15-20	500	500	205	2-97 0-38
0-20	0-20	300	300	214	1-78 0-22
0-20	—	3500 (No screen)	—	1116	3-00 0-40
20-12-0-12-20	—	700 (D/C)	—	221	1-55 0-30
0-15-20	0-15-20	1000	1000	206	3-80 0-38
0-15-27	0-15-27	500	500	203	3-08 0-38
0-15-27	0-15-27	1000	1000	204	3-24 0-38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 85p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 59p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p



PLEASE ADD 10% FOR V.A.T.

ADD 10p P. & P. PER ORDER

A.S.P. LTD. BYRE HOUSE · SIMMONDS ROAD · WINCHEAP CANTERBURY · KENT · Canterbury (0227) 52436

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME: _____

ADDRESS: _____ EB74

BLOCK CAPS please

MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/volt High Sensitivity Meter
£14-40.

4 1/2 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £3-65.

TAPE RECORDER LEVEL METER
500µA, 70p

MULTI-METER
Model 200H
20,000 ohm/volt, £6-60.

CARDIOID DYNAMIC MICROPHONE
Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £6-40.

3 WATT STEREO AMPLIFIER
£4-30

All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 8. Special prices for quantity quoted on request.

M. DZIUBAS
158 Bradshawgate · Bolton · Lancs. BL2 1BA

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- SA35** £4.45 Carriage free
35W RMS 25-50V
7 transistors, 7 diodes
- SA50** £5.65 Carriage free
50W RMS 25-65V
7 transistors, 7 diodes
- SA100** £10.90
100W RMS 45-70V
11 transistors, 6 diodes
- ★ 25Hz-25kHz
 - ★ 0.2% distortion
 - ★ Noise—80dB
 - ★ 500mV into 20K
 - ★ 4-16 ohms
 - ★ Simple wiring
 - ★ Short and open circuit proof
 - ★ Continuously rated
 - ★ Top-grade components



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED

- PU45** Suits 2 SA35 or 1 SA50 £4.90 Carriage 30p
- PU70** Suits 2 SA50 or 2 SA100 £7.75 Carriage 40p

STABILISED

- PS45** Suits 2 SA35 or 2 SA50 £3.50 Carriage free
- MT45** Transformer for above £3.50 Carriage 30p
- PS70** Suits 2 SA100 £4.90 Carriage free
- MT70** Transformer for above £4.90 Carriage 40p

N.B. PS70 is not suitable for the SA50

120 watt module complete with built-in supply—extra heavy duty £19.75 Carr. 60p

Mk II STEREO DISCO MIXER £19.75 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



DISCO MODULE £8.00 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add VAT 10% to all orders


MULTI-PURPOSE MIXERS

M4HL £18.50 Carr. 50p
M6HL £27.50 Carr. 50p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.50 Carr. free

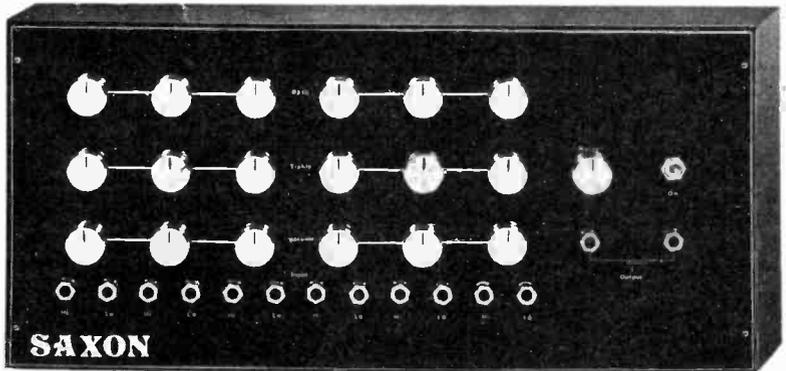
This is the basic channel 1 module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



SAXON CSE 100 COMPLETE AMPLIFIER

£34.90 Carr. free

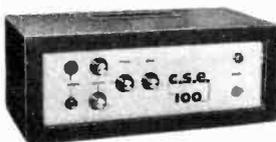100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynid case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29.50 Carr. free



sockets. Sturdy case, and an attractive facia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker sockets. Sturdy case, and an attractive facia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

SAXON 100 COMPLETE AMPLIFIER £53.00 Carr. free

SAXON 50 £37.50 Carr. free

CALLERS AND MAIL ORDER:


SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. 5 p.m. — LUNCH 12.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385

SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products. TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge. Please include S.A.E. with all enquiries. VAT at 10% must be added to all orders including postage and carriage charges.

BIG Discounts

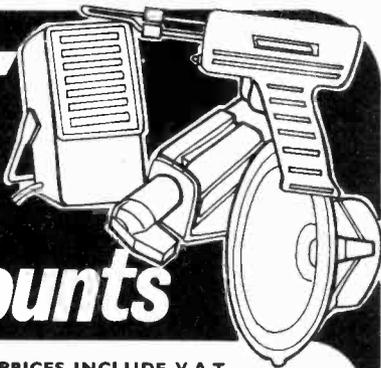

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£		
EMI 13in x 8in 3, 8 or 15 ohm			ELAC 10in 8 ohm Dual cone	3-85
Plain	2-00		GOODMANS 6in 8 ohm Dual cone	2-20
With Co-Axial Tweeter	2-20		FANE, 7in x 4in, 3 or 8 ohm	1-00
Twin Tweeter	3-55		CELESTION 8in, 15 ohm	1-85
Type 350, 8 or 15 ohm, 20W	7-50		ADASTRA 10in, 8 or 15 ohm, 10W	3-06
6in, 8 ohm, 10W	2-30		BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-65
8in, 8 ohm, 10W	3-75			P. & P. 0-25
12in, 8 ohm, 20W	8-50		5in, 8 ohm, 5W C/Mag.	0-85
8in x 5in, C/Mag. 5W	1-20		2 1/2in, 8 ohm or 64 ohm	0-60
8in x 5in, Dual cone 8 ohm, 10W	2-45			P. & P. 0-10
ELAC 8in 8 ohm Dual cone	2-25			

TWEETER AND CROSSOVER		£		
EMI 3 1/2in, 3 or 8 ohm C/Mag.	1-00		Dome Tweeter 8 ohm, 30W	4-85
Cone Tweeter 8 or 15 ohm, 10W	2-40		Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-05
Cone Tweeter 8 ohm, 3W	1-40			P. & P. 0-10
Horn Tweeter 8 ohm, 20W	5-85			

KIT FORM CABINETS, TEAK		£		
VEEER, 12in x 12in x 6in with 8in, 8in x 5in or 6in and 3 1/2in cutout	2-45		13in x 8in cutout	3-50
17in x 10in x 9in with 8in or			18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-25
				P. & P. each 0-35

MICROPHONES		£		
CM70 Planet, alkali metal, switch crystal	1-55		TW206 CONDENSER MIKE 600 ohm, uni-dir	5-75
DM160 Dynamic omni-dir, ball metal	4-95		Cassette Stick Mike with R. Control on/off switch (2-5 and 3-5mm J/Ply)	1-50
UD130 50K/600 ohm, uni-dir, ball metal	5-50			P. & P. 0-15

SOLDERING IRONS		£		
ANTEK CN24 15W	1-90		spare Btb, etc.)	3-80
SK1 Kit (10 watt iron, 2)			X25 25W (low leakage)	1-90
				P. & P. 0-10

CARTRIDGES		£		
ACOS GP91/28C or GP91/38C Stereo comp.	1-00		BSR SC5M Stereo ceramic	2-70
GP93/1 Stereo crystal	1-35		SX6H Stereo crystal	1-75
GP94/1 Stereo crystal	1-35		SX6M Stereo crystal	1-75
GP96/1	1-75		X5H Mono/stereo	1-45
GP101	0-75		X5M Mono/stereo	1-45
GP104	1-60		GOLDRING G800	3-85
SONOTONE 9THAC Stereo ceramic, diam.	1-80		G850	2-95
19-TT Stereo crystal	0-80		G800E	7-50
			STYLLI FOR ABOVE	P. & P. 0-05
			Sapphire 35p D. Diamond	1-25
			GOLDRING G800/G850	1-85
			G800E	3-85

BATTERY ELIMINATORS		£		
240V input 6, 7.5 or 9 300mA	2-20		output) 6, 7.5 or 9 d.c. output at 300mA	2-20
12V d.c. input (please specify)				P. & P. 0-10

TAPES		Std.	LP	DP	7in	70p	1-00	1-30
5in	45p	55p	70p		P. & P. 1-3 each			0-09
5 1/2in	55p	65p	85p		4 or more lot			0-30

LOW NOISE CASSETTES		£			
C60	35p	35p	30p	Cassette Head Cleaner	0-85
C90	45p	48p	40p	P. & P. 1-5 each	0-03
C120	55p	52p	50p	6-10 lot	0-15
				11-20 post free	

PLASTIC LIBRARY CASES for		£		
5in Reels	0-18		7in Reels	0-25
5 1/2in Reels	0-22		CASSETTE CASES	0-10
			P. & P. 1-3 each 5p; 4 or more	0-20

BIB ACCESSORIES		£		
Tape Editing Kit, Ref. 23	1-30		UNREPEATABLE SPECIAL OFFER!!	
Recording Tape Splicer, Ref. 20	1-15		De-Luxe CASSETTE RECORDER, MAINS/BATTERY, PORTABLE, REMOTE CONTROL MIKE, ETC. FANTASTIC VALUE AT	
Cassette Tape, Editing, Ref. 24	1-40		£14.95 ALL INC.	
Cassette Salvage Kit, Ref. 29	0-40		WORTH DOUBLE !!	
12" Cassette Case, Ref. 34	1-00			
Stylus Balance, Ref. 32A	1-15			
Spirit Level, Ref. 46	0-50			
Hi-Fi Stereo Test Cassette	1-90			
Groove-Kleen Record Cleaner	1-90			
	P. & P. 0-10			

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED

Riversdale Electronics
Mail Order Department PE/7
P.O. Box 470, Manchester M60 4BU

FOR QUALITY COMPONENTS

MOTOROLA

F. M. Multiplex Stereo Decoder	MC1310P	2.93	each
Four Channel SQ Decoder	MC1312P	1.75	
O/P Power Transistor	2N3055	0.65	

SIGNETICS

1/C Timer	NE555V	0.80
Dual 1/C Timer	NE556A	1.40
High Phased Locked Loop	NE560B	4.20
High Phased Locked Loop with AM Demod	NE561B	4.20
High Phased Locked Loop with Open VCO	NE562B	4.20
Precision Phased Locked Loop	NE565A	2.90
Function Generator	NE566V	1.55
Tone Decoder	NE567V	2.90

G.I.

Eight Digit Calculator Chip	C500	11.00
Eight Digit Calculator Chip	C550	9.50
3 1/2 Decade DVM Chip	AY-5-3510	6.40

MONSANTO

(MAN3M) 0.115" LED Seven Segment Display Q2501	1.10
--	------

FERRANTI

Radio Receiver	ZN414	1.20
----------------	-------	------


Data information supplied with each device.

Write for free catalogue of our large stocks of Ferranti, Motorola, G.I., Monsanto, Mullard, Signetics and R.C.A. components.
Add 20p Postage and Packing + 10% V.A.T. on total of order

S.C.S.
P.O. Box No 26,
(Dept PE)
Wembley,
Middlesex HA0 1SD,
England



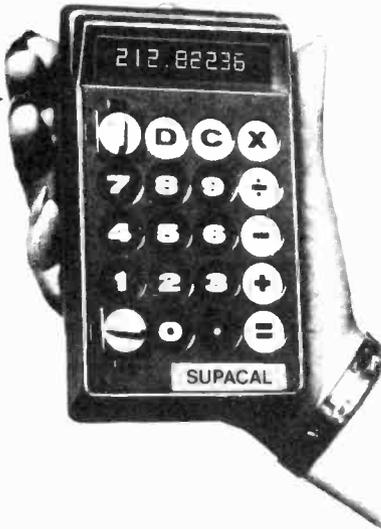A POCKET CALCULATOR FROM S.C.S. £4 DISCOUNT TO READERS OF P.E.



Just look at some of these features :

- 8 digit, fully floating decimal point.
- 4 function with a constant on all functions.
- Does not limit on over or underflow.
- Provides 8 significant figures plus decimal point position over 99 decades.
- Rechargeable batteries.
- Carrying case.
- Charger.
- Touch key board.
- Weighs just 8 oz.
- Measures 5½" x 3" x 1½".
- Full after-sales service.
- 1 year guarantee.

A unique, three-way link up between S.C.S., a major calculator manufacturer and Practical Electronics allows us to offer you a fully guaranteed pocket calculator. Powered by a second generation MOS LSI chip from General Instrument Microelectronics.

Available for £24 + V.A.T. (tested and guaranteed). **LESS SPECIAL £4 DISCOUNT TO ALL P.E. READERS** – don't forget to use your discount voucher.

A limited number of home constructor kits are available at £15 + V.A.T. (no discount).

£4 DISCOUNT VOUCHER

I enclose a cheque to the value of £20 + V.A.T. to cover the cost of the S.C.S. Pocket Calculator. (All cheques should be made payable to S.C.S. Components Ltd.) Total £22.

NAME _____

ADDRESS _____


S.C.S. Components Ltd. P.O. Box No. 26, Wembley, Middlesex HA0 1YY
Registered in London No. 888454.



ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO & MONO

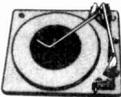Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSE reliability with 18 months' guarantee. AC 200/250V. Size 13" x 11 1/2". Above motor board 3 1/2". Below motor board 2 1/2". with STEREO and MONO XTAL **£6.75** Post 25p.




PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Padded lid. Chrome fittings. Size 17 1/2" x 15 1/2" x 7 1/2". Few only in red rexine. **£4.50** Post 25p. Motor board cut for BSR deck

4 Transistor Mono Amplifier

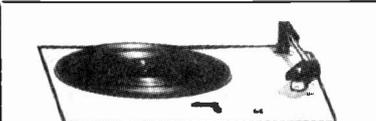Powerful 3 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. Size 8 1/2" wide x 4 1/2" deep x 3 1/2" high. Suitable 7 1/2" x 4 1/2" speaker. **£5.95** Post 25p



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop. Acoustereo mono cartridge. Base plate. Size 11 1/2" x 8 1/2". Turntable. Size 7 1/2" diameter. A.C. mains. 200, 250V motor has a separate winding 14 volt to power a small amplifier.

£5.50 Post 25p

METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position. 12 1/2" x 14 1/2" x 7 1/2". Covered in black leatherette. **£4.95** Post 45p

ALSO AVAILABLE IN SOLID NATURAL MAHOAGANY WAX POLISHED FINISH—£5.95

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2" x 10" x 3 1/2". 3 watts per channel. plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 240V AC Mains.



SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0 TO 60 MINUTES

Single pole two-way surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Fully insulated. Makers' last list price £4.50. Brand new and fully guaranteed. **OUR PRICE £1.65** Post 25p



BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2" sides 6 x 4 1/2" 45p; 8 x 6 1/2" 53p; 10 x 7 1/2" 65p; 12 x 8 1/2" 81p; 14 x 9 1/2" 90p; 16 x 10 1/2" 92p; 18 x 11 1/2" 101p; 20 x 12 1/2" 110p. **ALUMINIUM BOXES** 3 x 3 x 3 1/2" 60p; 4 x 4 x 4 1/2" 70p; 6 x 4 x 4 1/2" 80p; 8 x 4 x 4 1/2" 112p; 12 x 4 x 4 1/2" 130p. **ALUMINIUM PANELS** 18 s.w.g. 8 x 4 1/2" 12p; 8 x 6 1/2" 19p; 14 x 3 1/2" 90p; 10 x 7 1/2" 24p; 12 x 5 1/2" 29p; 12 x 8 1/2" 34p; 16 x 6 1/2" 34p; 14 x 9 1/2" 40p; 12 x 12 1/2" 47p; 18 x 10 1/2" 60p. **PAXOLIN PANEL** 10 x 8 1/2" 20p. 1 1/2" inch DIAMETER WAVECHANGE SWITCHES. 30p ea. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way. 1 p. 1. 2-way, or 4 p. 2-way, or 4 p. 3-way. **TOGGLE SWITCHES.** sp. 14p; dp. 22p; dp. dt. 25p. Sub-miniature, sp. 33p; dp. dt. 50p.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. **£2.20** Post 20p. Details S.A.E. Size 8 1/2" x 1 1/2" x 1 1/2".

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2" x 1 1/2" x 1 1/2". Response 25 c/s to 25 kc/s, 26 dB gain. For use with valve or transistor equipment. **99p** Post Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/850V 14p	250/25V 14p	50 + 50/300V	50p
4/50V 4p	500/25V 20p	80 + 100/350V	85p
8/450V 18p	1000/25V 35p	32 + 32/250V	20p
16/450V 25p	1000/50V 47p	32 + 32/450V	60p
32/500V 50p	8 + 8/450V 22p	350 + 50/325V	55p
25/25V 10p	8 + 16/450V 22p	16 + 16 + 16/275V	45p
50/50V 10p	16 + 16/450V 40p	32 + 32 + 32/350V	65p
100/25V 10p	32 + 32/350V 40p		

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0.01mF. 4p. Silver Mica 5 to 5000pF. 4p.
PAPER 350V-0.1 4p; 0.5 13p; 1mF 15p; 2mF 150V 15p.
500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 8p; 1.0 8p.
SILVER MICA. Close tolerance 1%. 2.2-500pF 8p; 560-2,200pF 10p; 2,700-5,800pF 20p; 6,800pF-0.01, mfd 30p each.
TWIN GANG. "0-0" 208pF, 176pF, 65p.
Slow motion drive 365pF + 365pF with 25pF + 25pF, 50p; 500V standard 25pF, 100V 50p. **£1.60**
SHORT WAVE SINGLE. 10pF, 30p; 25pF, 55p; 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. **50p** each. Values up to 100pF. Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS 250V AC/DC. Amber 20p. RESISTORS 1W, 1/2W, 1/4W, 20% 1p; 2W, 5% 10p. 10Ω to 10M. HIGH STABILITY. 1/2W 2%; 10 ohms to 8 meg. 10p. DITTO 5%. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2 watt, 0.5 ohm to 8.2 ohms 10p. TAPE OSCILLATOR COIL Valve type 35p. FERRITE ROD 8 x 1/2" 20p; 6 x 1/2" 20p; 3 x 1/2" 10p.

MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12V 50mA 90p
250-0-250 80 mA. 6.3V 3-5A 6.3V 1A or 5V 2A £2-50
350-0-350 80 mA 6.3V 3-5A 6.3V 1A or 5V 2A £3-00
300-0-300V 100mA. 6.3V 4A C.T.; 6.3V 2A C.T. £4-25
MINIATURE 200V 20mA, 6.3V 1A 2 1/2" x 2 1/2" 75p
MIDGET 220V 45mA, 6.3V 2A 2 1/2" x 2 1/2" 90p
HEATER TRANS. 6.3V 1 amp 85p, 1 1/2 amp 75p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £3-00
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3-00
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4-00
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2-75
3 amp, 5, 8 and 13V £1-00; Ditto 5 amp £1-20, 3 amp; 3, 5, 8, 10, 13 and 6-0-5V £1-30, Ditto 5 amp £1-50; 6-0-6V 500mA 90p 9V 1 amp 95p 12V 300mA 75p 12V 500mA 85p 12V 750mA 95p. 40V 1 amp £1-75.
AUTO TRANSFORMERS. 115V to 250V or 250V to 115V 150V £2-80; 500V £2-25; 750V £10; 1000V £15
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1 1/2 amp £1-50; 2 amp £1-80; 4 amp £2-50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4-50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **£10** Carr. 50p. Famous make (Value £19) OUR PRICE Can be used as 800 watt auto transformers 240-110V.

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK

£2.50 Post 50p

VOLUME CONTROLS 80 ohm Coax 5p yd.

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p. Wire Wound controls 1 1/2" diam. 3 Watts. 10 ohms to 100K British Made with long spindles 1/2" dia. 45p each. HELICAL POT 10K LIN. List £3. 45p. DUAL CONCENTRIC POT 500K LOG AND 500K LIN D.P. switch. Inner spindle 3 1/2"; outer spindle 2 1/2" 75p.

E.M.I. 1 1/2" x 8in. SPEAKER SALE!

With twin tweeters. **£4.50** Post 25p. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p. With dard tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p



Bookshelf Cabinet 16" x 10" x 8in. Teak finish Post 35p **£6.60**

E.M.I. 6 1/2in. HI-FI WOOFER

8 ohm 10W. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12" x 8" x 24" Suitable Tweeter £2 **£4**



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2" x 2 1/2" deep. Rating 10W, 3 ohm. Crossover £1-25 **£1.90** Post 25p.

GOODMANS 8in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass response 35 cps. Frequency response 30-8,000 cps. Ideal bass unit for Hi-Fi system. **£3.75**



SPECIAL OFFER LOUSPEAKERS ALL BRAND NEW

3 ohm, 2 1/2"; 2 1/2"; 3 1/2"; 5in. 8 ohm, 2 1/2"; 2 1/2"; 5in x 3in; 5in. 15 ohm, 3 1/2"; 6in; 6 x 4in; 5 x 3in; 7 x 4in; 8 x 5in. 25 ohm, 2in; 3in; 5 x 3in; 5in. 35 ohm, 2in; 3in; 5in. **£1** EACH

LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in £1-25; 6 1/2in £1-50; 8 x 5in £1-60; 8in £1-75; 10 x 6in £1-90; 10in £2-50
RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in diameter 4W £2-50, 10 in diameter 6W £2-50; Post 25p. 12in diameter, 6W, £2-95; 3 or 8 or 15 ohm model.
SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kc/s. 8W 8 ohm or 15 ohm £2-20. De Luxe Horn Tweeters 2-18Kc/s, 15W, 15 ohm £2-50. TWO-WAY 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm £1-25.

TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 3 1/2" x 4 1/2" with control knob, tweeter and woofer leads and input terminals. Suitable for 3 or 8 ohm impedance. **£3.80** Post 20p

VALVE OUTPUT TRANSFORMER 40p. MIXER TRANSFORMER MU metal 100-1 £1-25. PUSH-PULL VALVE OUTPUT TRANSFORMERS. 50 watt £12-50 100 watt £16-00

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 200 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electric magnetism or for metronome. **95p** 20p

R.C.S. RECORD PLAYER AMPLIFIER

2 stage triode pentode valve. 3 watts output. Volume on/off and tone control. Printed circuit. A.C. mains complete and tested. **£4.50** 25p

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p OUTLET BOXES, SURFACE MOUNTING 25p. BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd. JACK SOCKET Std. open-circuit 14p. closed circuit 20p; Chrome Lead Socket 45p. Phono Plugs 7p. Phono Socket 7p JACK PLUGS Std. Chrome 20p; 3.5mm Chrome 15p DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

ALL PRICES INCLUDE VAT • 20p MINIMUM POST AND PACKING • CALLERS WELCOME •

RADIO COMPONENT

Illustrated Colour Brochure, Radio Books & Components Lists 10p Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£6.75 THE PAIR, Post 25p. (Available separately. Woofer £5.25; Tweeter £1.50)

Comprising a fine example of a Woofer 10" x 6 1/2" with a massive Ceramic Magnet, 44oz Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2" square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps
SUITABLE ENCLOSURE 20 x 13 x 9 in.
MODERN DESIGN. TEAK WOOD FINISH.



£9.90
Post 45p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

10in round **£4.50**.

£3.75

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts

MODEL "A". 20 x 13 x 9 in. For 12 in. dia. or **£9.90** Post 25p

MODEL "B". 18 x 10 x 9 in. For 13 x 8 in. or **£6.60** Post 8 in. speaker **£25p**
MODEL "B" 2 ditto. Triangular Corner Version.

MODEL "C". 18 x 8 x 6 in. For 8 x 5 in. **£4.95** Post speaker **£25p**

LOUDSPEAKER CABINET WADDING 18in wide, 15p fl.



BARGAIN AM TUNER.

Medium Wave. Transistor Superhet Ferrite aerial. 9 volt. **£4.95**

BARGAIN 4 CHANNEL TRANSMITTER MONO MIXER.

Add highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£4.50**

STEREO VERSION OF ABOVE £5.95.

BARGAIN FM TUNER.

88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. **£12.85**

BARGAIN FM TUNER. £8.85

As above less cabinet.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£4.50**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£3.50** Post 20p



BAKER MAJOR 12" £9.90



Post Free
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12.50**
Post Free

Please state 3 or 8 or 15 ohms. Post free

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8.80**
12in 25 watt
3, 8 or 15 ohms.
Post Free

GROUP "35" **£9.90**
12in 35 watt
3, 8 or 15 ohms.
Post Free

GROUP "50" **£22.00**
15in. 50 watt
8 or 15 ohms.
50 watt 12in VERSION £17.60



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E.



£49 Carr. £1.00

CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm Loudspeaker matching. **£69**

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

Sizes 1"	74p	Sizes 1 1/2"	£1.70
Key "A" for above	83p	Key "B" for above	10p
Key "T" for above	6p	2"	22-25
1 1/2"	90p	2 3/32"	22-50
1 1/4"	92p	2 1/2"	23-30
1 1/8"	99p	Key "C" for above	12p
Key "A" for above	6p	2 1/2"	24-50
1 1/2"	11" £1.00	2 1/2"	25-75
1 1/4"	11" £1.15	3"	29-00
1 1/8"	11" £1.20	Key "E" for above	20p
1 1/2"	11" £1.35	1" Square, with key	22-10
1 1/4"	11" £1.55		

SPECIAL OFFER

20 Watt 100 ohm Rheostat 2 1/2 in dia. Ceramic former screw terminals 1/2 in dia. spindle. 95p. Post 25p.

SPECIAL OFFER £1.75. Post 25p.

3in Panel Meter 50 uA. Unusual scale requires re-calibration. Few only 25p. a same price.

WEYRAD COILS

P50/LAC	40p	RA2W	85p
P50/2CC	40p	OPT1	85p
P50/3CC	40p	LFDT4	85p
PCA1	60p	Twin gang	75p



DELUXE 4 POLE MOTOR

1,400 r.p.m. reversible 42 Watt, spindle 1 1/2 in x 7/32 in, size 3 1/2 in x 3 in. As illustrated. 240V a.c. mains. **£1.95** Post 25p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2 1/2" x 2 1/2" in. **£1.00** Post 25p

BAKER HI-FI SPEAKERS HIGH QUALITY - BRITISH MADE REGENT

12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000 gauss
Useful response 45-13,000cps
8 or 15 ohm models.

£8.80

Post Free

DE-LUXE Mk II

12in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£11

Post Free

SUPERB

12in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures a clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£16.50

Post Free

AUDITORIUM

12in. 25 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs, Ideal for Hi-Fi and Discotheques.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£15.40

Post Free

AUDITORIUM

15in 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£22

Post Free

Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free.

CUSTOMERS FREE CAR PARK

OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD · CROYDON

(Export: Remit cash and extra postage.)


Buses 50, 68, 159. Rail Selhurst

Telephone 01-484-1665

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK, 9.00 a.m.-6.00 p.m.



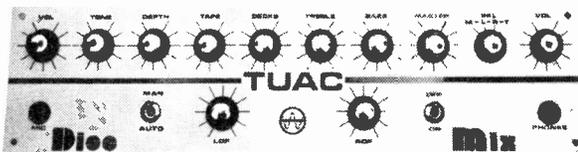TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD.
DEPT. E
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080



TUAC DISCOTHEQUE MIXER WITH AUTO FADE
Designed for the discerning D.J. of professional standard.
£27.00
Offering a vast variety of functions.
Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw, Tape Vol, L & R Deck Faders, Deck Volume, Treb. & Bass, H. Phon Vol, Selector, Master Vol, on/off sw, Max. output 1V RMS. Specification: Vol. Treb and Bass Controls, 8mV sensitivity, Treb + 28 - 15dB at 12kHz; Bass = 18dB at 40Hz;
PANEL SIZE 18 x 4 1/2in. DEPTH 3in.


POWER SUPPLY £4.75

NEW! 3 channel Light Modulator

- ★ 1,000 watts per channel
- ★ Operates from 1/8 watt to 100 watts
- ★ Full wave control
- ★ Fully fused and suppressed
- ★ 12 easy connections

£15.25

Single channel version £6.75

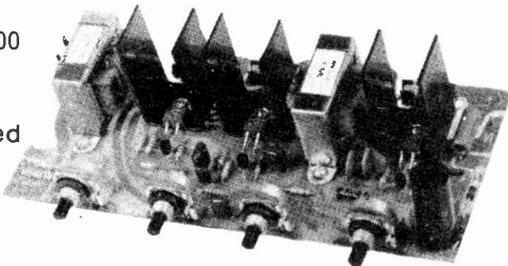

NEW! NEW! NEW!

TUAC FLASHING BEACONS:
AS USED BY AMBULANCE, FIRE SERVICES, ETC.


- ★ Instant stop and start motor for precise control.
- ★ Choice of 4 models, 12V, 24V, 110V and 240V.
- ★ Magnetic base—may be attached to any metal surface.
- ★ 240V model suitable for use with light modulator.
- ★ Available in 4 colours—red, blue, amber and clear.
- ★ Only £22.

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING
ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT PRICES

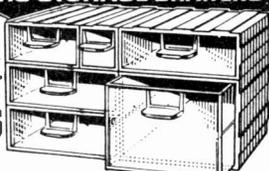

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES
ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2 1/2ins x 2 1/2ins). £1.75 DOZEN.
DOUBLE UNITS (2D) (5ins x 4 1/2ins x 2 1/2ins). £3 DOZEN.

TREBLE (3D) £2.90 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4.25 for 8.

EXTRA LARGE SIZE (6D1) £3.90 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7 1/2% in the £
Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES
Please add 10% V.A.T. to total remittance

FLAIRLINE (Dept. PE7) 124 Cricklewood
Boulevard, London, N.W.2
Tel. 01-450 4844

OSMABET LTD.

We make transformers amongst other things.

AUTO TRANSFORMERS, 110/200/220/240V.
30W, £1.70; 50W, £2.40; 75W, £2.85; 100W, £3.80; 500W, £10.80; 750W, £14.25; 1000W, £18.00, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 1.5A, £1.20; 3A, £1.50; 6A, £2.55; 12V 1.5A, £1.50; 3A, £2.55; 6A CT, £3.40; 18V 1.5A CT, £2.55; 24V 1.5A CT, £2.55; 3A CT, £2.45; 5A, £4.80; 8A, £7.35; 12A, £10.85; 40W 3A CT, £4.50; 50V 6A CT, £13.50; 25V 2A+25V 2A, £4.90; 12V 4A+12V 4A, £4.90.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V 0-10-12-14-16-18V 2A, £2.60; 4A, £3.75; 0-12-16-20-24-30V 2A, £3.40; 4A, £4.50; 0-5-20-30-40-60V 1A, £3.40; 2A, £4.50; 0-40-50-60-80-90-100-110V 1A, £4.90.

MIDGET RECTIFIER TRANSFORMERS.
For FW rect. 200/240V a.c. 9-0-9V 0.3A; 12-0-12V 0.25A; 20-0-20V 0.15A; 6V 0.5A + 6V 0.5A; 9V 0.35A + 9V 0.35A; 12V 0.25A + 12V 0.25A or 20V 0.15A + 12V 0.15A at £1.65 each; 9-0-9V 1A, £1.35; 12-0-12V 1A or 20-0-20V 0.75A £1.50 each.

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec., 425-0-425 500 Ma, 6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A, £16.50; TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £9.75; MT3 Prim. 0-110-240V sec., 250V 100 Ma, 6.3V 2A, F/S, £2.70.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3-8-15ohms, A-A 6.6K 0 30W, £6.70; A-A 3K 0 30W, £9.90; 100V (EL34 KT88, etc.), £15.75; tapped Multi O/P 10W £3.

G.E.C. MANUAL OR POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W, £7.80; 35W, £8.40; HI-FI Major Module 20W w/tweeter Xover, £11.80; Baker-speaker lts: FANE 50W, £10.50; 60W, £13.50; HI-FI speakers, EMI bass 15 x 8in 3 or 15 in, £2.00; 8in 8 in, £1.15; 7 x 4in 15 in, £1.60; 8 x 5in 3, 4, 15, 25 or 80 in, £1.75 each.

LOUDSPEAKERS
2 1/2in 8, 16 or 75 in, 2 1/2in 8 or 25 in, 3in 3, 8, 25 or 35 in, 3 1/2in 8, 15 or 80 in 90p each; 5in 3, 8 or 25 in, 5 x 3in 3 or 8 in, £1.05; 7 x 4in 3 or 15 in, 6 1/2in 3 in, £1.25; 10 x 8in 3 in, £1.50.

SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15 in up or down £1.80.

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads. 200/240V a.c. £3.25.

CODENERS
Paper block 4in x 800V, 75p; Electrolytic 1000µf 350V, 50p; 200 + 100 + 100µf 350V, 50p.

Carrriage and VAT on all orders

S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 9YG
Tel. 01-958 9314

4-STATION INTERCOM



£13.95

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft and other accessories. P. & P. 47p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £22.95 per pair. P. & P. 60p extra.

INTERCOM/BABY ALARM



£6.50

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Doot Phone. Complete with 6ft connecting wire. Complete with battery. P. & P. 30p.

Transistor TELEPHONE AMPLIFIER



£4.95

Why not boost business efficiency with this incredible Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/5)
160 KENSINGTON HIGH STREET, LONDON, W.8

C. T. ELECTRONICS

267 Acton Lane, London W4 5DG

Tel. 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

semiconductors

AC107	35p	BCY33	45p	MJE370	75p	OC77	40p	ZTX504	50p	2N2907	30p
AC125	25p	BCY34	45p	MJE371	80p	OC81	25p	ZTX531	30p	2N2926G	13p
AC126	25p	BCY36	60p	MJE520	80p	OC83	25p	ZTX550	30p	2N3053	25p
AC127	25p	BCY39	80p	MJE521	75p	OC84	25p	1N914	8p	2N3054	60p
AC128	25p	BCY55	£1.20	MJE2955	£1.95	OC139	40p	1N916	8p	2N3055	65p
AC176	25p	BCY70	22p	MJE5055	85p	OC140	25p	1N4001	7p	2N3232	70p
AC187	25p	BCY71	20p	MM1913	43p	OC170	25p	1N4002	8p	2N3440	60p
AC188	30p	BCY72	20p	MM1712	60p	OC171	25p	1N4003	9p	2N3702	14p
AD140	55p	BD121	75p	MPF102	45p	OC200	50p	1N4004	10p	2N3703	12p
AD149	85p	BD123	75p	MPF103	40p	OC201	60p	1N4005	12p	2N3704	12p
AD161	44p	BD124	75p	(2N5457)	35p	OC202	75p	1N4006	13p	2N3705	12p
AD162	44p	BD131	75p	MPF104	40p	OC205	80p	1N4007	14p	2N3706	12p
AF114	25p	BD132	75p	(2N5458)	40p	TIP29A	50p	1N4148	7p	2N3707	12p
AF115	25p	BD153	75p	MPF105	40p	TIP30A	60p	2N696	30p	2N3708	12p
AF116	25p	BD156	75p	(2N5459)	40p	TIP31A	65p	2N697	25p	2N3709	14p
AF117	25p	BDY11	£1.40	NKT135	35p	TIP32A	75p	2N698	25p	2N3771	£2.80
AF118	50p	BF152	20p	NKT222	25p	TIP33A	£1.05	2N706	12p	2N3772	£3.00
AF172	30p	BF194	14p	NKT401	75p	TIP34A	£1.55	2N706A	15p	2N3773	£3.40
BA102	30p	BF195	15p	NKT404	80p	TIP35A	£3.35	2N708	15p	2N3819	35p
BA112	60p	BF196	15p	NKT773	25p	TIP36A	£3.85	2N930	20p	2N3820	55p
BA114	18p	BF209	30p	NKT774	25p	TIP41A	75p	2N1132	25p	2N3866	85p
BC107	14p	BFX84	30p	OA5	25p	TIP42A	95p	2N1302	20p	2N3904	22p
BC108	14p	BFX85	30p	OA10	50p	TIP29B	60p	2N1303	20p	2N3905	22p
BC109	14p	BFX86	30p	OA47	10p	TIP30B	70p	2N1304	25p	2N4058	12p
BC109c	16p	BFX87	30p	OA70	12p	TIP31B	75p	2N1305	25p	2N4059	12p
BC147	12p	BFX88	30p	OA81	10p	TIP32B	85p	2N1306	25p	2N4060	12p
BC148	12p	BFY44	50p	OC10	10p	TIP33B	£1.20	2N1307	25p	2N4061	14p
BC149	12p	BFY50	25p	OA81	10p	TIP34B	£1.75	2N1308	35p	2N4062	17p
BC157	14p	BFY51	25p	OA200	10p	TIP35B	£2.90	2N1309	35p	2N4286	15p
BC158	14p	BFY52	25p	OA202	10p	TIP36B	£3.80	2N1613	25p	2N4287	15p
BC159	14p	BFY53	25p	OA210	35p	TIP29C	75p	2N1711	25p	2N4288	15p
BC169c	15p	BFY90	60p	OA211	35p	TIP30C	85p	2N2160	85p	2N4289	15p
BC182	13p	BSW63	80p	OC16	90p	TIP31C	90p	2N2217	25p	2N4290	15p
BC183	13p	BSW68	75p	OC19	85p	TIP32C	£1.10	2N2218	30p	2N4444	£1.90
BC184	13p	BSY95a	12p	OC22	55p	TIP33C	£1.35	2N2219	35p	2N4871	35p
BC212	15p	BY127	20p	OC26	65p	TIP34C	£2.00	2N2222	25p	2N5191	95p
BC213	15p	BY164	60p	OC28	65p	TIP35C	£3.25	2N2224	25p	2N5194	£1.10
BC214	15p	IS103	15p	OC35	60p	TIP36C	£4.25	2N2398	70p	40360	50p
BC238	14p	MJ340	50p	OC44	20p	TIS50	40p	2N2846	50p	40361	50p
BC239	14p	MJ481	95p	OC45	20p	ZTX107	15p	2N2846	£1.50	40362	55p
BCY30	40p	MJ2801	£1.20	OC71	17p	ZTX300	15p	2N2904	30p		
BCY31	55p	MJ2801	£2.20	OC75	25p	ZTX500	18p	2N2905	45p		
BCY32	95p	MJE340	50p	OC76	25p	ZTX501	20p	2N2906	25p		

Semiconductor QUANTITY DISCOUNTS—12+ 10%, 25+ 15%, 100+ 20% mixed types, transistors and I.C.s. Larger quantity discounts. Phone for details.

74 SERIES I.C. s (TTL)

SN7400	20p	SN7411	23p	SN7430	20p	SN7474	38p	SN7494	85p
SN7401	20p	SN7412	23p	SN7432	30p	SN7475	44p	SN7495	85p
SN7402	20p	SN7413	30p	SN7433	43p	SN7476	46p	SN7496	£1.00
SN7403	20p	SN7416	30p	SN7437	45p	SN7477	50p	SN7497	£4.32
SN7404	20p	SN7417	30p	SN7438	43p	SN7478	45p	SN74100	£2.16
SN7405	20p	SN7420	20p	SN7440	20p	SN7480	80p	SN74107	51p
SN7406	40p	SN7422	28p	SN7441A	85p	SN7482	87p	SN74110	57p
SN7407	40p	SN7423	40p	SN7442	85p	SN7483	£1.20	SN74111	86p
SN7408	25p	SN7425	37p	SN7450	20p	SN7484	£1.00	SN74118	£1.00
SN7409	33p	SN7427	37p	SN7451	20p	SN7485	£1.50	SN74119	£1.82
SN7410	20p	SN7428	43p	SN7453	20p	SN7490	75p	SN74121	57p

TRIACS

TXL228B 8A 400V	95p
SC40D	£1.40
SC40E	£1.85
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.82
DIAC	25p

VEROBOARD

25 x 34	0.1 0.15
25 x 5	24p 19p
31 x 3	27p 28p
31 x 5	27p 28p
31 x 5	31p 31p
17 x 2 1/2	89p 68p
17 x 3 1/2	£1.10 87p
17 x 5 (plain)	98p 90p
Pin insert tool	57p
Spot face cutter	46p 46p
Plk 36 Pins	20p 20p

S.C.R.'s

CRS1/05	40p
CRS1/10	56p
CRS1/20	60p
CRS1/40	65p
CRS1/60	90p
CRS3/10	62p
CRS3/20	62p
CRS3/40	62p
CRS7/40	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.60
C106B	45p
C106D	70p
40669	90p
TIC44	35p
2N4444	£1.90

V41 Vu meter

£2 50
The V41 is calibrated -20 to -3 and 0-100% making it suitable for use as a recording level meter or as a power output indicator.
Sensitivity: 130 µA Internal resistance 800 ohms Dimensions: 40 x 40 x 29mm

3A 200V Rec. Diode

LM7309K 5V 1A voltage reg	£2.10
LM723C 2-37V 150mA voltage reg	£1.05
MFC4000 250mW audio	60p
TBA800 5W audio	£1.50
7090 OP Amp OIL T099	45p
741C OP Amp 8 1/4 OIL T099	55p
748C OP Amp OIL	75p
747C Dual OP Amp	£1.20
2N414 Radio I.C	£1.25
TAD100 Radio I.C inc filter	£1.90
CA3014	£1.55
CA3018	£1.90
CA3028	£2.00
CA3036	£1.00
CA3046	95p
CA3048	£2.35
CA3075	£1.00
CA3090D	£4.85
MC1303L	£2.20

D.I.L SKTS

8 Pin	18p
14 Pin	18p
16 Pin	18p

ZENER DIODES

BZY88 series 400mW	10p
3 3V-33V 5%	25p
1.5W range	45p
10W range	

L.E.D.

TIL209	28p
HP5082	28p
MA2082R	25p

L.D.R.

ORP12	60p
ORP71	90p

NE555

Timer I C 90p
POWER SUPPLY. 12V 6.5A Stabilised Power Supply. Contains 18-5V 8.5A sec Transformer. 4 x 4,000µF 25V Mullard capacitors. 2 x 2N3055 on 2 Redpoint heatinks. 12A, 120V Bridge rectifier, stabilised p.c.b circuit diagram. The parts alone are worth the asking price of £13 each, inc carriage

BRIDGE RECTIFIERS

W02 1A 200V	38p
BY164 1-4A 200V	57p
MDA952/6A 100V	80p

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 10% to all orders. Carriage orders under £5 + 20p Over £5 post free U.K.

NEW SERIES TRANSISTOR DATA BOOKS

- DTA3 USA Band 3 Transistor Characteristics; 2N21-2N6269 numbers.
 - THT Thyristor, Triac, Diac, Put, UJTs.
 - DTJ5 Japanese Transistor Characteristics, 2SA, 2SB, 2SC, 2SD numbers.
 - DVT Diode Comparison Tables.
 - Band 1. Transistor Characteristics, European numbers AC, AF, BC, BF, etc.
 - TVT Transistor Equivalent Tables.
- All books contain pin connections and semiconductor outlines.
Price: £1.10 per book; £6 per 8 books inc. post.

AUDIO ACCESSORY SHOP

17 TURNHAM GREEN TERRACE, CHISWICK, W.4

VALVE AMPLIFIERS

5 Watt	£12.50	50 Watt	£36.25
15 Watt	£24.50	150 Watt	£75.90
30 Watt	£29.50	500 Watt	£124.50

TRANSISTOR AMPLIFIERS

FAL Phase 50W	£39.93	FAL Phase 100W	£89.95
---------------	--------	----------------	--------

DISCO CONSOLES

FAL Disco Mk 2	£82.99	FAL Power Disco (with 70W rms Amp)	£123.75
----------------	--------	------------------------------------	---------

HEAVY DUTY LOUDSPEAKERS

* SPECIAL OFFER PRICE *	3 channel sound-light Oilwheel 6in dia. Stroke 4 joule	£22.50
15 in. 70W. E.M.I. 8 ohm	15 in. 70W. E.M.I. 8 ohm	£5.25
Decca 8in. 10 watt Hi-Fi Speaker	Strobe 4 joule	£1.00
plus matching tweeter. £7.50 complete. Suitable 2-way cross-over	Triple flash box (100W Red, Blue, Gn. Yel.)	£7.50
	DISCO LIGHTING	
	Triple flash box	£18.25
	Sound-lighting module	£7.90
	150W Projector and Wheel	£25.00

TEAK VENEERED SPEAKER CABINETS

For 8 x 5in Speaker	Size 7 1/2in x 11 1/2in x 5 1/2in	£3.50
For 8in x Tweeter	9 1/2in x 13 1/2in x 5 1/2in	£5.00
For 13 x 8in	10 1/2in x 17in x 6in	£5.75
For 13 x 8in - Tweeter	12in x 18in x 8 1/2in	£7.50
For 12in - Tweeter	15 1/2in x 18in x 8 1/2in	£9.00

REXINE COVERED SPEAKER CABINETS

Suitable for P.A. or DISCO use takes 12in speaker unit. Size approx. 18in x 18in x 8in £9.00

SPEAKER CLOTH

Available in Black or Green approx width 54in £1.75/yd

HEADPHONES

Type H-202 Features Mono/stereo switch Volume controls on each channel. Freq response 20-20,000Hz Impedance 4-16 ohms £4.50

ALUMINIUM BOXES

AB7	2 1/2 x 5 1/2 x 1 1/2in	50p	AB14	7 x 5 x 2 1/2in	84p
AB8	4 x 4 x 1 1/2in	50p	AB15	8 x 6 x 3in	£1.08
AB9	4 x 2 1/2 x 1 1/2in	50p	AB16	10 x 7 x 3in	£1.22
AB10	4 x 5 1/2 x 1 1/2in	50p	AB17	10 x 4 1/2 x 3in	£1.08
AB11	4 x 2 1/2 x 2in	60p	AB18	12 x 5 x 3in	£1.20
AB12	3 x 2 x 1in	44p	AB19	17 x 8 x 3in	£1.60

ELECTRONIC COMPONENTS


BARGAIN COMPONENT PACKS

look!

electronics really mastered

... practical
... visual
... exciting!

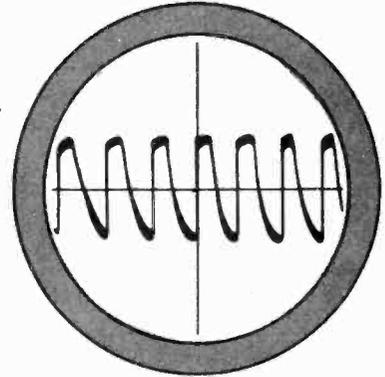no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

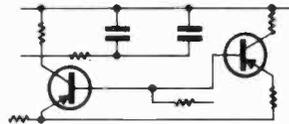2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

**3/ CARRY OUT
OVER
40 EXPERIMENTS
ON BASIC ELECTRONIC
CIRCUITS & SEE HOW
THEY WORK, including :**

valve experiments, transistor experiments
amplifiers, oscillators, signal tracer, pho-
to electric circuit, computer circuit, basic
radio receiver, electronic switch, simple
transmitter, a.c. experiments, d.c. experi-
ments, simple counter, time delay circuit,
servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL74

special free gift also to all our students

PE

SOUND POWER

AUDIO power amplifiers find their way into a very extensive and diverse range of equipments and systems, quite apart from the domestic entertainment area. The exuberant folk music of today, whether originated "live" or recreated from discs, is borne along on hundreds of watts. Public Address systems reach out as never before to cajole or inform captive audiences or, just as probably, innocent passers by. Just two of the more blatant uses of sound power.

No one can avoid the fact that amplified sound is very much part of the contemporary scene. The propriety of its widespread use can be argued about but its presence is real and, presumably, permanent.

Those concerned with technical matters can, at any rate, do their best to ensure that the amplifying medium, for its part, is beyond reproach and does not introduce gratuitously any (further) distortion. In fact, it is generally agreed that this branch of the technology has made impressive progress and audio engineering has reached almost the ultimate in the quest for faultless performance. The evidence lies among the huge variety of amplifier designs which have been developed.

Yet the question could well be posed: are there not too many designs?

The need for off-the-shelf designs to meet the constantly occurring demands for certain basic units (such as audio power amplifiers and power supply units) which form indispensable sections of many electronic systems, has been a theme of discussion among electronics people over the years. The logic behind this thought is undeniable, but the ideal general purpose design has never materialised, save in certain rather limited areas. So designs for standard routine functions still proliferate.

The continual up-dating of the technology through the introduction of new components is the stumbling block. Electronics is synonymous with change. A well proven standard device, equipment, or system is likely to have a limited life before the inevitable innovation or improvement happens.

Yet even within this volatile field there has perhaps been a rather excessive outpouring of amplifier designs than is altogether warranted.

There is still a reasonable life expectancy for many designs; and when considering a widely used item such as an a.f. amplifier there is good sense in stabilising the position as long as possible by fully exploiting one single design. If the design is capable of being produced in a number of different "sizes" so catering for the majority of power-requirements commonly called for through the simple expedient of changing component values, the attractiveness of this policy is unquestionable.

This idea materialises in our pages with the introduction of a family of audio power amplifiers. The P.E. Power Slaves comprise a family of four amplifiers having outputs of 20, 40, 65 and 100 watts respectively, suitable for use with hi fi pre-amplifiers. Furthermore any unit can easily be built in a two-channel form with a doubling of output power. Good performance, with low harmonic distortion and good signal to noise ratio, justify the claim that the P.E. Power Slaves are a step towards that goal of a universal power amplification block for embodiment in all kinds of sound reinforcement systems.

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*

Phone: 01-634 4301

Editorial & Advertising Offices:


Fleetway House, Farringdon St.,
London EC4A 4AD

Phone: Editorial 01-634 4452

Advertisements 01-634 4202

PE POWER SLAVES

BY R. B. REESON

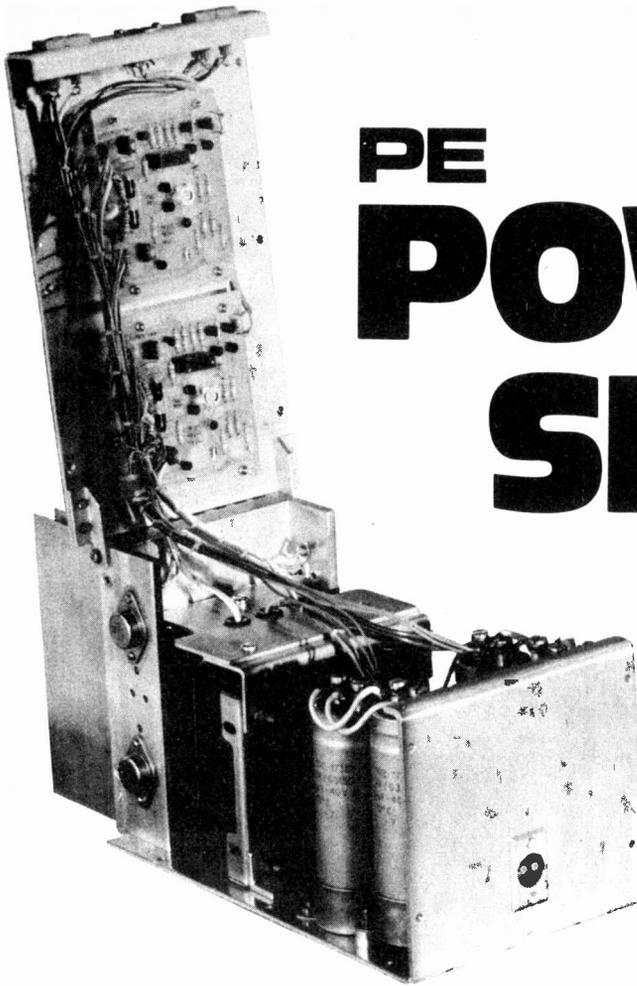

THE purpose of any audio chain is the accurate reproduction of live or recorded information, be it speech, music or just plain "sound".

Due to the low efficiency of transducers generally, with the possible exception of horn loaded systems, considerable power must be expended in order to produce sounds at an acceptable level; this level will obviously be different for different transducers in different applications. As the basic function is the same, it was felt that, rather than produce a flood of designs for specific purposes, a better approach was to produce a single basic design to fulfil all requirements.

From this article four amplifiers can be built all of them being based on a single circuit configuration. To realise the range of outputs of 20W, 40W, 65W and 100W component changes should be made according to the relevant parts lists.

Although a single amplifier is described the prototype units were designed as double channel, that is, where two amplifiers are contained on a single chassis. This, of course, means a doubling of output capability to 20 + 20W, 40 + 40W, 65 + 65W and 100 + 100W in each case.

DESIGN CRITERIA

Where a low power system is required, there is little to be gained, and much to be lost in producing a power amplifier with an output capability of less than twenty watts into eight ohms, as cost and

physical size will not be significantly affected, and performance criteria such as transient handling capability, signal to noise ratio and distortion are not likely to improve.

Turning to the upper end of the power scale, choice of maximum power can be arrived at by examination of the transducers to be driven. Modern composite high power speakers, and individual drive units, will accept continuous sine wave outputs of between 10 and 50 watts r.m.s. Unfortunately audio signals are rarely as predictable as sine waves, but it can be assumed that twice the continuous power can be handled on transients of short duration, thus a power capability of 80 to 100 watts will be required.

When two or more speakers are connected in series, or series-parallel to maintain impedance, then the power requirement can be greatly increased. No allowance has been made for this method of use, as the damping effect of the amplifier is lost, except when units are connected by separate leads to the amplifier terminals, and thus it is felt to be a bad policy.

A further problem arises when two speakers in parallel are driven to a peak level of 100 watts each, that is, a current handling capability of at least 10 amps is required, both in the amplifier and power supply unit, and this is dangerously close to the maximum current of a TO3 transistor (generally 15 amps).


Thus a high quality amplifier should be capable of driving up to 100 watts into a single 8 ohm load, and, to satisfy the requirements of all applications, must have very low harmonic and intermodulation distortion figures, be overload protected, have a high damping factor, and a very high signal to noise ratio.

This final parameter is often neglected, and in most designs a figure of 80dB is considered good. However, a better figure to aim for is 100dB.

Power amplifiers can be functionally split into two sections, namely a voltage amplifier with low current gain, followed by a current amplifier with unity voltage gain, and at this stage the two sections will be considered separately.

Specification . . .

Power bandwidth	-6dB from 8Hz to 45kHz
Total harmonic distortion	0.02%
Intermodulation distortion	0.04%
Signal/Noise ratio	100dB
Input sensitivity into 200k Ω	1V r.m.s.
Input matched to 600 Ω line	
Overload protected	
May be d.c. coupled throughout for use as a servo amplifier	
Full bridge output to eliminate "turn-on plop"	

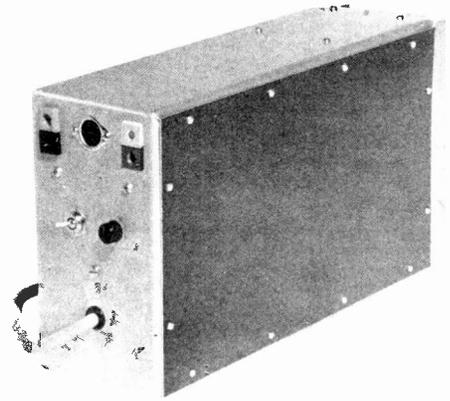

PROVIDING OUTPUTS OF 20, 40, 65, & 100 WATTS FROM ONE COMMON CIRCUIT CONFIGURATION

VOLTAGE AMPLIFIER

The basic voltage amplifier configuration used for the power amplifiers is shown in Fig. 1. It has the advantage of providing adequate performance without undue complexity and requires no setting up.

The input resistor R1 provides bias current for TR1 and defines the slave amplifier input impedance.

R12, R2 and C2 form an attenuator which determines the proportion of the output fed back to TR2 and hence defines the gain of the amplifier. C2 allows full d.c. feedback to stabilise the output at, or close to 0 volts. Transistors TR1 and TR2 form a differential amplifier, as do TR3 and TR4, the output of this second stage being fed to a common emitter amplifier TR5.

The overall combination will have a very high open loop gain, and will be non-inverting, as a positive going input tends to increase current in TR1 at the expense of TR2, so that TR4 turns on and

TR3 off. This reduces the current drawn by TR5 base and gives a positive going output at TR5 collector. Resistors R4, R5, R7, R8 and R9 enable a sensible standing current to be established in each stage, and eliminate any chance of leakage currents unbalancing the amplifier.

The problem of non-linearity in TR5 is overcome by operating this transistor at a constant collector current by bootstrapping the junction of R10 and R11 to the output by means of C3, providing an almost constant current in R11.

COMPOUND TRANSISTORS

The output stage is basically a Class AB compound amplifier using quasi-complementary transistors being made up of groups of three as seen in Fig. 3.

These triplet configurations have a number of advantages chief of which are (a) high current gain, (b) the inputs are presented through a single base

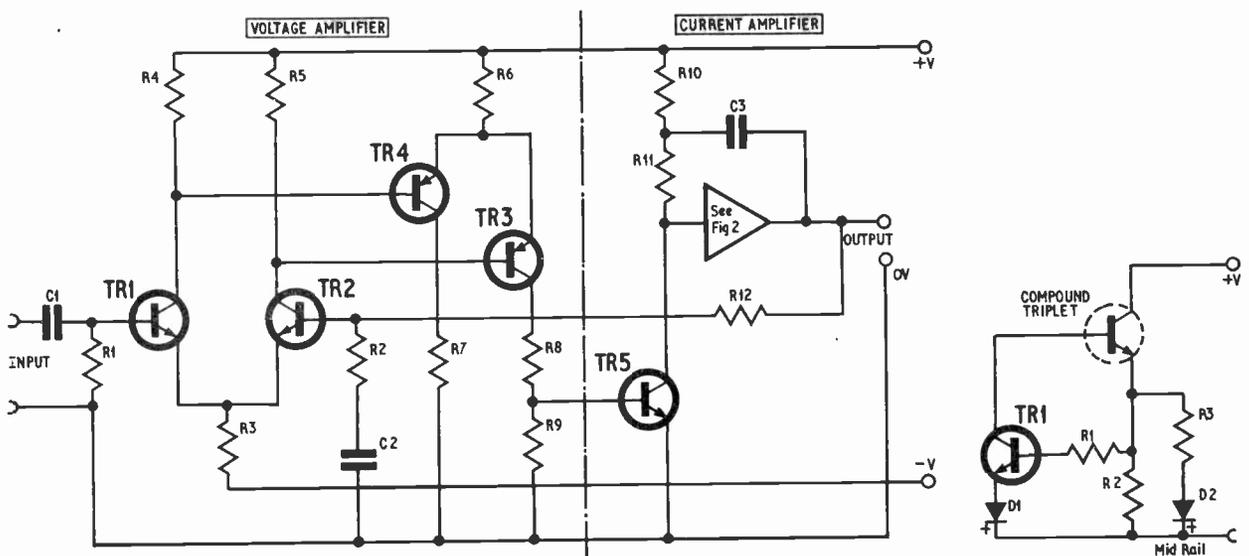


Fig. 1. Basic circuit arrangement for voltage amplifier

Fig. 2. Showing how current limiting is achieved

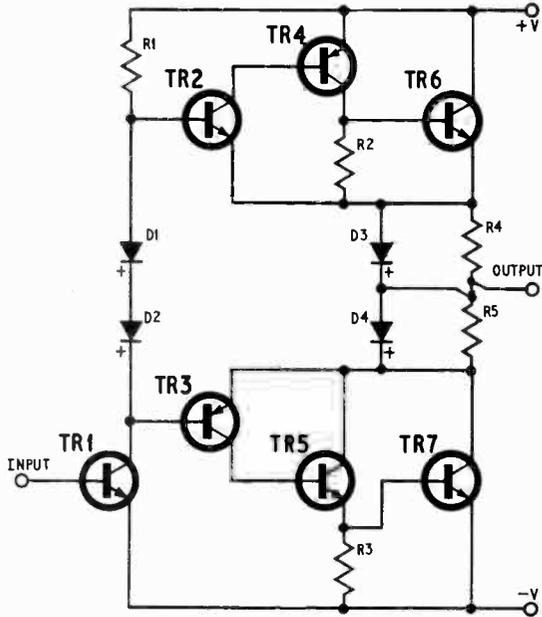


Fig. 3. Compound triplet arrangement for current amplifier

emitter junction which means that the output transistor junction temperature will not affect stability and (c) *npn* output transistors are relatively cheap and readily available.

In the quiescent condition the driver transistor TR1 is biased to provide a mid-rail voltage at the

output. With a signal applied the collector applies alternate drive conditions to the compound triplets so that first one group is conducting and then the other.

A "two stage" resistor is used to link the triplets to the output terminal, consisting of a fairly high value resistor shunted by a power diode and resistor.

The high value of resistance gives good quiescent stability, and the diodes limit the voltage drop under full drive conditions. To ensure reliable operation of the overload protection, a low value resistor is connected in series with each diode, and maximum current can be adjusted by means of this resistor.

OVERLOAD PROTECTION

Overload protection is provided by limiting the output current supplied by either compound triplet. The circuitry that achieves this is shown in Fig. 2 for one triplet only, a complementary circuit being used on the other.

The current supplied to the output terminal generates a voltage across the combination of R3, R2 and D2 which is related to the current flowing. When the current rises to a level sufficient to provide approximately 1.5V, base current is directed through TR1 and D1. Conduction of this transistor means that bias is removed from the triplet so that the output current is limited.

The peak current available before limiting must be higher than the peak current to be supplied to the load, and as this may be 5A, a dissipation of 225W can occur with a short circuit at the output. Because of this, a fuse circuit must be inserted (FS1) to give protection.

The complete circuit configuration for the basic amplifiers is given in Fig. 4.

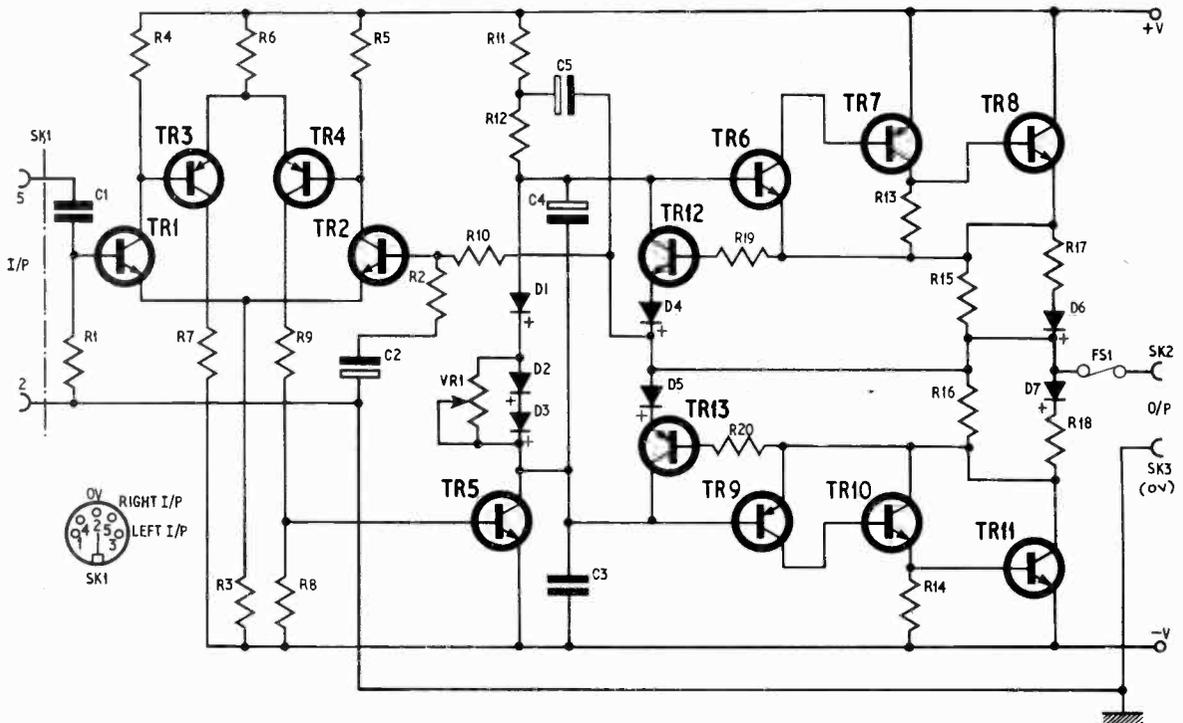


Fig. 4. Basic single channel (right) configuration common to all slave amplifiers. For component value variations, see components lists. The inset shows wiring for a 180 degree, 5 pin socket for two channel. When connecting a remote preamplifier the screen is connected to earth (0V) only at the slave to obviate hum loops

POWER SUPPLIES

Power supplies in a design such as this must provide a fairly steady supply voltage, with a high current capacity when required. As an example, 100 watts into 8 ohms will require a peak current of 5 amps per channel. This implies that for a stereo amplifier with a common power supply a peak requirement of 10 amps is necessary. The mean current drain will be 1/2.8 of this value, or 3.5 amps, and so a transformer rated at 4 amps continuous current would be suitable.

Decoupling should maintain the supply within about two volts of nominal, at full power, for one half cycle of mains current so that:

$$C = \frac{IT}{V} \text{ at peak output}$$

COMPONENTS . . .

where I is in amps, T in seconds and V volts. The equation then is:

$$C = \frac{10 \times 0.01}{2} \text{ Farads} = 50,000\mu\text{F}$$

A composite musical signal can be shown to have a short term mean level at least 12dB below maximum output. Occasional transients will reach maximum output, but these will generally be of short duration, two milliseconds or less being typical.

From similar calculations as above the decoupling requirement for music at -12dB is 5,000 μ F and for a 2mS transient, 6,000 μ F.

DESIGN CHOICE

If the amplifier is intended for home entertainment (domestic) reservoir capacitors of 6,000 μ F are

AMPLIFIERS					POWER SUPPLIES				
Resistors	20W	40W	65W	100W	Resistors	20W	40W	65W	100W
R1	200k Ω	200k Ω	200k Ω	200k Ω	R1	12k Ω	15k Ω	18k Ω	20k Ω
R2, R6	39k Ω	56k Ω	68k Ω	86k Ω	R2	100 Ω	100 Ω	100 Ω	100 Ω
R3, R4, R5	430k Ω	620k Ω	750k Ω	910k Ω	R3, R4	200 Ω	300 Ω	360 Ω	470 Ω
R7	91k Ω	120k Ω	150k Ω	160k Ω	R5	300 Ω	300 Ω	300 Ω	300 Ω
R8	6.2k Ω	6.2k Ω	6.2k Ω	6.2k Ω	R6	10 Ω	10 Ω	10 Ω	10 Ω
R9	82k Ω	110k Ω	130k Ω	150k Ω	R7	see text			
R10	200k Ω	200k Ω	200k Ω	200k Ω	R8	10k Ω	12k Ω	15k Ω	18k Ω
R11, R12	15k Ω	20k Ω	24k Ω	27k Ω	R9	1k Ω	1k Ω	1k Ω	1k Ω
R13, R14	100 Ω	100 Ω	100 Ω	100 Ω	R10, R11	2k Ω (1W)	2k Ω (1W)	2k Ω (1W)	2k Ω (1W)
R15, R16	10 Ω (1W)	10 Ω (1W)	10 Ω (1W)	10 Ω (1W)	Potentiometers				
R17, R18	0.11 Ω	0.08 Ω	0.07 Ω	0.06 Ω	VR1	1k Ω	1k Ω	1k Ω	1k Ω
R19, R20	4.7k Ω	4.7k Ω	4.7k Ω	4.7k Ω		all carbon linear			
All $\frac{1}{2}$ W 5% metal oxide except where otherwise stated	0.03 Ω /cm, 26 s.w.g. resistance wire				Capacitors				
Capacitors					C1, C2	10,000 μ F (40V)	10,000 μ F (50V)	10,000 μ F (63V)	10,000 μ F (63V)
C1	0.1 μ F	0.1 μ F	0.1 μ F	0.1 μ F	C4, C5	10,000 μ F (40V)	10,000 μ F (50V)	10,000 μ F (63V)	10,000 μ F (100V)
C2	10 μ F	10 μ F	10 μ F	10 μ F		All electrolytic			
C3	100pF	100pF	100pF	100pF	C3	100pF	100pF	100pF	100pF
C4	22 μ F	22 μ F	22 μ F	22 μ F	Transistors				
C5	1 μ F	1 μ F	1 μ F	1 μ F	TR1	BC204	BC204	BC204	BC204
					TR2, TR3	MPS-U01	MPS-U01	MPS-U01	MPS-U01
					TR4	MPS-U51	MPS-U51	MPS-U51	MPS-U51
					TR5	2N3055	SDT9203	SDT9203	SDT9203
Potentiometers					Rectifiers				
VR1	2.2k Ω	2.2k Ω	2.2k Ω	2.2k Ω	D1-D4		REC46 (150V, 10A)		
					D5		BZY88—C6V8		
Diodes					Transformer				
D1-D5	1N914	1N914	1N914	1N914	T1	24-0-24V @ 4A	30-0-30V @ 4A	33-0-33V @ 5A	36-0-36V @ 6A
D6-D7	1N5401	1N5401	1N5401	1N5401					
Transistors					Changes for Standard Supplies (Domestic and Monitoring versions)				
TR1, TR2	2N2484	2N2484	2N2484	2N2484	Capacitors				
TR3, TR4	BC212	MPS-L51	MPS-L51	MPS-L51	C1, C2	6,000 μ F (25V) (Domestic)	6,000 μ F (35V)	6,000 μ F (40V)	6,000 μ F (50V)
TR5	ME1120	ME1120	ME1120	ME1120	C1, C2	10,000 μ F (25V) (Monitoring)	10,000 μ F (35V)	10,000 μ F (40V)	10,000 μ F (50V)
TR6	BC182	MPS-L01	MPS-L01	MPS-L01	Rectifiers				
TR7	MPS-U57	MPS-U57	MPS-U57	MPS-U57	D1-D4		REC 43A (100V, 4A)		
TR8, TR11	2N3055	2N3055	SDT9203	SDT9203	Transformer				
TR9	BC212	MPSL51	MPSL51	MPSL51	T1	18-0-18V @ 3A	22-0-22V @ 4A	25-0-25V @ 4A	30-0-30V @ 4A
TR10	MPS-U07	MPS-U07	MPS-U07	MPS-U07				Douglas	Douglas
TR12	BC184	BC184	BC184	BC184				MT106	MT123
TR13	BC214	BC214	BC214	BC214	Miscellaneous				
Miscellaneous					FS1—	1A	1A	1A	1A
Heatsink	60D-0600-A-1 (Marston)		(100W and 65W)		S1—Double pole mains on/off, LP1—mains neon				
					FS1—IA				

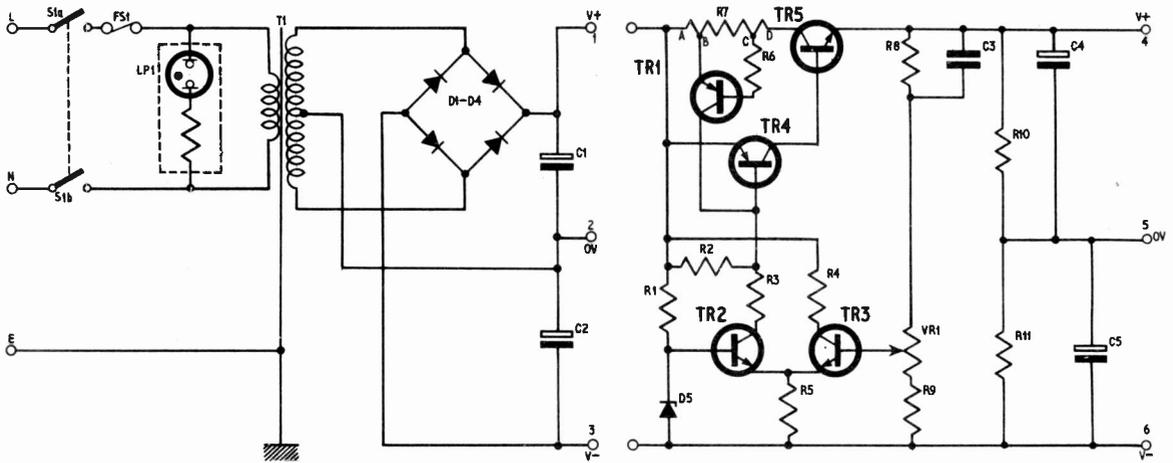


Fig. 5. Circuit for p.s.u. For the domestic version of amplifier the power rails are pins 1, 2 and 3. The monitoring version takes its supply from pins 4, 5 and 6. The current sensor R7 is made up from 26 s.w.g. Constantan resistance wire (0.03 ohm/cm). The tapping resistances are as follows: A to B ≤ 0.02 ohms; B to C = 0.07 ohms; C to D ≤ 0.02 ohms. Supply voltages for the 20, 40, 65 and 100W versions are approximately $\pm 25V$, $\pm 32V$, $\pm 36V$ and $\pm 46V$ respectively

adequate assuming that neither transients nor very loud passages coincide exactly in time if two channels are being used.

For "monitoring" quality, a higher value capacity, possibly 10 or 15,000 μF should be used, or alternatively a stabilised supply particularly when used for stereo to reduce cross talk.

A composite circuit diagram for the domestic and monitoring versions of the p.s.u. is shown in Fig. 5.

For the former points 1, 2 and 3 are connected to the amplifier. For the latter points 1 and 2 connect to the stabiliser circuit; no connection is made to 2.

The output mid-point in this case is derived using resistor and capacitors.

OPTIMUM LOAD

Optimum load impedance for all versions is 8 ohms but any load can be accommodated at reduced power, bearing in mind the peak voltage and current limitations.

Fig. 6 shows typical impedance curves for high quality domestic speakers demonstrating that the impedance is anything but constant. Indeed, it is not unusual to find dips of impedance as low as 1.5 or 2 ohms, causing severe current overload at critical frequencies.

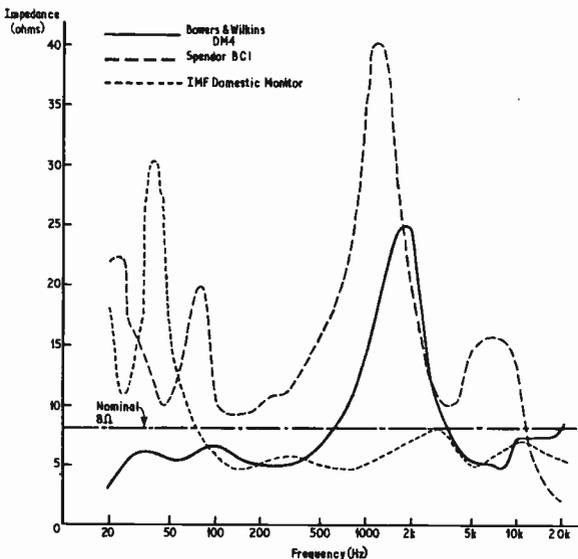


Fig. 6. Showing how speaker impedance changes with frequency

IMPORTANT

Two BA148 diode suppressors **MUST** be added to Fig. 4 as follows—Cathode and anode to $\pm V$ and SK2 and SK2 and $-V$ respectively. In Components List for all versions TR7 and TR10 should be MPS-U57 and MPS-U07; for the p.s.u. TR2, TR3 should be MPS-U07 and TR4, MPS-U57. (See next month.)

Next month constructional details for the amplifiers will be given

THE SUN, BY SKYLAB

From the last of the experiments aboard *Skylab* has come new knowledge and exciting data. There is no doubt that a new era has opened for astronomers and as a result of what has been noted many programmes will be instituted in solar physics.

Much of the success is due to the (ATM) Apollo Telescope Mounting. It enabled a new view of the solar system, the galaxy and, most important, the Sun itself.

Free of the atmospheric absorption the telescope showed that the Sun, far from being "quiet" at the near sunspot minimum was extremely active. This alone has justified the mission and also confirmed the need for man in space.

Practical Electronics received an invitation from the Institution of Radio and Electronic Engineers to attend the Clerk-Maxwell Lecture, "Man in Space" by Werhner von Braun. More than twice the number of persons attended than the seats available. Before the lecture began the writer had a conversation with Werhner von Braun and certain definite conclusions regarding the progress of physics emerged. In his words "... the time has come for another Maxwell to re-order our thoughts and set in their proper place the ever increasing number of particles, the black holes and the quasars." He also gave some information based on the early examination of some of the data.

The medical evidence is now clear and it is accepted that man could live in space indefinitely. The adaptability is not confined to man for the spider which was taken aboard *Skylab* was able to spin a perfect web. The pictures of the first attempts were not only comic but extremely interesting. It needed only a short while of accommodation before things were under control. The peculiar zigzag of the circles and the cross ties soon assumed the familiar shape and life went on.

The astronauts also attempted to move round the walls at a high rate to set up artificial gravity. In this they were not successful.

GREAT BALLS OF FIRE

One of the most spectacular events was a pulsing stream of plasma from the Sun which had a regular rhythm. More than forty of such events were recorded. An unexpected bonus was the ability to observe with the coronagraph these great blobs, as large as the



BY FRANK W. HYDE

Sun itself, as they moved up through the corona at a speed of 400km per second.

The variation of the intensity of the corona over the two hemispheres of the Sun were not anticipated. One section of the Sun seemed to be in the nature of a hole at a lower temperature than the rest of the surface. This was borne out by the X-ray pictures. It also appears that the corona is composed of closed loops which fit the magnetic line structure. In both the X-ray measurements and the white light coronagraph pictures this appears.

There were a number of instances, where the conditions for sunspot appearance appeared outside the normally observed belts. Some of the "holes" indicate the source of disturbances of the solar wind which effect terrestrial conditions.

There have been tens of thousands of frames taken of the coronal conditions, more than has been observed in a thousand years of eclipses. Continuous observations with the facility to select and also combine different types of telescope, made the *Skylab* control console a sort of astronomical organ on which the melody of the heavens could be produced. Nothing like this success was expected and now the knowledge of what can be done in this field must ensure that the next decade will add an unprecedented amount of data for study.

More than 600 pictures a day were recorded and the number of bits in each picture amounted to 10^8 . Among the many and continuous hours of study covering everything in the vicinity of the Sun there were two solar eclipses,

many eruptions and flares on the Sun itself, the perihelion of Kohoutek and a transit of Mercury.

The combination of control from the Johnson Spaceflight Centre and the astronauts aboard *Skylab* resulted in a magnificent scientific achievement. It is worth noting that the planned tasks for the crew were restricted to the pointing of the telescopes, target control and to collect and replace cameras and film. But, in fact, the crew did much more than that and it was their resource that made possible the full speed running of the observations. Despite some early difficulties, which were overcome, the crew settled down to do a job for which posterity must ever be grateful.

The cost of this mission was high and many thought wasteful. None would say this now and indeed, there is in this very extensive period of man in space, the certainty that money for the future missions will be forthcoming.

MORE OF VENUS


The Venus fly-by of *Mariner 10* has been a successful mission. But some of the data obtained will need months to extract the information sought.

The spacecraft approached Venus from the dark side and the first pictures showed the cusps which appear extended far beyond the normal. This is thought to be due to the atmospheric refraction. The scattering of light beyond the terminator will help to an understanding of the upper atmosphere. Haze shells were observed and these will reveal more data after computer processing.

One important aspect is the layering observed in the atmosphere. This is not yet understood nor is the material of the cloud strata.

There was great penetration of the atmosphere by the two radio probe signals. Though physical occultation began at about 10.17a.m. radio signals were still being received up to 17 minutes later. The aerial on *Mariner 10* was designed to change its pointing direction in order to compensate for the bending of the radio waves which takes place when travelling through the Venus atmosphere.

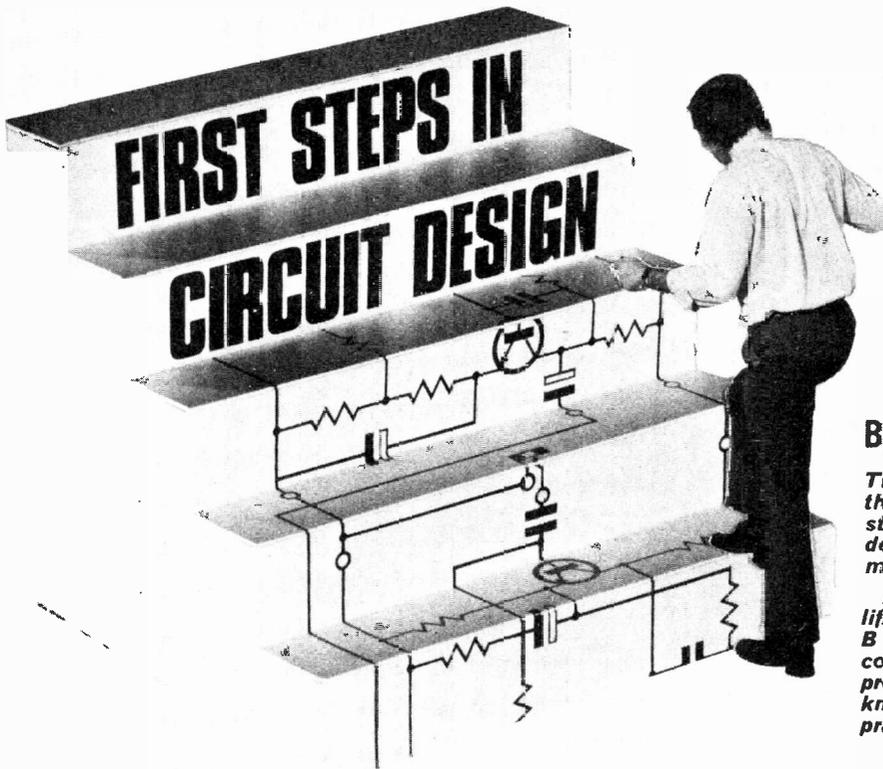Much is expected of this technique in the observation of the density of the atmosphere and it is hoped also to resolve the differences of temperature given by earlier *Mariner* missions and by the USSR spacecraft *Venera*. Helium is known to be a constituent but it would have to be at least 3 per cent to account for the differences of temperature found.



4

By A. P. Stephenson

This series, specially written for the beginner, takes you step-by-step through transistor circuit design in a simple, non-mathematical way.

Design of a small signal amplifier will be followed by a Class B amplifier and the series will conclude with a constructional project so that your theoretical knowledge can be put into practice.

SO FAR we have only looked at the voltage divider method of biasing a transistor stage. This month we will look at another method which is simple and economical. These advantages are, however, at the expense of other parameters.

Once we are satisfied with a single stage amplifier, the

problem then arises of how to connect this into the system so that it does not disturb the driving or driven circuits. Sometimes direct coupling is possible but often we must make use of a d.c. blocking capacitor. The value of this component must be such as to maintain the required bandwidth of the system.

4.1. ALTERNATIVE BIASING ARRANGEMENT

There is an alternative to the R_1, R_2 divider (Part 3) known as "collector to base feedback bias". Only one resistor is needed instead of two and some bias stability is possible even without the inclusion of R_E (see Fig. 4.1).

The resistor R_B provides bias and also some negative feedback which tends to stabilise the collector current against changes in h_{FE} .

Suppose that h_{FE} is higher than predicted: this would tend to increase I_C which in turn would cause the output voltage to fall. This fall would be passed via R_B to the base causing a decrease in I_C . The base bias conditions are therefore stabilised.

HIDDEN FEATURES

Although the method appears delightfully simple and economic, there are certain hidden features which the designer must understand.

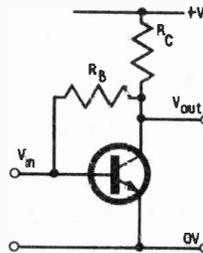


Fig. 4.1 Simple circuit illustrating collector to base feedback (left)

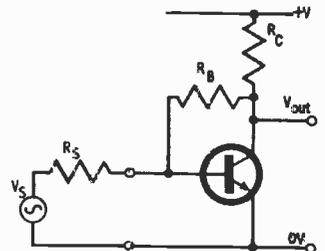


Fig. 4.2 The source resistance can be seen to be an important parameter in the calculation of the circuit gain (right)

(a) The feedback is in parallel with the input signal and therefore requires extra current drive from the signal input to the stage. In other words, the stage input resistance R_{IN} is lowered. In fact, the input resistance consists of two resistors in parallel, one of them being the normal $r_{IN} = h_{te} \times r_e$ and the other equal to R_B divided by the gain A . This is easily understood when it is realised that the signal voltage is at one end of the R_B and the output voltage (A times the input signal) is at the other.

Thus A times as much current must be provided by the signal, which is equivalent to saying that R_B behaves as if it were $A + 1$ times smaller and across the signal input.

(b) There is no actual reduction in voltage gain, as far as the gain from base-in to collector-out is concerned. The voltage gain is still

$$A = R_C/r_e \text{ or } R_C/(r_e + R_E)$$

(If R_E is present).

However the lower input resistance has the effect of lowering the gain measured from signal e.m.f. to collector output. The source resistance of the signal (R_S) in conjunction with R_E forms a kind of operational amplifier configuration (see Fig. 4.2).

If A was very high, the total gain from V_S to V_{out} would be approximately

$$A' = R_B/R_S$$

where A' is defined as the gain with feedback. Thus the gain is independent of the transistor.

This, however, is a gross oversimplification of the situation because the transistor gain A in such a simple single stage amplifier would not be "very high" and $A' = R_B/R_S$ would be greatly incorrect.

This analogy with the operational amplifier was only given as an aid to comprehension. It is always good practice to view circuit ideas from widely differing angles.

4.2. AN ALTERNATIVE EQUATION FOR GAIN

The previous circuit had no emitter resistor R_E which was the reason why the gain A was so high. Although a high gain may often be a desirable feature, there are two main reasons against achieving it by the omission of R_E .

(a) The gain is not too predictable because of its absolute dependency on r_e . The equation $r_e = 25/I_C(\text{mA})$ is very useful as a rough guide but it is well to remember that the equation is only approximate. The inclusion of R_E in the gain formula, although lowering the gain increases the accuracy of the equation (particularly if $R_E \gg r_e$).

(b) A more important reason is the rather remarkable twist of the gain equation when the bias is set to allow the collector to rest at half the supply voltage.

If $V_{out} = \frac{1}{2}V_{cc}$ then $R_C = \frac{1}{2}V_{cc}/I_C$. Now $A = R_C/r_e = \frac{\frac{1}{2}V_{cc}}{I_C} \div \frac{25}{I_C} = V_{cc}/50$.

But remembering that the figure "25" is millivolts, we must multiply by 1,000, giving

$$A = \frac{V_{cc} \times 1,000}{50}, \text{ thus } \boxed{A = 20V_{cc}}$$

This means that the gain of any grounded emitter stage operating without an emitter resistor is simply 20 times the supply voltage (assuming the collector is at half the supply voltage).

This applies whatever collector current we use, so it is impossible to set the gain at any other value than $20V_{cc}$ (unless of course we use negative feedback).

It is easy to see why R_E is almost always present in grounded emitter amplifiers.

4.3. COUPLING CAPACITORS

It is often required to connect two stages together by allowing the output signal of one stage to become the input signal of the next.

Sometimes the coupling can be achieved without disturbing the d.c. bias conditions, but this is sometimes unavoidable.

This problem can be overcome with the use of a "coupling capacitor" which enables the signal to pass relatively easily but blocks any d.c. from affecting the next stage.

CAPACITOR VALUE

The question is how big must the capacitor be. The answer depends on two pieces of information—the lowest frequency that the signal is likely to be, and the input resistance of the stage which the capacitor is to feed.

The skeletal circuit is shown in Fig. 4.3.

The capacitive reactance (X_C) and R_{IN} form a voltage divider, so it is clear that X_C should be considerably less than R_{IN} at the lowest frequency which it is desired to pass.

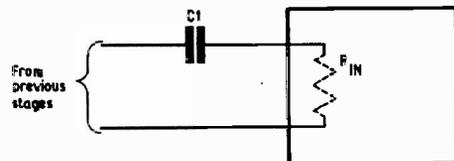


Fig. 4.3 The calculation of the coupling capacitor value is determined by the input resistance R_{IN} of the following stage

The simplest way is to find the value of C which makes $X_C = R_{IN}$ and then use the next highest preferred value.

Suppose the lowest frequency to be passed is 100Hz and $R_{IN} = 1k\Omega$.

Then if $X_C = R_{IN}$, then $1/2\pi fC = R_{IN}$ which gives $C = 1/2\pi fR_{IN}$.

Inserting values gives $C = 1.59\mu F$ so the next highest preferred value, $2\mu F$ would be used.

RULE OF THUMB

A neat little rule of thumb to save a lot of fiddling with powers of ten is

$$C = 0.2/f \times R_{IN}$$

where f is in kHz, R_{IN} in kilohms and C in μF .

The value for C is in no way critical, providing it is at least the value calculated by the method above. Twice or even ten times larger will not matter apart from the cost.

4.4. USE OF THE EMITTER FOLLOWER STAGE

An emitter follower stage provides an easy solution to the problem of matching from a high resistance signal source to a low resistance load.

Unlike the normal grounded emitter stage, the emitter follower has no voltage gain, in fact, there is a slight voltage loss. There is, however, a substantial current gain as a signal is passed through, because of the apparent change in source resistance.

Treating the emitter follower as a black box, the effect on the input signal is as shown in Fig. 4.4.

The figures shown in the figure are purely arbitrary and are chosen only to illustrate how the source

resistance can be substantially lowered by passing through the stage.

CURRENT GAIN

The concept of current gain can be appreciated by calculating the two short circuit currents.

If the original circuit was shorted out the current would be

$$i = 1\text{V}/100\text{k}\Omega = 0.01\text{mA}$$

If the output was shorted, the current would be

$$i = 1\text{V}/1\text{k}\Omega = 1\text{mA}$$

This shows that a theoretical current gain of 100:1 has been achieved. (The short circuit current dodge is used on paper only—don't take it literally and start sticking screwdrivers across the terminals.)

It must not be supposed that an actual emitter follower would provide a magical solution. The successful design of such a stage requires quite a bit of fiddling with values to get the input resistance as high as possible.

For example, Fig. 4.4 presupposes that the input resistance of the emitter follower stage is much higher than the $100\text{k}\Omega$ signal resistance. Unless this is so, it is clear that the signal would be attenuated by voltage divider action between the $100\text{k}\Omega$ and R_{IN} of the emitter follower.

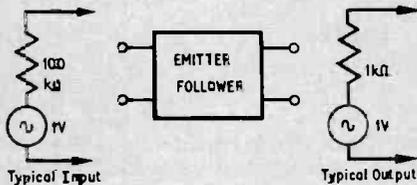


Fig. 4.4 An emitter follower transforms a high input impedance into a low output impedance

4.5. TYPICAL CIRCUIT AND EQUATIONS OF THE EMITTER FOLLOWER

An emitter follower circuit using voltage divider feed for base bias is shown in Fig. 4.5.

We are not concerned with the design factors for setting up the correct d.c. conditions, this problem is dealt with elsewhere. Instead, we state some important equations which decide the voltage gain, input resistance and output resistance.

1. VOLTAGE GAIN

For most practical purposes, the voltage gain is nearly unity, though it is as well to know the following formula in case some badly chosen values for R_E lower the gain to a small fraction.

Voltage gain from V_{in} to $V_{out} = R_E/(r_e + R_E)$.

Since r_e is the internal emitter resistance and will seldom be in excess of 100Ω or so, it is easily seen that the gain will be about 1, providing R_E is in excess of $1\text{k}\Omega$.

2. INPUT RESISTANCE (R_{IN})

This is the same basic formula which has already appeared in connection with the grounded emitter stage

$$R_{IN} = R_1, R_2 \text{ and } r_{in} \text{ in parallel}$$

(remember that $r_{in} = h_{ie}(r_e + R_E)$).

3. OUTPUT RESISTANCE (R_{OUT})

This is a bit complicated unless dealt with in two parts.

$$R_{OUT} = R_s/h_{ie} \text{ in parallel with } R_E$$

where $R_s = R_1, R_2$ and r_s in parallel.

If this is too wearisome to calculate and a very rough equation is all that is needed, then use

$$R_{OUT} = r_s/h_{ie}$$

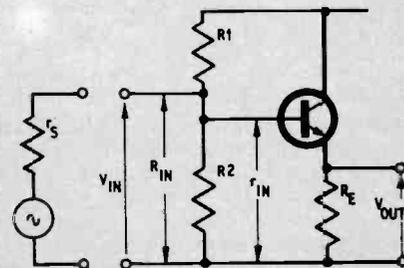


Fig. 4.5 Typical emitter follower with voltage divider for base bias

4.6. D.C. COUPLING

Two stages may be coupled together directly *only* if the d.c. voltage output of the first stage is compatible with the d.c. bias requirements of the second stage.

A typical example which serves to illustrate the system is the circuit of Fig. 4.6 which shows a normal grounded emitter amplifier feeding an emitter follower stage.

Transistor TR1 provides the voltage gain and TR2 provides a low resistance (high current) output.

The gain of the first stage = $R_C / (r_e + R_E) = (84k\Omega / 1k\Omega + 250\Omega) = 67$.

The second stage contributes no further voltage gain.

STAGE INPUT RESISTANCE

The stage input resistance is r_{in} , R1 and R2 in parallel, although it is reasonable to ignore R1.

Now, $r_{in} = h_{ie}(r_e + R_E) = 100(250\Omega + 1k\Omega) = 125k\Omega$, which, in parallel with R1 gives a value for R_{IN} of about $45k\Omega$.

Currents through TR2 would be determined first. 1mA is chosen for collector current, so assuming a pessimistic h_{FE} of 100, the base current of TR2 would be $10\mu A$.

The divider feed for the bias of TR2 is the chain R_C , TR1 and R_E of the first stage which is passing 0.1mA (which is ten times the base current of TR2).

Again taking an h_{FE} of 100 for TR1, the base current would be $1\mu A$, which is fed by a divider chain taking $10\mu A$.

The "rule of ten" has thus been used throughout.

OUTPUT RESISTANCE

The output resistance of the emitter follower is a bit tricky. The equation, as stated previously, is $R_{OUT} = R_S / h_{ie}$ in parallel with R_E . The term R_S is the source resistance of the signal feeding the base, which, in this case, is the output resistance of the first stage.

To a rough approximation this may be taken as the collector resistance, R_C , which is $84k\Omega$. Thus $R_{OUT} = 84k\Omega / 100 = 840\Omega$. (The $9k\Omega$ R_E which strictly is in parallel may be disregarded.)

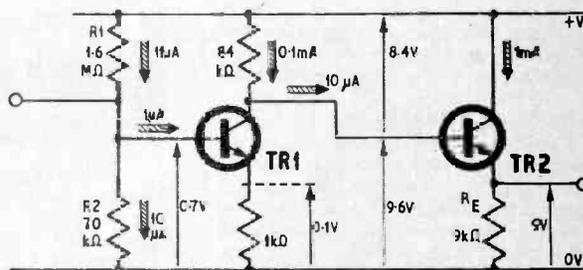


Fig. 4.6 A two stage d.c. coupled amplifier showing typical component values

4.7. D.C. FEEDBACK LOOPS

Leaving the emitter resistor unbypassed has so far been the only example of negative feedback. A more obvious example is frequently used in direct-coupled stages and, to illustrate such a system, the circuit previously discussed will be modified to include a d.c. feedback loop (see Fig. 4.7).

The circuit, including the voltages and currents are exactly the same, apart from the method of biasing the first stage.

Instead of the customary divider across the supply rail, the bias feed is taken from across the output resistor.

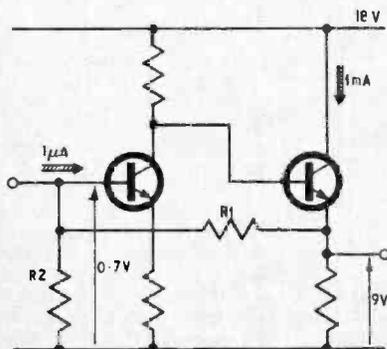


Fig. 4.7 Negative feedback stabilises the output voltage but reduces gain

This is not such a violent change as appears at first sight. After all, there are nine volts available so why not use them and obtain the added advantage of a d.c. feedback loop?

In choosing the values for R1 and R2 we must be careful not to disturb the output circuit too much. It is drawing 1mA so it will hardly be aware of the theft if we divert say $10\mu A$ from R_E to feed a divider.

Since R2 must drop 0.7V, R1 must drop the remaining 8.3V which means that if $10\mu A$ is flowing the values of R1 and R2 are calculated as follows:

$$R_1 = 8.3V / 10\mu A = 830k\Omega$$

$$R_2 = 0.7V / 10\mu A = 70k\Omega$$

STABILITY

Such a circuit has very good stability in spite of wide tolerances in the resistors R1 and R2. In fact, it is astonishing how the output appears to lock at 9V.

Suppose that the output tends to drift downwards: this will pull the base of TR1 down which causes the collector of TR1 and base of TR2 to rise. The output tendency is therefore to rise which, due to the feedback loop is providing a correcting influence on the tendency for the input to fall.

The original gain before feedback is, of course, reduced from its previous value. This is one of the penalties to be paid for the benefits of negative feedback.

Continued next month

THERE must be many PE readers who would never call themselves musicians but who have an interest in music, be it as listeners or as vamping-left-hand pianists. Some of them are no doubt in the throes of building the units which go to make up Mr. Shaw's Synthesiser and are wondering what on earth to do with it when it's completed. Others may not want to begin any musical project because they feel that their creative or re-creative talent is nil.

Yet others may be musicians like myself who have a smattering of electronic theory and practice up their sleeves but are afraid to launch any large-scale project because they fear they may never get the finished article to function. I hope this feature may allay the fears of all these people and, indeed, offer some constructive help.

Facilities in the U.K.

Until quite recently the musician, particularly the composer and/or arranger has had to sit on the periphery of technological progress, using a small amount of electronic equipment in a limited kind of way, unable, through lack of know-how, to extend his innate creativity.

In this country it is not just know-how that has been lacking, but the facilities needed to acquire expertise. Although there has been a tremendous surge of interest in electronically produced or processed sound over the past decade or so we still have not managed to produce a chain of national studios where the musician can work with first-rate equipment and expert technical assistance.

It is true that we have the BBC Radiophonic Workshop, well-equipped and staffed by experts, but, alas, Auntie Beeb tends to hog the show by restricting its output to broadcast material in the shape of incidental music and sound effects and a few (all too rare) commissions from composers outside the Corporation.

Numerous private studios exist too — those of Tristram Cary, Daphne Oram and Peter Zinovieff immediately spring to mind, along with such institutions as the University of York and Goldsmith's College, London—yet most of us cannot hope to experience this kind of Utopian dream. Those of us who live and work away from the metropolis are, as in many things, particularly poorly off.

A studio at home

However, having said that, there is not too much cause for gloom. Magazines like PE have made it abundantly clear that the imaginative person can build quite a sizeable and versatile studio at home, quite apart from the commercial market.



Over the past few years PE has included in its pages features dealing with some of the electronic equipment available to the musician. More frequently there have appeared constructional projects specifically geared to the amateur musician: Waa Waa, Fuzz, Phase, and Sound Bender effects units; and complete instruments such as the Electronic Organ, Electronic Piano, and the Voltage Controlled Synthesiser.

The time is ripe, then, for the musician to join in and help bring the electronics engineer or experimenter and the creative artist together. As a professional musician whose creative work calls increasingly for more and more electronic equipment, I welcome the appearance of this page as a meeting place for the exchange of information, ideas, and ventilating of nagging questions.

Until projects such as the PE Synthesiser appeared (as far as I know the first design to be published for the home constructor to build from scratch) most of us tended to sink further into the slough of despond in the belief that only a fabulous win on the pools could get us reasonably well-equipped.

By beginning in a modest way, building our equipment module by module, we can now keep pace with our pockets whilst steadily increasing our versatility in the creative music sense.

Getting started

I am often asked, particularly by secondary school music teachers who (quite rightly) feel that there is an honourable place for electronic music in the curriculum, what is necessary by way of basic equipment in order to get started.

Assuming that "canned" rather than "live" electronic music is envisaged, then I would suggest a decent half-track stereo tape machine with three or more speeds, sound-on-sound facilities and a couple (maybe only one, at first) of reasonable quality microphones; this should keep you going for quite some time.

You may be wondering why I recommend a half-track tape machine when the present-day quality of quarter-track machines is very high indeed. It's not a matter of quality in this instance. Amongst the tricks used in the manipulation of recorded sound one of the simplest is reverse playback, and on a standard quarter-track machine, stereo or mono, or a half-track mono machine, reversal of the tape direction merely gives playback of the recorded material on the new channel(s) in a forward direction. On a half-track stereo machine turning the tape over reverses the material on both channels, incidentally reversing the stereo direction too.

Tape manipulation

Strictly speaking, using only microphones, you are not going to produce electronic music, since the microphone will only pick up air-borne sounds, most of which may well be "natural" in origin—dried peas in a can, hand claps, vocal sounds, or the jangle of keys, and maybe acoustic musical instruments. But by varying the tape speeds in recording, superimposition and reverse playback an amazing variety of sounds can be achieved. For the price of an editing block and a reel of splicing tape the sounds can be linked together to form a satisfactory sequence.

Anyone who has persevered with this kind of tape manipulation—and it is, believe me, a time-consuming activity—will tell you that the results can be miraculously electronic in effect.

In case you think this approach to creative sound a bit limiting, then I suggest you go out and buy a recording of "Variations for a door and a sigh" by Pierre Henry (Philips 4 FE 8504). Henry is one of the leading lights in the French movement which began in the early post-war years and produces so-called "musique concrète".

What can be more limiting than the creakings of an old barn door? Yet Pierre Henry manages, through careful handling of the granary door and a bit of superimposition back at the studio, to produce an incredibly wide range of sounds which are as musical as they are amusing.

There is a little paperback, too, by Terence Dwyer entitled "Composing with Tape Recorders" which offers invaluable advice.

42p ✓

Marshall's

Everything you need is in our New Catalogue
available now price 20 pence

(100 pages of prices and data)
Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

A. Marshall & Son (London) Limited
42 Cricklewood Broadway London NW2 3HD, Telephone 01-452 0161
& 65 Bath Street Glasgow G2 2BX Telephone 041-332 4133

Popular Semiconductors

2N436	0.75	2N3705	0.12	AD150	0.83	BC308A	0.12	BFY19	0.35
2N436A	0.75	2N3706	0.09	AD161	0.45	BC308B	0.09	BFY20	0.50
2N437A	1.35	2N3707	0.13	AD162	0.45	BC309	0.10	BFY21	0.40
2N490	3.15	2N3708	0.70	AD161	1.00	BC309A	0.10	BFY50	0.23
2N491	3.55	2N3709	0.11	AD162	1.05	BC309B	0.10	BFY51	0.21
2N492	3.99	2N3710	0.12	AF109R	0.40	BC327	0.21	BFY52	0.19
2N493	4.20	2N3711	0.11	AF115	0.24	BC328	0.19	BFY53	0.18
2N696	0.18	2N3712	0.96	AF116	0.25	BC337	0.19	BFY90	0.16
2N697	0.18	2N3713	1.20	AF117	0.20	BC338	0.19	BRY39	0.23
2N698	0.25	2N3714	1.33	AF118	0.50	BCY30	0.43	BU104	1.42
2N699	0.29	2N3715	1.50	AF124	0.24	BCY31	0.52	BU105	2.25
2N706	0.18	2N3716	1.80	AF125	0.20	BCY32	1.15	CI06A	0.48
2N706A	0.18	2N3721	2.20	AF126	0.19	BCY33	0.34	CI06B	0.55
2N708	0.14	2N3722	1.80	AF127	0.20	BCY34	0.37	CI06C	0.65
2N709	0.35	2N3723	2.65	AF139	0.39	BCY38	0.83	CI06E	0.43
2N711	0.30	2N3729	3.15	AF170	0.25	BCY39	1.05	CA3020A	1.80
2N718	0.21	2N3730	2.40	AF172	0.55	BCY40	0.87	CA3046	6.70
2N718A	0.49	2N3791	2.35	AF178	0.55	BCY41	1.15	CA3048	2.11
2N720	0.50	2N3792	2.60	AF179	0.65	BCY58	0.22	CA3089E	1.06
2N721	0.55	2N3794	0.10	AF180	0.50	BCY59	0.21	CA3090Q	4.23
2N914	0.22	2N3819	0.37	AF186	0.40	BCY70	0.17	LM3001A	0.48
2N916	0.41	2N3820	0.38	AF200	0.35	BCY71	0.22	LM3004A	2.03
2N918	0.47	2N3823	0.42	AF233	0.51	BCY72	0.13	LM309K	1.88
2N929	0.30	2N3900	0.21	AF240	0.72	BCY82	0.42	LM324K	0.75
2N1302	0.19	2N3901	0.32	AF279	0.54	BCY88	0.42	LM709	0.40
2N1303	0.19	2N3903	0.24	AF280	0.54	BCY89	0.97	T099	0.48
2N1304	0.24	2N3904	0.27	AF102	0.75	BD115	0.75	BD11L	0.38
2N1305	0.24	2N3905	0.24	AL103	0.70	BD116	0.75	LD11L	0.38
2N1306	0.33	2N3906	0.27	BC107	0.18	BD121	0.75	LM723C	0.75
2N1307	0.24	2N3907	0.24	BC108	0.18	BD122	0.62	LM729	0.40
2N1308	0.25	2N4037	0.42	BC109	0.19	BD124	0.47	T099	0.40
2N1309	0.36	2N4058	0.16	BC113	0.13	BD131	0.80	BD11L	0.46
2N1671	1.44	2N4059	0.09	BC115	0.15	BD132	0.60	LD11L	0.38
2N1671A	1.54	2N4060	0.11	BC116	0.15	BD135	0.43	LM747	1.00
2N1671B	1.72	2N4061	0.11	BC118A	0.18	BD136	0.48	LM748	0.30
2N1671C	1.32	2N4062	0.11	BC117	0.21	BD137	0.55	BD11L	0.70
2N1711	0.45	2N4126	0.23	BC118	0.11	BD138	0.62	LD11L	0.38
2N1907	5.50	2N4289	0.13	BC119	0.29	BD139	0.71	MC1303P	1.26
2N2102	0.50	2N4919	0.64	BC121	0.23	BD140	0.87		1.26
2N2147	0.70	2N4920	0.99	BC125	0.15	BDY20	1.05	MC1310	2.92
2N2148	0.94	2N4921	0.73	BC126	0.20	BF115	0.25	MC1458CP1	
2N2160	0.60	2N4922	0.84	BC132	0.30	BF116	0.23		0.78
2N2192	0.40	2N4923	0.85	BC134	0.11	BF117	0.43	MJ480	0.90
2N2192A	0.40	2N5172	0.12	BC135	0.11	BF119	0.58	MJ481	1.14
2N2913	0.40	2N5174	0.22	BC136	0.15	BF121	0.25	MJ490	0.98
2N2193A	0.61	2N5175	0.28	BC137	0.16	BF123	0.27	MJ491	1.38
2N2194	0.73	2N5176	0.32	BC138	0.24	BF125	0.25	MJ493A	0.42
2N2194A	0.30	2N5190	0.92	BC140	0.34	BF122	0.20	MJ495	1.12
2N2194B	0.50	2N5191	0.95	BC141	0.29	BF123	0.25	MPSA05	0.28
2N2219	0.45	2N5192	0.24	BC142	0.24	BF124	0.18	MJ496	0.88
2N2219A	0.60	2N5195	1.46	BC143	0.21	BF158	0.23		0.68
2N2220	0.45	2N5245	0.43	BC145	0.21	BF159	0.27	MP8111	0.32
2N2221	0.41	2N5457	0.49	BC147	0.12	BF160	0.23	MP8112	0.40
2N2221A	0.40	2N5458	0.46	BC148	0.13	BF161	0.42	MP8113	0.47
2N2222	0.40	2N5459	0.49	BC149	0.12	BF163	0.32	MPF10	0.59
2N222A	0.50	40361	0.48	BC153	0.18	BF166	0.32	MPSA05	0.28
2N2368	0.21	40362	0.50	BC154	0.18	BF167	0.21	MPSA06	0.28
2N2369	0.37	40363	0.61	BC157	0.14	BF173	0.24	MPSA55	0.28
2N2369A	0.41	40389	0.48	BC158	0.14	BF177	0.29	MPSA56	0.27
2N2646	0.77	40394	0.58	BC159	0.14	BF178	0.35	NE555V	0.90
2N2647	1.12	40395	0.65	BC160	0.37	BF179	0.43	NE560	4.48
2N290	0.50	40406	0.56	BC167	0.15	BF178	0.45	NE561	1.46
2N290A	0.40	40407	0.63	BC168A	0.13	BF181	0.34	NE561A	4.48
2N2905	0.48	40408	0.50	BC168C	0.11	BF182	0.40	OC23	0.56
2N2905A	0.50	40409	0.52	BC169B	0.13	BF183	0.40	OC28	0.76
2N2906	0.31	40410	0.52	BC169C	0.13	BF184	0.30	OC35	0.56
2N2906A	0.37	40411	2.25	BC170	0.11	BF185	0.17	OC42	0.35
2N2907	0.40	40414	0.33	BC168	0.13	BF184	0.16	OC45	0.32
2N2907A	0.45	40430	0.85	BC172	0.11	BF186	0.17	OC71	0.12
2N2924	0.14	40583	0.23	BC182	0.12	BF196	0.15	OC72	0.13
2N2925	0.17	40601	0.67	BC182L	0.12	BF197	0.15	OC81	0.20
2N2926	0.42	40602	0.46	BC183	0.09	BF198	0.18	OC83	0.20
Green	0.12	40603	0.53	BC183L	0.09	BF199	0.18	ORP12	0.50
Yellow	0.11	40604	0.58	BC184	0.11	BF200	0.40	SC35D	1.68
Orange	0.06	40606	1.10	BC185	0.10	BF201	0.11	SC38D	1.46
0.11	40669	1.00	BC186	0.25	BF237	0.22	SC40D	1.89	
2N3053	0.32	40673	0.70	BC187	0.27	BF238	0.22	SC41D	1.32
2N3054	0.60	AC107	0.25	BC207	0.12	BF244	0.16	SC45D	1.89
2N3055	0.75	AC113	0.16	BC208	0.11	BF245	0.33	SC46D	1.98
2N3380	0.26	AC117	0.20	BC212K	0.10	BF246	0.43	SC50D	2.80
2N3391	0.28	AC119	0.27	BC212L	0.10	BF247	0.43	SC51D	2.80
2N3391A	0.29	AC127	0.25	BC211	0.21	BF254	0.18	SL414A	4.80
2N3392	0.13	AC128	0.25	BC237	0.09	BF255	0.17	SL623	4.59
2N3393	0.18	AC151V	0.14	BC238	0.09	BF257	0.46	TAA263	0.70
2N3394	0.13	AC152V	0.17	BC239	0.09	BF258	0.59	TAA350	2.10
2N3402	0.18	AC153	0.25	BC251	0.20	BF255	0.55	TAA621	2.00
2N3403	0.19	AC153K	0.26	BC252	0.18	BF254	0.27	TAA661B	1.30
2N3440	0.20	AC154	0.20	BC253	0.23	BF258	0.21	TD100	1.32
2N3441	0.97	AC176	0.18	BC257	0.09	BF261	0.20	TAD110	1.50
2N3442	1.69	AC176K	0.25	BC258	0.09	BF269	0.20	Filter	0.70
2N3414	0.10	AC187K	0.23	BC259	0.13	BF229	0.30	TBA271	0.64
2N3415	0.10	AC188K	0.34	BC261	0.20	BFX30	0.25	TBA641B	
2N3416	0.15	ACY18	0.24	BC262	0.18	BFX44	0.33		2.25
2N3417	0.21	ACY19	0.24	BC263	0.23	BFX62	0.23	TBA800	1.50
2N3638	0.15	ACY20	0.22	BC300	2.12	BFX68	0.30	TBA810	1.50
2N3638A	0.15	ACY21	0.26	BC301	0.34	BFX84	0.24	TIL209	0.35
2N3639	0.27	ACY28	0.20	BC302	0.29	BFX85	0.30	TIP29A	0.49
2N3641	0.17	ACY30	0.42	BC303	0.54	BFX87	0.28	TIP30A	0.58
2N3702	0.11	AD142	0.30	BC307	0.10	BFX88	0.25	TIP31A	0.62
2N3703	0.12	AD143	0.45	BC309	0.10	BFX89	0.43	TIP32A	0.74
2N3704	0.14	AD149V	0.66	BC308	0.09	BFY18	0.35	TIP33A	1.01

New from Siemens
Liquid Crystal Type AN 4131 complete with data. From stock now. Price £13.00 complete with holder ideal for battery operated Quartz clock using two of the latest CMOS ICs from Solid State Scientific. 15v battery operated, minimum of discrete components required. Send SAE for details.

Seven Segment Read Out
Minirion 3015F £1.55
DL707 Litronix £2.35
All data in our new catalogue price 20p

Printed Circuit Marker Pen
DALO 33PC - complete with instructions. No masking! No mess! Red or blue. Price 87p

400mW Zeners 3.3v to 43v
New low price 11p each £8.20 for 100

A large selection of heatinks for all types of transistors from Redpoint, in stock now.
T05-6p T01B-7p
6W1-6" x 4" un drilled £1.00
4W1-4" x 4" un drilled £0.80
2W1-2" x 4" un drilled £0.45

Resistors

Power W	Tol	Price	Tantalum Bead Caps
1/4	5%	1p	Value
1/4	5%	1-5p	1/35v
1/4	5%	2p	22/35v
1	10%	2-5p	47/35v
2	10%	6p	1u/35v
2 1/2	5%	7p	2-2/35v
5	5%	9p	4-7/35v
10	5%	10p	2-2/16v

Veroboard Largest stockist

	Copper	Plain
	-15	-1
2.5 x 3 1/2	20	28
2.5 x 5	30	30
3 1/2 x 3 1/2	30	30
3 1/2 x 5	35	34
2 1/2 x 17	67	89
3 1/2 x 17	95	121

trade or retail supplied

Thermistors
Millard E299DD Series 12 1/2p
E298ED Series 10p
Neg temp Coef VOA1000 Series 20p
RS3E12p
Full details of ranges in our catalogue 20p

Equivalents Books
Transistors 90p
ICs 70p

1-15 Face Cutter 46p
Pins 36pc 24 Insertion Tools 64p
200ppc 89 92

VAT
Please include 10% Vat with all orders
Prices quoted are all exclusive of Vat
Post and Package
13p postage and package charges
Prices correct July 1974


TIP34A	1-51	TIP3055	0-60
TIP35A	2-09	ZTX300	0-12

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR Tel. 021-327 2339

SILICON P.N.P.				SILICON N.P.N.			
Type	Voltage	Frequency	Price	Type	Voltage	Frequency	Price
BCY 71	45	200 MHz	12p	2N 3053	60	100 MHz	17p
BFS 92	100	70 MHz	20p	2N 3707	30	900 MHz	12p
BFS 95	40	70 MHz	17p	2N 5179	20		40p
BFX 12	25	210 MHz	10p	GERMANIUM P.N.P.			
2N 2908	60	200 MHz	18p	ACV 44	50	1 MHz	10p
2N 3702	40	100 MHz	11p	ADY 26	80	75 watts	£1
2N 3703	50	100 MHz	12p	AF 124	20	75 MHz	20p
SILICON N.P.N.				AFY 19	32	350 MHz	20p
BC 106	30	150 MHz	15p	ASV 32	25	5 MHz	10p
BC 109	30	150 MHz	18p	ASZ 21	15	450 MHz	20p
BF 179	225	125 MHz	40p	GET 113	32		10p
BF 180	30	625 MHz	25p	GET 120	32	2 watts	10p
BFW 58	80	80 MHz	15p	OC 123	50	1 MHz	10p
BFX 43	30	500 MHz	20p	OC 70		Light-sensitive	20p
BFX 86	40	50 MHz	17p	2N 1307	30	10 MHz	15p
BFY 53	60	50 MHz	10p	2N 1309	30	15 MHz	15p
2N 687	80	40 MHz	13p	2N 443	60	150 watts	£1
2N 709	15	900 MHz	30p	HIGH FREQUENCY POWER			
2N 718	60	60 MHz	12p	BFR 64	40	1,200 MHz	£1
2N 753	25	250 MHz	12p	BLV 89A	35	650 MHz	£2
2N 744	20	300 MHz	12p	BLV 83A	60	500 MHz	£5
2N 1813	75	60 MHz	17p	BLV 218	36	1,200 MHz	£1
2N 2220	60	250 MHz	18p	2N 709	15	800 MHz	18p

MICROWAVE DEVICES			
CL 8300	Gunn effect oscillator	9-4 GHz	£40
CL 8370	ditto	9-5 GHz	£10
CL 8380	ditto	10-5 GHz	£10
CL 8390	ditto	11-5 GHz	£10
CL 8430	ditto	9-35 GHz	£40
CL 8450	ditto	9-35 GHz	£40
CL 8470	ditto	9-35 GHz	£40
BXY 27	Varactor Diode "S" Band, Cut-off	70 GHz	£1
BXY 28	Varactor Diode, Cut-off	100 GHz	£1
BXY 32	Frequency Multiplier "X" Band	150 GHz	£1
BXY 35A/C	ditto	25 GHz	£1
BXY 36C/D	ditto	75 GHz	£1
BXY 37C/D	ditto	100 GHz	£1
BXY 38C/E	ditto	120 GHz	£1
BXY 39C/D	ditto	150 GHz	£1
BXY 40C/E	ditto	180 GHz	£1
BXY 41C/D/E	ditto	200 GHz	£1

12 VOLT FLUORESCENT LIGHTING

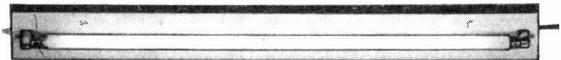

Inverter Transformers 13/15 watt (circuit included) **70p**
 "Current Economy" Transistor (600mA) **50p**
 "Maximum Light" Transistor (1.3A) **50p**
 Resistors/Capacitors to suit **15p**
 Lampholders:
 (Long lead) (pair) **30p**
 (Short lead) (pair) **20p**
 White Enamelled Case, 18 or 21in **70p**
 Tube, 18in/15 watt or 21in/13 watt **45p**
 (Note: tube only supplied if Case also ordered, to prevent postal damage)
 13 watt fitting, ready built and tested (including tube) **£3.75**

ALL GOODS PLUS 10% V.A.T. POST/PACKING 20p PER ORDER

£1 100 1/2 WATT RESISTORS
 100 CERAMIC CAPACITORS
 100 DIODES
 POSTAGE 20p PACK No. 1

£1 1 VEROBBOARD CUTTER
 5 2 1/2 in. x 1 in. x 9-15 BOARDS
 50 SO. INS. "ODD PIECES"
 VERO
 POSTAGE 20p PACK No. 3

£1 20 ASSORTED UNUSED
 MARKED, TESTED
 TRANSISTORS
 BC108, ETC.
 POSTAGE 20p PACK No. 5

£1 8 COMPUTER PANELS
 CONTAINING MASSES OF
 DIODES, TRANSISTORS,
 INDUCTORS, RESISTORS
 & CAPACITORS
 POSTAGE 27p PACK No. 7

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 100 POLYSTYRENE CAPACITORS
 POSTAGE 20p PACK No. 2

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 50 MULLARD POLYESTER CAPACITORS
 POSTAGE 20p PACK No. 4

£1 1 TRANSISTORISED SIGNAL TRACER KIT
 1 TRANSISTORISED SIGNAL INJECTOR KIT
 POSTAGE 20p PACK No. 6

£1 100 RESISTORS
 100 CAPACITORS (ASSORTED TYPES)
 POSTAGE 20p PACK No. 8

TO SPARK YOUR IMAGINATION!
NEW the **SPARKRITE** Mk II
Electronic Ignition Kit
only £11.62

Kit comprises EVERYTHING
 Case, cables, coil connectors,
 Silicon grease,
 8 page instruction leaflet.


Fascinating to build Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £11.62 inc. V.A.T. and postage. (12 volt only State Pos or Neg. earth). Ready built unit also available £14.85 inc. V.A.T. and postage GUARANTEED 5 YEARS.

ORDER NOW—send P.O./Cheque direct to:
ELECTRONICS DESIGN ASSOCIATES, Dept. PE7
 82 Bath St., Walsall WS1 3DE. Phone: 33652

NEW SCORPIO Mk. 2

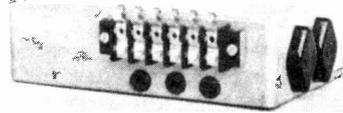

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V. and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board. —Uses original plugs, points, and coil.—No special parts or extras required. (Case size 7 1/2 in x 4 1/2 in x 2 in)

* All components available separately.—S.A.E. with enquiries.
 * Construction manual available separately 25p.
 Cost £12.95 incl. carr., ins. and VAT. (Carriage at cost outside U.K. —Export enquiries welcome.)

CONVERSION KIT FROM Mk. 1 to Mk. 2. FOR CONSTRUCTORS ALREADY POSSESSING Mk. 1 KITS.—Miniature P.C. assembly £1.10 incl. Carr., Ins. and VAT with full conversion instructions.

DABAR ELECTRONIC PRODUCTS
 98 LICHFIELD STREET
 WALSALL, Staffs WSI 1UZ

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

PATCHBOARDS FOR SYNTHESISER

SYNTHESISER patchboards consist of a matrix of jack sockets by which any combination of input and output signals may be connected by inserting a shorted jack plug into the appropriate socket. A patch board for a medium sized synthesiser would require about 14 inputs and 20 outputs, making a total of 280 jack sockets which at 10p each plus the cost of plugs adds up to around £30.

The system to be described has two advantages: a system as previously described would cost only £6, and this type of patchboard can be used to programme the synthesiser.

The patchboard is made from 20 sixteen-way edge connectors, the 0.15in matrix size being the most practical. Each connector has its first and last pins wired to the output (Fig. 1). The remainder are wired to separate inputs.

In practice a piece of Veroboard also of 0.15in matrix is plugged into the connector. The first and

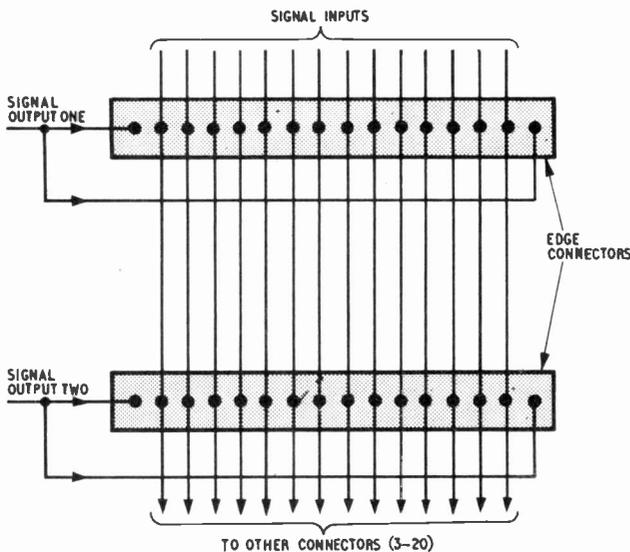


Fig. 1. Suggested wiring for the edge connectors

last copper strips on the board are joined by means of a link wire which also connects to one or more intermediate strips. This forms a link between the output and one or more of the inputs according to how the board is wired.

By removing the board it can be turned over and plugged into the same connector making a completely different link or patch between the inputs and outputs. The opposite end of the board can also be used in this way making a total of four different connections available from each board (see Fig. 2).

The programme cards can be numbered for their particular function, e.g. board No. 5 will connect output 3 to input 7, etc.

J. A. Knife,
Dagenham, Essex.

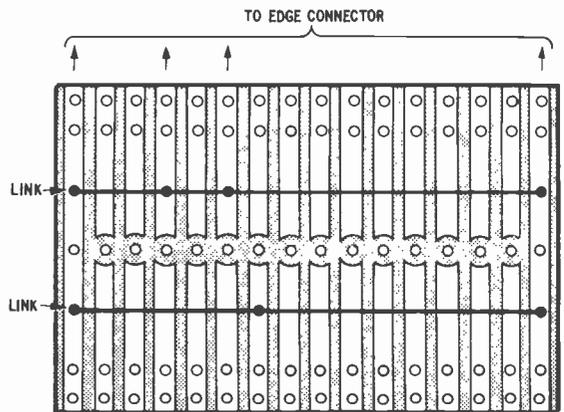


Fig. 2. Wiring details for a programme card

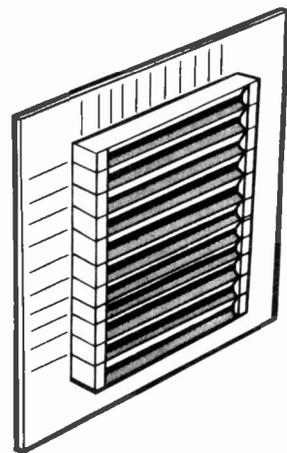


Fig. 3. Typical arrangement of connectors mounted on panel of synthesiser



BOOK REVIEWS

ELECTRONICS — A handbook for Engineers and Scientists

By G. H. Olson

Published by Butterworths

482 pages. Price £7

EVER increasingly the influence of electronics is felt by more and more people whose disciplines would traditionally have been unrelated. Probably the biggest contribution to this has come in the application of electronic techniques to measurement and control in various forms of sophisticated instrumentation. All of this has demanded an understanding of the subject, be it ever so superficial.

As a lecturer with an awareness of the "language" problem of the non-electronic specialist the author has provided a course which is qualitative and informative and will be prized as a valuable reference. The depth of subject treatment is not superficial nor does it lean towards being an examination textbook. In these, usually very little attention is paid to practical details in rigorous analyses. In the handbook these aspects are common and some useful circuits are given with details of the components.

From an introductory chapter on passive components, simple circuits containing them are analysed. Semiconductor devices are then examined (thermionic valves are eschewed throughout) followed by a chapter on indicating instruments. Next comes power supplies, then a massive chapter on the various genre of amplifier.

The concluding chapters embrace oscillators, an introduction to logic and digital circuits and measuring instruments.

Useful references for further reading are included after chapters and appendices provide the means to resolve some of the finer points mathematically.

At £7 pricey, but a good investment for the d.i.y. tyro.

G.G.

RECORDING WITH COMPACT CASSETTES

Published by Agfa-Gavaert

91 pages, 210mm × 150mm. Price 65p

THE THEORY and practice of cassette tape recording are combined in this concise, non-technical, well-illustrated book.

Besides the cassette itself there is an excellent description of the theory behind tape recording, from the conversion of sound into an electronic signal to the actual recording of the signal by the head.

The book is full of hints and suggestions for getting the most out of a cassette recorder.

Many of the illustrations are in full colour, and overall the book seems excellent value for money.

This book is just one of a series on tape recording and photography and can be obtained direct from Agfa-Gavaert Ltd., Great West Road, Brentford, Middlesex.

S.R.L.

QUESTIONS AND ANSWERS ON INTEGRATED CIRCUITS

By R. G. Hibberd

Published by Newnes-Butterworths

96 pages, 6½in × 4½in. Price 75p

AS ANY regular reader of Practical Electronics will realise, the integrated circuit is now a well-established component in modern electronics. However, the development of these devices from the unusual to the commonplace has been so rapid that many people will no doubt be feeling a little left behind.

For anyone in this position, this little book provides an excellent introduction to the field. In the form of questions and answers it gives the reader information about how integrated circuits are made, their advantages and disadvantages over discrete components, and their uses, both in the area of digital and linear electronics.

In the section on Digital Integrated Circuits there is a useful introduction to logic which is essential to the understanding of digital systems.

The book is written for students and technicians who require a simple, mainly non-mathematical, text on this rapidly widening facet of electronics.

S.R.L.

INSTRUMENT TECHNOLOGY (Volume 1)

By E. B. Jones

Published by Newnes-Butterworths Ltd.

402 pages, 9½in × 6½in. Price £5-00

THIS is a new (third) edition of a book which was first published in 1953 and forms the first volume of a three volume set dealing with Instrument Technology. The coverage of this volume is restricted to the measurement of pressure, level, flow and temperature and the treatment uses S.I. units throughout. The presentation is lucid and the mathematics have been kept as simple as possible. Together with the other two volumes of the set, this book should provide a good coverage of much of the material normally found in technician and craftsman level courses dealing with process control and instrument technology and should also prove useful as a reference text for engineers and other personnel who are not experienced in this field.

The text is well illustrated with clear diagrams, photographs and exploded views of numerous instruments which should prove useful to students especially, since they do not normally have access to such a comprehensive range of instrumentation.

Electronic devices and techniques such as the pressure sensitive transistor and the application of lasers to level measurement are not covered and the brief section on transistors, diodes and photocells does not reflect present day technology. In a work such as this the selection of material is difficult due to the wide range of instruments in current use. The author's stated aim has been to give a reasonably complete picture of the more common and more important devices in present use and this has been achieved. It is unfortunate that the price of this book will put it out of the range of the average student's pocket.

P.R.A.

BI-PRE-PAK

STEREO DECODER £4.95




incl. P. & P. and V.A.T.

Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tell tale light can be connected. The unit is a small printed circuit, no further alignment necessary. L.E.D. is recommended as the indicating light, suitable device available from us at 36½p. Instructions included.

3 W.R.M.S. I.C. AMP only £1.65

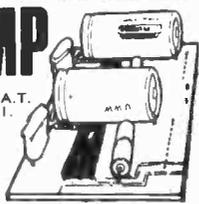
incl. P. & P. and V.A.T.
Order Code I.C.A.1.



On P.C. Board with all components or 2 on one board for £2.86. Order Code I.C.A.1/S.

These amps. are supplied with a free booklet on connecting up, specifications and easy-to-build projects using the I.C.A.1

5W & 10W AMPS

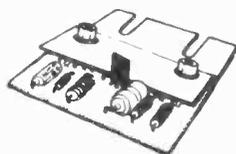

5W ONLY £1.98
10W ONLY £2.49

incl. P. & P. and V.A.T.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2½in × 1½in. The 5W Amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the U.K. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2in × 3in available in stereo only, will fit 0-15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain or ceramic pick-up cartridges. **£1.21**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. **£1.69**

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.21**

Instruction leaflet supplied with all units. Post and packing and V.A.T. included in prices.

enclose £.....for
.....Decoders/.....3W Amps/.....5W Amps
.....10W Amps/.....Stereo Pre-Amps 1
.....Stereo Pre-Amps 2.....Stereo Tone Controls
(Please insert quantities and delete those not applicable).

Name

Address

BI-PRE-PAK

Dept. A, 212/214 West Road,
Westcliff-on-Sea, Essex SS0 9DF.
Telephone: Southend (0702) 46344.

Ca. Regn. No. 820919

Great Holiday Project



In only two evenings you can build one of these Heathkit Professional Metal Locators. Your kit comes complete down to the last nut and bolt—all you have to do is follow our simple step-by-step instructions and you're ready to go. You'll be really amazed at how easy it is.

Ideal for:

- Treasure hunting
- Beachcombing
- Locating dropped coins and other metal objects
- Tracing hidden piping underground and many other uses in and around the home.

For details about these and many more models in our range, send for your FREE copy of the Heathkit Catalogue—today!

Please send me the FREE Heathkit Catalogue plus details of your low deposit terms. Without obligation.

NAME

ADDRESS

.....

.....



Heath (Gloucester) Ltd.,
Dept. PE/7/74, Bristol Road,
Gloucester GL2 6EE

WILMSLOW AUDIO

THE Firm for Speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£7-75
Baker Group 35, 3, 8 or 15 ohm	£8-50
Baker Group 50/12, 8 or 15 ohm	£12-50
Baker Deluxe	£10-75
Baker Major	£8-50
Baker Superb	£14-50
Baker Regent	£7-75
Celestion PST8 (for Unilex)	£2-55
Celestion MF1000, 8 or 15 ohm	£10-45
Celestion HF1300 Mk. II	£6-16
Celestion G12M, 8 or 15 ohm	£12-00
Celestion G12H, 8 or 15 ohm	£15-00
Celestion G15C, 8 or 15 ohm	£24-00
Celestion G18C, 8 or 15 ohm	£33-00
EMI 13 x 8in, 3, 8 or 15 ohm	£2-15
EMI 13 x 8in d/c, 3, 8 or 15 ohm	£2-35
EMI 13 x 8in U/w, 3, 8 or 15 ohm	£3-60
EMI 13 x 8in type 350, 8 ohm	£8-25
EMI 8 x 5in cer. mag., 8 or 15 ohm	£1-65
EMI 8 x 5in, 10 watt, d/c roll, surr., 8 ohm	£2-50
EMI 6 1/2in, 93850, 4 or 8 ohm	£2-80
EMI 5in, 98132CP, 8 ohm	£2-30
Elac 9 x 5in, 59RM109 15 ohm, 59RM114 8 ohm	£2-65
Elac 6 1/2in d/c roll surr., 8 ohm	£3-35
Elac 6 1/2in d/cone, 8 ohm	£2-65
Elac Tweeter TW4 4in	£1-21
Elac 10in, 8 ohm	£2-65
Fane Pop 100 watt, 18 in	£22-50
Fane Pop 60 watt, 15in	£13-00
Fane Pop 50 watt, 12in	£11-00
Fane Pop 25/2, 12in	£6-40
Fane Pop 15 watt, 12in	£4-40
Fane Crescendo 12A or 12B	£29-00
Fane Crescendo 15	£36-00
Fane Crescendo 18	£47-50
Fane 807T 8 in d/c roll surr., 8 or 15 ohm	£3-85
Fane 808T 8in d/c, 8 or 15 ohm	£2-75
Goodmans 8P, 8 or 15 ohm	£4-49
Goodmans 10P, 8 or 15 ohm	£4-70
Goodmans 12P, 8 or 15 ohm	£11-65
Goodmans 15P, 8 or 15 ohm	£18-00
Goodmans 18P, 8 or 15 ohm	£31-00
Goodmans 12P-D, 8 or 15 ohm	£15-25
Goodmans 12P-G, 8 or 15 ohm	£14-50
Goodmans 12AX Audiomax, 8 or 15 ohm	£39-65
Goodmans Audiom 100	£9-50
Goodmans Axent 100	£6-60
Goodmans Axiom 401	£15-10
Goodmans Twinaxiom 3, 8 or 15 ohm	£6-79
Goodmans Twinaxiom 10, 8 or 15 ohm	£7-61
Kef T27	£4-75
Kef T15	£5-75
Kef B110	£6-75
Kef B200	£7-50
Kef B139	£11-75
Kef DN8	£1-92
Kef DN12	£4-12
Kef DN13	£2-75
Richard Allan 12in d/c, 3 or 15 ohm	£2-50
Richard Allan CG8T 8in d/c, 8 ohm	£6-35
WMT1 speaker match. trans., 3-15 ohm	£1-10

Wharfedale Super 10 RS/DD	£9-80
2 1/2in 64 ohm, 70mm 8 ohm, 70mm 80 ohm	65p
7 x 4in, 3, 8 or 15 ohm	£1-38
8 x 5in, 3, 8 or 15 ohm	£1-38
10 x 6in, 3, 8 or 15 ohm	£1-92
S.T.C. 4001G Super Tweeter	£6-19

Speaker Kits

Wharfedale Linton 2 (pair)	£19-25
Wharfedale Glendale 3 (pair)	£34-50
Wharfedale Dovedale 3 (pair)	£52-00
Richard Allan Twinkit (each)	£8-25
Richard Allan Triple 8 (each)	£13-00
Richard Allan Triple (each)	£18-50
Richard Allan Super Triple (each)	£21-50
Goodmans DIN 20 (each)	£8-75
Fane Mode 1 (each)	£9-90
Peerless 3-15 (3SP.) (each)	£15-00
Kefkit 2 (each)	£23-50
Kefkit 3 (each)	£34-00
Helme XLK25 (pair)	£18-17
Helme XLK50 (pair)	£37-18
Helme XLK30 (pair)	£14-95
Baker Major Module	£10-75
P.A. and Hi-Fi speaker cabinets. Send for Free booklet "Choosing a Speaker". Carr. and Insurance 75p per kit (£1-50 pair).	

PA/Disco Amplifiers

(Carriage and Insurance £1)	
Baker Major 100 watt	£46-00
Linear 30/40	£25-00
Linear 40/60	£30-00
Linear 80/100	£55-00

Radios/Cassettes

Grundig Soio Boy	£16-00
Grundig Top Boy	£17-75
Grundig Party Boy 500	£22-75
Grundig Melody Boy 500	£26-75
Grundig Elite Boy 500	£26-75
Grundig Signal 500	£26-50
Grundig Yacht Boy 210	£34-00
Grundig Melody Boy 1000	£38-75
Grundig Satellite 2000	£121-00
Grundig C410 Cassette	£28-50
Grundig RF430 mains radio	£26-75
Grundig RF310 mains radio	£22-00
Tanberg TP41	£43-00
ITT Weekend Auto	£18-00
ITT Golf Preset	£24-50
ITT Colt	£11-50
ITT Europa	£20-50
ITT SL53 cassette	£25-75
ITT Studio 60M cassette	£32-75
ITT Studio 73 cassette	£48-00
Bush VTR178, 5 band (inc. air)	£29-00
Koyo KTR1770 11 band	£58-95
Koyo KTR1663 or 1664, 8 band	£42-00
Koyo KTR1883, 5 band	£22-00
Murphy BA209 radio/cassette	£32-75
Carriage and Insurance 75p. FREE with each radio—World radio stations book.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage 35p per speaker (tweeters and crossovers 20p).

ALL PRICES QUOTED INCLUDE VAT


WILMSLOW AUDIO

Dept. PE

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.

Radios, etc.: 10 Swan Street, Wilmslow, Cheshire. Telephone: Wilmslow 29599

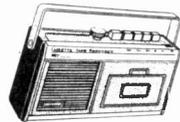The items below are from the April Supplement to our 1974 Catalogue. You can receive this Catalogue and the next 12 supplements by sending 86p.



THIS MONTH'S SNIP Cassette Tape Player Recorder

With dynamic microphone. First class Jap. made tape recorder and player. Pushbutton operated and with automatic level control of recording. Standard cassettes clean jacks for intc. (which has motor stop/start switch) for recording from radio and for being powered by mains. A bargain at £89.95 plus 35p post, etc.

Mullard Unilex. The 4 Mullard modules—2 EP9000, 1 EP9001, 1 EP9002, for £7.50 plus 30p post. The control panel kit, with spun aluminium faced knobs and silk screened front plate cannot be added, but at least we will hold the price at £3.80 despite increases in prices.

Spartan Portable Radio. Long and medium wave band, telescopic pull up aerial, leather carrying case, size approx. 6in x 4in x 2in. 7 transistors ferrite rod aerial. Uses comparatively large speaker, so tone better than average. Brand new in original packing case, untested, only £1.95 each.

Instant Start! Fluorescent Lighting bargains. Starter-less control gear, resin filled, super-silent cool running, by very famous maker. 4ft 40W £1.50, 5ft 65W £1.60, 5ft 80W £1.75, 6ft 85W £1.95. These at about one half of maker's current prices and can't be repeated once stocks are cleared: Add 20p per piece carriage.

Bulk head aerial lead out. 2 cone shaped porcelain insulators with cork wafers for waterproofing and OBA brass rod passing through centre, terminal heads top and bottom. Price 75p each.

Message tapes. 250ft best quality PVC tape (USA made) on a 3in spool. Packed in small mailing box. 30p each. 3 for 75p.

Mains transformer 12V-0-12V 1 amp. Small construction for instruments, size approx. 1in cube, upright mounting with fixing lugs. £1.84.

Output Transformer. Ratio 140:1 midget size 1in x 1 1/2in x 1 1/2in. Primary impedance 450 ohms, connections by flying leads, upright mounting. 46p.

Output Transformer. Ratio 80:1, small size, approx. 1 1/2in x 1in x 1in, printed circuit board connection. 56p.

Light cell. Has almost no resistance in sunlight but increases to over 200k in the dark. Size not much more than the top of a pencil with wire leads. 22p. Clock movement has hour and minute hands which are fairly easy to extend in any length required. Mains operated, has switches but these are easy to remove. The movement made by Smiths, very reliable, price £2.

Planning for your holiday! Don't forget your *mini immersion heater* to make your hot drinks. Room service is usually not all that can be desired in holiday hotels and you will save the cost of your immersion heater on your first holiday, even though they have gone up slightly in price. Post and VAT paid, £1.90 each. If going camping, we have a 12V battery model, 10p more.

Mains induction motor. 1in stack with 1in diameter spindle protruding from each end. This motor is particularly well made and quiet running, good quantities in stock. Price 65p.

0-100 micro amp meter. Large oblong, full vision front, size 4 1/2in x 3 1/2in approx. Good quality Japanese made, moving coil meter. £3.85.

Mains suppressor adaptor for preventing or reducing interference caused by office machines, vacuum cleaners, sewing machines, etc. This plugs into a 3 amp socket and takes a 3 amp plug. Its rating, however, is 4 amps. Limited quantity. 45p each. 50 cycle to 60 cycle inverters. For operating American instruments and other equipment made for 60 cycles 115V from 230/240 50 cycle mains. These units have an output of 115V a.c. and will handle a load of up to 100W. These are precision made and have a reed type frequency meter which vibrates when the frequency is exactly 60 c.p.s. Adjustment of the frequency is by a knob on control panel. Input by 3 core output from 3 pin socket. Original cost of this in excess of £60. A limited quantity available £25 each.

Reed Relay. Glass encapsulated reed switch in 24V solenoid, neatly enclosed in neat metal case, size 2 1/2in x 1 1/2in x 1 1/2in. Operates from 24V d.c. or from a.c. mains. Price 35p each.

Battery Model, Balfour Auto-charger. As mains model but for 24V operation, also these are new ex-factory stock not returned export. Less carriage £6 each plus £1 post and insurance.

TERMS: Add 10% V.A.T.


Send postage where quoted—other terms, post free if order for these items is £6.00, otherwise add 20p.

J. BULL (ELECTRICAL) LTD.

(Dept. PE), 7 Park Street
Croydon CR0 1YD Callers to:
102/103 Tamworth Road, Croydon

RANDOM LIGHT DISPLAY

By K.L. SPENCE

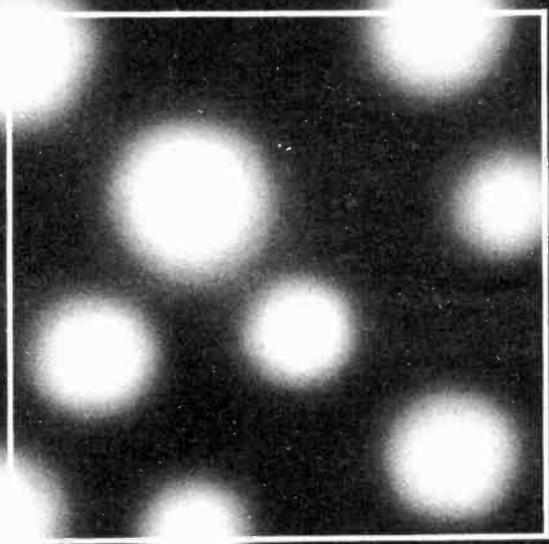

THIS article describes a Random Light Display which, unlike most light displays, is not driven by an audio signal.

The unit consists of nine or more coloured lamps positioned behind a semi-transparent screen. Each lamp flashes on and off in an apparently random manner, without an overall fixed sequence. The resulting effect is to fill the screen with a blaze of mixing and changing colours forming a fascinating display.

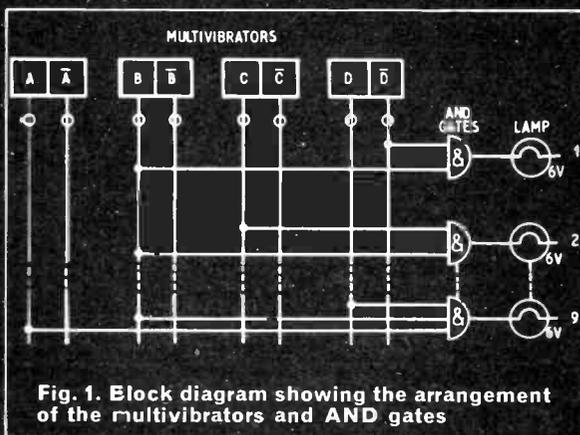


Fig. 1. Block diagram showing the arrangement of the multivibrators and AND gates

METHOD OF OPERATION

The apparent random effect is achieved by using four slow-running multivibrators each with different frequencies and mark-space ratios.

Each lamp is driven by gating together the outputs of two or more multivibrators using a logic AND gate. The system is illustrated in Fig. 1, which shows the overall arrangement of the multivibrators and AND gates.

It can be seen that lamp LP1 will only light when multivibrator outputs B and D are high, i.e. logic 1; lamp LP2 requires outputs B and C high, and lamp LP9 requires A, B and D high.

CIRCUIT DETAILS

The circuit diagram of a multivibrator is shown in Fig. 2. Four of these are required, the values of the timing capacitors C1 and C2 being given in the table.

The AND gate and lamp driver circuit is shown in Fig. 3.

The gate may have two, three or four diode inputs. If any of the inputs is taken to 0V by a multivibrator output then current will flow down resistor

COMPONENTS . . .

MULTIVIBRATORS—4 OFF REQUIRED

Resistors


R1, R4 5.6k Ω (2 off)
R2, R3 33k Ω (2 off) } 1/4W 10% carbon

Capacitors

C1, C2 see table


Transistors

TR1, TR2 2N708 (2 off)

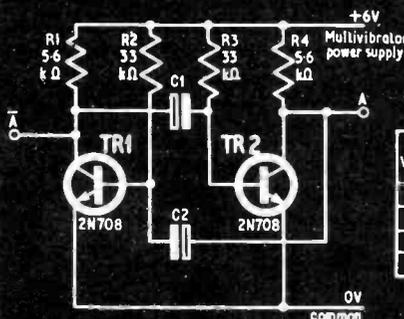

MULTI VIBRATOR	C1 μ F	C2 μ F	CYCLE TIME SECS
A	100	50	3 1/2
B	250	150	9
C	50	25	2
D	250	100	8

Fig. 2. Circuit diagram of a single multivibrator circuit. The table shows the values of the timing capacitors for the four multivibrators required

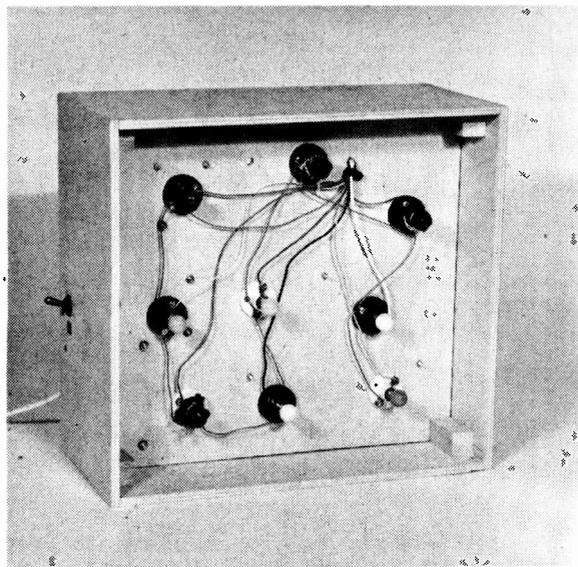

Photograph showing a front view of the completed unit with the cover removed

R1 and the voltage at TR1 base will not be sufficient to switch on transistors TR1 and TR2 which need about 1.4V to be forward biased.

However, if all inputs are at 6V then the diodes will be reverse biased and the current through R1 will flow into the base of TR1 causing it and TR2 to conduct and the lamp to light.

COMPONENTS . . .

AND GATE/LAMP DRIVERS—9 OFF REQUIRED

Resistors

R1 8.2kΩ ½W 10% carbon

Diodes

D1-D4 OA200 (4 off, or as required)

Transistors

TR1 2N708

TR2 BFY52

Lamps

LP1 6V 0.3A m.e.s. with lampholder

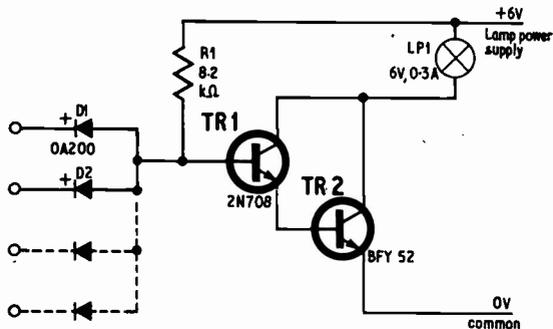


Fig. 3. Circuit diagram of a single AND gate/lamp driver circuit. Nine of these are required. The number of diode inputs may be two, three or four

COMPONENTS . . .

POWER SUPPLY

Resistors

R1 82Ω ½W 10% carbon

Capacitors

C1 500μF 12V elect.

C2 250μF 12V elect.

Diodes

D1-D4 50V 5A bridge rectifier

D5-D8 50V ½A bridge rectifier

D9 6.2V 400mW Zener

Transformer

T1 Mains primary, 6.3V 3.6A secondary

T2 Mains primary, 6.3V ½A secondary

Miscellaneous

S1 2 pole mains on/off

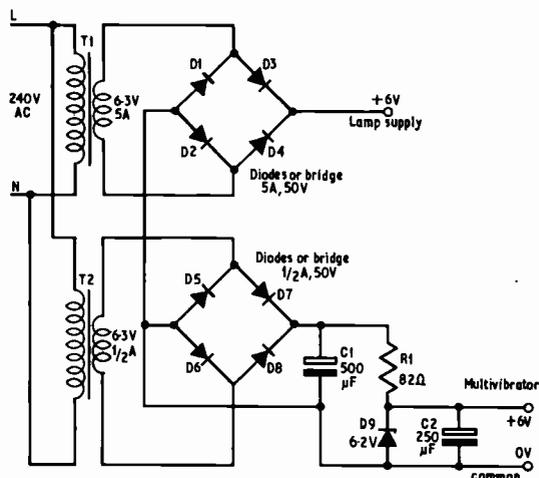


Fig. 4. Circuit diagram of the power supply. This provides a smoothed supply for the multivibrators and unsmoothed supply for the lamps

POWER SUPPLY

The power supply is shown in Fig. 4. It has two 6V outputs, one is smoothed for the multivibrators and the other is unsmoothed for the lamps.

The components specified are widely available, though discrete diodes instead of a bridge may be used if desired.

CONSTRUCTION


Component layout is not at all critical and the circuits may be built on any type of wiring board.

The author used a large piece of 0.1in Veroboard, the general arrangement being seen in the photograph. Fig. 5 shows the multivibrator circuits and the lamp driver circuits in more detail. Four of the multivibrators and nine lamp drivers are required.

It is useful to provide a wiring pin for every multivibrator output and gate input as this greatly simplifies the cross-connections.

It is advisable to first construct and test all the multivibrators and gates and then make the connections between them.

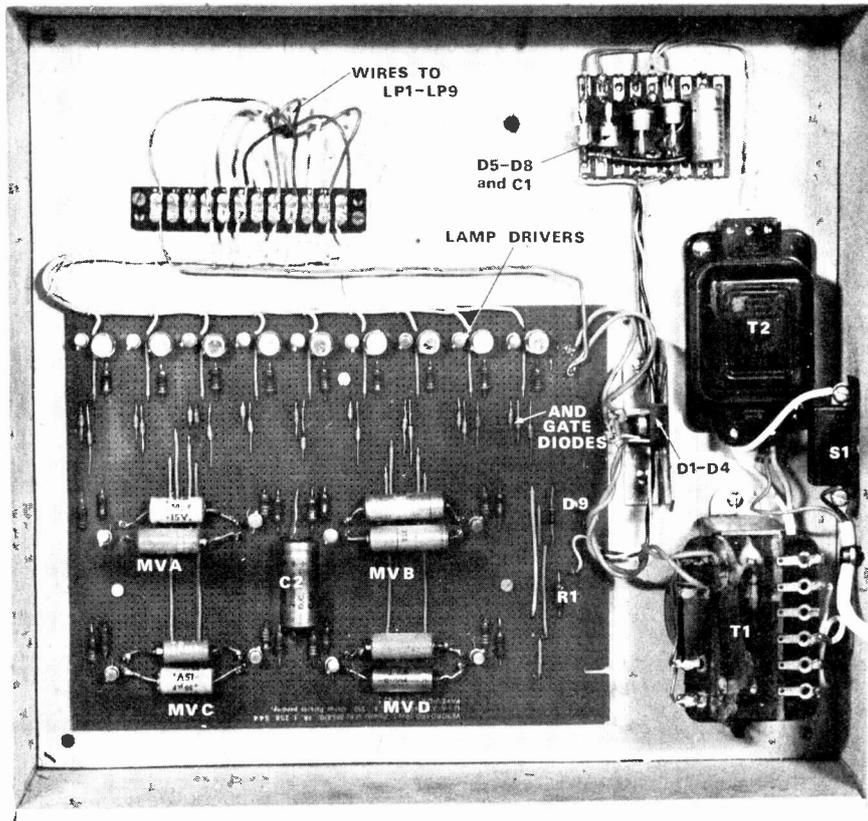The constructor is free to choose for himself which outputs to connect to each gate, the only restriction being that both the outputs of a particular




Photograph showing the general arrangement of the components at the rear of the box. The power supply Zener diode, resistor R1 and capacitor C2 are mounted on the Veroboard which carries four multivibrators (MVA to MVD) and nine AND gate/lamp drivers

multivibrator must not be connected to the same gate, as this would mean the lamp would never light.

Fig. 5. Suggested Veroboard layout for the multivibrators and for an AND gate/lamp driver circuit. The circuits shown are typical; breaks should be repeated as shown between circuits.

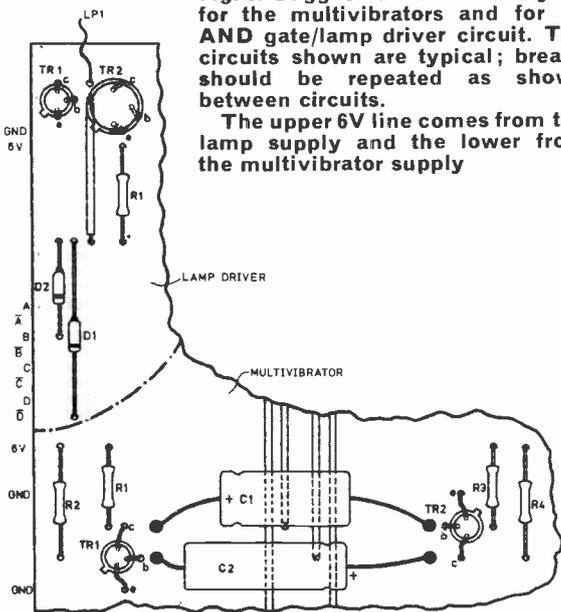The upper 6V line comes from the lamp supply and the lower from the multivibrator supply



The gates may have two, three or four inputs but it should be remembered that gates with four inputs will only be enabled very infrequently compared with the two-input gates.

Photographs illustrate the general manner of construction with lamps in the front of the box and the circuits behind.

The overall size is governed by the number of lamps the constructor decides to use. The prototype measured 15in × 15in × 6in and had nine lamps.

FRONT SCREEN

The front screen consists of a wooden frame covered with thin white cloth or tracing paper. A sheet of Perspex is then fixed on the front for protection.

The lamps may be any 6V types and they may be covered with coloured Cellophane or painted.

MODIFICATIONS

The unit described in this article may be extended to many more lamps and multivibrators providing the transformer can handle the power output.

Higher wattage lamps could be used by incorporating thyristors in the lamp driver circuits. It could also be interesting to have a mixture of AND and OR gates instead of only AND gates.

The values of the timing capacitors can be changed to give more rapid or slower changes as the constructor desires.

F.M. STEREO TUNER

BY R.A. COLE

THE Rondo system is designed specifically to accept a variety of inputs to suit individual constructor's tastes. However, the initial design concept included the basic idea of providing as many facilities as possible within the one unit. One of the most important to many constructors will of course be the stereo tuner and associated decoder and Part 8 will initiate the discussion of these two items.

GENERAL CIRCUIT

The basic system for an f.m. tuner and decoder is shown in block form in the accompanying Fig. 8.1 and the complete circuit in Fig. 8.2. A varicap-tuned head feeds its output to a wide-band amplifier, a ceramic filter, a further i.f. amplifier and finally to the stereo decoder. Movement of the varicap potentiometer VR1 is indicated on a suitable tuning dial and a tuning meter indicates signal level.

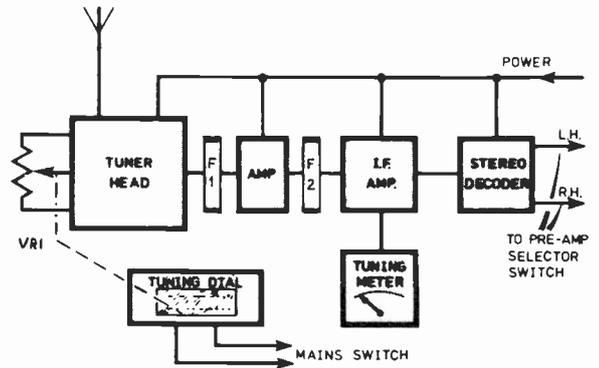


Fig. 8.1. Block diagram of the f.m. stereo tuner/decoder arrangement for the Rondo system

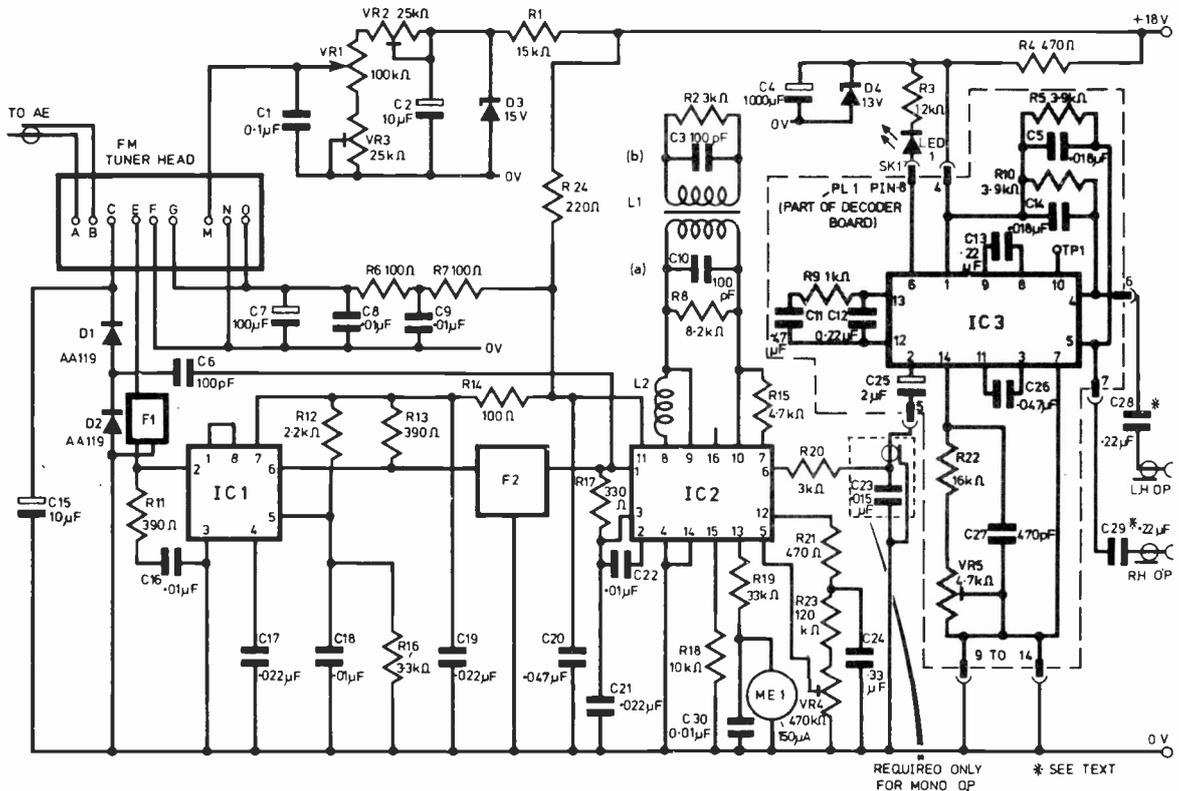


Fig. 8.2. Full circuit diagram of the tuner and decoder with the decoder board shown shaded

STEREO DECODER

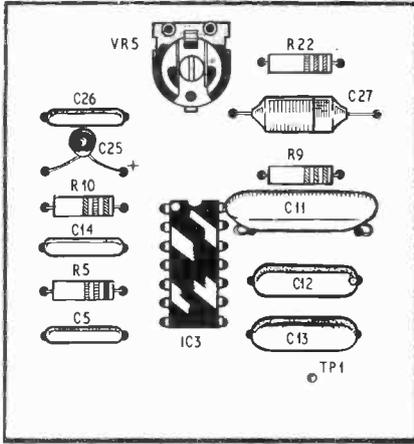


Fig. 8.4. Component layout on p.c.b. for the stereo decoder



Fig. 8.5. Master p.c.b. copper layout for the decoder board


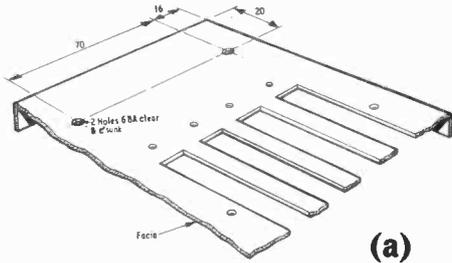


Fig. 8.6. (a) Rear right-hand corner of fascia panel (see Fig. 4.1). (b) Details for the mounting of the decoder board edge connector and associated carrying brackets, their location in the main assembly, and the positioning of some off-board components

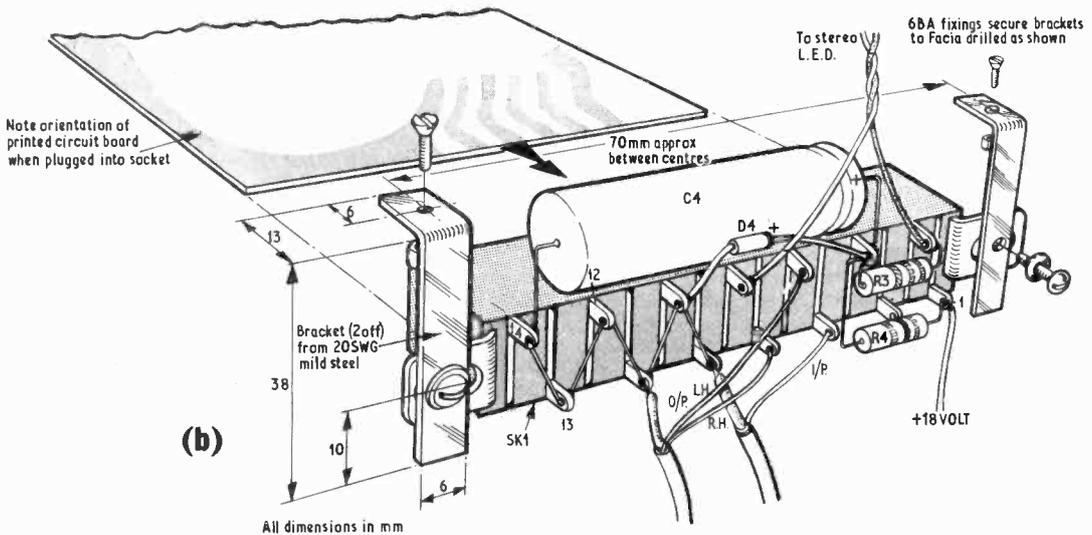

PE RORDO

COMPONENTS . . .

Resistors

R1	15k Ω	R13	390 Ω
R2	3k Ω	R14	100 Ω
R3	1.2k Ω	R15	4.7k Ω
R4	470 Ω	R16	3.3k Ω
R5	3.9k Ω	R17	330 Ω
R6	100 Ω	R18	10k Ω
R7	100 Ω	R19	33k Ω
R8	8.2k Ω	R20	3k Ω
R9	1k Ω	R21	470 Ω
R10	3.9k Ω	R22	16k Ω , $\frac{1}{2}$ W, 2%
R11	390 Ω	R23	120k Ω
R12	2.2k Ω	R24	220 Ω

All $\frac{1}{2}$ W, 5% except where stated

Capacitors

C1	0.1 μ F	C18	0.01 μ F
C2	10 μ F, 25V	C19	0.022 μ F
C3	100pF Polystyrene	C20	0.047 μ F
C4	1,000 μ F	C21	0.022 μ F
C5	0.018 μ F	C22	0.01 μ F
C6	100pF Polystyrene	C23	0.015 μ F, De-emphasis
C7	100 μ F, 16V	C24	0.33 μ F
C8	0.01 μ F	C25	2 μ F or greater, Tantalum bead preferred
C9	0.01 μ F	C26	0.047 μ F
C10	100pF	C27	470pF, 2% Polystyrene
C11	0.47 μ F	C28	0.22 μ F
C12	0.22 μ F	C29	0.22 μ F
C13	0.22 μ F	C30	0.01 μ F
C14	0.018 μ F		
C15	10 μ F, 25V		
C16	0.01 μ F		
C17	0.022 μ F		

Potentiometers

VR1	100k Ω Lin
VR2	25k Ω Lin preset
VR3	25k Ω Lin preset
VR4	470k Ω Lin. preset
VR5	4.7k Ω Lin. preset

Diodes

D1	AA119
D2	AA119
D3	BZY88, 15V Zener, 400mW
D4	BZY88, 13V Zener, 400mW
LED1	Light emitting diode

Integrated Circuits

IC1	CA 3053
IC2	CA 3089E or TDA 1200
IC3	MC1310P or CA1310E

Inductors

L1	Single quadrature, KACS K586 HM or Double quadrature TKACS 34343 AVO and TKACS 34342 AVO from Toko U.K.
L2	R.F. Choke, 22 μ H

Miscellaneous

Head	Larsholt 8317-501 stereo tuner head, f.m.
Tuning meter ME1	0-150 μ A Full-View panel meter
Ceramic Filters F1, F2	CFS 107M (Toko)
Assorted wire, co-axial cable, p.c.b., 14-way edge connector, metalwork brackets, nuts and screws etc.	

decoder switching to stereo mode when the audio is too weak to give good signal-to-noise ratio.

Indication of stereo presence is given by the light emitting diode LED1 which is wired in series with a 1.2k Ω resistor. This latter drops the voltage across the diode to around 1.6V at 20mA. As most diodes give adequate light emission at this current this seems sensible even though the i.c. is capable of driving up to 100mA if necessary.

The decoder and associated de-emphasis components are mounted on one board as shown in Fig. 8.4. The master negative for this board is shown in Fig. 8.5 and two combined scrap views show the orientation of the board in its edge connector and the mounting of this latter under the master tone control board in Fig. 8.6.

Assembly of the decoder board follows normal p.c.b. assembly procedure although it will be noted that several components from the decoder and tuner-associated circuitry are in fact mounted in the wiring, as it were. Thus R3 and R4, C4 and D4 are all mounted on the edge connector carrying the decoder board. The l.e.d. is mounted in the tuner fascia just above the tuning meter. C28 and C29 can be mounted on the pre-amplifier board.

Wiring from the decoder board is passed down the side of the fascia to the fanning-strip/switch assembly described in the last part for interconnection to the remainder of the looming.

OSCILLATOR ALIGNMENT

When the tuner/decoder system has been completed it is necessary to set the decoder oscillator. This is a simple procedure requiring that one tunes to a known broadcast and then adjusts VR5 until the pilot light illuminates. This of course assumes a stereo broadcast is taking place.

Stereo output should now be heard from the loudspeakers.

If an oscilloscope is to hand the adjustment can be made perhaps more accurately by connecting the scope to the v.c.o. test point TP1 (pin 10 of the i.c.) and adjusting VR5 until a 19kHz waveform (55 μ s cycle time) appears. Equally, a counter/timer could be used to register 19kHz.

Tolerance of this value is ± 3 per cent or 580Hz either side of 19kHz.

I.C. HOLDERS


An important point is the use of i.c. holders with these types of i.c.s. It is always advisable to use holders since this gives the obvious advantage of being able to remove the i.c. later and in any case some manufacturers revoke their guarantee if their particular products have been soldered in position as there is always the risk of thermal damage occurring.

It will be appreciated that each additional item of equipment inserted in the Rondo is an extra load applied to the power supply. In general terms this is no problem since the p.s.u. is well able to deal with the demand placed on it. However, the problem is easily overcome if it does arise by simply turning TR6 of Fig. 3.1 in Part 3 "on" a little more. This can be achieved by simply lowering the value of R32 in the same figure to 470 Ω .

Next month: Construction details for the tuner board and mechanical assembly

CAR SYSTEMS MONITOR

BY J.P. PERRY

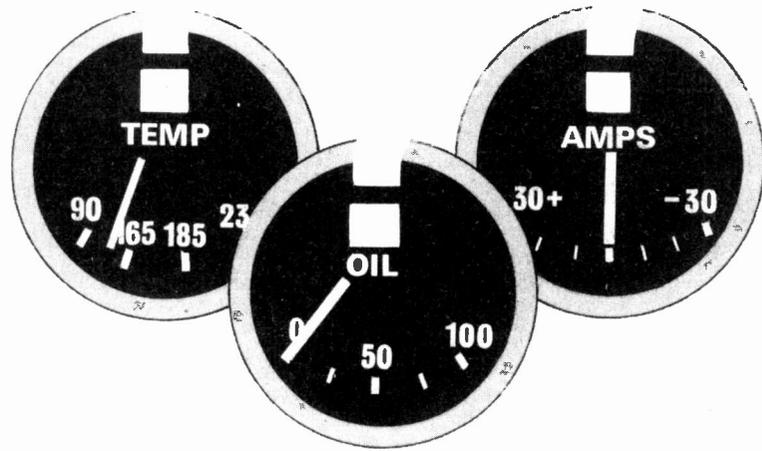

EVEN in this day and age it is not unusual to find cars stranded at the side of a motorway after having suffered boiling perhaps through loss of a fan belt or a burst hose.

Remembering that most vehicles are fitted with some form of temperature indicator for water temperature this sort of event only serves to indicate just how little attention is paid to the various dials by a driver, particularly when coping with things like motorways.

Oil, water and indeed battery charge, are all indicated visually and their loss, which can occur quietly and seemingly unnoticed, can have very damaging results including seized engine bearings or the like. So clearly what is needed is some form of audible indication in the event of failure of these parameters.

The present circuit was designed to give an instantaneous audible alarm if water temperature, oil pressure or generator output assume a fault condition.

The circuit is fairly simple and would probably cost in the region of £3 which is cheap in comparison with the cost of replacing a damaged engine or even carrying out a minor repair with labour costs in the £3 per hour region.

PRACTICAL CIRCUIT

A circuit is shown in Fig. 1. Three inputs can be connected to detect the presence or absence of voltage at for example the car temperature gauge, the ignition warning light and the oil pressure switch. In each case if the respective point is connected to chassis (earth) an alarm condition can be said to exist.

If this occurs current is taken by the associated one of the three diodes D1, D2 or D4. TR3 becomes saturated and 12V is applied to the astable TR4/TR5. Protection diodes D6 and D7 prevent the breakdown of the base/emitter junctions of these latter devices.

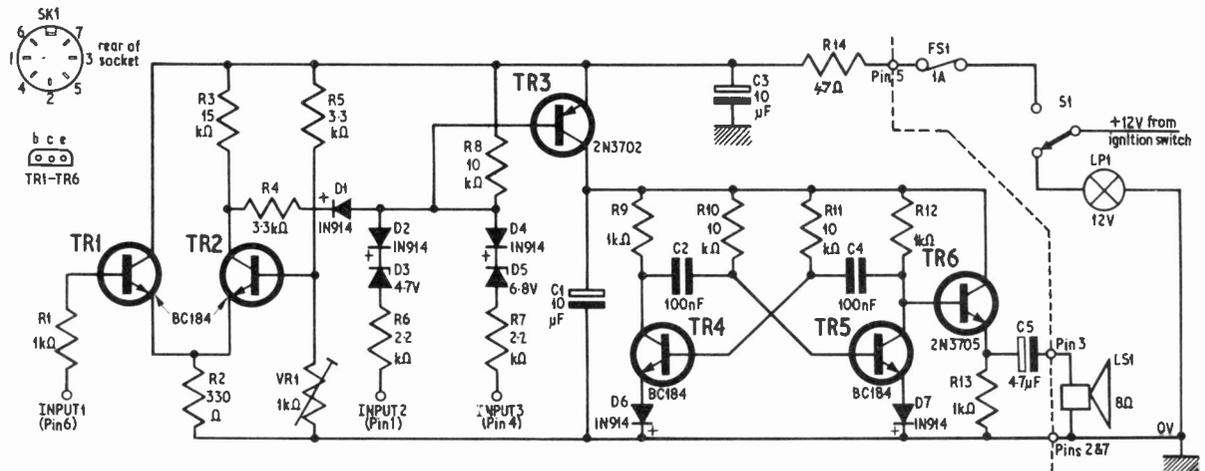


Fig. 1. Circuit diagram of Monitor

The astable is connected to a final transistor TR6 to drive a loudspeaker which may be any 2 to 3 inch 3 to 30 ohm device. The level of output is variable by choice of a suitable value for R13, 1k Ω being a suitable value to start with.

LAYOUT

Veroboard is used for the layout and cutting pattern and component locations are shown in Fig. 2.

No particular problems exist as far as the board is concerned except perhaps with the diodes with which care should be taken when bending the leads to avoid cracking the glass bead.

Whilst the circuit is shown for negative earth vehicles, the positive earth version can be catered for quite simply. It only requires that the *nnp* transistors be replaced with *pnp* and the *pnp* with *nnp*, that the diodes be reversed and the electrolytic capacitors similarly turned round.

Whilst BC184's are specified together with 2N3702's and 1N914's almost any small signal transistors and diodes can be used.

TESTING

Before wiring in to a vehicle it is best to check that all is functioning properly. Simply apply the 12 to 15V supply and temporarily connect input 1, the water temperature gauge input, to +12V. There should be no output.

If now any one of the inputs are connected to ground, an output should be obtained at the loudspeaker.

The volume of this buzz can be varied by selecting R13 to suit requirements.

CASE

Thus far we have only discussed a Veroboard assembly which, for use in a vehicle, should obviously

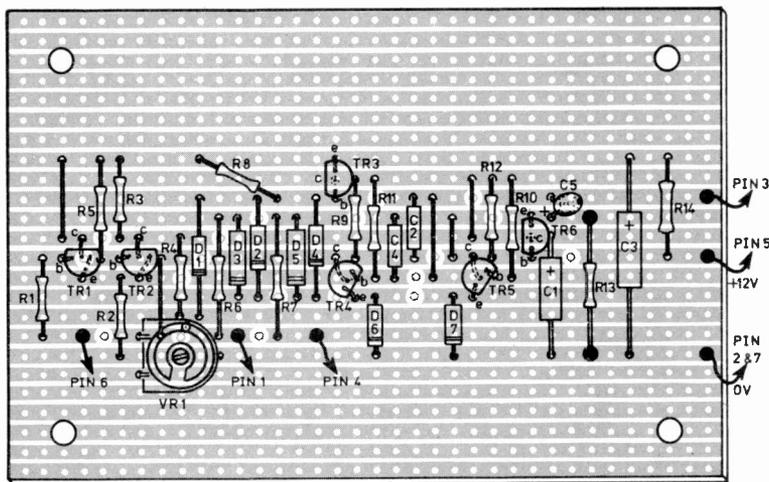


Fig. 2. Component layout on Veroboard, the copper track cuts being shown as white cut-outs

COMPONENTS . . .

Resistors

R1	1k Ω	R8	10k Ω
R2	330 Ω	R9	1k Ω
R3	15k Ω	R10	10k Ω
R4	3.3k Ω	R11	10k Ω
R5	3.3k Ω	R12	1k Ω
R6	2.2k Ω	R13	1k Ω (see text)
R7	2.2k Ω	R14	47 Ω

All $\frac{1}{4}$ W carbon film

Potentiometers

VR1 1k Ω preset

Capacitors

C1	10 μ F electrolytic 16V
C2	100nF ceramic
C3	10 μ F electrolytic 16V
C4	100nF ceramic
C5	4.7 μ F Tant. bead. 35V

Transistors

TR1, TR2, TR4, TR5	BC184 or BC182, BC183, BC107, BC108, BC109
TR3	2N3702 or 2N3703
TR6	2N3705 or 2N3704, BC182, BC183, BC184, "L" types


Note that when selecting alternatives care should be taken with the pin connections.

Diodes

D1, D2, D4, D6, D7	1N914 or 1S914, 1S44, 1N4148
D3	BZY88 4.7V Zener, 400mW
D5	BZY88 6.8V Zener, 400mW

Miscellaneous

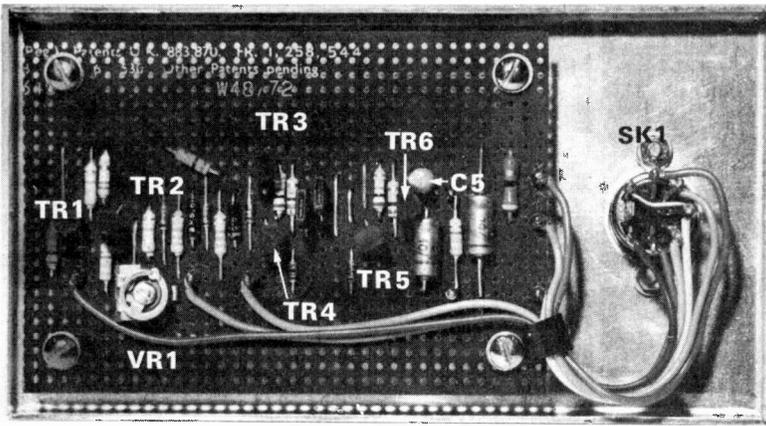SK1 6-pin DIN.
Veroboard, Veropins, aluminium box, connecting wire, fuseholders, switch and lamp if required, solder, etc.



Interior view of Systems Monitor showing completed unit

be cased in some form of protective box. In the prototype this took the form of a simple aluminium case and lid, with the Veroboard mounted on support pillars in the lid.

Wiring access to and from the circuit is provided via a 6-pin DIN socket SK1 mounted in the lid. As the whole assembly of lid and board is only a matter of an inch deep clearly the box can be quite shallow but it is best to use a box which can be screwed up and properly sealed against ingress of moisture from the engine compartment or wherever it is located on the vehicle.

INSTALLATION

It is probably wisest when installing any equipment in a vehicle to first of all disconnect the battery so as to avoid any damage from inadvertent shorts. Power supply to the unit is connected from the ignition switch, switched side and the inputs 1, 2 and 3 are connected respectively to the water temperature warning light or thermometer, the oil pressure warning light or block switch and the

generator output terminal or terminal "A" on the ignition light.

The battery may now be reconnected and no output should be obtained.

If the constructor has wired in the extra components S1, FS1 and LP1, then when the ignition is switched on LP1 should come on but there should still be no output. Switching S1 to the "on" position should extinguish LP1 and the unit is now "armed" for operation. In fact an output should be obtained because of course there is no oil pressure or generator output.

Starting the car should silence the output but if this fails it may be necessary to adjust VR1.

The vehicle should now be driven round for a while till engine temperature reaches its normal level and VR1 is again adjusted till the output buzz is just extinguished. This is all the setting up required with the possible exception of small adjustment to make up for the difference between summer and winter temperatures.



BOOK REVIEWS

I.E.E. REGULATIONS FOR THE ELECTRICAL EQUIPMENT FOR BUILDINGS
224 pages. Price £1.50

IN Great Britain, the Institute of Electrical Engineers has, since 1882, issued rules and regulations relating to electrical installations in general.

The regulations delineate the essential requirements for inspection, installation, testing and maintenance of consumers installations.

From time to time these are revised and amended, and this reprint incorporates all those amendments up to May 1974.

They are completely accepted by the Electricity Board, Local Authorities, Insurance Companies and consulting engineers as standard practice in the industry.

Issues are available from I.E.E., P.O. Box 8, Southgate House, Stevenage.

NEWS BRIEFS

OBITUARY

THE name Bulgin must be one of the best-known in the electronics field in Britain. Certainly every follower must have used plugs, sockets and so on bearing this name.

Thus it is with great sadness that we mourn the passing of Arthur F. Bulgin, O.B.E. the founder of the company bearing his name. He has served our industry for 51 years and, indeed, his country as well, and it is a mark of his astute judgement that the A. F. Bulgin company is the only one in the industry to show a steady rate of growth since the last war.

Chairmanship of the company continues in Mr Bulgin's son, Mr Ronald Bulgin, M.A., C.Eng., M.I.E.E., who also shares joint managing directorship with A.F.B.'s brother, Mr Stanley Bulgin.

.....tuning in to ESP

Our correspondent, Peter Verwig, recently attended the IEEE Intercon show in New York. Among the usual mass of technical and marketing papers read at the conference was a session on "New Advances in Parapsychology".

The chairman of the technical programme committee, Jack Raper, was one of the doubters on the advisability of including a parapsychology session in the International Convention and Exposition of the Institute of Electrical and Electronic Engineers in New York. In the end, the session went ahead and, if not exactly a sensation, it certainly caused a stir among the coolly-calculating, logically-minded scientists and engineers who formed the audience.

LECTURERS

The one aspect in favour of the session was that though the speakers may have had odd ideas, some of which might be classified as kinky, they did at least have the credibility of being engineers with normal levels of engineering objectivity and were clearly not the crankier type of mystic living on emotion rather than scientific fact.

Two of the speakers, E. Douglas Dean and John Mihalasky were from the Newark College of Engineering and the third, James B. Beal, hails from NASA, Huntsville, though he was careful to point out that he was speaking as a private person and NASA was in no way involved.

All three speakers were firmly convinced that such phenomena as extrasensory perception (ESP), precognition and telepathy were not only possible but also capable of detection and measurement in the scientific sense although much remains to be done.

TELEPATHY

The main practical work of E. Douglas Dean has been in telepathy. For his experiments he uses the plethysmograph, an instrument used in medicine for over a hundred years. It records a change in volume with correlation against blood circulation in the extremities of the body, for example the finger tip.

In the ordinary way a person has no control over any variations, but it has been shown that what we might loosely term "emotion" causes involuntary vaso-constriction leading to a lowering of blood volume in the measured part of the body. Dean's apparatus is considerably more sensitive than the old medical

plethysmograph and incorporates a pressure capacitance diaphragm pick-up and a continuous chart recorder which records the normal pulse of the heartbeat and any vaso-constriction as a pronounced dip below the average baseline.

The "subject" lies on a couch with a finger connected to the instrument and in an adjacent room the "agent" picks up a card on which is inscribed a name which may or may not have significance for the subject. Some cards are blank. The subject doesn't know what is on the cards, or the order in which they are shuffled.

The agent looks at each card for twenty seconds. Blank cards showed no response and cards with names only showed subject response on the recording pen when they had some emotional significance, for example a close relative, and the pen deflection was most pronounced when there had been recent anxiety or other strong emotion in connection with the name.

In one test the subject's two-day old new-born baby's name was on the card and the resulting vaso-constriction was so severe it took over a minute for the recorder to return to baseline.

The experiments were repeated with the agent enclosed in a fully electrically screened room and this had no effect, indicating that whatever the communication medium between agent and subject it was not affected by screening. Long distance tests have been completed north to south from New York to Florida, a distance of 1,200 miles, and east-to-west from Newark, New Jersey, to Bordeaux, France. Amazingly, the effect was also recorded with the agent 35ft under water in Florida and the subject 4,000 miles away in Zurich, Switzerland.

The underwater test opens up the possibility of communicating with submarines submerged at great depth, of greatest potential value in the event of disabling disaster. The technique would involve the use of pre-arranged time slots and the Morse code with stimulus, for example, representing a dot and non-stimulus being a dash. The data rate would be very slow but over a period of hours it is thought that comprehensible communication could be possible.

An important finding by Déan is that using electronic equipment to establish emotional response shows scientifically that one person in every four has some level of ESP ability.

FIELD EFFECTS

James B. Beal maintains that electric fields have important effects on the body. He has gone as far as to fit a 500V positive field generator in his car to alleviate fatigue. He has also reared beans in a 2,000V positive electrostatic field and recorded a four-day earlier germination compared with a control group outside the field.

The same apparatus was used on a badly asthmatic child with beneficial results. Tests on typists showed an enormously lowered error-rate if they sat in a strong field.

Beal recalls that the ancient Chinese knew, perhaps instinctively, that beneficial health, mental and spiritual qualities could be obtained by proper geophysical orientation of homes and religious shrines in relation to the earth's magnetic poles, subterranean streams, geology and topology. It is even suggested that many mental patients are not ill but merely hypersensitive to field effects and, of course, it is well established that natural phenomena such as hot winds containing an excess of positive ions, especially in the Middle East, induce both physical and mental maladies in the population.

It was also suggested by Beal that ESP can be developed in suitable subjects by teaching machines. One such is commercially available.

SEEING THE FUTURE

Working on precognition (seeing into the future), especially in the realm of creative ideas in engineering and business has been studied for many years by Dr. John Mihalasky.

The successful engineer or businessman is often said to have intuition or insight in addition to ordinary levels of logical thought. The brilliant solution to a problem is often conceived "in a flash" from the unconscious mind spontaneously and frequently at very odd times and in peculiar circumstances.

SOLAR POWER AND ITS APPLICATIONS FOR TODAY

BY P. S. WOODCOCK*

THE oldest known power source is the sun and there have been many ways devised to use its energy. Until very recently none have withstood the march of technological progress. Modern technology is now able to provide ways of making use of a very small fraction of that power that is always available.

The utilisation of solar energy has also been limited by economic reasons; the techniques for many applications have been known and fully proven but the cost of using them has made it totally uneconomic.

PHOTOCELLS AND SATELLITES

The basic component for the conversion of solar power into electrical power is the photocell and this was introduced, as a production device, in 1957.

This cell, in the form of a silicon photovoltaic semiconductor diode, has been the prime power source on earth orbiting satellites since the first was launched in 1957. It is therefore not surprising that industry is now using this well established, fully proven space technology as a source of pollutionless terrestrial power.

GROWING SILICON CRYSTALS

The photovoltaic cell is produced from silicon, the second most abundant element on earth.

A seed of pure single crystal silicon is dipped into a bath of molten silicon and rotated and slowly withdrawn, in an inert atmosphere, producing a bar of almost pure single crystal silicon.

The silicon is required to be doped with small quantities of impurities to control its conductivity. These impurities are introduced into the bath of molten silicon so that the withdrawn bar contains the correct level of dopants.

Early technology imposed a limit on the diameter of bar that could be pulled of about one inch, but recent developments have seen this increased very significantly, and it is now usual for 2½in diameter bars to be used.

The bar of silicon is then cut so that circular slices of defined thickness are produced. The majority of cells produced for satellite applications have used silicon slices 300 micron (one micron = 10^{-6} metre) thick but a new generation requires cells of 200 micron thick. The thickness of silicon used does not affect production processing.

Almost all silicon produced for cell applications is boron doped so that it will conduct by means of positive charges or holes, and for this reason is called *p*-type.

PHOTOCELL PRODUCTION

The production of a photocell involves several basic steps and these may be listed as follows:

1. Diffusion of *pn* junction
2. Contact formation
3. Coating

The creation of the *pn* junction is achieved by the controlled diffusion of an impurity into the *p*-type silicon slice. The impurity used is phosphorus which is introduced into the diffusion furnace as a vapour, the depth of the diffusion being a function of time and temperature.

The basis of operation of the photocell is such that when photons (light particles) strike the cell surface, close to the *pn* junction, positive charges (holes) and negative charges (electrons) are produced. The electrons will tend to travel towards the *n*-type silicon and the holes towards the *p*-type silicon. If connections are made to the *n*- and *p*-regions electric current can flow into an external load.

METALLISED CONTACTS

The next vital production stage is thus the deposition of a metallised contact structure. The *p*-contact, on the rear face of the cell, can cover the total cell area, but the design of the *n*-contact, on the front or active surface, is critical to the performance of the cell.

*Electronic Components Division, Ferranti Ltd.

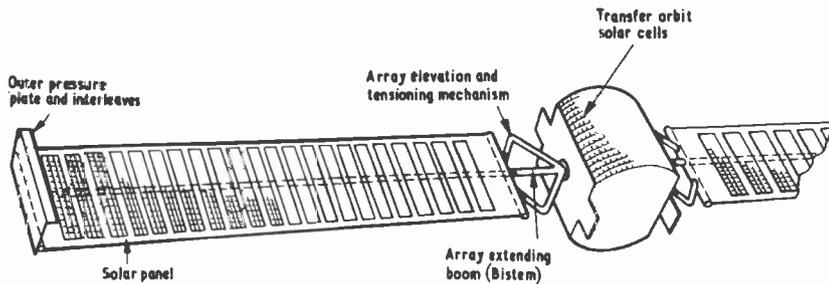


Fig. 2. Drawing of a flexible fold-up solar array. Each paddle is about one metre wide by five metres long

The requirements are many and varied and, in some cases, conflicting. For maximum cell output the contact must mask minimum cell area but must have sufficient cross-sectional area to handle the photon generated current.

Thick metallisation must be avoided as severe stresses can be set up on thermal cycling and, in the extreme, this stress could be sufficient to break the silicon. The metallisation must have good electrical and thermal conductivity, must be easily contactable, and should not degrade or cause degradation in any encountered environment.

The process by which the metallisation pattern is defined must also be of sufficient accuracy that overall pattern tolerances are maintained. Pattern definition is achieved by a photographic mask and the metallisation used on the satellite cell is a composite structure of nickel, copper and gold.

The nickel gives the ohmic contact to the cell, the copper gives the electrical conductivity and the gold prevents contact tarnishing.

The pattern defined on the satellite cell is a narrow top contact bar and then 24 narrow fingers running down the length of the cell. These fingers are typically 25 microns wide and five microns thick. The multiplicity of these fingers optimises the collection efficiency of the photon generated electric current.

OPTIMISING CELL PERFORMANCE

On bare silicon, light striking the active cell surface will be partially absorbed but a certain percentage will be lost due to reflection. This percentage can be significantly reduced if a quarter wavelength thick transparent dielectric layer is deposited on the cell surface.

The refractive index of this layer is chosen to optimise cell performance. Early cells used either silicon monoxide or dioxide but the latest technology uses titanium oxide.

The almost universally used cell size for satellite applications has been 2 cm sq and the output power from a cell of this type is typically 62mW at 25°C when illuminated with air mass zero sunlight at 140mW/cm². This gives an overall power conversion efficiency of 11 per cent.

Fig. 1 shows the output characteristics of a typical solar cell.

The power requirements for a satellite have always demanded a cell of maximum power, from minimum area, at minimum weight and this has dictated that the cell produced to satisfy this requirement is of the highest possible performance.

SATELLITE SOLAR ARRAYS

Satellite solar array design has followed two distinct channels, both of which offer advantages and disadvantages in the satisfying of an overall system requirement.

In one case the cells are mounted on a cylindrical body which spins with its axis perpendicular to the sun. In the other case the cells are mounted on deployed paddles which are sun orientated.

To give some idea of sizes involved, the recently launched communications satellites designated *Intelsat 4*, each carry 50,000 cells mounted on a cylindrical body, nine feet in diameter and ten feet high.

This initially will provide almost 900W of power and will provide power for 5,000 simultaneous telephone channels or ten colour television transmissions. To provide 1kW of power from a deployable array would require approximately 17,000 cells and, using two paddles, each paddle being typically one metre wide and five metres long (see Fig. 2).

THE ADVANTAGES OF SILICON

The justification for the choice of silicon is simple. As previously stated it is the second most abundant element and it has been the foundation of the semiconductor industry. As such it has seen an investment in its technology many orders greater than all other basic semiconductor materials.

The basis of using the experience gained from developing and producing solar cells for satellite

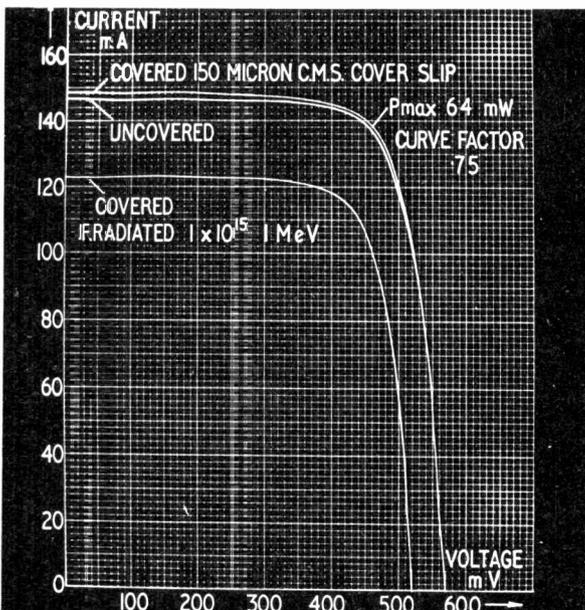


Fig. 1. Power output characteristics of a typical solar cell

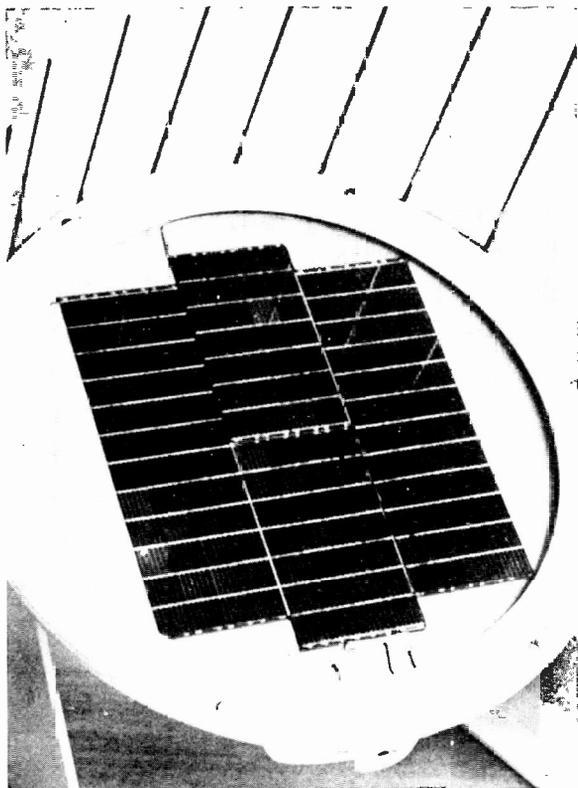


Fig. 3. A terrestrial solar panel as used for marine applications

applications is that the silicon voltaic cell has been the prime power service in over 700 American and some 500 Russian spacecraft of varying type.

From this background the selection of a silicon photovoltaic cell as a design start point for terrestrial power applications was inevitable and inarguable.

POSSIBLE ALTERNATIVES TO SILICON

It should not be thought that silicon is the only material suitable, and some effort has been devoted to other semiconductors.

The most notable of these have been gallium arsenide and cadmium sulphide. The former is able to withstand high temperatures and thus is able to generate at intensities 1,000 times greater than sunlight. The problems of heat dissipation must still be solved, however, before it can be considered to be technically competitive, but on cost it must be extremely doubtful if it can ever be considered to be an economic alternative.

Cadmium sulphide offers a cheap means of producing a photocell of considerable area in a flexible sheet form. It does, however, suffer the disadvantage of much lower conversion efficiency, and hence will only ever be able to be suitable for that market segment that can accept no restrictions on area.

TERRESTRIAL SOLAR POWER

The initial choice of cell for terrestrial use was dictated by availability, and 2×2 cm reject satellite cells were used. These were cells that failed to fully satisfy the most stringent electrical and physical requirements of a space satellite specification but

which would work quite happily when mounted on a terrestrial panel.

The panel was designed to provide 400mA at 15V in the equivalent of bright sunlight, and required for this output 156 cells interconnected as 39 cells in series with four cell strings in parallel.

MARINE ELECTRONICS

The design and construction of this panel, ideal for off-shore repeater or navigation aids, is not really suitable for the larger volume commercial business. A fast expanding market is that of marine power generation. The use of instrumentation and electronics on yachts and power boats is ever increasing with very little regard for the state of the onboard battery.

A small solar panel permanently mounted on the boat is extremely attractive from an economical and environmental standpoint. The use of solar panels in marine applications will, however, be limited by price considerations and only when a panel can be produced at a low enough price will full market penetration be achieved.

LARGER SLICES

The techniques for the production of refined single crystal silicon have not stayed stationary and manufacturers now have readily available large area slices. This realises a slice diameter of typically 6cm and allows the use of cells of this size and proportional power rating.

Based upon expected conversion efficiencies the output from a circular cell of diameter 6cm should be 500mA at 470mV when measured under $100\text{mW}/\text{cm}^2$ simulated sunlight at 25°C .

The front active cell surface will have a simple metallised contact pattern and the back face will be fully metallised. The interconnection of cells must be performed simply, easily and reliably, to permit the building of the basic power modules.

Based upon the major market requirement for recharging nominal 12V batteries the voltage capability of the module is defined as greater than 13.8V. Thus a basic power module can be defined as 30 cells interconnected in series.

The expected output from the package under simulated bright sunlight conditions will be 500mA at 12V. The calculation for overall charging rate must be subject to some hypothesis as to expected weekly hours of sunlight and at what illumination intensity.

AVERAGE SUNLIGHT

The average daily hours of daylight during summer can be considered to be 15 hours. The Meteorological Office estimate for hours of sunshine on the South coast of England is a daily average of 7 hours. Assuming this to be at 75 per cent intensity, this is equivalent to 5.25 hours at full sun.

Thus the daily output charge from the panel will be 2.6amp-hours. Based upon a five-day week for charging and the boat being in use the other two days this gives an average weekly charging capability of 13amp-hours, neglecting any charging that can still take place during the time the boat is in use.

The expected current drain, based upon estimated usage of electronics and ancillary electrical equipment, is of this same order, 10 to 15amp-hours, so the projected panel size would seem suitable for this market.

OTHER APPLICATIONS

Usage of this type of panel is by no means limited to marine applications. A similar application, and one that is being studied closely, is for use with caravan trailers.

The power output requirements for a solar panel in this application are almost the same as on board a boat and hence the market can, hopefully, be catered for with an identically produced product.

Remote or unmanned automatic operation of road signs is receiving great attention, especially in the use of danger signs for such hazards as road works. The often seen flashing amber lights denoting road repairs could be easily solar powered.

Built-in rechargeable batteries could be charged during daylight hours for operation at night. The use of this type of power source could easily be extended to cover motorway hazard lights, emergency telephone systems and many monitoring devices.

Solar power gives to these applications the advantage of freedom from main power links and must improve their suitability for utilisation in many more wide ranging areas.

FORESTRY AND METEOROLOGY



These applications are ones that are commonly encountered by a wide cross section of the public but extensive markets exist in less well known areas. Forestry requires extensive use of remote automatic equipment for such applications as fire warning and portable or remote communications. The use of this type of power source is also available for weather monitoring, rain gauges, flood warning, seismic detection. The list can be almost endless.

Two application areas that will demand a high reliability factor are those of remote area repeater links for communications and off-shore navigation aids.

REPEATER STATIONS

Microwave relay stations and telephone repeater stations are often situated in some of the remotest parts of the world and are required to remain in unattended trouble-free operation for periods of a year or longer. It can cost a great deal of money to transport people and spares to these sites for servicing and repair and it is therefore essential that frequency of visits is as low as possible.

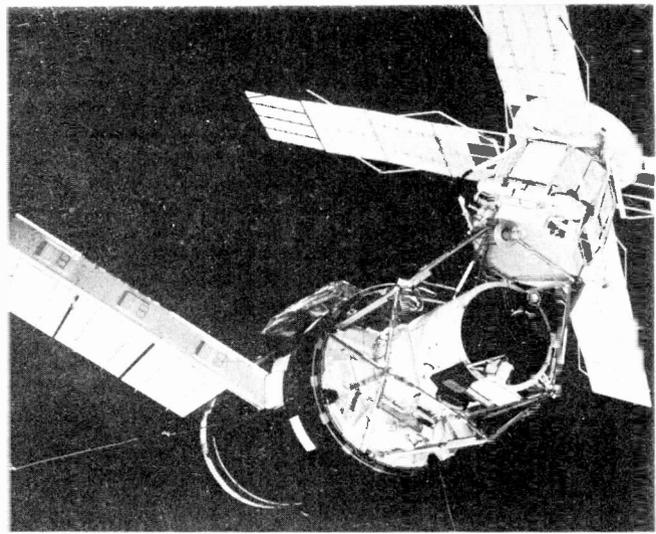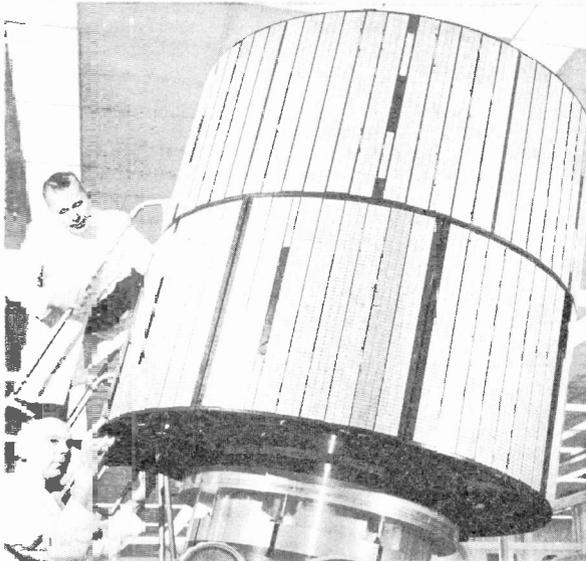Photograph of a satellite built by the Hughes Aircraft Company for NASA and launched in 1966



Photograph taken from Skylab 3 showing the deployed solar arrays

POWER PRODUCTION

The present major energy crisis has spurred even greater discussion and thought towards ways of producing, economically, consumer electrical power, such that it can be considered a realistic alternative to power produced from fossil fuels.

Two ideas, once considered close to science fiction, are being discussed. One involves a large solar farm in a flat desert region and the other a large solar array in synchronous orbit above the earth beaming r.f. power to a terrestrial station.

Power would be taken away on a National Grid type system. The problems of maintaining the solar blankets can be imagined and no acceptable solution has been found.

ORBITING SOLAR ARRAYS

The orbital power station having two large arrays, totalling 7.3×2.7 miles, is the current design thought and these would flank a microwave transmitting antenna that would be 0.63 miles in diameter.

It is intended to try and fly a prototype satellite in 1990 and a commercial version could be flying at the end of the century.


THE SOLAR POWER AGE

The world markets for small commercial systems currently demand a high technology product in large volume at low cost but this is only the smallest tip of some vast technological iceberg. A technological miracle is in the making and it is one that could revolutionise our outlooks.

The photovoltaic cell and the solar array will become everyday commodities known to all. They offer a method of saving our precious and dwindling stocks of fossil fuels for processes that require these and they will provide an economic pollution free energy solution based upon a natural power source that will never be diminished.

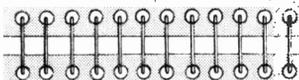We have seen the Stone Age, the Iron Age, the Industrial Revolution, the Space Age. The possibility of a Solar Power Age must not be dismissed or taken lightly.





INDUSTRY NOTEBOOK

By Nexus



WHAT'S IN A NAME?

We are all certain to be subjected during the next few months to growlings, grumbings, even open hostility directed towards the so-called multinational companies. In fact the very word multinational has now joined other political jargon words like racist, fascist, red, speculator, capitalist, terrorist in a fully emotive sense.

Multinational, in short, has become a word of abuse. Nothing to do with injection of capital and creating employment and wealth in underdeveloped or otherwise needy areas, and everything to do with faceless (indeed, probably heartless as well) exploiters counting their gold in plush offices thousands of miles away. No wonder some of the great multinational companies are keeping a low profile and, for one or two of them, with very good reasons.

Most of the outcry is directed against US-based multinationals but it has to be remembered that nearly all the great British companies operate multinationally, as do those of France, Germany and Italy.

I rather liked the argument put forward recently by the German Siemens group to an American audience in defence of their penetration of the US market by acquisition of US companies as well as direct sales from Germany. Siemens, said their spokesman Bernard Mayer, is a World Company and this has been true ever since the company was founded by Werner von Siemens, 126 years ago. He quoted the installation by Siemens of the 7,000 mile London to Calcutta telegraph completed in 1870 as an example of operating on a world scale. And he pointed

out that Siemens' advanced technology products, which demand two million dollars R and D expenditure alone every working day, could not be supported by domestic sales alone.

In the United States, Siemens has now grown from a handful of market research men 20 years ago to a sales and production force of 2,000. Steady, rather than dynamic growth, and still only a drop in the vast ocean of the US electronics and telecommunications industry.

My own rough guide lines for goodness factor in multinationals operating in Britain are that they should be British-managed, have good export potential, have some element of in-house R and D (i.e. not be just an overseas production unit), and make a genuine contribution to the economic and social life of the country. Fortunately, there are more companies like this than of any other sort.

I suppose Mullard (Dutch-owned) is the most notable example and of the more recently established companies, Hewlett-Packard (US-owned) has an impeccable record. But there are many others and it will do us all good when confronted with mindless political slogans to pause and think.

CUTTING THE COST

Electronics, because of its steady advance in solid-state technology, is uniquely running against the tide of rising world prices. You get more value per unit cost every year. The electronic watch which last year cost £100 will cost you £30 by 1978 according to industry forecasts.

It's all to do with volume. Last year solid-state watch sales were 250,000 in a world market of 185 million watches, only 0.14 per cent. But by 1978, say the pundits, in a projected market of 227 million watches, the solid state watch will have 51 million sales or 22.46 per cent of the total market. By that time the cost of the C/MOS LSI chip will have dropped from 10 US dollars to 2.50 dollars, the digital display from 9 US dollars to 2 dollars, the quartz crystal from 3 US dollars to 2 dollars and even labour (presumably through automation) from 5 US dollars to 2 dollars.

Take a single-chip electronic calculator. In 1970 the semiconductor manufacturers made an "introductory offer" at 30 US dollars per chip. Last year, the price of the chip had plummeted to 5 dollars. This year the price is 4.50 dollars and the l.e.d. display is now 50 cents a digit instead of a dollar. The complete handheld calculator, albeit of the simplest type, is expected to fall

in cost to 20 US dollars by 1975, well under £10 at UK prices, the limiting factor being promotional costs because intense competition encourages heavy expenditure on advertising.

The cost of a single planar transistor in 1959 was 50 US dollars. By 1976, when it should be possible to buy the cheapest calculator chip of some 3,000 transistors for 3 US dollars, the cost per transistor will work out at 0.001 of a US dollar. That's not the end of the story because if all these transistors were discrete and had to be hand-wired with external wiring at a cost, say, of 10 US cents a wire installed, then the total cost would be astronomical.

The big question now is whether the semiconductor wizards can achieve the same order of cost reductions in solar cells for commercial and domestic use to alleviate the energy crisis? One line of research is to fabricate the cells in continuous ribbons instead of individually, but even the optimists concede that it may be another ten years before a hundredfold reduction in cost is achieved. This is the order of cost reduction needed to make economic the direct conversion from solar to electrical energy.


INSPIRATION

We could all kick ourselves at times for not spotting the obvious. The trembler bell in a telephone has been around ever since the telephone was patented by Alexander Graham Bell in 1876. If ever a mechanism needed up-dating it's that "oldy" in the base of your phone.

Mitel Canada Ltd. have come across with the answer, and it's an answer with enormous market potential. A replacement panel incorporating a 2-inch loudspeaker, amplifier and control circuits.

The all-electronic bell gives a pleasant ringing tone, as good or better than any electro-mechanical bell, and it has the advantage that it can also be used for ordinary loud-speaking messages. On a PABX system in a hotel, for example, the operator can make an emergency announcement to all rooms simultaneously or individual announcements to selected guests without the receiver being off its rest. If you are using the phone at the time, then the announcement automatically breaks into your conversation.

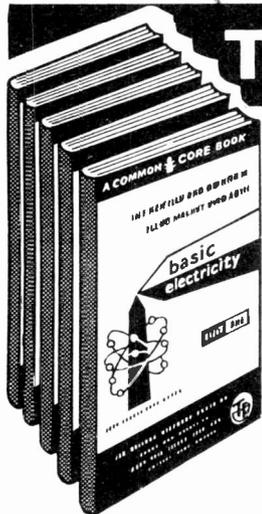It is claimed that the Mitel "Mitone" signalling system can be manufactured to sell at the same cost as the old-fashioned single-purpose bell. Another advantage is that drive voltage is much lower and more in line with the requirements of modern electronic switchboards.



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

I would like to say how easy your books are to study.
B.B., London

I purchased Basic Electricity and I have found them to be the best books of their kind that I have ever read. Will you please send Basic Electronics.
G.S., Portsmouth

"EVERYTHING IS MADE SIMPLE" which makes reading a pleasure.
V.S., Farley

"BOOKS ARE WONDERFUL" thank you.
A.C.S., Colwyn Bay

I earnestly believe these manuals make the subject become a "Cake Walk".
S.S., Lewisham

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP


Please find enclosed P.O./Cheque value £.....
 BASIC ELECTRICITY 5 parts £5.30
 BASIC ELECTRONICS 6 parts £6.40
 BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
 BLOCK LETTERS
 FULL POSTAL.....
 ADDRESS

POST NOW FOR THIS OFFER!

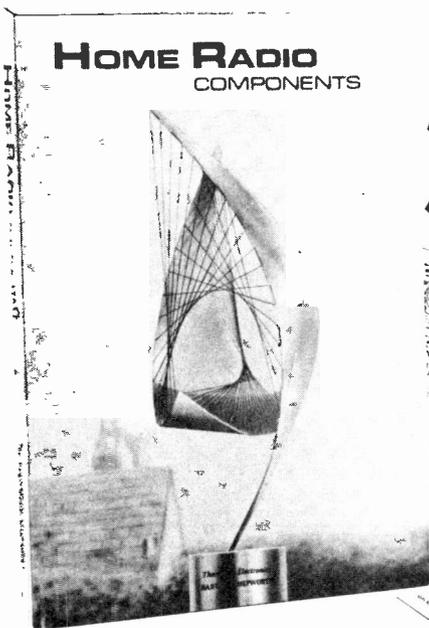

- 250 pages 11 1/4" x 8 1/4"
- 6,785 electronic components clearly listed and indexed
- 1,750 pictures
- 10 free Vouchers each worth 5p.
- Price list regularly updated
- Book mark with useful list of technical abbreviations

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p.
plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

Name _____

Address _____

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

The price of 77p. applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System - with a big plus over all the other kits - the Electro Spares Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES

The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888

TRAMPUS

MONEY BACK IF NOT SATISFIED

all brand new, full spec. Top grade.

Free fabulous NEW catalogue. Send S.A.E.

red+ data source **LEO's 17p!** TIL209 & clip 22p
BIG 1/4 panel clip & RED LED 28p. GREEN & clip 59p
INFRA RED LED EL. IC photo amp 44p. & amp/switch 85p

Digital Display LEO 1/3 0-9DP.DIL. £1-69

Minitron type 0-9pDIL. £1-19. SOCKETS 13p.

IC DIGITAL CLOCK CHIPS.

Texas etc with 4 displays £12. 6 displays & chip £14. pcb £1-89

Mostek date & alarm chips with 6 displays £19.

hit: All parts & case. National chip. 4 digit £20. 6x £23.

with data **integrated circuits**

741-8pin 29p, to99 & 14pin 27p. 748 33p 709 21p

710 35p 723 59p. 555 timer 79p. ZN414 rx. £1-10

703 rf if 28p mc1310 & led £2-76 mc1339 £1-20 TAD100 & il £2

IAMP+ REGULATOR 7805,5 (&7-20)V. also 12 & 15V £1-49

AUDIO AMPS: mfc40 o o 50p; 1 & 2W £1-19; 3W £1-29; 6W...

gates 7400 etc 16P 7413 32P 7447 £1-25

7470/72 32P 7474/76 39P 7490 63P

7492 69P 74121 49P & all others in cat. low prices.

NEW 16pin counter/driver 90/47 £2-25 DALO pcb. PEN 69p.

DIL SOCKETS: Professional / gold P.Pins hi or lo Profile 8,14,16 Pin 13p

2N3055 33p. four £1. BC107, BC108, BC109 all 7p ea

IN914 3p ZENERS BZY88 8p. 1A RECTS 50v 3 1/2 400v 5p. BRIDGE 20p

FETS: 2N3819 19p 2N3823E 20p 4410E 25p BC182/3/4 10p

BC212/3/4 11p BCY70 13p BD131/2 35p ea. BFY5 V23 15p TIS43 25p

2N2926 0y. 7p 2N3053 15p 2N3702/3/4/5/6/7/8/9/10/11 all 9p ea

2N3904/6 14p HEATSINKS 5F/TO5 18F/TO18 5p. TO3: 4YL 29p TVJ 14p

CAPACITORS 25V10, 50, 100uf 5p. DISCS 4p. PRESETS 5p. CARBON -

POTS [IP, Switch] I.P. Dual 5 1/2 P. ULTRASONIC TRANSDUCERS £2 ea

TRAMPUS ADD 10% VAT TO PRICES. P&P 10P CWO.

electronics P.O. BOX 29, BRACKNELL, BERKS.

PSYCHEDELIC LIGHTING UNIT IN KIT FORM

Make this fascinating three-channel unit from a kit which contains all components needed to produce an ever changing light display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will drive a total of 2kW of coloured lamps at 240 volts. Supplied complete with PVC covered steel cabinet with holes ready punched for controls and cable outlets. Master control included. Coloured lamps not supplied. Price per kit £12-80.

METAL CABINETS

These attractive steel cabinets are PVC covered in a range of colours, and offer an economically priced unit for the home constructor. The chassis, which has a white satin PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with stick-on feet. Colours available include Green, Grey, Black, White and Blue. Every effort will be made to supply a selected colour, but please give alternatives if possible.



Approx. size in ins.			Price
l.	w.	d.	
4	5	2 1/2	75p
8	6	3	£1-60
11	6 1/2	3	£2-04

Other sizes to special order. HOLES PUNCHED in front or back panels to your own requirements. Please send S.A.E. for quotation.

FIXED VOLTAGE REGULATORS

TO3 case. Gives stabilised supply. MVR 5 V, MVR 12 V, MVR 15 V. All priced at £1-98

VEROBOARD

0-1	0-15
2 1/2 x 1in	10p 10p
2 1/2 x 3 1/2 in	27p 20p
2 1/2 x 5in	29p 29p
3 1/2 x 3 1/2 in	29p 29p
3 1/2 x 5in	31p 32p

D.I.L. REED RELAY

Operates direct from 5 volt TTL logic elements. Normally open contact rated at 0.25A, 100V d.c. Price each £1-50

Our CATALOGUE, priced at 25p post free in U.K., shows most of the R.S. range of professional components. Prices include VAT. All orders over £1 POST FREE—U.K. only. Overseas postage at cost. S.A.E. with all queries please.

CELETRON-E

P.O. Box No. 1, Llantwit Major, Glamorgan, Wales CF6 9YN

NEWS BRIEFS

MARCONI CENTENARY EXHIBITION

TO MARK the centenary of Guglielmo Marconi's birth, the Science Museum in Exhibition Road, London, is holding a special exhibition which will run throughout the summer to about October.

The exhibition consists of a large selection of documents, and a display of early apparatus together with many of Marconi's personalia and commemorative material.

Experiments with radio waves were carried out in 1888 by Hertz and were extended by various physicists in following years. It was not until 1894 when Hertz died, that the young Marconi, 20 years of age, appeared on the scene.

After reading a commemorative article on Hertz he began experimenting in the attic of his parents' large villa near Bologna, Italy. By the summer of 1895 he had transmitted a signal over a few yards using a simple spark gap transmitter, and coherer type detector.

By August 1895 Marconi had achieved transmission over 1½ miles. The Italian government remained unimpressed and so Marconi set sail for England.

Following preliminary demonstrations in his laboratory the chief engineer of the Post Office, William Preece, to whom Marconi had been introduced by his cousin, arranged formal demonstrations to Post Office officials.

Observers were suitably impressed and in a second demonstration six months later the range was extended to seven kilometres. An historic lecture at Toynbee Hall followed this and Marconi soon became a celebrity.

The scientific community was, however, less enthusiastic suspecting Marconi of plagiarism. In particular, Professor Oliver Lodge, who first developed the coherer and had in fact transmitted Morse signals over 60 metres before Marconi began his experiments, was deeply offended.

In 1897 Marconi established "The Wireless Telegraph and Signal Company Limited" much to the disgust of the Post Office who did not favour experiments being carried out without their involvement.

In 1899 cross-channel transmissions were successfully achieved and the possibility of transatlantic radio was soon realised.

On the 12th December, 1901 the first transatlantic message, a single Morse letter S, was transmitted from England to Newfoundland giving Marconi success against all the odds.

Photograph of Marconi in London in 1896, showing the original apparatus brought by him from Italy. (Marconi Company Ltd.)



PRACTICAL ELECTRONICS

NEXT MONTH...

PROJECT

HIGH IMPEDANCE VOLTMETER

Simple circuitry opens up a world of sophisticated measurement. Examine biophysical and physiological potentials, look at the outputs of high impedance transducers. All with two operational amplifiers.



PROJECT

UNDERWATER PHOTOGRAPHY

This Sub-Aqua Colour Temperature Indicator has been specially designed for the underwater photographer. It is compact, uses very little power, and has no external controls so that it is easily waterproofed. The indicator is perfectly suitable for colour work on dry land.

SPECIAL FEATURE

ELECTRONICS IN SEISMIC EXPLORATION


Seismic exploration is a quest for the world's subterranean sources of natural wealth. Oil and gas, as we know, are two of our most eagerly sought after resources. What are the techniques used to achieve these discoveries? To answer this you must read next month's feature article.

AUGUST ISSUE ON SALE JULY 12, 1974

PRACTICAL ELECTRONICS

Remember, back numbers are not available so why not place a regular order with your Newsagent. Or, why not take out a yearly Subscription (Inland £3.25, Overseas £3.50). Orders should be addressed: Subscription Dept., IPC Magazines Ltd., 66-68 Great Queen Street, London, W.C.2.

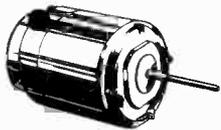"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can

be applied to give DC to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120r. 50Hz Speed 60 rpm at 60Hz. 72 rpm. STEPPING Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/4". Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. OUR PRICE ONLY £15

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant. Ideal for P.C.B. Size 12" x 12" 24" x 12" 24" x 24" FULL SHEET 43" x 37" (11 sq ft.). Single-sided Copper with thickness of 3/64" 3/32" Also double-sided 1/2" 3/32" £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω. output 60 or 80 DB at 1 Kc. As used in deaf aios, bugging device, etc. Size (60 DB) 1/4" x 1/4" x 1/4" (80 DB) 1/4" x 1/4" x 1/4". Ex-equipment, all tested. £1.20 each. P. & P. FREE

Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 V a.c. Very powerful and silent running. 5 1/2" dia. 3" inlet/dia. Outlet flange 3" x 2 1/2". Limited number only £8.95. P. & P. 40p


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow" Bracket Incorporates 2 fixing screws. Length of arm. 2 1/2". 240V AC Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities



SOLENOIDS by WESTOOL

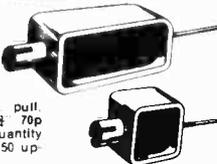240AC type MM6 3/8" pull, 2 1/2" x 1" x 1" Travel 1" 90p each P. & P. 10p 240AC type MM4 2 1/2" pull, 1 1/2" x 1 1/2" x 1" Travel 1/2" 70p each P. & P. 10p. Quantity discounts 10-50 10%, 50 up wards 25%



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm. NEW HIGH TORQUE, approx overall size 3 1/2" x 3 1/2" 2 1/2" spindle 1/2" dia. as illustrated £2.70. P. & P. 30p Similar to above, 19rpm. £2.70. P. & P. 30p 110rpm with pressed steel gear case (similar to above but SLIGHTLY SMALLER). £2.70. P. & P. 30p




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1amp at 240v. Size (approx.) 1 1/2" long x 1 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10. P. & P. 15p. 50 for £8; 100 for £15.50. FREE P. & P. over 10.

AMPEX 7.5V. D.C. MOTOR

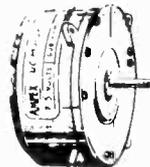

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 80ma on run. 800rpm = speed adjustment. Internal AF/RF suppression 1/2" dia. x 1 1/2" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Quantities available. Mu-metal enclosure available 75p each. FREE P. & P.

ALL PRICES INCLUDE V.A.T. Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580

PE RONDO QUADRAPHONIC SYSTEM

NEW ITEMS INCLUDE FM TUNER!

RAPID ORDER

← PLEASE TEAR OUT

Garrard SP25/4, Elac STS 144/17, wired in plinth with cover
Set of 4 Patchboards, Fanning Strip, Plug, Socket, 24W Edge connector
Set of 4 new style edge connectors
Set of 4 Pillars, 2 End Caps, Bridge and Side Trim
FM Tuner kit, very high performance
AM/FM Tuning Scale assembly, c/w meter and calibrated Electroluminescent dial
Tuner Section Fascia with window and printed trim
Quadrasonic System Selector Switch
Knob Pack (7 slider knobs plus Tuner knob)
CBS-SQ* Matrix Decoder kit (CBS-SQ T.M. CBS INC)
Matrix decoder as a built and tested module
Full pre-amplifier with selector switch
Power supply board kit
Main smoothing capacitors and clips (per pair)
Mains Transformer—wound to specification
Punched chassis with both screens
Control Section Fascia with printed trim
Phase Locked Loop Stereo Decoder kit using 1310P plus LED
Pre-built and tested Stereo Decoder Module includes LED
Deutsche Elac STS 144/17 Magnetic Cartridge list £17.90 only
Rondo Loudspeakers, pair, built, Teak or sheer white
Rondo Loudspeaker kits, Teak or sheer white pair
SPECIAL 4 Speaker kits, (complete)
Bass Drive units, 2 per cabinets (each unit)
Tweeters, 2 per cabinet (each unit)
New style crossover kits (built 50p each extra)
Quadrasonic Headphones—to hear is to believe
SUPERB ADVANCE CALCULATORS—MADE IN BRITAIN!
Incredible 40 Step programmable, type 162P
Pocket 2 memory, %, square root type 88
Pocket four function % ultra dependable type 80
OTHER MODELS AVAILABLE—S.A.E. FOR LISTS PLEASE.
COMPLETE PE RONDO AVAILABLE AS PUBLISHED.
TRADE ENQUIRIES WELCOMED ON ALL ITEMS, ADVERT CORRECT AS AT 1.5.74. OVERSEAS ORDERS, ADD POST, SEND TO STUDIO ELECTRONICS INTERNATIONAL. U.K. ORDERS: ALL PRICES POST FREE, ADD 10% VAT TO TOTAL.


£19.50	SP25/4, P. & C., 144/17
£3.54	PATCHBOARDS
£1.44	Edge Conn. Set
£3.30	Pillar Set
£17.50	FM Tuner
£10.42	Tuner Scale
£3.85	TSFW
£1.43	QSSW
£1.25	KNOB
£8.00	SQ. DEC. K
£11.00	SQ. DEC. B. & T.
£3.30	PRE-AMP
£5.50	PSV
£1.65	CAPS
£6.87	TRANS
£3.57	CHASSIS
£3.85	CSF
£5.95	SESD-K
£6.95	SESD-B. & T.
£7.90	144/17
£44.00	LS-PR, BT. TEAK/WHITE
£37.50	LS-PR, K. TEAK/WHITE
£66.00	LS-4 K TEAK/WHITE
£4.25	BASS
£1.20	TWEET
£2.75	X O KIT-B. & T.
£18.70	PHONES

only £199.00
only £99.00
only £39.90

NAME _____

ADDRESS _____


PE 7/74

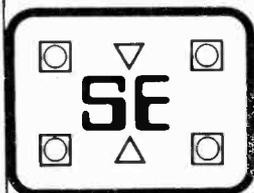

Studio Electronics

P.O. BOX 18 HARLOW
CM 18 6SH ESSEX.

Telephone: Harlow (std 0279) 25457

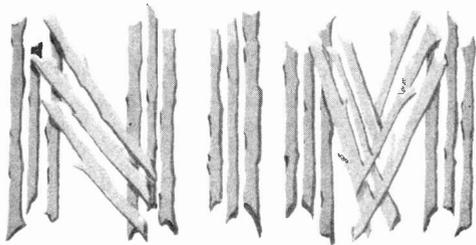

MACHINE

BY R.D. MOUNT

AN INFALLIBLE COMPUTER

FOR PLAYING THE GAME OF NIM



NIM is a game for two players. At each move a player may take any number of sticks from one, and only one, of several piles. He must remove at least one stick and the winner is the person to take the last stick. In an alternative form of the game it is the loser who is forced to take the last stick.

The game reputedly comes from ancient China, but was first analysed at the beginning of this century at Harvard, U.S.A. Clearly one or other of the players must win—there can be no draw—and it transpires that the winning strategy is closely related to the binary representation of the number of sticks in the piles.

Various designs for Nim playing machines have appeared over the years since the development of the digital computer and this article presents a contemporary one using readily available TTL digital integrated circuits.

WINNING STRATEGY

The prescription for winning at Nim relies on the fact that any arrangement of piles may be categorised as either a winning or a losing position. Further, if the arrangement represents a winning position the next move is certain to create a losing position, whilst it is always possible to play so that a losing combination is converted to a winning one again.

Thus if player A starts with a winning position, player B is bound to leave a losing one after his move. At this point A is able to convert the position to a winning one by making the correct move. The game is now back where we started and will continue to cycle in this way until A finally wins.

Should A make a wrong move at any stage the way is open for B to take over the winning strategy. As there are many more losing combinations than winning ones it is unlikely that even a player who commences with a winning position in his favour should make all the moves appropriate to his being sure of winning.

BINARY REPRESENTATION

To discover whether a given arrangement represents a winning position or not we must first write down the numbers in the piles in the binary notation. For example, suppose that there are three piles containing 3, 6 and 7 sticks then we can write these numbers in binary form as three columns

3	0	1	1
6	1	1	0
7	1	1	1
	2	3	2

Each column of this binary set should now be summed so that in this case we find the numbers 2, 3, 2, as shown. Now, a winning combination is one in which each power of two is represented an even number of times. Hence our example is a losing position because the second column, indicating the number of times that 2^1 occurs, adds up to 3 which is an odd number.

To convert such a losing position to a winning one a player must remove sticks from any pile containing the highest unpaired power of 2. In this example the highest unpaired power is 2^1 , the middle column, and as each pile contains this power it is possible to produce a winning combination by taking sticks from any pile. In fact the combinations 1,6,7 3,4,7 and 3,6,5 are all winning positions.

Should the players choose the alternative game in which the last player loses, then the above strategy follows through unchanged until no pile contains more than one stick. In this case a winning position is one in which there is an *odd* number of piles of one match each. It will be seen that this is the opposite condition to that imposed by the normal game in this case.

BASIC DESIGN

Fig. 1 presents a block diagram for a machine which will implement the principles outlined. Rotary wafer switches represent the numbers of sticks in

four piles 1 to 4, containing up to seven sticks each. These switches give outputs in binary coded form, so that, for example, if switch S1 is set to 5 then A₀ will be a logical 1 representing 2⁰, A₁ will be a logical 0 representing 2¹ and A₂ will be a logical 1 representing 2². For each power of 2 the four outputs from the four switches are taken to a Summer which produces an output equal to logical 0 if the sum is even and logical 1 if it is odd.

The Analyser takes these outputs and decides whether a winning or a losing position is set. In the former case the win output goes low and the 'Your Move' indicator lights. In the latter case the 'My Move' indicator lights and the Analyser initiates a search of the switches to find one which has the highest unpaired power of two present at its output. When this switch is found the appropriate lamp indicator lights.

The last-to-play (L.T.P.) circuitry simply tests for the simultaneous occurrence of no pile containing more than one stick and S5 being set to 'Loser'. In such a situation the control line L goes to logical 1 and the quantity NOT Σ₀ is presented to the Analyser in place of Σ₀. A little thought will show that this fits the prescription outlined above.

METHOD OF PLAY

The challenger is free to set any initial combination on the switches S1 to S4. The machine should now be switched on and one of the move indicators

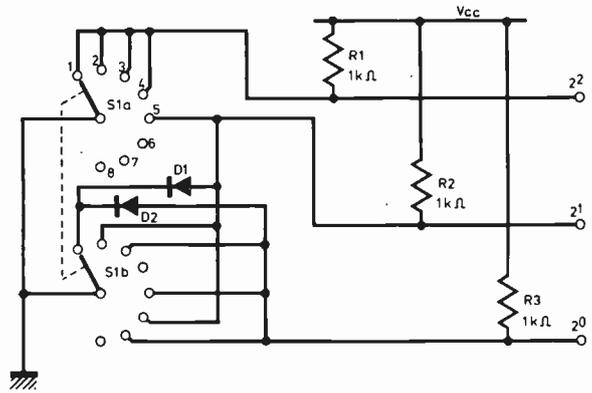


Fig. 2. Wiring detail for one of the decimal to binary switch encoders. Four such arrangements are needed

will immediately light. If 'Your Move' lights the challenger should make some legal Nim move. If the 'My Move' indicator lights then one of the lamps will also be lit and the player should turn the corresponding switch back until the 'Your Move' lamp lights. This represents the machine's move. By continuing in this way, the challenger will invariably lose.

Fig. 2 shows the suggested arrangements of one of the four Encoders S1 to S4, all of which are wired in the same way.

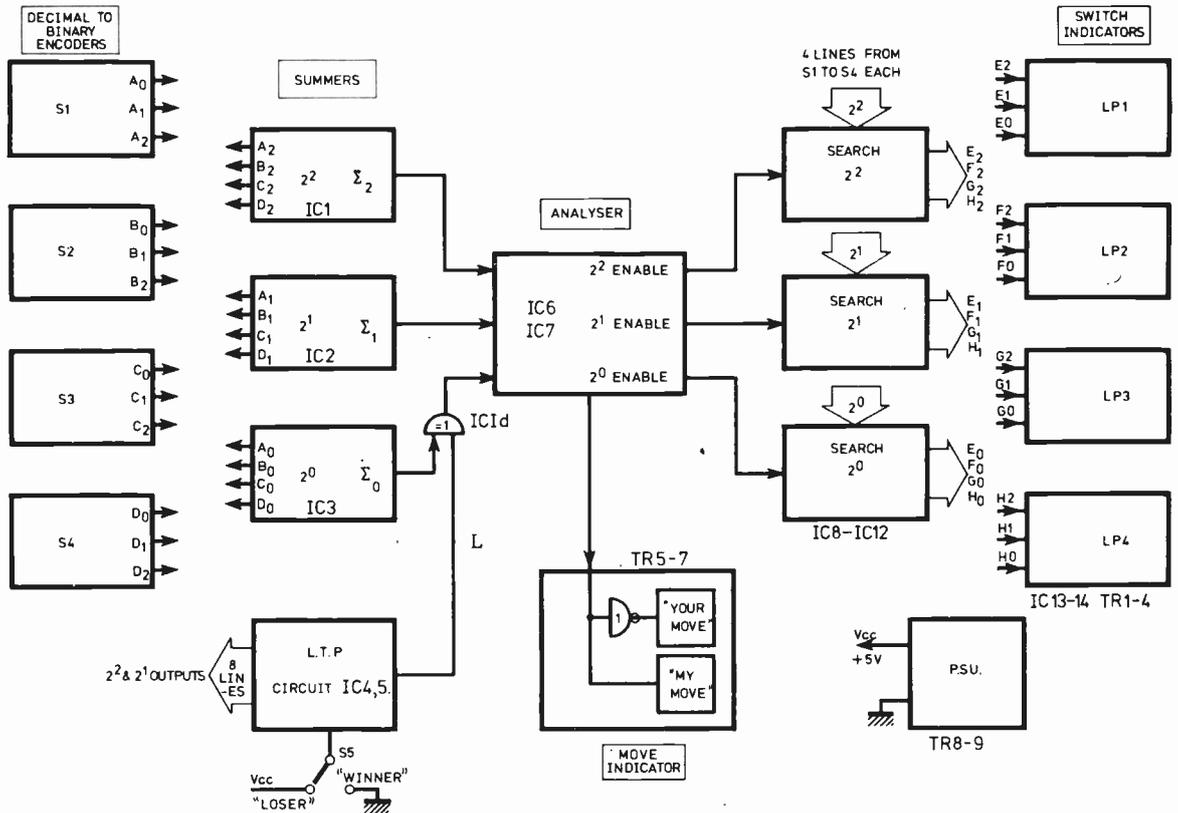


Fig. 1. Block diagram of NIM machine. For detailed wiring of sub-assemblies, see following figures

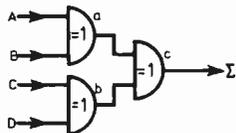


Fig. 3. Three exclusive OR gates make up each Summer. Three such circuits are required

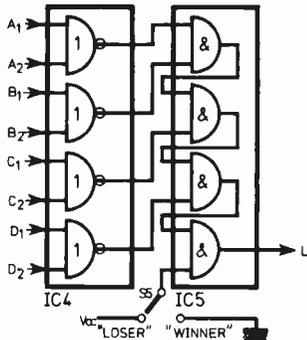


Fig. 4. Arrangement for last-to-play (L.T.P.) circuitry. See Fig. 1 for interwiring detail

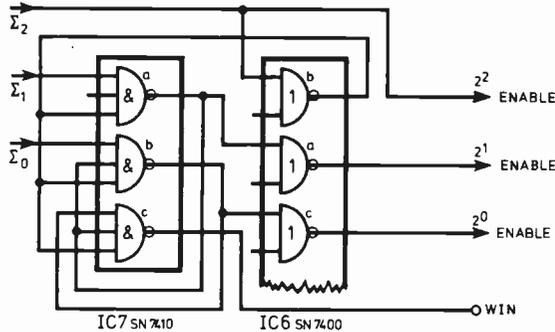


Fig. 5. Circuit diagram of Analyser gates

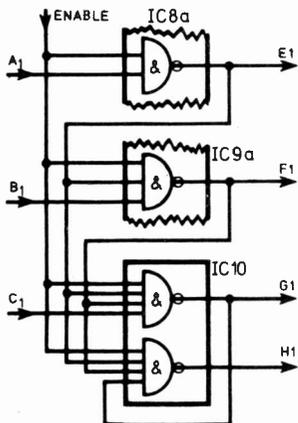


Fig. 6. The Search circuit. Three of these are required

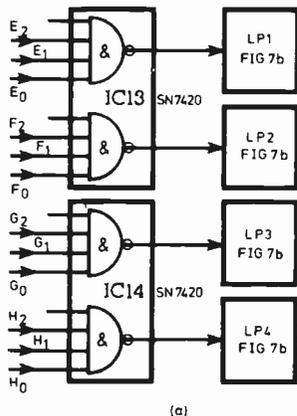


Fig. 7. Switch Indicator circuit (a) output lamp logic (b) lamp driver circuit

SUMMER

It will be seen from Fig. 3 that the Summer is a very simple circuit block. Each gate employed here is the exclusive OR gate, or half adder. Whenever the inputs are identical, the output is 0 but when the inputs differ the output is 1. That this is the function we need may be seen by realising that for our purposes all even numbers are equivalent to 0 and all odd numbers to 1.

Repeated application of the truth table to this arrangement of three gates will show that the final output is 1 if the power of 2 is represented an odd number of times and 0 otherwise.

L.T.P. CIRCUITRY

The control line output, L, of the L.T.P. circuit comes from IC5 which is wired as a five input AND gate (Fig. 4) needs only to invert Σ_0 when no pile contains more than one stick and the last person to play is deemed the loser. IC4 recognises the former condition by testing the 2^2 and 2^1 outputs from each switch. Only if these are simultaneously zero can that switch be displaying nought or one, and in this case the NOR output is a logical 1.

When the output from each of the NOR gates is 1 and the selector is set to "Loser" a control level 1 is produced which causes IC1d (Fig. 1) to invert the Σ_0 output.

ANALYSER

The purpose of the Analyser circuit (Fig. 5) is to find the highest unpaired power of 2. If all powers are paired then the game is set in a winning position, and the Analyser indicates accordingly.

Working from the top we see that if Σ_2 is high then the 2^2 enable line is high also, but IC6b inverts this level which forces both the other enable lines to stay low and forces the 'Win' output high. Similarly if Σ_2 is low but Σ_1 is high the 2^1 enable line is high but the 2^2 and 2^0 enable lines are low and the 'Win' output is high. Only if Σ_2 , Σ_1 and Σ_0 are all low does the 'Win' output go low and, in this case, all the enable lines are also low. Thus a logical 0 at the 'Win' output corresponds to a winning arrangement.

The Win output controls the Move Indicator directly.

SEARCH CIRCUITS

Suppose that the 2^1 enable line is high (this explanation follows in the same way for both of the other enable lines) then one of the three search circuits in Fig. 1 will be activated. These work in much the same way as the Analyser circuit once they are enabled.

Consider one search circuit in Fig. 6. If the A_1 level is high then E1 goes low and the other gates in the circuit are disabled forcing a high condition

COMPONENTS . . .

Resistors

R1-R17	1k Ω (17 off)	R20	68 Ω
R18	6.8k Ω	R21	1k Ω
R19	2.7k Ω		

Capacitors

C1-C3	0.1 μ F (line supply decoupling capacitors for every five i.c.s)
C4	3,300 μ F elect. 16V

Potentiometer

VR1	1k Ω preset
-----	--------------------

Diodes

D1-D8	OA81 (8 off)
D9-D12	W005 full wave rectifier (50 p.i.v., 1A)
D13	ZL3-3, 3.3V, 1.5W Zener

Transistors

TR1-TR7	BC108 (7 off)	TR8	2N3054	TR9	BC109
---------	---------------	-----	--------	-----	-------

Integrated Circuits

IC1-IC3	SN7486 (3 off)	IC8	SN7400
IC4	SN7402	IC9	SN7410
IC5	SN7408	IC10-IC14	SN7420 (5 off)
IC6	SN7400		
IC7	SN7410		

Switches

S1-S4	2 pole, 8 way rotary wafer switches (4 off)
S5	Single pole change-over
S6	Double pole mains on/off toggle

Transformer

T1	Mains transformer—primary 240V; secondary 6.3V, 1A
----	--

Lamps

LP1-LP6	6V, 0.04A filament lamps (6 off)
---------	----------------------------------

Miscellaneous

Contil Case No. 975—West Hyde Developments

at each of the other outputs F1, G1 and H1. This will cause lamp LP1 to light. Similarly, if B₁ is high then F1 goes low and the other outputs are forced to stay high so that only LP2 will light.

If A₁, B₁ and C₁ are all low then H1 goes low and LP4 lights, since the enable line tells us that one of the switches must be presenting a 2¹ contribution.

SWITCH INDICATORS

Each Switch Indicator comprises a NAND gate coupled to a lamp driver and lamp as in Fig. 7. When all three inputs are high the output of the NAND gate is low and the lamp stays off. When a low condition is received from one of the search circuits the output of the NAND gate goes high, and so the lamp lights up. So long as no fault exists, only one lamp can be lit at any one time.

The driver transistors should have a current gain of at least 50—the higher the better—and should be capable of passing up to 100mA. The power dissipation is very small, however, since each transistor is either fully conducting or completely off.

MOVE INDICATOR

The Move Indicator (Fig. 8) consists of two lamp driver circuits coupled by an inverter. The philosophy here is that if it isn't your go, it must be mine!

A discrete circuit is used for the inverter in the prototype, but one of the odd unused gates from the main circuit would work just as well.

The same comments as above apply to the characteristics of the driver transistors used here.

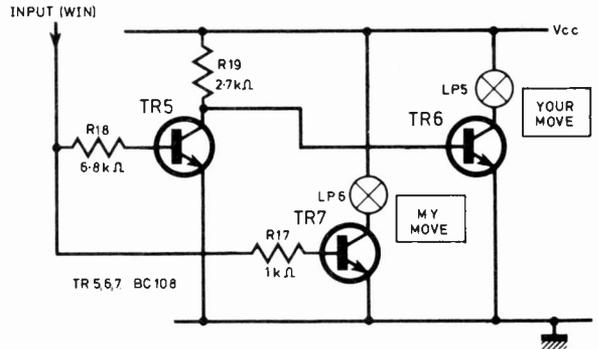


Fig. 8. The Move Indicator consists of two lamp drivers coupled by an inverter

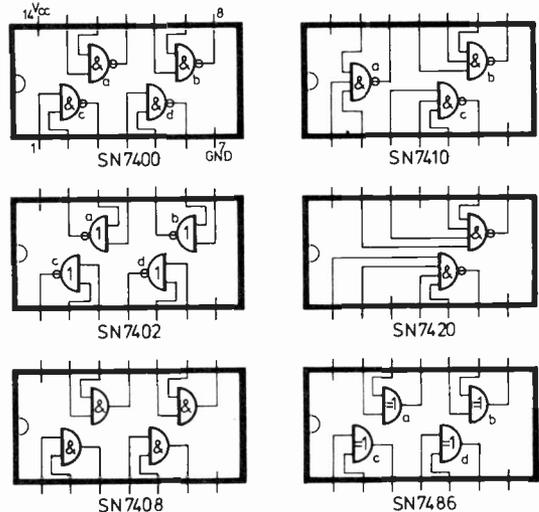


Fig. 9. Pin diagrams for the i.c.s used

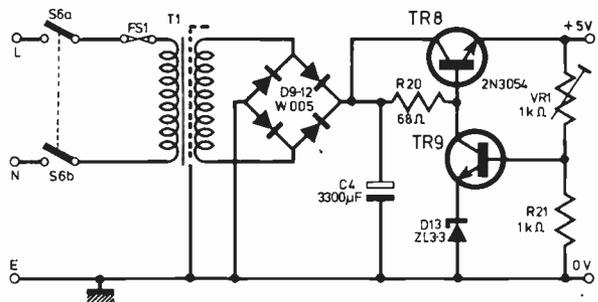


Fig. 10. Suitable power supply for the NIM machine

CONSTRUCTION

Providing all interconnecting leads are kept below 10in component layout is not critical. The sub-assemblies given in the figures should be individually assembled and checked electrically before interwiring the complete machine according to Fig. 1.

The pin wiring for the i.c.s is given in Fig. 9 and a suitable power supply in Fig. 10.

The normal i.c. practice of decoupling every 5 to 10 packages with a capacitor of about 0.1 microfarads should be followed.

The use of i.c. holders is not recommended on grounds of cost. The simple gates used in these circuits are available very cheaply, often at prices comparable with the cost of holders. ★

PATENTS REVIEW

PATENTS LIBRARY

Some remarks and reminders on general patent matters bear making. As most readers will understand, the British Patents reported in these columns are selected from the latest batches published (at the rate of around 4,000 a month) by the British Patent Office.

Once a week a new issue of patent specifications is laid out for public inspection in the library attached to the British Patent Office in Southampton Buildings, just off London's Chancery Lane. Similarly, issues are laid out at other libraries round the country. At the same time copies of the specifications are made available for purchase from the Patent Office Sales Branch by any member of the public at 25p each, post free.

At first sight this publishing of protected ideas seems a contradiction in terms. A patent application is made by an inventor who wishes to protect or monopolise his idea for a number of years. While the application is examined by the British Patent Office it is kept rigidly secret from the public; only the title, name and application date are listed in the public card indexes kept in the library. But when the application has been accepted and is published, its content is there for all to read. So what protection is a patent providing for the inventor? And would it not have been better for them simply to keep the details of his invention secret and not involve himself in the expense of securing a patent (likely to be at least £100 if handled by a Patent Agent)?

PATENT CONTENTS

A patent specification is worded in a language which many people regard as an incomprehensible mixture of legal and technical jargon. After a legally worded preamble, every specification launches into a general description of the invention and then moves on to a specific description (usually with drawings) which explains in detail how one or more practical embodiments of the invention actually work.

Every patent specification ends with a set of claims which are the

most important part when monopoly and infringement are considered. The claims define the scope of monopoly which the Patent Office has agreed to allow the inventor, having carried out searches through previously published patents.

If a claim is too broad, it may "catch" a large number of "infringing" articles, but it may also embrace articles that are known to be old. So the claim is in practice invalid. And anyone concerned and believing that the claims of a freshly published patent are obviously invalid can either ignore them or legally oppose them at a Patent Office Hearing.

ADVANTAGES OF PUBLISHING

Publishing patents also serves to enhance the richness of human knowledge and once a patent has expired (even if the full £300 worth of annual renewal fees are paid, a British patent can only last 16 years) all that it discloses and claims becomes part of the public domain. The basic reasoning is that the inventor is granted a limited monopoly in return for disclosing his idea rather than keeping it secret. Incidentally, laying open the details of an invention to the public also serves as something of an advertisement for the owner of the patent, who may be approached by manufacturers who wish to make what he claims under a licence.

It is a basic canon of patent law throughout the world that (subject to a very few exceptions) no one can patent an invention once it has been disclosed to the public. Thus, usually, once an invention has been published (e.g. in a book or magazine, or offered for sale) no one, the inventor included, can subsequently patent it. But it is perfectly safe for an inventor to lodge an application (even if it is accompanied only by a Provisional Specification, which simply lies fallow at the Patent Office for a year) and then immediately publish his invention. Making the patent application generates a priority date which safeguards subsequent disclosure.

Where details of a circuit or construction are given in a magazine with d-i-y slant, e.g. Practical Electronics or Everyday Electronics, it would not normally be possible for anyone to apply for a patent,

for anything disclosed, after publication. However, if a contributor had already applied for a patent before the appearance of the article describing his design, then the appearance of that article would not in itself invalidate any patent subsequently granted.

LEGAL ACTION

Because the long arm of patent law moves slowly, there is often a gap of several years between original application and final acceptance and grant. Thus it is perfectly possible that a circuit or design published in a magazine such as this could already be the subject of a pending patent application which will not come into legal force until months or even years after the appearance of the relevant magazine issue.

Usually no action for infringement can ever be taken on a pending patent application (remember, they are kept secret so it would be grossly unreasonable if such action could be taken) this could under certain circumstances mean that designs to be found in some back numbers are only now protected by patents.

In practice these circumstances have never presented problems and are unlikely ever to do so, largely because the law is not often an ass. For instance, it is so unlikely as to be inconceivable that the owner of a patent would ever be in a position to know who was making a "one-off" model of his design in the privacy of his own home or garden shed.

But anyone considering an expensive production run of any construction should always try and discover whether or not patent rights (perhaps owned by some completely different third party) are involved before embarking on such a project. For this reason it would seem in the interests of everyone if contributors with d-i-y projects included a reference by number to any relevant patents or patent applications.

Finally, readers believing that they have a patent problem on their hands should seek advice from a Patent Agent; no one on Practical Electronics can enter into correspondence on such matters.

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 25p each

Save a massive £10 on the popular Sinclair Cambridge kit...

now only £14.95!

(PLUS VAT)

An advanced 4-function calculator in kit form

The Cambridge kit is the world's largest-selling calculator kit.

It's not surprising — no other calculator matches the Sinclair Cambridge in functional value for money; and buying in kit form, you make a substantial saving.

Now, simplified manufacture and continuing demand mean we can reduce even the kit price by a handsome £10. For under £15 (plus VAT), you get the power to handle complex calculations in a compact, reliable package — plus the interest and entertainment of building it yourself!

Truly pocket-sized


With all its calculating capability, the Cambridge still measures just $4\frac{1}{3}'' \times 2'' \times \frac{1}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience — it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of normal use before replacement.

Easy to assemble

All parts are supplied — all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £16.45!

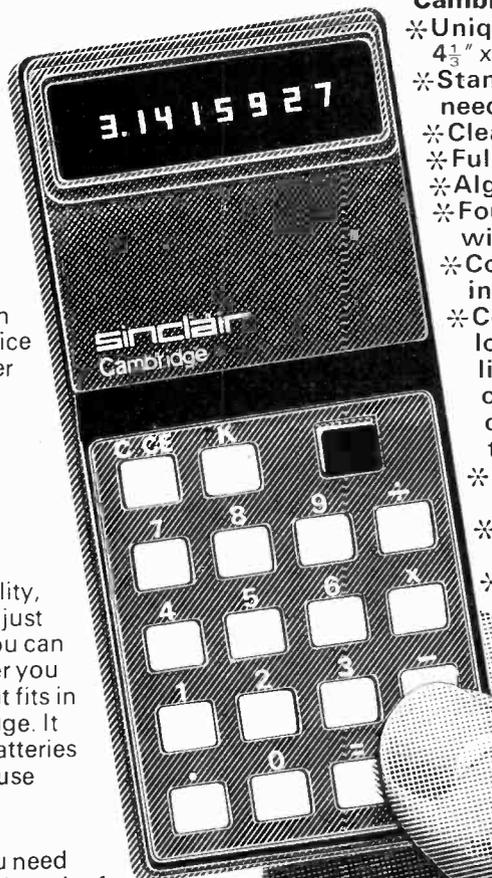The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £27.45 — so you're saving £11! Of course we'll be happy to supply you with one ready-assembled if you prefer — it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package. $4\frac{1}{3}'' \times 2'' \times \frac{1}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £17.
- * Calculates to 8 significant digits.
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries.

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

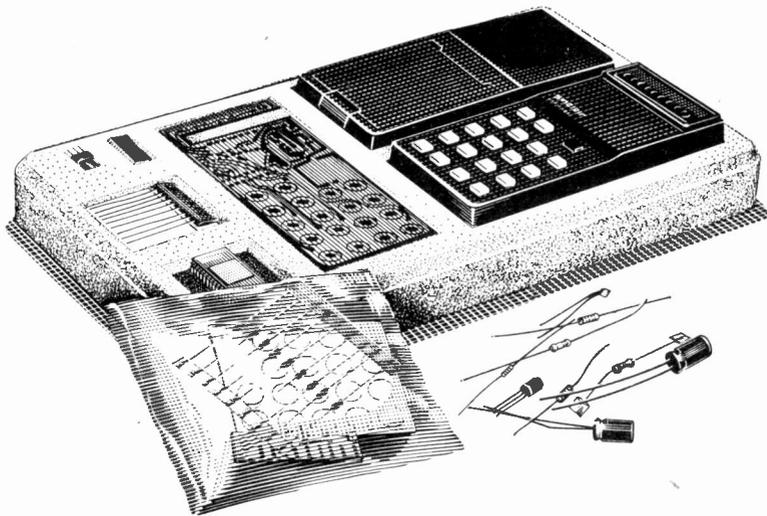
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

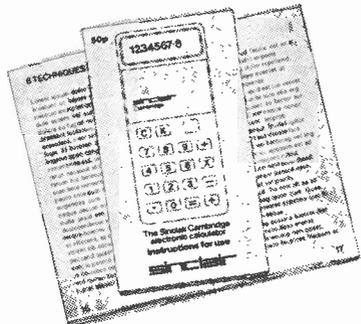But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 80 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology. *And you benefit!*

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year. Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £14.95 + £1.50 VAT. (Total: £16.45)
Price fully built: £24.95 + £2.50 VAT. (Total: £27.45)

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me Name _____

a Sinclair Cambridge Calculator kit at
£14.95 + £1.50 VAT (Total: £16.45) _____

a Sinclair Cambridge calculator ready
built at £24.95 + £2.50 VAT
(Total: £27.45) Address _____

*I enclose cheque for £ _____, made
out to Sinclair Radionics Ltd, and
crossed. _____

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required.

PLEASE PRINT

Readout —

A SELECTION FROM OUR POSTBAG

Good olde days!

For over twenty years, I have been an inveterate constructor. In my early days they were the designs of people more clever than myself. Then, with increasing knowledge and experience, I began to try my hand at designing my "own" circuits.

An essential part of my apprenticeship was acquiring the expertise essential if one was to become a skilful "chassis basher", out of aluminium, mild steel or tin plate. A chassis was an essential prerequisite for use with valves, which were, for the benefit of those who haven't seen one, made of glass with bits of metal inside them. The valves usually glowed dull red (that's the filament, son), sometimes got very hot, and sometimes "bit" hard if one got careless. I ended up in hospital once when I got careless whilst working on high power transmitters.

A well laid out, and carefully constructed chassis, imbued its constructor with a feeling of euphoria, whilst he sniffed at the delicate aroma of hot valves, warm Bakelite and warm transformer impregnant, occasionally enlivened by over heated resistors.—What joy! What contentment!

Then along came the transistor. I had to discard most of my painfully acquired wisdom and start learning again. Early results were most discouraging, but I persevered, and, slowly, success came my way. But some of the pleasure had gone. A tag board here, a turret tag there. The resulting rat's nest on an s.r.b.p. board possibly worked, but it looked ghastly and meant that one less skill to be exercised.

To cap it all, along came i.c.s. and, again, less skill was required on the part of the constructor. A few i.c.s. and sundry components mounted on a bit of "holey" s.r.b.p. board (Veroboard) and there it was. It may have worked, but did it really take much "constructing"?—I personally don't think so.

Over the period of time since I first entered the world of electronics, the individual constructor has had to exercise less and less skill, more and more is done for him. In this world of "instant" instants, who has the time to learn a new set of skills to really build or construct something different, something unique?

It is a chastening thought, and, I think, a saddening one, to reflect on the electronics constructors lot in, say, ten years' time. You want to "build" a radio, son? You'd like to build a 50W stereo amplifier? Here are three "cubular modules", press the top of that one, there's the radio you built. Plug the other two into the mains, plug in your sound source and there's the stereo amplifier you built.

Where's the fun? Where's the pleasure of actually constructing something with your own hands? Fun? Pleasure? I for one, mourn the passing of the valve; the passing of the early transistor days.—Those were the days.

H. T. Kitchen,
Bulkington, Warks.

Fog warning system

Sir,—With the perennial concern for Motorway safety I feel you should know about a fog warning system I have devised after a considerable period of experimentation.

In principle it monitors the whole of the Motorway, is automatically triggered by fog or smoke and provides advance warning to motorists 300m prior to the affected area.

The basic system is as follows (See Fig. 1). A light beam is directed along the Motorway verge in the direction of oncoming traffic to an optical receiver 300m away. While the beam is maintained a relay controls another signal lamp directed to a receiver a further 300m along the Motorway verge and so on. Such a chain is optically possible since Motorways are practically

straight and level and there are no obstructions along the verges.

If the beam is interrupted by fog, heavy rain, snow or smoke the receiver causes the relay to change over and transfer power from the following signal lamp to multivibrator controlled warning lamps. The net result is that all lamps in the chain are cancelled and warning lamps are left to flash warning of danger.

The optical receiver consists of a long collimator tube, matt black inside, which directs the light beam from the lamp to a 4½in concave mirror and light dependent resistor which almost forms the focus. Similarly the transmitter has a 4½in concave mirror fed from a 10V, 1A bulb. This supply is obtained from a tapped car battery (older kind) which also sources two groups of six 3.5V, 0.3A bulbs in a series parallel arrangement making up the collector loads to a multivibrator circuit.

A modification to the system is the inclusion of a lamp pulser (multivibrator). This permits the system to be used over long distances. If, say, fog were only affecting a section of the Motorway the closing of the relay would operate the warning lamps and the pulser. For that transmitter path where there was no fog the pulser would cause the lamp to flash, this would restore the "all-clear" to the other units along the Motorway.

By carefully timing the pulses and adding a suitable delay to each receiver it is possible to have two fog affected units showing a warning and the rest of the chain showing "all-clear."

From the circuits devised, field trials have been encouraging. Some further experiments have been conducted using modulated light, but it is a matter for further study as to which of these ideas is the most suitable, but the writer believes that it should not be beyond the abilities of, say, students working for A level physics to devise a practical solution, working on these lines, to a national problem.

G. Cozens,
Bartley,
Southampton

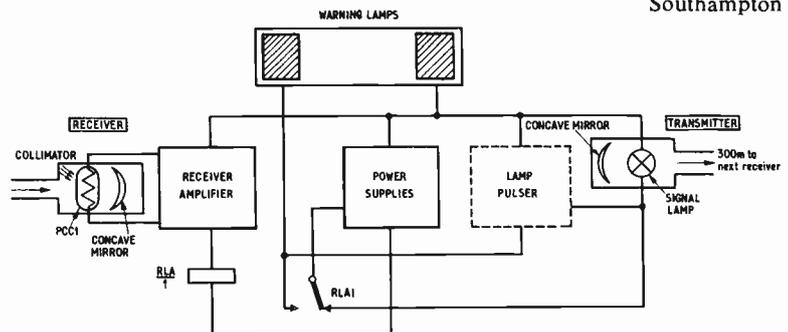


Fig. 1. Basic receiver/transmitter unit for controlling fog warning lamps on the Motorway

Psycho-sensitive semiconductors ?

Sir—With reference to Mr. Brian Baily's article in P.E. April '74 about ESP I should like to propose the following explanation of the results he obtained from his experiments on plants. I wish to point out that this is merely a hypothesis and that I have no evidence other than that which I state:

In one of the programmes in the recent BBC T.V. series "Young Scientist of the Year!" the results of a group of boys' experiments on growing plants in magnetic fields, were presented. They found that plants grown in a magnetic field bent and grew along the lines of force. Could this not be something to do with the fact that there is an atom of iron at the core of the chlorophyll molecule, which may render it magnetically sensitive?

It is possible that the molecules align themselves along the lines of force, presenting a coherent chain of electrically resistive molecules, whereas normally they would be in an amorphous distribution. This migration of the vital chlorophyll towards one point would explain the tropic response of the plants in the magnetic fields.

Is it not possible then, that if a large, strong field is enough to cause the plant to change its direction of growth, the weak field surrounding an electrically active brain would be sufficient to align one or two

chains of molecules and thus cause a change in the cells' resistance?

The shrimps' nervous system on contact with the boiling water would radiate a field of far greater strength than normal, this would be selected by the plant and the appropriate change in resistance would occur. I propose that a concentrating mind, regardless of the subject of that concentration, produces a field strong enough for the plant to detect.

Assuming this theory to be correct, there must be other chemicals possessing the same property, in which case it is not hard to imagine, in the not-too-distant future, the invention of a psycho-sensitive semiconductor device. This would be a boon for handicapped people who would be able to turn on equipment merely by thinking about it, no physical help required.

P. Watson,
Bedfordshire.

Hot line

Sir—A short while ago, my wife and I decided to change the position of the furniture in our lounge. The arrangement we chose meant that the colour television would not plug directly into the socket, so I decided to use an extension cable. The only one which was available was a 150ft cable which I use with the electric lawn mower.

Being the cautious type I checked that the television would not overload the cable and as the cable

was rated at 5A and the television consumption 245W, which is just over 1A at 240V, I decided that it would be safe. As you can imagine, 150ft of cable across a lounge leaves quite a lot to spare so I coiled it neatly and put it behind the television.

I offered a neighbour of mine the use of my lawn mower as he was having trouble coping with a thick growth. As the cable on the machine was not long enough I also offered the extension cable, this was when I found to my horror that the neatly coiled cable had welded itself together, it had apparently acted as a heating coil with 1A being sufficient to create enough heat to ruin all but 15ft of the cable. During this time the cable has not short circuited or failed but it has left a nasty burn mark on the carpet.

I had wondered why the cat had taken to sleeping under the television, she usually finds the warmest position to curl up.

R. F. Burgin,
Witham,
Essex.

According to I.E.E. regulations current ratings for cable are based on a fixed ambient air temperature. Any heat arising from the cable caused through coiling must derate this figure. The combination of heat generated in a long cable magnified by coiling and the cat probably contributed to the thermoplastic insulation deteriorating.—Ed

SOUND SYNTHESIS FOR THE AMATEUR

Due to the unprecedented number of letters we have received from readers stating their disappointment at not being able to attend the P.E. Audio Fair lectures, and more recently the lecture given at Essex University, we have decided to make available (at a small fee) to Clubs, Schools and Universities a taped recording and colour slides of the lecture.

Entitled "SOUND SYNTHESIS FOR THE AMATEUR" the tape runs for approximately 45 minutes at 7½ i.p.s. and was recorded on a Philips N4450 domestic recorder. The colour slides contain waveforms, block diagrams and circuits on the various sections of the P.E. Synthesiser. Only two sets of tapes and slides are available and requests will be dealt with in strict rotation of receipt.

It is regretted that this service can only be offered to CLUBS, SCHOOLS, and UNIVERSITIES. The charge is £1 to cover handling and postal charges. A refundable deposit of £5, to cover any damage to tapes or slides, is also required.

Requests for the tape and slides (with date of proposed use) should be addressed to:

The Editor, Practical Electronics, Fleetway House, Farringdon Street, London, E.C.4.

It is regretted that we can only handle postal requests.


SONAX ELECTRONICS

FANTASTIC KIT OFFER

PE RONDO

complete quadraphonic Hi-Fi System

AS FEATURED IN
PRACTICAL ELECTRONICS

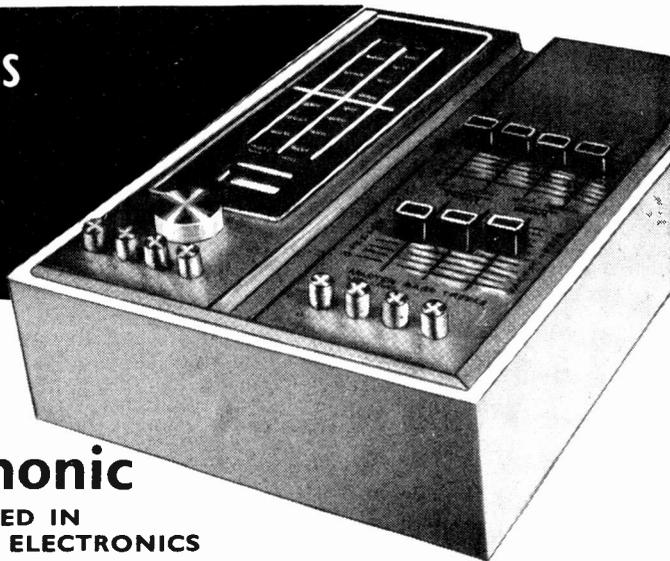

There's never been an offer like it! Construct this 80 watt RMS Quadraphonic System with 4 matched high performance speakers. All finishes including polishing of cabinets and brushing and anodising of metal work are already completed. You can achieve the finest production finish and the styling will do justice to any room setting.

PLEASE SEND ME	PLEASE TICK BOX	ADDITIONAL ITEMS	
CBS SQ* MATRIX DECODER	£8.00 <input type="checkbox"/>	RONDO CASE	£1.92 <input type="checkbox"/>
*TM CBS Complete kit. Post Free. Inc. CBS Licence Fee + VAT 80p		Post Free. + VAT 19p	COMPLETE SET OF 4 EDGE-CONNECTORS
PREAMPLIFIER BOARD	£3.30 <input type="checkbox"/>	HARDWARE PACK	£2.20 <input type="checkbox"/>
Complete kit. Post Free. + VAT 33p		Post Free. + VAT 22p	Post Free. + VAT 14p
MASTER VOL./TONE/BALANCE BOARD	£9.35 <input type="checkbox"/>	CONTROL SECTION FASCIA	£3.85 <input type="checkbox"/>
Complete kit. Post Free. + VAT 93p		Post Free. + VAT 38p	COMPLETE SET OF PATCH BOARDS AND FANNING STRIP
POWER AMP BOARD AND HEATSINK (Stereo Pair)	£8.25 <input type="checkbox"/>	STEREO DECODER KIT INC. BEACON	£5.95 <input type="checkbox"/>
Complete kit. Per Board. Post Free. + VAT 82p		Post Free. + VAT 59p	Plug and socket and 24 way edge-connector. Post Free. + VAT 35p
POWER SUPPLY BOARD COMPLETE	£5.50 <input type="checkbox"/>	STEREO DECODER READY BUILT AND TESTED	£7.64 <input type="checkbox"/>
Post Free. + VAT 55p		Post Free. + VAT 76p	TUNER SECTION FASCIA AND WINDOW
MAIN SMOOTHING CAPACITORS (Two reqd.)	£1.65 <input type="checkbox"/>	ALSO—Suitable record playing equipment	£3.85 <input type="checkbox"/>
Post Free. + VAT 16p			Post Free. + VAT 38p
MAINS TRANSFORMER	£6.87 <input type="checkbox"/>	GOLDRING G101/2 TURNTABLE	£1.25 <input type="checkbox"/>
Post Free. + VAT 68p		Less Cartridge	QUAD SELECTOR SWITCH
CHASSIS-PUNCHED AND DRILLED WITH SCREENS	£3.57 <input type="checkbox"/>	DEUTSCHE ELAC STS 144/17 CARTRIDGE	£1.43 <input type="checkbox"/>
Post Free. + VAT 35p		Post Free. + VAT 79p	Post Free. + VAT 14p
			4 PILLARS AND 2 END CAPS AND CENTRE BRIDGE AND SIDE TRIMS
			Post Free. + VAT 33p
			NEW RONDO ADDITION
			F.M. TUNER KIT 1µV Sensitivity High Performance
			Post Free. + VAT £1.75
			TUNING DIAL ASSEMBLY Complete with Meter and Calibrated Electro-luminescent Dial
			Post Free. + VAT £1.04

SPEAKER KITS All components parts for "Rondo" loudspeaker assemblies are available, including special precision machined wrapround cabinets for very easy construction and perfect professional finish—as shown in fig. 7.9 of January 1974 issue.

COMPLETE SPEAKER KIT WITH 4 DRIVE UNITS, CROSSOVER WADDING, ETC. INCLUDING CABINETS
Price Per Pair **£34.50**
Post £1. + VAT £3.55

SPECIAL OFFER - SAVE £7

4 Speaker kits (as required for Rondo) **£62.00**
Post £2. + VAT £6.40

Comprising 16 loudspeaker drive units, FOUR 5 element crossover networks including 12 prewound coils, four fully machined and polished wrap-round cabinets, four routed front and four routed back panels. 72 feet of coded coloured wire, four recess panels containing din and 4mm sockets, 24 lengths of 2" thick special acoustic wadding and latest acoustically transparent Declon fronts to complete the finish.

MONEY ENCLOSED £

NAME

ADDRESS

POST TO:

SONAX ELECTRONICS, Spencer House, Brettenham Rd., Edmonton, London, N.18

BASS DRIVE UNITS (2 per cabinet) **£4.25**
Post Free. + VAT 42p

TWEETERS (2 per cabinet) **£1.20**
Post Free. + VAT 12p

CROSSOVER KIT (1 per cabinet) **£2.75**
Post Free. + VAT 27p

DETAILS OF ANCILLARY KITS

We apologize to our customers for any inconvenience caused by delay in delivery. This is due to tremendous demand for our products and we are endeavouring to clear back-log with all possible speed.

**BLOCK CAPITALS PLEASE
CHEQUE/P.O./MONEY ORDER**

RST

VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 3p for first transistor, 1p thereafter, over ten post free. INTEGRATED CIRCUITS 5p + 1p each added

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P		
1N21	0-17	FAZ11	1-15	BY213 0-25	0AZ206 0-25	ES170 0-18
1N23	0-25	AFZ12	2-00	BY210 0-45	0AZ206 0-45	ZS271 0-18
1N85	0-50	ASB28	0-25	BYZ11 0-40	0AZ207 0-45	ZT21 0-25
1N293	0-50	ASB27	0-20	BYZ12 0-40	0AZ208 0-40	ZT43 0-25
1N265	0-50	ASB28	0-25	BYZ13 0-25	0AZ209 0-40	ZTX107 0-18
1N645	0-16	ASB29	0-20	BYZ15 1-25	0AZ210 0-40	ZTX108 0-10
1N725A	0-20	ASB36	0-25	BZ116 0-40	0AZ211 0-40	ZTX300 0-14
1N914	0-06	ASB51	0-40	BZY88 0-10	0AZ222 0-45	ZTX304 0-24
1N4007	0-12	ASB53	0-20	CL11 0-55	0AZ224 0-45	ZTX503 0-18
1B131	0-25	ASB55	0-20	CR81/05 0-80	0AZ241 0-25	ZTX531 0-25
1B131	0-18	ASB55	0-20	CR81/40 0-45	0AZ242 0-15	
1B202	0-25	ASB62	0-25	CR84B 1-90	0AZ244 0-25	
2G371	0-40	ASB66	0-25	CB10B 0-80	0AZ246 0-15	
2G381	0-22	ASB221	1-00	DD000 0-15	0AZ290 0-25	
2G414	0-30	AU101	1-50	DD003 0-15	OC16 1-00	
2G417	0-25	AUY10	1-00	DD006 0-25	OC16T 1-00	
2N404	0-25	BC107	0-12	DD007 0-40	OC19 0-20	
2N897	0-15	BC108	0-12	DD008 0-25	OC20 0-20	
2N898	0-20	BC109	0-12	DD008 0-25	OC22 1-00	
2N706	0-10	BC110	0-18	GD 4 0-10	OC24 1-20	
2N706A	0-12	BC113	0-16	GD5 0-10	OC28 1-10	
2N708	0-15	BC116	0-20	GD8 0-25	OC29 0-40	
2N709	0-40	BC116A	0-22	GD12 0-10	OC28 0-40	
2N1091	0-20	BC118	0-20	GET102 0-20	OC28 0-70	
2N1131	0-25	BC121	0-20	GET103 0-40	OC29 0-25	
2N1132	0-25	BC122	0-20	GET113 0-25	OC30 0-40	
2N1303	0-18	BC126	0-25	GET114 0-20	OC36 0-25	
2N1304	0-22	BC128	0-25	GET118 0-25	OC38 0-25	
2N1306	0-22	BC147	0-12	GET120 0-50	OC42 0-70	
2N1307	0-25	BC148	0-10	GET872 0-20	OC43 0-70	
2N1308	0-22	BC149	0-12	GET875 0-40	OC44 0-18	
2N2147	0-75	BC167	0-14	GET880 0-55	OC44M 0-17	
2N2148	0-60	BC168	0-12	GET881 0-25	OC45 0-18	
2N2160	1-00	BC180	0-22	GET882 0-25	OC45M 0-18	
2N2218	0-22	BC189	0-22	GET885 0-25	OC46 0-27	
2N2219	0-25	BCY31	0-45	GEX44 0-08	OC57 0-20	
2N2369A	0-10	BCY32	1-20	GEX45/1 0-45	OC58 0-20	
2N2444	1-00	BCY33	0-25	GEX941 0-45	OC59 0-20	
2N2613	0-25	BCY34	0-45	GJ3M 0-50	OC68 0-50	
2N2646	0-50	BCY38	0-55	GJ4M 0-25	OC70 0-18	
2N2904	0-20	BCY39	1-00	GJ5M 0-25	OC71 0-15	
2N2904A	0-25	BCY42	0-20	HG1005 0-50	OC72 0-25	
2N2906	0-20	BCY70	0-15	H8100A 0-20	OC74 0-20	
2N2907	0-20	BCY71	0-20	MAT100 0-20	OC75 0-20	
2N2924	0-18	BCZ10	0-20	MAT101 0-25	OC76 0-20	
2N2925	0-15	BCZ11	0-65	MAT120 0-20	OC77 0-55	
2N2926	0-10	BD121	1-00	MAT121 0-25	OC78 0-25	
2N3054	0-50	BD123	1-00	MJ220 0-20	OC79 0-20	
2N3055	0-20	BD124	0-80	MJ2205 1-10	OC81 0-20	
2N3702	0-11	BDY11	1-45	MJ2305 0-75	OC81D 0-20	
2N3708	0-18	BF115	0-22	MJ2340 0-50	OC81M 0-20	
2N3706	0-11	BF117	0-50	MPP102 0-40	OC81DM 0-18	
2N3707	0-18	BF167	0-25	MPP103 0-20	OC81Z 0-25	
2N3709	0-10	BF173	0-22	MPP104 0-25	OC82 0-22	
2N3711	0-11	BF181	0-22	MPP105 0-45	OC82D 0-25	
2N3819	0-20	BF184	0-25	NKT129 0-45	OC83 0-20	
2N3819	0-20	BF185	0-25	NKT129 0-20	OC84 0-20	
2N3819	0-20	BF186	0-25	NKT211 0-25	OC84 0-20	
2N3819	0-20	BF187	0-25	NKT212 0-25	OC85 0-20	
2N3819	0-20	BF188	0-25	NKT213 0-25	OC86 0-20	
2N3819	0-20	BF289	0-25	NKT314 0-25	OC187 0-20	
2N3819	0-20	BF29				

44p ?

Trannies

4 Bush House,
Bush Fair, Harlow,
Essex.

- * PRICES INCLUSIVE OF V.A.T.
- * Retail Shop open 9 to 5.30 Mon. to Sat.
- * Post & Package 15p.
- * 1974 Catalogue 20p.

TRANNIES DISCO UNIT



- Includes
- * DJ 100W discotheque amp. with full mixing and PFL facilities. £94.75.
- * Stereo headphone with boom microphone. £9.90.
- * Trannies disco console with 2 Garrard SP25 Mk. IV turntables. £59.00
- * Pair 50W Speakers £47.00

OR COMPLETE SYSTEM £189.97, carriage £5.00. Terms available, no deposit. £10.16 monthly for 24 months.

We stock a full range of Disco Equipment. Send for list or pay a visit.

£1 BARGAIN PACKS

- £1 10 Silicon NPN Power transistors (like 2N3055). Below spec.
- £1 30 Plastic FET's unmarked/untested, similar to 2N3819 (random test showed good yield).
- £1 20 TO5 transistors NPN or PNP, state which, 2 to 5 amp w/tested.
- £1 20 TO18 transistors PNP like BC178, BC179, etc. U/tested.
- £1 30 Plastic Power NPN transistor TO220 case like 2N3055. U/tested.
- £1 10 General Purpose fully tested FET's.
- £1 200 mixed capacitors
- £1 250 mixed resistors.
- * Any 5 packs £4.50 *

SEMICONDUCTORS	BRIDGE RECTIFIERS	THYRISTORS	TUBES
AC126 14p	OC44 16p		
AC127 16p	OC45 10p	1 Amp	
AC128 15p	OC71 11p	100V	22p
AC141K 26p	OC81 12p	200V	24p
AC142K 26p	2N706 14p	600V	27p
AC176 18p	2N1131 24p		
AC187 24p	2N1132 28p		
AC188 24p	2N304 20p	1 Amp	
AC187K 23k	2N2926 11p	50V	29p
AC188K 23p	2N3053 26p	100V	32p
AD149 49p	2N3054 55p	200V	34p
AD161 33p	2N3055 49p	400V	44p
AD162 40p	2N3702 14p	3 Amp	
AF114 20p	2N3703 13p	50V	39p
AF115 20p	2N3704 14p	100V	44p
AF116 20p	2N3705 13p	200V	48p
AF117 20p	2N3706 12p	400V	66p
BC107 13p	2N3707 13p	5 Amp	
BC108 12p	2N3708 11p	50V	46p
BC109 13p	2N3709 12p	100V	57p
BC147 13p	2N3710 12p	200V	66p
BC148 13p	2N3711 12p	400V	77p
BC149 13p	2N3819 35p		
BC182 13p	40361 55p	2 Amp	
BC183 11p	40362 55p	100V	33p
BC184 14p	40363 69p	200V	55p
BC212 13p	1N914 8p	400V	77p
BC213 13p	1N916 8p	6 Amp	
BC214 13p	1N4001 7p	100V	66p
BD131 68p	1N4002 8p	200V	88p
BD132 90p	1N4003 10p	400V	99p
BF194 16p	1N4004 10p	10 Amp	
BF195 17p	1N4006 15p	100V	99p
BF244 27p	1N4148 6p	200V	1.32
BFY50 18p	1N5400 16p	400V	1.43
BFY51 18p	1N5401 17p	400mW	
BFY52 17p	1N5402 19p	ZENER	
MP8111 36p	1N5404 24p	DIOIDES	
OC28 50p	1N5406 28p	3.3 to 33	
OC26 50p		volt 11p each	

Resistors

- 1/2 watt 5% carbon 1p
- 1 watt 5% carbon 3p
- 1 watt 10% carbon 1p
- range 10 ohms to 4.7 megohms.
- 1/2 watt m/o 2% 4p
- range 10 ohms to 1 megohms.

VEROBOARD

0-1	0.15
2 1/2 x 3 1/2	24p 19p
2 1/2 x 5	27p 23p
3 1/2 x 3 1/2	27p 23p
3 1/2 x 5	31p 31p
17 x 2 1/2	82p 63p
17 x 3 1/2	£1.10 87p
17 x 5 (Plain)	80p
Pin insertion tool	57p 57p
Spot face cutter	46p 46p
Pk. 36 Pins	20p 20p

Electrolytic Capacitors

6.3 VOLT	220µF	9p	40 VOLT
68µF	64p	680µF	17p
150µF	64p	1000µF	17p
170µF	11p	1500µF	25p
680µF	13p	2000µF	43p
1500µF	18p		
1500µF	18p		
3300µF	26p		
		25 VOLT	
		10µF	64p
		22µF	64p
		47µF	64p
		100µF	8p
		150µF	8p
		220µF	10p
		470µF	13p
		470µF	10p
		1000µF	11p
		1500µF	20p
		2200µF	24p
		5000µF	68p
		16 VOLT	
		15µF	64p
		33µF	64p
		150µF	64p
		150µF	8p
		40 VOLT	
		6.8µF	64p
		15µF	64p
		33µF	64p

VOLUME CONTROLS

Potentiometers
Carbon track 500Ω to 2.2MΩ.
Log or Linear.
Single 13p. Dual gang (stereo) 44p.
Single-type with D.P. switch 13p extra.

CARBON SKELETON PRESETS

Small high quality type (linear only). All valves 100-5 meg ohms.
- 1 watt 6p each
- 2.5 watt 64p each

VISIT OUR RETAIL SHOP AT BUSH FAIR Monday to Saturday 9 to 5.30.


SLIDE SWITCH SPST 11p each D.P.D.T. 13p each.

MINIATURE NEON LAMPS 240V or 110V 1.4 Sp. 5 plus 44p each.

Mullard Polyester Capacitors

C280 SERIES
250V P.C. mounting: 0.01µF, 0.015, 0.022 34p, 0.033, 0.047, 0.068 4p, 0.1 44p, 0.15, 0.22 54p, 0.33 7p, 0.47 94p, 0.68 12p, 1µF 14p, 1.5µF 22p, 2.2µF 27p.

C296 SERIES
400V: 0.001µF, 0.0015, 0.0022, 0.0033, 0.0047 3p, 0.0068, 0.01, 0.015, 0.022, 0.033 34p, 0.047, 0.068, 0.1 44p, 0.15 64p, 0.22 84p, 0.33 12p, 0.47 144p, 0.68 34p, 0.1 4p, 0.15 4p, 0.1 44p, 0.15, 0.22 54p, 0.33 7p, 0.47 94p, 0.68 12p, 1µF 14p, 1.5µF 22p, 2.2µF 24p.

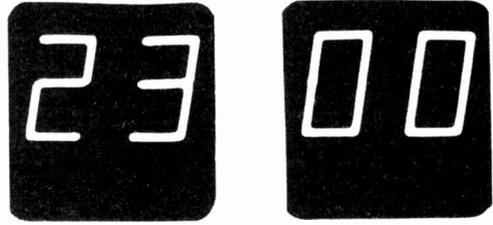

SP352

SP352

MK50250N—NEW MOSTEK ALARM CLOCK IC £6.00 + VAT = £6.60
24hr format—Alarm—Snooze—Multiplexed 4 to 6 digit display—etc. This is a high performance clock IC from Mostek Corporation at a break-through price.

BUILD AN ATTRACTIVE DIGITAL ALARM CLOCK WITH RADIO TURN-ON
A kit of all parts except case and switches for a digital alarm clock with radio turn-on using the MK5020N and highly attractive SP352 0.55in displays (see above). The kits include: Building instructions, MK50250N, SP352 displays, all semiconductors, resistors and capacitors, radio turn-on relay, miniature loudspeaker for alarm, soldercon pins for IC socket, main PCB and digit mounting PCB. Both PCBs have been designed so that constructors of the 4 digit clock may easily expand their unit to 6 digits at a later date.

4 digit Kit £26.00 + VAT = £28.60
6 digit Kit £31.40 + VAT = £34.54
Send for free information on low-cost kits using the MK50250N with LEDs, Minitrans, etc. For details of the SP352 and other Beckman Displays available from us, see our P.E. June or W.W. April ads, or send for free information.

CT5001 4 FUNCTION CALCULATOR IC £4.80 + VAT = £5.28
We have designed an exciting low-cost calculator for the amateur constructor using this device—send for free information.

SLA7 0.33in RED LED DIGITAL DISPLAYS plug-in replacements for DL707
Pack of 4: 4 x £1.70 £6.80 + VAT = £7.48
Pack of 6: 6 x £1.70 £10.20 + VAT = £11.22

CT7001 £16.50 + VAT = £18.15
This is the most sophisticated alarm clock IC on the market. Our data includes circuit for 6 digit clock using 3 x SP352.

MMS316N £15.00 + VAT = £16.50

Data supplied with all devices.
Also available separately at 10p per device.
NO P. & P. CHARGE for U.K. orders. Overseas P. & P. 50p.

SINTEL, 53 ASTON STREET, OXFORD

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!
Tick or state subject of interest. Post to the address below.

- | | | | | | | | |
|---|--------------------------|--------------------------------------|--------------------------|---|--------------------------|---|--------------------------|
| Practical Radio and Electronics (Technical) | <input type="checkbox"/> | Electronic Engineering | <input type="checkbox"/> | C. & G. Radio, TV Electronics, Mechanics | <input type="checkbox"/> | C. & G. LI Installations and Wiring | <input type="checkbox"/> |
| Electronic Engineering | <input type="checkbox"/> | Television Maintenance and Servicing | <input type="checkbox"/> | Radio Amateurs | <input type="checkbox"/> | General Electrical | <input type="checkbox"/> |
| General Radio and TV Engineering | <input type="checkbox"/> | General Radio and TV Engineering | <input type="checkbox"/> | Practical TV | <input type="checkbox"/> | Engineering | <input type="checkbox"/> |
| Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> | Slide Switch | <input type="checkbox"/> | Colour Television | <input type="checkbox"/> | Society of Engineers (Electrical Engineering) | <input type="checkbox"/> |
| | <input type="checkbox"/> | Miniature Neon Lamps | <input type="checkbox"/> | Computer Electronics | <input type="checkbox"/> | Electrical Installations and Wiring | <input type="checkbox"/> |
| | <input type="checkbox"/> | | <input type="checkbox"/> | C. & G. LI Radio TV Servicing cert. | <input type="checkbox"/> | C. & G. Electrical Technicians (Prim. y) | <input type="checkbox"/> |
| | <input type="checkbox"/> | | <input type="checkbox"/> | Post Master General 1st & 2nd class cert. | <input type="checkbox"/> | C. & G. Telecommunications | <input type="checkbox"/> |
| | <input type="checkbox"/> | | <input type="checkbox"/> | C. & G. Electrical Engineering Practise | <input type="checkbox"/> | | <input type="checkbox"/> |

To B.I.E.T. BPE 05 Aldermaston Court, Reading RG7 4PF QK **BPE 05**

NAME (Block Capitals Please)
ADDRESS


Other subjects Accredited by C.A.C.C.

Age Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

You've asked for it!

Time and again we are asked for reprints of Wireless World constructional projects: tape, disc, radio, amplifiers, speakers, headphones. Demand continues long after copies are out of print. To meet the situation we have collected fifteen of the most sought after designs and put them in one inexpensive book. And we've updated specifications where necessary to include new components which have become available. A complete range of instruments is presented, from the Stuart tape recorder and Nelson-Jones f.m. tuner, through the Bailey, Blomley and Linsley Hood amplifiers, to the Bailey and Baxandall loudspeakers – some of which have been accepted as standard in the industry.

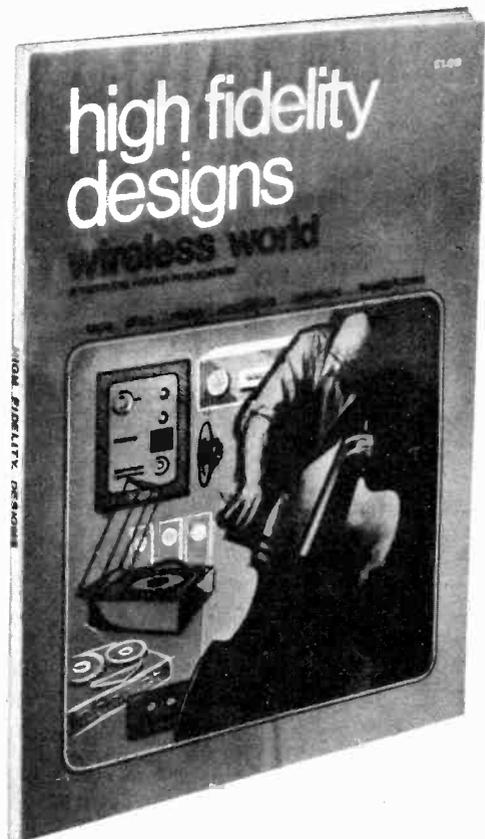

high fidelity designs

£1 from newsagents and bookshops. A book from

Wireless World

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50, 3 for ONLY 55p + p & p 30p
SPECIAL. As above PLUS Power Transistors ONLY 55p each + p & p 15p
STABILISED POWER MODULES
 Completed with circuit diagrams, etc. 99p each + p & p 15p
FAXOLINE BOARDS 7½ x 9" approx. 4 for 80p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½ x 4" approx. 2 for 55p

DECON-DALO 33pC Marker

Eth resistant printed circuit marker pen 90p each

VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 0.1 metric 55p

REPANCO CHOKES & COILS

RF Chokes
 CH1 2.5mH 25p CH2 3.0mH 25p
 CH3 7.5mH 25p CH4 10mH 25p
 CH5 1.5mH 25p

COILS

DRX1 Crystal set 31p DRB2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 7p
 2" Cores & Formers 8p

SWITCHES

1P/DT Toggle 25p 8P/ST Toggle 18p

FUSES

1" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
 QUICK-BLOW 4p ea. ANTI-SURGE 5p ea.

EARPHONES

Crystal 2.5mm plug 33p
 Crystal 3.5mm plug 33p
 8 ohms 2.5mm plug 22p
 8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223, 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007, 80 ohms Imp. Insertion loss 3dB £1.21

SELECTED RESISTORS

R1. Our mix, ½ watt carbon—50 for 55p

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	4"	3"	90p
BV2	11"	6"	3"	£1.20

ALUMINIUM BOXES

BA1	3½"	4"	1½"	42p
BA2	4"	4"	1½"	41p
BA3	4"	2½"	1½"	41p
BA4	5½"	4"	1½"	47p
BA5	4"	2½"	1½"	41p
BA6	3"	2"	1"	34p
BA7	7"	3"	2½"	86p
BA8	8"	6"	3"	84p
BA9	6"	4"	2"	64p

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)


Open Monday-Sat. 9-5.30 p.m. Tel. 61593

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.84

Chrome Finish Model 60 £1.50

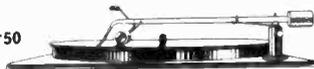

Ref. 36A Record/Styleus Cleaning Kit 28p

Ref. 43. Record Care Kit £2.35

Ref. 31. Cassette Head Cleaner 64p

Ref. 32. Tape editing Kit £1.64

Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p

Ref. 32A. Stylus Balance £1.36

Ref. J. Tape Head Cleaning Kit 51p

Ref. 34. Cassette Case £1.27

Ref. 56. Hi-Fi Stereo Hints & Tips 32p

ANTEX SOLDERING IRONS

X25, 25 watt £1.98

CCN 240, 15 watt £2.15

Model G, 18 watt £2.15

SK2. Soldering Kit £2.88

STANDS: ST1 £1.21. ST2 77p

SOLDER: 188WG Multicore 7oz 82p

228WG 7oz 82p. 188WG 22ft 78p

228WG Tube 22p

ANTEX BITS and ELEMENTS

Bits No.

102 For model CN240 ½"

102 For model CN240 ¾"

1100 For model CCN240 ½"

1101 For model CCN240 ¾"

1102 For model CCN240 1"

1020 For model G240 ½"

1021 For model G240 ¾"

1022 For model G240 1"

50 For model X25 ½"

51 For model X25 ¾"

52 For model X25 1"

ELEMENTS

ECN 240 £1.16 ECCN 240 £1.32

EG 240 £1.16 EX 25 £1.16

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No. Qty.	Description	Price
C1 250	Resistors mixed values approx. count by weight	0.65
C2 200	Capacitors mixed values approx. count by weight	0.65
C3 50	Precision Resistors 0.1%, 0.01% mixed values	0.65
C4 75	1/4 W Resistors mixed preferred values	0.55
C5 5	Pieces assorted Ferrite Rods	0.55
C6 2	Tuning Gangs, MW/LW VHF	0.55
C7 7	Pack Wire 50 metres assorted colours	0.55
C8 10	Reed Switches	0.55
C9 3	Micrn Switches	0.55
C10 15	Assorted Pots & Pre-Sets	0.55
C11 5	Jack Sockets 3 x 3.5m Standard Switch Type	2 x 0.55
C12 40	Paper Condensers preferred types mixed values	0.55
C13 20	Electrolytics Trans. types	0.55
C14 1	Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0.55
C15 4	Mains Slide Switches	0.55
C16 20	Assorted Tag Strips & Panels	0.55
C17 10	Assorted Control Knobs	0.55
C18 4	Rotary Wave Change Switches	0.55
C19 3	Relays 6—24V Operating	0.55
C20 4	Sheets Copper Laminate approx. 10" x 7"	0.55

PLUGS AND SOCKETS

SOCKETS

P8 35 DIN	2 Pin (Speaker)	0.06
P8 36 DIN	3 Pin	0.10
P8 37 DIN	5 Pin 180°	0.10
P8 38 DIN	5 Pin 240°	0.10
P8 39	Jack 2.5mm Switched	0.09
P8 40	Jack 3.5mm Switched	0.10
P8 41	Jack 1" Switched	0.17
P8 42	Jack Stereo Switched	0.28
P8 43	Phono Single	0.08
P8 44	Phono Double	0.10
P8 45	Car Aerial	0.08
P8 46	Co-Axial Surface	0.09
P8 47	Co-Axial Flush	0.14

INLINE SOCKETS

P8 21	D.I.N. 2 Pin (Speaker)	0.13
P8 22	D.I.N. 3 Pin	0.17
P8 23	D.I.N. 5 Pin 180°	0.17
P8 24	D.I.N. 5 Pin 240°	0.17
P8 25	Jack 2.5mm Plastic	0.10
P8 26	Jack 3.5mm Plastic	0.12
P8 27	Jack 1" Plastic	0.24
P8 28	Jack 1" Screened	0.28
P8 29	Jack Stereo Plastic	0.22
P8 30	Jack Stereo Screened	0.28
P8 31	Phono Screened	0.14
P8 32	Car Aerial	0.15
P8 33	Co-Axial	0.17

PLUGS

P8 1	D.I.N. 2 Pin (Speaker)	0.11
P8 2	D.I.N. 3 Pin	0.12
P8 3	D.I.N. 4 Pin	0.15
P8 4	D.I.N. 5 Pin 180°	0.14
P8 5	D.I.N. 5 Pin 240°	0.15
P8 6	D.I.N. 6 Pin	0.15
P8 7	D.I.N. 7 Pin	0.10
P8 8	Jack 2.5mm Screened	0.09
P8 9	Jack 3.5mm Plastic	0.12
P8 10	Jack 3.5mm Screened	0.13
P8 11	Jack 1" Plastic	0.18
P8 12	Jack 1" Screened	0.18
P8 13	Jack Stereo Screened	0.28
P8 14	Phono	0.06
P8 15	Car Aerial	0.15
P8 16	Co-Axial	0.10

CABLES

CP 1	Single Lapped Screen	0.06
CP 2	Twin Common Screen	0.08
CP 3	Stereo Screened	0.23
CP 4	Four Core Common Screen	0.08
CP 5	Four Core Individually Screened	0.30
CP 6	Microphone Fully Braided Cable	0.10
CP 7	Three Core Mains Cable	0.07
CP 8	Twin Oval Mains Cable	0.06
CP 9	Speaker Cable	0.04
CP 10	Low Loss Co-Axial	0.10

CARBON POTENTIOMETERS

Log and Lin		
47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M		
VC1	Single Less Switch	0.14
VC2	Single D.P. Switch	0.28
VC3	Tandem Less Switch	0.44
VC4	1K Lin Less Switch	0.14
VC5	100K Log anti-Log	0.44

HORIZONTAL CARBON PRESETS

0.1 watt 0.06 each
 100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

WORLD SCOOP

JUMBO

SEMICONDUCTOR PACK
 Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, I.C.s and Zeners. ALL NEW AND CODED.

APPROX. 100 PIECES
 Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

ONLY £2 P. & P. 20p.

EX-COMPUTER BOARDS—BY THE BOXFUL!

20 Boards packed with Semiconductors and other Electronic Components. Each board approx. size 8in x 7in. All known type numbers and easily recognisable.

FANTASTIC VALUE AT £2.20 per Box. P. & P. 52p.

SPECIAL PURCHASE

2N3055, Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able! 115W, T03, Metal Case.

OUR SPECIAL PRICE 8 for £1

LOW COST CAPACITORS

0.01µF 400V. 3p each
 500µF 50V. Elect. 10p each

RECORD STORAGE/CARRY CASES

7in EP, 18½in x 7in x 8in (50 records) £2.10
 12in LP, 13½in x 7½in x 12½in (50 records) £2.95

CASSETTE CASES

Holds 12, 10in x 3½in x 5in. Lock and handle, £1.30.

8-TRACK CARTRIDGE CASES

Holds 14, 13in x 5in x 6in. Lock and handle, £1.95
 Holds 24, 13½in x 8in x 5½in. Lock and handle, £2.70.

COLOURS: Red, black and tan, please state preference

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tapings 4V, 7V, 8V, 10V, 14V, 15V, 17V, 19V, 21V, 23V, 31V, 33V, 40, 50 and 25V 0-25V.

Type	Amps	Price	P. & P.
MT60/1	1	£1.93	30p
MT50/1	1	£2.42	35p
MT50/2	2	£3.20	40p

CARTRIDGES

ACOS GP91-18C, 200mV at 1.2cm/sec £1.16
 ACOS GP93-1, 280mV at 1cm/sec £1.65
 ACOS GP96-1, 100mV at 1cm/sec £2.65
 TTC J-2005, Crystal/Hi Output 99p
 TTC J-20 100 Crystal/Hi Output Compatible £1.10
 TTC J-200 CS Stereo/Hi Output £1.60
 TTC J-2105 Ceramic/Med. Output £1.64

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, ½ watt available in PAK 8 of 50 pieces, assorted into the following groups:—

R1	50 Mixed 100 ohms-820 ohms	40p
R2	50 Mixed 1K ohms-8.2K ohms	40p
R3	50 Mixed 10K ohms-82K ohms	40p
R4	50 Mixed 100K ohms-1 Meg. ohms	40p

THESE ARE UNBEATABLE PRICES—LESS THAN 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW-NOISE CASSETTES

C50, 32p; C90, 41p; C120, 62p

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

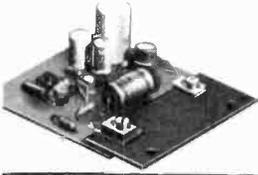

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE -3dB	Po = 2 WATTS	50 Hz-20KHz
SENSITIVITY for RATED O/P	Vs=25V, R1=8 Ω f=1KHz	75mV, RMS
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8 Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2-19
AL 20. 5 watts	£2-59
AL 30. 10 watts	£3-01

POWER SUPPLIES

PS 12. (Use with AL10 & AL20)	85p
PSM 80. (Use with also AL30 & AL50)	£3-25
FRONT PANELS PA 12 with Knobs	£1-00

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20)	£4-35
PA 100. (Use with AL30 & AL50)	£13-15

TRANSFORMERS

T461 (Use with AL10)	£1-38 P & P 15p
T538 (Use with AL20)	£1-93 P & P 15p
BMT80 (Use with AL30 & AL50)	£2-15 P & P 25p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with *Ceramic cartridges while the auxiliary input will suit most ↑Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.


Frequency response—	20Hz-50KHz (-3dB)
Bass control—	± 12dB at 60Hz
Treble control—	± 14dB at 14KHz
*Input 1. Impedance	1 Meg. ohm
Sensitivity 300mV	
†Input 2. Impedance	30 K ohms
Sensitivity 4mV	

LOOK FOR OUR
SEMICONDUCTOR ADVERTISEMENTS IN
Practical Wireless and *RADIO CONSTRUCTOR*

ALL PRICES INCLUDE VAT


The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested in a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls, transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 0.0mV into 1M. Freq. res. 20Hz-50KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14KHz.

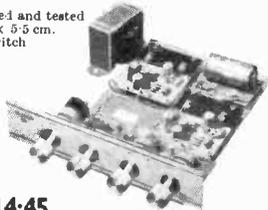

£14-45

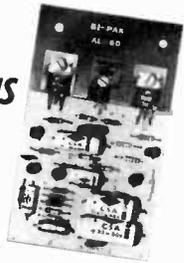NOW WE GIVE YOU
50w PEAK (25w R.M.S.) PLUS
THERMAL PROTECTION!
The NEW AL60
Hi-Fi Audio Amplifier
FOR ONLY £3.95




- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- 0.1% Distortion
- Distortion better than 1% at 1KHz
- Supply voltage 10-35 volts
- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

FULLY BUILT — TESTED and GUARANTEED

STABILISED POWER MODULE SPM80

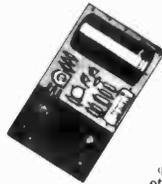

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address, Intercom Units, etc. Handbook available 10p PRICE £3-25

TRANSFORMER BMT80 £2-15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz—20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs: 1. Tape Head	1.25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1.5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than -60dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £13-15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25-30 FREE p. £ p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.

11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY

TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 130cm
Supplied complete with Fixing Bracket and plus 25p Control Switch. **£6-75** P. & P.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box

approx. 4" x 3" x 2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7-50 plus 10p.

"CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour.

Specification—Projector: 100W. convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour.

The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15-6in Liquid Wheel, £5-£20 + 75p cart.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7 or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Our Price **£2-75** plus 10p P. & P. Same model suitably wired for the Phillips Cassette £3 plus 10p P. & P.

7in x 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: **£1-60**. Free postage on this item.



- | | | |
|-------|------------------------------|---------------|
| UK65 | Transistor Tester | £1-86 |
| UK92 | Telephone Amp | £2-26 |
| UK115 | Hi-Fi Amp—8W | £4-50 |
| UK130 | Mono Control Unit | £4-15 |
| UK145 | Amp—1-5W | £3-81 |
| UK165 | RIAA Equalised Stereo Amp | £5-30 |
| UK195 | Mini-Amp—2W | £3-86 |
| UK220 | Signal Injector | £2-65 |
| UK230 | AM-FM Aer. Amp | £3-29 |
| UK275 | Mike Pre-Amp | £2-98 |
| UK300 | 4 Channel Radio Control T.X. | £6-61 |
| UK310 | Radio Control Receiver | £3-29 |
| UK515 | MW Radio Receiver | £7-92 |
| UK520 | AM Tuner | £4-60 |
| UK710 | 4 Channel A.F. Mixer | £12-59 |
| UK715 | Photoelectric Cell Switch | £9-97 |
| UK835 | Guitar Pre-Amp | £4-98 |
| UK875 | Cap. Discharge Ignition | £13-19 |
| UK915 | R.F. Amp 12-170MHz | £2-86 |
| UK935 | Wide Band Amp 20Hz to 150MHz | £2-86 |

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in x 3 1/2in x 1 1/2in. This converter supplies 6, 7 or 9 volts and is transistor regulated. A real money saving device for **£2-50**. 10p P. & P.

"C.300" DISCO CONTROL PACK

A control unit which when connected to twin decks makes a disc of professional quality. We supply a smart front panel which incorporates controls, switch and input sockets. The control module, I.C. construction incorporating mixing, pre-amp and headphone listening amplifier. The power pack enables this unit to work from the standard mains. * Inputs include Mic, Tape/Cassette and Twin Decks. * Controls include Mic, Tape, Each Deck, Mono, £14. Stereo, £17 plus 20p cart.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18-50** plus 38p P. & P.

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. **£1-75** plus 13p P. & P.

200/250V MAINS RELAY

Heavy duty contacts. 2,500Ω coil. All new and unused D.P.D.T. Mains relays 50p + V.A.T. Carr. Free. Special quantity price: **£40** per 100 relays.

MINI LOUDSPEAKERS

2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P. & P. on each L.S.


EnCase ENVIRONMENTAL HOUSING

A cleverly designed protected polycarbonate enclosure... weatherproof, hoseproof and damp and dust protecting. It's high impact strength will withstand rough handling. The seven sizes can interconnect and any case will extend vertically or horizontally or both while maintaining full protection. Send for new catalogue. Many extras available incl hinges, etc.

EnCase includes chassis, retaining screws, cover, gasket and cover retaining screws, price includes P. & P and VAT.


ENA	7 1/2" x 7 1/2" x 5"	£4-93
ENB	11" x 7 1/2" x 5"	£6-33
ENC	15" x 7 1/2" x 5"	£8-43
END	11" x 11" x 5"	£8-62
ENE	15" x 11" x 5"	£11-05
ENF	22" x 11" x 5"	£15-30
ENG	22" x 15" x 7"	£21-18

Prices correct to 1st May

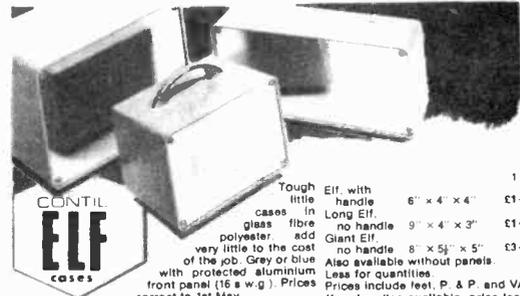

Tough Elf, with little handle 6" x 4" x 4" **£1-92** **£1-76**
cases in Long Elf.
glass fibre no handle 9" x 4" x 3" **£1-98** **£1-92**
polyester add Giant Elf.
very little to the no handle 8" x 5 1/2" x 5" **£3-19** **£3-08**
of the job. Grey or blue with protected aluminium front panel (16 g w g). Prices correct to 1st May. Also available without panels. Less for quantities. Prices include test, P. & P. and VAT. If no handles available, price less 9p.

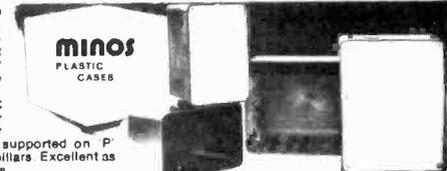
A smart miniature case in tough, rigid, high-gloss black A.B.S. Front panels in either aluminium or white PVC/Steel.



Built-in slots for PC cards, dividers, or screens. Chassis or PC boards can be supported on P clips from internal pillars. Excellent as encapsulation boxes.

M2	65mm x 100mm x 50mm 2 1/2" x 3 1/2" x 2"	51p 45p
M3	100mm x 130mm x 50mm 3 1/2" x 5" x 2"	67p 58p

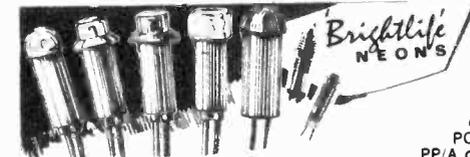
Prices include P. & P. and VAT. Less for quantities. Also available without panel and screws. Minimum order £1. Prices correct to 1st May.



Brightlife neons, illustrated are PC/A or C, PC/G or P, PP/A or B, Q & S, are brighter and give an average of 25,000 hrs. life. The 0.375" dia. are red or white. The 0.375" dia. are red, amber or white; these have 3 cap shapes and all may be supplied for 115, 240V or the PP neons in 110, 240 and 440V with 6" or 30" leads. Send for details in new catalogue.

dia	leads	volts	10 off	100 off
PC/A to 1	6"	110 or 160-260	17 1/2p	16 1/2p
PC/A to 1	30"	110 or 160-260	19 1/2p	18 1/2p
PP/A	6"	110 or 160-260	17 1/2p	16 1/2p
PP/A	30"	110 or 160-260	19 1/2p	18 1/2p
Q type	none	110 or 160-260	29p	27p
S type	none	160-260	23p	21p

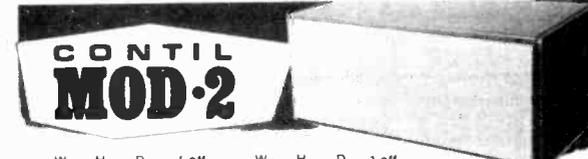P. & P. inc. any quantity, then add 10% VAT. Minimum quantity each type 10 off. Prices correct to 1st May.



A	4.5"	3"	6.5"	£3-60	M	4.5"	3"	13"	£4-44
B	4.5"	7"	6.5"	£4-44	N	4.5"	7"	13"	£5-44
C	4.5"	10"	6.5"	£4-91	O	4.5"	10"	13"	£6-91
D	9"	3"	6.5"	£4-91	P	9"	3"	13"	£5-44
E	9"	7"	6.5"	£5-44	Q	9"	7"	13"	£6-91
F	9"	10"	6.5"	£6-28	R	9"	10"	13"	£8-41
G	13"	3"	6.5"	£5-44	S	13"	3"	13"	£6-91
H	13"	7"	6.5"	£6-28	T	13"	7"	13"	£8-41
I	13"	10"	6.5"	£6-91	U	13"	10"	13"	£10-20
J	18"	3"	6.5"	£6-28	V	18"	3"	13"	£8-41
K	18"	7"	6.5"	£8-41	W	18"	7"	13"	£10-20
L	18"	10"	6.5"	£10-20	X	18"	10"	13"	£12-21

Woodgrain D at £5-44, E & G at £6-28, H at £6-91. Includes screws, feet, chassis, according to size, and P. & P. and VAT. Prices correct to 1st May.

WEST HYDE

WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRES., NORTHWOOD HILLS, MIDD. HA8 1NN. Tel: Northwood 24941 or 28732 Telex: 923231

CRESCENT CATALOGUE

If you construct you should own one. Send 20p inc. carriage.

VAT

★ Please include 10% VAT on goods plus carriage.

PRICES INCLUDE VAT
SUPERSOUND 13 HI-FI
MONO AMPLIFIER




A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 9db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. A.C. 200/250V.

PRICE £12.00 P. & P. 60p.

DE LUXE STEREO AMPLIFIER

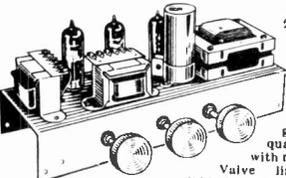

A.c. mains 200-240 volts. Using heavy duty fully integrated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2 ECL86 Triode Pentodes.

1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £10.40.** P. & P. 50p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7.1V and 9V and 12V at 1 amp on load.

Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" x 3 1/4" x 2 1/4". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £5 P. & P. 35p.

HI-GRADE COPPER LAMINATE BOARDS. 8" x 6". Five for 60p plus 30p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10-20-30-30-30, at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. **Price £2.31.** P. & P. 40p

FEW ONLY. High grade mains transformers with grain orientated lamination. Primary 200/240 secondary 18-5 volts at 0-5 amps and 4-6 volts at 0-3 amps. Size 2 1/2" x 2 1/4" W. x 2 1/2" overall. **£1.25 plus 25p P. & P.**

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V Sec. 9-0-9 at 500mA. **£1.10 P. & P. 25p.** Pri. 200/240V Sec. 12-0-12 at 1 amp. **£1.21 P. & P. 25p.** Pri. 200/240V Sec. 10-0-10 at 2 amp. **£1.82 P. & P. 25p.**

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U., Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/4 in. Brand new—complete with instructions. **Price £1.** P. & P. 15p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS, covering theory, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed. Diode Equivalents 80p
 Transistor Equivalents 90p
 Transistor Characteristics **£1.20**
 All three together **£2.90** **POST FREE**

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. **ONLY 40p.** Post 5p.

NEW ISSUE—Thyristor, Triac, Diac, etc. encyclopedias 95p Post Free.

Open 9.30-5.30 Mon. to Fri.
 9.30-5.30 Sat. Closed Wed.

A few minutes from South Wimbledon Tube Station.

FOR PERSONAL CALLERS ONLY! Limited number of Stereo Radiogram chassis covering LW/MW/FM bands. Mono radio and stereo gram. Overall size approx. 16 1/2" W. 6 1/4" H. 8" D. 4 Watts per channel output. **ONLY £16.50.**

SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. **ONLY £8.00** plus P. & P. 60p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, EL86B, AT80, etc. or B.S.R. C123, C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in x 14 1/2in x 3 1/2in high (approx. 7 1/2in high, including rigid smoked acrylic cover). P. & P. 70p. **Now only £4-95**

8 pole 3 way 2 bank low loss Xaley type switches 14" sections. Standard spindle. 2 switches 86p + 10p P. & P.

LATEST ACOS GP91/180 Mono Compatible Cartridge with 1/6 stylus for LP/EP/78. Universal mounting bracket. **£1.50.** P. & P. 15p.

SONOTONE STEREO COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. **ONLY £2-30.** P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£2-30.** P. & P. 15p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. **£1-63.** P. & P. 15p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment **£1-50.** P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6 h. Ready built and tested. **PRICE £5-00.** P. & P. 50p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £8-30.** P. & P. 60p.

SPECIAL OFFER!!
HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high x 10in wide x 6in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 16 ohm impedance.

Our Price £9-25 Carr. 75p

CABINET AVAIL. SEPARATELY £4-95. Carr. 65p. Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. **£7-15.** Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely BRAND NEW, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE **£3-85** P. & P. 40p

LOUDSPEAKER BARGAINS

5in 3 ohm £1-25. P. & P. 15p. 7 x 4in 3 ohm £1-40. P. & P. 20p. 10 x 6in 3 or 15 ohm £2-10. P. & P. 30p. E.M.I. 8 x 3in 3 ohm with high flux magnet £1-70. P. & P. 20p. E.M.I. 12 1/2 x 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm £3-50. P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two built-in tweeters and crossover network £4-65. P. & P. 30p.

EMI CERAMIC MAGNET HEAVY DUTY TWEETER. approx. 3in. Av. 3 or 8 or 15 ohms. **£1-25 plus 20p P. & P.**
BRAND NEW. 12in 15W H/D Speakers, 3, 8 or 15 ohm (state which). Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly **£9-90.** Guitar models: 25w **£9-90.** 35w **£11-00.** P. & P. 45p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticised cone surround, 8 ohm impedance. **£3-70.** P. & P. 35p.

Also available specification as above but size 10" x 6" **£2-70 P. & P. 35p.**


12in "RA" TWIN CONE LOUSPEAKER 10 watts peak handling, 3 or 8 or 15 ohm (state which). **£2-95.** P. & P. 35p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. **Only £6-55 each.** P. & P. 34p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-16,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £3-30.** P. & P. 25p.

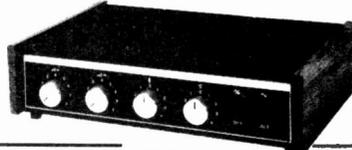HARVERSONIC SUPER SOUND
10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact Design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodized aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 6 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1-0 amp. Overall size—12" wide x 8" deep x 2 1/2" high.

Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.


PRICES AMPLIFIER KIT, £11-55 P. & P. 125p. (Magnetic input components 33p extra)
POWER PACK KIT, £3-50 P. & P. 35p.
CABINET, £3-50 P. & P. 35p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, **£25-10.** Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

3-VALVE AUDIO AMP. HA34 MK II


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£8-00.** P. & P. 45p.

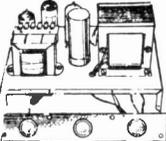

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£5-00.** P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

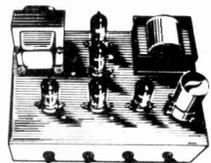A stylishly finished non-aerial amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.



Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving loud lift and cut. Valve line-up 2 EL84s, ECC83, E868 and EZ80 rectifier. Simple instruction booklet 15p plus S.A.E. (Free with parts). All parts sold separately. **ONLY £9-00.** P. & P. 60p. Also available ready built and tested **£13-00.** P. & P. 70p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 5 1/2in. wide. Our price £1-10 yd length. P. & P. 10p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W. 19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V

SHROUDED TYPE
 0.5 KVA (21 amp) (MAX) £10 00
 1 KVA (5 amp) (MAX) £14 70
 2 KVA (10 amp) (MAX) £28 10
 3 KVA (15 amp) (MAX) £31 25
 4 KVA (20 amp) (MAX) £32 50
 37.5 amp (MAX) £102 50
CARRIAGE AND PACKING EXTRA



L.T. TRANSFORMERS

All primaries 220-240V

Type No.	Sec. Taps	Price Post
1	30, 32, 34, 36V at 5A	£6.90 + 45p
2	30, 40, 50V at 5A	£9.15 + 60p
3	10, 17, 18V at 10A	£7.30 + 50p
4	6, 12V at 20A	£8.60 + 60p
5	17, 18, 20V at 20A	£9.15 + 60p
6	6, 12, 20V at 20A	£8.65 + 60p
7	12, 20, 24V at 10A	£6.75 + 50p
8	4, 6, 24, 32V at 12A	£8.60 + 60p
9	6 and 12V at 10A	£4.30 + 40p

VOLTAGE CHANGING TRANSFORMER


M.f.g. to highest W.D. spec. Auto wound, and tapped 0-130-160-200-250 at least 2kVA. Can also be used as 230-240V input, 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30-40-50-70-90V at 10 amps. Weight 40lb, length, 260mm, height 190mm, width 230mm. In original maker's wooden case, £8. Carr. £1.

300 VA ISOLATING TRANSFORMER

115/230-230V isolating. Screened. Primary two separate 0-115V for 115 or 230 volts. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb.
SPECIAL OFFER PRICE £5. Carr. 80p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2. Post 20p. (Total incl. VAT and Post £2.42).

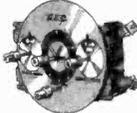

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted diecast case. Tested and in perfect condition £4.75. Post 25p.



FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp. 250 volt. Price 75p. Post 15p.



A.C. MOTOR 'Mfg. by AEI'

Smooth running, powerful, continuously rated, reversible motor. 230/250V a.c., 50 cycle 1/50 H.P., RPM 900, 0.25A. £3.50 post 50p.



METERS NEW! 2 1/2 in.

Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, Voltmeter 0-300V A.C. All types £2. Post 15p.



230/240 VOLT A.C. EXTRACTOR FAN KIT

Comprising of impeller, continuously rated motor, motor housing and fixings as illustrated. Price £1.75. Post 25p. (Total incl. VAT and Post £2.20).



MINIATURE UNISELECTOR SWITCHES

2 Bank, 12 position, 24 volt D.C. operation, full wiper with ancillary contacts. NEW Price £2.50. Post 20p. As above but with 5 Bank, 12 position. Price £3.50. Post 20p.



Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
 Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30. Post 30p.

INDUSTRIAL KIT
 Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. 1/2 output of Hy-Light. Price £12.00. Post 50p.

HY-LIGHT STROBE MK III
 For use in large rooms, halls and utilises a silica tube. Printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12. Post 50p.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

● Variable speed from 1-13 flash per sec.
 ● Reactor control circuit producing an intense white light. ONLY £20. Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Light Kit including reflector £5.75. Post 25p.
 Super Hy-Light case including reflector £8. Post 60p.

7-INCH POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 55p. Post 15p.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel, 100 watt lamp, 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p.
6 INCH COLOUR WHEEL
 As used for Disco lighting effects, etc. Price £4.50. Post 30p.



BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16. Post £1.
 Spare bulb £7. Post 40p.



BLACK LIGHT FLUORESCENT U.V. TUBES
 4ft 40 watt. Price £5.50. Post 30p. 2ft 20 watt, £4.25. Post 25p. (For use in standard bi-pin fittings.)

MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube, £1.70. Post 25p. (9in and 12in measures approx.)

AUTO FADE COLOUR BLEND MODULE

Will control up to 750V. of lighting. Automatic fade-up, fade-down at a manually pre-selected timing, which may be varied between 1 second to 1 minute. Based on 10 amp triac for maximum reliability. Ready built with switch and Time Control, on 4 1/2 x 5 1/2 glass P.C. board. Three modules or more can be sequenced to obtain fantastic colour blending effects. Price £12.50. Post 30p per module.

PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.
 4 cam model. £2.50 post 30p.
 6 cam model. £3.25 post 30p.
 12 cam model. £4.00 post 35p.
 6 cam model. 3 r.p.m. £3.25 post 30p.



TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS
 10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SCI46D 10 amp, 400 PIV, £1. Post 5p. Type SCI46E 10 amp, 500 PIV, £1.30. Post 5p. (Inclusive of data and application sheet.) Suitable Base 18p.

All prices are subject to

10% VAT. (10p in the £)

To all orders add 10% VAT to total value of goods including carriage/packaging.



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/ohm £1-15. Post 10p.
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/ohm £1-60. Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £2.35. Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats, 22p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1) Coil ohms	1	2	3	4
Col. (2)	52	4-6	6M	60p*
Working d.c. volts	58	5-9	6 c/o	80p*
Col. 3	150	4-9	2 c/o	70p*
Contracts	185	8-12	6M	60p*
Col. (4)	308	9-14	4 c/o	75p*
Price	700	16-24	4M/4B	60p*
HD =	700	16-24	4 c/o	80p*
Heavy duty	700	6-12	1 c/o HD	70p*
	700	20-30	6 c/o	50p*
	2,500	31-43	2 c/o HD	60p*
	2,500	36-45	6M	60p*
	2,400	30-48	4 c/o	60p*
Incl. Base	5,800	24-26	2 c/o	60p
All prices incl. P. & P.	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

6 VOLT D.C. 1 make contacts 35p. Post 5p.
9 VOLT D.C. 2 make contacts 75p. Post 5p.
3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.
12 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 5p.
24 VOLT D.C. 3 c/o 75p. Post 5p.



ITT LOW PROFILE RELAY
 500 ohm coil, 12-24 volts D.C., 4 c/o. Price 85p. Post 5p each.

CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o, 70p post paid.
100 VOLT A.C. 2 c/o sealed type, octal base £1. Post 10p.

24 VOLT A.C. Mfg. by ITT. 2 h.d. c/o contacts. 55p. Post 5p.

240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C. 10 amp h.d. c/o contacts. Octal pin base. (Similar to illustration below). Price 75p. Post 5p.

HEAVY DUTY A.C. SEALED RELAYS
 230/240 V. 2 c/o. 20 amp contacts. 110 Volt. 2 c/o 20 amp contacts. Either type £1-25. Post 10p.



DRY REED RELAYS

Mfg. by ERG, 12 volt d.c. encapsulated. Single c/o 65p, post paid. 2 c/o 85p, post paid. STC 280 ohm coil/6/12V d.c. 3 make metal shrouded. 60p post paid. Other types available, state your requirement.

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amp/240V A.C. Black knob in. Fixing hole 1/2 in. ONE bank 40p; TWO bank 40p; THREE bank 50p. Quote for quantity.



HIGH VISIBILITY PANEL MOUNTING LED'S

0.25 inch mounting, 0.16 inch lens. Typical parameters 2V, 20M amps all type. Supplied complete with snap in mountings and data. Red 4 for £1, Green 3 for £1, Yellow 3 for £1. Post 5p. (in order) (£1).

VERY SPECIAL OFFER

MINIATURE ROLLER MICRO SWITCH. 5 amp. c/o contacts. Mfg. BONEBRA. NEW. Price 10 for £1.50. Post 10p. (Min. order 10).



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.



24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two approx. 1lb pull 1 inch travel. 6 x approx. 4oz. pull 1 inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2.50 P + p 60p. **ABSOLUTE BARGAIN.**

Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET LONDON WC2H 7JJ
 Phone 01-437 0576

SERVICE TRADING CO

All Mail Orders—Callers—Ample Parking
Dept. PE7, 57 BRIDGMAN ROAD CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.



and make no mistake

People ask Laskys because of their keenly competitive pricing policy. People ask Laskys because of their staggering range of choice. People ask Laskys because every item they sell is fully guaranteed for a year with no sneaked in charges for labour or parts. People ask Laskys because they give advice that can be trusted.

AUDIOTRONIC Model ATM1
Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.

OUR PRICE £3.25 P&P 15p

AUDIOTRONIC Model ATM5
Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0/3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). 0.300 uA/0.300mA DC. Resistance: x 10 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.

OUR PRICE £3.50 P&P 15p

MODEL TH12
20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/100uA/25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.

OUR PRICE £5.95 P&P 15p

HIOKI Model 720X VOM
A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0.5/50uA/250mA. 0.20k/2 Megohms.

OUR PRICE £5.97 P&P 20p

MODEL PL436
20,000 opv DC. 8000 opv AC. Mirror scale. 0/1/12/30/120/60V DC. 3/30/120/600V DC. 50/600uA/60/600mA. 10/100k/1 Meg/10 Meg Ohm. -20 to +46dB.

OUR PRICE £6.97 P&P 15p.

U4323 MULTIMETER
20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance x 10, x 100, x 1,000, x 10,000 (50k). 50k(1, 50k)(2) centre scale. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.

OUR PRICE £7.00 P&P 20p

MODEL HIOKI 730X
30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/1200V AC. 60 uA. 30mA/300mA. 2K/200K. 2 Meg Ohm. -10 to +63dB.

OUR PRICE £7.50 P&P 15p

MODEL TE300
30,000 opv. Mirror scale. Overload protection. 0/0.5/3/15/60/300/1200V DC. 0/6/30/120/600/1200V AC. 0/300uA/60mA/60mA/300mA/600mA. 0/8k/80k/800k/8 Meg ohms. -20 to +63dB.

OUR PRICE £7.50 P&P 15p

U4324 MULTIMETER
High sensitivity, overload protected. 20,000 opv. Ranges: 0.6/1/2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.

OUR PRICE £8.00 P&P 20p

U435 MULTIMETER
20,000 opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 5/25/100mA/0.5/2.5A AC. Resistance: 0.3/3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.

OUR PRICE £8.75 P&P 20p

U91 Clamp VOLT AMMETER
For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500mA. Accuracy 4%. Size 283 x 34 x 36mm. Complete with carrying case, leads and fuses.

OUR PRICE £10.50 P&P 20p

TMK MODEL TW50K
46 ranges, mirror scale. 50kV DC. 50kV AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000V AC. AC Volts: 1.5/3/5/10/25/50/125/250/500/1000V DC. DC current: 25/50/100/2.5/5/25/50/250/500mA/5/10A. Resistance: 10k/100k/1 Meg/10 Meg ohm. -20 to +81.5dB.

OUR PRICE £12.50 P&P 17p

U4312 MULTIMETER
extremely sturdy instrument for general electrical use. 66700V. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV/0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/6/15/50/60/600mA/1/1.5/6A DC. 0/1.5/6/15/60/150/600mA. 1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.

OUR PRICE £9.75 P&P 25p

MODEL 500
30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/5/10/50/100/250/500mA/500mA. 12A DC. 0/60k/6 meg/60 megohms.

OUR PRICE £13.95 Carr. paid
Leather case for above £1.75

HIOKI 750X VOLT-OHM-MILLIAMETER
43 ranges. 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1,200V DC. 0.0/0.1/0.2/0.5/1/2/5/10/20/300/600/1,200V AC. Current: 0.30/600mA/1.5/3/15/30/150/300mA/6A/12A. Resistance: 0-3/300k/3/30Megohms. Decibels: -10 to +17dB. Output: -0.3/6/15/30/60/120/300V. Accuracy: 3% DC. ± 4% AC. Sensitivity: 50,000 opv DC. 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.

OUR PRICE £11.95 P&P 40p

HIOKI Model 700X
100,000 opv. Overload protection. Mirror scale. 0.3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/50/150/300mA/6/12A DC. 2k/20k/200/20M Ohms -20 to +63dB.

OUR PRICE £14.95 P&P 20p

Model HT10084 MULTIMETER
Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/1.5/5/25/500/1,000V DC. 2.5/10/50/250/1,000V AC. DC resistance: 0-20/200k/2/20 Meg. ohms. DC current: 10/250mA/2.5/25/250 mA/10A. AC current: 0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.

OUR PRICE £17.50 P&P 40p

MODEL AS.1000 VOM
100,000 opv. Mirror scale. Built-in meter protection. 0.3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA. 12 Amp. 0.2K. 200K/2M/200 Meg Ohm. -20 to 17dB.

OUR PRICE £17.50 P&P 20p.

TMK 100K LAB TESTER
100,000 opv. 6 1/2" scale. Buzzer short circuit check. Sensitivity 100,000 opv DC. 5kV AC. DC Volts: 0.5/2.5/10/50/250/1000V AC. 1/10/50/250/500/1000V DC. current 10/100uA/10/100/500mA/2.5/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: -10 to +89dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.

OUR PRICE £19.95 P&P 25p

370WTR MULTIMETER
Features AC current ranges. 20,000 opv. 0/0.5/2.5/10/50/250/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.

OUR PRICE £19.95 P&P 25p

KAMODEN 72.200 Multitester
High sensitivity tester. 200,000 opv Overload protected. Mirror scale. Ranges: 0/0.6/3/30/120/600/1200V DC. 0/3/12/60/300/1120V V AC. 0/6uA/1.2mA/12A DC. 600mA/1/2A DC. 0/12A AC. -20 to +63dB. 0.2k/200k/2 Meg/200 Megohms.

OUR PRICE £22.50 P&P 30p

U4317 MULTIMETER
High sensitivity instrument for field and laboratory work. Knife edge pointer. 86mm. mirror scale. Ranges: 100mV/0.5/1/5/10/25/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. 0.25/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

OUR PRICE £15.00 P&P 20p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter
Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750uA/1.5/3/7.5/15/30/75/150/300/750mA/1/1.5/3/7.5/15/30/75V. 7.5A AC. 0/3/7.5/15/30/75/150/300/750mA. 1.5/3/7.5A AC. 0/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V DC. 0/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.

OUR PRICE £49.00 P&P 50p

TE65 VALVE VOLT METER
28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. AC Resistance up to 1000 Megohms. 200/240V AC operation. Complete with probe and instructions.

OUR PRICE £17.50 P&P 30p
Additional probes available: RF £2.12, HV £2.50

MODEL AF.105 VOM
50,000 opv Mirror scale Meter protection 0 3 12 60 120 300 600 1200V DC. 0 6 30 120 300 600 1200V AC. 0.30uA 6 60 300 mA 12 Amp. 0.1k 1m 10m 100 Meg Ohms -20 to 17dB.

OUR PRICE £12.50 P&P 20p.

L83 TRANSISTOR TESTER
Tests ICO and B. PNP/NPN. Operates from 9V battery. Instructions supplied.

OUR PRICE £3.95 P&P 20p

L84 TRANSISTOR TESTER
Tests PNP or NPN transistors. Auto indication. Operates on two 1.5V batteries. Complete with instructions etc.

OUR PRICE £4.50 P&P 20p

U4341 Multimeter & Transistor Tester
27 ranges. 16,700 opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 1.5/7.5/30/150/300/600V AC. Current: 0.06/0.6/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.08/0.6/2/6/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 90mm.

OUR PRICE £10.50 P&P 20p

S100TR MULTIMETER TRANSISTOR TESTER
100,000 opv. Mirror scale. Overload protected. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/6/30/120/600/1200V AC. 0/12/600uA/12/300mA/6/12A DC. 0/10k/1 Meg/100 Meg. -20 to +50dB. 0.01-0.2 MFD. Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.

OUR PRICE £19.95 P&P 25p

KAMODEN HMG500 insulation resistance tester
Range 0-1,000 Megohms. 500V. Battery operated. Wide range clear meter 4" x 4". COME with deluxe carrying case, batteries and instructions.

OUR PRICE £19.95 P&P 30p

C15 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25; HORIZ. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000uscc. Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V AC.

OUR PRICE £39.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE
5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2uscc. to 100 milli-sec/cm. Free running time base. 50Hz-1MHz. Built-in time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.

OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID OIP METER
Transistorised. Operates at Grid Dip. Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.

OUR PRICE £19.95 P&P 20p

Also see following pages

ALL PRICES EXCLUDE VAT

SWR METER Model SWR3
Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedance 52 Ω . Input current 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.
OUR PRICE £4.25 P&P 25p

AT201 Decade ATTENUATOR
Frequency range 0-200kHz. Attenuator 0-111dB, 0.1dB steps. Impedance 600 ohms. Input power maximum 30dBm. Size: 180 x 90 x 55mm.
OUR PRICE £12.50 P&P 37p

TRANSISTORISED L.C.R. A.C. BR. 8 MEASURING BRIDGE
A new portable bridge offering excellent range and accuracy at low cost. Resistance 0.1 ohm-11.1 megohm \pm 1% inductance: 6 ranges. 1 microhenry-111 henries \pm 2%. Capacity: 6 ranges. 10pF-1110 mfd \pm 2%. Turns Ratio: 6 ranges. 1:1-1000:1 11100 \pm 1%. Bridge Voltage at 1.000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 7 1/2" x 5" x 2".
OUR PRICE £25.00 P&P 25p

TE16A TRANSISTORISED SIGNAL GENERATOR
5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.
OUR PRICE £8.97 P&P 25p

MODEL TE20 RF SIGNAL GENERATOR
Six bands, 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy \pm 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.
OUR PRICE £17.50 P&P 40p

TE-200 RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable RF attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions.
Size 140mm x 215mm x 170mm.
OUR PRICE £17.50 P&P 30p

TE22 SINE SQUARE WAVE AUDIO GENERATOR
Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.
OUR PRICE £24.95 P&P 37p

ARF 300 AF/RF SIGNAL GENERATOR
All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £37.50 P&P 50p

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR
Range 19 220,000Hz Sine Wave 19-100,000 Hz Square Wave Output Sine or Square wave 10V p.p. to P. Size 180 x 90 x 90mm Operation 220/240V a.c.
OUR PRICE £19.95 P&P 37p

PS200 Regulated POWER SUPPLY UNIT
Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size 190 x 136 x 98mm.
OUR PRICE £19.95 P&P 25p

POWER RHEOSTATS
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wear. Continuous rating. Wide range available ex stock. Single hole fixing. 1/4" diameter shafts. Bulk quantities available.
25 WATT 10/50/100/250/500/1000 Ohms **£1.15** P&P 10p
50 WATT 10/25/50/100/250/500/1000 Ohms **£1.62** P&P 10p
100 WATT 1/10/25/50/100/250/500/1000/2500 Ohms **£2.34** P&P 15p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS
Excellent quality at low cost. Input 230V 50/60Hz. Output 0-260V. **MODEL S260 BENCH MOUNTING**
1A £10.50 30p
2.5A £12.00 35p
5A £17.50 37p
8A £30.35 50p
10A £33.75 75p
12A £29.50 75p
20A £85.00 125p
25A £95.00 125p
40A £120.00 150p
MODEL S260B PANEL MOUNTING
1A £10.00 30p
2.5A £12.00 35p

BVD5 Vernier TUNING DIAL
App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. deep including knob and coupling. 1/4" diam. shaft.
OUR PRICE £1.62 P&P 15p

240° Wide Angle 1mA METERS
MW 1-6 60x60mm **£6.50** P&P 15p
MW 1-8 80x80mm **£6.90** P&P 15p

CP110 CHASSIS PUNCH SET
Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.
OUR PRICE £3.00 P&P 40p

HITACHI FLUORESCENT LANTERN L1901
A portable battery operated lantern ideal for home motoring, camping etc. Approx. 10 tall. Provides brilliant light from 9 1.5v batteries (not supplied).
OUR PRICE £7.19 P&P 25p

KE630 3 Station INTERCOM
Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries.
OUR PRICE £5.25 P&P 50p

WALKIE TALKIES
LIMITED STOCKS

SKYFON 100mW
OUR PRICE £24.95 per pair
P302 Two Channel 300mW
OUR PRICE £52.50 per pair
P1003 Three Channel 1 Watt
OUR PRICE £71.25 per pair
P&P 50p per pair
N.B. Unlicencable in U.K.

DT56G DIGITAL CLOCK MECHANISM
Features 24 hour alarm setting, on/off switch and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.
OUR PRICE £5.95 P&P 30p

SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER
complete with printed circuit mounting board
OUR PRICE £2.35 P & P 15p

LH02S STEREO HEADPHONES
Light weight head phones with padded ear pieces, 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug.
OUR PRICE £1.97 P&P 30p

TE1018 Deluxe Mono High Impedance Headset.
Sensitive magnetic headset with soft ear pads. Impedance 2,600 ohms (600 ohms DCI). Frequency response: 200-4,000Hz.
OUR PRICE £2.25 P&P 30p

TE1035 Stereo HEADPHONES
Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.
OUR PRICE £2.60 P&P 30p

SHRDV MONO/STEREO HEADPHONES
Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.
OUR PRICE £4.97 P&P 30p

BH001 HEADSET and Boom Microphone
Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.
OUR PRICE £5.95 P&P 30p

EMI LDUSPEAKERS
Model 350 13 x 8" with single tweeter/crossover 20-20,000Hz 15 watts RMS. Available 8 or 15 ohms.
OUR PRICE £7.50 each P&P 37p
Model 450 13 x 8" with twin tweeter/crossover 55-13,000Hz 8 watts RMS. Available 8 or 15 ohms.
OUR PRICE £3.62 each P&P 25p

SPECIAL PURCHASE LIMITED QUANTITY!
Tannoy 12" DR 8 Bass Speakers
8 ohms 30 watt Heavy duty, ideal for Hi-Fi. P.A. Group
OUR PRICE £12.50 P&P 50p

SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS
High quality 2 way speaker systems. 25 Watts, 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 225mm. Approx. Wood grain finish with black fronts.
OUR PRICE £26.95 P&P £1

SPECIAL BARGAIN!! STEREO SOUND SPEAKERS
Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 368 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with Din lead.
OUR PRICE £12.95 P&P 50p

FM TUNER CHASSIS
6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.
OUR PRICE £8.95 P&P 20p
Stereo Multiplex Adaptor £5.95 extra

Model A1018 FM TUNER
6 transistor high quality unit - 3IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.
OUR PRICE £13.50 P&P 30p
Stereo multiplex adapter £5.95 extra.

SINCLAIR "SCIENTIFIC" CALCULATOR
8 digit display. Four functions plus logarithms to base 10, antilog, sine, cosine, tangent, arcSine, arcCosine and arcTangent. Complete with instructions, case and batteries. Rec. Price £49.00
OUR PRICE £44.50 P & P 25p plus VAT

SINCLAIR SYSTEM 2000 STEREO AMPLIFIER AND TUNER
OUR PRICE £28.50 P & P 60p

AMPLIFIER
Amplifier output 8 watts per channel RMS. Distortion less than 0.06%. Silicon transistors. Two pick-up plus radio and tape inputs. Tape output and scratch filter. Excellent Value.
OUR PRICE £28.50 P & P 60p

FM TUNER
Excellent selectivity and sensitivity. Twin dual-varicap tuning. 4 pole ceramic filter. 19 transistor stereo demodulator giving 4dB separation. Distortion 0.2% output. Fantastic Value.
OUR PRICE £28.50 P & P 60p.

SINCLAIR Project 80 Modules
Z60 Power Amplifier £5.45
Z60 Power Amplifier £6.95
Stereo 80 Pre-Amplifier £11.95
Active Filter Unit £6.95
Project 805 £26.95
P25 Power Supply £4.98
P26 Power Supply £7.98
P28 Power Supply £7.98
Transformer for P28 £4.05

SINCLAIR Project 80 Packages
2 x 240/Stereo 80/P25 £25.00
2 x 240/Stereo 80/P26 £27.75
2 x 260/Stereo 80/P28 £30.45
POST & PACKING 35p each.

MPT MIXER-PREAMPLIFIER
5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k-2.2k mV 600 ohms. Phono. Mag. 4mV 50k. Phono Ceramic 100mV 1 Meg. Output 250mV 100k.
OUR PRICE £8.97 P&P 20p

JOSTY KIT HIGH QUALITY CONSTRUCTION KITS
WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.
Post and Packing 15p per kit.
AF20 Mono amplifier £4.80
AF25 Mixer £3.60
AF30 Mono pre-amplifier £2.61
AF35 Emitter amplifier £2.27
AF80 0.5W mc. amplifier £5.22
AF85 Intercom £5.52
AF130 Mono amplifier £5.91
AT5 Automatic light control £2.58
AT25 Window wiper robot £5.82
AT30 Photo cell switch unit £5.70
AT50 400W triac light dimmer/speed control £4.80
AT55 200W triac light dimmer/speed control £6.90
AT60 1 channel light control £7.80
AT65 2 channel light control £14.55
GP304 Circuit board £4.94
GP310 Stereo pre-amplifier for use with 2 x AF310 £21.27
GP312 Circuit board £11.45
GU330 Tremolo unit £7.50
HF61 Diode detector £3.32
HF65 4W transmitter £3.71
HF75 FM receiver £2.87
HF10 FM tuner £15.81
HF310 Deluxe FM tuner £24.12
HF320 Decoder (HF310/325) £9.36
HF380 W/hf aerial amplifier £4.94
HF395 broadband aerial amp. £1.77
LF380 Quadraphonic device £11.36
M160 Multi-vibrator £4.50
M191 VU Meter £4.55
M192 Stereo balance meter £4.97
M1302 Transistor tester £8.45
NT10 Stabiliser 100mA, 9V £6.15
NT300 Stabilised p. supply £12.51
NT310 Voltage converter £4.50
NT315 Power supply 240V AC to 4.5V/15V DC, 500mA £9.57

Amateur Electronics by Josty Kit, the professional book for the amateur - covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.
OUR PRICE £3.30 (No VAT) P&P 25p plus VAT.

AE1 100mW output stage £1.50
AE2 Pre-amplifier £1.15
AE3 Diode receiver £1.82
AE4 Flasher 99p
AE5 Astable multi-vibrator 95p
AE6 Monostable multi-vibrator 95p
AE7 RC generator 97p
AE8 Bass filter 90p
AE9 PAF filter 90p
AE10 OCR filter 90p

1021 Stereo Listening Station
For balancing and gain selection of loudspeakers with 400W amplifier facility for stereo headphone switch. Two gain controls, speakers on-off slide switch, stereo headphone socket.
OUR PRICE £2.25 P&P 15p

AUDIOTRONIC LOW NOISE CASSETTES
TYPE 5 10 25
CR60 £1.57 £2.00 £7.08
C90 £2.24 £4.25 £10.00
C120 £2.73 £5.17 £12.24

AUDIOTRONIC Cr20 CASSETTES
TYPE 5 10 25
CR60 £5.32 £7.12 £19.12
CR90 £5.32 £10.46 £25.22

AUDIOTRONIC 8 TRACK CARTRIDGES
TYPE Each 5 10
40M 85p £4.00 £7.50
80M £1.15 £5.40 £10.25
P&P Cassettes 3p, Cartridges 5p each
OVER 10 of either POST FREE!

AUDIOTRONIC AH4101 Stereo Headphone Amplifier
All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs. Twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. (INPUTS 5mV and 100mV)
OUTPUT: 50mV per channel.
OUR PRICE £8.50 P&P 20p

EA41 REVERBERATION AMPLIFIER
Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverbation control. Walnut cabinet, 184 x 77 x 108mm.
OUR PRICE £7.50 P&P 20p

ALL PRICES EXCLUDE VAT


SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.80	10V DC	£3.65
100uA	£3.75	20V DC	£3.65
200uA	£3.70	50V DC	£3.65
500uA	£3.65	100-0-100uA	£3.75
50-0-50uA	£3.75	1mA	£3.65
100-0-100uA	£3.70	5mA	£3.65
1mA	£3.65	10mA	£3.65
5mA	£3.65	50mA	£3.65
10mA	£3.65	100mA	£3.65
500mA	£3.65	50V DC	£3.65
1A DC	£3.65	300V AC	£3.65
5A DC	£3.65	15V AC	£3.75
10A DC	£3.65	300V AC	£3.75
15V DC	£3.65	VU Meter	£3.90

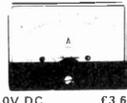

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm


50uA	£4.30	10V DC	£4.10
100uA	£4.25	20V DC	£4.10
200uA	£4.20	50V DC	£4.10
500uA	£4.15	100-0-100uA	£4.25
50-0-50uA	£4.25	1mA	£4.10
100-0-100uA	£4.20	5mA	£4.10
1mA	£4.10	10mA	£4.10
5mA	£4.10	50mA	£4.10
10mA	£4.10	100mA	£4.10
500mA	£4.10	50V DC	£4.10
1A DC	£4.10	300V DC	£4.10
5A DC	£4.10	15V AC	£4.20
10A DC	£4.10	300V AC	£4.20
15V DC	£4.10	VU Meter	£4.40



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£3.95	10V DC	£3.80
100uA	£3.85	20V DC	£3.80
200uA	£3.80	50V DC	£3.80
500uA	£3.75	100-0-100uA	£3.85
50-0-50uA	£3.85	1mA	£3.70
100-0-100uA	£3.80	5mA	£3.70
1mA	£3.70	10mA	£3.70
5mA	£3.70	50mA	£3.70
10mA	£3.70	100mA	£3.70
500mA	£3.70	50V AC	£3.80
1A DC	£3.70	150V AC	£3.80
5A DC	£3.70	300V AC	£3.90
10A DC	£3.70	500V AC	£3.80
15A DC	£3.70	S Meter 1mA	£4.10
20A DC	£3.70	VU Meter	£3.70
30A DC	£3.70	1A AC	£3.70
40A DC	£3.70	5A AC	£3.70
50A DC	£4.05	10A AC	£3.70
5V DC	£3.70	20A AC	£3.70
10V DC	£3.70	30A AC	£3.70
20V DC	£3.70	100mA AC	£3.70
50V DC	£3.70	200mA AC	£3.70
150V DC	£3.70	500mA AC	£3.70

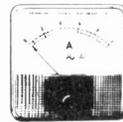

CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.60	150V AC	£4.45
100uA	£4.50	300V AC	£4.45
500uA	£4.40	VU Meter	£4.90
50-0-50uA	£4.50		
100-0-100uA	£4.45		
1mA	£4.30		
1A DC	£4.30		
5A DC	£4.30		
20V DC	£4.30		
50V DC	£4.30		
300V DC	£4.30		



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3.20	300V AC	£3.05
100uA	£3.15	S Meter 1mA	£3.40
200uA	£3.10	VU Meter	£3.40
500uA	£3.00	1A AC	£2.95
100-0-100uA	£3.15	5A AC	£2.95
100-0-100uA	£3.10	10A AC	£2.95
500-0-500uA	£2.95	20A AC	£2.95
1mA	£2.95	30A AC	£2.95
5mA	£2.95		
10mA	£2.95		
50mA	£2.95		
100mA	£2.95		
500mA	£2.95		
1A DC	£2.95		
5A DC	£2.95		
20V DC	£2.95		
20V DC	£2.95		
300V DC	£2.95		
15V AC	£3.05		



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.50	S Meter 1mA	£3.30
100uA	£4.45	VU Meter	£3.80
500uA	£4.20	1A AC	£3.30
100-0-100uA	£4.20	5A AC	£3.30
1mA	£4.20	10A AC	£3.30
5mA	£4.20	20V DC	£4.20
10mA	£4.20	50V DC	£4.20
50mA	£4.20	300V DC	£4.20
100mA	£4.20	300V AC	£4.30
500mA	£4.20	VU Meter	£4.70



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.15	100-0-100uA	£4.05
100uA	£4.10	50-0-50uA	£4.10
200uA	£4.05	1mA	£4.05
500uA	£3.90	10mA	£4.05
50-0-50uA	£4.10	50mA	£4.05
100-0-100uA	£4.05	100mA	£4.05
1mA	£4.05	500mA	£4.05
10mA	£3.95	1A DC	£4.30
300V AC	£3.95	5A DC	£4.30
VU Meter	£4.30	20V DC	£4.30



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm


50uA	£3.10	20V DC	£2.80
100uA	£3.05	50V DC	£2.80
200uA	£3.00	100V DC	£2.80
500uA	£2.85	150V DC	£2.80
50-0-50uA	£3.05	300V DC	£2.80
100-0-100uA	£3.00	500V DC	£2.80
100-0-100uA	£2.80	750V DC	£2.80
1mA	£2.80	1A DC	£2.80
10-1mA	£2.80	2A DC	£2.80
2mA	£2.80	5A DC	£2.80
5mA	£2.80	10A DC	£2.80
10mA	£2.80	20A DC	£2.80
20mA	£2.80	50V AC	£2.90
50mA	£2.80	100V AC	£2.90
100mA	£2.80	150V AC	£2.90
150mA	£2.80	300V AC	£2.90
200mA	£2.80	500V AC	£2.90
300mA	£2.80	S Meter 1mA	£2.80
500mA	£2.80	VU Meter	£3.20
750mA	£2.80		
1A DC	£2.80		
2A DC	£2.80		
5A DC	£2.80		
10A DC	£2.80		
20A DC	£2.80		
50V DC	£2.80		
10V DC	£2.80		
15V DC	£2.80		



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.70	S Meter 1mA	£3.30
100uA	£3.50	VU Meter	£3.80
500uA	£3.35	1A AC	£3.30
50-0-50uA	£3.50	5A AC	£3.30
100-0-100uA	£3.45	10A AC	£3.30
1mA	£3.30	20V DC	£4.20
5mA	£3.30	50V DC	£4.20
10mA	£3.30	300V DC	£4.20
50mA	£3.30	300V AC	£4.30
100mA	£3.30		
500mA	£3.30		
1A DC	£3.30		
5A DC	£3.30		
10V DC	£3.30		
20V DC	£3.30		
50V DC	£3.30		
300V AC	£3.30		

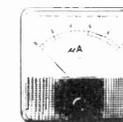

MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£8.50	20V DC	£7.60
100uA	£7.90	50V DC	£7.60
500-500uA	£7.90	300V DC	£7.60
1mA	£7.60	500mA/5A DC	£7.60
10-1mA	£7.60	5V/50V DC	£7.60
1A DC	£7.60	5V/15V DC	£7.60
5A DC	£7.60	1/5A DC	£7.60
5V DC	£7.60		
10V DC	£7.60		
15V DC	£7.60		



CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.60	10V DC	£3.30
100uA	£3.45	20V DC	£3.30
200uA	£3.40	50V DC	£3.30
500uA	£3.35	100V DC	£3.30
50-0-50uA	£3.45	150V DC	£3.30
100-0-100uA	£3.40	300V DC	£3.30
1mA	£3.30	500V DC	£3.30
10mA	£3.30	750V DC	£3.30
50mA	£3.30	1A DC	£3.30
100mA	£3.30	2A DC	£3.30
500mA	£3.30	5A DC	£3.30
1A DC	£3.30	10A DC	£3.30
5A DC	£3.30	20A DC	£3.30
10A DC	£3.30	50V AC	£3.45
15V DC	£3.30	100V AC	£3.45
		150V AC	£3.45
		300V AC	£3.45
		VU Meter	£3.65



BAKELITE MODEL MR 65A

Size: 80 x 80mm

25uA	£5.25	300V DC	£3.60
50uA	£4.00	30V AC	£3.60
100uA	£3.95	50V AC	£3.60
500uA	£3.60	150V AC	£3.60
50-0-50uA	£3.95	300V AC	£3.60
100-0-100uA	£3.90	500V AC	£3.60
500-0-500uA	£3.60	1A DC	£3.60
1mA	£3.60	2A DC	£3.60
10-1mA	£3.60	5A DC	£3.60
5mA	£3.60	10A DC	£3.60
10mA	£3.60	20A DC	£3.60
50mA	£3.60	50V AC	£3.60
100mA	£3.60	100V AC	£3.60
500mA	£3.60	150V AC	£3.60
1A DC	£3.60	300V AC	£3.60
2A DC	£3.60	500V AC	£3.60
5A DC	£3.60	S Meter 1mA	£3.60
10A DC	£3.60	VU Meter	£4.10
15A DC	£3.60		
30A DC	£3.60		
50A DC	£3.60		
100A DC	£3.60		
150V DC	£3.60		
50V DC	£3.60		
150V DC	£3.60		



POSTAGE & PACKING 15p

CALL INTO YOUR NEAREST LASKYS BRANCH OR ORDER WITH CONFIDENCE BY MAIL ORDER

CENTRAL LONDON

481 OXFORD ST.	01-493 8641
10 TOTTENHAM CT. RD.	01-637 2322
27 TOTTENHAM CT. RD.	01-636 3715
33 TOTTENHAM CT. RD.	01-636 2605
42-45 TOTTENHAM CT. RD.	01-636 0845
87 TOTTENHAM CT. RD.	01-580 3739
257-8 TOTTENHAM CT. RD.	01-580 0670
3 LITTLE ST. WC2	01-437 8204
34 LITTLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
407 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812
152/3 FLEET ST. EC4	01-353 2833

ESSEX

86 SOUTH ST. ROMFORD	70-20218
----------------------	----------

KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS	0892-23242
-----------------------------------	------------

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER	0533-53768
----------------------------	------------

SURREY

1046 WHITGIT CENTRE, CROYDON	
27 EDEN ST. KINGSTON	01-881 3027
32 HILL ST. RICHMOND	01-948 1441

WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM	021-236 3503
---------------------------------	--------------

ALL BRANCHES OPEN FROM 9am to 6pm MON. TO SAT.

BARCLAYCARD & ACCESS

Holders welcome call into any branch or telephone your order to head office. CREDIT TERMS available for Personal Shoppers

EXPORT Personal exports

arranged for overseas visitors at all our branches. Goods despatched to all parts of the world through our Export Mail Order Department. Immediate attention given to orders.

CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH BANKERS CARD.

All prices correct at 13.5-74 but subject to change

ALL PRICES EXCLUDE VAT



and make no mistake

ASK LASKYS FOR MAIL ORDER

TO LASKYS HEAD OFFICE AND MAIL ORDER DEPARTMENT
Audiotronic House The Hyde London NW9 6JJ Tel 01 205 5651 3735

Please send me the following items

TOTAL PURCHASE PRICE £


NAME

ADDRESS

Registered in England No. 34794 at 12, Tower Court, Grosvenor Place, London W1A 3LH

Signature

MINITRON

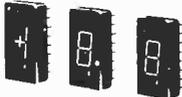

Filament Indicators; 16 Pin DIL 10mm Character Height
0-9 Digit Ref 3015F
-1 Overflow/Polarity Ref 3015G

NEW PRICE £1.29

74 SERIES TTL

1st GRADE BRANDED PRODUCTS

7400 20p	7442 81p	7490 82p
7401 20p	7445 £1.20	7491 £1.10
7402 20p	7447 £1.45	7492 82p
7403 20p	7447A £1.80	7493 82p
7404 20p	7448 £1.50	74100 £2.37
7406 25p	7470 33p	74121 45p
7409 29p	7473 41p	74122 80p
7410 20p	7474 41p	74141 £1.10
7413 31p	7475 63p	74154 £1.82
7420 20p	7476 44p	74192 £2.15
7430 20p	7486 45p	74193 £2.53
7441 81p	7489 £4.75	74196 £1.73

PHOTO-DARLINGTON



2N5777

V_{ceo}, V_{ceo} 25v, V_{ebo} 5v

V_{ceo}, V_{ceo} 25v, V_{ebo} 5v

Hg 2500; I_c 250 MA

OPTOELECTRONICS

Monsanto

Xalim

litronix



Red
Green
Yellow

Seven Segment
MAN 71
MAN 51
MAN 81

Overflow
(±1)
MAN 73
MAN 53
MAN 83

DL 707
0.3" high character
14 pin DIL

DL 747
0.6" high character
L.H. Dec Ph

DL 701
(±1)

Common Anode
Red Only

Common Anode
Red Only


All Common Anode; Left Hand Decimal Point
Character Height 0.3"

OUR PRICE £2.65 each

£2.19

£2.89

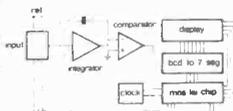3 1/2 DECADE DIGITAL VOLTMETER (INTEGRATED CIRCUIT)



This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet.

OUR PRICE ONLY £7.79

(booklet alone 10p)

SIEMENS



LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing. Ref AN41308 13mm character height. Can be directly driven by National Semiconductor Alarm Clock chip MMS316

OUR PRICE £14.37

LIGHT EMITTING DIODES



0.125" dia. TL1209 Type
Red 24p each, Yellow 99p each,
Green 41p each, White 35p each.

0.125" dia
Red (LED2) 20p ea

Green (LED4) 40p ea

0.175" dia. green (LED5) 75p ea

0.2" dia. MLED 650/750/850 Type

Red 28p each

Green 45p each

Yellow 99p each

1092 type MLED 500 still only 17p (RED)

NEW

LOW COST

RED (Led 7)
GREEN (Led 18)
YELLOW (Led 21)



all at £9.49 for 5

VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH
VAT INVOICES ON REQUEST.
P&P On U.K. Orders, min 10p. Overseas Orders at Cost

WE WILL QUOTE
FOR QUANTITIES
ON REQUEST.

EEMI ELECTRONIC ORGAN KITS

There are four excellent quality models for the do-it-yourself enthusiast



★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built-in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £470.65. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £665.00.

Also in stock M.O.S. Master Oscillators, I.C.'s, transistors, kit of parts for Wireless World Synthesiser and Electronic Piano, complete with reprinted instructions.

Send 50p for catalogue which includes 50p FREE voucher to be used against purchases, or send your own parts list, enclosing S.A.E., for quotation.

Elvins Electronic Musical Instruments

SUPPLIERS OF COMPONENTS TO THE MUSICAL INDUSTRY

12 Brett Road, Hackney, London, E.8. Tel: 01-986 8455
8 Putney Bridge Rd., London, SW18 1HU. Tel: 01-870 4949

GLUM?

SICK OF WAITING FOR COMPONENTS?
Try our express service (normally return of post) Prices very competitive—for example: 1/2W 5% carbon film resistors 1p; 1/2W 2% metal oxide 3 1/2p

BC 107/8/9	10p	2N 3702	13p	1N 4001/2	6p
BC 177	17p	2N 3703	14p	1N 4003/4	7p
2N 1502/3	16p	2N 3704	13p	1N 4148	5p
2N 3055	53p	2N 3707	13p	1N 5401	16p


SINCLAIR CAMBRIDGE CALCULATOR

Ready to use—only £26.50
PRICES EXCLUDE VAT. 10p P. & P.

Forward 15p for our illustrated catalogue to:
DART ELECTRO SERVICES
24 South Town, Dartmouth, Devon
Competitive prices and descriptions of hundreds of components, accessories, etc.

Name:

Address:

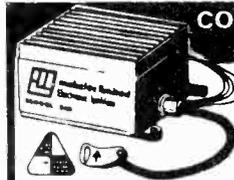

CONTACTLESS ELECTRONIC IGNITION BY MOBELEC


FROM ONLY £13.95 p&p 25p

We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year.

Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 and 6 cylinder NEG. AND POS. EARTH, £22.82. 8 cyl., £24.75. Post free.

SILHILL PRODUCTS

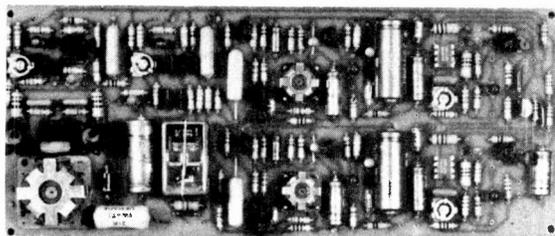Dept. PE/6, 226 Mary Street, Birmingham B12 9RJ. Tel. 021-440 3600



HI-FI TAPE LINK

(PE Mar./Apr. 73) S/c's, i.c's, Rs, Cs, Relay and pc-base, Pot Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, £12.78; Stereo, £20.41. PSU, £3.58. Main Circuit PCB (3½in x 9in) Stereo (also holds relay and stereo), £2.10. Sub-assembly PCB (2½in x 6½in), Stereo 80p.

BIOLOGICAL AMPLIFIER

(PE Jan./Feb. 73) P/A Set—S/c's, i.c's, Rs, Cs, Pots, PCB, £3.46. Output Stages—S/c's, Rs, Cs, Pots, Rotary Sw's and PCBs for Alphaphone, Cardio, Freq-Meter, Vis-Feed, £4.96. Audio Amps: PC7, £5.20; EA1000, £3.30.

ENLARGER EXPOSURE METER AND THERMOMETER

(PE Sept 73) S/c's, Thermistor, LDR, Rs, Pots, PCB, £3.90.

ELECTRONIC PIANO

(PE Sept. 72/Jan. 73) Details in lists

GEMINI STEREO AMPLIFIER

(PE Nov 70/Mar 71) Stereo Sets and PCBs Pre-amp—Rs, Cs, Pots, Sw's—with 1W MO Rs £14.18—with ½W CF Rs, £10.40. PCB as published, £2.20. Main Amp—Rs, Cs, Pots, £5.88. PCB (3½in x 5in), £1.28. Power supply—Rs, Cs, Pot, £4.56. PCB (2in x 4in), 65p.

AUDIO MILLIVOLTMETER

(PE Feb 74) S/c's, Rs, Cs, Pots, Sw's PCBs, £4.95.

MICROPHONE MIXER

(PE Apr. 69) S/c's, Rs, Cs, Pots, PCB (also holds pots), £4.12. While Stocks Last

8 WATT AMPLIFIER

(PW Nov./Dec. 72) Pre-amp—S/c's Rs Cs Pots, Sw—Mono, £2.50; Stereo, £6.03. PCB (3½in x 7½in) (Stereo) also holds rotary or slider pots and Sw, £1.66. Main Amp—S/c's, Rs, Cs, Pot—Mono, £4.18; Stereo, £8.36. PCB (2½in x 3in) (Mono), 72p. PSU, £3.90.

SOUND SYNTHESISER

(PE Feb. 73/Feb. 74)

RHYTHM GENERATOR

(PE Mar./June 74)

SOUND BENDER

(PE May 74)

Details of all these in List

REVERBERATION UNIT

(PW Nov./Dec. 72) S/c's, Rs, Cs, T/ormer—with Rotary Pots, £6.44 PCB (2in x 1½in), £1.40. 9in Spring Unit, £4.50.

LOUDHAILER AND SIREN

(PW Dec 72) Pre-amp and Siren Generator—S/c's, Rs, Cs, Pot, PCB (2½in x 2½in), £2.20. While Stocks Last. Main Amp Module PCB, £6.25.

MISCELLANEOUS PCBs (While Stocks Last)

LOGICAL RADIO CONTROL (PE Dec 71/Jan 72) PCBs '2A', '2B', 50p each
 MODEL SERVO CONTROL (PE Feb./Mar. 72) PCBs 'B', Fail-safe, 33p each
 DIGITAL PSU PCB (PE Aug 72), 50p. OSCILLOSCOPE P/A PCB (PE Aug 72) 33p.
 GEMINI STEREO TUNER PCB (PE Apr 72), £1.50. TRIFFID PCB (PE Feb 73) 60p.
 (The above PCBs are as published)
 DIGITRONIC (PW Mar. 73) Read-out PCB (1½in x 3½in), 50p. CALLERCORD (PE Jul 72) Main Control PCB (4in x 7½in)

RESISTORS

½W and ¼W
 CARBON FILM
 MANUFACTURED BY
 AEI TO DEF 6112A
 E24 SERIES
 ½W 5% 4E7 to 1M
 ¼W 5% 4E7
 to 2M2 then 10% to
 10M
 COMPREHENSIVE
 STOCKS
 FACILITATE RAPID
 PROCESSING
 AS APPOINTED
 DISTRIBUTORS
 WE WELCOME
 TRADE AND EXPORT
 ENQUIRIES
 Write or Phone
 Trade Dept -
 ERITH 30737

SEMICONDUCTORS

AC128	20p	2N2905	27p
AC176	20p	2N2907	27p
AD181	48p	2N3702	12p
BC107	13p	2N3703	12p
BC108	13p	2N3704	12p
BC109	13p	2N3819	35p
BC147	12p	2N3823E	35p
BC148	12p	2N4871	35p
BC149	12p		
BC157	12p		
BC158	12p		
BC159	12p		
BC182L	12p		
BC204	14p		
BC209c	14p		
BC212L	15p		
BCY71	22p		
BFY50	22p		
BFY52	22p		
BSY95A	12p		
MJE2955	115p		
MJE3055	75p		
NKT0033	112p		
OC2	65p		
OC71	14p		
OC84	25p		
ORP12	55p		
TIS43	30p		
2N706	22p		
2N914	22p		
2N1304	22p		
2N2219	27p		

INTEGRATED CIRCUITS

709	TO5	40p
723	TO5	95p
741	8P DIL	40p
747	14P DIL	115p
748	TO5	83p
7400		28p
7402		28p
7420		28p

ELECTROLYTIC (µF/V)

0 47 63	6p	100 10	6p
1 0 63	6p	100 25	6p
2 2 63	6p	100 40	7p
4 7 35	6p	100 63	12p
4 7 63	6p	150 16	6p
6 8 40	6p	150 63	12p
10 25	6p	220 10	6p
10 63	6p	220 16	6p
15 40	6p	220 25	10p
22 10	6p	220 40	14p
22 25	6p	220 63	21p
33 6 3	6p	330 10	6p
33 16	6p	470 6 3	6p
33 40	6p	470 10	10p
33 50	6p	470 25	14p
47 25	6p	470 40	20p
47 40	6p	500 64	40p
47 63	6p	680 6 3	35p
50 6 4	6p	680 25	20p
		680 40	25p
		1000 10	14p
		1000 16	20p
		1000 25	25p
		1000 40	35p
		1000 63	50p
		2200 25	45p
		2200 40	60p
		2200 63	80p
		3300 63	133p
		3300 100	350p
		4700 16	60p
		4700 25	75p
		4700 40	93p

POLYESTER (µF)

0 01	3p
0 015	3p
0 022	3p
0 033	31p
0 047	31p
0 068	31p
0 1	4p
0 15	5p
0 22	5p
0 33	7p
0 47	9p
0 68	11p
1 0	14p

TANTALUM BEAD (µF/V)

0 1 35	12p
0 22 35	12p
0 47 35	12p
1 0 35	12p
1 5 35	16p
2 2 35	12p
4 7 35	12p
10 16	12p
10 25	16p
15 6 3	16p
22 16	16p
47 6 3	16p
100 3	16p

ADD 15p P. & P.
 ADD 10% VAT to total cost (including P. & P.)
 SEND S.A.E. (Stamped Addressed envelope) for Free Itemised List (and with all enquiries please)
 OVERSEAS COSTS: P. & P. will be charged at cost (most kit weights and postal rates are shown in list). Send International Reply Coupon for Free List & with all enquiries. VAT does not apply to exports. EXPORT ORDERS ARE ALWAYS WELCOME.
 MAILING LIST SERVICE—details with list
 COLOUR CODE identification supplied with most kits and as part of list
 PCBs are Fibreglass, Drilled, Tinned, and designed by Phonosonics unless stated as published.
 PCB Layout and Circuit Diagram supplied free with Phonosonics-designed PCBs
 POTS are rotary unless stated as slider.
 PRICES correct at time of press E & OE
 DELIVERIES subject to availability

PHONOSONICS PCB's AND KITS

PHOTOPRINT PROCESS CONTROL

(PE Jan./Feb. 72) For Colour and B & W—finds exposure, controls timing, stabilises mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keywitch, T/frm, £7.98. PCB (3½in x 5½in) also holds pots, Sw, relay, £1.60.

RONDO


(PE Sept 73/Feb 74) Details in List

PROJECT Q4

(PW Oct 73/Jan 74) Multisystem Quadraphonic Decoder. S/c's, i.c's, Rs, Cs, Pots, Makeswitches, £12.48 PSU, £3.17. Set of PCBs, £2.60.

PHASING UNIT

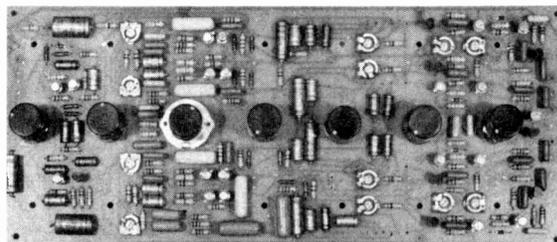(PE Sept 73) S/c's, Rs, Cs, Pots, PCB (1½in x 2½in), £2.20.



AURORA

(PE Apr./Aug 71) Multichannel Sound Controlled Light S/c's (Excl. SCRs), Rs, Cs, Pots, Cores—Pre-amp, Sync Generator and 4 Chans., £10.97; 4 extra chans., £8.35. Reg PSU, £4.32. PCB (4½in x 10½in) for Pre-amp and 4 Chans (also holds pots), £2.50. PCB (4½in x 5in) for Sync. Gen PSU, 8 Cores, 8 SCRs, £1.25.

AURORA AUXILIARY CONTROL UNIT

2 Variable Frequency Strobe Generators and 4 Variable Amplitude Frequency Generators S/c's, Rs, Cs, Pots, PCB (3½in x 5½in), £4.87.

SEMICONDUCTOR TESTER

(PE Oct 73) S/c's, Rs, Cs, Pots, Make-switches, Sub-assembly PCB, £5.30.

TAPE NOISE LIMITER

(PE Feb 72) S/c's, Rs, Cs, Pot, Sw, PCB (1½in x 3in), £2.30. Reg PSU and PCB (1½in x 2½in), £3.40.

ULTRASONIC TRANSMITTER-RECEIVER

(PE May 72) S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in x 5½in), £4.40. Transducers excluded.

VERSATILE LIGHT EFFECTS UNIT

Single Channel Sound Controlled Light with built-in variable strobe. (PE Jun 72). S/c's, Rs, Cs, Pots, T/frm, Keywitch, £11.28. PCB (3½in x 7½in) also holds pots and switch, £1.70. SCRs excluded

VIBRASONIC GUITAR PRE-AMP

(PW Sept 70) Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume S/c's, Rs, Cs, LDR, Rotary Pots, Lamps. Coupling T/frm, £7.64. PCB (3½in x 10½in) also holds pots, £1.92. Power Supply, £3.90.

VOICE OPERATED FADER

(PE Dec 73) S/c's, Rs, Cs, Pot, PCB (PE Dec 73) £2.95.


WIND AND RAIN EFFECTS

(PE Oct 73) S/c's (incl. special noise diode), Rs, Cs, Pots, £1.95.


PHONOSONICS, DEPT. PE27, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY

Sinclair Project 80

exciting

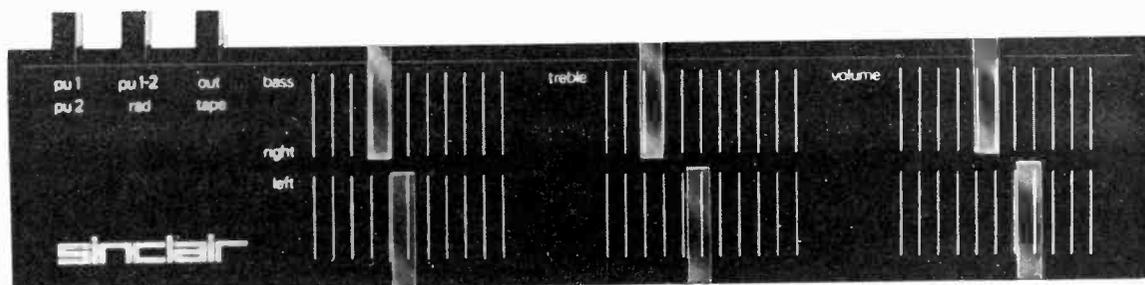

Stereo 80 pre-amplifier/control unit

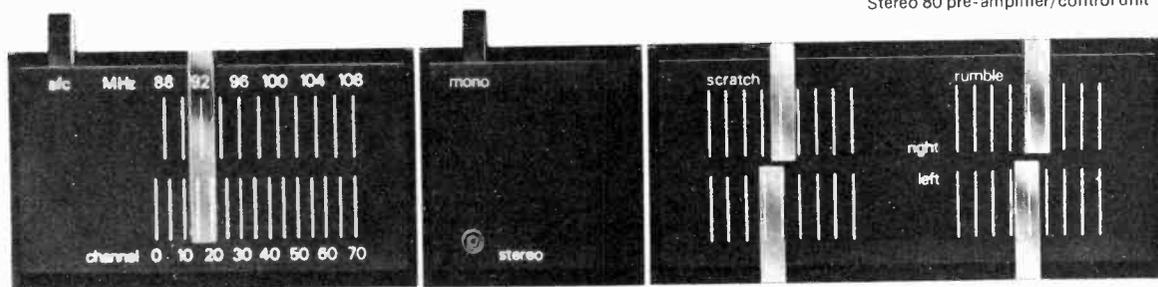

Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

only $\frac{3}{4}$ " deep x 2" high


Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

Typical Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 +54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 +£1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.6	£30.83 +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amp.	2 x Z.60s, Stereo 80; PZ.8	£33.83 +£3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14.93 +£1.49 V.A.T.

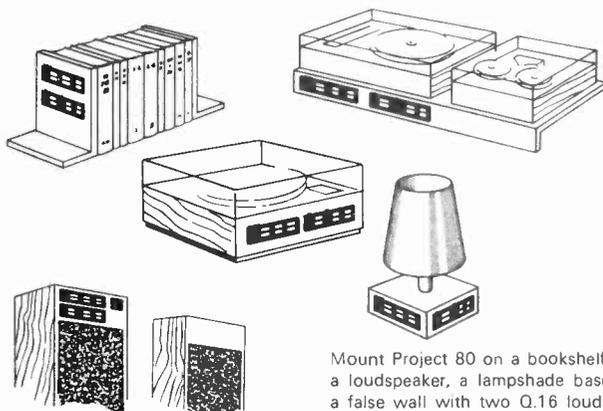
Project 80 FM tuner, decoder, and A.F.U. may be added as required



Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base a false wall with two Q.16 loudspeakers... almost anywhere.

new thinking in modular hi-fi

Stereo 80 pre-amplifier and control unit

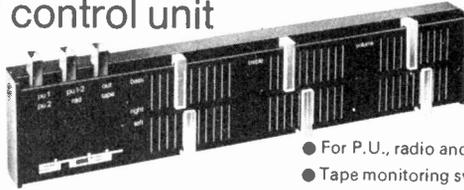

- For P.U., radio and tape
- Tape monitoring switch
- Simplest ever fixing


Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm (10 1/4 x 2 x 3/8 ins)
 Finish - Black with white indicators and transparent Sliders
 Inputs - Magnetic pick-up 3mV RIAA corrected; Ceramic pick-up 300mV
 Radio 300mV; Tape 30mV
 Signal/noise ratio - 60dB
 Frequency range - 20Hz to 15KHz \pm 1dB, 10Hz to 25KHz \pm 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV \rightarrow AB monitoring for tape
 Controls - Press button for tape, radio and P.U. Sliders for volume, bass (\pm 12dB to \pm 14dB at 100Hz) treble (\pm 11dB to \pm 12dB at 10KHz)

R.R.P. **£11.95** +£1.19 V.A.T.

Project 80 FM tuner and stereo decoder

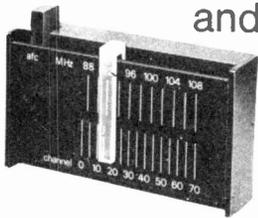

- Twin dual varicap tuning: 4 pole ceramic filter: switchable A.F.C.
- On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

TECHNICAL SPECIFICATIONS OF TUNER

Size - 85 x 50 x 20mm (3 1/4 x 2 x 3/8 ins)
 Tuning range - 87.5 to 108 MHz
 Detector - I.C. balanced coincidence for good A.M. rejection
 One I.C. equal to 26 transistors
 Distortion - 0.2% at 1 KHz for 30% modulation
 4 pole ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Output - 300 mV for 30% modulation
 Power requirements - 23 to 33 volts

DECODER
 Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/8 ins)
 One 19 transistor I.C.

R.R.P. **£11.95** +£1.19 V.A.T.

R.R.P. **£7.45** +0.74 V.A.T.


Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge.


sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ
 Telephone St. Ives (0480) 64646

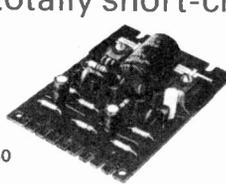Z.40 & Z.60 power amplifiers totally short-circuit proof



Z.40

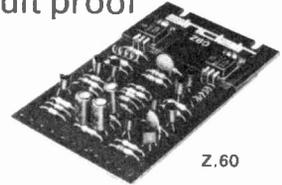

Z.60

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

Z.40 TECHNICAL SPECIFICATIONS

Size - 55 x 80 x 20mm (2 1/4 x 3 1/4 x 3/8 ins) 9 transistors
 Input sensitivity - 100mV
 Output - 15 watts RMS continuous into 8 Ω (35V)
 Frequency response - 10Hz - 100KHz \pm 1dB
 Signal/noise ratio - 64dB
 Distortion - at 10 watts into 8 Ω less than 0.1%
 Power requirements - 12 to 35 volts


Z.60 TECHNICAL SPECIFICATIONS

Size - 55 x 98 x 15mm (2 1/4 x 3 3/4 x 3/8 ins) 12 transistors
 Input sensitivity - 100-250mV
 Output - 25 watts RMS continuous into 8 Ω (45V).
 Distortion - typically 0.03%
 Frequency response - 10Hz to more than 200KHz \pm 1dB
 Signal/noise ratio - better than 70dB
 Built-in protection against transient overload and short circuiting
 Load impedance - 4 Ω min. max safe on open circuit

Z.40 R.R.P. **£5.45** + 0.54 V.A.T. Z.60 R.R.P. **£6.95** + 0.69 V.A.T.

Project 80 active filter unit

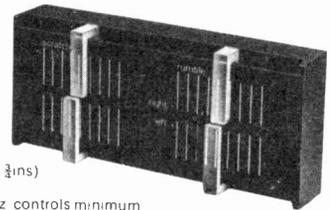Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.



TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/8 ins)
 Voltage gain - minus 0.2dB
 Frequency response - 36Hz to 22KHz controls minimum
 Distortion - at 1 KHz - 0.03% using 30V supply
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope
 L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct slope

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. **£6.95** +0.69 V.A.T.

Power supply units


PZ.8

Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.

R.R.P. £7.98 + 0.79p V.A.T.
 Without mains transformer

PZ.5 30V un stabilised
 R.R.P. £4.98 + 0.49p V.A.T.

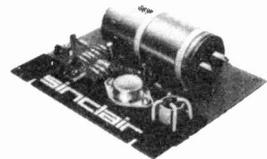PZ.6 35V stabilised
 R.R.P. £7.98 + 0.79p V.A.T.



To **SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ**

Please send post paid

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

SITUATIONS VACANT

MEN!
£70 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre
T59, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

THE POLYTECHNIC OF NORTH LONDON
HOLLOWAY ROAD, N7 8DB

Department of Electronic and Communications Engineering

LABORATORY TECHNICIAN GRADE 4

Applications are invited from candidates who are suitably qualified Electronics Technicians. Experience in microwave/radar technology would be an advantage.

This is a Laboratory Technician Grade 4 appointment with prospects of promotion for a man showing initiative. Five-day week totalling 35 hours.

Salary scale: £2,022 rising by annual increments to £2,337 per annum (including London Weighting).

Write stating age, experience and qualifications to:

THE ESTABLISHMENT OFFICER
THE POLYTECHNIC OF NORTH LONDON
HOLLOWAY ROAD, N7 8DB.

Enquiries to Mr. S. A. Elliott, 01-607 6767 Extn. 289.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 20p. S.A.E. enquiries, TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for televisions, radios, transistors, record players, tape recorders, etc., from 5p with free fault-finding guide. Over 10,000 models available. S.A.E. enquiries, Catalogue 20p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

LADDERS

LADDERS. "Special Offer" unvarnished triples. 9ft 7in closed—23ft 1in extended. £18-90 delivered. HOME SALES LADDER CENTRE (PEE2), Haldane (North), Halesfield (1), Telford, Shropshire. Tel. 0952 586644.

EDUCATIONAL

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on September 9th.

Prospectus from London Electronics College, Dept. A7, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

C AND G EXAM

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work and Technicians. Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits

Get the qualifications you need to success. Free details from

International Correspondence Schools, Dept. 730S, Intertech House, London SW6 4UJ. Or phone 01-622 9911

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types

KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

WANTED. Radio and TV Servicing books from 1964 onwards. £2 per copy, paid by return of post. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, Yorkshire. Telephone 0423 55885.

FOR SALE

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey TW9 2EQ
01-948 3702

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

SPECIAL OFFER—Indicators 3015F and G, CD43, CD66, only 95p. Chips 7447 (BCD-7 SEG), £1; IC12 6W amp, £1-50; 743PSU, 55p; BC182, 183, 108, 141, 8p each; MJ3001, £1. 150W npn, npn photo transistors, 25p. IN4001 4IN4148, 5p. 10A, 150V bridge, £1. Interested? Then get our cat. (10p P.O.). now! ALPHA ELECTRONICS, 73 Moorgate, London, EC2. (Mail order only. Prices exclude VAT.)

VALVES, VALVES AND MORE VALVES. Large stocks, many types, 1930 to 1974. S.A.E. for quotation. List 10p. COX RADIO, The Parade, East Wittering, Sussex.

LIGHTSHOW PROJECTORS from only £17, effect wheels from only £4. Many lightshow bargains at ROGER SQUIRE'S (Disco Centre), 176 Junction Road, London, N.19. Tel. 01-272 7474.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel, choice of 70 types, send for free list. BAZELLI INSTRUMENT CASES, Dept. 23, St. Wilfrids, Foundry Lane, Halton, LA2 6LT, Nr. Lancaster.

CHASSIS supplied in steel or aluminium. Send sketch and S.A.E. for quotation. FRAME ELECTRONICS, Knightcott Works, Banwell, Somerset.

OSCILLOSCOPE TYPE C116. Double beam, 14 months old but almost unused. £45. Telephone Ingatstone 2105.

RECEIVERS AND COMPONENTS

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 4x4½ 0-1 Matrix, 4 for £1.

12x3½ 0-15 Matrix, 75p each.

Memory Array Panels. Full of Ferrite Rings. £1-10 inc. P.P.

FM Tuner with R.P. Stage and A.G.C., 3 transistors, neg. earth, 2½x2x1½ in with circuit, £1-37½ inc. P.P.

Crouzet Geared Motors, 30 or 60 r.p.m. New. £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

Panels with I.C.'s on 7½p per I.C. min. order 10 I.C.'s.

Transformers. 7-5V+7-5V ½A, 88p inc. P.P.

12-0-12V, 100mA, 90p inc. P.P. 9-0-9V, 100mA, 90p inc. P.P. 29V 50mA, 70p inc. P.P.

Brand new Boxed Rola Celestion Reentrant Speakers SD 25 with 100V line transformer fitted 15Ω without transformer £14 inc. P.P.

Transformer. 45-0-45V, approx. 2 amp, £2-50 inc. P.P.

P.C. Board. S/S, 5½x5½in, 10 for 70p inc. P.P.

Panel with 2 5N7490, 2 5N7441 counting circuit with end connector, £2-20 inc. P.P.

Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions.

Brand new. £2 inc. P.P. Size 3" x 2" x 2".

Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2 1250 mfd capacitors, all new £1-25 per kit. P.P.

Electrolytic Capacitors, 4,000 MF, 50 VV, 4½" x 1½" 75p. inc. P.P.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—
EXTREMELY LOW LEAKAGE

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1µF (11" × 1")	50p	0.47µF	56p	46p 36p
0.22µF (11" × 1")	59p	1.0µF	86p	56p 46p
0.22µF (11" × 1")	62p	2.2µF	80p	65p 55p
0.47µF (11" × 1")	71p	4.7µF	±1.80	±1.05 86p
0.5µF (11" × 1")	74p	6.8µF	±1.64	±1.29 ±1.09
0.68µF (2" × 1")	80p	10.0µF	±2.00	±1.60 ±1.40
1.0µF (2" × 1")	91p	15.0µF	±2.75	±2.15 ±1.90
2.0µF (2" × 1")	±1.22			

TANTALUM BEAD CAPACITORS—Values available:
0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 16V/25V or 35V;
10.0µF at 16V/20V or 25V; 22.0µF at 8V/10V or 16V;
33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V.
ALL at 10p each, 10 for 85p, 50 for 44.

TRANSISTORS:

BC183/183L	11p	BFY50	20p
BC184/184L	12p	BFY51	20p
BC107/8/9	9p	BC212/212L	14p
BC147/8/9	10p	BC547/568A	12p
BC157/168	12p	BF194	12p
BC182/182L	11p	BF197	13p
		2N3055	50p

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p;
1N916 8p, 6 for 45p, 14 for 90p; 1N44 5p, 11 for 50p, 24 for 91p;
1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 51p; 1N4002 6p;
1N4003 61p; 1N4004 7p; 1N4005 7p; 1N4006 8p;
1N4007 81p.

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 15.5V, 18V, 18V, 22V, 24V, 27V, 30V. ALL at 7p each, 8 for 80p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5%, ¼W at 40°C, ½W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ resistors—£5.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p); 800 P.I.V. 11p (4 for 42p).
BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 500V 55p.

MINIATURE VERTICAL PRESETS—0.1W only: ALL at 8p each: 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 1.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 1MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW 45. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 10% V.A.T. TO ORDERS
Send S.A.E. for lists of additional ex-stock items.
Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. E7, The Maltings, Station Road,
Wren, Shropshire

Tel.: Nantwich (Cheshire) 83291 (STD 0270)
(Proprs.: Minicost Trading Ltd.)

MICROCIRCUIT ELECTRONICS

SYSTEM 30 HI-FI AUDIO MODULES

MEA30-2: 30W r.m.s. per channel stereo amplifier (s/c protection) **£10.00**

PS22-2: Twin stabilised heavy-duty (3.5A) power supply **£6.80**

Suitable Transformer **£3.00**

Simple power supply kit **£4.00**

MEP-32: Stereo pre-amp with rumble and variable scratch filters, full range tone controls, and 4 inputs (including magnetic) **£13.00**

DATA: 25p (not stamps, price refundable on purchase of any module)

All prices include post and VAT.

Mail Order Service Only, Orders to:

MICROCIRCUIT ELECTRONICS (E1)

23 Pages Lane, LONDON N10 1PU

UNIT IN SMART ALL CASE

11 × 11 × 4in. contains 8 silicon diodes 600V, 20A, 8 SCRs 3 OR 400V 16A, 4 Yinkors, 4 small, 2 large, together with other components, £6 (60p). M.C. METERS, 3 assorted 2-3in., £1.15 (35p). 5 FIGURE RESETTABLE COUNTER, 78/22V, works on 12V, £2.20 (25p). 7400 SERIES I.C.s, 10 on panel(s). £1.10, c.p. COPPER CLAD P.A. PANELS, 5½ × 5½in., 6 for 50p, c.p.; 7½ × 9in., 8 for £1.30, c.p.; 11½ × 9in., 3 for £1, c.p.; 15 × 9in., 3 for £1.30, c.p. SMALL UNIT WITH 4BFY51 with heatinks, 4 silicon diodes 650V 1½A plus resistors, 60p, c.p. ALL PANEL WITH 2 × AC128 and OCT5 plus electrolytics, 40p for 2, c.p. VALUPAKS, P9, 100 assorted s/mica caps, 55p; P11, 100 assorted polystyrene caps, 75p; P13, 10 wire ended neons, 50p; P22, 100 assorted capacitors, 55p, post 12p any number of Paks. Send 10p stamps for list of Valupaks, computer panels, etc. Refund on purchase. 7. B ASSORTED COMPONENTS, £1.75, c.p. 2. B FIRSTS COMPUTER PANELS, £1.75, c.p. 3. B SECONDS COMPUTER PANELS, £1.50, c.p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets Mail order only

DRY REED INSERTS



Overall length 1.85" (Body length 1.1").
Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 68p per dozen; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. VAT and post paid.
G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex O903 34897

ELECTRONIC COMPONENTS, WATFORD

Visit our Warehouse for your requirements of Resistors · Capacitors · Transistors · SCR's Speakers · Metal Boxes · Headphones · Intercoms · Meters · Audio Cables · Cartridges Microphones · wide range of Plugs and Sockets, etc., etc.

HILLS COMPONENTS LTD.

Unit 6, Melinite Industrial Estate, Brixton Road, Watford, Herts. Tel.: Watford 27711

STOCK UP NOW P. & P. FREE

RESISTORS AND CAPACITORS GALORE
1, 2, 5, 10, 20 watt, 5%, 10%, 20%, Silver Mica, Ceramic, High pulse, 2%, 5%, 10%, 20%.

ALL BRAND NEW — LONG LEADS — NO RUBBISH.

JUST SEND £1 AND WE WILL SEND YOU EITHER:

PAK 1. 400 Resistors—good selection.

PAK 2. 300 Capacitors—good selection.

SIMLA ELECTRONICS

First Ave., Hook End, Brentwood, Essex

BUILDING OR PURCHASING an AUDIO MIXER

Pre-amp, auto-fade, V.U. or audio monitor, V.E. mixer, driver or power supply, etc.

First consult:

PARTRIDGE ELECTRONICS

Ref. P.E., 21-25 Hart Road, Benfleet, Essex
Established 23 years.

BRAND NEW COMPONENTS by return

Electrolytics 16V, 25V, 50V-0.47, 1, 2.2, 4.7, 10MF, 4p, 22, 47, 4½p (50V, 5p); 100, 5½p (50V, 7p); 220, 6p (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V, 8p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 2½p; 0.04, 0.05, 3p. Polystyrene 63V E12 series 10pF-1000pF, 2p; 1,200pF-10,000pF, 3p. Miniature High-stab. resistors 5%, E12 series carbon film ¼W, 1Ω-10MΩ, (10% over 1MΩ). Metal film ¼W, 10Ω-2.2MΩ and 1W, 27Ω-10MΩ all 1p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

COMPONENTS GALORE.

Pack of 500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send £1 + 10p P. & P. C.W.O. to CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

RADIO & TELEVISION AERIAL BOOSTERS

£2-95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7-50. Carr. £1-50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

SEMICONDUCTORS—Marked: 2N4292 (570 MHz) 15p, 1N914A 3p. Tested, unmarked: n/pn similar to BC108 (Hfc 50-250, Vce 25V) 5p, FET similar to 2N3819 15p, 2N3055 20p. P. & P. 10p, mail order only. JOHN RIGG, 13 Paradise Road, Henley-on-Thames, Oxon.

5 N-CHANNEL FETs.

Type 3819E (2N3819) for £1 (inc. VAT). Full spec. transistors complete with circuit details for building voltmeter, timer, ohmmeter, etc. For complete list of FETs and other transistors available send 10p P.O. REDHAWK SALES LTD., 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

TURN YOUR SURPLUS capacitors, transistors,

etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

MISCELLANEOUS

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ **POCKET-SIZED MAXI-VOLT** Big ½ inch Spark Generator (instant 15,000 volts!) Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz (85g). Send £1.35 for your Maxi-volt now!

★ **UNIQUE TRANSMITTER/RECEIVER KIT.** No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5-90 for yours now!

★ **PSYCHEDELIC MINI-STROBE KIT.** Take a pocket-sized lightning storm to Disco's and Parties. "BRAIN-FREEZE" EM with vari-speed stop-motion flashes. Includes super case, too. Send £2.20 now! (All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey

(Mail order U.K. only)



Or for more details, send 20p for lists, plus free design project sheet

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0.06-3A-6 Ranges
A-AC 0.3-3A-5 Ranges
V-DC 0.6-120V-9 Ranges
V-AC 3-900V-8 Ranges
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5% DC ±4% AC Dimensions: 167 × 98 × 63mm

Only **£8.00**

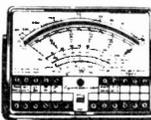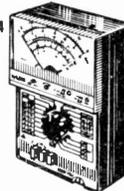

SUPERTESTER 680 RICE

10 Fields-80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC Temperature-50C to +200C Magnetic fields up to 15 KGauss-Phase indicator-EHT 25KV Electronic Volt Ohm-meter Transistor Diode Tester, etc

£18.50

Accessories Extra

ALPHANUMERIC NIXIE TUBES B7971

The alphanumeric NIXIE tube has the ability to display all the letters of the alphabet numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alpha numeric NIXIE tube provides many unique benefits including * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footcandle brightness * Long life with no loss of brightness * Character height 2½in.



Price only 99p each plus 16p P.P.

Add 10% VAT to all items + 35p P&P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road London NW1 2QB Tel 837 7781

HARDWARE SUPPLIES—Sheet aluminium

individual sizes or standard packs, drilled to spec. Screws, nuts, washers, etc., Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes, etc., 7p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks., CV37 9JP.

BUILD THE TREASURE TRACER MK III Metal Locator



- Variac tuning
- Britain's best selling metal locator kit
- Weights only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send a S.P. for leaflet

Complete kit Post 35p **£9.80** Built, tested and guaranteed Post 35p **£13.75**

MINIKITS ELECTRONICS, 35q LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order only)

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to: **METER REPAIRS, 39 Chesholm Road, London, N16 0DS.**

SLOW SPEED MOTORS required (about 1 r.p.m.) any quantity considered. Phone Mr. SMITH, 061-633 3527.

PRINTED CIRCUIT MANUFACTURERS offer any P.E. Project Print ready drilled. One Price 65p. C.W.O. Any P.C. work undertaken. For estimate by return post, send basic circuit, print design or print master. State quantity required. Print design, art work, photography undertaken. Orders, estimates, write or phone: **W.K.F. ELECTRONICS, Dept. P.C., Welbeck Street, Whitwell, Nr. Workson, Notts., S80 4TW. Tel. Whitwell (Derbys). 693.**

ELECTRONIC DRUMS, send 75p for full constructional details. **MEDAC, 21 Congers House, Bronze Street, London, SE8 3DT.**

LOW COST I.C. MOUNTING. Lengths of 100 I.C. pin sockets, 60p (P. & P. 5p). Quantity rates. S.A.E. for details and sample. **L.B.D. (MLE1500), 20p** each (post paid). **P.K.G. ELECTRONICS, "Oak Lodge", Tansley, Derbyshire.**

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

fibre optic suppliers

LIGHT SOURCES, DETECTORS: MV54 miniature (2mm) red LED; MLED500 TO-92 PC mounting red LED; MLED92 TO-92 infra-red emitter; 2N5777 high sensitivity silicon photo-darlington amplifier. Response Time 200 μ s, 25V max. Superior to CdS cell, OCP71. MRD150 miniature (2mm) silicon phototransistor. Fast response 3 μ s, 40V max. 10 25

MV54 22p 44p £1.10 £2.09 £3.52
MLED500 22p 44p £1.10 £2.20 £3.74
MLED92 33p 66p £1.54 £2.86 £6.60
2N5777 55p £1.10 £2.53 £4.62 £9.90
MRD150 66p £1.32 £3.19 £6.16 £14.85

ULTRASONIC TRANSDUCERS (for remote control 40kHz Tx/Rx pair £3.85).

CIRCULAR POLARISERS for glare reduction—enhance contrast ratio from LED display, nixies, 'scope. HRCP7 red, HACP24 amber, HGCP24 green, HNCPC37 neutral. 50mm \times 50mm 66p; 75mm \times 75mm £1.21; 150mm \times 150mm £4.40.

CROFON 1610 64 strand plastic light conduit, bundle dia. 1.8mm, O.D. 3.3mm. 1m £1.32; 5m £5.50; 10m £10.45; 25m £22.

PLASTIC OPTICAL MONOFIBRE for easy light circuitry, displays, effects. Diameter 0.5mm—FP20; 1.0mm—FP40; 1.5mm—FP60. Length 5 10 25 50 100 200
FP20 £1.32 £2.20 £3.85 £6.60
FP40 £1.10 £1.98 £3.85 £6.60 £12.10 £22.00
FP60 £1.98 £3.85 £7.70 £13.20 £24.20 £44.00

OPTIKIT 103: Experimenter pack, 2 metres Crofion 1610 + 5m each FP20, FP40, FP60—£4.84.

FIBROFLEX SIZE 1: Glass light conduit, 440 Strand, bundle dia. 1.14mm, O.D. 3.3mm (p.v.c. jacket). 5m £2.97; 10m £3.85; 25m £6.60; 50m £11.00; 100m £17.05. all inc. 10 ferrules + epoxy resin for terminations.

MAR'S TAILS: Decorative effects. 7,000 fibres in 18mm O.D. ferrule. Professionally finished. 22in diameter in use. Add lamp, stand, cover to make Fibre Optic Lamp. Eye catching in boardroom, hall or foyer.

NEW LOW PRICE £10.45 each. Send 9in \times 6in S.A.E. for details.

FIBRE OPTIC SUPPLIERS (Dept. PE), P.O. Box 702, London W10 6SL

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£1.40	80p
15-19	£1.40	80p
20-24	£1.43	83p
25-29	£1.52	91p
30-34	£1.57	97p
35-40	£1.69	£1.04

Please add 10% to all above prices to cover VAT
The above prices cover P. & P. in U.K. Supplied by
INDUSTRIAL SUPPLIES
102 Parrswood Rd., Wittington, Manchester 20
Telephone No. 061-224 3553

Build the Mullard C.C.T.V. Camera
Kits are now available with comprehensive construction manual (also available separately at 76p)
SEND 5 \times 7 S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

POWER SLAVE

COMPONENT KITS FOR THESE EXCITING PROJECTS 4p STAMP BRINGS DETAILS

RHYTHM GENERATOR SYNTHESIZER

SEMICONDUCTOR DEVICES

AC176	24p	HIGH VOLTAGE TYPES
BC182	9p	MPSL01 120V/300mW 35p
BC184	11p	MPSL1 100V/300mW 41p
BC204	11p	Complementary Pair MPSU07 100V/1W 69p
BC209C	11p	MPSU57 100V/1W 85p
BC213	9p	Complementary Pair (5 watt with H/F) SDT9203 100V/100W £1.50
BC213L	15p	
2N2905	27p	
2N2219	22p	
2N3819	46p	
MPF111	26p	

SIGNAL DIODES

IN914	5p	LINEAR I.C.'s
1S150	12p	741CS 37p
1G7	12p	748CS 48p
NOISE DIODES		ML3046P 78p
Z11	53p	SG3402T £1.74
Z1M(w/b)	£1.20	SG1495D £2.90
		MFC6040 £1

RECTIFIERS

IN5401	21p	ZENERS BZY88 SERIES
REC41A £1.20		3: 3; 6; 3; 9; 5: 1; 6; 2; 7: 5; 11: 0; 12: 0 all 22p
REC70 45p		BZX61 SERIES
		11: 0; 12: 0 all 27p

VREGULATORS

uA723	£1.80	ALL ITEMS LISTED ARE EX-STOCK AT TIME OF GOING TO PRESS
uA7815	£2.20	
MVR15	£2.04	

DIGITAL I.C.'s

74001	29p	7473N 48p
7402N	38p	7475 63p
7404N	27p	7476N 49p
7410PC	24p	7489j £6.60
7420N	24p	7493PC 85p
7430PC	23p	74121J 85p
7447PC	89p	74150N £2.10

POWER SLAVE P.C.B's

Designer's layout. Master Board £1.65 Stabiliser £1.10 Best quality epoxy glass roller tinned.

V.A.T.

Please add 10% to final total of order

RESISTORS

2% METAL OXIDE TYPE E12, E24 series from 10R to 1M Ω 16p for 5 5% CARBON FILM TYPE E12, E24 series from 10R to 1.2M Ω 9p for 5

MINIATURE PRESETS

100k: 100; 500; 1k Ω ; 25k Ω ; 10k Ω ; 50k Ω ; 100k Ω ; 42p each CARBON: 470; 10k Ω ; 470k Ω ; 100k Ω ; 11p each CERMET TRIMMER 1ST 200; 1k Ω ; 10k Ω ; £1.20 each SEMI-PRECISION W/W/POTS. 52p

POTENTIAL METER

MIG MOULDED CARBON. 24mm dia. LINEAR. 5k Ω ; 10k Ω ; 25k Ω ; 50k Ω ; 100k Ω ; 1M Ω . LOG. 10k Ω ; 25k Ω ; 50k Ω . 21p each GANGED. 100k Ω lin; 5k Ω log; 10k Ω log. 78p each

MIDG.W.C. SWITCHES

28mm dia. 1P 12W; 1P 6W; 3P 4W; 4P 3W. 43p each

MAKA TYPE DETENT MECHANISM

WAFERS: 1P 12W; 2P 6W; 3P 4W; 4P 3W; 6P 2W 39p each

SPACERS SCREENS

1p 0.68

10 TURN POTS.

10k Ω SPECTROL £3 1k Ω R.S. TYPE £3.90

10 TURN DIALS.

AMPHENOL £2 10/6-3; 10/16; 10/25 22/16; 47/6-3; 100/3 18p each

BEAD TANTALUMS.

0.1; 0.015 0.022; 0.033; 0.047 0.068 5p 0.1; 0.15; 0.22 0.33 9p 0.47 10p 0.68 14p

POLYSTYRENE

10; 47; 470 6p 680; 1,000; 1,500; 3,300 7p 10,000 11p

CAPACITORS

Tubular Electro. 14p 25V; 25 μ F; 47 μ F 100 μ F 16p; 470 μ F 29p 1000 μ F 46p 50V; 1000 μ F 57p 63V; 10 μ F 22p 1000 μ F 24p

PRINTED CIRCUIT ELECTROLYTIC.

47/40V; 10/63V 22/40V; 47/40V 13p each 100/63V; 470/16V 23p each

HIGH RIPPLE TYPE

3300 μ F 63V £2.20

C280A SERIES

0.01; 0.015 0.022; 0.033; 0.047 0.068 5p 0.1; 0.15; 0.22 0.33 9p 0.47 10p 0.68 14p

10 TURN POTS.

10k Ω SPECTROL £3 1k Ω R.S. TYPE £3.90

10 TURN DIALS.


AMPHENOL £2 10/6-3; 10/16; 10/25 22/16; 47/6-3; 100/3 18p each

POLYSTYRENE

10; 47; 470 6p 680; 1,000; 1,500; 3,300 7p 10,000 11p


EATON AUDIO P.O. BOX 3, ST. NEOTS HUNTINGDON PE19 3JB

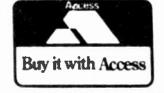TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.



Dimmit

range of light dimmers

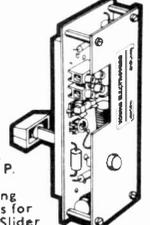

Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression, 60mm slider range; size 12 \times 5 \times 4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £6.50 inc. VAT, add 10p P. & P. Also available in 2kW, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800 watt. Full instructions. £7.60 inc. VAT, add 10p P. & P. Send 10p for complete illustrated catalogue and price list.

YOUNG ELECTRONICS Mail Order Dept.
54 Lawford Road, London NWS 2LN. Telephone 01-267 0201

WORLD RADIO & T.V. HANDBOOK 1974

A COMPLETE DIRECTORY OF INTERNATIONAL RADIO & T.V.

Price £3.20

- SIMPLE SINGLE CHANNEL RADIO CONTROL** by R. H. Warring. Price £1.60.
- SERVING WITH THE OSCILLOSCOPE** by G. J. King. Price £1.90.
- TRANSISTOR AUDIO AND RADIO CIRCUITS** by Mullard. Price £1.90.
- VIDEO RECORDING RECORD AND REPLAY SYSTEMS** by G. White. Price £3.45.
- IMPROVING YOUR HI-FI** by J. Earl. Price £3.20.
- ELECTRONIC HOBBYIST'S I.C. PROJECTS HANDBOOK** by B. Brown. Price £1.50.
- THE PYE BOOK OF AUDIO** by Pye Ltd. Price £1.10.
- HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS** by L. C. Lane. Price £1.70.
- RADIO TECHNICIAN'S BENCH MANUAL** by H. W. Hellyer. Price £3.20.
- THE MAZDA BOOK OF PAL RECEIVER SERVICING** by D. J. Seal. Price £4.
- ELECTRONIC SYSTEMS FOR RADIO, T.V. AND ELECTRONICS MECHANICS** by R. Lewis. Price £2.50.

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP


Phone 01-723 4185
Closed Saturday 1 p.m.

Please mention

PRACTICAL ELECTRONICS

when replying to ADVERTISEMENTS

Digital Clock Kits

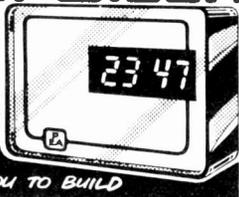

SPACE RESEARCH BRINGS YOU A DIGITAL CLOCK - WITH NO MOVING PARTS - FOR YOU TO BUILD

KIT 0 All components, including P.C.B. designed for easy home assembly. Bright and clear digits. Tough A.B.S. plastic case with contrasting front panel.

PRICE: £23.00 plus £2.30 VAT/Total £25.30 inc. post, pkg Only our advanced design techniques make this low price possible. Kits are tested before they leave us and are covered by the P.E.A. money-back guarantee.



P.E.A. Ltd.
35 High St, WELWYN, Herts. AL6 9EE

Please send me details of your clock kits

NAME _____

ADDRESS _____

SINCLAIR CALCULATORS

Cambridge kit	£19.95 (£2.25)
Cambridge Assembled	£21.95 (£2.50)
Executive	£27.95 (£3.05)
Executive with Memory	£34.95 (£3.75)
New Sinclair Scientific	£39.95 (£4.25)

FERRANTI ZN414

IC radio chip with data. £1.20 (23p). Also available kit of extra parts to complete a radio. £2.39 (40p). Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80

AFU	£8.95 (89p)
Z40	£5.45 (54p)
Z80	£6.70 (67p)
Q16	£7.70 (77p)
PZ5	£4.90 (49p)
PZ6	£7.98 (79p)
PZ8	£7.98 (79p)



Decoder. £7.45 (74p). Trans for PZ8. £3.35 (50p).
Tuner. £11.95 (£1.19). Stereo 80. £11.95 (£1.19).
Project 80S. £26.95 (£2.69).
2 x Z40/Stereo 80/PZ5. £25.00 (£2.50).
2 x Z40/Stereo 80/PZ6. £27.75 (£2.77).
2 x Z80/Stereo 80/PZ8/Transformer. £33.11 (£3.31).
Write for our most competitive quotation.


SINCLAIR GOES QUADRAPHONIC!

Introducing the Naporex QA10 self-contained matrix quadraphonic synthesizer. Just feed the output of a Project 80 stereo system into it and hook on 4 speakers to obtain the latest experience in sound. Send for free leaflet. Only £9.95 (£1.30)



SINCLAIR SUPER IC12

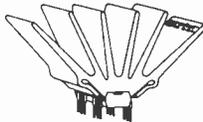6W r.m.s. power
With 44 page booklet and printed circuit £2.10 (43p).



SWANLEY IC TOMORROW

£1.80 (40p)

The world's most powerful IC amplifier. Similar to IC12 but rated at 10W r.m.s. power. Supplied with data but no printed circuit. Write for leaflet.

DE LUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version. £1.60 (27p). Stereo model with balance control. £3.60 (48p).

IC12 POWER KIT

Supplies 28V 0.5A. £2.87 (50p).

LOUDSPEAKERS FOR THE IC12

5in 8 ohm. £1.10 (27p). 5in x 8in 8 ohm. £1.55 (37p)

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics. and tuners. Mono model. £1.35 (25p). Stereo model. £2.40 (36p). Type 2 for ceramic or crystal pickups. Mono. 85p (18p). Stereo. £1.30 (25p).

SEND S.A.E. FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3.4A, 6.7A, 9 and 12V at 500mA. £4.15 (70p).

Other eliminators stocked:
250mA—3 way switched model giving 6.7A and 9V. £2.85 (50p).
50mA—6V. £1.80 (30p); 9V. £1.80 (30p); 7A cassette type. £2.25 (30p). Double 6V + 6V. £2.50 (35p); 9V + 9V. £2.50 (35p).



S-DECS AND T-DECS

S-DEC	£1.98 (31p)
T-DEC	£3.83 (47p)
U-DEC A	£3.98 (51p)
U-DEC B	£6.98 (81p)

IC carriers 16 diode—plain. 81p (15p); with sockets. £1.77 (25p). 10 TO5—plain. 78p (15p); with socket. £1.88 (24p).

Experiment guides: A £1.50 (26p); B £1.77 (29p); C 90p (15p); D £2.40 (35p); E £4.20 (53p).



SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ
Please add the sum shown in brackets after the price to cover the cost of post and VAT.
Official credit orders from schools, etc., welcome.
No VAT charged on overseas orders

PARTRIDGE MAINS ISOLATION TRANSFORMER
Pri: 130-250V. 5V steps. Sec: 240V. 13 amp. £15, carr. pack. £2.25.

GARDNER'S POTTED TRANSFORMER. Pri. 200-250V. Sec. 18V 500mA, 50V 150mA, 6V 250mA output. £1, p.p. 28p.

RIPLEY MAINS TRANSFORMER. Pri: 110V-240V. Sec: 12.5V. 0.125V 750mA/VA 7V:0.7V 1A. £1, p.p. 25p.

MAINS TRANSFORMER. Pri: 100-250V. Sec: 22:0-22 200mA. 22:0-22 100mA/VA 0:24V 20mA. 80p, p.p. 25p.

MAINS TRANSFORMER. Pri: 100-240V a.c. 36:3-0-36.5V. 27mA/VA. 0-21:5. 260 mA/VA. 80p, p.p. 25p.

TRANSISTOR OUTPUT TRANSFORMER. Ratio 8:1. 120mH. Centre tap 2 watts, output. 20p, p.p. 8p.

WODEN MAINS TRANSFORMER. Auto wound. Pri: 200-250V. Sec: 105-135V. 3kVA. £15. Carr. £1.50.

HADDON MAINS TRANSFORMER. Pri: 230V. Sec: 20V 1 amp. £1.60, p.p. 27p.

MIN. MAINS TRANSFORMERS. Type 606/1. Sec: 6V-0-6V. 100mA/VA. 75p. Type 909/1. Sec: 9V-0-9V. 100mA/VA. 81p. Type 1202/1. Sec: 12V-0-12V. 100mA/VA. 86p, p.p. 5p each.

SMOOTHING CHOKE. 11MH, 1 1/2in x 1 1/2in x 1 1/2in. 20p, p.p. 8p.

FINNED ALUMINIUM HEATSINK. 4 1/2in x 6in x 1 1/2in. 2 x 2N3055. £1, p.p. 13p.

GOODMANS 8in SPEAKERS 3Ω £1.50, p.p. 28p.
LOUDSPEAKER 2in Dia., 40Ω. 300m/watt. 50p, p.p. 5p.

FINNED ALUMINIUM HEATSINK. 9in x 8in x 1 1/2in. 4 x 2N3055. £2, p.p. 29p.

GARRARD MAG. TAPE DECKS: 1 1/2in. 50V. solenoid operated brakes, etc. Mains voltage motors £7.50 each, p.p. 60p.

10 REED SWITCHES operated by push buttons and magnets. 50p, p.p. 25p.

COMPONENT PANEL, 6 ser's (300V, 1.6A) 6 cond., 12 resistors, 6 diodes. 45p, p.p. 8p.

COMPONENT PANEL, 6 ser's (200V 4 amps), 6 condensers, 12 resistors. 30p, p.p. 8p.

COMPONENT PANEL, 1 ser: 100V, 1.5 amp, 1 diode, 1 cap., 500mfd 50V. 50p, p.p. 7p.

VEEDER ROOT ELECTRICAL IMPULSE COUNTER NON-RESETTING, A.C. 200-250V, £1.10, p.p. 13p.

GEC MAINS CIRCUIT BREAKERS, 2 amp or 3 amp. £1 each, p.p. 14p.

LEVER ACTION P.O. 1000 TYPE SWITCHES
Lock 4-pole changeover. 15p, p.p. 4p. Ex equip. Lock 2-pole changeover. 10p, p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4.500µF 64V, 7.100µF 40V, 50p each. 20,000 30V, 25,000 25V, 35,000 15V. 30p each, p.p. 21p.

MULLARD FULLWAVE RECTIFIERS 6-48V, 1.5 amp, 75p, p.p. 10p.

BELLING LEE 1.5 amp in-line rubber covered interference suppressor. 25p, p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT PULL ACTION 2 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 5p.

SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 1 1/2in, 50p, p.p. 9p.

SOLENOIDS. Manf. by Bensons. 240V a.c. Pull action 2 1/2in x 1 1/2in x 1 1/2in, 75p, p.p. 9p.

OMRON MK2 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New. 70p, p.p. 5p.

STC VARLEY, miniature relays 700Ω, 17.5-37V, perspex cover, 4 pole changeover. 40p, p.p. 5p.

POTTER BRUMFIELD 12V d.c. coil 3 pole c/o contacts rated 7 amp., £1, p.p. 10p.

I.T.T. LOW PROFILE RELAYS. 4 pole c/o vers. 500Ω 12-18V. 75p, p.p. 5p.

MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts. 50p, p.p. 7p.

KEYSWITCH RELAY, 12V d.c. Coil 3.8P.C.O. 80p, p.p. 5p.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base. 23p, p.p. 3p new.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200
Diodes: 1 reed relay: 1 AZ 229 zener ass. capacitor/resistor. Power supply 22V, 250 mA d.c. 240V a.c., £1, p.p. 25p. Ex. equip.

TAPE POSITION INDICATOR
Re-settable 3-digits. 30p, p.p. 3p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED

3 Shenley Road
Borehamwood, Herts.
Tel. 01-953 6009

BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs. 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. OFT-1 chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES

LATEST ADDITIONS INCLUDE PITCH-TO-VOLTAGE AND SEQUENCER MODULES! AND MANY OTHERS.

CASH SAVINGS

by buying modules and parts in bulk! All modules are available separately: Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5.50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

FERRANTI

- ★ ALL DEVICES BRAND NEW, TOP GRADE AND TO FULL SPECIFICATION. We sell only best quality stamped devices from the maker's current production.
- ★ WE HAVE STOCKS OF ALL DEVICES FOR IMMEDIATE DELIVERY.
- ★ WE CAN SUPPLY ANY FERRANTI DEVICE TO ORDER. Send S.A.E. for quotation.
- ★ WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS, WITH A STAFF OF EXPERIENCED ENGINEERS.

SCORPIO Mk. II Printed circuit 97p

FULL KIT OF SEMICONDUCTORS £4.70 (State 6V or 12V)		Siemens BStBO246 SCR £1.25
BFS59 18p	ZTX310 12p	ZTX504 55p
BFS60 21p	ZTX311 14p	ZTX510 17p
BFS61 21p	ZTX312 14p	ZTX530 29p
BFS96 19p	ZTX313 16p	ZTX531 34p
BFS97 23p	ZTX314 17p	ZTX550 25p
BFS98 23p	ZTX320 31p	ZTX551 27p
ZTX107 12p	ZTX330 21p	2N3055 76p
ZTX108 9p	ZTX331 23p	* DIODES *
ZTX109 14p	ZTX382 15p	ZS120 8p
ZTX112 14p	ZTX383 19p	ZS121 10p
ZTX213 15p	ZTX384 23p	ZS122 13p
ZTX214 19p	ZTX450 23p	ZS123 16p
ZTX300 16p	ZTX451 25p	ZS124 18p
ZTX301 17p	ZTX500 16p	ZS140 25p
ZTX302 23p	ZTX501 17p	ZS141 43p
ZTX303 18p	ZTX502 23p	ZS142 33p
ZTX304 29p	ZTX503 18p	ZS170 10p
		ZS171 13p
		ZS172 16p
		ZS174 17p
		ZS176 23p
		ZS178 38p
		ZS270 11p
		ZS271 16p
		ZS272 18p
		ZS274 19p
		ZS276 26p
		ZS278 37p
		* ZENERS *
		KS030A to
		KS180A
		all types 19p

MOTOROLA MJE2955 £1.30, MJE3055 75p each.
RCA PRICES SLASHED! CA3090Q £3.25 each.
PE TRIFFID ZT1711 24p, 2N1132 25p.

ZN414 £1.32 WITH CIRCUITS AND DATA

FREE! Our comprehensive catalogue giving data and connection diagrams for a wide range of Ferranti semiconductors. Just send an S.A.E. Copy sent with every order.

POSTAGE & PACKING 10p. FREE ON ORDERS OVER £2
ALL OUR PRICES INCLUDE V.A.T.

DAVIAN ELECTRONICS

P.O. BOX 38, OLDHAM, LANCS. OL2 6XJ

BAKER 12" MAJOR £11.55

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £14.85

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 12 1/2in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £10.45	Superb 12 in. 20W £18.70	New Group 50/12 12 in. 50W
Major 12 in. 20W £11.55	Group 25 12 in. 25W £10.45	30-16000 cps. £17.60
Deluxe 12 in. 15W £13.20	Group 35 12 in. 35W £11.55	

BAKER LOUDSPEAKER CO., BENSAM MANOR PASSAGE
THORNTON HEATH, SURREY. Tel. 01-684-1665
PRICES INCLUDE VAT. HI-FI ENCLOSURE PLANS 42p

VARICAP TUNER

LP1185/86	£10.25/pair
MC1310P Decoder I/C	£3.15
LP1400 Decoder Module	£4.96
MFC4060 Regulator I/C	£0.78
P.C. BOARDS MC1310P or LP1400	£1.87

(state which decoder)

READY BUILT BOARDS £24.25 (I/C) or £25.25 (LP1400)

Prices include V.A.T. P. & P. 25p.

B. & B. ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK, NOTTS.
Tel.: NEWARK 6895 (Anytime)

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course". — Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". — Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". — Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. Write to **B.I.E.T. Dept. BPE01, Aldermaston Court, Reading RG7 4PF.**

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd. Publishers' Subscription Rate (including postage): Inland £3.25, Overseas £3.50.

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know

about **Radio & Electronics**

maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers—A.M.S.E. (Mech.) <input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work <input type="checkbox"/> Eng. Inspection <input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) <input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Elec. Draughtsmanship <input type="checkbox"/> Architectural Draughtsmanship <input type="checkbox"/> Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works <input type="checkbox"/> Construction Surveyors Institute—L.C.S.I. <input type="checkbox"/> CITY & GUILDS General Building (all branches) <input type="checkbox"/> Heating & Vent. Inst. Clerk of Works <input type="checkbox"/> Site Surveying <input type="checkbox"/> Health Engineering <input type="checkbox"/> Road Construction Quantities, Estimates <input type="checkbox"/> Hydraulics <input type="checkbox"/> Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers—A.M.S.E. (Elec.) <input type="checkbox"/> CITY & GUILDS Gen. Electrical Engineering <input type="checkbox"/> Electrical Installations <input type="checkbox"/> Electrical Maths <input type="checkbox"/> Computer Electronics <input type="checkbox"/> Electronic Eng. <input type="checkbox"/> Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS CITY & GUILDS Radio, TV, Electronics <input type="checkbox"/> CITY & GUILDS Telecoms <input type="checkbox"/> Gen. Radio & TV Eng. <input type="checkbox"/> Radio Amateurs Exam <input type="checkbox"/> Radio Servicing <input type="checkbox"/> TV Servicing <input type="checkbox"/> Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. <input type="checkbox"/> Council of Eng. Institutions <input type="checkbox"/> Farm Science <input type="checkbox"/> Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Acctnts. <input type="checkbox"/> Computer Programming <input type="checkbox"/> Works M'nt. <input type="checkbox"/> Work Study <input type="checkbox"/> Gen. Production Eng. <input type="checkbox"/> Estimating & Planning <input type="checkbox"/> Storekeeping <input type="checkbox"/> Management Skills <input type="checkbox"/> Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I. MAA IMI <input type="checkbox"/> CITY & GUILDS Auto Eng. <input type="checkbox"/> Gen. Auto Eng. <input type="checkbox"/> Motor Mechanics <input type="checkbox"/> Auto Diesel Eng. <input type="checkbox"/> Garage M'nt. <input type="checkbox"/> ARB Aero Engineering Certs. <input type="checkbox"/> Gen. Aero Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
	<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers—A.M.S.E. (Civ.) <input type="checkbox"/> Institute of Building—L.I.O.B.	<input type="checkbox"/> G.C.E. — choose from 58 'O' & 'A' level subjects.
		<input type="checkbox"/> Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE01, Aldermaston Court, Reading RG7 4PF

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____

AGE _____

Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors—Up to date
Brochures on request

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept 1974

You pay less
VAT with Henry's
Low Prices



Now built and
used by thousands
of satisfied cus-
tomers.

FEATURES: slim
design, overall size in
cabinet 15 1/2in x 2 1/2in x 6 1/2in

6-IC's, 10 transistors, stabilisers,
Gardners low field transformer, Fibre
Glass PC Panel, complete chassis work.
Now available built and tested as well
as in kit form.

**HIGH QUALITY & STABILITY ARE
PREDOMINATE FEATURES—DEVELOPED
TEXAS ENGINEERS FOR PERFORMANCE, BY
RELIABILITY AND EASE OF CONSTRUCTION.**

FACILITIES. On/off switch indicator, headphones
socket, separate treble, bass, volume and balance controls,
scratch and rumble filters, mono/stereo switch, input selector:
Mag, P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc.
Constructional details Ref. No. 21, 30p.
Distributed by Henry's throughout UK.

FREE Teak cabinet with complete kit.

KIT (+ VAT + 50p
PRICE **£28.50** carr/packing) or
built and (+ VAT + 50p
£35.00 carr/packing)
tested as illustrated

BUILD THE TEXAN

**20 + 20 WATT IC STEREO
AMPLIFIER**

As featured by
Practical Wireless 1972



BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner.
Features variable capacity diode tuning, stabiliser power supply, IC
Decoder, high gain low noise, IF stages, LED
indicators, Tuning meter, AFC,
Easy to construct and use.
Mains operated. Slim
modern design with fibre
glass PC, teak cabinet,
etc. Available as a kit to
build or ready built.
Overall size: 8in x 7 1/2in
x 6 1/2in. Produced to give
high performance with a
realistic price. (Parts list
and constructional details
Ref. No. 5, 30p.) Henry's
are sole distributors UK and Europe.




Kit Price £21.00 (+ VAT)
or built and tested **£24.95 (+ VAT)**

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



DISCO MINI: A complete portable disco,
fitted mixer/preamp, 2 decks all facilities... £98.50
As above but with Slider Controls... £118.50
100 watt amplifier for above... £49.50
SDL5100: 100 watt mixer/amplifier with
slider controls... £69.00
R50: 50 watt mixer/amplifier... £49.50
R100: 100 watt mixer/amplifier... £57.50
DISCO AMP: 100 watt mixer/amplifier
Northcourt... £73.00
400 40 watt mixer amp... £37.50
800 80 watt mixer amp... £45.00
DISCO MIXER/PREAMPLIFIERS (O/P
for up to 6-100 watt amplifiers):
SDL1 (rotary controls)... £49.50
SDL11 (slider controls)... £58.50
DISCO VOX (slider controls): The com-
plete disco preamp... £72.00
DJ100: 100 watt power amplifier for above... £49.50
DJ30L Mk II 3 channel 3kW sound to light... £41.25
DJ30L Mk III. Slider Controls... £45.50
DJ DISCLITE. As 30L/II + Variable speed
flashes... £54.00
Carlsbro Reverberation Unit... £44.00
Disco anti-feedback microphone... £11.95
Colt 150 watt liquid wheel projector... £23.50
150 watt Q1 liquid wheel projector... £50.00
150 watt Q1 cassette wheel projector... £50.00
Spare Effects and Liquid cassettes, large
range of patterns... £6.00
6in liquid wheel Various Cassettes... £6.00
Mini spot bank fitted 3 lamps... £12.95
Auto Trilite (mini with flashers)... £17.00
Bubblemaker with 1 gal. liquid... £22.50
MIXERS/MICS/SPEAKERS/LIGHTING
U.K.'s largest range of Disco lighting
FREE STOCK LIST Ref. No. 18 ON REQUEST
**AKG/RESLO/DJ/CARLSBRO/EAGLE
CHASSIS AND COMPLETE SPEAKER
SYSTEMS, MEGAPHONES, TURNTABLES,
PUBLIC ADDRESS COMPONENTS, MICS.,
STANDS, MIXERS, CABINETS**

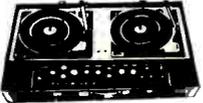

All prices carr. paid (UK) (VAT EXTRA).
Barclaycard/Access call, write or phone your order
01-723 6963—easy terms for callers.

EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter
systems. 8in Bass/Midbore
and Melinex Domed HF radiator plus
crossover £12.50 per pair of systems
(carr/packg. 40p) or built into ven-
eered cabinets, size 18 x 12 x 6 1/2in.
£19.50 pair (carr. £1).

HI-FI TAPE EQUIPMENT



U.K.'s largest range
with discounts and
demonstrations for
callers. Latest stock lists on request
(Ref. No. 17).
Phone 01-402 4736 for Barclay/Access
Card, Direct orders and latest prices.

TRANSISTORS/ SEMICONDUCTORS

U.K.'s largest range for every appli-
cation. Small quantity discounts.
Also Trade, Export and Industrial
enquiries invited. Latest stock list
(Ref. No. 36). Including valves on
request.

ELECTRONICS SUPPLIES

Specialists in electronics for more
than 30 years. Trade and industry
supplies—every type of component
and equipment.

SINCLAIR PROJECT 80



Stereo Preamplifier... £11.95
Audio Filter Unit... £6.95
Z40 15 watt Amplifier... £5.45
Z60 25 watt Amplifier... £6.95
PZ5 Mod. for 1 or 2 Z40... £4.98
PZ6 Mod. (S Tab) 1 or 2... £7.98
Z40... £7.98
PZ8 Mod. (S Tab) 1 or 2... £7.98
Z60... £7.98
TRANSFORMER FOR... £3.95
PZ8... £11.95
NEW FM TUNER... £7.45
STEREO DECODER... £7.45
All items post paid.

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN + REC. PRICES. COMPLETE WITH LIBRARY CASES.

	3 for	6 for	10 for	25 for
C60	£1.10	£1.98	£3.00	£7.40
C90	£1.46	£2.80	£4.60	£11.25
C120	£1.80	£3.45	£5.50	£13.45



Quantity and trade enquiries invited.

LEARN A LANGUAGE—complete with phrase book. German,
French, Spanish, Italian. £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS SPECIAL OFFERS

EMI 13in x 8in—full range speakers (post 20p each or 30p pair);
*150TC—8 ohms Twin Cone 10 watt, £2.20 each or £4 pair; *450 10
watt c/o Twin Tweeters 3, 8 or 15 ohms, £3.85 each; EW 15 watt 8
ohms c/o Tweeter, £5.25 each; 350 20 watt c/o Tweeters 8 or 15
ohms, £7.80 each.
* Polished wood cabinet: £4.80, post 35p.

8 ohms full range (post 20p)
FR4 4in 5 watt, £3.75; FR6 6 1/2in 10 watt, £6.30;
FR8 8in 15 watt, £8.50; FR23 9 x 6in 15 watt,
£8.40.



BASS AND MID RANGE—8 ohms (post 20p)
AA12 5in 15 watt, £3.75; B110 5 1/2in 15 watt,
£7.20; B200 8in 15 watt, £8.50; B139 2 1/2in x 8in
30 watt LF, £13.75.

TWEETERS AND CROSSOVERS (post 20p)
K2006 10 watt 8 or 15 ohms, £2.10; FH76 15 watt 8 ohms, £3.35; K2011
30 watt 8 ohms, £4.80; T27 KEF, £5.50; Axent 100 30 watt 8 ohms
£5.50; K4009 1kHz/5kHz c/o, £2.70; SN75 3kHz var. c/o, £3.10.

SPEAKER KITS (carr. etc. 35p)
20-2 Bin 30 watt, £24.50 pair; 20-3 Bin 40 watt, £35.95 pair; LINTON 2
20 watt, £18.30 pair; GLENDALE 3 30 watt, £32.95 pair; D QVEDALE E
50 watt, £51.50 pair; KEF KK2, £55.00 pair; KEF KK3, £78.00 pair.

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene con-
tainer and taking about 3 hours to assemble—
that's the Sinclair Cambridge pocket calculator
from Henry's. Some of the many features include
interface chip, thick-film resistor pack, printed
circuit board, electronic components pack.
Size: 4 1/2in long x 2in wide x 1 1/2in deep.
Free of charge with the kit for the more advanced
technologist is a 32-page booklet explaining how
to calculate Logs, Tangents, Sines, etc.



Price **£19.95 (+ VAT)**

Also assembled **£22.50 (+ VAT)**
ready to use

10% VAT to be added to all orders. EXPORT SUPPLIED. Prices and descriptions correct at time of proof. Subject to change without notice
E & O E. See page 571 of this magazine.

Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

**Henry's RADIO
LIMITED**
EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 PA—Disco—Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burns Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm six days a week
Hi-Fi—Tape Equipment
Discount Stock List
Free at all stores