


PRACTICAL

ELECTRONICS

AUGUST 1974

25p

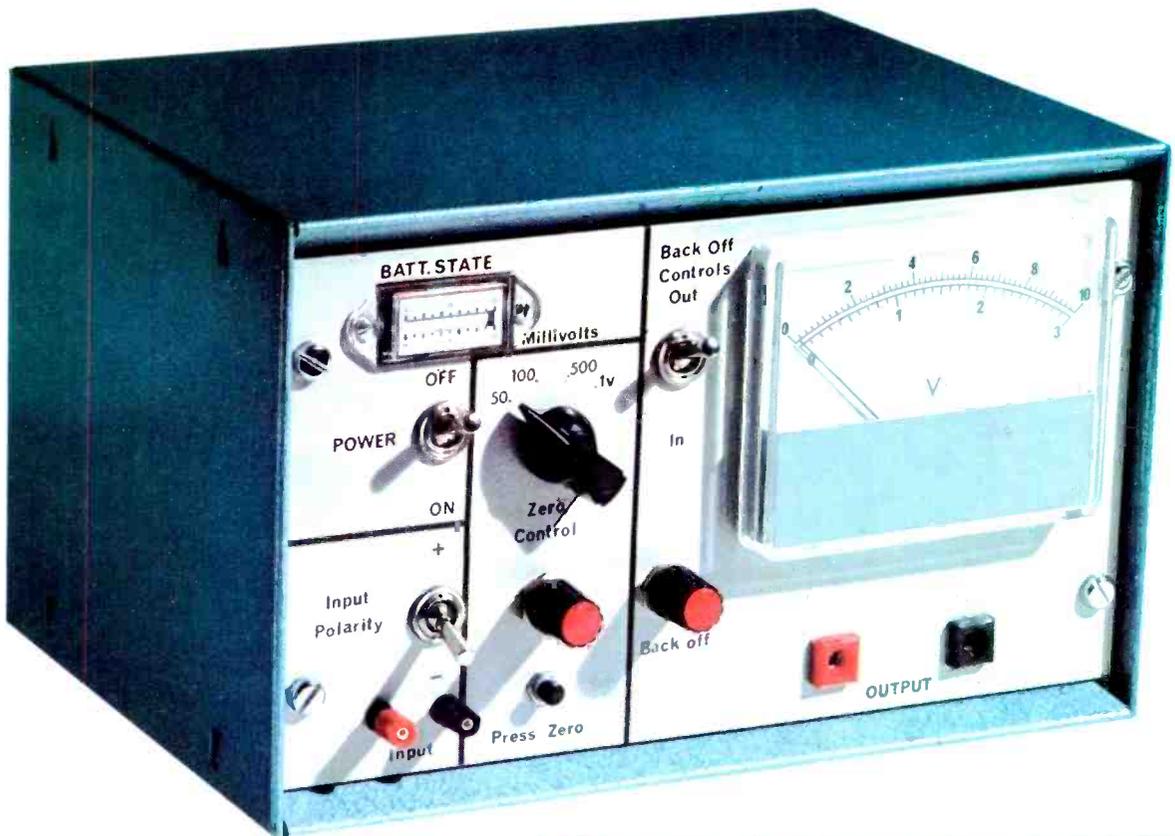OPEN THE DOOR TO LOW COST
SCIENTIFIC EXPERIMENTS ...



...WITH OUR **HIGH IMPEDANCE
VOLTMETER**

FOR UNDERWATER PHOTOGRAPHY

SUB-AQUA COLOUR TEMPERATURE INDICATOR

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN PNP
- 4 Transistor Push Pull Amplifier
- 6 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

TOTAL BUILDING COSTS


£7-23 P.P. & INS. 44p
(Overseas P.P. £1-85p)
(+10% VAT 72p)

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 31 Loudspeaker ● Earpiece ● Misc Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Timing Condenser ● 3 Knobs
- Really Wound MW/LW/SW Coils ● Ferrite Rod ● 61 yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 60p (free with parts)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

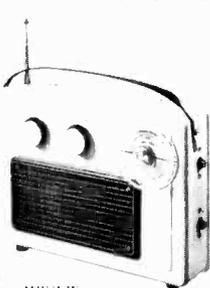

Nine Transistors, 9 Tunable wavebands, 8 Roamer Ten Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wave change controls. Attractive all white case with red grille and carrying strap. Size 9 1/2 in x 7 in x 2 1/4 in approx. Parts price list and plans 30p (FREE with parts).


TOTAL BUILDING COSTS **£6-95** P.P. & INS. 44p (OVERSEAS P. & P. £1 85) (+10% VAT 69p)

POCKET FIVE

3 Tunable wavebands, MW/LW and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 4 1/2 in x 1 1/2 in x 3 1/2 in approx. Plans and parts price list 15p (FREE with parts).

Total Building Costs

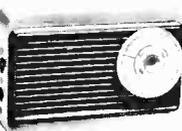£2-50 (+10% VAT 26p) P.P. & Ins. 26p (Overseas P.P. £1-25)



Total Building Costs **£2-75** P.P. & Ins. 26p (+10% VAT 27p) (Overseas P. & P. £1-25)

TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 16p (FREE with parts).

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker, 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 in x 3 1/2 in x 2 1/4 in approx. Push pull output. Battery commensur switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

£4-48 P.P. & INS. 33p (OVERSEAS P. & P. £1-25) (+10% VAT 44p)

ROAMER SIX CASE AND LOOKS AS TRANS EIGHT

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker, 8 stages, 5 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 in x 3 1/2 in x 2 1/4 in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS

£3-98 P.P. & IN. 31p (OVERSEAS P. & P. £1-85) (+10% VAT 39p)

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes, MW/LW. Powered by 41 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9 in x 3 1/2 in x 2 1/4 in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£2-95** P.P. & INS. 30p (OVERSEAS P. & P. £1-25) (+10% VAT 29p)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 31 loudspeaker, etc., MW/LW coverage, Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£3-60** P.P. & INS. 30p (OVERSEAS P. & P. £1-25) (+10% VAT 36p)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery. Push Pull Output. Telescopic Aerial for Short Waves. 3 Loudspeaker. Parts price list and easy build plans 20p. Free with parts.


TOTAL BUILDING COSTS **£4-08** P.P. & INS. 31p (OVERSEAS P. & P. £1-85p) (+10% VAT 40p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Air spaced gauged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 in x 7 in x 4 in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

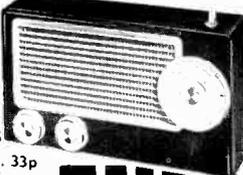TOTAL BUILDING COSTS **£6-98** P.P. & INS. 47p (OVERSEAS P. & P. £1 85) (+10% VAT 69p)



ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Gauged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone control. Attractive case in black with silver blocking. Size 9 in x 7 in x 4 in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£8-50** P.P. & INS. 52p (OVERSEAS P. & P. £1-85) (+10% VAT 85p)

5 units including master unit to construct.

Components include: Tuning Condenser, 2 Volume Controls, 2 Slider Switches, Fine tone 3" moving coil Speaker, Terminal Strip, Ferrite Rod Aerial, Battery Clips, 4 Tag Boards, 10 Transistors, 4 Diodes, Resistors, Capacitors, Three 1in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£5-50** P.P. & INS. 33p (OVERSEAS P. & P. £1-85) (+10% VAT 55p)



EDU-KIT

Build Radios Amplifiers, etc., from easy stage, diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser, 2 Volume Controls, 2 Slider Switches, Fine tone 3" moving coil Speaker, Terminal Strip, Ferrite Rod Aerial, Battery Clips, 4 Tag Boards, 10 Transistors, 4 Diodes, Resistors, Capacitors, Three 1in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52367 Reg. No. 788372

I enclose £ for
Name
Address

PEB

PRACTICAL ELECTRONICS

VOLUME 10 No. 8 AUGUST 1974

CONSTRUCTIONAL PROJECTS

- HIGH IMPEDANCE VOLTMETER** *by T. P. Manning & R. Hider*
Scientific measurements made possible with this simple but effective instrument 678
- P.E. POWER SLAVES** *by B. Reeson*
Concluding constructional information for the Power Slave family 699
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—9** *by R. A. Cole*
Completion of the F.M. Stereo Tuner construction 706
- SUB-AQUA COLOUR TEMPERATURE INDICATOR** *by O. N. Bishop*
Indicates which filter to use to obtain perfect colour photographs either above or below water 716

GENERAL FEATURES

- FIRST STEPS IN CIRCUIT DESIGN—5** *by A. P. Stephenson*
Circuits with high input impedance 684
- INGENUITY UNLIMITED**
D.C./D.C. Converter—Heatsink 691
- ELECTRONICS IN SEISMIC EXPLORATION** *by M. J. Hughes*
Techniques used to find the World's subterranean sources of natural wealth 692

NEWS AND COMMENT

- EDITORIAL**—The Constructor's Lot 677
- NEWS BRIEFS**
Information Retrieval—Calling China—Traffic Control—Next Decade 687
- SPACEWATCH** *Frank W. Hyde*
Technology Satellite—Domestic Satellite 688
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith*
Keyboard instruments 696
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 704
- IEA EXHIBITION REPORT**
A look at the latest trends from industry 710
- ESP ETC.** *by B. H. Baily*
Random timer results and news from overseas 713
- PATENTS REVIEW**
Motor Control—Light Operated Clock—False Start Detection 715
- READOUT**
A selection of readers' letters 722

Our September issue will be published on Friday, August 9, 1974

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £3.50. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors - Up to date
Brochures on request

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.



**UK's
LARGEST RANGE
OF KITS &
GADGETS**

TEST EQUIPMENT MULTIMETERS

- (Carr. etc. 30p)
- IT1-2 20K/Volt Slimline £5.95
- M110 (Case £1.25) 20K/Volt
- Slimline deluxe £6.75
- TLH33D 2K/Volt Robust £7.50
- U4323 (+IF BAF OSC) £7.00
- AF105 (Case £1.90) 50K/Volt £12.50
- U4313 20K/Volt AC current. Steel case 10.50
- U4341 Plus Built-in transistor tester 10.50
- Model 500 (Case £2.25), 30K/Volt 11.75



OTHER EQUIPMENT

- SE2508 Pocket Signal Injector 2.25 carr. 15p
- TE15 Grid Dip meter 440kHz 280mHz 16.50 carr. 30p
- TE40 AC Millivoltmeter 1 2mHz 19.75 carr. 35p
- TE65 28 Range valve voltmeter 22.50 carr. 40p
- TE20D 120kHz-500mHz RF Gen. 18.95 carr. 40p
- TE22D 20Hz-200kHz Audio Gen. 19.95 carr. 40p
- SE350A Deluxe Signal Tracer 12.95 carr. 20p
- SE400 Volts/ohms/IR-C sub./RF field/RF gen. 15.50 carr. 30p

New Revolutionary Supertester 680R

- | 680R Multi-tester £18.50 | Accessories | Price |
|--------------------------|----------------------|-------|
| Transistor tester | Electronic voltmeter | 11.00 |
| Amplifier | Temperature probe | 11.95 |
| Gauss meter | Signal injector | 11.95 |
| Phase Sequence | EHT Probe | 5.95 |
| Shunts 25/50/100A | | 4.50 |

A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester 6.95 p & p 15p
- Q4002 Photoelectric System £13.70
- E1310 Stereo mag. cart. preamp. 4.80 p & p 25p
- Exiphone D1201 telephone amp 7.50 p & p 25p
- D1203 Telemag. with PU coil 4.95 p & p 20p
- LL1 Door Intercomm. and chime 8.40 p & p 25p
- 9" Twin spring unit For 3.30 p & p 15p
- 16" Twin spring unit Reverbs 6.85 p & p 25p
- US50 Ultrasonic Switch Trans/Rec £12.75
- C3041 1-250mHz £4.25
- C3043 5CH 1-300mHz £5.75
- VHF 105 Aircraft Band Converter 4.50 p & p 15p
- B2005 4 Ch. mic. mixer 4.20 p & p 15p
- B2004 2 ch. Stereo mixer 6.75 p & p 15p
- PK3 Kit £1.95 p & p 20p

EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO
— Earth with speaker and fixings. £6.50 c/p 30p.
8 TRACK CAR STEREO
(— Earth) with speakers in Pods and fixings £12.50 c/p 40p. Portable Batt./Cass. Tape Player £7.25.
Car Lighter Plug and adaptor for all cassette and radio 6/7/9 V output (state width) £1.95 each.
Rotel Stereophones RH630 £6.80, RH700 £10.25, RH430 £4.14. Rotel RA310 15+15 watt Stereo Amplifier (List £52.00) £34.52. Vem W500 Battery/Mains Cassette Recorder £12.75.

PORTABLE CASSETTE TAPE PLAYER— for car or carry around. £7.25 c/p 20p. HANIMAX BC808 POCKET CALCULATOR WITH % KEY. £28.95. HANIMAX BC811M MEMORY VERSION £33.75. *BCM807 % key + memory £33.95. *MAINS UNIT £3.25 EXTRA. HANIMAX HI01 STEREO COMPACT RECORD PLAYER 2 7 watts. Complete with Speakers (List £54.50) Price £39.95 (Plus free pair of stereo phones).

BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600mV output. All parts £7.98 (battery 22p). carr. etc. 32p.



FIBRE OPTICS

0.01 diam. Mono Filament £5.50 per 100 metre reel
0.13 diam. 64 Fibres Sheathed £1.00 per metre.
SPRAYS 15mm diam. (Mare's Tail Spray £10.50).

SPECIAL PURCHASES

UHF TV TUNERS CHANNELS 21 TO 64
Brand new transistorised geared tuners for 625 Line Receiver IF output. £2.50. Post 20p.



EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

- | Model No. | £ p | Model No. | £ p |
|---------------------------------------|-------|--|-------|
| 310 Radio control receiver | 3.29 | 760 Acoustic switch | 12.57 |
| 300 4-channel R/C transmitter | 6.61 | 780 Metal Detector (electronics only) | 10.91 |
| 345 Superhet R/C receiver | 6.61 | 790 Capacitive Burglar alarm | 7.92 |
| 65 Simple transistor tester | 1.66 | 835 Guitar preamp. | 4.99 |
| 115 8 watt Amplifier | 4.50 | 840 Delay car alarm | 6.99 |
| 120 12 watt amplifier | 4.73 | 875 CAP Discharge ignition (for car engine—V.E. Earth) | 13.99 |
| 125 Stereo control unit | 6.01 | 80 Scope Calibrator | 2.65 |
| 130 Mono control unit | 4.16 | 255 Level Indicator | 6.98 |
| 605 Power supply for 115 | 5.31 | 525 120-160mHz VHF timer | 11.31 |
| 610 Power supply for 120 | 5.31 | 715 Photo cell switch | 8.97 |
| 615 Power supply for 2 - 120 | 6.64 | 795 Electronic continuity tester | 4.97 |
| 230 AM/FM aerial amplifier | 3.29 | 860 Photo timer | 15.51 |
| 240 Auto packing light | 6.90 | 235 Acoustic Alarm for driver | 8.61 |
| 275 Mic. preamplifier | 6.98 | 465 Quartz XTAL checker | 9.90 |
| 5705 LF generator 10Hz-1mHz | 21.45 | 220 Signal Injector | 2.30 |
| 5755 Sq. wave generator 20Hz-20kHz | 19.77 | 390 VOX | 15.50 |
| 590 SWR meter | 9.47 | 432 Testakit | 19.30 |
| 630 STAB Power supply 6-12V 0.25-0.1A | 9.24 | 670 Buffer Battery | 6.55 |
| 690 DC motor speed Gov. | 3.31 | 885 Capacitive Contact Alarm | 6.25 |
| 700 Electronic Chaffinch | 7.92 | 850 Electronic Keyer | 18.75 |
| | | 820 Electronic Digital Clock | 58.50 |



ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY
Prices correct at time of preparation.
Subject to change without notice.

BUILD THIS TUNER M13

MW/LW Radio Tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £5.25, carr. 15p.

MULLARD FM MODULES

- LPI186 Tuning Heart Module
- LPI185 IF Module complete with data Price £9.00 pair

FM TUNER MODULE

- FM 5231 12v FM Tuner £7.95
- SD4912 Stereo Decoder £7.95
- SF62H 6v Stereo FM Tuner £14.95

TBA800 5 WATT I.C.

Suitable alternative to SL403D. 5/30 volt operated. 816 ohm 5 watt output. With circuits and data £1.50

Kit with printed circuit panel £2.70
All kits available from stock

SINCLAIR SPECIAL OFFER

Stereo 60 Pre-amplifier—for use with most small amplifiers. Exclusive offer £6.75

STROBE TUBE

- ZFTA4 Suitable for Dec. 773 Pract. Electronics. £3.50
- MSU1/40 SCR 25p
- ZFT4 £3.50
- ZFT8 £4.00

PP9 ELIMINATOR KIT

Complete module kit 9v 100mA output £1.95 p & p 25p

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT to be added to ALL ORDERS. UK post, etc. 15p per order unless stated.



U.K.'s LARGEST RANGE OF TRANSISTORS & DEVICES

JUST A SELECTION

- *TBA800 5W IC £1.50
- *Sinclair IC12 6W IC £2.00
- *ZN4141C Radio IC £1.20
- *Ultrasonic Transducers £5.90 pr.
- *3015F 75EG Indicator £1.70
- TIL 209 LED 24p each 22p each per 10
- *With circuits/data sheet.

OVER 1,500 DIFFERENT SEMI- CONDUCTOR DEVICES IN STOCK

Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s, transistors, triacs, SCR's, LED's, etc. More types—better prices—discounts for quantity small or large.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9.50 carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).
Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.
Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 65p each.
(Quantity discounts available)
Complete with knobs.

MARRIOT TAPE HEADS

- 4 TRACK MONO or 2 TRACK STEREO
- "17" High Impedance
- "18" Med. Impedance £3.50
- "36" Med. Impedance £5.00
- R730/E73 2 track mono Record/Erase low imp. 75p pair
- Erase Heads for "17" "18" and "36" £1.00
- "63" 2 track mono High Imp. £1.75
- "43" Erase Head for "63" 75p
- (Post, etc. 15p any quantity).

SINCLAIR MINIATURE AMPLIFIERS & TUNER/DECODER

- AMPLIFIERS (carr., etc. 20p)**
- 4-300, 0.3 w 9 volt 1.75
 - 104, 1 watt 9 volt 3.10
 - 304, 3 watt 9 volt 3.95
 - 555, 3 watt 12 volt 4.10
 - IE1208, 5 w 12 volt 5.10
 - 608, 10 w 24 volt 4.95
 - 410, 10 w 28 volt 4.45
 - IE1206, 30 w 45 volt 9.95
 - IE1210, 2 1/2 w watts 12 volt 8.25
 - RES05, 5 watt IC mains operated Amplifier with controls 6.30
 - SAC14, 7 + 7 watt Stereo with controls 11.75
 - SAC13, 15 + 15 w Stereo with controls 14.95
 - SP40-5 22/40 Stereo 80/PZ5 25.00
 - SP40-6 22/40 Stereo 80/PZ6 27.75
 - SP60 22/60 Stereo 80/PZ8 30.45
 - Transformer PZ8 3.95

POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
470C 6/7/9 volt 300 mA (includes Multi-Adaptor for Tape Recorders, etc.) 2.25 post 20p
Car Lighter Voltage Adaptors 300mA (State voltage 6V, 7.5V, 9V) 1.95 ea. post 25p
SC202 3/6/7.5/9 volt 400mA 4.25 carr. 30p
HC244R Stabilised version 5.50 carr. 30p
P500 9 volt 500mA 3.20 post 20p
P11 24 volt 500mA (chassis) 2.90 post 20p
P15 26/28 volt 1 amp (chassis) 2.90 post 20p
P1080 12V 1 amp (chassis) 4.70 post 20p
P1081 45V 0.9 amp (chassis) 7.80 post 20p
P12 45-12 volt 0.4-1 amp 7.15 post 20p
SE101A 3/6/9/12 volt 1 amp (Stab.) 13.75 post 20p
RP164 6/7.5/9/12 1 amp (Stab.) 13.45 post 30p




Henry's RADIO LIMITED

EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 PA—Disco—Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

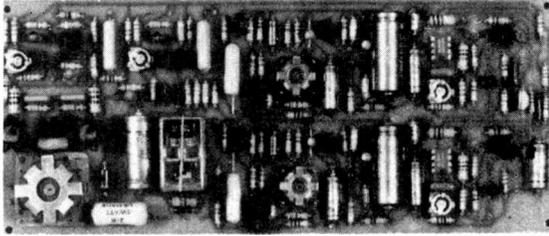All mail to 303 Edgware Road, London W2 1BW
All stores open 9 am to 6 pm six days a week
Hi-Fi—Tape Equipment Discount Stock List Free at all stores



HI-FI TAPE LINK

(PE Mar./Apr. 73). S/c's, i.c's, Rs, Ca, Relay and pc-base, Pot Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, £12.78; Stereo, £29.41. PSU, £3.98. Main Circuit PCB (3 1/2in x 9in) Stereo (also holds relay and cores), £2.10. Sub-assembly PCB (2 1/2in x 6 1/2in), Stereo 80p.

BIOLOGICAL AMPLIFIER

(PE Jan./Feb. 73). P/A Set—S/c's, i.c's, Rs, Ca, Pots, PCB, £3.46. Output Stages—S/c's, Rs, Ca, Pots, Rotary Sw's and PCBs for Alphaphone, Cardlo, Freq-Meter, Via-Feed, £4.96. Audio Amps: PC7, £3.20; EA1000, £3.30.

ENLARGER EXPOSURE METER AND THERMOMETER

(PE Sept. 73). S/c's, Thermistor, LDR, Rs, Pots, PCB, £3.98.

ELECTRONIC PIANO

(PE Sept. 72/Jan. 73). Details in lists.

GEMINI STEREO AMPLIFIER

(PE Nov. 70/Mar. 71). Stereo Sets and PCBs, Pre-amp—Rs, Ca, Pots, Sw's—with 1W MO Rs £14.18—with 1W OF Rs, £18.48, PCB as published, £1.28. Main Amp—Rs, Ca, Pots, £5.88. PCB (3 1/2in x 5in), £1.28. Power supply—Rs, Ca, Pot, £4.96. PCB (2in x 4in), 65p.

AUDIO MILLIVOLTMETER

(PE Feb. 74). S/c's, Rs, Ca, Pots, Sw's, PCBs, £4.95.

MICROPHONE MIXER

(PE Apr. 69). S/c's, Rs, Ca, Pots, PCB (also holds pots), £4.12. While Stocks Last.

8 WATT AMPLIFIER

(PW Nov./Dec. 72) Pre-amp—S/c's, Rs, Ca, Pots, Sw—Mono, £2.50; Stereo, £3.03. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots, and Sw, £1.68. Main Amp—S/c's, Rs, Ca, Pot—Mono, £4.18; Stereo, £3.36. PCB (2 1/2in x 3in) (Mono), 72p, PSU, £3.90.

SOUND SYNTHESISER

(PE Feb. 73/74)

RHYTHM GENERATOR

(PE Mar./June 74)

SOUND BENDER

(PE May 74)

Details of all these in List

REVERBERATION UNIT

(PW Nov./Dec. 72) S/c's, Rs, Ca, T/former—with Rotary Pots, £6.44. PCB (2in x 1 1/2in), £1.40.

LOUDMAILER AND SIREN

(PW Dec. 72) Pre-amp and Siren Generator—S/c's, Rs, Ca, Pot, PCB (2 1/2in x 2 1/2in), £2.20. While Stocks Last. Main Amp Module PCB, £3.25.

MISCELLANEOUS PCBs (While Stocks Last)

LOGICAL RADIO CONTROL (PE Dec. 71/Jan. 72) PCBs "2A", "2B", 50p each. MODEL SERVO CONTROL (PE Feb./Mar. 72) PCBs "B", Fall-safe, 33p each. DIGITAL PSU PCB (PE Aug. 72), 50p. OSCILLOSCOPE P/A PCB (PE Aug. 72), 33p. GEMINI STEREO TUNER PCB (PE Apr. 72), £1.90. TRIFFID PCB (PE Feb. 73), 60p. (The above PCBs are as published) CALLERCORD (PE Jul. 72) Main Control PCB (4in x 7 1/2in)

RESISTORS

1W and 1/2W CARBON FILM MANUFACTURED BY AEI TO DEF 6112A E24 SERIES 1/2W 5% 4E7 to 1M 1/2W 5% 4E7 to 2M2 then 10% to 10M COMPREHENSIVE STOCKS FACILITATE RAPID PROCESSING AS APPOINTED DISTRIBUTORS WE WELCOME TRADE AND EXPORT ENQUIRIES Write or Phone Trade Dept. ERITH 30737

SEMICONDUCTORS

AC128	26p	2N2905	27p
AC176	26p	2N2907	25p
AD181	40p	2N3702	12p
BC107	13p	2N3703	12p
BC108	13p	2N3704	13p
BC109	13p	2N3819	35p
BC147	12p	2N3823E	39p
BC148	12p	2N4871	36p
BC149	12p		
BC157	12p	DIODES	
BC158	12p	1N916	4p
BC159	12p	1N4001	6p
BC182L	12p	1N4002	7p
BC204	14p	1N4004	8p
BC206	14p	1N4005	8p
BC212L	15p	BA145	23p
BCY71	23p	OA91	7p
BFY50	23p	CA200	8p
BFY52	23p	IGP7	12p
BSY95A	12p	1SJ50	11p
MJE2955	116p		
MJE3005	75p		
NKT0033	112p		
OC25	85p		
OC71	140p		
OC84	25p		
ORP12	56p		
TS43	30p		
2N706	13p		
2N914	23p		
2N1304	23p		
2N2219	27p		

INTEGRATED CIRCUITS

709	T05	40p	7447	175p	
723	T05	95p	7473	64p	
741	8P DIL	40p	7488	432p	
747	14P DIL	115p	7815	T0220	220p
748	T05	83p	CA3046	89p	
7400	20p		PA283	168p	
7402	20p		SG342N	189p	
7420	20p				

ELECTROLYTIC (µF/V)

0.47/63	5p	100-10	8p
1.0/63	5p	100-25	8p
2.2/63	40p	100-40	7p
4.7/35	12p	100-63	12p
4.7/63	8p	150-18	8p
8.4/40	8p	150-63	12p
10/25	8p	220-10	8p
10/63	10p	220-18	8p
15/40	15p	220-25	16p
22/10	5p	220-40	14p
22/25	5p	220-63	21p
33/8	5p	470-25	12p
33/40	5p	470-40	18p
33/63	5p	470-63	26p
47/25	5p	680-25	26p
47/40	5p	680-40	48p
47/63	5p	680-63	48p
68/25	5p	1000-10	14p
68/40	5p	1000-18	14p
68/63	5p	1000-25	25p
100/18	5p	1000-40	40p
100/25	25p	1000-63	46p
200/18	5p	2200-25	45p
220/40	5p	2200-40	50p
220/63	5p	2200-63	50p
330/18	5p	3300-63	133p
330/25	35p	3300-100	350p
470/18	60p		
470/25	75p		
470/40	83p		

POLYESTER (µF)

0.01	3p
0.075	3p
0.22	3p
0.33	3p
0.47	3p
0.68	3p
1.0	3p
1.5	5p
2.2	5p
3.3	7p
4.7	9p
6.8	11p
10	14p

TANTALUM BEAD (µF/V)

0.1/35	12p
0.22/25	12p
0.47/35	12p
1.0/35	12p
1.5/35	12p
2.2/35	12p
4.7/35	12p
10/18	12p
15/8	12p
22/18	12p
47/8	12p
100/3	12p

ADD 15p P. & P. ADD 10% VAT to total cost (including P. & P.) SEND S.A.E. (Stamped Addressed Envelope) for Free Itemised List (and with all enquiries please). OVERSEAS COSTS: P. & P. will be charged at cost (most kit weights and postal rates are shown in list). Send International Reply Coupon for Free List & with all enquiries. VAT does not apply to exports. EXPORT ORDERS ARE ALWAYS WELCOME. MAILING LIST SERVICE—details with list. COLOUR CODE identification supplied with most kits and as part of list. PCBs are Fibreglass. Drilled, Tinned, and designed by Phonosonics unless stated "as published". PCB Layout and Circuit Diagram supplied free with Phonosonics-designed PCBs. POTS are rotary unless stated as slider. PRICES correct at time of press E & OE. DELIVERIES subject to availability.

PHONOSONICS PCB'S AND KITS

PHOTOPRINT PROCESS CONTROL

(PE Jan./Feb. 72). For Colour and B & W—finds exposure, controls timing, stabilises mains voltage. S/c's, SCR, LDR, Rs, Ca, Pots, Relay, Keyswitch, T/mtr, £7.98. PCB (3 1/2in x 5 1/2in) also holds pots, Sw, relay, £1.60.

RONDO


(PE Sept. 73/74) Details in List.

PROJECT Q4

(PW Oct. 73/Jan. 74). Multisystem Quadraphonic Decoder. S/c's, i.c's, Rs, Ca, Pots, Makeswitches, £13.74. PSU, £3.17. Set of PCBs, £2.60.

PHASING UNIT

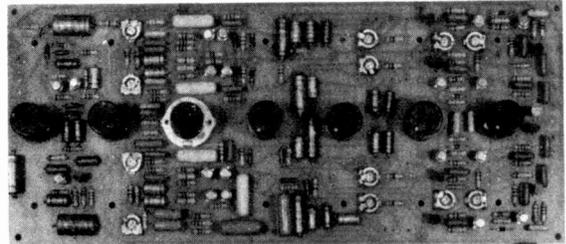(PE Sept. 73). S/c's, Rs, Ca, Pots, PCB (1 1/2in x 2 1/2in), £2.20.



AURORA

(PE Apr./Aug. 71). Multichannel Sound Controlled Light. S/c's (Excl. SCRs), Rs, Ca, Pots, Cores—Pre-amp, Sync Generator and 4 Chans., £18.97; 4 extra chans., £3.35. Reg. PSU, £4.32. PCB (4 1/2in x 10 1/2in) for Pre-amp and 4 Chans. (also holds pots), £2.50. PCB (4 1/2in x 5in) for Sync. Gen. PSU, 8 cores, 8 SCRs, £1.25.

AURORA AUXILIARY CONTROL UNIT

2 Variable Frequency Strobe Generators and 4 Variable Amplitude Frequency Generators. S/c's, Rs, Ca, Pots, PCB (3 1/2in x 5 1/2in), £4.87.

SEMICONDUCTOR TESTER

(PE Oct. 73). S/c's, Rs, Ca, Pot, Makerswitches. Sub-assembly PCB, £5.30.

TAPE NOISE LIMITER

(PE Feb. 72). S/c's, Rs, Ca, Pot, Sw, PCB (1 1/2in x 3in), £2.30. Reg. PSU and PCB (1 1/2in x 2 1/2in), £3.46.

ULTRASONIC TRANSMITTER-RECEIVER

(PE May 72). S/c's, Rs, Ca, Pot, Relay, Dual PCB (2in x 5 1/2in), £4.40. Transducers excluded.

VERSATILE LIGHT EFFECTS UNIT

Single Channel Sound Controlled Light with built-in variable strobs. (PE Jun. 72). S/c's, Rs, Ca, Pot, T/mtr, Keyswitch, £11.28. PCB (3 1/2in x 7 1/2in) also holds pots and switch, £1.70. SCRs excluded. While stocks last.

VIBRASONIC GUITAR PRE-AMP

(PW Sept. 70). Incl. Inc. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Ca, LDR, Rotary Pots, Lamps, Coupling T/mtr, £7.64. PCB (3 1/2in x 10 1/2in) also holds pots, £1.92. Power Supply, £3.90. While stocks last.

VOICE OPERATED FADER

(PE Dec. 73). S/c's, Rs, Ca, Pot, PCB (1 1/2in x 3 1/2in), £2.95.

WIND AND RAIN EFFECTS

(PE Oct. 73). S/c's (Incl. special noise diode), Rs, Ca, Pots, £1.95.

PHONOSONICS, DEPT. PE28, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY

NOW AVAILABLE IN THE U.K!

CHINAGLIA




PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

CORTINA MINOR

33 RANGE POCKET MULTIMETER

- SENSITIVITY 20,000 Ω/VOLT (D.C.), 4,000 Ω/VOLT (A.C.).
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0-100mV, 1.5V, 5V, 15V, 50V, 150V, 500V; 1,500V; D.C. CURRENT 0-50μA, 5mA, 50mA, 500mA, 2.5A; A.C. VOLTS, 0.75V, 25V, 75V, 250V, 750V, 1,500V; A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A; dB RANGES, -10 to +69; AF VOLTS RANGES 0-1,500V; RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100μF, 1F F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT ±0.5%; A.C. VOLTAGE AND CURRENT ±3.5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 x 85 x 40mm, 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

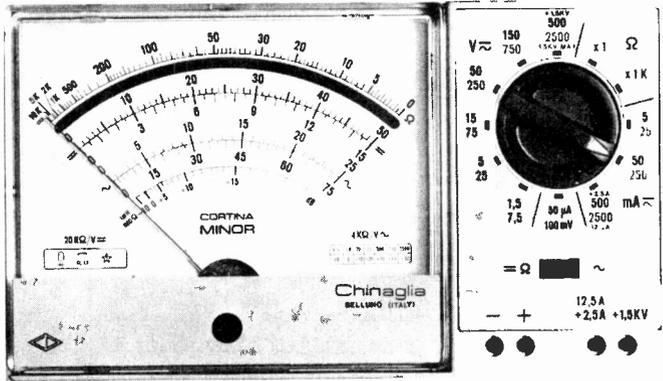

METER PRICE £13.75 (p & p 80p) PROBE £8.00 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone:—

CHINAGLIA (U.K.) LIMITED

19 Mulberry Walk, London S.W.3.

Telephone 01-352 1897

TRADE ENQUIRIES WELCOMED

SOLARTRON

Precision Laboratory Oscilloscope type CD 643. D.C.—15 MHz. 5" Flat face tube. £45 each Carr. £1.50

NEW WIDE RANGE WOBBLATOR

5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75p. P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each. P. & P. 25p (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each. P. & P. 5p. 12" Long Persistence CRT, full spec. Price £7.50 to include V.A.T. & carr. £1. WORTH OF "GIFTS". Six brand new capacitors all between 15V and 100V. Total capacitance not less than 7,000mF. P. & P. 45p.

Large quantity of good quality components — NO PASSING TRADE — so we offer 3lb of **ELECTRONIC GOODIES** for £1.50 post paid.

ROTARY SWITCH PACK. Six brand new switches (1 ceramic; 1 off, 4 pole, 2 way, etc.), 50p. P. & P. 20p.

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors ½ and ¼ watt, many high stabs, etc. Fine value at 50p. P. & P. 27p.

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College)

P.C.B. PACKS S & D. Quantity 2sqft

—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, 25p. P. & P. 15p.

SANGO 50 microamp meters. 2 1/2" diameter. Ex-new radiation equip. £1.25 each. P. & P. 17p.

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 20p.

POTS—10 different values. Brand new—50p. P. & P. 20p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

Replacement TUBES for Cossor 1035 Mk. 1, 2 and 2A and Cossor 1049 Mk. 1, 2 and 3. Used—guaranteed. £3 each. P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

PHOTOCCELL equ. OCP71, 13p each.

Mullard OCP70, 10p each.

CRYSTALS. Brand New. 4.43 MHz £1.25 each. P. & P. 10p.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. Two-tone green, £3.75 each. Black, £3.75 each. P. & P. 25p each.

IDEAL EXTENSION Telephones with standard GPO type dial, bell and lead coding. £1.75 each. P. & P. 25p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you, it could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | |
|---|---|--|
| <input type="checkbox"/> Practical Radio and Electronics (Technatron) | <input type="checkbox"/> Electronics. Mechanics | <input type="checkbox"/> C. & G. LI Installations and Wiring |
| <input type="checkbox"/> Electronic Engineering | <input type="checkbox"/> Radio Amateurs | <input type="checkbox"/> General Electrical |
| <input type="checkbox"/> Television Maintenance and Servicing | <input type="checkbox"/> Practical TV | <input type="checkbox"/> Engineering |
| <input type="checkbox"/> General Radio and TV Engineering | <input type="checkbox"/> Colour Television | <input type="checkbox"/> Society of Engineers (Electrical Engineering) |
| <input type="checkbox"/> Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> Computer Electronics | <input type="checkbox"/> Electrical Installations and Wiring |
| | <input type="checkbox"/> C. & G. LI Radio TV Servicing cert. | <input type="checkbox"/> C. & G. Electrical Technicians (Primary) |
| | <input type="checkbox"/> Post Master General 1st & 2nd class certs. | <input type="checkbox"/> C. & G. Telecom. munications |
| | <input type="checkbox"/> C. & G. Electrical Engineering Practise | |

To B.I.E.T. BPE95 Aldermaston Court, Reading RG7 4PF QK **BPE 95**

NAME (Block Capitals Please)

ADDRESS

Other subjects Accredited by C.A.C.C.


Age Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

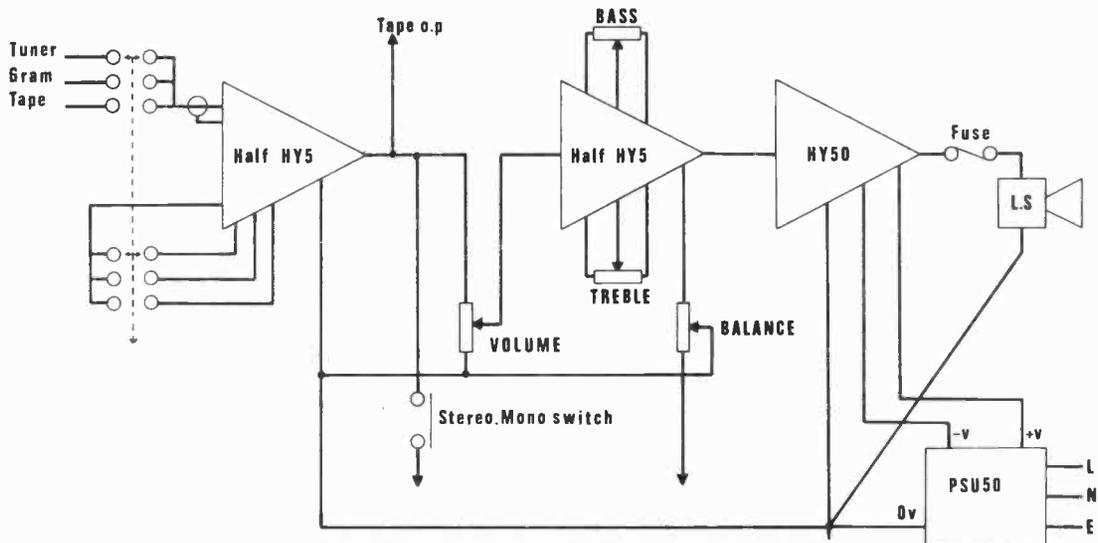

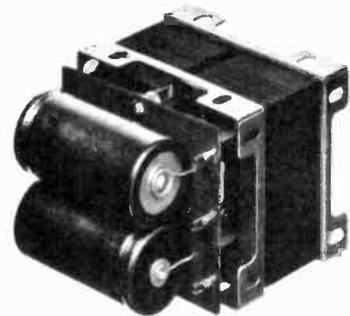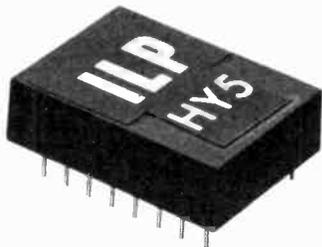MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier. Ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input impedance 47k Ω at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble \pm 12db at 10kHz; Bass \pm 12db at 100Hz. Distortion: 0.5% at 1kHz; Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: \pm 16-25V

PRICE £4.50

+45p VAT
P. & P. free

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8k Ω . Load Impedance: 4-16k Ω . Input Sensitivity 0db (0.775V RMS). Input Impedance: 47k Ω . Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz \pm 3db. Supply Voltage: \pm 25V. Size: 105 x 50 x 25mm.

PRICE £5.98

+59p VAT
P. & P. free

The PSU50 can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: 25V. Input voltage: 210-240V. Size: L 70, D 90, H 60mm.

PRICE £5


-50p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY (0227) 63218

PRINTED CIRCUIT BOARD TRANSFER SYSTEMS

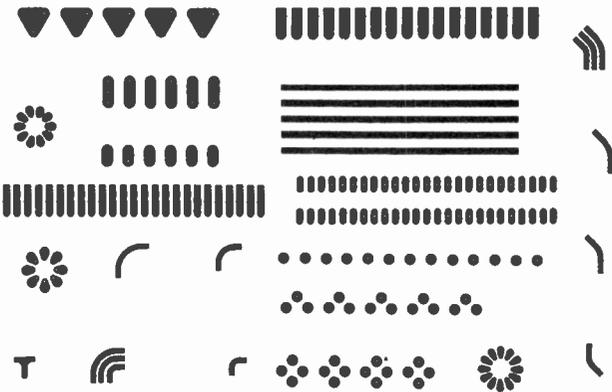

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes—i.e. edge connectors, lines, pads, dual in line I.C.'s, 8-10-12, T.O.5 Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry. A full money back guarantee is sent with each order, trade prices on application.

List of Prices

Complete system including post and VAT	£2.00
Individual sheets	22p
Sample sheet	22p
Copper laminate (boards) size 6" x 4 1/2" 6 sheets.....	50p
(with six months guarantee)	

Printed circuit board PCB transfer systems patent applied for.

E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE

TELEPHONE NUMBER : 061-480-2179

CHROMASONIC electronics

Dept 2
56, Fortis Green Road, London, N10 3HN
telephone: 01-883 3705

LINEAR I.C.'s				DIODES				TRANSISTORS															
709 (8 pin dip)	34p	MC1303L	£1.89	TAA300	£1.79	AA119	10p	82X70	27p	AC107	14p	AF239	41p	BC209	14p	BF179	33p	BSK21	22p	ZTX109	15p	2N43706	14p
709 (TO-99)	41p	MC1300P	£3.05	TAA310	£1.37	AA120	10p	Series		AC126	13p	ASV26	33p	BC212L	12p	BF180	33p	BSY95A	14p	ZTX300	12p	2N43707	12p
710 (14 pin dip)	35p	MC1310P	£5.05	TAA320	99p	AA129	10p	82Y98	11p	AC128	13p	BC108	11p	BC214L	13p	BF181	33p	BUI0502N1	92	ZTX301	13p	2N43708	10p
710 (8 pin dip)	35p	MC1312P (see below)		TAA350	81p	BA100	10p	Series		AC176	15p	BC109	12p	BC268	15p	BF185	28p	D40N3	61p	ZTX302	17p	2N43709	17p
710 (TO-99)	41p	MC1309P	88p	TAA370	£1.55	BA102	27p	0A47	11p	AC187	22p	BC117	22p	BC407	14p	BF174	15p	MA480	50p	ZTX304	21p	2N43711	11p
710 (14 pin dip)	39p	MC1339P	£1.55	TAD100	£1.55	BA110	45p	0A79	10p	AC187K	25p	BC147	15p	BCV70	17p	BF195	17p	MA481	£1.20	ZTX311	10p	2N43772	£2.75
711 (TO-99)	45p	MC1350	83p	TAD110	£1.85	BA115	17p	0A81	8p	AC188K	25p	BC148	10p	BCV71	22p	BF196	16p	MA490	£1.03	ZTX312	10p	2N43791	£3.20
711 (14 pin dip)	39p	MC1351	£1.10	TBA520	£2.71	BA144	20p	0A85	10p	AC188K	25p	BC149	10p	BCV72	17p	BF197	16p	MA491	£1.45	ZTX341	22p	2N43819	28p
722 (TO-99)	96p	MC1252	£1.10	TBA530	£1.96	BA145	22p	0A90	8p	AC197	39p	BC157	13p	BD115	74p	BF200	22p	MAJ90	£1.48	ZTX384	18p	2N43821	61p
722 (14 pin dip)	96p	MC1252	£1.10	TBA540	£2.00	BA148	22p	0A91	8p	AC199	25p	BC158	12p	BD123	91p	BF244B	27p	HJ1000	£1.24	ZTX500	12p	2N43823	99p
741 (8 pin dip)	42p	MC1358	£1.68	TBA560C	£2.98	BA154	20p	0A200	11p	ACY20	22p	BC159	14p	BD124	82p	BF262	25p	HJ2955	£1.82	ZTX531	13p	2N43903	163p
741 (TO-99)	45p	MC1375	£1.41	TBA625A	£1.04	BA155	15p	0A202	12p	AD180	40p	BC167	17p	BD131	55p	BF263	25p	HJ3055	£1.23	ZTX502	17p	2N43904	19p
741 (14 pin dip)	43p	MC1456CG	£1.75	TBA625B	£1.04	BA156	16p	Z5120	8p	AD189	49p	BC168B	11p	BD132	66p	BF272	£1.21	MA4000	£1.49	ZTX503	14p	2N43905	23p
747 (8 pin dip)	92p	MC1458CP1	£2.42	TBA625C	£1.04	BAK16	10p	Z5140	25p	AD161	36p	BC169	15p	BD133/29P	£1.19	BF507	25p	MA4010	£1.99	ZTX504	43p	2N43906	25p
748 (8 pin dip)	45p	MC1458G	£2.52	TBA651	£1.00	BB104	44p	Z5141	43p	AD162	39p	BC171	20p	BD135	42p	BF598	20p	MAJ340	50p	ZTX533	22p	2N46058	133p
748 (TO-99)	42p	MC1495	£5.65	TBA800	£1.59	BB105H	42p	Z5142	33p	AD162	39p	BC172	17p	BD136	44p	BFW10	66p	MAJ350	92p	ZTX550	17p	2N46059	19p
748 (14 pin dip)	43p	MC1495G	£1.49	TBA108B	£1.76	BY100	16p	Z5170	10p	AF114	17p	BC177	22p	BD201	£1.99	BFK29	42p	MAJ2955E1	82	ZTX607	16p	2N46062	16p
		MC1302	£1.33	TBA108AS	£1.44	BY103	22p	Z5270	11p	AF115	17p	BC178	22p	BD202	£1.49	BFK68	26p	MAJ3055	92	ZN706	16p	2N46269	19p
		MC3401	77p			BY105	16p	Z5271	10p	AF116	17p	BC179	24p	BF109	75p	BFY50	22p	MAJF102	27	ZN708	16p	2N46441	87p
AY-6-3510	£7.78	MC3302	77p	TCA940	£2.84	BY126	16p	Z5278	37p	AF117	17p	BC182L	11p	BF115	25p	BFY51	22p	MRF103	41p	ZN914	24p	2N46442	£1.06
BHA0002	£3.85	MFC4000B	49p	TDA1200	£2.15	BY127	16p	ZN914	8p	AF118	92p	BC183L	12p	BF160	25p	BFY90	£1.11	MRF104	45p	ZN920	22p	2N46443	£1.45
		MFC4002A	78p			BY133	23p	ZN916	10p	AF119	92p	BC184L	12p	BF167	24p	BFY100	22p	MRF105	45p	ZN930	20p	2N46444	£2.09
CA3046	95p	MFC6030A	83p	ULN2111A	£1.50	BY164	55p	IN4009	7p	AF120	33p	BC187	27p	BF173	24p	BFY139	44p	MRF106	49p	ZN933	24p	2N46871	60p
CA3065	£1.56	MFC6040	£1.10			BY176	£1.55	IN4148	53p	AF172	25p	BC204	14p	BF178	29p	BSX20	18p	MRF111	22p	ZN1304	24p	2N4901	£1.43
CA3075	£1.65					BY182	£1.65	IN4448	9p									MPSU56	54p	ZN1305	24p	2N5037	£1.09
CA3081	£1.64	MA5314	£7.92	ZN492E	£6.60	BY200	25p	IZS Series	18p									MPSU56	79p	ZN1306	24p	2N5129	11p
CA3082	£1.65	MA5316	£16.50	ZN414	£1.32													OC28	50p	ZN1307	27p	2N5172	16p
																		OC35	50p	ZN1308	35p	2N5191	75p
1005	£1.65	MVR5V	£1.65															OC36	50p	ZN1309	35p	2N5194	75p
1036	£1.65	MVR12V	£1.65															OC44	14p	ZN1711	26p	2N5295	53p
1037	£1.65	MVR15V	£1.65															OC45	14p	ZN1718	£4.45	2N5447	14p
1129	£1.65																	OC72	14p	ZN1899	52p	2N5449	14p
1130	£1.65																	OC73	14p	ZN2218	52p	2N5449	47p
1131	£1.65																	OC75	15p	ZN2219	59p	2N5458	44p
																		OC76	27p	ZN2646	59p	2N5459	44p
LM301 (TO-99)	60p	NE555	£0.59	NE540	£1.92	60p	MCR103	44p	106A	48p	2N4441	87p						OC81	14p	ZN2818	95p	2N5459	53p
LM301 (8 pin dip)	53p	NE568	£4.92	100p	MCR104	49p	106A	48p	106B	53p	2N4442	£1.06						OC83	25p	ZN2904	33p	2N5477	49p
LM307 (TO-99)	60p	NE568	£4.92	200p	MCR120	51p	106B	53p	2N4443	£1.06								OC87	14p	ZN2905	31p	2N46008	45p
LM307 (8 pin dip)	53p	NE568	£2.80	400p			106M	£1.50	2N4444	£2.09								OC89	17p	ZN2924	16p	2N4609	57p
LM308 (TO-99)	£1.29	NE566	£2.70															OC97	£1.57	ZN2925	18p	2N4670	59p
LM308 (8 pin dip)	99p	NE567	£2.85															ORP12	66p	ZN2926G	10p	2N4671	63p
LM309K	£2.41																	TI29	54p	ZN3053	19p	2N4673	66p
LM339	£3.76	SL414	£1.76															TI31	68p	ZN3054	51p	2N4675	£1.49
LM371	£2.08	SL415	£2.29															TI31A	66p	ZN3055	52p	2N4676	18p
LM372	£2.48	SL440	£2.89															TI32A	81p	ZN3375	£3.63	2N4611	55p
LM373	£2.10																	TI31A	81p	ZN3442	£1.21	2N4628	61p
LM377	£2.97	SN75491	£1.69															TI32A	99p	ZN3456	95p	2N4670	£1.01
LM380	£1.40	SN75492	£1.69															TI543	36p	ZN3538	20p	2N4141	89p
LM381	£2.31																	TI588A	37p	ZN3702	13p	2N4153	89p
LM382	£2.24																	TI591	33p	ZN3703	12p	40321	53p
LM900	77p	MC 1312 CBS SQ Decoder inc all parts & leaflet	£6.49															ZTX107	10p	ZN3704	12p	40321	53p
																		ZTX108	10p	ZN3705	12p	40673	55p

THYRISTORS SCR's

V	800mA	32p	4A	3p	8A
	30p	MCR102	106Y	106F	2N4441
	50p				
	60p	MCR103	44p		

MAPLIN ELECTRONIC SUPPLIES

ORGAN BUILDERS



Keyboards: High quality adjustable type. Slipping from 49-note C to C. £14.35.
Flat front 48-note F to E. £14.35.
Contact blocks GB-2 (2 make contacts). 16p.
Palladium earth bar per octave length. 20p.
Stop tabs rocker type not engraved (white, red, grey or black) with DPDT switch. 49p.

BASIC ORGAN CIRCUIT

Leaflet MES 51 shows a complete circuit for a basic fully polyphonic organ. Send only 15p for leaflet and start building now! REMEMBER—when you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details.

REVERBERATION UNIT

Enhances the sound of any electronic musical instrument. Ready built spring line driver module suitable for use with almost any spring line. £3.34

Two types of spring line available:
Short line. £3.05.
Long line. £7.59.
S.A.E. please for details. Leaflet MES 24.



MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE b.f. master oscillator.
★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3.7in. x 4.5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL for full technical and fully guaranteed. ★ S.a.e. please for details.
DMO2T (with tremulant) ONLY £14.25.
DMO2 (without tremulant) £12.25.

Trade enquiries welcome.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.43 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ SAME DAY SERVICE



P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We are stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Verobords.

Send S.A.E. now for our detailed price lists.

E.T.I. SYNTHESISER

We stock all the parts for the "Electronics Today International" synthesiser including all the P.C.B.'s required and all the metalwork including a drilled and printed front panel for a truly professional finish.

Some of the circuits in this brilliant design are entirely original. Independent authoritative opinions agree the E.T.I. International Synthesiser is technically superior to practically all synthesisers available today. S.A.E. please for our detailed price lists.


CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd	V	Price	Mfd	V	Price
1	63	6p	68	6.3	6p
1	83	6p	68	16	6p
2	23	6p	68	63	10p
3	33	6p	100	4	6p
4	73	6p	100	10	6p
6	8	40p	100	25	6p
6	8	40p	100	40	6p
10	25	6p	100	63	12p
10	63	6p	150	6.3	10p
15	6	6p	150	16	6p
15	40	6p	150	25	6p
15	63	6p	150	40	10p
22	10	6p	150	63	12p
22	25	6p	220	4	6p
22	63	6p	220	10	6p
33	6.3	6p	220	16	6p
33	16	6p	220	25	10p
33	16	6p	220	40	12p
33	40	6p	220	63	12p
47	4	6p	220	63	18p
47	10	6p	330	4	6p
47	25	6p	330	10	6p
47	40	6p	330	16	10p
47	63	6p	330	63	22p
			4700	4	22p



PLUGS AND SOCKETS

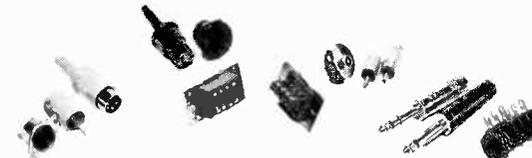

DIN PLUGS
2 pin (1 flat) 8p
3 pin 9p
4 pin, 5 pin A (180°) 5 pin B (240°) 6 pin 10p

DIN Sockets
2 pin 6p
3 pin, 4 pin, 5 pin A (180°) 5 pin B (240°) 7p, 6 pin 9p

MAINS
P360 3 pin 1.5A chassis plug with line socket. Per pair 28p
SA 2190 3 pin 5A SA 1862 Line socket for above 23p

McMURDO
RP8 8 way chassis plug 47p

RSR 8 way chassis socket 82p
PHONO
Plug plastic 5p
Plug screened 12p
Chassis socket 4p

JACK
Std. 1/4" mono plug Plastic 13p
Screened 21p

Std. 1/4" stereo plug Plastic 18p
Screened 30p
Open mono socket 1/4" 10p; Moulded mono socket 1/4" with 2 break contacts 14p; Moulded stereo socket 1/4" with 3 break contacts 18p; 3.5mm. plug plastic 9p; screened 15p; open socket 8p.

WE KNOW YOU NEED IT!



The MES 1974 CATALOGUE IS STACKED

with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue.

and leave the rest to us!

LINEARS

CA3046 Transistor array	69p
LM0042C. TO99 (TO5). FET 1/2 Op Amp	£4.25
LM301A. 8-pin DIL. Op Amp	39p
MC1303L. 14-pin. Stereo Pre-amplifier	£1.30
MC1310P. 14-pin DIL. FM Stereo Decoder (no coils needed)	£3.15
MFC4000B. 1W Audio Amp	36p
MFC6040 Electronic attenuator	86p
MFC8010. 8-pin case. 1W Audio Power Amp	£1.20
MFC9020. 10-lead case. 2W Audio Power Amp	£1.37
NE555V. 8-pin DIL. Precision Timer	69p
NE561B. 16-pin DIL. Phase Locked Loop	£4.40
SG1495D. 14-pin DIL. Four Quadrant Analogue Multiplier	£2.70
SG3402N Amplifier/Multiplier	£1.69
µA723C. TO99 (TO5). 2 to 37V Voltage Regulator	75p
µA723C. 14-pin DIL. 2 to 37V Voltage Regulator	75p
µA741C. 8-pin DIL. Op Amp	36p
µA741C. 14-pin DIL. Op Amp	45p
µA747C. 14-pin DIL. Dual Op Amp	69p
µA748C. 8-pin DIL. Op Amp	39p
ZN414. TO5. TRF Radio	£1.20

Full data, pin connexions, etc. on nearly all types above in our catalogue. Price 25p.

OMNIUM GATHERUM

PP3, 6, etc., battery clip dual min. 9p.
PP1, 9, etc., battery clip separate per pair 6p.
Pair crocodile clips. 1 red, 1 black insulated sleeve 10p.
Solder. Multicore 22 s.w.g. 10 metres 20p.
Silicone grease in special dispenser 20ml 43p.
Terminal Block 12-way 5A 14p.
Probe clips spring loaded per pair 30p.
Panel fuse holders 20mm 20p; 1 1/2in 35p.

Transformers
LT700 man output transformer Pri. 1-2kV Sec. 5Ω 200mW 50p.

Sub-main. Mains Transformer
6-6V 100mA 95p, 12-0-12V 50mA 95p.
Size: Both approx. 30 x 27 x 25mm.

Min. Mains Transformer
Size: 46 x 31 x 38mm.
0-12V 250mA, 0-12V 250mA £1.36.

Mains Transformer MT3AT
Pri. 200-220-240V. Sec. 12-15-20-24-30V 1A £3.31.

Mains Transformer MT206AT
Pri. 200-220-240V. Sec. 0-15-20V 1A. 0-15-20V 1A £3.80.

Hook-up wire, 7 strand 0.2mm. PVC covered tinned copper wire for light green connexions up to 1.4A. 11 colours: black, blue, brown, green, grey, orange, pink, red, violet, white, yellow. 10 metres of any one colour 20p. Pack of 11 (1 of each colour) 10m. coils £2.05.

Single core screened 8p per metre.
Twin individually screened 10p per metre.
High quality single screened 50Ω 100pF per metre. ideal for high grade audio connexions 15p per metre.

Mains 3-core sub-miniature 1A black PVC covered 19 strand 0.1mm per conductor. 71p per metre.

POTENTIOMETERS

Rotary miniature carbon track 1/4" spindle

Single gang Lin or Log
5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 14p



Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 44p

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 29p

PRESETS

Sub-miniature 0.1W Vert or Horiz
100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 200k, 500k, 1M 26p

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 32p.
Mains rotary DPST 250V 2A 20p.

Slide Sub-miniature DPDT 9p

Push to make non-locking 14p

Toggle 250V 1.5A with ON/OFF plate 25p.

High quality "sub-miniature" toggle switches.
SPDT 1.5A 240V a.c. 50p
DPDT 1.5A 240V a.c. 63p
DPDT 3A 240V a.c. 77p
Four Pole DT 3A 240V a.c. £1.37

VAT Please add 10% to the final total.

Post and Packing FREE in U.K. (15p handling charge on orders under £1.) First class post pre-paid envelope supplied free with every order.

Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea 0702 44101**

RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 11Ω to 910k E12 & E24 1p
Carbon Film 1W 5% 10Ω to 10M E12 34p
Metal Oxide 1/4W 2% 10Ω to 1M E12 & E24 4p
Wirewound 2 1/4W 10% 0.2Ωohms to 0.47ohms E12 12p
Wirewound 2 1/4W 5% 10hm to 270ohms E12 12p
E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 76, 91 and decades

TRANSISTORS

Popular types ex-stock. Special discounts for O.E.M., Trade and Educational Establishments

AC126	12p	BC109	10p	BF195	10p	2N1132	18p
AC127	12p	BC147	9p	BFY50	15p	2N2219	20p
AC128	12p	BC148	9p	BFY51	15p	2N2222	16p
AC176	14p	BC149	10p	BFY52	16p	2N2369	14p
AC187	14p	BC169	10p	MPF103	35p	2N2646	46p
AC188	14p	BC177	15p	MPF104	35p	2N2905	18p
AD149	40p	BC178	15p	MPF105	35p	2N2926	9p
AD161	33p	BC179	15p	MJE2955	98p	2N3053	18p
AD162	33p	BC182	11p	MJE3055	65p	2N3055	42p
AF114	14p	BC183	10p	OC26	35p	2N3702	12p
AF115	14p	BC184	12p	OC28	45p	2N3703	12p
AF116	14p	BC212	11p	OC35	46p	2N3704	12p
AF117	14p	BC213	11p	2N697	13p	2N3705	12p
AF139	30p	BC214	12p	2N698	15p	2N3706	13p
AF239	34p	BF184	20p	2N706	10p	2N3707	12p
BC107	9p	BF185	20p	2N930	18p	2N3709	8p
BC108	9p	BF194	10p	2N1131	18p	2N3819	27p

RECTIFIER DIODES	
BY100	13p
BY127	12p
1N4001	6p
1N4004	8p
1N4007	10p

SIGNAL DIODES	
OA47	7p
OA70	9p
OA81	8p
OA85	9p
OA90	7p
OA91	7p
1N914	5p
1N916	6p
1N4148	5p

ZENER DIODES	
3-3V to 33V	
E24 values	
400mW	10p
1-5W	25p

RECTIFIER BRIDGES

1 amp	25p	30p	1 amp	30p	45p
2 amp	35p	50p	3 amp	40p	65p
4 amp	55p	65p	7 amp	60p	85p
6 amp	65p	90p	16 amp	70p	£1-20

SCR

TRIACS	40430	6A	400 PIV		85p
--------	-------	----	---------	--	-----

AUDIO AMPLIFIER ICs

Features a wide range of supply voltages. High output current: 2-5A for TBA810, 1-5A for TBA800. Very low harmonic distortion; no crossover distortion.

	Power O/P	I/P Impedance	I/P Sens	
TBA820	2W	5 Mohms	16mV for 1-6W	90p
TBA800	5W	5 Mohms	80mV for 5W	110p
TBA810	7W	5 Mohms	80mV for 6W	160p

INTEGRATED CIRCUITS TTL74 Series

7400	18p	7472	28p	555 DIL	60p
7404	18p	7473	37p	709 DIL/TO99	33p
7408	22p	7475	55p	723 TO99	90p
7413	27p	7490	68p	741 8 pin DIL	38p
7430	18p	7493	65p	748 8 pin DIL	50p
7441	72p	74121	52p	TBA800 5W	£1-30
7447	£1-30	74141	£1-20	ZN414	£1-20

Linear

TGS SEMICONDUCTOR GAS SENSOR £1-50
(Data on request)

Minimum Order £3.
All prices exclusive of VAT.
Full catalogue to trade on request.
EXPORT inquiries welcome.
Despatch by return. No P. & P.

Technomatic Ltd

54 Sandhurst Road, London N.W.9
Tel. 01-204 4333



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME: _____

ADDRESS: _____ EB84

BLOCK CAPS please

TRAMPUS

MONEY BACK IF NOT SATISFIED
all brand new, full spec. Top grade.
Free fabulous NEW catalogue. Send SAE.

red+ data source **LEO's 17p!** **Til209** & clip 22p
BIG 1/4 panel clip & RED LED 28p. GREEN & clip 59p
INFRA RED LED £1. IC photo amp 44p. & amp/switch 85p

Digital Display LEO 1/3 0-9 D.P.DIL. £1-69
Minitron type 0-9 D.P.DIL £1-19. SOCKETS 13p.
IC DIGITAL CLOCK CHIPS.
Texas etc with 4 displays £12. 6 displays & chip £14. pcb £1-09
Mostek date & alarm chips with 6 displays £19.
hit: All parts & case. National chip. 4 digit £20. 6x £23.

with data **integrated circuits**
741: 8pin 29p, to99 & 14pin 27p 748 33p 709 21p
710 35p 723 59p. 555 timer 79p. ZN414 rx. £1-10
703 rf if 28p mc1310 & led £2-76 mc1339 £1-20 TAD100 & if £2

1AMP + REGULATOR 7805, 5 (& 7-20)V. also 12 & 15V £1-49
AUDIO AMPS: mfc40 0 0 50p; i & 2W £1-19; 3W £1-29; 6W...
gates 7400 etc 16p 7413 32p 7447 £1-25
7470/72 32p 7474/76 39p 7490 63p
7492 69p 74121 49p. & all others in cat. **low prices.**
NEW 16pin counter/driver 90/47 £2-25 DALO pcb. PEN 69p.
DIL SOCKETS: Professional/gold P.Pins hi or lo Prof file 8,14,16 Pin 13p

2N3055 33p. four £1. BC107, BC108, BC109 all 7p ea
IN914 3p ZENERS BZ88 8p. 1A RECTS 50v 3 1/2 400v 5p. BRIDGE 20p
FETS: 2N3819 19p 2N3823E 20p 4410E 25p BC182/3/4 10p
BC212/3/4 11p BCY70 13p BD131/2 35p ea. BFY52/3 15p TTIS4 25p
2N2926 0y 7p 2N3053 15p 2N3702/3/4/5/6/7/8/9/10/11 all 9v ea
2N3904/6 14p HEATSINKS 5t/TO5 18t/TO18 5p. TO3: 4YL 29p TV3 14p
CAPACITORS 25V10, 50, 100uf 5p. DISCS 4p. PRESETS 5p. CARBON -
POTS 11P. Switch 11P. Dual 5.5P. ULTRASONIC TRANSDUCERS £2 ea
FLUORESCENT LIGHTS 8W. 13 1/2V £2.59

Trampus electronics ADD 10% VAT TO PRICES. P.&P. 10P. CWO.
P.O. BOX 29, BRACKNELL, BERKS.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES
NORMAL HOUSEHOLD
TYPE

EX G.P.O. Only **£1-05p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.
Only **27 1/2p** POST & PACKING 16p

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long 1" dia. Highspeed P.O. type	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	55p
H66	4	40362. Type PNP Sil. transistors TO-5 can comp. to H65	55p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Transistors, manufacturers' rejects, AF, RF, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p
H67	10	3819N Channel FET's plastic case type.	55p

Make a rev counter for your car

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. **38 1/2p**

Cable can be sent by Parcel Post. Post and Packing per 50 yds.: 73p. Extension Telephones 71p each, p.p. 27p. £1-37 1/2 for 2, p.p. 55p. These phones are extensions and do not contain bells.

Electronic Transistor Ignition £6-60

Complete Kit incl. V.A.T. P. & P. 11p. Ready built and tested unit £9-90 incl. V.A.T. Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof-lock-up and automatic alarm, negative and positive compatibility.

New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available.

Essential for alignment of colour guns on all colour TV receivers. Featuring plug-in ICs and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—and only measures 3in x 5 1/2in x 3in. We have already received a large order from a major TV Rental company.

Ready built unit only **£10-92** Complete Kit **£8-72** (includes V.A.T. & P. & P. but no batteries)

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR £1-10p P. & P. 27 1/2p.

High Speed Magnetic Counter

4 digit (non-reset) 24V or 48V 4x1x1 in. 33p, p.p. 5p.



Plastic Power Transistors NOW IN TWO RANGES



These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	15	HFE Min.	15
		1-12		13-25
40 watt	22p			26-50
90 watt	26 1/2p			18p
				22p
Range 2	VCE Min.	40	HFE Min.	40
		1-12		13-25
40 watt	33p			26-50
90 watt	38 1/2p			29p
				33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 AUDIO I.C. as featured in Practical Wireless December issue. Complete with application data, £1-10.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16p each } Now new low
16 pin type at 18p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P. & P. on this Pak.
Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....
ADDRESS.....

ALL PRICES INCLUDE 10% V.A.T.
MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD.

Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344.

© Reg. No 820919

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £4.45

35W RMS 25-50V
7 transistors, 7 diodes

SA50 £5.65

50W RMS 25-65V
7 transistors, 6 diodes

SA100 £10.90

100W RMS 45-70V
11 transistors, 6 diodes

120 watt module complete with built-in supply—extra heavy duty £19.75 Carr. 60p

- Carriage free
- ★ 25Hz-25kHz
 - ★ 0.2% distortion
 - ★ Noise—80dB
 - ★ 500mV into 20K
 - ★ 4-16 ohms
 - ★ Simple wiring
 - ★ Short and open circuit proof
 - ★ Continuously rated
 - ★ Top-grade components



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED

PU45

Suits 2 SA35 or 1 SA50

£4.90

Carriage 30p

PU70

Suits 2 SA50 or 2 SA100

£7.75

Carriage 40p

STABILISED

PS45

Suits 2 SA35 or 2 SA50

£3.50

Carriage free

MT45

Transformer for above

£3.50

Carriage 30p

PS70

Suits 2 SA100

£4.90

Carriage free

MT70

Transformer for above

£4.90

Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £19.75

Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



DISCO MODULE £8.00

Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50

Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.50

Carr. free

Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add VAT 10% to all orders

MULTI-PURPOSE MIXERS

M4HL

£18.50

Carr. 50p

M6HL

£27.50


Carr. 50p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.50

Carr. free

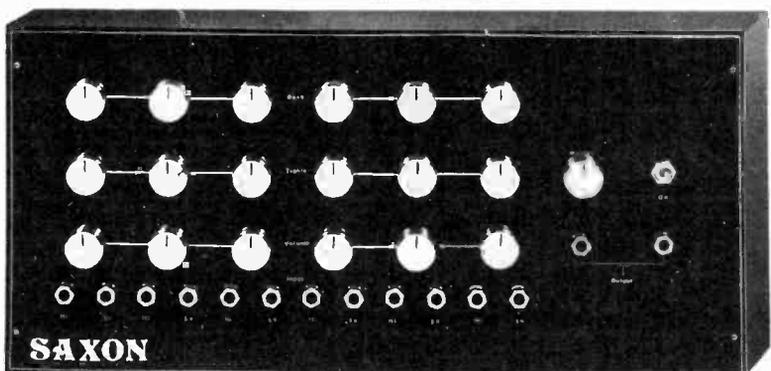This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)




SAXON CSE 100

COMPLETE AMPLIFIER

£34.90

Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.

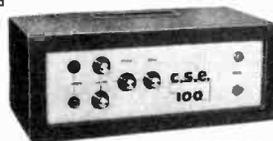

CSE 50

£29.50 Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker

SAXON 100 COMPLETE AMPLIFIER

£53.00

Carr. free

SAXON 50

£37.50

Carr. free

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. 5 p.m. — LUNCH 12.30 1.30 p.m. MAIL ORDER DESK: 10 a.m. 3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385

SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products. TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge. Please include S.A.E. with all enquiries. VAT at 10% must be added to all orders including postage and carriage charges.

C. T. ELECTRONICS

NOW AT 267 & 270 ACTON LANE, LONDON W4 5DG

New open—our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you speedier service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 a.m. through 6.0 p.m. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.

SEMICONDUCTORS

AC107	35p	BCY30	40p	MJ340	55p	OC36	65p	TIP41C	85p	2N2846	£1.50
AC125	50p	BCY31	55p	MJ423	65p	OC43	40p	TIP42C	£1.10	2N2904	25p
AC128	50p	BCY32	55p	MJ201	£1.25	OC44	20p	T1550	40p	2N2905	25p
AC127	27p	BCY33	45p	MJ201	£2.20	OC45	20p	T1550	15p	2N2906	25p
AC128	20p	BCY34	40p	MJ340	50p	OC70	15p	ZTX300	15p	2N2907	25p
AC178	27p	BCY38	85p	MJ370	75p	OC71	17p	ZTX500	15p	2N2926	25p
ACY17	25p	BCY39	£1.80	MJ371	75p	OC72	20p	ZTX501	20p	2N3053	25p
ACY18	30p	BCY55	£1.80	MJ520	85p	OC75	25p	ZTX504	30p	2N3055	25p
ACY19	30p	BCY70	22p	MJE2955	£1.95	OC78	25p	ZTX531	30p	2N3055	25p
ACY20	25p	BCY71	22p	MJE3055	85p	OC77	40p	ZTX550	25p	2N3232	75p
ACY38	55p	BD122	75p	MM1813	43p	OC81	25p	IN859	15p	2N3525	95p
ACY21	30p	BD121	75p	MM1712	80p	OC83	25p	IN914	15p	2N3525	95p
AD140	40p	BD123	75p	MPF102	45p	OC84	25p	IN918	15p	2N3703	12p
AD149	65p	BD124	90p	MPF103	45p	OC139	30p	IN4001	8p	2N3704	12p
AD161	40p	BD131	75p	MPF104	35p	OC140	30p	IN4002	8p	2N3705	12p
AD162	40p	BD132	75p	MPF105	35p	OC170	30p	IN4003	8p	2N3706	12p
AD211	£1.80	BD153	75p	(2N5458)	25p	OC171	30p	IN4004	10p	2N3707	12p
AF114	25p	BD156	75p	MPF105	35p	OC200	50p	IN4005	12p	2N3708	12p
AF115	25p	BDY11	£1.40	(2N5459)	40p	OC201	60p	IN4006	15p	2N3709	12p
AF116	25p	BDY17	£1.80	MPSA06	35p	OC202	75p	IN4007	15p	2N3771	£2.70
AF117	25p	BDY19	£1.85	MPSA16	30p	TIP29A	40p	IN4148	7p	2N3772	£2.75
AF118	60p	BF152	20p	MPSA56	35p	DIP30A	55p	MPS96	25p	2N3773	£2.95
AF172	30p	BF194	14p	MPSU06	75p	TIP31A	82p	2N697	20p	2N3819	35p
AF528	30p	BF195	30p	MPSU07	75p	TIP32A	74p	2N698	20p	2N3820	35p
AS221	60p	BFX29	30p	NKT135	25p	TIP33A	£1.05	2N706	12p	2N3864	55p
BA102	33p	BFX84	30p	NKT222	25p	TIP34A	£1.55	2N708A	15p	2N3904	25p
BA112	50p	BFX85	30p	NKT401	95p	TIP35A	£1.35	2N708	15p	2N3905	25p
BA156	15p	BFY51	25p	NKT404	95p	TIP36A	£1.95	2N930	20p	2N4058	12p
BC107	12p	BFY10	35p	NKT773	30p	TIP37A	75p	2N1132	25p	2N4059	12p
BC108	12p	BFY44	50p	OA5	20p	TIP29B	55p	2N1302	16p	2N4060	12p
BC109	12p	BFY50	25p	OA10	20p	TIP30B	60p	2N1304	25p	2N4126	17p
BC147	12p	BFY51	25p	OA10	20p	TIP31B	70p	2N1305	25p	2N4286	15p
BC148	12p	BFY52	25p	OA70	12p	TIP32B	82p	2N1306	25p	2N4287	15p
BC149	12p	BFY53	25p	OA79	12p	TIP33B	£1.12	2N1307	25p	2N4288	15p
BC153	13p	BFY90	85p	OA81	10p	TIP34B	£1.88	2N1308	25p	2N4289	15p
BC157	14p	BSW63	90p	OA90	10p	TIP35B	£2.81	2N1309	25p	2N4290	15p
BC158	13p	BSW68	90p	OA91	10p	TIP36A	£3.04	2N1613	25p	2N4444	£1.95
BC159	13p	BSY95A	12p	OA200	10p	TIP41B	83p	2N1711	25p	2N4871	35p
BC189C	14p	CS11	50p	OA202	10p	TIP42B	80p	2N2147	70p	2N4920	60p
BC182	14p	CA26	40p	OA10	10p	TIP20C	75p	2N2150	85p	2N5191	90p
BC183	14p	CA26	40p	OA211	30p	TIP30C	85p	2N217	75p	2N5194	90p
BC184	14p	BY126	20p	OC16	90p	TIP31C	85p	2N2218	25p	40390	50p
BC212	14p	BY127	20p	OC19	85p	TIP32C	£1.05	2N2219	25p	40361	50p
BC213	14p	BY184	85p	OC22	55p	TIP33C	£1.30	2N2220	25p	40382	55p
BC214	14p	IS100	15p	OC25	55p	TIP34C	£1.80	2N222A	25p		
BC238	12p	IS103	20p	OC28	65p	TIP35C	£2.20	2N2368	70p		
BC239	12p			OC30	90p	TIP36C	£4.10	2N2646	70p		

S.C.R.s

CRS1/05	40p	CRS1/10	50p	CRS1/20	60p	CRS1/40	80p	CRS1/60	90p	CRS1/100	1.00	CRS1/200	1.80	CRS16/100	85p	CRS16/200	90p	CRS16/800	£1.80
C106S	45p	C106D	70p	40669	90p	TIC44	35p	2N4444	£1.90	BT10/5004	90p								

TRIACS

TXL226B 8A 400V	95p	SC40D	£1.40	SC40E	£1.85	SC45D	£1.70	SC45E	£2.10	SC50D	£2.42	SC50E	£2.70	DIAC	25p
-----------------	-----	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	------	-----

★ SPECIAL OFFERS ★

MINIATURE MAINS TRANSFORMER
Pri. 240V. Sec. 12V. 100mA. Manuf. Hinchley. Size: 36 x 45 x 40mm. F.C. 53mm. Price £1.45. 100-80p. ea. 1000-50p. ea. 10,000-40p. ea.

3 CORE PVC INSULATED MAINS CABLE GREY ML6650. 3 x 7/0.2mm. Price 100m-£4.50. 1000m-£35. 10,000m-£330.

0.47µfd. 50V. MYLAR FILM CAPACITOR. Size: 1 x 0.35 x 0.85in P.C. Mount. Price 100-6.8p. ea. 1000-5p. ea. 10,000-4.3p. ea.

240V. A.C. SOLENOID. Reversible operation. Twin coil. Size approx. 2½ x 1½ x 1in. 80p. ea.

30 unmarked OC71 transistors. £1.25

25 Unmarked 250mW Zener diode. 4.7V. 5.1V. 6.2V. 7.5V. 9.1V. 10V. Measured and tested. £1. Please state voltages required.

50 GE Diode OA47 equivalent. £1.

Inc. Filter £1.80
CA3018 £1.55
CA3018 £1.80
CA3026 £1.20
CA3036 £1.00
CA3048 £2.35
CA3075 £1.60
CA3090Q £4.85
MC1303L £2.20
SN76023 6W Audio I.C. with circuit £1.75

BRIDGE RECTIFIERS

W02 1A 200V 38p	BY164 1-4A 200V 57p	MDA952/2	6A 100V 80p
-----------------	---------------------	----------	-------------

ZENER DIODES

BZ78 Series 400mW	3-3V-33V 5% 100p	1-5W range 25p	10W range 45p
-------------------	------------------	----------------	---------------

V41 VU METER

The V41 is calibrated -20 to +3 and 0-100%, making it suitable for use as a recording level meter or as a power output indicator.
Sensitivity: 130µA. Internal resistance: 600 ohms.
Dimensions: 40 x 40 x 29mm.

ALSO STOCKED

Electrolytic capacitors: Mullard, Sprague, Lorlin, etc.
Polyester, polystyrene, silver mica capacitors, etc.
Resistors: W-10W.
Potentiometers, carbon, wirewound, preset, rectangular multitrn.
Antex soldering irons.
Switches: rotary, slide, toggle, etc.
Cable, veroboard.

ALUMINIUM BOXES

AB7	2½ x 5½ x 1½in	50p	AB4	7 x 5 x 2½in	84p
AB8	4 x 4 x 1½in	50p	AB15	8 x 6 x 3in	£1.08
AB9	4 x 2½ x 1½in	50p	AB16	10 x 7 x 3in	£1.22
AB10	4 x 5½ x 1½in	50p	AB17	10 x 4½ x 3in	£1.08
AB11	4 x 2½ x 2in	80p	AB18	12 x 5 x 3in	£1.20
AB12	3 x 2 x 1in	44p	AB19	17 x 8 x 3in	£1.60

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 10% to all orders. Carriage: orders under £5 - 20p. Over £5 post free.

TRANSFORMER

Pri. 0, 115, 160, 205, 225, 245.
Sec. 35-0-35. 1-2A
£4.50 + 50p P & P

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)

Type 092 0.8-2.2pF. 801 0.8-2.2pF. 991 0.5-1.3pF. Price 10p ea.
Quantity discounts please telephone.

1000pF Feed through capacitor, 5p ea.

MINIATURE TUBULAR P.C. TRIMMERS

3.5-13pF. 6-30pF. 10p ea.
4pc/c VARLEY 7060 RELAY 50P ea.

DIGITAL INTEGRAL CIRCUITS

SN7400	20p	SN7428	50p	SN7473	40p	SN74107	50p	SN74186	£4.80
SN7401	20p	SN7430	20p	SN7474	40p	SN74110	80p	SN74187	£3.25
SN7402	20p	SN7432	40p	SN7475	50p	SN74118	£1.00	SN74170	£4.10
SN7403	20p	SN7433	85p	SN7476	85p	SN74119	£1.80	SN74174	£2.00
SN7404	20p	SN7437	85p	SN7477	85p	SN74121	£1.50	SN74175	£1.35
SN7405	20p	SN7438	85p	SN7478	85p	SN74122	£1.35	SN74176	£1.60
SN7406	30p	SN7440	20p	SN7481	£1.25	SN74123	£2.70	SN74177	£1.60
SN7407	30p	SN7441A	75p	SN7482	77p	SN74124	£1.80	SN74180	£1.55
SN7408	20p	SN7442	75p	SN7483	£1.80	SN74125	£1.80	SN74181	£7.00
SN7409	45p	SN7443	£1.80	SN7484	90p	SN74126	£1.80	SN74182	£2.00
SN7410	20p	SN7445	£2.00	SN7485	45p	SN74127	£1.80	SN74184	£2.45
SN7411	20p	SN7446	£2.00	SN7486	45p	SN74133	£1.35	SN74185A	£2.40
SN7412	42p	SN7447	£1.75	SN7487	75p	SN74134	£2.00	SN74186	£1.85
SN7413	30p	SN7448	£1.75	SN7488	75p	SN74135	£1.50	SN74191	£1.85
SN7416	30p	SN7450	20p	SN7489	80p	SN74136	£1.50	SN74192	£2.00
SN7417	30p	SN7451	20p	SN7490	80p	SN74137	£1.50	SN74193	£2.00
SN7420	20p	SN7453	20p	SN7491	80p	SN74138	£1.50	SN74194	£2.50
SN7422	48p	SN7454	20p	SN7492	80p	SN74139	£1.50	SN74195	£1.85
SN7423	48p	SN7460	20p	SN7493	80p	SN74140	£2.50	SN74196	£1.50
SN7425	48p	SN7470	20p	SN7494	80p	SN74141	£2.50	SN74197	£1.50
SN7427	42p	SN7472	20p	SN7495	80p	SN74142	£2.50	SN74198	£4.80
				SN7496	£1.00	SN74143	£2.50	SN74199	£4.80
				SN7497	£8.25	SN74144	£2.50		
				SN7498	£2.50	SN74145	£2.50		
				SN7499	£1.45	SN74146	£2.50		
				SN7500	£1.45	SN74147	£2.50		

QUANTITY DISCOUNTS—12+ 10%, 25+ 15%, 100+ 20%.

AUDIO ACCESSORY SHOP

17 Turnham Green Terrace, Chiswick W4

VALVE AMPLIFIERS

5 Watt	£12.50	50 Watt	£36.25
15 Watt	£24.50	150 Watt	£75.80
30 Watt	£28.50	500 Watt	£124.50

(Prices include VAT)

TRANSISTOR AMPLIFIERS

FAL Phase 50W	£39.93	FAL Phase 100W	£89.95
---------------	--------	----------------	--------

(Prices include VAT)

DISCO CONSOLES

FAL Disco Mk 2	£82.99	FAL Power Disco	£123.75
----------------	--------	-----------------	---------

(with 70W RMS Amp)
(Prices include VAT)

TEAK VENEERED SPEAKER CABINETS

For 8 x 5in Speaker	Size 7½ x 11½ x 5½	£3.50
8in + Tweeter	9½ x 13½ x 5½	£5.00
13 x 8in	10½ x 17 x 6	£5.75
13 x 8in + Tweeter	12 x 18½ x 8½	£7.50

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed Pak No.	EQVT
T1 8 203718	OC71
T2 8 D1374	OC75
T3 8 D1216	OC81D
T4 8 20381T	OC81
T5 8 20382T	OC82
T6 8 20344B	OC44
T7 8 20345B	OC45
T8 8 20378	OC78
T9 8 20399A	2N1302
T10 8 20417	AF117

All 55p each pak

ND120 NIXIE DRIVER TRANSISTOR

Suitable replacement for BX21. C407, 2N1893 120vcb.

1	25	100+
0-19	0-17	0-16

Sil. trans. suitable for P.E. Organ, Metal To-18

Eqvt. ZTX300 \$p each. Any Quantity.

GP100 T08 METAL CASE GERMANIUM

Vebo=80V. Vceo=50V. I.C.=10 amps. Ptot=30W. hfe=30-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-48	0-44	0-40

GP300 T03 METAL CASE SILICON

Vebo=100V. Vceo=60V. I.C.=15 amps. Ptot=115W. hfe=20-100IT=1MHz. Suitable replacement for 2N3055, BDY11 or BDY20.

1	25	100+
0-85	0-83	0-81

NEW 8th EDITION TRANSISTOR EQUIVALENTS BOOK

250 pages. Complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK, \$1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

U746 UNIJUNCTION TRANSISTORS

Direct replacement for T18 43rand BEN 3000 also electrically equivalent to 2N2840.

1	25	100+
0-30	0-28	0-22

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, DCY70. When ordering please state preference NPN or PNP.

20	For	0-55
50	For	1-10
100	For	1-92
500	For	8-25
1000	For	14-30

SIL. G.P. DIODES Ep

300mW	30	0-65
40PIV(Min.)	100	1-65
Sub-Min.	500	5-50
Full Tested	1,000	9-90

Ideal for Organ Builders.

RE400 T03 PNP SILICON HIGH VOLTAGE

Vebo=250V. Vceo=100V. I.C.=6 amps. Ptot=30W. hfe=typ. 20 IT=5MHz.

1	25	100+
0-85	0-80	0-44

ADI61/162

PNP M/P COMP. GERM. TRANS. OUR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

SILICON PHOTO TRANSISTOR TO-18 Lens end

NPN Sim. to BPX25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty.	1-24	25-99	100up
Price each	45p	40p	35p

INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
UIC00=12x 7400	0-55	
UIC01=12x 7401	0-55	
UIC02=12x 7402	0-55	
UIC03=12x 7403	0-55	
UIC04=12x 7404	0-55	
UIC05=12x 7405	0-55	
UIC06=8x 7406	0-55	
UIC07=8x 7407	0-55	
UIC10=12x 7410	0-55	
UIC20=12x 7420	0-55	
UIC30=12x 7430	0-55	
UIC40=12x 7440	0-55	
UIC41=5x 7441	0-55	
UIC42=5x 7442	0-55	
UIC43=5x 7443	0-55	
UIC44=5x 7444	0-55	
UIC45=5x 7445	0-55	
UIC46=5x 7446	0-55	
UIC48=5x 7448	0-55	
UIC50=12x 7450	0-55	
UIC51=12x 7451	0-55	
UIC53=12x 7453	0-55	
UIC54=12x 7454	0-55	
UIC60=12x 7460	0-55	
UIC70=8x 7470	0-55	
UIC72=8x 7472	0-55	
UIC73=8x 7473	0-55	
UIC74=8x 7474	0-55	
UIC76=8x 7476	0-55	
UIC80=5x 7480	0-55	
UIC81=5x 7481	0-55	
UIC82=5x 7482	0-55	
UIC83=5x 7483	0-55	
UIC85=5x 7485	0-55	

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q 1	20 Red spot transistors pnp	0-55
Q 2	10 White spot R.F. transistors pnp	0-55
Q 3	4 OC77 type transistors	0-55
Q 4	6 Matched transistors OC44/45/81/81D	0-55
Q 5	4 OC75 transistors	0-55
Q 6	5 OC72 transistors	0-55
Q 7	4 AC128 transistors pnp high gain	0-55
Q 8	4 AC126 transistors pnp	0-55
Q 9	7 OC81 type transistors	0-55
Q 10	OC71 type transistors	0-55
Q 11	2 AC127/128 Complementary pairs pnp/npn	0-55
Q 12	3 AF116 type transistors	0-55
Q 13	3 AF117 type transistors	0-55
Q 14	3 OC171 H.F. type transistors	0-55
Q 15	7 2N2929 Sil. Epoxy transistors mixed colours	0-55
Q 16	2 GET800 low noise Germanium transistors	0-55
Q 17	5 npn 2 x ST.141 & 3 x ST.140	0-55
Q 18	4 MADD'S 2 x MAT 100 & 2 x MAT 120	0-55
Q 19	3 MADD'S 2 x MAT 101 & 1 x MAT 121	0-55
Q 20	4 OC44 Germanium transistors A.F.	0-55
Q 21	4 AC127 npn Germanium transistors	0-55
Q 22	20 NKT transistors A.F. R.F. coded	0-55
Q 23	10 OA292 Silicon diodes sub-min.	0-55
Q 24	8 OA81 diodes	0-55
Q 25	15 IN914 Silicon diodes 75PIV 75mA	0-55
Q 26	8 OA35 Germanium diodes sub-min IN69	0-55
Q 27	2 10A 600 PIV Silicon rectifiers IS425R	0-55
Q 28	2 Silicon power rectifiers BYZ13	0-55
Q 29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-55
Q 30	7 Silicon switch transistors 2N706 npn	0-55
Q 31	6 Silicon switch transistors 2N708 npn	0-55
Q 32	3 pnp Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q 33	3 Silicon npn transistors 2N1711	0-55
Q 34	7 Silicon npn transistors 2N3369, 500MHz (code P397)	0-55
Q 35	3 Silicon pnp TO-5, 2 x 2N2904 & 1 x 2N2905	0-55
Q 36	7 2N3646 TO-18 plastic 300MHz npn	0-55
Q 37	3 2N3055 npn Silicon transistors	0-55
Q 38	7 pnp transistors 4 x 2N3703, 3 x 2N3702	0-55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales—Conversion of Frequency and Wavelength, Calculation of L, C and fo of Tuned Circuits, Reactance and Self Inductance, Area of Circles, Volume of Cylinders, Resistance of Conductors, Weight of Conductors, Decibel Calculations, Angle Functions, Natural Logs and "e" Functions, Multiplication and Division, Squaring, Cubing and Square Roots, Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22cm x 4cm. Complete with case and instructions. Price each: £3-69

NEW LOW PRICED TESTED S.C.R.'S

PIV	50	100	200	400	600	800
1A TO5	0-22	0-27	0-27	0-32	0-42	0-63
3A TO66	0-27	0-27	0-32	0-42	0-52	0-70
5A TO66	0-39	0-52	0-64	0-59	0-75	0-88
7A TO64	0-39	0-52	0-64	0-82	0-75	0-88
7A TO48	0-52	0-55	0-62	0-67	0-84	0-99
10A TO48	0-55	0-63	0-67	0-88	1-07	1-32
15A TO48	0-58	0-62	0-67	0-77	0-97	1-60
30A TO48	1-27	1-54	1-76	1-93	—	4-40

SIL. RECTS. TESTED

PIV	300mA 750mA IA	1-5A	3A	10A	30A
DO7	8016	8016	8016	8010	8010
50	0-05	0-06	0-05	0-08	0-15
100	0-05	0-07	0-06	0-10	0-17
200	0-06	0-10	0-07	0-12	0-25
400	0-08	0-15	0-08	0-16	0-30
600	0-08	0-17	0-10	0-18	0-38
800	0-12	0-19	0-11	0-20	0-38
1000	0-14	0-20	0-12	0-25	0-48
1200	—	0-35	—	0-30	0-58

POST OFFICE TELEPHONE DIALS

2N3819	31p
2N3820	55p
2N3821	30p
8N3823	31p

F.E.T.'S

2N5458	85p
2N5459	44p
BFW10	85p
MPF105	41p

CADMIUM CELLS

ORP12 48p

FREE

One 55p Pak of your own choice free with orders valued \$4 or over

2N3055

115 WATT SIL POWER NPN 55p EACH

DIACS

FOR USE WITH BR100 (D32) 41p each

TRIACS

VBOM 2A 6A 10A TO-9 TO-66 TO-48

10 amp POTTED BRIDGE RECTIFIER

on heat sink. 100PIV. 99p each

100V	33	55	88
200V	55	66	99
400V	77	88	1-21


All prices include V.A.T. Giro No. 388-7006 Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

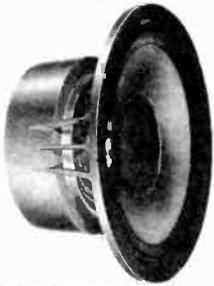

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3 8 or 15 ohm	£7-75
Baker Group 35 3 8 or 15 ohm	£8-50
Baker Group 50/12 8 or 15 ohm	£12-50
Baker Deluxe 12in d/cone	£10-75
Baker Major 12in d/cone	£8-50
Baker Regent	£7-75
Baker Superb	£14-50
Baker Auditorium 12	£12-50
Celestion MH1000, 8 or 15 ohm	£10-95
Celestion PST8 for Unilux	£2-55
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
Coral 6 1/2in d/cone roll surr. 8 ohm	£2-42
Coral 8in d/cone roll surr. 8 ohm	£2-11
EMI 13in x 8in 3 8 or 15 ohm	£2-15
EMI 13in x 8in 150 d/c 3 8 or 15 ohm	£2-35
EMI 13in x 8in 450 t/w. 3 8 or 15 ohm	£3-60
EMI 13in x 8in type 350 8 or 15 ohm	£8-25
EMI 13in x 8in 20W bass	£8-60
EMI 6 1/2in 93650 4 or 8 ohm	£2-11
EMI 5in 98132CP 8 ohm	£2-50
EMI 8 x 5 d/cone roll surr. 10W	£2-50
EMI 2 1/2in tweeter 97492AT	£0-85
Eagle DT33 30W tweeter	£5-45
Eagle HT15 horn tweeter	£3-80
Eagle CT5 cone tweeter	£1-50
Eagle CT10 tweeter 3 or 16 ohm	£2-54
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-20
Eagle FR4	£5-30
Eagle FR65	£7-15
Eagle FR8	£9-50
Elaic 9 x 5 59RM109 15 ohm, 59RM114 8 ohm	£3-00
Elaic 6 1/2in 6RM171 d/c roll surr.	£3-50
Elaic 6 1/2in 6RM220 d/cone	£2-85
Elaic 4in tweeter TW4	£1-21
Elaic 10in d/cone 10RM239 8 ohm	£2-85
Elaic 8in 8CS175 3 ohm	£2-50
Fane Pop 15W 12in	£4-85
Fane Pop 25/2 25W 12in	£8-85
Fane Pop 40W 10in	£8-50
Fane Pop 50W 12in	£11-00
Fane Pop 55 60W 12in	£12-50
Fane Pop 60W 15in	£22-50
Fane Pop 100W 18in	£29-00
Fane Crescendo 12A 100W 12in	£36-00
Fane Crescendo 12B bass	£48-95
Fane Crescendo 15in 100W	£7-00
Fane Crescendo 18in 150W	£3-85
Fane 80T1 8in d/c roll surr.	£2-75
Fane 80T2 8in d/c	£23-00
Fane 701 twin ribbon horn	£10-75
Fane 310 horn	£38-50
Fane 520 horn	£4-85
Goodmans 8P 8 or 15 ohm	

Goodmans 10P 8 or 15 ohm	£4-95
Goodmans 12P 8 or 15 ohm	£11-95
Goodmans 12P-D 8 or 15 ohm	£15-25
Goodmans 12P-G 8 or 15 ohm	£14-50
Goodmans Audiomax 12AX 100W	£39-65
Goodmans Audiomax 15AX	£42-00
Goodmans 15P 8 or 15 ohm	£19-50
Goodmans 18P 8 or 15 ohm	£33-00
Goodmans Midax 750	£15-00
Goodmans Axent 100 tweeter	£6-60
Goodmans Audiom 100 12in	£11-50
Goodmans Axiom 401 12in	£15-95
Goodmans Twinaxiom 8	£7-50
Goodmans Twinaxiom 10	£8-25
Kef T27	£4-75
Kef T15	£5-75
Kef B110	£6-75
Kef B200	£7-50
Kef B139	£11-75
Kef DNR	£1-92
Kef DN12	£4-12
Kef DN13	£2-75
STC4001G super tweeter	£6-19
Richard Allan CG8T 8in d/c roll surr.	£6-35
Wharfedale Super 10RS/DD	£9-80
2 1/2in 54 ohm, 70mm 80 ohm, 70mm 8 ohm	£0-65
2 1/2in 75 ohm	£0-50
7in x 4in 3 or 8 ohm	£1-38
8in x 5in 3 or 8 ohm	£1-38
10in x 6in 3 8 or 15 ohm	£1-92

SPEAKER KITS

Baker Major Module	each £10-75
Fane Mode One	each £9-90
Goodmans DIN 20	each £8-75
Helme XLK25	pair £18-17
Helme XLK30	pair £14-95
Helme XLK50	pair £37-18
Kerkit 2	each £23-50
Kerkit 3	each £34-00
Richard Allan Twinkit	each £3-25
Richard Allan Triple 8	each £12-50
Richard Allan Triple	each £18-50
Richard Allan Super Triple	each £21-50
Wharfedale Linton 2 kit	pair £19-25
Wharfedale Glendale 3 kit	pair £34-50
Wharfedale Doveclade 3 kit	pair £52-50

PA/DISCO AMPLIFIERS

Baker Major 100 watt	£48-75
Linear 30/40	£30-00
Linear 40/80	£35-00
Linear 80/100	£50-75
Linear 100 watt slave	£44-00

(carr. and ins. £1)

Eagle PA range in stock—ask for catalogue.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book.
All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 3p each, speaker kits 75p each (£1-50 pair), tweeters and crossovers 2p.
Send stamp for free booklet: "Choosing a Speaker".
ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.



Agfa Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!	C80	1	5	10
	C90	37p	£1-80	£3-96
	C120	83p	£3-10	£8-20
AGFA HIGH DYNAMIC SUPER	C80 - 8	50p	£2-40	£4-70
	C90 - 8	66p	£3-35	£8-60
	C120	99p	£4-90	£9-00
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C80	85p	£4-20	£8-30
	C90	£1-08	£5-35	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PE)
10 SWAN STREET, WILMSLOW,
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

PARTRIDGE MAINS ISOLATION TRANSFORMER.
Pri: 150-250V, 5V steps, Sec: 240V, 13 amps.
£16, carr. pack. £2.25.

GARDNER'S POTTED TRANSFORMER. Pri: 200-250V, Sec: 18V 500mA, 50V 160mA, 6V 250mA output. £1, p.p. 28p.

RIPLEY MAINS TRANSFORMER. Pri: 110V-240V, Sec: 12-5V: 0-12-5V, 750mA, 7V: 0-7V 1A, £1, p.p. 28p.

MAINS TRANSFORMER. Pri: 100-250V, Sec: 22-0-22 200mA, 22-0-22 100mA, 0-24V 20mA, 80p, p.p. 28p.

MAINS TRANSFORMER. Pri: 100-240V a.c. 36-5-0-36-5V, 27mA, 0-21-5, 280 mA, 80p, p.p. 25p.
TRANSISTOR OUTPUT TRANSFORMER. Ratio 8:1, 120mH. Centre tap 2 watts. output, 80p, p.p. 8p.

WODEN MAINS TRANSFORMER. Auto wound. Pri: 200-250V. Sec: 106-135V. 3kVA, £15. Carr. £1.50.

HADDON MAINS TRANSFORMER. Pri: 230V. Sec: 20V 1 amp, £1.60, p.p. 27p.

MIN. MAINS TRANSFORMERS. Type 606/1. Sec: 6V-0-6V, 100mA, 75p. Type 909/1. Sec: 9V-0-9V, 100mA, 81p. 100mA/8, 80p, p.p. 5p each.

SMOOTHING CHOKE. 11MH, 1 1/2in x 1 1/2in x 1 1/2in, 20p, p.p. 8p.

FINNED ALUMINIUM HEATSINK. 4 1/2in x 6in x 1in, 2 x 2N3055, £1, p.p. 13p.

GOODMANS 8in SPEAKERS 3Q £1-50, p.p. 28p.
LOUDSPEAKER 2 1/2in Dia., 40Q, 300m/watts, 60p, p.p. 8p.

FINNED ALUMINIUM HEATSINK. 9in x 8in x 1 1/2in. In C.C.: 4 x 2N3055, £2, p.p. 29p.

GARRARD MAG. TAPE DECKS: 1 1/2 p.s., 60V, solenoid operated brakes, etc. Mains voltage motors 27-80 each, p.p. 60p.

10 REED SWITCHES operated by push buttons and magnets, 50p, p.p. 28p.

COMPONENT PANEL, 6 scr's (300V, 1.6A) 6 cond., 12 resistors, 6 diodes, 45p, p.p. 8p.

COMPONENT PANEL, 1 scr: 100V, 15 amp, 1 diode, 1 cap., 600mfd 50V, 50p, p.p. 7p.

VEEDED ROOT ELECTRICAL IMPULSE COUNTER NON-RESETTING, A.C. 200-250V, £1-10, p.p. 13p.

GEC MAINS CIRCUIT BREAKERS, 2 amp or 5 amp, £1 each, p.p. 14p.

LEVER ACTION P.O. 1000 TYPE SWITCHES
Lock 4-pole changeover, 15p, p.p. 4p. Ex equip.
Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

MULLARD & MALLOY SCREW TERMINAL CAPACITORS 4,500µF 64V, 7,100µF 40V, 50p each. 20,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 21p. 10,000µ + 40V d.c. at 75p, p.p. 12p. 3,000µ + 50V d.c. price 45p, p.p. 7p. 2,000µ + 25V d.c. at 45p, p.p. 8p.

MULLARD PULLWAVE RECTIFIERS 6-48V, 15 amp, 75p, p.p. 10p.

BELLING LEE 1.5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 90p, p.p. 5p.

SOLENOIDS 12 VOLT FULL ACTION 8in x 1in x 1 1/2in, 40p, p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 8p.

SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 1 1/2in, 50p, p.p. 9p.

SOLENOIDS. Manf. by Bensons. 240V a.c. Pull action 2 1/2in x 1 1/2in x 1 1/2in, 75p, p.p. 9p.

OMRON MK8 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, 70p, p.p. 5p.

STC VARLEY, miniature relays 700Q, 17.5-37V perspex cover, 4 pole changeover, 40p, p.p. 5p.

POTTER BRUMFIELD 12V d.c. coil 3 pole c/o contacts rated 7 amp., £1, p.p. 10p.

I.T.T. LOW PROFILE RELAYS. 4 pole c/o/verts. 500Q 12-18V, 75p, p.p. 5p.

MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts, 60p, p.p. 7p.

KEYSWITCH RELAY, 12V d.c. Coil 3 8.P.C.O. 90p, p.p. 5p.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, 28p, p.p. 5p new.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200
Diodes: 1 reed relay: 1 AZ 229 zener ass. capacitor/resistor. Power supply 25V, 250 mA d.c. 240V a.c. £1, p.p. 25p. Ex. equip.

TAPE POSITION INDICATOR
Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED

3 Shenley Road

Borehamwood, Herts.

Tel. 01-953 6009

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types

SHROUDED TYPE

0.5 KVA (2 amp) (MAX) £10.00
 1 KVA (5 amp) (MAX) £14.70
 2 KVA (10 amp) (MAX) £28.10
 3 KVA (15 amp) (MAX) £31.25
 4 KVA (20 amp) (MAX) £72.50
 37.5 amp (MAX) £102.50

200 watt (1 amp) £9.00

CARRIAGE AND PACKING EXTRA

OPEN TYPE 1 amp (panel mount) £9.00



L.T. TRANSFORMERS

All primaries 220-240V

Type No.	Sec. Taps	Price	Post
1	30, 32, 34, 36V at 5A	£6.90	+45p
2	30, 40, 50V at 5A	£9.15	+60p
3	10, 17, 18V at 10A	£7.20	+50p
4	6, 12V at 20A	£8.60	+60p
5	17, 18, 20V at 20A	£9.15	+60p
6	6, 12, 20V at 20A	£8.65	+60p
7	12, 20, 24V at 10A	£6.75	+50p
8	4, 6, 24, 32V at 12A	£8.60	+60p
9	6 and 12V at 10A	£4.30	+40p


300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115V for 115 or 230 volt. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb.

SPECIAL OFFER PRICE £5. Carr. 80p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2. Post 20p. (Total incl. VAT and Post £2.42).

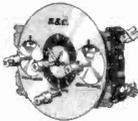

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted diecast case. Tested and in perfect condition £4.75. Post 25p.



FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp. 250 volt. Price 75p. Post 15p.



CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

2,750 r.p.m. Length 2 1/2 in. dia. 1/2 in. shaft 3/16 in. No load 40mA. Ideal for portable recorders, etc. £1.50. Post 15p.



A.C. MOTOR 'Mfg. by AEI'

Smooth running, powerful, continuously rated, reversible motor. 230/250V a.c., 50 cycle 1/50 H.P., RPM 900, 0.25A. £3.50 post 50p.



METERS NEW! 2 1/2 in. Flush round.

Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20. Voltmeter 0-300V A.C. All types £2. Post 15p.



PRECISION CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd. Heavy Duty continuously rated, smooth running, 230/240V a.c. motor. Size: 16 x 14cm (case only). OAL 15cm. Aperture 6 x 6cm. £6.50. Post 50p.



230/240 VOLT A.C. EXTRACTOR FAN KIT

Comprising of impeller, continuously rated motor, motor housing and fixings as illustrated. Price £1.75. Post 25p. (Total incl. VAT and Post £2.20).



MINIATURE UNISELECTOR SWITCHES

2 Bank, 12 position, 24 volt D.C. operation, full wiper with ancillary contacts. NEW Price £2.50. Post 20p. As above but with 5 Bank, 12 position. Price £3.50. Post 20p.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
 Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30. Post 30p.

INDUSTRIAL KIT
 Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. 1/2 output of Hy-Light. Price £12.00. Post 50p.

HY-LIGHT STROBE MK III
 For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12. Post 50p.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

● Variable speed from 1-13 flash per sec.
 ● Reactor control circuit producing an intense white light. ONLY £20. Post 75p.

ROBUST FULLY VENTILATED METAL CASE. For Hy-Light Kit including reflector £5.75. Post 25p.
 Super Hy-Light case including reflector £8. Post 60p.

7-INCH POLISHED REFLECTOR
 Ideally suited for above Strobe kits. Price 35p. Post 15p.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p.

6 INCH COLOUR WHEEL
 As used for Disco lighting effects, etc. Price £4.50. Post 30p.



BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16. Post £1.
 Spare bulb £7. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES
 4ft 40 watt. Price £5.50. Post 30p. 2ft 20 watt, £4.25. Post 25p. (For use in standard bi-pin fittings).

MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube, £1.70. Post 25p. (9in and 12in measures approx.)

AUTO FADE COLOUR BLEND MODULE

Will control up to 750W. of lighting. Automatic fade-up, fade-down at a manually pre-selected timing, which may be varied between 1 second to 1 minute. Based on 10 amp triac for maximum reliability. Ready built with switch and Time Control, on 4" x 5" glass P.C. board. Three modules or more can be sequenced to obtain fantastic colour blending effects. Price £12.50. Post 30p per module.

PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each can operate a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.

4 cam model. £2.50 post 30p.
 6 cam model. £3.25 post 30p.
 12 cam model. £4.00 post 35p.
 6 cam model. 3 r.p.m. £3.25 post 30p.



TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS
 10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV, £1. Post 5p. Type SC146E 10 amp, 500 PIV, £1.30. Post 5p. (Inclusive of data and application sheets.) Suitable Diac 18p.

LED READOUTS
 7 series, L/H d.p. one-third high character. 14 pin D.I.L. Available in RED or GREEN. Price £1.65. Post 10p. 4 for £6. Post paid.



All prices are subject to

10% VAT. (10p in the £)

To all orders add 10% VAT to total value of goods including carriage/packaging.

Superior Quality Precision Made

NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/ohm £1.15. Post 10p.
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/ohm £1.60. Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/ohm £2.35. Post 15p.
Black Silver, Skirted knob included in Nos. 1-9. 1 1/4 in. dia. brass bush. Ideal for above Rheostats. 22p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1)	1	2	3	4
Coil ohms				
Col. (2)	52	4-6	6M	60p*
Working d.c. volts	58	5-9	6 c/o	80p
Col. 3	150	4-9	2 c/o	70p*
Contracts	185	8-12	6M	60p*
Col. (4)	308	9-14	4 c/o	75p*
Price	700	16-24	4M 2B	60p*
HD =	700	16-24	4 c/o	80p*
Heavy duty	700	6-12	1 c/o HD	70p*
	700	20-30	6 c/o	50p*
	2,500	31-43	2 c/o HD	60p*
	2,500	36-45	6M	60p*
	2,400	30-48	4 c/o	60p*
	5,800	7-26	2 c/o	60p*
	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

*Incl. Base
 All prices incl. P. & P.

6 VOLT D.C. 1 make contacts 35p. Post 5p.
6 VOLT D.C. 2 make contacts 75p. Post 5p.

9 VOLT D.C. RELAY 70 ohm coil. 75p. Post 5p.
 3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.

12 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 5p.

24 VOLT D.C. 3 c/o 75p. Post 5p.

ITT LOW PROFILE RELAY
 500 ohm coil, 12-24 volts D.C., 4 c/o. Price 85p. Post 5p each.



CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.

100 VOLT A.C. 2 c/o sealed type, octal base £1. Post 10p.

24 VOLT A.C. Mfg. by ITT. 2 h.d. c/o contacts. 55p. Post 5p.

240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C. 10 amp h.d. c/o contacts. Octal plug in base. Price 75p. Post 5p.

220 240 VOLT A.C. RELAY
 3 c/o 5 amp contacts. Sealed. Incl. 11-pin base £1.25. Post 10p.

HEAVY DUTY A.C. SEALED RELAYS
 110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.

DRY REED RELAYS
 Mfg. by ERG. 12 volt d.c. encapsulated. Single c/o 65p. post paid. Two c/o 85p. post paid. ST 280 ohm coil/12V d.c. 3 make metal shrouded. 60p. post paid.

Other types available, state your requirement.

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V A.C. Black knob in. Fixing hole 1/2 in. ONE bank 30p; TWO bank 40p; THREE bank 50p. Quote for quantity.



HIGH VISIBILITY PANEL MOUNTING LED'S. 0.25 inch mounting, 0.16 inch lens. Typical parameters 2V, 20M amps all type. Supplied complete with snap in mountings and data. Red 4 for £1, Green 3 for £1, Yellow 3 for £1. Post 5p. (In order) (£1).


VERY SPECIAL OFFER

MINIATURE ROLLER MICRO SWITCH. 5 amp c/o contacts Mfg. BONNELLA. NEW. Price 10 for £1.50. Post 10p. (Min order 10)

AS above WITHOUT ROLLER 20 for £2. Post 10p.

INSULATION TESTERS NEW!

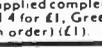Test to IEE Spec. Rugged metal construction. Suitable for bench or field work, constant speed clutch. Size L 8in, W 4in, H 6in. weight 6lb. 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.



24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull, 1 inch travel. Two approx. 1lb pull, 1 inch travel. 6 approx. 4oz pull, 1 inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2.50 P + p 60p.

ABSOLUTE BARGAIN.



All Mail Orders—Callers—Ample Parking
Dept. PE8, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

SERVICE TRADING CO

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
 Phone 01-437 0576

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System - with a big plus over all the other kits - the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888



ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS	£	ELAC 10in 8 ohm Dual cone	3-50
EMI 13in x 8in 3, 8 or 15 ohm		GOODMANS 6in 8 ohm Dual cone	2-15
Plain	2-05		
With Co-Axial Tweeter	2-20	FANE, 7in x 4in, 3 or 8 ohm	1-00
Twin Tweeter	3-70	CELESTION 8in, 15 ohm	1-55
Type 350, 8 ohm, 20W	2-40	ADASTRA 10in, 8 or 15 ohm, 10W	3-45
6in, 8 ohm, 10W	3-75	BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-50
8in, 8 ohm, 10W	5-70		P. & P. 0-30
12in, 8 ohm, 20W	1-25	5in, 8 ohm, C/Mag.	0-85
8in x 6in, C/Mag. 5W	1-25	2 1/2in, 8 ohm or 64 ohm	0-50
8in x 5in, Dual cone 8 ohm, 10W	2-25		P. & P. 0-15
ELAC 8in 8 ohm Dual cone	2-45		

TWEETER AND CROSSOVER	£	Dome Tweeter 8 ohm, 30W	5-40
EMI 3 1/2in, 3 or 8 ohm C/Mag.	1-00	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-10
Cone Tweeter 8 or 15 ohm, 10W	2-40		P. & P. 0-10
Cone Tweeter 8 ohm, 3W	1-45		
Horn Tweeter 8 ohm, 20W	6-40		

KIT FORM CABINETS, TEAK VENEER.	£	13in x 8in cutout <th>3-50</th>	3-50
8in x 5in or 6 1/2in and 3 1/2in cutout	2-45	18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-25
17in x 10in x 9in with 8in or			P. & P. each 0-45

MICROPHONES	£	TW209 <th>5-75</th>	5-75
CM70 Planet stick metal, switch crystal	1-55	CONDENSER MIKE 600 ohm, uni-dir	9-35
DM160 Dynamic omni-dir, ball metal	3-85	Cassette Stick Mike with R. Control on/off switch (2.5 and 3.5mm J/Ply)	1-45
UD130 50K/600 ohm, uni-dir, ball metal	5-75		P. & P. 0-20

SOLDERING IRONS	£	spare Bib, etc.) <th>3-30</th>	3-30
ANTEX CN240 15W	1-90	X25 25W (low leakage)	1-90
SE1 Kit (15 watt iron, 2			P. & P. 0-10

CARTRIDGES	£	8X6H Stereo crystal <th>1-70</th>	1-70
ACOS GP91/28C or GP91/38C Stereo comp.	1-00	8X6M Stereo crystal	1-70
GP93/1 Stereo crystal	1-25	X6H Mono/stereo	1-40
GP94/1 Stereo crystal	1-55	X6M Mono/stereo	1-40
GP95/1	1-35	GOLDRING G800	3-85
GP96/1	1-65	G850	2-95
GP101	0-80	G800E	7-15
GP104	1-65	STYLI FOR ABOVE	P. & P. 0-10
SONOTONE 9THAC Stereo ceramic, diam.	1-70	Sapphire 35p D. Diamond	1-25
19-TI Stereo crystal	0-80	STYLI FOR GOLDRING	1-95
B8R SC5M Stereo ceramic	2-70	G800/G850	3-55
		G800E	3-55
			P. & P. 0-05

BATTERY ELIMINATORS	£	output) 6, 7.5 or 9 d.c. output at 300mA <th>2-15</th>	2-15
240V Input 6, 7.5 or 9 300mA	2-15		P. & P. 0-15
12V d.c. input (please specify			

TAPES	Stnd.	LP	DP	7in	85p	1-15	1-55
5in	60p	65p	85p				0-09
5 1/2in	55p	80p	1-15p				0-30

LOW NOISE CASSETTES	£	Cassette Head Cleaner <th>0-85</th>	0-85
C60	1-5	6-10 lot	0-03
C90	25p	11-20 post free	0-15
C120	45p		
	55p		

PLASTIC LIBRARY CASES for	£	7in Reels <th>0-25</th>	0-25
5in Reels	0-18	CASSETTE CASES	0-10
7 1/2in Reels	0-22	P. & P. 1-3 each 5p; 4 or more	0-20

BIB ACCESSORIES	£	SPECIAL OFFER	
Tape Editing Kit, Ref. 23	1-25	SINCLAIR CAMBRIDGE CALCULATOR (Batt.)	
Recording Tape Splicer, Ref. 20	1-15	★ 4 1/2" x 2" x 1/2", wt. 3 1/2 oz.	
Cassette Tape, Editing, Ref. 24	1-40	★ FLOATING DEC. POINT	
Cassette Salvage Kit, Ref. 25	0-40	★ ALGEBRAIC LOGIC	
12" Cassette Case, Ref. 34	1-50	★ 4 OPERATORS with assistant	
Stylus Balance, Ref. 32A	1-15	★ 8 DIGIT DISPLAY	
Spirit Level, Ref. 46	0-50	Build £19.95 Kit £14.95	
Hi-Fi Stereo Test Cassette	1-90		
Groove-Kleen Record Cleaner	1-90		
	P. & P. 0-10		

Send 25p for COMPLETE CATALOGUE, refundable upon 1st order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics

Mail Order Department PE/8
P.O. Box 470, Manchester M60 4BU

ELECTROVALUE

Present

THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

EVERYTHING BRAND NEW ★ ATTRACTIVE DISCOUNTS ★ FREE POSTAGE (U.K.)

TRANSISTORS

and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc., etc.

MINITRON DIGITAL INDICATORS

30154F Seven segment filament, compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL, £1.20. Now available in 8mA or 15mA per segment rating. Suitable BCD decoder driver 7447, £1.15; 3015G showing + or - and 1 and dec. pt. £1.20.

CAPACITORS

DALY ELECTROLYTIC

In cans, plastic sleeved
1,000mF/25V, 28p; 5,000mF/25V, 62p; 1,000mF/50V, 41p; 2,000mF/50V, 37p; 5,000mF/50V, £1.18; 50,000mF/100V, £2.91; 2,200mF/100V, £1.56.

POLYESTER TYPE C280

Radial leads for P.C.B. mounting. Working voltage 240V d.c.
0-01, 0-015, 0-022, 0-033, 0-047, 3p each; 0-068, 0-1, 0-15, 4p each; 0-22, 5p; 0-33, 7p; 0-47, 8p; 0-68, 11p; 1-0, 14p; 1-5, 21p; 2-2, 24p.

SILVERED MICA

Working voltage 500V d.c.
Values in pF—2 to 820 in 32 stages, 6p each; 1,000, 1,500, 7p each; 1,800, 8p; 2,200, 10p; 2,700, 3,600, 12p each; 4,700, 5,000, 15p each; 6,800, 20p; 8,200, 10,000, 25p each.

TANTALUM BEAD

0-1, 0-22, 0-47, 1-0mF/35V, 14p each; 2-2/16V, 2-2/35V, 4-7/16V, 10/6-3V, 14p each; 4-7/35V, 10/16V, 22/6-3V, 18p each; 10/25V, 22/16V, 47/6-3V, 100/3V, 20p each.

POLYCARBONATE TYPE B32540

Working Voltage 250V.
Values in mF: 0-0047, 0-0068, 0-0082, 0-01, 0-012, 0-015, 3p each; 0-018, 0-022, 0-027, 0-033, 0-039, 0-047, 0-056, 0-068, 0-082, 0-1, 4p each.

CERAMIC PLATE

Working voltage 50V d.c.
In 26 values from 22pF to 6,800pF, 2p each.

POTENTIOMETERS

ROTARY, CARBON TRACK

Double wipers for good contact and long working life.
P20 SINGLE linear 100 ohms to 4-7M Ω , 14p each.
P20 SINGLE log, 4-7k Ω to 2-2M Ω , 14p each.
JP20 DUAL GANG linear 4-7k Ω to 2-2M Ω , 48p each.
JP20 DUAL GANG log, 4-7k Ω to 2-2M Ω , 48p each.
JP20 DUAL GANG log/antilog 10K, 22K, 47K, 1M Ω only, 48p each.
JP20 DUAL GANG antilog 10k only, 48p.
2A DP mains switch with any of above 14p extra. Decades of 10, 22 and 47 only available in ranges above. SKELETON CARBON PRESETS 6p each.

SLIDER

Linear or log, 4-7k Ω to 1M Ω in all popular values, 30p each.
Escutcheon plates, black, white or light grey, 10p each.
Control knobs blk/wht/red/yel/grn/blue/dk. grey/lt grey, 7p each.

JACKS AND PLUGS

Sockets
2-circuit, unswitched, S1/SS 11p
2-circuit/2 break contacts, S1/BB 13p
3-circuit, unswitched (not GPO), S3/SS 15p
3-circuit with 3 break contacts, S3/BBB 20p
2 circuit with chrome nut and black/white/red/green or grey unswitched, S5/SS 14p
2 circuit with chrome nut and black/white/red/green with 2 break contacts, S5/BB 17p
Miniature, 3-5mm, 2-circuit (black), 2 br. cont., S6/BB 8p

EV CATALOGUE 7

2nd Printing (Green and yellow cover)

112 pages, thousands of items, illustrations, diagrams, much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p post free and includes a refund voucher for 25p for spending when ordering goods list value £5 or more.

Plugs

2 circ. screened, top entry, P.1 24p
2 circ. screened, side entry, SEP1 36p
Line socket, mono, 231 40p
Line socket, stereo, 244 45p
3-circuit, unswitched, bl/grey/wh, P.4 46p
2-circuit, unswitched, bl/wh/red/bl/grn/grey, P.2 46p

P2

3-circuit, screened, top entry, P3 18p
3-circuit, screened, side entry, SEP3 55p
Miniature, 3-5mm, 2-circ., screened, P5 13p
Miniature, 3-5mm, 2-circ., unswitched, various colours, P6 10p

INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, tag and nuts. 15A/250V. In blk/brown/red/yel/grn/bl/grey/wh. Type TP.1, 14p each.

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4.7-470K	1-3	1-1	0-9 nett
C	1/2	4.7-10M	1-3	1-1	0-9 nett
C	3/4	4.7-10M	1-5	1-2	0-97 nett
MO	1	4.7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3.9	9	9	8
WW	3	1-10K	7	7	6
WW	7	1-10K	9	9	8

Codes:
C = carbon film, high stability, low noise.
MO = metal oxide, Electrofil TR5, ultra low noise.
WW = wire wound, Plessey.
Values: All E12 except C $\frac{1}{2}$ W, C $\frac{1}{3}$ W, and MO $\frac{1}{2}$ W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.
Tolerances: 5% except WW 10%,
±0.05 Ω below 10 Ω and MO $\frac{1}{2}$ W 2%.
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World". Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90.
The size and weight of this product obliges us to charge 70p part cost of carr. in U.K.
Equaliser Assembly: £2.30.
Loudspeaker Unit: 59RM109, £2.45.
Cabinet Kit (to Baxandall design), £10.45.
Cross-over choke for additional woofer to above, £1.50.

APPOINTED DISTRIBUTORS FOR SIEMENS FINE QUALITY PRODUCTS

ELECTROVALUE LTD
All postal communications, mail orders, etc., to Head Office at Egham address, Dept. PE8.
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475 Shop hours—9-5.30 daily. Saturdays 9-1 p.m.
Northern Branch: 680 BURNAGE LANE, BURNAGE, MANCHESTER M19 1NA
Telephone 061-432 4945 Shop hours—Daily 9-1 and 2-5.30 p.m. Saturdays 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081

ELECTROLYTICS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
uF	0-47	—	—	—	—	—	11p	8p
1-0	—	—	—	—	—	—	11p	8p
2-2	—	—	—	—	—	—	11p	8p
4-7	—	—	—	11p	—	—	8p	9p
10	—	—	—	—	8p	—	8p	9p
22	—	—	—	—	—	8p	8p	10p
47	8p	—	—	—	8p	8p	8p	10p
100	9p	8p	8p	8p	8p	10p	12p	19p
220	8p	8p	9p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

ZENER DIODES full range E24 values: 400mW: 2-7V to 36V, 14p each; 1W: 6-8V to 82V, 21p each; 1-5W: 4-7V to 75V, 67p each. Clip to increase 1-5W rating to 3 watts (type 266F) 3p.

VEROBORD

Copper clad 0-1 in. matrix—2.5 x 3.75 ins., 27p. 3.75 x 3.75 ins., 30p. 2.5 x 5 ins., 30p. 3.75 x 5 ins., 33p.
Copper clad 0-15 in. matrix—2.5 x 3.75 ins., 20p. 3.75 x 3.75 ins., 30p. 2.5 x 5 ins., 30p. 3.75 x 5 ins., 36p.
Vero spot face cutter (any matrix), 48p. 0-040 pins (for 0-1 matrix) per 100, 35p. 0-052 pins (for 0-15 matrix) per 100, 35p.

KNOBS

In a great variety of modern types, for $\frac{1}{2}$ in. shaft, from plastic to solid aluminium, from typically 63p per pack of two (Catalogue 7, page 62).

CONNECTORS

DIN from 2-way to 7-way plugs and sockets; phone types, mains connectors, etc. (Catalogue 7, page 88).

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14.99. 15% on orders £15 and over.

PACKING AND POSTAGE FREE

In U.K. for pre-paid mail orders. For orders £2 and under, there is an additional handling charge of 10p.

GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, "seconds" or sub-standard merchandise is offered for sale.


PRICES QUOTED DO NOT INCLUDE VAT, for which 10% must be added to total nett value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices are subject to alteration without notice. S.A.E. with written enquiries please.

GIRO ACCOUNT No. 38/671/4002

look! electronics really mastered


... practical
... visual
... exciting!

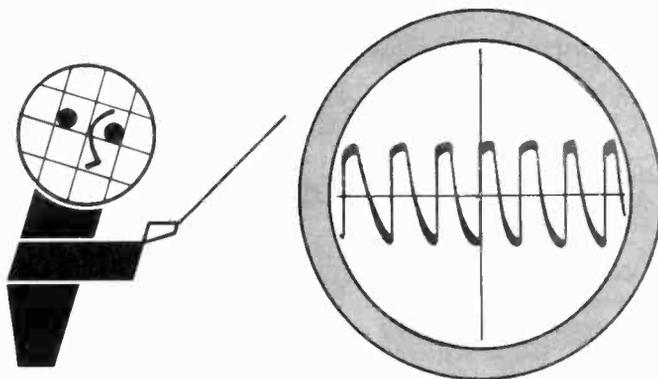no previous knowledge
no unnecessary theory
no "maths"



BUILD, SEE AND LEARN

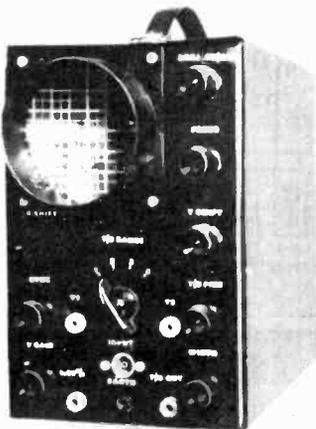step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.




RAPY

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

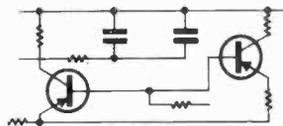2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL 84

special free gift also to all our students

THE CONSTRUCTOR'S LOT

A LETTER published last month must have stirred some memories. It also provokes this question: must technical progress necessarily mean an erosion of pleasure and satisfaction for the ordinary electronics constructor? For example, can a contemporary lightweight assembly on a small piece of s.r.b.p. match a robust chassis-mounted unit typical of the valve era in terms of pride in accomplishment engendered in the builder?

Nostalgia for the past is not to be derided, but it must not blind us to the very real practical advantages of modern techniques. Pride in achievement is not to be equated merely with size and mechanical complexity. A special craftsmanship is required to produce a first class miniature assembly; and generally more dexterity and patience is demanded than when working on a larger scale model. The constructional business is unmistakably different today—but it still offers its challenges and its rewards.

The fear of our correspondent H. T. Kitchen (*Readout* July) that in the next decade construction may be degraded to an operation of merely joining together modules has some basis, it is true. Yet there is a brighter compensatory side to the picture, we feel sure. To begin with, l.s.i. and circuit modules are in the main designed to meet the requirements of mass produced equipments. The private constructor is hardly likely to want to enter in competition in all such cases, but he can take advantage of the existence of particular components of the kind referred to and make use of them in less orthodox ways in circuits or systems of his own or some other's devising. In other words the private designer and constructor is better equipped to explore pastures new. And this has always been one of the reasons for amateur activity anyway. So really the only fears that one can envisage concerning the future are based upon the assumption that individual enterprise in initiating new designs and new applications will cease to be as prolific as in the past. A couple of moments reflection will surely convince any doubting Thomas that such a proposition goes entirely against human experience.

Without doubt the physical aspect of construction will continue to change, with an appreciable reduction in the amount of traditional workshop practices like "metal bashing" called upon. But this easing of the mechanical effort is likely to be adequately balanced by the greater possibilities arising from expanding areas of application.

To speculate about the future of electronics in general is of course always tempting and maybe some of our readers would like to do some crystal ball gazing on their own account. Our correspondent expressed fears—"... on the constructor's lot in say ten years time." Well, ten years from now brings us to that ominous date created by George Orwell. Nineteen eighty-four will also be of some (but happier, we hope) significance to this magazine, since come October of that year PRACTICAL ELECTRONICS will have completed its second decade.

Readers' own predictions concerning likely or possible developments in electronics and their effect upon the constructional field during the course of the next ten years are invited. Please refer to page 687 for details.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210


C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202



HIGH IMPEDANCE VOLTMETER

By T.P.MANNING & R.HIDER

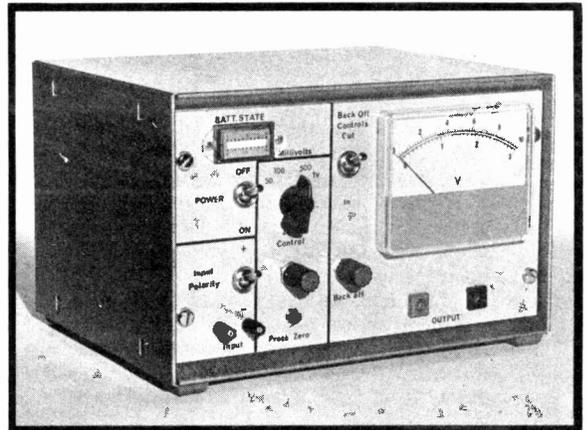

An instrument for biophysical and other sophisticated scientific measurements

AN INSTRUMENT capable of measuring the output from a circuit or a device without having any effect on the circuit or device is, of course, the scientist's dream, particularly when that instrument is also sufficiently sensitive to detect variations in state of some of the transducers around today.

Typical examples of difficult-to-measure areas include thermocouples, photoelectric cells, thermistors, pH electrodes, ionisation chambers, physiological and biological investigation, and of course quite a lot of current electronic circuitry. The problem in basis is that in most cases the signal to be measured comes from a very high impedance source and/or the source is not capable of delivering sufficient current to drive an ordinary indicator such as a moving coil meter.

A number of solutions have been proposed in the past to allow measurements to be made under these circumstances including the use of very sensitive galvanometers for thermocouples and the development of the so-called electrometer valve circuitry for the high impedance sources.

Both are expensive solutions and in the case of the latter, in fact a noisy (electrically) and fairly unstable instrument is produced unless a great deal of attention and money is paid to special circuit design. Instruments have in fact been made very successfully, the EIL pH meter to mention the most famous, but low costs and, in fact true flexibility were not their hall mark.

MODERN TECHNOLOGY

The advent of solid-state technology has done much to redress the situation. The first step being the appearance of the f.e.t. (field effect transistor)

with its ability to provide a circuit with very high input impedance not unlike a valve.

The second really useful item is the operational amplifier which cuts out a mass of discrete components and complex circuit design for the engineer and leaves him free to worry about the system.

The most useful device in the present context is the f.e.t.-input operational amplifier, of which several are available on the market now.

APPLICATION AREAS


Taking the availability of such devices as read, it becomes possible to consider just where they might be useful and obviously some form of replacement for the old electrometer voltmeter is feasible.

Such an instrument would be capable of indicating the condition of thermocouples, thermistors, light cells, perhaps even pH electrodes and ionisation chambers or photomultipliers. It would be possible to use such an instrument in the experiments where cell resistances, human body potentials and those in plants are measured. In fact a wide range of electronic and scientific measurements become possible without a great deal of expense.

Perhaps more important, the use of operational amplifiers facilitates the provision of an output dependent on the signal being examined but at a far higher level and power, which can be then used for chart recording, indication at remote points or even for control purposes.

Thus in the case of the plant cell measurements, a feedback potential dependent on the cell potential could be provided quite easily.

*The University of East Anglia

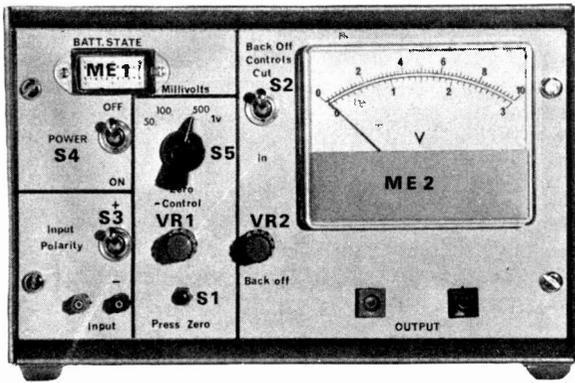

designation NE536T from Signetics (S.D.S. Components).

The output from the input amplifier is fed to the second i.c., in this case the 709 or 741 operational amplifier, which can now amplify the signal as required to give the desired sensitivity and can, at the same time provide a "back-off" feature where the zero of the instrument can be moved, in a voltage sense, within set limits to offset input voltages, measure particular levels with a greater sensitivity and so on.

In addition, of course, the 709 is capable of providing a fairly hefty output which means that within sensible limits the instrument can drive almost any indicator and still have sufficient spare output to drive a chart recorder if this is needed.

The basic circuit of such a system is shown in Fig. 1.

IC1 is the f.e.t.-input device which acts as a non-inverting amplifier with a gain of 1 because of the feedback link from output pin 6 to inverting input pin 2.

SENSITIVITY

IC2 provides all the amplification necessary for most purposes and, as can be seen, the gain of this stage is set by selection of the feedback resistor R3 using S5. It should perhaps be added that the capacitor C1 and the capacitor and resistor combination C2 and R9 are frequency-determining components which are specific to the 709 i.c. used. If a 741 device were used these would not be necessary but can be left on the circuit.

The output of IC1 is fed to the inverting input of IC2 and switch S3 serves to again invert the output of IC2 so that the meter acts in unison with the input. This switch can be used to reverse the meter connection so as to effectively reverse the input polarity if needed. R10 is a series resistor chosen to suit the meter ME2 so as to set the f.s.d. at 1V and this latter level is chosen in the prototype because there are chart recorders with this as a standard range.

Of course, other values may be used but it is advisable to ensure that the selected value does not approach too closely to the supply rail voltage, in the present instance 4.7V. In fact ME2 is a 100 μ A moving coil meter in the prototype.

The effective zero point of the meter may be adjusted by means of VR2 which is a ten-turn Helipot used to give sufficient resolution to this function. Whilst this device is expensive it will none-

theless be found very useful in practice. As can be seen, this "Back-off" function can be switched out using S2.

Back-off is limited to 1.5V with the arrangement shown but experiment will show that the value may be altered if desired. However, again care should be taken not to approach right up to rail potential which can produce non-linearity. In addition, whilst a ten-turn potentiometer is used here to give good resolution, particularly at low input potentials, VR2 can be replaced by a normal potentiometer if the resolution is not needed.

VR1, the "set zero" potentiometer, is a standard component and both potentiometers are brought out to the front panel.

The indicator ME1 is in fact a so-called "roller indicator" which both indicates the ON state of the instrument and gives some idea of the condition of the batteries.

POWER SUPPLY

In this latter area it can be seen that two PP9 units are used to give a + and a - supply. Resistors R5 and R11, in conjunction with Zener diodes D1 and D2 serve to regulate the supply to 4.7V on each rail. This has proved ample in the prototype and in fact in tests carried out with a 10mA load on the output as well as the meter ME2 indicating, the instrument has been run for several hours without any ill effect.

The main reason for selecting a lower power rail potential is to extend battery life and ensure in the meantime that rail potentials do not suffer since any unbalance in these can "throw" the meter completely.

The "set zero" shorting switch S1 is of the change-over type which is a must as IC1 input must be shorted to ground when zero is being checked to remove any input voltage. At the same time, it may well be that to short the circuit an object under examination might damage it, as is the case with plant cells for example.

It is suggested that battery operation of this equipment be accepted as normal. The drain is not high and the problems involving mains-borne interference and other items associated with anchoring a very high impedance device to main supply lines are almost impossible to avoid. In addition this is particularly the case if cost is important.

In any event, the present arrangement is both simpler, makes for portability and there is always the added point that many of the measurements which this type of instrument can effect need either a screened environment into which mains supply must not be passed or, more important can involve application of electrodes to person or animal or plant, with consequent risk of dangerous shock if mains supply is used.

CONSTRUCTION

As can be seen from the illustrations (Fig. 2 is the p.c.b. master and Fig. 3 the component layout), construction of the basic printed circuit board follows normal procedure with the exception that, for convenience of mounting ranging resistors, two edge

COMPONENTS . . .

Resistors

R1	47 Ω
R2	2.2k Ω
R3	See Text
R4	150k Ω
R5	100 Ω
R6	1k Ω
R7	47 Ω
R8	2.2k Ω
R9	1.5k Ω
R10	See Text
R11	100 Ω
All	$\pm 2\%$ $\frac{1}{4}$ W carbon

Potentiometers

VR1	10k Ω
VR2	1k Ω , Ten-turn Helipot or like, see Text

Capacitors

C1	22pF
C2	470pF

Diodes

D1	BZY88 4.7V Zener
D2	BZY88 4.7V Zener

Integrated Circuits

IC1	FET MOPA or NE536T
IC2	709 operational amplifier or 741

Switches

S1	2-pole changeover spring return push button
S2	1-pole changeover
S3	2-pole changeover
S4	2-pole on/off
S5	1-pole multi-way dependent on ranges required

Miscellaneous

Battery state/on/off indicator ME1; 100 μ A moving coil meter ME2; glass-fibre p.c.b.; terminals; wire solder; case and matching front, etc.

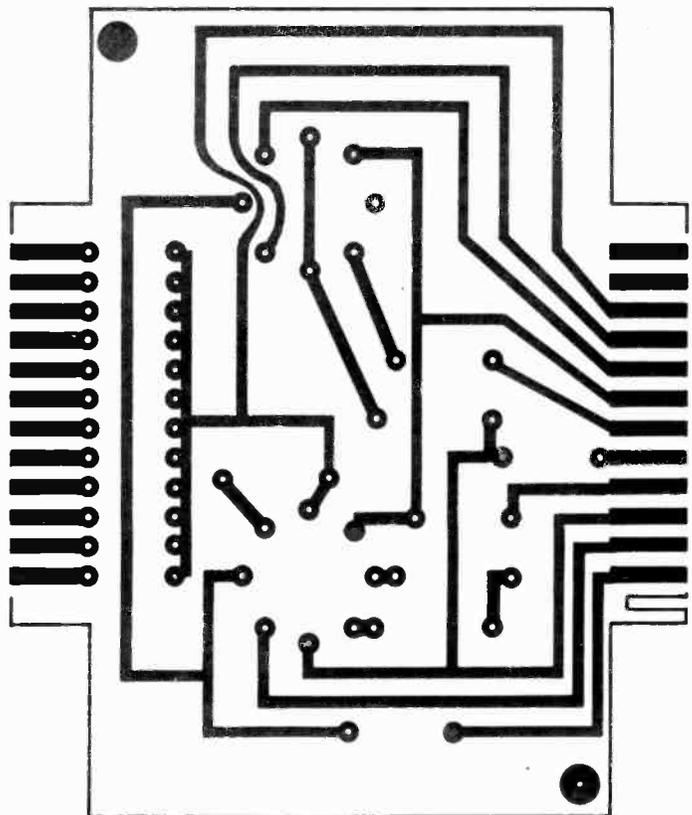


Fig. 2. A printed circuit layout for the circuit of Fig. 1 showing the use of two edge connectors so that all ranging resistors can be board mounted

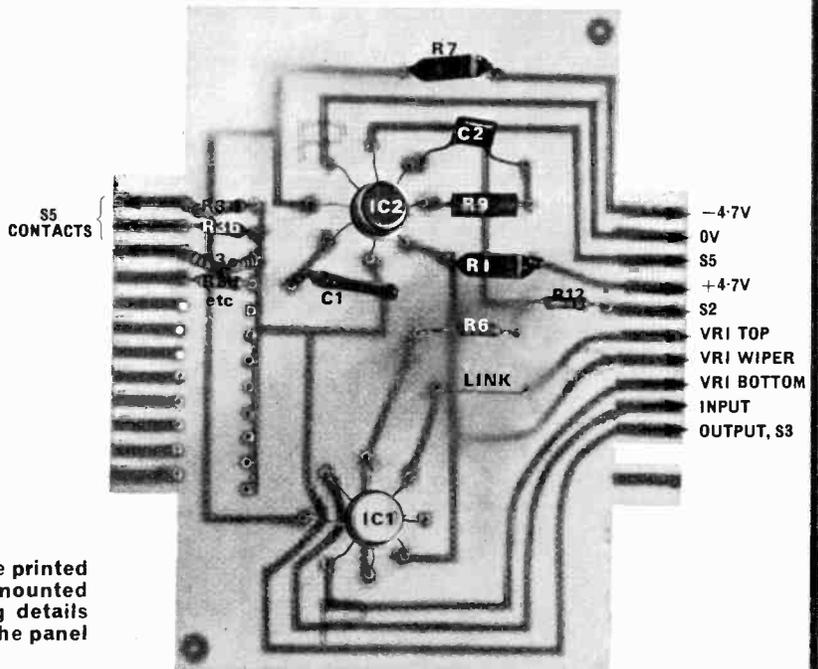


Fig. 3 (right). A photograph of the printed circuit board with components mounted and annotated, and with wiring details from the two edge connectors to the panel and case-mounted components

connectors are used to interconnect the board and the various switches and other controls. The case chosen for the prototype is in fact somewhat larger than is really required and could be replaced with a smaller box. Equally, some of the components could be omitted if required.

For example there is no real need for the indicator ME1 to also be a battery state indicator, a simple lamp would suffice or, indeed the device could be omitted altogether.

There is no particular mystery to the layout of the front panel. It was selected to show each control in a "functional" manner so as to be clear to students and others not familiar with this type of device.

One point which does require some care is the assembly of the input operational amplifiers on to the p.c.b. It should be remembered that these are f.e.t.-input devices and thus have somewhat sensitive inputs, not only to the signals you wish to amplify but to such problems as static electricity.

Whilst the devices are protected it is still much less expensive in the long run to, for example, disconnect the soldering iron from the mains when working on the board during or after having mounted IC1.



FEEDBACK SELECTION

The operational amplifier in the second stage is used to provide amplification of the input signal level to give a 0-1V output for the required level of input. The gain of this stage is equal to the feedback resistor value divided by the input resistor value.

In the present case the input resistance is R6, with a value of 1k Ω . Thus if the lowest (most sensitive) range is to be 0 to 50mV, the range resistor R3 needs to have a ratio relationship with the input resistor of 1V divided by 50mV which is 20. As R6 is 1k Ω R3 must be 20k Ω .

Thus we need R3 values of 20k Ω , 10k Ω , 2k Ω and 1k Ω , for ranges of 50mV, 10mV, 500mV and 1V f.s.d.

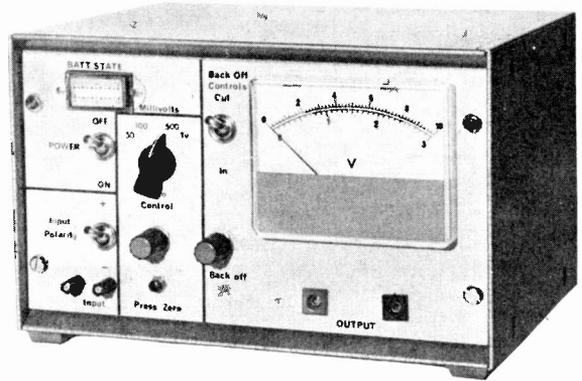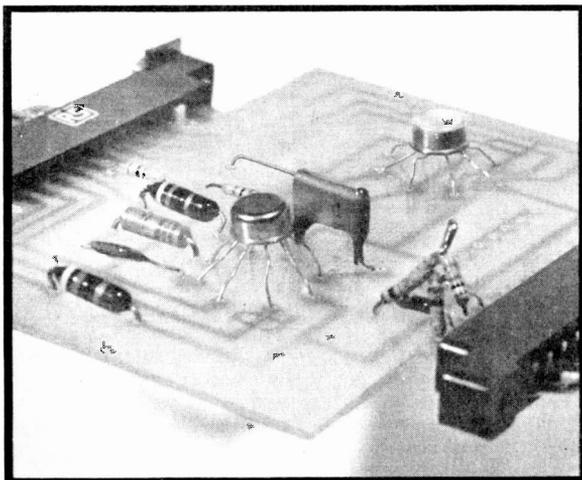The reader is of course free to set up his own range values to suit his meter or other factors.



INPUT IMPEDANCE

Whilst the specification figures for the FET MOPA mention 10¹⁴ Ω input impedance and 10¹¹ Ω to 10¹⁴ Ω for the NE 536T, these values are only properly obtainable if some very stringent precautions are taken with the construction of the input circuitry. In the first place most printed circuit board just could not match the sorts of figures mentioned, particularly the s.r.b.p. variety which is somewhat hygroscopic and thus leaky when considering the sorts of impedance being discussed here.

In all probability the input impedance of the instrument described will end up around 1kM Ω if good glass board material is used. For most purposes this is quite sufficient but if higher figures are needed then construction becomes critical.

The input conductors of the operational amplifier IC1 would have to be attached to terminal posts in the tops of p.t.f.e. pillars and the input leads would have to be taken directly to the pillars from the input terminals.

In addition, normal terminals mounted in the body of a metal case would be out of the question. The terminals would need to be mounted in something like a sheet of acrylic (Perspex) which would give each terminal about 25mm clearance from the metalwork and each other.

The limiting factor for the input impedance under these circumstances becomes perhaps the humidity of the atmosphere around and inside the meter or perhaps the presence of any dirt or damp on the underside of the i.c. itself.

One other factor of importance. If it is required to achieve the highest possible input impedance then both the input amplifier, standoff pillars, acrylic sheet and terminals should be washed in pure alcohol or some other similar solvent to remove any traces of dirt or grease and even moisture trapped on the surface of the devices. After such a washing the parts should be handled as little as possible since each fingerprint contains all the contaminants needed to reduce the impedance by quite a large amount.

DIFFERENTIAL INPUT

The basic instrument described here is adequate for most applications but there are occasions where a differential input can be of assistance. It is not too difficult to adapt the basic circuit as is shown in Fig. 4 by the addition of a further input amplifier.

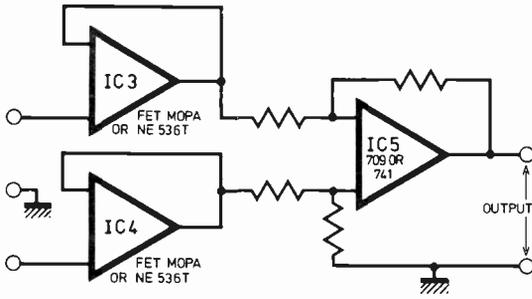


Fig. 4. Modification of the system of Fig. 1 to cope with differential measurements

DIFFERENTIAL pH METER

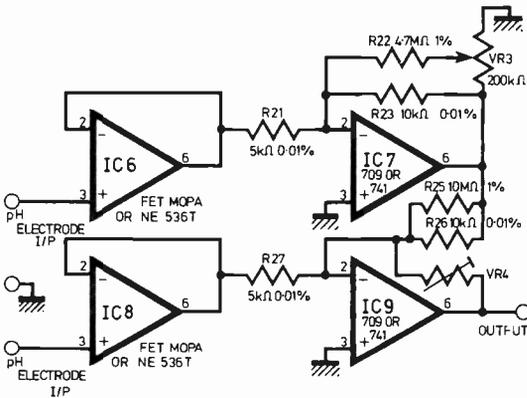


Fig. 5. A differential system with high sensitivity as suggested in a scientific paper in Analytical Biochemistry

PLANT CELL MEASUREMENTS

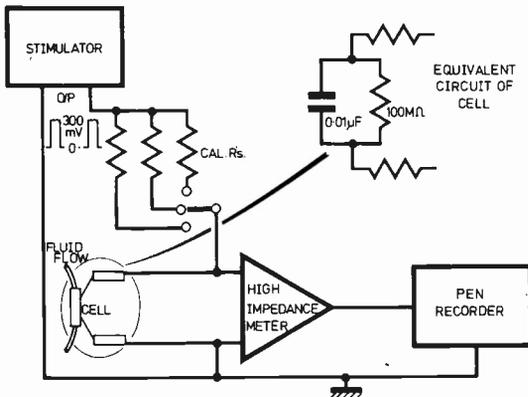


Fig. 6. Plant cell potential being measured using the basic high impedance meter

The only difference of any moment is that the upper of the two input amplifiers is set to zero using a skeleton potentiometer which is pre-set. The lower amplifier set-zero potentiometer is used on the front panel as in the basic circuit.

The output operational amplifier, the 709 or 741, is used in differential mode.

A modified form of differential instrument was the subject of a paper published in *Analytical Biochemistry* 13, 556-563 (1971) where the authors showed that it was possible to measure pH changes as low as 0.001pH using a high impedance voltmeter configuration as in Fig. 5.

Here the gain has to be adjusted to suit the scale of the recorder being used at the output and, of course, the instrument has to be kept in a very stable temperature environment if the claimed accuracy is to be achieved. Currently the authors are working on a version of this concept.

APPLICATIONS

The instrument described in detail is currently in use carrying out examination of the effects of electrical stimulation and of various materials being passed through plant cells. The general circuit is shown in Fig. 6 where it can be seen that the meter measures the output from the plant cell continuously and records the result on a pen recorder.

The plant cell is fed with various fluids which are continuously pumped through. Two micro-electrodes pierce the cell walls and the meter is connected across them.

The "High" side of the meter/cell interface is connected to a switch and a set of calibration resistors which are in turn connected to a stimulator which provides stimulus pulses as and when required.

The scientist needs to know how the cell reacts and what changes occur dependent on fluid and electrical stimulation. Using the arrangement shown he can monitor the cell continuously and can also calculate the value of the cell impedance. In most cases this is equivalent to an RC parallel circuit and the impedance varies with the type of cell. Measurements have provided results from 2MΩ up to 100MΩ.

In some experiments the stimulator can be replaced with a d.c. source and then the output of the meter used to control the rate of flow of the supply fluid.

MONITORING

Other obvious applications include the monitoring of thermocouples, particularly where fairly long leads are involved since the resistance of the latter, in conjunction with any indicator which required current to drive it, would sadly effect the accuracy of the system.

Monitoring the inputs to other high impedance devices such as f.e.t.s is possible with this instrument, as are many physiological experiments involving the resistance of the human body or the ability of muscles to produce potentials detectable at the skin surface. In this context this particular form of equipment offers itself for consideration in experiments involving the provision of a feedback signal which could be used for example to control other stimuli such as lights or sounds as well as for recording purposes.



FIRST STEPS IN CIRCUIT DESIGN

5

By A. P. Stephenson

This series, specially written for the beginner, takes you step-by-step through transistor circuit design in a simple, non-mathematical way.

Design of a small signal amplifier will be followed by a Class B amplifier and the series will conclude with a constructional project so that your theoretical knowledge can be put into practice.

THE MAIN theme of this month's article is methods of achieving high input impedance in amplifiers. The Darlington amplifier is a simple but costly way of producing the desired result whilst the much more subtle "bootstrapping" technique gives excellent results with the addition of only a capacitor and resistor to the basic emitter follower.

After this we take a quick look at negative feedback techniques. We have seen an example of nega-

tive feedback in the emitter follower, but it is usual to apply negative feedback over a stage or a series of stages in order to increase stability, reduce distortion and noise, and increase impedance.

We end this description of small signal amplifiers with a look at a well-designed amplifier designed by the Mullard team which makes use of the principles covered so far.

5.1. DESIGNING FOR VERY HIGH INPUT RESISTANCE

Some signal sources (crystal microphones, photo-diodes, etc.) only deliver very tiny currents because of their very high source resistance. An attempt to amplify such signals will only be successful if the input resistance of the amplifier is also very high.

Although emitter followers have this property, the possibility of achieving R_{IN} of the megohm order is still difficult.

A simple answer is the Darlington pair, the basic circuit of which is shown in Fig. 5.1.

Remembering a previous equation for a single stage emitter follower $r_{in} = h_{ie} r_e + R_E$ and assuming r_e is negligible in relation to R_E , we may simplify this to $r_{in} = h_{ie} R_E$.

However, this circuit uses two stages of amplification so that the formula becomes $r_{in} = (h_{ie1} \times h_{ie2}) R_E$ where h_{ie1} and h_{ie2} are the respective gains for the two transistors.

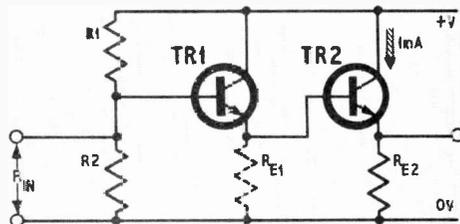


Fig. 5.1 Two transistors connected as a Darlington pair. The dotted resistor is not strictly part of the Darlington, its use is explained in the text

Assuming they are both the same, the equation becomes $r_{in} = h_{fe} R_E$.

For example, if R_E is $5k\Omega$ and h_{fe} is 100, r_{in} becomes about $50M\Omega$ which is so high in relation to the shunting of R_1 and R_2 that it can be ignored in the calculation of R_{IN} .

It is easy to see therefore that the R_{IN} of the stage is almost entirely determined by R_1 , R_2 values.

The R_{E1} resistor is to complete the divider chain for the base of TR2 and also to pump a little more collector current into TR1. Without it, the base current of TR2 would be the collector current of TR1 which would reduce its h_{fe} too much. A possible set of components is shown in Fig. 5.2. This circuit gives an R_{IN} of nearly $0.7M\Omega$ (R_1 and R_2 in parallel).

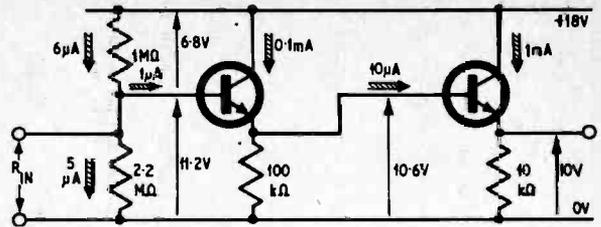


Fig. 5.2 Typical component values for a high input impedance, Darlington pair amplifier

5.2. INPUT BOOTSTRAPPING

There is a novel method of increasing the input resistance of an emitter follower stage known as "bootstrapping". The purpose is to increase R_{IN} by effectively removing the bias resistors from the signal path. Two extra components are needed as shown in Fig. 5.3.

BOOTSTRAPPING ACTION

Resistor R_3 is made small enough not to interfere with the d.c. bias. Note that the signal voltage V_{IN} is at one end of R_3 and the output voltage (via C_1) is at the other end.

Now V_{OUT} is in phase with V_{IN} and has almost the same amplitude (voltage gain = 1).

Thus, it follows that

Both ends of R_3 are at the same potential and no signal current can pass through.

This means that the signal can carry out its proper function of changing the base current without wasting half of its energy flowing down R_1 , R_2 .

Bootstrapping thus effectively removes R_1 and R_2 from the stage input resistance formula.

Thus $R_{IN} = r_{in}$ and r_{in} can be made very high.

CHOICE OF R_3

The choice of R_3 is not critical providing the base current does not produce any appreciable voltage drop (much less than 0.6V is the usual criterion).

Capacitor C_1 should have a reactance (X_c) less than R_3 at the lowest expected frequency. This ensures that the high input resistance is maintained at all signal frequencies.

Fig. 5.3 shows typical component values for a circuit having an input resistance of approximately $18M\Omega$.

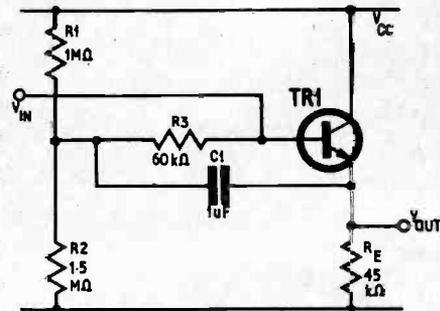


Fig. 5.3. By the addition of capacitor C_1 and resistor R_3 to the basic emitter follower circuit, one obtains the very high input impedance "bootstrap" configuration. The circuit shown here gives an input impedance approaching $18M\Omega$.

5.3. COUPLING LOSSES

Suppose we have one amplifier stage which, on its own, gives a gain (A) of 100 and we feed the output into another stage having a gain $A = 50$. A miserable disappointment is in store for those hoping the overall gain would be 5,000.

The output resistance of stage 1 and the input resistance of stage 2 form a voltage divider which causes a "coupling loss" between the stages.

OVERALL GAIN

To calculate the overall gain between signal e.m.f. and final output it is customary to treat coupling losses as "gains".

For example, if we lose half the signal at some point due to coupling loss, we can say the "gain" of the coupling is 0.5.

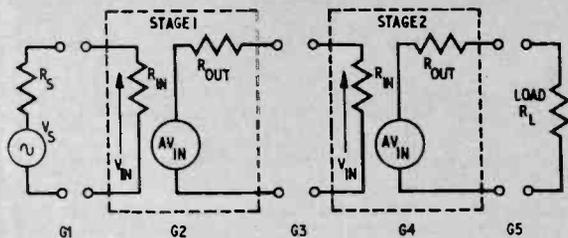


Fig. 5.4. A multistage amplifier may be envisaged as a series of blocks each having a "gain" G . The total gain is then obtained by multiplying the individual gains.

In this way we can work methodically through a multistage amplifier as if it consisted of isolated blocks, and by multiplying all the individual gains we can find the total gain.

EXAMPLE

To illustrate the procedure, consider the circuit shown in Fig. 5.4. In this example there are five "gains" in all. G_1 , G_3 , and G_5 are fractional gains (losses) and G_2 and G_4 are actual stage gains.

Let $G_1 = 0.2$, $G_2 = 100$, $G_3 = 0.1$, $G_4 = 100$, $G_5 = 0.5$.

Then the total gain = $0.2 \times 100 \times 0.1 \times 100 \times 0.5 = 100$.

It is advisable to use this method of analysis in all multistage amplifiers.

5.4. MINIMISING COUPLING LOSSES

To illustrate the seriousness of the problem consider the following system.

A pick-up has an output e.m.f. of 5mV , a source impedance of $5\text{k}\Omega$ and is feeding an amplifier having a gain A of 100. The R_{IN} of the amplifier is $10\text{k}\Omega$ and R_{OUT} is $2\text{k}\Omega$. The final load on the amplifier is $5\text{k}\Omega$.

Now the coupling loss between the pick-up and amplifier is

$$G_1 = \frac{10\text{k}\Omega}{10\text{k}\Omega + 5\text{k}\Omega} = 0.67$$

The gain of the amplifier gives

$$G_2 = 100$$

The coupling loss between the amplifier output and final load is

$$G_3 = \frac{5\text{k}\Omega}{5\text{k}\Omega + 2\text{k}\Omega} = 0.71$$

The total gain is $G_1 \times G_2 \times G_3 = 0.67 \times 100 \times 0.71 \approx 48$.

Thus a gain of supposedly 100 has been reduced to a mere 48.

RULES ON COUPLING

Some rules and tips on coupling designs are clearly worth memorising.

1. Keep output resistances low and input resistance high.
2. The R_{IN} tends to rise if I_c is lowered.

The R_{OUT} tends to fall if I_c is increased.

Thus we have a conflict of requirements—to satisfy the requirement of R_{IN} or R_{OUT} .

Mathematical analysis indicates that

Total losses will be minimal if the input and output coupling losses are arranged to be equal.

There is of course an easy way out—just put an emitter follower between every stage. This is a little extremist however, and could be rather costly if adopted as a general principle.

5.5. NEGATIVE FEEDBACK

DEFINITION

Negative feedback is the feeding of part, or the whole, of the voltage or current from some later stage of an amplifier back to an earlier stage. The phasing of the voltage must tend to *reduce the gain*.

CLASSIFICATION

Series voltage feedback—the voltage fed back is in series with the input. This increases R_{IN} .

Parallel voltage feedback—voltage fed back is in parallel with the input. This reduces R_{IN} .

EQUATIONS

If A is gain before feedback. A' is gain with feedback and β = fraction of output which is fed back then

$$A' = \frac{A}{1 + \beta A}$$

If βA is large, the equation reduces to

$$A' = 1/\beta$$

This indicates a remarkable property—the gain of the amplifier can be made independent of the components inside it, including the transistors themselves!

In addition to this obvious advantage, negative feedback will reduce distortion and internally generated noise, and change input and output resistances *in the same ratio as the gain is reduced*.

In view of this, it is good design practice to produce a gain higher than required and reduce it by negative feedback to the desired value.

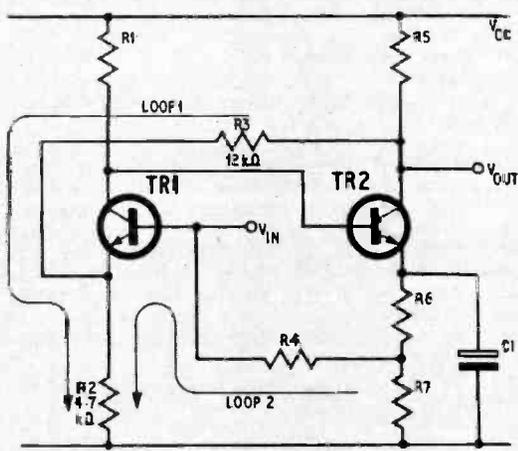


Fig. 5.5. An example of good amplifier design. The circuit shown here has two feedback loops for d.c. stability, as well as signal negative feedback

The circuit in Fig. 5.5 is from the Mullard design team and is an excellent example of the use of d.c. and signal negative feedback. By altering component values, gain can be increased to 100.

FEEDBACK LOOPS

There are two negative feedback loops, and their subtlety should be carefully studied.

Loop 1 is producing signal negative feedback, the feedback fraction being

$$\beta = \frac{R_2}{R_2 + R_3}$$

The total closed loop gain (A') is given by

$$A' = 1/\beta = \frac{R_2 + R_3}{R_2} = 3.4$$

The open loop gain is of course much higher because it is basically two grounded emitter amplifiers in cascade.

Note that the feedback is *series* type because it is applied back to the emitter of TR1.

Loop 2 is not acting on the *signal* because C1 is keeping TR2 emitter at ground. Therefore this loop is stabilising d.c. conditions only.

Continued next month

NEWS BRIEFS

New Information Retrieval System

During the course of the past five years many attempts, particularly by the large American multi-national companies, have been made to produce an efficient microfilm information retrieval system to reduce the ever demanding space requirements of documentation.

Many mechanical systems have been evolved, with extreme limitations on speed, accessibility and reliability. Now, a British company, Selectro-Micro Ltd. (part of the Westminster Holding Group) has developed a fully automatic, electronically-controlled information storage and retrieval system with print-out known as Selecta-copy.

This will provide, for the first time, an electronic facility for keeping over one million documents in one small room (as opposed to over 40 times the office and storage space required, and the staff costs involved) and making each document immediately available in just a few seconds.

Calling China

BRITAIN'S telephone service with the People's Republic of China, which until recently had been available for only three hours a day, became full-time with a switch over to satellite communications.


This facility is made possible by the opening in China of a satellite Earth station using the *Intelsat-IV* communications satellite positioned 22,300 miles above the Indian Ocean.

Telephone calls from Britain to China are now beamed from the Post Office satellite Earth station at Goonhilly Downs, Cornwall and received by China's new Earth station, near Peking.

Keep Moving

TRAFFIC signals in Nottingham will soon be controlled by a Ferranti data transmission and computer system as part of an integrated traffic scheme for the city centre. A dual Argus 700E system, valued at more than £250,000, ordered by Nottingham Corporation will be connected via data links to 128 out-stations.

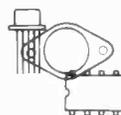The scheme is part of Nottingham's plans to avoid costly large scale road building and widening by concentrating on optimising traffic flow over a wide city area and making more efficient use of existing roads.



THE NEXT DECADE ?


What does the future hold in store for electronics in general, and for electronics constructors in particular?

Your views and predictions concerning likely developments in the next 10 years are invited.

A selection of readers' contributions to this debate will be published in our November and December issues to mark the completion of this magazine's first 10 years of publication.

Contributions (not exceeding 300 words and entitled "The Next Decade") should be addressed to *The Editor, Practical Electronics, Fleetway House, Farringdon Street, London, E.C.4* and posted in time to reach our offices by August 21, 1974.

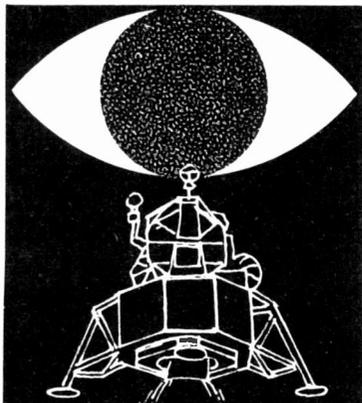A payment of £5 will be made for each letter published. Selection will be based upon originality of thought, technical credibility and general presentation.



SPACEWATCH

BY FRANK W. HYDE

APPLICATIONS TECHNOLOGY SATELLITE

In August, after trials are completed, the U.S. applications technology satellite will go into service. This satellite, the first of its kind, may well have far reaching effects on the shaping of future societies. Versatile and having the facilities for the transfer of command, the one and a half ton vehicle is the largest communications satellite built so far.

The facilities provide for education transmissions in the form of lessons where the students can be taught to read and write under direct supervision. The remote and developing areas, where illiteracy is still a major problem, can be covered by this one satellite. Many other uses will be made in the field of agriculture, medical service, hygiene, family planning and food preparation.

Another important application is the use of community television sets in places like India and Africa and will provide a service for the improvement of the people. In a "Spacewatch" report on the development of India's space projects mention was made of the cheap aerial systems to enable the signals of this powerful satellite to be received.

Under a contract with the American Government, India will not only have the use of the satellite facilities but it will be under their direct control. To bring this about, the satellite will be moved to a position near Africa and north of the equator. The only connection with operation that America will have during the year of loan, will be the loan of the satellite.

To bring all this about the satellite will first be put into a geostationary orbit near South America. From there the whole of the United States will be covered by the transmissions. Many uses are planned during the satellite's first run.

Medical contact with remote areas like Alaska will enable physicians to see patients direct on television screens and instruction will be given to medical assistants on the spot, as to treatments. A network will be available so that conference diagnosis can take place with a number of specialist hospitals.

Seminars will be set up by television links so that teachers in remote areas can continue their own training in advanced techniques of education. The complete facilities of instructor and student, with visual aids, are as would be available in the lecture room. Two-way voice communication will be used in a number of original experiments.

The satellite, which is 27 feet high and 30 feet in diameter, has solar panels which will provide 200 kilowatts of power. The power available is some 30 times more than any previous system. It is for this reason that extensive and continuous cover of these vast areas can be made, using the cheap receiving systems at the community centres. The transmitting aerial on the satellite is so shaped and steered that the whole of the area to which it is directed can be covered effectively.

After its period at the station in the 22,300 mile orbit above South America, the motors will be activated and the satellite will move to

the new station near Africa where it can serve India. This is expected to take place in mid-May 1975. During its stay there one of the experiments will be to observe the arrival of the monsoon in various parts of India. This will help in making predictions for the future, and setting the correct period for cropping the rice and timely replanting before the beginning of the monsoon.

After its sojourn in the area of India the satellite will once more return to its first orbit where it is expected to serve the United States for several years more. This is dependent on the life of the solar cells. Thus, this venture may pave the way to a world system making the facilities available to the whole world. Not the least of the benefits is the possible and more efficient control of aircraft in flight, and world wide network of medical facilities.

DOMESTIC SATELLITE

The recent launch of the domestic satellite, somewhat similar to that set in orbit for Canada, is in a synchronous orbit such that, with the shaped aerial, signals will be received over 48 states. The satellite is named *Westar* and is the first of a series to be launched by the Western Union Telegraph Company.

The weight of *Westar* is about 1,250 lbs. This is the first commercial satellite to be put in orbit and represents the change from national funding to private enterprise. Thus, another milestone in space history is set up.

Final checkout of Westar, America's first domestic communications satellite, at Hughes Aircraft.

The satellite's ribbed antenna is capable of transmitting a signal to cover the 48 states, and also has the capacity to reach Alaska, Hawaii and Puerto Rica



ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 16" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in.



with STEREO and MONO XTAL £6.75 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Chrome fittings.

Motor board cut for above BSR deck £4.50 Post 45p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 8 in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls.



240V a.c. mains. Bargain Price £25 85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-90 MINUTES



Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.

£1.95 Post 25p

WEYRAD P50 - TRANSISTOR COILS

RAZW Ferrite Aerial 85p
I.F. P50/2CC 470 kc/s 40p
3rd I.F. P50/3CC 40p
Spare Cores 3p
Driver Trans. LPDT4 85p
Printed Circuit, PCA1 85p
J.B. Tuning Gang 85p
Weyrad Booklet 10p
OPTI 85p

Mullard Ferrite Rod 8 x 1/2 in., 20p. 6 x 1/2 in., 20p. 3 x 1/2 in., 10p.

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or L.N. L/S 15p. D.P. 25p. STEREO L/S 50p. D.P. 75p. Edge 5K. S.P. Transistor 25p.

80 Ohm Coaxial 5p yd.

BRITISH AERIAL XE AERIAL-AIR SPACED 40 yd. £1.75; 80 yd. £2.60 FRINGE LOW LOSS. Ideal 625 and colour 10p yd

8in. or 10x6in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance, 5 watts, 8 m.w. power.



£3.75 Post 25p

E.M.I. 1 1/2 x 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p

£4.50

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p



£6.60

Bookshelf Cabinet Teak finish 13 1/2 x 8 in Bass Woofer, 20 watts, 15 ohms, £5.50

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK £2.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 a.w.g. 2; in sides 8 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 9 in 90p; 16 x 9 in 90p; 12 x 3 in 60p; 4 x 4 in 70p; 8 x 4 x 4 in 60p; 8 x 4 x 4 in £1. 2; 4 x 4 in £1.30. ALUMINIUM PANELS 18 a.w.g. 6 x 4 in 12p; 8 x 6 in 19p; 14 x 3 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p; 16 x 9 in 34p; 14 x 9 in 40p; 12 x 12 in 47p; 16 x 10 in 60p. S.R.P.B. PAXOLIN PANEL 10 x 8 in 20p.

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5in HI-FI SPEAKER TYPE 59RN This famous unit now available, 10 watts, 8 ohm.

Price £3.30 Post 25p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V a.c. Output voltages available 8 or 9 or 12 or 15 or 18 or 20V at 100mA or 150mA. PLEASE STATE VOLTAGE REQUIRED. £2.20 Post 25p Details S.A.E. Size 3 1/2 x 1 1/2 in.

RCS POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. £2.95 Post 25p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mika, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. £99p Post 25p Full instructions supplied. Details S.A.E.

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. 95p Post 20p

BRITISH FM/VHF TUNING HEART

88 to 108 M/C/S British made. 2 Transistors ready aligned requires 10-7 M/C/S J.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 Post 20p

MAINS TRANSFORMERS

Eagle MT12 12-0-12V 50 mA 90p
250-0-250 80 mA, 6-3V 3-5A 6-3V 1A or 5V 2A £2.50
350-0-350 80 mA, 6-3V 3-5A 6-3V 1A or 5V 2A £3.00
300-0-300V 120 mA, 6-3V 4A C.T.: 6-3V 2A £3.95
MINIATURE 200V 20 mA, 6-3V 1A 2 1/2 x 2 1/2 in. 75p
MIDCI 220V 45 mA, 6-3V 2A 2 1/2 x 2 1/2 in. 90p
HEATER TRANS. 6-3V 1.5A 85p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £3.00
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3.00
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.00
3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £5.00
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.75
5, 8 and 13V. 5 amp. £1.20; 3 amp. 3, 5, 8, 10, 13 or 5-0-5V £1.30, Dittos 5 amp. £1.50; 6-0-6V 500mA 90p 9V 1 amp. 95p, 12V 300mA 75p, 12V 500 mA 85p, 12V 750 mA 95p, 40V 1 amp. £1.75.

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V £5.00; 500W £6.25; 750W £10; 1000W £15
CHARGER TRANSFORMERS. Input 200/250V, for 6 or 12V, 1 1/2 amp £1.50; 2 amp £1.60; 4 amp £2.50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V output, 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. £10 50p
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS			
2/350V	14p	250/25V	14p
4/350V	14p	500/25V	20p
8/450V	18p	1000/25V	35p
16/450V	22p	1000/50V	47p
32/500V	50p	8/1450V	22p
25/25V	10p	8/16/450V	25p
50/50V	10p	18/1450V	40p
100/25V	10p	32/32/350V	65p

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 15p; 25V 35p; 50V 47p; 100V 70p.
2500mF 6V 25p; 25V 47p; 50V 57p.
5000mF 50V 85p; 3000mF 25V 47p; 50V 65p.
5000mF 8V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 85p.

CERAMIC. 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0.5 13p; 1mF 150V 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1-15p; 0.25-8p; 0.47-25p.
SILVER MICA. Close tolerance 1%. 2.2-500pF 4p; 580-2,200pF 18p; 2,700-5,800pF 20p; 8,000pF-9.81, mfd 30p each.
TWIN GANG. "0-9" 200pF-170pF 65p; 500pF standard 45p. 355F-385F with 25p-35p. Slow motion drive 50p.
SHORT WAVE BINGLE. 10pF, 30p, 25pF, 55p, 50pF, 55p.
NEON PANEL INDICATORS 250V AC/DC. Amber 20p.
RESISTORS. 1W, 1W, 20% 1p; 2W, 5p, 10p to 10M.
HIGH STABILITY. 1W 2% 10 ohms to 1 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each.
TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER", 12IN 50 WATT. GROUP 50/12. 6 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. £16

BAKER MAJOR 12" £9.90



30-14,500 c/s. 12in. double cone, woofer and tweeter cone, together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwellis. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50
Please state 3 or 8 or 15 ohms. Post free

BAKER "BIG-SOUND" SPEAKERS Post free

'Group 25' 12in. £8.80 25W 3 or 8 or 15 ohm
'Group 35' 12in. £9.90 35W 3 or 8 or 15 ohm
'Group 50' 15in. £20 50W 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER AND CABINETS
For 12in or 10in dia. speaker 26 x 13 x 9in. £10.50. Post 50p
For 13 in or 8in speaker 16 x 10 x 9in. £6.60. Post 35p
For 8in and Tweeter 16 x 8 x 8in. £5.00. Post 25p
For 8in and Tweeter 12 x 8 x 6in. £4.00. Post 25p
LOUDSPEAKER CABINET WADDING 18in wide. 20p ft

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response. 30-12,000 c/s. £4
Ideal P.A. Columns.
Hi-Fi Enclosure Systems, etc.
Suitable Cabinet 12 x 8 x 6 1/4 Suitable Tweeter £2

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in deep. Rating 10W, 3 ohm. Crossover £1.90 Post 20p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s. 10W 8 ohm or 15 ohm £2.25. De Luxe Horn Tweeters 2-16kc/s. 15W. £3.50.
CROSSOVERS. TWO-WAY 3,000 c/s 3 or 8 or 15 ohm £1.25. LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in., £1.25; 6 1/2in., £1.50; 8 x 5in., £1.60; 10in. £2.00; 8in. £1.75; 10 x 6in. £1.90.
SPECIAL OFFERS. 90 ohm, 2 1/2in. 2 1/2in. 35 ohm, 2in. 3in. 25 ohm, 2 1/2in. dia. 3in. dia. 5in. dia. 15 ohm, 3 1/2 in. dia. 6 x 4 in. 7 x 4 in. 8 x 5 in. 3 ohm, 2 1/2 in. dia. 3in. dia. dia. (6 x 4 in 8 ohm £1.50)
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in diameter 4W £2.50. 10in diameter 5W £2.50; 12in diameter 8W £2.95. 3/8/15 ohms, please state.
VALVE OUTPUT TRANS. 40p. MIKE TRANS. 50:1 40p. Mike trans. mu metal 100:1 £1.25.
Loudspeaker Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. 3in spindle. 65p each. Post 15p

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. £49 Carr. £1.00
PROFESSIONAL VALVE MODEL, 100W, callers only, £38.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 8V. TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, Treble and bass controls. 18 volt d.c. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 10p. OUTLET BOXES, SURFACE, FLUSH 60p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 300 ohms. 7p yd. JACK SOCKET Std. open-circuit 14p. closed circuit 23p; Chrome Lead-Contact 45p. Phone Plug 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p. 5-pin 10p. DIN SOCKETS lead 3-pin 10p; 5-pin 15p. DIN PLUGS 3-pin 10p; 5-pin 25p. VALVE HOLDERS, ser: CERAMICS 10p; CAMS 5p.

REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt. £2.20
applied: 1 1/2 x 1 1/2 in. size 3 1/2 x 3 1/2 in. As illustrated. With Cooling Fan. a.c. 240V. Post 25p

E.M.I. GRAM. MOTOR. £1

1,200 or 240V a.c.
2,400 r.p.m. 2 pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p

SPECIAL OFFER

106 Ohm 20W Rheostat 2 1/2 in. diam. Ceramic Former, screw terminals. 3in diam. spindle. 85p. post 25p.

337 WHITEHORE ROAD, CROYDON
Open 9-6, Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)
Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

RADIO COMPONENT SPECIALISTS

Radio Books and Component Lists 10p. (Minimum posting charge 20p.)

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR Tel. 021-327 2339

SILICON P.N.P.			SILICON N.P.N.		
Type	Voltage	Price	Type	Voltage	Price
BC 71	105	200 MHz	2N 3053	60	100 MHz
BFS 92	100	70 MHz	2N 3707	30	100 MHz
BFS 95	40	70 MHz	2N 5179	20	900 MHz
BFX 12	25	210 MHz			
2N 2906	60	200 MHz	GERMANIUM P.N.P.		
2N 3702	40	100 MHz	ACV 44	50	1 MHz
2N 3703	50	100 MHz	ADY 26	80	75 watts
			AF 124	20	75 MHz
			AFY 19	32	350 MHz
			ASY 32	25	5 MHz
			ASZ 21	15	450 MHz
			GET 113	32	2 watts
			GET 120	32	2 watts
			OC 73	30	1 MHz
			OCF 70	30	Light-sensitive
			2N 1307	30	10 MHz
			2N 1309	30	15 MHz
			2N 443	80	150 watts
			HIGH FREQUENCY POWER		
			BFR 64	40	1,200 MHz
			BLY 89A	35	650 MHz
			BLY 93A	60	500 MHz
			BLY 218	36	1,200 MHz
			2N 708	15	800 MHz

MICROWAVE DEVICES			Type	Price
CL 8300	Gunn effect oscillator	9.4 GHz		£40
CL 8370	ditto	9.5 GHz		£10
CL 8380	ditto	10.5 GHz		£10
CL 8390	ditto	11.5 GHz		£10
CL 8430	ditto	9.35 GHz		£40
CL 8450	ditto	9.35 GHz		£40
CL 8470	ditto	9.35 GHz		£40
BXY 27	Varactor Diode "S" Band, Cut-off	70 GHz		£1
BXY 28	Varactor Diode, Cut-off	100 GHz		£1
BX 32	Frequency Multiplier, "X" Band	150 GHz		£1
BXY 35A/C	ditto	25 GHz		£1
BXY 36C/D	ditto	75 GHz		£1
BXY 37C/D	ditto	100 GHz		£1
BXY 38C/E	ditto	120 GHz		£1
BXY 39C/D	ditto	150 GHz		£1
BXY 40D/E	ditto	180 GHz		£1
BXY 41C/D/E	ditto	200 GHz		£1

12 VOLT FLUORESCENT LIGHTING



Inverter Transformers 13/15 watt (circuit included) **70p**
 "Current Economy" Transistor (600mA) **50p**
 "Maximum Light" Transistor (1.3A) **50p**
 Resistors/Capacitors to suit **15p**
 Lampholders:
 (Long lead) (pair) **30p**
 (Short lead) (pair) **20p**
 White Enamelled Case, 18 or 21in **70p**
 Tube, 18in/15 watt or 21in/13 watt **45p**
 (Note: tube only supplied if Case also ordered, to prevent postal damage)
 13 watt fitting, ready built and tested (including tube) **£3.75**

ALL GOODS PLUS 10% V.A.T. POST/PACKING 20p PER ORDER

£1 100 1/2 WATT RESISTORS 100 CERAMIC CAPACITORS 100 DIODES POSTAGE 23p	£1 1 VEROBOARD CUTTER 5 1/2 in. x 1 in. x 0.15 BOARDS 50 SQ. INS. "ODD PIECES" VERO POSTAGE 23p	£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC. POSTAGE 23p	£1 8 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS & CAPACITORS POSTAGE 23p
PACK No. 1	PACK No. 3	PACK No. 5	PACK No. 7
£1 100 RESISTORS 100 CERAMIC CAPACITORS 100 POLYSTYRENE CAPACITORS POSTAGE 23p	£1 100 RESISTORS 100 CERAMIC CAPACITORS 50 MULLARD POLYESTER CAPACITORS POSTAGE 23p	£1 1 TRANSISTORISED SIGNAL TRACER KIT 1 TRANSISTORISED SIGNAL INJECTOR KIT POSTAGE 23p	£1 100 RESISTORS 100 CAPACITORS (ASSORTED TYPES) POSTAGE 23p
PACK No. 2	PACK No. 4	PACK No. 6	PACK No. 8



...there are over 8,000 electronic components WITHIN A FEW FEET OF YOU!

That is, assuming you are on the telephone.

If you're not, the distance is between you and your nearest post box.

The first thing you need, to enable you to get your components quickly, easily, economically, is a copy of the 240 page Home Radio Components Catalogue. Apart from listing the vast range of lines we stock, it contains details of our popular Credit Account Service and many other items of useful information. For example, as there are several ways of ordering, several ways of paying and several ways of delivery, the pros and cons of all methods are clearly set out in the catalogue.

We have the reputation of providing the best-organised service ever offered to buyers of electronic components. Of course, to make good use of this service you need the catalogue. It costs 55 pence, plus 22p post and packing, and when you receive your copy you'll agree it's the best investment you've made for a long time. Moreover with the catalogue we give you 10 Vouchers each worth 5 pence against orders, an up-to-date price list and a Bookmark with a useful list of technical abbreviations.

Please write your Name and Address in block capitals



Name _____

Address _____


Send off the coupon today with cheque or Postal Order for 77p. It's your first step to solving your component buying problems.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses

Home Radio (Components) Ltd. Reg. No. 912886, London
 Dept. PE, 234-240 London Road, Mitcham, CR4 3HD.

INGENUITY UNLIMITED

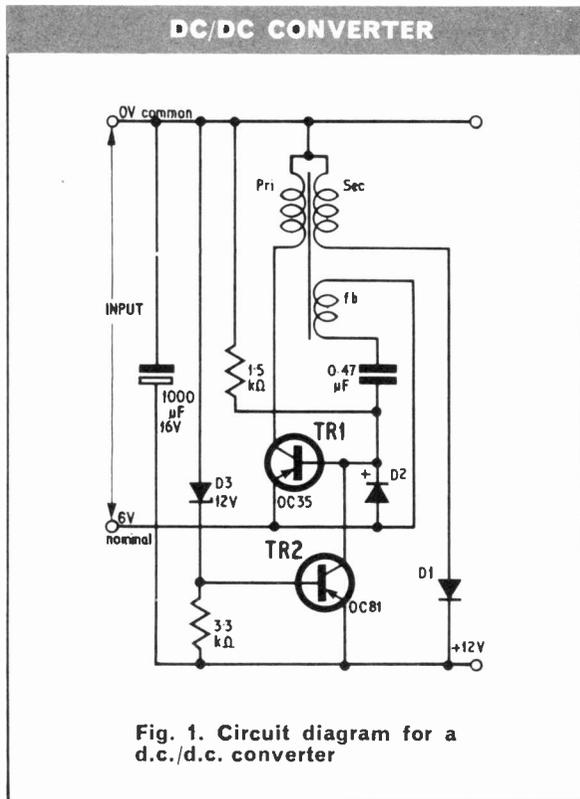A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.



THE diagram of Fig. 1 is a d.c./d.c. converter designed initially to provide 12V d.c. for a car radio from a 6V supply. In fact it can operate as is to provide the 12V from any input ranging from 4 to 8.5V.

Since the voltage of a nominally 6V car system can rise to 8.5V the transformer was constructed to suit the maximum voltage. It was wound on an old output transformer core, using 45 turns 22 s.w.g. for the primary, 130 turns 22 s.w.g. for the secondary, and 25 turns 28 s.w.g. for the feedback windings.

Diode D1, which provides rectification of the output, and D2, which protects TR1 base against excess reverse bias may be any silicon type with a current rating greater than 500mA. D3 is a 12V Zener diode.

If no oscillation is obtained the connections to the feedback windings should be reversed. Also,

since the output waveform is unsymmetrical it may be necessary to reverse the output windings to obtain maximum power. The quiescent current of the unit is around 125mA.

The regulation circuit is effective since, when the breakdown voltage of D3 is reached, TR2 conducts, making the base of TR1 positive with respect to its emitter and therefore turning the inverter off. When the voltage across D3 falls to below its breakdown voltage oscillation starts again and the output is thus accurately maintained.

The circuit is easily adapted to provide for other input and output voltages by winding the transformer accordingly, at five turns per volt, and choosing an appropriate Zener diode; neither the exact number of turns nor the gauge of wire used are critical.

G. Blackwell,
Stretford, Manchester.

THIRD HAND HEATSINK

WHEN building a radio recently, I reached a situation in which an octopus would have been hard-pressed to keep hold of components, soldering iron, solder, PCB, etc., and I needed yet another hand to hold my pliers on the transistor lead as a heatsink.

To overcome this problem I turned my mind to alternative self gripping heatsinks and being a medical student I hit on the idea of using Spencer Wells forceps. These are ideal for the job being long and able to reach inaccessible places, self locking to grip the wire or wires (usually grips an artery) and they have a thermal capacity high enough to act as an efficient heatsink. The ability to grip more than one lead at once makes soldering of multi-lead components much faster.

The forceps are about 5 inches long and cost approximately 55p from medical or scientific instrument dealers.

Mr. W. R. Saywell,
Oxford.

PRACTICAL ELECTRONICS

● INDEX

An index for volume 9 (January 1973 to December 1973) is now available price 11p inclusive of postage.

● BINDERS

Easi-binders with a special pocket for storing blueprints and data sheets, etc., are available price £1.34p including VAT and postage. State required volume, e.g., Vol. 1, 2, 6.

Orders for Binders and Indexes should be addressed to the Post Sales Department, IPC Magazines Ltd., Carlton House, 66 Gt. Queen Street, London, W.C.2.

THE times when a potential Texas millionaire could hammer a bean stick into his back garden and hit a gusher have, as we all know to our cost, long since gone. All the same, world economy is so tied to elusive "black gold" that life, without the potential energies of oil and natural gas, would be unthinkable—at least for the next few decades.

The energy shortage, increased industrial expansion, extended use of plastics and chemicals and exorbitant prices from some exporting countries have put more emphasis on the backroom boys of the oil business—the explorers.

This article deals with the ultimate method for locating potential oil sources—Reflection Seismology—and it shows the role electronics plays in keeping our cars running, gas stoves burning and polythene bags packing!

EVOLUTION OF OIL

Oil is usually found in areas of the world that are described, by the geologist, as sedimentary basins. These are areas that once, many millions of years ago, were covered by sea. As time went by the seas dried and left thick layers of sand and silt which contained an abundance of dead organic marine life. At the same time the sand was covered by salt from the sea and as millions of years went by further deposits were laid down on top of the salt—brought there by wind, rivers, floods, or even more recent seas.

Our experience shows that the most prolific geological period when these dead sea creatures were deposited was the Tertiary Era (approximately 70 million years ago) although there were significant

deposits during the Cretaceous period (150 million years ago) and as far back as Permian times (over 300 million years ago); and even before Carboniferous times, in the Ordovician period 500 million years ago.


During these millions of elapsed years the dead marine organisms were subjected to terrific pressures and temperatures, along with the sands and silts, from the shear weight of subsequent deposits. The thickness of deposits since the start of the Tertiary period alone conservatively exceed 8,000 feet in many parts of the world. These pressures and temperatures slowly compressed the sands together to form a solid, but porous rock—sandstone—and the organic matter trapped within this porous rock slowly changed in physical and chemical structure to form liquid hydrocarbons—crude oil and gas.

EARTH MOVEMENTS

As time went by the earth's crust was subjected to all sorts of deformations, as it still is today. Protracted earth movements gradually folded these "source" rocks into convolutions; more dramatic earthquakes might have sheared through rock beds giving rise to vertical displacements we know as faults and in some instances the two might have occurred together. Where we are lucky the earth might have moved to form a structure like an underground hill, we call a dome. The gas, oil and water trapped in the sandstone would percolate upwards through the pores in the rock to the top of the dome where they would meet the layer of salt—also solidified into rock.

The salt is impervious to liquids and gases and might prevent the minerals from further movement. Thus the thin layer of oil over a large region might migrate towards the top of a dome and be trapped there under pressure from the gas above and the water below. Similar processes could occur in the

*Seismograph Service (England) Ltd.

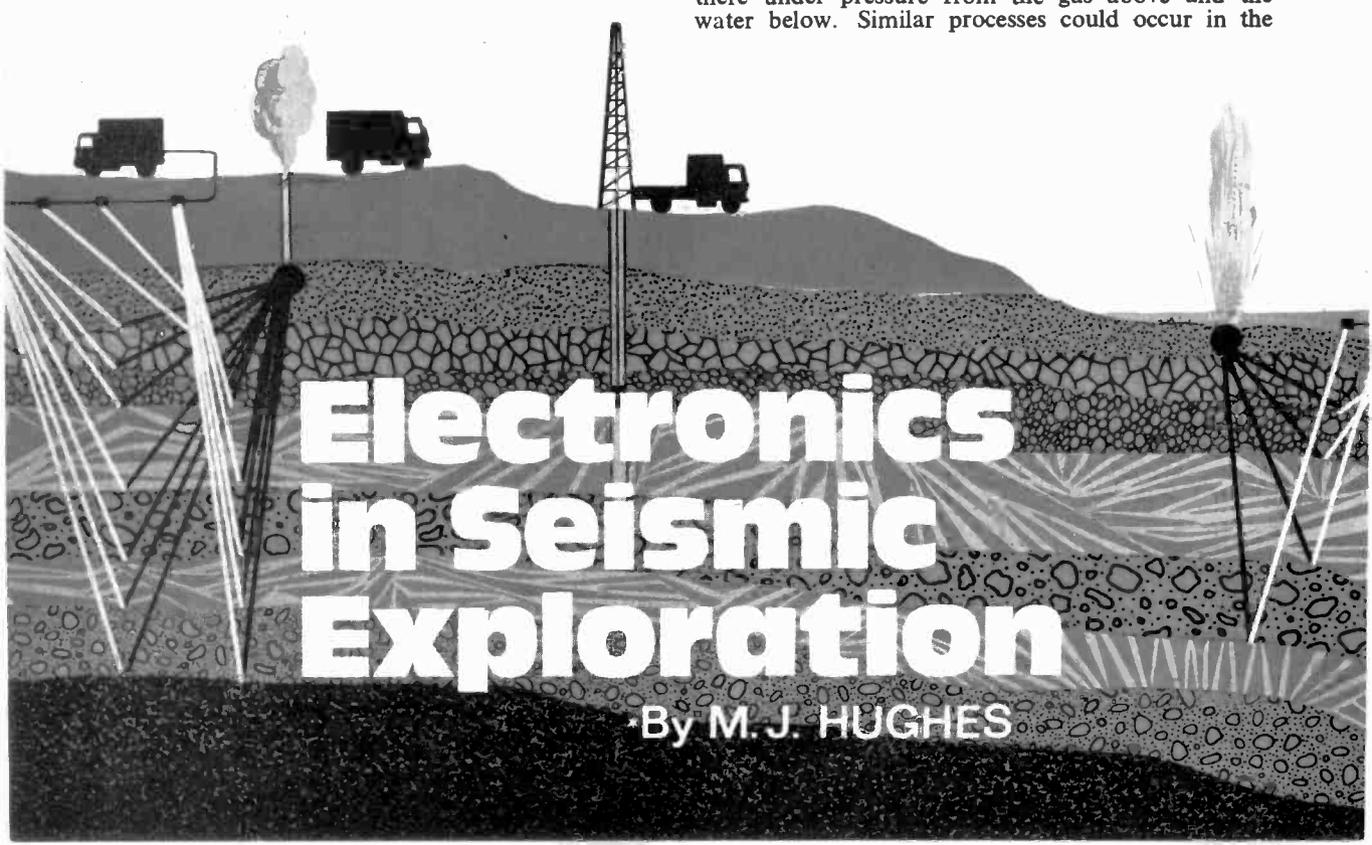

Electronics in Seismic Exploration

By M. J. HUGHES

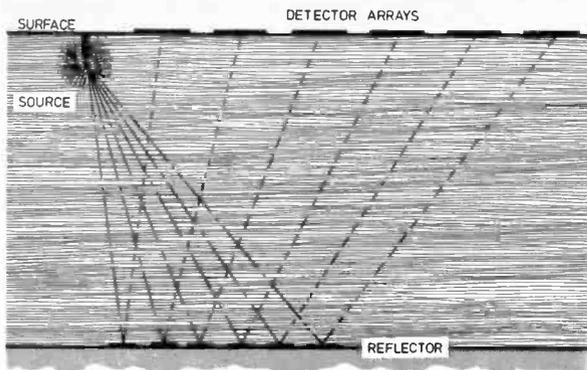


Fig. 1. Simple schematic of seismic ray paths

case of faulting or other unconformities in the laminar structures of rocks. Any structure that encourages this migration of oil into a large reservoir area is called a trap. The sediments in which oil and gas are found today are known as "reservoir" rocks.

Seismic exploration enables mapping of the sub-structure of the earth in precise detail and from its results the location of these traps. Provided the geological history of the area is correct and a trap structure found there just might be oil if it were drilled for. The chance of drilling into a reservoir of commercial value is still, however, ten-to-one against. A single "wild cat" oil well might well cost the best part of a million pounds so great confidence in the accuracy of a seismic survey is essential.

SEISMIC REFLECTIONS

The seismic reflection method is based on the same principles as ASDIC except the distances involved, through solids or water, are very much greater. An


acoustic signal is generated at the surface of the earth and this passes through the ground, downwards, as a spreading compressional wavefront (Fig. 1). As the wave passes through interfaces between rocks having dissimilar density, or velocity of propagation, a small proportion of the downward going energy is reflected (usually one or two per cent) the rest passes through to the next interface and so on.

Considerable wastage of energy occurs due to frictional losses, poor reflection coefficients, and downward reflections from horizons when a wave is on its way back to the surface. When a reflected signal does reach the surface it might, very well, have travelled over four miles.

GEOPHONES

To stand any chance, at all, of receiving a useful reflection signal there must be a lot of energy at the source. On land an explosive source is used—anything between 20 and 100lb of dynamite. This is placed at the bottom of drilled and tamped holes to try and deflect the energy downwards. In the simple case signals are received back at the surface with a geophone. This is a high sensitivity, low frequency response (down to about 8Hz) moving coil microphone—but there is a difference.

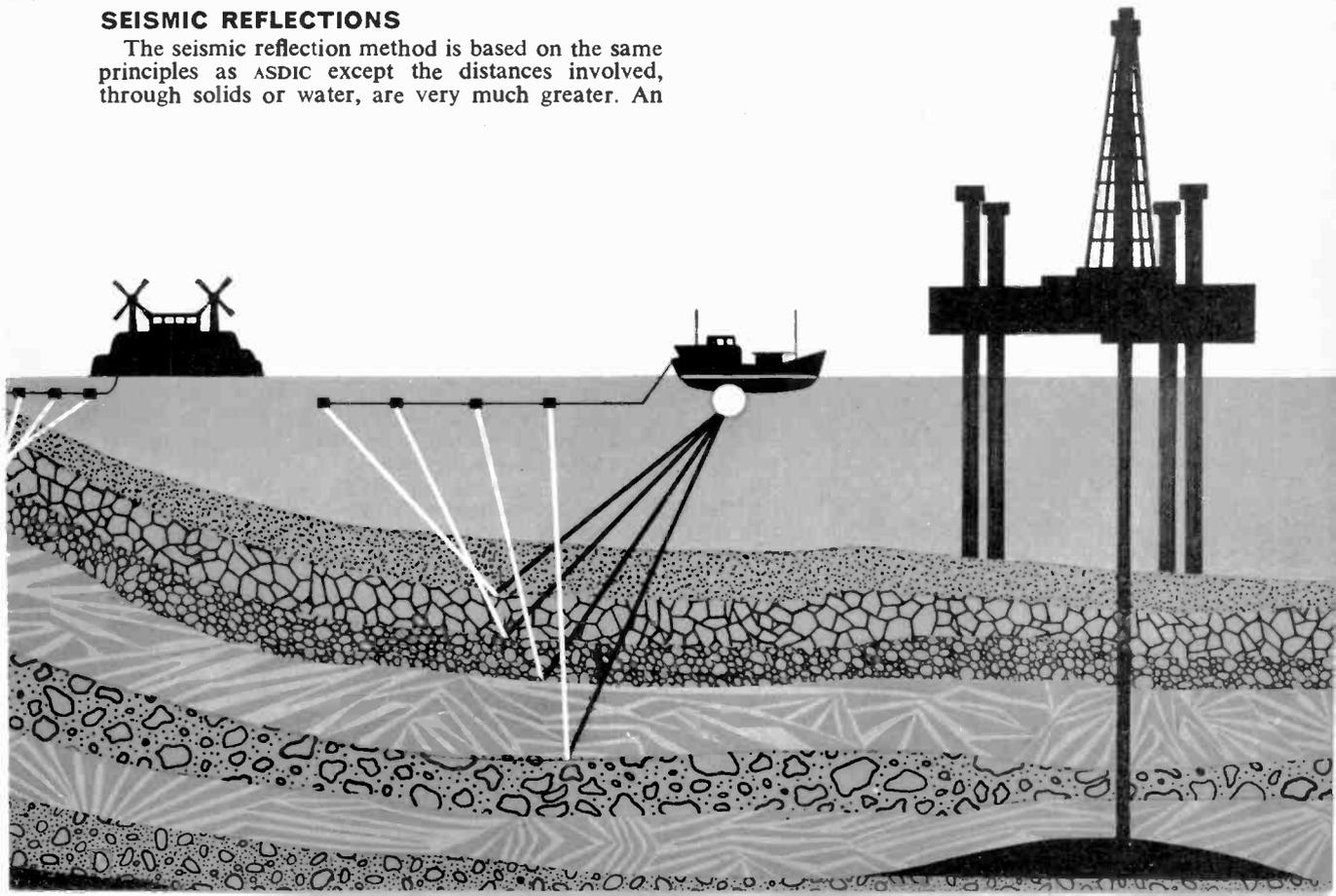The coil of the geophone has a certain amount of inertia and it is the magnet, forming part of the case, that moves up and down around the coil, when the surface of the earth moves, that generates the electrical signal. The output signal from such a geophone can range from over 500mV for a reflection near the surface to less than 0.5µV for a signal coming from a deep horizon.



In practice there is an infinite number of ray paths, from a source, that can give rise to reflections from a given horizon so reflections can be obtained from different points along our sets of horizons if we use geophone receiving stations set apart on the earth's surface. Typically 24 or 48 such stations are used separated by about 200 feet. Thus the horizontal range of a shot might be as great as 1½–2 miles.

NOISE PROBLEMS

Most electronics engineers will appreciate the problems of handling signals as low as half a microvolt at the best of times, but add to this the problem that the signal might have to be carried down 1½ miles of wire back to the recording amplifiers. Hum pick up (from underground and overhead cables) is a problem in populated areas; this is reduced by special hum cancelling bridges at the amplifier input and we ensure our amplifier input and geophone output impedances are low.

Low impedances help (to some extent) prevent induction of signals from static sources—nearby electric storms (very prevalent in tropical jungles) or high voltage caused by moving sand particles (in the desert).

Even that is not all; frequently, while working in foul swampy conditions, simple electrical leakage to ground can sometimes arise unless the cables' insulation qualities are constantly monitored.

Apart from the geophone responding to seismic reflections there is the problem of other noise sources—which can generate signals hundreds of times greater than those required. These can be man made noises—trains, trucks, people walking. They might come from the earth itself—underground rivers, microseisms, tree roots transmitting wind noise into the ground; rain, of course, is an eternal problem! Even animals do not help—a friendly elephant can devastate a seismic recording; it has even been known for a lion to chew a geophone to pieces and an unthinking grasshopper can obliterate a reflection from 3,000 feet by deciding to jump on to the geophone at the wrong moment.

To try to overcome some of these noises there might be in use as many as 60 geophones connected in a coherent series/parallel configuration at each geophone station. Hopefully they will all respond in unison to the desired signal giving an enhancement to its strength and incoherent signals should not reinforce each other!

Fortunately the range of frequencies the earth will propagate is fairly limited—in the range of 10–100Hz so electronic filtering helps remove some of the artifacts. Hum cancelling bridges—as opposed to filters—are obviously essential as 50Hz lies almost at the peak of the seismic spectrum.

AMPLIFYING THE SIGNAL

Typically, there are up to 48 geophone stations connected back to a recording centre which is ideally mounted in the back of a truck, but in the jungle all equipment might have to be portable for man handling in which case the amplifiers and recorders would be set up on the ground. In either instance accumulator power sources are used.

In the early stages of the amplifier the 48 channels are handled independently; they each enter a pre-amplifier with a pre-set gain. At that point the amplitude range considered is from 500mV down to 0.5µV, a dynamic range of 120dB (voltage ratio). The essential features to record are (a) the instant the shot went off and (b) the instances, in time, reflections arrive at the geophone station in question. The first is easily achieved but to log the latter it is necessary to record all acoustic signals in true hi-fi without clipping and distortion.

While it is possible to handle a 120dB dynamic range electronically (provided one has a low system noise) it is impossible to use conventional paper or tape recording to log such a signal unless considerable a.g.c. is used. A conventional a.m. tape recorder has a range of about 40dB while f.m. recording techniques offer up to 52dB normally which can be extended to 58dB by using special noise cancelling techniques.

Normal a.g.c. is unsuitable in this application because, depending on its rate of attack and release, it is bound to distort the wave shape—this would not be too bad if it was possible to record the actual gain of the amplifier (presumably by recording the a.g.c. level) as well as the signal. There would, at least, be a chance of recombining them later if so desired but this would require many recording tracks.

However, if one adopts the philosophy of recording both signal and system gain one must bear in mind that ultimately processing of data by computer can overcome the problem of recording in digital form from the word go.

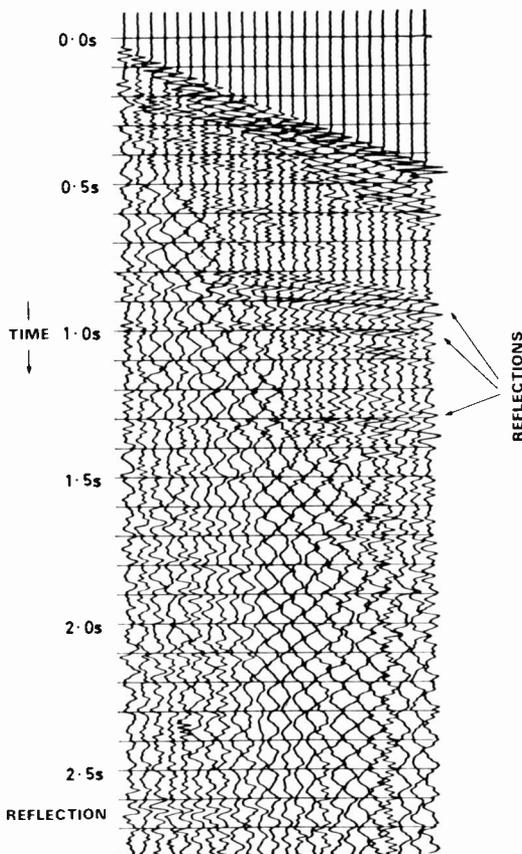


Fig. 2. A 24 trace record. The left hand trace is from a geophone station close to the shot. The right hand one is furthest away

DIGITAL RECORDING

The signal from one of the pre-amplifier channels is fed to a binary gain amplifier. This is an amplifier with electronically switchable gain; there may be 15 selectable gains operating in 6dB (factors of two) steps. The output is electronically monitored and if it appears to be going out of the top of a pre-determined amplitude window the gain is stepped down by 6dB; alternatively if the output falls, the gain is stepped up by 6dB. There being 15 possibilities we end up with a gain range of 90dB but at the same time the gain is precisely defined at every instance and can be described by a 4 bit binary number, for example:

Binary Code	Gain	Voltage Ratio
0000	= 0dB gain	Unity
0001	= +6dB „	X2
0010	= +12dB „	X4
0011	= +18dB „	X8
etc		
1111	= +90dB „	X32,768

The selected binary code defining the gain would be recorded alongside the amplitude. Firstly the residual amplitude has to be converted to digital format for recording. This is done by an A-D converter/multiplexer which samples the amplitude of each of the 48 channels in turn—going right round all of them in either 1 or 2mS—converts them to a 15 bit digital number and then records them on tape in sequential form together with their respective gain codes.

Most field recording systems have a read after write head on the digital recorder which allows instant check of signal quality and system accuracy by converting back to analogue for a compressed playback on paper together with parity checks.

The raw tapes are then sent to a Data Processing Centre where they are de-multiplexed and the data is analysed by computer to assess velocities of propagation, to remove the hyperbolic curvature from adjacent traces for a given shot, to assess the occurrence of multiple reflections by a process of auto correlation of the whole signal against itself, to add coherent signals together to enhance signal to noise ratio and to ascertain the predominant frequencies.

Usually the spectrum shows frequencies predominating at around 50Hz and average velocities of propagation are about 10,000ft per second. This gives a seismic wavelength of about 200 feet; this is the limiting resolution unless high frequency response can be enhanced.

H.F. ENHANCEMENT

Techniques are available which—by judicious use—enhance the higher frequencies by re-injecting signals we predict the earth may have filtered out and at the same time we can apply filtering to any part of the spectrum that will enhance features we wish to see. The final seismic cross section is really a composite of all the geophone signal traces butting against each other, the coherent line up of reflection depicting the structures.

Although no claim is made for identifying materials by the seismic method techniques are under development whereby excessively high or low velocity beds can be identified by analysing their reflection coefficient from the amplitude of signals received.

MARINE SURVEYS

Now that offshore drilling and oil transportation problems have been solved a lot of attention has turned to exploiting potential marine oil reserves; we, in the UK, are only too familiar with the potential wealth beneath the North Sea. As far as the seismic explorer is concerned, he now has extra problems to contend with in marine surveys. To start with he may have to operate in deep or shallow water, in surf and over coral reefs or sand bars. Different vessels have to be used to contend with the various conditions.

Most deep sea surveys are conducted from modified trawlers—capable of towing 1½ miles of buoyant cable. The cable contains pressure sensitive hydrophones at set positions along its length.

The cable has automatic hydrofoils mounted on it at various intervals and when towed along at the operating speed of 6 knots this causes the cable to dive and take up a stable depth of around 35 feet—deep enough to avoid surface and boat noise but not so deep that the piezo electric or variable reluctance hydrophones response is swamped by hydrostatic pressure.

The straightness of the cable is important and this is monitored by receiving radar reflections from a passive reflector towed at the cable's trailing end.

NAVIGATION TECHNIQUES

As on land positional accuracy is most important—it may ultimately be necessary to position a drilling rig within a few feet of the right spot—so specialised navigation techniques have had to be developed. Where possible high resolution hyperbolic positioning is used; the navigator works out where he is with respect to phases of signals radiated from shore based transmitters. Although of limited range the 2MHz signals give exceedingly precise fixes to within a few feet. This technique is not practicable for mid-ocean surveys due to its comparatively short range.

A spin off from space technology is the use of navigational satellites as a technique for getting a fix anywhere in the world. By picking up the signal transmitted by a satellite, measuring its doppler shift and knowing its orbital parameters we are able to obtain a fix on ourselves to within tens of feet. The computations are vast and this is carried out by computer on board ship.

Although accurate these fixes can only be obtained while a satellite is in transit—this might be every 20 minutes or every 2 hours depending on position on the world's surface. Between satellite fixes the position is logged by dead reckoning—this could be done using an inertial platform and monitoring tidal currents and wind velocity or, as is more common, doppler sonar is used to give heading details relative to the sea bed. This assumes that the depth of the sea does not exceed 600 feet—the limit for current doppler sonar equipment.

RELATIVE SHOT FREQUENCY

One big bonus from marine exploration is that once under way a survey can be conducted very quickly and more or less automatically. On a land survey it might only be possible to get 30 shots recorded in a day's work whereas at sea we are able to use fast cycling air guns as a source and operate with a shot every 15 to 20 seconds while progressing at 6 knots.



Strictly

by K. Lenton-Smith

OWNERS and constructors of electronic musical instruments generally fall into two categories—those whose primary interest is in electronics and those who are principally musical. People who combine musical talent with a good knowledge of circuitry are less common, so that most have to tackle one of the aspects of electronic music from scratch.

MUSICAL SIDE

The musical side is perhaps the more difficult as, with good constructional details, anyone with sufficient energy, time and spare cash should be able to construct a successful instrument. Keyboard instruments are in the main polyphonic these days, calling for fluent reading and good basic knowledge of chord formation. Sight-reading three staves simultaneously can be recommended as an excellent way of exercising the brain! Perhaps this is why many constructors never learn to play and the task of building an instrument may well have left them feeling exhausted. But anyone with the determination to build owes it to himself to master playing technique.

TUNING

Directly an instrument is considered finished, a musical friend will be asked round to try it out and offer an opinion. Amplified acoustic instruments are no real problem: guitarists seem to find no particular difficulty in handling six strings, and can make simple tuning adjustments to accord with anything—even a NAAFI piano!

Keyboard instruments are quite another matter, where any tuning inaccuracy is emphasised by sustained chords. Electric pianos and organs usually require twelve precise tunings at least, and a free phase instrument might require a hundred or so. Adjustments usually involve taking the back off the instrument, so that it is imperative that tone sources are stable and that accurate tuning methods are used initially.

STABILITY

Long term stability of frequency generators demands the use of stabilised power supplies as a number of oscillators are sensitive to voltage changes (ignoring, of course, the v.c.o. itself). Because polyphonic instruments are major constructional projects, it is as well to soak test oscillators before going into production. The proposed keying system ought to have the same treatment, as the final result will largely depend on both departments of the instrument.

Whether building to a published plan or from one's own design, exhaustive testing is a wise precaution. For example, testing the tone sources of a recently published design with a digital frequency meter, it was found that a two volt supply deviation resulted in a rise in frequency of half a semitone. Even with a stabilised supply, this circuit would be suspect.

Each semitone is divided into 100 cents for tuning purposes and, since a trained musician will hear errors of less than 10 cents, careful choice of circuitry is essential.

OSCILLATORS

Well designed Hartley or Colpitts oscillators are extremely stable, with supply variations having little if any effect on frequency. Semi-conductors used in these sources hardly affect the result as the tank circuit itself dictates frequency. Open coils should be avoided because of the danger of interaction: using screening cans will help but pot cores are better still in that they have no external magnetic fields. Although these cores are relatively expensive, only twelve will be required for many instruments.

R/C oscillators are more susceptible to changes in ambient temperature and supply voltage, even with sophisticated circuitry and high quality components. Divider stages are normally R/C circuits and, as they faithfully divide by two, their stability depends on the master oscillator.

PITCH STANDARD

The international pitch standard is A-440Hz, and the proposed oscillator could be soak tested against this standard. The BBC propagates this frequency at various times, the most convenient source being the BBC2 test card period. Each morning, the 440Hz signal is transmitted at half hour intervals between music. Tuned with this signal the A oscillator could be checked for any drift by leaving it running until the following day's test signal.

The BBC's standard frequency is an excellent starting point for tuning a completed instrument. A piano may be available, as a tuning reference; if the two are to be played together, all well and good. But, as the piano may not be at standard pitch, there could be problems. A pitch pipe is sold for tuning purposes, but wind pressure varies its pitch—so BBC2 is to be preferred.

BEATING


Sound A above middle C (which should be 440Hz) with the BBC2 pitch standard. In all probability, a distinct beat will be heard—the frequency difference between the two signals.

Tune the oscillator until any trace of beat disappears and, when satisfied the two are precisely in tune, turn off the television. This oscillator is now the standard for the instrument and is in no circumstances altered from this point. The remaining notes in the chromatic scale are tuned in fifths to zero beat and then flattened by a given number of beats per minute. First, play E below with the A just tuned, and adjust for zero beat: now flatten E until 90 beats per minute are counted. The rest of the scale is tuned as follows:—

B above E together, flattened by	67 b.p.m.
F # below B	100
C # below F #	76
G # above C #	57
D # below G #	85
A # above D #	64
F below A #	95
C below F	71
G above C	53
D below G	80

The next interval—A above to D—brings us the full circle and the beats should be 60 per minute. If this is not so, do not alter A but work backwards through the table and sharpen each note slightly until the error is corrected.

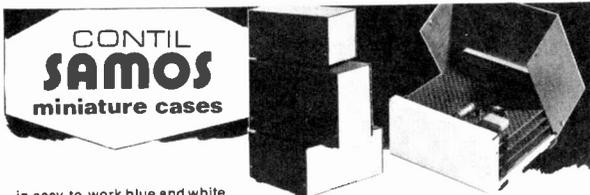With a little patience, this method of tuning should preclude criticism from a musical friend. This solution will only be temporary, however, unless the tone sources are stable in themselves.



CONTIL SAMOS miniature cases

in easy-to-work blue and white PVC/steel. Assemble in the lower half, complete before springing the cover into place — 4 Pozidrivs, two to hinge it, two to fasten it. Carries four P.C. boards horizontally, or two vertically, four required for each case (for 1 vertical board, two each case).

S1	100 × 50 × 50mm	1 off 89p
S2	100 × 100 × 50mm	£1-01
S3	100 × 150 × 50mm	£1-14
S4	125 × 50 × 75mm	£1-26
S5	125 × 100 × 75mm	£1-45
S6	125 × 150 × 75mm	£1-70
S7	125 × 200 × 75mm	£1-90

Much less for quantity. Prices include P & P. VAT, 4 feet and 4 plated screws. Special feet to carry printed circuit boards sold separately. Price, incl. VAT, 26p for 4 P.C. feet. Prices correct 31 May 1974.

CONTIL handles

Prices include VAT. Less for quantity.

(1) No 265 Anodised aluminium centre bar. Black plastic brackets with moulded-in core. 75mm, 97p. 5 more sizes up to 154mm.

(2) No 281 1 Nylon 112mm. Load 50kg, 45p.

(3) No 277 Al., ground, polished, anodised, 88mm, 94p., 120mm, £1-06.

(4) No 268. Satin. all 57.5mm, 94p., 102mm, £1-01, 145.5, £1-17.

(5/6) No 250 Black nylon. Very comfortable. 75mm, 29p., 110mm 41p., 155mm, 67p.

P & P 22p any quantity. Prices correct 31 May 1974.

Brightcase anodised cases

THE WEST HYDE PRESTIGE CASE

The smartest of the West Hyde cases, all anodised aluminium, with top and bottom panels only, in black PVC covered steel (plain or louvered). Free standing or 19in rack mounting with aluminium brackets. Supplied ex-stock, fully assembled with S.S. Pozidrive screws.

Prices include panels feet, P & P and VAT. State whether 1/2 or Full Panels required.

BC21 (3/4in whole rack)	£13-46	88p	74p
BC22 (3/4in half rack)	£10-90	85p	74p
BC31 (5/8in whole rack)	£15-53	£1-24	74p
BC32 (5/8in half rack)	£12-78	£1-24	74p

Prices correct 31 May 1974. Pr. brackets. Extra for louvers.

minos PLASTIC CASES

A smart miniature case in tough, rigid, high-gloss black ABS. Front panels in either aluminium or white PVC/Steel. Built-in slots for PC cards, dividers, or screens. Chassis or PC boards can be supported on "P" clips for internal pillars. Excellent as encapsulation boxes.

M2	65mm × 100mm × 50mm	2 1/2" × 3 3/4" × 2"	1 off 51p	10 off 45p
M3	100mm × 130mm × 50mm	3 3/4" × 5" × 2"	87p	58p

Prices include P. & P. and VAT. Less for quantities. Also available less panel and screws. Minimum order £1. Prices correct to 31 May 1974.

CONTIL MOD-2

The design of these cases permits the instrument to be built or serviced within their external panels 48 shapes. Low cost Blue PVC/steel with white PVC coated aluminium panels.

	Width	Height	Depth	1 off	Width	Height	Depth	1 off
	in	in	in	£	in	in	in	£
A	4.5	3	6.5	3-80 M	4.5	3	13	4-44
B	4.5	7	6.5	4-44 N	4.5	7	13	5-44
C	4.5	10	6.5	4-81 O	4.5	10	13	6-81
D	9	3	6.5	4-81 P	9	3	13	5-44
E	9	7	6.5	5-44 O	9	7	13	6-81
F	9	10	6.5	6-28 R	9	10	13	8-41
G	13	3	6.5	6-44 S	13	3	13	6-81
H	13	7	6.5	6-28 T	13	7	13	8-41
I	13	10	6.5	6-81 U	13	10	13	10-20
J	18	3	6.5	6-28 V	18	3	13	8-41
K	18	7	6.5	6-21 W	18	7	13	10-20
L	18	10	6.5	10-20 X	18	10	13	12-21


Woodgrain D, E, 44, E and G, E, 28, H, E, 81. Prices include screws rubber feet, one or two Cheese according to size and P & P and VAT.

Prices correct to 31 May

WEST HYDE

WEST HYDE DEVELOPMENTS LTD., Ryefield Cres., Northwood Hills, Northwood, Middx HA6 1NN
Tel. Northwood 24941/26732 Write or phone for new free catalogue Telex: 923231

Out now! Free

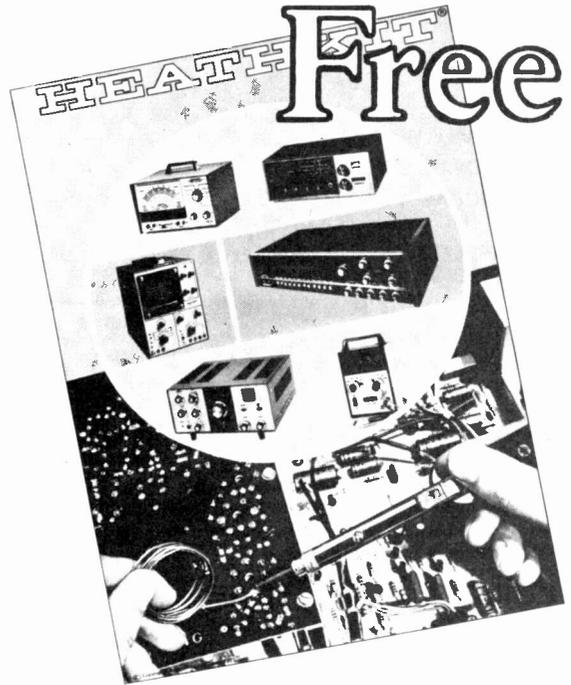

HEATHKIT offer you this colourful guide to electronic kits—FREE!

All our kits are designed to be built by you, whether beginner or professional. Even soldering experience is unnecessary as every kit contains a construction manual to lead you step by step through the assembly, testing and operation of your Heathkit.

Our extensive range includes Metal Detectors, Black and White TV, Intercoms, Burglar Alarm, Automotive, Amateur and Shortwave equipment, Portable Radios, Instruments and a complete range of Stereo Hi-Fi. All available on extended credit terms with our Monthly Budget Plan.

Post the coupon now for your free copy of the Heathkit Catalogue.

SHOWROOMS:

London: 233 Tottenham Court Road
Gloucester: Cole Ave. Roundabout, Bristol Rd
(Open office hours and Saturday mornings)

Free Please send me a FREE Heathkit Catalogue and details of your Monthly Budget Plans

NAME _____

ADDRESS _____

"SHARP 12"

THE ARISTOCRAT OF PORTABLE TELEVISIONS

- ★ FROM THE INTERNATIONALLY FAMOUS SHARP AUDIO & ELECTRONICS CORPORATION
- ★ INSTANTLY TUNABLE IN ALL U.K. AREAS
- ★ MAINS OR 12V BATTERY
- ★ ALL SOLID STATE CIRCUITRY FOR RELIABILITY AND INSTANT WARM-UP
- ★ REMOVABLE SUN SHIELD
- ★ IMPECCABLY STYLED CASE IN OFF-WHITE HIGH IMPACT ACRYLIC WITH FOLDAWAY HANDLE
- ★ COMPLETE WITH MAINS LEAD, PERSONAL EAR PHONE AND UHF AERIAL
- ★ GUARANTEED FOR 1 YEAR
- ★ RECOMMENDED RETAIL PRICE £75.95 (Exclusive of V.A.T.)

OUR PRICE
£44



NEW

**BASF
CASSETTE
RECORDER**

- ★ THE LATEST HIGH QUALITY PRODUCT FROM THE RENOWNED GERMAN BASF COMPANY
- ★ STYLISH, COMPACT MAINS OR BATTERY OPERATION
- ★ SUPERB TONE AND PROVISION FOR EXTERNAL LOUDSPEAKER
- ★ BUILT-IN HIGH SENSITIVITY CONDENSER MICROPHONE AND PROVISION FOR EXTERNAL MICROPHONE
- ★ PIANO KEY CONTROLS, RECORD METER AND AUTOMATIC RECORD LEVEL CONTROL
- ★ SUPPLIED WITH CARRYING CASE, MAINS LEAD AND 3 PIN DIN-DIN LEAD
- ★ RECOMMENDED RETAIL PRICE £36.35 (Exclusive of V.A.T.)

OUR PRICE
£30

BASF CASSETTES (TYPE LH IN SNAP-PACK)

	C30	C60	C90	C120
PRICE EACH:	47p	55p	76p	£1.13

PHIER 1/4 & 1/2 WATT CARBON FILM RESISTORS

E12 1/4 watt 10Ω — 1M
1/2 watt 10Ω — 10M

- ★ MINIMUM ORDER 100 RESISTORS
- ★ MINIMUM PER VALVE 25

75p/100

IF EXACT VALVE IS OUT OF STOCK THEN NEAREST WILL BE SUPPLIED

TERMS (TRADE AND BULK ENQUIRIES WELCOME)

- ★ PRICES DO NOT INCLUDE V.A.T.
- ★ PAYMENT WITH ORDER ONLY
- ★ TOTAL PAYMENT = COST OF GOODS + P/P + 10% V.A.T.


POSTAGE AND PACKING
TELEVISION—£1
CASSETTE RECORDER—75p
CASSETTES/RESISTORS—25p

MOTEC

P.O. BOX 14 · ABINGDON · OXON

PE POWER SLAVES

BY R. B. REESON

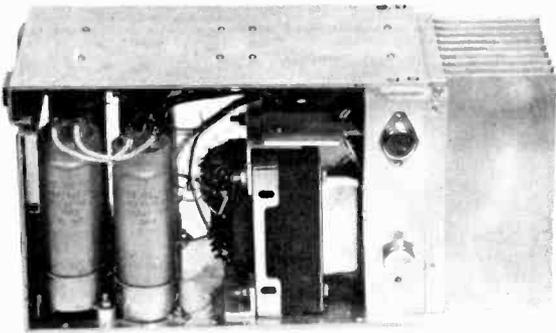

JUST as a basic circuit configuration is given for the family of Power Slaves, similarly we can use a basic constructional method based on the 100 + 100W prototype amplifier. This means that although the printed circuit board layouts and component placements will be common to all four amplifiers, a scaling down of the chassis piece part figures given should be made for the relevant lower powered amplifiers since lower rated components such as transformers and large electrolytics will correspondingly occupy less space.

100 + 100W CHASSIS

The method of construction of the 100W chassis is fairly straight forward and comprises only four basic parts plus two side panels.

The heatsink forms the entire rear face of the chassis box and also serves to stiffen the final assembly. Base plate and sub-chassis are constructed ideally from 12 or 14 s.w.g. aluminium for rigidity, although 16 s.w.g. would be easier to work for those without access to sheet metal folding equipment. The side panels may be of lighter material such as 18 s.w.g. plastic coated aluminium, sold commercially as "Bondene" and "Lamiplate."

Fig. 3 shows the main chassis parts with drilling details but it should be emphasised that the base plate and top cover may have to be extended to accommodate differing makes of large capacitor or transformer. These items should be purchased first before chassis dimensions are fixed.

The base plate is attached to the heatsink by means of five 4×10 mm bolts. Similarly the sub-chassis is attached to both the base plate and heatsink, a smear of thermal jointing compound being used at all three joints, so that a large composite heatsink is formed.

Due to the wide range of transformers which may be used in this design, no details are given for the cut-out in the vertical face of the sub-chassis. Thus this cut-out, and the transformer mounting holes, must be positioned to suit the particular transformer to be used.

The top cover carries the amplifier printed circuit boards, and hinges up for ease of servicing. To avoid lengthy wire-runs which might give rise to instability and hum pick-up, the input and output sockets are carried on the front face of this panel.

The heatsink used is supplied with a tongue along one side and a slot on the other, such that larger assemblies may be built up by stacking them side by side. The tongue must be carefully filed off, taking care not to score the surface which will carry the power transistors. For the sake of neatness, a strip of 10 s.w.g. aluminium $3\frac{1}{2}$ mm wide can then be Araldited into the slot on the opposite side and filed down flush.

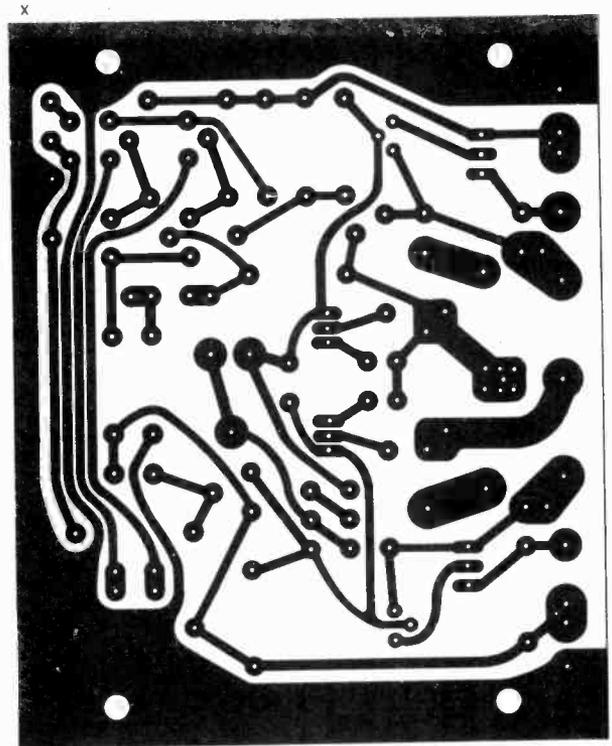


Fig. 1. Printed circuit master for amplifier boards

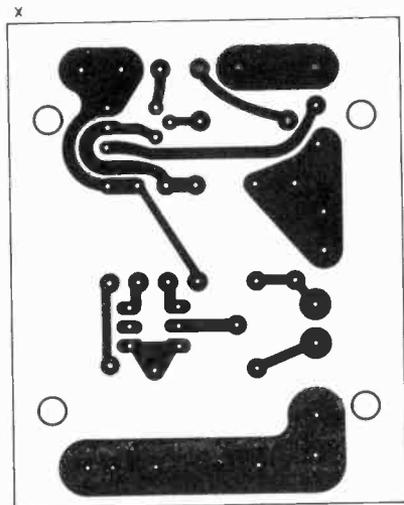


Fig. 2. Printed circuit master for p.s.u. stabiliser

CHASSIS CONSTRUCTION AND COMPONENTS

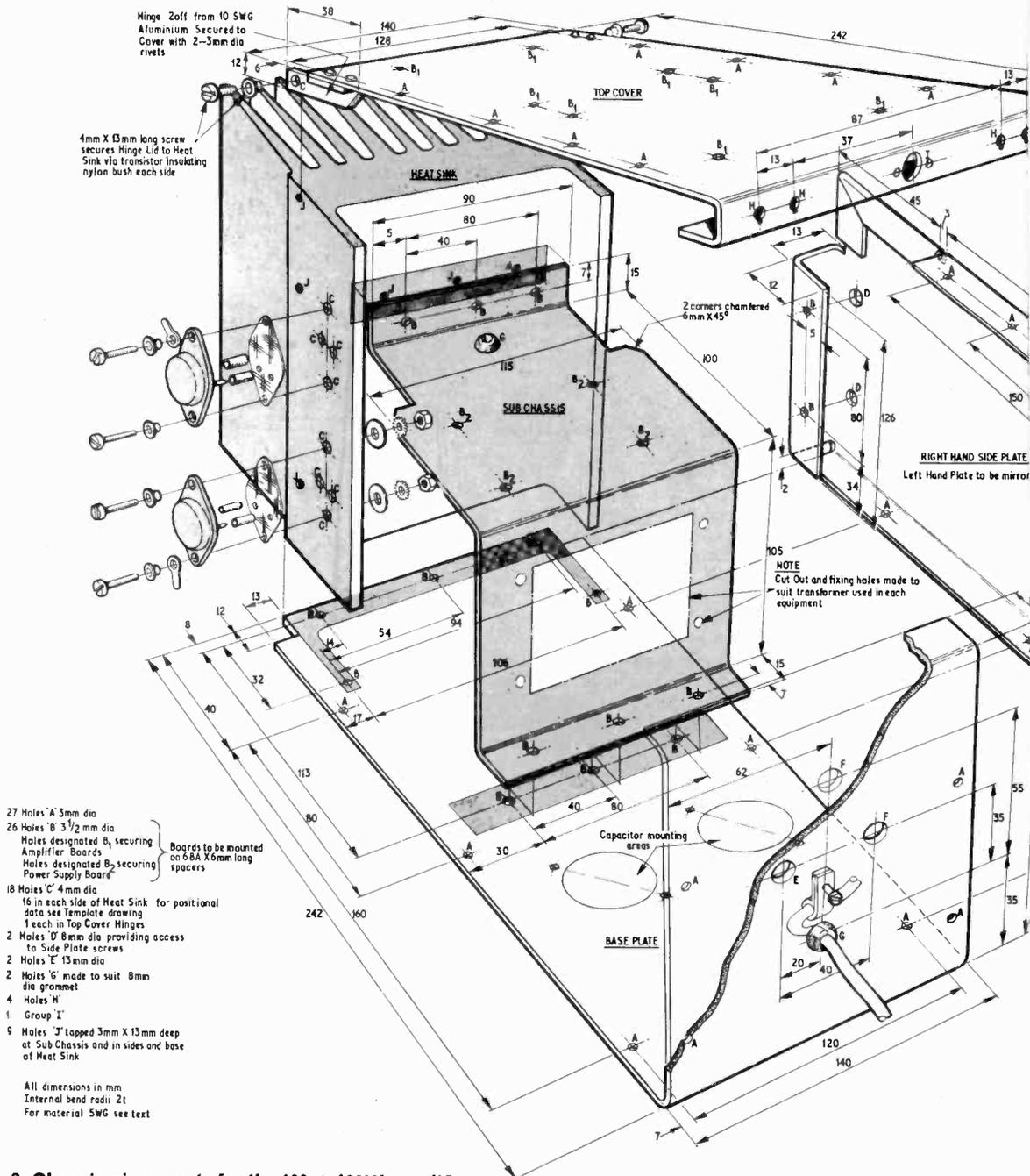


Fig. 3. Chassis piece parts for the 100 + 100W amplifier. For the lower power versions the dimensions should be sensibly scaled down

IT BOARDS

**PE
POWER
SLAVES**

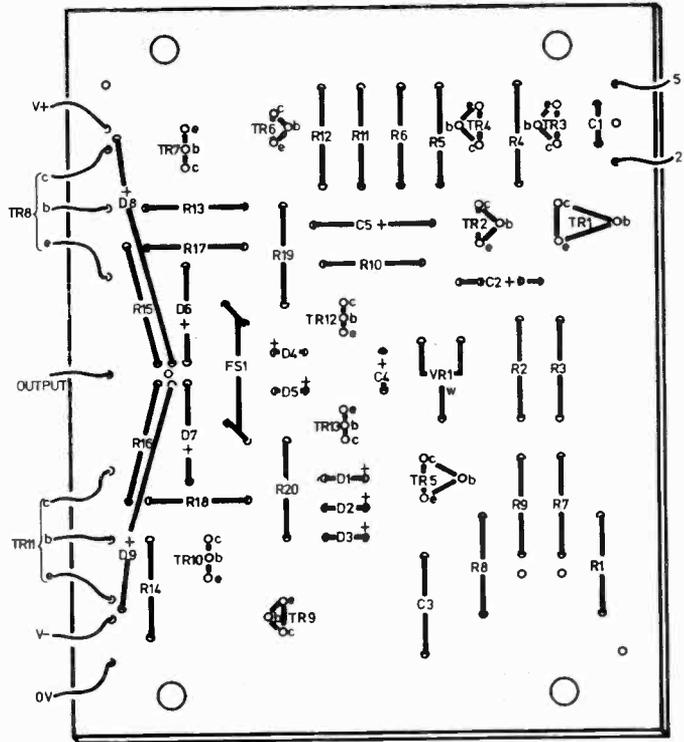
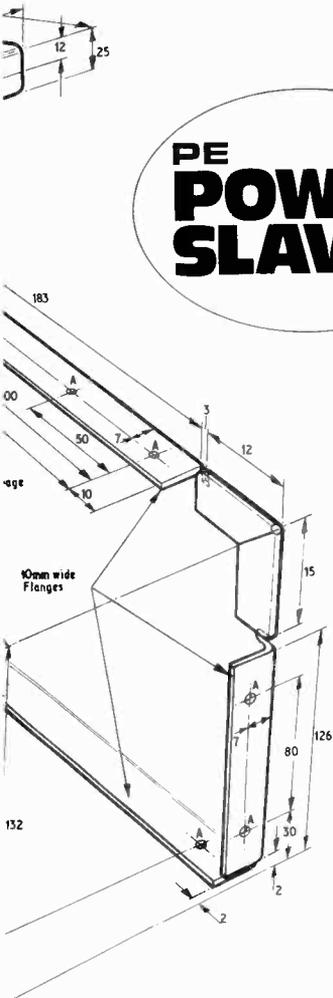


Fig. 4. Component layout for amplifier p.c.b.s

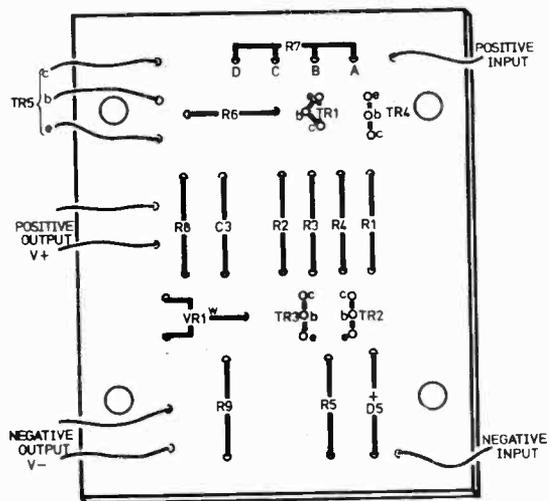


Fig. 5. Component layout for stabiliser board

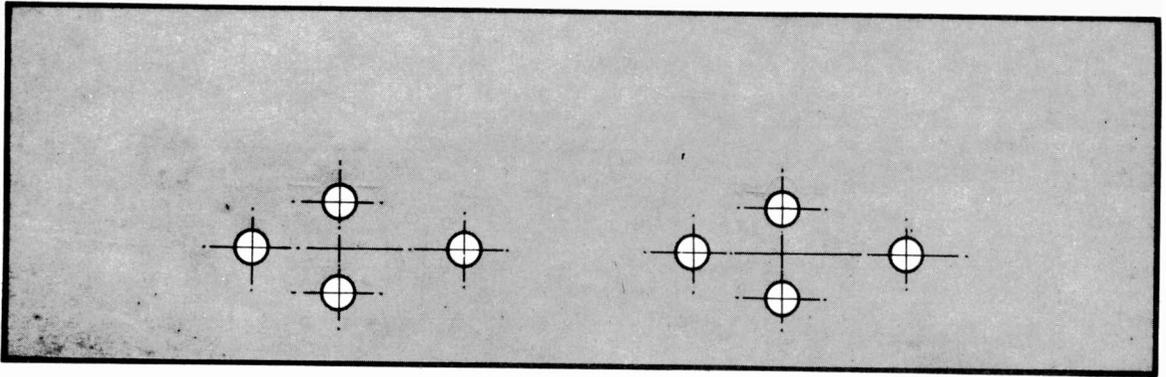


Fig. 6. Drilling template detail for power transistors

HOLE DRILLING

All holes in the heatsink, tapped 4mm, should be drilled No. 30 ($\frac{1}{16}$ in) to a depth of 12mm and tapped. Any constructors not familiar with the difficulties of tapping holes in aluminium would be wise to use self-tapping screws of a similar diameter, as a broken tap in a blind hole is difficult to remove to say the very least.

The only exceptions are the holes which take the bolts forming the hinge pieces for the top cover. These should be tapped 3mm to a depth of 10mm and the top cover mounted with the aid of two bolts onto which TO3 insulating washers have been placed to provide a nylon "bearing".

The mounting holes for the power transistors are best marked out on a template, made of scrap steel or aluminium as in Fig. 6. This template can then be drilled and checked against a TO3 case transistor before it is clamped to the side of the heat sink and drilled through. The same template can then be used for the other side.

AMPLIFIER BOARD ASSEMBLY

The majority of main amplifier components are carried on a printed circuit board. Two of these are required and can be etched using the master of Fig. 1. An overlay for component positioning is provided in Fig. 4. The X at the corner of each figure should coincide for correct orientation.

When assembling semiconductors particular care should be taken that leads are correctly positioned as many versions of BC182, 184, 212 and 214 transistors are produced.

Components should be mounted flush to the p.c.b. with the exception of the transistors which should be spaced off 5 to 10mm.

Resistors R17 and R18 consist of appropriate lengths of 26 s.w.g. Constantan wire soldered directly to the circuit board. Cutting lengths and the approximate height it should clear the p.c.b. for differing powers are given below:

Power	Resistance	Length	Height
20W	0.11 Ω	37mm	11mm
40W	0.08 Ω	27mm	6mm
65W	0.07 Ω	24mm	4.5mm
100W	0.06 Ω	21mm	3mm

ADDITIONAL DIODES


The addition of the two diodes mentioned at the end of last month's article now changes the Com-

ponents List for all versions of main amplifier as follows:—

- D1—D5 1N914
- D6—D7 1N5401
- D8—D9 BA148

OUTPUT FUSE

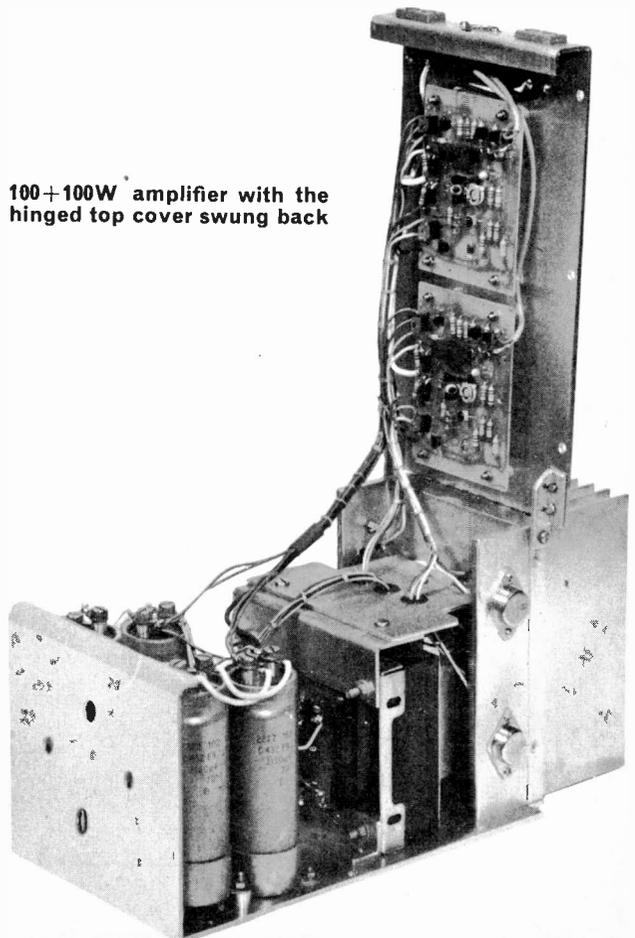The purpose of the output fuse FS1 is to give protection against short circuit loads and gross overloads, as opposed to the overloads of a few dB likely



100+100W amplifier with the hinged top cover swung back

to be met when working at full power. Thus the fuse should limit operation to the safe operating area of the output transistors, and should blow at peak current in less than two seconds. A value of 1A is generally suitable, but values above 2A are not recommended. This fuse should, of course, be of the normal, quick-acting type.

Where a very low output impedance is essential, FS1 may be replaced by a wire link, but greater care will be needed in use. Full protection can be restored by fusing the two power rails to each channel separately, hence a stereo amplifier would require a further four fuses. These could be mounted on either side of the front panel.

A small heatsink may be fitted to TR7 and TR10 if sustained high power operation is anticipated, as, for example, in some musical instrument applications. This may be of 18 s.w.g. aluminium approximately 15mm by 25mm fixed to the tab of each transistor by means of a 3mm or 6B.A. bolt. Care should be taken that this does not contact any other parts of the amplifier, as the heat sink tab is not isolated.

POWER SUPPLY

The prototype 100W amplifier has a "monitoring" type of supply. If stereo use is intended there is ample room for mounting a p.c.b., including the stabiliser electronics. An etching diagram and component layout for this are shown in Figs. 2 and 5. Like the amplifier board these are full size.

R7 is made up from 26 s.w.g. Constantan wire, the tapping values of which were given last month. Links to points B and C should be made with 22 s.w.g. copper wire wrapped around a couple of times.

As Constantan does not solder easily, the wire should be scraped where connections are intended.


With the power supply components assembled, initial wiring can be carried out between mains input connector, mains switch and fuse and transformer. When the mains wiring is complete, the capacitors may be fixed in place and the connections from them to bridge and transformer secondary made. At this point mains should be connected, and positive and negative rails measured.

The amplifier power transistors, and that for the stabilised p.s.u., if used, should next be mounted, using thermal jointing compound on both sides of the mica insulators. Silicone grease should not be used here, as it has only a fraction of the thermal conductivity of proprietary compounds, and so allows a substantial temperature difference to develop between the device and its heat sink.

The p.s.u. circuit board is mounted in place on the horizontal section of the sub-chassis by means of 3mm bolts and short spacers or nuts. Wiring to this board is straightforward, but leads should be kept fairly short and should be of 24/0.2mm copper wire or similar, as should all the wiring so far detailed. Resistors R10 and R11 are mounted on the tags of C4 and C5, and at this time, no part of the power supply circuit should be earthed, except for the electrostatic screen in the transformer.

P.S.U. CHECK-OUT

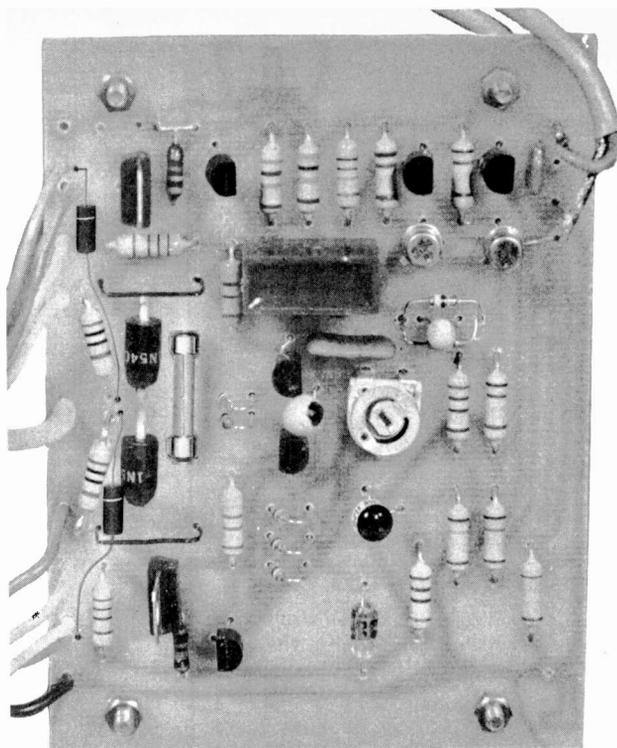The power supply should now be connected to the mains and turned on, with VR1 set fully anti-clockwise. VR1 may now be adjusted to give twice the nominal rail voltage between V+ and V-.



100+100W amplifier main board assembly

Bear in mind that the output capacitors on the power supply can have time constants as long as 30 seconds, so that adjustment must proceed slowly in stages.

When rail voltage has been set, the voltage drop across TR5 should be approximately 10 to 12 volts, and the voltages across C4 and C5 should be equal and within 5 per cent of nominal.

SETTING UP

The only amplifier setting up required is the adjustment of VR1 to give the desired quiescent current in the current amplifier. In general this figure should lie between 10 and 50mA. For high fidelity 30 to 40mA is recommended.


It is a wise precaution, before first turning on power, to wire a 240V 60W bulb in series with positive and negative supply leads to limit current in the event of a wiring fault. If all appears well, with the output at zero volts, and VR1 adjusted, a signal may be applied before the bulbs are removed. When connection is made directly to the positive and negative rails, a slight adjustment of VR1 will be necessary.

SERVO APPLICATION

If C2 is replaced by a shorting link, the amplifier may be used for servo applications, the input being taken directly to the base of TR1, bypassing C1. Here the gain of the amplifier may be adjusted by R2. Alternatively R10, R2 and C2 may be omitted and the base of TR2 fed from a servo potentiometer.

In this application the common-mode input voltage should be kept within $\pm 5V$ of the 0V line and a resistor of 200k Ω should be included in the feedback line to the base of TR2 to maintain a low offset voltage.

★

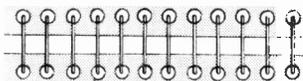

INDUSTRY NOTEBOOK

By Nexus

END OF THE IEA?

The last ever IEA (Instruments, Electronics, Automation) show to be held at Olympia, London, opened with a whimper and finished, literally, with a bang. I exaggerate slightly because there was another day to go when one of the exhibits on demonstration exploded with a sharp crack. A pure accident (no casualties) although a few people of the meaner sort imagined it was just another of Tom Jermyn's publicity stunts. In fact it wasn't. There was no need. Jermyn Industries stand had already set a standard for elegance and comfort combined with utility which was hardly improved by a gaping hole in the roof!

As far as business was concerned the first day of the show was a disaster with very few visitors. But attendance swelled during subsequent days and by the close there were plenty of smiling exhibitors.

It's quite amazing how quickly things become "old hat". For example any company with the slightest connection with space technology used to have pictures or models of lunar modules, space rockets blasting off, communications satellites or, nearer to earth, Concorde. All these image-building themes have now been relegated to the dustbin as if they had never existed. Today's in-thing is off-shore oil rigs and all the go-ahead publicity managers saw to it that their own companies were well identified with oil exploration and exploitation. Well, that's where the money is today, and money is what business is about.

Talking point of the show was how it will make out in 1976 when it is moved to the new National Exhibition Centre at Birmingham. Clearly a brand new exhibition site matching the best that Europe

can offer in comfort and convenience must be better than dreary old Olympia, but at the risk of offending readers in the Midlands I have to record that Birmingham hasn't quite the glitter of London. Few British exhibitors are attracted by the prospect of Birmingham so how will the foreigners feel? Will attendance by both exhibitors and customers be so low that IEA will die a natural death?

My own guess is that come hell or high water the Birmingham show will go on in 1976 if only because the following show, in 1978, will be the first of a three-year cycle together with Interkama (Germany) and Mesucora (France), each country having a major truly international show only once every three years. So in 1978, there will be nowhere else to go. It's Birmingham or nothing, and that could breathe new life into the show. But there is no law forcing people to Birmingham and if exhibitors and customers alike stay away then it really is curtains for Britain as a top electronics show case.

TV SLUMP

The January-April returns from the British Radio Equipment Manufacturers' Association confirmed the expected slump in TV deliveries compared with the 1973 boom. Domestically produced colour sets dropped to 600,000, ten per cent down on the corresponding period last year. Monochromes dropped to 208,000, a savage 44 per cent reduction.

This is bad news for component manufacturers but not disastrous. LCR Components, for example, is heavily geared to supplying tens of millions of polystyrene capacitors to the TV manufacturers. Kurt Balz, managing director of LCR's six factories, tells me he is still going ahead with plans to double output, the surplus being all for export. Last year LCR found itself turning down large export orders because of home demand.

OUR IMAGE OVERSEAS

At least LCR Components told overseas buyers they couldn't deliver. The damage comes when Britain takes the orders and falls behind on delivery, an unforgivable sin for which, in foreign eyes, there is no excuse—not even shortage of raw materials, strikes or three-day weeks.

Our sins in this respect were highlighted by Sammy Zilkha, the master mind behind Alphameric Keyboards and his sales director, Jim Denton, when they returned from a coast-to-coast sales trip in the United States and Canada. Overseas buyers, they say, have become evermore sceptical of

delivery promises or that our prices will be held within reasonable levels on repeat orders, always a consideration when trying to get a major sub-assembly such as a solid-state keyboard designed into a new piece of equipment.

It isn't only on account of delivery and price-stability that our overseas image is suffering. Who wants to trade with a country whose government and trade unions jointly operate a selective policy of supply based on an emotional attitude to the customer country's internal politics?

Hats off, then, to Marconi on the delivery front for supplying their latest Mark VIII colour TV camera in eight days to meet an emergency requirement from French independent TV Company COFCI for coverage of the Presidential election. And let us give all support to the Radio and Electronic Component Manufacturers' Federation proposal to mount a publicity campaign to counter what is described as "derogatory and misleading reports which have appeared in overseas journals".

JAPS LOSE OUT

In the 20 years from 1950 to 1970 the Japanese growth in electronics has been truly phenomenal. In 1950, production was 40 million dollars (about £16 million). By 1970 it had risen to 8,800 million dollars. Japan's export performance over the same period has been even more remarkable, rising from 3 million dollars in 1950 to 2,275 million dollars in 1970. These figures were quoted by Mullard managing director Jack Akerman at a recent London conference.

The golden days seem to be over. Labour costs now are more than 30 per cent up on last year, petrochemical products are 40 per cent, other raw materials are up 20 per cent. On top of all this there is growing resistance in many countries to Japanese imports in favour of protecting their own industries. In fact overall costs are now so high at home that major Japanese companies are establishing manufacturing units in high labour cost areas like France and the United States as well as Britain.

Forecasts are that cut-backs in consumer electronics production will be more than matched by increases in industrial electronics to give an overall result about the same as last year or perhaps a very small growth. But quite clearly the days of fantastic expansion are over and what hits the Japanese even harder is that to keep a competitive pricing policy, profits may be eroded by as much as 25 per cent.


NEXT MONTH...

The PE CCTV Camera

- ★ HOME ENTERTAINMENT
- ★ EDUCATION VISUAL AID
- ★ LECTURING
- ★ REMOTE MONITORING
- ★ SURVEILLANCE

A private monochrome television service can be yours when you construct our closed circuit television camera. It can be connected to a remote TV monitor via a single coaxial link or to a standard domestic TV receiver via the aerial socket. It is compatible with 625 line TV standards and provides quality pictures comparable with those provided by much more expensive cameras.

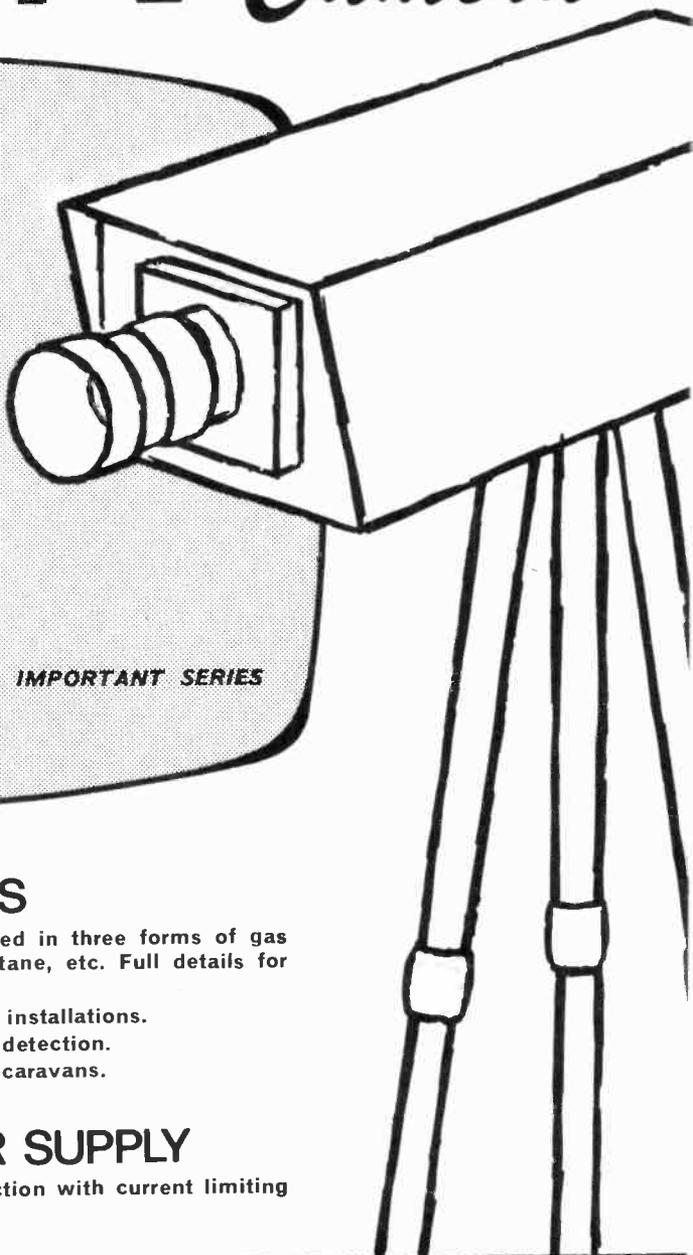DON'T MISS THE OPENING PART OF THIS IMPORTANT SERIES



VERSATILE GAS DETECTORS

The latest solid state gas/vapour sensor incorporated in three forms of gas detector. Monitors presence of North Sea Gas, Butane, etc. Full details for building the following equipments:

- (1) Mains operated unit for domestic and industrial installations.
- (2) Battery powered hand-held instrument for leak detection.
- (3) 12V or 24V version for installation in boats and caravans.

STABILISED BENCH POWER SUPPLY

Bench power supply providing digital voltage selection with current limiting protection


PRACTICAL ELECTRONICS

SEPTEMBER ISSUE ON SALE AUGUST 9, 1974

PERORDO

F.M. STEREO TUNER

BY R.A. COLE

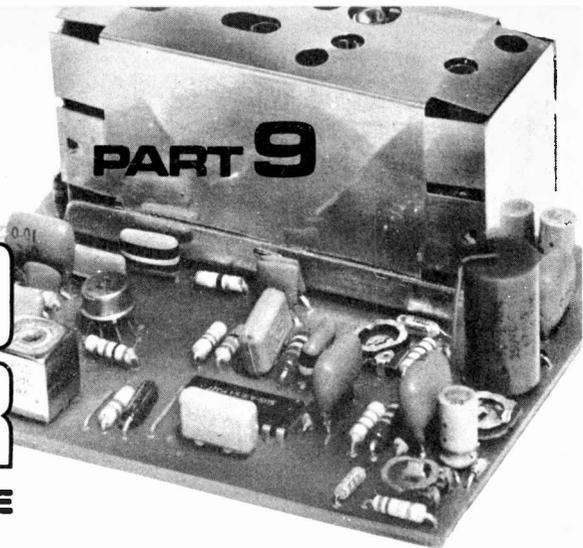

AS DESCRIBED in the last part of the Rondo series, dealing with the stereo decoder and the initiation of the f.m. tuner, the tuner and decoder circuits are mounted on separate boards. Apart from providing smaller boards which can be more easily located in what is now clearly becoming a fairly crowded assembly, this does allow for flexibility of system since some constructors may desire to use their own particular tuner or decoder.

In the Rondo f.m. tuner the Larsholt head used, together with associated circuitry, give a performance which will match most other equipments and in fact even using only a rudimentary simple dipole aerial it has proved possible in North London to pull in a number of Continental stations at good signal strengths apart from all the normal U.K. broadcasts which of course come in with ample strength.

Before describing the tuner board it should be mentioned in the above context that success or failure with stereo f.m. can, in many geographical locations, be dictated by the sensible use of a good aerial system so it is as well to bear this in mind before starting construction.

F.M. TUNER BOARD

The printed circuit master negative is shown in Fig. 9.1, and the component layout in Fig. 9.2. The negative is full scale and illustrates the compactness of design which can be adopted with the Larsholt head even though the latter is a discrete component unit.

Preparation of the board follows normal p.c.b. methods though when drilling the i.c. holes do not forget that it is best to use holders here rather than mount direct on the board.

The p.c.b. is mounted in the bottom of the Rondo trough chassis in the space in front of the power supply section. It is held away from the trough bottom by stand-offs and 4 or 6 B.A. screws. Wiring to the board is loomed where necessary and, of course, signal leads are screened.

Care should be taken when locating the board to ensure that there is no risk of shorting of track or conductors on any other part of the circuitry, switches and so on when the fascia is finally re-assembled. The packing density of the Rondo system can create this danger in some circumstances.

TUNING DIAL

Assembly of the tuning dial on the left-hand side of the fascia is straightforward and follows normal

procedure. The various parts, pulley wheels, large drive pulley, cord and pointer are available from a number of suppliers. Fig. 9.3 shows an exploded view of the arrangement used in the prototype.

The mechanical arrangement is self-explanatory, follows normal convention, and can be modified to suit individual requirements as they arise. Wherever possible fairly simple methods of construction have been used. Thus the tuning scale (of which more later) and tuning meter, are both held in position in the prototype using double-sided adhesive tape.

This is possible since both are light in weight and the system would not normally in any case be subject to great stresses and strains. Of course the reader is free to use any method of construction he feels is warranted but the present state-of-the-art adhesives are far stronger than is generally known.

In the Rondo, use has been made of the very latest in fascia illumination. In fact it is believed that the luminescent panel tuning scale used here, which is based on electroluminescence for its operation, is the first domestic environment application of this particular phenomena.

Fig. 9.4 is a diagrammatic section through the tuning scale which shows up the active parts of the panel. In basis the device is a capacitor with a phosphor material positioned between the electrodes. When electrical energy, in the present case 240V a.c. mains, is applied to the plates of the "capacitor" the phosphor material glows. Dependent on the frequency and voltage density applied the glow is brighter or dimmer.

As can be seen, a heavy glass sheet forms the main support member at the rear. On to this a copper electrode is evaporated to form one plate of the capacitor. A high dielectric material in a resin base is applied to the copper and the phosphor material is applied to this. The phosphor is itself carried in a resin base.

Finally, a transparent copper electrode, only a matter of microns thick, applied to a top glass sheet, forms a layer between the upper sheet and the phosphor layer.

Power to operate the device is applied to the two copper layers and consumption is in the region of 1mA per square inch.

The front glass sheet can now be suitably printed with any scale, figures or other information as required. In the present case a scale was prepared and silk-screened on in heavy black so that the scale and calibration numerals show up as illuminated figures.

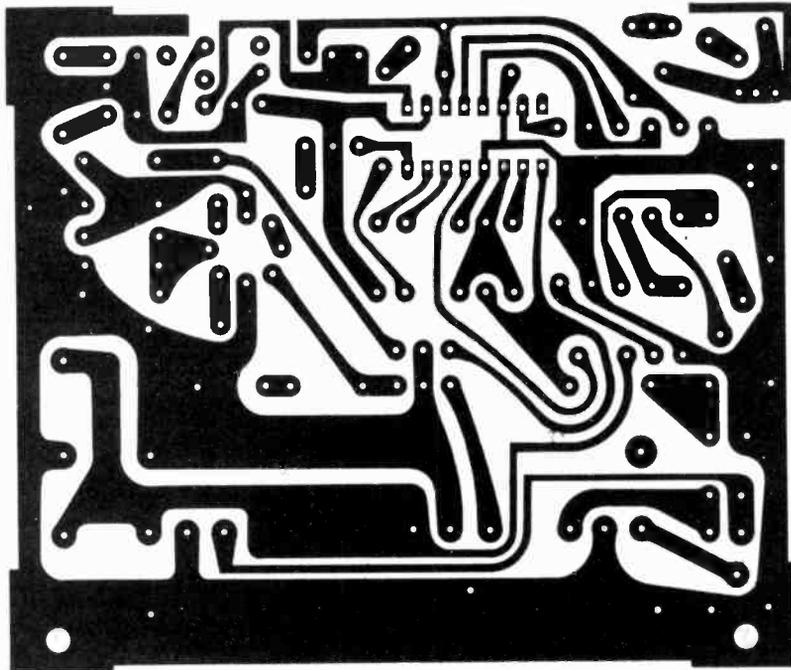


Fig. 9.1. Printed circuit master for the f.m. tuner using the Larsholt head

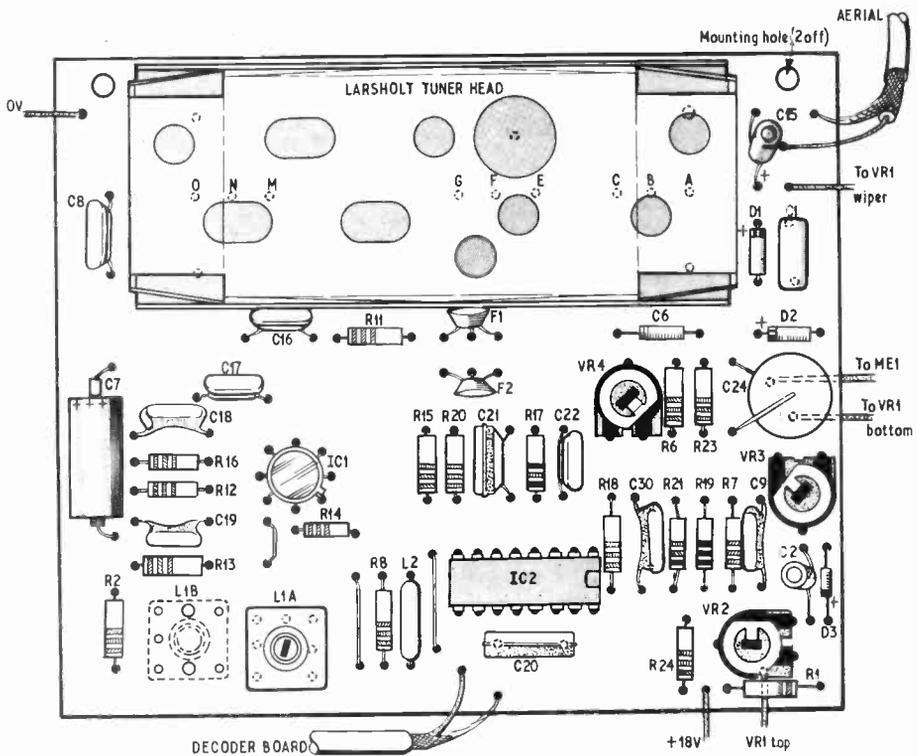


Fig. 9.2. Component layout for the tuner board. The L1B option is discussed in Part 8

PE BORDO

TUNER FASCIA


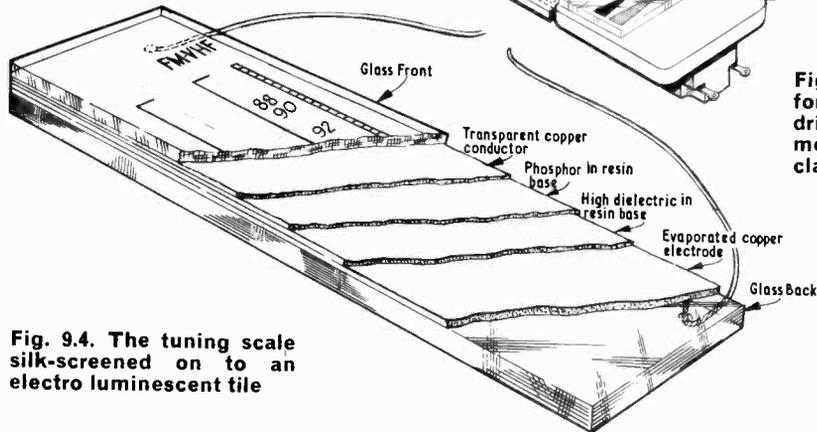
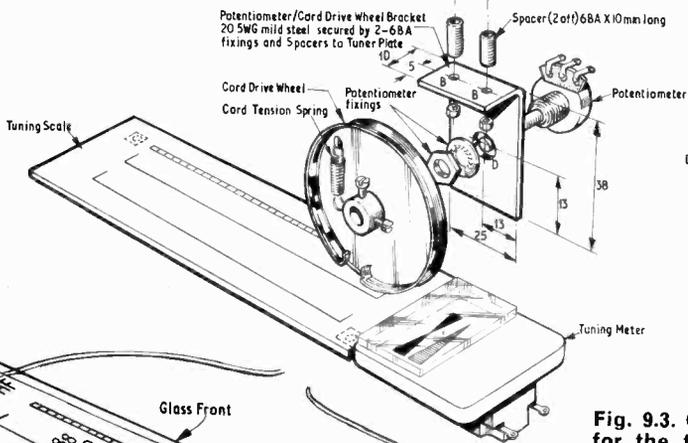
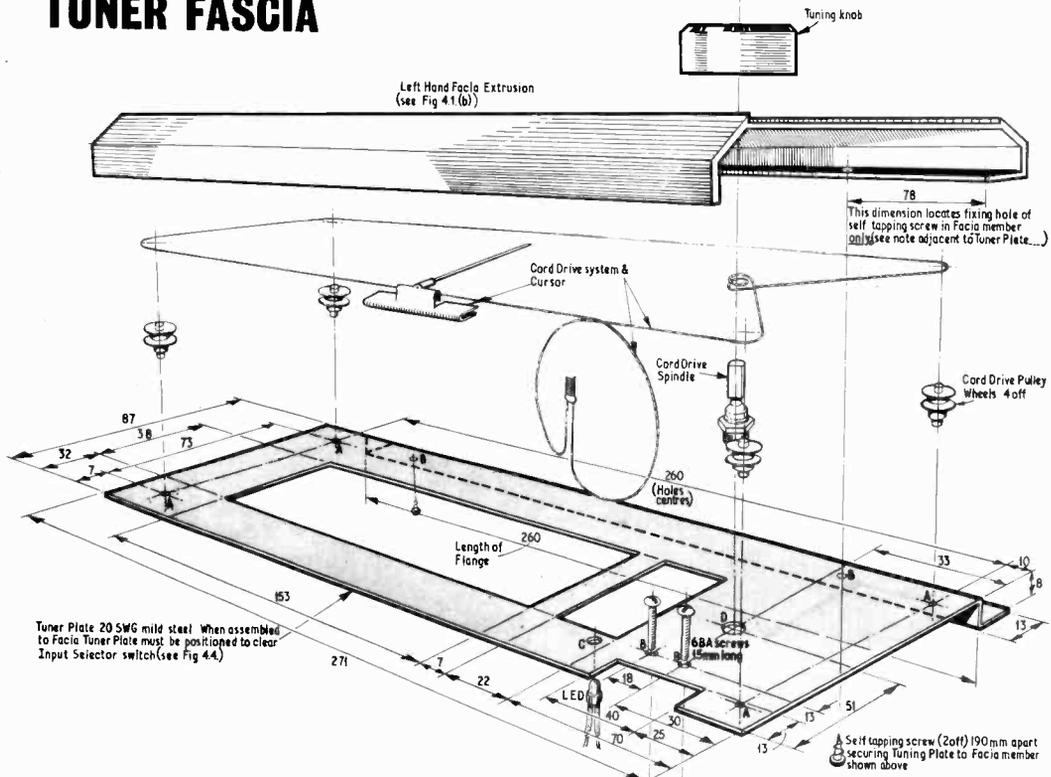


Fig. 9.4. The tuning scale silk-screened on to an electro luminescent tile

Fig. 9.3. General assembly for the tuner fascia, VR1 drive, scale and tuning meter shown exploded for clarity

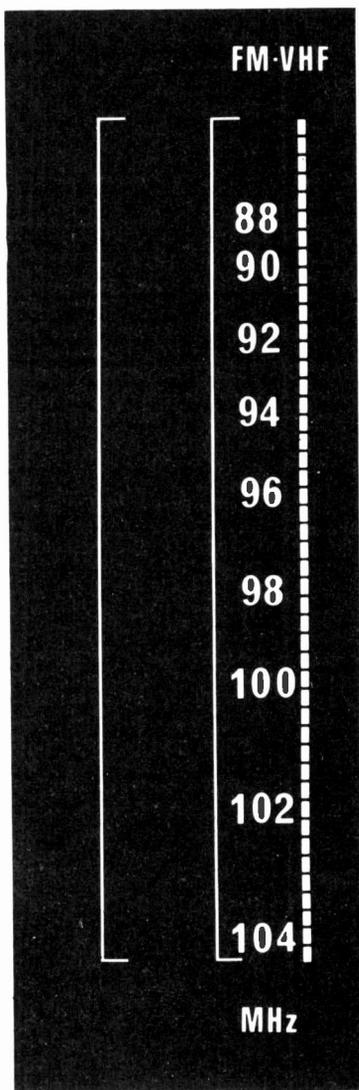

These electroluminescent devices, if fed at 400Hz, will give enough light to read by. The maximum frequency applicable is 2kHz and any increase above this or above 250V r.m.s. can considerably reduce device life.

SETTING UP

The tuner is wired up as shown and, after checking out the wiring the unit may be switched on. Selecting

MATERIALS . . .

Tuning dial—Electroluminescent panel 42×171mm (Sanders Roe Developments Ltd.).

Cord drive assembly, cursor, drive spindle, cord drive pulley wheels (4).

Drive support plate, 20 S.W.G. mild steel 262 × 120mm to be cut and bent to suit, together with 25 × 20mm and 25 × 52mm scraps for potentiometer bracket and extension piece if required. If main plate extended then latter not required.

Self-tapping screws, 4 and 6B.A. screws, nuts and washers, and spacers to suit.

the appropriate f.m. button on the pre-amplifier and with the volume controls set to a moderate level a rushing sound should be heard.

The detector coil in the Larsholt head is peaked for maximum audio output. The level of muting is adjusted by selecting a weak signal for reception and turning the mute control VR4 until the station just starts to fade. In this way interstation noise will be reduced.

Any further reduction in interstation noise will of course reduce the level of the weaker station.

The stereo decoder is set up by tuning to a station known to be broadcasting stereo and then adjusting the pre-set VR5 until the LED stereo beacon lights up. As described in Part 8, a signal generator may be used for this function if desired.

TRACKING

Operation of the tuning circuit depends, since it uses Varicap tuning, on the setting of the Varicap control potentiometer VR1 in Fig. 8.2.

The end frequency at the low end of the tuned scale is set by adjustment of VR3 whilst the tracking to match the graduated scale of the tuning dial is set by adjustment of VR2. The latter sets the potential across the potentiometer VR1.

Adjustment for correct tracking can be carried out using a signal generator of known accuracy or, probably more simply, by tuning to known stations and suitably adjusting till their reception and the correct frequency agree on the tuning dial. For readers' assistance a copy of the scale used in the prototype is shown in Fig. 9.5. The tuning potentiometer VR1 is a 100kΩ linear device and the scale should be found to agree with the tuning without too much difficulty.

If required, VR3, and for that matter VR2, can be replaced with fixed value resistors once their values have been ascertained.

Whilst calibration has been going on the tuning meter will, hopefully, have been swinging up and down and it will be seen that this is a "maximum reading for tune" indicator.

If required, the tuner alignment, using the scale shown here in Fig. 9.5, can be achieved using a voltmeter rather than relying on the existence of broadcast stations. The procedure is as follows.

The main tuning potentiometer VR1 is set to mid-scale and the pointer is adjusted to align with the 100MHz calibration. After readjusting the pointer, using the tuning knob, to 88MHz measure the voltage between the wiper of VR1 and 0V. This should be done using a fairly high impedance meter preferably above 20kΩ per volt so as to avoid loading of the circuit.

Now adjust VR3 till the reading is 2.4V. Tune to 104MHz and adjust VR2 till a reading of 12.4V is obtained.

The procedure should be repeated to optimise the readings and the following will give some idea of the level of readings obtained along the scale. 88MHz, 2.4V; 90MHz, 2.7V; 92MHz, 3.2V; 94MHz, 4.0V; 96MHz, 5.0V; 98MHz, 6.5V; 100MHz, 8.0V; 102MHz, 10.2V and 104MHz is 12V.

This completes the Rondo series. We hope to publish details of further circuit modifications and additions as these become available



EXHIBITION REPORT

Just a few years ago the IEA Exhibition, held at Olympia, was heralded on each occasion as an ever-growing shop-window in which the World could look at British products. This year has seen its last occurrence at Olympia as, in future, it is to be held at the new National Exhibition Centre near Birmingham from 1976.

It is perhaps an indication of the attitude with which these large events are currently viewed by many manufacturers that the 1974 show was graced by roughly half as many exhibitors as at the previous event. Whilst this is in a way a shame, these massive circuses always add interest to the annual round, it should allow quite a saving to the industry exchequer when one remembers just how much is spent on massive events of this type.

The largest IEA held in 1970 probably cost the industry upwards of £18m including all attributable and fringe costings. To cover this the industry needs to earn at least three times the amount in turnover and clearly many of the larger manufacturers have been asking themselves if there is not a more efficient way of advertising their existence other than at this sort of cost.

Equally, it has been long admitted that centres such as Olympia and Earls Court are far from the ideal viewed in the light of other exhibition centres in Europe. Hence the choice of the new Birmingham centre which is to be a purpose-built location within easy reach of rail, road and flight links to the rest of the country and, more important, the rest of Europe.

Usually it is possible to point to a dozen or so items which catch the imagination for their novelty, sparkle or wit. But this year the feeling was very much one of soldiering on in spite of it all, against a background of hope that the components supply situation—life-blood of the industry—would not worsen.

HEAT PIPES

Even though the show was not exactly full of sparkling new devices and equipments, there were still a few items worth noting. Many of the ideas which have come to the fore in the last few years are now being applied commercially with great effect such as is the case with

heat pipes. Jermyn Manufacturing of Sevenoaks, Kent, were displaying a variety of these with capacities up to 5kW and lengths up to 10ft.

In fact they also demonstrated a hot air engine being cooled by heat pipes and it would seem that this particular invention has a future in areas across the board of industry. This perhaps illustrates the way in which one art can provide a solution to problems in other arts.

SOLID STATE


Predictably devices were not too much to the fore as the IEA is basically an equipment show but there were still some very interesting semiconductors around if one cared to look in the corners.

NEW CLOCK CHIP

Constructors who find the present state of the art in clock integrated circuits rather off-putting what with the need for two supply voltages, the physical size of the package (up to 40 pins) not to mention the cost, will no doubt welcome the introduction of a new, much simplified i.c. from General Instrument Microelectronics.

Designated the AY-5-1224 Clock Circuit, this new device features

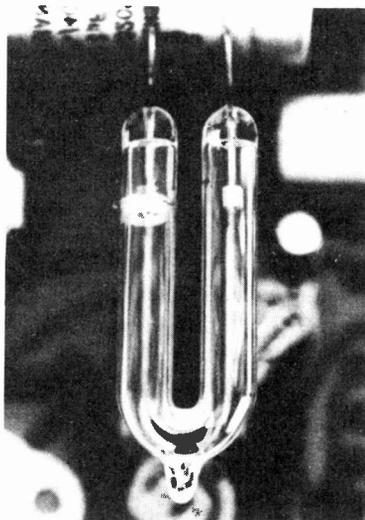One of the new long-life Heimann U-shaped flash tubes available from AEG-Telefunken. These devices are available in various standardised forms with ratings of 4 and 8W suited for use in flash and stroboscopic applications.



only a four digit readout as opposed to the usual six digits on the currently available chips and only a single 15V supply rail.

A single supply rail greatly simplifies the design of the power supply section of a clock which means that the whole circuit can be contained in a common 16-pin dual in line package.

The device was shown on the Semiconductor Specialists stand where it was demonstrated that the i.c. could drive a Monsanto MAN82 seven segment display directly.

Further details can be obtained from General Instrument Microelectronics, 57-61 Mortimer Street, London, W1N 7TD.

COLOURED LEDs

Light emitting diodes seem to be finding their way into more and more projects in PE but as yet the only widely available types have been red. Though the technology for producing other colours has been known for several years, it is only now that they are becoming a commercially viable proposition.


Firms such as Motorola, Hewlett-Packard and Monsanto all had l.e.d.s in various colours on their stands. The new colours available are amber, yellow and green.

At the present time the prices of the colours are about twice that of red l.e.d.s but no doubt they will soon come down.

The new colours are not restricted to discrete l.e.d.s but are also appearing in alpha-numeric displays.

In this field it seems that the price barrier has already been broken for Monsanto are able to supply 0·3in

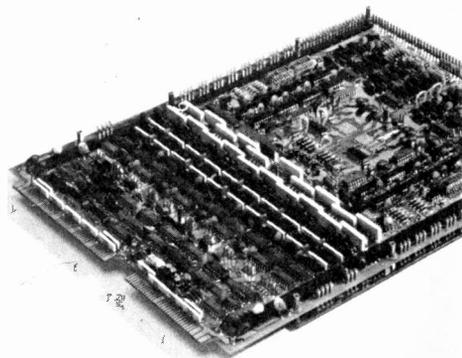Just to give some idea of the complexity and compressibility obtainable nowadays here is the latest Ampex core memory from the 1600 series which consists of a double-sided circuit board and a plug-in stack. These particular memories are available in capacities from 16·384k-word to 32·768k-word.



green, yellow or red seven segment displays all for the identical price of £2.50 (one off). For those who are interested these displays are designated MAN51, MAN81 and MAN71 respectively, and further details can be obtained from Semiconductor Specialists, Premier House, Fairfield Road, Yiewsley, West Drayton, Middlesex.

MOS LSI CIRCUITS

The new development in MOS that is destined to make quite an impact on the digital i.c. market is the production of *n*-channel circuits. This new technique makes it possible to take full advantage of the low cost and high density of MOS whilst retaining full compatibility with TTL circuitry now so cheaply available.


We have already seen the MOS circuit whose inputs and outputs were fully compatible with TTL in that they needed no interfacing, but they have still required a V_{SS} and a V_{EE} supply, usually +5V and -12V respectively, making it necessary to provide another supply line other than the +5V for TTL.

The *n*-channel devices only require +5V.

The new technique has also effected a reduction in price in MOS. A good example of the technique is the Intersil IM7552CPE which is a 1024 bit random access memory which uses *n*-channel silicon gate enhancement mode technology.

Power consumption is only 0.2 μ W per bit and access time is 1 μ S. The price is a mere £13.47 making a cost of less than 1½p per bit.

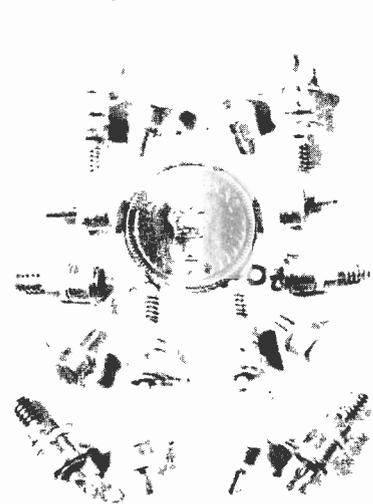These tiny devices are snap-action thermal switches ideal for use in cramped locations and capable of fast switching—making them useful in overheat detection and similar applications—and they are available from Jermyn Manufacturing.



WAVEFORM GENERATOR

Another interesting i.c. from Intersil, but this time using bipolar technology, is the IM8038CCPD.

Basically this is a voltage controlled oscillator but unlike most other similar devices it is capable of producing not only square and sawtooth outputs, but also sinewave. This makes it a really useful device for all sorts of sound effects systems and at a price of only £2.85 it should be within the range of most amateurs' pockets.

Further information on both the above mentioned Intersil i.c.s is available from Celdis, 37/39 Lovelock Road, Reading, Berkshire.

EDUCATION

Whilst most educational establishments now run some form of course in the measurement and control fields there is still a great deal of room for the development of equipment capable of demonstrating the various functions used. Feedback Instruments are specialists in this field and were showing a range of new devices.

Their electronic circuit constructor ECC 186 is a hand-case sized unit with a lift-up lid on which a circuit may be constructed using connectors and components housed in compartments formed in the other case part. The unit carries a power supply, indicating analogue meter in a multimeter circuit, and sufficient interconnections to make up many electronic circuits.

From the same source were a number of training aids in such areas as transducers. A kit TK 294 contains means for investigating variation of resistance with tem-

Exemplary of the trend in multiple cable testing equipment is the VD 36 unit shown here testing a cableform in backwiring. This instrument is capable of coping with up to 100 conductors and is available from Siemens U.K.



perature, strain or motion, variation of capacitance with motion, proximity and level, and variation of self- and mutual-inductance with motion.

Feedback Instruments, of Park Road, Crowborough, Sussex, also manufacture a wide range of test instrumentation suited to the educational and test markets but perhaps most interesting is their Cygnet telewriter, a desk-top equipment which can transmit and receive handwritten messages over telephone lines. Ideal for use in banks, factories and offices, this equipment offers various advantages, not the least of which is removal of ambiguity and the provision of a written copy of any message.

The use of patchboards, bread-board training aids as they used to be called, is a popular one in educational circles, as evidenced by the new products available from Limrose Electronics of 8-10 Kingsway, Altrincham, Cheshire, who showed a couple of integrated circuit patchboards. One, the PB100 system, is designed to cope with up to 40-pin d.i.l. packages and is suited to creating logic, analogue and hybrid circuitry of quite considerable complexity. For example a single patch-panel can accommodate up to 44 d.i.l. packages.

The basic unit includes power supplies, patching facilities and switched channels, and is able to accept any one of a number of patchboards which can be made up to meet the needs of the course.

A low-cost version, the Compukit 2, is designed for use with up to 16-pin d.i.l. packages or, indeed, discrete devices. Again, it includes power supplies and patching facilities but has only the one patch-board unit permanently wired in.

TEST

Of course, at the IEA a great deal of attention is paid to test and measurement, with a growing interest these days in the automation of test wherever possible. Many machines now exist to test actual equipments and these tend to follow fairly standard patterns but the area which has received least attention is the testing of cableforms or looms. These invariably present difficulty and usually require someone to spend laborious hours doing direct point-to-point tests of each conductor.

TJG Electronics, of 15 The Green, Poulshot, Devizes, Wiltshire, have developed a low cost automatic wiring tester which can be assembled in modular form to deal with various sizes of loom. It can test a wiring system with up to 2,600 connections and checks for continuity of each wire and that individual wires are not shorted together. The tests can be counted and faults can be made to arrest operation and give an indication.★

FAST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
 Express postage 3p for first transistor, p thereafter, over
 ten post free. INTEGRATED CIRCUITS 5p + 1p each added

sp	FAZ11	sp	BY213	sp	OAZ205	sp	28170	sp	0-10
1N21	0-17	FAZ12	0-00	BY210	0-48	OAZ206	0-18	28271	0-18
1N23	0-80	ASV26	0-26	BY211	0-40	OAZ207	0-48	Z721	0-28
1N55	0-50	ASV27	0-80	BY212	0-40	OAZ208	0-40	Z743	0-28
1N258	0-50	ASV28	0-26	BY213	0-25	OAZ209	0-40	ZTX107	0-12
1N645	0-18	ASV29	0-80	BY215	0-85	OAZ210	0-40	ZTX108	0-10
1N725A	0-80	ASV36	0-26	BY216	0-80	OAZ211	0-40	ZTX300	0-14
1N914	0-08	ASV50	0-14	BZV88	0-10	OAZ222	0-48	ZTX304	0-24
1N4007	0-12	ASV61	0-40	C111	0-55	OAZ223	0-48	ZTX500	0-15
18113	0-25	ASV65	0-20	CR81/06	0-80	OAZ224	0-48	ZTX503	0-16
18131	0-18	ASV62	0-26	CR81/40	0-85	OAZ241	0-25	ZTX531	0-25
18202	0-38	ASV66	0-33	CS4B	1-90	OAZ242	0-15		
2G371	0-40	ASZ21	1-00	CS10B	3-60	OAZ244	0-25		
2G381	0-22	ASZ23	0-75	DD000	0-15	OAZ246	0-15		
2G414	0-30	AU10	1-50	DD003	0-15	OAZ290	0-28		
2G417	0-25	AU10	1-00	DD006	0-25	OC16	1-00		
2N404	0-22	BC107	0-12	DD007	0-40	OC18T	1-00		
2N497	0-15	BC108	0-12	DD008	0-38	OC20	2-00		
2N698	0-30	BC109	0-12	GD3	0-33	OC22	1-00		
2N708	0-10	BC113	0-18	GD4	0-18	OC23	1-25		
2N708A	0-12	BC116	0-20	GD5	0-22	OC24	1-10		
2N708	0-15	BC118	0-20	GD8	0-25	OC25	0-40		
2N709	0-40	BC118A	0-28	GD12	0-10	OC28	0-40		
2N1091	0-65	BC118	0-20	GET102	0-50	OC28	0-70		
2N1131	0-20	BC121	0-20	GET103	0-40	OC29	0-65		
2N1132	0-25	BC122	0-20	GET113	0-35	OC30	0-40		
2N1302	0-18	BC125	0-28	GET114	0-30	OC35	0-55		
2N1303	0-18	BC126	0-25	GET115	0-75	OC38	0-65		
2N1304	0-22	BC129	0-20	GET116	0-25	OC41	0-25		
2N1305	0-22	BC147	0-18	GET120	0-50	OC42	0-40		
2N1306	0-22	BC148	0-10	GET872	0-30	OC43	0-70		
2N1307	0-22	BC149	0-18	GET875	0-40	OC44	0-18		
2N1308	0-22	BC157	0-14	GET880	0-55	OC44M	0-17		
2N2147	0-75	BC158	0-12	GET881	0-25	OC45	0-18		
2N2148	0-60	BC160	0-25	GET885	0-35	OC45M	0-18		
2N2160	1-00	BC169	0-30	GET887	0-45	OC46	0-27		
2N2162	0-28	BCY31	0-45	GEX44	0-08	OC57	0-27		
2N2169	0-22	BCY32	1-20	GEX45/1	0-45	OC58	0-60		
2N2365A	0-28	BCY33	0-38	GEX941	0-45	OC59	0-60		
2N2444	1-99	BCY34	0-45	GJ3M	0-50	OC66	0-50		
2N2613	0-28	BCY38	0-55	GJ4M	0-50	OC70	0-18		
2N2646	0-50	BCY40	1-00	GJ7M	0-60	OC71	0-15		
2N2904	0-20	BCY42	0-30	HG1005	0-80	OC72	0-50		
2N2904A	0-25	BCY70	0-15	HS100A	0-80	OC73	0-60		
2N2906	0-25	BCY71	0-20	MAT100	0-20	OC74	0-80		
2N2907	0-28	BCZ11	0-60	MAT101	0-25	OC76	0-80		
2N2924	0-18	BCZ11	0-60	MAT120	0-80	OC77	0-75		
2N2926	0-15	BD121	1-00	MJE520	0-65	OC78	0-25		
2N2926	0-10	BD123	1-00	MJE520	0-65	OC79	0-25		
2N3054	0-50	BD123	1-00	MJE2065	1-10	OC81	0-28		
2N3055	0-25	BDY11	1-45	MJE3055	0-70	OC81D	0-28		
2N3056	0-15	BF115	0-22	MJE340	0-60	OC81M	0-18		
2N3059	0-11	BF117	0-50	MPP102	0-40	OC81SD	0-18		
2N3076	0-18	BF177	0-25	MPT103	0-80	OC81Z	0-45		
2N3079	0-11	BF178	0-25	MPT104	0-85	OC82	0-28		
2N3079	0-11	BF181	0-55	MPP105	0-48	OC82D	0-28		
2N3111	0-21	BF184	0-22	NKT128	0-45	OC83	0-25		
2N3119	0-35	BF185	0-22	NKT129	0-30	OC84	0-30		
2N4289	0-20	BF194	0-18	NKT211	0-25	OC114	0-88		
2N5027	0-58	BF195	0-18	NKT213	0-25	OC122	1-00		
2N5068	0-35	BF196	0-15	NKT214	0-24	OC123	1-10		
28304	1-15	BF201	0-25	NKT217	0-45	OC138	0-50		
28501	0-75	BF281	0-25	NKT217	0-45	OC140	0-45		
28703	1-00	BF289	0-25	NKT218	1-13	OC141	0-80		
AA129	0-20	BFX12	0-20	NKT219	0-38	OC169	0-20		
AAZ12	0-75	BFX13	0-25	NKT222	0-80	OC170	0-25		
AAZ13	0-10	BFX29	0-28	NKT224	0-25	OC171	0-20		
A0107	0-35	BFX30	0-28	NKT251	0-24	OC200	0-55		
AC126	0-25	BFY30	0-25	NKT271	0-20	OC201	0-80		
AC127	0-25	BFY63	0-50	NKT272	0-20	OC202	0-80		
AC128	0-20	BFX84	0-25	NKT273	0-20	OC203	0-55		
AC187	0-20	BFX85	0-28	NKT274	0-20	OC204	0-65		
AC188	0-20	BFX86	0-25	NKT275	0-25	OC205	1-00		
ACY17	0-25	BFX87	0-25	NKT277	0-25	OC206	1-10		
ACY18	0-27	BFX88	0-28	NKT278	0-25	OC207	1-00		
ACY19	0-27	BFY11	0-50	NKT304	0-75	OC460	0-20		
ACY20	0-25	BFY17	0-40	NKT403	0-70	OC710	1-00		
ACY21	0-25	BFY18	0-45	NKT404	0-60	OC711	1-00		
ACY22	0-18	BFY19	0-55	NKT678	0-80	ORP61	0-45		
ACY27	0-25	BFY24	0-45	NKT713	0-80	ORP61	0-48		
ACY28	0-25	BFY44	1-10	NKT773	0-25	EX68	0-20		
ACY39	0-25	BFY50	0-20	NKT777	0-20	EX68	0-20		
ACY40	0-22	BFY51	0-20	OR78B	0-88	EX68	0-20		
ACY41	0-22	BFY52	0-20	OA5	0-60	EX640	0-75		
ADY44	0-28	BFY53	0-17	OA6	0-18	EX641	0-75		
AD140	0-50	BFY64	0-45	OA7	0-08	EX642	0-60		
AD161	0-39	BFY90	0-75	OA70	0-10	EX644	0-85		
AD162	0-39	BXK37	0-50	OA71	0-20	EX645	0-85		
AD186	0-30	BXK60	0-98	OA73	0-15	TIC44	0-29		
AF114	0-25	BXK75	0-18	OA74	0-15	V16/30P	0-75		
AF115	0-25	BXK76	0-17	OA79	0-10	V16/30P	0-75		
AF116	0-25	BXK77	0-20	OA81	0-10	V30/201P	0-75		
AF117	0-20	BXK78	0-20	OA85	0-18	V90/201	0-50		
AF118	0-20	BXK79	0-12	OA86	0-15	V60/201P	0-75		
AF119	0-20	BXK80	0-12	OA90	0-07	XA101	0-10		
AF124	0-20	BT109/500R	0-12	OA91	0-07	XA102	0-18		
AF125	0-20	BT109/500R	0-12	OA95	0-07	XA151	0-18		
AF126	0-20	BTY42	0-25	OA200	0-08	XA152	0-18		
AF127	0-20	BTY79/100R	0-25	OA202	0-10	XA161	0-25		
AF139	0-38	BTY79/400R	0-25	OA210	0-20	XA162	0-25		
AF178	0-55	BY213	0-25	OA211	0-25	XB101	0-43		
AF179	0-55	BY210	0-48	OA220	0-50	XB102	0-30		
AF180	0-55	BY106	0-15	OA221	0-45	XB103	0-35		
AF181	0-50	BY126	0-14	OA202	0-45	XB113	0-30		
AF186	0-40	BY127	0-15	OA203	0-45	XB113	0-30		
AFY19	1-13	BY182	0-85	OAZ204	0-45	XB121	0-43		

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
 Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
 Terms C.W.O. only • Tel. 01-677 2424-7
All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

Prices correct when going to press.

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
 (also) 13 SOUTH MALL, EDMONTON, N.9
 MAIL ORDER DEPT.
 11 MAYES ROAD, LONDON N22 6TL
 Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

Spec: 5 Section
 Extended Length 100cm
 Length under Fender 40cm
 Cable Length 120cm
 Supplied complete with Fixing Bracket and 1/2" plus 23p Control Switch. **£6.75** P. & P.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4" x 3" x 2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 100 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at **£7.50** plus 10p.

"CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour. Specification—Projector: 100W. convection cooled, at 30ft the projected image = 16ft; Motor: 1rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, **£15**; 6in Liquid Wheel, **£5** = **£20** + 75p carr.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7 or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Our Price **£2.75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.

7in x 4in LOUSPEAKER

A top quality speaker ideal where size is important. Manufactured by E.M.I. for a well known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 3W. Unbeatable. Price: **£1.80**. Express postage on this item.

200/250V MAINS RELAY

Heavy duty contacts, 2,500V coil. All new and unused D.F.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: **£40** per 100 relays.

MINI LOUSPEAKERS

2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 3p P. & P. on each L.S.

AMTRON KITS

- UK65 Transistor Tester **£1-68**
- UK92 Telephone Amp **£8-28**
- UK115 Hi-Fi Amp—8W **£4-50**
- UK130 Mono Control Unit **£4-15**
- UK145 Amp—1.5W **£3-81**
- UK165 RIAA Equalised Stereo Amp **£5-30**
- UK195 Mini-Amp—2W **£3-66**
- UK220 Signal Injector **£2-85**
- UK230 AM-FM Aer. Amp **£3-29**
- UK275 Mike Pre-Amp **£6-98**
- UK300 4 Channel Radio Control

TIMER RESULTS AND COMMENTS

Recently I promised some preliminary readings taken using the "Random Timer" described in the June issue. At the time it was mentioned that these were expected to be interesting, as there were indications of odd happenings. I was right!

Readers will remember the suggested method of taking timings involved starting a stop-watch on a timing click, then hurriedly noting the time of the next click, resetting the watch and logging the reading during the next interval. This was the method I used initially, having first established that the timer was behaving fairly randomly. Oddly enough, during checking, when readings varied between about 3 and 20 seconds, I noticed bunches of identical timings, three 5's, three 7's and a run of 16, 14, 14, 15, 15. Was this coincidence, and if so, why should it happen to me?

§ § §

During the tests I concentrated on slowing the timer over 10 firings, and got a total of 71 seconds, when added together. Next, concentrating on speeding the timer counts the results totalled 47. These seemed reasonable so I continued with the following results. Slow period totalled 95, fast 74; slow 81, fast 66; S 77, F 51; S 95, F 74; and finally S 81, F 66: each figure being total for 10 timer operations.

A quick glance at these figures shows a difference of about 20 seconds between fast and slow. If we assume that my thoughts had any influence they seem to be equal for fast and slow periods, this means 10 seconds per period might be presumed to be a fair assessment of the "swing of influence". Now, and here's the big snag, this works out at only half a second per reading, assuming each worked in the proper direction. Alas, with the best will in the world, a person timing himself, operating the stop-watch himself, could make an error of half a second per reading, and if he is looking for a certain result, it could easily be the case that the subconscious would delay resetting on slow timings and be a little livelier on the fast periods. This, together with errors in reading the watch with biased eyes, could explain the apparent willingness of the timer to respond to thought!

§ § §

It was only at this stage that it occurred to me to use a better system of taking readings, obvious though it may have appeared to readers. From this time on I timed events for a fixed period each time and where an event did not coincide with the end of a period the position of the watch hand was noted

prior to the end of a minute and the next firing time noted after the end of the period, so allowing a fraction of a timer count to be assessed.

Before making further readings, I had a visit from a friend, Mr Benson Herbert of the Paralab, Downton, Wilts, and he asked to check its randomness after I had showed him one or two successful results. I noticed his logged readings were a list of six counts per minute which continued for some time. I apologised and said the timer was obviously going berserk (or had gone) and that I would fix it before doing a series of trials at his laboratory.



It's a strange fact, you only have my word, but when Mr Herbert left the timer behaved normally from that time to this. When I say normally perhaps I should say "paranormally", the constant timings had completely gone and we were back to normal paranormality once more. I admit to one interference with the timer: I did adjust the preset setting since, but as explained in the timer description this sets only the longest timing duration, unless adjustment is overdone, which it was not. Mr Herbert assures me that he made no conscious effort to influence the timer during his visit.—Strange indeed!

OVERSEAS NEWS

Brazil . . . The design and construction of an "Electromagnetic Space Tensioner" has just been completed by Prof. H. G. Andrade, Director of Research Dept., of the Brazilian Institute for Psychobiological Research. It took five years to complete the machine.

The machine operates on a theory based on compressing empty space by magnetic forces, such that the tension so created would propagate into hyperspace, causing a secondary reaction in space as we know it, simulating a "biomagnetic" field. The biomagnetic field is presumed to surround and permeate living organisms.

Experiments using bacteria indicate increase in reproductive rates of some 12 per cent at maximum field strength. One wonders if this is the result of the elaborate system or simply the effect of any magnetic field, as reports from experimenters in plant biology indicate that certain levels of magnetic field above that of the earth's natural field, can increase plant growth. It is claimed that fields up to 2,000 gauss are used in experiments.

USA . . . According to one report, when chicks are placed close to a random timing device the timings tend to speed up. Fertilised eggs are reported to have a similar effect.

U.S.S.R. . . . Information transfer between living cells. Two colonies of cells were placed in adjacent compartments, separated by a quartz glass divider. One colony was deliberately killed by poisoning or by virus infection and each time the other colony was affected by the same sickness as the first colony.

Over 5,000 experiments were performed and it was found that if the divider was of ordinary glass, no transfer of "infection" occurred. Apparently, cells emit light in minute measures, and in sickness the light seems to be modulated into pulses. Transmission through quartz glass suggests that the radiation may be in the ultra violet spectrum and carries photo-communication information.

Madam Kulagina, Russia's answer to Uri Geller, has been demonstrating remarkable talents in psychokinesis (P.K.).

Having seen films of her feats which included the spinning of a compass needle with a simple pass of her hand over or around it. Hidden magnets was the first reaction until she turned the compass casing and moved it in a zig-zag with the needle only just moving as a result of disturbing its pivot. All objects to be moved were placed on a transparent box-like table of glass or clear plastic.

§ § §

In April 1973, Benson Herbert of Paralab investigated and witnessed many such experiments and results seem to rule out electrostatic or electromagnetic effects, at least, so far as d.c. fields are concerned, as special equipment was used to detect these and other side-effects. But an interesting point to note is that Kulagina was able to create burn-marks on people's arms by a simple touch of the finger. It leaves one wondering if she is capable of producing radio-frequency radiation in concentrated form, which the apparatus present at the time would not be expected to respond to.

Another feat of this lady was to split the bubble of a spirit-level.


CUSTOM CABINETS

328/30 The Banks, Rochester, Kent. Tel: Medway (0634) 404199


SPEAKER CABINETS IN KIT FORM REPRESENT **HUGE SAVINGS**



2' x 12" Cabinet

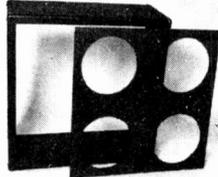

4' x 12" Cabinet

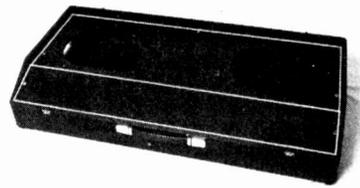

Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!


Kits are available in all specifications and all the kits contain everything you need as follows:-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!


PRICE & TYPE LIST

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 13"	£19.50	£12.50
4 x 12" (illustrated above)	31" x 31" x 13" x 13"	£24.50	£17.50
4 x 12" P.A. Column	48" x 27" x 13" x 13"	£30.00	£21.50
1 x 18"	31" x 31" x 13" x 13"	£24.50	£17.50
1 x 15" with two top horn cutouts	36" x 20" x 13" x 13"	£21.00	£13.50
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 8" x 8"	£20.00	£13.00
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 10"	£25.00	£18.50

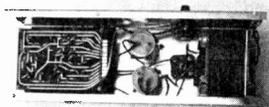Please ask for quotation on any other type or size of cabinet you may require.



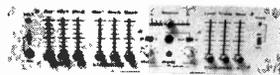- * 100 w RMS slave amp for Disco
- * 100 w RMS continuous sine wave output
- * Short and open circuit protection
- * Built to highest industrial spec.
- * Price £37.00 complete



- * Stereo studio disco mixer
- * Full PFL and Monitor facilities
- * As used by John Peel, Mark Wesley, Paul Burnett, DLT, Dave Christian, Tony Prince
- * Price £120.00




- * Concorde mono M400 mixer
- * Full PFL and Monitor facilities
- * Mike override
- * Magnetic inputs
- * Broadcasting quality
- £85.00

ALL OUR PRICES INCLUDE VAT AND UK DELIVERY



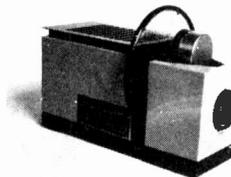- ERC 100 watt power amplifier
- * Electrolytic capacitors and second generation ICs
 - * Fully protected against short or open circuit
 - * Less than 0.1% distortion at all powers
 - * Rise time 4µS-stability - Unconditional Price £66.50



- Disco imp projector 150 watt tungsten
- unbeatable price £19.75**
- Includes liquid wheel and postage
- Normally £24-£27.50

TRADE AND EXPORT ENQUIRIES WELCOME

PATENTS REVIEW...

MOTOR CONTROL CIRCUIT

In BP 1 335 182 Smiths Industries describe circuitry for energising motors for short periods of time, a few milliseconds in every couple of seconds or minutes. Although the invention is concerned mainly with automatic aerosol operation (e.g. for kitchens, toilets, etc.), the invention principles have possibilities for much wider applications.

A charging circuit, Fig. 1, comprising fixed resistors and a variable resistor VR1 is connected between one side of a capacitor C1 and a 6 V positive supply. The capacitor is also connected via a resistor to the emitter of a *pnp* transistor TR1.

When the power supply is switched on, C1 charges via the resistors and potentiometer at a rate dependent on the setting of VR1. When the voltage across the capacitor rises above the base voltage of TR1 the latter switches on, causing the *npn* transistor TR2 to switch on which in turn holds TR1 hard on.

Whilst TR1 and TR2 are held on this provides a discharge path for C1 into the base of TR4, which allows the motor to run for as long as the charge on the capacitor holds TR1, TR2 on. Simultaneously TR3 is turned on so that C1 receives no charging current.

LIGHT OPERATED CLOCK

BP 1 334 640

As a rule this column does not report curious inventions. But there should be an exception to every rule. Arthur Pedrick of Selsey, Sussex, is by now well known for his numerous patents for odd inventions because usually his patents have more than a grain of sound sense behind them.

Pedrick describes, in BP 1 334 640, a clock which is supposedly regulated by the speed of light. According to the inventor, a light photon exerts a small but measurable pressure on whatever it strikes in a regular cycle of pulses. He believes that such pulses may be created by an electric spark produced between two electrodes located at the focus of a parabolic mirror so that a highly concentrated beam is projected.

The light pulses are received on a delicate, small, magnetically mounted target member. A small plate is secured to the opposite face of the target and has a tiny hole in it which acts as a light shutter.

Each time the target plate is moved, allegedly when struck by a light pulse, a minute quantity of light from a lamp is allowed to fall on a photocell through the small hole. The photocell output is amplified to operate a solenoid

which releases a trigger to allow a tooth wheel to rotate through one tooth angle to regulate a clock mechanism, driven in the conventional manner by a spring or weight.

Thus, the theory is that the minute movements of the target plate caused by the impingement of light pulses will result in accurate control of the mechanical member.

Even discounting physical theory doubts it seems highly unlikely that any target plate could be so delicately mounted as to move under the impact of light alone. But the idea behind the invention is sound for other applications.

A perforated target plate could be made which will respond to other stimuli (as, for instance, a Crookes windmill or radiometer responds to radiated heat) or could be coupled to a diaphragm sensitive to sound signals, or air disturbances. The latter application might well be relevant to audio visual displays or a solenoid (or solid state equivalent) triggering light or sound generators for alarm purposes.

FALSE START DETECTION

BP 1 330 569

According to BP 1 330 569 from Michael Weidacher, of Munich, previous attempts at electronically detecting false starts in athletic events have been unsatisfactory.

Some devices have worked on the principle that the first thing a runner does on hearing the starting pistol is to take his feet off the starting blocks. In reality the exact opposite is the case; the runner exerts a force back on to the starting blocks. Make and break contacts have been operated by this force but a switch travel of only 2mm can produce a switching lag of 1/1000th of a second, which is a distance of 10cm in sprint athletics.

The invention seeks to overcome these problems and has two main aspects in which an inertia switch and starting block design, with false start lamp, is suggested. The arrangement also incorporates a pistol cocking catch to prevent firing of the pistol in the event of false starts.

BP 1 335 182

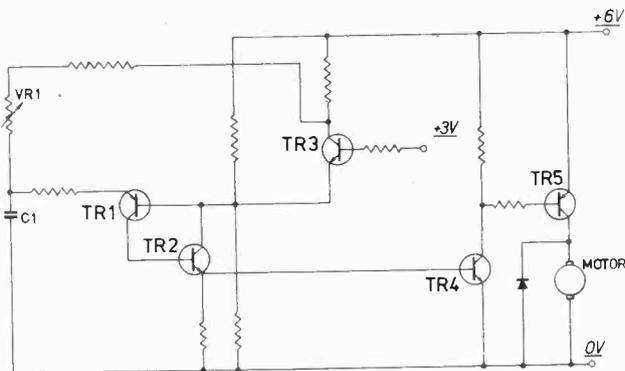


Fig. 1

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 25p each

SNORKELLING and scuba-diving have increased in popularity in recent years and, following this trend, the camera makers have produced a new range of underwater cameras. Many of these are relatively cheap and simple to operate, so the underwater photographer is by no means the rare fish that he was. But waterproofing the camera is not the only problem of sub-aqua photography.

Water absorbs some of the light passing through it, especially if it contains suspended material, and usually it absorbs more light from the red end of the spectrum. So, the deeper we go, the bluer the ambient light becomes. This blue cast spoils many underwater colour shots.

Unfortunately the human eye automatically compensates for variations in the colour temperature of ambient light, but colour film does not. The photographer is commonly unaware of the colour cast—until he views the processed slides, prints or movies!

The colour temperature of the ambient light varies with depth, suspended matter and other factors, and even at the same site may change from day to day. So the sub-aqua photographer needs some way of telling if the light is suited to the colour film he is using and, if not, what colour correcting filter he should use.

DESIGN FEATURES

The colour temperature indicator described here was designed especially for underwater use, though there is nothing to prevent its use for normal dry-land photography. Its main design features are:

1. **Small size**—achieved by compact layout and by avoiding the use of a milliammeter (which also makes it cheaper to build).

2. **Low power consumption**—power is provided by a small 9 volt radio battery (PP6).

3. **No external controls**—it is very awkward to provide waterproof seals for switches and the spindles of potentiometers, so this circuit was designed for use while completely sealed in a watertight container. For use at shallow depths it could be enclosed in a sealed glass preserving jar, or a Perspex box, but this gives the diver just one more item to handle under water.

It is preferable to put the indicator inside the camera housing, as described below. This is why its small size is so important.

CIRCUIT DESCRIPTION

As shown in Fig. 1, the circuit employs two photo-conductive cells PCC1, PCC2, connected in series between the positive (+9V) and negative (0V) rails. These are balanced (as described later) so that under all intensities of illumination their resistances are equal. The potential at point A thus remains at approximately 4.5V.

One photocell has a red gelatine filter covering it, the other has a blue filter. If the ambient light is of low colour temperature (relatively too much red light and too little blue), PCC1 will receive relatively more light than PCC2.

The resistance of PCC1 will fall and that of PCC2 will rise. This will cause the potential at point A to increase. So although the potential at A is not affected by changes in the *intensity* of illumination, it is affected by changes in the colour temperature.

Similarly, when colour temperature is high (too much blue, too little red) the potential at A will fall.

REFERENCE POTENTIAL

To detect the changes of potential at A we set up a reference potential at B, using the potentiometer VR1. This is set so that the potential at B is 4.5V.

Sub-Aqua Colour Temperature Indicator

By O. N. BISHOP



The operational amplifier IC1 is connected as a differential amplifier. Its output relative to the 4.5V line. (wiper of VR2) depends on the differential between its two inputs, the potentials of points A and B.

The integrated circuit amplifies potential swings, so that a small change of potential at A produces a large swing in the potential of the amplifier output. This large swing is used to operate the indicator lamps, D1, D2, which are light-emitting diodes.

If the output rises towards the 9V line a potential difference of up to 9 volts develops across R8 and D2 which glows brightly. The potential across D1 is correspondingly reduced and the lamp is almost extinguished.

Thus lack of balance due to low colour temperature causes the TOO RED lamp (D2) to be brightly lit. Conversely, as the output of the amplifier falls towards 0V, D2 no longer conducts and is extinguished, while the increasing potential difference between the output and the positive rail causes D1 to glow brightly—indicating TOO BLUE.

In operation VR1 is adjusted so that when the cells are illuminated by light of the correct colour temperature for the film being used, both lamps glow equally brightly. Then a departure from correct colour temperature will cause one lamp to glow more brightly than the other—indicating either TOO RED or TOO BLUE.

POWER CONSUMPTION

The use of light-emitting diodes helps to keep the device small and ensures low power consumption. The indicator uses about 30mA, rising to 70mA in full sunshine. The battery may be drained after an hour or so of use, and its output voltage will fall.


This does not affect the operation of the circuit, since the important potentials (at A, and at the wiper of VR1) are all obtained by potential-dividing

between the positive and negative lines. They maintain their *relative* values independently of the actual voltage of the supply.

Even with a flat battery, delivering only 7 volts, the circuit still works perfectly, though the light output from the lamp begins to weaken at this stage.

CONSTRUCTION

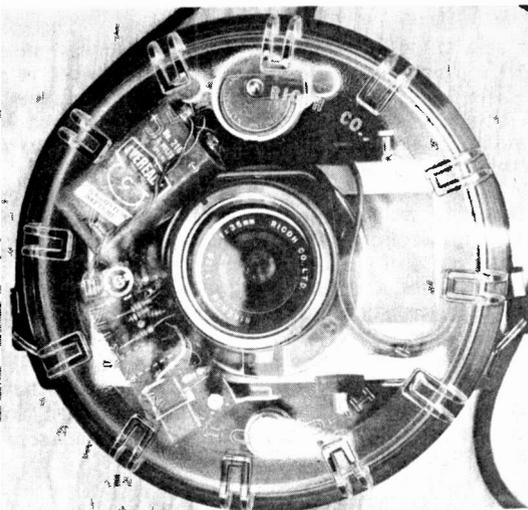Cut a rectangle of 0.1in matrix Veroboard, measuring 21 holes long and 9 strips wide. Bore



Photograph of the colour temperature indicator mounted inside the waterproof housing

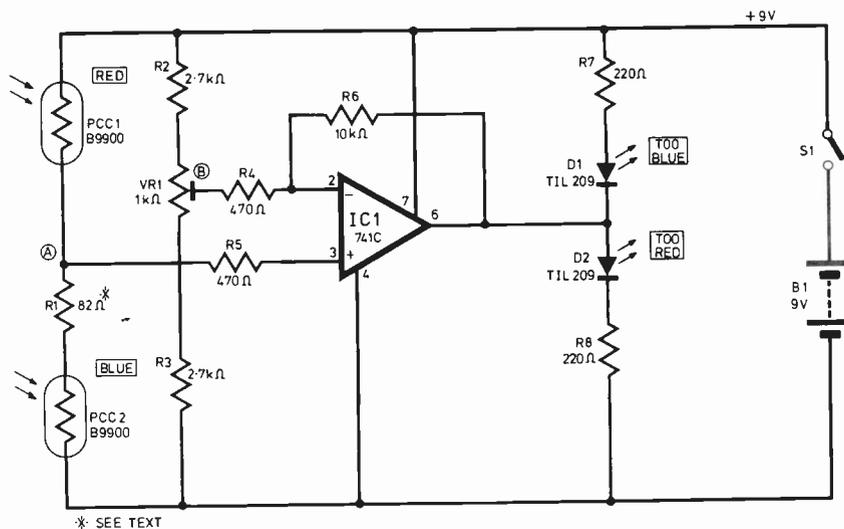


Fig. 1. Complete circuit diagram of the Sub-aqua Colour Temperature Indicator

mounting holes if these are required. The photograph shows that the author's model was mounted on a bracket made of aluminium which fits into the accessory shoe of the camera. This happened to be a convenient way of securing the circuit board where the cells could receive ambient light through the transparent front half of the housing.

With other camera housings, other means of attaching the circuit board may be devised. Construction follows the normal sequence of cutting away parts of the copper strips (Fig. 2) soldering on the resistors, and then the larger components. When working on such a small scale, with components crowded together, it is essential to prevent odd blobs of solder causing unintended shorts.

The metal ends of the photocells project beyond the body of the cell, so a small piece of card, folded and stuck to the circuit board, is used to separate the two cells to prevent short circuits.

LAMP MOUNTING

Some thought should be given to the mounting of the lamps, and this depends on the nature of the housing. If there is a viewfinder port it might be possible to mount the lamps to one side of this, so that they could be seen when using the viewfinder.

The lamps are very small and would easily fit in some kinds of housing. Leads would then be soldered to the circuit board, running to the lamps.

This scheme was not possible with the author's housing, and it was decided that with the housing pointing upward to receive light from above, it would be easy to view the lamps through the side of the transparent front half of the housing (even though this has a slightly frosted surface).

Accordingly the lamps were positioned so as to face out from the axis of the housing. They were at one end of the i.c., and in bright light they are shaded by a piece of rubber tubing, about one inch long pushed over both lamps. For permanency this could be stuck lengthways along the top of the i.c. To enable the lamps to be put in contact, the rim of each l.e.d. was gently filed away on one side.

Twin wires run from the Veropins to the battery. The battery can be fitted in any convenient space in the housing, and secured if necessary to prevent it fouling the camera mechanism. Since the indicator is to be operating continuously there is no point in providing the switch S1 in the sub-aqua version. However, if this is being constructed on a larger scale as a terrestrial version (see photograph of the prototype), a push-button is ideal, and the PP6 will last for months.

The prototype was built to test the circuit design, and afterwards housed in a spare plastic food container. The circuit board was bolted just below the translucent white plastic lid.

The cells are just beneath the circular area covered with 70% Letratone, placed there partly

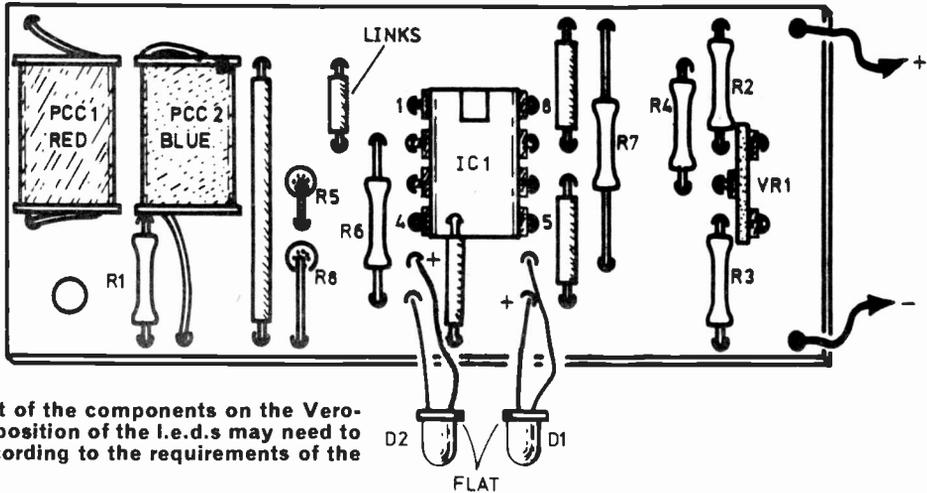


Fig. 2. Layout of the components on the Veroboard. The position of the l.e.d.s may need to be varied according to the requirements of the user

COMPONENTS . . .

Resistors

- R1 68Ω to 120Ω (see text)
- R2, R3 2.7kΩ (2 off)
- R4, R5 470Ω (2 off)
- R6 10kΩ
- R7, R8 220Ω (2 off)
- All 1/4W or 1/2W ±5% sub-miniature

Potentiometers

- VR1 1kΩ linear sub-miniature skeleton preset (or potentiometer, see text)


Semiconductors

- IC1 741C 8-pin DIL
- D1, D2 Light emitting diode TIL209 (2 off)
- PCC1, PCC2 B9900 photocells (2 off)

Miscellaneous

- S1 On/off switch (optional see text)
- 0.1in matrix Veroboard, 21 × 9 holes
- Veropins
- Photographic gelatine colour filters—tricolour red and blue

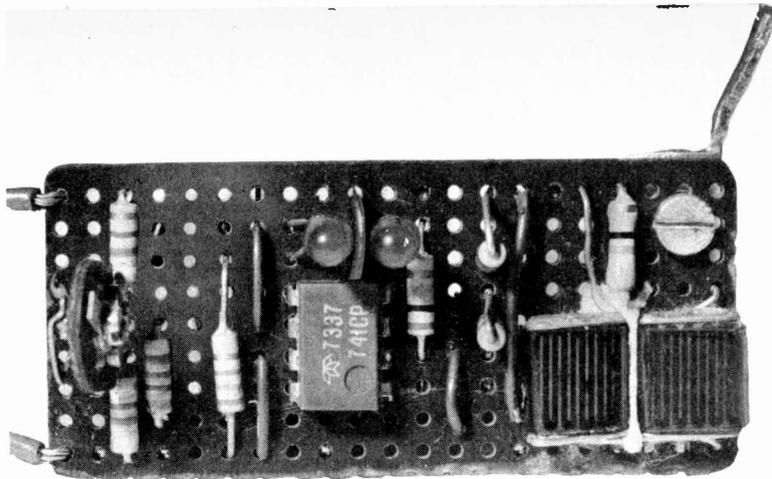Photograph of the prototype unit fitted with a small aluminium bracket for attachment to the camera accessory socket



to shade the cells and partly to indicate the location of the cells so that colour filters could be accurately placed over the cells when required.

The l.e.d.s were mounted on a piece of tag strip bolted to the rear wall of the box, and a light-proof plastic tube was placed across the box, making a sort of tunnel opening at the front of the box. This gave very effective shade, making it easy to see the lamps even in the brightest sunlight.

The control knob operates VR1, determining the potential of point B, with which the potential of point A is to be compared. There is no space for a potentiometer and knob in the sub-aqua version, its place being taken by the preset potentiometer.

SETTING UP THE CIRCUIT

Before colour filters are placed over the photocells, these must be balanced so they respond identically to variations in light intensity. This can be done when the connections to the positive and negative rails have been soldered, but the other connections are still loose.

Connect the battery to the circuit, and connect the negative probe of a test-meter to the negative terminal of the battery. Twist the lower (loose) leads of the photocells together and connect this joint to the positive probe of the meter. This should read 4.5 volts when the photocells are illuminated by indoor daylight or low power artificial light (e.g. 1ft from a 100W lamp).

If the meter reads other than 4.5 volts try putting a finger over one or other of the photocells and see what happens to the voltage. By this means it is easy to find out which of the photocells has too low a resistance. Part of this cell is blacked out by painting black ink on it, until the meter reads 4.5 volts.

In fact it is not necessary in this circuit to adjust exactly to 4.5 volts—somewhere between 4 and 5 volts is near enough, though the nearer the better.

Next take the circuit outdoors, still connected to the battery and voltmeter—place it in bright mid-day sunshine. There will probably be a change of meter reading. In bright light the resistance of both photocells falls markedly and probably not equally, so the voltage changes. One of the photocells now has too low a resistance, and this needs increasing by wiring a resistor (R1) in series with that photocell.

In Fig. 1 the resistor is in series with PCC2 (as in the model in the photograph) but it may be necessary to wire R1 in series with PCC1 instead. The exact value for R1 must be found by experiment.

Try various resistors of low value in series with PCC1 (or PCC2). The correct value is found when the circuit is carried from bright sunlight to deep shade (indoors) and the voltage changes by less than about 0.1 volts. The resistor may then be soldered in place.

PHOTOCELL FILTERS

The photocells may then be covered with coloured gelatine—using one, two, or three layers, depending on the depth of colour of the material available. Cadmium sulphide cells are especially sensitive to red light, so the red filter should be strongly red. The sharper the cut-off of the filters, the more sensitive will the indicator be to changes of colour temperature.

To calibrate the indicator, take it outdoors on a sunny day, between 10 a.m. and 2 p.m. and place it in direct sunlight. Adjust VR1 until the lamps both glow equally brightly. Now take the indicator in the shade and point it towards a bright blue sky—the TOO BLUE lamp should be bright and the other lamp dim. Take it indoors and expose it to artificial light (filament lamps — not fluorescent lamps)—the TOO RED lamp should be bright now and the TOO BLUE lamp dim.

By balancing the lamps in direct sunlight the indicator has been set for daylight colour film. Since the colour temperature of sunlight is modified by the presence of clouds in the sky it is worthwhile repeating this calibration on several occasions to find the mean setting for daylight. This can then be marked with a dot of paint on the preset. If you intend only to use daylight film (which is likely for sub-aqua work) calibration is now complete, and there is no further need to alter the preset. The indicator will always tell you if the light is correct for colour film (lamps equal) or TOO RED or TOO BLUE. In sub-aqua photography the latter is more likely.

UNDERWATER WORK

Colour correcting filters are available for compensating for incorrect colour temperature. For underwater work a set of pinkish filters of various strengths are useful for filtering out some of the excess blue light. To find out which filter to use, hold it over both cells of the indicator. If the lamps now glow equally, this filter is the correct one to

continued on page 723

Sinclair Cambridge kit.

Was £27.45.

Now only £14.95!

(INC VAT)

You save £12.50!

An advanced 4-function calculator in kit form

The Cambridge kit is the world's largest-selling calculator kit.

It's not surprising – no other calculator matches the Sinclair Cambridge in functional value for money; and buying in kit form, you make a substantial saving.

Now, simplified manufacture and continuing demand mean we can reduce even the kit price by a handsome £12.50. For under £15 you get the power to handle complex calculations in a compact, reliable package – plus the interest and entertainment of building it yourself!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{3}'' \times 2'' \times \frac{1}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of normal use before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £14.95!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £21.95 – so you're saving £7! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.

Features of the Sinclair Cambridge

- * Uniquely handy package. $4\frac{1}{3}'' \times 2'' \times \frac{1}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- * Calculates to 8 significant digits.
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries




A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

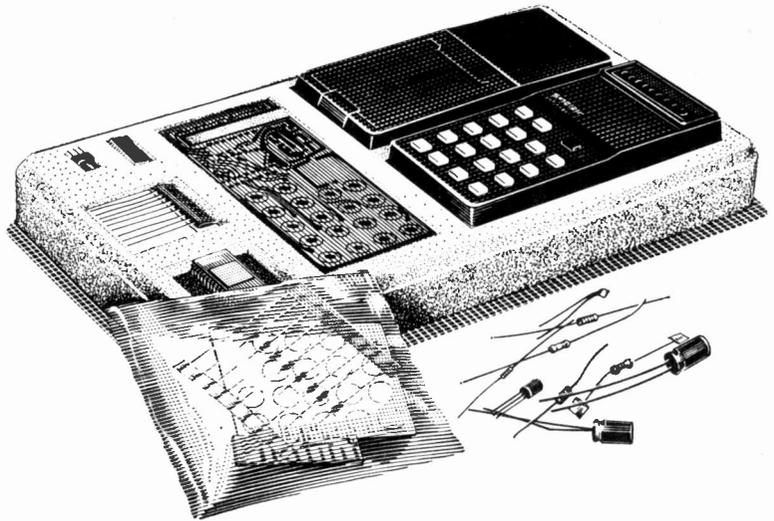
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

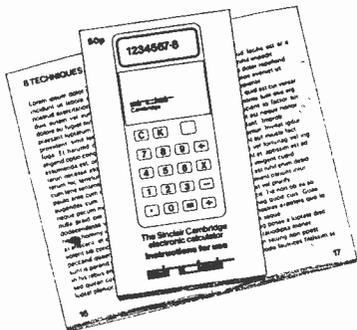But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 80 stereo modules. It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year. Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £13.59 + £1.36 VAT. (Total: £14.95)
Price fully built: £19.95 + £2.00 VAT. (Total: £21.95)

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me _____ Name _____

a Sinclair Cambridge Calculator kit at
£13.59 + £1.36 VAT (Total: £14.95)

a Sinclair Cambridge calculator ready
built at £19.95 + £2.00 VAT
(Total: £21.95) _____ Address _____

*I enclose cheque for £_____, made
out to Sinclair Radionics Ltd, and
crossed. _____

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required. _____

PE/B/74 PLEASE PRINT

Readout —

A SELECTION FROM OUR POSTBAG

Congratulations

Sir,—I would like to congratulate you on an extremely readable and very good magazine. In particular I liked the series "First Steps in Circuit Design."

I have followed many such series, but this is the first one that has really helped in getting down to actually building one's own circuits. I thank all concerned for publishing such a superb magazine.

Mr. E. Barton,
Craigellachie,
Banffshire.

Diode pump

Sir,—May I comment on Mr. Jones' "M.P.G. Meter" in your June issue, as I designed a meter on a related principle some time ago.

A meter of this type cannot respond accurately to, say, the increase in fuel consumption during sudden acceleration: it shows consumption correctly only after conditions have been steady for several seconds. Thus its main use is in comparing consumption during steady travel at various speeds or in different gears.

Before the meter can settle after a change in conditions, the pump must operate and C3 discharge, C3 charge again to the new peak value, the voltage on C4 follow this and the meter needle move. This will take around 5 seconds.

The meter scale is non-linear because of the behaviour of the diode pump C2, C3, D2, D3. For each operation of RLA, the voltage on C3 increases by


$$(V_s - V_3) C2 / (C2 + C3)$$

where V_s is the supply voltage

and V_3 the output voltage on C3 before the operation. Linearity is only obtained if V_3 always remains small compared with V_s .

The diode-transistor pump shown below is hardly more complex, but remains linear until V_3 rises to within 1V of V_s . In this circuit, when RLA1 closes, C2 charges via the diode. When RLA1 opens, the right-hand plate of C2 rises to

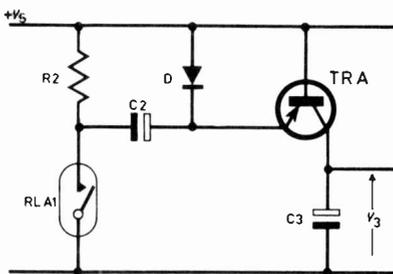above the supply potential, and discharges into TRA, with time constant $RC \times C2$. The current flowing from TRA collector is almost equal



Mr. Bradfield's transistor diode pump circuit

to the emitter current, irrespective of V_3 , so the increase in output voltage is $V_s C2/C3$ and operation is linear.

In the original circuit TR1/C4 is described as an emitter follower, but the circuit can only follow an increase in voltage above that already on C4. Fig. 2 shows the circuit functioning as a peak-value rectifier, which I would expect to be used. This operation is hampered by an excessive charging time constant $R4 \times C4 = 2.2$ sec. Reducing R4 to 100Ω improves this time constant while limiting peak collector currents to a safe value.

With linear operation obtained, the maximum voltage on C3 could be increased, but above 6V, reverse breakdown of TR1 emitter-base junction would upset operation when C3 discharges but C4 remains charged.

C. D. Bradfield
Kingston upon Hull

I find the points raised by Mr. Bradfield's letter very interesting.

With regard to the problem of linearity, it would seem to me that it is important to know whether one is doing 10 or 15 m.p.g. and relatively unimportant to know whether one is doing 75 or 80 m.p.g. This may not be so with a very small engined car, but the diode pump which produces this

non linear scale has, in my opinion, the advantage of increasing accuracy at the high consumption end of the scale.

Readers may wish to try Mr. Bradfield's modification, but to judge from the last paragraph, it would seem that some careful designing is necessary.

The response time may be a little slower than Mr. Bradfield would like, but with less than 20 components in the circuit, I am myself surprised that the Meter works as well as it does. It is not so many years since another magazine published a m.p.g. meter with over 50 transistors and a scale for each gear.

The response time of the m.p.g. meter depends on three factors. Firstly, the time between pump strokes—this will be the absolute minimum response time and with this type of pump is from 0.3sec. upwards, the average being perhaps 1.5secs. The other two factors are the charge and discharge times for C4. I agree that the charge time for C4 can be decreased by reducing R4, but in order to supply the increased current would it not be necessary to transistorise the stabilised power supply?

The discharge time of C4 depends on the resistance of ME1/VR1; more complexity would be needed to reduce this and could only result in the wild fluctuations C4 was put there to prevent. It is clearly explained in the text that C4 is something of a compromise and readers can reduce its value or that of R4 to obtain a response which suits them best.

TR1/C4 is not described as an emitter follower—the purposes of TR1 and C4 form two distinct paragraphs.

I hope that this satisfactorily clarifies the matter.—SJ

Telebell improvement

Sir,—I have read with interest the article "Telebell" in your June 1974 issue, a device for providing remote telephone bells wherever required without physical connection to the Post Office system.

It occurred to me that some signal other than a bell might be of greater use, either for the benefit of the deaf or in circumstances where an audible signal would be undesirable and I accordingly fitted a low voltage lamp in place of the bell. Obviously, this switches on and stays on until the supply is disconnected, due to the action of the CSR1, but this is no great disadvantage and works well.

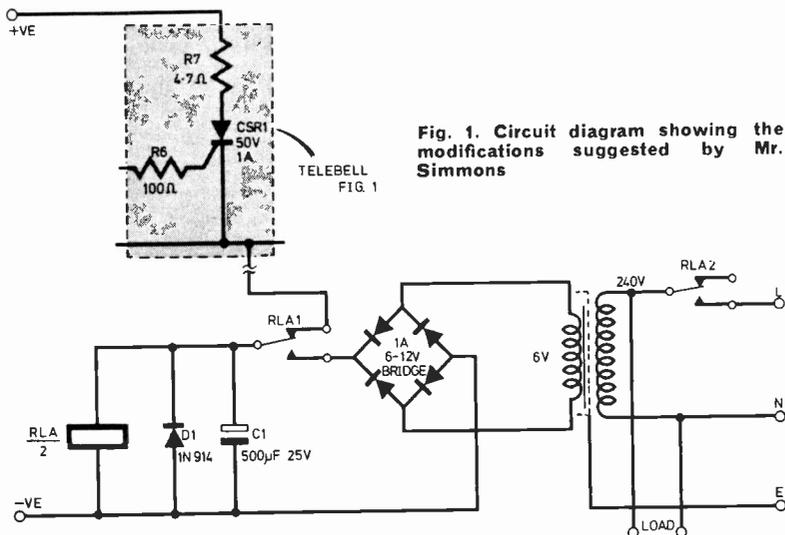


Fig. 1. Circuit diagram showing the modifications suggested by Mr. Simmons

A further thought then occurred and I replaced the bell/lamp by a 6V direct-current relay which has heavy-duty contacts, capable of handling several amperes, see Fig. 1. By making use of the various contacts as shown, I have produced a

device which has the advantage of working from a battery on negligible current in the stand-by condition, but which switches itself to mains operation when activated and disconnects the battery supply

through the thyristor CSR1. Moreover, the relay is capable of handling enough current to switch on a load of several hundred watts or, if greater capacity switching is required, of operating a further heavy-duty contactor.

The possibilities for use are endless; a toot on the horn as one drives up to the garage doors, with a suitably placed microphone, can activate lamps in the garage, the porch, switch on the fire and the TV, etc, etc.

Reverting to the original intention of the telephone bell providing the necessary activation, one might ring one's empty home while on a journey and bring about the same results as a security measure, though I am uncertain of the views of the local Telephone Manager on this use of the public equipment—it might constitute illegal use of his electricity! A deterrent from this sort of use, apart from any possible legal infringement, is that some other person may ring up during one's absence and bring about the same result at the wrong time of day!

C. H. Simmons, Wallingford.


SUB-AQUA COLOUR TEMPERATURE INDICATOR

continued from page 719

use under the prevailing lighting conditions. This procedure requires that you have filters which can be fitted over the lens port of the camera housing while under water, so it is possible to change filters while diving. Alternatively one can fit a filter to the camera before sealing it in its housing and place an identical filter over the photocells; the indicator will then show whether or not correct colour rendering will be obtained with this filter in use.

TERRESTRIAL CALIBRATION

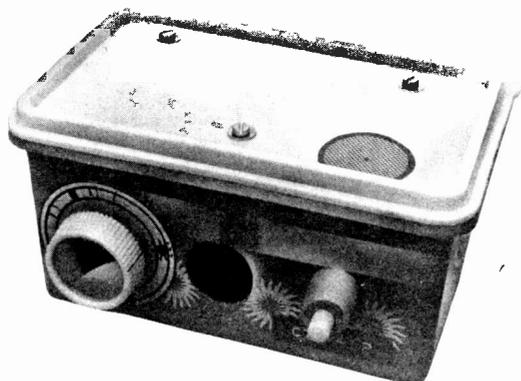For terrestrial use the indicator can also be calibrated for use in artificial light. Most "type A"



Photograph of a suggested box so that the colour temperature indicator can be used on dry land

colour films are balanced for the light from a photoflood lamp, so to calibrate the indicator, expose it to a photoflood and adjust VR1 until the l.e.d.s are balanced. Mark the position with a spot of paint.

If by any chance the lamps will not balance, even when the VR1 is at one end of its track, this is because the balance-point lies beyond the end of the track—somewhere along R2 or R3. With the values given, this should not happen, but if it does then R2 or R3 may be replaced with a resistor of greater or lesser value. Alternatively a 2.2kΩ preset could be used in place of VR1, though this would make it harder to adjust to exactly the correct balance point.

PRECAUTIONS

When the circuit has been adjusted and tested it is worth while to cover the underside of the board with a strip of self-adhesive tape. This will prevent the possibility of short-circuits through the metal parts of the camera and also protect the camera from scratching by the sharp cut ends of the component wires.

One final word of warning—the indicator is very sensitive to *all* coloured light reaching it—not just that from the intended source of illumination. When calibrating, turn off any lamps other than the one against which the indicator is being tested.

A fluorescent strip-light in the same room will throw calibration badly out. When the prototype was being calibrated some very inconsistent results were obtained, until it was realized that behind one of the lamps was a large blue window-curtain. So when calibrating, and when using the instrument, watch out for strongly coloured surfaces nearby; keep test sources away from walls and curtains—and don't wear a bright red shirt!



SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Base boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £12.00. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

A.C. mains 200-240V. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "Balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4". Overall height including valves 5". Ready built & tested to a high standard. PRICE £10.40. P. & P. 50p.

LOUDSPEAKER BARGAINS

5in 3 ohm £1.25. P. & P. 15p. 7in x 4in 3 ohm £1.40. P. & P. 20p. 10in x 6in 3 or 15 ohm £3.10. P. & P. 30p. E.M.I. 8in x 5in 3 ohm with high flux magnet, £1.70. P. & P. 20p. E.M.I. 13in x 8in with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm with two inbuilt tweeters and crossover network, £4.65. P. & P. 30p.

EMI CERAMIC MAGNET HEAVY DUTY TWEETER Approx. 54in. AV. 3 or 8 or 15 ohms, £1.25. P. & P. 20p. BRAND NEW E.M.I. 12in 15W P.D. speakers, 3, 8 or 15 ohm (state which). Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly, £9.90. Guitar models: 25W £9.90, 35W £11. P. & P. 45p each.

PRICES INCLUDE VAT

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high x 10in wide x 6in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9.25 Carr. 75p.

CABINET AVAILABLE SEPARATELY £4.95. Carr. 65p. Also available in 8 ohm with EM1 13in x 8in. bass speaker with parasitic tweeter. £7.15. Carr. 75p.

3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4" d x 4 1/2" h. Incorporates ECC83 EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £8. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.00. P. & P. 45p.

SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £8.00 plus P. & P. 60p.

SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10in TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £8.70. P. & P. 35p.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT

NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amplifier with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 16 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 90mV into 1M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -10dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide x 8" deep x 2 1/2" high.

Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E. PRICES AMPLIFIER KIT, £11.55 P. & P. 25p. (Magnetic input components 33p extra) POWER PACK KIT, £3.50 P. & P. 35p. CABINET, £1.00 P. & P. 35p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £25.10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

BATTERY OPERATED MEGA CIRCUIT TESTER

Made by Eveready and Vignoles, Ltd. Measures from 0.1 ohm to 200,000 ohms in 2 switched ranges. Used, but in perfect condition. Complete with test probes, leather carrying case and 4 1/2V standard battery. Only £7. P. & P. 40p.

Open 9.30-5.30 Monday to

Friday. 9.30-5 Saturday

Closed Wednesday

A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.


(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W. 19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA

NEW SCORPIO Mk. 2

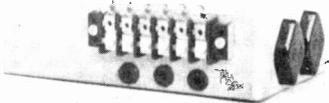

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V. and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board.—Uses original plugs, points, and coil.—No special parts or extras required.

(Case size 7 1/2in 4 1/2in 2in)

* All components available separately.—S.A.E. with enquiries.
* Construction manual available separately 25p.
Cost £12.95 incl. carr., ins. and VAT. (Carriage at cost outside U.K.—Export enquiries welcome.)

CONVERSION KIT FROM Mk. 1 to Mk. 2. FOR CONSTRUCTORS ALREADY POSSESSING Mk. 1 KITS.—Miniature P.C. assembly £1.10 incl. Carr., Ins. and VAT with full conversion instructions.

DABAR ELECTRONIC PRODUCTS

98 LICHFIELD STREET

WALSALL, Staffs WS1 1UZ



PRACTICAL PAPERBACKS FROM FOULSHAM-TAB


COLOUR TV REPAIR, by Martin Clifford ...	£1.40	MODERN RADIO REPAIR TECHNIQUE, by Art Margolis	£1.70
BASIC AUDIO SYSTEMS, by Norman H. Crowhurst ...	£1.60	PRACTICAL COLOUR TV SERVICE TECHNIQUES, by Robert L. Goodman ...	£1.95
EVERYMAN'S GUIDE TO CAR MAINTENANCE, by George Zwick ...	£1.50	TV TROUBLESHOOTERS HANDBOOK, by Editors of Electronic Technician/Dealer	£1.75
MATV SYSTEMS HANDBOOK, by Allen Pawlowski ...	£1.40	ACOUSTIC TECHNIQUES FOR HOME AND STUDIO, by F. Alton Everest ...	£1.50
MOBILE RADIO HANDBOOK, by Leo G. Sands ...	£1.50	199 COLOUR TV TROUBLES & SOLUTIONS, by R. L. Goodman ...	£1.50
RAPID RADIO REPAIR, by G. Warren Heath ...	£1.60	IC PROJECTS FOR AMATEUR AND EXPERIMENTER, by Wayne Green ...	£1.45
UNDERSTANDING AND USING THE VOM AND EVM, by John Cunningham ...	£1.50	JAPANESE COLOUR TV SERVICE MANUAL, by Hitachi, etc. ...	£1.90
HANDBOOK OF ELECTRONIC TABLES, by Martin Clifford ...	£1.40	RADIO ELECTRONICS HOBBY PROJECTS, by Editors of Radio-Electronics	£1.45
HOW TO USE YOUR VOM AND VTVM AND OSCILLOSCOPE, by Martin Clifford ...	£1.50		
INTRODUCTION TO MEDICAL ELECTRONICS, by Burton R. Klein ...	£1.70		



FOULSHAM-TAB LTD.
YEovil ROAD, SLOUGH, BUCKS.

SONAX ELECTRONICS FANTASTIC KIT OFFER

PE RONDO

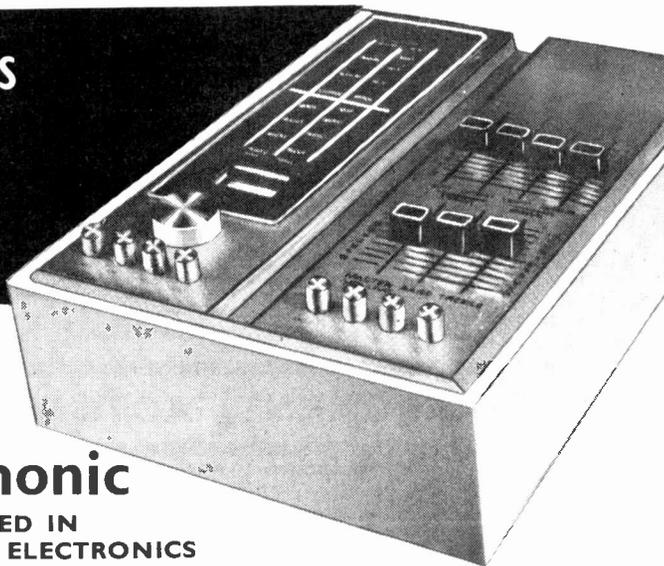

complete quadraphonic Hi-Fi System AS FEATURED IN PRACTICAL ELECTRONICS

There's never been an offer like it! Construct this 80 watt RMS Quadraphonic System with 4 matched high performance speakers. All finishes including polishing of cabinets and brushing and anodising of metal work are already completed. You can achieve the finest production finish and the styling will do justice to any room setting.

- | | | |
|--|---|---|
| <p>PLEASE SEND ME</p> <p>CBS SQ* MATRIX DECODER £8.00 <input type="checkbox"/></p> <p>*TM CBS Complete kit. Post Free.
Inc. CBS Licence Fee + VAT 80p</p> <p>PREAMPLIFIER BOARD £3.30 <input type="checkbox"/></p> <p>Complete kit. Post Free. + VAT 33p</p> <p>MASTER VOL./TONE/BALANCE BOARD £9.35 <input type="checkbox"/></p> <p>Complete kit. Post Free. + VAT 93p</p> <p>POWER AMP BOARD AND HEATSINK (Stereo Pair) £8.25 <input type="checkbox"/></p> <p>Complete kit. Per Board. Post Free. + VAT 82p</p> <p>POWER SUPPLY BOARD COMPLETE £5.50 <input type="checkbox"/></p> <p>Post Free. + VAT 55p</p> <p>MAIN SMOOTHING CAPACITORS (Two reqd.) £1.65 <input type="checkbox"/></p> <p>Post Free. + VAT 16p</p> <p>Per Pair</p> <p>MAINS TRANSFORMER £6.87 <input type="checkbox"/></p> <p>Post Free. + VAT 68p</p> <p>CHASSIS-PUNCHED AND DRILLED WITH SCREENS £3.57 <input type="checkbox"/></p> <p>Post Free. + VAT 35p</p> | <p>PLEASE TICK BOX</p> <p>RONDO CASE <input type="checkbox"/></p> <p>Post Free. + VAT 19p</p> <p>HARDWARE PACK <input type="checkbox"/></p> <p>Post Free. + VAT 22p</p> <p>CONTROL SECTION FASCIA <input type="checkbox"/></p> <p>Post Free. + VAT 38p</p> <p>STEREO DECODER KIT INC. BEACON <input type="checkbox"/></p> <p>Post Free. + VAT 59p</p> <p>STEREO DECODER READY BUILT AND TESTED <input type="checkbox"/></p> <p>Post Free. + VAT 76p</p> <p>ALSO—Suitable record playing equipment</p> <p>GOLDRING G101/2 TURNTABLE Less Cartridge £23.90 <input type="checkbox"/></p> <p>Post Free. + VAT £2.39</p> <p>DEUTSCHE ELAC STS 144/17 CARTRIDGE £7.90 <input type="checkbox"/></p> <p>Post Free. + VAT 79p</p> | <p>ADDITIONAL ITEMS</p> <p>COMPLETE SET OF 4 EDGE-CONNECTORS £1.44 <input type="checkbox"/></p> <p>Post Free. + VAT 14p</p> <p>COMPLETE SET OF PATCH BOARDS AND FANNING STRIP £3.54 <input type="checkbox"/></p> <p>Plug and socket and 24 way edge-connector Post Free. + VAT 35p</p> <p>TUNER SECTION FASCIA AND WINDOW £3.85 <input type="checkbox"/></p> <p>Post Free. + VAT 38p</p> <p>COMPLETE SET OF 7 SLIDER KNOBS AND 1 TUNING KNOB £1.25 <input type="checkbox"/></p> <p>Post Free. + VAT 12p</p> <p>QUAD SELECTOR SWITCH £1.43 <input type="checkbox"/></p> <p>Post Free. + VAT 14p</p> <p>4 PILLARS AND 2 END CAPS AND CENTRE BRIDGE AND SIDE TRIMS £3.30 <input type="checkbox"/></p> <p>Post Free. + VAT 33p</p> <p>NEW RONDO ADDITION F.M. TUNER KIT 1µV Sensitivity High Performance £17.50 <input type="checkbox"/></p> <p>Post Free. + VAT £1.75</p> <p>TUNING DIAL ASSEMBLY Complete with Meter and Calibrated Electro-luminescent Dial £10.42 <input type="checkbox"/></p> <p>Post Free. + VAT £1.04</p> |
|--|---|---|

SPEAKER KITS All components parts for "Rondo" loudspeaker assemblies are available, including special precision machined wrapround cabinets for very easy construction and perfect professional finish—as shown in fig. 7.9 of January 1974 issue.

COMPLETE SPEAKER KIT WITH 4 DRIVE UNITS, CROSSOVER WADDING, ETC. INCLUDING CABINETS Price Per Pair £34.50

Post £1. + VAT £3.55

SPECIAL OFFER - SAVE £7

4 Speaker kits (as required for Rondo) £62.00

Post £2. + VAT £6.40

- BASS DRIVE UNITS (2 per cabinet)** £4.25
- Post Free. + VAT 42p EACH
- TWEETERS (2 per cabinet)** £1.20
- Post Free. + VAT 12p EACH
- CROSSOVER KIT (1 per cabinet)** £2.75
- Post Free. + VAT 27p EACH

DETAILS OF ANCILLARY KITS

We apologize to our customers for any inconvenience caused by delay in delivery. This is due to tremendous demand for our products and we are endeavouring to clear back-log with all possible speed.

**BLOCK CAPITALS PLEASE
CHEQUE/P.O./MONEY ORDER**

MONEY ENCLOSED £

NAME

ADDRESS

POST TO:

SONAX ELECTRONICS, Spencer House, Brettenham Rd., Edmonton, London, N.18



GIRO NO. 331 7056

C.W.O. only P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments

ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS (Prices include Post and Packing)

10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.65 net
10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.35 net
25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.45 net
20E12 1/2W KIT: 20 of each E12 value, 22 ohms—2M, a total of 1220 (METAL FILM 5%), £11.05 net
15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £13.35 net
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £17.15 net

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3µp, 0.068µF, 0.1µF, 4µp, 0.15µF, 4µp, 0.22µF, 5µp, 0.33µF, 8p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V, 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 2µp, 0.0047µF, 3p, 0.0068µF, 0.01µF, 400V, 0.015µF, 0.22µF, 0.033µF, 3µp, 0.047µF, 0.068µF, 0.1µF, 4µp, 0.15µF, 6µp, 0.22µF, 8µp, 0.33µF, 12p, 0.47µF, 14p.

160V: 0.01µF, 0.015µF, 0.02µF, 3p, 0.047µF, 0.068µF, 3µp, 0.1µF, 4µp, 0.15µF, 5p, 0.22µF, 5µp, 0.33µF, 6µp, 0.47µF, 8µp, 0.68µF, 12p, 1µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.02, 0.03, 0.033, 0.047, 2µp each, 0.1, 30V, 4µp.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p, 10,000, 4µp.

RESISTORS

W.	Type	Range	1-99	100-499	500-999	1000+	Size mm
±	CF	22-1M	1	0.75	0.60	0.55	2.4 × 7.5
±	CF	22-2M	1	0.75	0.60	0.55	3.9 × 10.5
±	CF	22-1M	1	0.75	0.60	0.55	5.5 × 16
±	MF	10-2M7	2	1.54	1.32	1.1	3 × 7
±	MF	10-2M2	2	1.43	1.21	0.99	4.2 × 10.8
±	MF	10-10M	3	1.98	1.81	1.65	6.6 × 18
±	MF	10-10M	4.5	3.52	3.08	2.75	8 × 17.5

For value mixing prices, please refer to our catalogue (price in pence each).
VALUES AVAILABLE—E12 Series only. Net prices above 100.

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 6p each
1K, 2K2, 4K7, 10K, etc. up to 1MΩ
SUB-MIN. 0.05W Vertical, 100Ω to 220KΩ 5p each

Wavechange Switches

1P, 4W; 1P, 12W; 2P, 1P, 2W; 2P, 4W; 2P, 6W; 3P, 3W; 4P, 2W; 3P, 4W; 4P, 3W, 26µp

B. H. COMPONENT FACTORS LTD. (P.E.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS. LU7 9AQ
Tel.: Cheddington 668446 (Code 0296)
PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electronics

1.0µF 63V	6µp	68µF 16V	6µp
1.5µF 63V	6µp	68µF 63V	12p
2.2µF 63V	6µp	100µF 10V	6µp
3.3µF 63V	6µp	100µF 25V	6µp
4.0µF 40V	6µp	100µF 63V	14p
4.7µF 63V	6µp	150µF 16V	6µp
6.8µF 63V	6µp	150µF 63V	15p
8.0µF 40V	6µp	220µF 6.4V	6µp
10µF 16V	6µp	220µF 10V	6µp
10µF 25V	6µp	220µF 16V	8µp
10µF 63V	6µp	220µF 63V	21p
15µF 16V	6µp	330µF 16V	12p
15µF 63V	6µp	330µF 63V	25p
16µF 40V	6µp	470µF 6.4V	9p
22µF 25V	6µp	470µF 40V	20p
22µF 63V	6µp	680µF 16V	15p
33µF 10V	6µp	680µF 40V	25p
33µF 16V	6µp	1000µF 16V	20p
33µF 40V	6µp	1000µF 25V	25p
32µF 63V	6µp	1500µF 6.4	15p
47µF 10V	6µp	1500µF 16V	25p
47µF 25V	6µp	2200µF 10V	25p
47µF 63V	6µp	3300µF 6.4	26p

VEROBOARD

2 1/2 × 5"	0.1	0.15
2 1/2 × 3 1/2"	28p	28p
3 1/2 × 5"	26p	19p
3 1/2 × 3 1/2"	32p	33p
2 1/2 × 1 1/2"	28p	28p
2 1/2 × 1"	7p	7p
2 1/2 × 5" (Plain)	—	14p
2 1/2 × 3 1/2" (Plain)	—	12p
5 × 3 1/2" (Plain)	—	22p
Insertion tool	59p	59p
Track Cutter	44p	44p
Plugs, Pkt. 25	10p	10p

TRANSISTORS

AC126	16µp	BC212L	12p
AC128	22p	BC213L	12p
8C107	11p	BC214L	17p
8C108	12p	OC44	18p
8C109	13p	OC71	13p
8C148	12p	OC81	16p
8C149	12p	OC170	23p
8C182L	12p	TIS43	33p
8C183L	12p	2N2926	11p
8C184L	13p	2N3702	11p

POTENTIOMETERS

Carbon Track 5KΩ to 2MΩ, log or lin. Single, 16µp. Dual Gang 46p. Log Single with Switch 26p.

DIODES

IN4001	6µp
IN4002	7µp
IN4003	9p
IN4004	9µp
IN4005	14p
IN4006	14p
IN914	7p
IN916	7p
BA100	10p
OA5	42p
OA47	9p
OA81	11p
OA200	8p

SOCKETS

DIN 2 Pin	10p
DIN 3 Pin	10p
5 Pin 180°	12p
Std. Jack	14µp
2.5mm Jack	11p
Phono	5µp

Integrated Circuits

µA709C	50p
µA741C	55p
µA723C	£1
µL914	35p

PLUGS

DIN 2 Pin	12p
3 Pin	13p
5 Pin 180°	15p
Std. Jack	14µp
2.5mm Jack	11p
Phono	5µp

SOCKETS

DIN 2 Pin	10p
DIN 3 Pin	10p
5 Pin 180°	12p
Std. Jack	14µp
2.5mm Jack	11p
Phono	5µp

ELECTROLYTIC CAPACITORS. Tubular & Large Cans

(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 6µp, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 100p, 1000/50, 40p, 2000/10, 20p, 1000/100, 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1.10.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7µp, 1µF, 9p.
41V-VOLT: 4/450, 14p, 8/350, 19p, 8/450, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/500, 88p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7µp, 1µF, 9p.
41V-VOLT: 4/450, 14p, 8/350, 19p, 8/450, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/500, 88p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7µp, 1µF, 9p.
41V-VOLT: 4/450, 14p, 8/350, 19p, 8/450, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/500, 88p.

Base Mobile 1W, Stoalised Multi Channel 2 Meter band Transmitter for amateur band

A complete 2 meter band transmitter with 144-146 MHz frequency transmission. Suitable for home installation or as a quality portable transmitter completely self contained. Supplied ready to use and constructed on double-sided printed board using high quality components. Unit and power supply housed in strong case with metal fascia. Straightforward frontal controls. Hand-held dynamic microphone with stand. Internal 12V power supply. Connection for external battery eliminator. Overall size 6in × 4in × 2in app. Output 1W min. Aerial 19in whip. G.P.O. approved. Base Mobile supplied ready to use.

£39.50

1W Chassis with all connections and ready to use (complete with microphone). Specifications as Base Mobile Chassis size 4in × 1in.

£29.50

KIT 1W with all components and full assembly instructions. Specifications as Base Mobile.

£22

Radio Receiver covering FM AIR PB MW and 144-146 MHz. Suitable for above transmitters.

£20.50

Reg. P & P 45p all items
Full guarantee all items
Mail Order all items

MULHALL ELECTRONICS

Ardglass, Co. Down, U.K. BT30 7SF

Tel. 039684 461

(For use in U.K. an amateur transmitting licence is required)

4 1/2 in × 3 1/2 in METER. 30µA, 50µA or 100µA, £3.65.

MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/volt High Sensitivity Metre
£14.40.

TAPE RECORDER LEVEL METER
500µA, 70p


CARDIOID DYNAMIC MICROPHONE
Model UD-130. Frequency response 50-15,000/c/s. Impedance Dual 50K and 600 ohms.
£6.40.

MULTI-METER Model 200H
20,000 ohm/volt, **£6.60.**


3 WATT STEREO AMPLIFIER
£4.30

All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 8. Special prices for quantity quoted on request.

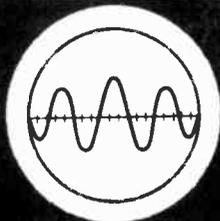
M. DZIUBAS
158 Bradshawgate • Bolton • Lancs. BL2 1BA



TUAC

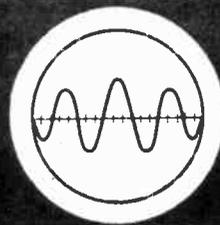

NEW TUAC POWER MODULES. Now in their third successful year offering more power and quality than ever before.

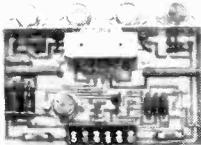

TP125

Illustrated
£17.25

- ★ 125 Watts RMS continuous sine wave output
- ★ 4 RCA 150 Watt 15 Amp output transistors
- ★ Special layer wound driver transformer
- ★ Short, open, and thermal overload protection
- ★ Compact size: 7 x 6½ x 3 in.

TL30

£9.50

- ★ 30 Watts RMS sine wave
- ★ Full thermal overload protection
- ★ Short and open circuit proof
- ★ Rugged transformer driver



TL100

Illustrated
£13.50

- ★ 100 Watts RMS sine wave
- ★ 2 RCA 15 Amp output transistors
- ★ Rugged transformer driver
- ★ Full thermal overload protection
- ★ Compact size: 5 x 5 x 3 in.

TL60

£11.75

- ★ 60 Watts RMS sine wave
- ★ RCA 115 Watt output transistors
- ★ Only six connections to make
- ★ Same size as TL100


Specification on all 4 power modules:

All output power ratings ± 0.5 dB Output impedance 8-15 Ohms. THD at full power 1% typically 0.5%
Input sensitivity 60mV into 10 k Ω . Frequency response 25Hz-25kHz ± 2 dB Hum and noise better than -70dB.

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 ± 50 volts for one TP100
PS 100 ± 45 volts for one TL100
PS 60 ± 40 volts for one TL60
PS 30 ± 50 volts for one TL30
PSU 2 for supplying Disco Mixer

£11.75
£10.75
£9.50
£7.00
£4.75

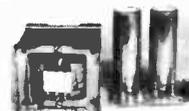

NEW FROM TUAC !!!

Rotary Flashing Beacons

100W 2 x 12 Disco Group cabs, fitted 2 50W RMS super heavy duty speakers £66.00 (carr. £1.00)
100W 4 x 8 P.A. Cols, fitted 4 75W heavy duty speakers. £75.00 pair (carr. £2.00).

- ★ 240V mains operation
- ★ Choice 5 colours, red, amber, blue, green and clear
- ★ Light source is from standard SBC filament bulb
- ★ Flash rate 140 per minute. Only £22.00

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED. JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS.



TUAC DISCOTHEQUE MIXER WITH AUTO FADE


Designed for the discerning D.J. of professional standard

Offering a vast variety of functions

Controls: Mic Vol Tone Over-ride depth. Auto Manual Sw Tape Vol. L & R Deck Faders Deck Volume Treb. and Bass. H. Phon Vol Selector Master Vol. on/off sw Max output 1V RMS Specification as VA06

£27.00

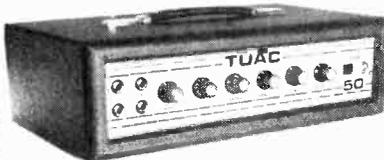TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last



50 WATT RMS SINE WAVE
ALL PURPOSE AMPLIFIER

Suitable for Disco PA. Guitar 4 inputs 2 volume controls Master volume treble middle and bass controls Rugged circuit rugged leathercloth covered case short and open circuit protection. Tone control specification as VA08 pre-amp FULLY FUSED



50 WATT £44.00

100 WATT £66.00

100 WATT SLAVE £49.50

TUAC MAIN DEALERS

BRISTOL DISCO CENTRE, 86 Stokes Croft, Bristol 1. Tel. Bristol 41666.


CALBARRIE AUDIO, 38 Cromwell Road, Luton, Beds. Tel. Luton 411733.

SOCODI, 9 The Friars, Canterbury, Kent. Tel. Canterbury 60948.

W.E.C. LIGHTING LTD., 35 Northam Road, Southampton, Hants. Tel. Southampton 28102.

CALLERS ONLY PLEASE

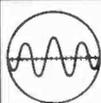MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.



TUAC

TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD. (DEPT. E)
163 MITCHAM ROAD LONDON SW17 9PG
01-672 3137/9080

R T V C FOR AUDIO ON A BUDGET

PUSH BUTTON CAR RADIO KIT



The Tourist II

**NO SOLDERING
REQUIRED!**

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

Technical specification:

- (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth.
- (2) **Integrated circuit** output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4 $\frac{5}{16}$ " deep approx

Car Radio Kit £7.70 + 55p post. & pack.

Speaker including baffle and fixing strip
£1.65 + 23p postage & packing

Car Aerial Recommended – fully retractable and locking
£1.35 post paid

STEREO 21



QUALITY SOUND^(*) FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, – no soldering required. Includes:—

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:—

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout.

Provision for auxiliary inputs – radio, tape, etc., and outputs for taping discs. **Overall Dimensions**. Speakers approx.

15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position

approx. 15 $\frac{1}{2}$ " x 12" x 6". Complete only **£18.95**

Extras if required.

Optional Diamond Stylus **£1.37**

£1.60 p & p.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs * 4 Electrically Mixed Inputs * 3 Individual Mixing controls. * Separate bass and treble controls common to all 4 inputs * Mixer employing F.E.T. (Field Effect Transistors). * Solid State Circuitry. * Attractive Styling.

INPUT SENSITIVITIES

—Input—1.) Crystal mic. guitar or moving coil mic. 2, and 10 mV. (selector switch for desired sensitivity.—Inputs—2), 3), 4. Medium output equipment—ceramic cartridge, tuner, tape recorder, organs etc.


— all 250mV sensitivity.

AC Mains 240V. operation.

Size approx. 12 $\frac{1}{2}$ " ins x 6 ins x 3 $\frac{1}{2}$ " ins

£15.00 + 60p. post & pack

DISCO 50

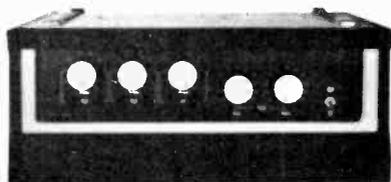

45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 $\frac{1}{4}$ " x 10 $\frac{1}{2}$ " x 8ins. approx. Amplifier **£27.50 + £1.50 p. & p**

Special Offer: Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). **Complete £57.00 + £4.00 p&p.**

COMPLETE (*) STEREO SYSTEM



£51.00

40 Watt Amplifier.
Viscount III - R102 now 20 watts per channel.
System I includes.
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/ stereo on/off function and bass and treble filters. Plus headphone socket.

Specification
20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0-1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within 1dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power).
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble -12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.
Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2".

Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.
Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 1/2" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter 10 watts handling

Complete System £51.00

£69.00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 (As System I)
Two Duo Type IIIA matched speakers - Enclosure size approx. 31" x 13" x 11 1/2". Finished in teak veneer. Drive units approx. 13 1/2" x 8 1/2" with 3 1/2" HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £69.00

PRICES: SYSTEM 1
Viscount III R 102 amplifier £24.20 + £1 p & p
2 Duo Type II speakers £14.00 + £2.20 p & p
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover £21.00 + £1.75 p & p.
total £59.20

Available complete for only £51.00 + £3.50 p. & p.
PRICES: SYSTEM 2
Viscount R102 amplifier £24.20 + £1.00 p. & p.
2 Duo Type IIIA speakers £39.00 + £4.00 p. & p.
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover £21.00 + £1.75 p. & p.
total £84.20

Available complete for only £69.00 + £4 p & p.

EMI SPEAKERS AT FANTASTIC REDUCTIONS

THE ULTIMATE COMPLETE SPEAKER SYSTEM
EMI LE 315 List Price £86.00



A professional standard five way speaker system with enclosure giving top quality performance
Enclosure Dimensions approx. (3ft. x 2ft. x 1ft.).
Drive Units
Hand built - 15" diameter bass with 3" voice coil, - two 5" diameter Mid Range units, - two 3 1/2" HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.
Power Handling
Continuous rating 35 W rms., Peak power rating 70 W.
Frequency Response
20 Hz 20,000 Hz. Imp. 8 ohms.

Our price £45.00 + £3.50 p. & p.



15" 14A/780 BASS UNIT
Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.
OUR PRICE £18.70 + £1.50 p & p + £1.50 p & p Special Offer



**950
KIT**

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz. Hugs 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3 1/2" dia approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00. **OUR PRICE £19.50**



BUILD YOUR OWN STEREO AMPLIFIER (*)

For the man who wants to design his own stereo - here's your chance to start with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£7.64 + 55p. p & p



8 TRACK CARTRIDGE PLAYER (*)

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification: Mains input, 240V, Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx.

Yours for only £10.95 + 90p. p & p



Just write your order giving your credit card number

**DO NOT SEND
YOUR CARD**

● Mail orders to Acton. Terms C.W.D.
All enquires Stamped Addressed Envelope.
Goods not despatched outside U.K.


● Leaflets available for all items listed thus (*)
Send stamped addressed envelope.

R T V C

Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG/D
323 Edgware Road, London W2

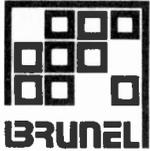Personal — Edgware Road: 9a.m.-5.30p.m. Half day Thurs.
Shoppers — Acton: 9.30 a.m.-5 p.m. Closed all day Wed.



**Brunel
Technical College
Bristol**

Ashley Down, Bristol BS7 9BU

Faculty of Communications

Radio and Electronic Officers

Interested in seeing the world and earning a good salary at the same time? There are excellent career prospects as a Marine Radio Officer and in the Civil Service. Full-time Courses in Radiocommunications, Radar and Marine Electronics start in September and January of each year.

Civil Aviation

Full-time Courses start in September of each year for prospective Licensed Aircraft Maintenance Engineers in either the Radio Category or in Airframes and Engines. The Courses are fully approved by the CAA and include practical work on College Aeroplanes.

Course Entry Requirements



Prospective entrants should have obtained CSE or GCE Ordinary level passes in Mathematics, English and a Science subject, or have appropriate experience. All applicants will be interviewed before acceptance.

For further details of the above and of Courses for experienced Marine and Aeronautical personnel please contact:
Mr. F. E. Bartrop, Head of Department of Marine and Aero Electronics, Brunel Technical College, Ashley Down, Bristol BS7 9BU. Tel. (0272) 41241

**10 WATTS PER CHANNEL RMS
STEREO AMPLIFIER**

at less than 0.1% distortion. Max. RMS output in excess of 15 watts per channel.

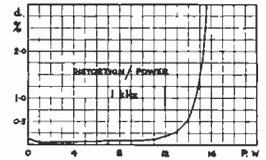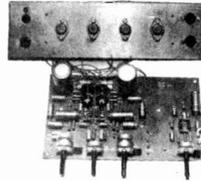- * 4-16 ohm Load
- * 15-50 kHz (-1dB)
- * 40 dB NFB
- * 150 mV input



Completely assembled PCB using top grade components (plus backplate/heatsink) including balance volume and tone controls plus mono-stereo switch. Operates from 22-24V d.c. Board also includes a single 2-stage mic. or guitar pickup preamp. (2 x BC149). Instructions are included for a simple mod. to adapt this for stereo operation giving 150mV at 1M ohm sensitivity. Full circuit supplied.

FANTASTIC AND UNREPEATABLE BARGAIN.
£9.90 plus 60p P. & P., inc. VAT. Power supply components to operate from the mains available, add £2.90 inc. VAT.

EDRICK ELECTRONICS LTD.

(DEPT. P6)

164 HIGH STREET, BARNET, HERTS.

GLUM?

SICK OF WAITING FOR COMPONENTS

Try our express service (normally return of post)

Prices very competitive — for example:—

- ½W 5% carbon film resistors — 1p.
- ½W 2% metal oxide — 3½p.

BC 107/8/9 — 10p	2N 3704 — 13p.
BC 177 — 17p.	2N 3707 — 13p.
2N 1302/3 — 16p.	1N 4001/2 — 6p.
2N 3055 — 53p.	1N 4003/4 — 7p.
2N 3702 — 13p.	1N 4148 — 5p.
2N 3703 — 14p.	1N 5401 — 16p.

SINCLAIR CAMBRIDGE CALCULATOR

Ready to use—only £26.50


PRICES EXCLUDE VAT. 10P P. & P.

Forward 15p for our illustrated catalogue to:—
DART ELECTRO SERVICES, 24 South Town,
Dartmouth, Devon. Competitive prices and descriptions of hundreds of components, accessories etc.

Name:

Address:

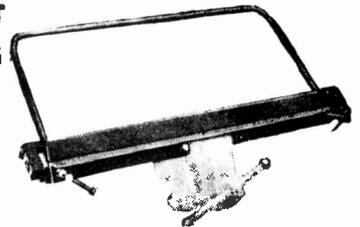**PARKERS SHEET
METAL FOLDING
MACHINES
HEAVY VICE
MODELS**



With Bevelled Former Bars

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £21 carr. free
 - No. 2. Capacity 18 gauge mild steel x 24in. wide ... £15 carr. free
 - No. 3. Capacity 16 gauge mild steel x 18in. wide ... £15 carr. free
- Also new bench models. Capacities 36in. x 18 gauge £40. 24in. x 16 gauge £38. Carriage free. Add 10% VAT to total price of machine.
End folding attachments for radio chassis. Tray and Box making. Steel Angle 36in. model, 40p per. ft. Other models 30p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.
A. B. PARKER, Folding Machine Works, Upper George St., Hedmondwike, Yorks. Telephone 403997



**CONTACTLESS ELECTRONIC
IGNITION BY MOBELEC**

FROM ONLY £13.95 p.p.p. 25p

We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year. Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 and 6 cylinder NEG. AND POS. EARTH. £22.82. 8 cyl.. £24.75. Post free.

SILHILL PRODUCTS

Dept. PE/6, 226 Mary Street, Birmingham B12 9RJ. Tel. 021-440 3600

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15 These fine motors are easily reversed starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC. to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120r 50Hz. Speed 60 rpm at 60Hz. 72 rpm. STEPPING Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia 4" body length 4 1/2" spindle length 2 1/2" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. OUR PRICE ONLY £15

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant ideal for P.C. boards. Size 12" x 12" 24" x 12" 24" x 24". FULL SHEET 43" x 37" (11 sq ft.) Single-sided Copper with thickness of 3/64". Also double-sided 3/64" x 3/64" £1 per sq ft. Cut sizes 11-10 sq ft 1.25p P & P. Full Sheet £8 each. Carr £1 for 1st sheet plus 25p each additional sheet.

SMITHS RINGER-TIMER



Reliable 15 minute times. spring wound (concurrent with time setting) 15 x 1min divisions. approximately 1/2 between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω. output 60 or 80 DB at 1 Kc. As used in deaf aids, bugling device, etc. Size (60 DB) 1/4" x 1/4" x 1/4" (80 DB) 1/4" x 1/4" x 1/4". Ex-equipment all tested £1.20 each P & P. FREE

Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 V a.c. Very powerful and silent running. 5/8" dia 3" inlet dia. Outlet flange 3" x 2 1/2". Limited number only £8.95. P & P 40p


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged elbow. Bracket incorporates 2 fixing screws. Length of arm 2 1/2". 240V AC. Pull at coil is approximately 1lb. £1. FREE P & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

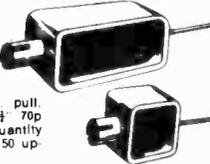240AC type MM6 3lb pull. 2 1/2" x 1 1/2" Travel 1" 90p each P & P 10p
240AC type MM4, 2lb pull. 1 1/2" x 1 1/2" x 1" Travel 1/2" 70p each P & P 10p. Quantity discounts 10-50 10%, 50 up wards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC. 28rpm. NEW HIGH TORQUE approx overall size 3 1/2" x 3 1/2" x 2 1/2" - spindle 1/2" dia. as illustrated £2.70. P & P 30p. Similar to above. 19rpm £2.70. P & P 30p. 110rpm with pressed steel gear case (similar to above but SLIGHTLY SMALLER). £2.70. P & P 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v, 1amp at 240v. Size: (approx.) 1 1/4" long x 1/2" dia. Ideal for burglar alarms, security systems etc. and wherever non-mechanical switching is required. 10 for £2.10. P & P 15p. 50 for £8.100 for £15.50. FREE P & P. over 10

AMPEX 7-5V. D.C. MOTOR

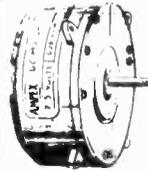


An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 50ma on run. 800rpm = speed adjustment. Internal AF/RF suppression. 1/2" dia x 1" spindle, motor 3" dia x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P & P 25p. Quantities available. Mu-metal enclosure available 75p each. FREE P & P.

ALL PRICES INCLUDE V.A.T. Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

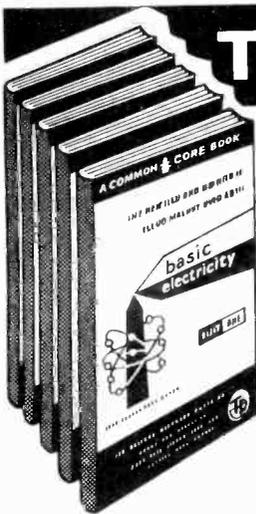315/317, EDGWARE ROAD, LONDON, W2. Tel: 01-723 5667 01-402 5580



The Pictorial Method

BASIC ELECTRICITY (5vols) ELECTRONICS (6vols) TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

WHAT READERS SAY

Delighted with the excellent publication. As a retired electrical engineer, Electronics is a new field for me to take up as a hobby. H.W., Leamington

Although they are very instructive they are very easily and quickly read. L.T., Swansea

Many thanks indeed including my own and heartiest appreciation of a fine set of volumes and at such an almost nominal price. B.L., Trowbridge

Having studied the first volume I find that learning about a subject which seemed almost out of reach has now become a relatively simple matter. H.F., Coventry

I am extremely satisfied with these fine books. C.K., Swindon

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....
 BASIC ELECTRICITY 5 parts £5.30
 BASIC ELECTRONICS 6 parts £6.40
 BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
 BLOCK LETTERS
 FULL POSTAL.....
 ADDRESS

POST NOW FOR THIS OFFER!

SPARKRITE Mk II

Electronic Ignition... Better on all points



Because you keep your points!

The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly — with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of normal, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Cleaner plugs — they last 5 times longer without attention.
- Faster acceleration. ● Faster top speeds.
- Coil and battery last longer. ● Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system and 6 page installation instruction leaflet.

WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite Mk II — full capacitive discharge electronic system — not just a transistorised inductive discharge booster

PRICES

D.I.Y. Kit only £11.62 incl. VAT and P & P
 Ready Built Unit £14.85 incl. VAT and P & P
 (Both to fit all cars with coil/distributor ignition up to 8 cylinders).
 We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition.
 Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES
 (Dept P E 8) 82 Bath Street,
 Walsall WS1 3DE Phone 33652

Please supply:

- Sparkrite Mk.2 D.I.Y. Kit(s) at £11.62 each incl. VAT and P & P (Will make pos. or neg. earth).
- Sparkrite Ready Built Neg. Earth Unit(s) at £14.85 each incl. VAT and P & P
- Sparkrite Ready Built Positive Earth Unit(s) at £14.85 each incl. VAT and P & P

NAME _____

ADDRESS _____

I enclose cheque/P.O. for £ _____
 Send SAE for brochure.

FERRIC CHLORIDE

Anhydrous to Mil-spec in 1lb sealed packs. 1lb 55p (20p). 3lb £1.32 (30p). 10lb £3.85 (60p)

VERSATILE POWER UNIT

Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1.7-10.5V output with 2 extra capacitors. Brand new. Only 83p (20p). Also available in a toy garage with press switch lamp, etc (Used for 'Hot Wheels') Only £1.65 (30p)

AMPLIFIER UNIT

In fully screened case 5 1/2 in x 5 in x 3 in 2 GET116 on heat sink. 2 zeners. 3 pot cores. 4 small transformers. 1% R.S. C.s. etc 70p (30p) with circuit

3W CASED AMPLIFIER

Polished wooden cabinet 14 in x 13 in x 9 in containing a sensitive (20µV) 4 valve amplifier with tone and volume controls. Gives 3 watts output to the 7 in x 4 in 3Ω speaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation. £3.50 (£1). Suitable cassette £1.10 (30p). Spare head 33p. Tape (ex-computer) 75p (20p). Amplifier chassis only, complete and tested (2 x ECC83 EL84, EZ80) — speaker £2.50 (40p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, pots, switches, + PC boards with transistors and diodes, also crystals and loads of odds and ends. Amazing value. £1.82 (40p).

Scopes in stock for callers, ring for details. S.A.E. List. All prices include VAT Carriage in brackets, small parts 5p

GREENWELD ELECTRONICS (PE5)

51 Shirley Park Road, Southampton

New wholesale/retail shop and mail order department. Other retail shops at 38 Lower Addiscombe Road, Croydon (Tel. 01-688 2950) and 21 Deptford Broadway, SE8 (Tel. 01-692 2009)

DEKATRON UNITS

Contain 2 CV2271 dekatrons. 2 4-digit electro-magnetic resettable counters. 2 sealed relays. 2 x ECC81. R's. C's etc. Only £1.70 (30p)

COMPUTER PANELS

31b asstd £1.10 (30p). 71b £2.20 (40p). 551b £12 (£2). 12 high quality panels with IC's, power transistors, trim pots etc. £2.20 (30p). 100 £13 (£1). Panel with 7 2kΩ trimpots 33p (10p) Pack containing 50 14 pin DIL IC's, inc. 7400, 04, 10, 20, 30, 7474, etc., also MC types £2.20 (20p)

COMPONENT PACKS

500 asstd resistors £1.10 (20p). 2 500 £4 (50p). 10 000 £13 (£1). 100 000 £88 — carr. 150 poly. ceramic, mica caps 66p (10p)

NEW COMPONENTS

400V 5A SCR 66p; 200V 44p; OC71 9p; 14 for £1.10; OC81D 8p; 100 £5 50; 741C TO99 35p; 2N3055 38p; 723C 77p (Data Book 10p); 710C 33p; CA3026 88p; SC40D 11ac £1; 3A 100 V Rec. 16p; 05 500V discs. 100 for £1.65; 80 + 200V 350V 10p; 10 for 83p (30p); 8µF 2 500V £2.20 (50p). 4-pole 8-way Yaxley switches 33p (8p); 2-pin DIN plug 10p; 5-pin 180° 11p; 3.5mm plug 8p; phono 5p; 7-pin DIN plug 11p; 6-pin DIN plug 11p; speaker cable spigette 4-core individually screened 20p metre

TRANSFORMERS

Mains Pri., 16-0-16V 1 1/2A. Sec with 9V tap. £1.85 (30p). Mains Pri., 360V at 375mA, 260V at 75mA, 6.3V at 1A, 6.3V at 4A. £2.20 (60p)

VARICAP TUNER

- LP1185/86 £10.25/pair
- MC1310P Decoder I/C £3.15
- LP1400 Decoder Module £5.15
- MFC4060 Regulator I/C £0.78
- P.C. BOARDS MC1310P or LP1400 £1.87

(state which decoder)

READY BUILT BOARDS £24.25 (I/C) or £25.25 (LP1400)

Prices include V.A.T. P. & P. 25p.

B. & B. ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK, NOTTS.
 Tel.: NEWARK 6895 (Anytime)

BAKER 12" MAJOR £11-55

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £14.85

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19 in x 12 in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

- Regent 12 in. 15W £10.45 Superb 12 in. 20W £18.70 New Group 50/12
- Major 12 in. 20W £11.55 Group 25 12 in. 25W £10.45 12 in. 50W
- Deluxe 12 in. 15W £13.20 Group 35 12 in. 35W £11.55 30-18000 cps. £17.60

BAKER LOUDSPEAKER CO., BENSAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684-1665
 PRICES INCLUDE VAT. HI-FI ENCLOSURE PLANS 42p



AMMS

and make no mistake

**LASKY'S
SUMMER SALE
AN EXTRA
10% OFF
ALL THESE PRICES
DURING JULY**

AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £3.25 P&P 15p

AUDIOTRONIC Model ATM5

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). 0.300 uA/0.300mA DC. Resistance: 10 & 8 x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £3.50 P&P 15p

MODEL TH12

20,000 opv. Overload protection. Slide switch selector. 0/0.2/5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50uA/25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.



OUR PRICE £5.95 P&P 30p

HIOKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA DC. 0-20k/2 Megohms.



OUR PRICE £5.97 P&P 30p

MODEL PL436

20,000 opv DC. 8000 opv AC. Mirror scale. Ranges: 6/3/12/30/120/600V DC. 3/30/120/600V DC. 50/600uA/60/600mA. 10/100k/1 Meg/10 Meg Ohm. -20 to 46 dB.



OUR PRICE £6.97 P&P 30p.

U4323 MULTIMETER

20,000opv. Simple unit with audio/1F oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5.5/50/500mA DC. Resistance x 10, x 100, x 1,000, x 10,000 (50k). 500g, 5kG, 50kG (centre scale). Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £7.00 P&P 30p

MODEL HIOKI 730X

30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60/uA/30mA/300mA. 2K/200K/2 Meg Ohm. Decibels: -10 to +63dB.



OUR PRICE £7.50 P&P 30p.

U4324 MULTIMETER

High sensitivity, overload protected. 20,000opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance. 25/500 ohms/0.5/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £8.00 P&P 30p

U435 MULTIMETER

20,000opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/5/2/5/25A DC. 5/25/100mA/0.5/2.5A AC. Resistance: 0.3/3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and self carrying case.



OUR PRICE £8.75 P&P 30p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 6670 opv. 0/0.3/1.5/5/30/60/90V DC & 75mV/0/0.3/1.5/5/30/60/90V AC. 0/300uA/1.5/6/15/150/60/60mA/1/1.5/6A DC. 0/1.5/6/15/60/150/600mA/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer. Metal carrying case. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £9.75 P&P 50p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 263 x 94 x 36mm. Complete with carrying case, leads and fuses.



OUR PRICE £10.50 P&P 30p

HIOKI 750X VOLT-OHM-MILLIAMETER

43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1,200V DC. 0-3/6/15/30/60/120/300/600/1,200V AC. Current: 0-30/60uA/1.5/3/15/30/150/300 mA/6/12A. Resistance: 0-3/300k/3/30Megohms. Decibels: -10 to +17dB. Output: 0-3/6/15/30/60/120/300V. Accuracy ± 3% DC, ± 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £11.95 P&P 40p

MODEL 500


30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 10/50uA/5/50/500mA, 12A DC. 0/60k/6 meg/60 megohms.



OUR PRICE £13.95 Carr. paid Leather case for above £1.75

HIOKI MODEL 700X

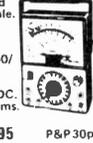100,000opv. Overload protection. Mirror scale. 0.3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/300mA/5/12A DC. -20 to +63dB.



OUR PRICE £14.95 P&P 30p

Model HT100B4 MULTIMETER

Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Battery current: 0.5/2.5/1.5/5/25/50/100/250/500/1000V DC. DC resistance: 0-20/200k/2/20 Meg. ohms. DC current: -10/250uA/2.5/25/250 mA/10A. AC current: 0-10A. -20 DC, 1% AC. Size: 180 x 134 x 79mm.



OUR PRICE £17.50 P&P 40p

MODEL AS. 1000 VOM

100,000 opv Mirror scale. Built-in meter. Protection: 0.3/12.60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA/12 Amp. 0/2k/200k/2M/20 Meg Ohm. 20 to 17dB



OUR PRICE £17.50 P&P 30p.

KAMODEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors. S.C.P.'s etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.



OUR PRICE £17.50 P & P 40p

KAMODEN 360 MULTIMETER


High sensitivity. DC 100kohm/V AC 10kohm/V 5" mirror scale, overload protected. Ranges: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100k ohms. Decibels -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads.



OUR PRICE £17.50 P & P 40p

TMK 100K LAB TESTER

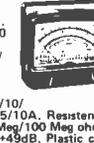100,000opv. 6 1/2" scale. Buzzer short circuit check. Sensitivity 100,000 opv DC. 5k/V AC DC Volt: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. current 10/100uA/10/100/500mA/2.5/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: -10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 98mm.



OUR PRICE £19.95 P&P 30p

370WR MULTIMETER

Features AC current ranges, 200,000opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 10/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg/500k/2.5 Meg/200 Megohms. Decibels: -20 to +62dB.



OUR PRICE £19.95 P&P 30p

KAMODEN 72.200 Multitester


High sensitivity tester. 200,000 opv Overload protected. Mirror scale. Ranges: 0.6/1.2/60/1.2/30/120/600/1200V DC. 0/3/12/60/300/1120V AC. 0.6uA/1.2mA/120mA/600mA/12A DC 0/12A AC. -20 to +63dB. 0/200/2 Meg/200 Megohms.



OUR PRICE £22.50 P & P 30p

U4317 MULTIMETER

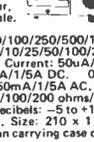High sensitivity instrument for field and laboratory work. Knife edge pointer. 36mm. mirror scale. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1.5/10/50/250mA/1.5A DC. Resistance: 0.5/10/100/200 ohms/1/3/20 Meg. Decibels: -3 to +100dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



OUR PRICE £15.00 P&P 40p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC, 1% AC. Scale length: 165mm. 0/300/750uA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5A DC. 0/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V DC. 0/750/1500V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.



OUR PRICE £49.00 P&P 50p

TE65 VALVE VOLTMETER

28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. Resistance up to 1000 Megohms, 200/240V AC operation. Complete with probe and instructions.



OUR PRICE £17.50 P&P 50p

LB3 TRANSISTOR TESTER

Tests ICO and B. PNP/NPN. Operates from 9V battery. Instructions supplied.



OUR PRICE £3.95 P&P 20p

MODEL AF.105 VOM


50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V DC. 0/30uA/6/60/300 mA/12 Amp. 0/10K/1M/10M/100M Meg Ohms -20 to 17 dB.



OUR PRICE £12.50 P&P 30p.

LB4 TRANSISTOR TESTER

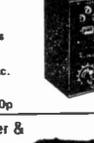Tests PNP or NPN transistors. Audio indication. Supplied complete with instructions etc. Operates on two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.50 P&P 20p

U4341 Multimeter & Transistor Tester

27 ranges. 16,700opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA/3A AC. Resistance: 0.05/0.6/2/6/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and self carrying case. Size: 115 x 215 x 90mm.



OUR PRICE £10.50 P&P 30p

S100TR MULTIMETER TRANSISTOR TESTER

100,000opv. Mirror scale. Overload protection. 0/0.1/2/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/6/30/120/600uA/12/300mA/6/12A DC 0/10k/1 Meg/100 to +50dB. 0.01-0.2 MFD Transistor tester measures Alpha, Beta and Ico. Complete with instructions, batteries and leads.



OUR PRICE £19.95 P&P 25p

KAMODEN HMG50 insulation resistance tester

Range 0-1,000 Megohms. 500V Battery operated. Wide range clear meter 4" x 4 1/2". Complete with deluxe carrying case, batteries and instructions.



OUR PRICE £19.95 P&P 30p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP. Bandwidth: 100MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25; HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-300µsec. Free running 200-2000 kHz in nine ranges. Calibrator pins. 220 x 360 x 430mm. 115-230V AC.



OUR PRICE £39.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2µsec. to 100 milli-sec/cm. Free running time 1-300MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied with all accessories and instruction manual.



OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip. Oscillates. Attenuation Wave Meter and Oscillating Detector. Frequency range 40kHz-280kHz in six coils. 500uA meter. 9V battery operation. Size: 150 x 80 x 40mm.



OUR PRICE £19.95 P&P 30p

Also see following pages
ALL PRICES EXCLUDE VAT

SWR METER Model SWR3

Handy SWR meter for
transm., or antenna align-
ment, with built-in field
strength meter. Accuracy
5%, impedance 52. Full
scale 5 section coil readable
antenna. Size 145 x 50 x
60mm.



OUR PRICE £4.25 P&P 30p

AT201 Octade ATTENUATOR

Frequency range 0-
200kHz. Attenuator
0-111dB, 0.1dB
steps. Impedance 600 ohms. Input
power maximum 30dBm. Size: 180 x
90 x 55mm.



OUR PRICE £12.50 P&P 50p

TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE

A new portable
bridge offering
excellent range and
accuracy at low
cost. Resistance: 6
ranges: 0.1
ohm-11.1 megohm ± 1% Inductance:
6 ranges: 1 microhenry-111
henries ± 2% Capacity: 6 ranges:
10pF-1110 mfd ± 2% Turns Ratio:
6 ranges: 1/1000-1/11100 ± 1%
Bridge Voltage at 1.000cps. Operated
from 9-volt battery. Size 71/8" x
5" x 2" OUR PRICE £25.00 P&P 30p

TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz
-50 MHz. An
inexpensive
instrument for the
handy-man.
Operates on 9V
battery. Wide
easy to read
scale. 800kHz
modulation.
Size: 149 x 149 x 92mm. Complete
with instructions and leads.



OUR PRICE £8.97 P&P 30p

MODEL TE20 RF SIGNAL GENERATOR

Six bands, 120kHz-
260MHz. Dual output
RF terminals. Separate
variable audio output.
Accuracy ± 2%. Audio
output to 8V. Power requirements:
106-125V, 220-240V AC. Size: 193
x 265 x 150mm. Complete with test
leads etc.



OUR PRICE £17.50 P&P 50p

TE-20D RF SIGNAL GENERATOR

Accurate wide range
signal generator
covering 120 kHz-500
MHz on 6 bands.
Directly calibrated.
Variable R.F.
attenuator audio output. Xtal socket
for calibration. 220/240V a.c.
Brand new with instructions.
Size 140mm x 215mm x 170mm
OUR PRICE £17.50 P&P 50p



TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to
200kHz. Output
on 4 bands.
Square 20
cps to 30
kHz. Output
impedance
5000 ohms.
200/250V
AC operation. Supplied brand new
guaranteed, with instruction manual
and leads.



OUR PRICE £24.95 P&P 50p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised
compact fully
portable. AF sine
wave 18Hz to 220
kHz. AF square
wave 18Hz to 100k
Hz. Output Square/
Sine wave 10V.
P.P. RF 100kHz to
200MHz. Output
1V maximum.
220/240V AC operation. Complete
with instructions and leads.




OUR PRICE £37.50 P&P 50p

Also see previous page

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR

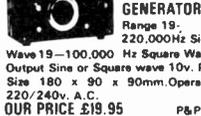Wave 19-100,000 Hz Square Wave.
Output Sine or Square wave 10V. P. to P.
Size 180 x 90 x 90mm. Operation
220/240V AC.
OUR PRICE £19.95 P&P 60p



PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable
output 5-20V DC
up to 2 Amp. Inde-
pendent meters to
monitor voltage and
current. Output
220/240V AC.
Size 190 x 136 x
98mm.
OUR PRICE £19.95 P&P 50p



POWER RHEOSTATS

High quality ceramic
construction. Wind-
ings embedded in
vitreous enamel.
Heavy duty brush
wiper. Continuous
rating. Wide range
available ext stock.
Single hole fixing. 1/2" diameter shafts.
Bulk quantities available.



25 WATT 10/25/50/100/500/1000/
250C ohms. £1.15 P&P 10p

50 WATT 10/50/100/250/500/
1500/5000 ohms. £1.62 P&P 10p

100 WATT 1/5/10/25/50/250/500/
2500 ohms 100 Ohms £2.34 P&P 15p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input:
230V 50/60Hz. Output 0-260V.
MODEL S260 BENCH MOUNTING

	P&P
1A £10.50	50p
2.5A £12.00	50p
5A £17.50	50p
8A £30.35	£1.00
10A £33.75	£1.00
12A £35.40	£1.00
20A £85.00	£1.50
25A £90.00	£1.50
40A £120.00	£1.50

MODEL S260B PANEL MOUNTING

1A	£10.00	50p
2.5A	£12.00	50p




240° Wide Angle 1mA METERS

MW 1-6 60x60mm
£6.50 P&P 15p



CP110 CHASSIS PUNCH SET

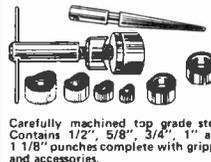Carefully machined top grade steel.
Contains 1/2", 5/8", 3/4", 1" and
1 1/8" punches complete with gripper
and accessories.
OUR PRICE £3.00 P&P 40p




HITACHI FLUORESCENT LANTERN L191

A portable battery
operated lantern
ideal for home,
motoring, camping
etc. Approx 10"
tall. Provides
brilliant light from 9
1.5v batteries (not
supplied).
OUR PRICE £7.19 P&P 50p



KE630 3 Station INTERCOM

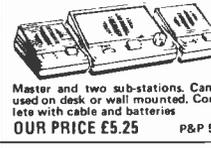Master and two sub-stations. Can be
used on desk or wall mounted. Com-
plete with instructions and cables.
OUR PRICE £5.25 P&P 50p



SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER

complete with
printed circuit
mounting board.
OUR PRICE £2.35 P&P 15p.



DT55G DIGITAL CLOCK MECHANISM

Features
24 hour
alarm
setting,
on/off
alarm 'sleep' switch. Illuminated rotary
dial with hours, minutes and sec-
onds. Automatically turns off radio,
TV, light etc. and with auto-switching
will turn on again when required.
240V AC operation. Switch rating
250V-3 Amp.
OUR PRICE £5.95 P&P 30p



SUMMER SALE
AN EXTRA
10% OFF
ALL THESE
PRICES
DURING JULY


LH025 STEREO HEADPHONES

Light weight head-
phones with padded
ear pieces. 4/16 ohms
20-20,000Hz.
Complete with 6'
lead and plug.
OUR PRICE £1.97 P&P 30p



DH025 STEREO HEADPHONES

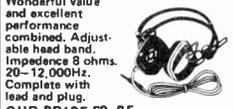Wonderful value
and excellent
performance
combined. Adjust-
able head band.
Impedance ohms.
20-12,000Hz.
Complete with
lead and plug.
OUR PRICE £2.25 P&P 30p



TE1035 Stereo HEADPHONES

Low cost with ex-
cellent response. Foam
rubber cups. Adjust-
able headband, 8 ohms
impedance. Frequency
response 25Hz-18kHz.
Complete with cable
and stereo jack plug.
OUR PRICE £2.60 P&P 30p



SH80V MONO/STEREO HEADPHONES

Volume control for
each channel. 4/16 ohms
impedance. Frequency
response 20Hz-18kHz.
Complete with 10ft.
coiled lead and jack plug.
OUR PRICE £4.97 P&P 30p



BH001 HEADSET and Boom Microphone

Moving coil. Ideal
for language
teaching, 10ft.
communications
etc. Headphone impedance 16 ohms. Micro-
phone impedance 200 ohms.
OUR PRICE £5.95 P&P 30p



EMI LOUDSPEAKERS

Model 350 13 x 8" with
single tweeter/crossover.
20-20,000Hz. 15 watts
RMS. Available 8 or 15 ohms.
OUR PRICE
£7.50 each P&P 37p
Model 450 13 x 8" with
twin tweeter/crossover.
55-11,000Hz. 8 watts
RMS. Available 8 or 15 ohms.
OUR PRICE £3.62 each P&P 35p



SPECIAL PURCHASE LIMITED QUANTITY!

Tannoy 12" DR/8
Bass Speakers
8 ohms 30 watt
Heavy duty, ideal
for Hi-Fi P.A.
Group
OUR PRICE £12.50 P&P 50p



SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS

High quality 2 way speaker systems.
25 Watts. 4-8 ohms. 40Hz-18kHz.
Size: 560 x 340 x 255mm. approx.
Wood grain finish with black fronts.
OUR PRICE £26.95 PR. P&P £1



SPECIAL BARGAIN !! STEREOSOUND SPEAKERS

Matched pair of
stereo bookshelf
speakers. Deluxe
teak veneered
finish. Size:
368 x 229 x
190mm. 8 ohms.
8 watts RMS. 16
watts peak.
Complete with
Din lead.
OUR PRICE £12.95 P&P 50p



FM TUNER CHASSIS

6 transistor
high quality
tuner. Size
only 153 x
101 x 63mm
3 IF stages.
Double tuned
discriminator.
Amps output to feed most amplifiers.
Operates on 9V battery. Covers 88-
108MHz. Ready built, ready for use.
Fantastic value for money.
OUR PRICE £8.95 P&P 20p
Stereo Multiplex Adaptor to 95 extra



Model A1018 FM TUNER

6 transistor high
quality unit.
3 IF stages and
double tuned
discriminator.
For use with most amplifiers. Covers
88-108MHz. Powered by 9V battery.
OUR PRICE £13.50 P&P 30p
Stereo multiplex adapter £9.55 extra.




SINCLAIR "SCIENTIFIC" CALCULATOR

8 digit display. Four
functions plus
logarithms to base 10,
antilog, sine, cosine,
tangent, arc sine,
arc cosine and
arc tangent.
Complete with
instructions, case and
batteries. Rec. Price
£49.00
OUR PRICE £44.50
P & P 25p plus VAT.



SINCLAIR SYSTEM 2000 STEREO AMPLIFIER AND TUNER

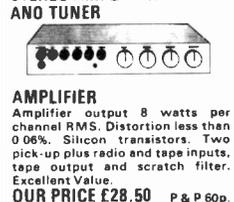Amplifier output 8 watts per
channel RMS. Distortion less than
0.05%. Silicon transistors. Two
pick-up plus radio and tape inputs,
tape output and scratch filter.
Excellent Value.
OUR PRICE £28.50 P & P 60p.



AMPLIFIER

Amplifier output 8 watts per
channel RMS. Distortion less than
0.05%. Silicon transistors. Two
pick-up plus radio and tape inputs,
tape output and scratch filter.
Excellent Value.
OUR PRICE £28.50 P & P 60p.



FM TUNER

Excellent selectivity and sensitivity.
Twin dual-varicap tuning.
4 pole ceramic filter. 19 transistor
stereo demodulator giving 40 dB
separation. Distortion 0.2% output.
Fantastic Value.
OUR PRICE £28.50 P & P 60p.



SINCLAIR Project 80 Modules

Z40 Power Amp..... £5.45 P & P 15p
Z50 Pre Amp..... £8.95 P & P 15p
Stereo 80 Pre-Amp..... £11.95 P & P 15p
Active Filter Unit..... £6.95 P & P 15p
Project 805..... £26.95 P & P 50p
P2 Power Supply..... £4.98 P & P 30p
P2B Power Supply..... £7.98 P & P 30p
Transformer for P2B, £4.05 P & P 50p
SINCLAIR Project 80 Packages
2 x Z40/Stereo 80/P25..... £25.00
2 x Z50/Stereo 80/P25..... £27.75
2 x Z60/Stereo 80/P2B..... £30.45
POST & PACKING 35p each.



AUDIOTRONIC AH101 Stereo Headphone Amplifier

All silicon,
transistor
amplifier oper-
ates from a sin-
gle ceramic
capacitor,
or tuner
inputs with
twin stereo headphone outputs and
separate volume controls for each
channel. Operates from 9V battery.
INPUTS: 5mV and 100mV.
OUTPUT: 50mV per channel.
OUR PRICE £8.50 P&P 30p



HIGH QUALITY CONSTRUCTION KITS WE ARE APPOINTED CHECKLISTS AT ALL BRANCHES

All kits are complete with compre-
hensive easy to follow instructions and
covered by full guarantee.
Post and Packing 15p per kit.

AF20 Mono amplifier.....	£4.80
AF25 Mixer.....	£3.80
AF30 Mono pre-amplifier.....	£2.81
AF35 Emitter amplifier.....	£2.27
AF80 0.5W mic. amplifier.....	£4.22
AF305 Intercom.....	£9.52
AT5 Automatic light control.....	£2.58
AT25 Window wiper robot.....	£5.82
AT30 Photo call switch unit.....	£5.70
AT50 400W triac dimmer/speed control.....	£4.80
AT56 2,200W triac light dimmer/speed control.....	£8.90
AT60 1 channel light control.....	£7.80
AT65 3 channel light control.....	£14.55
GP304 Circuit board.....	£4.94
GP310 Stereo pre-amplifier.....	£7.66
for use with 2 x AF310.....	£21.27
GP312 Circuit board.....	£11.45
GU330 Tremolo unit.....	£7.50
HF61 Diode detector.....	£3.32
HF65 FM transmitter.....	£2.70
HF70 FM receiver.....	£2.87
HF75 100kHz tuner.....	£16.81
HF325 Amplifier.....	£24.12
HF330 Decoder (HF310/325).....	£9.96
HF380 W/hifi aerial amplifier.....	£4.94
HF395 Oscillator serial amp.....	£1.77
HF390 Quartz phase meter.....	£1.36
M160 Multi-vibrator.....	£1.71
M191 VU Meter.....	£4.55
M192 200 balance meter.....	£4.97
M1302 Transistor tester.....	£8.45
NT10 Stabilised power supply 100mA, 9V.....	£8.15
NT30 Stabilised supply.....	£12.61
NT305 Voltage converter.....	£4.50
NT315 Power supply 240V AC to 4.5/15V DC, 500mA.....	£9.57

Amateur Electronics by Josty-Kit, the professional book for the amateur -covers the subject from basic prin- ciples to advanced electronic techniq- ues. Complete with circuit board for AE1 to AE10 listed below.

OUR PRICE £3.30 (No VAT)
P&P 25p plus VAT.

AE1 100mV output stage.....	£1.60
AE2 100mV amplifier.....	£1.15
AE3 Diode receiver.....	£1.82
AE4 Flasher.....	98p
AE5 Astable multi-vibrator.....	98p
AE6 Monostable multi-vibrator.....	98p
AE7 RC generator.....	97p
AE8 Bass filter.....	90p
AE9 Aerial filter.....	90p
AE10 CTR filter-amplifier.....	90p

1021 Stereo Listening Station

For balancing and
gain selection of
loudspeakers
with additional
facility for stereo
headphone
switching. Two
gain controls, speakers on-off slide
switch, stereo headphone socket.
OUR PRICE £2.25 P&P 15p



AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C80	£1.67	£3.00	£7.08
C90	£2.24	£3.50	£2.81
C120	£2.73	£5.17	£12.24

AUDIOTRONIC CrO2 CASSETTES

TYPE	5	10	25
CR60	£3.92	£7.72	£19.12
CR90	£5.32	£10.48	£26.22

AUDIOTRONIC 8 TRACK CARTRIDGES

TYPE	Each	5	10	50
40M	£0.95	£5.00	£7.50	
80M	£1.15	£5.40	£10.25	

P&P Cassettes 3p, Cartridges 5p each
OVER 10 of either POST FREE!

MP7 MIXER-PREAMPLIFIER

5 Microphone
inputs each with
individual gain
controls enabling
complete mixing
facilities. Battery operated. Size: 235
x 127 x 78mm. Inputs: Mics. 3 x 3mV
50k; 2 x 3mV 800 ohms. Phono. Mag.
4mV/50k; Phono. 100mV/1
Meg. Output 250mV/100k.
OUR PRICE £8.97 P&P 20p



EA41 REVERBERATION AMPLIFIER

Self contained,
transistorised
battery operated.
Simply plug in
microphone, guitar etc. and output to
your amplifier. Volume control and
depth of reverberation control. Beau-
tiful cabinet. 184 x 77 x 108mm.
OUR PRICE £7.50 P&P 30p



ALL PRICES EXCLUDE VAT

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock - other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL S0640

Size: 85 x 64mm

50uA	£3 80		
100uA	£3 75		
200uA	£3 70		
500uA	£3 65		
50.0-500uA	£3 75		
100.0-1000uA	£3 70		
1mA	£3 65		
5mA	£3 65		
10mA	£3 65		
50mA	£3 85	10V DC	£3 65
100mA	£3 85	20V DC	£3 65
500mA	£3 85	50V DC	£3 65
1A DC	£3 85	300V DC	£3 65
5A DC	£3 85	15V AC	£3 75
10A DC	£3 85	300V AC	£3 75
5V DC	£3 65	VU Meter	£3 90



*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm


50uA	£4 30		
100uA	£4 25		
200uA	£4 20		
500uA	£4 15		
50.0-500uA	£4 20		
100.0-1000uA	£4 20		
1mA	£4 10		
5mA	£4 10		
10mA	£4 10		
50mA	£4 10	10V DC	£4 10
100mA	£4 10	20V DC	£4 10
500mA	£4 10	50V DC	£4 10
1A DC	£4 10	300V DC	£4 10
5A DC	£4 10	15V AC	£4 20
10A DC	£4 10	300V AC	£4 20
5V DC	£4 10	VU Meter	£4 40



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£3 95		
100uA	£3 85		
200uA	£3 80		
500uA	£3 75		
50.0-500uA	£3 85		
100.0-1000uA	£3 80		
500.0-5000uA	£3 70		
1mA	£3 70		
5mA	£3 70		
10mA	£3 70		
50mA	£3 70	15V AC	£3 80
100mA	£3 70	50V AC	£3 80
500mA	£3 70	150V AC	£3 80
1A DC	£3 70	300V AC	£3 90
5A DC	£3 70	500V AC	£3 80
10A DC	£3 70	S Meter 1mA	£4 10
15A DC	£3 70	VU Meter	£3 70
20A DC	£3 80	1A AC	£3 70
30A DC	£3 85	5A AC	£3 70
50A DC	£4 05	10A AC	£3 70
50V DC	£3 70	20A AC	£3 70
10V DC	£3 70	30A AC	£3 70
15V DC	£3 70	50mA AC	£3 70
20V DC	£3 70	100mA AC	£3 70
50V DC	£3 70	200mA AC	£3 70
150V DC	£3 70	500mA AC	£3 70

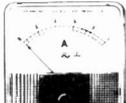

CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4 60		
100uA	£4 50		
500uA	£4 40		
50.0-500uA	£4 50		
100.0-1000uA	£4 45		
1mA	£4 30		
1A DC	£4 30		
5A DC	£4 30		
20V DC	£4 30	150V AC	£4 45
50V DC	£4 30	300V AC	£4 45
300V DC	£4 30	VU Meter	£4 90



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3 20		
100uA	£3 15		
200uA	£3 10		
500uA	£3 00		
50.0-500uA	£3 15		
100.0-1000uA	£3 10		
500.0-5000uA	£3 10		
1mA	£2 95		
5mA	£2 95		
10mA	£2 95		
50mA	£2 95	300V AC	£3 05
1A DC	£2 95	S Meter 1mA	£2 95
5A DC	£2 95	VU Meter	£3 40
10V DC	£2 95	1A AC	£2 95
20V DC	£2 95	5A AC	£2 95
50V DC	£2 95	10A AC	£2 95
300V DC	£2 95	30A AC	£2 95
15V AC	£3 05	30A AC	£2 95



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm


50uA	£4 50		
100uA	£4 45		
500uA	£4 20		
50.0-500uA	£4 45		
100.0-1000uA	£4 40		
1mA	£4 20		
1A DC	£4 20		
5A DC	£4 20		
20V DC	£4 20		
50V DC	£4 20		
300V DC	£4 20		
300V AC	£4 30		
VU Meter	£4 70		



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4 15		
100uA	£4 05		
200uA	£4 05		
500uA	£3 90		
50.0-500uA	£4 10		
100.0-1000uA	£4 05		
1mA	£3 85		
300V AC	£3 95		
VU Meter	£4 30		

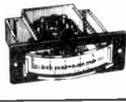

CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3 10		
100uA	£3 05		
200uA	£3 00		
500uA	£2 85		
50.0-500uA	£3 05		
100.0-1000uA	£3 00		
500.0-5000uA	£2 80		
1mA	£2 80		
1.0-1mA	£2 80		
2mA	£2 80		
5mA	£2 80		
10mA	£2 80		
20mA	£2 80		
50mA	£2 80	20V DC	£2 80
100mA	£2 80	50V DC	£2 80
150mA	£2 80	100V DC	£2 80
200mA	£2 80	150V DC	£2 80
300mA	£2 80	300V DC	£2 85
500mA	£2 80	500V DC	£2 85
750mA	£2 80	750V DC	£2 90
1A DC	£2 80	15V AC	£2 90
2A DC	£2 80	50V AC	£2 90
5A DC	£2 80	150V AC	£2 90
10A DC	£2 80	300V AC	£2 90
30V DC	£2 80	500V AC	£3 00
15V DC	£2 80	S Meter 1mA	£2 80
15V DC	£2 80	VU Meter	£3 20



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3 70		
100uA	£3 50		
500uA	£3 40		
50.0-500uA	£3 50		
100.0-1000uA	£3 45		
1mA	£3 30		
5mA	£3 30		
10mA	£3 30		
50mA	£3 30		
100mA	£3 30		
500mA	£3 30		
1A DC	£3 30		
5A DC	£3 30		
10V DC	£3 30		
20V DC	£3 30		
50V DC	£3 30		
300V DC	£3 30		
15V AC	£3 30		
300V AC	£3 40		
S Meter 1mA	£3 30		
VU Meter	£3 30		



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA	£8 50		
100uA	£7 90		
50.0-500uA	£7 90		
1mA	£7 60		
1.0-1mA	£7 60		
1A DC	£7 60		
5A DC	£7 60		
5V DC	£7 60		
10V DC	£7 60		
15V DC	£7 60		
20V DC	£7 60		
30V DC	£7 60		
50V DC	£7 60		
100V DC	£7 60		
150V DC	£7 60		
20V DC	£7 60	300V DC	£7 60
50V DC	£7 60	500mA/5A DC	£8 60
10V DC	£7 60	5V/50V DC	£8 60
15V DC	£7 60	5V/15V DC	£8 60
15V DC	£7 60	1/5A DC	£8 60
15V DC	£7 60	1A/15A DC	£8 60

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5 45		
100uA	£5 40		
200uA	£5 35		
500uA	£5 25		
50.0-500uA	£5 40		
100.0-1000uA	£5 35		
500.0-5000uA	£5 20		
1mA	£5 20		
1.0-1mA	£5 20		
5mA	£5 20		
10mA	£5 20		
50mA	£5 20		
100mA	£5 20		
500mA	£5 20	300V DC	£5 20
1A DC	£5 20	15V AC	£5 30
5A DC	£5 20	30V AC	£5 30
15A DC	£5 20	50V AC	£5 30
30A DC	£5 20	100V AC	£5 30
10V DC	£5 20	150V AC	£5 30
20V DC	£5 20	300V AC	£5 30
50V DC	£5 20	500V AC	£5 30
150V DC	£5 20	30A AC	£5 20



CLEAR PLASTIC MODEL S0460

Size: 59 x 46mm

50uA	£3 50		
100uA	£3 45		
200uA	£3 40		
500uA	£3 35		
50.0-500uA	£3 45		
100.0-1000uA	£3 40		
500.0-5000uA	£3 30		
1mA	£3 30		
5mA	£3 30		
10mA	£3 30		
50mA	£3 30		
100mA	£3 30	10V DC	£3 30
500mA	£3 30	20V DC	£3 30
1A DC	£3 30	50V DC	£3 30
5A DC	£3 30	300V DC	£3 30
10A DC	£3 30	15V AC	£3 45
5V DC	£3 30	300V AC	£3 45
5V DC	£3 30	VU Meter	£3 65



BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5 25		
50uA	£4 00		
100uA	£3 95		
500uA	£3 65		
50.0-500uA	£3 95		
100.0-1000uA	£3 90		
500.0-5000uA	£3 60		
1mA	£3 60		
1.0-1mA	£3 60		
5mA	£3 60		
10mA	£3 60		
50mA	£3 60		
100mA	£3 60		
500mA	£3 60		
1A DC	£3 60		
5A DC	£3 60		
10V DC	£3 60		
20V DC	£3 60		
50V DC	£3 60		
10V DC	£3 60		
15V DC	£3 60		
20V DC	£3 60		
50V DC	£3 60		
150V DC	£3 60		
300V DC	£3 60		
50V DC	£3 60		
150V DC	£3 60		



POSTAGE & PACKING 15p

CENTRAL LONDON

481 OXFORD ST.	01-493 8641
10 TOTTENHAM CT. RD.	01-637 2332
27 TOTTENHAM CT. RD.	01-636 3715
33 TOTTENHAM CT. RD.	01-636 2605
42 45 TOTTENHAM CT. RD.	01-636 0845
87 TOTTENHAM CT. RD.	01-580 3739
257 8 TOTTENHAM CT. RD.	01-580 0670
3 LITTLE ST. WC2	01-437 8604
34 LITTLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3371
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812

NEW from A.S.P.

Also available 1 watt @ 70°C Carbon Film Resistors E12. Range: 10Ω to 2-MΩ 5% tol., above 470kΩ 10% tol. Price 97p per 100.

CASED AUTO TRANSFORMERS


240 Volt Mains to 115 Volts, smart steel-cased units coated in tough resin, fitted with power lead, fuse and 115 Volt American type socket up to 500VA. above 500VA Cable entry

VA (Watts)	Price	P. & P.
200 ..	£5-56	£0-38
500 ..	£9-50	£0-67
1000 ..	£15-92	£0-92
2000 ..	£29-70	£1-50

20VA version uncoated, no fuse £2-52 £0-30

MAINS KEYNECTOR

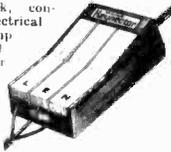The safe, quick, connector for electrical appliances, 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains, ideal for testing, demonstrating, window displays, etc. Warning Light, interlocked to prevent connecting when live.



Trade Price: £2-95. Post 25p.

ELECTRONIC MAINS TIMER

A reliable unit ideal for Timing Bathrooms/Toilet Ventilators, Staircase/Cloakroom Lighting, etc. Gives up to 30 mins. delay before switching off. Delay: 1-30 mins. adjustable. Max Load: 400VA or 1000 watts resistive. Ivory Case. 3 1/2" x 3 1/2" x 2". Fitting instructions included. Trade Price: £5-80. Post 20p.



TRANSFORMERS

SAFETY ISOLATING

Prim. 120/240V.		Sec. 120/240V.		Centre
Tap with screen.				
(watts)	No.	Case	Open	Post
60	149		£2-74	0-38
100	150		4-18	0-52
200	151	£9-48	7-48	0-52
250	152	12-06	9-77	0-65
350	153	14-00	11-44	0-80
500	154	16-80	13-20	1-00
1000	156	30-70	27-48	1-20
2000	158	60-95	55-44	
3000	159	79-53	72-49	

12 & 24 Volts Prim. 200-240V.

Amps	Type	No.	Price	Post
12V	24V			
0-3	0-16	242	1-34	0-22
0-5	0-25	111	1-34	0-22
1	0-5	213	1-59	0-23
2	1	71	2-09	0-22
4	2	18	2-76	0-38
6	3	70	3-66	0-42
8	4	108	3-98	0-52
10	5	72	4-87	0-52
12	6	116	5-87	0-52
16	8	17	6-64	0-52
20	10	115	10-23	0-69
30	15	187	13-75	0-97
40	20	232	18-26	1-00
60	30	226	22-52	1-10

30 Volts

Prim. 200-240V.		Sec. 12, 15, 20, 24, 30V.	
Amps	Type	Price	Post
0-5	112	£1-58	£0-22
1	79	2-20	0-38
2	3	3-19	0-38
3	20	3-98	0-42
4	21	4-88	0-52
5	51	5-80	0-52
6	117	6-93	0-52
8	88	9-00	0-67
10	89	10-00	0-67

50 Volts

Prim. 200-240V.		Sec. 18, 25, 33, 40, 50V.	
Amps	Type	Price	Post
0-5	102	£2-11	£0-30
1	103	3-08	0-38
2	104	4-29	0-42
3	105	5-77	0-52
4	106	7-48	0-52
6	107	11-00	0-67
8	118	14-19	0-97
10	119	17-60	0-97

60 Volts

Prim. 200-240V.		Sec. 24, 30, 40, 48, 60V.	
Amps	Type	Price	Post
0-5	124	£2-10	£0-38
1	125	2-97	0-38
2	127	5-77	0-42
3	125	7-15	0-52
4	123	9-36	0-67
5	40	11-55	0-67
6	120	13-67	0-82
8	121	18-00	1-00
10	122	19-40	1-00
12	189	21-62	1-10

MINIATURE AND EQUIPMENT

Prim. 240V with screen.		Milliamps		Type	Price	Post
Sec. 1	Sec. 2	Sec. 1	Sec. 2	No.	£	£
3-0-3	0-6	200	500	238	1-23	0-10
0-6-6	0-5	500	1000	234	1-30	0-10
0-6	—	1000	—	212	1-08	0-22
9-0-9	—	100	—	13	1-23	0-10
0-9	0-9	330	330	236	1-43	0-10
0-8-9	0-8-9	500	500	207	2-28	0-22
0-8-9	0-8-9	1000	1000	208	3-03	0-30
15-0-15	—	40	—	240	1-23	0-10
0-15	0-15	200	200	236	1-30	0-10
20-0-20	—	30	—	241	1-23	0-10
0-20	0-20	150	150	237	1-30	0-10
0-15-20	0-15-20	500	500	205	2-97	0-38
0-20	0-20	300	300	214	1-76	0-22
0-20	—	3500 (No screen)	—	1116	3-00	0-40
20-12-0-12-20	—	700 (D/C)	—	221	1-55	0-30
0-15-20	0-15-20	1000	1000	206	3-80	0-38
0-15-27	0-15-27	500	500	203	3-08	0-38
0-15-27	0-15-27	1000	1000	204	3-24	0-38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 85p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 59p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p



PLEASE ADD 10% FOR V.A.T.

ADD 10p P. & P. PER ORDER

A.S.P. LTD. BYRE HOUSE · SIMMONDS ROAD · WINCHEAP · CANTERBURY · KENT · Canterbury (0227) 52436

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT. PE, ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

CALLERS WELCOME Mon.-Sat. 9 a.m.-5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1/2W Iskra high stability carbon film—very low noise—capless construction
1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 1/2W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price 1-99	100+
1/2	5%	4.7Ω-2.2MΩ	E24	1.3p	1-1p
1/2	10%	3.3MΩ-10MΩ	E12	1.3p	1-1p
1	2%	10Ω-1MΩ	E24	3.5p	3-1p
1	10%	1Ω-3.9Ω	E12	1.3p	1-1p
1	5%	4.7Ω-1MΩ	E12	1.3p	1-1p
1	10%	1Ω-10Ω	E12	8p	7p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2-40. E24 pack 650 resistors £4-70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single, 14p. Dual ganged (stereo), 49p. Single D.P. switch 28p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for mains operated detector including GDI but excluding case, £3-60. Suitable case, £1-50. Kit of parts for 12 or 24V battery operation, including GDI and P.C. board, £7-70. As above for PP9 battery, £6-90. Note: The battery operated kits incorporate our patented circuit to minimise battery drain—typically 90mA for 24V.

PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, the immerse the board in the etchant. On removal the circuit remains in high relief. 97p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 3p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 33p, 0.047μF, 0.068μF, 0.1μF, 5p, 0.15μF, 6p, 0.22μF, 0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 33p, 0.15μF, 41p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 73p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 33p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 0.03μF, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 4p, each.

CERAMIC DISC CAPACITORS

TORS 100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD O15/67

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/63, 6.8/63, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1,000/4, 10p, 470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1,000/10, 12p, 470/25, 680/16, 1,500/6.3, 13p, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6.3, 18p, 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6.3, 4,700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V	12p
0.22μF 35V	4.7μF 35V	33μF 10V	
0.47μF 35V	6.8μF 25V	47μF 6.3V	
1.0μF 35V	10μF 25V	100μF 3V	

VEROBOARD

0-1	0-15
2 1/2 x 3 1/2	24p
2 1/2 x 5	28p
3 1/2 x 3 1/2	28p
3 1/2 x 5	32p
17 x 2 1/2	85p
17 x 3 1/2	120p
17 x 3 1/2 (plain)	76p
17 x 2 1/2 (plain)	41p
2 1/2 x 5 (plain)	12p
2 1/2 x 3 1/2 (plain)	11p
Pin insertion tool	62p
Spot face cutter	52p
Pkt. 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	28p	2.5mm insulated	12p
Standard insulated	18p	3.5mm insulated	12p
Stereo screened	40p	3.5mm screened	18p
Standard socket	20p	2.5mm socket	10p
Stereo socket	30p	3.5mm socket	11p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin, 7 pin
Plug 12p. Socket 8p.
4 way screened cable, 25p/metre.
6 way screened cable 30p/metre.

BATTERY ELIMINATOR

£1-70
9V mains power supply. Same size as PP9 battery.

Marshall's

A. Marshall & Son (London) Limited
42 Cricklewood Broadway London NW2 3HD, Telephone 01-452 0161
& 65 Bath Street Glasgow G2 2BX, Telephone 041-332 4133

Everything you need is in our
New Catalogue
available now price 20 pence

(100 pages of prices and data)
Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

Popular Semiconductors

2N466	0-80	2N3705	0-18	AD160	0-88	BC308A	0-12	BFY19	0-85
2N466A	0-85	2N3706	0-09	AD161	0-46	BC308B	0-06	BFY29	0-60
2N467A	1-20	2N3707	0-18	AD162	0-46	BC309	0-10	BFY50	0-23
2N490	8-16	2N3708	0-10	AD163	0-46	BC308A	0-10	BFY50	0-23
2N491	8-16	2N3709	0-11	AD162J	1-05	BC309B	0-10	BFY51	0-19
2N492	8-99	2N3710	0-12	AF109K	0-40	BC237	0-21	BFY62	0-21
2N493	4-20	2N3711	0-11	AF115	0-24	BC238	0-19	BFY63	0-21
2N696	0-22	2N3712	0-98	AF116	0-25	BC337	0-19	BFY90	0-80
2N697	0-22	2N3713	1-20	AF117	0-20	BC338	0-19	BFY99	0-82
2N698	0-40	2N3714	1-83	AF118	0-50	BC339	0-48	BU104	1-42
2N699	0-45	2N3715	1-50	AF119	0-24	BC331	0-52	BU105	2-26
2N700	0-20	2N3716	1-80	AF125	0-20	BCY32	1-15	C106A	0-48
2N706A	0-18	2N3771	0-80	AF126	0-19	BCY33	0-84	C106B	0-55
2N708	0-20	2N3772	1-80	AF127	0-80	BCY34	0-87	C106D	0-66
2N709	0-45	2N3773	2-65	AF139	0-39	BCY38	0-83	C106E	0-43
2N711	0-51	2N3789	2-00	AF170	0-25	BCY39	1-05	CA3020A	1-80
2N718	0-35	2N3790	2-40	AF172	0-25	BCY40	0-87	CA3046	0-70
2N718A	0-49	2N3791	2-85	AF178	0-25	BDY42	0-15	CA3048	2-11
2N720	0-50	2N3792	2-99	AF179	0-65	BCY58	0-21	CA3089E	1-20
2N721	0-55	2N3794	2-84	AF180	0-50	BCY59	0-22	CA3090Q	4-22
2N914	0-22	2N3819	0-87	AF166	0-40	BCY70	0-17	LM301A	0-88
2N916	0-41	2N3820	0-64	AF200	0-35	BCV71	0-22	LM304A	2-03
2N918	0-55	2N3823	0-78	AF239	0-51	BCV72	0-13	LM309K	1-88
2N929	0-30	2N3900	0-28	AF240	0-72	BCY87	3-64	LM702C	0-75
2N1302	0-19	2N3901	0-92	AF278	0-16	BF128	0-27	LM709	0-75
2N1303	0-19	2N3902	0-92	AF128	0-16	BCY89	0-97	TO99	0-48
2N1304	0-24	2N3904	0-27	AL102	0-75	BD115	0-75	8D1L	0-88
2N1305	0-24	2N3905	0-24	AL103	0-70	BD116	0-75	14D1L	0-88
2N1306	0-31	2N3906	0-27	BC107	0-16	BD121	0-75	LM723C	0-75
2N1307	0-22	2N4036	0-68	BC108	0-15	BD123	0-82	LM741	0-80
2N1308	0-40	2N4037	0-42	BC109	0-19	BD124	0-67	TO99	0-40
2N1309	0-36	2N4038	0-18	BC113	0-13	BD131	0-40	8D1L	0-46
2N1671	1-44	2N4039	0-99	BC115	0-15	BD132	0-50	4D1L	0-38
2N1671A-1.54	2N4080	0-11	BC116	0-15	BD135	0-48	LM747	1-00	
2N1671B-1.72	2N4061	0-11	BC116A	0-18	BD136	0-48	LM748	1-00	
2N1671C-1.82	2N4082	0-11	BC117	0-21	BD137	0-55	8D1L	0-70	
2N1711	0-45	2N4126	0-20	BC118	0-11	BD138	0-68	14D1L	0-88
2N1907	5-50	2N4289	0-13	BC119	0-29	BD139	0-97	MC1303P	1-22
2N2102	0-50	2N4919	0-84	BC121	0-22	BD140	0-87	MC1310	2-96
2N2147	0-70	2N5059	0-82	BC122	0-15	BDY20	1-05	MC1310	1-92
2N2148	0-94	2N4921	0-73	BC126	0-20	BF115	0-85	MC1458CP1	0-79
2N2160	0-90	2N4922	0-84	BC132	0-30	BF116	0-23	MJ460	0-90
2N2192	0-40	2N4923	0-88	BC134	0-11	BF117	0-48	MJ481	1-14
2N2192A	0-40	2N5172	0-12	BC135	0-11	BF119	0-58	MJ481	1-14
2N2193	0-88	2N5174	0-22	BC136	0-15	BF121	0-25	MJ480	0-98
2N2193A	0-41	2N5175	0-26	BC137	0-15	BF123	0-27	MJ491	1-38
2N2194	0-78	2N5176	0-32	BC138	0-24	BF125	0-25	MJ5340	4-42
2N2194A	0-30	2N5190	0-82	BC140	0-84	BF152	0-20	MJE2865	1-12
2N2218A	0-60	2N5191	0-95	BC141	0-29	BF153	0-21	MJE3055	0-68
2N2219	0-45	2N5192	1-24	BC142	0-28	BF154	0-20	MJE3055	0-68
2N2219A	0-60	2N5195	1-46	BC143	0-21	BF158	0-23	MP8A56	0-27
2N2220	0-45	2N5246	0-48	BC145	0-21	BF159	0-27	MP8A56	0-27
2N2221	0-41	2N5457	0-66	BC147	0-15	BF160	0-27	MP8A56	0-27
2N2221A	0-40	2N5458	0-45	BC148	0-13	BF161	0-42	MP8A56	0-27
2N2222	0-40	2N5459	0-49	BC149	0-12	BF163	0-32	MPF102	0-89
2N222A	0-60	40361	0-48	BC153	0-18	BF166	0-32	MP8A05	0-25
2N2368	0-31	40362	0-50	BC154	0-18	BF167	0-21	MP8A06	0-28
2N2369	0-27	40363	0-61	BC157	0-14	BF173	0-24	MP8A55	0-26
2N2369	0-41	40369	0-46	BC158	0-12	BF177	0-27	NE555V	0-90
2N2369A	0-77	40394	0-66	BC159	0-12	BF178	0-30	NE555V	0-90
2N2647	1-12	40395	0-65	BC160	0-87	BF179	0-43	NE560	4-48
2N2904	0-40	40406	0-44	BC167B	0-13	BF180	0-35	NE561	4-48
2N2904A	0-45	40407	0-83	BC168B	0-13	BF181	0-84	NE565A	4-48
2N2905	0-48	40408	0-50	BC168C	0-11	BF182	0-40	OC23	0-58
2N2905A	0-80	40409	0-52	BC169B	0-13	BF183	0-40	OC28	0-76
2N2906	0-21	40410	0-52	BC169C	0-13	BF184	0-80	OC35	0-80
2N2906A	0-37	40411	2-00	BC170A	0-11	BF185	0-17	OC42	0-35
2N2907	0-40	40414	3-55	BC171	0-13	BF194	0-16	OC45	0-32
2N2907A	0-45	40430	0-85	BC172	0-11	BF195	0-17	OC71	0-12
2N2924	0-14	40583	0-23	BC182	0-12	BF196	0-15	OC72	0-13
2N2925	0-17	40601	0-67	BC182L	0-12	BF197	0-15	OC81	0-20
2N2926	0-60	40602	0-46	BC183	0-09	BF198	0-18	OC83	0-20
Green	0-12	40603	0-53	BC183L	0-09	BF199	0-18	ORP12	0-50
Yellow	0-11	40604	0-56	BC184	0-11	BF200	0-40	RC35D	1-68
Orange	0-06	40636	1-00	BC184L	0-11	BF225J	0-19	RC36D	1-46
2N3053	0-25	40673	0-70	BC187	0-27	BF238	0-22	RC40D	1-89
2N3054	0-80	AC107	0-25	BC207	0-12	BF244	0-18	RC41D	1-32
2N3055	0-75	AC113	0-16	BC208	0-11	BF245	0-23	RC46D	1-89
2N3090	0-28	AC117	0-20	BC212C	0-18	BF246	0-18	RC50D	2-80
2N3391	0-28	AC126	0-25	BC212L	0-16	BF247	0-49	RC51D	2-39
2N3391A	0-28	AC127	0-25	BC214L	0-16	BF254	0-16	SL414A	1-80
2N3392	0-18	AC128	0-25	BC237	0-09	BF255	0-17	SL623	4-59
2N3393	0-18	AC151V	0-25	BC238	0-09	BF257	0-46	TAA263	0-70
2N3394	0-18	AC152V	0-17	BC239	0-09	BF258	0-59	TAA350	2-10
2N3402	0-18	AC153	0-25	BC251	0-20	BF244	0-58	TAA621	8-08
2N3403	0-19	AC153R	0-32	BC252	0-19	BF282A	0-30	TAA661B	0-20
2N3440	0-59	AC154	0-20	BC253	0-23	BF282	0-22	TAD100	1-50
2N3441	0-97	AC176	0-23	BC257	0-09	BF281	0-97	TAD100	1-50
2N3442	1-25	AC176K	0-23	BC258	0-09	BF288	0-20	Filter	0-70
2N3414	0-20	AC187K	0-28	BC259	0-13	BFX29	0-30	TBA271	0-64
2N3415	0-21	AC188K	0-34	BC261	0-20	BFX30	0-25	TBA680	1-95
2N3416	0-24	AC178	0-23	BC262	0-18	BFX44	0-58	TBA680	1-95
2N3417	0-24	AC153R	0-32	BC263	0-22	BFX63	0-48	TBA800	1-50
2N3638	0-15	ACY20	0-22	BC300	0-38	BFX68	0-30	TBA810	1-50
2N3638A	0-15	ACY21	0-26	BC301	0-84	BFX84	0-24	TIL209	0-85
2N3639	0-27	ACY28	0-20	BC302	0-89	BFX85	0-30	TIP29A	0-49
2N3641	0-17	ACY30	0-42	BC303	0-54	BFX87	0-28	TIP30A	0-88
2N3702	0-12	AD142	0-50	BC307	0-11	BFX98	0-25	TIP31A	0-22
2N3703	0-18	AD143	0-50	BC307A	0-18	BFX99	0-45	TIP32A	0-71
2N3704	0-14	AD148V	0-58	BC308	0-12	BFY18	0-35	TIP33A	1-04

New from Siemens
7 segment 4 digit Decimal Display
Liquid Crystal Type-AN 4131 complete
with data. From stock now. Price £13.00
complete with holder. Ideal for battery
operated Quartz clock using two of the
latest CMOS ICs from Solid State
Scientific. 15v battery operated, minimum
of discrete components required.
Send SAE for details.

Seven Segment Read Out
Minitor 3015F £1.55
DL707 Litronix £2.35
All data in our new catalogue price 20p

Printed Circuit Marker Pen
DALO 33PC-complets with instructions
No masking! No mess! Re-etch or blue.
Price 87p

400mW Zeners 3.5v to 43v
New low price 11p each £8.20 for 100

A large selection of heatinks for all types
of transistors from Redpoint, in stock now.
TC5-6p TO18-7p
6W1-6"x4" undrilled £1.00
4W1-4"x4" undrilled £0.80
2W1-2"x4" undrilled £0.45

Resistors

Power W	Tol	Price	Tantalum Bead
1/2	5%	1p	Value
1/4	5%	1-5p	1/35v
1/8	5%	2p	22/35v
1	10%	2-5p	47/35v
2	5%	6p	1p/35v
2 1/2	5%	7p	2-2/35v
3	5%	9p	4-7/35v
10	5%	10p	2-2/16v

Veroboard Large stockist

Copper	Plain
-15	1
-15	1
2-5x3/5	20
2-5x5	30
3x3x3/4	30
3x3x5	35
2x1x1/2	87
3x1x1/2	85
3x1x1/2	85

trade or retail supplied

Thermistors
Multard E298DD Series 12Vp
E298E Series 10Vp
Neg temp Coef VACO Series 20p
RES £1.20
Full details of ranges in our catalogue 20p

Equivalents Books
Transistors 70p
ICs 70p

Veropins 1 1/2 Face Cutter 46p
36pcs 24 21 Insertion Tools 64p
200pcs 89 82

VAT
Please include 10% Vat with all orders
Prices quoted are all exclusive of Vat
Post and Package
15p postage and package charges
Prices correct at July 1974

TIP34A	1-51	TIP42A	0-90	ZTX309	0-20
TIP35A	2-09	TIP45E	0-28	ZTX50	0-16
TIP36A	1-70	ZTX305	0-60	ZTX502	0-17
TIP41A	0-78	ZTX308	0-12	ZTX530	0-21


Kellner Construction Kits

Wear the sole distributors in U.K.

ES3 3 watt Mono Transistor Amplifier Kit £4-08
ES15 15 watt Hi-Fi Transistor Amplifier Kit (two for stereo) £9-20
with Tone Control and Pre-Amp £13-20
ES30

Project 80

a brilliant new concept in modular hi-fi

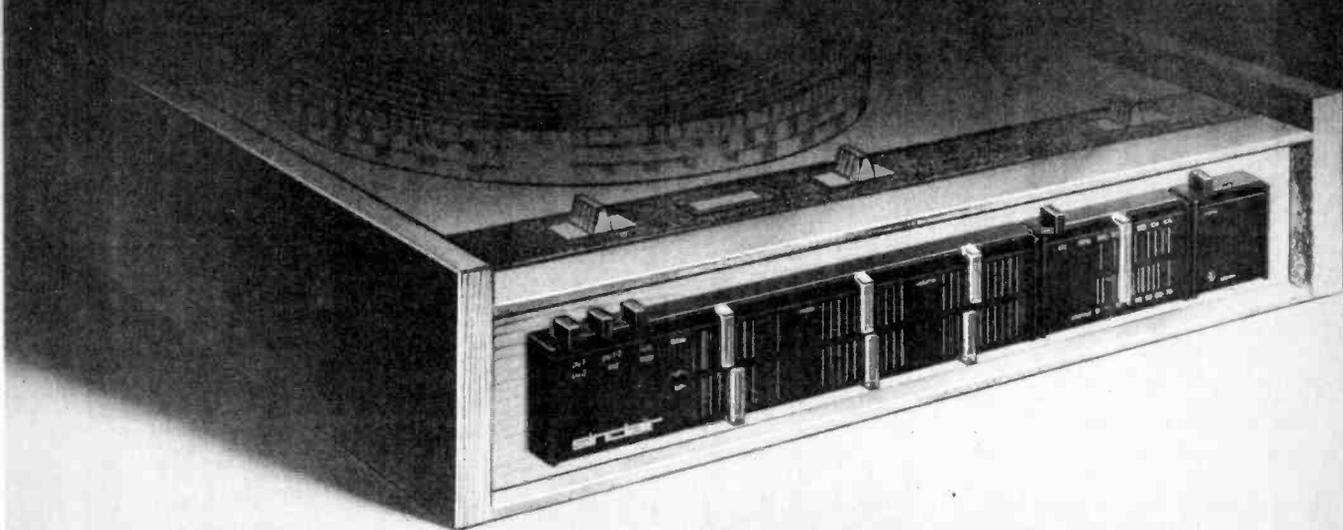


Project 80 is going to be the ultimate in modular hi-fi construction for a very long time to come. It combines the qualities most demanded of any modern domestic system – good circuitry, reliability and fine performance – with other features to be found nowhere else in the world. For example, *compactness* – Project 80 control units are $\frac{3}{4}$ " deep \times 2" high, and each one is completely self-contained.

Elegance – all of Sinclair's design leadership has been concentrated on producing designs of outstanding functional elegance unsurpassed for styling and simplicity. *Flexibility* – the size and styling of Project 80 modules makes them the most versatile units ever. Combine them how you will, where you will, the Project 80 System of your choice gives you the best.

sinclair

Sinclair Project 80

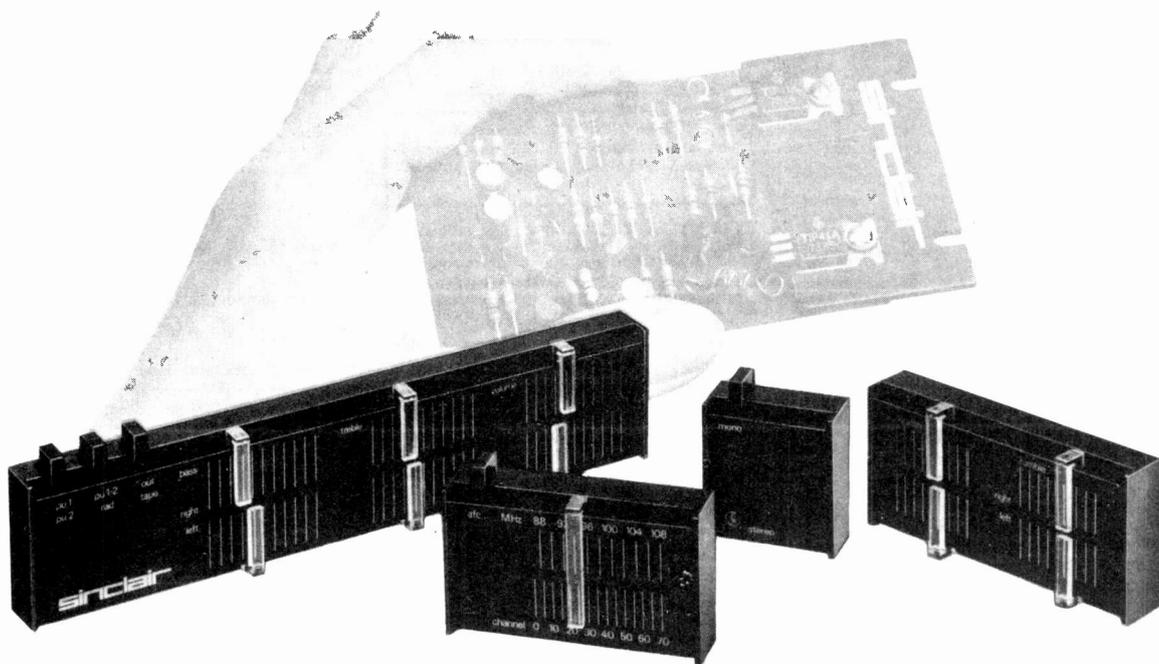

technically the world's most advanced

Project 80 gives you choice from a range of 9 different modules for combining in a variety of ways to suit your requirements. The Stereo 80 is a versatile pre-amp control unit designed to meet all domestic hi-fi requirements including tape monitoring, high sensitivity magnetic cartridge input, and of course, individual slide controls on each channel for precise output matching. By separating the F.M. tuner and stereo decoder, useful economies can be effected where stereo radio reception is not needed. Two power amplifiers - Z.40 (18 watts RMS continuous into 4 ohms using 35V) and Z.60 (25 watts RMS continuous into 8 ohms using 50V) are available with choice of 3 different power supply units. The PZ.8 with its virtually indestructible circuitry is particularly recommended. For the final word in system building, the Active Filter Unit puts the finishing touch of quality to what are easily the world's most technically advanced hi-fi modules. Any further units likely to be added to Project 80 range will be compatible with those already available.

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge.

sinclair

Sinclair Radionics Ltd
London Rd. St. Ives
Huntingdon PE17 4HJ
Telephone
St. Ives (0480) 64646

Stereo 80 Control Unit Size - 260 50 20mm (10 1/2 2 3/8 ins)
Finish - Black with white indicators and transparent sliders Inputs - Magnetic pick up 3mV RIAA corrected Ceramic pick up 350mV Radio 100mV, Tape 30mV Signal/noise ratio - 60db Frequency range - 20Hz to 15KHz - 1dB, 10Hz to 25KHz + 3dB Power requirements - 20 to 35 volts Outputs - 100mV - AB monitoring for tape Controls - Press button tape radio and P.U. Sliders on each channel for volume bass treble R R P £11.95
(add £1 19 V A T)

Project 80 FM Tuner Size - 85 50 20mm (3 3/8 2 3/8 ins)
Tuning range Dual varicap - 87.5 to 108MHz Detector - I.C. balanced coincidence One I.C. equal to 26 transistors Distortion - 0.2% at 1KHz for 30% modulation 4 pole ceramic filter in I.F. section Aerial impedance - 75 Ω or 240-300 Ω Sensitivity - 5 microvolts for 30cB S/N ratio Output - 300mV for 30% modulation Power requirements - 25 to 35 volts R R P £11.95
(add £1 19 V A T)

Project 80 Stereo Decoder Size - 47 50 20mm (1 7/8 2 3/8 ins)
One 19 transistor I.C. Channel separation greater than 30dB Power requirements - 25V Output 150mV per channel R R P £7.45
(add 74p V A T)

Active Filter Unit Separate controls on each channel Size - 108 50 20mm (4 1/4 2 3/8 ins) Voltage gain - minus 0.2dB Frequency response - 40Hz to 22KHz controls minimum Distortion - at 1KHz - 0.03% using 30V supply H.F. cut off (scratch) - 22 KHz to 5.5KHz 12dB/oct slope L.F. cut off (rumble) - 28dB at 20Hz 9dB/oct slope R R P £6.95
(add 69p V A T)

Z.40 Power Amplifier Size - 55 80 20mm (2 1/8 3 1/8 3/8 ins) 9 transistors Input sensitivity - 100mV Output 18 watts RMS continuous into 4 Ω (35V) Frequency response 30Hz 100KHz - 3dB S/N ratio - 64dB Distortion - at 10 watts into 8 Ω less than 0.1% Power requirements 12 to 35 volts, built in protection against overload R R P £5.40
(add 54p V A T)

Z.60 Power Amplifier Size 55 98 15mm (2 1/8 3 7/8 3/8 ins) 12 transistors Input sensitivity 100 250mV Output - 25 watts RMS continuous into 8 Ω (50V) Distortion - typically 0.03% Frequency response - 15Hz to more than 200KHz 3dB S/N ratio - better than 70dB Built in protection against transient overload and short circuiting Load impedance - 4 Ω min safe on open circuit R R P (add 69p V A T) £6.95

Power Supply Units PZ.8 Stabilised Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 50V R R P £7.98 - 79p V A T Without mains transformer PZ.6 35V stabilised R R P £7.98 - 79p V A T PZ.5 30V un stabilised R R P £4.98 - 49p V A T

To Sinclair Radionics Ltd, St. Ives Huntingdon PE17 4HJ

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V A T _____

Name _____

Address _____

PE8

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 20p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for televisions, radios, transistors, record players, tape recorders, etc., from 5p with free fault-finding guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

WANTED. Radio and TV Servicing books from 1984 onwards. £2 per copy, paid by return of post. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, Yorkshire. Telephone 0423 55885.

FOR SALE

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycroft
Road, Richmond, Surrey TW9 2EQ
01-948 3702

SEEN MY CAT? 5,000 Items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

LIGHTSHOW PROJECTORS from only £17, effect wheels from only £4. Many lightshow bargains at ROGER SQUIRE'S (Disco Centre), 176 Junction Road, London, N.19. Tel. 01-272 7474.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel, choice of 70 types, send for free list. BAZELLI INSTRUMENT CASES, Dept. 23, St. Wilfrids, Foundry Lane, Halton, LA2 6LT, Nr. Lancaster.

VALVES, VALVES AND MORE VALVES. Large stocks, many types, 1930 to 1974. S.A.E. for quotation. List 10p. COX RADIO, The Parade, East Wittering, Sussex.

PRACTICAL ELECTRONICS, December 1968 to February 1973 inclusive. Excellent condition. Offers. LIVINGSTON, 94a Broadgate, Beeston, Notts.

PRACTICAL ELECTRONICS. Most issues from 1966 to 1970 available. Apply: FRANK MORTON, 65 Malmsey House, Vauxhall Street, London, SE11 5LU.

PART-BUILT P.E. Sound Synthesiser. Details—B. LONG, "Riviere", Tewkesbury Road, Cheltenham, Glos.

LOGIC TEST PROBES: indicates logic levels single pulses, pulse trains. Excellent value, £7 inclusive. CRUDWELL ELECTRONICS, 7 The Dawneys, Crudwell, Nr. Malmesbury, Wiltshire.

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. KINGS PATENT AGENCY LIMITED (Est. 1886). B. T. King, Director, M.I.Mech.E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

SITUATIONS VACANT

Just one technician's opinion of his future with us.

David joined Marconi Communication Systems Ltd. in 1968 and has been in the Repair and Calibration Section for 12 months. He is currently studying for his City & Guilds Telecommunication Technician certificate on a day release basis. His work is varied and interesting and consists of checking and maintaining the performance of complex electronic test equipment used to test and develop the Company's products.

If you have some experience of modern circuitry and fault finding, why not find out more about a job alongside David? If you have C & G or ONC so much the better. There are also opportunities for people with experience in computers for our Automatic Test Department. We can offer good salaries and all the career opportunities that exist in a large Company together with generous removal expenses where necessary. The positions are based in Chelmsford, so why not clip the coupon and send it now to Gordon Short, Technical Recruitment Officer, Marconi Communication Systems Ltd., New Street, Chelmsford, Essex. Telephone Chelmsford 53221. Ext. 592.



"... I consider that the ever increasing knowledge that I am acquiring is the basis of an interesting and rewarding career".

David Orves Age 22
Calibration Technician.

Name _____

Address _____

**Marconi
Communication
Systems**

A GEC-Marconi
Electronics Company



Electronic Technician

Within our Group Engineering Department at St. Albans we have an increasing design and development work load, due to the continuing modernisation of existing factory facilities together with a programme of expansion of our production capacity throughout the United Kingdom.

The post requires a man who can interpret the engineer's requirements to construct and test electronic inspection and control equipment. This may be in the form of bottle inspection machines or control panels for furnaces. A knowledge of good wiring practice for both electric and electronic currents is required.

The successful applicant will from time to time assist in installing equipment at Group factories throughout the U.K. The post will suit an electrical tradesman who has obtained ONC or similar qualifications in electronics. It would also be helpful to have working knowledge of small bore pipework.

The appointment will involve some travel to our factory sites within the British Isles. The post offers excellent conditions, interesting work and opportunities for promotion within the Group.

Please apply in the first instance to :-

Mr. A. Raine Howe,
Design and Development Engineer,
Research & Development Centre,
Valley Road Industrial Estate,
Porters Wood, St. Albans, Herts.



UNITED GLASS

MEN!
£70 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. After training, our exclusive appointments bureau — one of the world's leaders of its kind — introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators
Training Centre
T60, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

IMPERIAL COLLEGE ELECTRONICS TECHNICIAN

(grade 5) required for electronics workshop to work on the maintenance of electrical and electronic equipment. Digital experience preferred with qualifications to at least ONC standard. 9 a.m. to 5.30 p.m. 5-day week. Four weeks' holiday plus generous leave at Christmas and Easter. This is a contract appointment with good prospects continuation. Starting salary on scale £2,182 to £2,557 including London weighting.

Please apply to:

Mr. T. W. Dickinson
Physics Department
Imperial College, London, S.W.7
Or ring 01-589 5111, Extension 2336

LADDERS

LADDERS. "Special Offer" unvarnished triples. 9ft 7in closed—23ft 1in extended. **£18-90** delivered. HOME SALES LADDER CENTRE (PEE2), Haldane (North), Halesfield (1), Telford, Shropshire. Tel. 0952 586644.

EDUCATIONAL

C AND G EXAM

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work and Technicians. Radio/TV/Electronics Technicians. Telecommunications Technicians and Radio Amateurs

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-built radio kits.

Get the qualifications you need to succeed. Free details from:

International Correspondence Schools,
Dept. 7368, Interfax House, London SW8
4UJ. Or phone 01-822 8811

RECEIVERS AND COMPONENTS

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 4x4 0-1 Matrix, 4 for £1.
12x3 0-15 Matrix, 75p each.

Memory Array Panels. Full of Ferrite Rings. £1.10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 1/2 in with circuit, £1.37 1/2 inc. P.P.

Crouzet Geared Motors, 30 or 60 r.p.m. New, £1.54 inc. P.P.

UHF TV Tuners. Transistorised, £1.65 inc. P.P.

Panels with I.C.'s on 7 1/2p per I.C. min. order 10 I.C.'s.

Transformers. 7.5V + 7.5V 1/2A, 88p inc. P.P. 12.0-12V, 100mA, 90p inc. P.P. 9.0-9V, 100mA, 90p inc. P.P. 29V 50mA, 70p inc. P.P.

Brand new Boxed Rola Celestion Reentrant Speakers SD 25 with 100V line transformer fitted 15Ω without transformer £14 inc. P.P.

Transformer. 45.0-45V, approx. 2 amp, £2.50 inc. P.P.

P.C. Board. S/S, 5 1/2 x 5 1/2 in, 10 for 70p inc. P.P. Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, £2.20 inc. P.P.

Transistorised Timer. Variable delay, 110 or 250V A.C. input. With instructions. Brand new, £2 inc. P.P. Size 3" x 2" x 2".

Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2 1250 mfd capacitors, all new £1.25 per kit. P.P.

Electrolytic Capacitors, 4,000 MF, 50 VV, 4 1/2" x 1 1/2" 75p. inc. P.P.

UNIT IN SMART ALI CASE 11 x 11 x 4in., contains 8 silicon diodes 600V, 20A, 8 SCRs 3 OR 400V 18A. Vintors, 4 small, 2 large, together with other components. £8 (80p). M.C. METERS, 3 assorted 2-3in., £1.15 (35p). 5 FIGURE RESETTABLE COUNTER, 18/22V, works on 12V. £2.20 (25p). 7400 SERIES I.C.'s, 10 on panel(s). £1.18, c.p. COPPER CLAD PAX. PANELS, 5 1/2 x 5 1/2 in., 6 for 80p, c.p.; 7 1/2 x 9 in., 6 for £1.30, c.p.; 1 1/2 x 9 in., 3 for £1, c.p.; 15 x 9 in., 3 for £1.30, c.p. SMALL UNIT WITH 4BFY81 with heatinks, 4 silicon diodes 850V 1/2A plus resistors. 80p, c.p. SMALL PANEL with 2 x AC128 and OC75 plus electrolytics. 40p for 2, c.p. VALUPAKS, P9, 100 assorted s/mica caps. 55p; P11, 100 assorted polystyrene caps. 75p; P13, 10 wire ended norm. 80p; P22, 100 assorted capacitors. 50p, post 12p any number of Paks. Send 10p stamps for list of Valupaks, computer panels, etc. Refund on purchase. 7LB ASSORTED COMPONENTS, £1.78, c.p. 2LB FIRSTS COMPUTER PANELS, £1.78, c.p. 3LB SECONDS COMPUTER PANELS, £1.80, c.p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets Mail order only

RADIO & TELEVISION AERIAL BOOSTERS £2-95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7-50. Carr. £1-50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE

440V AC (±10%)	63V Range			
0.1μF (1" × 1")	50p	±1%	±2%	±5%
0.22μF (1" × 1")	50p	0.47μF	50p	46p 36p
0.25μF (1" × 1")	50p	1.0μF	50p	56p 46p
0.47μF (1" × 1")	71p	2.2μF	50p	56p 56p
0.5μF (1" × 1")	75p	4.7μF	50p	51.00 50p
0.55μF (2" × 1")	80p	6.5μF	51.00	51.00 51.00
1.0μF (2" × 1")	91p	10.0μF	52.00	51.60 51.40
2.2μF (2" × 1")	11.25	15.0μF	52.75	52.15 51.90

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 8.2μF at 15V/20V or 35V; 10.0μF at 15V/20V or 25V; 22.0μF at 6V/10V or 15V; 33.0μF at 6V or 10V; 47.0μF at 5V or 6V; 100.0μF at 3V. ALL at 10p each, 10 for 95p, 50 for 64p.

TRANSISTORS	BC183/183L	11p	BFY50	30p	
BC107/8/9	8p	BC184/184L	18p	BFY51	30p
BC114	15p	BC212/212L	14p	BFY52	30p
BC147/18/9	10p	BC647/568A	18p	AF178	30p
BC183/7/8	15p	BF194	15p	OC71	15p
BC182/182L	11p	BF197	15p	2N3055	50p

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 90p; 1844 8p, 11 for 50p, 24 for 81; 1N4148 6p, 6 for 37p, 12 for 48p; 1N4001 51p; 1N4002 6p; 1N4003 61p; 1N4004 71p; 1N4005 71p; 1N4006 8p; 1N4007 81p.

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.6V, 4.7V, 5.1V, 6.8V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. ALL at 7p each, 6 for 39p 14 for 84p. SPECIAL OFFER: 100 Zeners for 45-50.

RESISTORS—High stability, low noise carbon film 5%, 1W at 40°C, 1W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 85.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27; 100 P.I.V. 7p (4 for 30p); 400 P.I.V. 8p (4 for 30p); 800 P.I.V. 11p (4 for 48p).

BRIDGE RECTIFIERS—2 1/2 amp; 200V 40p; 350V 45p; 600V 85p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 3p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 1MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW 45. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 10% V.A.T. TO ORDERS Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. E.8, The Maltings, Station Road, Wem, Shropshire
Tel.: Nantwich (Cheshire) 63291 (STD 0270)
(Proprs.: Minicost Trading Ltd.)

15 WATT AUDIO AMP I.C.'s

The BHA0002, £2.45 each. £4 pair with heat sink bracket and circuit information
W04. 1A. 400V bridge recs. ... 20p
BC107, 108, 109 ... 10p

ALL FULL SPEC. DEVICES

JACK PLUGS 1/2" mono ... 12p
OR SOCKETS 1/2" stereo ... 18p
3.5 mm ... 9p
3 & 5 PIN DIN 180° plugs ... 9p
3 & 5 PIN DIN 180° sockets ... 7p
PHONO PLUGS ... 5p
DOUBLE PHONO SOCKETS ... 6p

V.A.T. inclusive. 15p P. & P. under £2.

C.T.S., 20 Chatham Street
Ramsgate, Kent CT11 7PP

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 60p per dozen; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex 9003 34897

5 N-GHANCE FETs. Type 3819E (2N3819) for \$1 (incl. VAT). Full spec. transistors complete with circuit details for building voltmeter, timer, ohmmeter, etc. For complete list of FETs and other transistors available send 10p P.O. REDHAWK SALES LTD., 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V-0.47, 1, 2.2, 4.7, 10MF, 4p, 22, 47, 47p (50V, 5p); 100, 51p (50V, 7p); 22, 47, 47p (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/8V, 100/3V, 5p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 24p; 0.04, 0.05, 3p. Polystyrene 63V E12 series 10pF-1000pF, 2p; 1,200pF-10,000pF, 3p. Miniature High-stab. resistors 5%, E12 series carbon film 1W, 1Ω-10MΩ, (10% over 1MΩ). Metal film 1W, 10Ω-2.2MΩ and 1W, 27Ω-10MΩ all 1p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

NEW AND GUARANTEED AC 127, AC 128, AC 188, 11p each inclusive VAT. C.W.O. plus P. & P. 10p to S.R. INTERNATIONAL, 25 Clovelly Avenue, London, NW9 6DT.

ALL I.C.'s, SEMICONDUCTORS, Components and Hardware at discount prices, post free, for constructional projects. Kits assembled and repaired. S.A.E. enquiries for prompt quotation. POWELL, 25 Bowes Road, Walton, Surrey.

BOOKS AND PUBLICATIONS

ELECTRONIC ENGINEERS AND TECHNICIANS. You are worth more than a measly £40 or £50 a week. Much more, and you do not need to be highly qualified to get it. In the last year I earned £3,600 for a total of six months work. The other six months I had off. There's no selling involved, just general electronic and electrical engineering. I've written a book telling how I started and how you too could be doing the same as I am. It's 48p including P. and P. Not a very high price to pay when you consider it could be the turning point in your career. Send to D. G. JAMES, 13 Mill Lane, Acle, Norwich, NOR 60Z.

MISCELLANEOUS

fibres optic suppliers

NEW LENSES OPTIKIT L5 5 convex lenses for photoelectric devices, detector beams, tachometers, sensors. off each diameter/focal length 7/7, 14/12, 21/18, 26/23, 45/50mm, £2.20.

LIGHT SOURCES, DETECTORS: MV54 miniature (2mm) red LED; MLED500 TO-92 PC mounting red LED; MLED92 TO-92 infra-red emitter; 2N5777 high sensitivity silicon photo-darlington amplifier. Response Time 200 μs, 25V max. Superior to CdS cell, OCP71. MRD150 miniature (2mm) silicon phototransistor. Fast response 3 μs, 40V max.

1 2 5 10 25
MV54 22p 44p £1.10 £2.09 £3.52
MLED500 22p 44p £1.10 £2.20 £3.74
MLED92 33p 66p £1.34 £2.86 £4.60
2N5777 55p £1.10 £2.53 £4.62 £9.90
MRD150 66p £1.32 £3.19 £4.16 £14.85

ULTRASONIC TRANSDUCERS for remote control 40kHz Tx/Rx pair £3.85.

CIRCULAR POLARISERS for glare reduction—enhance contrast ratio from LED display, nixies, scope. HRCPT red, HACF24 amber, HGCP24 green, HNCPT3 neutral. 50mm x 50mm 66p; 75mm x 75mm £1.21; 150mm x 150mm £4.40.

CROFON 1610 64 strand plastic light conduit, bundle dis. 1.8mm, A.D. 3.3mm. 1m £1.32; 5m £5.80; 10m £14.85; 25m £23.

PLASTIC OPTICAL MONOFIBRE for easy light circuitry, displays, affects. Diameter 0.5mm—FP20; 1.0mm—FP40; 1.5mm—FP60. Length m 5 10 25 50 100

FP20 £1.10 £1.98 £3.85 £4.60 £12.10
FP40 £1.98 £3.85 £7.70 £13.20 £24.20

OPTIKIT 103: Experimenter pack, 2 metres Crofon 1610 + 5m each FP20, FP40, FP60—£4.84.

MARE'S TAILS: Decorative effects. 7,000 fibres in 18mm O.D. ferrule. Professionally finished. 22in diameter in use. Add lamp, stand, cover to make Fibre Optic Lamp. Eye catching in boardroom, hall or foyer.

NEW LOW PRICE £10.45 each. All prices include p. & p. VAT and data. Send 9in x 6in S.A.E. for details.

FIBRE OPTIC SUPPLIERS (Dept. PE), P.O. Box 702, London W10 6SL

PSYCHEDELICATESSEN

is the only way to describe the paradise of FREAKY gear now available from Boffin. LOOK!

Kits
NO LICENCE EXAM. Transmitter/Receiver £6.40
Variable-rate, BRIGHT-FLASH, Pocket Mini-Strobe £2.40

Ready-Made Modules
Maxi-Volt SPARK GENERATOR (1inch spark), 15,000 Volts. £1.35
Experimental Mini DREAM-LAB-ORATORY £2.20

SENSITIVE non-anatomical electronic STETHOSCOPE £2.20
Electronic 'VOICE-THROWER' £2.20
GHOST-HUNTING AID £2.20

PEOPLE DETECTOR £2.20
Experimental WATER-FONE £4.40
PSYCHEDELIC MEDITATION AID £2.20
Bird-Watchers' REMOTE MONITOR £2.20

Psychological CROSS-EYED EARS Device £4.40
Super SOUND-CATCHER £2.20

(All prices include VAT, packing & postage)

Send remittance to:
BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh Ewell, Surrey

(Mail order U.K. only)
Or for more details, send 20p for lists, plus free design project sheet


MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0.05-3A - 6 Ranges
A-AC 0.3-3A - 5 Ranges
V-DC 0.6-1200V - 9 Ranges
V-AC 3-300V - 8 Ranges
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm - 5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5% DC ±4% AC. Dimensions: 187 x 98 x 83mm.



Only £8.00

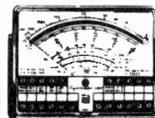

SUPERTESTER 680 R ICE

10 Fields - 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC. Temperature -50C to +200C. Magnetic fields up to 15 KGauss. Phase Indicator - EHT 25KV Electronic Volt Ohm-meter Transistor Diode Tester, etc.

Dimensions 128 x 95 x 32 mm
300 grams 20KOhm/V Accuracy
1% DC Ask for free catalogue

£18.50
Accessories Extra

ALPHANUMERIC NIXIE TUBES B7971

The Alphabetic NIXIE tube has the ability to display all the letters of the alphabet, numerals thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alpha-



numeric NIXIE tube provides many unique benefits including * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footcandle brightness * Long life with no loss of brightness * Character height 2 1/2in.

Price only 99p each plus 16p P./P.

Add 10% VAT to all items - 35p P&P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB Tel. 837 7781

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76p)

SEND 5" x 7" S.A.E. FOR DETAILS TO:

CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weights only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send a.s.e. for leaflet

Complete kit Post 35p **£9.80** Built, tested and guaranteed Post 35p **£13.75**

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order only)

PRINTED CIRCUIT MANUFACTURERS offer any P.E. Project Print ready drilled, One Price 65p. C.W.O. Any P.C. work undertaken. For estimate by return post, send basic circuit, print design or print master. State quantity required. Print design, art work, photography undertaken. Orders, estimates, write or phone: **W.K.F. ELECTRONICS, Dept. P.C., Welbeck Street, Whitwell, Nr. Worksop, Notts., S80 4TW. Tel. Whitwell (Derbys.) 6958.**

PUBLISHER'S ANNOUNCEMENT

Due to production difficulties existing at the time this issue went to press, we strongly advise readers to check with advertisers the prices shown, and availability of goods, before purchasing

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£1.90	£1.05
15-19	£2.00	£1.10
20-24	£2.05	£1.15
25-29	£2.10	£1.20
30-34	£2.20	£1.28
35-40	£2.35	£1.35

All the above prices are inclusive in U.K.

INDUSTRIAL SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone 061-224 3553

SINTEL 22 45 00

SP352's SP352's SP352's
CT5001 4 Function Calculator IC £4.80 + VAT = £5.28
MK50250N Alarm Clock IC £7.80 + VAT = £8.36
CT7001 Alarm/Calendar Clock IC £16.50 + VAT = £18.15
SP352 2 digits 55in for clocks, etc. £4.00 + VAT = £4.40
 No P. & P. Charge—data supplied with device
 Send 20p. stamps if you like, for full data and our circuits on all of above, or a 4p stamp for our product list.
SINTEL, 53 ASTON STREET, OXFORD

HARDWARE SUPPLIES—Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers, etc., Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes, etc., 7p for list. **RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks., CV37 9JP.**

LOW COST I.C. MOUNTING. Lengths of 100 I.C. pin sockets, 60p (P. & P. 5p). Quantity rates. S.A.E. for details and sample. L.E.D. (MLED500), 20p each (post paid). P.K.G. ELECTRONICS, "Oak Lodge", Tansley, Derbyshire.

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to: **METER REPAIRS, 39 Chesholm Road, London, N16 0DS.**

SLOW SPEED MOTORS required (about 1r.p.m.) any quantity considered. Phone Mr. SMITH, 061-633 3527.

ZN414, \$1. All in price. New unused. **ISLAND DEVICES, P.O. Box 11, Margate, Kent, CT9 1QX.**

SINCLAIR CALCULATORS

Cambridge kit	£14.95 (£1.80)
Cambridge Assembled	£16.95 (£2)
Executive with Memory	£27.95 (£3.05)
Executive with Memory	£34.95 (£3.75)
New Sinclair Scientific	£39.95 (£4.25)

FERRANTI ZN414

IC radio chip with data. £1.20 (23p). Also available kit of extra parts to complete a radio. £2.39 (40p). Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80

AFU	£8.95 (69p)
Z40	£5.45 (54p)
Z60	£6.95 (69p)
Q16	£7.70 (77p)
PZ5	£4.98 (49p)
PZ6	£7.98 (79p)
PZ8	£7.98 (79p)

Decoder. £7.45 (74p). Trans for PZ8. £3.35 (50p).
 Tuner. £11.95 (£1.19). Stereo 80. £11.95 (£1.19).
 Project 80S. £28.95 (£2.89).
 2 x Z40/Stereo 80/PZ5. £25.00 (£2.50).
 2 x Z40/Stereo 80/PZ5. £27.75 (£2.77).
 2 x Z60/Stereo 80/PZ8/Transformer. £33.11 (£3.31).
 Write for our most competitive quotation.




SINCLAIR GOES QUADRAPHONIC!

Introducing the Napoex QA10 self-contained matrix quadraphonic synthesizer. Just feed the output of a Project 80 stereo system into it and hook on 4 speakers to obtain the latest experience in sound. Send for free leaflet. Only £9.95 (£1.30).



SINCLAIR SUPER IC12

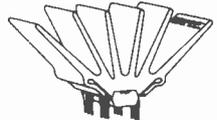6W r.m.s power. With 44 page booklet and printed circuit £2.10 (43p).



SWANLEY IC TOMORROW

£1.80 (40p)
 The world's most powerful IC amplifier. Similar to IC12 but rated at 10W r.m.s power. Supplied with data but no printed circuit. Write for leaflet.

DE LUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version. £1.60 (27p). Stereo model with balance control. £3.80 (48p).

IC12 POWER KIT

Supplies 28V 0.5A. £2.67 (50p).

LOUDSPEAKERS FOR THE IC12

5in 8 ohm. £1.10 (27p). 5in x 8in 8 ohm. £1.55 (37p).


PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics, and tuners. Mono model. £1.35 (25p). Stereo model. £2.40 (36p). Type 2 for ceramic or crystal pickups Mono. 65p (18p). Stereo. £1.30 (25p).

SEND S.A.E. FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAIN

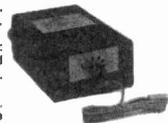
The most versatile battery eliminator ever offered. Switched output of 3, 4, 5, 7.5, 9 and 12V at 500mA, £4.15 (70p).
 Other eliminators stocked: 250mA—3 way switched model giving 5, 7.5 and 9V. £2.95 (60p). 50mA—6V. £1.80 (40p) 9V. £1.80 (40p); 7.5V cassette type. £2.25 (40p); Double 6V + 6V. £2.50 (45p); 9V + 9V. £2.50 (45p).



S-DECS AND T-DECS

S-DEC	£1.98 (31p)
T-DEC	£3.83 (47p)
u-DEC A	£3.98 (51p)
u-DEC B	£6.98 (81p)

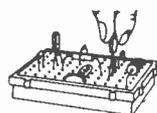IC carriers: 16 drill—plain, 81p (15p), with socket. £1.77 (25p); 10 TO5—plain, 78p (15p); with socket. £1.88 (24p).
 Experiment guides A £1.50 (26p), B £1.77 (29p), C 90p (15p), D £2.40 (35p), E £4.20 (53p).



SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ
 Please add the sum shown in brackets after the price to cover the cost of post and VAT.
 Official credit orders from schools, etc. welcome.
 No VAT charged on overseas orders

Digital Clock Kits



SPACE RESEARCH BRINGS YOU A DIGITAL CLOCK—WITH NO MOVING PARTS—FOR YOU TO BUILD

KIT O All components, including P.C.B. designed for easy home assembly. Bright and clear digits. Tough A.B.S. plastic case with contrasting front panel.

PRICE: £23.00 plus £2.30 VAT/Total £25.30 inc. post/pkg

Only our advanced design techniques make this low price possible. Kits are tested before they leave us and are covered by the P.E.A. money-back guarantee.




P.E.A. Ltd.
 35 High St, WELWYN,
 Herts. AL6 9EE

Please send me details of your clock kits

NAME _____

ADDRESS _____

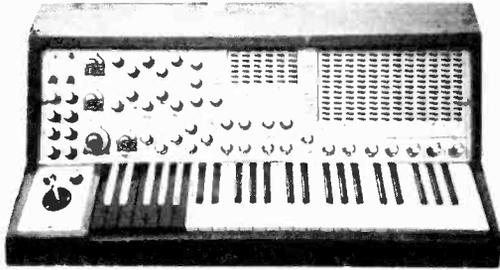BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. **OFT-1 chording module** £9. Modules (except VCO-1) guaranteed two years.

With over 10 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)
PROFESSIONAL MODULES

LATEST ADDITIONS INCLUDE PITCH-TO-VOLTAGE AND SEQUENCER MODULES! AND MANY OTHERS.

CASH SAVINGS

by buying modules and parts in bulk!

All modules are available separately:

Ring Modulator RM2, £8. Voltage-controlled Oscillator VC01, £10-50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5-50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

OSMABET LTD.

We make transformers amongst other things.

AUTO TRANSFORMERS, 110/200/220/240V.
30W, £1-70; 50W, £2-40; 75W, £2-85; 100W, £3-80; 500W, £10-80; 750W, £14-25; 1000W, £18-00, etc.

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c. 6.3V 1.5A, £1-80; 3A, £1-50; 6A, £2-55; 12V 1.5A, £1-50; 3A, £2-55; 6A CT, £3-40; 12V 1.5A CT, £2-55; 24V 1.5A CT, £2-55; 3A CT, £3-45; 6A, £4-80; 8A, £7-35; 12A, £10-85; 40V 3A CT, £4-50; 50V 6A CT, £13-50; 25V 2A + 25V 2A, £4-90; 12V 4A + 12V 4A, £4-90.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V

0-10-12-14-16-18V 2A, £2-80; 4A, £3-75; 0-12-15-20-24-30V 2A, £3-40; 4A, £4-50; 0-5-20-30-40-60V 1A, £3-40; 2A, £4-50; 0-40-50-60-80-90-100-110V 1A, £4-90.

MIDGET RECTIFIER TRANSFORMERS.

For FW rect. 200/240V a.c. 9-0-9V 0.3A; 12-0-12V 0.25A; 20-0-20V 0.15A, 6V 0.5A + 6V 0.5A; 9V 0.35A + 9V 0.35A; 12V 0.25A + 12V 0.25A or 20V 0.15A + 12V 0.15A at £1.65 each; 9-0-9V 1A, £1-35; 12-0-12V 1A or 20-0-20V 0.75A £1-50 each.

MAINS TRANSFORMERS

Prim. 200/240V a.c. TX6 sec., 425-0-425 500 Ma, 6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A, £16-50; TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £9-75; MT3 Prim. 0-110-240V sec.

250V 100 Ma, 6.3V CT, E/S, £2-70.

O/P TRANSFORMERS FOR POWER AMPLIFIERS

P.P. sec, tapped 3-8-10ohms, A-A 6-6K Ω 30W, £5-70; A-A 3K Ω 50W, £9-00; 100W (EL34 KT88, etc.), £15-75; tapped Multi O/P 10W £3.

G.E.C. MANUAL OF POWER AMPLIFIERS

Covering valve amplifiers of 30W to 400W 8p.

LOUDSPEAKERS FOR AMPLIFIERS

BAKER 25W, £7-60; 35W, £3-40; HI-FI Major Module 20W w/tweeter Xover, £11-80; Baker speaker lists; FANE 50W, £10-50; 60W, £13-50; HI-FI speakers, EMI bass 13 x 8in 3 or 15 Ω , £2-00; 5in 8 Ω , £1-15; 7 x 4in 15 Ω , £1-60; 8 x 5in 3, 8, 15, 25 or 80 Ω , £1-75 each.

LOUDSPEAKERS

7in 8, 15 or 75 Ω , 2in 8 or 25 Ω , 3in 3, 8, 25 or 35 Ω , 3in 8, 15 or 80 Ω 80p each; 5in 3, 8 or 25 Ω , 6 x 3in 3 or 8 Ω , £1-05; 7 x 4in 3 or 15 Ω , 6in 3 Ω , £1-25; 10 x 6in 3 Ω , £1-50.

SPEAKER MATCHING TRANSFORMERS

12W 3 to 8 or 15 Ω up or down £1-30.

"INSTANT" BULK TAPE/CASSETTE ERASER

Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads. 200/240V a.c. £3-25.

SYNCHRONOUS GEARED MOTORS, 230/240V.

Brand new, Smiths. Built-in gear box, 2 RPH, 75p each.

Carriage and VAT on all orders.

S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YQ
Tel. 01-958 9314

RADIO AMATEUR'S HANDBOOK 1974

by THE A.R.R.L.

Price £2-95

TEST EQUIPMENT FOR THE RADIO AMATEUR by H. L. Gibson. Price £2. 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. Price £1-30.

HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS by Leonard C. Lane. Price £1-70.

RAPID SERVICING OF TRANSISTOR EQUIPMENT by Gordon J. King. Price £2.

TELEVISION ENGINEERS' POCKET BOOK by P. J. McGoldrick. Price £2-65.

HOW TO USE INTEGRATED CIRCUIT LOGIC ELEMENTS by Jack W. Streater. Price £1-40.

WORLD RADIO AND T.V. HANDBOOK 1974 by J. M. Frost. Price £3-20.

THE MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal. Price £4.

ELECTRONIC ORGAN SERVICING GUIDE by R. G. Middleton. Price £2-40.

* ALL PRICES INCLUDE POSTAGE *


THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

INTER-LOCKING PLASTIC STORAGE DRAWERS

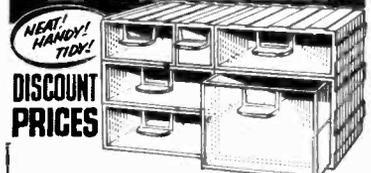

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £1-75 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). £3 DOZEN.

TREBLE (3D) £2-90 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4-25 for 8.

EXTRA LARGE SIZE (6DI) £3-90 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7½% in the £
Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES
Please add 10% V.A.T. to total remittance

FLAIR (Dept. PE8) 124 Cricklewood
Broadway, London, N.W.2
Tel. 01-450 4844

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE01, Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers—A.M.S.E. (Mech.) Institute of Engineers & Technicians (A.M.I.E.) CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) General Draughtsmanship Elec. Draughtsmanship Architectural Draughtsmanship Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works Construction Surveyors Institute—L.C.S.I. CITY & GUILDS General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities. Estimates Hydraulics Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers—A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS Radio, TV Electronics CITY & GUILDS Telecoms. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Acctnts. Computer Programming Works M'ment. Work Study Gen. Production Eng. Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I. MAA/IMI CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage M'ment. ARB Aero Engineering Certs. Gen. Aero Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers—A.M.S.E. (Civ.) Institute of Building—L.I.O.B.		G.C.E. — choose from 58 'O' & 'A' level subjects.

Supplementary courses for Nat. Certificates.

G.C.E.
— choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE01, Aldermaston Court, Reading RG7 4PF

QN

BPE01.

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____

AGE _____

Accredited by C.A.C.C.

Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/asia) Ltd. South Africa—Central News Agency Ltd. Publishers' Subscription Rate (including postage): Inland £3 25, Overseas £3 50

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi-Fi and Transistors - Up to date
Brochures on request

**HENRY'S
CATALOGUE**

Due to rapid price changes
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug. Sept 1974

You pay less
VAT with Henry's
Low Prices

Now built and
used by thousands
of satisfied cus-
tomers.

FEATURES: slim
design, overall size in
cabinet 15 1/2in x 2 1/2in x 6 1/2in

6-IC's, 10 transistors, stabilisers,
Gardners low field transformer, Fibre
Glass PC Panel, complete chassis work.
Now available built and tested as well
as in kit form.

**HIGH QUALITY & STABILITY ARE
PREDOMINATE FEATURES—DEVELOPED
TEXAS ENGINEERS FOR PERFORMANCE, BY
RELIABILITY AND EASE OF CONSTRUCTION,
FACILITIES.** On/off switch indicator, headphones
socket, separate treble, bass, volume and balance controls,
scratch and rumble filters, mono/stereo switch, input selector;
Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc.
Constructional details Ref. No. 21, 30p.
Distributed by Henry's throughout UK.


FREE Teak cabinet with complete kit.

KIT (+ VAT + 50p
PRICE **£28.50** carr/packing) or
built and tested **£35.00** (+ VAT + 50p
carr/packing) as illustrated

BUILD THE TEXAN

**20 + 20 WATT IC STEREO
AMPLIFIER**

As featured by
Practical Wireless 1972

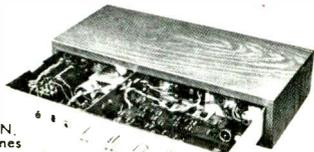

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner.
Features variable capacity diode tuning, stabiliser power supply, IC
Decoder, high gain low noise, IF stages, LED
indicators, Tuning meter, AFC,
Easy to construct and use.
Mains operated. Slim
modern design with fibre
glass PC, teak cabinet,
etc. Available as a kit to
build or ready built.
Overall size: 8in x 2 1/2in
x 6 1/2in. Produced to give
high performance with a
realistic price. (Parts list
and constructional details
Ref. No. 5, 30p.) Henry's
are sole distributors UK and Europe.



Kit Price £21.00 (+ VAT)
or built and tested **£24.95 (+ VAT)**

**LIVING SOUND LOW NOISE TOP QUALITY CASSETTES
MADE BY EMI TAPES LTD. TO INTERNATIONAL
STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID
LESS THAN 1 REC. PRICES. COMPLETE WITH LIBRARY
CASES.**

	3 for	6 for	10 for	25 for
C60	£1.10	£1.98	£3.00	£7.40
C90	£1.46	£2.80	£4.60	£11.25
C120	£1.80	£3.45	£5.50	£13.45



Quantity and trade enquiries invited.

LEARN A LANGUAGE—complete with phrase book. German,
French, Spanish, Italian. £1.36 per course. £5 for any 4.

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



DISCO MINI 1: A complete portable disco,
fitted mixer/preamp, 2 decks all facilities... **£98.50**
As above but with Slider Controls **£118.50**
100 watt amplifier for above **£49.50**
SDLS100: 100 watt mixer/amplifier with
slider controls **£69.00**
R50: 50 watt mixer/amplifier **£49.50**
R100: 100 watt mixer/amplifier **£57.50**
DISCO AMP: 100 watt mixer/amplifier
Northcourt **£73.00**
400 40 watt mixer amp **£37.50**
800 80 watt mixer amp **£45.00**

DISCO MIXER PREAMPLIFIERS (O/P
for up to 6-100 watt amplifiers):
SDL1 (rotary controls): **£49.50**
SDL11 (slider controls): **£58.50**
DISCO VOX (slider controls): The complete
disco preamp... **£72.00**
DJ100: 100 watt power amplifier for above
DJ30L Mk I: 13 channel 3kW sound to light **£49.50**
DJ30L Mk II: Slider Controls **£41.25**
DJ DISCLITE: As 30L/II + Variable speed
flashes... **£45.50**
Carlsbro Reverberation Unit... **£54.00**
Disco anti-feedback microphone... **£44.00**
Colt 150 watt liquid wheel projector... **£11.95**
150 watt QI liquid wheel projector... **£23.50**
150 watt QI cassette wheel projector... **£50.00**
Spare Effects and Liquid cassettes, large
range of patterns... **£50.00**
6in liquid wheels £5.00 Various Cassettes **£6.00**
Mini spot bank fitted 3 lamps... **£12.95**
Auto Trilite (mini with flashes)... **£17.00**
Bubblemaker with 1 gal. liquid... **£22.50**

MIXERS/MICS/SPEAKERS/LIGHTING
U.K.'s largest range of Disco lighting
FREE STOCK LIST Ref. No. 18 ON REQUEST
AKG/RESLO/DJ/CARLSBRO/EAGLE
CHASSIS AND COMPLETE SPEAKER
SYSTEMS, MEGAPHONES, TURNTABLES,
PUBLIC ADDRESS COMPONENTS, MICS.,
STANDS, MIXERS, CABINETS



All prices carr. paid (UK) (VAT EXTRA).
Barclaycard/Access call, write or phone your order
01-723 6963—easy terms for callers.

EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter
systems. Bin Bass/Midbore
and Melinex Domed HF Radiator plus
crossover **£12.50** per pair of systems
(carr/pack. 40p) or built into ven-
eer cabinets, size 18 x 12 x 6 1/2in.
£19.50 pair (carr. £1).

HI-FI TAPE EQUIPMENT



U.K.'s largest range
with discounts and
demonstrations for
callers. Latest stock lists on request
(Ref. No. 17).
Phone 01-402 4736 for Barclay/Access
Card, Direct orders and latest prices.

TRANSISTORS SEMICONDUCTORS

U.K.'s largest range for every applica-
tion. Small quantity discounts.
Also Trade, Export and Industrial
enquiries invited. Latest stock list
(Ref. No. 36). Including valves on
request.

ELECTRONICS SUPPLIES

Specialists in electronics for more
than 30 years. Trade and industry
supplies—every type of component
and equipment.

SINCLAIR PROJECT 80



Stereo Preamplifier... **£11.95**
Audio Filter Unit... **£6.95**
Z40 15 watt Amplifier... **£5.45**
Z60 25 watt Amplifier... **£6.95**
PZ5 Mod. for 1 or 2 Z40... **£4.98**
Z40... **£7.98**
PZ8 Mod. (S Tab) 1 or 2... **£7.98**
Z60... **£7.98**
TRANSFORMER FOR... **£3.95**
PZ8... **£11.95**
NEW FM TUNER... **£11.95**
STEREO DECODER... **£7.45**
All items post paid.

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene con-
tainer and taking about 3 hours to assemble—
that's the Sinclair Cambridge pocket calculator
from Henry's. Some of the many features include
interface chip, thick-film resistor pack, printed
circuit board, electronic components pack.
Size: 4 1/2in long x 2 1/2in wide x 1 1/2in deep.
Free of charge with the kit for the more advanced
technologist is a 32-page booklet explaining how
to calculate Logs, Tangents, Sines, etc.



SPECIAL OFFER
Price **£13.60 (+ VAT)**

Also assembled **£19.95 (+ VAT)**
ready to use

10% VAT TO BE ADDED TO ALL ORDERS. EXPORT SUPPLIED. Prices and descriptions correct at time of proof. Subject to change without notice
E & O E. See page 658 of this magazine.

ALWAYS BARGAINS FOR CALLERS

Henry's RADIO
LIMITED
EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
303 Bargains Store (Callers only) 01-723 6963
Home and Car Entertainment Centres London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm six days a week
Hi-Fi—Tape Equipment
Discount Stock List
Free at all stores

130 LOVE