

PRACTICAL



ELECTRONICS

DECEMBER 1974

25p

FREE! *in this issue*

TRANSISTOR LEAD IDENTICHART

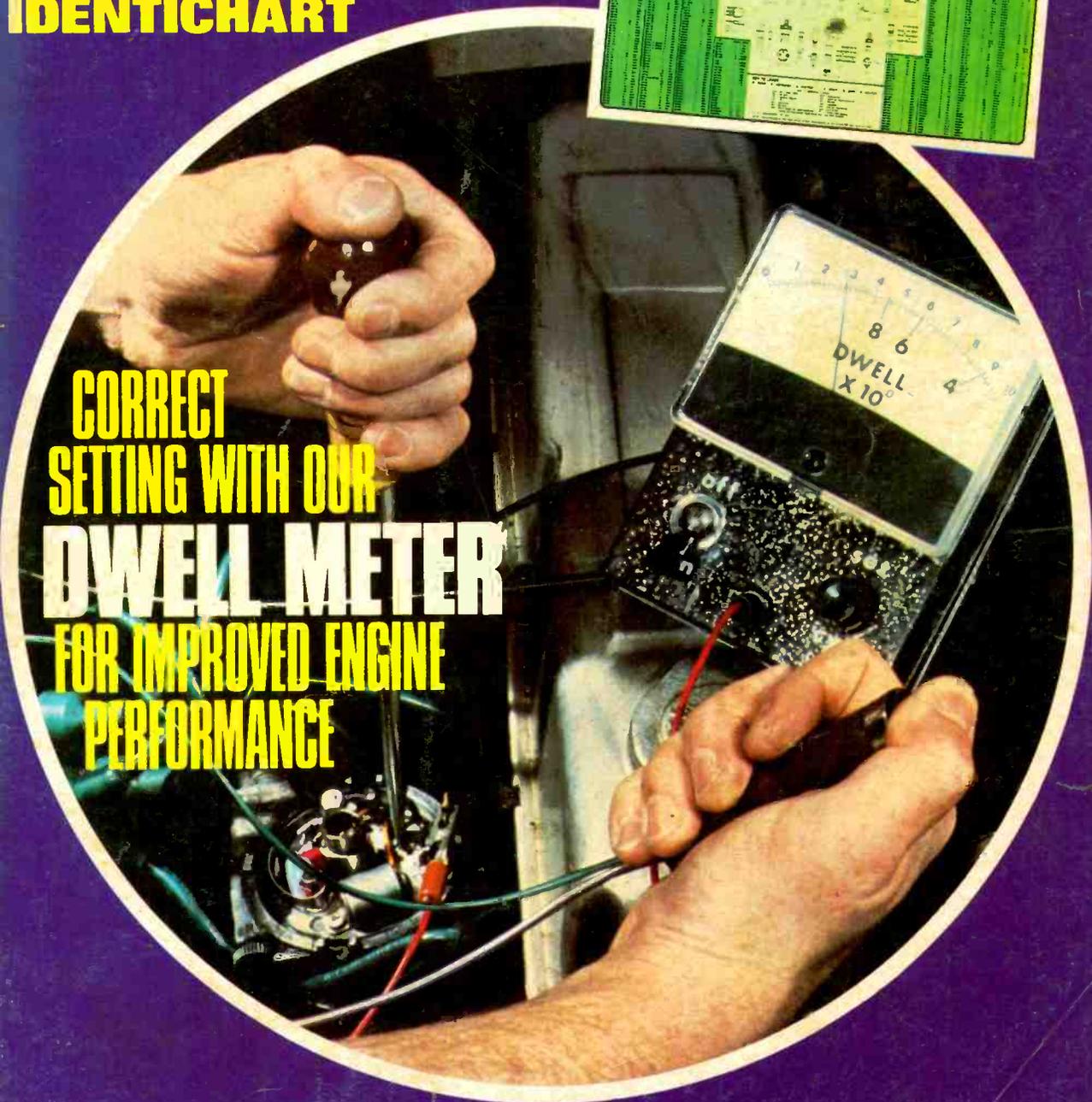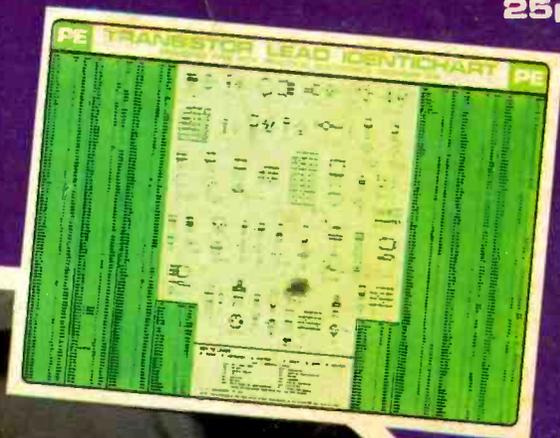

**CORRECT
SETTING WITH OUR
DWELL METER
FOR IMPROVED ENGINE
PERFORMANCE**

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- 7 Transistor Loudspeaker Radio MW/LW
- 2 Transistor Regenerative Radio
- Signal Tracer
- 5 Transistor Short Wave Radio
- 3 Transistor Regenerative Radio
- Transistor Tester NPN — PNP
- Electronic Metronome
- Audible Continuity Tester
- 4 Transistor Push Pull Amplifier
- Electronic Noise Generator
- Sensitive Pre-Amplifier
- 5 Transistor Push Pull Amplifier
- Batteryless Crystal Radio
- One Transistor Radio

TOTAL BUILDING COSTS

£7-23 P.P. & INS. 44p
(Overseas P.P. £1-85p)
(+8% VAT 37p)


Components include:

- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 31" Loudspeaker
- Earpiece
- Mica baseboard
- 3 12-way Connectors
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.
- Parts price list and plans 60p (free with parts)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7 1/2" x 2 1/2" approx. Parts price list and plans 30p (FREE with parts).

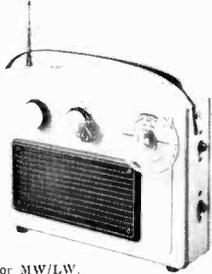


TOTAL BUILDING COSTS

£6-95 P.P. & INS. 44p
(Overseas P. & P. £1-85)
(+8% VAT 55p)

POCKET FIVE


NOW WITH 3" LOUDSPEAKER

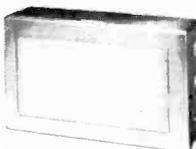3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 3 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and parts price list 15p (FREE with parts).



Total Building Costs

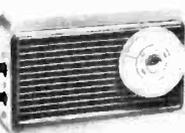£2-50 (+8% VAT 20p)
P.P. & Ins. 26p
(Overseas P.P. & P. £1-25)



TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).

Total Building Costs
£2-75 P.P. & Ins. 26p
(+8% VAT 21p)
(Overseas P. & P. £1-25)

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9 1/2" x 5 1/2" x 2 1/2" approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS
£2-95 (+8% VAT 23p)

P.P. & INS. 30p
(OVERSEAS P. & P. £1-25)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS
£3-60 (+8% VAT 29p)

P.P. & INS. 30p
(OVERSEAS P. & P. £1-25)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and easy build plans 20p. Free with parts.

TOTAL BUILDING COSTS
£4-08 (+8% VAT 32p)

P.P. & INS. 31p
(OVERSEAS P. & P. £1-85p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, L, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4 1/2 volt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 1/2" x 7 1/2" x 4 1/2" approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS
£6-98 (+8% VAT 56p)


P.P. & INS. 47p
(OVERSEAS P. & P. £1-85)

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

8 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW, and LW. Telescopic aerial for short waves. 3in speaker. 8 unproved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 1/2" x 5 1/2" x 2 1/2" approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

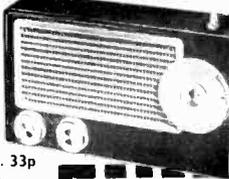£4-48 P.P. & INS. 33p
(OVERSEAS P. & P. £1-25)
(+8% VAT 36p)



ROAMER SIX CASE AND LOOKS AS TRANS EIGHT


8 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 1/2" x 5 1/2" x 2 1/2" approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS

£3-98 P.P. & IN. 31p
(OVERSEAS P. & P. £1-85)
(+8% VAT 32p)

ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4 1/2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9 1/2" x 7 1/2" x 4 1/2". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

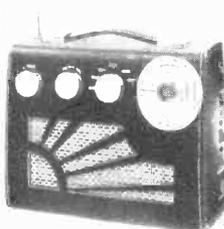

TOTAL BUILDING COSTS

£8-50 (+8% VAT 68p)

P.P. & INS. 52p
(OVERSEAS P. & P. £1-85)



EDU-KIT

Build Radios Amplifiers, etc., from easy stage, diagrams.

Five units including master unit to construct.

Components include: Tuning Condensers: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1in Knobs: Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

£5-50 (+8% VAT 44p)

P.P. & INS. 33p
(OVERSEAS P. & P. £1-85)

RADIO EXCHANGE LTD

*Callers side entrance "Lavells" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52867 Reg. No. 788372

I enclose £ _____ for _____

Name _____

Address _____

PE12

PRACTICAL ELECTRONICS

VOLUME 10 No. 12 DECEMBER 1974

CONSTRUCTIONAL PROJECTS

- DWELL METER** *by S. Jones*
Check points and distributor bearings with this novel vehicle instrument 1052
- P.E. CCTV CAMERA—4** *by G. D. Bishop*
A choice of two u.h.f. modulators 1056
- P.E. MINISONIC—2** *by G. D. Shaw*
Details of the voltage controlled oscillator, voltage controlled filter, and envelope shaper/voltage controlled amplifier 1066
- I.C. PULSE GENERATOR** *by M. E. Theaker*
A low-cost source of logic test pulses 1076
- THERMOMETER/CONTROLLER** *by J. N. Jones*
A -68°C to $+175^{\circ}\text{C}$ diode thermometer with analogue readout or control function abilities 1084

GENERAL FEATURES

- NEW DEVICES . . . APPLICATIONS**
Phase locked loop for high performance f.m. receivers 1082
- INGENUITY UNLIMITED**
Neon Oscillator—Zener Diode Check—Integrated Triffid—Optical Communication—555 Ramp Generator 1090

NEWS AND COMMENT

- EDITORIAL—Self Service** 1051
- THE NEXT DECADE**
Readers look to the future of electronics 1060
- SPACEWATCH** *by Frank W. Hyde*
The New Jupiter 1062
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith*
Electronics and music 1065
- NEWS BRIEFS**
Ceefax and Oracle 1083
- BOOK REVIEWS**
Selected new books we have received 1088, 1094
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 1089
- PATENTS REVIEW**
Thought provoking ideas on file at the British Patent Office 1097
- READOUT**
A selection of readers' letters 1098

SPECIAL DATA SHEET FREE INSIDE THIS ISSUE TRANSISTOR LEAD IDENTICHART


At-a-glance details on over 700 transistors

Our January 1975 issue will be published on Friday, December 13, 1974

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £4.10. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

NOW AVAILABLE IN THE U.K!

CHINAGLIA

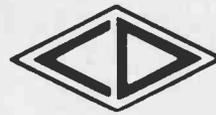


PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

**CORTINA MINOR
33 RANGE POCKET MULTIMETER**

- SENSITIVITY 20,000Ω/VOLT (D.C.), 4,000Ω/VOLT (A.C.).
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0-100mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1,500V, D.C. CURRENT 0-50μA, 5mA, 50mA, 500mA, 2.5A, A.C. VOLTS, 0-7.5V, 25V, 75V, 250V, 750V, 1,500V, A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A, dB RANGES, -10 to +69, AF VOLTS RANGES 0-1,500V, RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100μF, IF F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, ±2.5%, A.C. VOLTAGE AND CURRENT ±3.5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 x 85 x 40mm, 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

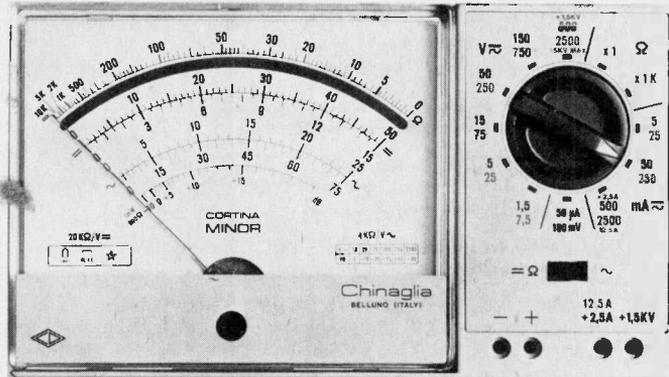

METER PRICE £15.40 (p & p 80p) PROBE £8.80 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone :-

CHINAGLIA (U.K.) LIMITED

19 Mulberry Walk, London S.W.3.

Telephone 01-352 1897

TRADE ENQUIRIES WELCOMED

NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

BASIC TV COURSE, by George Kravitz	£1-50	10 MINUTE TEST TECHNIQUES FOR PC SERVICING, by Art Margolis	£1-60
NEW SKILL-BUILDING TRANSISTOR PROJECTS AND EXPERIMENTS, by Louis E Gardner Jr	£1-45	TV BENCH SERVICING TECHNIQUES, by Art Margolis	£1-65
RADIO CONTROL HANDBOOK, by Howard G McEntee	£1-90	MINIATURE PROJECTS FOR ELECTRONIC HOBBYISTS, by Ken W Sessions Jr	£1-45
TRANSISTORS: THEORY AND PRACTICE, by Rufus P Turner	£1-40	FM STEREO/QUAD RECEIVER SERVICING MANUAL, by Joseph J Carr	£1-55
WORKING WITH SEMICONDUCTORS, by Albert C W Saunders	£1-50	TROUBLESHOOTING SOLID-STATE WAVE GENERATING AND SHAPING CIRCUITS, by Ben Gaddis	£1-55
CASSETTE TAPE RECORDERS—HOW THEY WORK—CARE AND REPAIR, by Walter Salm	£1-60	THE 2-METRE FM REPEATER CIRCUITS HANDBOOK, by Ken W Sessions	£1-90
ELECTRONIC MEASUREMENTS SIMPLIFIED, by Clayton Hallmark	£1-70	PINPOINT TRANSISTOR TROUBLES IN 12 MINUTES, by Louis E Gardner Jr	£2-50
SOLID-STATE CIRCUITS GUIDEBOOK, by Brice Ward	£1-75		



FOULSHAM-TAB LTD.
YEovil ROAD, SLOUGH, BUCKS.

A V.C.O. by Fhachi

1Hz to 100kHz

FOR £5.75 P. & P. 15p

Size: 2in long x 1½in wide x ½in high.
Input: 12-24V d.c. (not centre tapped), 18V input giving 10V constant amplitude output.
Requires only a 1MΩ pot to tune entire range—or can be swept with a saw tooth input.
Enormous possibilities—music, synthesisers, filters, communications, frequency modulation, etc.
Detailed application sheet with all purchases.

FHACHI RAMP MODULE FX21

24V d.c. input for 18V sawtooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100kHz (eg 50 mfd electrolytic gives sweep of approx. 1 cm per second). In or out sync capability. Price £5.75 P. & P. 15p

FHACHI FILTER MODULE FX31

Designed for use with VCO FX11 and RAMP FX21. This completes the 3 building blocks required for a basic low-frequency Spectrum Analyser that covers 100Hz to 50kHz. The additional components required are discrete resistors and capacitors, etc. (No inductances or specialised components are needed.) Price £13 P. & P. 30p.
Fibre glass P.C. board to mount FX11, 21 and 31 ready drilled. Connection details and list of additional components required supplied with each order £2.50. P. & P. 30p.

LOW FREQUENCY WOBBLATOR

Intended for alignment of AM Receivers, 250kHz to 5Mhz, but effective to 30MHz. 3 controls—RF level: sweep width and frequency. Requires 6V a.c. and any general purpose scope Model LX63—£8.50 P. & P. 35p. Model LX63E—as above. Can be extended down to 20kHz by addition of capacitors. Price £11.50. P. & P. 35p (not cased, not calibrated).
Both models are supplied connected for automatic 50Hz sweeping. An external sweep voltage can be used instead.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY



CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel. Reading 582605.65816



PHONOSONICS

SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light! Can be used with most audio systems and lamp intensities. A must for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors)	£11-48
8 channel component set (excl. thyristors)	£20-32
Power supply component set	£4-78
PCB for 4 frequency channels	£2-50
PCB for power supply and 8 lamp drivers	£1-25

CCTV CAMERA

Details in List

VOICE OPERATED FADER

For automatically reducing music volume during talk-over—particularly useful for Disco work, or for home-movie shows.

Component set, incl. PCB	£2-95
--------------------------	-------

GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system specifications for which are shown in detail in our list together with semiconductor requirements.

Main Amplifier:	
Set of resistors, capacitors and presets	£5-96
Stereo printed circuit board	£1-28
Pre-Amplifier:	
Set of resistors, capacitors, potentiometers and switches—	
Standard Tolerance Set	£10-57
Superior Tolerance Set	£16-04
Stereo PCB (as Published)	£2-20
Regulated Power Supply:	
Set of resistors, capacitors and preset	£4-58
Printed circuit board	72p

HI-FI TAPE LINK

Designed for use with reasonable quality tape decks this high performance pre-amp includes record playback and metering circuits.

Stereo component set (excl. panel meter)	£22-05
Mono component set (excl. panel meter)	£13-31
Power supply component set	£3-72
Stereo main PCB	£2-50
Stereo sub-assembly PCB	86p

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB)	£2-30
Regulated power supply (including printed circuit board)	£3-71

PROJECT Q4

Multi-system Quadraphonic Decoder

Decoder component set	£13-74
Power supply components	£3-22
Set of PCBs	£2-60

SEMICONDUCTOR TESTER

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and sub-assembly PCB (fuller details in list)	£6-06
--	-------

PHASING UNIT

A simple but effective manually controlled unit for introducing the phasing sound into live or recorded music.

Component set (incl. PCB)	£2-20
---------------------------	-------

SOUND SYNTHESISER


The well-acclaimed and highly versatile Synthesiser published in P.E. Feb. 1973 to Feb. 1974.

Component sets and printed circuit boards. Full details in list	
---	--

RHYTHM GENERATOR

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures.

Tempo, Timing and Logic Circuit	£17-25
Component set (excl. switches)	£2-30
Double-sided PCB for above	
Mixer, Pre-amp and Effects Circuits	£12-70
Component set	£2-67
PCB (Illustrated)	
Monitor Amplifier	£3-10
Component set and PCB	
Power Supply	£5-65
Component set and PCB	

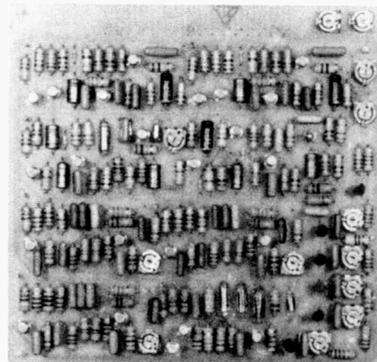

AUDIO MILLIVOLTMETER

Wide-ranges and good accuracy. Component set (excl. meter).

Component set (excl. meter)	£5-23
-----------------------------	-------

ULTRASONIC TRANSMITTER-RECEIVER

A highly sensitive and long range invisible beam detection circuit with numerous applications.

Component set with PCBs but excluding transducers	£4-40
---	-------

RONDO

PCB details in List.

POWER SLAVES

PCB details in List.

ELECTRONIC PIANO

Details in List.

HOME INTERCOM

Details in List.

SOUND BENDER

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency doubler.

Component set	£5-83
Printed circuit board	£1-44

REVERBERATION UNIT

A high-quality unit having microphone and line input, pre-amps and providing full control over reverberation level.

Component set (excl. spring unit)	£6-44
Printed circuit board	£1-40

MINISONIC

Details in List

8W AMPLIFIER

A moderately powered amplifier of more than average performance.

Main Amplifier:	
Mono component set	£4-18
Stereo component set	£8-36
Mono printed circuit board	72p
Pre-Amplifier:	
Mono component set	£2-50
Stereo component set	£6-46
Stereo PCB	£1-66
Power Supply	£3-90
Component set	

BIOLOGICAL AMPLIFIER

Multi-function circuits that with the use of other external equipment, can serve as lie detector, alphascope, cardiophone etc.

Pre-Amplifier Module	
Component set and PCB	£3-48
Basic Output Circuits	
Combined component set with PCBs for alpha- phone, cardiophone, frequency meter and visual feedback lamp driver circuits	£4-96
Audio Amplifier Module	
Type PC7	£5-20

PHOTOPRINT PROCESS CONTROL

For colour and B & W an indispensable dark-room unit for finding exposure, controlling enlarger timing and stabilising mains voltage.

Component set (excl. meter)	£8-85
Printed circuit board	£1-60

ENLARGER EXPOSURE METER AND THERMOMETER

Dual-purpose dark-room unit with good accuracy.

Component set with PCB but excluding meter	£4-00
--	-------

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set incl. PCB	£2-40
-------------------------	-------

PCB LAYOUT AND
CIRCUIT DIAGRAMS
SUPPLIED WITH ALL
PCBs DESIGNED BY
PHONOSONICS

P. & P.
Add 18p to all orders

VAT
Add 8% (or current
rate if different) to
total order cost, in-
cluding P & P

LIST
Send S.A.E. for free list
giving fuller details of
kits, PCBs and other
components

OVERSEAS
P & P will be charged at cost.
VAT does not currently apply. List
gives fuller details including kit
weights. Charge for list: Europe
10p other countries 20p

COLOUR CODE
IDENTIFICATION
SUPPLIED WITH MOST
KITS AND AS PART OF
LIST

Semiconductors				Integrated Circuits				Zeners				Electrolytic Capacitors (µF/V)				Polyester (µF)		Tantalum (µF)	
AC129	20p	MJE3055	75p	709 TO5	40p	723 TO5	95p	3 3V 400mW	12p	0 47 63V	6p	47 63	7p	470 40	20p	0 1 35	12p		
AC135	20p	NKT0033	112p	741 8-pin DIL	40p	742 TO5	20p	4 7V 1W	25p	1 0 83V	6p	50 6 4	48p	500 64	48p	0 22 35	12p		
BC107	13p	OC28	65p	747 14-pin DIL	115p	748 TO5	63p	6 2V 400mW	15p	1 5 83V	6p	100 10	20p	680 6 3	20p	0 47 35	12p		
BC108	13p	OC71	14p	748 8-pin DIL	63p	748 8-pin DIL	63p	6 2V 400mW	15p	2 2 83V	6p	100 25	10p	680 6 3	20p	1 0 35	12p		
BC109	13p	OC84	25p	748 14-pin DIL	63p	7400	20p	9 1V 400mW	15p	4 7 63	6p	100 40	7p	680 40	10p	2 2 35	12p		
BC147	12p	ORP12	55p	7400	20p	7402	20p	11V 1W	20p	6 8 40	6p	100 10	14p	1000 10	14p	4 7 35	12p		
BC148	12p	ZTX107	12p	7402	20p	7420	20p	12V 400mW	15p	10 63	6p	1000 16	25p	1000 16	25p	10 16	12p		
BC149	12p	ZTX593	15p	7420	20p	7447	175p	12V 1 3W	20p	10 25	6p	150 63	12p	1000 25	25p	10 25	16p		
BC157	13p	ZTX531	23p	7447	175p	7473	44p	16V 400mW	15p	20 25	6p	220 10	6p	1000 40	40p	15 6 3	16p		
BC158	13p	2N706	13p	7473	44p	7489	575p	18V 1W	20p	15 40	6p	220 16	6p	2200 25	45p	15 6 3	16p		
BC159	13p	2N914	22p	7489	575p	µA7815 TO3	250p	20V 400mW	15p	33 6 3	6p	220 40	50p	2200 40	50p	15 6 3	16p		
BC182L	12p	2N1304	22p	µA7815 TO220	250p	CA3046	69p	20V 1 3W	23p	33 16	6p	220 100	350p	2200 100	350p	15 6 3	16p		
BC204	14p	2N2219	27p	CA3046	69p	MFC6040	95p	27V 400mW	15p	33 40	6p	3300 63	133p	3300 100	350p	22 16	16p		
BC209	14p	2N2905	27p	MFC6040	95p	PA263	169p	Thyristors		47 25	6p	4700 16	60p	4700 16	60p	15 6 3	16p		
BC212L	15p	2N2907	22p	SG3402N	169p	Thyristors		1A 400V	75p	47 40	6p	470 10	10p	4700 16	60p	15 6 3	16p		
BC478	29p	2N3054	36p	Minitron 3015F	225p	Thyristors				47 40	6p	4700 10	75p	4700 10	75p	15 6 3	16p		
BCY71	22p	2N3055	30p							47 40	6p	4700 10	75p	4700 10	75p	15 6 3	16p		
BFY50	22p	2N3062	12p							47 40	6p	4700 10	75p	4700 10	75p	15 6 3	16p		
BFY52	23p	2N3703	12p							47 40	6p	4700 10	75p	4700 10	75p	15 6 3	16p		
BSY95A	12p	2N3704	12p							47 40	6p	4700 10	75p	4700 10	75p	15 6 3	16p		
MJE2955	110p	2N3819	35p							47 40	6p	4700 10	75p	4700 10	75p	15 6 3	16p		

PRICES ARE CORRECT AT TIME OF
PRESS. E. & O.E. DELIVERIES
SUBJECT TO AVAILABILITY.

PHONOSONICS, DEPT. PE2D, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL
Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and plus 25p Control Switch. **£7-50 P. & P.**



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at **£7-50 plus 10p.**

MINIATURE RELAYS
Brand new range of British made relays, size: 1 1/2in x 1in x 1/2in. All two changeovers with 250V 1-5A contacts and suitable for fitting on 0.1m veroboard.
Type Volts Current Ohms
27/A 12V 17mA 700 All
21/A 12V 23mA 430 £1.30
12/A 6V 33mA 195 each
200/250V Mains Relay
Heavy duty contacts 2,500 ohm coil. All main and unused D.F.D.T. mains relays 50p. Carr. free. Special quantity £40 per 100 off.

MIDGET MAINS TRANSFORMER
Varnish Impregnated
Size 45mm x 36mm x 31mm
PRI 240V
Sec 3-0-3 100mA
Sec 3-0-6 100mA
Sec 9-0-9 100mA
Sec 12-0-12 100mA
Sec 20-0-20 100mA
£1.23 10p P. & P.

CRESCENT BUBBLE LIGHTSHOW
This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 16ft.
Motor—1 rev. per 2 min.
Liquids—Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, £15; Wheel, £5; Total £20. Plus 75p carr.

7in x 4in LOUSPEAKER
A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1-80. Free postage on this item.

U.K. CARRIAGE 15p UNLESS OTHERWISE STATED
VAT 8% VAT TO BE ADDED TO ALL ORDERS
SEND 20p FOR A CRESCENT CATALOGUE

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (80W into 16 ohm).

★ THE PRE-AMP MODULE
Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ THE POWER SUPPLY
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. **£25, carr. 75p.** Send S.A.E. for further details on this or our ready built amplifiers.

12-0-12V 500M/A
240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our Price **£1-20.**

18V 500M/A
240V tapped 120V with screen. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our Price **£1 each.**

BARGAIN BOX
Loud buzzer mounted in a metal box complete with two U2 battery size holder. Designed and can be used as a fire alarm but is ideal as a door or Morse code practise buzzer. Approx. size: 2 1/2in x 6 1/2in x 1 1/2in. **OUR PRICE 50p**

ABS PLASTIC BOXES
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 45mm 50p; 1006, 150mm x 73mm x 47mm 65p; 1007, 184mm x 124mm x 60mm 85p; 1021, 106mm x 74mm x 45mm (sloping front) 50p.

BARGAIN BOARDS
Components galore for the experimenter. Ex-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boxes **£1.**

2in. PANEL METERS
Size 59mm x 46mm
0-50µA—ME6
0-100µA—ME7
0-500µA—ME8
0-1mA—ME9
0-5mA—ME10
0-10mA—ME11
0-50mA—ME12
0-100mA—ME13
0-500mA—ME14
0-1A—ME15
0-50V a.c.—ME16
0-300V a.c.—ME17
S meter—ME18
V.U. meter—ME19
£3 each. 10p P. & P.

POWER PACKS
PP1 Switched 3-6-7-9V 400M/A Transistor and Zener Stabilised On/Off switch and Polarity Reversal switch, in a black metal case, **£5-25 each.**
PP2 Switched 6-7-9V Battery Eliminator. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Ideal for cassette recorders, **£2-75 each** (Philips type **£3-00**).
PP3 Car converter. From 12V Pos. or Neg. to ± 6-7-9V. Easy to fit and transistor regulated. **£2-50 each.**

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18-50 plus 38p P. & P.

MINI LOUSPEAKERS
2 1/2in 8 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P. & P. on each L.S.



RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 5p for first transistor, 1p thereafter, over ten pence. INTEGRATED CIRCUITS 6p + 1p each added

1N21	1P	FAZ11	1-15	BY213	0-25	OAZ205	0-45	Z8170	0-10
1N23	0-35	AFZ12	0-45	BY210	0-45	OAZ206	0-45	Z8271	0-15
1N65	0-85	ASY26	0-25	BY211	0-40	OAZ207	0-45	Z8272	0-25
1N263	0-50	ASY28	0-25	BY213	0-35	OAZ208	0-40	ZT43	0-25
1N251	0-40	ASY29	0-30	BY215	0-25	OAZ209	0-40	ZTX107	0-12
1N645	0-16	ASY30	0-25	BY216	0-25	OAZ210	0-40	ZTX108	0-10
1N728A	0-20	ASY36	0-25	BY216	0-60	OAZ211	0-40	ZTX300	0-14
1N914	0-08	ASY60	0-20	BZY88	0-10	OAZ222	0-45	ZTX304	0-24
1N4007	0-12	ASY61	0-40	C111	0-55	OAZ224	0-45	ZTX305	0-15
18113	0-25	ASY63	0-20	CR81/05	0-30	OAZ241	0-25	ZTX503	0-18
18131	0-18	ASY62	0-25	CR81/40	0-05	OAZ242	0-15	ZTX531	0-25
18202	0-23	ASY63	0-20	CR84	1-90	OAZ244	0-25	INTEGRATED CIRCUITS	
2G371	0-40	ASY66	0-33	CR103	3-60	OAZ246	0-15	7400	0-30
2G381	0-22	ASZ21	1-00	D1000	0-15	OAZ290	0-38	7401	0-20
2G414	0-30	ASZ23	0-75	DD003	0-15	OC12	0-40	7402	0-20
2G417	0-25	AU101	1-60	DD006	0-25	OC12T	1-00	7403	0-20
2N404	0-22	BC107	0-12	DD007	0-40	OC19	0-50	7404	0-20
2N697	0-15	BC108	0-12	DD008	0-38	OC20	2-00	7405	0-20
2N698	0-20	BC109	0-12	GD3	0-38	OC22	1-00	7406	0-40
2N706A	0-12	BC113	0-16	GD4	0-10	OC23	1-25	7407	0-40
2N708	0-15	BC115	0-20	GD5	0-33	OC24	1-10	7408	0-25
2N709	0-40	BC116	0-20	GD8	0-25	OC28	0-40	7409	0-38
2N1091	0-65	BC118A	0-20	GD12	0-10	OC28	0-40	7410	0-20
2N1131	0-25	BC121	0-20	GET102	0-50	OC28	0-70	7411	0-25
2N1132	0-25	BC122	0-20	GET103	0-40	OC29	0-65	7412	0-28
2N1302	0-18	BC122	0-20	GET118	0-35	OC30	0-40	7413	0-30
2N1303	0-18	BC129	0-68	GET114	0-80	OC35	0-55	7416	0-30
2N1304	0-22	BC126	0-65	GET118	0-75	OC36	0-65	7417	0-30
2N1305	0-22	BC140	0-55	GET118	0-65	OC38	0-65	7418	0-30
2N1306	0-28	BC148	0-10	GET120	0-50	OC42	0-40	7419	0-30
2N1307	0-28	BC148	0-10	GET872	0-30	OC43	0-70	7420	0-20
2N1308	0-28	BC149	0-12	GET875	0-40	OC44	0-18	7422	0-40
2N1347	0-75	BC157	0-14	GET880	0-55	OC44M	0-17	7423	0-40
2N2148	0-60	BC158	0-12	GET881	0-25	OC45	0-18	7425	0-37
2N2160	1-00	BC180	0-63	GET882	0-65	OC45M	0-18	7427	0-37
2N2218	0-23	BCY31	0-45	GET883	0-40	OC46	0-27	7428	0-43
2N2219	0-25	BCY32	1-20	GEX44	0-08	OC57	0-60	7430	0-37
2N2389A	1-15	BCY32	1-20	GEX45/1	0-45	OC58	0-60	7432	0-43
2N2448	1-09	BCY33	0-38	GEX91	0-45	OC59	0-60	7433	0-43
2N2813	0-28	BCY34	0-45	GEX91	0-60	OC66	0-60	7438	0-43
2N2646	0-50	BCY38	0-65	GJ4M	0-50	OC70	0-18	7440	0-20
2N2904	0-20	BCY40	0-60	GJ7M	0-50	OC72	0-25	7441A	0-25
2N2904A	0-25	BCY42	0-30	HG1005	0-60	OC73	0-50	7442	0-25
2N2906	0-25	BCY70	0-15	H8100A	0-20	OC74	0-30	7450	0-20
2N2907	0-23	BCY71	0-20	MAT100	0-20	OC75	0-30	7451	0-20
2N2924	0-18	BCZ10	0-80	MAT101	0-25	OC76	0-30	7463	0-20
2N2925	0-15	BCZ11	0-65	MAT120	0-20	OC77	0-65	7464	0-20
2N2926	0-10	BD121	1-00	MAT121	0-25	OC78	0-25	7469	0-38
2N3055	0-60	BD124	0-60	MJE250	0-65	OC79	0-30	7470	0-38
2N3702	0-11	BD124	0-60	MJE255	1-10	OC81	0-28	7472	0-38
2N3705	0-15	BDY11	1-45	MJE305	0-75	OC81D	0-28	7473	0-48
2N3706	0-11	BF115	0-22	MJE340	0-50	OC81M	0-20	7475	0-59
2N3707	0-13	BF117	0-60	MPF102	0-60	OC81DM	0-18	7476	0-45
2N3709	0-10	BF167	0-25	MPF103	0-45	OC81Z	0-45	7480	0-30
2N3710	0-11	BF173	0-25	MPF104	0-35	OC82	0-25	7482	0-37
2N3711	0-11	BF184	0-22	MPF105	0-48	OC82D	0-25	7483	1-20
2N3819	0-25	BF184	0-22	NKT128	0-45	OC83	0-25	7484	1-00
2N4289	0-30	BF185	0-22	NKT129	0-30	OC84	0-30	7486	0-50
2N6227	0-53	BF194	0-13	NKT211	0-25	OC84	0-30	7488	0-50
2N6088	0-33	BF195	0-13	NKT213	0-25	OC112	1-00	7490	0-75
28301	0-59	BF196	0-15	NKT214	0-24	OC123	1-10	7492	0-75
28804	1-15	BF218	0-15	NKT216	0-40	OC139	0-40	7493	0-75
28601	0-75	BF218	0-25	NKT217	0-45	OC140	0-85	7494	0-85
28703	1-00	BF218	0-25	NKT218	1-13	OC141	0-80	7495	0-85
AA129	0-20	BF219	0-20	NKT219	0-38	OC169	0-20	7496	1-00
AA212	0-75	BFX13	0-25	NKT222	0-30	OC170	0-25	7497	4-22
AA213	0-10	BFX29	0-28	NKT224	0-25	OC171	0-20	74100	2-16
AO107	0-35	BFX30	0-28	NKT231	0-54	OC200	0-55	74101	0-51
AC126	0-25	BFX63	0-50	NKT271	0-20	OC20	0-50	74110	0-67
AC127	0-25	BFX63	0-50	NKT272	0-20	OC202	0-90	74111	0-68
AC128	0-25	BFX84	0-25	NKT273	0-20	OC203	0-55	74118	1-00
AC187	0-20	BFX85	0-28	NKT274	0-20	OC204	0-65	74119	1-92
AC188	0-20	BFX86	0-25	NKT275	0-25	OC205	1-00	74121	0-57
AOX17	0-35	BFX87	0-25	NKT277	0-20	OC206	1-10	74122	0-80
AOX18	0-27	BFX88	0-22	NKT278	0-25	OC207	1-00	74123	1-44
ACX19	0-27	BFY11	0-50	NKT301	0-85	OC209	0-20	74141	1-00
ACX20	0-22	BFY12	0-40	NKT304	0-75	OC470	0-30	74145	1-44
ACX21	0-22	BFY17	0-40	NKT403	0-70	OC7P1	1-00	74150	2-30
ACX22	0-16	BFY18	0-45	NKT404	0-60	ORP12	0-55	74151	1-15
ACX27	0-25	BFY19	0-55	NKT678	0-30	ORP60	0-45	74154	2-30
ACX28	0-25	BFY24	0-45	NKT713	0-30	ORP61	0-48	74155	2-15
ACX39	0-85	BFY44	1-00	NKT713	0-30	SX68	0-40	74156	1-15
AOY44	0-82	BFY60	0-20	NKT777	0-38	SX631	0-45	74157	1-09
AOY40	0-22	BFY51	0-20	O78B	0-38	SX635	0-55	74170	2-88
AOY41	0-22	BFY52	0-20	OA5	0-60	SX640	0-75	74171	1-80
AD104	0-50	BFY53	0-17	OA6	1-12	SX641	0-75	74174	1-80
AD149	0-50	BFY64	0-45	OA7	0-08	SX642	0-60	74175	1-29
AD161	0-39	BFY90	0-75	OA10	0-10	SX644	0-85	74176	1-44
AD162	0-89	B8X27	0-50	OA11	0-20	SX645	0-65	74190	2-30
AF108	0-80	B8X76	0-18	OA73	0-15	TIC44	0-29	74191	2-30
AF114	0-25	B8Y26	0-17	OA74	0-15	V158/30P	0-75	74192	2-30
AF115	0-25	B8Y27	0-20	OA81	0-10	V39/201P	0-75	74193	2-30

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE
 200 watt (1 amp) £9.00
 0.5 KVA (2½ amp) (MAX) £10.00
 1 KVA (5 amp) (MAX) £14.70
 2 KVA (10 amp) (MAX) £28.10
 3 KVA (15 amp) (MAX) £31.25
 4 KVA (20 amp) (MAX) £72.50
 37.5 amp (MAX) £102.50
CARRIAGE AND PACKING EXTRA OPEN TYPE 1 amp (panel mount) £9.00



300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0.115V for 115 or 230 volt. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb.
SPECIAL OFFER PRICE £5. Carr. 80p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2. Post 20p. (Total incl. VAT and Post £2.38).



PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.
 2 cam model. £2.00 post 30p.
 4 cam model. £2.50 post 30p. 6 cam model. 3 r.p.m. 6 cam model. £3.25 post 30p. £3.25 post 30p.

MINIATURE UNISELECTOR SWITCHES

2 Bank, 11 position, 24 V.D.C. operation, full wiper with any auxiliary contacts. **NEW PRICE £2.50. Post 20p.** As above but with 5 Bank, 11 position. Price £3.50. Post 20p.



COIN MECHANISM (Ex London Transport)

Unit containing selector mechanism for 1p, 2p and 5p coins. Micro switches, relays, solenoid operated hopper. 24 V.D.C. Precision built to high standard. Incredible **VALUE** at only £2.50. Post 60p.

230/250 VOLT A.C. SOLENOID

Approximately 1½ lb pull. Size of feet 11" x 1 1/2". Price £1.00. Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb pull 1 inch travel. Two x approx. 1 lb pull ½ inch travel. 6 x approx. 4oz. pull ½ inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2.50. Post 60p.
ABSOLUTE BARGAIN.

230V FAN ASSEMBLY

Continuously rated, removable aluminium blades. Price £1. Post 20p.



PRECISION CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd. Heavy Duty continuously rated, smooth running, 230/240V a.c. motor. Size: 16 x 14cm (case only). OAL 15cm. Aperture 6 x 6cm. £6.50. Post 50p.



230/240 VOLT A.C. EXTRACTOR FAN KIT

Comprising of impeller, continuously rated motor, motor housing and fixings as illustrated. Price £1.75. Post 25p. (Total incl. VAT and Post £2.16).



TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS 10 amp. Glass passivated plastic triac. Latest design from U.S.A. Long term reliability. Type SC146E 10 amp. 500PIV. £1.00. Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.



600 WATT DIMMER SWITCH Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. **EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £30. Post 30p.

INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. ½ output of Hy-Lyght. Price £14.00. Post 50p.

HY-LYGT STROBE MK III

For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £14. Post 50p.

THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

- Variable speed from 1-13 flash per sec.
- Reactor control circuit producing an intense white light. **ONLY £22. Post 75p.**

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector £5.75. Post 25p.


Super Hy-Lyght case including reflector £8. Post 60p.

7-INCH POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 55p. Post 15p.

COLOUR WHEEL PROJECTOR

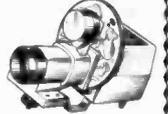Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p.



6 INCH COLOUR WHEEL

As used for Disco lighting effects, etc. Price £4.50. Post 30p.

BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. P.F. ballast is essential. Price of matched ballast and bulb £16. Post £1. Spare bulb £7. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt. Price £5.50. Post 30p. (4ft Personal callers only). 2ft 20 watt. £4.25. Post 25p. (For use in standard bi-pin. MINI. 12in 8 watt. £1.60. Post 15p. 9in 6 watt. £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube. £1.70. Post 25p. (9in and 12in measures approx.)

U.D.I. SINGLE CHANNEL

750 WATT MANUAL/AUTO DIMMER 750W Solid State Fader, with three functions. Manual fade; Auto fade-up; Auto fade-down. Automatic cycling up and down. Functions selected with 'three-position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" x 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. **PRICE £15. Post 30p.**



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.25. Post 35p.

50 IN 1 ELECTRONIC PROJECT KIT 50 easy to build projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 25p.

INSULATION TESTERS **NEW!**

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.



All prices are subject to 8% VAT. (8p in the £)
 To all orders add 8% VAT to total value of goods including carriage & packaging.

Superior Quality Precision Made

NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/150/500/1k/ohm £1-15. Post 10p.
50 WATT 15/10/25/50/100/250/500 1-5k/ohm £1.60. Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1-5k/2-5k/3-5k/5k ohm £2.35. Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9. 1 1/4in dia. brass bush. Ideal for above Rheostats. **22p each.**

RELAYS SIEMENS, PLESSEY, Etc MINIATURE RELAYS

Col.(1)	1	2	3	4
Coil ohms				
Col. (2)	58	5-9	6 c/o	80p.
Working d.c. volts	150	4-9	2 c/o	70p*
Col. 3	185	8-12	6M	60p*
Contracts	308	9-14	4 c/o	75p*
Col. (4)	410	12-20	4 c/o	80p*
Price	700	16-24	4M 2B	60p*
	700	16-24	4 c/o	80p*
	700	20-30	6 c/o	50p*
HD=	2,500	31-43	2 c/o HD	60p*
Heavy duty	2,500	36-45	6M	60p
	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

*Incl. Base. All prices incl. P. & P.

6 VOLT D.C. 1 make contacts 35p. Post 10p.

9 VOLT D.C. 2 make contacts 75p. Post 10p.

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 10p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 10p.

24 VOLT D.C. 3 c/o 75p. Post 10p.

DIAMOND 'H' Heavy Duty

230/240V a.c. 2 c/o, 25 amp RES. at 250V a.c. £2. Post 10p.

CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.

100 VOLT A.C. 2 c/o sealed type, octal base £1. Post 10p.

24 VOLT A.C. 3 c/o. 75p. Post 10p.

24 VOLT A.C. Mfg. by ITT. 2 h.d. c/o contacts. 55p. Post 10p.

240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C. 10 amp h.d. c/o contacts. Octal plug in base. Price 75p. Post 10p.

230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price £1. Post 10p.

220/240 VOLT A.C. RELAY

3 c/o 5 amp contacts. Sealed. Incl. 11-pin base £1.25. Post 10p.

HEAVY DUTY A.C. SEALED RELAYS

110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.

VERY SPECIAL OFFER

MINIATURE ROLLER MICRO SWITCH. 5 amp. c/o contacts. Mfg. BONNELLA. NEW. Price 10 for £1.50. Post 10p. (Min. order 10).

AS above WITHOUT ROLLER. 20 for £2. Post 10p.

230/240 VOLT A.C. MINIATURE MOTOR.

20 R.P.M. Price £1. Post 10p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 0.38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle 0.28 amp.

The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115V A.C. Supplied complete with transformer for 230/240V A.C. input.

Price, either type £6.25. Post 50p or less transformer £3.75. Post 40p.

'FRACMO' 240 VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR

31 r.p.m. 30 lb. ins. Reversible. Fitted with mounting feet. Brand New. £14. Post 60p. (Total price incl. VAT £15.77).

HIGH VISIBILITY PANEL MOUNTING LED'S. 0.25 inch mounting. 0.16 inch lens. Typical parameters 2V, 20M amps all type. Supplied complete with snap in mountings and data. Red 4 for £1, Green 3 for £1, Yellow 3 for £1. Post 10p. (In order) (£1).

LED READOUTS

7 series. L/H d.p. one-third high character. 14 pin D.I.L. Available in RED or GREEN. Price £1.65. Post 10p. 4 for £6. Post paid.

Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET


LONDON WC2H 7JJ

Phone 01-437 0576


All Mail Orders—Callers—Ample Parking
 Dept. PE12, 57 BRIDGMAN ROAD
 CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

SERVICE TRADING CO.

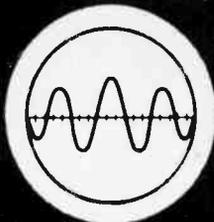Personal callers only. Open Sat.
 9 LITTLE NEWPORT STREET
 LONDON WC2H 7JJ
 Phone 01-437 0576



TUAC

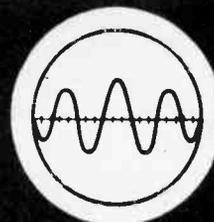

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1M Ω ; Deck Tone Controls—treble +20 - 10dB at 12kHz, Bass +22 - 15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47k Ω ; Power Requirements—30-45 volts at 100mA.

£26.50

PANEL SIZE
18 x 4½ in.
DEPTH 3 in.

HOW TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (PE)
or quote Access/Barclay Card No.
and post to TUAC LTD (PE)

163 Mitcham Road, London, SW17 9PG


We accept phone orders against Access/Barclay Card Holders
Phone: 672 3137

Stockists—Callers only

A1 Music Centre, 88 Oxford Street, Manchester 1. Tel. 061-236 0340.
Bristol Disco Centre, 86 Stokes Croft, Bristol 1. Tel. Bristol 41666.
Calbarrie Audio, 88 Wellington Street, Luton, Beds. Tel. Luton 411733.
Socodil, 9 The Friars, Canterbury, Kent. Tel. Canterbury 60948.
Wec Lighting, 35 Northam Road, Southampton, Hants. Tel. Southampton 28102.

NEW! 3 CHANNEL LIGHT MODULATOR

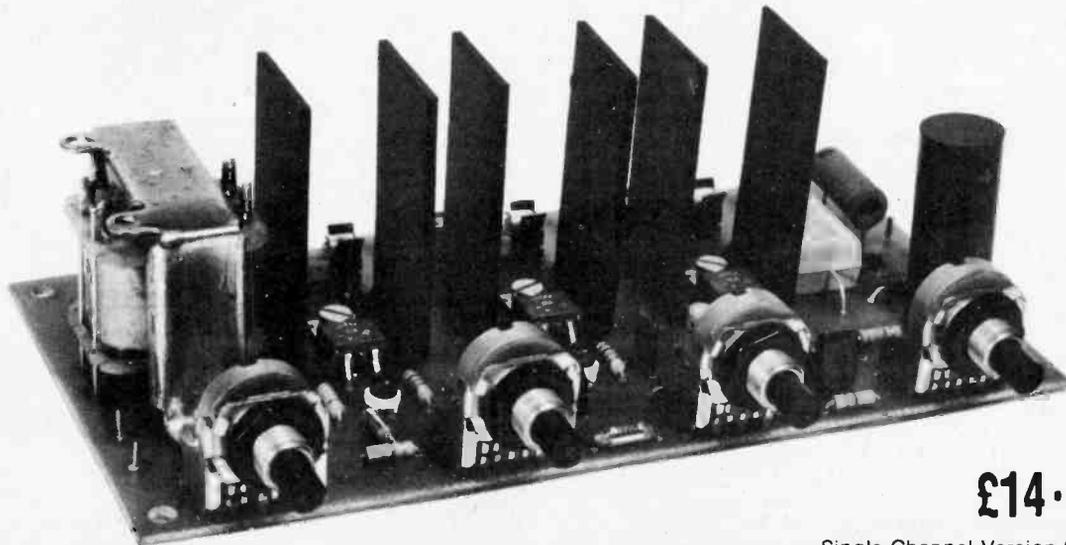
- R.C.A. 8 Amp Trlacs ● 1000W per channel ● Each channel fully suppressed and fused
- Master control to operate from 1W to 100W ● Full wave control—12 easy connections




£14.90

Single Channel Version £6.60

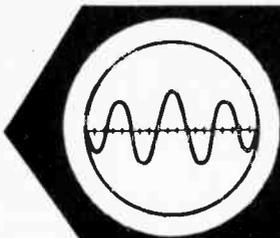MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT. OPEN 6 DAYS A WEEK 9.30am-6.00pm




TUAC

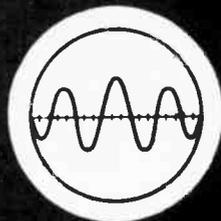

TRANSISTOR UNIVERSAL AMPLIFICATION CO.LTD.
163 MITCHAM RD·LONDON SW17 9PG 01-672 3137/9080

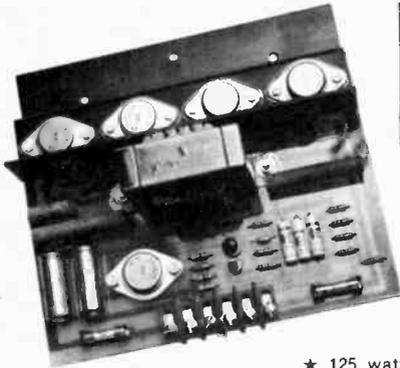NEW TUAC POWER MODULES offering more power and quality than ever before.



Specification on all power modules
All output power ratings ± 0.5 dB
Output impedance 8-15 ohms. THD at full power 2% typically 1%. Input sensitivity 60mV into 10k Ω . Frequency response 20Hz-20kHz ± 2 dB. Hum and noise better than -70dB


TP125

7 x 6 $\frac{1}{2}$ x 3in

£17.00

★ 125 watts RMS continuous sine wave output

★ 4 R.C.A. 150 watt 15 amp output transistors

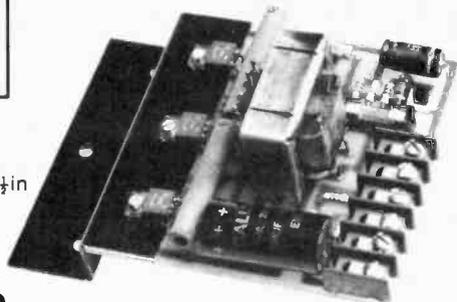


TL30

4 x 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in

£9.30

★ 30 watts RMS continuous sine wave output
★ 2 R.C.A. 40 watt output transistors

★ Rugged layer wound driver transformer
★ Short—Open—and Thermal overload protection
★ Only 6 connections

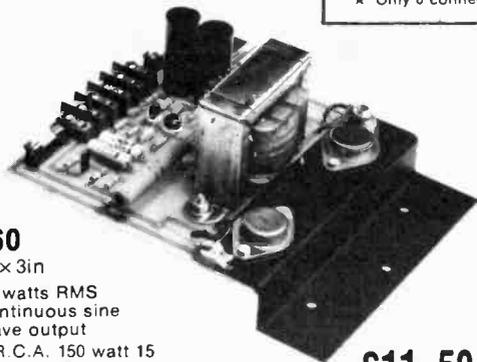

TL60

5 x 5 x 3in

★ 60 watts RMS continuous sine wave output

★ 2 R.C.A. 150 watt 15 amp transistors

£11.50


TL100

5 x 5 x 3in

★ 100 watts R.M.S. continuous sine wave output

★ 2 R.C.A. 150 watt 15 amp transistors

£13.20

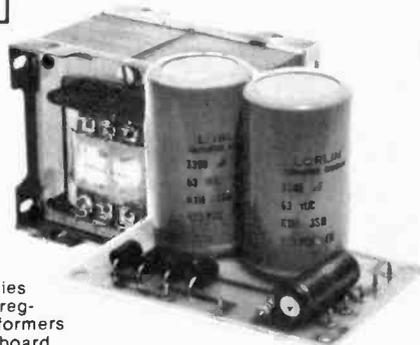

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 ± 50 volts for one TP125
PS 100 ± 45 volts for one TL100
PS 60 ± 40 volts for one TL60
PS 30 + 50 volts for one TL30
PSU 2 for supplying disco mixer

£11.50
£10.50
£9.30
£6.85
£4.65


PREAMPLIFIERS

All TUAC audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into various wide range tone control circuits producing superb sound quality from any signal.

VA08 Vol. Treble, Mid and Bass controls. Hi. IMP. FET. I/P, suitable Mid. Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20-15dB at 1kHz. Bass +20-10dB at 40Hz. **£4.90**

VA06 Vol. Treble and Bass controls. Sensitivity 8mV. Treble +28-15dB at 12kHz. Bass ± 18 dB at 40Hz. **£4.15**

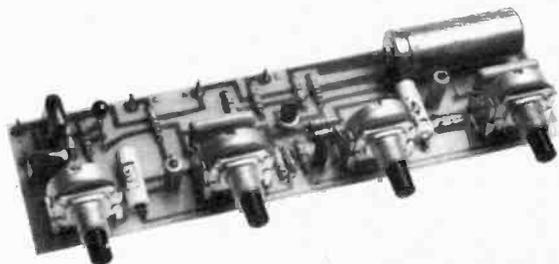AMF01 TUAC Auto Fade Unit fades music when you speak. Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade O/P to main Amp. 38mV operating level. Depth and Vol Controls. **£4.90**



ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED JUST SEND OR PHONE US YOUR NUMBER · H.P. ARRANGED THROUGH PAYBONDS

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System - with a big plus over all the other kits - the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888

Make light work
of wiring
with the NEW



SELF ADHESIVE WIRE STAPLES

Countless uses in industry and offices

- * QUICK AND EASY TO APPLY -
EVEN IN AWKWARD PLACES
- * SAVES DAMAGE TO WOOD AND PAINTWORK
- * STICKS ON INSTANTLY: HOLDS WIRE FIRMLY

You'll save enormous time and trouble with the new Brandauer adhesive staple. Just peel off the backing strip and press staple into place. Then bend clips over to hold wire firmly in position. No messing with pins, tacks, soldering or drilling. No damage to woodwork, e.g. skirting boards. Use the Brandauer Staple for any wall, frame or cabinet wiring jobs - it's wonderfully easy for fitting in those awkward corners.

Send now for details to:

SPECIAL PRODUCTS DISTRIBUTORS LTD.
81 Piccadilly, London W1V 0HL. Tel: 01-629 9556.

P. F. RALFE

10 CHAPEL ST. LONDON NW1

Phone 01-723 8753

MUFFIN INSTRUMENT FANS

Dimensions 4.5in x 4.5in x 1.5in. Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers etc. For 110V, a.c. operation (practise is to run from split primary of mains transformer or use suitable mains dropper). CC only 11 watts. List price over £10 each. Our price, in brand new condition, is £3.50.

ITT METRIX

Model 101B miniature oscilloscope. D.C. 10mHz. Sensitivity 100mV. Single-beam. Dimensions 20cm x 14cm x 13cm. Weight 5½lb. Sold brand new at nearly one half maker's list price. Only £50.



AVO VALVE TESTERS

Brief-case type 160. Full working condition throughout. £65.

DIGITAL FREQUENCY METER

Type FT300
Reads as frequency meter up to 99.99 kHz in three ranges or as tachometer. 99.990 r.p.m. Solid-state instrument. Clear read-out. Size only 8in x 5in x 2½in. Weight 4½lb. BCD outputs. Operating voltage 110.240V a.c. Made by famous manufacturer. These units are brand new in original makers cartons. Price £55.

EDDYSTONE 770R RECEIVER

Range 19-165mHz. As new. £125.

AERIAL CHANGE-OVER RELAYS

of current manufacture designed especially for mobile equipments. coil voltage 12V, frequency up to 250MHz at 50 watts. Small size only 2in x ¾in. Offered brand new, boxed. Price £1.50, inc. P & P.

TV WOBBLATOR Type '210'

Technical characteristics
Frequency: 5 to 220Mc/s In one range.
Accuracy: That of the marker generator (e.g. METRIX 936).

Output: Not less than 100 mV attenuable in steps of 10 down to 10µV.

Sweep width: 1-2-5-10-20Mc/s

Linearity: 10% at sweep width 10Mc/s

Amplitude modulation: Less than 10% at sweep width 10Mc/s

Power supply: 110-130-220V, 50-60c/s. 130V may be replaced by 160V. 220V may be replaced by 240V on demand.

Power Input: 35VA approx.
Tubes used: 2 x EC81, 1 x 6J6, 1 x 6X4

Weight: 20lb 8oz (9.300kg).
Dimensions: 20 x 11½ x 7½in. (510 x 295 x 195mm) overall. Price £48.50 inc. VAT.

Large selection of
RF PLUGS AND SOCKETS

Available ex-stock: BNC plugs 50 30p; BNC sockets 50 25p; N type plug 50 50p; Burndepth plugs 40p; Burndepth sockets 20p; All plugs and sockets are brand new.

Please add appropriate amount for postage.
DURATRAK VARIACS
Type 100L. 230V input 0-230V a.c. output. 8 amps. Brand new minus control knobs. Price only £15, carriage £1.

PLEASE ADD 8% VAT TO THE TOTAL AMOUNT
WHEN ORDERING. INCORRECT AMOUNTS WILL
CAUSE DELAY IN DESPATCH.


CUSTOM CABINETS

331 High Street, Rochester, Kent. Tel: Medway (0634) 404199


SPEAKER CABINETS IN KIT FORM REPRESENT **HUGE SAVINGS**



2' x 12" Cabinet

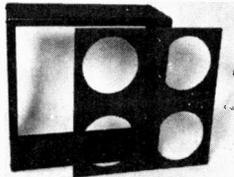

4' x 12" Cabinet

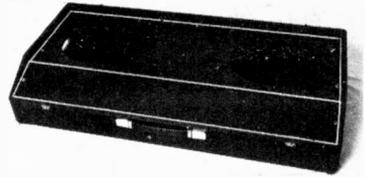

Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!


Kits are available in all specifications and all the kits contain everything you need as follows :-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!


PRICE & TYPE LIST

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£19.50	£12.50
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£24.50	£17.50
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£30.00	£21.50
1 x 18"	31" x 31" x 13" x 3/4"	£24.50	£17.50
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£21.00	£13.50
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 8" x 1/2"	£20.00	£13.00
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2"	£25.00	£18.50

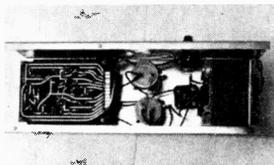Please ask for quotation on any other type or size of cabinet you may require.



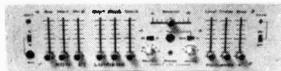- * 100w RMS slave amp for Disco
- * 100w RMS continuous sine wave output
- * Short and open circuit protection
- * Built to highest industrial spec.
- * Price £37.00 complete




- * Stereo studio disco mixer
- * Full PFL and Monitor facilities
- * As used by John Peel, Mark Wesley, Paul Burnett, DLT, Dave Christian, Tony Prince
- * Price £120.00



- ERC 100w power amplifier
- * Electrolytic capacitors and second generation ICs
- * Fully protected against short or open circuit
- * Less than 0.1% distortion at all powers
- * Rise time 4mµs-stability- Unconditional Price £66.50

ALL OUR PRICES INCLUDE VAT AND UK DELIVERY

VALUE!!

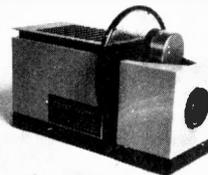

LOOK!!

Disco imp projector 150 watt tungsten
unbeatable price £19.75
Includes liquid wheel and postage
Normally £24-£27.50

UNBEATABLE NOW ONLY £18

TRADE AND EXPORT ENQUIRIES WELCOME

R T V C FOR AUDIO ON A BUDGET

PUSH BUTTON CAR RADIO KIT

The Tourist II



**NO SOLDERING
REQUIRED!**

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

Car Radio Kit £7.70 + 55p p & p

The Tourist I Kit For the experienced constructor
If you can solder on a printed circuit board you can build this model.
Same technical specification as Tourist II
Price £6.60 + 55p p & p.

Technical specification :

- (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth.
- (2) **Integrated circuit** output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.
Size chassis 7" wide, 2" high and 4 3/4" deep approx

Speaker including baffle and fixing strip **£1.65+23p.p&p.**

Car Aerial Recommended — fully retractable
£1.37+20p. postage & packing



* STEREO 21 QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes :- BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.
Two speakers with cabinets.


Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications : For the technically minded :-

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.
Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £19.95 + £1.60 p & p. Extras if required. **Optional Diamond Styli £1.37.**

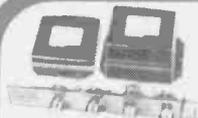Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



BUILD YOUR OWN * STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.
240V. AC only.

£7.64 + 55p p & p

8 TRACK HOME CARTRIDGE PLAYER *



Elegant self selector push button player for use with your stereo system.

Compatible with Viscount III system, Unisound module and the Stereo 21.

Technical specification Mains input, 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at £24.00 approx. Yours for only

£11.95 + 90p p & p.

COMPLETE* STEREO SYSTEM



System 1. £51.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System 1 includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone-socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within -1dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. **Tone controls and filter characteristics.** Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. **Signal to noise ratio:** (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 3/4" x 9" x 3 3/4".

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 1/4" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. 10 watts handling.

Complete System £51.00

System 2. £69.00

Viscount III amplifier (As System 1)

Garrard SP 25 Mk III deck (As System 1)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2"

Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters.

20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69.00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge and hinged cover	£21.00 + £1.75 p & p
total:	£59.20

Available complete for only:
£51.00 + £3.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge and hinged cover	£21.00 + £1.75 p & p
total:	£84.20

Available complete for only:
£69.00 + £4.00 p & p

EMI SPEAKERS AT FANTASTIC REDUCTIONS



20 WATT SPEAKER SYSTEM

System consists of a 13" x 8" (approx) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components.

Technical Specification:

Bass Unit

Flux density-100 K, speech coil-1 1/2" Cone, Triple laminated paper with P.V.C. surround.

Mid Range Unit

Flux density-33K, speech coil-1" with parasitic tweeter.

Power Handling

20 watts R.M.S., impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

OUR PRICE

£6.60. Complete

+ 90p p & p.




15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz, flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70 + £1.50 p & p

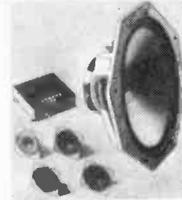

950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5" Recommended list price £44.00.

Special Offer

OUR PRICE £19.50 + £1.50 p & p


FOR DISCO PAGE AND DETAILS OF HOW TO ORDER - TURN OVER...



PORTABLE DISCO CONSOLE

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges. The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record. The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

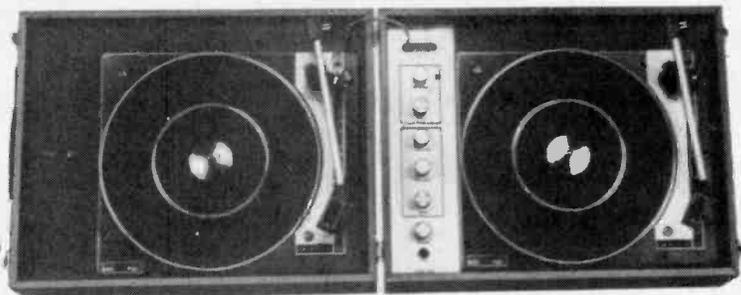

TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV. Auxiliary inputs - 200mV and 750mV into 1 meg.
 Mic input - 6mV into 100K. 240 volt operation.
 Turntables capacity - 7", 10" or 12" records.
 Rumble, wow and flutter - Rumble - Better than -35dB. Wow - Better than 0.2%. Flutter - Better than 0.06% (Gaumont kalee meter).
 Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size - Unit Closed - 17 3/4" x 13 3/4" x 8 3/4" (approx.)
 Unit Open - 35 3/4" x 13 3/4" x 4 3/4" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier. The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.


Yours for only £45.00 + £3.50 P. & P.

DISCO 50



45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/4" x 10 1/2" x 8" (approx.) Amplifier £27.50 + £1.50 p. & p.

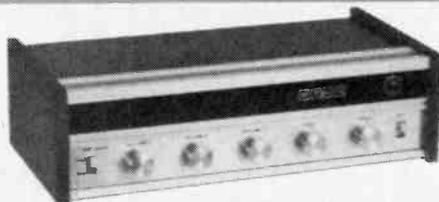

DISCO AMPLIFIER


Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms). Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES

-Input - 1.) Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).
 -Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2".

£15.00 + 60p. post & pack.

BARCLAYCARD

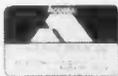

DO NOT SEND YOUR CARD

Just write your order giving your credit card number

● Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

● Leaflets available for all items listed thus *
 Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG
 323 Edgware Road, London W2

Personal Shoppers Edgware Road: 9a.m.-5.30p.m. Half day Thurs.
 Acton: 9.30a.m.-5p.m. Closed all day Wed.

SPARKRITE Mk II

Electronic Ignition... Better on all points




The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly — with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of normal, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Cleaner plugs — they last 5 times longer without attention. ● Faster acceleration. ● Faster top speeds. ● Coil and battery last longer. ● Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

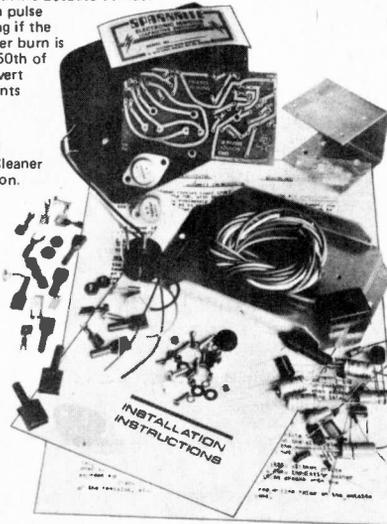WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite Mk II — full capacitive discharge electronic system — not just a transistorised inductive discharge booster.

Because you keep your points!

PRICES

D.I.Y. Kit only £10.93 incl. VAT and P & P
Ready Built Unit £13.86 incl. VAT and P & P
(Both to fit all cars with coil/distributor ignition up to 8 cylinders)

We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES
(Dept P E 12) 82 Bath Street,
Walsall WS1 3DE Phone 33652

- Please supply
- Sparkrite Mk. 2 D.I.Y. Kit(s) at £10.93 each incl. VAT and P & P (Will make pos or neg earth)
 - Sparkrite Ready Built Neg. Earth Unit(s) at £13.86 each incl. VAT and P & P
 - Sparkrite Ready Built Positive Earth Unit(s) at £13.86 each incl. VAT and P & P

NAME _____
ADDRESS _____

I enclose cheque/P.O. for £ _____
Send SAE for brochure.

TRANSISTORS—

Wide variety ex-stock

OC201 80p	2N2218 21p	2N3733 230p
BC108 10p	2N2219 20p	2N3819 20p
BC109 10p	2N2220 18p	2N3900 50p
BC117 23p	2N2221 20p	2N3923 48p
BC128 11p	2N2222 20p	2N3966 70p
BC147 7p	2N2268 14p	2N3903 4 15p
BC148 7p	2N2369 14p	2N4058 15p
BC149C 8p	2N2484 30p	2N4059 10p
BC158 12p	2N2646 32p	2N4060 13p
BC159 14p	2N2904 20p	2N4062 13p
BC163C 11p	2N2905 18p	2N4071 35p
BC169C 11p	2N2906 20p	2N4244 180p
BC182 7p	2N2926 8p	2N5457 38p
BC187 7p	2N2926 8p	2N5458 35p
BC188 11p	2N2926 8p	2N5459 35p
BC189C 11p	2N2926 8p	2N5460 35p
BC193C 11p	2N2926 8p	2N5461 35p
BC194 11p	2N2926 8p	2N5462 35p
BC195 11p	2N2926 8p	2N5463 35p
BC196 14p	2N2926 8p	2N5464 35p
BC197 15p	2N2926 8p	2N5465 35p
BC198 15p	2N2926 8p	2N5466 35p
BC199 15p	2N2926 8p	2N5467 35p
BC300 15p	2N2926 8p	2N5568 35p

2N2218 21p	2N3733 230p
2N2219 20p	2N3819 20p
2N2220 18p	2N3900 50p
2N2221 20p	2N3923 48p
2N2222 20p	2N3966 70p
2N2268 14p	2N3903 4 15p
2N2369 14p	2N4058 15p
2N2484 30p	2N4059 10p
2N2646 32p	2N4060 13p
2N2904 20p	2N4062 13p
2N2905 18p	2N4071 35p
2N2906 20p	2N4244 180p
2N2926 8p	2N5457 38p
2N2926 8p	2N5458 35p
2N2926 8p	2N5459 35p
2N2926 8p	2N5460 35p
2N2926 8p	2N5540 35p

250mA 14p	50V 400V 600V
1A 20p	25p 25p
2A 30p	45p 45p
4A 48p	80p 70p
6A 50p	78p 95p

50V 100V 400V 600V	1A 42p 46p 60p 78p	3A 43p 50p 78p 96p	7A — 80p 84p 114p	16A — 78p 96p —
--------------------	--------------------	--------------------	-------------------	-----------------


BY100 15p	BY126 12p	BY127 12p	CA79 7p	BYZ10 35p	BYZ11 35p	BYZ12 35p	1N4001 5p	1N4004 6p	1N4007 7p	PL4004 10p	PL7004 20p
-----------	-----------	-----------	---------	-----------	-----------	-----------	-----------	-----------	-----------	------------	------------

BA100 10p	OA47 7p	OA70 8p	OA79 7p
-----------	---------	---------	---------

Connoisseur

THE B.D.2 TURNTABLE ASSEMBLY

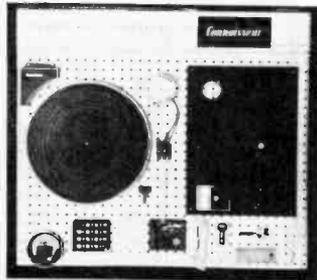The Famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed mat and brushed aluminium trim, and the perspex cover has an easy 'hinged-on, hinged-off' movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth.



B.D.1 TURNTABLE KIT

The B.D.1 well known for its superb performance and quality is available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

Contact your dealer for information or send a stamp for brochure.

A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoisseur, Brighouse

MINISONIC

TRANSISTORS	VOLTAGE REGULATORS	POWER SLAVE
BC204 11p	MVR15 200p	P.C.B.'s
BC209C 11p	MA7815 220p	Designers Layout
BC182 10p	723 180p	Master Board £1-65
BC184 11p		Stabiliser £1-10
BC212 14p	ARRAYS	HUTCHINSON
BC214 16p	ML3046P 75p	TONE CONTROL
BC215 15p	CA3096AE 120p	(with data sheets)
BC213L 15p	OP. AMPS	Few only at 95p
2N2484 24p	748 48p	V.A.T.
2N2904 30p	FETMOPA 450p	Please add 8% to final total of order
2N2905 27p	SPECIAL PURPOSE LINEARS	TRANSFORMERS
2N2219 22p	SG3402N 174p	220/240V Pri. Min. type.
2N3054 100p	SG3402T 174p	0-12; 0-12V @ 6VA
2N3055 65p	SG1495D 290p	0-20; 0-20V @ 6VA
High Voltage	MFC6040 100p	£1-84 each
MPSL01 39p	T.T.L.	0-19; 25; 33; 40; 50V
MPSL51 41p	7400J 29p	@ 500mA £2-35
MPSU07 69p	7402N 38p	0-17.5V @ 1.6A £2-73
MPSU57 85p	7404N 27p	0-25V 2A +0-25V 2A
SDT9203150p	7410PC 24p	£6
FETS	7420N 24p	HEATSINKS
2N3819 46p	7430PC 23p	Marston type for POWER SLAVE 65W and 100W versions.
2N5459 60p	7473N 48p	£2-85 each
DIODES	7475N 49p	Type 154 for T05 9p each
1N5401 21p	7476N 49p	CONSTANTAN WIRE
1N914 5p	7478N 660p	0-03 ohms/cm as specified for the POWER SLAVES. 20cm lengths 10p
BA148 25p	7493PC 89p	
1SJ50 12p	74121J 85p	
1GP7 10p	74122N 80p	
NOISE DIODES	74123N 144p	
Z11 53p	74150N 210p	
Z1M 120p	RESISTORS	
RECTIFIERS	2% METAL OXIDE	
REC41A 120p	16p for 5	
REC43A 139p	5% CARBON FILM	
REC46 255p	9p for 5	
REC70 40p		
EA100/10 40p		
MDA942A/1 210p		

COMPONENT KITS NOW AVAILABLE.
4½p STAMP BRING DETAILS. ASK ALSO FOR "POWER SLAVE" DETAILS.

UNREPEATABLE OFFER

741 OP. AMPS
MINI D.I.P.
28p each

For this month only or until stocks are exhausted. Mnfrs. full spec. branded devices.

POTENTIAL METERS
MIN MOULDED CARBON
24mm dia.

LINEAR 5kΩ; 10kΩ; 25kΩ; 50kΩ; 100kΩ; 1M.
LOG. 10kΩ; 25kΩ; 50kΩ all at 21p each
GANGED. 100kΩ 1in; 5kΩ log; 10kΩ log. all at 78p each

PRECISION TURN 10
1kΩ R.S. TYPE £3-40

CAPACITORS
Tubular Electro. 14p
25V. 25μF; 47μF
100μF 16p; 470μF 29p
1000μF 46p
50V. 1000μF 57p
63V. 100μF 22p
100μF 24p


PRINTED CIRCUIT ELECTROLYTIC
4-7/40V; 10/63V
22/40V; 47/40V
13p each
100/63V; 470/16V
23p each

HIGH RIPPLE TYPE
3300μF 63V £2-20
7100μF 40V 75p
10000μF 40V £1-44

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT PRICES

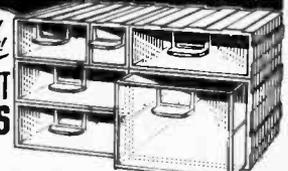

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label-slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £2 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). £3-50 DOZEN.

TREBLE (3D) £3-50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4-90 for 8.

EXTRA LARGE SIZE (6DI) £4-50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7½% in the £

PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Order £10 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance


FLAIRLINE (Dept. PE12), 124 Crickiewood
Broadway, London, N.W.2
Tel: 01-450 4844

EATON AUDIO
P.O. BOX 3, ST. NEOTS
HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.



Henry's

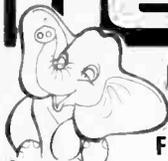

CASH & CARRY PRICES

For CALLERS or BY POST

(GB carr/Pack 15p per item)

Ref. No.	Description	Price £ p
1	D1203 Telephone amplifier—action	4.95
2	D1201 Telephone amplifier—cradle	7.50
3	T1206 2 station intercom	4.95
4	T1306 3 station intercom	9.95
5	T1406 4 station intercom	12.50
6	T1A1A 2 station telephones intercom	13.50
7	W12 2 station wireless intercom	18.20
8	DP303 Door phone intercom	7.00
9	PK3 ETCH your own printed circuits	2.25
10	EA41 Reverbation amplifier	11.75
11	U550 Ultrasonic switch	18.45
12	XP4002 Photoelectric alarm system	13.50
13	Solid state tachometer	11.30
14	Power dash transistor assisted ignition	13.50
15	Car auto lock	2.75
16	AA-6-12V battery charger	4.85
17	FP21 Car radio/tape cued adaptor	10.50
18	Fully disappearing car aerial	2.00
19	Electric disappearing car aerial	7.80
20	ET (F1009) Morse code key/buzzer	1.70
21	VH105 Aircraft band converter	10.50
22	LM300 50K Diaco mic	12.95
23	DF50B 50K Communications mic	5.75
24	Car lighter plus 1W voltage adaptors 300mA (each)	1.95
State 6 7/9V		
25	STC Time delay module	1.50
26	Genavire 931A photo-electric unit (with data)	3.50
27	3 cw 3x500W sound to light	21.50
28	3 cw 3x1,000W sound to light + override	41.25
29	150W light display projector with wheel	23.50
30	MM1 (B2005) 4 channel 9V mixer	4.20
31	MX100 deluxe 4 channel mixer	6.78
32	HP7 (G1320) Stereo headphone amplifier	10.50
33	MR12 6-Ch Channel mixer	27.95
34	RE208 Stereo phone adaptor	2.25
35	MD802 Stereo phones	2.29
36	CIS200 Stereo phones	2.75
37	CIS250 Stereo phones	6.50
38	G1301 and G1305 Stereo phone controls	2.85
39	Car stereo speakers in pods. Special offer	2.95
40	Crystal lapel microphone	0.60
41	E1052 Car speakers (front/rear fader)	0.60
42	Bib groove clean (Ref. No. 42)	1.76
43	Bib Record care kit (Ref. No. 43)	2.20
44	Bib cassette recorder care kit (Ref. No. 26A)	1.95
45	Bib cassette tape applying kit (Ref. No. 24)	5.64
46	BASF reel-reel hobby box	2.40
47	2000 OHM Headphones	1.50
48	4000 OHM Headphones	1.50
49	Cassette recorder mic. (2mm and 3mm plugs)	5.70
50	423 ES Microscope	1.70
51	UP050 Low cost 9V eliminator	2.25
52	RE 527 Tape head	1.11
54	BC208 Percentage pocket calculator	16.65
55	BC817 Memory pocket calculator	10.30
56	BCM850 Percentage and memory calculator	27.95
60	Antex soldering iron kit (SK1)	3.30
61	Bib record care kit (Ref. No. 59)	1.55
62	5pc Chassis punch kits	5.50
63	Longs desoldering tool	5.50
64	1A in line mains suppressors	2.50
65	B5S2 (E1013) 7 way stereo speaker switch	7.50
66	Weller 820D—PK expert gun kit	6.20
67	S Dec breadboard	1.88
68	2 Dec breadboard	4.29
69	4 Dec breadboard	7.50
70	T Dec breadboard	3.85
71	Instant heat soldering gun	2.30
72	40W soldering iron	1.90

ELECTRONIC COMPONENTS AND EQUIPMENT

More selection—bigger stocks of electronic components and equipment for supply purposes. Let us quote for your requirements. (Please enclose large SAE with all enquiries)

BUILD IT YOURSELF



MW/LW portable radio £7.98 (P & P 32p) MW/LW radio tuner £5.25 (P & P 20p). 9V regulated power supply £2.15 (P & P 15p). 15W inverter £5.20 (P & P 20p). 40W inverter £6.80 (P & P 40p). Sinclara micromatic radio £2.25 (P & P 15p).

MULTI-KITS

Ready to use and use again. Educational and practical.

All transistor circuits with full handbooks.
10 in 1 10 projects £5.95 (post 20p)
50 in 1 50 projects £13.95 (post 25p).
150 in 1 150 projects £21.50 (post 30p).
Radionic X 20 20 (Elec.) projects £4.95 (post 20p).
Radionic X 40 40 (Radio) projects £9.45 (post 20p).

TRANSISTORS, VALVES AND SEMI-CONDUCTOR DEVICES—ANY QUANTITIES
UK'S LARGEST STOCKISTS

ELECTRONIC COMPONENTS

(Post/Packing 15p per 1-6 items G.B. unless stated)

Ceramic Filters
Miniature 10.7 MHz filters
40p pair
IC Filter
CA3089 10.7 MHz IC
£2-94

IC Clock
MM 5314 single chip clock with CCO T9.

Radio IC Chip
ZN414 Radio IC with circuit
£1.20.

Ultrasonic Transducers
With data/circuits
£5.90 pair

Strobe tubes
ZFT8A (similar to 4A)
£4
ZFT12A £5.

7 segment Indicators
3015F with data
£1.70 each

Spring delay units
HP42 9in twin spring £3.30
(P & P) 20p HRI 9in twin spring £6.85 (P & P) 25p

Fibre optics
0.25in dia mono filament
£5.50 per 100 metres. 0.13in dia 64 fibres £1 per metre. 15mm dia. mares tails £10.50 each.

Radio Control XTALS
Matched pair for 465 kHz IF
£2 pair for all superhet trans. RX's.

Handsets
Lightweight telephone handsets brand new complete with diagrams for intercoms
£3 pair

MARRIOT TAPE HEADS
17 High Impedance £2.50
18 Med. Impedance £3.50
36 Med. Impedance £5.00
63 2 track mono High Imp £1.75
Erase Heads for 17 75p
18 and 36 75p
43 Erase Head for 63 75p
Stereo Cassette Head £1.20
Belden UL90 Erase £1.50
(Post. etc. 15p any quantity.)

QUALITY CASSETTE TAPES

"Living Sound" made specially for Henry's by EMP Tapes Ltd. 5 screw type with library case. Post paid (G.B.).

	£ for	6 for	12 for	25 for
C60	1.10	2.00	3.15	7.50
C90	1.47	2.85	4.65	11.37
C120	1.83	3.54	5.60	14.00

SPECIAL OFFER CASSETTE STORAGE

Rotating unit up to 32 cassettes stackable
£3.60 (P & P 15p). Car unit with bracket for 10 cassettes £2.80 (P & P 10p).

AMTRON KITS

Model No	Description	£ p
127	Noise reduction unit	£9.55
707	Windscreen wiper timer	£7.97
157	Private TV loop trans	£4.95
5250	120-160 MHz VHF tuner	£11.31

Description	£ p	Description	£ p
310 Radio control receiver	£3.29	690 DC motor speed Gov.	3.31
300 4-channel R/C transmitter	6.61	700 Electronic Chaf-finch	7.92
345 Superhet receiver	6.61	760 Acoustic switch	12.57
65 Simple transistor tester	1.66	780 Metal Detector (electronics only)	10.91
115 8 watt amplifier	4.50	790 Capacitive Burglar alarm	7.92
120 12 watt amplifier	4.73	835 Guitar preamp	4.99
125 Stereo control unit	6.61	840 Delay car alarm	6.99
130 Mono control unit	4.16	875 CAP Discharge ignition for car engine (-Ve Earth)	13.19
605 Power supply for 115	5.31	80 Scope Calibrator	2.65
610 Power supply for 120	5.31	255 Level indicator	6.98
615 Power supply for 2x120	6.64	525 120-160MHz VHF timer	11.31
230 AM/FM aerial amplifier	3.29	715 Photo cell switch	8.97
240 Auto packing light	6.90	795 Electronic continuity tester	4.97
275 Mic preamplifier	6.98	860 Photo timer	15.51
5705 LF generator 10Hz-1mHz	21.45	235 Acoustic Alarm for driver	8.61
5755 Sq wave generator 20Hz-20KHz	19.77	465 Quartz XTAL checker	9.90
590 SWR meter	9.47	220 Signal injector	2.65
630 STAB Power supply 6-12V 0.25-0.1A	9.24	350 VOX	13.62
		432 Testakit	21.83
		670 Buffer Battery Charger	7.59
		850 Electronic Keyer	16.37

FREE NEW '74/75 SEMI-CONDUCTOR AND VALVE LISTS
Ref No. 36 on request

TEST EQUIPMENT MULTI-METERS



Description	£
(Carr. packing 35p) U4324 20kV with case 9-25	8.25
U4325 20kV with steel case	8.75
U4313 20kV with steel case	12.50
U4317 20kV with case 16-50	10.50
U4341 33kV plus transistor tester steel case	10.50
U4323 20kV plus 1kHz 465kHz OSC with case	7.70
ITL-2 20kV slim type	5.95
THL33D (L33DX) 2kV Robust	7.50
TP55N 20kV (Case E2)	6.25
TP10S 2kV	6.25
TW20S 20kV	10.00
TW50S50kV	11.25
EP10KN 10kV	9.95
AF10S 50kV Deluxe (case £1.90)	12.50
S100TR 100kV Plus transistor tester	22.50

GENERAL TEST EQUIPMENT

Description	£
(Carr. packing 50p) (Carr. packing 30p) NEW REVOLUTIONARY SUPERTESTER 680R	18.50
680R 680R Multi-tester	18.50
Accessories	
Transistor tester	11.00
Electronic voltmeter	18.00
Amplclamp	11.95
Temperature probe	11.95
Gauss meter	11.95
Signal injector	5.95
Phase sequence	5.95
EHT probe	5.95
Shunts 25/50/100A	4.50
*13100 IMA Strip chart recorder	44.00
*TK40 AC Multivoltmeter	19.75
*TK15 Grid dip meter 440kHz-28MHz	19.50
*TK65 28 Range valve voltmeter	22.50
*TK20D RF Generator 120kHz-500mHz	18.95
*TK22D AF Generator 20Hz-200kHz	19.95
*HM350 In circuit transistor tester	19.50
*C3025 Deluxe meter 1-300mHz	6.95
*TT145 Compact transistor tester	14.75
*TG3-36 R/C osc 20Hz-200kHz	19.75
*C3042 SWR Meter	5.75
*SE350A Deluxe signal tracer	12.55
*SE400 Min-Tab. all in one tester	15.50
*HM3 Scope 500 000kHz (Carr. £1)	43.00
*C3043 5 CH F/A meter 1-300mHz	5.75
Resistance sub box (post. etc.)	2.40
Capacitor (20p)	2.10
2A variable transformers (carr. £1)	6.55
Radio activity counter 0-10r (carr. £1)	9.97
Mains unit for above (carr. 50p)	3.75

NEW REVOLUTIONARY SUPERTESTER

Description	£
680R 680R Multi-tester	18.50
Accessories	
Transistor tester	11.00
Electronic voltmeter	18.00
Amplclamp	11.95
Temperature probe	11.95
Gauss meter	11.95
Signal injector	5.95
Phase sequence	5.95
EHT probe	5.95
Shunts 25/50/100A	4.50
*13100 IMA Strip chart recorder	44.00
*TK40 AC Multivoltmeter	19.75
*TK15 Grid dip meter 440kHz-28MHz	19.50
*TK65 28 Range valve voltmeter	22.50
*TK20D RF Generator 120kHz-500mHz	18.95
*TK22D AF Generator 20Hz-200kHz	19.95
*HM350 In circuit transistor tester	19.50
*C3025 Deluxe meter 1-300mHz	6.95
*TT145 Compact transistor tester	14.75
*TG3-36 R/C osc 20Hz-200kHz	19.75
*C3042 SWR Meter	5.75
*SE350A Deluxe signal tracer	12.55
*SE400 Min-Tab. all in one tester	15.50
*HM3 Scope 500 000kHz (Carr. £1)	43.00
*C3043 5 CH F/A meter 1-300mHz	5.75
Resistance sub box (post. etc.)	2.40
Capacitor (20p)	2.10
2A variable transformers (carr. £1)	6.55
Radio activity counter 0-10r (carr. £1)	9.97
Mains unit for above (carr. 50p)	3.75

PA-DISCO LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses etc. etc.

FREE stock lists (Ref. No. 18) on request. CALL US AND SEE FOR YOURSELF at Henry's Disco Centre, 309 Edgware Road Tel. 01-723 6963

8% TO BE ADDED TO ALL ORDERS (EXPORT V.A.T. FREE)
FOR MORE ELECTRONICS SEE BACK PAGE

Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. E.B.O.E.
Hi Fi and Electronic Centres Open 9 am - 6 pm

- the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed
Pak No. EQVT
T1 8 263713 OC71
T2 8 D1374 OC75
T3 8 D1216 OC81D
T4 8 26381T OC81D
T5 9 26392T OC82
T6 8 26344B OC44
T7 8 26345B OC45
T8 8 26378 OC78
T9 8 26399A 2N1302
T10 8 26417 AF117
All 55p each pak

ND120 NIXIE DRIVER TRANSISTOR.
Suitable replacement for BSX21, C407, 2N1893 120vch.
1 25 100+
0.19 0.17 0.16

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqt. ZTX300 8p each. Any Quantity.

GP100 TO3 METAL CASE GERMANIUM
V_{beo}=80V, V_{ceo}=50V, I.C.=10 amps, P_{tot}=30W, h_{fe}=30-170.
Replaces the majority of germanium power transistors in the OC, AD and NKT range.
1 25 100+
0.48 0.44 0.40

GP300 TO3 METAL CASE SILICON
V_{beo}=100V, V_{ceo}=60V, I.C.=15 amps, P_{tot}=115W, h_{fe}=20, 1000T=1MHz. Suitable replacement for 2N3055, BDY11 or BDY20.
1 25 100+
0.55 0.53 0.51

NEW 8th Edition
250 pages

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK, £1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in T.P. Sins. to 2N2906, BCY70. When ordering please state preference NPN or PNP.
20 For 0.55
50 For 1.10
100 For 1.92
500 For 8.25
1000 For 14.30

SIL. G.P. DIODES 5p
300mA 30 0.55
40PIV(Min.) 100 1.85
Sub-Min. 500 5.50
Full Tested 1,000 9.90
Ideal for Organ Builders.

ADI161/162
M/P COMP. GERM. TRANS. OUR LOWEST PRICE! Or 75p PER PAIR.

LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS

PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-33V 300mA (DO-7 Case) 12p ea. 1.1W (Top-Hat) 18p ea. 10W (SO-10 Stud) 32p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Price 5p
Q 1 20 Red spot transistors pop	0.55
Q 2 16 White spot R.F. transistors pop	0.55
Q 3 4 OC77 type transistors	0.55
Q 4 6 Matched transistors OC44/45/81/81D	0.55
Q 5 4 OC74 transistors	0.55
Q 6 5 OC72 transistors	0.55
Q 7 4 AC128 transistors pop high gain	0.55
Q 8 4 AC126 transistors pop	0.55
Q 9 7 OC81 type transistors	0.55
Q 10 7 OC71 type transistors	0.55
Q11 2 AC127/128 Complementary pairs pop/pop	0.55
Q12 3 AF116 type transistors	0.55
Q13 3 AF117 type transistors	0.55
Q14 3 OC171 H.P. type transistors	0.55
Q15 7 2N2924 Sil. Epoxy transistors mixed colours	0.55
Q17 5 npn 2 x ST.141 & 3 x ST.140	0.55
Q18 4 MDT'S 2 x MAT 100 x 2 x MAT 120.	0.55
Q19 3 MDT'S 2 x MAT 101 x 1 x MAT 121.	0.55
Q20 4 OC44 Germanium transistors A.P.	0.55
Q21 4 AC137 npn Germanium transistors	0.55
Q22 20 NKT transistors A.P. R.F. coded	0.55
Q23 10 OA202 Silicon diodes sub-min.	0.55
Q24 8 OA81 diodes.	0.55
Q25 15 IN914 Silicon diodes 75PIV 70mA	0.55
Q26 8 OA95 Germanium diodes sub-min IN56B	0.55
Q27 2 10A 600 PIV Silicon rectifiers 18425R	0.55
Q28 2 Silicon power rectifiers BYZ13	0.55
Q29 4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.55
Q30 7 Silicon switch transistors 2N706 npn	0.55
Q31 6 Silicon switch transistors 2N708 npn	0.55
Q32 3 pop Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q33 3 Silicon npn transistors 2N1711	0.55
Q34 7 Silicon npn transistors 2N2369, 100MHz (Co-Le P397)	0.55
Q35 3 Silicon pop TO-5, 2 x 2N2904 & 1 x 2N2907	0.55
Q36 7 2N3646 TO-18 plastic 300MHz npn	0.55
Q37 3 2N3053 npn Silicon transistors	0.55
Q38 5 pop transistors 3 x 2N3703, 2 x 2N3702	0.55

555IC 65p each

MAMMOTH I.C. PAK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS' FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS. MANY CODED also SOME UNKNOWN TYPES—YOU TO IDENTIFY.

PAK NO. M.I.C. 200

PRICE £1.25 per PAK including P. & P. and VAT

1974 CATALOGUE NOW READY 10p

INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0.55	UIC46	= 5 x 7446	0.55	UIC86	= 5 x 7486	0.55
UIC01	= 12 x 7401	0.55	UIC48	= 5 x 7448	0.55	UIC90	= 5 x 7490	0.55
UIC02	= 12 x 7402	0.55	UIC50	= 12 x 7450	0.55	UIC91	= 5 x 7491	0.55
UIC03	= 12 x 7403	0.55	UIC51	= 12 x 7451	0.55	UIC92	= 5 x 7492	0.55
UIC04	= 12 x 7404	0.55	UIC53	= 12 x 7453	0.55	UIC93	= 5 x 7493	0.55
UIC05	= 12 x 7405	0.55	UIC54	= 12 x 7454	0.55	UIC94	= 5 x 7494	0.55
UIC06	= 8 x 7406	0.55	UIC60	= 12 x 7460	0.55	UIC95	= 5 x 7495	0.55
UIC07	= 8 x 7407	0.55	UIC70	= 8 x 7470	0.55	UIC96	= 5 x 7496	0.55
UIC10	= 12 x 7410	0.55	UIC72	= 8 x 7472	0.55	UIC100	= 5 x 74100	0.55
UIC20	= 12 x 7420	0.55	UIC73	= 8 x 7473	0.55	UIC121	= 5 x 74121	0.55
UIC30	= 12 x 7430	0.55	UIC74	= 8 x 7474	0.55	UIC141	= 5 x 74141	0.55
UIC40	= 12 x 7440	0.55	UIC76	= 8 x 7476	0.55	UIC142	= 5 x 74151	0.55
UIC41	= 5 x 7441	0.55	UIC80	= 5 x 7480	0.55	UIC193	= 5 x 74193	0.55
UIC42	= 5 x 7442	0.55	UIC81	= 5 x 7481	0.55	UIC199	= 5 x 74199	0.55
UIC43	= 5 x 7443	0.55	UIC82	= 5 x 7482	0.55			
UIC44	= 5 x 7444	0.55	UIC83	= 5 x 7483	0.55			
UIC45	= 5 x 7445	0.55						

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC1X.

2 Amp. BRIDGE RECTS.
50 v RMS 35p each
100 v RMS 40p "
200 v RMS 45p "
400 v RMS 50p "
1,000 v RMS 55p "
Size 16 mm x 16 mm.

D1699 NPN SILICON DUAL TRANSISTOR
(Similar to 2N2069)
1 25 100+
0.28 0.28 0.23

LINEAR INTEGRATED CIRCUIT PAKS

Pak No.	Contents	Price
UIC709	10 x 709	0.55
UIC710	7 x 710	0.55
UIC741	7 x 741	0.55
UIC747	5 x 747	0.55
UIC748	7 x 748	0.55

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	60 Mixed Germanium Transistors AF/RP	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA3, OA47	0.55
U 4	40 Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 Sil. Planar Trans. NPN like BS95A, 2N706	0.55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0.55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0.55
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1332, 2N2904	0.55
U 13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0.55
U 14	150 Mixed Silicon and Germanium Diodes	0.55
U 16	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.55
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.55
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.55
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.55
U 19	25 Silicon NPN Transistors like BC108	0.55
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U 21	30 AF. Germanium Alloy Transistors 2N300 Series & OC71	0.55
U 23	30 MDT's like MHz Series PNP Transistors	0.55
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.55
U 25	25 300MHz NPN Silicon Transistors 2N708, B8Y27	0.55
U 26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U 29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1.15
U 32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.55
U 33	15 Plastic Case 1 Amp Silicon Rectifiers 1N4000 Series	0.55
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2N3024	0.55
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.55
U 36	25 Silicon Planar NPN Transistors TO-5 BFY20/51/52	0.55
U 37	30 Silicon Alloy Transistors 80-2 PNP OC200, 2N322	0.55
U 38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0.55
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.55
U 40	10 Dual Transistors 5 lead TO-5 2N2060	0.55
U 43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.55
U 44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0.55
U 45	7 3A SCR. TO66 up to 600PIV	1.10
U 46	20 Unijunction transistors similar to T1843	0.55
U 47	10 TO229AB plastic triacs 50V 6A	1.10
U 48	9 NPN Sil. power transistors like 2N3055	1.10
U 49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	1.10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE
One 55p Pak of your own choice free with orders valued £4 or over

SIL. RECTS. TESTED
PIV 300mA 750mA 1A 1.5A 3A 10A 30A (DO7)(SO16) Plastic (SO16) (SO10) (SO10) (TO48)

	P	P	P	P	P	P	P	P
50	05	08	1N4001	05	08	15	21	60
100	05	07	1N4002	08	10	17	23	75
200	08	10	1N4003	07	12	22	25	1.00
400	08	15	1N4004	08	15	30	38	1.35
600	09	17	1N4005	10	18	38	45	1.90
800	12	19	1N4006	11	20	38	55	2.10
1000	14	30	1N4007	12	25	48	65	2.50
1200		35		30	58	75	3.00	

CADMIUM CELLS

ORP12 48p

PIV	50	100	500	400	600	800
1A	TO5	0.22	0.27	0.32	0.42	0.70
3A	TO66	0.27	0.32	0.42	0.52	0.70
5A	TO66	0.39	0.52	0.54	0.59	0.75
5A	TO4	0.39	0.52	0.54	0.62	0.75
7A	TO48	0.52	0.55	0.82	0.87	0.84
7A	TO48	0.55	0.83	0.87	0.93	1.07
10A	TO48	0.58	0.82	0.67	0.77	0.97
30A	TO48	1.27	1.54	1.78	1.93	4.40

NEW LOW PRICED TESTED S.C.R.'S

PIV	50	100	500	400	600	800
1A	TO5	0.22	0.27	0.32	0.42	0.70
3A	TO66	0.27	0.32	0.42	0.52	0.70
5A	TO66	0.39	0.52	0.54	0.59	0.75
5A	TO4	0.39	0.52	0.54	0.62	0.75
7A	TO48	0.52	0.55	0.82	0.87	0.84
7A	TO48	0.55	0.83	0.87	0.93	1.07
10A	TO48	0.58	0.82	0.67	0.77	0.97
30A	TO48	1.27	1.54	1.78	1.93	4.40

2N3055
115 VATT SIL POWER NPN
55p EACH

All prices include V.A.T. Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE - HERTS
Postage and packing add 15p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.
Guaranteed Satisfaction or Money Back

DISCOUNTS UP TO 60%

FANTASTIC OFFER GARRARD SP25 Mk. IV PLINTH AND COVER

Garrard SP25 Mk IV
deck Goldring G800
Cartridge Teak fin-
ished Plinth Cover
(non hinged). All
Leads

GLOBAL'S PRICE £19.80
Carr & Ins £1.93

TURNTABLES

Please add £1.05 for P. & P. & Ins.

Garrard SP25 Mk IV Chassis £12.95
Garrard 86SB P.C. Cart (Hinged
Cover) £47.50
Garrard 86SB Chassis £22.40
Garrard 401 Chassis £32.00
Goldring 101 Mk. II P.C. G800 £23.70
Goldring GL75 P.C. G800 £39.95
Goldring GL78 P.C. G800 £44.40
Goldring GL85 P.C. £63.50
Pioneer PL12D P.O.A. £12.95
Sansui SR 212 P.O.A. £72.25
Thorens TD125 Mk II

Thorens TD125AB Mk II £111.95
Thorens TD160 ABC £59.95
Thorens TD165 ABC £52.95
Transcriptor Saturn with Vestigal
Arm £53.95

AMPLIFIERS

Please add £1.05 for P. & P. & Ins.

Amstrad Integra 4000 Mk II £25.75
Amstrad IC2000 Mk II £31.95
Amstrad 8000 Mk III £18.50
Eagle AA4 £43.10
Eagle AA6 £51.25
Metro-Sound ST20E Mk II £26.15
Metro-Sound ST40 £33.25
Metro-Sound ST60 £46.75
P.O.A. £9.10
Sinclair 2000 £29.95
Sinclair 4000 £44.95
Teleton GA202 £30.50
Teleton SAQ206B £23.95
Teleton SAQ307D £27.20

COMBINATION UNITS

Please add £1.10 for P. & P. & Ins.

Goodmans Compact 80 (Teak) £131.15
Goodmans Compact 90 £169.99
Goodmans Compact 1-10 (Teak) £191.00

TUNERS

Please add £1.05 for P. & P. & Ins.

Amstrad MLX 3000 £26.25
Eagle AA6 £45.95
Eagle TST 152 £32.95
Metro-Sound FMS 20 Mk II £33.35
P.O.A. £9.10
Teleton ST202 £36.60
Sinclair 2000 £29.95
Sinclair 4000 £37.45

TUNER/AMPLIFIERS

Please add £1.21 for P. & P. & Ins.

Amstrad 5000 £56.95
Goodmans Module 80 £72.50
Goodmans Module 90 £92.90
Goodmans 1-10 Module £108.50

CARTRIDGES

Please add 12p for P. & P. & Ins.

Goldring G800H £3.85
Goldring G800E £8.20
Goldring G800 £3.40
Shure V15 Type 3 £28.40
Shure M75EJ Type 2 £7.90
Shure M75ED Type 2 £9.10
Shure 91ED £8.20
Shure M3D £3.10
Sonotone 9 TACHD £13.10

SPEAKERS

Add £1.82 P. & P. & Ins. per Pair

Amstrad 1500 £25.65
Amstrad 2500 £29.95
Collection County £45.25
Collection Ditton 10 Mk II £42.65
Collection Ditton 15 £65.50
Collection Ditton 25 £129.95
Collection Ditton 44 £108.45

Collection Ditton 66 £198.95
Collection Hadleigh £39.25
Goodmans Dimension 8 £127.95
Goodmans Havant SL £44.50
Goodmans Magisters £107.75
Goodmans Magnum K2 SL £84.85
Goodmans Minster £36.00
Goodmans Mozo 3SL £64.50
Marsden Hall 110F/C £27.85
Marsden Hall 150F/C £31.95
Marsden Hall 200F/C £39.45
Marsden Hall 300F/C £29.25
Wharfedale Denton 2 £77.80
Wharfedale Dovedale £72.85
Wharfedale Glendale £52.65

AMSTRAD IC2000 Mk. II STEREO SYSTEM

Amstrad IC2000 Mk II with increased power
25 + 25W amplifier. Complete with a pair
of Amstrad Acoustica 2500 speakers
Garrard SP25 Mk IV deck G800 Cart.
Plinth Cover (non hinged). All leads.

GLOBAL'S PRICE £80.75

Carr & Ins £3.30

STEREO HEADPHONES

Please add 42p for P. & P. & Ins.

Koss ESP 6 £47.85
Koss ESP 9 £64.50
Koss K7/11 Red Devil £9.99
Koss K8 £11.70
Koss K6 LC £12.25
Koss KD 727E £14.90
Koss 747 £18.35
Koss HV1 £19.95
Koss HV1/LC £23.60
Koss PRO 5/LC £27.15
Koss K7/11 Black £9.90
Sennheiser HD414 £10.75
Sennheiser HD424 £15.55

GLOBAL AUDIO

Please Note Every effort is
made to ensure prices listed are
correct at time of going to press
but are subject to alteration
without prior notice. © G&E

FULL 12 MONTH AFTER SALES SERVICE

We give a FULL 12 MONTH GUARANTEE on all
products purchased at any branch parts and labour
absolutely FREE

BIRMINGHAM

Tivoli Shopping Centre
1536 Coventry Road, Yardley
Tel: 021 706 9949

ESSEX

4 High View Parade
Redbridge Lane East,
Woodford Avenue, Ilford
Tel: 01 550 1086

LONDON

378 Edgware Road W2
Tel: 01-262 3847
174 Pentonville Road, N1
Tel: 01 278 1769
120 Notting Hill Gate, W11
Tel: 01-229 1437
50 Stamford Hill, N16
Tel: 01-805 4699

PORTSMOUTH

17 London Road, North End
Tel: 0705 68321

READING

46 Market Place,
Tel: 0734 595331

WATFORD

105 St Albans Rd. Tel. 39832

H. P. FACILITIES

AVAILABLE FOR
PERSONAL CALLERS ONLY
MAIL ORDERS
TO 174 PENTONVILLE
ROAD, LONDON, N1
Order with confidence
Send Postal Order,
Cheque, Money Order,
Bank Draft, Giro or
Cash by Reg. Mail

**NO HIDDEN PRICES AT GLOBAL
AUDIO - ALL OUR PRICES ARE
SHOWN WITH VAT INCLUDED**

PERSONAL CALLERS VERY WELCOME!
COMPARE OUR PRICES WITH ANY IN THE BOOK!
OPEN MONDAY TO SATURDAY 9.30am - 6pm
LATE NIGHT FRIDAY OPEN UNTIL 7pm

PLEASE NOTE All Cheques,
Money Orders, Postal Orders,
Bank Draft, or Giro to be
made payable to
MAUTOMEAD LTD.



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB124, P.O. BOX 156, JERSEY

NAME :

ADDRESS :

EB114

BLOCK CAPS please

VARICAP TUNER


LP1185/86 ... £10.25/pair
MC1310P Decoder I/C ... £3.15
LP1400 Decoder Module ... £5.15
MFC4060 Regulator I/C ... £0.78
P.C. BOARDS MC1310P or LP1400 ... £1.87
SPEAKER BRACKETS 2-way swivel ... £8.00/pair
READY BUILT BOARDS £24.25 (I/C) or
£25.25 (LP1400)

Prices include V.A.T. P. & P. 25p.

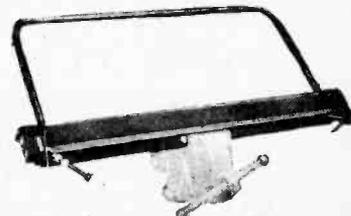B. & B. ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK, NOTTS.
Tel.: NEWARK 6895 (Anytime)

PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel x 36in. wide ... £21 carr. free
No. 2. Capacity 18 gauge mild steel x 24in. wide ... £15 carr. free
No. 3. Capacity 16 gauge mild steel x 18in. wide ... £15 carr. free
Also new bench models. Capacities 36in. x 18 gauge £40. 24in. x 16 gauge £38.
Carriage free. Add 8% VAT to total price of machine.
End folding attachments for radio chassis. Tray and Box making. Steel Angle
36in. model, 40p per ft. Other models 30p. The two smaller models will form
flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Telephone 403997

MAPLIN ELECTRONIC SUPPLIES

ORGAN BUILDERS



Keyboards: High quality adjustable type
Slipping front 61-note C to C. £18.50.
Slipping front 49-note C to C. £14.35.
Flat front 48-note F to E. £14.35.
Contact blocks GB-2 (2 make contacts). 15p.
Palladium earth bar per octave length. 15p.
Stop tabs rocker type not engraved (white, red, grey or black) with DPDT switch. 49p.
Gold clad phosphor-bronze contact wire per yard 25p.

BASIC ORGAN CIRCUIT

Leaflet MES 51 shows a complete circuit for a basic fully polyphonic organ. Send only 15p for leaflet and start building now! REMEMBER—when you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details.

LEAFLET MES 52 shows how to extend your MES 51 basic organ to two keyboards with lots more stops. Just send 5p (stamp) with an S.A.E. and we will send you a copy.

REVERBERATION UNIT

Enhances the sound of any electronic musical instrument. Ready built spring line driver module suitable for use with almost any spring line. £5.34.

Two types of spring line available:

Short line. £3.05.

Long line. £7.59.

S.A.E. please for details. Leaflet MES 24.

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator.
★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the 8AJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3.7in. x 4.5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed. DMO2 (with tremulant) ONLY £14.25.

DMO2 (without tremulant) £12.25.

8AJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. 8AJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.

★ SAME DAY SERVICE



P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We are stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards.

Send S.A.E. now for our detailed price lists.

E.T.I. SYNTHESISER

We stock all the parts for the "Electronics Today International" synthesiser including all the P.C.B.'s required and all the metalwork including a drilled and printed front panel for a truly professional finish.

Some of the circuits in this brilliant design are entirely original. Independent authoritative opinions agree the E.T.I. International Synthesiser is technically superior to practically all synthesisers available today.

S.A.E. please for our detailed price lists.


CAPACITORS

Sub-miniature Axial lead electrolytic

Mid V	Price	Mid V	Price
1.63	6p	68	6p
1.5-63	6p	68	16p
2-2.63	6p	68	63 14p
3-3.63	6p	100	4 6p
4-7.63	6p	100	10 6p
6-8.40	6p	100	25 6p
6-8.63	6p	100	40 6p
10	25 6p	100	63 16p
10	63 6p	150	6 6p
15	16 6p	150	16 6p
15	16 6p	150	25 6p
15	63 6p	150	40 14p
22	10 6p	150	63 16p
22	25 6p	220	4 16p
22	63 6p	220	10 16p
22	63 6p	220	16 25p
33	6 6p	220	16 25p
33	16 6p	220	25 14p
33	16 6p	220	40 16p
33	25 6p	220	63 25p
47	4 6p	220	63 25p
47	10 6p	330	4 25p
47	25 6p	330	10 25p
47	40 6p	330	16 28p
47	63 6p	330	25 28p
47	63 6p	330	40 28p



PLUGS AND SOCKETS

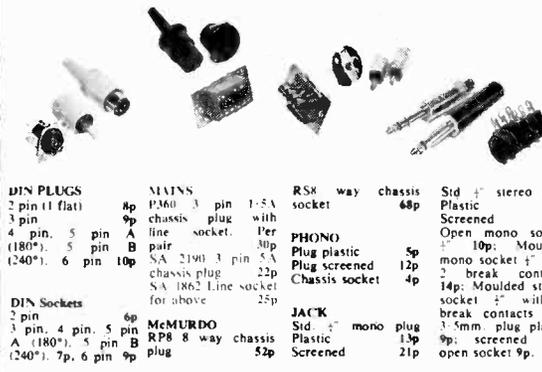

DIN PLUGS
2 pin (1 flat) 8p
3 pin 9p
4 pin, 5 pin A pair 10p
(180°), 5 pin B pair 10p
(240°), 6 pin 10p

MAINS
P.M60 3 pin 1-5A line socket. Per pair 30p
SA 2300 3 pin 5A chassis plug 22p
SA 1862 Line socket for above 25p

RSK way chassis socket 68p

PHONO
Plug plastic 5p
Plug screened 12p
Chassis socket 4p

JACK
Std. 1/2" mono plug Plastic 13p
RFS 8 way chassis plug 52p
Screened 21p

Std. 1/2" stereo plug Plastic 18p
Screened 30p
Open mono socket 10p
Moulded mono socket 1/2" with 2 break contacts 14p
Moulded stereo socket 1/2" with 3 break contacts 18p
3.5mm plug plastic 9p
screened 15p
open socket 9p.

WE KNOW YOU NEED IT!



The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

LINEARS

CA3046 Transistor array £4.25
LH0042C TO99 (TO5) FET up Op Amp £4.25
LM301A 8-pin DIL Op Amp 3p
MC1301L 14-pin Stereo Preamplifier £1.39
MC1310P 14-pin DIL FM Stereo Decoder (no coils needed) £3.15
MFC4000B 1/4W Audio Amp 38p
MFC6040 Electronic attenuator 86p
MFC8010 8-pin case, 1W Audio Power Amp £1.20
MFC9070 10-lead case, 2W Audio Power Amp £1.37
NES55V 8-pin DIL Precision Timer 69p
NE561B 16-pin DIL Phase Locked Loop £4.48
SG1495D 14-pin DIL Four Quadrant Analogue Multiplier £2.70
SG3402N Amplifier/Multiplier £1.69
µA723C TO99 (TO5) 2 to 37V Voltage Regulator 75p
µA723C 14-pin DIL 2 to 37V Voltage Regulator 75p
µA741C 8-pin DIL Op Amp 36p
µA741C 14-pin DIL Op Amp 45p
µA747C 14-pin DIL Dual Op Amp £1.05
µA748C 8-pin DIL Op Amp 39p
ZN414 TO5 TRF Radio £1.20

Full data, pin connexions, etc., on nearly all types above in our catalogue. Price 25p.

OMNIUM GATHERUM

PP3 6 etc. battery clip dual min 9p.
PP1 9 etc. battery clip separate per pair 6p.
Pair crocodile clips 1 red 1 black insulated sleeve 10p.
Solder Multicore 22 s.w.g. 10 metres 25p.
Silicone grease in special dispenser 20ml 54p.
Terminal Block 12-way 5A 14p.
Probe clips spring loaded per pair 30p.
Panel fuse holders 20mm 20p; 1-in 41p.

Transformers
LT700 min output transformer Pri 1 2kΩ Sec 4Ω 200mW 50p.

Sub-main. Mains Transformer
6-0-6V 100mA 95p, 12-0-12V 50mA 95p.
Size: Both approx. 30 x 27 x 25mm.

Min. Mains Transformer
Size: 46 x 31 x 38mm.
0-12V 250mA 0-12V 250mA £1.36.

Mains Transformer MT3AT
Pri. 200-220-240V Sec. 12-15-20-24-30V 1A £3.60.

Mains Transformer MT206AT
Pri. 200-220-240V Sec. 0-15-20V 1A 0-15-20V 1A £3.88.

POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle

Single gang Lin or Log
5k 10k 25k 50k 100k 250k
500k 1M 2M (and 1k 1in 16p)

Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 49p.

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 31p.

PRESETS
Sub-miniature 0-1W Vert or Horiz 100, 250, 600, 1k, 2.5k, 5k, 10k, 25k, 60k, 100k, 250k, 500k 1/4W 7p

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 to 3 way each 36p.
Mains rotary DPST 250V 2A 20p.

Slide Sub-miniature DPDT 9p

Push to make non-locking 14p

Toggle 250V 1.5A with ON/OFF plate 25p.

High quality "sub-miniature" toggle switches
SPDT 1.5A 240V a.c. 58p
DPDT 3A 240V a.c. 77p
Four Pole DT 3A 240V a.c. £1.37

RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 11Ω to 910k E12 & E24 1p
Carbon Film 1W 5% 10Ω to 10M E12 3p
Metal Oxide 1/4W 5% 10Ω to 1M E12 & E24 1p
W1-wound 2 1/2W 10% 0.2Ωohms to 0.47ohms E12 14p
Wirewound 2 1/2W 5% 10ohm to 270ohms E12 12p


E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 66, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

VAT Please add 8% to the final total.

Post and Packing FREE in U.K. (15p handling charge on orders under £1)
First class post pre-paid envelope supplied free with every order

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea 0702 44101

'BIG' Discounts

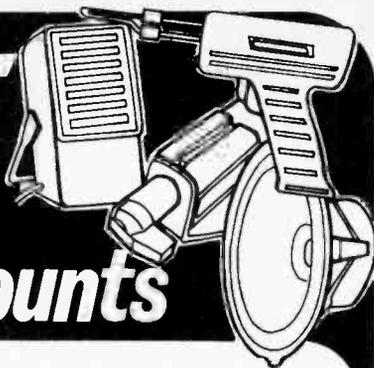

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	ELAC 10in 8 ohm Dual cone	3-50
EMI 13in x 8in 3, 8 or 15 ohm			GOODMANS 6in 8 ohm Dual cone	2-15
Plain	2-05		FANE, 7in x 4in, 3 or 8 ohm	1-00
With Co-Axial Tweeter 8 ohm only	2-20		ADASTRA 10in, 8 or 15 ohm, 10W	3-45
Twin Tweeter	3-70		BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-85
Type 350, 8 ohm, 20W	7-50			P. & P. 0-30
6in, 8 ohm, 10W	2-40		5in, 8 ohm, C/Mag.	0-85
8in, 8 ohm, 10W	3-75		2 1/2in, 8 ohm or 64 ohm	0-15
12in, 8 ohm, 20W	6-70			
8in x 3in, C/Mag. 5W	1-25			
8in x 5in, Dual cone 8 ohm, 10W	2-45			
ELAC 8in 8 ohm Dual cone	2-25			

TWEETER AND CROSSOVER		£	Dome Tweeter 8 ohm, 30W <th>5-40</th>	5-40
EMI 3 1/2in, 3 or 8 ohm C/Mag.	1-20		Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-20
Cone Tweeter 8 or 15 ohm, 10W	2-40			P. & P. 0-10
Cone Tweeter 8 ohm, 3W	1-45			
Horn Tweeter 8 ohm, 20W	6-40			

KIT FORM CABINETS, TEAK VENEER.		£	13in x 8in cutout <th>3-50</th>	3-50
12in x 12in x 6in with 8in, 8in x 6in or 6in and 3 1/2in cutout	2-45		18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-25
17in x 10in x 9in with 8in or				P. & P. each 0-45

MICROPHONES		£	TW209 CONDENSER MIKE 600 ohm, uni-dir <th>9-85 </th>	9-85
CM70 Planet stick metal, switch crystal	1-55		Cassette Stick Mike with R. Control on/off switch (2.5 and 3.5mm J/Fly)	1-45
DM150 Dynamic omni-dir, ball metal	3-85			P. & P. 0-20
UD130 50K/600 ohm, uni-dir, ball metal	5-95			

SOLDERING IRONS		£	spare Bib, etc.) <th>3-30</th>	3-30
ANTEX CN240 15W	1-90		X25 25W (low leakage)	1-80
SK1 Kit (15 watt iron, 2				P. & P. 0-10

CARTRIDGES AND STYLI		£	SONOTONE 9TAHC or 9TAHC/G	1-80
ACOS G191/28C or 38C Stereo comp.	1-00		1 1/2in 3509 Stereo ceramic diam.	1-90
GP93/1 or 95/1 Stereo crystal	1-35		GOLDRING G850 (G800)	2-95
GP94/1 or 96/1 Stereo ceramic	1-75		G800E	3-95
GP101 Crystal comp.	0-80			P. & P. 0-10
GP104 Stereo ceramic	1-85		D. Diamond Stylil for above	1-25
BSR X5M or XH Crystal comp.	1-70		G800/G850	1-95
8X6M or 8X8H Crystal comp.	1-90		G800E	3-95
SC5M Stereo ceramic	2-80			P. & P. 0-05

BATTERY ELIMINATORS		£	output 6, 7.5 or 9 d.c. output at 300mA	2-30
240V input 6, 7.5 or 9 300mA	2-95			P. & P. 0-15
12V d.c. input (please specify)				

TAPES		Std.	LP	DP	PLASTIC LIBRARY CASES
5in	50p	65p	1-25p	5in Reels 18p. 3 1/2in. 22p. 7in. 25p.	
5 1/2in	65p	80p	1-45p		P. & P. 1-39p each. 4 or more lot 30p
7in	85p	1-10p	1-80p		

LOW NOISE CASSETTES		£	Cassette Head Cleaner <th>0-35</th>	0-35	
C60	1-5	6-10	11-20	Cassette Cases	0-10
C90	35p	33p	30p	P. & P. 1-5 each	0-03
C120	45p	43p	40p	6-10 lot	0-15
	55p	52p	50p	11-20 post free	

BIB ACCESSORIES		£	CALCULATORS	£19-00
Tape Editing Kit, Ref. 23	1-35		SINCLAIR Cambridge Scientific	£29-00
Recording Tape Splicer, Ref. 20	1-15			
Cassette Tape, Editing, Ref. 24	1-50		WHARFEDALE SPEAKER BARGAINS	P. & P.
Cassette Salvage Kit, Ref. 29	0-45		Linton 2 Kit (pr.)	19-00 1-00
12's Cassette Case, Ref. 34	1-50		Glendale 3 Kit (pr.)	33-50 1-50
Stylus Balance, Ref. 32A	1-20		Dovedale 3 Kit (pr.)	52-00 1-50
Spirit Level, Ref. 46	0-50		Denton 2 Speaker (pr.)	30-00 2-00
Hi-Fi Stereo Test Cassette	2-10		Linton 2 Speaker (pr.)	39-50 2-00
Groove-Kleen Record Cleaner	1-90		Dovedale 3 Speaker (each)	42-00 2-00
	P. & P. 0-10		Glendale 3 Speaker (pr.)	57-00 3-00
			Kingdale 3 Speaker (each)	59-95 3-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics

Mail Order Department PE12
P.O. Box 470, Manchester M60 4BU



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5 Savbit alloy 18 swg, 32p (illustrated).
Size 19A 60/40 alloy 18 swg, 34p
Size 15 60/40 alloy 22 swg, 36p

IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 56p



Size 12 REEL for Service Engineers and Electricians. 18 swg Savbit alloy. £1-72



BIB WIRE STRIPPER AND CUTTER

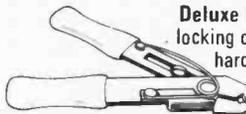

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 90p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP



Phoenix Electronics (Portsmouth) Ltd.

139-141 Havant Road, Drayton, Portsmouth, Hants PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

THIS MONTH'S BARGAIN OFFER

Professional soldering kit, 25W iron, spare tips, tool and solder, together with 10 x ACY30, 10 x 2N3394, 2 x WO2 bridges, and 2 x PP3055 Plastic Power Transistors.—Current List Value £6-50.

Bargain Pack PEP/1A—£4-30

Please send your catalogue—free!

Name

Address

PEP/1A

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT. PE, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK, BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue sent free on request, 10p
stamp appreciated.

PLEASE ADD 8% VAT

RESISTORS

½W and ¼W PIHER.
¼W 2% ELECTROSIL

Power watts	Tolerance	Range	Values available	Price
½	5%	4.7 Ω - 2.2M Ω	E24	1-99 100+
½	10%	3.3M Ω - 10M Ω	E12	1.3p 1.1p
¼	2%	10 Ω - 1M Ω	E24	3.5p 3p
¼	10%	1 Ω - 3.9 Ω	E12	1.3p 1.1p
¼	5%	4.7 Ω - 1M Ω	E12	1.3p 1.1p
¼	10%	1 Ω - 10 Ω	E12	8p 7p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5%, Piher resistors 5 off each value 4.7 Ω to 1M Ω.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5k Ω to 2M Ω, log or linear (log ½W, lin ¼W).
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch, 29p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5M Ω. Horizontal or vertical P.C. mounting
(0-1 matrix).
Sub-miniature 0.1W, 6p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	16p	BC109	14p	BD115	75p	BF337	46p	ZTX300	18p
AC126	18p	BC115	16p	BD116	60p	BFY50	22p	ZTX302	20p
AC127	18p	BC116	15p	BD124	81p	BFY51	22p	ZTX341	18p
AC128	18p	BC117	23p	BD131	60p	BFY52	22p	ZTX500	18p
AC141K	22p	BC125	15p	BD132	64p	BRY39	41p	ZTX503	25p
AC142	25p	BC142	24p	BD140	66p	MJE340	47p	2N2646	60p
AD149	79p	BC143	21p	BDY32	57p	MJE370	68p	2N2904	28p
AC176	18p	BC147	12p	BF115	32p	OC26	90p	2N2905	32p
AC187	22p	BC148	12p	BF158	22p	OC28	90p	2N2926	12p
AC188	22p	BC149	12p	BF159	22p	OC35	90p	2N3053	31p
AC193K	28p	BC153	18p	BF160	23p	OC42	16p	2N3054	60p
AD140	53p	BC154	18p	BF161	26p	OC44	12p	2N3055	60p
AD143	73p	BC157	15p	BF164	22p	OC45	12p	2N3702	15p
AD149	79p	BC158	15p	BF173	28p	OC70	12p	2N3703	14p
AD161	42p	BC159	14p	BF177	29p	OC71	12p	2N3704	20p
AD162	42p	BC169	15p	BF178	43p	OC72	12p	2N3705	20p
AF114	25p	BC171	13p	BF179	41p	OC75	12p	2N3706	19p
AF115	25p	BC172	22p	BF180	42p	OC81	12p	2N3707	20p
AF116	25p	BC177	20p	BF181	32p	OC82	12p	2N3708	20p
AF117	25p	BC182	15p	BF182	41p	OCF71	35p	2N3709	19p
AF118	50p	BC182L	16p	BF183	43p	ORP12	65p	2N3710	19p
AF121	50p	BC183	15p	BF184	32p	TIP29A	49p	2N3711	19p
AF126	50p	BC183L	16p	BF185	32p	TIP30A	58p	2N3819	32p
AF127	50p	BC184	18p	BF194	14p	TIP31A	62p	2N4062	25p
AF139	53p	BC186	25p	BF195	17p	TIP32A	74p	40360	46p
AF178	48p	BC187	25p	BF196	15p	TIP33A	98p	40361	43p
AF180	50p	BC212	13p	BF197	16p	TIP34A	148p	40362	45p
AF186	39p	BC212L	15p	BF200	40p	TIP41A	79p	40363	88p
AF239	48p	BC214L	19p	BF259	25p	TIP42A	90p	40406	44p
BC107	13p	BCY70	21p	BF262	26p	TIP43	35p	40486	90p
BC108	13p	BD112	52p	BF263	26p	ZTX108	18p		

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

WIREWOUND POTS. 3W, 10, 25, 50 Ω and decades to 100k Ω, 50p.

DIODES

RECTIFIER

BY127	1250V	1A	12p
IN4001	50V	1A	7p
IN4002	100V	1A	8p
IN4004	400V	1A	8p
IN4006	800V	1A	10p
IN4007	1000V	1A	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

SLIDER POTENTIOMETERS

86mm × 9mm × 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log. or lin. 50p.

DUAL GANG, 10K + 10K etc. log. or lin. 60p.

KNOB FOR ABOVE, 12p.

FRONT PANEL, 90p.

18 Gauge panel 12in × 4in with slots cut for use with
slider pots. Grey or matt black finish complete with
fixings for 4 pots.

BRUSHED

ALUMINIUM

PANELS

12in × 6in, 37p

12in × 2½in, 14p

9in × 2in, 12p

THYRISTORS

2N5060 50V 0.8A 65p

2N5064 200V 0.8A 80p

106F 50V 5A 55p

106D 200V 5A 80p

HEATSINKS—REDPOINT

2W	24p	4W	45p	T05 Clip	5p	T01 Single	5p
3W	36p	6W	60p	T018 Clip	5p	T01 Double	8p

TRANSFORMERS

All have 240V primary

MT30/2 0-12-15-20-24-30V 2A £3.85

MT50/½ 0-19-25-33-40-50V ½A £2.50

MT50/1 0-19-25-33-40-50V 1A £3.15

MT50/2 0-19-25-33-40-50V 2A £4.30

MT60/½ 0-24-30-40-48-60V ½A £3.30

MT60/1 0-24-30-40-48-60V 1A £4.80

MT60/2 0-24-30-40-48-60V 2A £6.80

MULLARD POLYESTER CAPACITORS C180 SERIES

250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p; 0.068µF, 4p;
0.1µF, 4½p; 0.15µF, 5p; 0.22µF, 5½p; 0.33µF, 7p; 0.47µF, 9p; 0.68µF, 12p;
1.0µF, 14½p; 1.5µF, 22p; 2.2µF, 26p.

MYLAR FILM CAPACITORS 100V

0.001µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF,
3p. 0.04µF, 0.05µF, 0.068µF, 0.1µF, 6p.

CERAMIC DISC

CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(µF/v) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40,
15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3,
68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63,
100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4,
10p, 470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16,
1500/6.3, 13p, 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p, 330/63, 680/40,
1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1µF	35V	2.2µF	35V	22µF	16V
0.22µF	35V	4.7µF	35V	33µF	10V
0.47µF	35V	6.8µF	25V	47µF	6.3V
1.0µF	35V	10µF	25V	100µF	3V

VEROBOARD

0.1	0.15
2½ × 3½	26p
2½ × 5	28p
3½ × 3½	28p
3½ × 5	34p
17 × 2½	95p
17 × 3½	130p
17 × 5 (plain)	86p
17 × 2½ (plain)	—
2½ × 5 (plain)	—
2½ × 3½ (plain)	—
Pin insertion tool	62p
Spot face cutter	52p
Pkt. 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	32p	2.5mm insulated	13p
Standard insulated	18p	3.5mm insulated	13p
Stereo screened	44p	3.5mm screened	22p
Standard socket	15p	2.5mm socket	14p
Stereo socket	22p	3.5mm socket	14p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
72p
Plug 12p. Socket 8p.
4 way screened cable, 26p/metre.
6 way screened cable, 31p/metre.

BATTERY ELIMINATOR

£1.70
9V mains power supply. Same size as PP9 battery.

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01µF	12p	0.047µF	16p	0.22µF	28p
0.022µF	14p	0.1µF	20p	0.47µF	38p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of
gas or smoke into an electrical signal. The sensor decreases its electrical resis-
tance when it absorbs depoxidizing or combustible gases such as hydrogen, carbon
monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust
containing air or smoke. This decrease is usually large enough to be utilized
without amplification. Full details and circuits are supplied with each detector.
Detector GDI £2. Smoke and Gas Detector Kits, mains operated with audible
alarm £5.60. Mains operated Meter Indicator £7.90. Mains/Battery Gas Leak
Detector £12.60. 12/24V Battery operated £8.40. 12V Battery operated Two
Remote Sensors £12.80. NOTE: The battery operated kits incorporate our
patented circuit to minimise battery drain. Typically 120mA for 12V. These kits
contain all parts required with the exception of case. Suitable case mains operated
kit £1.60. Battery operated kits £5.

PRINTED BOARD MAKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to
dry, and immerse the board in the etchant. On removal the circuit remains in high
relief.

METERS

2" Scale-500µA, 1mA, 10mA, 100mA

£3.30

BULGIN MAINS CONNECTORS

3 Pin 1½A	Chassis Plug	18p	3 Pin 1½A	Chassis Socket	30p
	Line Socket	22p		Line Plug	24p
3 Pin 3A	Chassis Plug	24p	3 Pin 3A	Chassis Socket	34p
	Line Socket	28p		Line Plug	40p
3 Pin 5A	Chassis Plug	24p			
	Line Socket	32p	2 Pin 5A	Line Plug	20p

THERMISTORS

VA1005	15p
VA1026	15p
VA1033	15p
VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.35

ROTARY MAINS SWITCH


D.P. 2A 35p

LINEAR IC'S

709	14 pin DIL	40p
741	8 pin DIL	40p
741	14 pin DIL	38p
723	14 pin DIL	95p
747	8 pin DIL	85p
748	8 pin DIL	45p
	DIL Sockets 14 pin and 16 pin	16p

WAVECHANGE SWITCH 33p

1p 12W, 3p 4W, 2p 2W, 2p 6W,
4p 3W

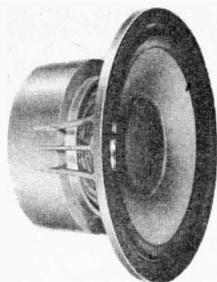

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3. 8 or 15 ohm £7-75
 Baker Group 35 3. 8 or 15 ohm £8-50
 Baker Group 50 12 8 or 15 ohm £12-50
 Baker Deluxe 12in d/cone £10-75
 Baker Major 12in d/cone £8-50
 Baker Regent £7-75
 Baker Superb £14-50
 Baker Auditorium 12 £12-50
 Celestion MH1000, 8 or 15 ohm £10-95
 Celestion PS18 for Unilex £2-55
 Celestion G12M 8 or 15 ohm £12-00
 Celestion G12H 8 or 15 ohm £15-00
 Celestion G15C 8 or 15 ohm £24-00
 Celestion G18C 8 or 15 ohm £33-00
 Coral 6 1/2 in d/cone roll surr 8 ohm £2-50
 Coral 8 in d/cone roll surr 8 ohm £3-25
 EMI 13in x 8in 3. 8 or 15 ohm £2-25
 EMI 13in x 8in 150 d/c 3. 8 or 15 ohm £2-50
 EMI 13in x 8in 450 t/w 3. 8 or 15 ohm £3-75
 EMI 13in x 8in type 350 8 or 15 ohm £8-25
 EMI 13in x 8in 20W bass £6-60
 EMI 6 1/2 in 93850 4 or 8 ohm £3-00
 EMI 5in 98132CP 8 ohm £2-50
 EMI 8 x 5 d/cone roll surr 10W £2-50
 EMI 2 1/2 in tweeter 97492AT £0-65
 Eagle DT33 30W tweeter £5-45
 Eagle HT15 horn tweeter £3-80
 Eagle CTS cone tweeter £1-75
 Eagle CT10 tweeter 8 or 16 ohm £2-55
 Eagle MHT10 horn tweeter £3-80
 Eagle crossover CN23 CN28 CN216 £1-50
 Eagle FR4 £5-30
 Eagle FR5 £8-35
 Eagle FR8 £10-65
 Elac 9 x 5 59RM109 15 ohm, 59RM114 8 ohm £10-65
 Elac 6 1/2 in 6RM171 d/c roll surr £3-50
 Elac 6 1/2 in 6RM220 d/cone £2-65
 Elac 4 in tweeter TW4 £1-21
 Elac 10 in d/cone 10RM239 8 ohm £2-65
 Elac 8 in 8CS175 3 ohm £2-50
 Fane Pop 15W 12in £4-80
 Fane Pop 25 2 25W 12in £6-95
 Fane Pop 40W 10in £8-50
 Fane Pop 50W 12in £11-00
 Fane Pop 55 80W 12in £12-50
 Fane Pop 60W 15in £13-00
 Fane Pop 100W 18in £22-50
 Fane Crescendo 12A 100W 12in £29-00
 Fane Crescendo 12B bass £29-00
 Fane Crescendo 15in 100W £36-00
 Fane Crescendo 18in 150W £49-95
 Fane 801T 8in d/c roll surr £7-00
 Fane 807T 8in d/c roll surr £3-85
 Fane 808T 8in d/c £2-75
 Fane 701 twin ribbon horn £35-00
 Fane 910 horn £12-75
 Fane 920 horn £33-00
 Goodmans 8P 8 or 15 ohm £5-00

Goodmans 10P 8 or 15 ohm £5-30
 Goodmans 12P 8 or 15 ohm £12-95
 Goodmans 12P-D 8 or 15 ohm £16-75
 Goodmans 12P-G 8 or 15 ohm £15-75
 Goodmans Audiomax 12AX 100V £39-65
 Goodmans Audiomax 15AX £42-00
 Goodmans 15P 8 or 15 ohm £21-00
 Goodmans 18P 8 or 15 ohm £36-00
 Goodmans Midax 750 £16-00
 Goodmans Axent 100 tweeter £7-25
 Goodmans Audiom 100 12in £12-00
 Goodmans Axiom 401 12in £17-25
 Goodmans Twinaxiom 8 £8-25
 Goodmans Twinaxiom 10 £9-00
 Kef T27 £5-25
 Kef T15 £6-00
 Kef B110 £7-25
 Kef B200 £8-25
 Kef B139 £14-25
 Kef DN8 £2-00
 Kef DN12 £4-95
 Kef DN13 £3-30
 STC4001G super tweeter £6-15
 Richard Allan CG81 8in d/c r/surr. £6-35
 Wharfedale Super 10RS/DC £9-80
 2 1/2 in 84 ohm, 70mm 80 ohm, 70mm 8 ohm £0-65
 2 1/2 in 75 ohm £0-50
 7in x 4in 3 or 8 ohm £1-40
 8in x 5in 3 or 8 ohm £1-50
 10in x 6in 3. 8 or 15 ohm £2-30

SPEAKER KITS

Baker Major Module each £10-75
 Fane Mode One each £9-90
 Goodmans DIN 20 each £9-75
 Helme XLK25 pair £11-00
 Helme XLK30 pair £14-95
 Helme XLK50 pair £39-95
 Kefkit 2 each £24-75
 Kefkit 3 each £36-75
 Richard Allan Twinkit each £8-95
 Richard Allan Triple each £13-75
 Richard Allan Triple each £19-95
 Richard Allan Super Triple each £23-75
 Wharfedale Linton 2 kit pair £19-25
 Wharfedale Glendale 3 kit pair £34-50
 Wharfedale Dovedale 3 kit pair £52-50

PA/DISCO AMPLIFIERS

(carr and ins £1)
 Baker Major 100 watt £49-75
 Linear 30/40 £30-00
 Linear 40/60 £35-00
 Linear 80/100 £59-75
 Linear 100 watt slave £44-00
 Eagle PA range in stock—ask for catalogue.

FREE with speaker orders over £7

Hi-Fi Loudspeaker Enclosures: book
 All units guaranteed new and perfect. Prompt despatch. Carriage and packing speakers 3 p each, speaker kits 75p each (£1-50 pair), tweeters and crossovers 20p
 Send stamp for free booklet: 'Choosing a Speaker'
 ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.
 Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.



Agfa Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!			
C80	1 37p	5	11-80
C90	50p	5	12-48
C120	163p	5	13-10
5 10			
AGFA HIGH DYNAMIC SUPER			
C80 - 6	50p	5	12-40
C90 - 6	68p	5	13-35
C120	99p	5	14-90
5 10			
AGFA STEREO-CHROM CHROMIUM DIOXIDE			
C80	1 85p	5	14-20
C90	1 08	5	15-35
5 10			

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO
 (DEPT. PE)
 10 SWAN STREET, WILMSLOW,
 CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

BEGINNER'S GUIDE TO ELECTRONICS

by Squires Price £2.10

- ELECTRONIC SECURITY SYSTEMS by Leo G. Sands. Price £3.30.
- UNDERSTANDING SOLID STATE ELECTRONICS by Texas. Price £1.30.
- TELEVISION ENGINEERS' POCKET BOOK by P. J. Goldrick. Price £2.70.
- HANDBOOK OF IC CIRCUIT PROJECTS by J. Ashe. Price £1.60.
- TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price £2.
- TEST EQUIPMENT FOR THE RADIO AMATEUR by Gibson. Price £2.
- HOW TO USE INTEGRATED CIRCUIT by J. W. Streater. Price £1.60.
- MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal. Price £4.
- HIGH FIDELITY DESIGNS by Wireless World. Price £1.20.
- ELECTRONIC ORGAN SERVICING GUIDE by R. G. Middleton. Price £2.45.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books
 19-21 PRAED STREET LONDON W2 1NP
 Phone 01-723 4185
 Closed Saturday 1 p.m.

BUILD A PROFESSIONAL TELEVISION CAMERA

Complete kits available as designed by "Mullard" includes a comprehensive construction manual, lens tube and lens at £60.00 + VAT. Lens and tubes also available from stock. UHF Modulator Kits at £7.19 including P. & P. + VAT. Allows standard domestic TV to be used as monitor (Modulator also suitable for TV, Tennis and other similar games).


Send 5p stamp for illustrative brochure and price sheet.

CROFTON ELECTRONICS
 124 Colne Road, Twickenham Middlesex TW2 6QS
 Tel. 01-898 1569





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

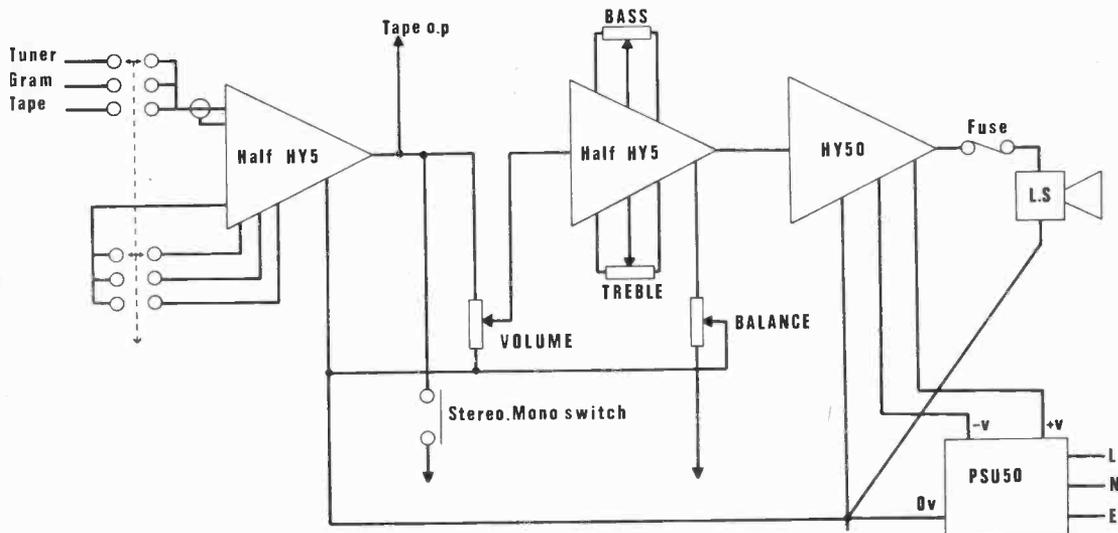

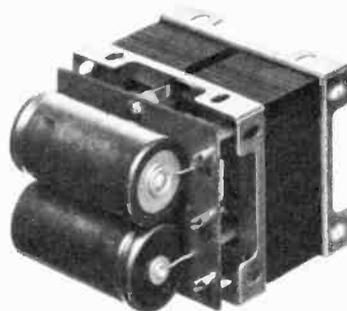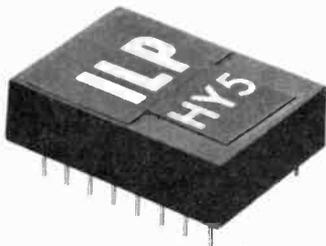MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA, Ceramic Pick-up 30mV, Microphone 10mV, Tuner 100mV, Auxiliary 3-100mV; Input Impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble = 12db at 10kHz; Bass = 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 58db. Overload Capability: 40db on most sensitive input. Supply Voltage: ±16-25V.

PRICE £4.50

+ 36p VAT
P. & P. free

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8kΩ. Load Impedance: 4-16kΩ. Input Sensitivity 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 × 50 × 25mm.

PRICE £5.98

+ 48p VAT
P. & P. free

The PSU50 can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: ± 25V. Input voltage: 210-240V. Size: L.70, D.90, H.60mm.

PRICE £5

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS


I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply
Total Purchase Price
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name and Address
Signature

12 VOLT FLUORESCENT LIGHTING



INVERTER TRANSFORMERS 13/15W (CIRCUIT INCLUDED) **70p**
 "CURRENT ECONOMY" TRANSISTOR (600 ma.) **50p**
 "MAXIMUM LIGHT" TRANSISTOR (1.3A) **50p**
 RESISTORS/CAPACITORS TO SUIT **15p**
 LAMP HOLDERS (LONG LEAD) **30p PAIR**
 (SHORT LEAD) **20p PAIR**
 WHITE ENAMEL CASE, 18in or 21in (POSTAGE 30p) **70p**
 TUBE, 18in-15W or 21in-13W **45p**
 (NOTE: TUBE ONLY SUPPLIED IF CASE ORDERED, TO PREVENT POSTAL DAMAGE)
 13W FITTING READY BUILT AND TESTED—INCLUDING TUBE (POSTAGE 30p) **£3.75**
 POST/PACKING, 25p PER ORDER EXCEPT WHERE SHOWN

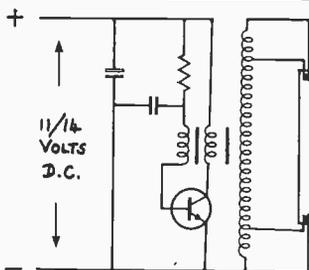

NEW IMPROVED CIRCUIT!
 Drives 21in 13W
 18in 15W
 or adaptable for
 2 x 12in 8W

SMALL ELECTROLYTICS

Ref No.	Capa- city	Volt- age	Price
H8/3	3µF	50V	4p
H8/3A	4µF	50V	4p
H8/5	5µF	10V	4p
H8/6A	10µF	10V	4p
H8/8A	16µF	16V	4p
H8/9A	20µF	70V	4p
H8/10	22µF	50V	4p
H8/11	25µF	12V	4p
H8/12A	30µF	10V	4p
H8/13A	32µF	50V	4p
H8/14	40µF	25V	5p
H8/14A	40µF	16V	4p
H8/15A	40µF	35V	4p
H7/1A	50µF	10V	4p
H7/2A	64µF	2.5V	2p
H7/4	64µF	15V	4p
H7/9A	125µF	4V	4p
H7/10A	160µF	2.5V	3p
H7/11	160µF	25V	6p
H7/11A	150µF	16V	5p
H7/14	220µF	50V	10p
H7/14A	220µF	16V	6p
H7/15	220µF	25V	5p
H7/15A	220µF	35V	10p
H6/1A	250µF	4V	3p
H6/3A	320µF	2.5V	3p
H6/4	320µF	10V	4p
H6/5	330µF	25V	10p
H6/5A	330µF	35V	15p
H6/8A	470µF	35V	20p

Postage 25p per order

£1 100 1/4 WATT RESISTORS
 100 CERAMIC CAPACITORS
 100 DIODES
 POSTAGE 25p PACK No. 1

£1 1 VEROBORD CUTTER
 5 2 1/2 in x 1 in x 0.15 BOARDS
 50 sq. ins. ODD PIECES
 VERO
 POSTAGE 25p PACK No. 3

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.
 POSTAGE 25p PACK No. 5

£1 6 COMPUTER PANELS CONTAINING MASSES OF INDUCTORS, RESISTORS & CAPACITORS
 POSTAGE 30p PACK No. 7

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 100 POLYSTYRENE CAPACITORS
 POSTAGE 25p PACK No. 2

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 50 MULLARD POLYESTER CAPACITORS
 POSTAGE 25p PACK No. 4

£1 1 TRANSISTORISED SIGNAL TRACER KIT
 1 TRANSISTORISED SIGNAL INJECTOR KIT
 POSTAGE 25p PACK No. 6

£1 100 RESISTORS
 100 CAPACITORS (ASSORTED TYPES)
 POSTAGE 25p PACK No. 8

NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

ADCOLA SOLDERING KITS

INCLUDES THE FAMOUS 'INVADER' SOLDERING INSTRUMENT

£5.11
 INCLUDES VAT
 POSTAGE
 FREE!



A quality soldering kit at a price which may never be repeated due to rising costs. The kit comprises of the renowned Invader Soldering Tool (high safety standards low leakage with easily removable bits). Two spare specially shaped bits (heavy duty and P.C.B. work). Safety stand with bit storage provision, dispenser of multi cored solder, and hints and tips soldering leaflet, all in a presentation styrene pack. Attach your plug and solder with Adcola.



POST NOW TO!

ADCOLA PRODUCTS LTD ADCOLA HOUSE GAUDEN ROAD LONDON, SW4 6LH
 V.A.T. REGD. No. 235 6153 72 REGD. No. 442762

ENCLOSING P/O, CHEQUE FOR SOLDERING KITS/ £
 NAME

ADDRESS

PE

ALL OUR PRICES INCLUDE V.A.T.

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5in HI-FI SPEAKER TYPE 59RN

This famous unit now available, 10 watts, 8 ohm.

Price **£2.95** Post 25p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less PLEASE STATE VOLTAGE REQUIRED

£2.20 Post 25p

RCS POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions.

£2.95 Post 25p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or 1.5V. Line 200-300 Ω operation. Size: 1 1/2 x 1 1/2 x 1/2 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Details S.A.E. **99p** Post 20p

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronomes, strobe, etc. **95p** Post 20p

BRITISH FM/VHF TUNING HEART

88 to 108 M/C/S British made. 2 Transistors ready aligned requires 10-7 M/C/S I.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price £3.95 Post 20p

10-7 M/C/S I.F. strip **£4.95** DECODER **£4.95**

MAINS TRANSFORMERS

	ALL POST 25p each
250-0-250V 70mA, 6.3V 2A	£2.00
250-0-250 80 mA, 6.3V 3.5A 6.3V 1A or 5V 2A	£2.50
350-0-350 80 mA, 6.3V 3.5A, 6.3V 1A or 5V 2A	£3.00
300-0-300V 120 mA, 6.3V 4A C.T., 6.3V 2A	£4.25
MINIATURE 200V 20 mA, 6.3V 1A 2 1/2 - 2in	95p
MIDGET 220V 45 mA, 6.3V 2A 2 1/2 - 2in	£1.10
HEATER TRANS. 6.3V 1/2 amp 85p, 3 amp	£1.20
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £3.00	
1 amp, 6, 8, 10, 12, 16, 20, 24, 30, 36, 40, 48, 60 £3.00	
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.00	
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00	
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.75	
3, 5, 8, 10, 13 or 5-0-5V 5 amp. £1.50, 6-0-6V 500mA 90p, 9V 1 amp. 95p, 12V 300mA 75p, 12V 500 mA 85p, 12V 750 mA 95p, 12V, 36V, 48V, 2 amp. £2.20, 20V 3 amp. £2.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £3.00; 500W £6.25; 750W £10; 1000W £15	
CHARGER TRANSFORMERS. Input 200/250V, for 6 or 12V, 1 1/2 amp £1.50; 2 amp £1.80; 4 amp £2.50. BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4.50.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR PRICE £12** Carr. Famous make. (Value £19).

NEW ELECTROLYTIC CONDENSERS

2/350V	14p	250/25V	14p	50 - 50/300V	50p
4/350V	14p	500/25V	20p	900/350V	95p
8/350V	22p	1000/25V	35p	32 - 32/250V	20p
16/350V	25p	1000/50V	47p	32 - 32/450V	60p
32/500V	50p	8 - 8/450V	22p	350 - 50/325V	85p
25/25V	9p	100 - 50/50	25p	100 - 50/350V	85p
50/50V	10p	16 - 16/450V	40p	32 - 32/350V	65p
100/25V	10p	32 - 32/350V	40p	4700/63V	95p

LOW VOLTAGE ELECTROLYTICS.

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 15p; 25V 20p; 50V 30p; 100V 70p. 2000mF 6V 25p; 25V 42p; 50V 57p. 2500mF 50V 62p; 3000mF 25V 47p; 50V 85p. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p. CERAMIC, 1pF, 10pF, 100pF, 1000pF, 10000pF, 4p. PAPER 350V-0-1.4p, 0-5.15p; 1mF 150V 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0-1.5p; 0-2.5p; 0-4.7 25p. MICRO SWITCH LEVER ACTION 20p.

SUB-MIN MICRO SWITCH 25p. Single pole change over. TWIN GANG: "0-0" 200pF - 170pF £1.20; 500pF standard 75p 385pF - 385pF with 25pF - 25pF. Slow motion drive 50p. 1000mF 12V 15p; 25V 42p; 50V 57p. 50pF, 55p. NEON PANEL INDICATORS 250V AC/DC. Amber 30p. RESISTORS: W, 1W, 1W, 20% 1p; 2W, 5p, 10 Ω to 10M. HIGH STABILITY. 1W 2% 10 ohms to 6 meg., 10p. Ditto 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each. TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER": 12IN 50 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. **£12.95**

BAKER MAJOR 12" £8.50

30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10.95** Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS

'Group 27' 12in. 25W 3 or 8 or 15 ohm **£7.75**
'Group 35' 12in. 35W 3 or 8 or 15 ohm **£8.50**
'Group 50/12' 12in. 50W 8 or 15 ohm **£12.95**

TEAK VENEERED HI-FI SPEAKER AND CABINETS For 12in or 10in dia. speaker 20 x 13 x 9in. £10.50. Post 75p For 12 x 8in or 8in speaker 16 x 10 x 9in. £6.60. Post 45p For 8 x 5in speaker 16 x 8 x 6in. £5.00. Post 25p For 6in and Tweeter 12 x 8 x 6in. £4.00. Post 25p LOUDSPEAKER CABINET WADDING 16in wide. 20p ft

GOODMANS 6 1/2in. HI-FI WOOFER

4 ohm or 8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Twin cone. Frequency response, 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12x8x6 £4. Suitable Tweeter £2 **£4**

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 2in deep. Rating 10W, 3 ohm. **£1.90** Post 20p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £2.25. De Luxe Horn Tweeters 2-16kc/s, 15W, 15 ohm £4. CROSSOVERS, TWO-WAY 3,000 c/s 3 or 8 or 15 ohm £1.25. LOUDSPEAKERS P.M. 3 OHMS. 7x4in. £1.25; 6in. £1.50; 8x5in. £1.60; 10in. £2.00; 8in. £1.75; 10x6in. £1.90. SPECIAL OFFER: 8in. £1.90; 6in. £1.50; 2in. 3in. 3in., 25 ohm, 2in. dia., 3in. dia., 5in. dia., 1in. dia., 1/2 in. dia., 15 ohm, 3 1/2 in. dia., 6x4in., 7x4in., 8x5in., £1 each 3 ohm, 2 1/2 in., 2 1/2 in., 5in. dia., 6x4in 8 ohms £1.50. RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4W £2.50. 10in. diameter 5W £2.50; 12in. diameter 6W £2.95. 3 or 15 ohms. Bass state. VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50.1 40p. Mike trans. mu metal 100:1 £1.25.

Loudspeaker Volume Control 15 ohms 10W with one inch threaded bush for wood panel mounting. 1in spindle. 65p each. Post 15p.

MAJOR 100 WATT

ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music, 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. **£49** Carr. NEW MODEL MAJOR—50 watt, 4 input, 2 vol. controls, treble and bass £39.95.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. With mix Microphone, records, tape and tuner with separate controls into single output. 9V. **£4.50**

TWO CHANNEL STEREO VERSION

£5.95

BARGAIN 3 WATT AMPLIFIER, 4 Transistor

Push-Pull Ready built, with volume, Treble and bass controls. 18 volt d.c. **£4.50**

COAXIAL PLUG 10p; PANEL SOCKETS 10p; LINE 18p. OUTLET BOX, SURFACE 25p; FLUSH 60p; TWIN 85p. BALANCED TWIN RIBBON FEEDER 30 ohms 7p. JACK SOCKET STD. open-circuit 14, closed circuit 20p; Chrome Lead-Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS STD. Chrome 20p; 3.5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p, 5-pin 10p. DIN SOCKETS lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, SP; CERAMICS 10p; CANS 5p.

REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt, spindle 1 1/2" x 7/8", 2" dia. **£2.20** Illustrated. With Cooling Fan, a.c. 240V. Post 25p

EMI TAPE MOTOR

E.M.I. TAPE MOTORS. 120V or 240V a.c. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. Size 3x2 1/2x2 1/2in (illustrated). Post 25p. **£1.85**

BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V Size 13 1/2 x 11 1/2 in.



Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO CARTRIDGE **£6.95** Post 45p.

PORTABLE PLAYER CABINET

Modern design. Rexine covered. Vynal front grille. Chrome fittings. Size: 17 x 15 x 8 1/2 in approx. Motor board cut for BSR deck **£4.50** Post 45p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 8 1/2 in., 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains.



Attractive Teak finish Weight 13 lb. **£25** 85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-60 MINUTES **£1.95** Post 25p Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and full guaranteed.



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board. Size 18 x 10 1/2 in—75p. 10 1/2 x 7 1/2 in—45p

WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial 85p Driver Trans. LFDT4. 65p I.F. P50/2CC 470 kc/s 40p Printed Circuit, PCA1 85p 3rd I.F. P50/3CC 40p J.F. Tuning Gang. £1.20 Spare Cores 3p Weyrad Booklet 10p P50/1A 60p OPT 85p Mullard Ferrite Rod 8 x 1/2 in, 20p. 6 x 1/2 in, 20p. 3 x 1/2 in, 10p.

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. EDGE 5K. S.P. Transistor 25p

80 Ohm Coax 5p yd.

BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £2; 60 yd. £3 FRINGE LOW LOSS Ideal 625 and colour 10p yd

8in. or 10 x 6in. ELAC

HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 c/s. Bass resonance 55 c/s, 8 ohm impedance, 10 watts, music power. **£3.75** Post 25p



E.M.I. 13 1/2 x 8in.

SPEAKER SALE!

With twin tweeters. And crossover, 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p **£4.50**

With flared tweeter cone and ceramic magnet, 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p **£2.75**



Bookshelf Cabinet Teak finish 16 x 10 x 9in.

13in x 8in. Bass Woofer, 20 watts **£6.60** Post 45p

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK

£1.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides 6 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 9 in 95p; 16 x 8 in 50p; 12 x 3 in 50p; 16 x 10 in 70p. ALUMINIUM BOXES, 3 x 3 x 3 in 60p; 4 x 4 x 4 in 70p; 6 x 4 x 4 in 80p; 9 x 4 x 4 in £1; 12 x 4 x 4 in £1.30. ALUMINIUM PANELS 18 s.w.g. 8 x 4 in 12p; 8 x 6 in 19p; 14 x 3 1/2 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p; 16 x 8 in 34p; 14 x 8 in 40p; 12 x 12 in 47p; 16 x 10 in 60p. S.R.P.B. PAKOLIN PANEL 10 x 8 in 30p.


RADIO COMPONENT SPECIALISTS

Radio Books and Component Lists 10p. (Minimum posting charge 20p.)

337 WHITEHORSE ROAD, CROYDON

Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)

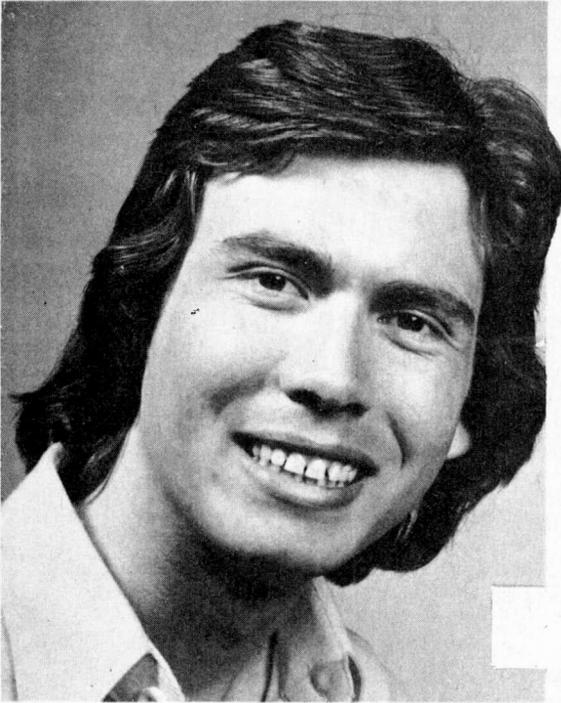Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665



*I've often wondered -
How CAN you compare
one catalogue with
another?*

After all, few firms can give you more than a brief description. Take the *Home Radio Components Catalogue* for instance. They could have said that the cover is in full colour and shows Barbara Hepworth's beautiful "Theme on Electronics". Or that it consists of no less than 240 pages of quality art paper, has over 1,700 illustrations, and lists about 6,800 different items.

What really counts, however, is *the organisation behind the catalogue*, and in this connection I give full marks to Home Radio Components, because from my experience they really care about helping their customers. But don't merely take my word for it—find out for yourself. The best way to do that is to get a copy of their catalogue right away. Just send them a cheque or postal order for 98p (65p for the catalogue and 33p for postage, packing and insurance). By the way, they include 14 coupons in the catalogue, each worth 5p if used as directed, so you can get not only the cost of the catalogue back, but 5p towards the postage as well. If that's not philanthropy I don't know what is! It's just one of the ways Home Radio Components think of their customers. *Send for your catalogue today—you'll never regret it.*



65p plus 33p POST AND PACKING

Send off the coupon today. It's your first step to solving your component buying problems.

The price of 98p applies only to customers in the U.K. and to B.F.P.O. addresses

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....



HOME RADIO (Components) LTD., Dept. PE,
234-240 London Road, Mitcham, Surrey, CR4 3HD

Regd. No
912966 London

SELF SERVICE

IT is a healthy sign that the throw-away philosophy which has pervaded so many aspects of life is now being questioned, mainly because of the disregard for conservation of natural resources it encourages. The uncontrolled and thoughtless exploitation of irreplaceable materials has finally become a major concern, throughout the world.

In this connection, the role of electronics cannot escape some censure. The vast growth of electronic products has been paralleled by a fall-off in servicing facilities generally available. Clearly many of the cheaper consumer products are not intended to receive any drastic servicing treatment in the course of their normal life. When they prove troublesome their destination, all too commonly, is the dustbin. On a commercial basis this makes sense, it must be admitted, for the cost of a skilled repairman's time would very quickly exceed the market value of the article. It is only the non-profit orientated private enthusiast who is likely to undertake such uneconomical work.

With larger and more expensive equipment, e.g. colour television sets, servicing still remains an indispensable feature during the normal working life of the product. Modular construction aids rapid on-the-spot servicing, although an element of the throw-away philosophy undoubtedly persists at the individual module level.

It has always been claimed that the increased use of i.c.'s will enhance the reliability factor and so reduce the number of failures in electronic equipment. This should help ease the demand upon the overtaxed service technicians. Yet, as in other branches of engineering, the supply of competent service technicians is likely to continue to lag far behind the demand.

One consequence of this shortage of skilled professionals and the accompanying rise in labour charges is the growth of do-it-yourself enterprise, in many different fields. The private motorist offers perhaps the most obvious example of the greatly increasing application of "self service". Car maintenance depends upon specialist knowledge and working experience. It is also a field where electronic instruments can play quite an important part—not least for the amateur. In many instances the electronics constructor can apply his interest in this subject to help out if or when he is compelled to undertake his own car maintenance. The Dwell Meter described in this issue is another valuable instrument that seems destined to repay its cost over and over again in the austere times which we have been warned lay immediately ahead.

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*

Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD

Phone: *Editorial* 01-634 4452

Advertisements 01-634 4202

DWELL METER



BY S. JONES

THIS dwell meter was designed to facilitate automobile contact breaker adjustments without the use of feeler gauges. In this way worn contact breaker points can be adjusted, a task not otherwise possible.

Distributor mechanical wear and vacuum advance operation can also be checked. The prototype was checked against the most expensive commercial dwell meters available and no variation between them could be detected.

WHAT IS DWELL ANGLE?

During the time when the points are closed, called the dwell time, the primary current through the coil builds up producing a magnetic field around the coil. If this magnetic field does not reach sufficient strength, due to too short a dwell time, its collapse when the points open may not produce sufficient voltage to cause a spark at the plug.

Dwell time is therefore very important. However, measuring it is difficult as obviously it decreases with increasing engine speed. Thus the angle for which the points remain closed is used and this remains constant through the speed range provided that the points are not moved.

This measurement can be made by examining the potential across the points during their operation.

DESIGN PROBLEMS

Although most ignition systems work on a 6V or 12V supply, an alternating voltage with a peak of up to 300V is produced across the points when they open (see Fig. 1). If this 300V were applied to a transistorised circuit without some modification it is unlikely that the transistors would survive the voltage peaks and for this reason the voltage across the contacts is first rectified and stabilised to produce a voltage suitable for transistor switching as in Fig. 1, lower curve.

CIRCUIT

A full wave rectifier formed by diodes D1 to 4 (Fig. 2) is fed with the signal from the points under test; this rectifies the oscillations shown in the upper part of Fig. 1 to give the lower waveform. R1 limits the current flow to Zener D5 which stabilises the output from the rectifier at 4.7V.

The voltage developed across R3 when the contacts are open makes the base of TR1 positive, turning it on. This in turn switches off TR2 and no current flows through the meter ME1.

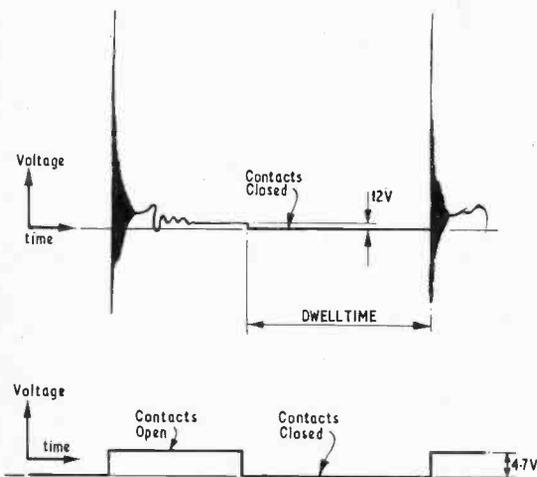


Fig. 1. The waveform at the contact breaker points shown here in the upper graph. The voltage level during the closed-points period is only 12V just to give an idea of scale. The lower graph shows the output from the bridge rectifier used in the following circuit diagram

COMPONENTS . . .

Resistors

- R1 1k Ω
- R2 1k Ω
- R3 1k Ω
- R4 3.3k Ω
- All 10% $\frac{1}{4}$ W carbon

Potentiometer

- VR1 4.7k Ω Lin

Diodes

- D1 1N4001
- D2 1N4001
- D3 1N4001
- D4 1N4001
- D5 4.7V, 1W Zener

Transistors

- TR1 2N2926 (Orange)
- TR2 2N2926 (Orange)

Miscellaneous

- ME1 1mA or see text
- S1 SPST on/off
- B1 1.5V battery (Alkaline cell size AA preferable)
- Veroboard, 0.1in matrix, 29 \times 24 hole rows. Case, 4 \times 6 \times 1.5in.
- Wire, solder, nuts, screws etc.

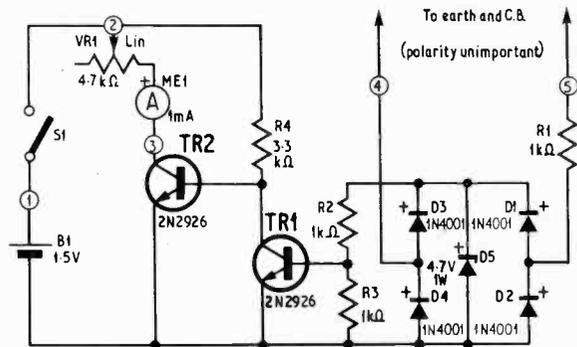


Fig. 2. The circuit diagram of the dwell meter showing the simplicity of the arrangement

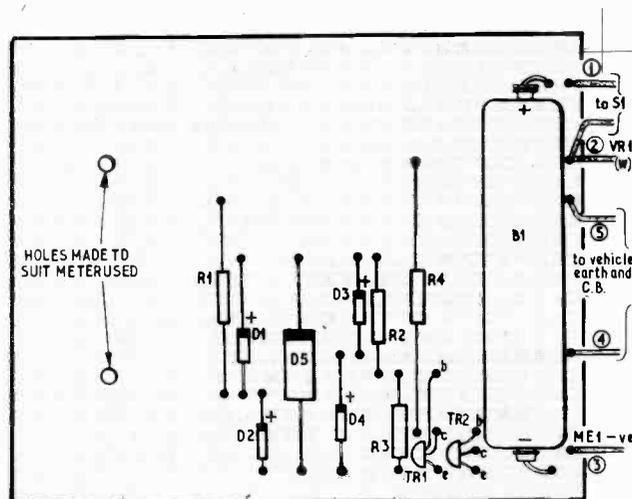


Fig. 3. Component layout and Veroboard cut details for the dwell meter



The Dwell Meter together with the starter switch push unit. Of course, they are not connected electrically, one going to the starter solenoid whilst the other goes to the points

When the contacts close the input to the rectifier is short-circuited by the contacts and the voltage across R3 falls, causing TR1 to be turned off and TR2 on. Current now flows through the meter via VR1.

The "earth" of the vehicle is unimportant as the input to the dwell meter is via a full wave rectifier and for the same reason it is unimportant which way round the input wires are connected across the contacts.

The ratio of on to off periods of TR2 determines the average current through ME1 and this is used to assess the actual dwell angle.

The use of the vehicle battery as a power source, even if stabilised, has been found unsatisfactory and so a 1.5V alkaline cell is recommended. This has a shelf life of 2 years and is totally leak-proof. A standard pen cell could be used, but leakage could be a problem.

The meter ME1 can be almost any value, both 1mA and 100 μ A have been used and VR1 set accordingly.

CONSTRUCTION


All components are mounted on 0.1in matrix Veroboard 3in \times 2.5in which can, if desired, be mounted direct onto the meter terminals. A board layout is shown in Fig. 3. Holes may be drilled anywhere in the last inch of the board as this has been isolated from the rest of the circuit.

The board can be mounted with the copper side outwards if a shallow case is to be used, but the case itself, if metal, must not be connected to the circuitry as the case will no doubt come into contact with the vehicle chassis during normal use.

The battery is soldered direct to the Veroboard though if preferred small clips could be used, or the battery mounted separately.

CALIBRATION

With a normal 0 to 10 scaled meter, all that is required is to change the figures to 0 $^\circ$ to 100 $^\circ$. Then zero the meter needle on to 90 $^\circ$ for a 4-cylinder engine using VR1. The meter is then ready for use reading dwell angle from 0 to 90 $^\circ$ with a linear scale. For 6-cylinder engines set the needle to 60 $^\circ$, 8-cylinder to 45 $^\circ$, 12-cylinder to 30 $^\circ$, i.e. 360 divided by the number of cylinders. These zero marks can be put onto the scale for future reference as can be seen in the photographs.

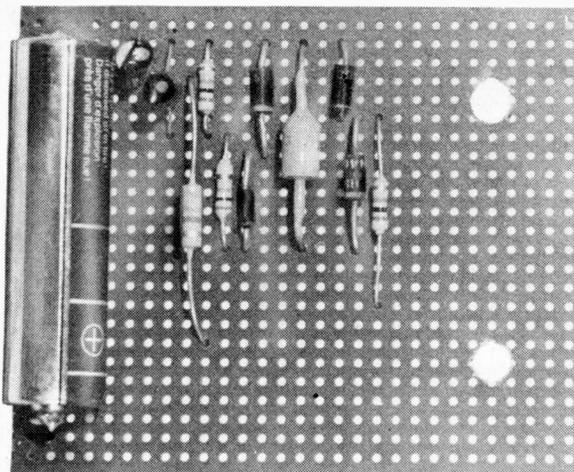

Component layout on the Veroboard used in the prototype. Note the use of the alkaline cell power source

USING THE DWELL METER

Switch on and zero the dwell meter as explained above to suit the engine being examined. Connect one of the input cables to a good earth and the other to the terminal on the coil which is connected to the distributor contacts; this may be marked CB, positive or negative, depending on the age and "earth" of the vehicle.

Remove the distributor cap and rotor arm and loosen the contact breaker fixing screws so that with a screwdriver in the adjusting slot the points can be adjusted but are not loose. Switch on the ignition and while the starter motor turns over the engine, move the contact breakers with the screwdriver in the adjusting slot until the dwell is correct for your vehicle.

Tighten the screws, replace the rotor arm and distributor cap. The points are now adjusted. It is now advisable to time the engine using the timing lamp in the January issue. Always dwell then time, not the other way about.

Whilst this is a normal procedure in commercial workshops, some owners might prefer to remove the spark-plugs before turning the engine over so as to reduce the load on the starter.

DWELL ANGLES

If the dwell angle only requires checking then connect the dwell meter as described above, but run the engine at idle speed and read the dwell angle in the normal way.


The dwell angles for 4-cylinder engines are as follows:

Autolite distributor	40°	Vauxhall/Bedford
Lucas distributor	60°	B.L.M.C.
A.C. Delco distributor	37°	Ford


With the Autolite and Delco 4-cylinder distributors the dwell angle will increase when the vacuum advance mechanism operates. This is normal.

The great variety of distributors fitted to 6, 8 and 12-cylinder engines makes listing dwell angles difficult, but most libraries now carry a good selection of manuals as do book shops and they will be only too glad to let you peruse the relevant pages.

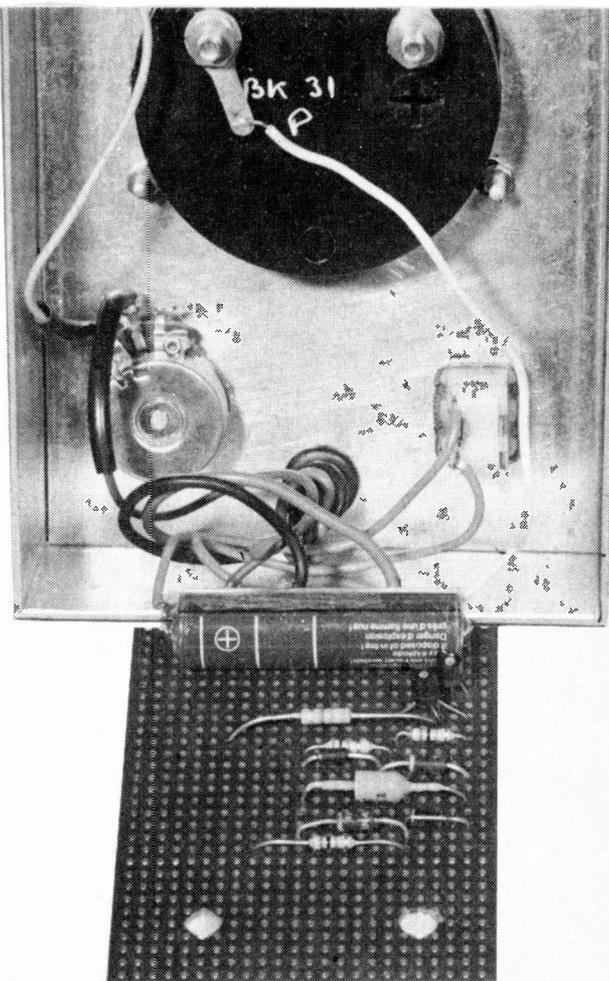To check distributor wear, disconnect the vacuum unit and note the dwell angle at idle speed. Increase speed to 3,000 r.p.m., noting the dwell angle again. A variation of more than 3° indicates distributor bearing wear which may, depending on the exact nature of the wear, affect the running of the engine.



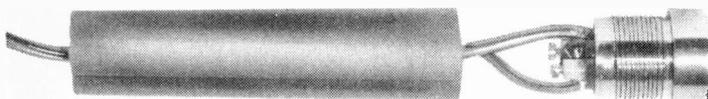View inside the prototype Dwell Meter showing the simple interwiring between the meter, board and external vehicle circuit



The manual starter switch is simply a push-switch which is itself a push fit in a length of plastic tube to make a comfortable handle. The cable can be locked in position using wax or sealing compound

REMOTE STARTER

Some readers may have considerable difficulty in operating the starter, as in the case where it is actuated by the ignition switch, and at the same time moving the contacts. Where the starter solenoid is not operable mechanically, a remote starter overcomes the problem.

Obtain a length of stout cable, to one end fit a crocodile clip and to the other a ¼in Lucar connector. At the centre break the cable and fit a push-to-make switch rated at least 5A. In the version shown here a Bulgin switch was pushed into a length of plastic tube for convenience.

Locate the starter motor solenoid, which may be mounted on top of the starter motor or elsewhere in the engine compartment, and look for a single wire

feeding to an isolated Lucar spade. Remove the distributor cap and then have someone turn the engine over briefly with the ignition key and disconnect this cable, the starter motor should stop if the correct cable has been selected.


If you are confronted by two small Lucar spades, one on either side of the solenoid, remove each in turn until the starter motor stops. The other forms part of the ignition system and should be left in place.

Now attach the crocodile clip to the unearthed battery terminal and the Lucar connector to the solenoid operating terminal previously located. Push the button and the starter will operate. On no account remove or make a connection to the two bolt connections of the solenoid or any wire attached to them.

Turning the engine over with the starter for what may seem quite lengthy periods to some readers is normal in the garage trade when setting tappets for instance. No damage will be caused unless the time taken for adjustment is excessive, but for those who wish, the load may be considerably lightened by removing the spark plugs.



PART FOUR

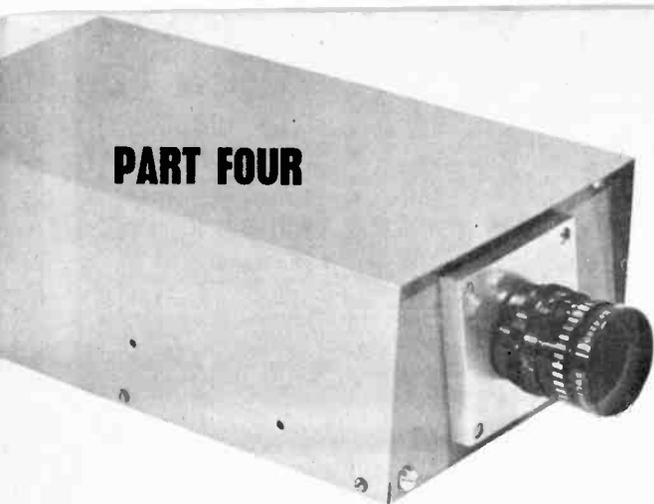

PE CCTV MONOCHROME CAMERA

By G. D. BISHOP

U.H.F. MODULATORS: A CHOICE OF TWO

A CCTV system normally consists of a camera or group of cameras connected via a fade or switch unit to a CCTV monitor. The monitor is merely a cathode ray tube which is driven by a video amplifier and the normal scan coils and timebase circuits as would be found in a domestic television receiver. A domestic TV set can, therefore, be used as a monitor in one of two ways; the CCTV camera signal can be fed to the video amplifier input direct necessitating internal modifications to the TV set, or the camera signal can be modulated onto the normal u.h.f. carrier frequencies and applied to the usual aerial socket.

No modifications to the receiver are needed if the latter method is adopted and this article describes the construction of such a modulator using a standard domestic receiver u.h.f. tuner as the modulating circuit. The CCTV signal could be applied direct to the modulator but to avoid any distortion of the signal a small video amplifier is included, together with a low voltage power supply.

For those constructors who would prefer to build from a simple kit with instructions, an excellent modulator is available from Crofton Electronics for £7.30. Details are given in Fig. 4.5.


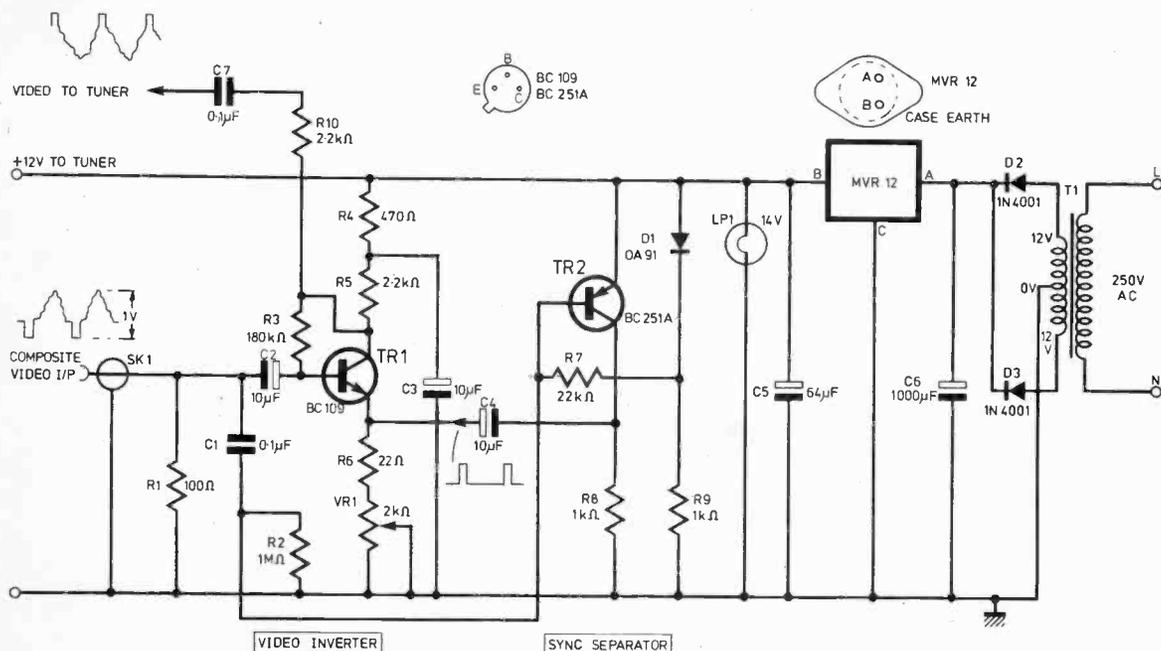


Fig. 4.1. Circuit diagram of sync separator and video inverter

Fig. 4.2. Showing modifications and connections to typical u.h.f. tuner. All straight line inductances are lecher bars

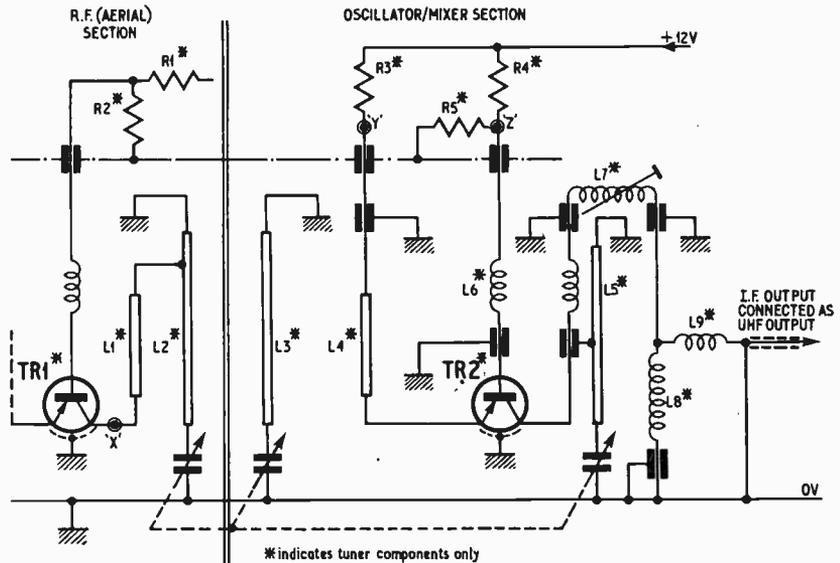

BASIC PRINCIPLES

Part of the modulator (the modified oscillator section of a u.h.f. tuner) comprises a grounded base *pnp* or *npn* transistor connected as a regenerative ultra-high-frequency oscillator and mixer circuit. In this design the aerial signal which would normally be fed to this transistor to mix with the oscillator sine-wave is disconnected and replaced by the CCTV signal. The signal is applied to the transistor emitter (grounded base input) and in order to generate negative modulation, identical with normal u.h.f. transmissions an inverted signal must be provided. Camera signal outputs are usually positive video signals and so a single transistor inverter precedes the tuner input.

THE CIRCUIT

Fig. 4.1 shows the video inverter and sync separator with a conventional power supply centred around a 12 volt regulator unit MVR-12, providing +12V to the tuner, TR1, TR2 and an indicator lamp. The input CCTV signal is correctly matched at 75 ohms by R1 and the transistor input impedance and is amplified with approximately unity gain in TR1. The video gain can be adjusted with VR1, a front-panel control, which with R6 provides negative feedback to increase the bandwidth. R4 and C3 decouple TR1 and the output signal is taken via R10 and C7 to the tuner.

The input signal is also taken via C1 to TR2, connected as a sync separator which is switched on only by the negative sync pulses at its base, this being a *pnp* transistor in common emitter connection. D1 provides constant bias to the base and the amplified inverted sync pulses are fed through C4 to TR1 emitter where they add to the video signal at the collector. Any *pnp* transistor which is silicon planar will suffice.

TUNER MODIFICATIONS

Before any u.h.f. tuner modifications are undertaken a few words on general tuner construction might enable prospective constructors to approach this task with more confidence.

The tuner, like many other radio/TV tuners comprises an r.f. section where the aerial signal is selected and amplified, and an oscillator/mixer stage where a generated sinewave is mixed with the r.f. to produce a constant carrier frequency i.f. of 39.5MHz in the case of 625-line TV.

Tuning is carried out with very small inductances called lecher bars which are strips of metal as seen in Fig. 4.3. Each lecher bar is tuned with one section of the tuning gang capacitance in parallel with a small trimmer capacitor. The tuner casing is split into four or five mechanical sections, each of which is a resonant cavity and which is critically tuned to the required frequency. The placing of every component is critical and no component other than those indicated must be touched.

The r.f. section is disconnected by cutting TR1 collector at point X in Fig 4.2. The next step is to


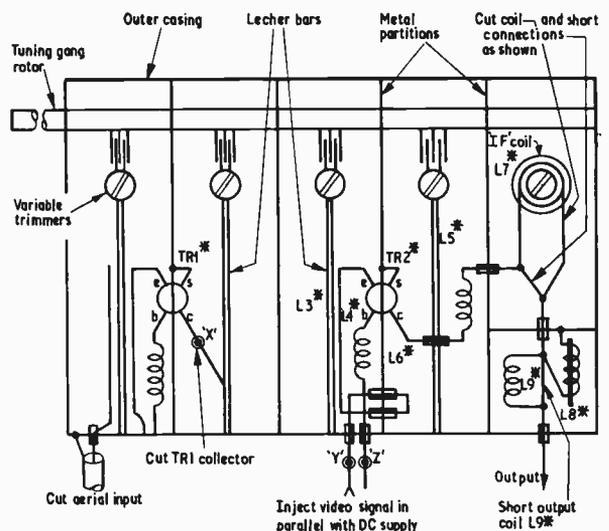


Fig. 4.3. Physical details of modifications and connections to typical tuners

disconnect the output tuned circuits which, if still tuned to 39.5MHz, would attenuate the u.h.f. signal on 450 to 850MHz approximately. The i.f. coil L7 is cut and its place taken by a shorting link. Similarly the output coil L9 is shorted out. No other modifications are necessary inside the tuner casing.

The shorting links are of tinned 20s.w.g. or 22s.w.g. copper wire and are as short as possible and not grounding to chassis.

The aerial input coaxial lead is cut or desoldered and a coaxial lead is soldered on the output connection where the i.f. lead was situated, making the braiding as short as possible. Position Y is then located on the circuit diagram and on the component layout as in Fig. 4.2 and 4.3, this being the point which is to be connected to the video amplifier of Fig. 4.3. There will be d.c. voltage on this point of about 6 volts from R3*. If difficulty is experienced in

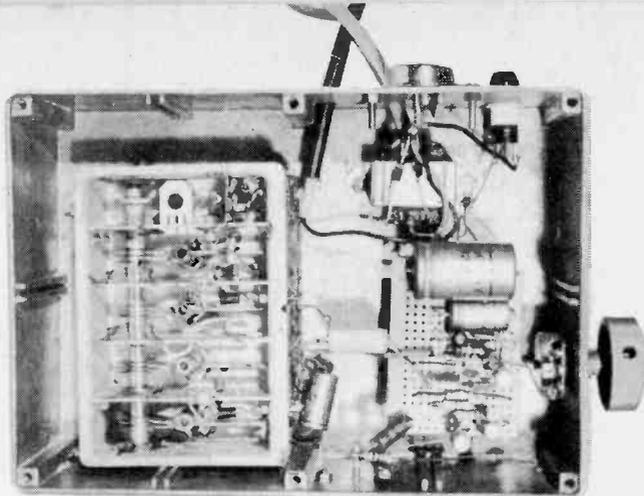

COMPONENTS . . .

Resistors

R1	100 Ω
R2	1M Ω
R3	180k Ω
R4	470 Ω
R5	2.2k Ω
R6	22 Ω
R7	22k Ω
R8, R9	1k Ω
R10	2.2k Ω
All $\frac{1}{4}$ watt 10% carbon	

Capacitors

C1	0.1 μ F polyester
C2-C4	10 μ F elect. 10V (3 off)
C5	64 μ F elect. 25V
C6	1,000 μ F elect. 25V

Potentiometer

VR1	2k Ω lin.
-----	------------------

Transistors

TR1	BC109
TR2	BC251A or BC477

Diodes

D1	OA91
D2, D3	IN4001

Transformer

T1	Mains transformer 240V
	pri. 12-0-12V, 50mA
	sec.

Miscellaneous

Transistor u.h.f. tuner assembly (type immaterial) SK1—75 Ω coaxial chassis mounting socket LP1—14V miniature indicator lamp, Veroboard 0.1in matrix, 4cm x 5cm, metal case 12cm x 17cm x 4cm.

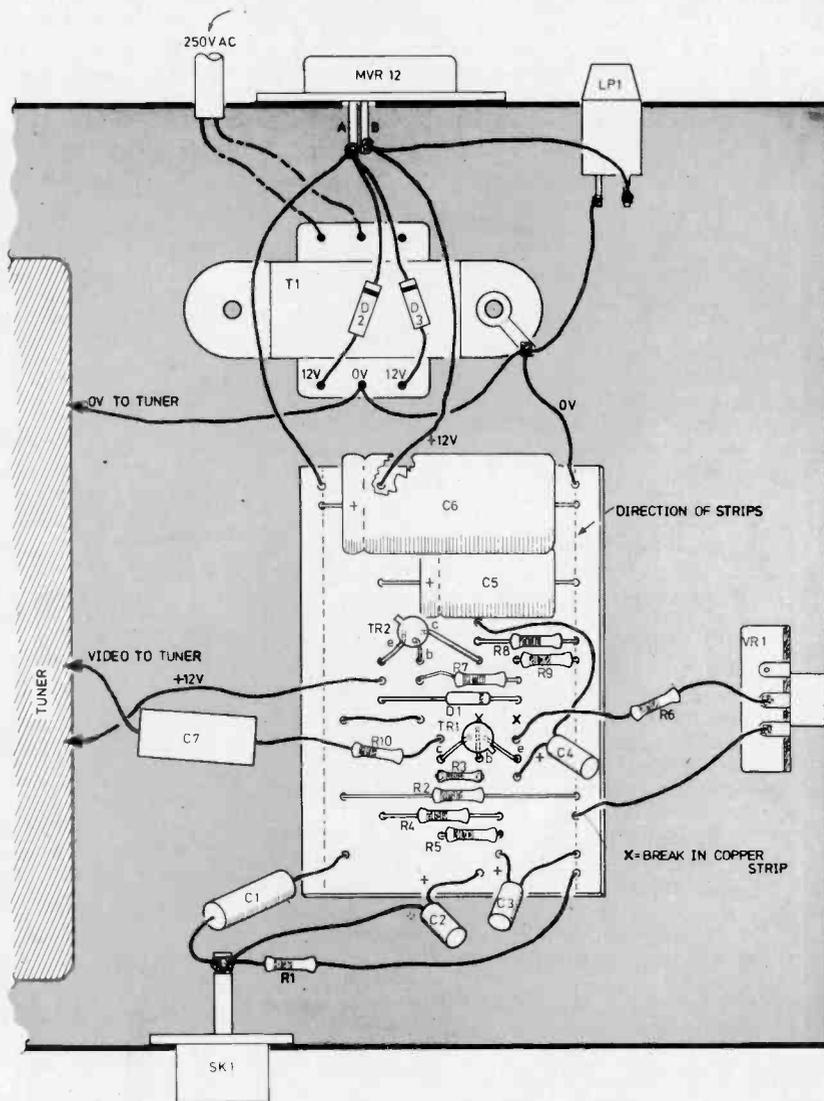


Fig. 4.4. Component layout of sync separator, video inverter and power supply. Tuner unit is adjacent

obtaining good results from point Y, point Z can be substituted this time there being phase inversion in TR2*. (components with an asterisk merely refer to those components in a typical tuner). The cause of the trouble possibly being the fact that the tuner chosen has a negative supply voltage or the CCTV input is inverted.

SCREENING ESSENTIAL

The push-button switch assembly is not required for the tuner but the copper screening cover is essential to avoid interference pick-up. Most transistor tuners require a 12 volt supply with the casing connected to the negative (earth) potential as in Fig 4.2. Location of this 12 volt rail must be carried out with reference to the circuit diagram of the tuner used.

On many receivers, this is obtained via a suitable dropper resistor (10 kilohms or thereabouts) from the 200V valve supply in the i.f. strip. If this is the case then bypass this dropper resistor together with any r.f. gain control, a.f.c. connection or a.g.c. connections which can be ignored or disconnected.


A varicap tuner can also be used as a modulator, similar modifications being necessary using the correct circuit diagram. Two points to mention on varicap tuners are the absence of mechanical tuning gang capacitors and small internal size. If a carrier frequency control is used therefore a potentiometer must be taken to the outside case which will vary the varicap tuning voltage. Due to the small size, great care must be taken when shorting the coils L7* and L9*.

Finally, all TV transistor tuners are different in appearance and their circuits are not identical, their operations, however, are similar and it is not a difficult task for the experienced electronics constructor to relate the circuit and layout of Fig 4.2 and 4.3 to the tuner in question.

Any tuner from a monochrome or colour receiver, single standard in preference, will be suitable. Integrated tuners with u.h.f./v.h.f. combined are too complex and cannot be used, also valve tuners cannot be used.

CONSTRUCTION

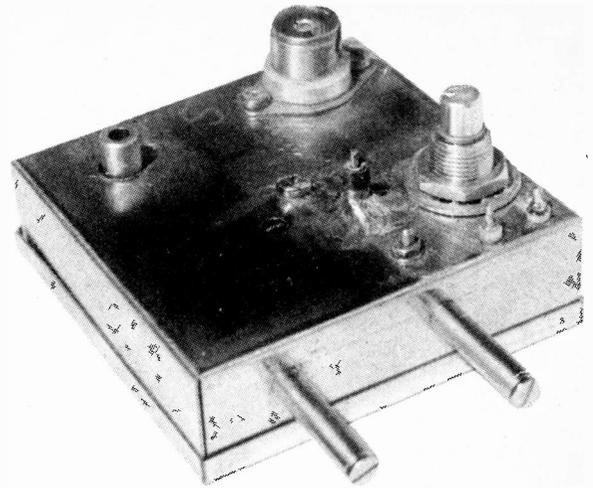The tuner, video printed veroboard panel and power supply will fit into a metal case of dimensions 12cm by 17cm by 4cm deep and are laid out as



The completed Crofton unit

seen in Fig. 4.4. The power supply leads must be kept as short as possible to prevent hum pick-up and the video leads to and from the video panel should be short to avoid interference pick-up. The tuner spindle is passed through a hole in the case so that a knob can be screwed on for carrier frequency adjustment, similarly the video gain potentiometer is screwed onto the case as shown. The power supply regulator is screwed to the chassis after drilling 4mm holes for the input and output leads, the case of the MVR-12 is earthed.

TESTING

The camera is connected to the input socket and the output plugged into a TV aerial socket. A picture should appear on the screen when the carrier frequencies are adjusted to be the same. Adjustment of the gain control will give 'contrast' control and loss of sync when very high or very low. If trouble is experienced in obtaining good results it might be advisable to check the tuner modifications, the polarity of the input video signal or move the carrier frequency up or down the band since the

continued on page 1074

CROFTON MODULATOR.

Kit available from Crofton Electronics, 124, Colne Road, Twickenham, Middlesex, TW2 6QZ. Price £7.30 including p.p. and VAT.


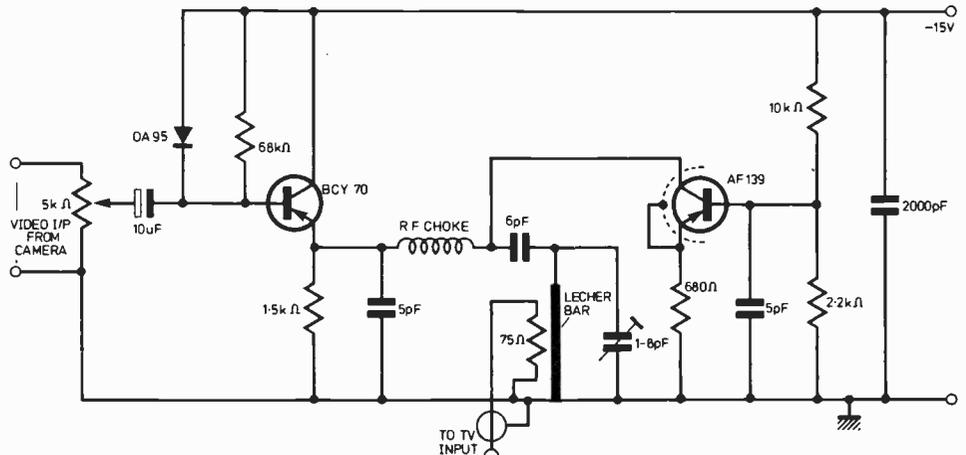


Fig. 4.5. Circuit of Crofton Modulator. For effective operation layout is critical

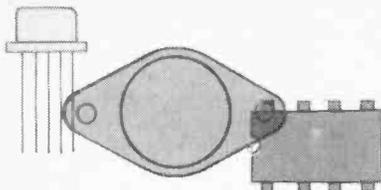

THE NEXT DECADE?

Tomorrow's world of electronics as our readers see it . . .

PULSING AHEAD

IT IS the cheapness of integrated circuits and their ability to produce and manipulate pulses that has given the filip to computers and produced the calculator market. Coded systems (pulse code modulation) have already started taking over the telephone system and we shall see the existing network used for other purposes: vision phones, document transmission, remote reading of gas and electricity meters, etc. An inexpensive print-out device would add a new dimension to the phone service and then amateurs would send photos and letters to each other by phone and P.E. will print the results!

Nor are we limited to telephone lines. The national grid could also be used to carry additional information. A start might be made by having an extension speaker system that simply plugs into any mains outlet in the home. This is feasible now.

We could well see sound and vision broadcasts change to a pulse code system so that our receivers will be minicomputers receiving and decoding pulses. This will keep us busy so we may first have time to build our own video tape recorder using present techniques before it becomes obsolete!

In the home those unreliable timing devices on washing machines, etc. will be replaced by an electronic package. Any mechanical function that can be performed electronically will be fair game and this leads us to motor cars, where manufacturers have already made a start. The lighting harness could be replaced by a ring main operated by pulses. An l.e.d. display could give a direct indication of speed, braking, fuel consumption, visibility and other hazards ahead. Scope here for the enthusiastic constructor to keep his banger up to the same standard (electronically) as the most expensive in the land!

William A. L. Smith

BUY BRITISH

THE increasing use of quadrasonic high fidelity sound reproduction and the decreasing quality of the contents so that we end up listening to quadrasonic silence.

The first Megawatt discotheque amplifier goes on sale. A computer process is developed to produce colour information

from monochrome films of video recordings enabling all television programmes ever made to be repeated in pseudo-colour.

TV personalities and recording stars are elected Gods by electronic vote counting. Suits are made with more pockets to cater for pocket telephone, pocket television, pocket computer, pocket stereo/quadrasonic receiver, pocket aspirin dispenser.

The BBC announces that the experimental octophonic broadcasts will not become a regular feature.

A new electronic timer is developed for sports events and is adopted for the 1984 Olympics. It enables timing to a nanosecond.

I.c. chips become so small that Mullard issue a photograph of one being engulfed by a bacterium.

British viewers now have a choice of six television channels during the 1984 Olympics; this enables them to watch a different event on each channel.

Sony, National Panasonic, Hitachi, having built factories in this country, urge people to "buy British".

January 1984 issue of Practical Electronics carries the announcement that with effect from February 1984 price will go up to £2.50.

R. N. Soar

GOOD HEALTH

THE following indicates an approach to good health which is positive, as compared with the present system which treats lack of good health, i.e. illness, as the positive factor. When an electrical machine is regularly monitored for its insulation resistance, a progressive lowering of the resistance figure (taking the weather into account) can indicate approaching trouble before disaster actually occurs, and suggest the need for inspection and repair.

It is reasonable to suppose that human beings could be monitored in a similar manner, not for their insulation resistance, but as regards temperature, pulse rate, weight, and as many other biological parameters as are quickly measurable by today's techniques, many of which employ electronic means. These measurements could be fed into a computer, say once a month, and changes over a period compared with the changes expected for a standard person of the age, sex, weight and blood group concerned, probably

also taking into account such factors as environment, weight, food intake and type of occupation.

Any unexpected changes developing over the period would then indicate the approach of trouble. After enough experience has been gained with the technique, and if enough biological factors were included in the measurements, it might even be possible to indicate the imminent susceptibility of an individual to a particular disease, and steps taken to counter this.

The great advantage of this method of treatment would be that the patient need not actually become "ill" before treatment is undertaken, and so treatment should be that much easier. Another point is that the biological measurements referred to could be made by technicians, thereby freeing doctors for more urgent tasks. On the one hand, whilst subjects would hopefully be kept in peak condition, on the other the cost of the nation's medical service would be reduced.

W. Higson

OLD AND NEW

POSSIBLY the one sure thing that anyone could predict for electronics in the next ten years would be that the production of valves will cease. Although even the home constructor uses i.c.'s it is surprising to know that valves are still moderately common. When the transistor was first released professional men stuck to the valve. For this reason the valve has hung on and on and so too will the transistor now, and in its turn the i.c.

I would like to see massive efforts (particularly from the Government) in the direction of solar energy control. Alas it will be 50 years or so before the householder hires his "solar energy generator" from the M.E.B. instead of his two-part tariffmeter!

Could it be that periodicals will act as an interface between the old and new, providing the "old timer" with information to help him understand the new techniques and provide food for thought and ideas for the more advanced readers.

I would like to see more modern test equipment being designed, giving top priority to producing an oscilloscope with the capability of a Tektronix or Hewlett Packard, which might be able to deal with the more advanced projects that you might come up with.

G. R. Wates

NO BOUNDARIES

WHEN making auguries for the next decade, one's imagination must take flight because of what has been born from I.S.I. electronics. Solid state TV is a reality with large scale chip miniaturisations now replacing discretés. Plausibly one could predict a standardised chip TV in the near future just like the standard a.m. discrete superhet of today. Predictions in this area include three dimensional pictures using laser display techniques. This is not just pie-in-the-sky but a possibility raised in a recent RTRA/RRI Conference.

Ceefax and Oracle are words which have insinuated themselves into the language now bristling with electronic acronyms. The U.K. leads the world in this field and recent Government approval of a two year experimental period promises much. This would mean up-to-the-minute print-outs of national and international news providing continuously revised news items, blow-by-blow accounts of stock market dealing, sports news, local news and weather forecasts, all displayed in page form on the screen at the flick of a switch.

In radio, quadrasonic reception will be a certainty since pioneering spadework is already underway.

As a sop to the inevitable neurosis all this surfeit of goodies will cause, electronics will slavishly function as an unpaid locum with the dial-a-complaint computer; another feasibility which will take the mundane work load from the G.P., returning him to his true role of family counsellor and N.H.S. clerk.

In automobiles, digital metering of fuel, temperature, speed, etc. is a certainty since I.e.d. displays are becoming cheaper than their analogue counterparts.

Electronics is a science which has, of necessity, crossed the boundaries of so many disciplines, such as medicine, chemistry, automobile engineering, etc. that it is inevitable that its effects or spin-off in ideas must increase to the benefit of humanity.

G. Rapson

INFORMATION DESK

THE public's requirement to be kept up to date with such things as public services, entertainment and general information creates a market for message systems and information retrieval.

To enable this market to be satisfied the minicomputer in the form of a desk top model completely self-contained will supply the service. The computer will be fully programmable by either cassette tape or disposable read only memories (ROM) with visual display output (VDU) and/or permanent copy by thermal printing for availability of users' information.

In order that the public can make use of the service the computers will be located at such places as libraries and

railway stations and the service will work in the following way.

As the computer is completely pre-programmed by use of either disposable ROM's or cassette tapes programmed at a central bureau, the programme material will include such things as the entertainment available in the area served by the library, updated monthly on the basis of disposable programmed devices.

Other services offered could be timetables of buses, trains serving that area, hours of opening for public buildings, half day shopping, hotels and many other services.

For more than one user a number of displays will be available driven from the computer using time sharing techniques; also a number of inquiry points will be accommodated. The systems can be further extended to such places as large supermarkets giving information on best buys, present prices and availability of items.

R. Cepa

IT'S ALL CHEMISTRY

WHEN thinking of the future one must take into consideration, that although a decade is not long, it is sufficient time for major development or cultivation of a revolutionary idea.

For example, ten years ago the transistor was making its debut for home constructors; now it is an indispensable component. Similarly the laser was invented a little over ten years ago; now it holds a definite place in industry and technology.

Although not fully conversant with the intricacies of modern electronics, I feel that changes are inevitable and possibly will involve chemistry, where the exploitation of the heavy metal compound crystals (i.e. the rarer ones, e.g. Neodymium) is by no means exhausted.

As components become more intricate and delicate, soldering will lose its popularity. The introduction of a conductive heat resistant adhesive/resin for securing components may prove suitable. "Deresinification" (desoldering) would be carried out using a non corrosive solvent (actuated at time of use to prevent spillage the consequences of such an accident can be imagined).

Similarly the copper strips on Vero or p.c. boards could be replaced with electrically conductive plastic. (The price of copper rarely fluctuates from the steady rise.)

Laser development will advance to the high degree of household necessity, for some inappropriate capability.

T.V.s will change for the commercial market. All colour, quad or stereo (personal preference), even the collaboration of holography and T.V. for 3D viewing.

B. Theiss

MATURITY

OUR TECHNOLOGY has been developing exponentially for a century, and is now approaching maturity.

The significance of maturity in technology lies in the freedom from standardisation that it brings; it allows a huge increase in the range of goods available without an equivalent rise in cost at the end of the production line.

At first sight, such abundance might gladden the electronics constructor. The range of projects open to him would widen dramatically, and the price of short-run chips, anti-log pots and other expensive oddities would be decimated. Design and performance would be near-perfect; integration of circuitry would be combined with flexibility of application. But the home constructor enjoys his hobby because it tests his skill, and the hobby magazines reflect this fact, suggesting projects that (a) are not available in the shops (or not so cheaply), (b) involve some skill in construction and "tuning" and (c) give enjoyment through the intelligent use of the latest technological developments. A maturing technology combined with an aggressive electronics industry will force the home constructor into beyond-the-fringe gadgetry if he wants to retain any of these features.

The start of this trend is already evident. If the history of other technology-based hobbies can be trusted to repeat itself, the electronics constructor will soon be tempted to return to the comfortable past when his radio needed him. Like a vintage car enthusiast a plate photographer, or a steam fanatic, he will gladly exchange the boring best for the challenge and involvement that previous eras provided.

D. Beattie.

IDEAS IN INK

IT IS my opinion that the next ten years will bring a much wider application of plastics within the field of electronics. I envisage the development of synthetic materials with various electronic properties.

Not only will this include the simple properties of conductivity, resistivity, capacitance, etc. but it seems quite possible that a substitute for silicon and germanium could be produced.

Taking this idea a little further, it is easy to imagine the evolution of kits containing special resins and "inks" with templates and equipment for printing one's own "giant size" integrated circuits on little more than sheets of paper.

The key factor here of course is the price of the plastics involved. If they are to be particularly expensive this might more than compensate for the cheap production of i.c.s and put them out of reach of the home constructor. However, if this is not to be so then the potential of the amateur could be greatly extended.

D. Gowe

... a further selection of readers' predictions will appear next month

THE NEW JUPITER

An analysis of the data provided by *Pioneer 10* reveals some startling facts. Many of the previous conjectures about the constitution and structure of the giant planet will have to be abandoned. No doubt the first findings will be confirmed by *Pioneer 11*, which will fly past the planet in the first week of December, a year from the time that *Pioneer 10* collected the initial data.

One of the puzzles of Jupiter has been the great Red Spot. For something like three hundred years there have been many observations and almost as many theories. These range from the possibility of a sub-merged satellite, suggested by Firssoff, to the Taylor column. This is an effect that could take place if there was a high projection of, say, a mountain and the consequence of hydrodynamic waves in the atmosphere. In fact it does appear that the red spot might be caused by an updraught of hurricane force. The red spot would be the vortex centre. The size of the spot, some 40,000km (25,000m), could be the visible evidence of this. If such is the case then the views of Professor Raymond Hide would be relevant.

The severe atmospheric effects would be expected on the new facts. From the analysis of the gravity sensing experiment, Dr J. Henderson of the Jet Propulsion Laboratory and Dr W. B. Hubbard of the University of Arizona, it appears that Jupiter is largely liquid. If there is a core at all, it would be molten and very small. The temperature would be very high and pressures would be high. It is worth remembering that the late B. M. Peek in his book "The Planet Jupiter" discusses these early models in detail.

COLOURED BELTS

The coloured belts have been a continuous study particularly by the amateur astronomers. The periods of revolution of some of the white and grey areas have resulted in thousands of sketches of great accuracy by members of the Jupiter section of the Astronomical Association.

The new thoughts on this subject are that the white and grey areas are in fact cloud tops only some 240km (150m) below the upper limit of the planet's atmosphere. The brown and orange areas would be troughs. It would appear that the clouds on Jupiter are stretched round the planet, rather than in circular groups as they are in the Earth's atmosphere. The stretching out round Jupiter is most likely due to the rapid rotation of Jupiter on its axis, some 9 hours 55 minutes. The actual speed at the equatorial belt is of the order of 35,000km (22,000m) an hour.

Another problem that has been the subject of conjecture is the



excess of heat radiated by Jupiter. This level is some two and one half times that which Jupiter receives from the Sun. The new model of the planet suggests that it is cooling off and growing smaller, this would account for the high level of heat being given off. The model of the planet which now emerges is that of a body of four conditions. The first is the possible core which would have a temperature of 29,000°C. Next there is a level extending for many thousands of kilometres where the hydrogen has become metallic with a temperature in the region of 11,000°C. In this area pressures could be as high as 45,000,000 lbs/sq.in. The next region which starts at about 1,000km into the atmosphere is a transitional zone where there is liquid hydrogen.

The magnetic field has already been described in *Spacewatch* (Sept. '74) with considerable detail. One new point to be added is that as a result of the high level of the radiation belts, which are of a similar configuration to those surrounding the Earth, high energy particles have been radiated and detected on Earth.

The four large satellites, almost of planetary size, all appear to have atmospheres of their own. The densities are proportional to the distance between them and the planet. Pictures were obtained of the satellite Ganymede, these are being processed but first findings do indicate that there are highlands and lowlands similar to Mars and the Moon. The composition of the satellites do indicate the possible combination of ice and rock, in the case of Ganymede and Callisto. Io and Europa are certainly rock.

After *Pioneer 11* has made its fly-past it will be on the way to Saturn. It will pass between the main body of Saturn and the innermost ring.

LARGEST KNOWN OBJECTS

Two radio galaxies of immense size have been discovered by A. G. Willis, R. Strom and A. Wilson, using the Westerbork radio telescope.

One of these, the largest object so far known in the universe is 3C 236. The radio components of this galaxy are spread over the vast distance of 18 million light years. The second object is DA 240 and is 6.6 light years across.

The measurements were made by the synthesis telescope which comprises 12 parabolic reflectors working in a linear base line of 1.5km. This provides a beam of resolution of 1.0 arc minute, with a field of 1.5°. The frequency of operation is 49cm.

It is certain that more of these objects will be found. They are on such a vast scale and the density as low as 30 atoms per cubic centimetre, that is almost the mean density of the universe. The energy in these extensive objects must be so high that there are electrons moving at almost the speed of light.

One thing is certain and that is that if more of these objects exist, then rather drastic remodelling will need to take place. With objects like these the radio clouds will have spread relativistic plasma throughout a volume of space equal to that of large galaxies or even clusters of galaxies. Estimates of the age of these radio sources is increased by a factor of ten. Obviously some rethinking is likely to be extensive, for the effect on cosmological theory will be profound.

MOVEMENTS OF THE CRUST OF THE EARTH

A project by NASA called Astronomical Radio Interferometric Earth Surveying (ARIES) will provide information about continental drift and improve earthquake prediction.


The technique is to receive radio emissions from extra-galactic sources at two places, and time the arrival differences. In practice this means that the antenna at Goldstone and the antenna at the Jet Propulsion Laboratory are focused on a quasar. The difference of the time of the arrival of the signals at the two places can be measured to 0.1 of a billionth of a second. These data can then be resolved in terms of distance between the two stations. This can be done at the moment with an accuracy of 10cm; later it will reach an accuracy of 2cm. Any difference in the measurements will indicate movement and strain.

It will be possible to use portable antennas for this work so that by changing the position of any two an almost three dimensional picture can be built up. Thus the movement and strain along the San Andreas fault can be detected.

ACOS FOR SOUND ENJOYMENT

Magnificent Martin Speakers

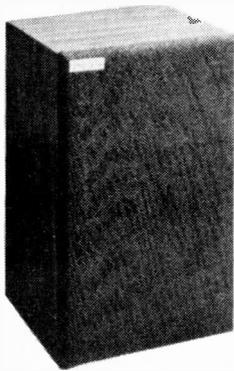These restyled, popular Hi-Fi speakers are available with an attractive wrap-around grill and a performance range to suit any system. Brilliance controls are provided which help to fit them into any setting.




Acos Rega Record Deck

Elegant, modern styling with first-class performance.




The Acos M6 Range of Magnetic Cartridges

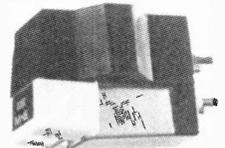are acknowledged to give high performance at low cost for two channel and four channel stereo.



Acos Lustre Tone Arm

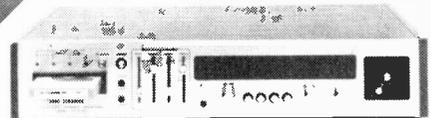Proven quality tone arm for the enthusiast, incorporating 'dial-a-magnet' anti-skating.



Acos Eleanor Range of two channel and four channel stereo tuner amplifiers

provide a new concept of sound enjoyment in any home setting.

Record and Tape Care Accessories

Use Acos care accessories for your sound enjoyment.

Cosmocord Ltd, Eleanor Cross Rd, Waltham Cross, Hertfordshire EN8 7NX

Telephone: Waltham Cross 27331, Telex 24294.

Please send me full details of



NAME

ADDRESS

Come and hear a Thousand Pound Sound at Lindair...



At Lindair House, 227 Tottenham Court Road, you'll find 3,500 sq. ft. of demonstration studios with all that's best in Hi-Fi. And now we've added Studio 1000+ - a demo studio totally devoted to the top line in stereo equipment.

With names like **TEAC, Revox, JBL, Tannoy, Marantz** and others, you can hear systems which cost over £1,000 and which sound like a million.

Only Lindair give you the sort of service to match this standard of equipment. Come and have a demonstration in the relaxed atmosphere of Studio 1000+ - and you'll hear what we mean.

If Quadrophonic takes your fancy - our 4-channel demo studio is just next door to Studio 1000+.

Studio 1000+ is just the beginning of a whole complex of facilities serving the sounds enthusiast - Stereo, 4-channel and Home Tape Studios. All the best - and all at Lindair.

Come in soon and sound us out.



Lindair House, 227 Tottenham Court Road, London W1. 01-580 7383



Telephone orders accepted. Access and Barclaycard welcome. H.P. available to all callers from AVCO Financial Services.

Strictly

Instrumental

by K. Lenton-Smith

WITH many electronic projects, there are no half measures—they either work or fail when first tested. Where audio applications are concerned, the project could work but only after a fashion and then some very critical faculties (sic) will come into play!

The listener with anything approaching perfect pitch will find tuning discrepancies particularly objectionable. He will stomach single note melodies, perhaps, but sustained chords produce violently noticeable beats—even to those that are tone deaf: the more upper harmonics in the chord, the worse the effect.

VOLTAGE

The last article in this series dealt with tuning generally and its main purpose was to warn the constructor to take great care in choosing his generator system. That article prompted a letter from a reader experiencing tuning drift, due to mains voltage fluctuation, with a commercially made electronic accordion. The instrument concerned uses astable multivibrators as master oscillators, followed by bistable multivibrator dividers. I decided to confirm the comments about R/C oscillators in the previous article by making up the accordion's master oscillator to see how voltage changes affected it. Using a frequency meter, a one volt change in supply in either direction caused a frequency change of about 6 per cent—or a semitone in musical terms.

If such an instrument was only played solo, very few listeners would object. After all, the key of C sharp sounds better than C—provided the whole system is in tune with itself! But the problems arise when playing with other instruments and the player will find himself at odds with a well-tuned piano. Nothing will throw a small band into confusion quicker than this type of problem—or encountering a continental pitch piano!

SPACE PROBLEMS

It is essential that any electronic instrument can be accurately tuned and will stay that way. The keen amateur may be itching to get with the problem, but commercial instruments may present difficulties because of lack of space due to the use of i.c.s, and general condensation of circuitry. Reorganisation of master oscillators may have to be ruled out, therefore.

As we have seen, R/C oscillators require a precise supply voltage to stay in tune, so it might pay to look carefully at the power pack. There will probably be an array of voltages for generators, keying, pre-amplifiers, power amplifier, etc. but the most important supply is that to the generators and in particular the master oscillators. Regulation should be checked with the instrument in operation and, if this is found lacking, one of the TO3 encapsulated regulators (MVR type) might be incorporated. Both load and line regulation of these devices are better than a fraction of one per cent, if their output voltages match the circuit's requirements.

MAINS REGULATOR

If it can be proved that mains voltage fluctuation is the root cause of tuning instability, the simplest course would be to fit a mains voltage stabiliser between the a.c. supply and the instrument. If the load is fairly light, the type sold by photographic shops (for stabilising brightness and colour temperature of enlarging lamps) might be one solution.

No apologies are due for labouring the point concerning tuning: building a polyphonic keyboard instrument is a major operation. It is as well to be absolutely sure that the home constructed instrument will not require an expensive and time consuming modification after completion because the back has to be taken off every week to re-tune it.

TREMULANT

Tremulant is an amplitude modulation effect, and should not be confused with vibrato which is frequency modulation. It is fairly easy to arrange by connecting the signal across an l.d.r. and modulating this resistor by means of a lamp. The lamp could form part of the collector load of a multivibrator, or it could be a miniature neon in a relaxation oscillator circuit. Whilst the filament lamp is best suited for tremulant effect, the more precise pulsing of a neon enables it to be used for higher speed chopping—repeat effects such as mandolin and banjo.

In early instruments, tremulant was often obtained by using a motor driven variable resistor across the signal source, but these were noisy and tended to wear rapidly. Devices such as the ORP12 l.d.r. have since come on the market and are both dependable and noiseless.

VIBRATO

Good vibrato is by no means easy to obtain, especially if the oscillators are really stable. The fact is that, if you have a stable oscillator, you must expect stability! When the oscillator refuses to be modulated by an electronic vibrato, the effect is best obtained by mechanical means—such as the Leslie speaker.

The vibrato oscillator should ideally produce a sine wave, although multivibrators are often used commercially. A fair amount of drive will be required, in some cases of almost medium power proportions, to the base of the oscillator transistor. A good deal of care is required in setting up, too much signal making the oscillator fail on peaks and too little producing nothing more than a mild tremulant.

DELAY LINE


Electronic vibrato often sounds uninteresting as its effect is similar for all frequencies. The Hammond delay line system overcomes this problem as its effect is more prominent at higher frequencies. The line consists of some 18 L/C sections and, according to the vibrato depth chosen by the player, sections are switched to the stators of a multi-element variable capacitor whose rotor picks up the modulated signal. By scanning back and forth along the line, phase differences are converted to frequency differences: this contributes to chorus effect as modulation takes place per section of the line according to frequency.

PE MINISONIC

By D. SHAW

PART TWO

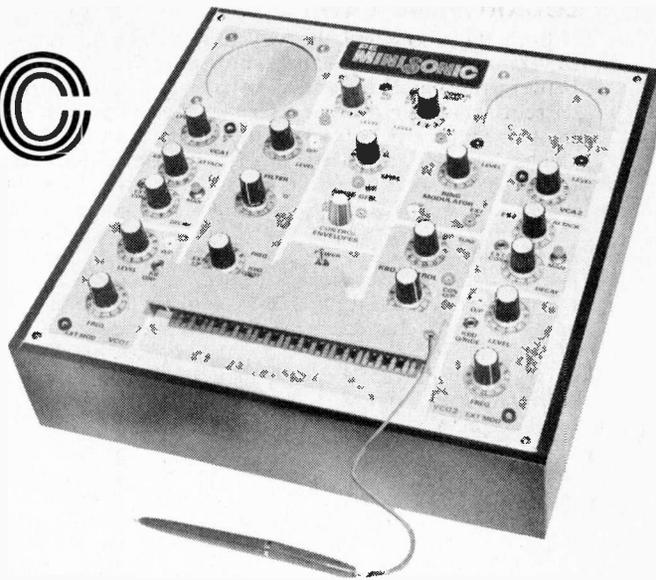- Voltage Controlled Oscillators
- Voltage Controlled Filter and Envelope Shaper
- Voltage Controlled Amplifiers



THIS month we begin the circuit construction of the P.E. Minisonic series by detailing the vco's, vcf and Envelope Shaper/vca's.

BATTERY LIFE

The average current drawn by the P.E. Minisonic is about 62mA, so it is estimated that a pair of PP9 batteries will provide up to 50 hours of useful life. Much depends, of course, on the length of the periods during which the instrument is switched on. When usage is restricted to around two to four hours per day then maximum battery life can be expected.

On the current price of PP9's, therefore, the running costs of the P.E. Minisonic are likely to vary between 1.4p per hour and 2.33p per hour depending on usage and this seems, on the basis of comparison with other forms of entertainment, to represent pretty good value for money.

One of the drawbacks of battery operation is that the voltage falls in a manner proportional to the drain and to the charge remaining, and thus circuits which are voltage sensitive could begin to perform in an erratic and unreliable manner.

In the P.E. Minisonic this problem has been overcome by the establishment of voltage reference rails, considerably below nominal battery potential, in order to serve those circuits which are particularly voltage sensitive.

In practical terms the vco's and vcf will operate without any change in performance down to ± 7.5 volts and, indeed, will tolerate supply voltages up to ± 12 volts also without change in performance.

The worst effect of falling battery voltage on these circuits not served by the reference rail is that the gain/attenuation ratio of the vca's diminishes by between 6 to 8dB and the noise generator will cease to operate at about ± 7.8 volts.

The great advantage of battery operation is that the instrument becomes a perfectly safe proposition for the younger enthusiast who can dabble about to his heart's content without the attendant fear of electrocution.

COMPONENTS . . .

VOLTAGE CONTROLLED OSCILLATOR (2 required)

Resistors

R1, R2	6.8k Ω (2 off)
R3-R6	47k Ω (4 off)
R7	22k Ω
R8	1.2k Ω
R9	1k Ω
R10	2.7k Ω
R11	1k Ω (see text)
R12	750 Ω
R13	22k Ω
R14	82k Ω (see text)
R15, R16	10k Ω (2 off)
All	$\pm 5\%$ $\frac{1}{4}$ W or $\frac{1}{2}$ W carbon

Potentiometers

VR1	10k Ω skeleton horizontal preset
VR2	10k Ω linear carbon
VR3	100k Ω skeleton horizontal preset
VR4	10k Ω linear carbon

Capacitors

C1	0.1 μ F
C2	22 μ F 16V tantalum
C3	3.3pF

Semiconductors

D1	1N914
TR1	BC184
TR2	BC213
IC1, IC2	Type 741 8-pin d.i.l. (2 off)
IC3	Type 748 8-pin d.i.l.

Miscellaneous

JK1	3.5mm jack socket
SK1, SK2	2mm sockets (2 off)
0.1in Veroboard, 115 \times 34 holes (This board also carries Keyboard Control, Mixers and Ring Modulator)	

LOGARITHMIC LAW

Both the vco's and the vcf have a logarithmic—or, more accurately—an exponential relationship between the applied control voltage and the control current which, in turn, prescribes the frequency of the vco and the pass-band of the vcf.

The so-called "log-law" has been adopted because it allows for a considerable simplification in the keyboard and pitch determining systems—an important factor in an instrument which is to be used for musical purposes and which, hopefully, is to remain in tune over relatively long periods.

In simple terms the "log-law" enables linear increments of control voltage to cause frequency changes of one octave in the case of the vco or passband variations of one octave in the case of the vcf.

In the P.E. Minisonic the control voltage increment required is 600mV per octave but there is provision for adjusting this from about 220mV per octave to 1.2V per octave in order that the instrument may be matched to other synthesiser systems.

Since the control voltage increment is the same value for both vco and vcf this enables the control node for both circuits to be identical save for two minor variations.

THE CONTROL NODE

The circuit of the control node is shown in Fig. 2.1, which shows the vco but an almost identical control node is used in the vcf. IC1 is a four-input summing inverter in which two inputs are committed to providing bias and manual control voltages while the

remaining two can be coupled to external programming sources.

The overall gain of the inverter is prescribed by VR3 which is used to set the so-called "law" of the system, i.e.—the relation of frequency or pass-band to voltage. VR1 provides a fixed bias to the inverter which serves to set the minimum frequency, or to position the overall frequency range in manual control, while VR2 provides the voltage swing, in manual, required to give a nominal ten octave range.

The input via R5 is coupled through the normally-closed contacts of JK1 to the keyboard controller "hold" circuit (which will be described next month).

Insertion of an open circuit jack plug will override the "hold" input or, alternatively, an external signal wired in to a jack plug may be routed into this input.

The input via R6 is wired to a 2mm socket so that an external programming signal may be employed in combination with the keyboard.

The output of IC1 drives a divider, R7-R8, which sets the bias on transistor TR1—a constant current generator. It is in TR1 that the exponential relationship between control voltage and control current is derived.

TRANSISTOR CHARACTERISTICS

Reference to the characteristic curves of almost any small signal transistor in which V_{be} is plotted against I_C will show that there is a fixed relationship between these factors which extends over a range of three or four decades.

V.C.O.

PERFORMANCE

Frequency Range	10 octaves, nominally 5Hz to 5kHz in manual control
Control Voltage Law	600mV per octave
Waveform	Sawtooth, 400mV p-p
Current Drain	5mA


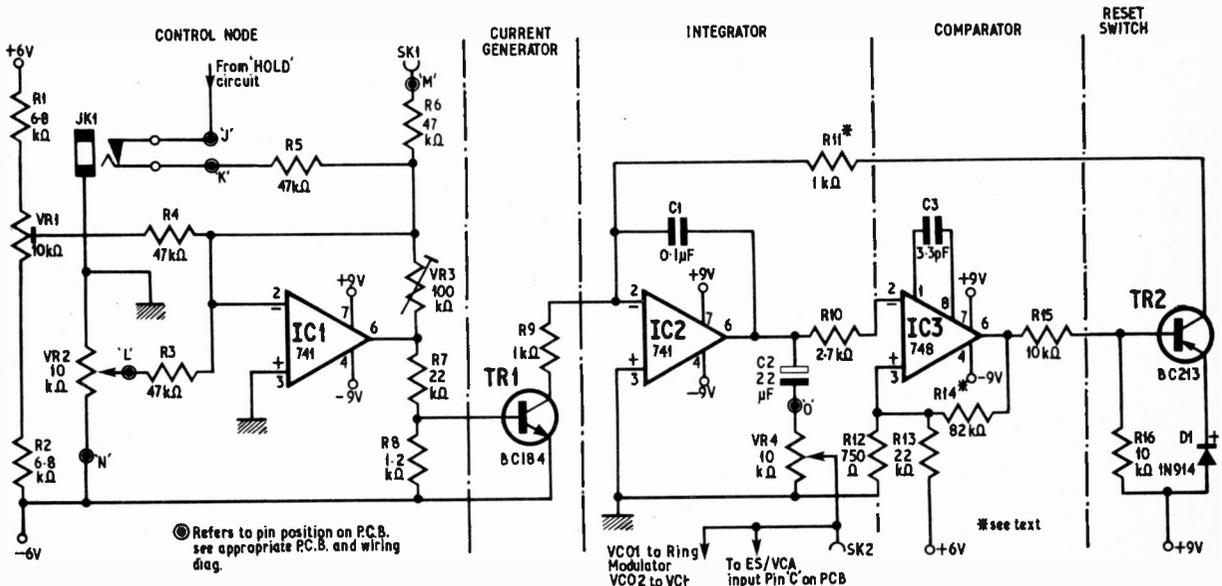


Fig. 2.1. Circuit diagram of the Voltage Controlled Oscillator. Letters in inverted commas refer to connections from the Veroboard panel to the front panel

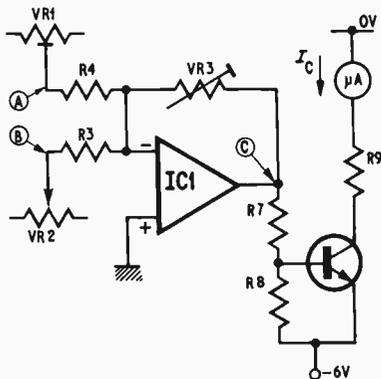

Voltage readings with A at -1.4V and C at 0.95V

B(-V)	0	0.6	1.2	1.8	2.4	3.0	3.6	4.2	4.8	5.4	6.0
$I_c(\mu\text{A})$	—	—	0.5	1.0	2.0	4.0	8.0	16.0	35.0	82.0	190.0

Fig. 2.2. Simplified circuit of the control node used in both the VCO and the VCF. The table shows typical current readings for different settings of VR2. Note that tolerance on R7 and R8 can cause significant departures from values shown. These may be compensated by adjustment of VR1. The important relationship is between the voltage at B and I_c .

Above a minimum level of V_{be} , the collector current will double for each successive increment in V_{be} of the order of 20 to 25mV. Over the straight line portion of the curve, if it is assumed that the V_{be} increment is 24mV, then increments of 2mV will cause the collector current to increase successively in the ratio $1:12\sqrt{2}$ — which musicians will immediately recognise as being identical to the ratio in pitch between any two consecutive notes in an equal tempered scale. Indeed, this relationship serves to explain why the "log-law" circuit is so much more useful in a musical sense than its linear counterpart.

SETTING-UP PROCEDURE

The efficiency with which the vco's and vcf function relative to their respective control voltages is entirely dependent upon the accuracy with which the setting-up of the control node is accomplished.

The principal aim is to ensure that successive increments of 600mV supplied by VR2 result in successive doublings of the current through the constant current generator TR1. Fig. 2.2. illustrates a simplified control node together with a table of typical results obtained with the prototype instrument.

With the wiper of VR2 at ground potential, VR1 should be adjusted so that the wiper is at -1.4V . VR3 should now be adjusted so that the output of IC1 is at $+0.95\text{V}$. These adjustments will set the operating points of the control node to within close limits of the required values.

A multimeter switched to the microamp range should now be connected between R9 and the 0V rail and VR2 swung through the range of values shown in the table.

It should be noted that the current readings recorded will not necessarily correspond exactly with those quoted in the table since tolerance variations in R7 and R8 can cause significant differences.

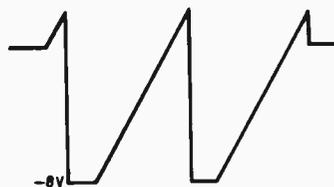


Fig. 2.3a. The integrator output with resistor R11 removed

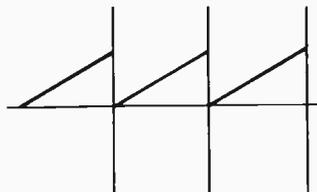


Fig. 2.3b. Output of the integrator showing large spikes during the reset period. These are too fast to be audible

During the first swing of VR2 it is almost certain that errors will be present and it is important, at this stage, to determine whether the current through TR1 is greater or less than the doubling required for each increment of 600mV at the wiper of VR2.

For this purpose it is best to carefully record the current readings obtained over a range of input voltages—say from 1.2V to 4.8V—in order to establish whether the error is consistent.

If the current through TR1 is greater than the doubling required for each 600mV increment then the gain of IC1 has to be reduced by adjustment of VR3. Conversely for less than the required doubling.


When the required relationship has been established the control nodes for the vco's may be matched by making a further adjustment to VR1 so that, for a given voltage supplied by VR2, the current through TR1 is identical in both nodes.

It should be noted that the current/voltage relationship in the control nodes need not be precisely 600mV per current doubling. Indeed the range of adjustment afforded by VR3 allows that the relationship may be set at any value lying between approximately 220mV and 1.2V. What is important however is that the relationship adopted should be *exactly* the same for all control nodes. If it is not then the circuits will not track accurately and the overall performance of the instrument will be marred.

The design of the Keyboard Controller is such that it can accommodate any voltage/current relationship which it is possible to set up with the component values given for the control nodes.

THE VOLTAGE CONTROLLED OSCILLATOR

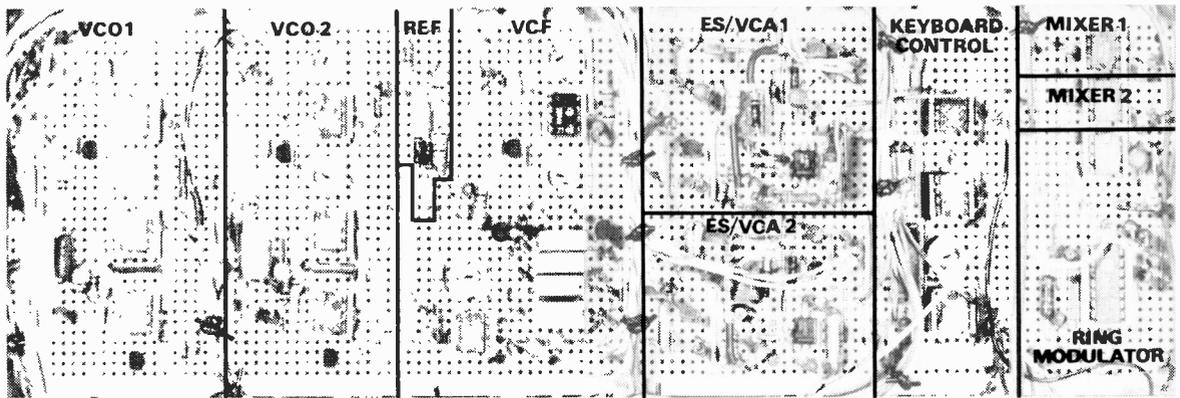The complete circuit of the vco is illustrated in Fig. 2.1. Apart from the control node and current generator the vco comprises a linear integrator around IC2, a comparator around IC3 and a reset switch TR2.



Photograph of complete board on which VCO's, VCF, Voltage Reference and ES/VCA's are mounted. (Note: some minor changes have been made to this layout)

HOW IT WORKS

If we assume that the reset cycle has just completed, the output of IC2 will be zero volts, the output of IC3 will be positive due to the voltage applied by divider R12-R13, and TR2 will be hard off. C1 although nominally uncharged will, in fact, have a charge in relation to the negative rail and thus TR1 will draw on that charge at a constant rate thereby causing the output of IC2 to ramp in a positive direction.

The maximum positive level of the ramp is determined by two factors. Firstly there is a positive threshold voltage set by divider R12-R13 which is equal to:

$$\frac{750}{22750} \times 6 = 200\text{mV}$$

Secondly there is a positive feedback factor applied to IC3 by R14. This has the effect of determining a further threshold value on the basis of the currents applied differentially to IC3 through R10 and R14.

If x be a voltage at the output of IC2 then the secondary threshold value is determined by:

$$I_{R10} = \frac{x}{2700} = \frac{8}{82000} = I_{R14}$$

i.e. approximately 250mV.

The overall threshold value is thus theoretically 450mV. Although the 450mV threshold could be derived from divider R12-R13 alone the adopted method is preferable because it has the effect of speeding up the switching process.

When the output of IC2 reaches the threshold value the output of IC3 will try to go negative. However, the biasing on TR2 is such that when the output of IC3 has moved about 200mV, TR2 turns on and sends a relatively large pulse of current into C1 in order to restore the original state.

At this point the output of IC2 moves rapidly in a negative direction and when it falls below 200mV, i.e. below the minimum threshold value on IC3, then IC3 will switch to positive saturation again before the output of IC2 actually reaches its minimum level. At this point the cycle repeats.

The overall effect is to provide a very rapid reset which results, in relation to the integrating rates employed, in a sawtooth waveform of almost perfect shape.

The reset time occupies a period of approximately $8\mu\text{s}$. On most oscilloscopes the reset pulse

will be invisible at low frequencies and its presence will generally only be detectable at frequencies of the order of 5kHz and greater.

RESET TIME

Resistor R11 sets a limit on the reset current supplied by TR2 and thus has an effect on the reset time. With R11 significantly greater than $1\text{k}\Omega$ it will be found that the reset will terminate at a point about +100mV or so above zero volts, at which point integration will re-commence.

With R11 removed altogether the output of IC2 will go hard negative at each reset resulting in an output waveform as shown in Fig. 2.3a and a very slow rate of oscillation.

The ideal situation is when the value of R11 is such that the reset, as measured at the output of IC2, terminates on the zero volt rail. The output waveform of the integrator is shown in Fig. 2.3b.

Resistor tolerances being what they are there could, in a worse case, be as much as 20 per cent variation in the integrator output waveform peak-to-peak value between oscillators. This means that, with matched control nodes and for a given control voltage, the vco with the greater amplitude waveform will run at a proportionately lower frequency.

Fortunately this error is constant over the whole frequency range and may thus be compensated for by adjustment of the bias control VR1. It is more elegant however to make the adjustment on the vco itself so that the greater level in output waveform will not introduce any impairment of performance in relation to the sound treatment circuits.

Resistor R14, in view of its value and position on the circuit board is the most convenient resistor to adjust. Any adjustment should be directly proportional to the error variation in output waveform level, i.e. if the output waveform is 10 per cent high in relation to the other vco then the value of R14 should be increased by 10 per cent—to $91\text{k}\Omega$ say—and vice versa.

From Fig. 2.3b it will be seen that the integrator output waveform exhibits a substantial positive and negative going spike at the reset point. This is due to the differentiation of the reset pulse by C1.

Although rather unsightly, the spike is too fast to have any effect on the audio output.

V.C.F.

PERFORMANCE	
Passband	3Hz to 15kHz (-6dB)
Dynamic Range	-54dB (referred to peak output signal)
Resonance Range	5kHz to 25kHz
Current Drain	4mA (min), 8mA (max)

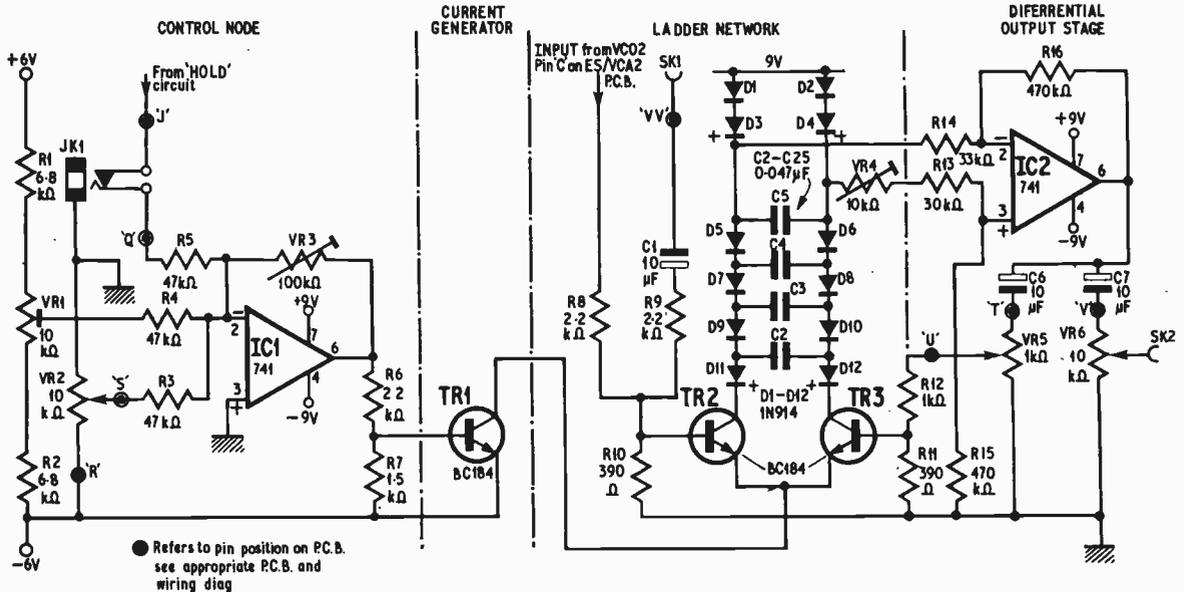


Fig. 2.4. Complete circuit diagram of the Voltage Controlled Low-pass Filter

VOLTAGE CONTROLLED LOW-PASS FILTER

The complete circuit of the filter is shown in Fig. 2.4 and comprises, in addition to the control node and current generator, a ladder network and a differential output stage. The ladder network, in which the filtering action takes place, is based on the design by Dr R. A. Moog.

The diode may be considered to be an impedance which varies inversely as the current through it, i.e. at low currents the impedance is high and vice versa. The a.c. signal is superimposed on to the diode current flow as shown in Fig. 2.5 which represents the lower half of the ladder network.

The ladder terminates in transistors TR2 and TR3 which are effectively biased on by referring their bases to the 0V rail. Thus any current drawn through the network by means of the constant current generator passes, without restriction, through these transistors.

If an a.c. signal is now applied to the base of TR2 there will be a proportional variation in the current through the transistor and thus also a voltage variation at each diode junction in the ladder.

This applies over virtually any current drawn by the constant current generator so that, for a given level of a.c. signal, the smaller the current through the network, the smaller will be the proportional variation induced by the signal. Thus the concept of variable impedance is, in fact, due to the combined effect of diode, transistor and current generator.

FILTER PERFORMANCE

The range extends over several decades and, in the circuit given, the -6dB passband at maximum is from 3Hz to 15kHz.

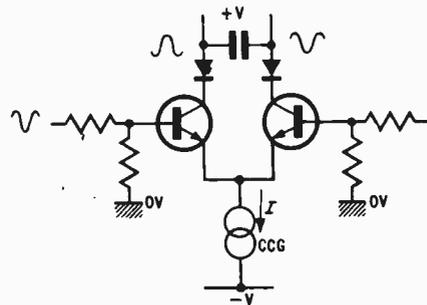


Fig. 2.5. Simplified circuit diagram of the lower section of the VCF showing how the a.c. signal is superimposed on the ladder current

Four filter stages are cascaded in the ladder network and since each stage has a theoretical roll-off of 6dB per octave the maximum roll-off of the filter should be 24dB per octave. Efficiency in this respect can only be achieved, however, if every precaution is taken to prevent loading the network both at the point of entry of the a.c. signal and also at the point of extraction.

In the interests of simplicity and economy the buffer stages have not been included in the circuit but, even so, the roll-off possible is around 12 to 15dB per octave and, for the majority of purposes, this will be found to be quite sufficient.

FEEDBACK

The output from the filter network is amplified differentially by IC2, with VR4 being employed to cancel out any d.c. imbalance due to variations in

COMPONENTS . . .

VOLTAGE CONTROLLED FILTER

Resistors

R1, R2	6.8k Ω (2 off)
R3-R5	47k Ω (3 off)
R6	22k Ω
R7	1.5k Ω
R8, R9	2.2k Ω (2 off)
R10, R11	390 Ω (2 off)
R12	1k Ω
R13	30k Ω
R14	33k Ω
R15, R16	470k Ω (2 off)
All $\pm 5\%$ $\frac{1}{4}$ W or $\frac{1}{8}$ W carbon	

Potentiometers

VR1	10k Ω skeleton horizontal preset
VR2	10k Ω linear carbon
VR3	100k Ω skeleton horizontal preset
VR4	10k Ω skeleton horizontal preset
VR5	1k Ω linear carbon
VR6	10k Ω linear carbon

Capacitors

C1	10 μ F 6.3V tantalum
C2-C5	0.047 μ F (4 off)
C6, C7	10 μ F 6.3V tantalum (2 off)

Semiconductors

D1-D12	1N914 (12 off)
TR1-TR3	BC184 (3 off)
IC1, IC2	Type 741 8-pin d.i.l. (2 off)

Miscellaneous

JK1	3.5mm jack socket
SK1, SK2	2mm socket (2 off)

diode characteristics. The output signal from IC2 is capacitatively coupled into two potentiometers. VR6 is simply the output level control while VR5 is the feedback or *Q* control.

With the *Q* control at zero the base of TR3 is referred closely to the 0V rail and thus TR2 and TR3 behave essentially as a differential pair. The output of IC2 is therefore nominally in phase with the input signal at the base of TR2.

As VR5 is advanced from zero a proportion of the output signal appears at the base of TR3 thereby tending to induce a signal in the collector circuit which is 180° out of phase with the signal which is already there due to the effect of the signal on TR2. The result is that the output signal will become significantly attenuated except at the frequency whose period is equal to the adjusted time-constant of the network.

At this critical frequency the output of the filter will peak up, the bandwidth of the signal depending on the degree of feedback applied.

Further application of feedback will cause the filter to oscillate. The frequency of oscillation is proportional to the current through the ladder network and the oscillation, which is of sine form, will be superimposed on the filter output signal. The P.E. Minisonic filter oscillates over the range 5kHz to 25kHz.

The filter may be operated in a number of modes each of which finds a place in the tone colour spectrum of the synthesiser. An outline of the various possibilities will be given in a later part of the series.

SETTING-UP THE VCF

The setting up of the control node for the vcf should follow exactly the same procedure as the vco with the exception that, having established the correct voltage/current relationship, VR1 is adjusted so that the maximum current through TR1 with an applied voltage of -6V at VR2 should be of the order of 3mA instead of the 190 μ A quoted in the table shown in Fig. 2.2.

In order to achieve this result the value of R7 in the vcf is 1.5k Ω instead of the 1.2k Ω specified for R8 in the vco control nodes. Increasing the value of R7 requires that the gain setting of IC1 be reduced by adjustment of VR3 and, in relation to an initial setting at VR1 of -1.4V, the output of IC1 should be approximately +0.84V at the commencement of the setting-up procedure.

The setting-up of the filter proper is essentially concerned only with providing the optimum balance between extreme d.c. conditions arising in the ladder due to current variations. With a high resistance voltmeter directly monitoring the output of IC2, VR5 at zero, and with the audio inputs uncommitted, the frequency control (VR2) should be moved from one extreme to the other.

The meter readings at extreme settings of VR2 should be noted and VR4 adjusted to reduce the voltage swing at the output of IC2 to a minimum. It may require several iterative adjustments to get the best possible balance.

This adjustment is not too critical since the output of IC2 is capacitatively coupled although, if the filter is being programmed by a fairly rapid envelope, any significant change in d.c. level at the output of IC2 can be differentiated by the coupling capacitor and induce an unpleasant click on to the audio signal.

THE ENVELOPE SHAPER AND VOLTAGE CONTROLLED AMPLIFIER

Two distinct but very closely related circuits are covered by this section. The first is the envelope shaper which is of considerable importance in the scheme of the synthesiser since, by variation of just two controls, a whole range of differing characteristics can be imparted to an otherwise uninteresting sound.

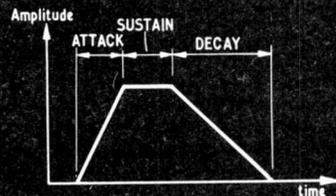


Fig. 2.6a. Typical Envelope Shaper output waveform showing the three variable parameters: attack, sustain and decay

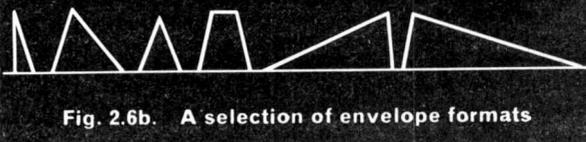


Fig. 2.6b. A selection of envelope formats

E.S./V.C.A.

PERFORMANCE

Attack	Variable 30ms to 4s
Decay	Variable 100ms to 16s
Attenuation Range	48 to 54dB (referred to peak output)
Nominal Input	400mV p-p
Nominal Output	1.25V p-p
Operating Voltage Range	±9V to ±7.5V

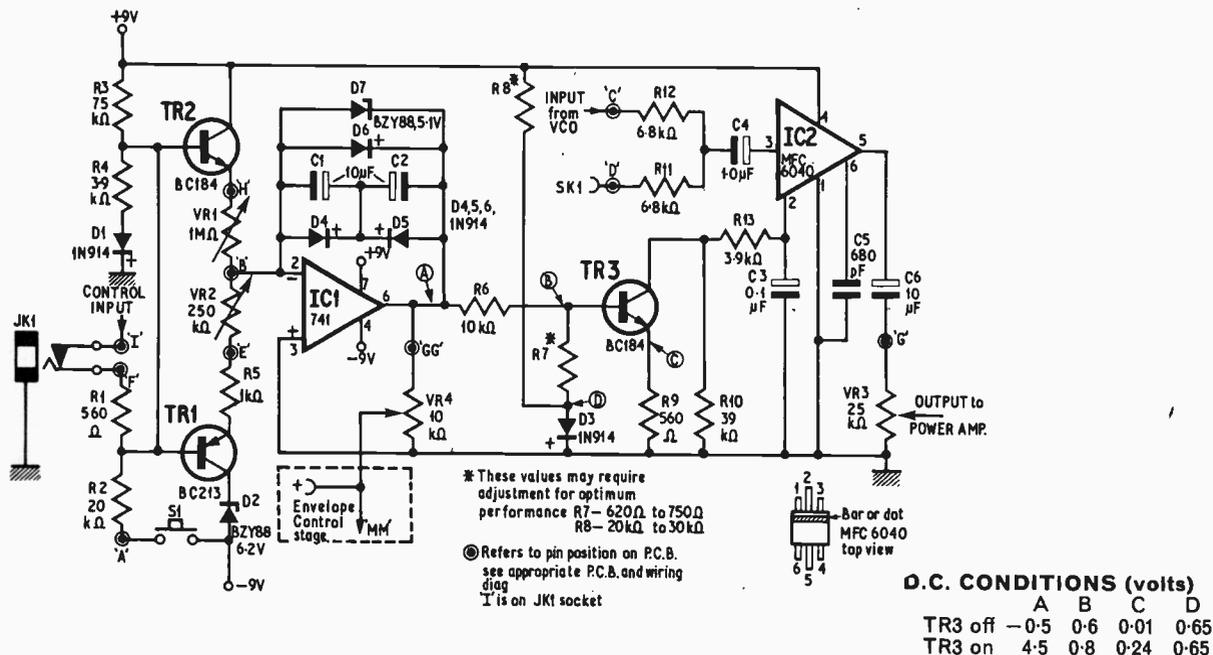


Fig. 2.7. Complete circuit diagram of the Envelope Shaper/Voltage Controlled Amplifier. Note that potentiometer VR4 is fitted only to ES/VCA 1 to provide positive and negative going control envelopes (see block diagram Fig. 1.1)

Essentially the envelope shaper generates a control voltage which, if plotted graphically, will be found to conform with the basic waveform illustrated in Fig. 2.6a. If this waveform is applied to the control input of a VCA the amplitude of the audio signal will vary proportionately, i.e. with the envelope at zero the output of the VCA will be at its minimum volume (in the P.E. Minisonic about 54dB below the peak output signal level).

The first excursion of the envelope shaper output voltage is known as the "attack" and is variable, in the P.E. Minisonic, between about 30 milliseconds and four seconds.

The flat topped portion shown in the illustration is known as the "sustain" and represents the period of time that the VCA output is maintained at maximum volume while, finally, the return to zero volts is known as the "decay" and is variable between about 100 milliseconds and 16 seconds. The period of sustain is determined entirely by the length of time that the envelope shaper trigger signal is present and no separate control is provided. Some idea of the kind of envelope formats possible with this arrangement is given by Fig. 2.6.

CIRCUIT DESCRIPTION

The complete circuit of the ES/VCA is shown in Fig. 2.7. IC1 is a linear integrator whose output voltage is bounded, in a negative direction, by D6 and

in a positive direction by D7. Thus the output voltage excursions of the envelope shaper range between -0.5V and +4.5V.

In the quiescent condition R3, R4 and D1 set the bias on TR1 and TR2 such that TR1 is off and TR2 is on. Current reaching the inverting input via TR2/VR1 charges C1/C2 and thus, with the aid of D6, holds the output of IC1 at -0.5V.

When a negative trigger signal is applied TR2 turns off and TR1 turns on. The charge on the integrating capacitors C1/C2 thus leaks away via VR2/TR1 and the integrator output ramps in a positive direction until it reaches the bounded value set by D7.

Triggering signals may be applied in one of three ways:

- (i) Through the manual push button S1.
- (ii) From an h.f. detector (to be described next month) operated from the stylus or external keyboard.
- (ii) From an external source via JK1, thereby overriding the connection to the h.f. detector.

The integrator output is linked through a divider network R6-R7 to the base of TR3 which, with the output of IC1 at -0.5V, is held at the point of conduction by means of a current supplied from the positive rail by means of R8. The table in Fig. 2.7 gives the "on" and "off" d.c. conditions which have proved to be ideal in practice.

COMPONENTS . . .

ENVELOPE SHAPER/V.C.A. (2 required)

Resistors

R1	560Ω
R2	20kΩ
R3	75kΩ
R4	3.9kΩ
R5	1kΩ
R6	10kΩ
R7	620Ω to 750Ω
R8	20kΩ to 36kΩ
R9	560Ω
R10	39kΩ
R11, R12	6.8kΩ (2 off)
R13	3.9kΩ

see text

All ±5% ¼W or ½W carbon

Potentiometers

VR1	1MΩ linear carbon
VR2	250kΩ linear carbon
VR3	25kΩ log carbon
VR4	10kΩ log sub. min. carbon (ES/VCA1 only)

Capacitors

C1, C2, C6	10μF 16V tantalum (3 off)
C3	0.1μF 35V tantalum
C4	1.0μF 35V tantalum
C5	680pF

Semiconductors

D1	1N914
D2	BZ88C6V2 6.2V 400mV Zener
D3-D6	1N914 (4 off)
D7	BZY88C5V1 5.1V Zener
TR1	BC213
TR1, TR3	BC184 (2 off)
IC1	Type 741 8-pin d.i.l.
IC2	Motorola MFC6040

Miscellaneous

JK1	3.5mm jack socket	SK1	2mm socket
S1	Miniature pushbutton		

SETTING-UP THE ENVELOPE SHAPER

Setting-up is restricted to the establishment of the bias conditions on TR3 as shown in the table of Fig. 2.7. With the output of IC1 at -0.5V, R8 should be adjusted so that a slight positive potential is apparent at the emitter of TR3. This indicates that the transistor is just beginning to conduct.

The actual d.c. level is fairly critical since too much conduction will restrict the gain/attenuation range of the vca whilst too little will result in a propagation delay between the occurrence of the envelope shaper trigger pulse and the appearance of the audio signal at the output of the vca.

After setting the bias the envelope shaper should be triggered manually and the button held down in order to check that the bias on the base of TR3 rises from +0.600V to +0.800V with the envelope at maximum level.

It is a good thing, at this time, to run a check on the vca output with an input signal of 0.4V peak-to-peak. With correct biasing on TR3 the vca output should be around 1.25V peak-to-peak.

It may be necessary to adjust the value of R7 in order to achieve the vca output signal specified and, if this is the case, it is well to recheck the biasing with the envelope in the off state and re-adjust R8 as necessary to establish the ideal minimum bias point.

No setting up is required on the vca as such except as explained above in relating input/output signal levels with the vca on.

ELECTRONIC ATTENUATOR

The vca, or to give it the proper title, electronic attenuator, is a purpose designed i.c. by Motorola.

The specification of the device is to provide an attenuation of 77dB and a gain of 13dB, relative to the input signal which should not exceed 500mV r.m.s., when the current sink from the control input (pin 2) is varied from minimum to maximum respectively.


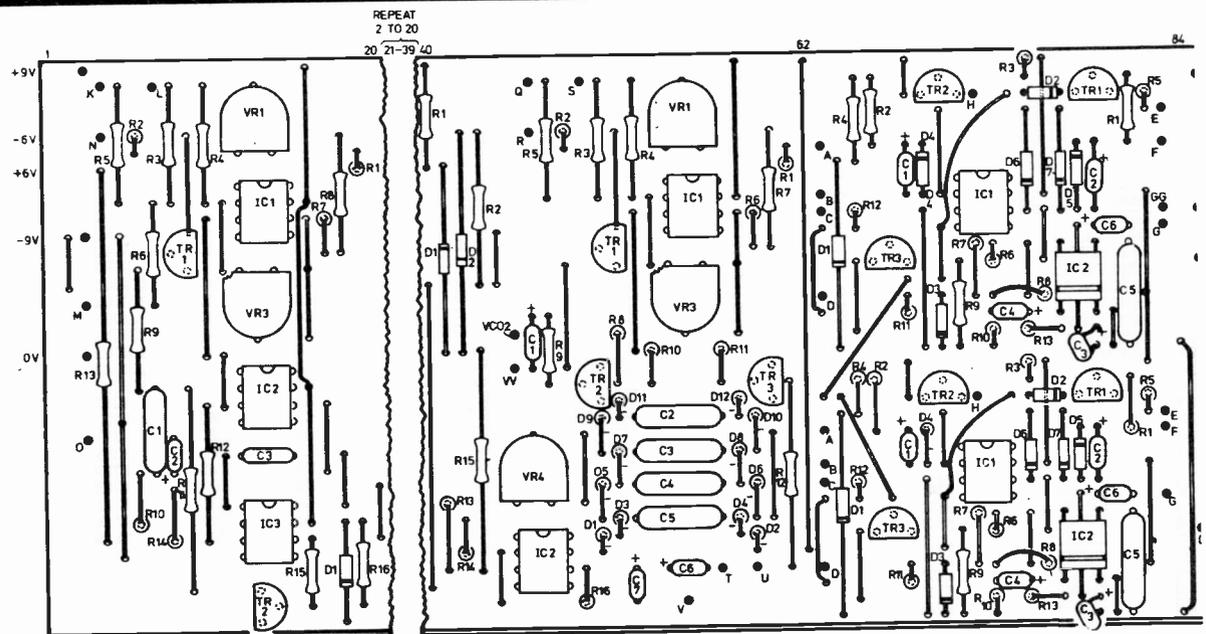


Fig. 2.8. Layout of the components on the Veroboard. Note that two identical VCO's are required side by side on the panel, only one is shown. Both Envelope Shapers are shown in full. Letters next to Veropins are for wiring to the front panel and correspond with those on the circuit diagrams

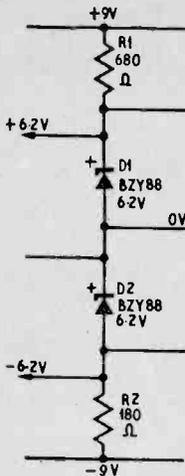

VOLTAGE REFERENCE

Resistors

R1 680Ω } ±5% ½W carbon
R2 180Ω }

Diodes

D1, D2 BZY88C6V2 6.2V Zener (2 off)

Fig. 2.9. Circuit of the voltage reference section giving ±6V

In the P.E. Minisonic the relatively low operating voltages result in a reduction of the overall attenuation/gain range to about 54dB which is sufficient for most practical purposes.

The current sink from pin 2 of IC2 is, in the off condition, restricted by the series combination of R10 and R13. As TR3 turns on it progressively short circuits R10 with the result that the current sink increases proportionately to a maximum which is limited by R13. It should be mentioned, of course, that the linear envelope of IC1 is converted into a negative exponential characteristic by TR3.

Although this is not ideal for an audio signal envelope, experience has shown that it is extremely difficult to differentiate subjectively between a negative exponential envelope and a positive exponential, or square law, envelope which is considered to give the best effect.

CONSTRUCTION

All the prototype circuits have been built in a number of alternative layouts and there appears to be no particular layout which gives rise to problems. The recommended Veroboard layout is shown in Fig. 2.8.


Also mounted on this section of Veroboard is the voltage reference section the circuit of which is shown in Fig. 2.9 (see photograph). This gives the stabilised ±6V rail for use in the vco's and vcf.

It is recommended that all circuits in the P.E. Minisonic be bench tested and adjusted before any attempt to link the circuit boards with the front panel.

Next month: More of the P.E. Minisonic electronics plus details for wiring and setting-up.

P.E. CCTV CAMERA

continued from page 1059

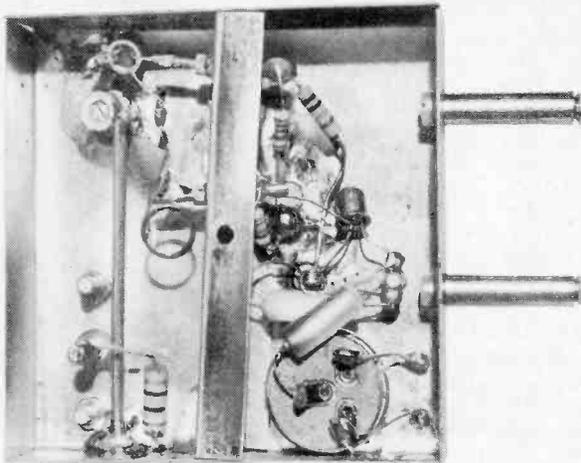

Interior view of Crofton unit

camera u.h.f. signal might be beating with a normal transmitted signal giving patterning on the screen. Loss of sync is usually due to overloading of the signal and if the tuner has too much gain R10 can be increased until satisfactory results are obtained.

ALTERNATIVE MODULATOR

From what has gone before it can be seen that this form of modulator with a separate tuner might deter some constructors particularly if their involvement has never extended to u.h.f. It is for this reason that a commercial kit, the Crofton modulator, is recommended as an alternative, its obvious attractions being simplicity and small completed size.

The circuit for this is shown in Fig. 4.5 for which we are indebted to Crofton Electronics.

The kit comes complete with detailed building instructions. Numbered packs of piece parts with contents detailed means that instructions can be ticked off in the manual as construction proceeds until the unit is completed.

A step-by-step testing procedure is also included.

SCAN COIL CHANGES

Since the publication of the camera series a run on the specified EMI scan/focus coil assembly and a surprise discontinuation from the contracted manufacturer has meant finding a new coil assembly.

The author has found that the Japanese KV-13 assembly was not only a suitable substitute but provided an improvement in picture quality. Features include an automatic vidicon target connection and vidicon lens focusing by the turn of a small screw.

Both the coils and fitting data can be obtained from EMI, 243 Blythe Road, Hayes, Middlesex. The price is £14 plus VAT.

The only electrical modifications to be made is in the focus coil current supply. For this R50 and C31 in Fig. 2.10 are not required. The supply line input is +15V and should be taken from the Regulator circuit of Fig. 2.8.

Note that in the Components List for Part 1, R39 is 2.7kΩ, R8 - 4.7kΩ and R42 - 390Ω. These values are correctly shown in the circuits.



NEXT MONTH...

Quality need not cost the earth with
the **PE ORION**

HI-FI STEREO AMPLIFIER

From the same stable as the now-famous P.E. Gemini, comes the P.E. Orion. A medium power stereo amplifier contained in a compact cabinet offering a high performance for a modest outlay. The 20 + 20 watt output will satisfy almost all domestic requirements.

- ★ Output: 20 + 20W into 8 ohms
- ★ Distortion less than 0.1%
- ★ Excellent transient response
- ★ Will drive electrostatic loudspeakers
- ★ Will accept inputs from radio, tape and disc



LIGHT PIPE

Flexible decorative effect for the home, discotheque or shop. Can be shaped to almost any desired form.

DIGITAL LEAF

Automatic moisture control for greenhouse plants.

Controls a mist watering system so that your plants get just the right amount of water.

PRACTICAL

ELECTRONICS

JANUARY 1975 ISSUE ON SALE DECEMBER 13, 1974

I.C.

PULSE GENERATOR

BY M.E. THEAKER

DURING the course of work with logic circuits it has been found useful to have a source of suitable digital waveforms to hand. However, the popular sine/square-wave generator is not ideal for this task as its signals are not compatible with the two most commonly used logic families, TTL (transistor-transistor logic) and DTL (diode-transistor logic). Whilst complex signal generators, which provide suitable signals, are available at great expense, using one of these for most amateur purposes is rather like using a sledgehammer to crack a nut.

For this reason a simple and compact source of various digital waveforms was developed. It will provide a mechanically switchable output at either of the two logic levels corresponding to 0 and 1, a continuous train of square-wave pulses variable in frequency from 10MHz down to a pulse every few seconds, a monostable multivibrator for providing single pulses of any given duration from seconds to microseconds, a Schmitt trigger circuit and, lastly, a lamp indicator circuit to show whether the logic state of a circuit is high or low (1 or 0).

LOGIC LEVELS

Some basic rules are common not only to 74 series but also to most other TTL and DTL logic families.

First, the signal level should never exceed 5.5V, or be less than -0.6V. It should occupy one of two

states, "0" which is typically 0.2V (maximum 0.4V), and "1" which is typically 3.0V (minimum 2.4V).

The next important requirement is that the time taken to go from the low state (0) to the high state (1), which is known as the rise time, or the reverse which is known as the fall time, should not exceed one microsecond ($1\mu\text{s}$).

The reason for this is that both TTL and DTL are saturated logic circuits which operate in one of two stable states corresponding to 1 and 0. As they switch from one state to the other they pass through an unstable linear zone where the circuit can act as an amplifier or an oscillator.

If the signal input to a logic circuit has an unduly long rise or fall time, oscillation of the circuit will occur and is highly undesirable. If the rise and fall times are less than $1\mu\text{s}$ for gates (150ns for flip-flops), then spurious oscillation will not occur.

THE CIRCUITS

The first requirement for testing logic circuits is to be able to provide a steady output corresponding to logic state 1 or 0 and to be able to switch between these two states at will. It might be thought that a simple switch connected to either 0.2V or 3V as shown in Fig. 1a would suffice, but this circuit would not give a single transition from one state to the other, instead it gives rise to a number of pulses due to contact bounce as at Fig. 1b.

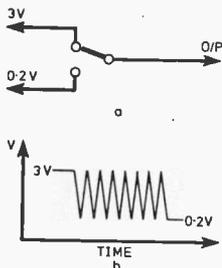


Fig. 1. Illustrating the effect of contact "bounce" when using a normal switch

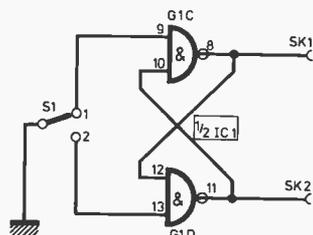


Fig. 2. Eliminating switch bounce using half an SN7400N

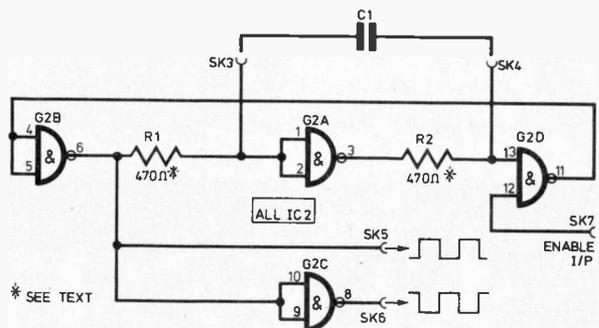


Fig. 3. The frequency of operation of this free-running multivibrator is selected using various values for C1

SWITCHED LOGIC LEVELS

In order to overcome contact bounce problems the switch can be used in conjunction with a flip-flop, which is made up from two 2-input NAND gates as shown in Fig. 2.

With the switch shorting S1.1 to ground one input to gate G1C is low (0 state). As S1.2 is not grounded it is high (1 state). Thus the output at SK2, gate G1D is low. Since both inputs to gate G1C are low its output at SK1 is high.

When the switch is moved to short S1.2 to ground, G1D output goes high. Since S1.1 is no longer connected to ground, it is now high and G1C output goes low. The outputs at SK1 and SK2 are now reversed and the transition is free from contact bounce. Returning the switch to position S1.1 restores the circuit to its original condition once again without contact bounce.

FREE-RUNNING MULTIVIBRATOR

Besides being able to switch at will from one logic level to the other, it is also useful to have a continuous source of pulses variable in speed from very slow to very fast. A suitable circuit is shown in Fig. 3 and consists of four 2-input NAND gates G2A, G2B, G2C and G2D. R1 and R2 affect the symmetry of the waveform and are nominally 470Ω. When they are equal in value the output waveform is nominally square, i.e. the waveform has a 1:1 mark/space ratio. The repetition rate or frequency of the signal is determined by capacitor C1.

The 2-input NAND gates G2A, G2B and G2C, are connected with their two inputs tied together as inverters.

To explain the operation of the circuit, consider the moment when the output of gate G2B goes from 0 to 1. Gate G2A inverts this signal and its output goes from 1 to 0.

The charge on C1 cannot change instantaneously and so the input to gate G2D also goes to 1 and the output goes to 0.

Now capacitor C1 begins to charge through R2 since G2A input is high whilst its output is at 0. As the capacitor charges so the voltage at pin 13 falls until it is sufficiently low to force the output of gate G2D into the high state, which in turn forces the output of gate G2B to go low, thereby commencing the second half of the cycle.

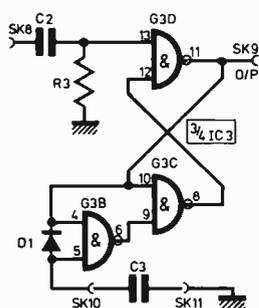


Fig. 4. A three-gate monostable provides a source of single pulses with adjustable duration

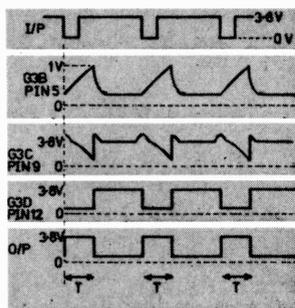


Fig. 5. The waveforms appearing at points in the circuit of Fig. 4

The input to gate G2A now being low forces its output high. Once again the charge on the capacitor cannot change instantaneously and so pin 13 is also low. Capacitor C1 now charges through R2 until the voltage at pin 13 is sufficiently high for gate G2D to change state and its output to go low, causing the output of gate G2B to go high, completing the cycle and starting another.

The process continues indefinitely as long as input to G2D at pin 12 is high. As soon as this input is taken low by an external circuit or is connected to earth, it stops the cycle. So pin 12 can be used to switch the oscillator on and off or, in other words, to "gate" or enable the oscillator. Gate G2C is used merely as an inverter and provides a complementary output from socket SK6.

Values of capacitance C1 for various frequencies are given in Table 1.

MONOSTABLE MULTIVIBRATOR

The third requirement is for a source of single pulses of adjustable duration and such a circuit is shown in Fig. 4. This forms a three-gate one-shot (or monostable) multivibrator circuit.

Varying C3 alters the output pulse duration and approximate values of capacitance for various pulse durations are given in Table 2.

A negative-going edge at the input produces a positive pulse at the output. The various waveforms of the circuit are shown in Fig. 5.

TABLE 1

C1	Period	Frequency
None	60 ns	16.7 MHz
47 pF	120 "	8.33 "
100 "	170 "	5.88 "
220 "	280 "	3.57 "
470 "	515 "	1.94 "
1 nF	1 μs	1.0 "
2.2 "	2.1 "	476 kHz
4.7 "	4.3 "	233 "
10 "	8.1 "	123 "
22 "	19 "	53 "
47 "	37 "	27 "
100 "	70 "	14 "
220 "	190 "	5.3 "
470 "	430 "	2.3 "
1 μF	909 "	1.1 "
100 "	91 ms	11 Hz

TABLE 2

C3	Pulse width
None	180 ns
47 pF	230 "
100 "	300 "
220 "	430 "
470 "	900 "
1 nF	1.5 μs
2.2 "	3.0 "
4.7 "	5.8 "
10 "	12 "
22 "	25 "
47 "	50 "
100 "	110 "
220 "	260 "
470 "	680 "
1 μF	1.3 ms
10 "	2.3 ms



SCHMITT TRIGGER

As mentioned earlier, TTL circuits require a pulse waveform with a fast rise time. If this requirement is not met, positive feedback between the output and input of the circuits will give rise to high frequency oscillation.

In order to be able to feed signals with slow rise times such as sinusoidal waveforms into TTL circuits a Schmitt trigger is incorporated as shown in Fig. 6. Positive feedback is applied via R5 in order that the

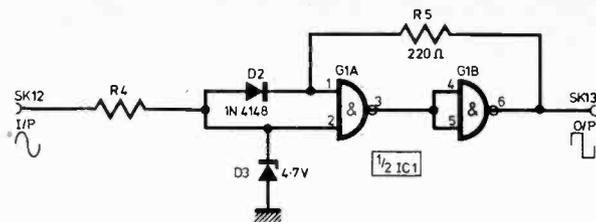


Fig. 6. A simple Schmitt trigger circuit using half of a SN7400N

output switches swiftly from one state to the other when the threshold is reached. The Zener diode D3 protects the circuit from overvoltage and the resistor R4 protects D3 from exceeding its maximum power dissipation. With R4 equal to 330Ω, inputs of up to 20V r.m.s. can be accommodated and the circuit will trigger on 2.8V r.m.s. With R4 equal to 100Ω, the maximum input is 6V r.m.s. and the minimum input 2V r.m.s.

LAMP INDICATOR

In order to check whether a circuit under test is at high or low level a lamp indicator circuit is included. The circuit is shown in Fig. 7 and consists of a transistor, TR1, a lamp LP1 and a base resistor R6 to limit the input current to the transistor.

COMPONENTS . . .

Resistors

- R1 470Ω
- R2 470Ω
- R3 22kΩ
- R4 330Ω
- R5 220Ω
- R6 470Ω or 1kΩ (see text)
- R7 180Ω
- All ½W, 5%

Capacitors

- C1 68pF Polystyrene (see Table 1)
- C2 150pF "
- C3 68pF polystyrene (internal)
(internal see Table 2)

Semiconductors

- IC1 SN7400N or equivalent
- IC2 " "
- IC3 " "
- D1 1N4148
- D2 1N4148
- D3 4.7V, 400mW Zener
- TR1 BFY51 or similar

Miscellaneous

- LP1 Miniature 6V, 0.36W Lilliput lamp and holder
(Or i.e.d.)
- S1 Miniature toggle switch, SPC0
- SK1 to 16 16 single-pole miniature 1mm sockets,
colour to suit

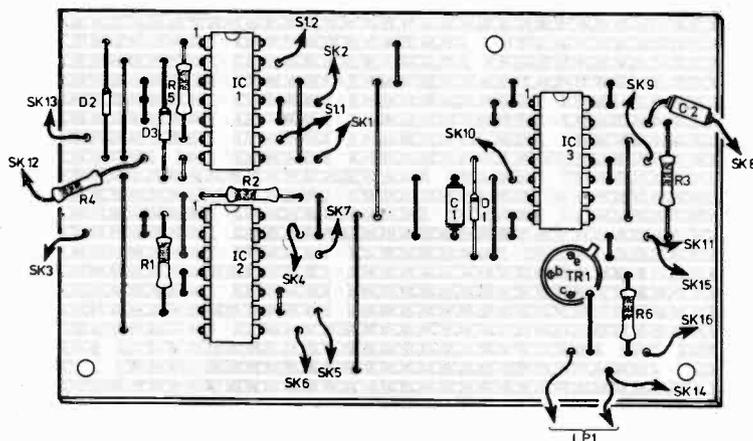


Fig. 9. Veroboard and component layout for the pulse generator

Single-pole miniature 1mm plugs in colour and quantity to suit for leads and supply lines
Veroboard, 0.1in pitch, 3.4in × 2.0in. Veropins.
Case (Prototype used 2 × 2oz tobacco tins),
wire, solder etc.

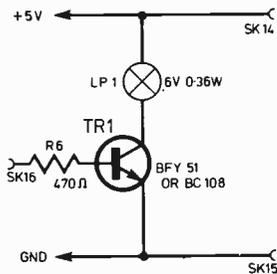


Fig. 7. Lamp indicator using a filament lamp. Note that the power supply is fed to sockets 14 (+5V) and 15 (0V) from an external battery or p.s.u.

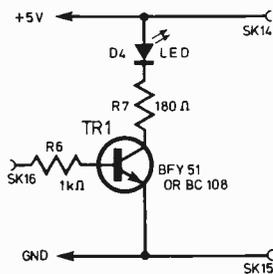


Fig. 8. Indicator using an l.e.d.


When logic 0 is applied at SK16 the transistor is cut off and no current passes through the lamp, but when logic 1 is applied the transistor is switched on and current passes through the lamp which lights.

A further version of the lamp circuit using an l.e.d. is shown in Fig. 8.

CONSTRUCTION

The circuits are all constructed on one piece of 0.1in pitch Veroboard, 3.4in by 2.0in. Whilst the layout is not critical leads should be kept as short as possible and the suggested layout of Fig. 9 works well.

The easiest way of constructing such a board is first to cut it to size, then drill the three 6B.A. clearance holes required for mounting the board in the case. Next the pins should be inserted and then the cuts in the copper strips should be made. Following this, the wire links should be inserted and soldered in place, followed by the discrete components and finally the transistor and three integrated circuits.

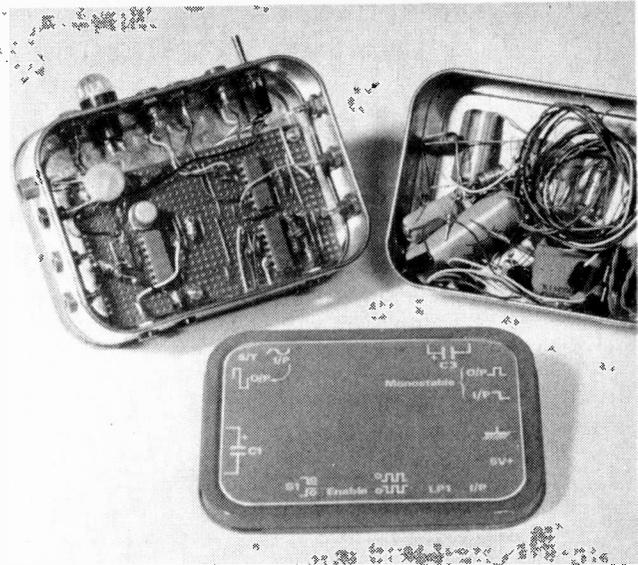

CASE

The case for the prototype pulse generator was made from a standard two-ounce tobacco tin. Three 6B.A. screws approximately half an inch long should be screwed through the bottom and Araldited in place to accept the Veroboard. The top of a further tin can be rubbed down to remove the paint from the top rim and then Araldited underneath the bottom of the case and allowed 24 hours to set.

Bonding a lid underneath the case prevents the heads of the 6B.A. screws (which are now hidden) from scratching other equipment or furniture and means the generator may be stacked on to a second tin containing the leads and spare timing capacitors.

When the Araldite has set, the case should be painted and the sockets labelled as shown in the photograph. "Letraset" was used for the prototype and then varnished, which provides a very durable finish.

The capacitors used for adjusting the frequency of the astable multivibrator and the pulse width of the monostable multivibrator should have Veroboard (or similar) pins soldered to their leads for connection into the sockets provided on the case. A number of leads should be made up, some with a plug on one end for connection to external circuits, and some with plugs on both ends for interconnecting the sockets of the generator. These leads should preferably not exceed 1ft length for reliable operation.

The 1mm sockets used here are probably the only ones small enough to use in a tobacco tin. However, if a larger unit is used different output arrangements could be adopted. If component switching and other refinements are added care will be required over length of leads and interaction between signals. ★

Now two fascinating ways to enjoy saving money!

NEW! Sinclair Scientific kit **£19.95** (INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range – features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £32.35 (including VAT).

And as a kit it costs under £20!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle *directly*

- sin and arcsin,
- cos and arccos,
- tan and arctan,
- automatic squaring and doubling,
- log₁₀, antilog₁₀, giving quick access to x^Y (including square and other roots),
- plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer – they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

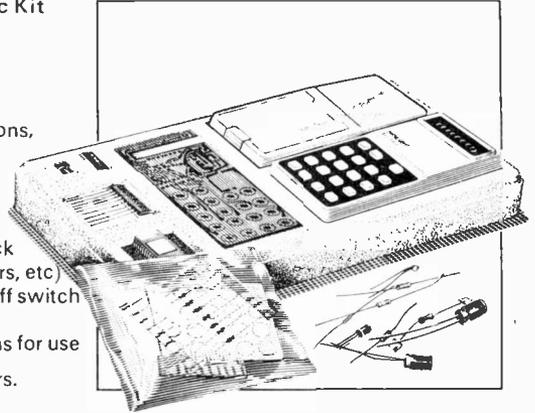

Features of the Sinclair Scientific



- **12 functions on simple keyboard**
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.

- **Scientific notation**
Display shows 5-digit mantissa, 2-digit exponent, both signable.

- **200-decade range**
10⁻⁹⁹ to 10⁺⁹⁹.

- **Reverse Polish logic** Post-fixed operators allow chain calculations of unlimited length – eliminate need for an = button.

- **25-hour battery life**
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

- **Genuinely pocketable**
4 1/3" x 2" x 11/16". Weight 4 oz. Attractively styled in grey, blue and white.

Sinclair Cambridge kit

Now only
£14.95
 (INC. VAT)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below – then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific

Price in kit form £19.95 inc. VAT.


Price built £32.35 inc. VAT.

Cambridge

Price in kit form £14.95 inc. VAT.

Price built £21.55 inc. VAT.

Features of the Sinclair Cambridge

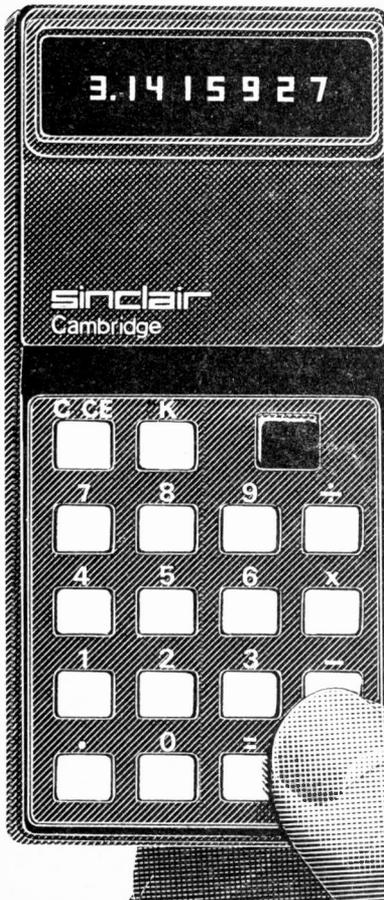

- Uniquely handy package. 4 1/3" x 2" x 11/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, x, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,
 FREEPOST St Ives,
 Huntingdon, Cambs. PE17 4BR

- Please send me
- Sinclair Scientific kit at £19.95
 - Sinclair Scientific built at £32.35
 - Sinclair Cambridge kit at £14.95
 - Sinclair Cambridge built at £21.55

All prices include 8% VAT.

*I enclose a cheque for £....., made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/ Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--

*Delete as required.

Signed _____

Name _____

Address _____

Please print. FREEPOST – no stamp needed.

PE/12/74

sinclair
 Sinclair Radionics Ltd,
 FREEPOST St. Ives,
 Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

NEW DEVICES ... APPLICATIONS

PHASE LOCKED LOOP FOR HIGH PERFORMANCE F.M. RECEIVERS

THE SIGNETICS International Corporation have recently introduced a new type of phase locked loop integrated circuit known as the NE563. This device employs new techniques to provide an extremely good performance in high quality f.m. receivers.

PERFORMANCE

The NE563 can provide an audio output signal having a total harmonic distortion of less than 0.5 per cent when fed with a 10.7MHz input signal having a 75kHz deviation at a 1kHz modulation frequency. This distortion level is lower than that of any other f.m. demodulator circuit known to the writer.

However, the NE563 not only excels in its low distortion, the a.m. rejection is 70db, far greater than that of most other circuits which seldom exceed 50db. The signal-to-noise ratio of 70db also illustrates the performance of this new device.

Although it provides such good performance figures, the NE563 is also convenient to use, since it functions as a complete i.f. strip without any coils whatsoever.

It also contains a built-in limiter circuit which itself has a gain of up to 60db.

POWER SUPPLY

The NE563 operates from power supply voltages in the range 10V to 15V, this being less than that required by the earlier NE560, 561 and 562 series. The supply current is about 35mA. The NE563 is more sensitive than these earlier devices, having an input sensitivity of typically 5 μ V (maximum 10 μ V) for a 30db signal-to-noise ratio.

A further added bonus provided by the 563 is the high audio output level of 500mV r.m.s. (which may be compared with the typical value of 60mV obtainable from the NE560 series of devices). The maximum load which can be applied to the audio output is 2K Ω .

The NE563 also incorporates facilities for inter-station muting and for the operation of a signal strength meter.

The 563 device is encapsulated in a 16 pin dual-in-line case with the connections shown in Fig. 1.

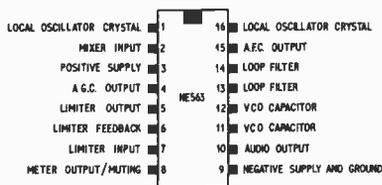


Fig. 1. The connections of the NE563 device

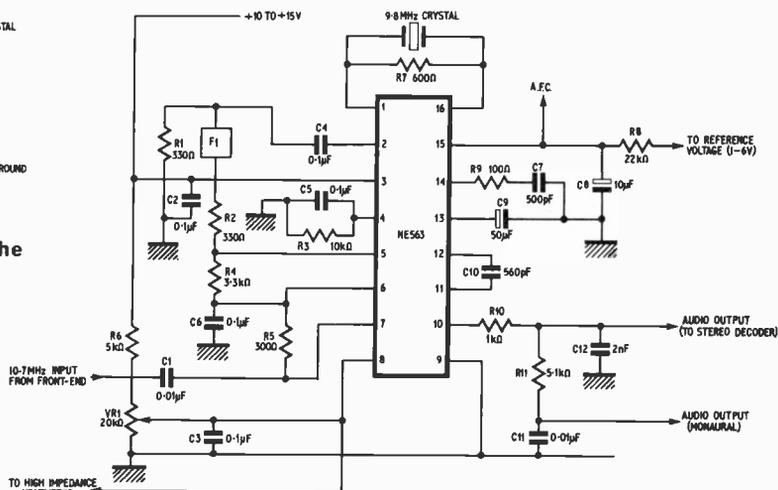


Fig. 2. Recommended circuit for the NE563. (R11 has been reduced from the value of 7.5k Ω suitable for the 75 μ s pre-emphasis used in the U.S.A.)

CIRCUIT OPERATION

The basic circuit recommended by the manufacturers of the 563 is shown in Fig. 2. The excellent performance is, of course, related to the techniques employed in this circuit.

A 10.7MHz signal from the front-end unit is capacitively coupled into the limiter input at pin 7 of the device. The limited output signal from pin 5 is passed through the 10.7MHz miniature ceramic filter marked F1 into the mixer input at pin 2.

The two resistors R1 and R2 on each side of the filter F1 are required for matching the filter impedance to that of the circuit. If they are omitted, the band-pass characteristics of the filter will be impaired.

The 10.7MHz signal entering the device at pin 2 is mixed with a 9.8MHz local oscillator signal generated by the crystal controlled oscillator connected in the circuit of pins 1 and 16. A difference frequency of 0.9MHz is thereby generated.

Table 1: Showing the typical readings of a high resistance voltmeter connected to pin 8 at various input signal levels

Input	Meter Reading (V)
1 μ V	0.3
10 μ V	0.35
50 μ V	0.6
100 μ V	0.85
500 μ V	1.4
1mV	1.6
5mV	2.3
10mV	2.75
50mV	3.6
100mV	4.0

The centre frequency of the voltage controlled oscillator of the phase locked loop is determined by the value of the capacitor C10 connected between pins 11 and 12 of the device; this capacitor is selected to provide a free-running or centre frequency of about 0.9MHz. The loop therefore becomes locked to the frequency of the difference signal.

The error signal voltage which keeps the loop in lock is the required audio output. The audio signal is filtered by R10 and C12 (time constant 2 μ s) to reduce the amplitude of any radio frequencies present, whilst leaving the high frequency components of the stereo signal virtually unaffected.

The audio signal is also filtered by R11 and C11 which provide the required de-emphasis of 50 μ s for monaural signals.

The 563 provides an automatic frequency control output signal from pin 15 which may be fed to the front end unit. A voltage is provided by pin 8 which can be fed to a high resistance voltmeter to provide an indication of the signal level at pin 7. Typical values of the meter reading for various input voltages are shown in the table.

CONCLUSION

The use of this new device should lead to both an improvement in the performance of high quality f.m. receivers and also a simplification in their circuitry. Although a 9.8MHz crystal is required for use with the NE563, the circuit is extremely simple and requires no coils or alignment. It seems to be equally suitable for use by the manufacturer of high quality commercial receivers and by the amateur constructor.

Approval of Ceefax and Oracle experiments

THE Home Secretary has approved the introduction for a two-year experimental period, of the broadcasting of live information on television by means of the techniques known as CEEFAX (BBC) and ORACLE (IBA).

The purpose of the experiment, whereby those in possession of the necessary receivers will be able to receive printed information over a wide range of topics on their television screen, is to enable an assessment to be made of the demand for the service, to determine what form it should take and to estimate the scope for the manufacture of the equipment. It is assumed that the Annan Committee on the Future of Broadcasting will consider the techniques involved against its review of broadcasting policy as a whole.

Oracle demonstration

JUST prior to the Home Secretary's approval a "live" demonstration of the "Oracle" system was staged at Crawley Court near Winchester, headquarters of IBA's engineering division. There direct feeds from ITN, the Meteorological Office and the A.A. provided information which could be immediately up-dated. The display material was coloured with upper and lower case letters, included graphics and whole words could be flashed to rivet the attention of the viewer to an important item.

"Oracle," an acronym for Optional Reception of Announcements by Coded Line Electronics, can provide such presented information at the touch of a button.

This "broadcasting of the written word" is obtained by inserting a digital signal during part of the field blanking interval of a 625 line waveform. Since the details of the signal coding differed for the experimental BBC and IBA systems it has been necessary to draw up a common data broadcast standard which has now been ratified.

Up to 100 different pages of data, each page comprising up to 150 words or diagram could be transmitted continuously. Viewers having the necessary decoder (which will be integral to future generation receivers) will have immediate access to any of the pages being transmitted on the channel tuned. This can be displayed on a neutral background or superimposed on the television picture.

Whilst a regular transmission of live broadcasts by the BBC was started on September 23rd, the IBA experimental service is not expected to commence till next year.



-68°C to +175°C THERMOMETER / CONTROLLER

By J. N. JONES


THE relationship between the forward voltage drop of a diode and the temperature of the surroundings often causes problems in electronic circuitry. The present project makes use of this drawback to measure temperature.

The circuits described are simple, easily constructed and linear. The diode used is the very common 1N914 (equiv. 1S914) which can be obtained for as little as 3p and, since it is physically small, can be used to sense the temperature of small as well as large objects. Also, the size leads to a fast response rate.

Silicon diodes have one limitation, the range extends only from -65°C up to +175°C but this is wide enough for most applications and the instrument can be calibrated anywhere in this range.

APPLICATIONS

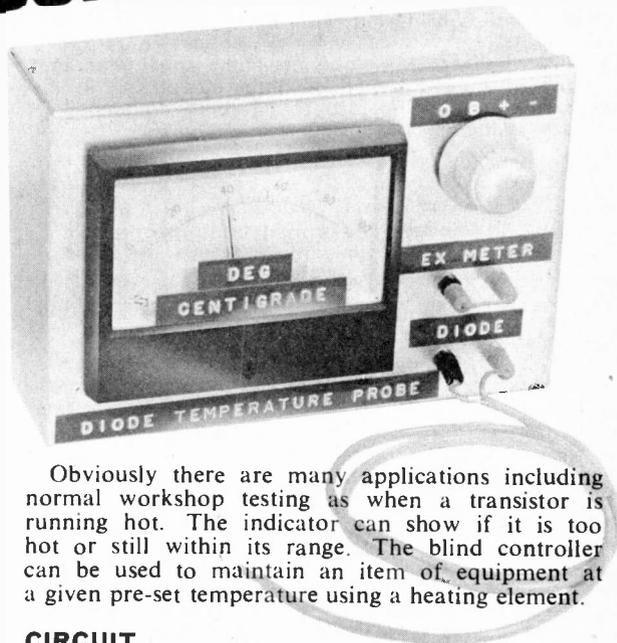The article describes four basic circuits, a simple indicator in detail and an indicator/controller with set-point display, a blind (non-indicating) controller and a switched range version of the first indicator. The first mentioned is taken to the prototype stage in detail whilst the others are described in basis only.



Obviously there are many applications including normal workshop testing as when a transistor is running hot. The indicator can show if it is too hot or still within its range. The blind controller can be used to maintain an item of equipment at a given pre-set temperature using a heating element.

CIRCUIT

A basic indicator circuit is shown in Fig. 1. Here a stable reference voltage for the diode probe and operational amplifier inputs is provided by an integrated circuit IC1 which is in fact a 723 which also carries an amplifier used elsewhere in the circuit (IC3).

The diode probe is connected in the feedback loop of IC2, connected to the inverting input. By careful adjustment of the potentiometer VR1, the bias provided to the non-inverting input of IC2 is held to about 600mV below the V_{ref} (Pin 6) provided by IC1. (Actually the diode D1 forward voltage drop at 0°C or whatever temperature zero meter current represents.)

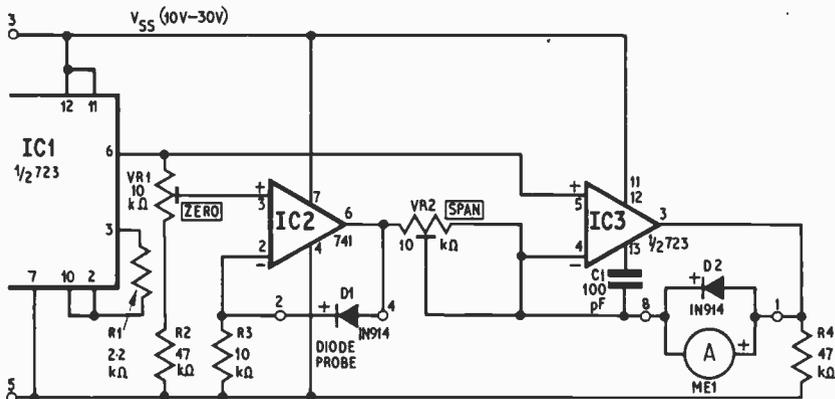


Fig. 1. Circuit diagram of the heart of the indicating diode thermometer showing the use of integrated circuits to provide sophisticated circuit functions in a very simple manner

IC2 works in the inverting mode feeding current through D1 to R3 so that the inverting input is held at the same potential as the non-inverting. The output is thus one diode drop greater than the bias voltage provided by VR1.

The sensitivity of a silicon diode is about $-2\text{mV}/\text{degree C}$, thus the p.d. is in fact about 600mV at 0°C and 400mV at 100°C . IC2 output thus changes from V_{ref} at 0°C (or zero meter current temperature) to approximately $V_{\text{ref}} - 200\text{mV}$ at 100°C .

Amplifier IC3 also operates in the inverting mode, passing current through the indicator ME1 to maintain the two input pins at the same potential. As the input impedance of IC3 is high all the meter current passes through VR2. Thus one end of VR2 is held at V_{ref} by IC3 whilst the other varies from V_{ref} to $V_{\text{ref}} - 200\text{mV}$ (at 100°C).

Thus VR2 value determines the current per unit temperature flowing in ME1. A $100\mu\text{A}$ indicator, to correspond to 0°C to 100°C requires VR2 of about $2\text{k}\Omega$ and thus a $10\text{k}\Omega$ potentiometer is suitable.

VOLTAGE REGULATOR

A circuit of this type, to retain accuracy, needs to be supplied with reasonably constant voltage at the probe and other operational amplifier inputs. Hence the use of the 723 regulator chip. These can be obtained for about 57p and contain the required 7V reference source and an amplifier which is useful.

In the circuit, R1 provides short circuit protection for the amplifier section and C1 is necessary for frequency compensation.

The 741 amplifier chip was selected for IC2 and either the 8 or 14-pin d.i.l. packages may be used in the Veroboard layout of Fig. 2. This device has its own internal frequency compensation.

R4 is required if negative (below 0°C) temperatures are to be investigated and for setting to zero since IC3 can only drive the V_{ref} in one direction.

METER PROTECTION

Since removal of the diode probe with the instrument switched on will cause heavy meter current, apart from any other reasons, meter protection is a good idea. Hence diode D2 which protects the meter against large overloads but does not affect normal readings.

In addition, the 723 amplifier, IC3, has programmable short circuit protection which can be selected to lie close to the sum of meter f.s.d. current and R4 current. Programming is by selection of R1 from the following equation:

$$I \approx \frac{0.65\text{V}}{R1}$$

As R4 is selected to sink enough current to give reverse f.s.d. on the meter then I must equal (current through R4 plus the current through the meter) $\times 1.5$. The factor 1.5 is to ensure that normal IC3 currents do not enter the range where

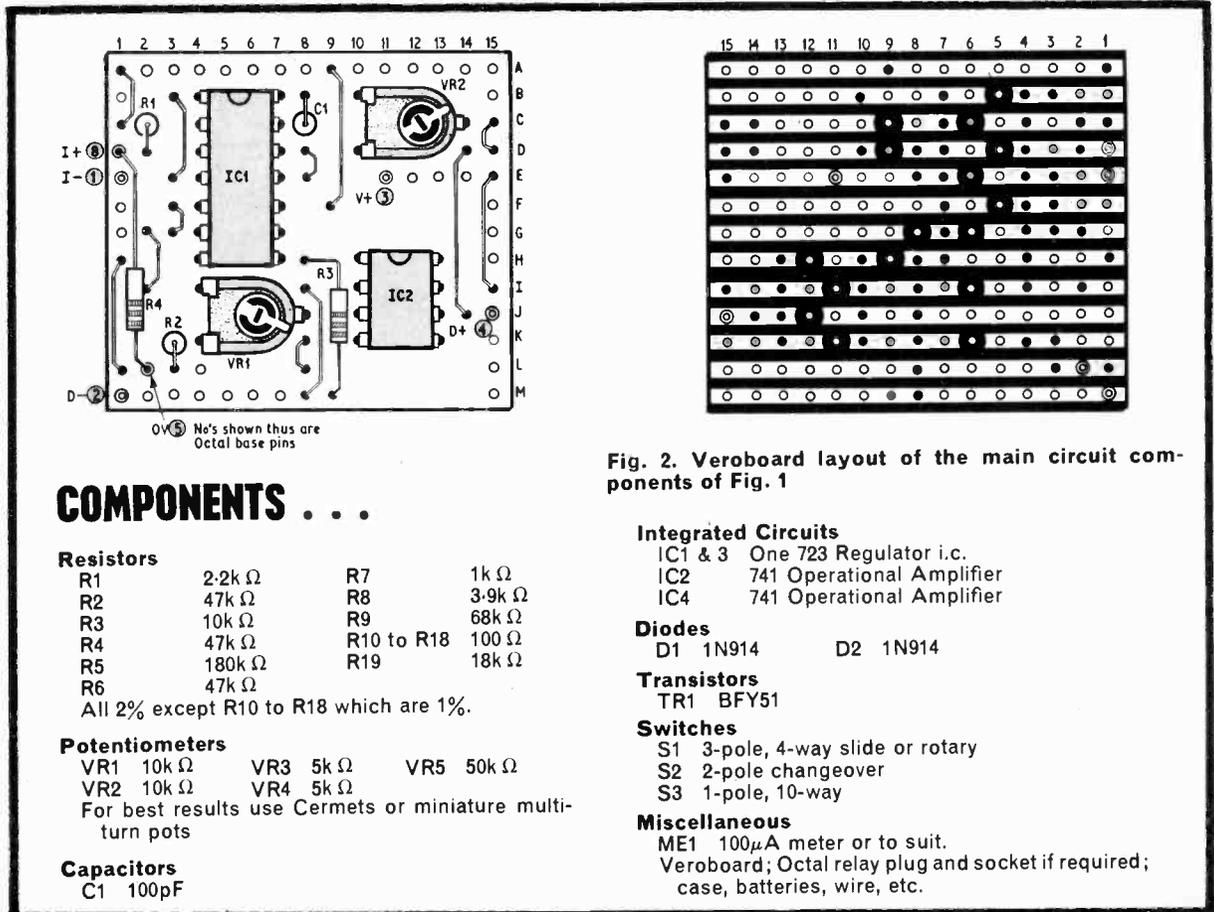


Fig. 2. Veroboard layout of the main circuit components of Fig. 1

COMPONENTS . . .

Resistors

R1	2.2k Ω	R7	1k Ω
R2	47k Ω	R8	3.9k Ω
R3	10k Ω	R9	68k Ω
R4	47k Ω	R10 to R18	100 Ω
R5	180k Ω	R19	18k Ω
R6	47k Ω		

All 2% except R10 to R18 which are 1%.

Potentiometers

VR1	10k Ω	VR3	5k Ω	VR5	50k Ω
VR2	10k Ω	VR4	5k Ω		

For best results use Cermets or miniature multi-turn pots

Capacitors

C1	100pF
----	-------

Integrated Circuits

IC1 & 3	One 723 Regulator i.c.
IC2	741 Operational Amplifier
IC4	741 Operational Amplifier

Diodes

D1	1N914	D2	1N914
----	-------	----	-------

Transistors

TR1	BFY51
-----	-------

Switches

S1	3-pole, 4-way slide or rotary
S2	2-pole changeover
S3	1-pole, 10-way

Miscellaneous

ME1 100 μA meter or to suit.
Veroboard; Octal relay plug and socket if required; case, batteries, wire, etc.

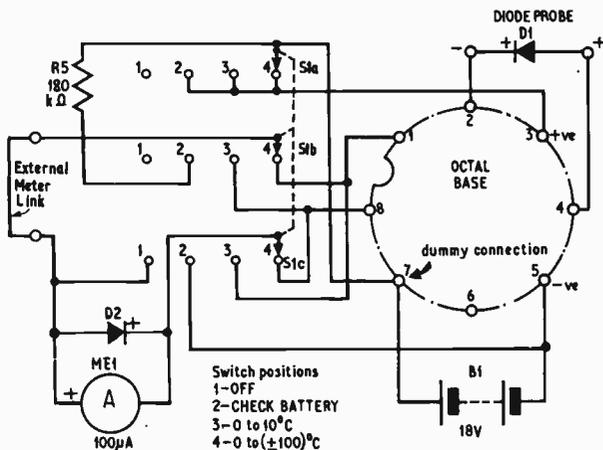


Fig. 3. The assembled circuit of the indicating instrument developed from the basis of Fig. 1

short circuit protection begins as scale non-linearity could result.

PROTOTYPE CONSTRUCTION


For convenience and neatness the original was made up in an octal-based relay case and the pin numbers used are shown in both Fig. 1 and Fig. 3. These are not firm and can be modified. Pin 7 for example was used to retain the battery lead for convenience but is not connected to the Veroboard.

SWITCHING

The 3-pole, 4-way switch S1 of Fig. 3 provides on/off, battery check, 0 to $\pm 100^\circ\text{C}$ (in fact only to -60°C). In the off position the meter is shorted out for added protection.

In the battery check position the 180k Ω resistor R5 converts ME1 to an approximately 18V voltmeter. This is effected with the load connected so a proper test is indeed performed.

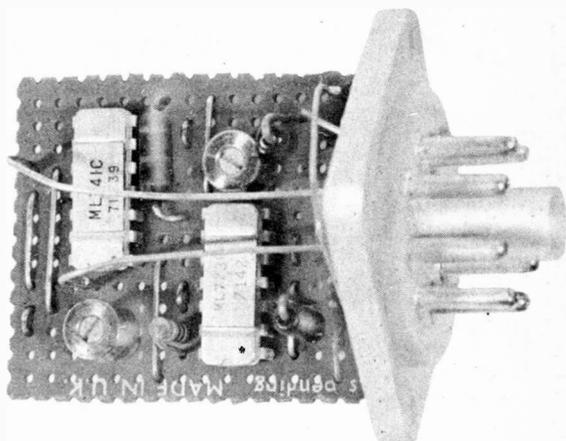In fact the instrument can function with battery voltage as low as 10V with very little loss in accuracy.



An assembled circuit board mounted on its octal plug carrier and with the cover removed

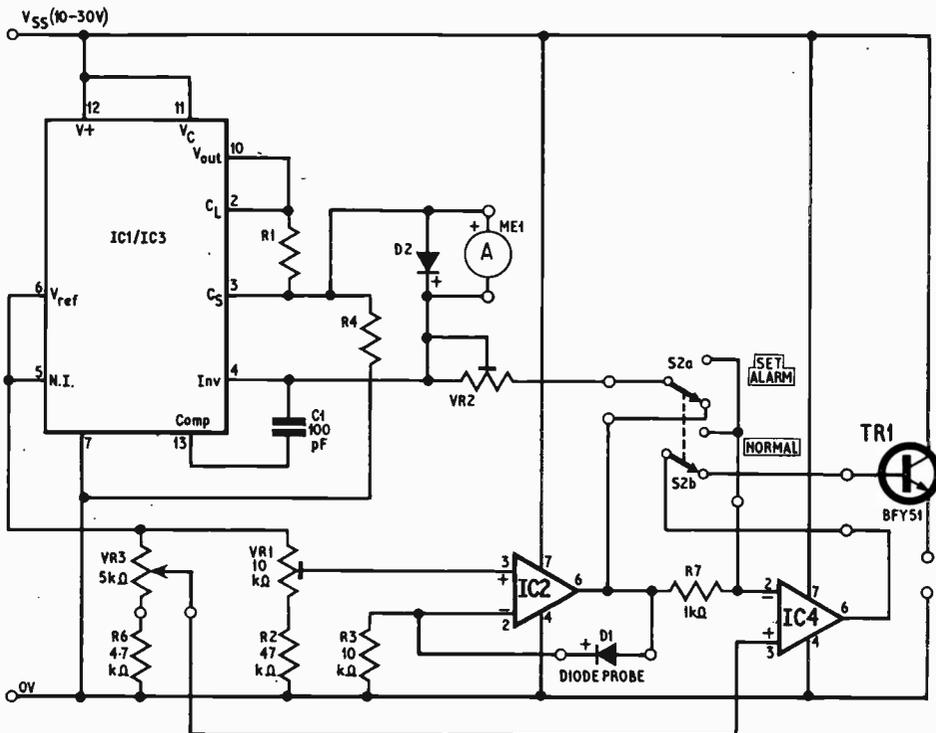


Fig. 4. A variation of the diode thermometer designed to give both control and indication functions

METER

Provision is made for an external meter if this is required. It should of course match the existing meter (100 μ A). Normally the link is left in place.

If it is required to substitute a 1mA movement for the 100 μ A suggested in Fig. 1 then R1 becomes 220 Ω , VR2 becomes 1k Ω , and R4 becomes 4.7 Ω . Other meter values between these two limits can be accommodated if desired by interpolation.

CALIBRATION

Instrument calibration is in fact fairly simple. After assembly and circuit checking the instrument is now ready. Due to characteristic variations from diode to diode, calibration is needed each time a diode is changed.

In addition, the diodes themselves need some form of protection. Thus it is best to coat them with material such as cellulose varnish, synthetic resin, silicone rubber or the like to both prevent ingress of damaging fluids and, of course, to avoid faulty readings due to conductive fluids altering the diode characteristics.

Of course the coating will to some extent reduce the speed of reaction of a diode but this can be accepted happily in many applications.

The easiest way to calibrate is to use boiling water for the 100 $^{\circ}$ C standard and melting ice for the other 0 $^{\circ}$ C level. Thus a simmering pan of water and a thermos flask containing a water/ice mix are convenient.

With the instrument switched on, place the probe first in the ice/water mix and adjust VR1 to set the meter zero value. Now place the probe in the simmering water and adjust VR2 to set the end-of-scale 100 $^{\circ}$ C correctly to the f.s.d. mark on the meter if it is a 0 to 100 scale.

An interesting point is that whilst Fahrenheit is now out of fashion it is just as easy to calibrate a scale to Fahrenheit if one wants.

It will probably be necessary to repeat the procedure to check calibration. Of course, the scale can be compressed or expanded as required.

INDICATOR/CONTROLLER

By using an extra amplifier IC4 as in Fig. 4, in the comparator mode, the signal at IC2 output can be compared to any preset value and a resulting switching action used to provide control or alarm functions. With the switch S2 in the "Normal" position the circuit of Fig. 4 provides both visual indication of temperature and a switching output function. IC4 comparator controls TR1 which in turn controls the required external circuits.

With S2 in the "Set Alarm" position IC4 is connected as a voltage follower, buffering the set-point potential of VR3 and presenting it to IC3 and the meter. Thus the meter indicates the setpoint value.

BLIND CONTROLLER

The circuit of Fig. 5 can be used to drive lamp or relay circuits in order to effect a blind (non-indicating) control function.

SWITCHED RANGE INSTRUMENT

The circuit of Fig. 1 can be modified as in Fig. 6 to provide a scale expansion function in which the indicator gives a 0 to 10 degree indication and the

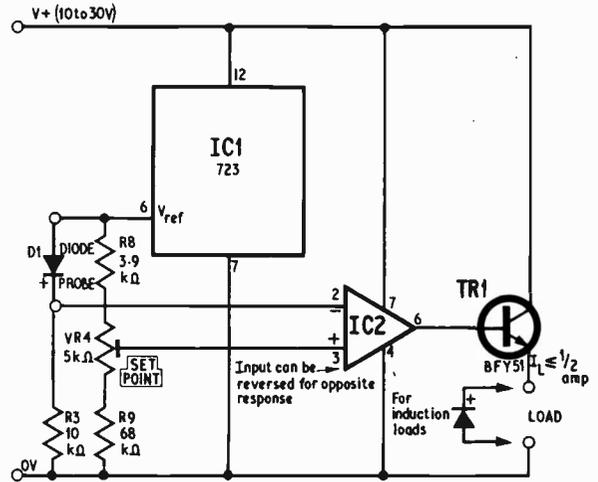


Fig. 5. A "blind" controller based on the diode thermometer. The output is "on" when the sensed temperature is below the set point

switch S3 selects the lower point of the indicated scale. Thus as shown the 10 $^{\circ}$ C scale can start at 0 $^{\circ}$ C, 10 $^{\circ}$ C, 20 $^{\circ}$ C and so on up to 90 $^{\circ}$ C as selected by the switch.

This gives a scale expansion of one order of magnitude which can be useful in many applications.

When calibrating this version of the instrument VR1 is adjusted as before with S3 in the 0 $^{\circ}$ C position, VR2 is adjusted to give a 10 $^{\circ}$ C range indication, and then VR5 is adjusted with S3 at 90 $^{\circ}$ C position and the probe in boiling water to give f.s.d. The VR2 adjustment will probably require the use of a normal thermometer. ★

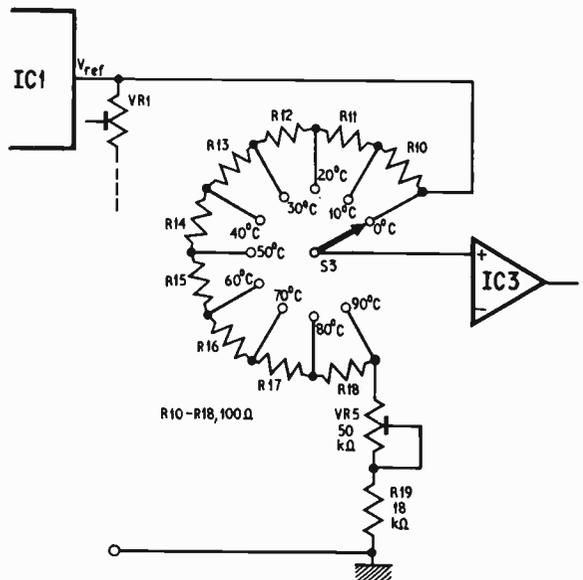


Fig. 6. A modification of Fig. 1 which gives an expanded scale covering 10 $^{\circ}$ C but switchable to start at any of a number of selected temperatures



BOOK REVIEWS

PIEZOELECTRIC CERAMICS

By J. van Randerdaat and R. E. Settingington
Published by Mullard Ltd.
211 pages. Price £4 clothbound

THIS latest addition to the Mullard technical library offers, in one volume, a comprehensive textbook on the subject of piezoelectric ceramics from basic theory through mechanics and associated mathematics to the practical application of a wide range of devices manufactured by the publishers.

This volume is up to the usual high Mullard standards with plenty of back-up information provided in the form of recognised symbols used in the art, tables of information on the various shapes and forms of device available and details of behaviour under temperature variation.

Apart from the in-depth technical information, space is given to discussion of the main application areas for this recently developed material, such as in gas ignition, in flexure elements (those which move on application of electric current) and in resonant devices as in filters and ultrasound equipment.

A variety of circuits are worked through, even as far as production of p.c.b., and suggestions are put forward for such items as a depth sounder, control transmitter/receiver installations and intruder alarms.

Following the usual Mullard tradition this book will be of use anywhere this type of device is considered from the educational establishment to the industrial workshop and is undoubtedly of value in current terms.

Available from technical bookshops or directly from the distributor, Technical Press Ltd., Freeland, Oxford, OX7 2AP.

R.D.R.

SL600 SERIES APPLICATIONS MANUAL

By James M. Bryant
92 pages, 6in x 8½in

THIS is the second edition of collected applications information specific to the Plessey Semiconductors SL600 series i.c.s.

Completely updated, the contents break down to three sections with appendices. Section 1 covers circuit data; section 2—system design and section 3 on relevant technical data.

In section 1 chip circuitry is explained and the area of applications detailed. The remainder of the manual looks at complete communications systems including the devices with an end section on product characteristics with operating notes.

Copies of the manual are available from Plessey Components Ltd., Plessey Semiconductors, Cheney Manor, Swindon, Wiltshire SN2 2QW. Price 50p.

G.G.

RADIOISOTOPE EXPERIMENTS IN PHYSICS, CHEMISTRY AND BIOLOGY

By J. B. Dance
Published by Hutchinson Educational
246 pages, 8½in x 5½in (softback). Price £1.75

THE study of nuclear radiation is receiving increasing attention in schools and colleges. It offers opportunities to demonstrate the fundamental nature of matter with quite simple equipment, such as the well-known Geiger counter.

This book describes in full detail more than 70 experiments that can be performed using either naturally occurring radioisotopes or artificially produced isotopes. The topics covered include those of interest to students of physics, chemistry, statistics, and biology, up to G.C.E. Advanced Level.

The collection of experiments (well catalogued for immediated reference in the Contents) makes up rather more than half of this book. It is preceded by five sections dealing with theoretical and practical matters, which collectively form an excellent introduction to the subject.

Appendices give valuable information and data; in particular, the regulations and codes of practice governing the use of radioisotopes in educational establishments and addresses of suppliers of equipment and radioactive sources.

This book is an expanded and updated version of the author's *Radioisotope Experiments for Schools and Colleges* which was first published by Pergamon Press in 1967.

F.E.B.

RECEIVING PAL COLOUR TELEVISION

By A. C. Priestley
Published by Argus Books Ltd.
261 pages. Price £5

TO readers of our companion magazine *Television*, the author's name is no doubt familiar. With a background of many years in TV design and the creator of correspondence courses in colour TV one would assume these were the ingredients for producing a successful book on the subject.

With a publishing date that coincides nicely with the start of a new term of evening and day classes it will obviously attract engineers, technicians and students who already have a working knowledge of the principles of monochrome television and wish to extend their knowledge to embrace PAL colour systems.

Since the mathematical explanations are marginal, the enthusiastic amateur might get better results from his set with judicious reading.


Chapter one deals with the origins of the PAL system, basic light theory and a short review of monochrome fundamentals.

Subsequent chapters include analyses of the transmitted colour signal, display tubes, decoding, colour display adjustment and servicing which includes test gear requirements, interpretation of results along with rudimentary troubleshooting procedures.

The reading is made so much easier by the abundance of sideheads which break up each chapter. They also prove a useful reference, being included in the contents page.

There are many line drawings and a number of colour plates. Final appendices cover vectors, phasors and colour bar signal waveforms.

G.G.

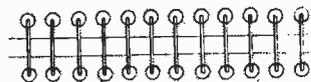

INDUSTRY NOTEBOOK

By Nexus



CALCULATOR NEWS

Sinclair Radionics, Britain's largest calculator manufacturer with an output of 50,000 units per month, of which 70 per cent are exported, is on the brink of its biggest deal ever. This is a completely new calculator which will be marketed by the Gillette Company of Boston, U.S.A. First reports suggest that the calculator is unlike any of the five Sinclair models currently available and is being designed to an original Gillette specification. Details are hush-hush at the time of writing, but I understand a test marketing by Gillette in the United States is imminent. If the market responds satisfactorily, big production contracts will follow. And it is hinted that "big" is measured in millions of units.

Advance Electronics is offering a version of the Model 162P fully programmable calculator in kit form at £99 plus VAT. The assembled 162P is listed at almost £200 which suggests that assembly and testing is a tedious and time-consuming affair. But Advance say that the kit can be assembled "in a matter of minutes without requiring any special tools". This is another example, it seems to me, of the erratic pricing structure in the calculator business. Even in these days of wage inflation, £70 or so for "a matter of minutes" in assembly seems somewhat excessive.

Mullard's new MOS i.c.s for calculators enable any would-be calculator manufacturer to get into business. Announcing the new range, Mullard say all you need is a keyboard, a display and a few interface components. There are four i.c. kits for desk models of all complexities, including memory circuits and print-out drives, and a couple of single-chip i.c.s for the simpler pocket calculators. But

before leaving the car in the drive and setting up an assembly plant in the garage, remember that it's easier to make things than market them. I have been told that in the early days it cost one manufacturer £15 in press advertising for each calculator he sold.

BARGAINS

With share prices at an all-time low it's a wonder more companies haven't been snapped up by bargain hunters than have been. Who would have imagined a few years ago that one of the real high flyers, Advance Electronics, would change hands for a mere £4.25 million? But so it was after weeks of rumour. Advance, who was once well fancied as a possible buyer of Marconi Instruments, now finds itself a wholly-owned subsidiary of Gould Inc., of Chicago.

As long ago as November 1971 Gould was known to be shopping for European companies with over £25 million to invest and is now operating in nine European countries. It's hard to believe that this go-ahead concern runs its European operations not from some lush office suite in one of the great financial centres but from the Epping home of Gould Europe's director Richard A. Holmes.

Advance Electronics is a good buy. Chairman Sir Edward Howard reported record pre-tax profits of £709,793 for 1973 and full order books for 1974. And the Advance product range in no way conflicts with Gould's own range.

Whether George Kent will be a bargain for GEC remains to be seen. Kent was about to conclude a deal with the Swiss company Brown Boveri in which the latter would have acquired a majority shareholding. With remarkable suddenness, and apparently with Government support, GEC put in a counter-bid which would give GEC 50 per cent ownership, the other shares being owned 41 per cent by the Government and nine per cent by Rank. The new alignment was not firm at the time of writing but few observers doubted that the deal would go through. The odd thing about the offer, apart from its speed and timing, was that it is entirely contrary to GEC's normal policy of total control. But these are strange times.

SEMICONDUCTOR PRICE WAR

Following dire warnings from Fairchild, reported in last month's *Industry Notebook*, there is evidence that a new round of price-cutting has started. The European SGS-ATES concern has reacted to reports of U.S. underpricing by slashing their own prices by up to 50 per cent on some consumer

i.c.s and by up to 40 per cent on some professional devices.

We all know that demand for consumer i.c.s has slackened but I feel it is perhaps going too far to talk of a "semiconductor mountain". But it is true that stocks have been building up and first reports suggest that the SGS-ATES price cuts apply only to the U.K. market—at least for the time being. Whatever the decline in the demand, a spiral down in prices on a world scale can hardly do anyone any good. As it is, today's prices for i.c.s average out at less than 50 per cent of what they were four years ago in spite of inflation.

AEROSPACE FLIES HIGH

Britain's aerospace industry stood up well in comparison with foreign exhibits at last September's Farnborough Air Show. In round figures the output of the industry is £800 million including £500 million of exports with a labour force of under 200,000 people. And the electronics sector looked really good with plenty of advanced technology products ranging in size from Plessey's new 3-D radar down to a tiny hand-held laser rangefinder shown by Barr & Stroud which, in size and appearance, is like a pair of binoculars and yet has a range of three miles with L.E.D. digital read-out, and all operating from internal batteries.

Industry leaders were clearly pleased with the performance of their companies but with the threat of nationalisation over their heads I can only sum up the general atmosphere as one of nervous optimism.

The most honoured guests were those from the oil-rich nations whose multi-million pound orders were gratefully received. It's a straight swap of technology against the purchase price of oil.

BRIGHT BOYS

Keep an eye on Membrain, already big in automatic test equipment and growing at a phenomenal pace. It's manned by a youthful team of enthusiasts headed by C. A. (Tony) Davies, now aged 30, who started the company in July 1970. Average age of Membrain staff is 33 years and 42 per cent of the 140 staff are under 30.

Starting from zero they have built a business which is now turning over £1.5 million a year. It is still on the cards that Membrain will acquire the ATE interests of Honeywell, though both sides are currently dismissing the rumour. Not bad going for a bunch of youngsters who, apart from building a fine business, won the Queen's Award for Technological Innovation earlier this year.

INGENUITY UNLIMITED



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

NEON OSCILLATOR

THIS circuit is simple for the beginner to both build and understand and, using readily available components it can be assembled very cheaply. The frequency range is quite wide, from one pulse per second or less up to the higher audio frequencies.

In the circuit of Fig. 1 the capacitor C1 charges via R1 and R2 and the primary of T1, an old valve output transformer of 20 or 30 to 1 turns ratio. When the voltage across C1 reaches the striking voltage of the neon, the latter discharges, producing a flash at the neon and an

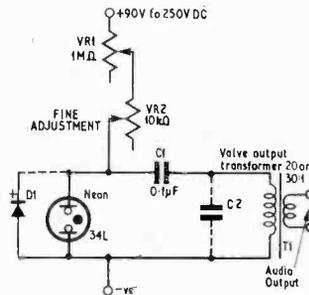


Fig. 1

output pulse from the secondary of T1.

After the circuit is constructed R1 should be adjusted from its highest value until oscillation starts and then R2 is adjusted to set the rate of charge of C1 and thus the frequency of oscillation. In this way one can use R1 as a coarse adjustment and R2 as a fine adjustment increasing the resistance to reduce the frequency.

With C1 at 0.1μF oscillations vary from a slow flash to about 50Hz. Smaller values of C1 produce higher frequencies. Capacitor C2 is really optional and is used to alter the tone of the audio output. The output can be fed to a small loudspeaker or an amplifier as desired.

Applications are numerous. The circuit can form a useful voltage indicator or can perhaps be the basis of a synthesiser. Powering is either from the mains using a suitable rectifier and smoothing or using a battery of the valve receiver type (90V). With the former it is possible to obtain a descending audio note on switching off and a continued illumination of the neon for some time after that because of smoothing capacitor charge holding. This could perhaps have timing applications.

The diode D1 can be used to replace the neon if only an audio output is required. This should be a low reverse breakdown device so that C1 discharges through it when the breakdown voltage is reached.

M. J. Maynard
Wednesbury.

ZENER DIODE CHARACTERISTICS

AN OSCILLOSCOPE is a fairly usual adjunct to the workshop these days and most oscilloscopes are fitted with a sawtooth output from the ramp generator. This can be used to great advantage to measure the characteristics of Zener diodes.

All that is required in addition to the oscilloscope is a potential divider network which is connected up as shown in Fig. 1. The sawtooth potential is divided down so that it can be applied to the device under test, the same points being connected to the Y-amplifier input.

With no device connected, or one which is open circuit, the oscilloscope will display the plain ramp waveform, an evenly increasing voltage. With a short-circuit device connected the display will be a simple horizontal line as there will be no input to the Y amplifier.

A good device will cause the display to assume the normal ramp shape until the voltage across the diode reaches the Zener voltage value when the trace will become horizontal. Thus the Zener voltage can be read from the scope graticule and Y amplifier setting.

A device with an intermittent fault will show a display which oscillates between the two possible other displays, depending on the fault failing to short or open circuit.

The characteristics of any diode can be investigated using this method and for other voltages the potential divider is suitably modified using Ohms Law to give a voltage level which exceeds the Zener voltage of the device under test. Of course, the sawtooth output must not be overloaded or the diode parameters exceeded.

R. Beck
Romney Marsh.

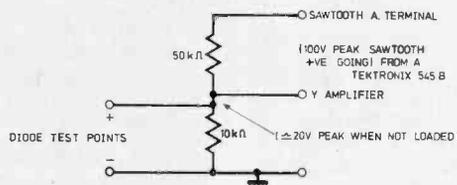


Fig. 1



Now there's Doram, you need never wait for electronic components.

7-day service.

Buy the new Doram catalogue and you could have your components within 7 days of our receipt of your order.

If you don't, you'll have your money back and no questions asked.

What you won't get is a tedious wait. Which goes on. And on. And on. And on. You know just where you are with Doram.

Millions of components.

Doram is a brand-new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

You buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint) and then you order from it.

We're big enough to offer you stocks of millions of components on over 4,000 product lines.

And so confident of our service that if we can't supply the part you want within 7 days of receiving your order, we'll give you your money back. Immediately.

No-quibble guarantee.

It's just about impossible to buy a defective part from us. Because our checking is so pains-taking.

But even if the unthinkable does happen—and you're unlucky—then we'll still make you happy quickly.

Because we offer a no-quibble replacement part service.

And our guarantee is guaranteed by the fact that we belong to the biggest electronics distribution Group in Britain.

All branded goods.

All goods supplied are branded goods. Made by big-name manufacturers like RS, Mullard, SGS-ATES, Ferranti, Siemens etc.

Doram brings the amateur the sort of service only professionals have enjoyed before.

So don't delay. Use the coupon. Send today for your first Doram catalogue. It can make your life a whole lot easier.

For 25p that can't be bad, can it?

I ENCLOSE 25p* PLEASE SEND ME THE NEW DORAM CATALOGUE.

Name

Address

Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM

PE12174

ELECTROVALUE

Present

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

top quality electronic components for price-minded buyers

112p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

A 100 OF THE BEST From our transistor stock

2N1307	47p	BC149C	14p
2N2646	51p	BC158B	15p
2N3053	26p	BC159	15p
2N3054	60p	BC167B	13p
2N3055	80p	BC168B	12p
2N3702	11p	BC169B	12p
2N3703	10p	BC169C	15p
2N3704	11p	BC179B	26p
2N3705	10p	BC182L	26p
2N3794	18p	BC184L	26p
2N3819	25p	BC212L	14p
2N4062	11p	BC214L	14p
2N4443	52p	BC257A	14p
2N5052	42p	BC259B	14p
2N5163	20p	BC758	30p
2N5459	32p	BD130	90p
40361	48p	BD131	48p
40362	44p	BD132	52p
40602	46p	BD135	37p
40636	£1.36	BD136	39p
40669	£1.10	BDY20	83p
AC128	17p	BF194	15p
AC151R	23p	BFR39	23p
AC153	27p	BF797	23p
AC153K	31p	BFX29	33p
AC176	24p	BFX184	27p
AC176K	38p	BFY51	23p
AC187K	31p	BRV39	45p
AC188K	29p	BY164	51p
AD133	£1.92	C106B1	42p
AD136	£1.11	C106D1	82p
AD149	65p	C1406	73p
AD161	42p	MJ461	£1.20
AD162	40p	MJ491	£1.35
AF200U	70p	MJ2955	80p
AF239	80p	MJE371	89p
B1906	36p	MJES21	81p
BA138	31p	MJE2955	£1.12
BB103	24p	MJE3055	68p
BB105	34p	OA91	8p
BB109	18p	SD4	8p
BC107A	15p	TIP31A	70p
BC107B	15p	TIP32A	80p
BC106B	14p	TIP41A	80p
BC108C	14p	TIP42A	£1.00
BC109B	18p	WO2	30p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	23p
BC147B	13p	ZTX500	14p
BC148B	12p	ZTX504	45p

100s MORE IN CATALOGUE 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in 'Wireless World'. Simple to assemble fantastically good results and a greater money saver. Carries 10 watts RMS 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2.30. Loudspeaker Unit 9SRM109, £2.45. Cabinet Kit to Baxandall design, £10.45. Cross-over choke for additional woofer to above, £1.50.

DISCOUNTS

Available on all items except those shown with NETT PRICES 10% on orders from £5 to £14.99. 15% on orders £15 and over.

FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders—charge levied at cost. Giro A/C No. 38/671/4002

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
(see note below)					
C	1/3	4.7-470K	1-3	1-1	0.9 nett
C	1/2	4.7-10M	1-3	1-1	0.9 nett
C	3/4	4.7-10M	1-5	1-2	0.9 nett
C	1	4.7-10M	3-2	2-5	1.92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0.22-3.9Ω	11	10	8
WW	3	1-10K	9	8	6
WW	7	1-10K	11	10	6

Codes:
C - carbon film, high stability, low noise.
MO - metal oxide. Electrofil TR5 ultra low noise.
WW - wire wound, Pluesley.

Values: All E12 except C ½W, C ½W and MO ½W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:
5% except WW 10% ± 0.05Ω below 10Ω and MO ½W 2%.
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

POTENTIOMETERS

Rotary	Carbon	Track
Double wipers for good contact and long working life.		
P.20 SINGLE linear	100 ohms to 4.7 megohms	each 14p
P.20 SINGLE log	4.7 Kohms to 2.2 megohms	each 14p
JP.20 DUAL GANG lin.	4.7 Kohms to 2.2 megohms	each 48p
JP.20 DUAL GANG log.	4.7 Kohms to 2.2 megohms	each 48p
JP.20 DUAL GANG Log/antilog	10K, 22K, 47K, 1 megohm only	each 48p
JP.20 DUAL GANG antilog	10K only	48p
2A DP mains switch	for any of above	14p extra

Decades of 10, 22 and 47 only available in ranges above.
Skeleton Carbon Presets. Type PR, horizontal or vertical, each 6p

SLIDER

Linear or log mono 4.7K to 1 meg. In all popular values, each 30p
STEREO, matched tracks, lin or log in all popular values from 4.7K to 1 meg, 80p
Escutcheon plates, mono, black, white or light grey, each 10p
Control knobs, blk/wht/red/yel/grn/blue/dk grey, lt grey, each 7p

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	—	—	—
1.0	—	—	—	—	—	11p	—	8p
2.2	—	—	—	—	—	—	8p	8p
4.7	—	—	—	11p	—	—	8p	8p
10	—	—	—	—	8p	8p	8p	8p
22	—	—	8p	—	—	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	13p
100	8p	8p	8p	8p	8p	10p	12p	19p
220	8p	8p	8p	8p	10p	10p	11p	17p
470	8p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

MINITRON DIGITAL INDICATORS
3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point. 9mm characters in 16 lead DIL.
Suitable BCD decoder driver 7447 £1.15
3015G showing - or - & 1 & dec pt £1.20
LEDS (Light Emitting Diodes) 25p
Photo Cells, each 40p

ANTEX Soldering Irons

CN340	£1.95	Spare bits	32p
CCN240	£2.30	Spare bits	40p

DESOLDER BRAID

6ft strip 66p

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way
3 pole 4 way; 4 pole 3 way each 29p
TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 28p; 6BA NUTS 28p
4S Screws 28p; 6S Screws 24p
Threaded pillars 6BA, hexagonal
Plain spacers 1/4 round £1.68
Other sizes available £1.12

ENAMEL COPPER WIRE IN 2 ounce reels

16, 18, 20, 22 SWG 34p
24, 26, 28, 30 SWG 40p
32, 34 SWG 46p; 36, 38, 40 SWG 54p

DIN CONNECTORS

1 way loudspeaker	Socket	Plug
3 way audio	10p	12p
5 way audio 180	10p	12p
5 way audio 240	12p	15p
6 way audio	12p	15p

EV CATALOGUE 7

2nd printing—Green and yellow Cover
112 pages, thousands of items—illustrations, diagrams, much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 25p post free, including refund voucher for 25p for spending when ordering goods list value £5 or more.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale.
Prices quoted do not include V.A.T. for which 8% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PE12, S.A.E. with enquiries requiring answers.
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily; Sat. 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

555 RAMP GENERATOR

ENGINEERS are often on the lookout for a better linear voltage sweep generator for their deflection, ramp, and function generator circuit designs. The recently introduced MC1555 timer can be used to make a simple linear voltage sweep circuit.

In the usual MC1555 timing circuit, it senses the exponentially rising voltage across the capacitor in an RC network. Essentially, from a discharged state, the capacitor begins receiving charge until the voltage across it rises to $2/3V_{CC}$, at which time it is discharged in preparation for the next charging (trigger) pulse.

By replacing the resistor in the RC network with a constant current source, the voltage across the timing capacitor is caused to increase linearly.

The charging time can be determined as follows:—


$$t = \frac{2/3 V_{CC} \cdot C}{I}$$

$$\text{where: } I = \frac{V_{CC} - V_E}{R_E} =$$

$$\frac{V_{CC} - V_B - V_{BE}}{R_E}$$

(t in seconds, V in volts and C in farads)

Fig. 1

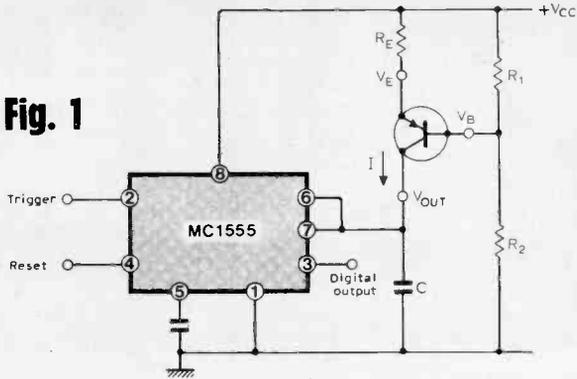

By setting $V_{CC} - V_B$ so that V_{BE} is negligible:

$$I = \frac{V_{CC} - V_B}{R_E}$$

Since V_B is directly proportional to V_{CC}

$$I = \frac{V_{CC} - K \cdot V_{CC}}{R_E} = \frac{V_{CC} - V_B}{R_E}$$

$$\text{where: } K = \frac{V_B}{V_{CC}}$$

$$\text{or: } t = \frac{2/3 V_{CC} \cdot C}{V_{CC}(1-K)} = \frac{2/3 C \cdot R_E}{1-K}$$

From this equation, it can be seen that the time period is essentially

independent of the supply voltage if the voltage across the emitter resistor of the current source is much larger than the V_{BE} of the transistor.

Since the capacitor voltage must reach at least $2/3V_{CC}$, the current source may be operated on a higher voltage supply than the timer although this is not necessary if the supply voltage is well regulated. The constant current source should be kept larger than $1\mu A$ so that it is always large compared to the current needed for the comparators.

Motorola Semiconductors Ltd.
Geneva



BOOK REVIEWS

NEW DIRECTIONS IN PARAPSYCHOLOGY

Edited by J. Beloff, B.A., Ph.D.

Published by Elek Science

174 pages, 8 $\frac{1}{4}$ in \times 5 $\frac{1}{2}$ in. Price £3-00

PSYCHICAL research with its considerable involvement in spiritualism was treated with scepticism by the scientific world following its inception towards the end of the 19th century despite the fact that two of its most important and earliest supporters were those eminent men of science, Sir Oliver Lodge and Sir William Crookes. In later times investigations into the supernatural or paranormal have taken on a more respectable guise and the field of investigation has been extended to cover all phenomena that cannot be explained by the accepted laws of physics.

The number of workers in parapsychology—which is the present day term that has more or less replaced psychical research—is large and includes distinguished academics working in universities and other learned establishments in various countries. It may be “a struggling science” as the Editor of this book describes it, but there can be no doubt of the sincerity and devotion of its apostles.

In *New Directions In Parapsychology* seven specialists who are all actively engaged in research in one or another aspect of ESP or PK have contributed accounts of their experiments and results obtained. Only one of these contributions has direct relevance to electronics, but since most paranormal experiments are based upon

statistical data, electronic equipment plays a major role. In the chapter *Instrumentation In The Parapsychology Laboratory*, Helmut Schmidt describes the use of automated equipment, data recording equipment, random number generators, PK test machines, and provides circuit and technical details of a remote number generator designed by the author for ESP and PK experiments. This chapter makes clear the heavy dependence of parapsychology upon modern electronic techniques.

Through this association many people involved in electronics will already have become aware of parapsychology and some begun to apply their circuit expertise to the devising of circuits for ESP and PK investigations, if not actually undertaking an active part themselves in such investigations. Such individuals and others wishing to learn more about this unusual science will find this book a useful acquisition. The *Glossary of Technical Terms and Abbreviations* is in itself a good guide for the uninitiated around this strange science.

The Editor John Beloff, who is Senior Lecturer in Psychology at the University of Edinburgh, contributes a reasoned introduction to Parapsychology, arguing that sufficient evidence exists now for a general acceptance of this new “borderland” science, whilst at the same time also acknowledging some embarrassment from the activities of earlier “spiritist” workers and from the current wave of handwagon jumpers (many associated with fanciful and unscientific occult and religious bodies) who offer a threat to the credibility of Parapsychology as a reputable science.



Arthur Koestler contributes a postscript and appears to support a “chance” basis for paranormal phenomena: this is in contradiction to the “orthodox” philosophy which considers that the prime aim of all PSI experiments is to achieve repeatability and thus establish a clearly defined *cause* as the basis for all extra-sensory experiences. A most fascinating and pregnant argument to round off this instructive and authoritative book.

F.P.R.

look! electronics really mastered

... practical
... visual
... exciting!

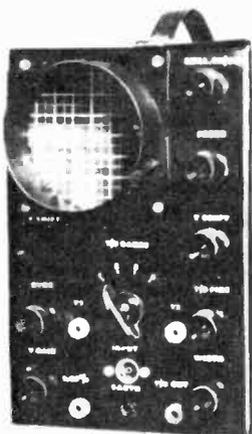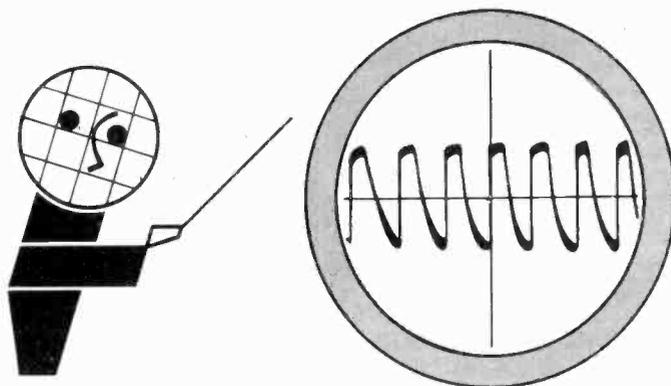no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

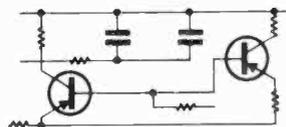2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, DEPT. EL124, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE

special free gift also to all our students

FIRST TIME EVER! SAVE £15.12!
BRAND NEW AC/DC BATTERY/MAINS

Cassette
TAPE
RECORDER
& PLAYER

With remote control microphone.



FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!
OUR PRICE £11.85
POST ETC. 50p

Due to price we cannot name makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) and AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels just "slap-in" a cassette. Superb taping and reproduction! Takes 30, 60 or 90 minute standard cassette tapes. Beautiful tone from a whisper to a roar! Remote control microphone! Rapid rewind! Fast forward! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V, A.C. mains. Separate jacks for remote-control microphone etc. 9 1/2" x 5 1/2" x 2 1/2" approx. Designs can vary slightly. With carry handle. WRITTEN G.T.E.E. and instructions. (Importers recommended selling price £26.97) OUR PRICE £11.85, post. etc. 50p. * Send quickly test on mail order 7 days approval from receipt of goods. Refund if not delighted. BONUS OFFER: Cassette tape, batteries and microphone stand 55p if required. ALSO Super de luxe model with VHF AM/FM radio (recommended retail price £44), only £22.95, carr. 50p (batteries and cassette tape 45p extra if required).

CALLERS: ACCESS AND BARCLAYCARDS ACCEPTED AT STORES.

SHOPERTUNITIES LTD

SAVE £21.56!

FABULOUS BRAND NEW
SOLID STATE AC/DC
MAINS/BATTERY

COMBINED V.H.F.
AM/FM RADIO
AND CASSETTE TAPE RECORDER
AND PLAYER



IMPORTERS RECOMMENDED
SELLING PRICE £44.51!

OUR PRICE £22.95
car. etc. 50p

Latest sensation in the world of sound! First class makers! Fabulous VHF AM/FM RADIO and CASSETTE TAPE RECORDER AND PLAYER combined! Run off standard batteries or mains (simply plug in mains 220 240v A.C. line cord supplied)—NOW you can record and play back anything, anywhere! IMPORTERS RECOMMENDED SELLING PRICE £44.51! WE OFFER AT ALMOST HALF PRICE! Fantastic specification. * Automatic recording level control! * Monitor switch! Expensive calibrated 'slider' volume and tone control! * Latest "MASTER SWITCH" fast forward, stop, play and rapid rewind control! * Superb built-in Speaker! * Takes standard 30, 60, or 90 minute cassette tapes obtainable everywhere * Earphone and extension speaker sockets PLUS separate input/output DIN Jack socket! * Built-in swivel 7 section telescopic aerial (25in approx.). * Magnificent case (approx. 10in high) in luxurious Black and Silver finish with "leak-finish" speaker grille. * Built-in carry handle. * Wonderful VHF AM/FM Radio with instant switch-over waveband selection and pin-point station tuner. Superb clarity and tone. Amazing station selection home and abroad including local reception of city and regional stations in every part of the country (even those scheduled for the future) plus BBC National VHF. Also fabulous in Car! You could pay £££ more for a Radio or Car Cassette player ALONE! Yes, only £22.95, carr. etc., 50p, complete with remote control microphone, etc. Written Guarantee and simple instructions. BONUS OFFER: Batteries, Cassette Tape, personal listening earpiece, and microphone stand, all for only 55p extra, if required. Send total £24 (to include Bonus, car, etc.) and test on 7 days mail order approval from receipt of goods. REFUND IF NOT DELIGHTED or call.

Dept. PE/39, 164 UXBRIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AG. (Thurs 1 Fri 7) Also at 37/39 HIGH HOLBORN (opposite Chancery Lane) LONDON, W.C.1 (Thurs 7 p.m.). BOTH OPEN MON. TO SAT. 9 TILL 6

TRAMPUS ELECTRONICS LTD
58-60 GROVE ROAD,
WINDSOR, BERKS.

FAST SERVICE. SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.

WONEY BACK IF NOT SATISFIED. LARGE STOCKS. LOW PRICES. ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME.

CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays



MINITRON 3015F
 0-9DP £1.15 ea
LED 0.3" digit
 0-9DP £1.49 ea
JUMBO LED 0.6"
 0-9DP £2.25 ea
LIQUID CRYSTAL
 6 digit £18

MINI PIN SOURCE OR RED DIFFUSE
 LEDS. 209 STYLE. NO CLIP. 14P ea
T1L209 RED LED & CLIP 17P ea
BIG 1" RED LED & CLIP 18P ea

ORANGE & GREEN LEDS:
 MINI 25P ea. BIG & CLIP 33P ea
INFRA RED LED £1.2N5777 33P.
PS12 PHOTO IC/amp/switch £1.

DIGITAL CLOCK

MOIS INTEGRATED CIRCUITS.
 AYS1224 4 DIGIT CLOCK supplied with 14pin socket & data 14.25
 MM5311/14 6 DIGIT CLOCK with 28 pin socket & data £7.50
 3DIGIT DVM AYS3500 47.50
 4DIGIT COUNTER/DRIVER £7.50

CASSETTE mechanics £12.50

STEREO CASSETTE MECHANISM.
 As used in imported types costing £100. Only requires a case & electronics, leads supplied. Send for data 15p.

IC's & Semiconductors

702 OPA	69p	MFC4000 1w AF	35p
703 RF/IF	28p	MFC4060	54p
709 T099	21p	MFC6030	52p
709 DIL 14	29p	MFC6040	90p
710 DIL 14	36p	MFC8010	£1.10
720 Radio £1.39		MFC8040	£1
723 Regulator 67p		NE531 35V/us £2	
741 T099	29p	NE536 FET OPA12	
741 D1L8	31p	NE540 Driver £1	
741 D1L14	31p	NE546 AM Rxl1.50	
747 Dual 741 89p		NE550 2v ref 79p	
748 D1L 8	36p	NE555 TIMER 67p	
1505 IC A/D		NE556 Dual £1.30	
Converter £7		NE560 PLL £3.15	
7805 1ASV £1.59		NE561 PLL £3.15	
7808 1A8V £1.69		NE562 PLL £3.19	
7812 1A12V £1.69		NE565 PLL £2.69	
7815 1A15V £1.69		NE566 Gen £2.49	
76009 1w AF 75p		NE567 code £2.69	
76013 6w AF £1.39		SN72709 709 29p	
8038 Sig Gen £3		SN72741 741 31p	
CA5046	69p	SN72748 748 36p	
LM301 OPA	49p	SN76131	£1.20
LM307 OPA	49p	SN76660 FMIF £1	
LM308 HiPoPa	95p	SN76611 1F £1.25	
LM309A Reg. £2.29		TAD 100 & 1F £2	
LM371 RF/IF £2		2N400E	£3
LM372n AF/IF £2		2N402T	£1.75
LM373n	£3	2N403 Servo £2.50	
LM377 2x2W £2.69		ZN414 AM Rxl1.09	
LM380 2w AF 99p			
LM3812 2xprc. £2			
LM382amp £2			
LM3900 4xOPA 69p			

SPECIAL OFFERS

741 29p MFC4000 35p
 555 67p 2N414 £1.09
 BC107, BC108, BC109 9p ea
 2N3055 39p Three for £1
 115W/T03 or 90W plastic
 2N3819E 16p 2N3053 17p
 BFY50/51/52/53 all 18p
 LA50Vrect 4p ea IN914 4p

Price each:-
 AC127/128 16p
 AC187/188 19p
 AD161/162 35p
 BC107/8/9 9p
 BC132/4/7 18p
 BC147/8/9 10p
 BC157/8/9 12p
 BC177/8/9 18p
 BC182/3/4 11p
 BC212/3/4 12p
 *A or L
 BCY70/1/2 15p
 BD131/2 39p
 BFY50/1/2 18p
 BFY53 17p
 BSX20 12p
 MJE2955 95p
 MJE3055 62p
 MPU131put 49p
 OA91 8p
 TIP29A 48p
 TIP30A 48p
 TIP31A 61p
 TIP32A 73p
 TIP41A 78p
 TIP42A 89p
 ZB Y88 400mW
 ZENERS 9p
 BRIDGE RECT 1A 50V 20p
 GAS SENSOR £2
 GAS * KIT £5

TIP2955 90p
 TIP3055 55p
 T1S43 UJT 25p
 IN4001 4p
 IN4004 6p
 IN4148/914 4p
 2N697 13p
 2N706/8 10p
 2N2646 49p
 2N2901/5 20p
 2N2926royg 9p
 2N3053 17p
 2N3055 39p
 2N3614 49p
 2N3702/3 9p
 2N3704/5 10p
 2N3706/7 9p
 2N3708/9 8p
 2N3710/11 9p
 2N3563/64 16p
 2N3566/67 16p
 2N3658 16p
 2N3641/2 16p
 2N3819E 16p
 2N3832E 17p
 2N3904/6 14p
 2N4249 16p
 TAG 1/400 55P
 CI07D1 SCR
 4A/400V 55p

vero

VERO PINx36 25p.
 COPPER CLAD VEROBROAD 0.1"
 21x5" 27p. 21x3" 24p. 31x3" 27p.
 31x5" 29p. 31x17" £1.50
 DIL IC's BOARDS 6x41" £1.50
 24 way edge connector 60p
 36way 90p. PLAIN 31"x17 £1
 FACE CUTTER 45p. FEC ETCHANT

DALOpen69p

PRINTED CIRCUIT BOARD KIT £1.69
 COPPER BOARD 6x4" 40p.
 DESOLDER BRAID reel 59p

HEATSINKS

5E/T05 & 18E/T018 5p ea.
 TV4 12p. TV3/T03 16p. 4Y1/T03 29p.

CAPACITORS

22pF to 0.1uF 4p ea. ELECTROLYTIC
 25V 2/10/50/100uF 6p. 1000uF 20p
 PRESETS VERT: 5p. RESISTORS 51p

POTS A B or EGIN

ROTARY: 12p. SWITCH 15p. DUAL 38p.
 SLIDERS: SINGLE 26p. DOUBLE 48p.
 SWITCHES: SPST 18p. DPDT 25p.
 MINI 1" SPST 39p. PUSH 39p.

BENCH POWER SUPPLY 3-12V 55.

DIN PLUGS all 13p ea. Sockets 9p
 TRANSFORMERS 1A 6/12V £1.34
 BHA 0002 MODULE 15WAT AMP 55
 EA1000 4W AF MODULE £2.49
 BW/12V FLUORESCENT LIGHT 53.
DI sockets
 PROFESSIONAL GOLD PLATED & GREY NYLON. 8, 14 or 16 PIN ONLY 15p each.

PATENTS REVIEW...

AUDIBLY DETECTING SPEED CHANGES

BP 1 352 030

In BP 1 352 030 Customflex Inc. of Ohio, USA, describes a simple gadget for use with a transistor radio to provide an audible indication of speed change, for instance of a boat through water.

As the inventors point out, the ear has difficulty in detecting the difference between 500 clicks per second and 505 clicks per second, but has no trouble in detecting the same difference between 10 clicks and 15 clicks.

With this premise in mind, the inventors suggest an arrangement consisting of a small brass rod, pivoted at one end. A water resistant thread passes from the end of the rod through a coiled compression spring to a ferrite core. All these elements are contained in a hollow, plastic cylinder, which is wrapped with an insulated reaction coil.

This arrangement is mounted on the underside of a boat. As the boat moves through the water, the rod is repeatedly moved in an arc to pull the thread and with it the ferrite core, down against the spring. This movement of the ferrite core changes the induction of the reaction coil.

The coil is connected to an ordinary portable transistor radio by two leads and a miniature jack plug which is inserted in the jack socket provided on most radios for ear-plug use.

According to the inventors this produces a change in the oscillator and thus the sound produced by the radio which is indicative of the rate of the boat movement.

Also described is a circuit for a transistor converter which combines the functions of oscillator and mixer. A capacitor and a variable induction coil is incorporated in a series tuned circuit which imposes an electrical load on the converter to produce controlled "motor boating" clicks. Varying the radio set tuning capacitor by turning the tuning dial will adjust the basic rate of digital clicks heard on the radio.

Few further details of the transistor converter are given because the inventors regard the circuit as sufficiently well known already.

KEYBOARD INSTRUMENT

BP 1 354 407

Electronic musical instruments having 12 keys to the octave are well known. These instruments can produce only semitones and in BP 1 354 407, a Japanese inventor suggests that under certain circumstances it may be desirable for exotic musical effects to produce quarter tones as well.

The circuit achieves this in a very simple manner. A keyboard of the conventional semitone type operates twelve switches of an array, and a d.c. power source circuit which produces d.c. voltages to control a v.c.o.

In conventional manner, individual operation of the keys of the chromatic octave produces individual semitones from the loudspeaker. But, when adjacent keys are simultaneously depressed, the v.c.o. is supplied with a voltage which is substantially one half of the sum of the voltages representative of the keys pressed. The frequency produced is substantially a quarter tone between the two keys simultaneously pressed.

ELECTRONIC AID TO CURE STAMMERING

In BP 1 352 682, George Donovan and Charles Hansel of Swansea claim electronic circuitry for use in speech therapy with particular relevance to the suppression, treatment and study of stammering. The object is to produce speech-masking signals in the lower part of the audio frequency band of various duration and type. For instance, it has been found that a continuous masking sound is effective in most cases to suppress a stammer but, for therapy, bursts of masking sound are required.

As shown in Fig. 1, a Schmitt trigger Q1 is connected as a free running multivibrator with fixed and adjustable resistors R1, VR1 and a 10 μ F capacitor C1 to generate a masking signal of which the frequency, 180Hz, is controlled by adjustment of VR1. The output of trigger Q1 is coupled to the first

input of NAND gate G1, of which the output is coupled to an earphone.

A second Schmitt trigger Q2 is connected with 2000 μ F capacitor C2 as a free running multivibrator, and generates a lower frequency, for example 60 or 90Hz, adjustable by R3, VR2. The output of Q2 is coupled to trigger a monostable multivibrator, with parallel capacitances C3, C4, selectively switchable by switch S1. The switch S1 also controls connection of the output of the monostable to the second input of the gate G1.

When the supply switch S2 is closed and with switch S1 in position A, the masking input of the gate G1 is not inhibited and a substantially continuous masking noise is delivered through gate G1 to the earphone. Switching S1 to positions B and C will cause the continuous output of trigger Q1 to be inhibited and an accurately shaped output of adjustable width delivered by the monostable to gate G1. Adjustment of VR3 controls the pulse width, for instance, to give a short burst of speech masking sound producing a metronomic beat in the earphone or a pulse with a mark-to-space ratio of 1 or more, equivalent to long bursts of speech-masking sound. The socket SK1 is provided for coupling auxiliary apparatus to the output of G1.

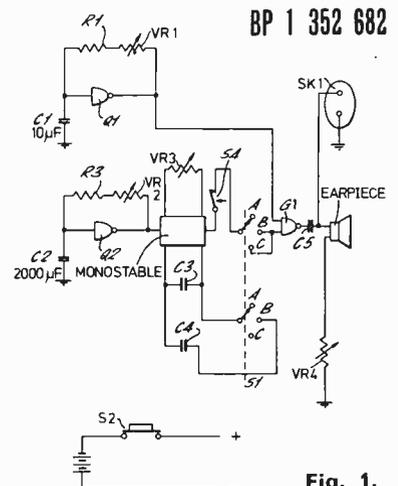


Fig. 1.

Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Visual monitor

Sir,—A musician myself, I frequently end up advising other musicians on p.a. equipment, not infrequently building units to their requirements. Although most users seem rather unconcerned with it, a point that always worries me is that of the keen performer who turns his volume controls full on automatically (yes! they are still around—you don't have to look for them, just listen!) Distortion and ruined speakers may be prestige symbols to some, but work out expensive.

Whilst it is possible to straddle Vu meters on pre-amplifier outputs it is usually fairly messy to do, and is still only a rough guide (honest) to how rough you are being.

Recently, however, after building a power amplifier that delivered about 100W with an input of 1V, I thought of a very simple way of having a visual indication of overload on the input. I simply put an l.e.d. across it; I used a TIL 209 straight across the input. This device needs just over 1V across it before it will light up and goes on up to about 3V quite happily. Its current consumption is exceedingly low and at worst it puts about 20k Ω across the input. The effect on the input is acoustically unnoticeable.

I've given it a good try out and it does its job very well. Those unavoidable peaks give a pleasing little red flash and on real overload (don't watch the speaker) it works like a traffic light.

It doesn't matter which way round it is connected, of course, since the signal will be a.c. and scanning the market should provide a device of suitable voltage to suit most high power amplifiers.

I know the idea sounds too simple but who cares? It works!

Peter Quinn,
Portsmouth

Russian roulette

Sir,—In his novel "The Gambler", the Russian author Fyodor Dostoyevsky writes the following:

"However, I deduced from the scene one conclusion which seemed to me reliable—namely,

that in the flow of fortuitous chances there is, if not a system, at all events a sort of order. This is, of course, a very strange thing. For instance, after a dozen middle figures there would always occur a dozen or so outer ones. Suppose the ball stopped twice at a dozen outer figures; it would then pass to a dozen of the first ones, and then, again, to a dozen of the middle ciphers, and fall upon them three or four times, and then revert to a dozen outers; whence, after another couple of rounds, the ball would again pass to the first figures, strike upon them once, and then return thrice to the middle series—continuing thus for an hour and a half, or two hours. One, three, two; one, three, two. It was all very curious. Again, for the whole of a day or a morning the red would alternate with the black, but almost without any order, and from moment to moment, so that scarcely two consecutive rounds would end upon either the one or the other. Yet, next day, or, perhaps, the next evening, the red alone would turn up, and attain a run of over two score, and continue so for quite a length of time—say, for a whole day".

Alexei Ivanovitch's observations concerning the phenomena of roulette seem to tally very well with Mr. Bailly's experiences with the "Random Timer". Perhaps the tense atmosphere which must be in evidence in places where roulette is played is a factor which should be taken into account.

A. J. Fisher,
Hereford

Discord

Sir—I would like to take to task your correspondent Mr Malcolm Pointon regarding his article "Electromuse" in the September issue of P.E. He is altogether making too big a deal about synthesisers and electronic music generally.

What is this new phase we are entering in 1974? Evidently Mr Pointon overlooks the fantastic new phase of electronic music (in its own right) in the early 50's when no-one

knew where it was leading—except Stockhausen; or the pioneers of voltage control whose work was consolidated by R. A. Moog in the mid-sixties. No, Mr Pointon, the only new phase entered into in 1974 was my acquisition of a synthesiser and an incredible education in electronics thanks to Messrs. G. D. Shaw and P.E. Music, I'm afraid, is always wallowing in primeval mud waiting for the particles to settle (at least it has been ever since someone discovered the great polyphonic era was not the musical ultimate).

What seven modes were used in early music? As far as I know only six were used. The seventh (Locrian) has never been used except as a joke—no doubt because of its peculiar interval relationships, there being no perfect fifth from the "keynote".

Regarding the emancipated second half of the twentieth century, I cannot see how this suddenly makes the aural universe boundless and open to anyone. It always has been for someone having the will to pursue it. Wagner, Stravinsky *et al.* chose dynamics from the inaudible to the painful; Alois Haba played "between the cracks"; Liszt and Paganini are known for playing music unperformable by a human being... In any event, how much of our human-being music can be played by machine? I'd be delighted to hear from anyone who has patched Stravinsky's "Rite of Spring" or Ravel's "Daphnis and Chloe" on a synthesiser.

Lastly, how are we "widening our horizons beyond the natural?" With electronics? If Mr Pointon is suggesting that acoustic instruments are natural, a quote from "Studio Sound", May 1972, page 33, would be in place:


"The synthesiser is no more artificial than a saxophone. The one produces sound from vibrating electronics, the other from a vibrating reed, the harpsichord from vibrating strings... etc."

Coming to terms, the synthesiser is nothing more than a labour-saving device. Most of the gadgets contained therein have been around for a long time in one form or another. Dr Moog spotted the commercial value of putting them all in the same box, and Mr G. D. Shaw repackaged this to the less wealthy, like myself, who could not afford Dr Moog's prices.

Tragically, many synthesisers will fall to a fate best summarised by a further quote from the above journal: "But, for the love of music, avoid the trap which faces composers of electronic pop: using a £7,500 synthesiser to imitate unconsciously but all too successfully a cheap divider organ. It has been done and it degrades the most promising invention since the development of the chromatic keyboard."

Ivor Stuart-Colwill,
London, S.W.16.

Quadraphonic Project 80

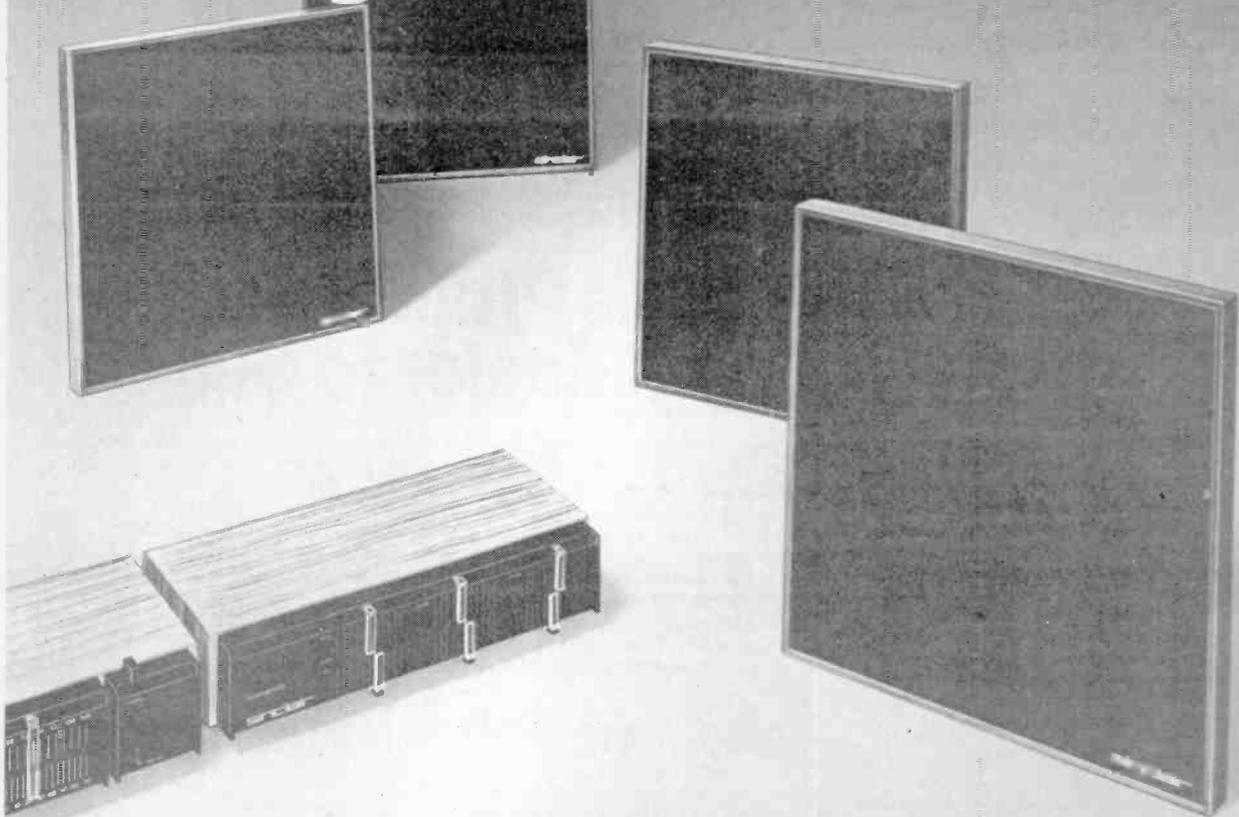

Sinclair's 4th dimension in high fidelity

Project 80

The slim modules for building stereo, hi-fi with FM.

Project 805

Project 80 made even easier to build

Project 805SQ

The add-on assembly that gives you quadraphony

Q16 Loudspeakers

The square speakers for 4 channel listening

Four channel listening has arrived!

Thanks to Project 80 versatility and marvellous compactness, adding two more channels is easy, efficient and economical – you simply add on Project 805SQ, or select the necessary modules from the Project 80 range detailed on the fourth page of this advertisement. Another way is to start with the new Project 805 (which is Project 80 complete in one pack) and add B05SQ to it. Our technicians have adopted the CBS SQ matrix principle to carry the rear left and right channels since it is already clearly the most widely used method in quadraphonic recordings. The decoder, however, can be modified to discrete systems without difficulty. Sinclair suitability for quadraphonics by no means stops with Project 805SQ. The Q.16, always a superb loudspeaker in its own right becomes one of the best ways of creating effective ambience without taking up too much space or money. Project 80 quadraphonic modules are ready now for you to enjoy both stereo and true quadraphonics right away with better reproduction from mono records as well.



Stereo 80 pre-amp/control unit



Project 80 F.M. tuner



Project 80 stereo decoder




Project 80 active filter unit



Project 805SQ quadraphonic decoder

sinclair

Forward with Project 80 into

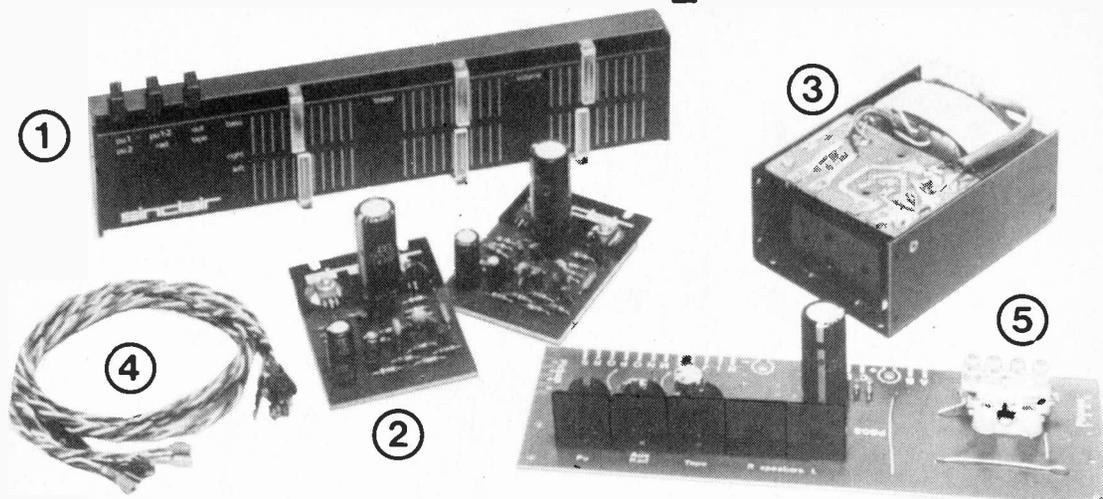

Everything you want in one pack to build the world's most advanced modular hi-fi WITHOUT SOLDERING

- 1 Stereo 80 Control Unit
For mag. and ceramic cartridges, radio and tape.
- 2 Project 80 power amplifiers
Two Z.40s to give 8/8 watts R.M.S. output per channel.
- 3 Power supply unit
One PZ.5.
- 4 Connecting wires
All wires plus nuts, bolts, screws etc.
- 5 Project 805 Masterlink
For input and output connections.
- 6 Mains switch block and instructions manual (not illustrated).

This is Project 80 made even easier to build

You have seen how the marvellously compact Project 80 modules (only 2" high \times $\frac{3}{4}$ " deep) are so adaptable and easy to install. Now, with Project 805, this wonderful system is made easier still to put together. In this, you have not only all the Project 80 modules in one pack for building an 8/8 watt R.M.S. hi-fi amplifier – there is also a loom of colour coded wires cut to length and tagged for clipping on so that you don't even have to solder! Input and output connections go via the 805 Masterlink panel. With the explicit stage-by-stage large 32 page instructions manual included, it becomes easy for anyone, no matter how inexperienced to install an ultra-modern assembly so advanced in appearance and design that it sets brand new concepts in domestic hi-fi – and of course, you can convert to quadraphony just whenever you wish by adding 805SQ. Only Sinclair know-how and manufacturing facilities could hope to bring you such quality and versatility.

TAGGED WIRES CUT TO LENGTH · NO SOLDERING


Project 805

the complete ready-to-build hi-fi
STEREO AMPLIFIER

Project 805 comprises a Stereo 80 Pre-amp/Control Unit with input for both magnetic and ceramic cartridges, radio, tape; separate bass and treble cut/lift, and volume controls 2 \times Z.40 power amplifiers, PZ.5 power unit, 805 Masterlink, wire loom, instructions manual, etc. down to nuts, bolts and washers. For technical specifications, see fourth page of this advertisement.

£39.95


+£3.20 VAT (R.R.P.)

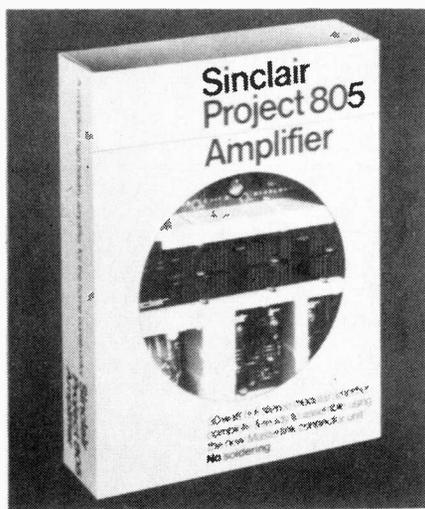


SINCLAIR RADIONICS LTD
London Rd, St. Ives, Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64646

sinclair

true quadraphonics... *NOW!*

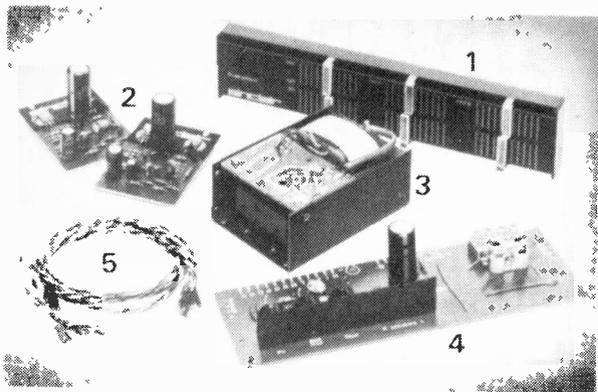

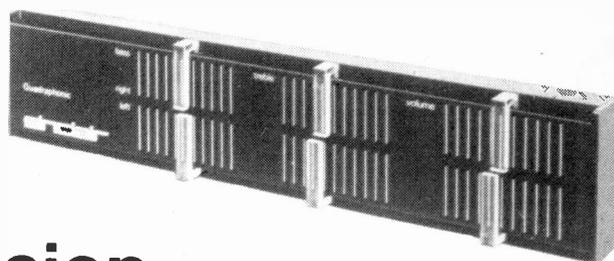The most effective and economical way to enjoy this spectacular breakthrough in hi-fi listening



1. Project 80SQ decoder with controls.
2. Two Z.40 power amplifiers.
3. PZ.5 power pack
4. Project 80Q Masterlink unit.
5. Wire loom, with clip-on tags - NO SOLDERING!
6. (Not illustrated) Instructions manual, nuts bolts, washers, etc.


Add a fourth dimension to your stereo sound

It's so simple to convert to quadraphonics when you already have Project 80, or are about to start with Project 805. Project 805SQ is a complete add-on system at the heart of which is the Project 80SQ decoder. It uses the CBS.SQ matrix principle, by now the widest used method of containing four sound channels within the groove of the record. Project 805SQ includes two power amplifiers, power supply unit, connecting wire loom, 805Q Masterlink, switch block and instructions manual. The 80SQ decoder (also obtainable separately) has independent tone and volume slider controls on the two rear channels for matching true four channel sound to domestic environment. Project 805SQ is money saving too since you do not have to scrap existing Project 80 equipment to enjoy the newest and most exciting form of home listening in the entire history of sound, and your Project 80 quadraphonic assembly is compatible with stereo and mono records.

- Frequency response $\pm 3\text{db}$ 15 Hz-25kHz
- Rated output 100mV
- S/N ratio 58dB
- Distortion 0.1%
- Power requirements 22-35 volts
- Phase shift network $90^\circ \pm 10^\circ$ 100 Hz-10kHz
- Adaptable to discrete (CD4) use



Project 805SQ

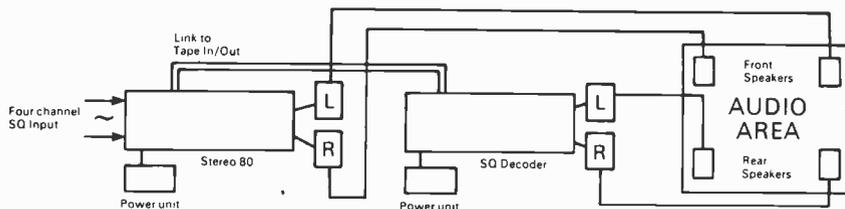

The output from any good stereo cartridge feeds into Stereo 80 and passes via the tape outlet to the 80SQ decoder. Here the signal is separated into its constituent 4 channels, those for the front being accepted by the Stereo 80, those for the rear going from the decoder to the two additional power amplifiers and speakers.

£44.95

+£3.60 VAT (R.R.P.)


Guarantee If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair Appointed Stockists also offer this guarantee. Should any defect arise in normal use within 2 years, we will service it without charge. For damage arising from mis-use a nominal charge will be made.

Project 80 quadraphonic modules may be purchased separately if required. The Project 80SQ decoder may be used with any other amplifier having tape and monitoring facilities. Z40 or Z60 power amps can be used as required.

The Project 80 programme to date

KEEP THIS PAGE FOR HANDY REFERENCE USE THE PRIORITY ORDER FORM IN CASES OF DIFFICULTY


Stereo 80 pre-amp/control unit

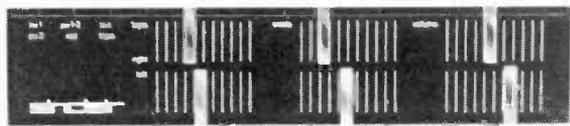

260x50x20mm (10 $\frac{1}{4}$ x2x $\frac{3}{4}$ ins.) separate slider controls on each channel for treble, bass and volume. INPUTS - Mag. P.U. 3mV (RIAA corrected) ceramic - 300mV, Radio 100mV, Tape 30mV S/N ratio 60dB. Frequency range - 20Hz to 15KHz \pm 1dB. OUTPUTS - 2.5V rms max (30V supply) and tape plus AB monitoring. PRESS BUTTONS for P.U., Radio and Tape. Operating power - 20 to 35V. Black case with white indications

£13.95 ^{+£1.12} VAT (R.R.P.)

Project 80 F.M. tuner

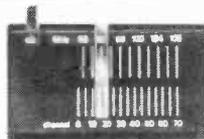

Size 85x50x20mm (3 $\frac{3}{4}$ x2x $\frac{3}{4}$ ins.). Tunes 87.5 to 108MHz. DETECTOR - I.C. balanced coincidence (I.C. equivalent to 26 transistors) Distortion - 0.2% at 1KHz for 30% modulation. SENSITIVITY - 5 microvolts for 30dB quieting. Output - 300mV for 30% modulation. Aerial imp. - 75 Ω or 240-300 Ω . Dual Varicap tuning. 4 pole ceramic filter. Switchable A.F.C. Operating power 23-30 volts.

£13.95 ^{+£1.12} VAT (R.R.P.)


Project 80 stereo decoder

Size 47x50x20mm. For adding to Project 80 FM tuner. With one I.C. equal to 19 transistors, and LED indicator which glows on tuning in stereo signal.



£8.95 ^{+72p} VAT (R.R.P.)

Project 80 active filter unit (A.F.U.)

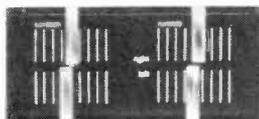

Size 108x50x20mm. Useful where there is need to eliminate unwanted high frequencies (scratch, whistle, etc) or low (rumble). Voltage gain - minus 0-2dB. Frequency response (filter at zero) 36Hz to 22KHz. H.F cut (scratch) variable from 22KHz to 5.5KHz 12dB/octave slope. L.F cut (rumble) - 28dB at 28Hz, slope 9dB/octave.

£7.45 ^{+60p} VAT (R.R.P.)

Project 80 power amplifiers

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced

Z.40

Size - 55x80x20mm
9 transistors

Input sensitivity - 100mV

Output - 12 watts RMS continuous into 8 Ω (35V)

Frequency response - 10Hz - 100KHz \pm 1dB

S/N ratio - 64dB

Distortion - 0.1% at 10 watts into 8 Ω at 1KHz

Power requirements - 12 to 35 volts



£5.95 ^{+48p} VAT (R.R.P.)

Z.60

Size - 55x98x20mm

12 transistors

Input sensitivity - 100-250mV

Output - 25 watts RMS

continuous into 8 Ω (50V).


Distortion - 0.02% at 10W/8 Ω /1KHz

Frequency response - 10Hz to more than 200KHz \pm 3dB

S/N ratio - better than 70dB

Built-in protection against transient overload and short circuiting

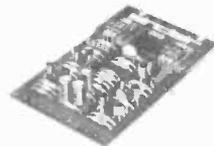Load impedance - 4 Ω min; max. safe on open circuit



£7.45 ^{+60p} VAT (R.R.P.)

Power-supply units

PZ.5 Unstabilized 30 volts. Suitable for Z.40 assemblies, etc.

£5.95 ^{+48p} VAT (R.R.P.)

PZ.6 Stabilized. Output voltage adjustable between 20 and 50 volts approx. Protecting fuse.

£8.95 ^{+72p} VAT (R.R.P.)

PZ.8 Stabilized. Output adjustable from 20 to 60V. approx. Re-entrant current limiting makes damage from overload or even shorting, impossible. Without mains transformer.


£8.45 ^{+68p} VAT (R.R.P.)



Project 805 (previous pages) **£39.95** ^{+£3.20} VAT (R.R.P.)

Project 805SQ quadraphonic add-on kit **£44.95** ^{+£3.60} VAT (R.R.P.)

Project 80SQ quadraphonic decoder

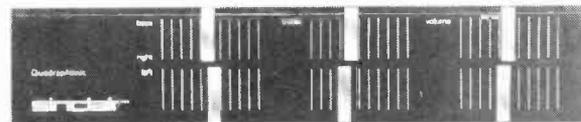


Size 260x50x20mm, matching Stereo 80 in style. Connects with tape socket on stereo 80 or similar facility on any stereo amplifier. Frequency response 15Hz to 25KHz \pm 3dB. Distortion 0.1%. S/N ratio 58dB. Rated Output - 100mV. Separate bass and treble slider controls on each channel, also volume. Phase shift network 90 \pm 10; 100Hz to 10KHz. Operating power - 22-35V.

£18.95 ^{+£1.52} VAT (R.R.P.)

Sinclair Q.16 loudspeaker

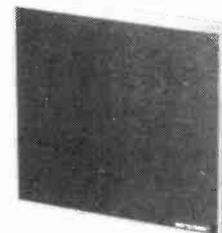An original and uniquely designed speaker of outstanding efficiency. Balanced sealed sound chamber and special driver assembly. Loads up to 14 W./R.M.S. 8 ohms imp. Size 248mm squarex120mm deep. Pedestal base. All-over black front, teak surround.



£8.95 ^{+72p} VAT (R.R.P.)

sinclair

Sinclair Radionics Ltd.,
London Road St. Ives
Huntingdonshire PE17 4HJ
Telephone St. Ives (0480) 64311
R.O. St. Ives: Reg No. 6994583 Eng.

USE THIS PRIORITY ORDER FORM IN CASES OF DIFFICULTY

To Sinclair Radionics Ltd.
Please send, (carriage paid in U.K.)

NAME

ADDRESS

For which I enclose £ cash/
cheque/money order INCLUDING V.A.T.



FREE SCREWDRIVER

(ACTUAL SIZE 2 7/8 INCHES LONG)

Specially made for readers of *Practical Wireless* this mini-screwdriver is ideal for the intricate work involved in radio construction – and it comes, exclusively, in this month's issue of *Practical Wireless*.


START BUILDING THE PRACTICAL WIRELESS 'KEMPTON' CAR STEREO CASSETTE PLAYER

This issue of *Practical Wireless* also contains Part 1 of a new series giving full constructional details for making this unique cassette tape unit.

DECEMBER ISSUE ON SALE NOW. 25p.



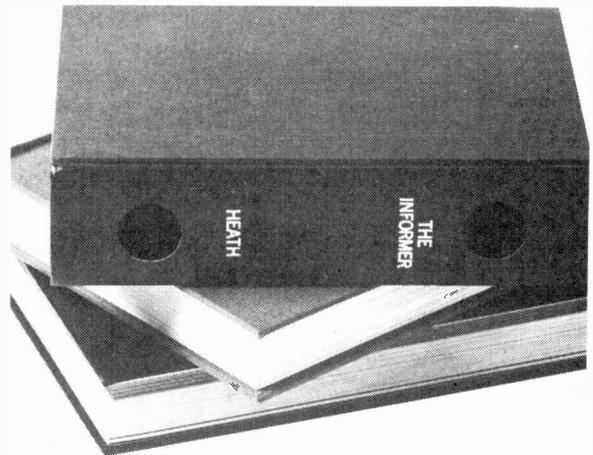Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.

A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.


The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylights out of a burglar.

For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

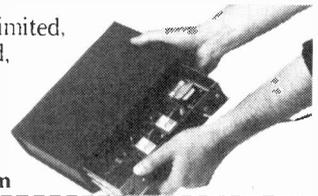Heath (Gloucester) Limited,
Dept. PE124, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.



The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PE124, Gloucester GL2 6EE. Please send me a free Heathkit catalogue.




Name _____

Address _____

Postcode _____

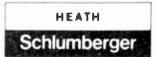Remember easy terms are available with the Heathkit Monthly Budget Plan.



CHROMASONIC electronics

Dept. 2.
56, Fortis Green Road, London, N10 3HN
Telephone: 01 883 3705

OPTOELECTRONICS

Monsanto

Xalton

litronix



Red
Green
Yellow

Common Anode
MAN 72 MAN 74
Common Cathode
MAN 52 MAN 54
MAN 82 MAN 84
Overflow (-1)
MAN 73
MAN 53
MAN 83
L/H Dec. Pt. R/H Dec. Pt.

DL 707
0.3" high character
14 pin DIL
DL 701
(-1)
Common Anode
Red Only

DL 747
0.6" high character
L.H. Dec Pt.
DL 746
(±1)
Common Anode
Red Only

OUR PRICE £2.59

£1.83

£2.65

LIGHT EMITTING DIODES

Free snap-on plastic retainer

0.125" dia

0.2" dia

TIL209 size

MLED650 size



10 RED
10 GREEN
10 YELLOW
10 WHITE
10 ORANGE

Our Usual price

Special Pack Price

Our Usual price

Special Pack Price

0.175" dia T092 size

10 RED

OUR PRICE £1.39

LINEAR I.C.'s

709 (8 pin dip)	33p	LM377	£2.91	SL414	£1.725
709 (TO-99)	39p	LM380	£1.08	SL415	£2.24
709 (14 pin dip)	34p	LM381	£2.26	SL440	£2.84
710 (8 pin dip)	34p	LM382	£2.19	SN75491	£1.43
710 (TO-99)	39p	LM3900	73p	SN75492	£1.63
710 (14 pin dip)	38p			TAA263	80p
711 (TO-99)	44p	MC 1303L	£1.85	TAA300	£1.76
711 (14 pin dip)	38p	MC 1306P	54p	TAA310	£1.34
723 (TO-99)	94p	MC 1310P	£3.05	TAA320	97p
723 (14 pin dip)	64p			TAA350	£2.51
741 (8 pin dip)	31p	MC 1312	£2.42	TAA370	£5.05
741 (TO-99)	44p	MC 1314	£4.05	TAA550	80p
741 (14 pin dip)	42p	MC 1315	£5.37	TAA570	£1.62
747 (14 pin dip)	90p			TAA700	£3.56
748 (8 pin dip)	41p	MC 1330P	86p	TAD100	£1.53
748 (TO-99)	44p	MC 1339P	£1.26	TBA231	88p
748 (14 pin dip)	42p	MC 1350	81p	TBA500	£2.85
		MC 1352	£1.08	TBA530	£1.94
AY-1-0212	£5.99	MC 1357	£1.56	TBA540	£1.96
AY-5-1224	£4.59	MC 1358	£1.65	TBA560C	£2.92
AY-5-3507	£7.45	MC 1375	£1.38	TBA625A	£1.03
AY-5-3510	£6.92	MC 1456CG	£1.71	TBA625B	£1.03
		MC 1456CG	£1.71	TBA625C	£1.03
BHA0002	£3.87	MC 1458CP1	£2.37	TBA651	£1.62
CA3046	93p	MC 1468G	£2.47	TBA800	96p
CA3065	£1.53	MC 1495G	£5.54	TBA810S	£1.07
CA3075	£1.62	MC 3302	£1.30	TBA810AS	£1.07
CA3081	£1.61	MC 3401	75p	TBA820	74p
CA3082	£1.62	MFC 4000B	40p	TCA940	£1.94
		MFC 4006A	76p	TDA1200	£2.10
100571	£1.45	MFC 4033A	81p	TDA1405	97p
103671	£1.45	MFC 6040	£1.08	TDA1412	97p
103771	£1.45			TDA1415	97p
L129	£1.39	MMS314	7.76	ULN 2111A	1.56
L130	£1.39	MMS316	£16.17	ZN402E	1.94
L131	£1.39			ZN414	1.29
LM301 (TO-99)	59p	MVESV	£1.62		
LM301 (8 pin dip)	52p	MVR12V	£1.62		
LM307 (TO-99)	59p	MVR15V	£1.62		
LM307 (8 pin dip)	52p	NE540	£1.29		
LM308 (TO-99)	£1.26	NE555	70		
LM308 (8 pin dip)	97p	NE556	£1.62		
LM309K	£2.36	NE568	£4.82		
LM339	£3.68	NE561B	£4.82		
LM371	£2.04	NE562S	£4.82		
LM372	£2.43	NE565	£2.74		
LM373	£3.04	NE566	£2.69		
		NE567	£2.74		

Back in stock again!

HC244R

The Stabilized Power supply for which demand always exceeds supply switched 3, 6, 7, & 9 volts up to 400 mA

Polarity reversal switch; Neon Mains Indicator; on/off switch; 4ft Lead

Multi-Way output plug adaptor; Metal Case; Rubber Feet

£4.89 * p & p 16p

74 SERIES TTL

1st GRADE BRANDED PRODUCTS

7400	17p	7442	90p	7490	68p
7401	17p	7445	1.20	7491	1.10
7402	17p	7447	1.15	7492	80p
7403	17p	7447A	1.76	7493	70p
7404	17p	7448	1.47	74100	2.32
7406	25p	7470	32p	74121	50p
7409	29p	7473	33p	74122	85p
7410	17p	7474	40p	74141	1.07
7413	29p	7475	62p	74154	1.76
7420	17p	7476	42p	74192	2.11
7430	17p	7486	35p	74193	2.45
7441	90p	7489	4.65	74196	1.70

F.M. STEREO TUNERS

SIEMENS LCD's

Transistor F.M. Tuner Chassis, 9 volt. Operation. A1005 5 £8.04



New Mini F.M. Tuner * 12 volt supply £6.76 Matching Stereo Decoder £4.86

Stereo Decoder to match A1005 M5 £6.08




LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing; Ref AN4132R 13mm character height. Can be directly driven by National Semiconductor Alarm Clock chip MMS316.

OUR PRICE £13.99

24 HOUR DESPATCH NOW IN OPERATION

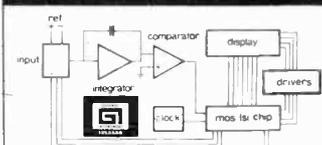3 1/2 DECADE DIGITAL VOLTMETER INTEGRATED CIRCUIT



This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £7.46

(booklets alone 20p)

PHOTO-DARLINGTON

Mullard



2N577
V_{ceo}, V_{cb} 25v; V_{eb} 0v
V_{ceo}, V_{cb} 25v; V_{eb} 0v
I_{fe} 2500; I_c 250 mA



LP1186 Diode - tuned Front End £4.65
LP1185 F.M. I.F. Amplifier £5.38
LP1400 Stereo Multiplier/Decoder £4.86


This trio make one of the most fabulous F.M. tuners of all time. Typical channel separation 50 db.

SPECIAL OFFERS

Left Hand Decimal Point
All Common Anode.
Character Height 0.3"

4 for £5.99
5 for £7.45
6 for £8.93

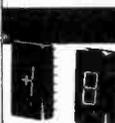RED (Led 7)
GREEN (Led 18)
YELLOW (Led 21)



MINITRON

Filament Indicators, 16 Pin DIL 10mm Character Height
0-9 Digit Ref 3015F
- 1 Overflow/Polarity Ref 3015G

NEW PRICE £1.26

VAT INCLUDED AT 8%

OVERSEAS CUSTOMERS DEDUCT 2/27
VAT INVOICES ON REQUEST
P&P On U.K. Orders min 15p

CALLERS WELCOME

RESISTORS

The standard ranges of Resistors stocked are either E12 or E24 and the values are all in multiples of ten times the decade shown below. The E12 items are only those in bold type. The E24 items are both those in bold and light type.

10	18	33	56
11	20	36	62
12	22	39	68
13	24	43	75
15	27	47	82
16	30	51	91

CARBON FILM $\frac{1}{2}$ watt \pm 5% tol. 2p ea.
E12 Series 10 to 330K

CARBON FILM $\frac{1}{2}$ watt \pm 5% tol. 1p ea.
E24 Series 10 to 10M

'CERMET' THICK FILM $\frac{1}{2}$ watt \pm 2% tol. 8p ea.
E12 series 56 to 150K

METAL OXIDE FILM $\frac{1}{2}$ watt \pm 2% tol. 4p ea.
E12 series 10 to 1M

CARBON COMPOSITION $\frac{1}{2}$ watt 4p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; \pm 0.5 tol.
5.6 ; 6.8 ; 8.2 \pm 10% tol.

CARBON COMPOSITION 1 watt 5p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; \pm 0.5 tol.
5.6 ; 6.8 ; 8.2 \pm 10% tol.

CARBON FILM 1 watt \pm 5% tol. 3p ea.
E12 series 10 to 10M

CARBON FILM 2 watt \pm 5% tol. 6p ea.
E12 series 10 to 10M

WIREWOUND 2 $\frac{1}{2}$ watt \pm 5% tol 0.22 to 0.47 15p
E12 series \pm 10% tol 1 to 270K 13p

WIRE WOUND 5 WATT 13p ea.

1	25	250	1.5K
1	30	270	1.8K
1.8	39	300	2K
2.2	50	330	2.2K
2.7	60	350	2.5K
3.3	88	400	2.7K
3.9	75	470	3K
4.7	82	500	3.3K
5	100	560	3.5K
5.6	125	600	3.9K
6.8	133	680	4.7K
8.2	150	750	5K
10	180	820	5.6K
15	200	1K	4.8K
21	220	1.2K	8.2K

WIRE WOUND 10 watt 14p ea.
All the values shown in bold in the 5 watt range

WIRE WOUND 10 watt \pm 5% tol. 20p ea.
10K ; 15K ; 20K ; 25K

WIRE WOUND 15 watt 13p ea.
All the values from 10 upward shown in bold in the 5 watt range.

POTENTIOMETERS



5K 250K Log or Lin Less Switch (and 1K Lin) 14p
10K 500K Log or Lin with Switch 26p
25K 1 Meg Dual Less Switch 46p
50K 2 Meg 1 Meg Log only 57p
100K 10K Log + 10K Anti-log Less Switch 46p

Sliders
10K Single 33p
50K DUAL 55p
100K

Presets Vertical or Horizontal
1 Watt 5p 25 Watt 7p
100 1K 10K 100K 1Meg
250 2.5 25K 250K 2.5 Meg
500 5K 50K 500K 5Meg

Cermets
100 2.5K 25K 250K
500 5K 50K 500K
1K 10K 100K 1Meg
40p

CAPACITORS

Ceramic Plate
Mullard C333 Series 63 Volts Wkg.
all at 5p each
1.8pF \pm 0.2pF 12pF \pm 2% 88pF \pm 2%
2.2pF 15pF 82pF
3.3pF 18pF 100pF
3.9pF 22pF 120pF
4.7pF 27pF 150pF
5.6pF 33pF 180pF
6.8pF 39pF 220pF
8.2pF 47pF 270pF
10 pF 56pF 330pF

Mullard 630 series 40 volts \pm 10% tol
629 series 100 volts
all at 5p each
390 pf 1000 pf 3300 pf
470 pf 1200 pf 3900 pf
560 pf 1500 pf 4700 pf
680 pf 1800 pf * 10 nf
820 pf 2200 pf * 22 nf
2700 pf

Eric Monolithic Ceramic 30 Volts Wkg.
27 nf 11p; 47 nf 13p; 100 nf 17p

Low Voltage Disc Ceramics
all at 5p each
0.01 uF 18v ; 0.1 uF 30v
0.022 uF 18v ; 0.22 uF 6v
0.047 uF 18v ; 0.47 uF 3v

Mylar Film 100 Volts Wkg.
1000 pf 23p ; 0.05 uF 33p
2000 pf 23p ; 0.068uF 5p
5000 pf 23p ; 0.1 uF 5p
0.01 uF 33p ; 0.2 uF 63p
0.02 uF 33p ; 0.47 uF 7p
0.04 uF 33p

Polystyrene
MULLARD C295 Series 63 volts
Tolerance = 1% Polystyrene
6.800pF (6.8nF) C295 AH D8K8 11p
8.200pF (8.2nF) C295 AH D8K2 11p
13.000pF (13nF) C295 AH D13K 15p
16.000pF (16nF) C295 AH D18K 15p
20nF (0.02uF) C295 AH D20K 15p
30nF (0.03uF) C295 AH D30K 18p
39nF (0.039uF) C295 AH D39K 18p
51nF (0.051uF) C295 AH D51K 25p

Polystyrene 160 volts Wkg
Tolerance = pF up to 33pF = 5% 47pF up
10 pF to 10,000 pF (0.01 uF) in multiples of:
10 ; 15 ; 22 ; 33 ; 47 ; 68.
all 5p each
Nimarks 0.22uF : 5% 1000 11p
Wima MKS 0.22uF
: 5% 100V 11p

Mullard C280 Series 250 Volts Wkg.
Metalized Polyester Film
0.01 uF 33p ; 0.22 uF 53p
0.015 uF 33p ; 0.33 uF 7p
0.022 uF 33p ; 0.47 uF 9p
0.033 uF 33p ; 0.68 uF 12p
0.047 uF 33p ; 1.0 uF 14p
0.068 uF 4p ; 1.5 uF 22p
0.1 uF 43p ; 2.2 uF 26p
0.15 uF 43p

Mullard C281 series 400 volts Wkg
Metalized Polycarbonate Film 10%
0.01 uF 5p ; 0.1 uF 8p
0.015 uF 5p ; 0.15 uF 9p
0.022 uF 5p ; 0.22 uF 11p
0.033 uF 6p ; 0.33 uF 15p
0.047 uF 6p ; 0.47 uF 16p
0.068 uF 6p ; 0.68 uF 16p
0.1 uF 6p ; 1.0 uF 16p

VDR's & Thermistors

CZ1 17p
CZ4 18p
CZ13A 18p
CZ19 18p
E298CDA258 13p
E298DA260 13p
E298DA262 13p
E298DA265 13p
E298DP268 13p
E298Z205 13p
E298Z206 13p
E299DDP336 14p
E299DDP338 14p
E299DDP342 14p
E299DDP348 14p
GL16 E1 21
GL23 E1 21
R53 E1 49
R54 E1 61
VA1005 16p
VA1026 16p
VA1033 16p
VA1034 16p
VA1039 16p
VA1040 16p
VA1053 16p
VA1055S 16p
VA1056S 16p
VA1066S 17p
VA1067S 19p
VA1077 21p
VA1098 31p
VA1104 29p
VA1107 29p

CAPACITORS

Silvered Mica 350V.
Tol. \pm 0.5pf 11p each
2.2 pf 18pf 30pf
3.3 pf 20pf 33pf
5 pf 22pf 39pf
10 pf 25pf 47pf
Tol. \pm 1% 11p each
50pf 150pf
56pf 82pf 180pf
68pf 100pf 200pf
75pf 120pf 220pf
12p each
250pf 330pf 560pf
270pf 390pf 680pf
300pf 470pf 820pf
300pf
E1 21 17p each
E1 21 17p each
R53 1500pf 220pf
R54 1800pf
26p each
2700pf 3600pf 5000pf
4700pf
33p each
6800pf 8200pf 10000pf

Mixed Dielectric 600 Volts Wkg.
0.01 uF 8p ; 0.1 uF 9 p
0.022 uF 8p ; 0.22 uF 173p
0.033 uF 8p ; 0.47 uF 263p
0.047 uF 8p ; 1 uF 363p
0.068 uF 9p
Mixed Dielectric 1000 Volts Wkg.
1000 pf 63p ; 0.022uF 11p
2200 pf 63p ; 0.047uF 13p
3300 pf 7p ; 0.1 uF 13p
4700 pf 7p ; 0.22 uF 243p
0.01 uF 10p ; 0.47 33p

Solid Tantalum Beads
all at 18p
0.1 uF 35v ; 10 uF 6.3v
0.22 uF 35v ; 10 uF 16v
0.47 uF 35v ; 10 uF 25v
1.0 uF 35v ; 22 uF 16v
2.2 uF 35v ; 47 uF 6.3v
4.7 uF 35v ; 100 uF 3v

Feed-through Ceramics
1000 pf 350v 6p

Disc Ceramics 750 Volt Wkg.
all at 5p each
470 pf; 1000 pf; 5000 pf; 0.01 uF

Tubular HI-K Ceramics 750 Volts Wkg.
1000 pf 5p 3000 pf 5p
1500 pf 5p 5000 pf 5p
2000 pf 5p 0.01 uF 5p

Pulse Ceramics all at 10p each
12 kv D.C. Wkg
10pf 120pf 200pf
22pf 140pf 220pf
48pf 150pf 250pf
82pf 100pf 270pf
100pf 200pf 300pf

VAT INCLUSIVE PRICES AT 8% OVERSEAS CUSTOMERS DEDUCT 2/27
VAT INVOICES ON REQUEST
R.&P. On U.K. Orders 15p. Overseas Orders at Cosl

C. T. ELECTRONICS

NOW AT 267 & 270 ACTON LANE, LONDON W4 5DG

Now open—our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you speedier service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 a.m. through till 6.0 p.m. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.

SEMICONDUCTORS

AC107	35p	BCY30	40p	MJ340	55p	OC36	85p	TIP41C	95p	2N2846	£1.50
AC125	25p	BCY31	55p	MJ481	85p	OC42	40p	TIP42C	£1.10	2N2904	25p
AC126	25p	BCY32	55p	MJ2801	£1.25	OC44	20p	T1550	40p	2N2905	25p
AC127	27p	BCY33	45p	MJ2901	£2.20	OC45	20p	ZX1701	15p	2N2906	25p
AC128	28p	BCY34	80p	MJE340	50p	OC70	15p	ZX3000	15p	2N2907	25p
AC176	27p	BCY38	85p	MJE370	75p	OC71	17p	ZX5000	16p	2N2926	25p
ACV17	25p	BCY39	£1.00	MJE371	80p	OC72	20p	ZX5001	20p	2N3053	25p
ACV18	30p	BCY55	£1.80	MJE520	85p	OC75	25p	ZX5004	50p	2N3054	85p
ACV19	30p	BCV70	22p	MJE2955E	18p	OC76	25p	ZX5011	30p	2N3055	85p
ACV20	25p	BCV71	22p	MJE3555	45p	OC77	40p	ZX5050	25p	2N3232	78p
ACV21	30p	BCV72	25p	MM1613	43p	OC81	25p	IN659	8p	2N3255	85p
ACV39	55p	BD121	75p	MM1712	80p	OC83	25p	IN914	8p	2N3702	44p
AD140	60p	BD123	75p	MPF102	45p	OC84	25p	IR1616	8p	2N3703	12p
AD142	65p	BD124	80p	MPF103	45p	OC89	30p	IN4001	9p	2N3705	12p
AD149	85p	BD131	75p	(2N5457)	35p	OC170	25p	IN4002	9p	2N3705	12p
AD161	40p	BD132	75p	MPF104	45p	OC171	30p	IN4003	9p	2N3706	12p
AD162	40p	BD153	75p	(2N4580)	35p	OC200	60p	IN4005	10p	2N3707	12p
AF114	25p	BD156	75p	MPF105	45p	OC201	60p	IN4005	10p	2N3707	12p
AF115	25p	BDY11	£1.40	(2N5459)	40p	OC202	75p	IN4006	15p	2N3709	12p
AF116	25p	BDY17	£1.80	MPS400	35p	TIP29A	49p	IN4007	17p	2N3771	£2.75
AF117	25p	BDY19	£1.85	MPSA16	30p	TIP30A	49p	IN4148	7p	2N3772	£2.75
AF118	60p	BF152	20p	MPSA56	35p	TIP31A	80p	2N696	25p	2N3773	£2.85
AF172	30p	BF194	14p	MPSU06	75p	TIP32A	74p	2N697	20p	2N3819	35p
ASV28	30p	BF195	15p	MPSU56	70p	TIP33A	£1.05	2N698	25p	2N3820	55p
ASZ21	60p	BFX29	30p	MPSU57	70p	TIP32B	£1.55	2N706	12p	2N3866	85p
BA102	33p	BFX34	30p	NKT221	25p	TIP35A	£1.35	(2N706A)	15p	2N3775	£2.85
BA112	50p	BFX35	30p	NKT401	85p	TIP36A	£2.25	2N708	15p	2N3905	25p
BA114	16p	BFX36	80p	NKT404	80p	TIP41A	75p	2N930	20p	2N4058	12p
BA156	15p	BFX38	30p	NKT405	90p	TIP42A	90p	2N1332	25p	2N4059	12p
BC107	14p	BFY10	10p	NKT774	25p	TIP29B	80p	2N1302	18p	2N4061	12p
BC108	14p	BFY44	50p	OA10	20p	TIP30B	80p	2N1303	16p	2N4061	12p
BC109	15p	BFY50	25p	OA47	10p	TIP31B	70p	2N1304	25p	2N4126	17p
BC147	12p	BFY51	25p	OA79	12p	TIP32B	85p	2N1305	25p	2N4286	15p
BC148	12p	BFY52	25p	OA81	12p	TIP33B	£1.12	2N1306	25p	2N4287	15p
BC149	12p	BFY53	25p	OA79	12p	TIP34B	£1.68	2N1307	25p	2N4288	15p
BC153	15p	BFY90	80p	OA90	10p	TIP35B	£2.81	2N1308	25p	2N4289	15p
BC157	14p	BSW68	80p	OA200	10p	TIP36B	£3.64	2N1309	80p	2N4290	15p
BC158	15p	BSW68	80p	OA200	10p	TIP41B	85p	2N1613	35p	2N4291	15p
BC159	15p	BSY95A	12p	OA202	10p	TIP42B	80p	2N1711	25p	2N4871	35p
BC189C	14p	CI11	50p	OA210	35p	TIP29C	71p	2N2147	70p	2N4920	80p
BC182	14p	BY100	15p	OC16	80p	TIP31C	80p	2N5191	80p	2N5192	£1.10
BC183	14p	BY100	15p	OC16	80p	TIP31C	80p	2N5191	80p	2N5192	£1.10
BC184	14p	BY126	20p	OC19	85p	TIP32C	£1.05	2N2218	25p	40360	50p
BC212	14p	BY127	20p	OC22	55p	TIP33C	£1.30	2N2219	25p	40361	50p
BC213	14p	IS100	15p	OC28	85p	TIP35C	£2.00	2N2222	20p	40362	55p
BC214	14p	IS100	15p	OC28	85p	TIP35C	£2.00	2N2222A	50p	40362	55p
BC238	12p	IS103	20p	OC30	80p	TIP36C	£4.10	2N2398	70p	2N2646	50p
BC239	12p							2N2646	50p		

S.C.R.s

CRS105	40p
CRS110	50p
CRS120	60p
CRS140	60p
CRS160	60p
CRS210	62p
CRS310	62p
CRS410	90p
CRS7400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.60
CI06B	45p
CI06E	70p
40869	90p
2N4444	£1.90
BT10/5004	90p

TRIACS

TXL228B 8A 400V	95p
SC400	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

BRIDGE RECTIFIERS

W02 1A 200V 3P	
BY164 1/4A 200V 5P	
MDA952/2	
6A 100V 80p	
ZENER DIODES	
BZ88 Series 400mW	
3-V-33V.5% 11p	
1.5W range 25p	
10W range 45p	
L.E.D.	
TL120	20p
HP5082	20p
MA2082R	25p
L.D.R.	
ONP12	60p
NE55 Timer	90p

LINEAR I.C.s

LM309K 5V 1A, Volt- age Reg	£2.10
LM723C 2.37V, 150mA Voltage Reg	£1.05
MF4000 250mW Audio 6.5p	
TS800 5 Watt Audio IC	50p
709C Op Amp D.I.L. T099	45p
741C Op Amp 8:14 D.I.L. T099	55p
748C Op Amp D.I.L.	75p
757C Dual Op Amp	£1.20
ZN414 Radio IC	£1.25
TAD100 Radio IC inc Filter	£1.90
CA3014	£1.55
CA3018	£1.00
CA3028	£1.20
CA3036	£1.00
CA3046	95p
CA3048	£2.35
CA3075	£1.60
CA3090Q	£4.85
MC1303L	£2.20

SPECIAL OFFERS

MINIATURE MAINS TRANSFORMER, PRI. 240V SEC. 12V 100MA Manuf. Hinchley Size 30 x 45 x 40mm F.C. 53mm Price 1.85p, 100-80p ea. 1.000-50p ea. 10.000-50p ea.	
3 CORE PVP INSULATED MAINS CABLE, GREY MLE650 3/70 2mm Price 100- £4.90, 1000m-£35, 10.000-£35p	
0.47mf. 50V MYLAR FILM CAPACITOR Size 1in x 0.35in x 0.63in P.C. Mount Price 100-4p ea. 1000-3p ea.	
240V A.C. SOLENOID, Reversible opera- tion, twin coil Size approx 2 1/4 x 1 1/4 90p ea.	
30 unmarked OC71 transistors £1.00	
25 UNMARKED 250mW Zener diodes, 4.7V, 5.1V, 5.6V, 7.5V, 9.1V, 10V Measured and tested	£1.00
Please state voltage required	£1.00
50 GE Diode O447 equivalent	£1.00
TRANSFORMER: DOUGLAS PRI. 0, 1.15, 2.00, 2.20, 240 SEC. 25-0.25-0.6V, 2JA £4.50 + 50p	
TRANSFORMER PRI. 0 1.15, 1.60, 2.05, 2.25, 24S, SEC. 35-0.35, 7.2A 14.5V - 50p, p.p.	
MULTI-PURPOSE CERAMIC VOLT- TRIMMERS (PROFESSIONAL) Type 092 0-8-2 2p } Price 10p ea. 101 801 102 802 103 803	
QUANTITY DISCOUNTS PLEASE TELE- PHONE	
1000pF Feedthrough capacitor 7p ea.	
Miniature PNP P.C. Trimmers 3.5-13pF	10p ea.
40 pin Variator 7000 relay	50p ea.
TO3 VOLTAGE REGULATORS L005 5V 650mA L038 12V 500mA L037 15V 450mA	£1.60 ea.

VEROBORD

2 1/2 x 3 1/2	0	1	0	15
2 1/2 x 3 1/2	32p	23p	35p	35p
3 1/2 x 3 1/2	35p	35p	35p	35p
3 1/2 x 5	40p	41p		
17 x 2 1/2	£1.45	75p		
17 x 3 1/2	£1.45	£1.12		
17 x 5	£1.84	—		
PIN INS TOOL	75p	75p		
SP F CUTTER	30p	50p		
100 PINS SS	30p	30p		
100 PINS SS	30p	30p		
500 PINS SS	£1.90	£1.20		
500 PINS DS	£1.20	£1.20		
Prices Correct June 12				

NEW SERIES TRANSISTOR DATA BOOKS

- 1 DTA3 USA Band 3 Transistor Characteristic 2N21-2N268 all numbers
 - 2 THT Thyristor, Triac Diac, PUT, LJT
 - 3 DTT5 Japanese Transistor Characteristic 2SA 95B, 2SC 25D numbers
 - 4 DVT Diode Comparison Tables
 - 5 Band 1 Transistor Characteristics and component numbers AC, AF, BC, BF etc
 - 6 VTY Transistor Equivalent Tables
- All books contain pin connections and semiconductor cutlines
PRICE £1.10 per book £8 per 6 books inc

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE OF V.A.T. Please add 8% to all orders. Carriage orders under £5 - 20p Over £5 post free

DIGITAL INTEGRAL CIRCUITS

SN7400	20p	SN7428	50p	SN7473	40p	SN74107	50p	SN74166	£4.00
SN7401	20p	SN7430	20p	SN7474	40p	SN74110	80p	SN74167	£5.25
SN7402	20p	SN7432	40p	SN7475	40p	SN74118	£1.00	SN74170	£4.10
SN7403	20p	SN7433	70p	SN7476	45p	SN74119	£1.80	SN74172	£2.00
SN7404	20p	SN7437	85p	SN7480	80p	SN74121	65p	SN74175	£1.80
SN7405	20p	SN7438	85p	SN7481	£1.25	SN74122	£1.35	SN74176	£1.80
SN7406	20p	SN7440	20p	SN7482	80p	SN74123	£2.70	SN74177	£1.80
SN7407	30p	SN7441A	75p	SN7483	£1.00	SN74124	£1.50	SN74178	£1.80
SN7408	20p	SN7442	75p	SN7484	80p	SN74125	£1.50	SN74179	£1.80
SN7409	45p	SN7443	£1.00	SN7485	45p	SN74126	£1.00	SN74180	£1.55
SN7410	20p	SN7445	£2.25	SN7486	80p	SN74127	£1.80	SN74181	£1.00
SN7411	23p	SN7446	£2.00	SN7487	80p	SN74128	£2.00	SN74182	£2.00
SN7412	42p	SN7447	£1.50	SN7488	75p	SN74129	£1.50	SN74183	£2.45
SN7413	30p	SN7448	£1.75	SN7489	75p	SN74130	£1.50	SN74184	£2.40
SN7416	30p	SN7450	20p	SN7494	80p	SN74131	£1.40	SN74185	£2.40
SN7417	30p	SN7451	20p	SN7495	80p	SN74132	£1.55	SN74191	£1.85
SN7420	20p	SN7453	20p	SN7496	£1.00	SN74133	£1.80	SN74192	£2.00
SN7422	48p	SN7454	20p	SN7497	£1.25	SN74134	£2.40	SN74193	£2.00
SN7423	48p	SN7455	20p	SN7498	£1.50	SN74135	£1.40	SN74194	£2.50
SN7425	48p	SN7470	30p	SN74104	£1.45	SN74136	£2.00	SN74195	£1.85
SN7427	42p	SN7472	30p	SN74105	£1.45	SN74137	£1.50	SN74196	£1.50
				SN74106	£1.45	SN74138	£1.50	SN74197	£1.50
				SN74107	£1.45	SN74139	£1.50	SN74198	£1.50
				SN74108	£1.45	SN74			

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £5.45 Carriage free
35W RMS 25-50V
7 transistors, 7 diodes

SA50 £6.90 Carriage free
50W RMS 25-50V
7 transistors, 7 diodes

SA100 £12.50 Carriage free
100W RMS 25-70V
10 transistors, 7 diodes

120 watt module complete with built-in supply—extra heavy duty £22.50 Carr. 60p

- ★ 25Hz-25kHz
- ★ 0.2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED

PU45 Suits 2 SA35 or 1 SA50 (4 ohm) £5.45 Carriage 30p

PU70 Suits 2 SA50 or 2 SA100 (8 ohm) £8.45 Carriage 40p

STABILISED

PS45 Suits 2 SA35 or 2 SA50 (4 ohm) £4.45 Carriage free

MT45 Transformer for above £3.50 Carriage 30p

PS70 Suits 2 SA100 £5.45 Carriage free

MT70 Transformer for above £4.90 Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £22.50

Carr. 30p
This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



DISCO MODULE £9.50

Carr. 20p
Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50

Carr. 30p
Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add 8% VAT to all orders


MULTI-PURPOSE MIXERS

M4HL £19.50 Carr. 50p
M6HL £29.50 Carr. 50p


Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.50

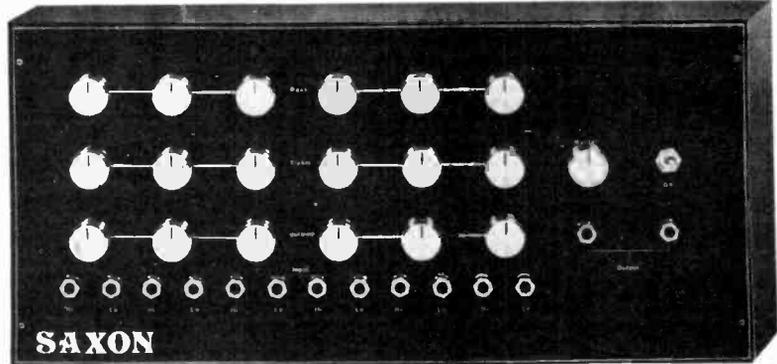Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



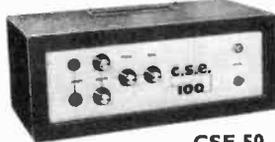SAXON CSE 100 100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29.50 Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

SAXON 100 COMPLETE AMPLIFIER £53.00 Carr. free
SAXON 50 COMPLETE AMPLIFIER £37.50 Carr. free

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.—5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 10p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.
Please include S.A.E. with all enquiries.
VAT at 8% must be added to all orders including carriage charges.

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened

ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 0	7.0 x 6.0 x 6.0	2.55 38
149	60	3 12	9.9 x 7.7 x 8.6	3.79 45
150	100	5 8	9.9 x 8.9 x 8.6	4.17 45
151	200	8 0	12.1 x 9.3 x 10.2	7.39 53
152	250	13 12	12.1 x 11.8 x 10.2	9.45 73
153	350	19 0	14.0 x 10.6 x 11.8	11.35 73
154	500	19 8	14.0 x 13.4 x 11.8	13.30 91
155	750	29 0	17.2 x 14.0 x 14.0	21.05 *
156	1000	38 0	17.2 x 16.6 x 14.0	27.20 *
158	2000	60 0	21.6 x 15.3 x 18.1	50.25 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.34 30
64	75	2 4	6.1 x 5.8 x 4.8	0-115-210-240	2.64 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	3.29 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.29 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.02 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.50 91
93	1500	30 4	14.0 x 15.9 x 14.3	"	17.50 *
95	2000	32 0	17.2 x 16.6 x 14.0	"	25.35 *
73	3000	40 0	21.6 x 13.4 x 18.1	"	32.80 *

CASED AUTO TRANSFORMERS
115V mains lead input and U.S.A. 2-pin outlets, 20VA £2.64, P & P 38p.
500VA £9.50, P & P 80p. 1000VA £15.92, via B.R.S.

LOW VOLTAGE SERIES (ISOLATED) PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0 25	4 8	2.9 x 3.5 0-12V at 0.25A x 2	1.34 23
213	1.0	0 5	4 8	2.9 x 3.5 0-12V at 0.5A x 2	1.58 30
71	2	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.09 38
18	4	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.60 38
70	6	3 3 8	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.52 45
108	8	4 5 8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.96 45
72	10	5 6	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.67 53
116	12	6 12	9.9 x 10.2 x 8.6	0-12V at 5A x 2	5.51 53
17	16	8 8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.62 60
115	20	10 11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	10.20 73
187	30	15 15 8	14.0 x 12.1 x 11.8	0-12V at 15A x 2	13.70 85
226	60	30 32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	22.50 *

30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.58 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.18 38
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.18 38
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.12 45
21	4.0	6 4	9.9 x 9.6 x 8.6	"	4.67 53
51	5.0	6 12	12.1 x 8.6 x 10.2	"	5.83 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	6.94 60
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.00 67
89	10.0	13 12	14.0 x 10.2 x 11.8	"	9.80 73

50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.09 30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.08 38
104	2.0	5 8	7.9 x 8.9 x 8.6	"	4.26 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.79 53
106	4.0	10 0	12.1 x 10.5 x 10.2	"	7.41 67
107	6.0	12 0	14.0 x 10.2 x 11.8	"	11.00 67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	13.40 85
119	10.0	25 0	17.2 x 12.7 x 14.0	"	17.60 *

60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60V	2.12 38
126	1.0	3 4	8.9 x 7.7 x 7.7	"	2.97 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.40 45
125	3.0	8 12	12.1 x 9.9 x 10.2	"	7.11 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	9.20 67
40	5.0	12 0	14.0 x 10.2 x 11.8	"	10.83 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	13.35 85
121	8.0	25 0	14.0 x 14.7 x 11.8	"	15.01 *
122	10.0	25 0	17.2 x 12.7 x 14.0	"	19.60 *
189	12.0	29 0	17.2 x 14.0 x 14.0	"	21.60 *

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P £ p
238	200	2	2.8 x 2.6 x 2.0	3-0-3	1.40 10
212	1A, 1A	1 4	6.1 x 5.8 x 4.8	0-6, 0-6	1.67 30
13	100	4	3.9 x 2.6 x 2.9	9-0-9	1.28 13
235	330, 330	4	4.8 x 2.9 x 3.5	0-9, 0-9	1.42 19
207	500, 500	0 0	6.1 x 5.4 x 4.8	0-9, 0-8-9	2.23 30
208	1A, 1A	1 12	7.0 x 6.4 x 6.1	0-8-9, 0-8-9	3.00 38
236	200, 200	1 4	4.8 x 2.9 x 3.5	0-15, 0-15	1.30 19
214	300, 300	1 4	6.1 x 5.8 x 4.8	0-20, 0-20	1.76 30
221	700 (d.c.)	1 8	7.0 x 6.1 x 6.1	20-12-0-12-20	1.98 38
206	1A, 1A	2 12	8.3 x 7.7 x 7.0	0-15-20, 0-15-20	3.78 38
203	500, 500	2 4	8.3 x 7.0 x 7.0	0-15-27, 0-15-27	3.06 38
204	1A, 1A	3 4	8.9 x 7.7 x 7.7	0-15-27, 0-15-27	3.27 38

PLEASE ADD 8% FOR V.A.T. INCLUDING P. & P.

BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & ALDGATE EAST



MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/volt High Sensitivity Meter £14.40.

TAPE RECORDER LEVEL METER
500µA, 70p



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000/c/s. Impedance Dual 50K and 600 ohms, £6.55.



4 1/2 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £3.65.

MULTI-METER

Model D62
20,000 ohm/volt, £7.00.



3 WATT STEREO AMPLIFIER
£4.30

All above prices include 8% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 10. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB



WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

POST NOW

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Practical Radio and Electronics (Technatron)	<input type="checkbox"/>	Electronic Engineering	<input type="checkbox"/>	Television Maintenance and Servicing	<input type="checkbox"/>	General Radio and TV Engineering	<input type="checkbox"/>	Radio Servicing, Maintenance and Repairs	<input type="checkbox"/>	C. & G. Radio, TV Electronics, Mechanics	<input type="checkbox"/>	Radio Amateurs	<input type="checkbox"/>	Practical TV	<input type="checkbox"/>	Colour Television	<input type="checkbox"/>	Computer Electronics	<input type="checkbox"/>	C. & G. LI Radio TV Servicing cert.	<input type="checkbox"/>	Post Master General 1st & 2nd class certs.	<input type="checkbox"/>	C. & G. Electrical Engineering Practise	<input type="checkbox"/>	C. & G. LI Installations and Wiring	<input type="checkbox"/>	General Electrical Engineering (Electrical Engineering)	<input type="checkbox"/>	Electrical Installations and Wiring	<input type="checkbox"/>	C. & G. Electrical Technicians (Primary)	<input type="checkbox"/>	C. & G. Telecommunications	<input type="checkbox"/>
--	--------------------------	------------------------	--------------------------	--------------------------------------	--------------------------	----------------------------------	--------------------------	--	--------------------------	--	--------------------------	----------------	--------------------------	--------------	--------------------------	-------------------	--------------------------	----------------------	--------------------------	-------------------------------------	--------------------------	--	--------------------------	---	--------------------------	-------------------------------------	--------------------------	---	--------------------------	-------------------------------------	--------------------------	--	--------------------------	----------------------------	--------------------------

To B.I.E.T. **To ALDERMASTON COLLEGE**
Dept BPE95 Reading RG7 4PF **OK** **BPE95**

NAME (Block Capitals Please) _____
ADDRESS _____

Other subjects Accredited by C.A.C.C. Age _____
Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Marshall's

Everything you need is in our
New Catalogue
available now price 20p
(100 pages of prices and data)

A. Marshall (London) Ltd. Dept. PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0167/2 Telex 27492
& 85 West Regent Street Glasgow G2 2QD Telephone 041-332 4133

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

Popular Semiconductors

2N456	0-80	2N2907	0-22	2N4061	0-11	AD150	0-53	BC171	0-13	BD135	0-43	BFY19	0-62	MJE2955	1-12
2N456A	0-85	2N2907A	0-24	2N4062	0-11	AD161	0-45	BC172	0-11	BD136	0-48	BFY20	0-50	MJE3055	0-68
2N457A	1-20	2N2924	0-14	2N4125	0-20	AD162	0-45	BC182	0-12	BD138	0-63	BFY50	0-23	MPB111	0-32
2N490	3-16	2N2925	0-17	2N4289	0-34	AD161	PR	BY182L	0-12	BD139	0-71	BFY51	0-23	MPB112	0-40
2N491	3-58	2N2926	0-19	2N4919	0-84	AD162	J	BC183	0-09	BD140	0-87	BFY52	0-21	MPB113	0-47
2N492	3-99	Green	0-12	2N4920	0-99	AF109R	0-40	BC183L	0-09	BDY20	1-05	BFY53	0-18	MPF102	0-39
2N493	4-20	Yellow	0-11	2N4921	0-73	AF115	0-24	BC184	0-11	BF115	0-25	BFY90	0-75	MPSA05	0-25
2N596	0-22	Orange	0-11	2N4922	0-84	AF116	0-25	BC184L	0-11	BF116	0-23	BFY99	0-23	MPSA06	0-26
2N597	0-16	2N3053	0-25	2N4923	0-83	AF117	0-20	BC185	0-25	BF117	0-43	BU104	2-00	MPSA56	0-27
2N598	0-40	2N3054	0-60	2N5172	0-12	AF118	0-55	BC187	0-27	BF119	0-58	BU105	2-25	NE555V	0-70
2N599	0-45	2N3055	0-75	2N5174	0-22	AF124	0-30	BC207	0-12	BF121	0-25	C106A	0-46	NE560	4-48
2N706	0-14	2N3390	0-26	2N5175	0-26	AF125	0-30	BC208	0-11	BF123	0-27	C106B	0-55	NE561	4-80
2N706A	0-16	2N3391	0-23	2N5176	0-32	AF126	0-28	BC212K	0-10	BF125	0-25	C106D	0-65	NE565A	4-95
2N708	0-17	2N3391A	0-29	2N5190	0-92	AF127	0-28	BC212L	0-16	BF152	0-20	C108E	1-80	OC23	1-35
2N709	0-42	2N3392	0-13	2N5191	0-95	AF139	0-39	BC214L	0-16	BF153	0-21	CA3020A	1-96	OC28	0-76
2N710	0-32	2N3393	0-13	2N5192	1-24	AF170	0-25	BC237	0-09	BF154	0-20	CA3046	7-00	OC35	0-60
2N718	0-23	2N3394	0-13	2N5195	1-46	AF172	0-25	BC238	0-09	BF158	0-23	CA3048	2-11	OC42	0-50
2N718A	0-28	2N3402	0-18	2N5245	0-43	AF178	0-55	BC239	0-09	BF159	0-27	CA3089E	1-96	OC45	0-50
2N720	0-50	2N3403	0-19	2N5457	0-49	AF179	0-65	BC251	0-20	BF160	0-23	CA3090Q	4-23	OC47	0-20
2N721	0-55	2N3440	0-59	2N5458	0-45	AF180	0-58	BC252	0-18	BF161	0-42	CD4001	0-51	OC71	0-20
2N914	0-22	2N3441	0-97	2N5459	0-49	AF186	0-46	BC253	0-23	BF162	0-32	CD4002	0-51	OC83	0-25
2N916	0-28	2N3442	1-07	40361	1-48	AF200	0-35	BC259	0-09	BF166	0-21	CD4009	1-07	OC88	0-25
2N917	0-32	2N3443	0-20	40362	0-50	AF201	0-51	BC258	0-09	BF167	0-21	CD4010	1-07	ORP12	0-55
2N929	0-20	2N3415	0-21	40363	0-88	AF240	0-72	BC259	0-13	BF173	0-24	CD4010	1-07	ORP21	0-55
2N1302	0-19	2N3416	0-34	40389	0-46	AF279	0-54	BC261	0-20	BF177	0-29	CD4011	1-51	RL54	0-15
2N1303	0-19	2N3417	0-24	40394	0-56	AF280	0-54	BC262	0-18	BF178	0-35	CD4015	2-66	RL54	1-68
2N1304	0-24	2N3638	0-15	40395	0-65	AL102	0-75	BC263	0-23	BF179	0-43	CD4016	1-02	SC35D	1-46
2N1305	0-24	2N3638A	0-15	40406	0-44	AL103	0-70	BC300	0-36	BF180	0-35	CD4020	2-96	SC40D	1-89
2N1306	0-31	2N3449	0-27	40407	0-33	BC107	0-16	BC301	0-34	BF181	0-35	CD4023	0-51	SC41D	1-32
2N1307	0-22	2N3641	0-17	40498	0-50	BC108	0-15	BC302	0-29	BF182	0-40	CD4024	1-50	SC45D	1-89
2N1308	0-40	2N3702	0-12	40409	0-52	BC109	0-19	BC303	0-54	BF183	0-40	CD4028	2-56	SC45D	1-96
2N1309	0-36	2N3703	0-13	40410	0-52	BC113	0-15	BC307	0-11	BF184	0-30	CD4028	2-56	SC50D	2-60
2N1671	1-44	2N3704	0-14	40411	2-00	BC115	0-17	BC307A	0-10	BF185	0-30	CD4029	2-56	SC51D	2-39
2N1671A	1-54	2N3705	0-12	40414	3-55	BC116	0-17	BC308	0-12	BF184	0-12	CD4041	2-11	SL41A	1-80
2N1671C	4-32	2N3707	0-09	40430	0-85	BC116A	0-19	BC308A	0-42	BF195	0-13	CD4044	2-11	SL623	4-59
2N1711	0-45	2N3708	0-10	40601	0-67	BC118	0-11	BC309	0-10	BF197	0-15	CD4049	1-65	SL263	4-59
2N1907	5-50	2N3709	0-11	40602	0-46	BC119	0-29	BC309A	0-10	BF198	0-18	CD4050	9-00	TAA263	1-00
2N2102	0-50	2N3710	0-12	40603	0-53	BC121	0-23	BC309B	0-10	BF199	0-18	LM301A	0-48	TAA621	2-03
2N2147	0-78	2N3711	0-11	40604	0-56	BC125	0-16	BC237	0-21	BF200	0-40	M304A	1-19	TAD100	1-50
2N2148	0-94	2N3712	0-96	40636	1-16	BC126	0-23	BC238	0-19	BF201	0-22	LM309K	1-88	Filter	0-70
2N2160	0-93	2N3713	1-20	40659	0-70	BC132	0-30	BC308	0-19	BF237	0-22	LM702C	0-75	TAD100	1-50
2N2192	0-40	2N3714	1-33	40673	0-10	BC133	0-13	BC338	0-19	BF238	0-22	LM709	0-21	TBA271	0-64
2N2192A	0-40	2N3715	1-50	AC107	0-51	BC135	0-13	BCY30	0-64	BF244	0-21	TO99	0-48	TBA64B	2-25
2N2193	0-58	2N3716	1-80	AC113	0-16	BC136	0-17	BCY31	0-64	BF245	0-33	8D1L	0-38	TBA801	1-50
2N2193A	0-61	2N3771	2-20	AC117	0-20	BC137	0-17	BCY32	1-15	BF246	0-58	14D1L	0-40	TBA810	1-50
2N2194	0-73	2N3772	1-80	AC126	0-20	BC138	0-24	BCY33	0-45	BF247	0-49	TO99	0-40	TIP29A	0-49
2N2194A	0-30	2N3773	2-65	AC127	0-20	BC140	0-34	BCY34	0-49	BF254	0-16	8D1L	0-38	TIP30A	0-58
2N218A	0-22	2N3789	2-06	AC128	0-20	BC141	0-29	BCY38	0-55	BF255	0-17	14D1L	0-60	TIP31A	0-62
2N2219	0-24	2N3790	2-40	AC151V	0-25	BC142	0-23	BCY39	1-50	BF257	0-46	LM747	1-00	TIP32A	0-74
2N2219A	0-26	2N3791	2-35	AC152V	0-17	BC143	0-25	BCY40	0-87	BF258	0-59	8D1L	0-38	TIP33A	1-01
2N2220	0-25	2N3792	2-69	AC153	0-25	BC145	0-21	BCY42	0-28	BF259	0-55	14D1L	0-40	TIP34A	0-58
2N2221	0-18	2N3794	0-24	AC153K	0-33	BC147	0-12	BCY58	0-21	BF259	0-55	LM747	1-00	TIP35A	2-09
2N2221A	0-21	2N3819	0-37	AC154	0-20	BC148	0-13	BCY59	0-17	BF259	0-55	8D1L	0-38	TIP36A	3-70
2N2222	0-20	2N3820	0-64	AC175	0-23	BC149	0-12	BCY70	0-22	BF259	0-55	14D1L	0-40	TIP41A	0-79
2N222A	0-25	2N3823	0-78	AC176K	0-33	BC153	0-18	BCY71	0-22	BF259	0-55	MC1310	2-92	TIP295	0-93
2N2368	0-25	2N3900	0-28	AC187K	0-23	BC154	0-18	BCY72	0-13	BFX29	0-30	MC1458CP	0-79	TIP305	0-60
2N2369	0-37	2N3901	0-32	AC188K	0-34	BC157	0-14	BCY87	3-54	BFX30	0-27	MC1303P	1-26	TIP305	0-60
2N2369	0-41	2N3903	0-24	ACY18	0-24	BC158	0-13	BCY88	2-42	BFX44	0-33	1-26	1-26	TIP41A	0-79
2N2369	0-55	2N3904	0-27	ACY19	0-27	BC159	0-14	BCY89	0-97	BFX48	0-37	MC1310	2-92	TIP42A	0-90
2N2646	1-12	2N3905	0-27	ACY20	0-26	BC160	0-17	BD115	0-75	BFX68	0-30	MC1458CP	0-79	TIP295	0-93
2N2904	0-22	2N3906	0-27	ACY21	0-26	BC167B	0-13	BD116	1-00	BFX84	0-24	MJ481	1-38	TIP305	0-60
2N2904A	0-24	2N4036	0-63	ACY28	0-20	BC168B	0-13	BD121	0-75	BFX85	0-30	MJ480	0-90	ZTX300	0-13
2N2905	0-24	2N4037	0-42	ACY30	0-58	BC168C	0-11	BD123	0-32	BFX87	0-28	MJ481	1-14	ZTX302	0-20
2N2905A	0-26	2N4058	0-16	AD142	0-59	BC169B	0-13	BD124	0-67	BFX88	0-25	MJ490	0-98	ZTX500	0-15
2N2906	0-19	2N4059	0-09	AD143	0-60	BC169C	0-13	BD131	0-40	BFX89	0-45	MJ491	1-38	ZTX502	0-18
2N2906A	0-21	2N4060	0-11	AD149V	0-58	BC170A	0-11	BD132	0-50	BFY19	0-52	MJE340	0-45	ZTX530	0-21

PW TELETENNIS KIT

As featured on BBC Nationwide and in the Daily Mail 2 Oct 74. Ideal game for whole family. No need to modify your TV set just plugs in to aerial socket.
Parts list as follows: A Resistor Pack £1 P & P 20p B Potentiometer Pack £1 25 P & P 20p C Capacitor Pack £3 10 P & P 20p D Semiconductor Pack £14 50 P & P 20p E IC Sockets £4 P & P 20p F Transformer £1 15 P & P 25p G PCBs £7 50 P & P 20p H Switches £4 50 P & P 20p I UHF Modular Kit £7 20 P & P 20p
Special Prices—complete kit excluding case £42 P & P 50p Sections A-F incl £23 50 P & P 30p Assembly instructions with complete kit or 75p on request

P.C. Marker Pen Dalo 33PC

Price 87p
Zeners 400MW 2 7V-43V 11p. 1W3 3V-120V
IC Sockets 8 D 16L 1p. 14 DIL 17p. 16 DIL 20p
Liquid Crystals—£13
Ex-stock S.A.E. for details of CMOS battery operated clock kit using LCD s
Scope/Cr Car Ignition Kit—£11 50—VAT
1 IMF440V 1440V £1 10.
BSTB0246 £1 05. Transformer £2 75.
Minitron £1 55.
DL707 £2 35 or 4 for £8.

Resistors

W	Tol	Price	Value	Price
1/4	5%	1p	0 1/35	14p
1/2	5%	1 1/2p	0 22/35	14p
1	5%	2p	0 47/35	14p
1	10%	2 1/2p	2 35	14p
2	10%	6p	4 7/35	18p
2 1/2	5%	7p	10/16V	18p
3	5%	9p	47/6 3V	20p
10	5%	10p	100/3V	20p

Veroboard

	Copper	Plain
2 1/2 x 3 1/2in	0 1 0 15	0 1 0 15
2 5 x 5in	28p 20p	— 14p
3 1/2 x 3 1/2in	30p 30p	—
3 1/2 x 5in	34p 35p	— 24p
3 1/2 x 17in	£1 21 95p	76p 69p

Trade and Retail supplied.

Integrated Circuits—TTL Reductions!

SN7400	0-16	SN7409	0
--------	------	--------	---

DISCO, SHOP, SOUND TO LIGHT, STAGE PHOTO-FLOOD LIGHT FITTINGS

TYPE B 3-BANK UNIT

Has two brackets to accept P/C Board. Transformers. Also has holes in ends for Potentiometers, Jack Socket, Cable, etc. Ideal for making Sound to Light and Strobes. Base Cover included. Less Lamps. only **£6.50**

inc. VAT. P. & P. 40p.

SOUND TO LIGHT

Three channel, using Type B unit. Ideal for small disco's and home entertainment. Complete with Lamps. Ready wired.

£25

inc. VAT. P. & P. 40p.

STROBE UNIT

Using Type B unit. Adjustable frequency. Single knob control. Complete with Lamps, just plug into mains—that's it.

£25

complete, inc. VAT. P. & P. 40p.

100 WATT SPOT LAMPS

Red, Pink, Green, Yellow, Blue, Violet, Clear. Only

80p

each. Minimum 3 Lamps - £2.40 inc. VAT. P. & P. 25p.



TRAFALGAR SUPPLIES

Dept H.T. • Standish Street • Burnley • Lancs

GET IT WHILE IT'S GOING

This is the first ever Wireless World Annual. It's got 140 pages of features covering all aspects of electronics and communications — new and established techniques, some practical, some theoretical — all written to the high standard you'd expect from Wireless World. Contents include: A General Purpose Audio Oscillator by L. Nelson Jones (a constructional project specially commissioned for the annual); Constructional Design for a Small Boat Echo Sounder by John French; Scientific Calculations with an Arithmetic Calculator by R. E. Schemel. There is also a reference section packed with useful information.

£1 from newsagents or £1.35 inclusive by post from the publishers.

Wireless World Annual 1975

To: General Sales Department, Room 11, Dorset House, Stamford Street, London SE1 9LU.

Please send me copy/copies of Wireless World Annual 1975 at £1.35 each inclusive. I enclose remittance value £..... (cheques payable to IPC Business Press Ltd).

Name (please print)

Address

Company registered in England No. 677128
Regd. office: Dorset House, Stamford Street, London SE1 9LU

wireless world annual 1975

£1.00

COMMUNICATIONS • ELECTRONICS



BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

NORMAL HOUSEHOLD TYPE

EX G.P.O. **Only 99p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only 25p POST & PACKING 16p

Tested and Guaranteed Paks



- B79 4 IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic 50p
- B81 10 Reed Switches, 1" long 1/2" dia. Highspeed P.O. type 50p
- H35 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked 50p
- H38 30 Short lead Transistors, NPN Silicon Planar types 50p
- H39 6 Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945 50p
- H41 2 BD131/BD132 Complementary Plastic Transistors 50p
- H65 4 40361 Type NPN Sil. transistors TO-5 can comp. to H66 50p
- H66 4 40362. Type PNP Sil. transistors TO-5 can comp. to H65 50p



Unmarked Untested Paks

- B1 50 Germanium Transistors PNP, AF and RF 50p
- B66 150 Germanium Diodes Min. glass type 50p
- B83 200 Transistors, manufacturers' rejects, AF, RF, Sil. and Germ. 50p
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 50p
- B86 100 Sil. Diodes sub. min. IN914 and IN916 types 50p
- H20 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts 50p
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can 50p
- H67 10 3819N Channel FET's plastic case type. 50p

Make a rev counter for your car

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each

Electronic Transistor Ignition £6.00

Complete Kit P. & P. 11p

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Extension Telephones

Ideal for children's toys, 70p each. P. & P. 25p.


New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available.

Will align the colour guns on a colour TV receiver. Featuring plug-in ICs and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—and only measures 3in X 5 1/2in X 3in.

Ready built unit only **£9.95** Complete Kit **£7.95**

(includes P. & P. but no batteries)

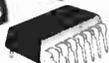

LM380 AUDIO IC

We have just received a large consignment of LM380 ICs. These are specially selected to a higher grade and are marked with the number 5L60745.

This fantastic little 3w audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special **£1 each** complete with data and projects book price

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "P" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.

8 RELAYS FOR £1


P. & P. 27p.

UHF TV Tuner Units

Brand new by a famous manufacturer

Data supplied **£2.50**

Plastic Power Transistors

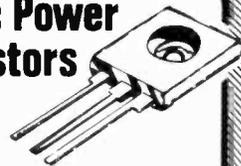

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	15	HFE Min.	15
40 watt	20p	13-25	18p	26-50
90 watt	24p		22p	16p
				20p
Range 2	VCE Min.	40	HFE Min.	40
40 watt	30p	1-12	13-25	26-50
90 watt	35p		28p	26p
			33p	30p

Please state NPN or PNP on order.

HIGH-SPEED MAGNETIC COUNTERS
EX G.P.O. 4 digit (non-reset) 4 X 1 X 1 3/8"

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size. 12p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS
14 pin type at 15p each } Now new low
16 pin type at 17p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE Bi-Pre-Pak Catalogue.

I enclose large S.A.E. with 5p stamp

Please add V.A.T. at Current Rate

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 15p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BUY THESE GOODS WITH ACCESS


BI-PRE-PAK LTD

Co Reg No 820919

Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHDEN (0702) 46344.

SOLID STATE TIME!

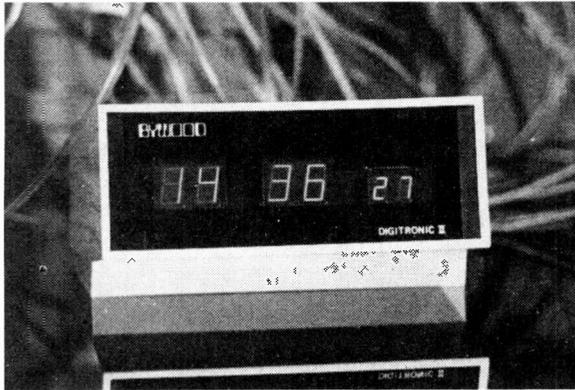

DIGITRONIC II


- Reads: Hours, minutes, seconds
- Bright, clear display
- No moving parts
- Executive styling
- Solid state reliability

KIT CLOCK

Complete with all components, case, etc., plus full instructions **£29-65***

Built, tested and fully guaranteed **£33-65***

Completely Electronic No moving parts

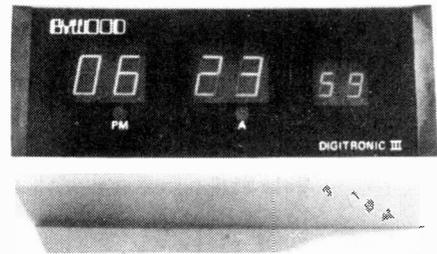

The DIGITRONIC III
£46-50

DIGITRONIC III


- Reads: Time, Date and Alarm
- Electronic "beep" alarm tone
- Ten-minute "snooze" feature
- Four-year calendar
- Attractive "woodgrain" case

BYWOOD

Mail orders: BYWOOD ELECTRONICS
Callers welcome (2m from M1/M10 junction)
Payment: Cash, Cheque, PO. Access
VAT: All prices exclude VAT

181 Ebbens Road,
Hemel Hempstead,
Herts. HP3 9RDA
Tel: 0442-62757

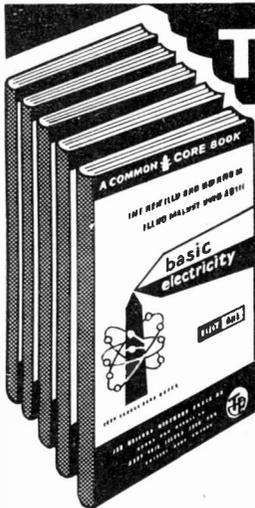DIGITRONIC Clocks and Kits are also available from:
AMBIT, Brentwood, Goddards, St. Albans, HENRY S
RADIO, SINTEL, Oxford, STUDIO ELECTRONICS, Harlow,
and by the time this ad. appears many other electronics
shops and office equipment dealers



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR
100%
GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

- At such a low cost they are a magnificent set of books.
W.I., Ladywell
- My sincere congratulations on describing everything so simply.
J.B., Retford
- I have received both enlightenment and pleasure from reading your manuals.
V.S., Huddersfield
- I am very satisfied with these carefully written and well expressed manuals.
A.W., Sandown
- They are concise and easily understood and I agree with everything that other readers have said in their favour.
W.W., Stockton
- Expressing my great delight with your excellent manuals.
S.S., Paddington

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £6.50
- BASIC ELECTRONICS 6 parts £7.50
- BASIC TELEVISION 3 parts £4.25

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS


POST NOW FOR THIS OFFER!

OUTSTANDING OFFER!

For one month only* we are offering to PE readers the opportunity to own a superb British-made calculator by Advance Electronics.



Advance 88 — a fully user-orientated hand-held machine with 2 independent memories, %, $\sqrt{\quad}$, 16 digits. Algebraic logic.

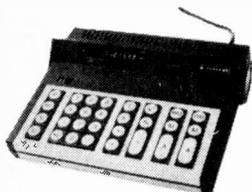

Advance 161R — a first-class desk-top machine with full 16 digits, %, $\sqrt{\quad}$, independent memory and full algebraic logic (enter the problem as you would write it).

All other Advance machines available. Also full program service.

* Offer ends November 30.

We also stock calculators by Mortek, T.I., National, etc. New 6 digit frequency counter kits from £45!



P.E. Rondo

Complete kit with 4 speakers, u/c decoder, FM tuner and turntable. Value approx. £209 + £16.72 VAT.

Fully built Rondo, complete as above. Value £266 + £21 VAT. Delivery on complete systems may be 6/8 weeks from date of order.

Set of 4 speakers fully to specification with pre-built cabinets—very professional finish. Very comprehensive kits.

We supply all Rondo parts and modules.

Quadraphonic headphones—a new experience!

Stereo Headphones—padded with volume controls.

ALL ITEMS ARE POST FREE.

We are appointed distributors for Uher quality tape recorders and Videosonic Dolby processors.

Have you had our book list?

88—complete set with desk stand, charger, rechargeable batteries and case. List price £115 + VAT.

Offer price only

£89

+ £7.12 VAT

161R—List price £130 + VAT.

Offer price only

£100

+ £8 VAT

£195 + £15.60 VAT

£245 + £19.60 VAT

£62 + £4.96 VAT


£18.50 + £1.48 VAT

£4.80 + 38p VAT

NAME _____

ADDRESS _____

PE 11/74

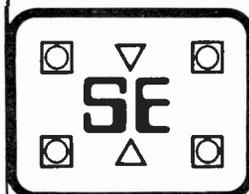

Studio Electronics
 P.O. BOX 18 HARLOW
 CM 18 6SH ESSEX.
 Telephone: Harlow (std 0279) 25457

Practical Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words), Box No. 30p extra. Semi-Display £8.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

VALVES, VALVES AND MORE VALVES. Large stocks 1930-1974, many obsolete. Also available many types of transistors and styli. Price lists available 15p. COX RADIO, The Parade, East Wittering, Sussex. West Wittering 2023.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel, choice of 212 types, send for free list. BAZELLI INSTRUMENT CASES, Dept. 23, St. Wilfrids, Foundry Lane, Halton, LA2 6LT, Nr. Lancaster.

"PRACTICAL ELECTRONICS" 73 Issues offer for the lot to Box No. 56.

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. KINGS PATENT AGENCY LIMITED (Est. 1886). B. T. King, Director, M.I.Mech.E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

LADDERS

LADDERS. "Special Offer". Unvarnished triples. 9ft 7in closed to 23ft 1in extended, £18.52, delivered. Tel.: Telford 586644, order, and pay cash on delivery.

RECEIVERS AND COMPONENTS

LED	dia.	0.125"	0.2"	D.I.L. SOCKET
RED	17p	20p		pin 12p
GREEN	32p	35p		pin 14
YELLOW	32p	35p		pin 13p

AC127	20p	2N706	10p	IN914	3p
AC128	20p	2N3053	15p	IN4001	5p
AF117	25p	2N3055	50p	IN4002	6p
BC107	14p	2N3702	12p	IN4148	4p
BC108	12p	2N3704	12p	OA47	6p
BC109C	14p	2N226(R)	7p	OA81	7p
BCY70	17p	2N226(G)	12p	OA91	5p
BCY71	22p	T1S43	25p	OA95	5p
BCY72	12p	MPF102	45p	OA200	6p
BFY50	18p	2N3819	30p	OA202	7p
OC71	10p	2N3823	30p	IN4004	6p

TELE TENNIS	Kits post free	555.70p
12 NE555, 16 7400	£11	
24 IN914, 2 BC108		
SOCKETS 14 8-pin, 16 14-pin £3.50		
ZN414 £1-10, 7400 TTL 18p		

PRICES INCLUSIVE + 10p P. & P.

ISLAND DEVICES, P.O. Box 11, Margate, Kent

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE

440V AC (±10%)	50p	63V Range	±1%	±2%	±3%
0.1µF (1"×1")	50p	0.47µF	50p	46p	36p
0.25µF (1"×1")	62p	1.0µF	68p	56p	46p
0.47µF (1"×1")	71p	2.2µF	80p	65p	55p
0.5µF (1"×1")	75p	4.7µF	£1.30	£1.05	85p
0.68µF (2"×1")	80p	6.8µF	£1.64	£1.29	£1.09
1.0µF (2"×1")	81p	10.0µF	£2.00	£1.60	£1.40
2.0µF (2"×1")	£1.22	15.0µF	£2.75	£2.15	£1.90

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 95p, 50 for 44.

TRANSISTORS:	BC183/183L	11p	BFY50	20p
	BC107/8/9	9p	BC184/184L	12p
	BC114	12p	BC212/212L	14p
	BC147/8/9	10p	BC547/548A	12p
	BC163/7/8	12p	BF194	12p
	BC182/182L	11p	BF197	13p
			2N3055	50p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p; IN916 8p, 6 for 45p, 14 for 90p; 1844 5p, 11 for 50p, 24 for £1; IN4148 5p, 6 for 27p, 12 for 48p; IN4001 51p; IN4002 6p, IN4003 81p; IN4004 7p; IN4005 71p; IN4006 8p; IN4007 81p

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, ALL at 7p each, 6 for 39p 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5%, ¼W at 40°C, ¼W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 45p.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27, 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p); 800 P.I.V. 11p (4 for 42p).

BRIDGE RECTIFIERS—2¼ amp; 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 10kΩ, 2.5M, 5M, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250Ω, 680kΩ, 1MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. E.12, The Old School, Edinston, Nr. Wem, Shropshire
Tel.: Whixall 464 (STD 094 822)
(Proprs.: Minicost Trading Ltd.)

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 7"×5" app. 0.1 Matrix, 2 for £1-10 P.P. 12×3 0.15 Matrix, 75p each.

12 Volt 1 Amp Trickle Charger, £1-85 P.P. FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2½×2×1½ in with circuit, £1-37½ inc. P.P.

Crouzet Geared Motors, 30 r.p.m. New, £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

Panel with I.C.'s on 7½p per I.C. min. order 10 I.C.'s.

Transformers. 7.5V + 7.5V ½A, 88p inc. P.P. 12-0-12V, 100mA, 90p inc. P.P. 9-0-9V, 100mA, 90p inc. P.P. 29V 50mA, 70p inc. P.P.

Brand new Boxed Rola Celestion Reentrant Speakers SD 25 with 100V line transformer fitted 15Ω without transformer £14 inc. P.P.

Transformer. 20 volt, 1 amp, £1-10 P.P. Transformer. 45 volt, 2 amp, £2-75 P.P.

Pot Cores. LA1225. Brand new. 4 for £1-10 P.P.

P.C. Board. S/S, 5½×5½ in, 10 for 70p inc. P.P. 3EG1 Scope Tubes with base and connections, £3 inc. P.P.

Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, £2 inc. P.P. Size 3"×2"×2".

Power Unit Components Transformer. 18 volt 1 amp F/VW bridge rectifier, 2 1250 mfd capacitors, all new £1-25 per kit. P.P.

Electrolytic Capacitors, 4,000 MF, 50V/V, 4½"×1½" 75p. inc. P.P.

ALLARD ELECTRONICS

Branded Components—Full Specification

TRANSISTORS	SCR's	Price	DIODES	Price	
AC125/6/7/8	0-15	CRS1/05-	0-30	1N914	0-05
AD140/149	0-49	CRS1/10	0-56	1N4001/2/3/4	
AD161/162	0-37	CRS1/20	0-60		0-06
AF114/5/6/7	0-15	CRS1/40	0-45	1N4005/6/7/8	
AF118	0-35	CRS3/40	0-55		0-06
BC107/8/9	0-09	CRS7/400	0-88		
BC147/8/9	0-10	CRS16/100	0-85		
BC182/3/4	0-10	CRS16/200	1-50		
BC212/3/4	0-11	CRS16/600	1-85		
BCY70/11/720-15	L.C's				
BD131/132	0-35	TBA800	1-35	Connecting Wire with every order (5 × 5m in various colours)	
BF194/5/6	0-13	free data			
BFY60/51/52/53					
	0-16				
BY127	0-25				
MC370	0-62				
MLJ371	0-73				
OC28	0-50				
OC35	0-50				
OC83	0-20				
TIL209	0-22				
2N2906	0-19				
2N2906	0-12				
2N2926 all	0-11				
2N3053	0-15				
2N3054	0-40				
2N3055	0-50				
2N3702/3/4	0-10				
2N3705/6	0-10				
2N3707/8/9	0-10				
2N3819	0-28				

SPECIAL OFFER	FREE INTRODUCTORY OFFER	FULL RANGE
ZN414	25 Metres	SN7400 series, Veroboard, Pots, Caps, etc., etc. Send for Free List S.A.E. please
RADIO 1/C	Connecting Wire with every order (5 × 5m in various colours)	
£1 Free circuit		
ZENERS		
All voltages		
BXZ61 series		
1-3W		

BRIDGE RECTIFIERS	Price each		
p.i.v. 1A	2A	4A	6A
50V 0-24	0-34	0-54	0-64
100V 0-24	0-39	0-54	0-69
200V 0-27	0-44	0-58	0-70
400V	0-49	0-64	0-80
600V 0-29	0-74		

299301 BALLARDS LANE

LONDON N12 8NP

MAIL ORDER ONLY. Telephone enquiries: 01-445 5188 Cash with order. Add V.A.T. Orders under £2 plus 12p P. & P.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers' surplus plus fall out. Pack includes resistors, carbon and W.W., capacitors, various transistors, diodes, trimmers, potentiometers, etc.

Send £1 plus 15p P. & P. C.W.O. To:

CASCADE COMPONENTS COMPANY
Bankhead Farm, South Queensferry, West Lothian

COPPER CLAD FIBRE GLASS PANELS 12in x 7in 75p c.p. Double sided 85p c.p. NEGOS. BANK OF FIVE, WITH 5-C407 driver transistors, 60p c.p. M.C. METERS, 3 assorted 2-3in. £1-30 (30p) 5 FIGURE RESETTABLE COUNTER, 18/22V, works on 12V. £2-25 (25p). D.I.L. ICs ON PANELS, 10 for 60p (10p).

COPPER CLAD PAX PANELS: 5½×5½in, 6 for 50p; 6×5in, 3 for 50p; 1½×5in, 3 for £1.12; 12in, 2 for £1. All post paid. SMALL UNIT WITH 4BFY71 with heat sinks, 4 silicon diodes 650V 1A, 65p c.p. THREE TRANSISTOR AUDIO/AMP. Transistors equiv. to AC128, OC72, 40p (10p). 3 for £1 c.p. 22-WAY STEPPING SWITCH WITH RESET. A.c. mains operated, £1 (25p). VALUPAKS. P9, 100 5r mica caps, 55p. P11, 100 polystyrene caps, 75p. P16, 3 small panels with 3 unit transistors on each, 30p. Post 12p. Any number of paks. Send 10p stamps for list of Valupaks, Computer Panels, etc. Refund on purchase

71b ASSORTED COMPONENTS £1-75 c.p.
31b COMPUTER PANELS £1-50 c.p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets. Mail order only.

Disc Ceramics: 100p, 220p, 470p, 1n, 2n2, 4n7 4p each. Miniature Electrolytics: 1000u 25 22p, 47u/63 8p. 3u3/100, 1u/63, 3u3/50, 10u/25, 47u/25, 6p each. 150u/40 10p. BC147 11p. BC148 9p. BC149 13p. BC157, 15p. BC158, 13p. BD131 50p. BD132 55p. BD139 50p. BD140 55p. IN4002 8p. IN4005 10p. Crystalline Ferric Chloride 1 lb Bag 43p - 20p P. & P.

STAG ELECTRONICS

90 Kingsdale Gardens, Drighlington, Bradford BD11 1EZ
Tel. 097-330 2075

RESISTORS. ¼W Carbon Film, Type UPM 050 1p each plus VAT, post free. GREENBANK ELECTRONICS, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

TTL AT LOW PRICES!

(All devices ex-stock. Prices include VAT)

	1/24	25/99		1/24	25/99
7400	0-17	0-15	7402	0-17	0-15
7404	0-20	0-18	7410	0-17	0-15
7420	0-17	0-15	7430	0-17	0-15
7440	0-17	0-15	7442	0-74	0-73
7445	1-03	0-96	7447AN	0-98	0-98
7451	0-17	0-15	7473	0-36	0-34
7474	0-36	0-34	7475	0-56	0-50
7576	0-35	0-32	7480	0-53	0-50
7483	1-02	0-95	7489	3-56	3-33
7490	0-57	0-55	7492	0-57	0-53
7493	0-59	0-56	74121	0-37	0-35
74123	0-72	0-67	7486	0-36	0-34
74157	0-87	0-81	74175	1-01	0-95

All devices full spec. by famous manufacturers. Devices may be mixed for 25/99 prices. S.A.E. for full list. 10p P. & P. on orders under £1, otherwise post free.

J. C. JONES
46 BURSTELLARS, ST. IVES
HUNTINGDON PE17 4XX
 (Mail Order only)

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.
 40/42 Portland Road, Worthing, Sussex O903 34897

BRAND NEW COMPONENTS BY RETURN. Electrolytics, 15V, 25V, 50V—0.47, 1, 2.2, 4.7, 10 mF, 4p; 22, 47, 47p; (50V, 5p); 100, 51p; (50V, 7p); 220, 6p; (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V, 9p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02, 21p; 0-04, 0-05, 3p. Mullard Tubular Polyester 400V E6 series, 0-001-0-022, 3p; 0-033-0-1, 4p. Mullard miniature C333 ceramics E.12 series 2% 1.8pF-47pF, 21p; 56pF-330pF, 3p. Polystyrene 63V. E12 series 10pF-1000pF, 21p; 1200pF-10000pF, 31p. Miniature Highstab Carbon Film Resistors 1/4W E12 series 5% 1Ω-10MΩ (10% over 1MΩ), 1p. Postage 8p. Prices VAT inclusive. **THE C.R. SUPPLY CO.**, 127 Chesterfield Road, Sheffield, S8 0RN.

ABSOLUTELY UNBEATABLE VALUE. Our quality pack of 550 components is a must for every experimenter. Pack comprises loads of transistors, diodes, potentiometers, resistors, capacitors, etc., plus 2 free panels packed with components. Send only £1.50 for speedy delivery to **CAPITAL COMPONENTS**, BCM 3276, LONDON, WC1V 6XX.

"**GAS SENSOR TGS105** with circuits £1.90 post free. **BARON ELECTRONICS**, 176 Brookhurst Avenue, Bromborough, Wirral, Merseyside, L63 0PF."

LED's. Red, Green, Yellow. Sizes: 0.1in, 0.125in, 0.16in, 0.2in. Mixed bags all sizes and colours. 50 £5, 100 £9, including postage, VAT. C.W.O. Individual types and larger quantities by negotiation. **INDUSTRIAL ELECTRONIC SUPPLIES (STOCKPORT) LTD.**, 181a Bramhall Lane, Davenport, Stockport, Cheshire.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO.**, P.O. Box 5, Frome, Somerset. Immediate cash settlement.

SITUATIONS VACANT

INTERNATIONAL DISCOTHEQUE company requires experienced Audio/Installation Engineer for work in England and abroad. Tel. 01-491 7455.

NATIONAL PHYSICAL LABORATORY, DIVISION OF MARITIME SCIENCE

VACANCIES

AT TEDDINGTON, MIDDLESEX AND HYTHE, HAMPSHIRE

ELECTRONIC DEVELOPMENT

A number of interesting posts with a wide range of duties are available at the above locations.

We use analogue and digital circuits, audio and radio frequencies, land and sea based equipment, together with computers to handle our results.

Assistant Scientific Officers, with an interest in electronics, are required to join small teams at both sites to help us maintain and develop our systems, and to assist in trials on ships and offshore structures.

Excellent opportunities exist to obtain broad practical experience and to study for higher qualifications leading to a worthwhile career.

The minimum qualifications are 4 GCE or CSE Grade 1 subjects, to include Maths, Science and English Language.

Salary ranges from £887 (at age 16) to £1,547 (at age 25) rising to £1,899.

If you would like further details you may telephone Mr R. F. Johnson or Mr R. W. Cuffe at the numbers shown.

Mr R. F. JOHNSON: 01-977 3222 Ext. 4165 during working hours or Woking 65942 evenings and weekends.

Mr R. W. CUFFE: Hythe (Hants) 3065 (STD 042-14) in working hours, or Hythe 6804 evenings and weekends.

Alternatively, write to Mr H. B. Boyle, Officer-in-Charge, Department of Industry, National Physical Laboratory, Division of Maritime Science, St John's Street, Hythe, Southampton, Hampshire, SO4 6YS, quoting Reference MS/INST.

MEN!
£70 p.w.
can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators
Training Centre
 T63, Oxford House
 9-15 Oxford Street, W.1
 Telephone 01-734 2874

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 20p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for over 6000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only 30p, plus S.A.E. with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. S.A.E. enquiries. Catalogue 20p plus S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

EDUCATIONAL

C AND G EXAM

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work and Technicians. Radio/TV/Electronics Technicians. Telecommunications Technicians and Radio Amateurs

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits

Get the qualifications you need to success. Free details from:

International Correspondence Schools, Dept. 730X, Intertext House, London SW8 4UJ. Or phone 01-622 9911

MISCELLANEOUS

Build the Mullard C.C.T.V. Camera Kits are now available with comprehensive construction manual (also available separately at 80p).

SEND 5" x 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
 124 Colne Road, Twickenham
 Middlesex TW2 6QS

Sinclair Calculators SENSATION!

Cambridge 8D £15.95
 Scientific £26.95
 On 7 days' paid approval
 Write now:

BRETT EXPORTS
 Dept. P., 16 Hengistbury Road,
 Southbourne, Bournemouth
 Please add 6% VAT - 45p P. & P.



BUILD THE TREASURE TRACER MK III Metal Locator



- Vertical tuning
- Britain's best selling metal locator kit
- Weights only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC 1 & BBC 2 TV

Send s.a.e. for leaflet

Complete kit P & P 45p + 78p VAT **£9.80** Built tested and guaranteed P & P 45p + £1.10 VAT **£13.75**

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order Only)

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

- A-DC 0.06-3A - 6 Ranges.
- A-AC 0.3-3A - 5 Ranges.
- V-DC 0.6-1200 V - 9 Ranges.
- V-AC 3-900 V - 8 Ranges.

Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm - 5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5%. DC +4% AC. Dimensions: 167 x 98 x 63mm.

Only £8.85



SUPERTESTER 680 R ICE

10 Fields - 80 Ranges Plus a lot of accessories for measurements of 500A-AC 100 A-DC - Temperature -50C to -200C - Magnetic fields up to 15 KGauss - Phase indicator - EHT 25KV Electronic Volt Ohm - meter Transistor Diode Tester, etc.

Dimensions 128 x 95 x 32 mm. 300 grams 200OhmV Accuracy 1% DC Ask for free catalogue

£18.50 Accessories Extra



ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet numerals 0 thru 9 and special characters in a single tube. From the stand point of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including *

- All dc operation *
- Uniform continuous line characters of equal height *
- Memory with simple solid state drive circuits *
- Readability in high ambient light *
- 200 footlamberts brightness *
- Long life with no loss of brightness *
- Character height 2 1/2in.

Price only **99p** each plus 16p P.P.



SPECIAL OFFER

The Sinclair Scientific. Logs, trig and arithmetic. All at the touch of a button.

At last there's a pocket calculator which gives you log and trig functions instantly. Full 12 function machine. With the functions available on the Scientific keyboard, you can handle directly log, anti-log, sin and arsin, cos and arcos, tan and arctan, automatic squaring, automatic doubling, x² (including square and other roots) plus, of course, addition, subtraction, multiplication, division and any calculations based on them. 7-digit scientific notation, 200-decade range. Reverse Polish logic and 25-hour battery life.

Send for further information. **£27.50**

Add 8% VAT to all items + 35p P&P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781



SLOW SPEED MOTORS required (about 1 r.p.m.) any quantity considered. Phone Mr. SMITH, 061-638 3527.

PSYCHEDELICATESSEN

is the only way to describe the paradise of FREAKY gear now available from Boffin.

LOOK!

Kits

- NO LICENCE EXAM. Transmitter/Receiver **£6.90**
- Variable-rate, BRIGHT-FLASH, Pocket Mini-Strobe **£2.90**

Ready-Made Experimental Modules

- Maxi-Volt SPARK GENERATOR (1 inch spark), 15,000 Volt **£1.90**
- Mini DREAM-LABORATORY **£3.20**
- SENSITIVE non-anatomical electronic STETHOSCOPE **£3.20**
- Electronic 'VOICE-THROWER' **£3.20**
- GHOST-HUNTING AID **£3.20**
- PEOPLE DETECTOR **£3.20**
- SPEAK-THRU-WATER-FONE **£6.40**
- PSYCHEDELIC MEDITATION AID **£3.20**
- Bird-Watchers' REMOTE MONITOR **£3.20**
- Psychological CROSS-EYED EARS Device **£6.40**
- 'Big Ear' SOUND-CATCHER **£3.20**

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh Ewell, Surrey

(Mail order U.K. only)
Or for more details, send 20p for lists, plus free design project sheet

fibre optic suppliers

MARE'S TAILS. Build your own decorative lamp unit and save £ts. Over 7,000 fibres in 18mm ferrule, professionally finished, 22in dia. Looks absolutely stunning in boardroom, foyer or hall. Price £9.70 + VAT. (Airmail Australia/New Zealand £2).

CROFON 1610. 64-strand plastic light conduit, bundle dia. 1.8mm, O.D. 3.3mm. 1m £1.20, 5m £5, 10m £9.70.

FIBROFLEX SIZE 1. 1.14mm. 40 glass fibre light conduit, very flexible. 40p per metre.

ULTRASONIC TRANSDUCERS SE05B. 40kHz Tx/Rx pair for remote control £3.50.

CIRCULAR POLARISERS. Cut that glare on crt, LEDs, nixies, meters or almost any sort of display. Enhance contrast ratio by up to 20 times. If you have ever used polaroid sunglasses to see through glare on water you will know just how effective these can be. Available in red, amber, green or neutral. 50mm square 80p, 75mm £1.20, 150mm £4.

LINEAR POLARISERS. Turn your walls into living kinetic art. Use a pair of KN42 (high transmission, high temp.) polarisers to convert your slide projector into a multi-colour light show. 50mm square. £1.20 per pair.

PHOTODETECTORS. 2N5777 High Sensitivity Medium Speed Photodiode, 25V (Gain 2,500X). 50p (10 + 45p). MRD150 Miniature High Speed Silicon Phototransistor. 40V max. 60p (10 + 57p).

LIGHT EMITTING DIODES. MLED500, T092 style red 20p (10 + 18p), MLED92, infra-red emitter 30p (10 + 27p). XE209, 3mm case red 20p (10 + 18p). XE209, amber or green 30p (10 + 27p).

PLASTIC OPTICAL MONOFIBRE. We stock plastic fibres in diameters from 0.125mm to 1.5mm. Low cost, easy to use.

FREE OFFER. During November we will send 2m FP20 (0.5mm monofibre) FREE to P.E. readers, together with our short form cat. with full details of prices. OPTIKITS, LENSES and ACCESSORIES. Send 9 x 6in S.A.E. and mark 'Nov Offer'.

VAT. Please add 8% VAT to all prices above.

FIBRE OPTIC SUPPLIERS
(Dept. PE), P.O. Box 702
London W10 6SL

Lighting Modules and Kits Bought Direct From The Manufacturers

SOUND TO LIGHT: 3 x 1 1/2 kW channels with bypass, sensitivity and dimming controls. This unit was designed for use by hire firms and has proved to be very reliable.

MODULE (ready built), £16.99. KIT, £14.99.

DIMMERS: 2-way wallmounting units, 89p.

THEATRE AND DISCO/CLUB DIMMERS

CUSTOM BUILT

Written enquiries and Mail Order only to:

SELEKTION
21 Priors Road, Windsor, Berks. SL4 4PD

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to **METER REPAIRS**, 21 Mount Road, Thundersley, Benfleet, Essex, SS7 1HA.

FLUORESCENT LIGHT KIT

12 v 8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B.s, instructions, etc.

Price only **£3-19** Inc VAT post & packing
Ready built **£3-78**
Diffuser only 59p extra

ALUMINIUM BOXES

Prices include lid, screws and V.A.T. Post and packing too extra on all orders.

7	5 1/2"	by 2"	by 1 1/2" high	39p
8	4"	by 4"	by 1 1/2"	39p
9	4"	by 2 1/2"	by 1 1/2"	39p
10	5 1/2"	by 4"	by 1 1/2"	49p
11	4"	by 2 1/2"	by 2"	39p
12	4"	by 2 1/2"	by 1 1/2"	29p
13	6"	by 4"	by 2"	59p
14	7"	by 5"	by 2 1/2"	69p
15	8"	by 6"	by 3"	82p
16	10"	by 7"	by 3"	96p

Order now to—

ELECTRONIC DESIGN ASSOCIATES
DEPT PE
82 Bath St., Walsall, WS1 3DE. Phone 33652

TELERADIO ELECTRONICS ARE STOCKING THE MODULES FOR THE P.E. RONDO QUADRAPHONIC SYSTEM

- F.M. Tuner ... **£17.50**
- Power Amp ... **£8.25**
- Pre-Amp ... **£3.30**
- Stereo Decoder ... **£7.64**
- P.S.U. ... **£5.50**
- Transformer ... **£6.87**
- Chassis ... **£3.57**

TAX EXCLUDED POST FREE
Further information gladly supplied on request

TELERADIO
325-7 Fore Street, London N9 0PE
01-807 3719
CLOSED THURSDAYS

P.C. BOARDS FOR THE P.E. CCTV CAMERA

Manufactured from highest grade glass fibre material, drilled, roller tinned and ready to assemble.

PCB1—£110 plus 9p VAT.
PCB2—90p plus 7p VAT.

Or supplied cut to size but undrilled, £1'25 the pair plus 12p VAT. All Post Eree.

WASCO ELECTRONICS
Queen Street, Lancaster LA1 1RX

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£1.90	£1.05
15-19	£2.00	£1.10
20-24	£2.05	£1.15
25-29	£2.10	£1.20
30-34	£2.20	£1.28
35-40	£2.35	£1.35

All the above prices are inclusive in U.K.

COPPER SUPPLIES
102 Parrswood Rd., Withington, Manchester 20
Telephone 061-224 3553

LOUD 6V SIRENS for burglar alarms, etc. (new and boxed) **£1.20**. Add 10p P & P. List No. 9 6p. **GRIMSBY ELECTRONICS**, 64 Tenyson Road, Cleethorpes, Lincs.

AUDIOSCAN, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send s.a.e. for bargain list to: **AUDIOSCAN**, Dept. PE7, 4 Princes Square, Harrogate, Yorkshire.

HARDWARE SUPPLIES—Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers, etc., Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes, etc., 7p for list. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwks., CV37 9JP.

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

PRINTED CIRCUIT MANUFACTURERS offer any P.E. Project P.C. ready drilled. One Price 65p. C.W.O. Also P.C. production, Design, Art-Work and Photography undertaken. Send basic circuit, P.C. layout or P.C. Master stating quantity required for estimate by return or Phone: **W.K.F. ELECTRONICS**, Dept. P.C., Welbeck Street, Whitwell, Workson, Nott's., S80 4TW. Telephone Whitwell (Derbys) 695.

0.014in TRANSFORMER LAMINATIONS. Opportunity to purchase small quantities. E's and I's 6 1/4in x 5 1/4in tongue. Winding space 3 1/4in x 1 1/4in. Twelve to the pound at 48p/lb plus 50p per 10lb postage. C.W.D. to: **DIATHERM FURNACES**, 23 Greencourt Road, Petts Wood, Kent.

AERIAL BOOSTERS 23. We make three types of aerial boosters: L45—UHF025, L12—VHF405, L11—VHF radio. TELEVISION VALVES. Most types. Any 5 45p. S.A.E. leaflets. **LANCASHIRE MAIL-ORDER**, 6 William Street, Stubbins, Ramsbottom, Buty, Lancs.

ALUMINIUM PIECES for Practical Electronics COTV Camera. Set of 4, £2 inc. P. & P. Terms C.W.O. Quotes for other projects. **NEW ERA**, "Ravenstor", Lower Stock Road, Stock, Essex.

ALUMINIUM BOXES. All sizes, sheet aluminium, stock sizes, metal cases, etc. Send S.A.E. for complete list. **S. BLAKE**, 21 Widmore Road, Hillingdon Middx.

P.C.B.'s. 1/4in glass fibre, ready drilled; for most P.E. projects, 8p/sp, in plus P. & P., 10p. **M. & G. PYWELL**, 16 Gerverton Square, Bulwell, Nottingham.

OSMABET LTD.

We make transformers amongst other things.

AUTO TRANSFORMERS, 110/200/220/240V. 30W, £1.70; 50W, £2.40; 75W, £2.85; 100W, £3.80; 500W, £10.80; 750W, £14.85; 1000W, £18.00, etc.
LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 1.5A, £1.20; 3A, £1.50; 6A, £2.55; 12V 1.5A, £1.50; 3A, £2.55; 6A CT, £3.40; 18V 1.5A CT, £2.55; 24V 1.5A CT, £2.55; 3A CT, £3.45; 6A, £4.80; 8A, £7.35; 12A, £10.85; 40V 3A CT, £4.50; 50V 6A CT, £13.50; 25V 2A+25V 2A, £4.90; 12V 4A+12V 4A, £4.80.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V 0-10-12-14-16-18V 2A, £2.80; 4A, £3.75; 0-12-15-20-24-30V 2A, £3.40; 4A, £4.50; 0-5-20-30-40-60V 1A, £3.40; 2A, £4.50; 0-10-50-60-80-90-100-110V 1A, £4.90.

MIDTET RECTIFIER TRANSFORMERS.
For FW rect. 200/240V a.c. 9.0-9V 0.3A; 12.0-12V 0.25A; 20.0-20V 0.15A, 6V 0.5A + 6V 0.5A; 9V 0.35A + 9V 0.35A; 12V 0.25A + 12V 0.25A or 20V 0.15A + 12V 0.15A at £1.65 each; 9.0-9V 1A, £1.35; 12.0-12V 1A or 20.0-20V 0.75A £1.50 each.

MAINS TRANSFORMERS
Prim. 200/240V a.c. 1X6 sec. 425-0-425 500 Ma. 6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A, £16.50; TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £9.75; MTS Prim. 0-110-240V sec. 250V 100 Ma, 6.3V 2A, E/S, £2.70.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec, tapped 3-8-15ohms, A-A 6.6kΩ 30W, £5.70; A-A 3kΩ 50W, £9.00; 100W (EL34 KT88, etc.), £15.75; tapped Multi O/P 10W £3.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W, £7.80; 35W, £9.40; HI-FI Major Module 20W w/tweeter Xover, £11.80; Bakerspeaker lists: PANE; 50W, £10.50; 60W, £13.50; HI-FI speakers, EMI bass 13x8in, £2.00; 5in 8Ω, £1.15; 7x4in 15Ω, £1.80; 8x5in 3, 8, 15, 25 or 80Ω, £1.75 each.

LOUDSPEAKERS
2 1/2in 8, 16 or 75Ω, 2 1/2in 8 or 25Ω, 3in 3, 8, 25 or 35Ω, 3 1/2in 8, 15 or 80Ω 90p each; 3in 3, 8 or 25Ω, 5x3in 3 or 8Ω, £1.05; 7x4in 3 or 15Ω, 6 1/2in 3Ω, £1.25; 10x6in 3Ω, £1.50.

SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15Ω up or down £1.30.
"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads. 200/240V a.c. £3.25.
SYNCHRONOUS GEARED MOTORS, 230/240V.
Brand new, Smiths. Built-in gear box. 2 RPH, 75p each.

Carriage and VAT extra on all orders.
S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YQ
Tel. 01-958 9314

SINCLAIR CALCULATORS



New Cambridge Memory £20.95 (E1 95)
Cambridge Assembled £15.95 (E1 55)
Sinclair Scientific £22.45 (E2 05)
Executive with Memory £25.95 (E2 49)

FERRANTI ZN414

IC radio chip with data. £1.20 (22p) Also available kit of extra parts to complete a radio. £2.45 (42p) Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80


AFU £6.38 (73p)
Z40 £5.12 (63p)
Z60 £5.38 (73p)
Q16 £7.21 (80p)
P25 £5.11 (63p)
P26 £7.79 (84p)
P28 £7.36 (80p)



Decoder E7.75 (84p) Trans for P28, £3.85 (50p). Tuner E11.62 (E1 37) Stereo 80, E11.62 (E1 37) Project 805 £28.95 (E2 80) Project 80550, £33.95 (E3 10)

ECONOMICAL QUADRAPHONICS

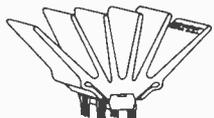Introducing the Napolex Q410 self-contained matrix quadraphonic synthesizer. Just feed the output of any stereo system (including Project 80 or 60) into it and hook on 4 speakers to obtain the latest experience in sound. Send S.A.E. for free leaflet. Only £10.15 (E1.10).



SINCLAIR SUPER IC12

6W rms power
With 44 page booklet and printed circuit £1.80 (40p).

NEW SINCLAIR IC20

High power IC audio amplifier chip. £8.45 (E1.05)

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version. £1.70 (26p). Stereo model with balance control. £3.70 (43p).

IC12 POWER KIT

Supplies 28V 0.5A, £2.77 (48p).

LOUDSPEAKERS FOR THE IC12

5in 8 ohm, £1.20 (27p) 5in x 8in 8 ohm, £1.65 (37p).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners Mono model, £1.40 (25p) Stereo model, £2.50 (33p) Type 2 for ceramic or crystal pickups. Mono, 70p (19p) Stereo, £1.40 (24p).

SEND S.A.E. FOR FREE LEAFLET ON KITS


BATTERY ELIMINATOR BARGAINS

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500mA.
£3.90 (70p)
Other eliminators stocked 250mA—3 way switched model giving 6, 7, and 9V. £2.25 (55p).
50mA—6V, £1.95 (40p). 9V £1.95 (40p). 7V cassette type, £2.50 (40p) Double 6V—6V, £2.75 (43p) 9V—9V, £2.75 (43p).
500mA—Heavy duty deluxe models 6V £2.78 (55p) 7.5V, £2.78 (55p) 9V, £2.78 (55p)



S-DECS AND T-DECS

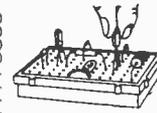
S-DEC £1.98 (31p)
T-DEC £3.63 (47p)
w-DEC A £3.99 (51p)
w-DEC B £5.99 (81p)
IC carriers 16 dil—plain, 81p (15p). With socket, £1.77 (25p). 10 T05—plain, 78p (15p). With socket, £1.68 (24p).
Experiment guides—A, £1.50 (26p). B, £1.77 (29p). C, 90p (18p). D, £2.40 (35p). E, £4.20 (53p).



SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ
Please add the sum shown in brackets after the price to cover the cost of post and new VAT.
Official credit orders from schools, etc. welcome.
No VAT charged on overseas orders

SYNTHESISER Modules by Dewtron®

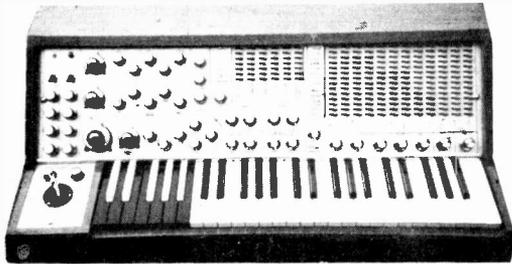


The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p/s; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 15p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown Dorset BH22 9AR

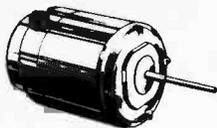"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC, to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120v, 50Hz Speed 60 rpm at 60Hz, 72 rpm STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4", spindle length 2" x 1/4" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price.

OUR PRICE ONLY £15

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant. Ideal P.C. & Sizing. Size 12" 24" x 12" 24" x 24" FULL SHEET 43" x 37" (11 sq. ft.) Single-sided Copper with thickness of 3/64" Also double-sided 3/64" x 3/64" £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p P & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

SMITHS RINGER-TIMER



Reliable 15 minute times spring wound (concurrent with time setting) 15 x 1min divisions. Approximately 1/2 between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging device etc. Size (60 DB) 1/2" x 3/8" x 1/8" 80 DB 1/2" x 1/2" x 1/8" Ex-equipment, all tested £1.20 each P & P FREE

Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 V a.c. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2". Limited number only £8-95. P & P 40p.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged elbow. Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V AC Pull at coil is approximately 1lb. £1. FREE P & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

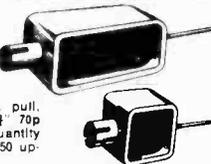240AC type MM6 3lb pull, 2 1/2" x 1 1/2" x 1 1/2" Travel 1" 90p. each P & P. 10p. 240AC type MM4. 2lb pull, 1 1/2" x 1 1/2" x 1 1/2" Travel 1/2" 70p. each P & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 5 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated £2-70. P & P 30p. Similar to above, 19rpm £2-70. P & P 30p. 110rpm with pressed steel gear case (similar to above but SLIGHTLY SMALLER) £2-70. P & P 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 5amp at 120v, 15amp at 240v. Size (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 100 for £2-10; P & P 15p. 50 for £8; 100 for £15-50. FREE P & P. over 10.

AMPEX 7-5V. D.C. MOTOR

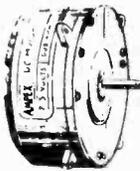

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run 600rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16-50. OUR PRICE £3-30. P & P 25p. Quantities available. Mu-metal enclosure available 75p each. FREE P & P.

ALL PRICES INCLUDE V.A.T. Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH

COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2. Tel: 01-723 5667 01-402 5580

LOOK! LOWEST PRICES IN THE BOOK!

7400-5	0-20	7437	0-36	7476	0-42	72702	0-45	IN4001	0-06
7406-7	0-48	7438	0-36	7482	0-89	72709	0-31	IN4002	0-06
7408-9	0-20	7440	0-36	7483	0-70	72710	0-37	IN4003	0-07
7410	0-20	7442	0-88	7485	1-65	72723	0-80	IN4006	0-09
7412	0-26	7445	1-60	7486	0-46	72741	0-36	IN4007	0-12
7413	0-38	7447	1-30	7489	4-95	72747	1-00	IN4148	0-05
7416	0-44	7450	0-20	7490	0-66	72748	0-36	OA47	0-07
7417	0-30	7451	0-20	7491	1-10	ZN414	1-25	OA90	0-08
7420	0-20	7453	0-20	7492	0-70	TAA350	2-10	OA91	0-06
7422	0-28	7454	0-20	7493	0-66	LM301B	0-75	OA200	0-06
7425	0-36	7460	0-20	7494	0-90	CA3046	0-70	OA202	0-09
7427	0-45	7470	0-34	7495	0-82	CA3036	1-00	IN916	0-06
7428	0-45	7472	0-34	7496	0-99	CA3028	1-20	BB105	0-45
7430	0-20	7473	0-45	74100	2-20	CA3090C	4-50	IS44	0-05
7432	0-45	7474	0-42	74141	0-99	NE555	0-85	TIL209	0-27
7433	0-45	7475	0-60	74192	2-12	TAA661B	1-40	OA61	0-07
BC107	0-10	BCY70	0-13	OC23	0-48	2N930	0-20	2N3702	0-10
BC108	0-10	BCY71	0-12	OC24	0-47	2N1131	0-22	2N3703	0-10
BC109	0-10	BCY72	0-12	OC28	0-70	2N1132	0-28	2N3705	0-10
BC117	0-22	BC121	0-78	OC35	0-60	2N1171	0-18	2N3706	0-10
BC178	0-22	BFY50	0-25	OC170	0-25	2N1893	0-52	2N3707	0-10
BC179	0-24	BFY51	0-21	OC171	0-25	2N2219	0-40	2N3819	0-20
BC182	0-10	BFY52	0-22	TIP30A	0-82	2N2904	0-40	2N3820	0-45
BC183	0-10	BSX20	0-18	TIP29A	0-52	2N2905	0-23	2N3823	0-21
BC184	0-10	OC44	0-20	TIP41A	0-85	2N3053	0-18	2N3442	1-45
BC212	0-12	OC45	0-20	TIP42A	0-90	2N3054	0-48	3N140	0-98
BC213	0-12	OC71	0-13	ZTX30A	0-26	2N3055	0-48	3N141	0-88
BC214	0-12	OC84	0-25	ZTX50A	0-35	2N3391	0-28	3N142	0-85


Electrosil TR5 resistors 2%, 3p; TR6, 4p; TR4, 10p. Wirewound resistors, all values 2-5W, 10p; 6W, 10p; 9W, 12p; 12W, 15p. Diecast boxes 4 1/2" x 2 1/2" x 1 1/2", 4 1/2" x 2 1/2" x 2 1/2", 7 1/2" x 4 1/2" x 2 1/2", £1-25. Solder 18 s.w.g., £1-80/lb. Dalo pen, 75p. Litesold irons, 10W, £1-75; 25W, £1-75; spare bits, 6p. Fibreglass P.C.B., cut to size, 1p per sq.in. Presets, 5p. Disc ceramics, all values, 3p. Tantalum beads, all at 13p. I.C. sockets, 8-pin, 18p; 16-pin, 18p; 14-pin, 15p. BZY68 series zeners. Full range, 400mW, 10p; 20W, 80p. Siemens polycarbonate capacitors, full range, 4p up to 0-1/250V. Bulgin miniature 3-pin mains sockets, 17p, plugs, 16p. Full specification devices discounts for quantity. Many more items available. Send for lists, etc. Cash with order. Mail order only. P & P 12p.

Buy it with Access

VAT INCLUSIVE! POST FREE OVER £2!

P.E.C. 49-51 St. Mary's Road, Oatlands Village, Weybridge, Surrey

NEW PE SCORPIO Mk. 2

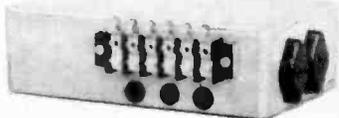

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V. and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board.—Uses original plugs, points and coil.—No special parts or extras required. (Case size: 7 1/2" x 4 1/2" x 2 1/2")

- * All components available separately.—S.A.E. with enquiries.
 - * Construction manual available separately 25p.
- Cost £11-78 incl. carr. and ins. or ready built and tested £14-49
Conversion kit from Mk. 1 to Mk. 2. For constructors already possessing Mk. 1 Kits.—Miniature P.C. assembly £1 incl. carr. and ins. With full conversion instructions.

PLEASE ADD VAT TO ALL U.K. ORDERS

(Carriage at cost outside U.K.—Export enquiries welcome.)

DABAR ELECTRONIC PRODUCTS



98 LICHFIELD STREET

WALSALL, Staffs WS1 1UZ




SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 3 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz $\pm 3dB$. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £11.80. P. & P. 60p.

DE LUXE STEREO AMPLIFIER

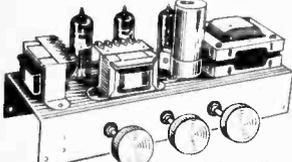

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes, 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. £10.22. P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 71v. and 9v. and 12v. at 1 amp on lead. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. Price £4.90. P. & P. 35p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1.10 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 6 1/2" high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 40p. BARGAIN PRICE £3.78

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary 210-240v. Secondary combinations 0-5v 10-15v 20-25v 30-40v 50-60v half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps fulls wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.31. P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1.10. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.21. P. & P. 25p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.82. P. & P. 35p.

HI-GRADE COPPER LAMINATE BOARDS 8" x 6". Five for 80p plus 30p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve transistor equivalents. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 98p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS. AND SUBS. A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristic, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents 80p. Transistor Equivalents 90p. Transistor Characteristics £1.15. POST FREE. All three together £2.60.


NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 95p. Post Free. 8 pole 3 way 2 bank low loss Yaxley type switches 14 sections. Standard spindle. 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

A few minutes from South Wimbledon Tube Station

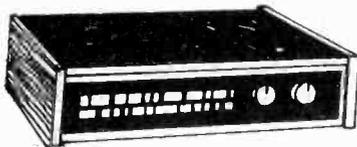HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to 'lock on' station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2in wide x 5in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £21.60. Post and Packing 50p.

STEREO-DECODER SIZE 2" x 3" x 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5 plus 10p P. & P. Stereo beacon light if required 40p extra.



PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge 'Colorcoat' plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2020TC, 2500, 6000, 2500, 5100, SP25 11 and 111, SL65B, AT69 etc. for B.S.N. C109, C120, A21 etc. Black leather finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high including rigid smoked acrylic cover). NOW ONLY £4.78. P. & P. 70p.

LATEST ACOS GP91/1SC mono compatible cartridge with 1/8" stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

SONOTONE 8TACH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.27. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.76. P. & P. 15p.

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1.80. P. & P. 15p.

LATEST RONETTE T/C MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II

A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2in wide x 3in deep x 6in high. Ready built and tested. PRICE £4.91. P. & P. 50p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £8.20. P. & P. 60p.

HI-FI LOUSPEAKER SYSTEMS

Beautifully made task finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance. Carr. 75p.

OUR PRICE £9.10. Carr. 75p. Cabinet Available Separately £4.86. Carr. 65p. Also available in 8 ohm version. E.M.I. 13" x 8" bass speaker with parasitic tweeter £7.80. Carr. 75p.

LOUSPEAKER BARGAINS

5in. 3ohm £1.25. P. & P. 15p. 7 x 4in. 3ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 6in. 3ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.50. P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two built-in tweeters and crossover network £4.65. P. & P. 30p. E.M.I. tweeter. Approx. 3". Available 3 or 8 or 15 ohms. £1.25 + 20p. P. & P.


BRAND NEW. Bakers Loudspeakers at substantial discounts. 12in. 15w. H/B Speaker. 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly £7.50. Guitar models: 25w. £7.50. 35w. £8.50. P. & P. 45p.

12in. "RA" TWIN CONE LOUSPEAKER. 10 watts peak handling. 3 or 8 or 15 ohm (state which) £2.70. P. & P. 36p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6.43 each. P. & P. 34p.

SPECIAL BARGAIN OFFER! Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £7.88 + p. & p. 60p.

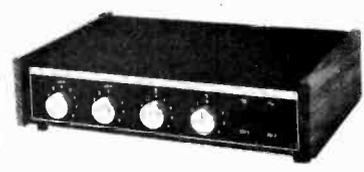HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridges. Instructions included. Output stage for speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response $\pm 3dB$ 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: $\pm 3dB$ 12-15,000 Hz. Bass boost approx. to $\pm 12dB$. Treble cut approx. to $-16dB$. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp.

Overall Size 12 1/2" x 8 1/2" x 2 1/2". Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. **AMPLIFIER KIT £11.34 P. & P. 30p** (Magnetic input components 33p extra) **POWER PACK KIT £3.46 P. & P. 40p** **CABINET £3.46 P. & P. 40p** (Post Free if all units purchased at same time)


Also available ready built and tested £24.60. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.

3-VALVE AUDIO AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7 1/2" w. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.90. P. & P. 45p.

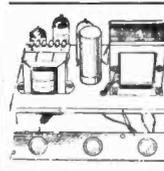HSL FOUR VALVE AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.92. P. & P. 45p.



10/14 WATT HI-FI AMPLIFIER KIT A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15 ohm speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 15p x S.A.E. (Free with parts). All parts sold separately. ONLY £9.60. P. & P. 60p. Also available ready built and tested £12.75. P. & P. 70p.

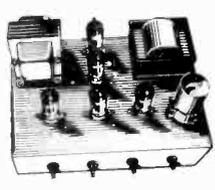

HI-FI STEREO HEADPHONES Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.24. P. & P. 25p.

PRICES INCLUDE VAT AT 8%

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

FREE!

Over 150 ways to engineer a better future



Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained *thousands* of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course."—Student D.J.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects."—Student J.A.O., Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold."—Student C.C.P., Bucks

FIND OUT FOR YOURSELF

These letters, and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. **Write to:**

ALDERMASTON COLLEGE
 Dept. BPE80, Reading GR7 4PF
HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

CUT OUT THIS COUPON
 Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers— A M S E (Mech) Institute of Engineers & Technicians (A M I E) CITY & GUILDS Gen Mech Eng Maintenance Eng. Welding Gen Diesel Eng Sheet Metal Work Eng Inspection Eng Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A M I E D) General Draughtsmanship Elec Draughtsmanship Architectural Draughtsmanship Technical Drawing	<input type="checkbox"/> Construction Surveyors Institute I C S I CITY & GUILDS General Building (all branches) Heating & Vent Inst Clerk of Works Site Surveying Health Engineering Road Construction Quantities Estimates Hydraulics Structural Eng
<input type="checkbox"/> ELECTRICAL & ELECTRONIC CITY & GUILDS Gen Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS CITY & GUILDS Telecoms Gen Radio & TV Eng Radio Amateurs Exam Radio Servicing	<input type="checkbox"/> GENERAL Agricultural Eng Council of Eng Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Accnts Computer Programming Works M'nt Work Study Gen Production Eng Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A M I I MAA/IMI CITY & GUILDS Auto Eng Gen Auto Eng Motor Mechanics Auto Diesel Eng Garage M'nt AFC Aero Engineering Exams Gen Aero Eng	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
	<input type="checkbox"/> CONSTRUCTIONAL Institute of Building L I O B A B I Clerk of Works	<input type="checkbox"/> Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, Dept. BPE80, Reading RG7 4PF BPE80

NAME _____
 Block Capitals Please
 ADDRESS _____

OTHER SUBJECTS _____
 AGE _____
 Accredited by C.A.C.C. Member of A.B.C.C.

Published approximately on the 15th of each month by IPC Magazines Ltd, Fleetway House, Farringdon Street, London, EC4A 4AD Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/S) Ltd South Africa—Central News Agency Ltd. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £4.10. International Giro facilities Account No. 5122007 Please state reason for payment. "message to pay".
 Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever

Henry's SO MUCH MORE - AND YOU PAY LESS VAT WITH HENRY'S LOW PRICES



You can build the Texan and Stereo FM Tuner TEXAN 20 - 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer, 6 ICs, 10 transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's (and P.W. 1972). Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 2 1/2" x 6 1/2". Mains operated. Free teak sleeve with every kit. £28.50 (G.B. post paid). BUILT AND TESTED £35.00.



STEREO FM TUNER

Features capacity diode tuning, led and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8 1/2" x 2 1/2" x 6 1/2". Complete kit with teak sleeve. £21.00 (G.B. post paid). BUILT AND TESTED £24.95.

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

NEW CATALOGUE available December. 75p with vouchers


JOSTY KITS IN STOCK (Post etc. 15p each)



- AF20 Mono transistor amp. 5-61
- AF25 Mixer. 3-30
- AF30 Mono transistor pre-amp. 3-20
- AF35 Emitter amplifier. 2-43
- AF80 Small 0.5W amp for mic. 4-86
- AF305 Intercom. 7-68
- AF310-2 Mono amp. (for stereo use two). 7-56
- M160 Multivibrator. 2-19
- M1302 Transistor tester. 8-34
- M191 Vu-Meter. 5-37
- M192 Stereo balance meter. 5-94
- LF380 Quadrophonic device. 8-43
- AT60 Psychedelic light control. single channel/10-82
- AT65 Psychedelic light control. 3 channel/16-53
- AT25 Window wiper robot. 5-82
- AT30 Photo cell switching unit. 6-69
- AT50 400W triac light dimmer speed control. 5-19
- AT56 2-200W triac light dimmer speed control. 6-75
- AT5 Automatic light control. 3-75
- GU330 Tremolo unit for guitars, etc. 8-10
- HF61 Diode detector. 3-87
- HF65 Frequency modulated FM transmitter. 3-21
- HF75 FM transistor receiver. 3-68
- HF310 FM tuner unit. 16-31
- HF325 De-Luxe FM tuner unit. 26-34
- HF330 Stereo decoder, for use with HF310/325/10. 5-6
- GP310 Stereo pre-amp (for use with 2 AF310). 22-98
- GP312 Basis circuit board. 10-02
- GP304 Basis circuit board. 5-33
- HF380 Aerial amp. for LW to VHF. 6-03
- HF395 Broadband aerial amp. 2-10
- NT10 Power supply 100mA 5V stab and 12V unstable. 6-27
- NT300 Prof. stab. power supply. 13-17
- NT310 Power pack 2 x 15V 2A. 5-64
- NT305 Voltage converter. 5-64
- NT330 Power pack AF310/GP304. 6-27
- NT315 P/S 240V a.c. to 4.5-15V d.c. 500mA. 12-06

TRANSISTORISED MODULES

Tuners-Power Suppliers-Amplifiers

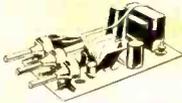


EXCLUSIVE DECCA KELLY SPEAKERS

12W speaker Tweeter systems. 8in bass mid-range. Melinex domed HF radiator plus crossover. Built into veneered cabinets size 18in x 12in x 6 1/2in. Price £19.50 pair (carr., etc. £1).



EMI SPEAKERS SPECIAL PURCHASE

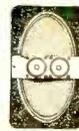13in x 8in chassis speakers (carr./packing 30p each or 50p pair). * 150 TC 10W 8 ohm twin cone £2.20. * 450 TC 10W 4. 8. 15ohm with twin tweeters and crossover £3.85 each. EW 15W 8 ohm with tweeter £5.25 350 20W 8. 15 ohm with tweeter each £7.80 * Polished wood cabinet £4.80 (carr., etc. 35p each or 50p pair).



PHILIPS 8 WATT FLUORESCENT UNIT

EXCLUSIVE PURCHASE

Brand new Philips 12V operated 8W fluorescent tube units for standby lighting. Complete with tube and instructions. Price £3.50 (P. & P. 25p).



EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5W output, 8-16 ohm load. 30V max. d.c. operation complete with data. Price £1.50 each or 2 for £2.85. Printed Circuit Panels 50p.



UHF TV TUNERS

625 line receiver UHF transistorised tuners FM U.K. operation. Brand new (P & P 25p each). TYPE C variable tuning £2.50. TYPE B 4-button push-button (adjustable) £3.50.

FREE STOCK LISTS

No. 36 Transistors, valves, semiconductors. No. 18 Disco lighting, high-power sound. No. 17 Hi-Fi, TV-tape equipment. Send large S.A.E. with all enquiries. Phone or call any centre for best prices. Barclay/Access cards welcome. Credit terms for callers.

Amplifiers (All single channel unless stated)

	9V	300mW O/P 3-8 ohm	1-10mV I/P	£	P
4-300	9V	300mW O/P 3-8 ohm	1-10mV I/P	1	75
2004	9V	250mW O/P 3-8 ohm	10-100mV I/P	2	70
104	9V	1W O/P 8-16 ohm	10mV I/P	3	10
304	9V	3W O/P 4-8 ohm	10mV I/P	3	95
555	12V	3W O/P 8-16 ohm	150mV I/P	4	10
555S2	12V	1 1/2in x 1 1/2in O/P 8 ohm	150mV I/P	5	95
E1208	12V	5W O/P 4-16 ohm	25-50mV I/P	5	10
608	24V	10W O/P 4-8 ohm	30-50mV I/P	4	95
410	28V	10W O/P 8 ohm	160mV I/P	4	95
620	45V	30W O/P 4-8 ohm	150mV I/P	9	95
Z40	30/35V	15W O/P 4-8 ohm	100mV I/P	5	45
260	45/50V	25W O/P 4-8 ohm	100-250mV I/P	6	95
SA6817	24V	6-6 O/P 8 ohm	100mV I/P	10	20

Amplifiers with controls

	12V	2 1/2 - 2 1/2W	8 ohms	8-25
E1210	12V	2 1/2 - 2 1/2W	8 ohms	8-25
R500	Mains	5W	4-16 ohms	6-30
SAC14		7-7W	8 ohms	11-75
SAC30		15-15W	8 ohms	14-95
CA038	9V	1 1/2 - 1 1/2W	8 ohms	6-95
CA068		3-3W	8 ohms	10-50

FM Modules

Mullard LP1186 FM tuner (front end) with data 10.7 MHz O/P	4-85
Mullard LP1185 10.7 MHz IF unit with data	4-50
Gorler Permeability FM tuner (front end) 10.7 MHz O/P	4-20

FM and AM tuners and decoders

FM5231 (Tu 2) 6V FM tuner	7-95
TU3 12V version (FM use with decoder)	7-95
SD4912 Decoder for Tu3-12V	7-95
Stereo	14-95
SP62H 6V stereo FM tuner	4-80
A1007 9V MW-AM tuner	11-95
Sinclair 12.45V FM tuner stereo recorder for above	7-45
A1018 9V FM tuner in cabinet	13-95
A1005M (S) 9-12V stereo decoder FM for above	7-50
1062 12V stereo decoder, general purpose	6-50

Preamplifiers

Sinclair	Stereo 60 Preamplifier	6-75
E1300	Cart./Tape/Mic inputs	2-85
E1310	Stereo 3-30mV mai cart	4-75
FF3	Stereo 3mV tape head	4-95
3042	Stereo 5-20mV Mag. cart. mains	5-95
EQ25	Mono 3-250mV Tape/Cart./Play	1-95

Power Supplies—Mains input (* chassis-rest cased)

47C	6.7; 9V 300mA with adaptors	2.25	P12	4; 12V 0.4-1A	7.15
PS02	9V 500mA	3.20	SE10 A	3.6; 9 12V 1A stabilised	12.75
HC244R	3.6; 7; 9V 400mA stabilised	5.50	P1076	3.4; 6.7; 9 12V 1A	4.20
*P11	24V 1A £3.30 *P15 28V 1A	3.30	SE800A	1-15V 0-1A stabilised	17.50

TRANSISTORS/SEMICONDUCTORS

U.K.'s largest stockists of branded guaranteed devices at low prices

EXTRA DISCOUNTS

Any one type
Extra 10% for 12. 15% 25 x 20% 100-
The above also applies to mixed
SN74 series IC. Get your free stock list now—new
1974-75 edition now available (Ref. No. 36)

HENRY'S HOME ENTERTAINMENT CENTRES

London:
354/6 Edgware Rd., W2 (01-402 5854), 376/8 Edgware Rd., W2 (01-723 0818), 372 Edgware Rd., W2 (01-402 8140), 120 Shaftesbury Ave., W1 (01-437 9652), 230 Tottenham Court Rd., W1 (01-580 1785), 144 Burnt Oak B way, Burnt Oak Edgware (01-952 7402), 190/4 Station Rd., Harrow, Middx. (01-863 7788).
Out of Town:
256 Banbury Rd., Summertown, Oxford (08665 53072), 55 Gloucester Rd., Bristol 7 (0272) 45791.

SINCLAIR MODULES AND KITS

	£
SINCLAIR PROJECT 80	
ST80 Stereo pre-amp	11-95
Audio Filter unit	6-95
Z40 15W amp.	3-45
Z60 25W Amp.	6-95
PZ5 Power supplier for 1 or 2 Z40	4-98
PZ6 Power supplies (S Tab) for 1 or 2 Z40	7-98
PZ8 Power supplies (S Tab) for 1 or 2 Z60	7-98
TRANSFORMER FOR PZ6	3-95
FM TUNER	11-95
STEREO DECODER	7-95
All above post paid (G.B. only)	
IC20 power amp kit	7-95
PZ20 power supply for 1 or 2 IC20	5-45

PACKAGE DEALS (carr. p/ 35p)
2 x Z40, ST80, PZ5 25-00
2 x Z60, ST80, PZ6 27-75
2 x Z60, ST80, PZ6 + trans. 34-40
Cambridge calculator kit £13.84 (post 15p)

Sinclair Special Purchases
*Project 60 stereo preamp 66-75 (post)
*Project 605 Kit £19.95 (post 25p) 20p
K12 6W Amp £2.26 (post 15p)

SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS. 8% VAT TO BE ADDED TO ALL ORDERS. VAT—UK ONLY.

Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, Londop W2 1BW

Hi Fi and Electronics Centres Open 9am - 6pm

Prices correct at time of preparation. Subject to change without notice. E.&O.E.

Transistor Lead Identichart

TYPE	DIAG.	MAKE	TYPE	DIAG.	MAKE	TYPE	DIAG.	MAKE
AC107	26	Mul	BC177	11	SGS	BF195	15b	Mul
AC121	2	Sle	BC178	11	SGS	BF196	15b	Mul
AC126	2	Mul	BC179	11	NAS	BF197	15b	Mul
AC127	2	Mul	BC182	11	TI	BF198	16d	AEG
AC128	2	NKT	BC182L	11	TI	BF199	16d	AEG
AC151	2	Sle	BC183	11	TI	BF200	7a	Mul
AC152	2	Sle	BC184L	16a	TI	BF222	7a	SGS
AC153	2	Sle	BC186	16a	TI	BF237	36a	TI
AC153K	34	Sle	BC202	28	Sle	BF238	36a	TI
AC176	2	NKT	BC207	12	SGS	BF240	16d	AEG
AC176K	34	Sle	BC208	12	SGS	BF243	36a	TI
AC187	2	Mul	BC209	12	SGS	BF244	16e	TI
AC187K	34	Sle	BC212L	16a	TI	BF246	16e	TI
AC188	2	Mul	BC214L	16a	TI	BF246A	16e	TI
AC188K	34	Sle	BC237	16c	AEG	BF254	16d	AEG
ACY17	3	Mul	BC238	16c	AEG	BF255	16d	AEG
ACY18	3	Mul	BC239	16c	AEG	BF257	14	SGS
ACY19	3	Mul	BC257	16a	Sle	BF258	14	SGS
ACY20	3	Mul	BC258	16a	Sle	BF259	14	SGS
ACY21	3	Mul	BC259	16a	Sle	BF310	16c	AEG
ACY22	3	Mul	BC261A	11	ITT	BF311	16d	AEG
ACY28	2	NKT	BC261B	11	ITT	BF362	10	Sle
ACY29	2	NKT	BC262A	11	ITT	BF379	16c	AEG
ACY30	2	NKT	BC262B	11	ITT	BF411	16c	AEG
ACY39	3	NKT	BC263A	11	ITT	BF412	16c	AEG
ACY40	3	NKT	BC263B	11	ITT	BF440	16d	AEG
ACY41	3	NKT	BC264L	16e	TI	BFS92	14	NAS
ACY44	3	NKT	BC288	14	SGS	BFS93	14	NAS
AD133	35	Sle	BC297	11	SGS	BFX29	3	NKT
AD136	4	Sle	BC300	14	SGS	BFX30	3	NKT
AD140	5	NKT	BC301	14	SGS	BFX84	3	NKT
AD142	5	NKT	BC302	14	SGS	BFX85	3	NKT
AD143	5	NKT	BC303	14	SGS	BFX86	3	NKT
AD149	5	NKT	BC307	16c	Sle	BFX87	3	NKT
AD150	5	Sle	BC308	16c	Sle	BFX88	3	NKT
AD161	6	Sle	BC309	16c	Sle	BFX89	7a	Ph
AD162	6	Sle	BC327	16c	Sle	BFX93A	11	TI
AD163	5	Sle	BC328	16c	Sle	BFX98	14	SGS
ADZ11	1	Mul	BC337	16c	Sle	BFY10	3	Ph
AF109R	7a	Sle	BC338	16c	Sle	BFY11	3	Ph
AF114	8	Mul	BCX70	18	Sle	BFY18	11	SGS
AF115	8	Mul	BCY30	3	Mul	BFY19	11	SGS
AF116	8	Mul	BCY31	3	Mul	BFY51	3	NKT
AF117	8	Mul	BCY32	3	Mul	BFY52	3	NKT
AF118	8	Mul	BCY33	3	Mul	BFY53	3	NKT
AF124	7a	NKT	BCY34	3	Mul	BFY56	3	SGS
AF125	7a	NKT	BCY38	3	Mul	BFY56A	3	SGS
AF126	7a	NKT	BCY39	3	Mul	BFY57	14	SGS
AF127	7a	NKT	BCY40	3	Mul	BFY63	14	SGS
AF139	7a	SGS	BCY42	11	Fer	BFY74	11	SGS
AF178	9	Mul	BCY43	11	Fer	BFY75	11	SGS
AF179	9	Mul	BCY54	5	Mul	BFY76	11	SGS
AF180	9	Mul	BCY58	11	AEG	BFY79	11	SGS
AF200U	7b	Sle	BCY58A	11	TI	BFY80	11	AEG
AF201U	7b	Sle	BCY59	11	AEG	BFY85	3	AEG
AF239	7a	Sle	BCY66	11	Sle	BFY86	3	AEG
AF239S	7a	Sle	BCY70	11	Mul	BFY90	7a	AEG
AF240	7a	Sle	BCY71	11	Mul	BLY47	5	TI
AF279	10	Sle	BCY72	11	Mul	BLY48	5	TI
AF280	10	Sle	BCY78	11	AEG	BLY49	5	TI
AF306	16c	Sle	BCY79	11	AEG	BLY50	5	TI
AFY42	7a	Sle	BCZ11	1	Mul	BLY50A	6	TI
AL102	5	SGS	BD127	19	AEG	BLY61	14	TI
AL103	5	SGS	BD128	19	AEG	BSV15	14	AEG
ASY26	3	Sle	BD129	19	AEG	BSV16	14	AEG
ASY27	3	Sle	BD130	5	Sle	BSV46	11	ITT
ASY28	3	NKT	BD131	19	Mul	BSV49A	11	ITT
ASY29	3	NKT	BD132	19	Mul	BSV57	16g	AEG
ASY48	2	Sle	BD135	19	Sle	BSV60	14	AEG
ASY70	2	Sle	BD136	19	Sle	BSV69	14	AEG
AUY21	35	Sle	BD137	19	Sle	BSX19	11	NKT
AUY22	35	Sle	BD138	19	Sle	BSX20	11	NKT
BC107	11	SGS	BD139	19	Sle	BSX27	11	NKT
BC108	11	SGS	BD140	19	Sle	BSX28	11	SGS
BC109	11	SGS	BD234	19	Sle	BSX29	11	SGS
BC113	12	SGS	BD236	19	Sle	BSX30	14	SGS
BC114	12	SGS	BD238	19	Sle	BSX32	14	SGS
BC115	13	SGS	BD433 to BD438	19	Sle	BSX33	11	SGS
BC116	13	SGS	BD439 to BD442	19	Sle	BSX36	11	SGS
BC116A	13	SGS	BD533 to BD538	31	Sle	BSX39	11	SGS
BC117	13	SGS	BDY10	5	Mul	BSX60	3	NKT
BC119	14	SGS	BDY11	5	Mul	BSX61	3	NKT
BC121	28	Sle	BDY20	5	Mul	BSX77	11	Mul
BC122	28	Sle	BDY38	5	Mul	BSX78	11	Mul
BC125	13	SGS	BDY60	5	Mul	BSX87	11	SGS
BC126	13	SGS	BDY61	5	Mul	BSX88	11	SGS
BC140	14	SGS	BDY62	5	Mul	BSX93	11	SGS
BC141	14	SGS	BF115	7b	Mul	BSY17	11	Sle
BC142	14	TI	BF152	12	SGS	BSY18	11	Sle
BC143	14	TI	BF154	12	SGS	BSY34	14	Sle
BC148	15a	Sle	BF158 to BF160	12	SGS	BSY38	11	Mul
BC149	15a	Sle	BF161	7a	SGS	BSY39	11	Mul
BC153	12	SGS	BF163	12	SGS	BSY40	11	Mul
BC154	12	SGS	BF166	7a	SGS	BSY41	11	Mul
BC157	15a	Sle	BF167	7b	SGS	BSY58	14	Sle
BC158	15a	Sle	BF173	7b	SGS	BSY62	11	Sle
BC159	15a	Sle	BF179	3	Mul	BSY63	11	Sle
BC160	14	SGS	BF180	7a	Mul	BSY95A	11	NKT
BC161	14	SGS	BF181	7a	Mul	BU204	5	AEG
BC168	16a	Sle	BF184	7b	AEG	BU205	5	AEG
BC169	16a	Sle	BF185	7b	AEG	BU208	5	AEG
BC172	16b	ITT	BF194	15b	Mul	BU209	5	AEG

TYPE	DIAG.	MAKE
BU310	5	Sle
BU311	5	Sle
BU312	5	Sle
BUY21	5	TI
BUY48	14	SGS
BUY68	14	SGS
C451	3	SGS
C452	3	SGS
GET895	3	Mul
GET896	3	Mul
GET897	3	Mul
GET898	3	Mul
GET914	11	GE
GET929	11	GE
GET930	11	GE
MAT100	2	Sin
MAT101	2	Sin
MAT120	2	Sin
MAT121	2	Sin
MJ480	5	Mo
MJ481	5	Mo
MJ490	5	Mo
MJ491	5	Mo
MJE2955	37a	Mo
MJE2955K	37b	Mo
MJE3055	37a	Mo

KEY TO LEADS

b base c collector e emitter

KEY TO MANUFACTURERS

- AEG AEG-Telefunken
- Fer Ferranti
- GE General Electric
- ITT ITT
- Mo Motorola
- Mul Mullard
- NAS North American Semiconductor

(Some devices shown have more than 3 leads)

© I.P.C. MAGAZINES LTD. 1974

NOTE: The publishers of this chart cannot accept responsibility for errors.

