


PRACTICAL

ELECTRONICS

JUNE 1976

35p

RADIO CONTROL

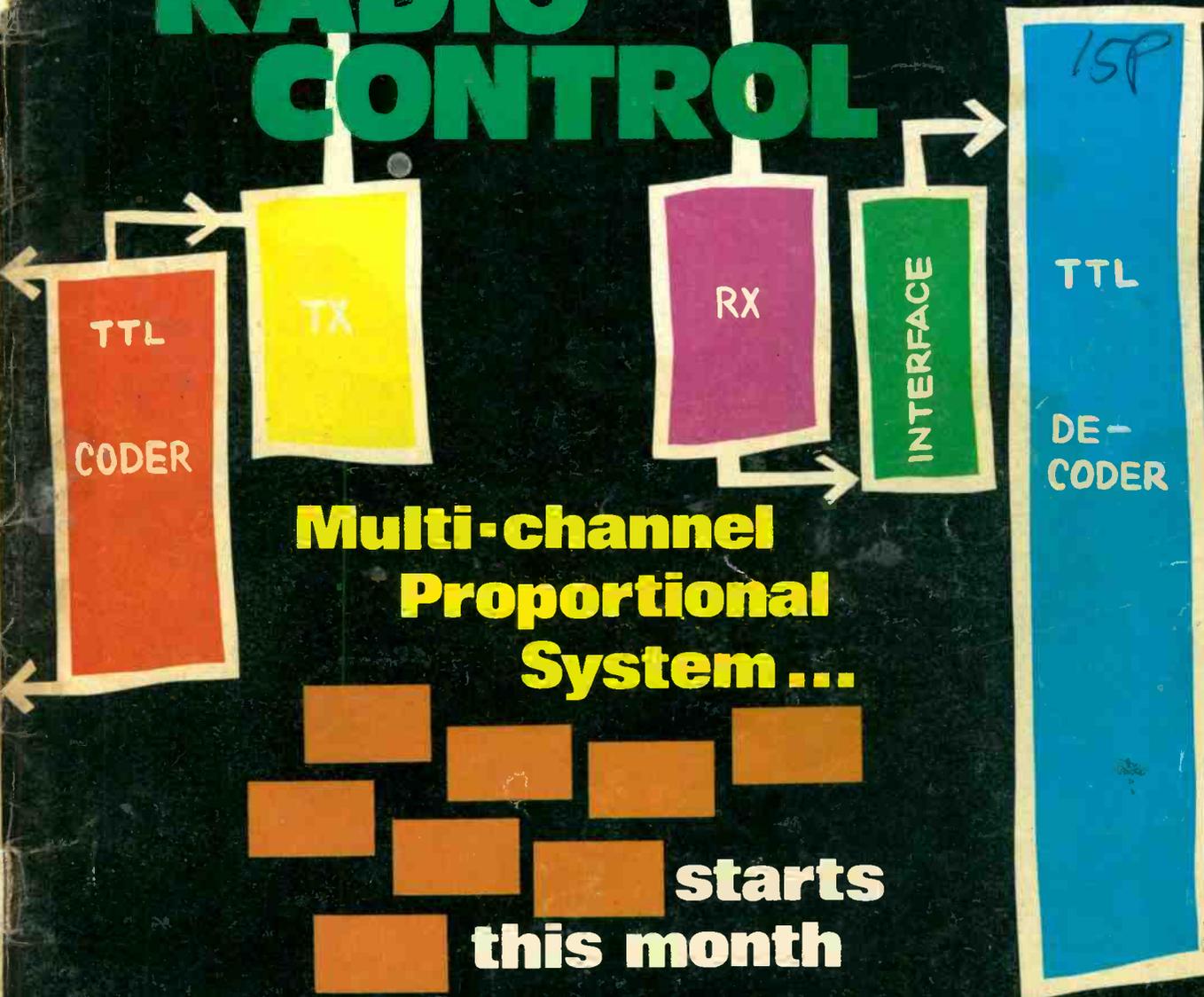

**Multi-channel
Proportional
System ...**

**starts
this month**

ALSO INSIDE ...

**RALLY
MILOMETER**




RADIO EXCHANGE LTD.

REDUCTIONS ON ALL KITS FOLLOWING VAT CHANGE

NEW EDU-KIT MAJOR

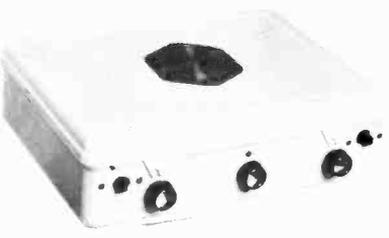COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN - PNP
- 4 Transistor Push Pull Amplifier
- 24 Resistors
- 21 Capacitors
- 3 12-way Connectors
- 2 Volume Controls
- Ready Wound MW/LW/SW Coils
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- 10 Transistors
- 8 1/2" Loudspeaker
- 2 Slider Switches
- Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier.
- Earpiece
- Mica Baseboard
- 3 Tuning Condensers
- 3 Knobs

Complete kit of parts including construction plans
Total building costs £9.00 P.P. and Ins. 65p
 (Overseas Seamail P. & P. £3.50)

V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the long wave band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc.

All parts including case and plans


£3.95 P.P. & Ins. 40p



POCKET FIVE

Now with 3in Loudspeaker 3 tunable wavebands. MW, LW and trawler band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2in x 1 1/2in 3 1/2 in approx.

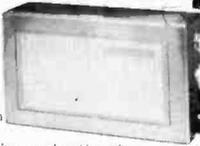Complete kit of parts including construction plans.
Total Building Costs: £3.60 P.P. and Ins. 50p



NEW Everyday Series

Build this exciting new series of designs.

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5 1/2in. x 2 1/2in. approx. All parts including Case and Plans.

Total Building costs £4.30 P. & P. + Ins. 50p



E.V.6. Case and looks as above. 6 Transistors 3 diodes. Powered by 9V battery. Ferrite rod aerial, 3in. loudspeaker, etc. MW/LV coverage. Push/Pull output.

All parts including Case and Plans.

Total Building costs £4.95 P.P. & P. + Ins. 55p

E.V.7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9V battery. Push pull output. Telescopic aerial for short waves. 3in. Loudspeaker.

All parts including Case and Plans.


Total Building Costs £6.35 P. & P. + Ins. 50p

ELECTRONIC CONSTRUCTION KITS

E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3in loudspeaker, gain control, superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

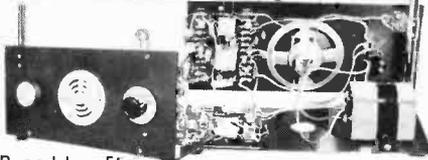Complete kit of parts **£7.15 P.P. and Ins. 55p**



Including Construction Plans

E.C.K. 4

7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5in x 3in loudspeaker. Push pull output stage, gain control, and rotary switch. 7 transistors and 4 diodes. 6 section chrome-plated telescopic aerial. 8 in sensitive ready wound ferrite rod aerial, tuning capacitor, resistors, capacitors, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

Complete kit of parts **£6.55 P.P. and Ins. 55p**



Including Construction Plans


EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including loudspeaker, earpiece, MW ferrite rod aerial, capacitors, resistors, transistors, etc.

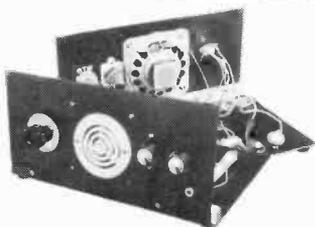Complete kit of parts including construction plans **£6.55 P. & P. + Ins. 55p**



ROAMER TEN MARK 2

WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket. 10 transistors. Latest 5" x 3" loudspeaker. 9 tuneable wavebands. MW1, MW2, LW, SW1, SW2, SW3, trawler band, VHF and local stations, also aircraft band. Built in ferrite rod aerial for MW/LW. Chrome plated, 6 section telescope

aerial, can be angled and rotated for peak short wave and VHF listening. Push pull output using 600mW transistors. Car aerial socket. 10 transistors plus 3 diodes. Canged tuning condenser with VHF section. Separate coil for aircraft band. Volume on/off. Wave change and tone controls. Attractive Case in rich chestnut shade with gold blocking. 9in. x 7in. x 4in. Easy to follow instructions and diagrams. **Total build- £10.68 P.P. and Ins. 65p** costs:



EDU-KIT

Build Radios, Amplifiers, etc., from easy stage diagrams



Five unit including master unit to construct

Components include:

Tuning condenser, 2 volume controls, 2 slider switches, fine tone 3in moving coil speaker, terminal strip, ferrite rod aerial, battery clips, 4 tag boards, 10 transistors, 4 diodes, resistors, capacitors, 3 in knobs. Units once constructed are detachable from master unit, enabling them to be stored for future use. Ideal for schools, educational authorities and all those interested in radio construction.

All parts including case and plans. **£6.30 P.P. and Ins. 55p**

JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Complete with earpiece, jack plug and socket resistors, capacitors, components, etc.

Complete kit of parts including construction plans **£2.85 P. & P. + Ins. 30p**



To: RADIO EXCHANGE LTD.

61A High Street

Bedford MK40 1SA

Tel.: 0234 52387, REG NO. 788372

- Callers side entrance "Lavelis" Shop.
- Open 10-1, 2.30-4.30 Mon Fri. 9-12 Sat.

I enclose £..... for

Name

Address

PE676

PRACTICAL ELECTRONICS

VOLUME 12 No. 6 JUNE 1976

CONSTRUCTIONAL PROJECTS

- RALLY MILOMETER** *by P. Leah*
Designed to aid navigation and map reading on car rallies 464
- AUDIO MILLIVOLTMETER** *by R. A. Penfold*
An essential piece of test gear in the design of audio equipment 476
- PROPORTIONAL RADIO CONTROL—1** *by D. J. Whiteley*
A 9-channel 27MHz system with options of proportional or switched control on each channel. This month the transmitter and coder 484
- DIGITAL FREQUENCY METER—2** *by A. J. Buxton*
This final article deals with construction, a high impedance input buffer and a v.h.f. prescaler 499

GENERAL FEATURES

- USING CMOS DIGITAL I.C.s—6** *by D. B. Johnson-Davies & A. M. Marshall*
Retriggerable monostables, digital filters and three-state output devices 470
- SEMICONDUCTOR UPDATE** *by R. W. Coles*
A look at some recently released devices 492
- INGENUITY UNLIMITED**
Digital Calendar—Electronic Doorbell—Irregular Waveform Production—Square Wave Generator 494

NEWS AND COMMENT

- EDITORIAL—Rising to the Challenge—A Welcome Cut** 463
- NEWS BRIEFS**
- Quad Achievements—Night Attack Missile—New Exchange—Army on the Air 472-489
- SPACEWATCH** *by Frank W. Hyde*
Space Telescope—Space Traffic Jam?—Note for Posterity 475
- READOUT**
A reader's protest 496
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 510
- PATENTS REVIEW**
Thought provoking ideas on file at the British Patents Office 512
- COMPETITION**
- How Inventive are You?**
A LIST OF PRIZE WINNERS 490

Our July issue will be published on Friday, June 11, 1976
(for details of contents, see page 493)

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



TRAMPUS

ELECTRONICS LTD. WINDSOR

58-60 GROVE RD.
WINDSOR, BERKS. SL4 1HS.

ADD 8% VAT TO PRICES MARKED *
ADD 12% VAT TO ALL OTHER PRICES
SEND C.W.O. (EXCEPT GOVT' DEPTS)
POST & PACKING 20p FOR THE UK

NEW FAST SERVICE. LOW PRICES.
MONEY BACK IF NOT SATISFIED.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME
NEW CATALOGUE LIST FREE BY RE.
BARCLAYCARD & ACCESS BY POST
OR TELEPHONE ON 15 MINIMUM

FAST SERVICE



ALL FULL SPEC.
DL707 COM. ANODE &
DL704 COM. CATHODE
0.3" 0-9DP 89p. ea.*
747 JUMBO 0.6" CA
LED DISPLAY £1.75*
3015F 0-9DP £1.25*

DISCO etc STROBE
ZENON TUBE £5 ea.*

LEDS red 12p.

209 STYLE OR 0.2" NO CLIP 11p*
TIL209 or 0.2"RED & CLIP 13p*
GREEN LARGE/SMALL & CLIP 22p*
ORANGE LARGE/SMALL & CLIP 22p*
ORP12 57p* 2N5777 33p* 7EC12 50p*

DIGITAL CLOCKS MM5316 £5*
MM5314 £3.39* MM5311 £5*
AY51224 £3.49* PCB £1*

CAPACITORS

CERAMIC 22pf-0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf 10 or
25V 7p. 50V 9p. 2uf/10V. 6p.
1000uf 25V 18p. 200/500uf 9p.
POTENTIOMETERS LIN/LOG 6p ea
PRESSETS 6p. RESISTORS 1 P ea

HEATSINKS T05/18 7p. T03 15p.
SWITCHES: SPST 19p. DPDT 24p.*
DIN PLUGS ALL 12p. SOCKETS 9p.
ALL CASES: A95/A97 50p AB13 65p
TRANSFORMERS 100mA 89p ea*
1A/1A 6/12 or 12/24 £2 each.

NEW AUDIBLE WARNING BLEEPER £1

TRAMPUS FULL SPEC PAKS ALL £1 ea
PAK A 10 RED LEDS our choice £1
PAK B 5 741C OP AMP 8 PIN £1*
PAK C 4 2N3055 £1*. D 12 BC109 £1*
PAK E 10 BC182 £1*. F 11 2N3704 £1
PAK G 8 BPFY51 £1*. H 9 2N3819 £1*
PAK J 9 2N3053 £1*. K 40 1N914 £1
NEW PAK M 4 PLASTIC 3055 90W £1*

IC's LOW PRICES

703 RP/IF	26p	MC1303	£1.47
709 T099	22p*	MC1310	£2.09
709 DIL 14	28p*	MC1312 SQ	£1.50
710 DIL 14	31p*	MC1318	£2.50
723 Regul'r	45p*	MC1330	75p
741 DIL 8	30p*	MC1339	£1.49
741 DIL 14	31p*	MC1350/1/2	75p
741 T099	31p*	MC1466 /9	£3
747 2x741	67p*	MFC4000 1W	59p
748 DIL 8	27p*	NE536 PETOPA £2*	
7805 5V	£1.39*	NE540	£1.10*
7812 12V	£1.39*	NE550 2vR' 1*	
7815 15V	£1.39*	NE555 TIMER 41p*	
7900 Series £3*		NE556 2x' 84p*	
76013 6W AF 75p		NE560 PLL £4.00	
CA3046	59p	NE561 PLL £4.00	
CA3048	£2.20	NE562 PLL £4.00	
CA3054	£2	NE563	£2.25
ICL8038	£2.69*	NE565	£2.50
LM300	£1.50*	NE566	£1.55
LM301 OPA	41p*	NE567	£2.20
LM304 0-40V	£3*	SN72741 741 20p*	
LM308 H1 BO 95p*		SN76660 1F 75p	
LM309K 5V £1.75*		SN76611 1F £1	
LM372 IF £2.00		TAD100 & 1F £2	
LM377 2x2W	£3	TBA800	89p
LM380 80745	89p	TBA810 7WAF 80p	
LM381	£2	TBA820	£1.49
LM3900 40PA 63p*		ZN414 RX	99p

740 TTL

FULL SPEC. 5% off 100MIX			
7400	9p*	7474	27p*
7401	10p*	7476	27p*
7402/3	11p*	7490	37p*
7404	13p*	7491	60p*
7405/6/7	25p*	7492/93	43p*
7408/9/10	9p*	7494	43p*
7413	26p*	7496	68p*
7420/30	12p*	74100	£1
7440	12p*	74121	26p*
7441	64p*	74123	58p*
7447	67p*	74141	64p*
7470	25p*	74174	£1*
7472	22p*	74175	95p*
7473	26p*	74196	£1*

TRANSISTORS

PRICE EACH:-	MATCHING	20p*	
AC127 & 128	10p*	INS. BUSH SET 6p*	
AC176	15p*	TIP29 & 30 43p*	
AC187 & 188	18p*	TIP31 & 32 54p*	
AD149	45p*	TIP41	63p*
AD161 & 162	33p*	TIP42	67p*
BC107	8p*	TIP2955	99p*
BC107B	8p*	TIP3055	67p*
BC108	7p*	TIS43 UJCT*	26p*
BC108B	12p*	ZTX107/8/9	11p
BC109	8p*	ZTX300 & 304	20p
BC109C	12p*	ZTX500 & 504	42p
BC147/8/9	9p	2N706 & 708	11p*
BC157/8/9	12p	2N2646 UJT	38p*
BC167/8/9	12p	2N2904 & 5	20p*
BC177/8/9	18p	2N2926 broyg	9p
BC182/3/4/44L10p		2N3053	16p*
BC212/3/4/44L12p		2N3054	42p*
BCY70/1/2	16p*	2N3055 115V	37p*
BD131 & 132	39p*	2N3055 RCA	60p*
BF888	250V 35p	2N3702/3/4/5	8p
BFY50	14p*	2N3706/7/8/9	8p
BFY51	14p*	2N3710 & 11	8p
BFY52 & 53	14p*	2N3819E PET	12p
BSX19/20/21	16p*	2N3820 PET	40p
MJ2955 T03	75p*	2N3823E PET	16p
MJ2955	89p*	2N3904/5/6	15p
MJE3055	64p*	2N4289 mini	31p
MU131 PUT	49p	2N4547 PET	45p

CMOS LOGIC

NEW MOTOROLA	CD14533	£2.35*	
CD4000	15p*	CD4028	73p*
CD4001	16p*	CD4048	£1*
CD4002	16p*	CD4047	73p*
CD4009	45p*	CD4049	45p*
CD4011	17p*	CD4054	94p*
CD4013	45p*	CD4055	£1*
CD4016	45p*	CD4060	90p*
CD4017	82p*	CD4071	17p*
CD4018	82p*	CD4081	17p*
CD4022	77p*	CD4510	£1.19*
CD4023	16p*	CD4511	£1.90*
CD4024	63p*	CD4528	£1.10*
CD4027	45p*	CD4528	£2.35*

TELEPHONE 54525

DIODES

0A81 & 0A91 GERMANIUM 5p.
1N4001 1A50V & 1N4002 5p.
1N4004 6p* 1N4007 9p*
1N4148 & 1N914 SILICON 4p.
ZENERS BZY88 400mV 9p.
ZENERS 11W 17P. Z1Jnoiset1
BRIDGE RECTIFIER 1A50 18p
1A400V 25p. 4A100V 45p

SCR'S TRIACS

SCR'S TAG1/400 1A400V 50p*
1A50V 38p* 1A 60V 70p*
C106D 4A400V SCR 00V 47p*
TRIAC SC146D 10A400V £1*
TRIAC DISCO 16A400V £1.75*
DIACS: ST2 20p. BR100 25p

Verob

36PINS 28p* FACE CUTTER 49p*
COPPERCLAD 0.1 PITCH VERO
24"x5" 32p* 24"x31" 29p*
31"x5" 37p* 31"x31" 32p*
31"x17" £1.70*
31"x17" PLAIN 0.1" £1.06*
DIL BREADBOARD 6x4" £2*

DALO 69P pen

DALO ETCH RESIST PEN 69p*
FEC ETCH PAK 500g 89p*
6x4" COPPER BOARD 50p*
PCB KIT 3 ITEMS £2*

OIL sockets

TOP QUALITY NYLON
SOCKETS 8PIN 12p*
14PIN 12p* 16PIN 12p*
SOLDERCON PINS:
100 65p* 1000 £3.50*

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 44 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Practical Radio and Electronics (Technetron)	<input type="checkbox"/> C & G Radio TV & Electronics Mechanics	<input type="checkbox"/> Radio Amateurs	<input type="checkbox"/> Practical TV	<input type="checkbox"/> Colour Television	<input type="checkbox"/> Servicing	<input type="checkbox"/> Computer Electronics	<input type="checkbox"/> C & G I.I. Radio TV Servicing cert.	<input type="checkbox"/> Post Master General 1st & 2nd class Certs	<input type="checkbox"/> C & G Electrical Engineering Practice	<input type="checkbox"/> C & G I.I. Installations and Wiring	<input type="checkbox"/> General Electrical Engineering	<input type="checkbox"/> Society of Engineers (Electrical Engineering)	<input type="checkbox"/> Electrical Installations and Wiring	<input type="checkbox"/> C & G Electrical Technicians (Primary)	<input type="checkbox"/> C & G Telecom-munications
---	---	---	---------------------------------------	--	------------------------------------	---	--	--	--	--	---	--	--	---	--

To **ALDERMASTON COLLEGE** Dept EPE 18 Reading RG7 4PF
Also at our London Advisory Office, 4 Fore St. Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-428 2721.

NAME (Block Capitals Please) _____
ADDRESS _____
POSTCODE _____
Other subjects _____ Age _____
Accredited by C.A.C.C. Member of A.B.C.C.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dimmit

range of light dimmers and lighting control systems

Illustrated is the popular PMSD1000 module. A 1kW slider control dimmer, interference suppressed, 60mm slider range size 4 1/4 x 2 x 1 1/4 in. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £9.06 inc. VAT and postage and packing.

Complete compact light dimmer systems for stage, club and disco lighting, etc.

DD61M (illustrated). Six 1kW channels, six outlet sockets, master control, mains on/off switch, size 23 x 8 1/2 x 5 in. Price £140.40 inc. VAT.

DD61-B. Six 1kW channels, using module PMSD1000, lowest cost system. Size 16 1/2 x 8 x 5 in. Price £64.50 inc. VAT.

DD62M. As DD61M but with six 2kW channels, size 25 x 10 1/2 x 6 in. Price £205.20 inc. VAT.

Add £2.20 postage and packing for all systems.

The Dimmit range includes rotary and slider control dimmers and sound to light converters for home, entertainment and professional applications. Ratings 1kW, 2kW, 3kW.

All products are guaranteed and are supplied with full instructions and applications. Full after-sales service. Technical advice given.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Callers welcome, visit our showroom for a demonstration of any of the modules or systems. Mon.-Fri. 9.30 to 6.0 p.m. Sat. by arrangement.

YOUNG ELECTRONICS LTD.

184 Royal College Street, London NW1 9NN Tel. 01-267 0201

15-240 WATTS!

HY5 Preamplifier


The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; input impedance 47k Ω at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 18-50V.

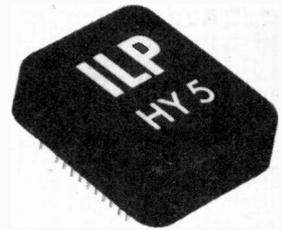Price \pounds 4.75 + \pounds 1.19 VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit; low distortion; short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz - 3dB.

Price \pounds 4.75 + \pounds 1.19 VAT. P. & P. free

AVAILABLE
JUNE 1976

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price \pounds 6.20 + \pounds 1.55 VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm

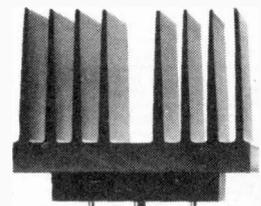Price \pounds 14.40 + \pounds 1.16 VAT. P. & P. free



HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

APPLICATIONS: hi-fi; disco; monitor; power slave; industrial; public address

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 45V. Size—114 x 100 x 85mm

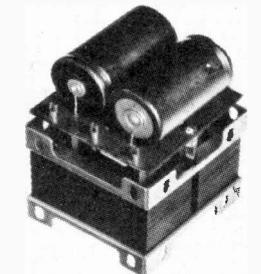Price \pounds 21.20 + \pounds 1.70 VAT. P. & P. free



HY400 240W into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price \pounds 29.25 + \pounds 2.34 VAT. P. & P. free

POWER SUPPLIES: PSU36—suitable for two HY30s \pounds 4.75 + \pounds 1.19 VAT. P. & P. free. PSU50—suitable for two HY50s \pounds 6.25 + \pounds 1.56 VAT. P. & P. free. PSU70—suitable for two HY120s \pounds 12.50 + \pounds 1.00 VAT. P. & P. free. PSU90—suitable for one HY200 \pounds 11.50 + 92p VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 \pounds 21 + \pounds 1.68 VAT. P. & P. free.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

SEMI-CONDUCTORS

TRANSISTORS

BRAND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC117K	*0.39	AF179	*0.51	BC169C	0.10	BC440	*0.37	BF117	*0.46	OC75	*0.18	2N706A	*0.09	2N2846	*0.34	2N3703	*0.09	2N3704	*0.14	2N3704	*0.08
AC126	*0.14	AF180	*0.51	BC170	0.09	BD115	*0.03	BF119	*0.71	BSX20	*0.16	OC77	*0.26	2N708	*0.11	2N2904A	*0.18	2N3705	*0.08	2N3706	*0.08
AC127	*0.11	AF181	*0.51	BC171	0.09	BD116	*0.07	BF152	0.56	BSY25	*0.16	OC81	*0.16	2N914	*0.15	2N2905	*0.18	2N3706	*0.08	2N3707	*0.08
AC128	*0.11	AF186	*0.51	BC172	0.09	BD121	*0.07	BF153	0.48	BSY26	*0.16	OC81D	*0.16	2N918	*0.18	2N2905A	*0.18	2N3707	*0.08	2N3708	*0.08
AC128K	*0.26	AF239	*0.38	BC173	0.09	BD123	*0.07	BF154	0.48	BSY27	*0.16	OC82	*0.16	2N1131	*0.18	2N2906	*0.12	2N3708	*0.08	2N3709	*0.08
AC141	*0.10	AL102	*0.75	BC174	0.15	BD124	*0.70	BF155	*0.71	BSY28	*0.16	OC82D	*0.16	2N1132	*0.18	2N2906A	*0.14	2N3709	*0.08	2N3710	*0.09
AC141K	*0.20	AL103	*0.75	BC175	*0.22	BD125	*0.36	BF156	*0.48	BSY29	*0.16	OC83	*0.26	2N1302	*0.15	2N2907	*0.15	2N3710	*0.09	2N3711	*0.09
AC142	*0.10	BC107	*0.08	BC177	*0.18	BD132	*0.40	BF157	*0.56	BSY38	*0.19	OC139	*0.20	2N1303	*0.15	2N2907A	*0.18	2N3711	*0.09	2N3712	*0.09
AC142K	*0.26	BC108	*0.08	BC178	*0.18	BD133	*0.41	BF158	0.56	BSY39	*0.19	OC140	*0.23	2N1304	*0.18	2N2923	0.15	2N3819	*0.14	2N3820	*0.40
AC153K	*0.24	BC109	*0.08	BC179	*0.16	BD135	0.41	BF159	0.51	BSY40	*0.29	OC169	*0.26	2N1305	*0.18	2N2924	0.15	2N3820	*0.40	2N3821	*0.16
AC178	*0.11	BC113	0.10	BC180	*0.25	BD136	*0.41	BF173	*0.15	BSY41	*0.29	OC170	*0.26	2N1306	*0.21	2N2925	0.15	2N3823	*0.16	2N3903	0.12
AC176K	*0.26	BC114	0.16	BC181	0.25	BD137	0.48	BF176	0.38	BSY95	*0.13	OC200	*0.26	2N1307	*0.21	2N2926G	0.09	2N3903	0.12	2N4290	0.18
AC180	*0.20	BC115	0.16	BC182	0.09	BD138	0.51	BF179	*0.31	BSY95A	*0.13	OC200	*0.26	2N1308	*0.24	2N2926Y	0.09	2N3904	0.12	2N4291	0.18
AC180K	*0.30	BC116	0.15	BC182L	0.09	BD139	0.56	BF180	*0.31	BU105	*1.90	OC201	*0.29	2N1309	*0.24	2N2926O	0.08	2M3905	0.14	2N4292	0.18
AC181	*0.20	BC117	0.19	BC183	0.09	BD140	0.41	BF181	*0.31	MJE521	*0.56	OC202	*0.29	2N1613	*0.18	2N2926R	0.07	2N3906	0.14	2N4293	0.18
AC181K	*0.30	BC118	0.09	BC183L	0.09	BD155	*0.81	BF194	0.10	MJE2955	*0.88	OC203	*0.26	2N1711	*0.18	2N2926S	0.07	2N4287	0.18	2N4288	0.18
AC187	*0.17	BC119	*0.31	BC184	0.09	BD175	*0.81	BF195	0.10	MJE3055	*0.57	OC204	*0.26	2N1711	*0.18	2N2926T	0.07	2N4287	0.18	2N4288	0.18
AC187K	*0.23	BC120	*0.81	BC184L	0.09	BD176	*0.81	BF196	0.92	MJE3440	*0.51	OC205	*0.26	2N1711	*0.18	2N2926U	0.07	2N4287	0.18	2N4288	0.18
AC188	*0.19	BC137	0.18	BC186	*0.29	BD177	*0.87	BF197	0.12	MPF132	*0.28	OC206	*0.26	2N2218	*0.18	2N3055	*0.40	2N4290	0.18	2N4291	0.18
AC188K	*0.23	BC139	*0.41	BC187	*0.29	BD178	*0.87	BF198	0.12	MPF104	*0.28	ORP12/		2N2218A	*0.18	2N3402	*0.21	2N4290	0.18	2N4291	0.18
AD140	*0.49	BC140	*0.31	BC207	0.11	BD179	*0.71	BF199	0.12	MPF105	*0.28	NSL4931	*0.46	2N2219	*0.18	2N3403	*0.21	2N4292	0.18	2N4293	0.18
AD142	*0.55	BC141	*0.31	BC208	0.11	BD180	*0.71	BF257	*0.28	OC19	*0.36	ORP60	*0.41	2N2219A	*0.18	2N3404	*0.21	2N4293	0.18	2N4294	0.18
AD143	*0.49	BC142	*0.31	BC209	0.12	BD185	*0.87	BF258	*0.36	OC20	*0.80	ORP61	*0.41	2N2220	*0.22	2N3405	*0.43	2N4294	0.18	2N4295	0.18
AD149	*0.45	BC143	*0.31	BC212	0.10	BD186	*0.87	BF259	*0.46	OC22	*0.47	TIP29	*0.48	2N2221	*0.18	2N3614	*0.09	2N4547	*0.28	2N4548	*0.28
AD150	*0.85	BC145	0.48	BC212L	0.10	BD187	*0.71	BF262	0.56	OC23	*0.48	TIP30	*0.45	2N2222	*0.18	2N3615	*0.16	2N4549	*0.28	2N4550	*0.28
AD161	*0.32	BC147	0.09	BC213	0.10	BD188	*0.71	BF263	0.56	OC24	*0.57	TIP31A	*0.52	2N2365	*0.18	2N3616	*0.16	2N4550	*0.28	2N4551	*0.28
AD162	*0.36	BC148	0.09	BC213L	0.10	BD189	*0.71	BF270	*0.36	OC25	*0.39	TIP32A	*0.60	2N2369	*0.12	2N3646	0.09	40361	*0.30	40362	*0.35
AD161A		BC149	0.09	BC214	0.10	BD190	*0.77	BF271	*0.31	OC26	*0.38	TIP41A	*0.65	2N2369A	0.17	2N3732	0.09	40361	*0.30	40362	*0.35
AD162(MP)		BC150	0.10	BC214L	0.10	BD195	*0.87	BF272	*0.81	OC28	*0.60	TIP42A	*0.72								
AF114	*0.22	BC152	0.20	BC225	0.28	BD196	*0.87	BF273	0.38	OC29	*0.60	TIS43	*0.25								
AF115	*0.22	BC153	0.20	BC251	0.10	BD197	*0.92	BF274	0.38	OC35	*0.45	UT46	*0.20								
AF116	*0.22	BC154	0.20	BC301	*0.28	BD199	*0.98	BF284	*0.19	OC41	*0.20	ZTX108	0.07								
AF117	*0.22	BC157	0.11	BC302	*0.25	BD200	*0.98	BF285	*0.25	OC42	*0.25	ZTX109	0.07								
AF118	*0.32	BC158	0.11	BC303	*0.31	BD205	*0.81	BF286	*0.22	OC44	*0.16	ZTX300	0.07								
AF124	*0.28	BC159	0.11	BC304	*0.37	BD206	*0.81	BF287	*0.22	OC45	*0.13	ZTX500	0.09								
AF125	*0.26	BC160	*0.11	BC327	0.36	BD207	*0.81	BF288	*0.22	OC70	*0.10	ZN696	*0.10								
AF126	*0.26	BC161	*0.51	BC328	0.12	BD208	*0.98	BFY50	*0.13	OC71	*0.10	2N697	*0.11								
AF127	*0.26	BC167	0.10	BC337	0.12	BDY20	*1.02	BFY51	*0.13	OC72	*0.15	2N698	*0.20								
AF139	*0.11	BC168	0.10	BC338	0.12	BF115	*0.15	BFY52	*0.13	OC74	*0.15	2N699	*0.36								

VAT CHAT
Please add 8% to prices marked *
Remainder add 12 1/2%. Do not add VAT to prices marked †.

SUPER UNTESTED PAKS

Pak No.	Description	Price
U 1	120 Glass Sub-min. General purpose Germ. diodes	0.60
U 4	30 Germanium transistors like OC81, AC128	0.60
U 5	60 200mW sub-min. silicon diodes	0.60
U 11	20 PNP Sil. planar trans. TO-5 like 2N132, 2N2904	0.60
U 15	20 NPN Sil. planar trans. TO-5 like 2N696, 2N697	0.60
U 19	20 Silicon NPN transistors like BC108	0.60
U 26	30 Fast switching silicon diodes like IN914 Micro-Min.	0.60
U 29	10 1 Amp SCR's TO-5 can. up to 600 CR5/25-60	£1.20
U 32	25 Zener diodes 400mW D-7 case 36 volts mixed	0.60
U 36	20 Silicon planar NPN transistors TO-5 BFY50/51/52	0.60
U 45	7 3A SCR. TO66 up to 600 PIV	£1.20
U 46	20 Unijunction transistors similar to TIS43	0.60
U 48	9 NPN Sil. power transistors like 2N3055	£1.20

Code No. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
BA100	*0.10	BB104	*0.15	OA10	*0.14	OA91	*0.07
BA116	*0.21	BY100	*0.16	OA47	*0.07	OA95	*0.07
BA126	*0.22	BY126	*0.15	OA70	*0.07	OA200	*0.07
BA148	*0.05	BY127	*0.16	OA79	*0.07	OA202	*0.07
BA154	*0.12	BY128	*0.16	OA81	*0.07	1N914	0.06
BA158	*0.14	BY164	*0.51	OA85	*0.09	1N916	0.06
BA173	*0.15	BYX38/30	*0.43	OA90	*0.07	1N4148	*0.06

THYRISTORS

PIV	0.6A	0.8A	1A	3A	5A	5A	7A	10A	16A	30A
	TO18	TO92	TO5	TO66	TO66	TO64	TO48	TO48	TO48	TO48
10	*0.13	*0.15	—	—	—	—	—	—	—	—
20	*0.15	*0.13	—	—	—	—	—	—	—	—
30	*0.19	*0.22	—	—	—	—	—	—	—	—
50	*0.22	*0.20	*0.20	*0.25	*0.36	*0.36	*0.48	*0.51	*0.54	*1.18
100	*0.25	*0.30	*0.25	*0.25	*0.48	*0.48	*0.51	*0.57	*0.58	*1.43
150	*0.31	*0.38	—	—	—	—	—	—	—	—
200	*0.38	*0.44	*0.25	*0.30	*0.50	*0.50	*0.57	*0.62	*0.62	*1.63
400	—	—	*0.30	*0.39	*0.55	*0.57	*0.62	*0.71	*0.77	*1.79
600	—	—	*0.39	*0.48	*0.69	*0.69	*0.78	*0.89	*0.90	—
800	—	—	*0.58	*0.65	*0.81	*0.81	*0.92	*1.22	*1.39	*4.07

SILICON RECTIFIERS

PIV	300mA (DO 7)	750mA (SO 16)	1 Amp Plastic	1.5 Amp (SO 15)	3 Amp (SO 10)	10 Amp (TO 48)	30 Amp (TO 48)
50	0.05*	0.06*	IN4001	0.05*	0.07*	0.14*	0.19*
100	0.05*	0.07*	IN4002	0.06*	0.09*	0.16*	0.21*
200	0.06*	0.09*	IN4003	0.07*	0.12*	0.20*	0.23*
400	0.07*	0.14*	IN4004	0.08*	0.14*	0.28*	0.35*
600	0.08*	0.16*	IN4005	0.09*	0.18*	0.33*	0.42*
800	0.11*	0.18*	IN4006	0.10*	0.18*	0.35*	0.44*
1000	0.13*	0.28*	IN4007	0.11*	0.23*	0.44*	0.60*
1200	—	0.32*	—	—	0.28*	0.54*	0.69*

SIL. G.P. DIODES

300mW 400 PIV (min) SUB-MIN FULLY TESTED
Ideal for Organ builders
30 for *50p, 100 for *£1.50, 500 for *£5, 1,000 for *£9.

TRIACS

	Case TO5	100V	200V	400V
2 Amp	TO5	*0.31	*0.51	*0.71
6 Amp	TO66	*0.51	*0.61	*0.77
10 Amp	TO48	*0.77	*0.92	*1.12

GP 300

115 WATT SILICON TO3 METAL CASE
Vceo 100V. Vceo 60V. IC 15A. Hfe. 20-100 suitable replacement for 2N3055, BDY11 or BDY20.

1-24 *50p 25-99 *48p 100+ *46p

GP Switching Trans

TO18 SIM. TO 2N706/8 BSY27/28/95A
All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906, BCY70.
20 for *50p, 50 for *£1, 100 for *£1.80, 500 for *£8, 1,000 for *£14.
When ordering please state NPN or PNP

WORLD SCOOP!!

JUMBO SEMICONDUCTOR PAK
Transistors-Germ and Silicon
Rectifiers-Diodes Triacs-Thyristors-I.C.s and Zeners
ALL NEW AND CODED
Approx. 100 pieces only *£1.85p

ZENER DIODES

FULL RANGE IN STOCK. 2-33 Volts
400mW *8p 1.5W *17p 10W *30p

HANDBOOKS

TRANSISTOR DATA BOOK
DTE 1 227 Pages packed with information on European Transistors. Full specification including outlines. Price

COMPONENTS

ALUMINIUM BOXES

No.	Length	Width	Height	Price
BA1	5 1/2" x 2 1/2"	1 1/2"	1 1/2"	*0.45
BA2	4" x 4"	1 1/2"	1 1/2"	*0.45
BA3	4" x 2 1/2"	1 1/2"	1 1/2"	*0.45
BA4	5 1/2" x 4"	1 1/2"	1 1/2"	*0.54
BA5	4" x 2 1/2"	1 1/2"	1 1/2"	*0.45
BA6	3" x 5"	2 1/2"	1 1/2"	*0.39
BA7	3" x 5"	2 1/2"	1 1/2"	*0.79
BA8	8" x 6"	2 1/2"	1 1/2"	*1.02
BA9	6" x 4"	2 1/2"	1 1/2"	*0.65

(Each complete with 1/2" deep lid and screws). PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX.

COMPONENTS

CARBON RESISTOR PAKS

These Paks contain a range of Carbon Resistors, assorted into the following groups:

R1	50 Mixed 100Ω-820kΩ	1W.	0.60
R2	50 Mixed 1kΩ-8.2kΩ	1W.	0.60
R3	50 Mixed 10kΩ-82kΩ	1W.	0.60
R4	50 Mixed 100kΩ-820kΩ	1W.	0.60
R5	30 Mixed 100Ω-820kΩ	1/2W.	0.60
R6	30 Mixed 1kΩ-8.2kΩ	1/2W.	0.60
R7	30 Mixed 10kΩ-82kΩ	1/2W.	0.60
R8	30 Mixed 100kΩ-820kΩ	1/2W.	0.60

THESE ARE UNREPEATABLE PRICES

REPANCO CHOKES & COILS

RF Chokes	CH1	2.5mH	0.27
	CH3	7.5mH	0.29
	CH5	1.5mH	0.26
	CH2	5.0mH	0.28
	CH4	10mH	0.31
COILS DRX1	Crystal set	0.29	DRR2
Dual range			0.42

CARBON POTENTIOMETERS

Log and Lin	4.7k, 10k, 22k, 47k, 100k, 220k, 470k, 1M, 2M.	
VC1	Single Less Switch	0.20
VC2	Single D.P. Switch	0.40
VC3	Tandem Less Switch	0.60
VC4	1K Less Switch	0.20
VC5	100K Log anti-Log	0.60

HORIZONTAL CARBON PRESETS

0.1 Watt	100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M	4.7M.
----------	--	-------

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tapings 4V, 7V, 8V, 10V, 40V, 50V and 25V-0-25V.	
Type	Amps Price P. & P
MT/50 1/2	1 £3.00 0.45
MT/50 1	1 £4.00 0.48
MT/50 2	2 £5.00 0.60

COIL FORMERS & CORES

NORMAN 1/2" Cores and Formers	0.07
3/4" Cores and Formers	0.09

VEROBOARDS

VBI containing approx. 50 sq.in. various sizes all 0.1 matrix	*0.60
VB2 containing approx. 50 sq.in. various sizes all 0.15 matrix	*0.60

CABLES

CP1	Single lapped screen	Per Metre	*0.08
CP2	Twin Common Screen		*0.11
CP3	Stereo Screened		*0.12
CP4	Four Core Common Screen		*0.21
CP5	Four Core Individually screened		*0.28
CP6	Microphone Fully Braided Cable		*0.11
CP7	Three Core Mains Cable		*0.11
CP8	Twin Oval Mains Cable		*0.08
CP9	Speaker Cable		*0.06
CP10	Low Loss Co-Axial		*0.14

C280 CAPACITOR PAK

Containing 75 of the C280 range of capacitors assorted in values ranging from 0.1µF to 2.2µF. Complete with identification chart.

FANTASTIC VALUE ONLY £1.20

Add 8% VAT to all prices marked *.
Remainder add 12 1/2%.

PLEASE NOTE THE ABOVE DIRECTIONS


COMPONENT PAKS

Pak No.	Qty.	Description	Price
C1	200	Resistors, mixed values approx. count by weight	0.60
C2	150	Capacitors, mixed values approx. count by weight	0.60
C4	75	1/2 width Resistors, mixed preferred values	0.60
C5	5	Pieces assorted Ferrite Rods	0.60
C7	1	Pak Wire 50 metres assorted colours	*0.60
C8	10	Reed Switches	*0.60
C9	3	Micro Switches	*0.60
C10	15	Assorted Pots and Pre-salts	0.60
C12	30	Paper Condensers preferred types, mixed values	0.60
C13	20	Electrolytics Trans. types	0.60
C14	1	Pak assorted Hardware—Nuts, Bolts, Grommets, etc.	*0.60
C16	20	Assorted Tag Strips and Panels	0.60
C19	2	Relays 6-24V Operating 0.60 Sheets Copper Laminate approx. 200 sq.in.	*0.60

Please add 20p post and packing on all component paks, plus a further 10p on pack nos. C1, C2, C19 and C20.

AVDEL* BOND

SOLVE THOSE STICKY PROBLEMS

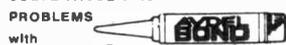

with **CYANOACRYLATE C2 ADHESIVE**
The wonder bond which works in seconds, bond plastic, rubber, transistors, components permanently, immediately!

OUR PRICE ONLY 70p for 2gm phial

AUDIO LEADS

S221	5 pin DIN plug to 4 photo plugs length 1.5m	£1.08
S222	5 pin DIN plug to 5 pin DIN socket length 1.5m	89p
S237	5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m	£1.20
S238	2 pin DIN plug to 2 pin DIN socket length 5m	68p
S270	2 pin DIN plug to 2 pin DIN socket length 10m	89p
S271	5 pin DIN plug to 2 photo plugs connected to pins 3 and 5 length 1.5m	70p
S275	5 pin DIN plug to 2 phono sockets connected to pins 3 and 5 length 23cm	68p
S318	5 pin DIN socket to 2 phono plugs connected to pins 3 and 5 length 23cm	68p
S404	Coiled stereo headphones extension cord extends to 7m	£1.40
S217	3 pin DIN plug to 3 pin DIN plug length 1.5m	80p
S219	5 pin DIN plug to 5 pin DIN plug length 1.5m	80p
S474	3.5mm Jack to 3.5mm Jack length 1.5m	68p
S600	5 pin DIN plug to 3.5mm Jack connected to pins 3 and 5 length 1.5m	80p
S700	5 pin DIN plug to 3.5 Jack connected to pins 1 and 4 length 1.5m	80p

SWITCHES		
DP/DT Toggle		0.28
SP/ST Toggle		0.22

VAT

P&P

Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.00.

BIB ACCESSORIES

REF 200	2 Hi-Fi Cable and Flex Tidy Kit	*34p
REF 201	Tape Head Cleaning Kit 72p	
REF 202	Hi-Fi Cleaner	*30p
Model 9	Wire Stripper	*£1.00
REF 23	1/2" Tape Editing Kit	*£1.80
REF 24	1/2" Cassette Ed ng Kit	*£1.84
REF 29A	Salvage Cassette	*44p
REF 32A	Stylus Balance	£1.28
REF 33	Splicing Tape	*38p
REF 36A	Record and Stylus Cleaning Kit	*35p
REF 41	8 Track Cartridge Head Cleaner	*85p
Model 42	Groov-Kleen	*£1.84
REF 42/S	Roller and Brush for REF 42 and 2000	*24p
REF 43	Record Care Kit	*£2.76
REF 45	Auto Changer Groov-Kleen	*98p
REF 46	Spirit Level	*72p
REF 48	Record Dust-Off	*26p
REF 52A	Cassette Tray	54p
REF 53	Hi-Fi Stereo Test Cassette	*£2.40
REF 56	Hi-Fi Hints and Tips Book	*48p
Model 60S	Groov-Kleen	*£1.72
REF 60/S	Replacement Brush Velvet Pad and Base Sticker for Model 60	*24p
REF 62	Cassette Head Cleaner (Liquid)	*48p
REF 71	Record Dust Off (Displays of ten)	*66p
REF 71A	Record Dust Off (Bubble Pack)	*70p
REF 75	Indexa Record	*£1.50
REF 76	Stylus Cleaner	*36p
REF 78	Cassette Fast Hand Winder	*98p
REF 83	Cassette Title and Container Labels (20 and 10)	*36p

DYNAMIC MIKES

TYPE B1223. 200 ohms impedance. Complete with stand, on/off switch and 2.5mm and 3.5mm plugs. Suitable for cassette tape recorders. PRICE £1.67

ANTEX Equipment

SOLDERING IRONS	
X25. 25 watt	*£2.45
Model G. 18 watt	*£2.70
CCN240. 15 watt	*£2.90
SK2. Soldering Kit	*£3.90

BITS	
102 for model CCN240	*42p
104 for model CCN240	*42p
106 for model CCN240	*42p
1100 for model CCN240	*42p
1101 for model CCN240	*42p
1102 for model CCN240	*42p
1021 for model G240	*42p
1021 for model G240	*42p
1022 for model G240	*42p
50 for model X25	*44p
51 for model X25	*44p
52 for model X25	*44p

ELEMENTS	
Model ECN240	*£1.10
Model EG240	*£1.35
Model ECCN240	*£1.55
Model EX25	*£1.20

SOLDERING IRON STAND	
ST3 Suitable for all models	*£1.10
Antex heat shunt	*10p

PLUGS & SOCKETS

PLUGS	Price
PS1 DIN 2 Pin (Speaker)	0.10
PS2 DIN 3 Pin	0.10
PS3 DIN 3 Pin	0.14
PS4 DIN 5 Pin 180°	0.15
PS5 DIN 5 Pin 240°	0.15
PS6 DIN 6 Pin	0.16
PS7 DIN 7 Pin	0.17
PS8 Jack 2.5mm Screened	0.17
PS9 Jack 3.5mm Plastic	0.11
PS10 Jack 3.5mm Screened	0.17
PS11 Jack 1/2" Plastic	0.14
PS12 Jack 1/2" Screened	0.20
PS13 Jack Stereo Screened	0.33
PS14 Phono	0.09
PS15 Car Aerial	0.14
PS16 Co-Axial	0.14

INLINE SOCKETS

PS21 DIN 2 Pin (Speaker)	0.13
PS22 DIN 3 Pin	0.19
PS23 DIN 5 Pin 180°	0.19
PS24 DIN 5 Pin 240°	0.19
PS25 Jack 2.5mm Plastic	0.15
PS26 Jack 3.5mm Plastic	0.15
PS27 Jack 1/2" Plastic	0.28
PS28 Jack 1/2" Screened	0.32
PS29 Jack Stereo Plastic	0.28
PS30 Jack Stereo Screened	0.35
PS31 Phono Screened	0.17
PS32 Car Aerial	0.20
PS33 Co-Axial	0.20

SOCKETS

PS35 DIN 2 Pin (Speaker)	0.07
PS36 DIN 3 Pin	0.09
PS37 DIN 5 Pin 180°	0.09
PS38 DIN 5 Pin 240°	0.10
PS39 Jack 2.5mm Switched	0.11
PS40 Jack 3.5mm Switched	0.11
PS41 Jack 1/2" Switched	0.19
PS42 Jack Stereo Switched	0.28
PS43 Phono Single	0.07
PS44 Phono Double	0.09
PS46 Co-Axial Surface	0.09
PS47 Co-Axial Flush	0.19

INSTRUMENT CASES

In 2 sections. Black or Blue Vinyl covered top and sides and bezels.

No.	Length	Width	Height	Price
BV1	8" x 5 1/2" x 2"			*£1.25
BV2	11" x 6" x 3"			*£1.62
BV3	6" x 4 1/2" x 1 1/2"			0.92
BV4	9" x 5 1/2" x 2 1/2"			£1.39

20p P. & P. Per Box.

RECORD CASES

7" E.P. 18 1/2" x 7" x 8" (50 records)	*£2.48
12" L.P. 13 1/2" x 7 1/2" x 12 1/2" (50 records)	*£3.30

CASSETTE CASES

Holds 15. 10" x 3 1/2" x 5". Lock and handle	*£1.50
--	--------

8-TRACK CARTRIDGE CASES

Holds 14. 13" x 5" x 6". Lock and handle	*£2.20
Holds 24. 12 1/2" x 8" x 5 1/2". Lock and handle	*£3.20

BI-PAK

P.O. BOX 6, WARE · HERTS

DIGITAL : CLOCKS : KITS : CALCULATORS

"ALPHA": 4 GREEN 0.5in HIGH DIGITS 12/24 hr

	Alarm	Std
Alpha Module (excl. case)	Kit	£13.00 £10.00
Alpha Module (excl. case)	Built	£14.00 £11.00
Alpha complete: Perspex Case	Kit	£15.50 £12.50
Alpha Clock: Perspex Case	Built	£21.50 £17.50

ALARM

- Tilt Snooze ● AM/PM ●
- Mains failure indicator ●
- Auto-Control Brightness by Photocell ●

"DELTA": 4 RED 0.5in HIGH LEDs 12 hr

	Alarm	Std
Delta Module (excl. case)	Kit	£11.50 £9.00
Delta Module (excl. case)	Built	£12.00 £9.50
Delta complete: Perspex Case	Kit	£15.00 £12.00
Delta Clock: Perspex Case	Built	£21.00 £17.00
Delta complete: Teak Case	Kit	£15.70 £12.70
Delta Clock: Teak Case	Built	£21.70 £17.70

Perspex Case Colours: Black, White, Red, Green, Blue, Orange
Teak case in real Teak veneer.
Complete Clocks: 2 year guarantee.

"NOVUS" CALCULATORS Send for brochures

650 Mathbox	£5.40	850 Mathbox	£6.75
4510 Mathematician	£16.20	6020 Statistician	£21.60

Module kits
£9.00

INCL. VAT. P & P
SATISFACTION GUARANTEED

- Modern 2 Part Case
- Drilled P.C.B.
- 4 Digit Display 0.5 inch high
- All components included
- Even Mains lead included
- Full Instructions
- Assembly Drawing
- Circuit Diagram


You supply only mains plug and standard tools. Easy!

C.W.O. PULSE ELECTRONICS LTD (PE13), 202 Shefford Road, Clifton, Shefford, Beds. S.A.E. complete range. Phone Hitchin (0462) 814477

SILICON SOLAR CELLS 0.5V 15mA at 35p, 0.5V 50mA at 50p, 0.5V 100mA at 60p, 0.5V 200mA at £1.
POWER TRANSISTORS 3W MP8112 npn at 15p, MP8512 pnp at 15p.
STACKPOLE ROCKER SWITCHES 5A 250V at 15p or 4 for 50p.
PLASTIC SCR's 50 PIV 6A at 15p, 400 PIV 6A at 40p.
1,000µf 40VW. Size 1 1/2" x 1/2" at 3 for 35p.
50 ASSORTED RADIO and TV KNOBS at 57p.
100 ASSORTED 1/2 and 1/4 W RESISTORS 17 values at 57p.
VHF DUAL GATE MOS FET like 40673 at 33p, 4 for £1.10.
50 AC 128 TRANSISTORS Branded but untested at 57p.
20 ASSORTED TUNING VARACTORS untested at 45p.
GERMANIUM TRANSISTORS AC153K, AC176K, AC187K, AC188K, AC141K, AC142K. All at 20p each.
LINE OUTPUT TV TRANSISTORS R2008 at 75p, R2010B at £1.25.
60 ASSORTED WIRE WOUND RESISTORS 1 to 10 W at 57p.
100 SUB-MINIATURE CERAMIC PLATE CAPACITORS ASSORTED from 3.3pF to 0.01µF 60VW at 57p.
POSTAGE STAMP TRIMMERS 10pF, 30pF, 50pF, 150pF, 750pF, 1,000pF at 6p each.
TEXAS BC 212 TRANSISTORS 6 for 57p.
ZN 414 RADIO I.C. with circuit at £1.20.
ITT 100µF 16VW size 1/2" x 1/2" 6 for 35p.
500 yd Reel of PVC 14 Strand 0.0048 CABLE at £3.
PLASTIC TRIACS 400 PIV 6 amp at 60p each.
50 PLASTIC NPN TRANSISTORS 85% good at 57p.
50 PLASTIC PNP TRANSISTORS 85% good at 57p.
SINGLE POLE MAKE 5A contacts KACO 12V RELAY at 50p.
20 ASSORTED BRANDED ITT 25mW ZENERS at 75p.
20 ASSORTED BRANDED STC 750mA DIODES at 50p.
BD 187 4A PLASTIC npn TRANSISTOR at 40p each, 4 for £1.30.
20 P CHANNEL MOS FET's with circuits for 68p.
5W TO-39 POWER DARLINGTON TRANSISTORS at 20p each.
7 ASSORTED JAPANESE and CONTINENTAL VOLUME CONTROLS at £1.
27 volt 400 mW ZENERS at 10p each, 6 for 50p.
50 ASSORTED TRANSISTOR ELECTROLYTICS at 57p.

Please add 20p for post and packing for orders under £2

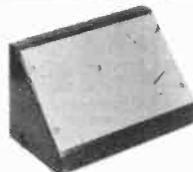J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln, LN2 1JF
Tel: 20767



New sloping cases from OLSON

Type	Panel Dim	Depth	Height	Price
1	150mm x 100mm	95mm	95mm	£1.55
2	200mm x 100mm	95mm	95mm	£1.75
3	250mm x 100mm	95mm	95mm	£1.95

PLEASE ADD 40p P. & P. and VAT


New range of cases at 45° sloping panels. Attractively designed, of robust construction, and finished in two tone colour. supplied complete with four rubber feet. Available from stock in three different widths.

MATERIALS

Cases made from 20g steel. Front panels made from 20g aluminium.

COLOURS

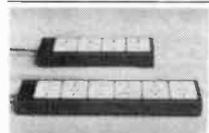Cases sprayed in light brown hammer finish.
Front panels sprayed in light grey semi gloss enamel.



PORTABLE POWER DISTRIBUTION

Complete with 6ft cable and 13A plug.
4 sockets 13A £8.80
6 sockets 13A £10.45
4 sockets 13A + SW £10.06
6 sockets 13A + SW £11.11

Please add 60p post and packing plus VAT

Trade counter is open for personal callers from 9 a.m.-5 p.m., Monday-Friday

OLSON ELECTRONICS LTD.
5-7 LONG STREET, LONDON E2
Tel. 01-739 2343

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1)	1	2	3	4
Coil ohms				
	52	4-8	2 c/o	75p*
Col. (2)	58	5-9	6 c/o	85p*
Working d.c. volts	185	8-12	6M	85p*
Col. 3	230	9-18	2 c/o HD	85p*
	430	15-24	4 c/o	85p*
Contacts Col. (4)	600	10-20	6M	85p*
	700	12-24	2 c/o	65p*
	700	16-24	4 c/o	85p*
	700	16-24	4M2B	65p*
Price	1,250	18-36	2 c/o	65p*
	2,500	31-43	2 c/o HD	65p*
HD=	2,500	36-45	6M	65p*
Heavy duty	15k	85-110	6M	65p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS

6 VOLT D.C. 1 make contacts 45p. Post 15p.
9 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 70 ohm coil. 85p. Post 15p.
12 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 120 ohm coil. 85p. Post 15p.
100 VOLT A.C. 2 c/o 75p. 3 c/o 85p. Post 15p.
ENCLOSED TYPE RELAYS
24 VOLT D.C. 3 c/o 85p. Post 20p. Base 15p extra.
24 VOLT A.C. Mfg. by ITT. 3 d.c. c/o contacts. 65p. Post 20p. Base 15p.
55 VOLT A.C. RELAY
 3 h.d. c/o contacts. Price 65p. Post 20p. Base 15p.
230 VOLT RELAY
 3 h.d. c/o contacts. Price 85p. Post 20p. Octal plug in base 15p extra.
230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price £1-10. Post 20p.
220/240 VOLT A.C. RELAY
 3 c/o 5 amp contacts. Sealed. Mfg. ISKRA. £1-35. Post 20p. Base 15p extra.
CLARE-ELLIOTT TYPE RP7641 G8
 Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 80p post paid.

LATCHING RELAY

Twin latching relay, "flip-flop" 2 c/o each relay. Mains contacts. 115V A.C. or 50V D.C. operation. 240V A.C. with 2.5K resistor. 85p. Post 20p.



C/O MICRO SWITCH

VERY SPECIAL OFFER. Mfg. by C.E.M. 3 amp 250 volt. 10 amp 125 volt. 50 for £3. Post 36p. 100 for £5. Post 50p. £1,000 for £45. Post paid. Bulk purchase means LOW/LOW prices.
DOUBLE POLE C/O or 2 make/2 break micro switch. 10 amp 250v a.c. With detachable roller assembly. 10 for £2-50. Post 50p (min. order 10).



MINIATURE C/O ROLLER MICRO SWITCH

OMRON Type V15 FL22/IC. 10 for £2-50. (Min. order 10).



230/250 VOLT A.C. SOLENOID

Approximately 1½ lb pull. Size of feet 1½" x 1½". Price £1-00. Post 20p.
HEAVY DUTY TYPE. 10 lb. (approx.) pull. £2-50. Post 50p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two x approx. 1lb pull x 1 inch travel. 6 x approx. 4oz. pull x 1 inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2-50. Post £1. **ABSOLUTE BARGAIN.**



600 WATT DIMMER SWITCH
 Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. £2-75. Post 25p.
 1,000 watt model. £4. Post 25p.
 2,000 watt model. £8. Post 40p.

CENTRIFUGAL BLOWER

Mfg by Smiths Industries. 230/240V a.c. Miniature Model. Series SE/200. Size 95mm x 82mm x 82mm. Aperture 38mm x 31mm. 12 c.f.m., £2-75. Post 50p.
 Mfg. by Airflow Developments Ltd. Precision made, continuously rated, smooth running. 220/240V a.c. motor, 80 c.f.m. As illustrated but with round aperture, £6-50. Post 75p.
 Mfg. by Woods. Extremely powerful. 220/250V a.c. 0-3A 2,700 r.p.m. continuously rated. Capacitor start. Cast construction. Aperture 66mm x 50mm, O/A 200mm. £12. Post £1.
 Mfg. by Parvalux Type SD38B. 220 volt A.C. 50Hz. 0.95 amp. Continuously rated 2800 r.p.m. 120 cfm. Brand New. Fraction of makers price. £10. Post £1.



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp) £10-00

0.5 KVA (2½ amp) (MAX) £11-50

1 KVA (5 amp) (MAX) £16-50

2 KVA (10 amp) (MAX) £30-00

3 KVA (15 amp) (MAX) £33-00

4 KVA (20 amp) (MAX) £60-00

37.5 amp (MAX) £102-50

CARRIAGE AND PACKING EXTRA



L.T. TRANSFORMERS

0, 6, 12 Volt at 10 amp. £6-15. Post 70p.

0, 10, 17, 18 Volt at 10 amp. £8-70. Post £1-00

0, 4, 6, 24, 32 Volt at 12 amp. £10-90. Post £1-00

0, 6, 12 Volt at 20 amp. £9-90. Post £1-00

0, 12, 24 Volt at 10 amp. £10-30. Post £1-00

0, 6, 12, 17, 18, 20 Volt at 20 amp. £11-80. Post £1-00

Other types to order at short notice—Phone your enquiries.

AUTO TRANSFORMERS

Step up, step down, 0-115/200/220/240 volts at 75 watt £3. Post 40p. 150 watt £4-30. Post 50p. 300 watt £6-20. Post 60p. 500 watt £9-20. Post 75p. 1000 watt £13-50. Post 90p.

STROBE! STROBE! STROBE!

HY-LIGHT STROBE MK IV

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes £15-40. Post 75p.

XENON FLASHGUN TUBES

Range of Xenon tubes available from stock. S.A.E. for details.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt, £6-05 (callers only). 2ft 20 watt, £4-68. Post 60p. (For use in standard bi-pin). MINI. 12in 8 watt, £1-76. Post 25p. 9in 6 watt, £1-43. Post 25p. Complete ballast unit and holders for 9in and 12in tube, £1-87. Post 30p. (9in and 12in measures approx.)

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watt of spot lights, flood lights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically new. Price only £60. Post 75p. S.A.E. (Foolsap) for further details.



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

6" graphic wheels, 3½" cassettes. S.A.E. (Foolsap) for details.

TIME SWITCH

'Horstmann' Type V Mk. II Time switch. 200/250 volt A.C. Two on/two off every 24 hours, at any manually pre-set time. 30 amp contacts. 36 hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board Spec. individually tested. Price £7-75. Post 50p. (Total incl. VAT £8-91)



WHY PAY MORE?

MULTI RANGE METER. A.C. volts 2.5-500, D.C. volts 2.5-500 (Sensitivity 2000Ω/V d.c. and a.c.). D.c. current 0/1/10/100 mA, Ohms range. Sturdy compact moving coil instrument with 21 ranges. Dimensions 120 x 80 x 44mm. Weight 0.32kg.
SERVICE TRADING CO. Price £5-00. Post 50p. (Total price incl. VAT and post £5-94). Incl. leads and battery.



VAT

VAT AT 8% MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

SERVICE TRADING CO.

ROTARY VACUUM AIR PUMP AND COMPRESSOR

Carbon vane, oilless, 100/115V a.c., ½ h.p. motor, 50/60 cycle, 2875/3450 r.p.m., 20 in vacuum, comp. 1.25 c.f.m., 10 p.s.i. (approx. figures). New unused surplus stock. Supplied with electrical connection data. FRACTION OF MAKERS' PRICE £12. Post £1-00. Suitable 110/240V, 150 watt auto transformer £3-50, Post 50p. (Both items together Post £1-25).



GEARED MOTORS

100 R.P.M.

115 lb. ins. 110 volt, 50Hz. 2.8 amp, single phase, split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250 mm. Dia. 135 mm. Spindle dia. 15.5 mm. Length 145 mm. Ex-equipment tested £14. Post £1-50. Suitable transformer 230/240 volt operation £8. Post 75p.

60 R.P.M. REVERSIBLE

220/240V a.c. Small, powerful, continuously rated, reversible motor. M.f.g. Berger (Germany). Size 80mm x 65mm x 65mm. Spindle dia. 6mm x 15mm long. Weight 725g. £5-50. Post 50p.

BODINE TYPE N.C.I.

(Type J) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. 50Hz. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50Hz. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115V A.C. Supplied complete with transformer for 230/240V A.C. input. Price, either type £6-25. Post 75p or less transformer £3-75. Post 65p.



15 R.P.M.

Type SD48 80 lb. in. input 100/200 volt A.C. Length incl. gearbox 270 mm. Height 135 mm. Width 150 mm. drive shaft 16 mm. Weight 8.5 Kilos. BRAND NEW. Price £10. Carr. £1. Suitable transformer for use on 220/240 volt A.C. £3-85. Post 50p.

20 R.P.M.

230/240 volt a.c. miniature motor. Price £1. Post 20p.

REVERSIBLE MOTOR

General Electric, 230V a.c. 1,600 r.p.m. 0.25A. Complete with anti-vibration mounting bracket and capacitor. O/A Size 110mm x 95mm. Spindle ½ in. dia. 20mm long. Ex. equipment tested, £3. Post 50p.



INSULATION TESTERS

NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. Bin. W. 4in. H. 6in. weight 6lb. 500V, 500 megohms, £36. Post 80p. 1,000V, 1,000 MΩ, £44. Post 80p.



TRIAC

Raytheon Tag symmetrical Triac. Type TAG. 250/500V, 10 amp, 500 p.i.v. Glass passivated plastic triac. Swiss precision product for long term reliability £1-00. Post 10p. (Inclusive of Data and application sheet.) Suitable Diac 18p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135mm x 130mm x 60mm. Price £2-25. Post 40p. (Total incl. VAT and Post £2-87).



POWER RHEOSTATS !!!

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
 25 WATT 10/25/50/100/150/250/500/1k/1-5k ohm. £1-70. Post 20p.
 50 WATT 1/5/10/25/50/100/250/500/1k ohm. £2-10. Post 25p.
 100 WATT 1/5/10/25/50/100/250/500/1k/1-5k/2-5k/3-5k/5k ohm £3-30. Post 35p.
 Back Silver, Skirted knob calibrated in Nos. 1-9 1½ in. dia. brass bush. Ideal for above 22p each.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
 LONDON WC2H 7JJ
 Phone 01-437 0576

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All mail order and callers to this address please—callers only to 21 Deptford Broadway, SE8 (Tel. 01-692 2009) and 38 Lower Addiscombe Road, Croydon (Tel. 01-688 2950)

Brand new full spec components by return of post:

TRANSISTORS	
AC127	20p
AC128	20p
AC151	20p
AC176	20p
AC187	25p
AC188	25p
ACY17	22p
ACY19	31p
ACY20	19p
ACY21	28p
ACY39	27p
AD181	40p
AD182	40p
m/pr:	80p
AF117	20p
AFY19	32p
AF239	44p
ASY26	29p
ASY27	33p
ASZ23	27p
BC107	10p
BC108	10p
BC109	10p
BC116A	15p
BC118	11p
BC119	21p
BC126	20p
BC139	24p
BC140	21p
BC143	22p
BC147	12p
BC148	11p
BC149	13p
BC157	12p
BC158	11p
BC159	13p
BC161	22p
BC171	13p
BC172	14p
BC182	11p
BC183	12p
BC184	13p
BC206	9p
BC212	12p
BC213	13p
BC214	14p
BC267	13p
BC297	16p
BC328	13p
BC347	13p
BC348	10p
BC461	28p
BC548	11p
BCY43	22p
BCY70	15p
BCY71	15p

All types: 25+ less 15%, 100+ less 25%

RECTIFIERS

1N4001 8p; 1N4002 7p; 1N4003 8p; 1N4004 9p; 1N4005 10p; 1N4006 11p; 1N4007 12p; 1N4148 4p; BY127 17p; OA5 60p; OA10 40p; 100V3A 15p; 400V3A 20p; 1300V1A 16p.

TRANSISTOR PACKS

200 assorted mainly out of spec transistors, mostly unmarked—NPN, PNP plastic, TO5, TO18, RF, AF, small signal and TO3 power devices. About 75% usable devices. Only £1.60. 1,000 unmarked 1N4148 diodes, 95% OK. Only £4.

100 unmarked BC108, untested £2.10.

SCR's

2N1595 30p; 2N2323A 34p; 500V5A (TO66 case) 80p; 600V 1A 75p.

RESISTORS

Mullard CR25 ½W 5% (10% over 1MΩ). All values in E12 Series from 1 ohm to 10MΩ 1½p each. Metal Film 1W 5%. All values in E12 series from 27 ohms to 10MΩ 2½p each. 2½W wirewound 8p; 5W wirewound 16p; 15W wirewound 12p. 1% and better. S.A.E. for list

ZENERS

400 mW BZY88 series, all voltages from 3V to 30V 10p each. 1 Watt plastic: all voltages from 3V to 200V 20p each.

See Practical Wireless for details of packs of components, surplus goods, etc. All prices quoted include VAT at new rate. Add 15p postage on orders under £2. SAE with enquiries or for List please. Send 10p for Multimeter catalogue—free on request on orders over £3. Official Orders accepted from Schools, etc. Export/Wholesale enquiries welcome. Surplus components always wanted.

IC's

723 TO99 60p; 741C 6 pin DIL 30p; 748C 14 pin DIL 40p; 555 55p; LM301A 50p; SL521B E5-62; SN76013ND E1-12; TAD100 E1-17; TCA270Q E3-60; ZN414 E1-35

ELECTROLYTIC CAPACITORS

Wire ended horizontal mounting (some of the smaller values may be vertical mounting)

0.47µF	25V	5p	250µF	16V	7p
1µF	25V	8p	470µF	16V	9p
2.2µF	25V	6p	470µF	25V	11p
4.7µF	25V	6p	470µF	35V	13p
10µF	25V	6p	470µF	63V	16p
22µF	25V	6p	1000µF	10V	11p
47µF	25V	6p	1000µF	16V	15p
47µF	40V	7p	1000µF	25V	16p
47µF	63V	7p	1000µF	50V	32p
100µF	10V	6p	1000µF	63V	40p
100µF	25V	7p	2200µF	10V	16p
100µF	40V	8p	2200µF	16V	22p
200µF	10V	6p	2200µF	25V	27p
200µF	50V	9p	2200µF	40V	46p
220µF	25V	9p	4700µF	16V	40p
220µF	30V	10p			

POLYESTER C280 250V

0-01, 0-015, 0-022, 0-033, 0-047, 0-068, all 3p each. 0-1, 0-15, 4p; 0-22, 6p; 0-33, 7p; 0-47, 8p; 0-68, 10p; 1µF, 13p; 2-2µF, 16p; 3-3µF 63V, 22p.

CERAMIC PLATE 50V

22pF to 820pF E12 series 2p each; 1000pF 3p.

VEROBXES AND CASES

Case type:
1410, 205 x 140 x 40mm £2-90
1411, 205 x 140 x 75mm £3-25
1412, 205 x 140 x 110mm £4-20
Plastic Boxes—Professional quality, two tone grey polystyrene boxes with threaded inserts for mounting PC boards.

Type 2518, 120 x 65 x 40mm £1-52; 2520, 150 x 80 x 50mm £1-75; 2522, 188 x 110 x 60mm £2-40; sloping front type: 220 x 174 x 100/52mm £4-20.

ALUMINIUM BOXES

Supplied complete with base and PK screws. Big reduction for quantity.
AB7 133 x 70 x 38mm 80p
AB8 102 x 102 x 38mm 80p
AB9 102 x 70 x 38mm 55p
AB10 102 x 133 x 38mm 80p
AB11 102 x 64 x 51mm 55p
AB12 76 x 51 x 25mm 48p
AB13 152 x 102 x 51mm 80p
AB14 178 x 127 x 64mm £1-06
AB15 203 x 152 x 76mm £1-42
AB16 254 x 178 x 76mm £1-70
AB17 254 x 114 x 76mm £1-22
AB19 305 x 203 x 76mm £2-10

BATTERY HOLDERS

For 4 x HP7 2 by 2 or side by side. Both types 16p. For 4 x HP11, 2 by 2 or side by side. Both types 24p.

RF CHOKES

10, 47, 68µH 9p. 1.5, 2.5, 5, 7.5 10mH 30p.

OPTO DEVICES

Light sensor type H61. Only 15mm long by 2.1mm dia. Dark current 0.01µA. Light current 250µA 70p. MRD450 Photodiode 50p. LED's red or green 0.2in 22p. TIL 209 red LED 15p.

DEVELOPMENT PACKS

50V ceramic plate capacitors, 5%: 10 of each value 22pF to 1,000pF, total 210 caps., £2-70.
CR25 carbon film ½W resistors, 5%: 10 of each value 10 ohms to 1MΩ, total 610 resistors, £6.
Electrolytics, wire ended 25V working, 10 each of: 1.2-2, 4.7-10, 22, 47 and 100µF. 70 capacitors for £3-20.
400mW zeners 5%, 10 each 3V to 30V, 260 in all. Only £14.

P. F. RALFE

10 CHAPEL ST. LONDON NW1 Phone 01-723 8753

MUFFIN INSTRUMENT FANS

Dimensions 4.5in x 4.5in x 1.5in. Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers, etc. For 110V, a.c. operation (practice is to run from split primary of mains transformer or use suitable mains dropper). CC only 11 watts. List price over £10 each. Our price in brand new condition, is £4-50.

AVO VALVE TESTERS

Brief-case type 160. Full working condition throughout, £85.

CO-AXIAL CHANGE OVER RELAYS

Suitable for frequencies up to 1000MHz. 48V d.c. coil. Brand new £5-50. "N"-type plugs available (3 required) at 50p each.

MINIATURE OEAC NI-CADMIUM

batteries type 70DK, 3 cells in package making 3-7V. 25 x 17 x 15mm. 75p each.

DIGITAL FREQUENCY METERS

Manufactured by Schnelder, type FT300. Reads as frequency meter up to 99.99kHz or as tachometer to 99.990rpm. Solid state. Size only 8 x 5 x 3in., 4½lb. Brand new in original packaging. Price only £55.

ALL GOODS QUOTED ARE INCLUSIVE OF POSTAGE AND PACKING BUT EXCLUSIVE OF 8% VAT. USUAL DESPATCH TIME FOR GOODS 1-3 DAYS.

500V TRANSISTORISED INSULATION TESTERS

Small size, light-weight, 13 x 7 x 4cm. Reads insulation from 0.2 to 100MΩ. Brand new, only £16-50. Battery (PP3), leads and case £1 extra.

ADVANCE type 63A AM/FM R.F. signal generators, 7.5-230MHz Dev. 0-22.5 and 0-75kHz. X-sweep output. Crystal calibrator. Scope output, £75.

250V WEE MEGGER

Insulation testers (wind-up type). Quantity of secondhand, good condition, available at only £8-50.

METRIX TYPE 210 WOBBLATORS

0-25mHz. Sweep width 0.5-20mHz. Output 100mV attenuable in steps of 10 to 10µV. Last few of these left at only £15 each to callers only.

ICL 8-hole tape readers. As new £80.

TELETYPE 8-hole tape punches. £75.

APT POWER SUPPLY UNITS. Variable 4-7V at 2A. Brand new in original packing, £22.

SWISS HOUR METERS National Watch Co. 110V 50Hz. 5 digits. Size approx. 5 x 3.5 x 2.5cm. Digit height 3mm. Brand new, £1-50.

ELECTROVALUE

The good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

CATALOGUE 8 ISSUE 2 READY NOW!

Second printing (Green cover) with up-dated information, 144 pages. New items. Opto-electronics. Diagram of components, applications, I.C. circuits, etc. Post free 40p, including voucher for 40p for use on order over £5-00 list value. A must for careful buyers.

DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT.
5% on orders list value £5 or more 10% on orders list value £15 or more

FREE POST AND PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 15p handling charge.

PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months. Next review period effective from July 1st.

QUALITY GUARANTEE

On everything in our Catalogue—No manufacturers rejects, seconds or sub-standards merchandise.

ELECTROVALUE LTD

All communications to Dept. 8-2, 28 ST. JUDAS ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 9HB. Telephone Egham 3603. Telex 284475. Shop hours 9-5.30 daily, 9-1 pm Sat.

NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4845. Shop hours Daily 9-5.30 pm; 9-1 pm Sat.

10% Off on orders over £10
15% Off on orders over £50
20% Off on orders over £100

SHIPMENT MADE VIA AIR-POSTAGE PAID—3 DAYS FROM RECEIPT OF ORDER

TTL

7400	E0-11	74151	E0-13	74155	75
7401	11	7453	13	74156	71
7402	11	7454	14	74157	71
7403	11	7460	11	74161	95
7404	13	7464	21	74163	10
7405	13	7465	21	74164	10
7406	22	7472	22	74165	1-25
7407	22	7473	26	74166	1-15
7408	14	7474	26	74173	95
7409	14	7475	41	74175	95
7410	11	7476	26	74176	95
7411	16	7483	70	74177	85
7413	29	7485	80	74180	80
7416	22	7486	24	74181	2-50
7417	22	7489	1-50	74182	80
7420	11	7490	40	74184	1-55
7422	22	7491	71	74185	1-30
7423	22	7492	44	74190	95
7425	22	7493	44	74191	95
7426	23	7494	49	74192	90
7427	22	7495	49	74193	85
7430	12	7496	55	74194	95
7432	22	74100	1-00	74195	72
7437	25	74105	60	74196	1-00
7438	21	74107	27	74197	75
7440	11	74121	28	74198	1-70
7441	60	74122	50	74199	1-70
7442	55	74123	55	74200	3-90
7443	55	74125	50		
7444	60	74126	50	74132	-50
7445	75	74141	68		
7446	85	74145	75		
7447	73	74150	75		
7448	80	74151	60		
7450	12	74153	71		

LOW POWER TTL

74100	E0-16	74151	E0-16	75190	E0-93
74102	16	74155	18	74191	80
74103	16	74171	18	74193	89
74104	18	74172	27	74195	89
74106	18	74173	38	74198	1-53
74110	16	74174	38	74164	1-53
74120	16	74178	44	74165	1-53
74130	16	74185	85		
74142	89	74186	38		

LOW POWER SCHOTTKY

74LS00	E-23	74LS32	25	74LS95	1-20
74LS02	23	74LS40	30	74LS107	35
74LS04	23	74LS42	80	74LS164	1-20
74LS08	25	74LS74	40	74LS193	1-30
74LS10	23	74LS90	80	74LS197	1-20
74LS20	23	74LS93	80		

SCHOTTKY

74500	23	74508	30	74522	23
74502	30	74510	23	74532	35
74503	23	74520	23	74574	23
74504	30				

HIGH SPEED TTL

74H00	E0-16	74H22	E0-18	74H61	E0-25
74H01	16	74H30	18	74H62	20
74H04	16	74H40	16	74H74	32
74H08	16	74H50	16	74H103	35
74H10	16	74H52	18	74H102	35
74H11	16	74H53	20	74H103	40
74H20	16	74H55	20	74H106	40
74H21	16	74H60	21	74H108	40

8000 SERIES

8091	E0-33	8214	E0-93	8811	E0-38
8092	33	8220	93	8812	60
8095	76	8230	1-42	8822	1-42
8121	49	8520	71	8830	1-42
8123	98	8511	91	8831	1-42
8130	1-20	8552	1-37	8836	27
8200	1-42	8554	1-37	8880	73
8210	1-92	8810	44		

9000 SERIES

9002	E0-21	9109	E0-49	9601	E0-54
9101	63	9312	49	9602	49

DTL

930	10	937	10	949	10
932	10	944	10	962	10
936	10	946	10	963	10

Zener Diodes, Diodes & Rectifiers

IN 486B	Diode	250V	E0-15	10/E-90
IN 715A	Zener	11V	-15	10/-90
IN 756A	Zener	3.6V	-15	10/-90
IN 756A	Zener	8.2V	-15	10/-90
IN 756A	Zener	8.2V	-15	10/-90
IN 904	Sw. Diode	30V	-7	10/-50
IN 914	Sw. Diode	100V	-7	10/-50
IN 967B	Zener	18V	-15	10/-90
IN 2990A	Zener	33V	-75	10/S-
	(Stud Mt.)			
IN 3064	Sw. Diode	75V	-12	10/-80
IN 3600	Sw. Diode	50V	-12	10/-80
IN 3604	Sw. Diode	75V	-12	10/-80
IN 4148	Sw. Diode	75V	-7	10/-50
IN 4858	Zener	120V	-15	10/-90
IN 5230A	Zener	4.7V	-15	10/-90
IN 5242B	Zener	12V	-15	10/-90

MISC. DEVICES

ULN2288	FM gain block	34dB mDIP	-90
ULN2299	FM gain block	48dB mDIP	-90
2513	64 x 8 x 5 character generator		6-
CA3046	Transistor array	14 pin DIP	-50

CMOS

4000A	E	18	4016A	40	4049A	42
4001A	18	4017A	85	4050A	42	
4002A	18	4020A	1-06	4066A	63	
4006A	96	4021A	98	4068A	31	
4007A	19	4022A	78	4069A	31	
4008A	1-27	4023A	18	4071A	19	
4009A	41	4024A	63	4072A	25	
4010A	38	4025A	18	4073A	28	
4011A	19	4027A	42	4075A	28	
4012A	18	4028A	70	4078A	28	
4013A	32	4030A	32	4081A	19	
4014A	1-06	4035A	90	4082A	25	
4015A	1-06	4042A	1-05	4528A	1-14	
				4585A	1-49	

74C00	E0-21	74C74	E0-63	74C162	E1-70
74C02	30	74C76	93	74C163	1-78
74C04	41	74C107	82	74C164	1-92
74C08	41	74C151	1-59	74C173	1-59
74C10	36	74C154	1-92	74C195	1-65
74C20	36	74C157	1-20	80C95	82
74C42	1-18	74C160	1-78	80C97	82
74C73	85	74C161	1-78		

TANALUM CAPACITORS

.1 mfd	35V	12p	6.8 mfd	6V	15p
.33 mfd	35V	12p	6.8 mfd	50V	18p
1 mfd	35V	12p	10 mfd	25V	18p
2.2 mfd	20V	12p	15 mfd	10V	18p
2.2 mfd	35V	12p	33 mfd	10V	20p
4.7 mfd	16V	15p	47 mfd	6V	20p

LED's

MV10B	Red TO 18	E0-14
MV50	Axial leads	8
MV50Z0	lumbo Vis. Red (Red Dome)	18
	lumbo Vis. Red (Clear Dome)	18
ME4	Infra red diff. dome	18
MAN1	Red 7 seg. .270"	1-38
MAN2	Red alpha num. .32"	2-72
MAN3	Red 7 seg. .127" straight pins	16
MAN4	Red 7 seg. .190"	1-18
MAN5	Green 7 seg. .270"	1-62
MAN6	5" high solid seg.	3-81
MAN7	Red 7 seg. .270"	74
MAN8	Yellow 7 seg. .270"	2-17
MAN66	5" high spaced seg.	2-55
MCT2	Opto-iso transistor	38

MULTIPLE DISPLAYS

NSN33	3 digit .12" red led 12 pin ITC I/O skt.	E-90
HP45582	5 digit .11 led magn. lens com. cath.	1-80
7405		
HP5082	4 digit .11 led magn. lens com. cath.	1-70
SP-425-09	9 digit .25" neon direct interface with MOS/LSI. 180 VDC. 7 seg.	98

SHIFT REGISTERS

MM5013	1024 bit accum. dynamic mDIP	E1-20
MM5016	500/512 bit dynamic mDIP	1-10
SLS-4025	QUAD 25 bit 2504 1024 bit multiplexed dynamic shift register	4-95

JUNE SPECIALS

CT5005 CALCULATOR CHIP
12 Digit - 4 function with memory - chain operation £8-00

DVM CHIP 4 1/2 DIGIT
MM 5330 - P channel device provides all logic for 4 1/2 digit voltmeter. 16 pin DIP with data £8

UV ERASABLE PROM
1702A - 2048 bit static PROM 256x8 elect programmable & erasable TTL/DTL comp. 24 pin DIP £8

8038 FUNCTION GENERATOR
Voltage controlled oscillator sine, square, triangular output 16 pin DIP with data £2-50

7001 CLOCK CHIP
4-6 digit, 12-24 hr. alarm, timer & date circuits with data £4-00

6 DIGIT LED CLOCK KIT

INCLUDES:
MM314 clock circuit
6 PN079 LED displays (250° red 7 segment)
All necessary transistors, resistors & capacitors
1 double sided PC board accommodates LED's & clock circuitry
Schematic & instructions
Does not include 12V-300 ma transformer, switches & case £ 7

UNIVERSAL BREADBOARD

Silver plated copper circuit board 3-3/16" x 5-1/16". 2 rows of 27 holes for DIP IC's + space for transistors, resistors & capacitors. Versatile and simple for bread-boarding IC circuitry £1


Data included with order on request. Add 20p ea. if item is priced below 50p. Add 40p ea. if item is not ordered.

LINEAR CIRCUITS

300	Pos V Reg (super 723) TO-5	£43
301	Hi Peril Op Amp mDIP TO-5	18
302	Volt follower TO-5	43
304	Neg V Reg TO-5	49
305	Pos V Reg TO-5	52
307	Op AMP (super 741) mDIP TO-5	38
308	Micro Pwr Op Amp mDIP TO-5	60
309K	SV 1A regulator TO-3	91
310	V follower Op Amp mDIP	65
311	Hi Peril V Comp mDIP TO-5	58
319	Hi Speed Volt Comp DIP	74
320	Neg Reg 5.2, 12 TO-3	74
320T	Neg Reg 5, 12, 15 TO-220	89
322	Precision Timer DIP	60
324	Quad Op Amp DIP	1-07
339	Quad Comparator DIP	92
340K	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-3	1-20
340T	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	1-07
370	ACC/Squelch AMPL DIP	80
372	AF-Inf Strip detector DIP	44
373	AM/FM/558 Strip TO-5	30
376	Pos V Reg mDIP	33
380	2w Audio Amp DIP	81
380-8	.6w Audio Amp mDIP	69
381	Lo Noise Dual preamp DIP	98
382	Lo Noise Dual preamp DIP	98
531	High Slew rate Op Amp	£1-80
540	Power driver TO-5	1-20
550	Pre V Reg DIP	44
555	Timer mDIP	54
556A	Dual 555 Timer DIP	89
560	Phase Locked Loop DIP	1-94
562	Phase Locked Loop DIP	1-94
565	Phase Locked Loop DIP TO-5	1-20
566	Function Gen mDIP TO-5	1-20
567	Tone Decoder mDIP	1-20
709	Operational AMP TO-5 or DIP	27
710	Hi Speed Volt Comp DIP	21
711	Dual Difference Compar DIP	38
723	V Reg DIP	38
733	Diff. video AMPL TO-5	-55
739	Dual Hi Peril Op Amp DIP	65
741	Comp Op Amp mDIP TO-5	25
747	Hi Peril Op Amp DIP or TO-5	44
748	Freq Adj 741 mDIP	27
1304	FM Multis Stereo Demod DIP	65
1307	FM Multis Stereo Demod DIP	45
1456	Int. compensated Op Amp mDIP	-79
1458	Dual Comp Op Amp mDIP	38
1800	Stereo Multiplexer DIP	1-50
1800	Quad Amplifier DIP	1-07
LH2111	Dual LM 211 V Comp DIP	33
3900	Quad Amplifier DIP	1-07
7524	Dual core memory sense Amp	1-94
7525	Dual core memory sense Amp	-80
8038	Voltage contr. osc. DIP	3-20
8864	9 DIG Led Cath Dvr DIP	1-37
75150	Dual Line Driver DIP	1-10
75451	Dual Peripheral Driver mDIP	21
75452	Dual Peripheral Driver mDIP	21
75453	(351) Dual Periph Driver mDIP	21
75481	Quad Seg Driver for LED DIP	50
75492	Hex Digit driver DIP	55

MEMORIES


1101	256 bit RAM MOS	96
1103	1024 bit RAM MOS	2-72
2102-2		

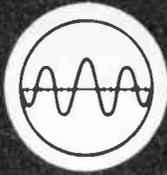

TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137 9080

PRE AMPLIFIERS

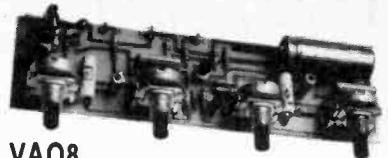

VA08

Designed for use with TUAC power amplifier modules. Extensive research has gone into various wide range tone control circuits to produce superb sound quality. Thousands are already in use in high quality professional amplification systems.

VA08 Vol. Treb, Mid and Bass controls. HI. IMP. FET. I/P suitable Mid. Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1kHz Bass x20 -10dB at 40Hz.

£6.50

VA06 Vol, Treb, and Bass controls. Sensitivity 8mV. Treb +28 -15dB at 12kHz. Bass ±18dB at 40 Hz.

£5.50

SVA08 STEREO PRE AMP Vol, Treb, Mid and Bass controls, I/P suitable, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 4kHz Bass +20 -10dB at 40Hz Plus Full Balance Control. Full I/C operation supply voltage ±15VDC.

£12.50

MONO DISCO MIXER WITH AUTO FADE




Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth, auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS. Specification: Deck Inputs—50mV into 1MΩ; Deck Tone Controls—treble +20 -10dB at 12kHz, Bass +22 -15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47kΩ; Power Requirements—30-50 volts at 50mA.

£31.50
PANEL SIZE
18 × 4½ in
DEPTH 3 in

★ TUAC AMPLIFIER MODULES ★ POWER AND QUALITY ★

- 125 watts R.M.S. continuous sine wave output

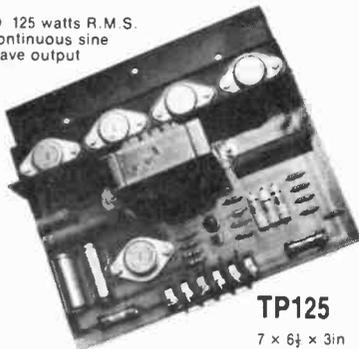

TP125


7 × 6½ × 3 in

£19.50


- 4 R.C.A. 150 watt 15 amp output transistors

- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

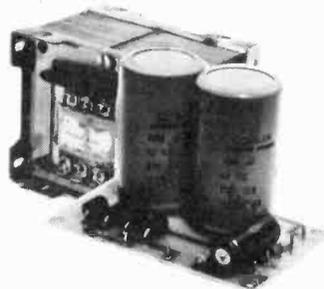Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply



PS 250 for supplying 2 TP125s £22.00
PS 60/60 for supplying 2 TL60s £19.50
PS 125 = 45 volts for TP125 £13.75
PS 100 = 43 volts for TL100 £12.00
PS 60 = 38 volts for TL60 £11.50
PS 30 = 25 volts for TL30 £7.50
PSU 2 for supplying disco mixer £5.50

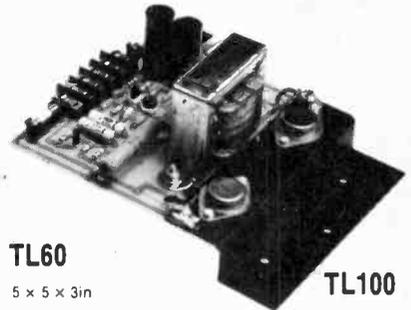

TL60

5 × 5 × 3 in

- 60 watts R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£13.50

TL100

5 × 5 × 3 in

- 100 watts R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

£16.25

Specification on all power modules: All output power ratings ±0.5dB. Output impedance 8-15 ohms THD at full power 2% typically 1%. Input sensitivity 60mV into 10kΩ. Frequency response 20Hz-20kHz ±2dB. Hum and noise better than -70dB.

STOCKISTS—CALLERS ONLY

Geo Mathews, 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)

Arthur Sallis Ltd., 28 Gardner Street (Tel. Brighton 65806)

Bristol Disco Centre, 26 The Promenade, Gloucester Road (Tel. Bristol 41666)

Socodi, 9 The Friars (Tel. Canterbury 60948)

Cookies Disco Centre, 132 West Street (Tel. Crewe 4739)

Leighton Electronics Centre, 59 North Street (Tel. Leighton Buzzard 2316)


A1 Music Centre, 88 Oxford Street, Manchester (Tel. 061-236 0340)

Damon Electronics, 99 Carrington Street (Tel. Nottingham 53880)

Electra Centre, 58 Lancaster Road (Tel. Preston 58488)

Mitchell Electronics, 64 Winchester Street (Tel. Salisbury 23689)

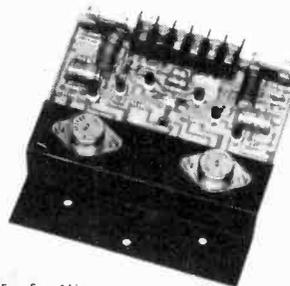Mitchell Electronics for Southampton area



5 × 5 × 1½ in

TL30

NEW FROM TUAC TL30 D.C. COUPLED POWER AMPLIFIER MODULE

- Output power 30 watts R.M.S. continuous sine wave
- Output impedance 8-15 ohms
- T.H.D. at full power 0.5%
- Signal to noise ratio -85dB
- Input sensitivity 60mV into 50k ohms
- Frequency response 25Hz-50kHz
- 8 transistors
- 4 diodes
- Only six connections

£9.75

Send large stamped addressed envelope with all enquiries or send £1 (refundable against purchase) for fully illustrated 20 page catalogue.

FUZZ LIGHT




**RED GREEN
BLUE AMBER**

240V a.c. Long Life Candle Bulb, Revolving Reflector, adds a new dimension to disco lighting effects.


£19.50

TUAC

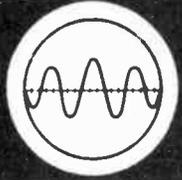MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
PERSONAL SHOPPERS MON. TUES. THURS. FRI and SAT
9 a.m. - 6 p.m. WED 9 a.m. - 1 p.m.



TUAC STEREO DISCO MIXER

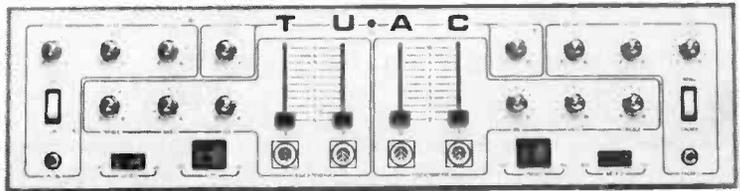

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble, and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls $\pm 18\text{dB}$ at 60Hz. Treble controls $\pm 18\text{dB}$ at 15kHz.
OUTPUT: Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz-25kHz $\pm 1\text{dB}$. P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.
Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switch. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

£97.50

Size: 25in long x 6in high x 3in deep



**TWIN
60**

£80.00

Output power 60 watts R.M.S. Four inputs, two channels each with volume, treble, middle and bass controls. Variable wave form control.


- ★ Lo-Line Twin 125 (125 watts version) **£98.00**
- ★ Lo-Line 60 (single pre-amp version) **£65.00**
- ★ Lo-Line 125 (single pre-amp version) **£81.00**
- ★ Lo-Line 125 slave output power 125 watts R.M.S. **£70.00**

▲ All Lo-Line Amplifiers are 25in long x 11in high x 6in deep ▼

NEW TUAC LO-LINE STEREO 250 125 WATTS PER CHANNEL — £130

3 CHANNEL LIGHT MODULATOR

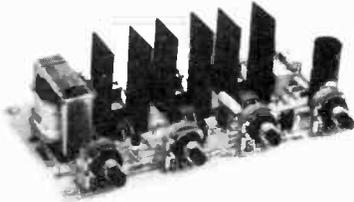
- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections



£15.50 (Single Channel Version 1500 Watts £7.25)


4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER—4LSMI

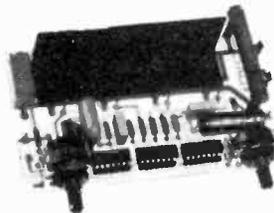- RCA 8A Triacs
- 1000V per channel
- Fully suppressed and fused
- Switched master control for sound operation from $\frac{1}{2}$ W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections



Patents applied for **£17.25**

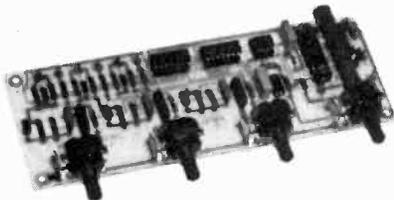ADD SEQUENCE CHASING AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel
- 9 easy connections

SEQUENCE DIMMER MODULE—3SDMI

£11.75

HOW TO ORDER BY POST


Make cheques/P.O.s payable to
TUAC LTD (PE6)
or quote Access/Barclaycard No.
and post to TUAC LTD: (PE6)
163 Mitcham Road, London, SW17 9PG
We accept phone orders against
Access/Barclaycard holders
Phone: 01-672 3137/9080.

ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING FREE

ACCESS AND BARCLAYCARD ACCEPTED—JUST SEND OR PHONE US YOUR NUMBER

HP ENQUIRIES INVITED

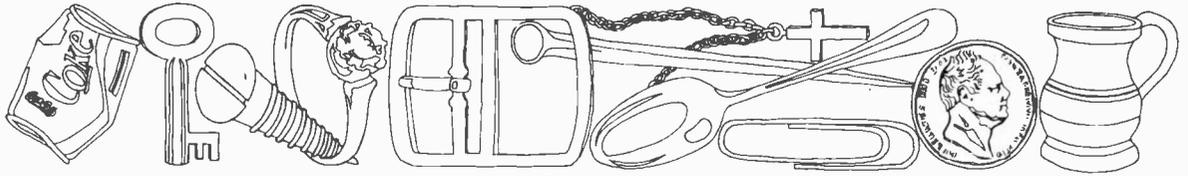A few interesting (and not so interesting) things you could find with a Heathkit Metal Locator.



With a Heathkit Metal Locator in your hand you can find buried metal objects as small as a halfpenny.


And, unlike many other locators, the Heathkit uses a special induction balance search system, which means you hear no tone at all until a metal object enters the locator's search field.

But, once a metal object is located you'll hear a signal through the loudspeaker (or optional headphones) which increases in volume the closer you get.

Two models are available: the GD-348 Deluxe Locator and the GD-48 Economy Locator.

Both models have a front panel meter to pinpoint your find. And the Deluxe model even allows you to differentiate between ferrous and non-ferrous metals.

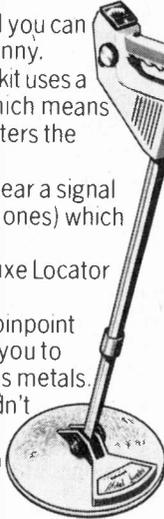And of course, being Heathkits, they couldn't be easier to build. The kits come absolutely complete—with a comprehensive instruction manual that takes you step by step through the assembly.



You'll find them both in the latest Heathkit catalogue. Just send us 10p for postage and we'll send you your copy. Besides the metal locators, you'll find a lot of other interesting things in it.

Heath (Gloucester) Ltd., Bristol Road, Gloucester, GL2 6EE. Tel: (0452) 29451. Showrooms in Gloucester and Tottenham Court Road, London. **HEATHKIT**

To: Heath (Gloucester) Ltd., Dept. PE-66,
Bristol Road, Gloucester, GL2 6EE.
Please send me a Heathkit catalogue.
I enclose 10p for postage.



Name _____

Address _____

Postcode _____

**EASY TERMS AVAILABLE
WITH HEATHKIT MONTHLY
BUDGET PLAN**

FND500 Jumbo 0.5" C.C. Red LED display now only £1.02

ADVANCED CLOCK KIT

(P.E. Mains Clock Feb./Mar. 76)

Complete kit including attractive slim case for 6 digit alarm clock with bleep alarm, snooze, high brightness driving of Jumbo LED displays, automatic intensity control—with optional add-ons of touch switch snooze control and crystal control/battery back-up. **£26.80**

P.E. CAR CLOCK with Journey Timer

6 digit clock for use in any car with 12V battery, with an independent journey timer incorporated. Bright Jumbo LED display comes on with ignition—automatic intensity control. Complete kit of all parts needed including case, PCB's and all components. Full instructions. **£39.50**

Easy to Build E.E. DIGITAL CLOCK (Jan. issue). Kit of all components, including case etc., for this attractive clock with 12mm green display. Full instructions. **£15.70**

50 Hz Xtal Timebase Kit for clocks (incl. advanced kit above). **£6.28**

CMOS ICs	CD4029 0-99	CD4059 4-77	CD4510 1-18	Displays
RCA MOT ONLY	CD4030 0-48	CD4060 0-97	CD4511 1-36	5LT-01 5-80
	CD4031 1-92	CD4061 18-92	CD4514 2-72	DL704E 0-75
CD4000 0-18	CD4032 0-92	CD4062 7-77	CD4515 2-72	FND500 1-02
CD4001 0-18	CD4033 1-21	CD4063 0-95	CD4516 1-18	Display Int.
CD4002 0-18	CD4034 1-65	CD4066 0-61	CD4518 1-08	SN75491 0-81
CD4006 1-02	CD4035 1-02	CD4067 3-12	CD4520 1-98	SN75492 1-02
CD4007 0-18	CD4036 2-23	CD4068 0-20	CD4527 1-37	CA3130 0-88
CD4008 0-83	CD4037 0-83	CD4069 0-20	CD4532 1-25	Flat Cable
CD4009 0-48	CD4038 0-93	CD4070 0-48	CD4555 0-78	20WAY 1M
CD4010 0-48	CD4039 2-23	CD4071 0-20	CD4556 0-78	10M for 8-50
CD4011 0-18	CD4040 0-92	CD4072 0-20	MC14528 1-38	10WAY 1M
CD4012 0-18	CD4041 0-73	CD4073 0-20	MC14534 6-04	0-60
CD4013 0-48	CD4042 0-73	CD4075 0-20	MC14553 5-29	10M for 4-80
CD4014 0-87	CD4043 0-87	CD4076 1-34	MC14566 1-21	IC Socket
CD4015 0-87	CD4044 0-81	CD4077 0-48	MCM14552 8-05	Pins
CD4016 0-48	CD4045 1-22	CD4078 0-20	CD4081 0-20	MM50253 5-60
CD4017 0-87	CD4046 1-16	CD4081 0-20	CD4082 0-20	MM5314 4-44
CD4018 0-87	CD4047 0-78	CD4082 0-20	MM5314 4-44	AY1553 3-50
CD4019 0-48	CD4048 0-48	CD4085 0-62	MM50250 5-00	AY1502 2-99
CD4020 0-97	CD4049 0-48	CD4086 0-62	CMOS	P & P
CD4021 0-87	CD4050 0-48	CD4089 1-34	751410J 2-64	ua78L12WC 0-60
CD4022 0-83	CD4051 0-81	CD4093 0-69	751411D 2-94	
CD4023 0-18	CD4052 0-81	CD4094 1-62	751412K 4-00	
CD4024 0-67	CD4053 0-81	CD4095 0-91		
CD4025 0-18	CD4054 1-01	CD4096 0-91		
CD4026 1-50	CD4055 1-14	CD4097 3-12		
CD4027 0-48	CD4056 1-14	CD4099 1-59		
CD4028 0-78	CD4057 21-56	CD4502 1-07		

ADD VAT at 8% (Higher rate does not apply to any of above).
25p P & P on all orders. Despatch is by 1st Class Post.
Price list and data sent FREE with an order, or on request (an SAE helps).
Official orders welcomed (written or phoned)—Univs. Polys. Govt. Cos. etc.
Export orders: No VAT, add 50p (Europe) £1 (overseas) for Airmail P & P.
(No Export outside Europe for databooks and transformers).

SINTEL, 53b Aston Street, Oxford. Tel. 0865 49791

ORION stereo amplifier


Complete Kit of semiconductors **£9.40**
High quality glass fibre P.C.B. **£2.75**

Screen printed with component locations

PHASE LOCKED STEREO DECODER

To MOTOROLA specification
COMPLETE KIT - £3.50

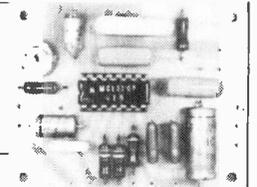Includes MC1310P, Glass fibre p.c.b., all resistors & capacitors, LED indicator and full instructions.



FERRANTI

BC107P 11p	ZTX108 9p	ZTX330 17p	ZTX530 18p	ZS176 33p
BC108P 9p	ZTX109 11p	ZTX331 18p	ZTX531 19p	ZS178 54p
BC109P 11p	ZTX212 15p	ZTX382 19p	ZTX550 19p	ZS270* 14p
BC415P 17p	ZTX213 15p	ZTX383 15p	ZTX551 17p	ZS271* 23p
BFS59 14p	ZTX214 17p	ZTX384 17p	2N3055* 70p	ZS272* 24p
BFS80 15p	ZTX239 10p	ZTX450 18p		ZS274* 29p
BFS81 15p	ZTX300 12p	ZTX451 19p	DIODES	ZS278* 36p
BFS96 14p	ZTX301 13p	ZTX500 14p	ZS142* 38p	ZS278* 57p
BFS97 15p	ZTX302 15p	ZTX501 14p	ZS170 13p	
BFS98 15p	ZTX303 16p	ZTX502 18p	ZS171 18p	ZENERS
ZTXA20 19p	ZTX304 19p	ZTX503 17p	ZS172 23p	BZV19 series
ZTX107 11p	ZTX320 18p	ZTX504 20p	ZS174 25p	4 ? to 47V 10p

FERRANTI CDI INTEGRATED CIRCUITS. All with circuits and data
ZN414 radio microcircuit £1. ZN1034E* precision timer i.c. £2.75. ZN424E low noise audio i.c. £1.
ZN1040E* universal count/display i.c. £8.25.

PE TV SOUND SEPARATOR

Complete kit of semiconductors £2.30. High quality glass fibre p.c.b. £1. Murata ceramic filters—SFE8.0MA 35p, CDA8.0MC 35p each.

MOTOROLA MC1310P only £1.80

with circuits and data

Glass fibre p.c.b. to suit MC1310P 66p. Red LED with clip 27p. MOTOROLA MC1357PQ £1.85;

BD699* £1.14; BD700* £1.28; MJ4032* £5.17; MJ4035* £4.95.

PE OPTO REV COUNTER FERRANTI M54A photocells £1.35*. PE JOANNA 77 ZTX108 for £15.

183 ZS170 diodes for £15.

POSTAGE AND PACKING 15p per order. Orders over £5 post free. All devices top grade, brand new and to full manufacturers spec. We do not sell seconds or rejects. Send SAE for our data sheet and price list!

PRICES DO NOT INCLUDE VAT—ADD 8% TO ITEMS MARKED * AND 12% TO ALL OTHERS

DAVIAN ELECTRONICS
PO BOX 38 . OLDHAM . LANCs . OL2 6XJ

DORAM


A PROFESSIONAL DEAL FOR AMATEURS

*ORDERS BY RETURN OF POST *NO QUIBBLE REPLACEMENT PART SERVICE
*QUALITY BRANDED PRODUCTS *FREE UP-DATE INFORMATION SERVICE

TOOLS

The handy EXPO 12V d.c. drill is supplied complete with drill kit containing 4 small drills, two spare collets, two cutters, wire brush, soft buffer, grindstone and 9 various milling and reaming tools.

Drill & kit £9.50 + s
Kit only £4.75 + s

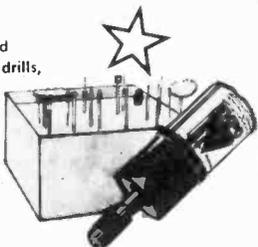

ORYX 50W SOLDERING IRON



Temperature can be altered between 200-400°C.

Iron 240V £6.90 + s
Stand £2.80 + s

ISO-TIP CORDLESS IRON

Mains and 12V d.c. versions available
£11.50 + s



DE-SOLDER TOOLS

Three high-suction models available

SR2 £6.20 + s
SR3 £5.20 + s
SR3AS £4.80 + s
Spare nozzle 60p ea. + s
Please state type



NICKEL - CADMIUM RECHARGEABLE CELLS

	Sim. to dry cell	nom. capacity	charge cur. (mA)	
HP7	None	0.5Ah	50	£1.10 s
HP11	None	1.2Ah	100	£1.24 s
HP2	None	2.0Ah	200	£1.80 s
HP2	None	4.0Ah	400	£2.70 s

ELECTRONIC IGNITION UNIT

- * High performance
- * For 2 & 4 stroke engines
- * Improved start/running
- * 'Crisper' throttle response
- * Reduce battery drain

Neg. earth or pos. earth

£15.00 + s

Please state type required



BATTERY ELIMINATOR

Switched output 6, 7.5 or 9V at 250mA.
D.C. pos. or neg. earth
£3.15 + s



SEMI-CONDUCTOR DEVICES

RECTIFIERS


IN 4001 - 5p ea.)
IN 4002 - 6p ea.) + s
IN 4003 - 6p ea.)

1-0A bridge (400V) - 32p + H
1-6A " (200V) - 48p + H
1-6A " (800V) - 70p + H
2-0A " (200V) - 72p + H
2-0A " (600V) - 90p + H



MULLARD MODULES

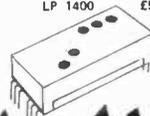LP 1173 - £6.10 + H
LP 1184/2 - £6.58 + H
LP 1185 - £4.50 + H
LP 1186 - £6.32 + H
LP 1400 - £5.15 + H



BIG PRICE REDUCTIONS

TRANSISTORS

BC 107 - 12p +
BC 108 - 11p +
BC 109 - 12p +
BFY 50 - 20p +
BFY 51 - 19p +
BFY 52 - 20p +
2N 3055 - 62p +
2N 2646 - 94p +
TIP 2955 £1.14 +
TIP 3055 - 61p +
BC 237B - 71p H
BC 238C - 10p H
BC 239C - 12p H
ZTX 107 - 10p H
ZTX 108 - 9p H
ZTX 109 - 12p H
ZTX 300 - 13p H
ZTX 500 - 14p H
MJE 340 - 62p H
TIP 31A - 36p H
TIP 32A - 40p H
2N 3819 - 27p H
3N 141 - 65p +
CS 715 - 18p H
10 for £1.50 H



I.C.'s

T05 Reg - £1.10 s
MVR 5 - £1.55 s
MVR 12 - £1.55 s
MVR 15 - £1.55 s
LM 309K - £1.95 s
7805 - £1.50 s
7812 - £1.50 s
7815 - £1.50 s
7824 - £1.50 s
±15V D.I.L. - £2.82 s
TBA 231 - £1.50 H
TBA 800 - £1.20 H
TBA 810S - £1.30 H
TBA 820 - £1.00 H
ZN 414 - £1.30 H
ZN 424 - £1.25 H
741 Op-amp - 36p s
747 Op-amp (Dual 741) - 95p s
748 Op-amp - 48p s
555 TIMER - 56p s
556 (dual 555) - £1.10 s
HA 1156 - £1.60 H (similar to MC1310P)
ORP12 - 72p s
8A Triac - £1.18 s
ZN 1034E - £4.70 s

'INTERNATIONAL 25'

Build yourself a **BIG SOUND amp** at a budget price



As featured in 'ETI' Oct. 75 edition

FEATURES

- * Triple Op-amp pre-amplifier
- * Power 'Darlington's'
- * Modern styling
- * 25W per channel into 8 ohms.

Complete kit with assembly instructions

Overseas orders £34.50
S.A.E. for full spec.


£29-95
+ £3.74 VAT

BOOKS (Z)

Hi-fi hints and tips
Towers international transistor selector
Electronic Components
PCB assembly
Electronic diagram

'SAMOS' CASES

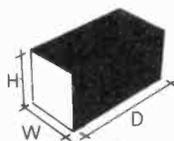Low-cost blue cover and white base PVC steel cases



S1 50W x 50H x 100D £1.03 + s
S2 100W x 50H x 100D £1.17 + s
S3 150W x 50H x 100D £1.31 + s
S4 50W x 75H x 125D £1.47 + s
S5 100W x 75H x 125D £1.68 + s
S6 150W x 75H x 125D £1.97 + s
S7 200W x 75H x 125D £2.19 + s


SPECIAL OFFER!!

If catalogue ordered simultaneously with order for SAMOS cases - case price less 25%

CONDITIONS OF SALE

All prices are ex-VAT
If affixed with s add 8%
If affixed with H add 12½%
Z - Zero rated
Package & posting free for orders over £3.00
Overseas orders add 15%
Cash with order. Cheques/Postal
Orders to Doram Electronics Limited.
P.O. Box TR8, Leeds, LS12 2UF
Small order handling charge of 40p for orders under £3.00

DORAM'S NEW CATALOGUE - THE AMATEURS GOOD COMPANION

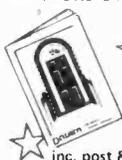

ONLY 60p

inc. post & packing.
Free up-date service until Aug. 1976.

DORAM "The Doorway to Amateur Electronics"


An Electrocomponents Group Company PE 6/76

NAME.....

ADDRESS.....

POST CODE.....

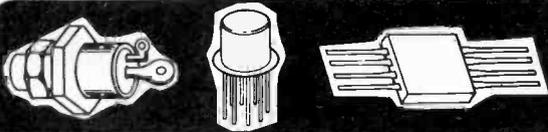I enclose 60p. Please send me by return my Doram Catalogue.
(Overseas orders except B.F.P.O. please add 30p for post and packing surface only).



Newnes Technical Books

Books of top quality written by popular experienced authors and designed for the beginner, student and those who just want to know more about their subject.

Here is a selection of Newnes Technical Books on electronics.

BEGINNER'S GUIDE TO TRANSISTORS—2nd Ed.
I.R. Sinclair & J.A. Reddihough 160 pages £2.25

BEGINNER'S GUIDE TO ELECTRONICS—3rd Ed.
T.L. Squires 240 pages £2.25

ELECTRONICS POCKET BOOK—3rd Ed.
P.J. McGoldrick 350 pages £3.75

50 PHOTOELECTRIC CIRCUITS & SYSTEMS
P.S. Smith 92 pages £1.80 limp £3.20 cased

FOUNDATIONS OF WIRELESS & ELECTRONICS
9th Edition
M.G. Scroggie 550 pages £3.75

GUIDE TO BROADCASTING STATIONS—17th Ed.
206 pages £1.20

QUESTIONS AND ANSWERS ON ELECTRONICS
Clement Brown 112 pages £1.15

QUESTIONS AND ANSWERS ON INTEGRATED CIRCUITS
R.G. Hibberd 95 pages £1.00

QUESTIONS AND ANSWERS ON TRANSISTORS
Clement Brown 96 pages £1.00

RADIO VALVE & SEMICONDUCTOR DATA
10th Edition
Compiled by A.M. Ball 180 pages £2.00

TELECOMMUNICATIONS POCKET BOOK
T.L. Squires 152 pages £2.50

TRANSISTOR POCKET BOOK
R.G. Hibberd 312 pages £3.90

COMING JULY...

New Constructors Guides:

SIMPLE CIRCUIT BUILDING and PROJECT PLANNING AND BUILDING both by M.A. Colwell

PRACTICAL ELECTRONIC PROJECT BUILDING
by Alan C. Ainslie and M.A. Colwell

FREE COLOUR BROCHURE

Write to the address below for your free copy of our full colour brochure that gives details of all the Newnes Technical Books

Please order from your bookseller

Newnes Technical Books
Borough Green, Sevenoaks, Kent

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44 page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest.
Post to address below.

- | | | | |
|---|--------------------------|--|--------------------------|
| ELECTRICAL & ELECTRONICS | | Air Registration Board Certs. | <input type="checkbox"/> |
| Practical Radio & Electronics (with kit) | <input type="checkbox"/> | MAA/IMI Dip. | <input type="checkbox"/> |
| Electronics (with kit) | <input type="checkbox"/> | CONSTRUCTIONAL | |
| Electronics Engineering Certificate | <input type="checkbox"/> | Heating Ventilating & Air Conditioning | <input type="checkbox"/> |
| General Elect. Eng. Certificate | <input type="checkbox"/> | Architectural Draughtsmanship & Design | <input type="checkbox"/> |
| C. & G. Elect. Installations | <input type="checkbox"/> | L.I.O.B. | <input type="checkbox"/> |
| Elect. Install. & Work | <input type="checkbox"/> | Carpentry & Joinery | <input type="checkbox"/> |
| C. & G. Elect. Technicians | <input type="checkbox"/> | Plumbing Technology | <input type="checkbox"/> |
| | | General Building | <input type="checkbox"/> |
| | | Painting & Decorating | <input type="checkbox"/> |
| RADIO & TELECOMMUNICATIONS | | MECHANICAL | |
| Colour TV Servicing | <input type="checkbox"/> | A.M.S.E. (Mech.) | <input type="checkbox"/> |
| C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> | General Mech. Eng. | <input type="checkbox"/> |
| C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> | Inst. Engineers & Technicians | <input type="checkbox"/> |
| Radio & TV Engineering Course | <input type="checkbox"/> | Maintenance Engineering | <input type="checkbox"/> |
| Radio, Servicing & Repairs | <input type="checkbox"/> | Welding | <input type="checkbox"/> |
| Radio Amateur's Exam | <input type="checkbox"/> | MANAGEMENT & PRODUCTION | |
| | | Computer Programming | <input type="checkbox"/> |
| AUTO & AERO | | Inst. of Cost & Managements Accts. | <input type="checkbox"/> |
| Motor Mechanics | <input type="checkbox"/> | DRAUGHTSMANSHIP & DESIGN | |
| C. & G. Motor V. Mechanics | <input type="checkbox"/> | General Draughtsmanship | <input type="checkbox"/> |
| General Auto Engineering | <input type="checkbox"/> | A.M.I.E.D. | <input type="checkbox"/> |
| A.M.I.M.I. | <input type="checkbox"/> | Electrical Draughtsmanship | <input type="checkbox"/> |

POST NOW

G.C.E.

—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPE 19, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals)


ADDRESS

Postcode

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

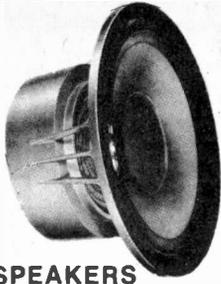HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm
 Baker Group 35, 3, 8 or 15 ohm
 Baker Group 50/12 8 or 15 ohm
 Baker Group 50/15 8 or 15 ohm
 Baker Deluxe 124, 8 or 15 ohm
 Baker Major 3, 8 or 15 ohm
 Baker Superb 8 or 15 ohm
 Baker Regent 12in 8 or 15 ohm
 Baker Auditorium 12in 8 or 15 ohm
 Baker Auditorium 15in 8 or 15 ohm
 Castle 8RS/DD 4 or 8 ohm
 Celestion G12M 8 or 15 ohm
 Celestion G12H 8 or 15 ohm
 Celestion G12/50 8 or 15 ohm
 Celestion G12/50TC 8 or 15 ohm
 Celestion G12/50 2236 s/cone
 Celestion G12/50 2239 s/cone, alum. dome
 Celestion G15C 8 or 15 ohm
 Celestion G18C 8 or 15 ohm
 Celestion HF1300 8 or 15 ohm
 Celestion HF2000 8 ohm
 Celestion MH1000 8 or 15 ohm
 Celestion C03K
 Decca London ribbon horn
 Decca London CO/1000/8 crossover
 Decca DK30 ribbon horn
 Decca CO/1/8 crossover (DK30)
 EMI 150 13 x 8in d/cone 8 ohm
 EMI 13 x 8in 20W bass 8 ohm
 EMI 14 x 9in bass 8 ohms, 14A770
 EMI 8 x 5in, 10W, d/cone, roll surr.
 EMI 6in d/cone, roll surr., 8 ohm
 EMI 8in roll surr. bass
 EMI 5in mid range
 Elac 59RM 105 (15 ohm), 59RM114 (8 ohm)
 Elac 6in d/cone, roll surr., 8 ohm
 Elac 10in 10RM239, 8 ohm
 Eagle FR4
 Eagle FR65
 Eagle FR8
 Eagle FR10
 Eagle HT15
 Eagle HT21
 Eagle MHT10
 Eagle FF28 Multicell, horn
 Fane Pop 15, 8 or 16 ohm
 Fane Pop 33T, 8 or 16 ohm
 Fane Pop 50, 8 or 16 ohm
 Fane Pop 55, 8 or 16 ohm
 Fane Pop 60, 8 or 16 ohm
 Fane Pop 70, 8 or 16 ohm
 Fane Pop 100, 8 or 16 ohm
 Fane Crescendo 12A, 8 or 16 ohm
 Fane Crescendo 12BL, 8 or 16 ohm
 Fane Crescendo 15/100A, 8 or 16 ohm
 Fane Crescendo 15/125, 8 or 16 ohm
 Fane Crescendo 18, 8 or 16 ohm
 Fane 910 Mk II horn

SPEAKERS

£8-64 Fane 920 Mk II horn
 £10-25 Fane HPX1 crossover 200W
 £14-00 Fane 13 x 8in, 15W dual cone
 £18-62 Fane 801T 8in d/c, roll surr.
 £12-38 Gauss 12in 200W
 £10-96 Gauss 15in 200W
 £16-31 Gauss 18in 200W
 £9-00 Goodmans Axent 100
 £14-65 Goodmans Audiom 200 8 ohm
 £19-41 Goodmans Axiom 402 8 or 15 ohm
 £9-28 Goodmans Twinaxiom 8, 8 or 15 ohm
 £12-95 Goodmans Twinaxiom 10, 8 or 15 ohm
 £15-95 Goodmans 8P 8 or 15 ohm
 £16-50 Goodmans 10P 8 or 15 ohm
 £18-00 Goodmans 12P 8 or 15 ohm
 £16-50 Goodmans 12PG 8 or 15 ohm
 £17-00 Goodmans 12PD 8 or 15 ohm
 £26-95 Goodmans 12AX 8 or 15 ohm
 £34-50 Goodmans 15AX 8 or 15 ohm
 £7-75 Goodmans 15P 8 or 15 ohm
 £9-50 Goodmans 18P 8 or 15 ohm
 £13-50 Goodmans Hifax 750P
 £4-46 Goodmans 5in midrange 8 ohm
 £28-80 Jordan Watts Module, 4, 8 or 15 ohm
 £6-75 Kef T27
 £17-25 Kef T15
 £4-50 Kef B110
 £2-94 Kef B200
 £9-00 Kef B139
 £11-92 Kef DN8
 £3-56 Kef DN12
 £3-93 Kef DN13 SP1015 or SP1017
 £5-73 Lowther PM6
 £3-50 Lowther PM6 Mk 1
 £3-38 Lowther PM7
 £3-83 Peerless KO10DT 4 or 8 ohm
 £1-57 Peerless DT10HFC 8 ohm
 £5-51 Peerless KO40MRF 8 ohm
 £8-66 Peerless MT225HCF 8 ohm
 £11-08 Richard Allan CA12 12in bass
 £14-06 Richard Allan HP8B
 £3-96 Richard Allan LP8B
 £8-13 Richard Allan DT20
 £4-00 Richard Allan CN8280
 £8-10 Richard Allan CN820
 £5-25 Richard Allan Super Disco 60W 12in
 £9-25 Richard Allen CG15 15in bass
 £12-50 Richard Allan Super Disco 12in 60 watt
 £15-50 Richard Allan Super Disco 10in 50 watt
 £17-95 Richard Allan Super Disco Bin 50 watt
 £18-75 Radford BD25
 £27-95 Radford MD9
 £37-95 Radford MD5
 £39-95 Radford TD3
 £49-95 Radford Cross Over Network
 £59-95 STC 4001G
 £67-95 Tannoy 10in HPD
 £15-75 Tannoy 12in HPD

Tannoy 15in HPD £88-15
 Wharfedale Super 10 RS/DD 8 ohm £13-50

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohm each £13-28
 Fane Mode One Mk II 15W each £10-35
 Goodmans DIN 20 4 or 8 ohm each £13-28
 Goodmans Mezzo Twin kit pair £42-47
 £7-60 Helme XLK 30 pair £17-10
 £13-46 Helme XLK 35 pair £21-60
 £19-80 Helme XLK 40 pair £31-50
 £9-86 Helme XLK 50 pair £50-40
 £5-95 Kefkit 1 pair £44-10
 £6-25 Kefkit III each £39-38
 £14-95 Peerless 20-2 each £15-70
 £16-50 Peerless 30-28 each £21-95
 £16-95 Peerless 20-3 each £23-90
 £39-00 Peerless 50-4 each £36-45
 £45-00 Peerless 1060 pair £50-40
 £22-50 Peerless 1070 each £41-40
 £39-00 Peerless 1120 each £45-00
 £16-00 Richard Allan Twin assembly each £13-46
 £4-05 Richard Allan Triple 8 each £20-25
 £15-38 Richard Allan Triple 12 each £25-16
 £5-18 Richard Allan Super Triple each £29-25
 £6-25 Richard Allan RA8 Kit pair £37-80
 £6-75 Richard Allan RA82 Kit pair £59-40
 £7-85 Richard Allan RA82L Kit pair £65-70
 £15-08 Wharfedale Linton II kit pair £20-81
 £2-08 Wharfedale Glendale 3XP kit pair £47-70
 £5-39 Wharfedale Dovedale III kit pair £59-40

HI-FI ON DEMONSTRATION in our showrooms:

Akal, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc.—ask for our Hi-Fi discount price list.

THIS MONTH'S SPECIALS!

Pioneer PL12D £43-00
 Pioneer PL15R £53-00
 Pioneer SX434 £98-95
 Rotel RX202 £80-00
 Videotone Minimax II £39-00

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

ALL PRICES INCLUDE VAT
(PRICES CORRECT AT 9.4.76)

Send stamp for free 32 page booklet "Choosing a Speaker"

ALL UNITS GUARANTEED NEW AND PERFECT
 Carriage and Insurance: Speakers 50p each (12in and up 75p each); Kits 80p each (£1-80 per pair); Tweeters and Crossovers 30p each.

WILMSLOW AUDIO

Dept PE

Loudspeakers, mail order and export:
 Swan Works, Bank Square, Wilmslow.
 Hi-Fi, Radio and TV: Swift of Wilmslow,
 5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi and Accessories: Wilmslow
 Audio, 10 Swan Street, Wilmslow,
 Cheshire.

Telephone: Loudspeakers, mail order and
 export—Wilmslow 295599; Hi-Fi, Radio,
 etc.—Wilmslow 26213.

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, Hi-Fi Answers Monitor (Rogers), Hi-Fi News No Compromise (Frisby), Wireless World Transmission Line (Bailey), Practical Hi-Fi and Audio Monitor (Giles), Practical Hi-Fi and Audio Triangle (Giles), Popular Hi-Fi (Colloms), etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi Answers Monitor, free on request.

P.A. amplifiers, microphones, etc., by Shure, Linear, Eagle, Beyer, AKG, etc.

FREE with orders over £10—"Hi-Fi Loudspeaker Enclosures" book.

from SAXON ENTERTAINMENTS LTD.

■ Absolutely complete

■ Transportable

■ Twin B.S.R. turntables

■ Sound-light sequencer

■ Condenser mic.

■ Monitoring headphones

■ X-fade and P.F.L.

■ Strong Vynide covered wood cabinets

■ Size 32in x 18in x 18in (81 x 46 x 46cm) closed

IT'S GOT LIGHT—IT'S GOT SOUND IT'S GOT POWER—IT'S GOT VALUE

Here's a winner from Saxon—a complete ready-for-instant-play stereo discotheque WITH ITS OWN BUILT-IN SOUND TO LIGHT CONVERTOR for under £200* delivered in U.K. It's got Saxon uncompromising quality standards. Saxon craftsmanship and Saxon's superb value-for-money to make the Centaur supreme in its class. Being transportable, with a 100 watts RMS sound output, and specially developed light system makes the assembly capable of use in the widest possible variety of applications.

* Plus V.A.T. at current rate

Compare the features—compare the price

MIXER

Low-noise silicon circuitry
Ample monitoring power
Left-right cross fade control
Full-range treble and bass controls
Additional inputs for tape and mic.
Well printed, easy to read facia to give everything at your finger tips.

AMPLIFIERS

Twin pure complementary symmetry integrated amplifiers giving a total output of 100 watts R.M.S. with superb quality.

LOUDSPEAKERS

Specially designed twin wood cabinets, with extra heavy duty full range matched drive units and connected cable control console.

LIGHTING CONTROL

FOUR CHANNEL sound-to-light converter with variable speed sequencing built in a scintillating four-colour display.

ACCESSORIES

Condenser microphone (cardioid) monitoring headphones and all leads.

IT'S STEREO

COMES TO READY PLAY AT


SYSTEM 7000

UNITS AND MODULES THAT LOOK BETTER, PERFORM BETTER AND ARE KINDER TO YOUR POCKET

SA 1208D

120 WATT RMS POWER AMP

USES 150W
16A RCA
DEVICES

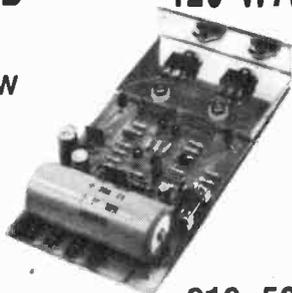

Send large
S.A.E. for leaflet

£19.50

- 10 Transistors 4 Diodes—Fibre Glass P.C.B.
- Typical Distortion—0.4%: Noise—minus 80dB
- Short, Open Circuit proof—Load line limiting
- Only FOUR Connections—Simplicity!
- High sensitivity (240mV) suits most mixers
- 30H—40kHz ± 1db Frequency response
- Single supply line—No output capacitor needed (95V)
- Standard 8Ω output—will operate on other impedances
- Compact—6" x 3" x 1½" (15 x 8 x 4cm)
- All units individually tested and guaranteed

In the same series
SA608

with the same features as SA 1208D but 60W RMS into 8Ω (65V)

£12.50

SA308

with same features as SA 1208D but 30W RMS into 8Ω (48V)

£9.50

SYSTEM 700 MODULAR MIXING

■ UP TO 20 CHANNELS MONO, STEREO OR MIXED

- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- Only one mixing module required
- 1W monitor power outlet
- Feeds most amplifiers
- Modern low noise circuitry
- 20Hz-30kHz ± 1dB
- Echo send/return facility
- Complete—ready to plug in or solder
- 5cm matrix—bold panel
- Individual monitor buttons
- Send for details

IN PCB MODULAR FORM

With same facilities and performance as complete units. On glass-fibre PCBs Soldered or edge connections.

IM7001/M
mono Input £5.50

IM7001/S
stereo input £9.00

IM7002/M
mono mixing £5.50

IM7002/S
stereo mixing £9.00

INPUT

Mono £8.50

Stereo £12.00

MIXER

Mono £8.50

Stereo £12.00

Power supply

P10M18 £7.50



POWER SUPPLY UNITS FOR SYSTEM 700 AMPS

on glass-fibre P.C.B., high grade transformer, fully fused and ready to wire.

PM1201 FOR ONE SA1208D £11.60

PM1202 for two SA1208D £15.30

PM601/2 for one or two SA608 £10.50

PM301/2 for one or two SA308 £8.80


SAXON ENTERTAINMENTS LTD

the fantastic 100 watt r.m.s.

Centaur

mobile stereo disco
complete with built-in
sound-light converter

YOU
TO
ONCE

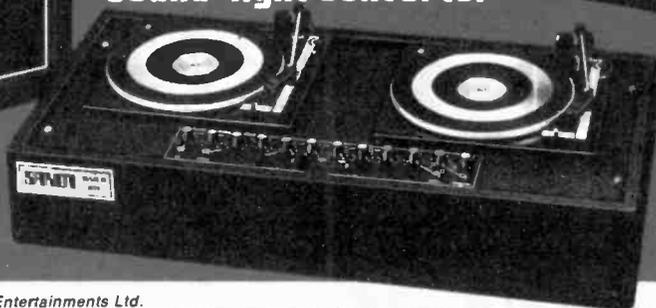

£199

CARR. PAID U.K.
+ VAT

Designed and made in the UK by Saxon Entertainments Ltd.

SYSTEM 7000 DISCO CONTROL UNIT



- Complete and ready to plug in
- Totally encased—no soldering at all
- Tough, bold, two tone stainless panel—for panel mounting or freestanding
- Inputs for 2 ceramic cartridges/tape/microphone
- Individual deck controls AND left/right fader
- Low noise (-80dB) 20Hz-50kHz ± 1dB
- Suits all Saxon amplifiers and most other makes,
- ½ watt headphone monitor—five position switch with mute positions

■ CONTROLS—L. to R.: Mic Vol/Treble/Bass, Auto-fade depth, L/Deck Vol, R/Deck Volume, Tape Volume, Treble, Bass, Master, Monitor Volume, Monitor Selector-On-Off

Mono £34.50 Stereo £49.50


IN MODULAR FORM

Printed circuit sub-assembly version of disco control unit. All electronics included. Only plugs, socket and one switch required.

Mono £18.50 Stereo £27.50

Front panel for either version
£3.50

SYSTEM 7000 LIGHTING CONTROL UNIT

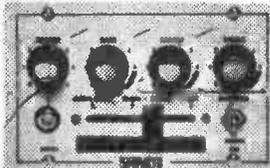

- Full control of 3kW of lights (1W/channel)
- Audio control plus sequence plus override
- Variable speed sequence with slider function control
- Stainless steel two tone panel—matches mixer
- 13 transistors & diodes—advanced control circuitry
- High audio sensitivity—operates from any amplifier
- Attractive Bondene case—free standing or panel mounting
- Individual tone controls plus master audio control

SUPERFECT MODULE

On P.C.B. Requires only plug/socket/panel for mounting as desired £27.00

£38.00 inc. case and plug—ready to use

SOUNDLITE 3kW Converter Module

O/P up to 1kW/ channel. Individual tone and master controls. RCA 8A Triacs. Scintillating Light Display. Operates from any amplifier. Glass-fibre PCB. Unbeatable value at

£15.50

HOW TO ORDER

When ordering by post, make cheques or crossed P.O.s payable to Saxon Entertainments Ltd. Prices include carriage and packing. You may send or phone your

- ACCESS OR
- BARCLAYCARD

number if you wish. After 4 pm leave your message on our Answer-phone (01-684 6385)

TERMS OF BUSINESS

Cash with order. If C.O.D. add 65p. S.A.E. with all enquiries. Prices and specs. subject to alteration without notice

V.A.T. must be added to total value of order at 8%

GUARANTEE

Purchases are guaranteed for twelve months from date of purchase subject to them being used as published instructions.

TRADE ENQUIRIES TO NORMAN ROSE ELECTRICAL LTD.

London: 01-837 9111
Birmingham: 021-236 4710
Manchester: 061-273 1498
Bradford: 0274 26104

SAXON STROBES



SUPERSTROBE

- 1 flash/2 sec up to 20 flashes/sec
- Compact black Bondene case
- Ideal for the mobile disco or smaller club

£24.75

PRO-STROBE

- Giant 80 watt tube. Discharge energy up to 6 Joules
- External trigger—audio up to 240V
- Use with Soundlite for rainbow strobe effect
- Smart, tough Bondene case 8in x 8in x 5in approx.

£38.50

150 WATT LIQUID WHEEL PROJECTOR



- Complete with wheel
- 150 watt tungsten lamp
- Wide range of extra effects may be attached
- Sturdy construction
- Adjustable feet
- Spare wheels £4.90

£29.20

LOUDSPEAKERS

12"/50W high grade chassis units. 14000 gauss; presence dome: £14.50

CABINETS

Attractive range of speaker and other cabinets at our showrooms. Enquiries welcomed

327-333 WHITEHORSE RD. CROYDON CRO 2HS

Telephone 01-684 0098/6385

Shop Hours 9am-5pm (Lunch 12.30-1.30); Sat. 9.30am-5pm ● Mail Order desk 10am-4pm Mon-Fri

VAT NO. 218 6921 49 RGD ENGLAND 1091983

It's here!

The Minisonic Mk. 2 has arrived—available NOW for the first time in kit form, the Minisonic 2 probably represents the best value for money in electronic music today.

Kits are available for complete instruments or individual sections, or for the conversion of Mk. 1 Minisonics to Mk. 2 specification. (Conversion details apply to Eaton Audio P.C.B.s, but may be adapted to suit others.)

In order to ensure that the appearance of the complete instrument enhances its performance, a complete cabinet kit is available, incorporating a fully finished black enamelled, silk-screened front panel, with matching back and base, and solid Afromosa end-cheeks. This kit also includes all switches, knobs, sockets, screws and panel indicators. Suitable keyboards and contact assemblies are also in stock.



READY-MADE INSTRUMENTS AVAILABLE

SEPARATE KITS		CONVERSION KITS		SEPARATE ITEMS	
Cabinet Kit (inc. Keyboard, etc.) MS/2-1 & 2	192-54	Ring Modulator MS/2-9	3-75	P.C. Boards—Main PCB EA014	3-80
Keyboard Controller MS/2-3	8-67	Noise Generator MS/2-10	2-00	Power Supply EA015	1-80
Voltage Controlled Oscillator MS/2-4	16-96	Output Amplifiers MS/2-11	6-93	Dual Transistor MD8001	1-20
(Note—2 off MS/2-4 required)		Control Envelope Inverter MS/2-12	0-81	Operational Amplifier LM318N	2-00
Sync. Kit MS/2-4sync		Stabilised Power Supply MS/2-13	9-00	Field Effect Transistor 2N5459	0-48
Envelope Shaper/VCA MS/2-5	8-88			Multi-Turn Preset Pots 1K, 10K, 20K	0-96
(Note—2 off MS/2-5 required)					
H.F. Oscillator/Detector MS/2-6	1-94				
Hold Isolator MS/2-7	3-24				
Voltage Controlled Filter MS/2-8	7-54				

SOME SALE ITEMS STILL AVAILABLE. HURRY, WHILE STOCKS LAST		VERO CARDFRAME SYSTEM	
LINEARS	£	Case KMV1F	£
C3346	0-80	End Angles (PR) HWV1F	11-50
MC1306P	0-53	Bin Module KBV1F	0-55
MFC4000B	0-45	4in Module K4V1F	2-40
ZN424E	1-00	2in Panel F2V1F	0-85
741	0-22	1in Panel F1V1F	0-50
741 SCP	1-10	Plug 19124/SS31	0-80
PANELS & PCBs	£	Socket 19125/SF31	0-70
PE Minisonic EA008	2-50	Card Handles (10 off)	0-60
		Veroboard Panel E100	0-75
		Module M28/19012	0-70

EATON AUDIO

DEPT. PE, P.O. BOX 3
ST NEOTS, CAMBS
PE19 3JB

TERMS: MAIL ORDER ONLY C.W.O. MINIMUM ORDER £1 VAT. Please add 25% to value of order inc P & P unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P & P otherwise please add 10p in the £1.

London College of Furniture

Electronics for Musical Instrument Technology

A full-time three year course is offered in those aspects of electronics related to the design, building and repair of all types of equipment associated with music. Students will be encouraged to involve themselves in project work in the fields of acoustics, group amplification, electronic organs, synthesizer design, etc. Prospective students should have some knowledge of electronics or some basic science and mathematics at 'O' level GCE or the equivalent.



For details apply to: Dept. of M.I.T., London College of Furniture, 41-71 Commercial Road, London E1 1LA. Telephone: 01-247 1953.

orchard electronics

A FEW TRANSISTORS FROM OUR LIST				
AC125 80p	AS167 70p	BC147A 90p	BC205A 15p*	BC300B 18p*
AC126 80p	BA14n 15p*	BC147B 10p*	BC206A 15p*	BC317A 15p*
AC127 80p	BA154 10p	BC148 9p*	BC207A 11p*	BC319B 15p*
AC128 80p	BA155 12p	BC148B 10p*	BC208A 11p*	BC322B 15p*
AC132 85p	BAX12 10p	BC149B 11p*	BC209B 13p*	BC327 20p*
AC141 20p	BAX13 4p	BC149C 11p*	BC212A 13p*	BC328 18p*
AC142 17p	BAX16 6p	BC153 18p*	BC212L 15p*	BC337 18p*
AC161 24p	BC107 11p	BC154 18p*	BC213B 12p*	BC338 16p*
AC153 27p	BC107A 12p	BC157B 12p*	BC213L 14p*	BC461 35p
AC176 20p	BC108 10p	BC158A 12p*	BC214 15p*	BC557 9p
AC188 20p	BC108B 11p	BC159A 12p*	BC214L 17p*	BC558 9p
AD161 42p	BC109 11p	BC167A 11p*	BC237A 16p*	BC559 9p
AD162 42p	BC109B 12p	BC168B 14p*	BC238A 15p*	BCV70 15p
AF114 24p	BC109C 13p	BC171A 14p*	BC239B 15p*	BCV71 18p
AF115 24p	BC115 15p*	BC172A 15p*	BC261A 16p	BCV72 14p
AF116 24p	BC116 15p*	BC173B 16p*	BC262A 15p	BD115 60p
AF117 24p	BC117 18p*	BC177 17p*	BC266A 18p	BD121 90p
AF118 47p	BC118 10p*	BC178B 18p	BC267A 14p	BD123 90p
AF124 80p	BC119 28p	BC179B 19p	BC268B 13p	BD124 68p
AF125 30p	BC125 14p*	BC182B 10p*	BC269 13p	BD131 38p
AF126 28p	BC132 11p*	BC182L 11p*	BC287 20p	BD132 38p
AF139 34p	BC135 12p*	BC183B 10p*	BC300 27p	BD133 68p
AF186 80p	BC136 16p*	BC183L 10p*	BC302A 28p	BD135 37p*
AP239 37p	BC137 16p*	BC184B 12p*	BC302 24p	BD136 38p*
ASB26 30p	BC138 15p	BC184L 11p*	BC303 30p	BD137 44p*
ASB27 34p	BC139 35p	BC186 25p	BC304 27p	BD138 47p*
ASB28 80p	BC142 22p	BC187 28p	BC307A 16p*	BD139 54p*
ASB29 34p	BC143 24p	BC204A 16p*	BC308A 14p*	BD155 76p*


SILICON/REC	RESISTORS	ICs TTL/DIG.	S.A.E. for full list of components.
60V 3A 13p	1½ watt E12 range	7400 18p	Same day despatch to Mail Order Customers. Min. order £1. P. & P. 25p. Callers Mon.-Sat. incl.
100V 3A 15p	1Ω—10MΩ	7401 20p	
200V 3A 18p		7402 18p	
		7403 18p	
		7404 23p	
		7405 23p	
		7406 40p	
		Plus C/MOS.	

ICs LINEAR	ZENERS (400mW)	VOLTAGE REG. (TO8)	LED
709 (8 pin Dill) 40p*	BZX83/BZY88	REG. (TO8)	125 Red 20p { Like TIL 209
741 (8 pin Dill) 33p*	3V3, 3V6, 3V9,	1A, 5V, 12V,	125 Grn 27p { 0.125in.
NE555 80p*	4V3, 4V7, 5V3,	15V, £1.35	TIL 200 Red 25p
NE566 180p*	5V8, 6V2, 6V5,	1A, 5V, 12V,	TIL 200 Grn 28p
NE567 270p*	7V5, 8V2, 9V1,	15V, £1.75	TIL 200 Grn 28p
SN76013N 157p*	10V, 12V, 13V,		
TAA550 86p*	15V, 18V, 30V,		
TBA800 135p*	All at 12p each*		

VAT—Items marked * add 12½%, remainder at 8%.
Flint House, High Street, Wallingford, Oxon OX10 0DE
Tel.: Wallingford (0491) 35529 Telex 45PWALFRD 849349

ELECTROTIME

ELECTRONIC DIGITAL ALARM CLOCK MODEL EC3

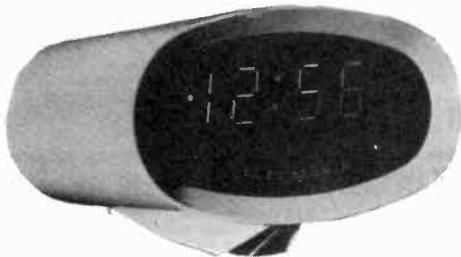

- ★ LARGE 4 DIGIT DISPLAY ★ 24 HOUR ALARM ★ A.M./P.M. INDICATOR
- ★ BRIGHTNESS CONTROL ★ FLASHING SECONDS INDICATOR
- ★ ATTRACTIVE WHITE CASE ★ 5 MINUTE REPEATING SNOOZE ALARM

Complete Built Clock

£14 inc. VAT

THE "MISTRAL" 1 DIGITAL CLOCK



- ★ PLEASANT GREEN DISPLAY ★ PULSATING COLON ★ 12/24 HOUR READOUT
- ★ PUSH BUTTON SETTING ★ FULLY ELECTRONIC ★ BUILDING TIME 1 HOUR

Complete Kit

£11.07 inc. VAT

Built Clock

£14.95 inc. VAT

LCD MODEL TLC4

Continuous Readout utilising Liquid Crystal Display with Backlight for night reading

Features:

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE



Rhodium Gold

£39.95 inc. VAT
£41.50 inc. VAT

LED MODEL TLE5



Features:

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE
- ★ DAY OF WEEK

£29.50 inc. VAT


Gold or Rhodium plated

LED MODEL TLE3

Features:

- ★ HOURS
- ★ MINUTES
- ★ SECONDS

£19.95 inc. VAT

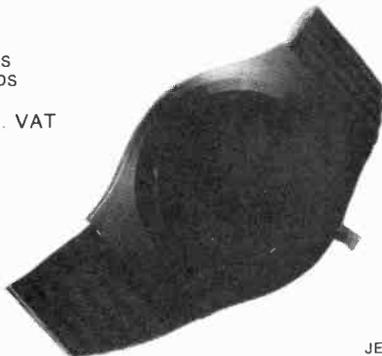

JET BLACK
STAINLESS STEEL
CASE AND BRACELET

COME TO THE EXPERTS IN DIGITAL TIMEKEEPING



MONEY REFUNDED IF NOT COMPLETELY SATISFIED. ONE YEAR GUARANTEE WITH ALL MODELS

**ELECTROTIME, Dept. 2/6, 111 Storforth Lane Trading Estate
Chesterfield, Derbyshire. Tel. (0246) 35804**

Please supply
I enclose cheque/postal order

NAME

ADDRESS


.....

.....

RTVC

ELIZABETHAN STEREO TUNER AMPLIFIER

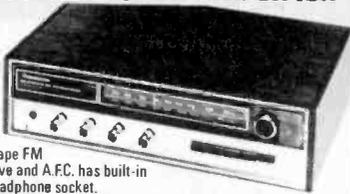
This compact Tuner Amplifier gives you full medium wave and V.H.F. coverage and FM stereo. With inputs for your turntable and tape recorder. It has rotary tuning, Volume, Balance, Bass and Treble controls and push button selection switches for Phono/tape FM Stereo, FM mono, Medium wave and A.F.C. has built-in stereo beacon and switched headphone socket.



Technical Specifications 15 transistors, 11 diodes, integrated circuit. Power output 8 watts. Size of tuner amplifier: 4" x 10" x 15 1/2" approx. Finished in selected rosewood veneer with brushed aluminium front panel and matching controls. Output into 15 ohms speakers only. **£29.00** + p&p £1.50

*STEREO 21

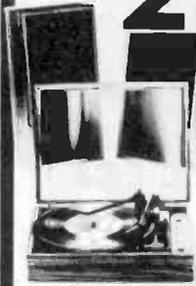INCORPORATING A GARRARD DECK
Garrard 3 speed Deck automatic, manual facilities together with stereo cartridge and cueing device.



Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in Sim Teak and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes - 3 speed deck, automatic manual facilities together with stereo cartridge and cueing device.

Two speakers with cabinets.
Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications - For the technically minded.
Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker output. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs.

Overall Dimensions. Speakers approx 12" x 9" x 5". Complete deck and cover in closed position approx 15 1/2" x 12" x 6".

Extras if required. Optional Diamond Stylus £1.60.
Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80.**

COMPLETE ONLY
£23.20 + p&p £4.00

BSR DECKS WITH PLINTHS AT FANTASTIC REDUCTIONS



MP 60 Type (illustrated) £16.00
Less Cartridge p&p £2.00
C141 (not illustrated) £12.00
Auto. with Cue p&p £1.50
Fitted Stereo Cartridge
All plinths finished in matching Teak veneer.


EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3" tweeter and matching crossover.

Easily put together with just a few basic tools.
Specification (each speaker); Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£22.00 pair complete
+ £5.20 p&p

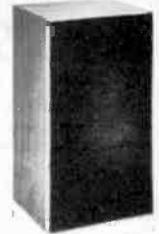Complete with crossover Components and circuit diagram.



THE 'COMPACT' EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitted and professionally finished, and fix together with masking tape till glue dries.

The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 2 1/2" magnet size 2 1/2" approx. **£6.00** + p&p £1.70
PAIR INCLUSIVE



EMI 350 KIT

£7.25 + £1.20 p & p.

Complete with crossover Components and circuit diagram

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)



VISCOUNT IV STEREO AMP

NOW AVAILABLE IN KIT FORM! **30x30**
WATTS RMS

COMPLETE 20x20 SYSTEMS

SYSTEM 1A £69.00

The new 20 + 20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance mono/stereo, mode selector, and scratch filter.
Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion at 10 watts better than 0.2%. Six switched inputs: 1. Magnetic PU - 3 millivolts at 47 K ohms (R.I.A.A.); 2. Crystal/ceramic PU - 50 millivolts at 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. - 140 millivolts at 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts at 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket, Aux. mains output. Frequency response: 25 Hz to 25 kHz at full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB at 50 Hz; Treble ±12 dB at 10 KHz. Power requirements: 250V A.C. mains at 60 watts.

Approx size: 15 1/2" x 3" x 10". MP60 type deck with magnetic cartridge, de luxe plinth and cover. Two Duo Type 11a matched speakers - Enclosure size approx. 19 1/2" x 10 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling. 30 watts peak.

SYSTEM 2 £85.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type 11a matched speakers - Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS. 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these speakers **£85.00** + £7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV R103 amplifier £27.50 + £1.90 p & p.

2 Duo Type 11a speakers £30.00 + £6.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 - £3.30 p & p.

Total if purchased separately: £79.50

Available complete for only: **£69.00**

+ £6.50 p & p.

PRICES: SYSTEM 2

Viscount IV R103 amplifier £27.50 + £1.90 p & p.

2 Duo Type 11a speakers £46.00 + £7.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.

Total if purchased separately: £95.50

Available complete for only: **£85.00**

+ £7.60 p & p.



20x20 SYSTEM

Complete System with these speakers **£69.00** + £6.50 p&p.

Scotland and the Orkneys P & P Surcharge System 1a £1.75 System 2 £3.50

Note. 30x30 kit available only as a separate item.

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



*If you can solder correctly on a Printed circuit board, you can build this kit correctly.

NOW YOU CAN BUILD YOUR OWN PUSH-BUTTON CAR RADIO!

This construction kit comprises of a fully built and aligned R.F. I.F. module; Printed circuit board, with ready mounted integrated circuit output stage and all other components. The push button tuning mechanism is full built and tested ready to mate with the printed circuit board (once it is assembled). Note: No test equipment is required for alignment, but remember you must have the ability to solder on a printed circuit board. **TECHNICAL SPECIFICATION:** (1) Output 4W RMS output. For 12V operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF

Module. Controls volume—manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size: chassis 7in wide, 2in high and 4 1/2in deep approx. Speaker including baffle and fixing strip £2 + 45p P. & P. Car Aerial Recommended—fully retractable £1.60 + 40p P. & P.

Price **£8.20** P. & P. £1.05

SPECIAL OFFER

The Tourist 1 Kit. Complete with speakers, fixing kit and fully retractable aerial.

£10.50 P. & P. £1.50

STEREO CASSETTE TAPE DECK KIT*

Kit comprises of ready built cassette tape transport mechanism. Featuring pause control, solenoid assisted auto-stop, 3 digit tape counter, belt-driven balanced fly wheel, DC motor with electronic speed control, ready built and mounted record/replay PC board, and two VU meters, power supply, PC board, mains transformer. Input and output sockets and two level controls. Specification power source 240 AC 50Hz. Output more than 0.5v input mike — 65dB 10KΩ. DIN — 47dB 100KΩ. Track system 2 channel stereo record play-back. Tape speed: 4.8CM/SEC. Frequency response 50-12,000Hz signal to noise ratio — 42dB. Recording system AC Bias. Erasing system AC erase. Bias frequency 57KHz. Size of mechanism 8" x 5" x 3 1/2" approx. unit easy to mount into your cabinet. 3" required to clear base of mechanism approx.

This is an advanced kit not suitable for those without electrical knowledge and those unable to solder

£32.50
+ p & p £1.50
or send SAE for complete details.



*DISCO AMPLIFIER



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms). Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling. **INPUT SENSITIVITIES** — Input — 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2"

£20.00 + £1.35 p & p.

8 TRACK HOME CARTRIDGE PLAYER



Yours for only

£14.00 + £1.70 p & p.

Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV.

SPECIAL OFFER

As above but complete with build yourself Unisound Amplifier Kit (see opposite panel) + 2 'Compact' easy to build speaker kits (see opposite page) **£25.00** + p & p £2.00

BUILD YOUR OWN STEREO AMPLIFIER*



For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7"x4") **£10** + £1.75 p & p. **£8.95** £1.05 p & p. Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50** + £2 p & p

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

PORTABLE DISCO CONSOLE*



TECHNICAL SPECIFICATION:
Pre-amp — Output — 200mV.
Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation.
Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than — 35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaugmont kalee meter).
Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —
Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only **£49.00** + £6.50 p & p.

All prices include VAT at current rates



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.D. All enquiries stamped addressed envelope. Goods not despatched outside U.K.


Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st April 1976 and subject to change without notice

Minimum order on ACCESS/BARCLAYCARD — £11.





21D HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

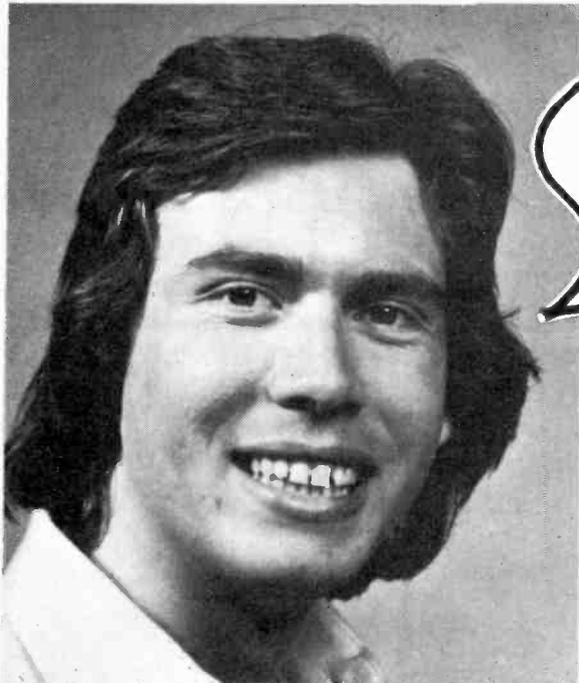Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.



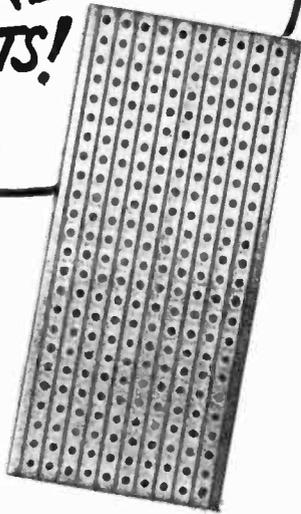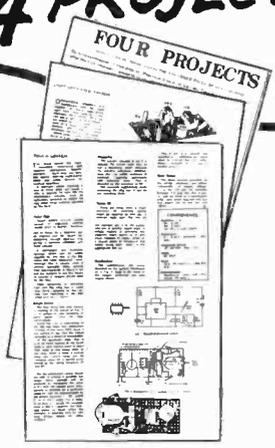FREE! A PIECE OF VERO BOARD....PLUS 4 PROJECTS!



As you know, I'm fairly well in with the Managing Director of Home Radio Components Ltd. He was deep in thought when I called on him the other day. "Cooking up something new?" I said. "Yes," he replied, "I'm thinking of giving a piece of Vero Board to everybody who buys one of our catalogues, but I'm wondering if the idea is a bit gimmicky." "Certainly not," I assured him, "several electronic magazines have done it before and I'm sure lots of customers appreciate it." Encouraged, he went on, "I thought that if I offered four projects for which the board could be used it would make it even more useful and interesting." That set the ball rolling, and with the co-operation of Vero Electronics Ltd. and of Mr. Fred Bennett, Editor of "Practical Electronics" he is now able to make this unique offer . . . to every purchaser of a

Home Radio Components Catalogue will be sent a piece of Vero Board and four projects for using it. The offer lasts for one month from the publication date of this journal. If you have not already got a current Home Radio Components Catalogue here is a wonderful opportunity to correct the omission (no constructor should be without one) and at the same time to win a useful piece of material and four interesting projects—A Touch Switch, a Thermometer, a Waa Waa Unit and a Light Operated Switch. The catalogue costs only 99p (including 34p for packing and postage) and it includes vouchers to the value of 30p if used as directed. This is too good to miss—send the coupon below with your cheque or P.O. for 99 pence. Why delay? Do it today!

Today's finest Components Catalogue
65p plus 34p POST & PACKING

The price of 99p applies only to customers in the U.K. and to BFPO Addresses.



Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. PE
 234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No. 912966, London



POST THIS COUPON
 with cheque
 or p.o. for
99p

HOME RADIO (Components) LTD Dept. PE · 234 · 240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

RIISING TO THE CHALLENGE

A FAIRLY tough task faced entrants for the *How Inventive Are You?* competition, the results of which appear this month. The starting point was a circuit developed for use in a gas ignitor. Not perhaps the most exciting of topics or the most versatile of circuits to provide the trigger to the thought processes. But any such beliefs were soon dispelled when the astonishing range of ideas sent in was examined. Clearly the opportunity to pit one's wits against a simple circuit in order to extract further usefulness from it was irresistible to a great number of our readers.

Recognising the limitations presented by the selected circuit, the ideas submitted were all the more laudable. Clearly much midnight oil was burnt in many instances. Some of the proposed applications were refreshingly new and not a little surprising. All in all they caused light to be cast upon many unsuspected or neglected regions. The results were both revealing and encouraging to our industrial co-sponsor no less than to ourselves.

An exercise such as this inevitably prompts the question—how much untapped inventive wealth lies within the minds of people who would not ordinarily consider themselves to be designers, inventors, or what have you? Our competition has revealed but the tip of the iceberg, that is our confident guess.

The sad fact is that the importance of harnessing or channelling the inventive powers of private persons is hardly recognised nationally. And now we are thinking in broad terms, not merely within the confines of the electronic territory. Maybe it will be claimed that anything akin to officialdom and organisation is the antithesis of the inventive spirit. And yet we know this is not true: war time innovations give the lie to such belief.

The talents are there, unrecognised and mostly unsuspected even by the individual owners, until the challenge comes. This much has been proved, on a modest scale at anyrate, by the outcome of the Plessey/Practical Electronics *How Inventive Are You?* competition.

A WELCOME CUT

The halving of the 25 per cent rate of V.A.T. in the April Budget is warmly welcomed. Electronic components that come under the higher rate of V.A.T. will now be rated at 12½ per cent, like consumer goods such as electrical appliances and home entertainment equipment.

In view of this easing of the constructors' burden it may seem ungrateful to carp at the Chancellor's proposals. But the continuance of a two-level tax system with the arbitrary division of goods into luxury and non-luxury categories is to be regretted. The administrative and accountancy problems it creates when dealing with orders for miscellaneous components and kits of parts are only too well known by component suppliers. The Chancellor should keep in mind the overall advantages of one rate of V.A.T., as the trade has strongly recommended.

F.E.B.

Editor
F. E. BENNETT

Editorial
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
R. W. LAWRENCE, B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Editorial Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: 01-634 4452

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-261 5148

P. J. MEW
Phone: 01-261 5190

C. R. BROWN *Classified*
Phone: 01-261 5000

Advertising Offices:
King's Reach Tower, Stamford St.
London SE1 9LS
Phone: 01-261 5000

THIS Digital Milometer was designed specifically for use on car rallies or applications where accurate map reading and navigation from a car are essential. The basic requirements for such a unit are summarised below:

(a) Compactness: The design must be capable of fitting into an already overcrowded dashboard without hindrance to other equipment.

(b) Accuracy: The design should be capable of reliably measuring at least to the accuracy that a map can be read.

(c) Visibility: The display should be easily visible, during day and night, by both driver and navigator.

(d) Robustness: The milometer must be capable of withstanding vibration and shock associated with the rough handling experienced on a car rally.


(e) Cost: The cost should be kept to a minimum.

CHOICE OF TECHNOLOGY

To avoid interface problems, it was decided that the counting and display driving should use a single type of technology, which would preferably drive the display directly and use a single supply voltage.

The voltage supply should be reliable even when the car is starting up, and should be derived from the 12V car battery. The technologies considered were TTL, CMOS, and a MOS counter and display chip.

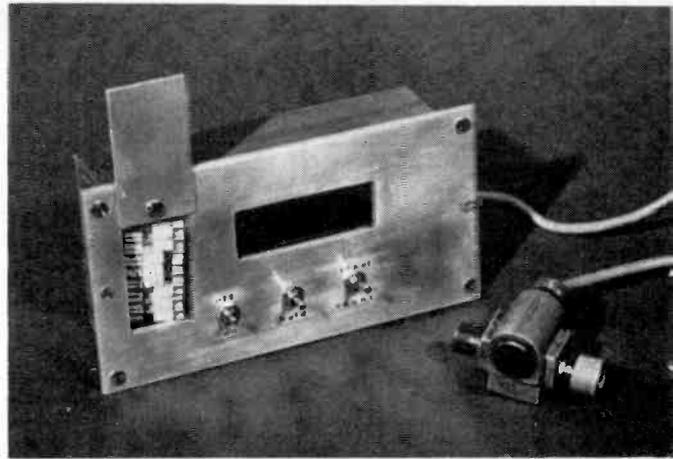The MOS counter and display chip was rejected initially because of its cost but also because the high supply voltages could not be derived directly from the 12V car battery. Further, the displays best suited to this type of integrated circuit are high voltage low current types which introduce similar voltage supply problems.



The completed unit showing the pulse sender unit and the cutouts for the displays and switches S2, 3a-d

Complementary MOS (CMOS) technology was also rejected because of the difficulties of directly driving the display and the higher component cost as compared with TTL. The advantages of low power consumption and high noise immunity do not outweigh the disadvantages, since the car battery is easily capable of supplying high currents and the noise immunity of TTL is adequate for the environment of a car.

Consequently, normal TTL was chosen for counting and display driving, mainly because of its low cost and easy availability. Also the regulated 5V supply



MILOMETER

By P. LEAH

voltage could readily be derived from the car battery and the 7447 seven-segment display drivers could drive directly a Minitron display from the 5V regulated supply.

Minitrons were preferred to an l.e.d. display only because of their lower cost.

ACCURACY

The accuracy of the milometer is dependent on the method of taking the basic measurement. In a car two possibilities are open:

- (1) Measure the revolutions of the wheel.
- (2) Measure the revolutions of the speedometer cable.

The wheel on a Mini is approximately two yards in circumference. If wheel revolutions are counted to measure a distance of one tenth of a mile the accuracy is within $2 \div 176 = 1.1$ per cent. If the milometer is required to measure to one tenth of a kilometer the accuracy is reduced to 1.8 per cent which is less than the accuracy with which an Ordnance Survey metric map may be read.

Further, the pick up from the wheel would need to be particularly resistant to shock since it would not have the protection afforded by the shock absorbers and the car suspension which the chassis and engine enjoy.

Measurement from the speedometer cable has the advantages of shock protection and greater accuracy. The speedometer cable rotates approximately 144 times per tenth of a mile in a Mini giving an accuracy of 0.7 per cent. This reduces to 1.1 per cent when measuring tenths of a kilometer.

It was thought necessary to only measure to one tenth of a mile as this is equivalent to the distance which an O.S. map can be measured. Measuring to one hundredth of a mile would only be accurate to seven per cent without introducing a pulse multiplier, and even then the accuracy would not be improved when measuring to one tenth of a mile.

ELECTRONIC REV COUNTER

The method of converting revolutions of the speedometer cable to pulses again offers a number of alternatives.

The speedometer relies on the rotation of a permanent magnet for its operation; the higher the speed of the car, the faster the rotation of the magnet. However, speedometers in most cars are sealed units and this magnet is difficult to utilise. The magnetic field is too weak to operate a reed relay and a magnetic coupler was rejected owing to the difficulty in accurately positioning the coil and the inaccuracy of the method at low speeds when the change on the magnetic flux would be too slow to pick up.

The method used employed a magnet fixed to the cable whose rotation was sensed by a Hall effect integrated circuit. Fig. 1b shows how the device is mounted.

The pick up unit consists of a Halda T-piece, which is attached to the back of the speedometer, and a Sprague Hall effect chip type ULN-3000M. Halda manufacture an accurate mechanical milometer and produce T-pieces for every different type of speedometer.

The Hall effect chip is mounted inside the T-piece while a magnet is attached to the barrel of the T-piece. Once every revolution of the speedometer cable, the magnetic field is at a maximum with respect the chip which produces an output pulse.

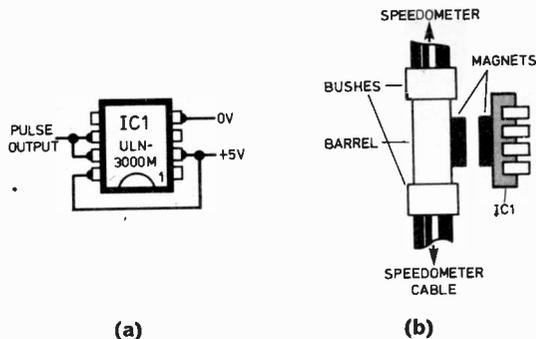


Fig. 1. Details of the pulse sender unit. (a) shows the pin connections to the ULN-3000M Hall-effect i.c. and (b) shows the method of mounting in the T-piece

The ULN-3000M is TTL compatible, the output pulses being fed directly to the counting unit. Three wires run from the pulse sending unit to the main box: one for the output pulses, one for 5V and one for 0V. Fig. 1a shows the connections to the i.c. which comes in an 8-pin dual-in-line package.

The i.c. is fixed into the T-piece using epoxy resin to obtain a rigid support. Two small magnets are necessary, one being attached to the barrel of the T-piece the other being fixed to the top of the i.c. to give magnetic bias to the Hall effect probe. Both magnets are attached using epoxy resin.

CIRCUIT OPERATION

The electronics in the main part of the milometer take the pulses from the Hall effect chip and when the number of pulses equivalent to one tenth of a mile have been received the display is incremented by one. The pulse counter then resets to zero and begins to count again. The milometer may thus be separated into three parts: the pulse sender; the pulse counter; and the display counter and display.

PULSE COUNTER

The pulse counter, Fig. 2, consists of two presettable up/down counters (IC2, IC3) in cascade. The required number of pulses to indicate one tenth of a mile is programmed into the unit using eight switches contained in two dual-in-line packages (S2, S3a-d).

The number (up to 256) is set on the switches which are accessible from the front panel for easy adjustment. The switches are "on" to give a logical 0 and off to give a logic 1, the $1k\Omega$ pull-up resistors (R4 to R11) acting to give the required voltage at the counter inputs.

Each time a pulse is received from the pulse sender the counters count down by one. After counting the programmed number of pulses the counters are at zero which produces a pulse to the display counters and also resets the counters to the number programmed on the switches.

The clock pulses from the pulse sender are fed to a two-input Schmitt gate (IC4a) which prevents the slow rise time of the received pulses causing false triggering of the counters. The other input to gate IC4a is counted to the HOLD switch S1. To inhibit counting the HOLD switch is closed which holds the output of gate IC4a at logic 1, thus preventing any clock pulses reaching the counters.

The capacitor across the switch (C1) prevents contact bounce on the reset switch (S4) which could cause false triggering.

Gates IC4b and IC4c perform the PRESET and RESET functions. A logic 0 at either input of gate IC4c will cause the output to go to logic 1 which causes the two counter i.c.s to be preset to the programmed number. When counting normally, both inputs to gate IC4c are at logic 1.

No capacitor is required to prevent contact bounce on the reset switch (S4) since the first pulse will preset the counters and any subsequent pulses will have no effect. Gate IC4b is simply connected as an inverter to produce the correct polarity PRESET pulse.

DISPLAY AND COUNTER

The counter for the display consists of three decade counters in cascade (IC8 to IC10). The binary coded decimal (b.c.d.) output from each counter is decoded by a b.c.d. to seven-segment display driver (IC5 to IC7) which drives the Minitrons directly, Fig. 3.

The maximum count is 99.9 miles but this can easily be extended to 999.9 miles by the addition of another counter/decoder/display stage but it was not thought necessary and did not warrant the extra space.

The RESET is common to all counters, operation of switch S4 causing them all to be set to zero.

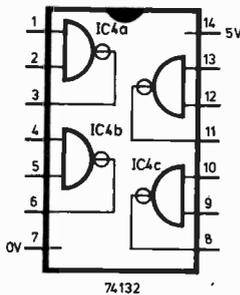


Fig. 2. Circuit diagram of the pulse counting section of the Digital Milometer. The internal configuration of IC4 is shown above. Wiring of the component boards should be ascertained from the Figs. 2, 3 and 4

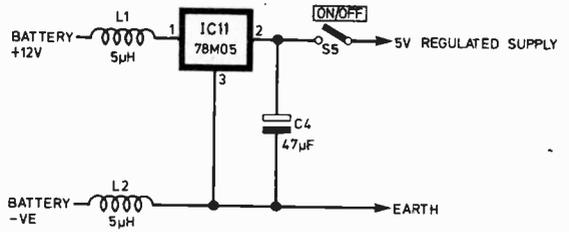
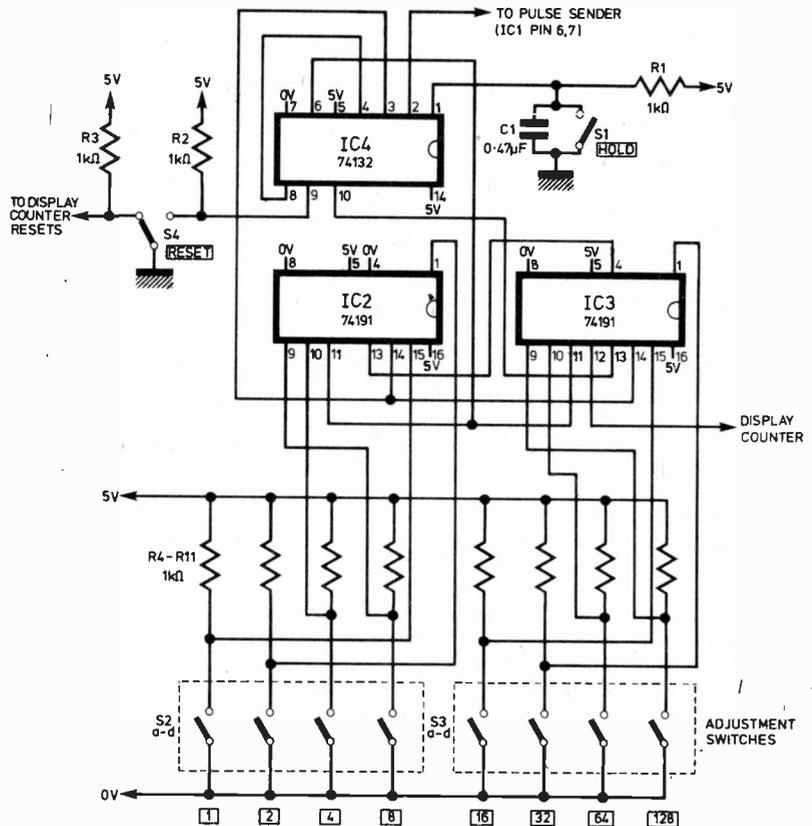


Fig. 4. Circuit diagram of the 5V regulator section. The chokes suppress transients in the leads

POWER SUPPLY

The 5V regulated power supply for the integrated circuits is derived from the car battery using a 5V 500mA regulator chip (IC11). The complete circuit is shown in Fig. 4.

The battery voltage may fluctuate between 9V and 15V which is within the input limits of the regulator.

The capacitor (C4) decouples the output and two 0.01μF capacitors on the logic board again decouple the supply. Two chokes (L1, L2) are inserted in the supply rails from the car battery to suppress any noise on the leads.

COMPONENTS . . .

Resistors

R1-R11 1kΩ ½W carbon (11 off)

Capacitors

C1 0.47μF polycarbonate
 C2, C3 0.01μF disc ceramic (2 off)
 C4 47μF 6.3V tantalum

Inductors

L1, L2 5μH chokes (2 off)

Integrated circuits

IC1 ULN-3000M (Sprague)
 IC2 SN74191N
 IC3 SN74191N
 IC4 SN74132N
 IC5-IC7 SN7447 (3 off)
 IC8-IC10 SN7490 (3 off)
 IC11 78M05 5V ½A regulator

Displays

LP1-LP3 Minitron 3015F (3 off)

Switches

S1 Sub miniature toggle
 S2, S3 4-pole 2-way dual-in-line switch (2 off)
 S4 Sub miniature toggle
 S5 Sub miniature toggle

Miscellaneous

0.1in matrix Veroboard 114 × 66mm.
 d.i.l. printed circuit board 114 × 66mm.
 Aluminium box 133 × 70 × 38mm.
 Perspex 65 × 40mm, 1.5mm aluminium 153 × 83mm.
 Three way terminal block. Halda T-piece (Halda Ltd., Taximeters, 4 Brandon Rd., London N7).
 Two small magnets.


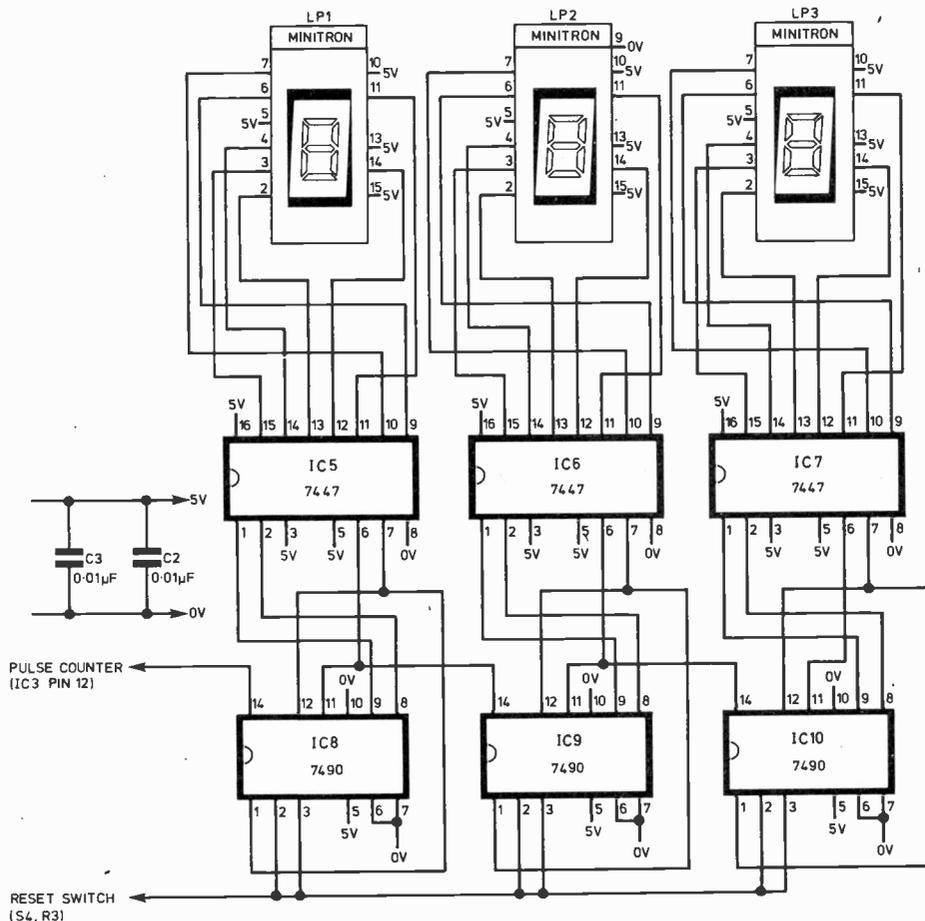


Fig. 3. Circuit diagram of the display counter, decoder and display section of the Milimeter

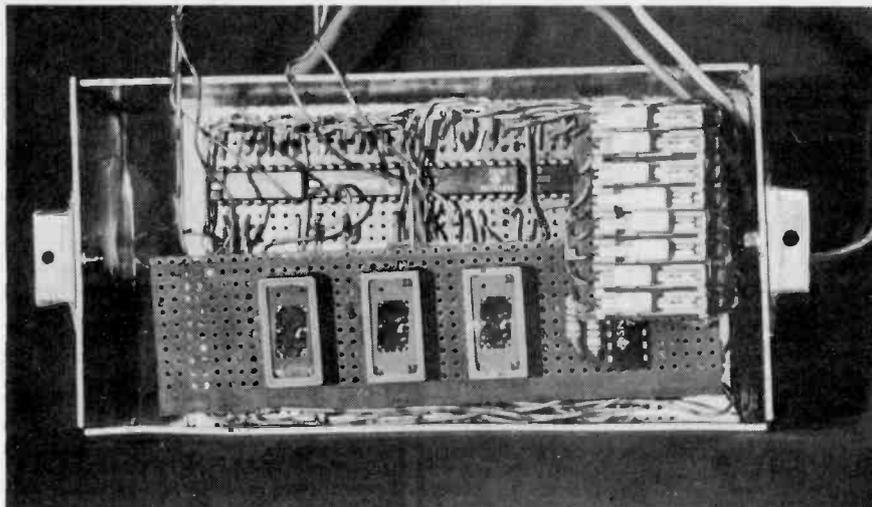

Interior view of the Milometer showing the dual-in-line switches and general layout of display board

CONSTRUCTION

The components for the Digital Milometer were mounted on two boards which fit on top of one another in a small aluminium box. All the counters and display drivers were mounted on the lower board (Fig. 6) which was part of a board designed specifically for dual-in-line i.c.s.

The display, the 74132 and the dual-in-line switches were mounted on an L-shaped piece of 0.1in matric Veroboard, see photograph above for rough guide.

The front panel was made from 1.5mm aluminium sheet in which a rectangular hole was cut to view the display (see Fig. 5). The hole was backed with red Perspex to enhance visibility. Another hole is cut in the panel for access to the dual-in-line switches.

The three switches for RESET, HOLD and ON/OFF are also mounted on the front panel.

The interconnecting cable between the main unit and the pulse sender could not be a permanent fixture as the milometer fitted into the dashboard whilst the sender fitted onto the speedometer. A three-way terminal strip connector was mounted on the back of the milometer which terminated the cable and allowed the pulse sender to be easily separated from the main unit.

A twisted-pair screened cable was used for the interconnection which was screened to the milometer earth and used one wire for the pulse, and one for the 5V supply.

The regulator chip was mounted on the aluminium case of the milometer which acts as a heatsink. It was found necessary to completely isolate the car chassis from the milometer voltage supplies, particularly on positive earth cars such as Minis.


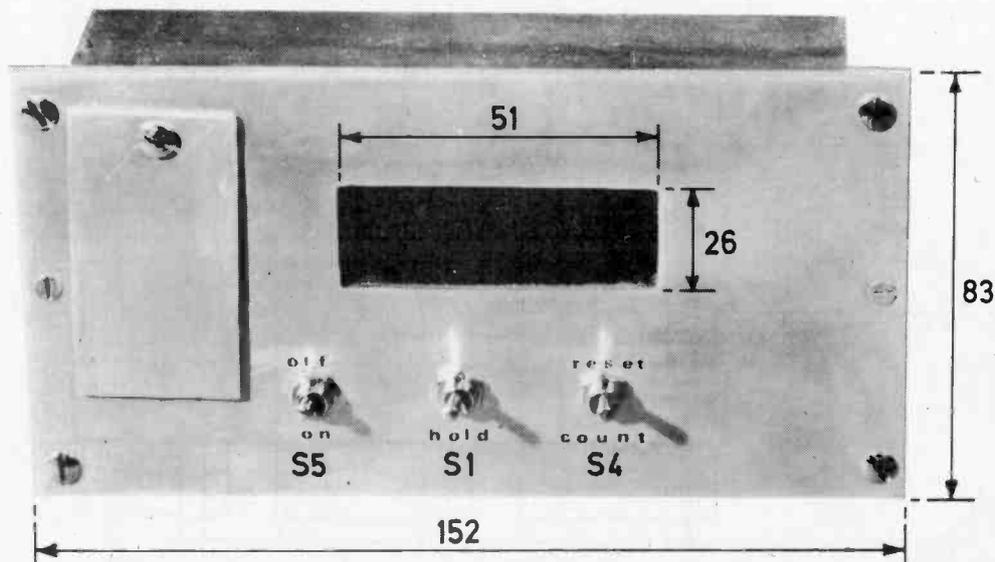


Fig. 5. Front panel details and overall measurements. The dual-in-line switches cutout measures 32 x 45mm

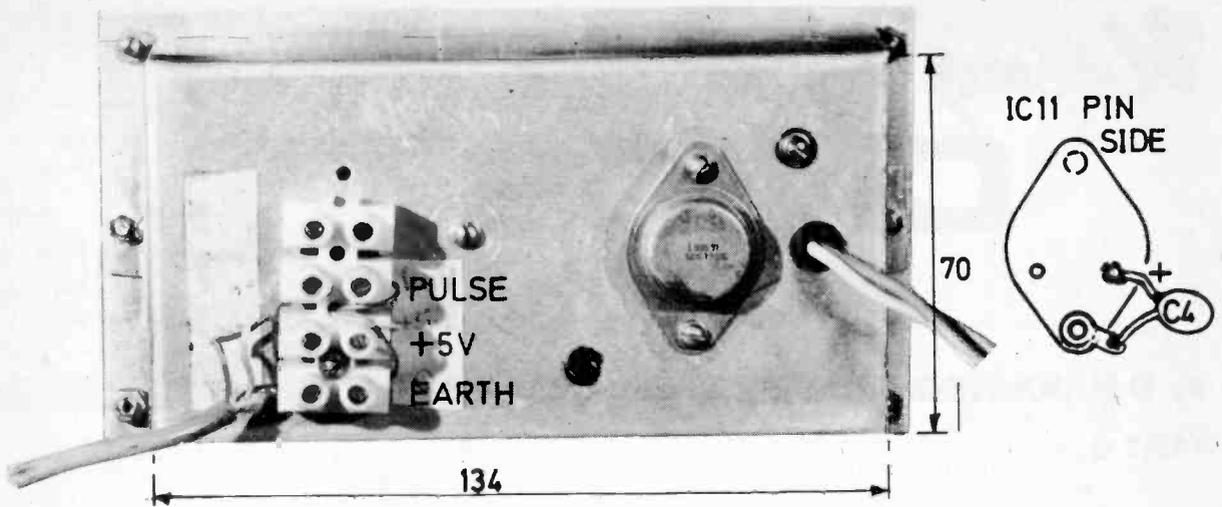

Rear view of the Milometer showing the three-way terminal block, regulator i.c. and measurements. Note that C4 is wired directly to the i.c. as shown on the right

TESTING

Testing the circuit is relatively easy as logic circuits are used, and each input or output will be at either a logic 1 or 0.

Connect the 12V and 0V leads to a suitable supply point. The programme switches S2 and S3 determine the number of pulses to be counted within the range 16 to 256, counting in binary. To work out the required number set the switches to 100 (decimal) which is 01100100 in binary. Then drive a known distance—the longer and straighter the route the greater the accuracy.

The distance indicated on the milometer display will be a percentage of the actual distance. The milometer should then be calibrated by changing the setting of 100 by the percentage error.

$$\text{New setting} = \frac{100 \times \text{Actual distance}}{\text{Indicated distance}}$$

The milometer could then be double checked by driving back along the same route when the reading should then be correct.

Once set up the only recalibration found necessary has been caused by tyre changes and wear, and then the change was only a few per cent.

Should any faults be encountered the following procedure should be used. First check that pulses are being correctly received from the sender by observing the output of gate IC4a with a multimeter as the barrel of the T-piece is revolved with a screwdriver. The outputs of the 74191 counters should then be checked. The counters should count down as pulses are fed in and should preset to the number set on the switches when zero is reached.

The 7490 counters can be tested by observing the Minitron displays. With each pulse from the 74191 counters the display should increment by one.

The voltage supply from the regulator should be between 4.75V and 5.25V. Under no circumstances should it exceed 5.5V as damage to the TTL i.c.s will result.

When testing for logic levels, the logic 0 state should be between 0 and 0.8V and logic 1 at least 2V. ★

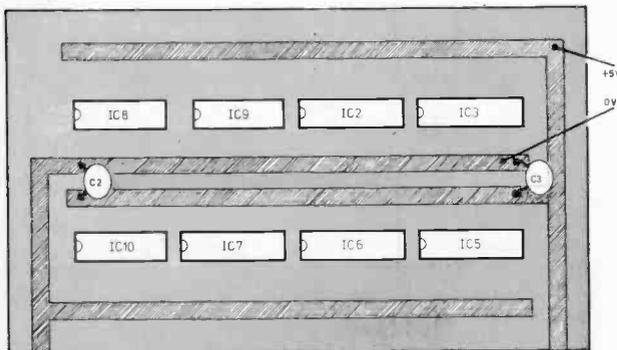


Fig. 6. Layout of the components on the dual-in-line board



Using CMOS digital I.C.s

By D.B. JOHNSON-DAVIES & A.M. MARSHALL & A.

PART 6

THIS month retriggerable monostables, digital filters and three-state output devices will be discussed.

RETRIGGERABLE MONOSTABLE

In some circumstances it is very useful to be able to retrigger the monostable; in other words, start the timing period afresh at each new input pulse. The difference between these two types of operation is shown in the waveforms of Fig. 6.2 (a) and (b). A large amount of additional gating is needed to provide this retriggering facility, and so it is very convenient that two such circuits are available in a single package in the CMOS family, designated either 4098 or 4528 according to the manufacturer (Fig. 6.1).

Two inputs are provided, the TR+ triggering on the leading edge of the input pulse and the TR- triggering on the trailing edge. If not used they should be tied to V_{SS} or V_{DD} respectively. To prevent retriggering when this facility is not required the output can be fed back to the input to inhibit the input for the duration of the pulse. The four different possible modes of operation are shown in Fig. 6.2.

The period of the output pulse is determined by the externally connected timing capacitor and resistor, and can be varied over the range 1 sec. to 100 nanosecond. It is approximately equal to RC seconds, but can vary by 10 per cent between two monostables in a package and by as much as ±80 per cent between different devices. Where a precise pulse width is required the need for initial calibration


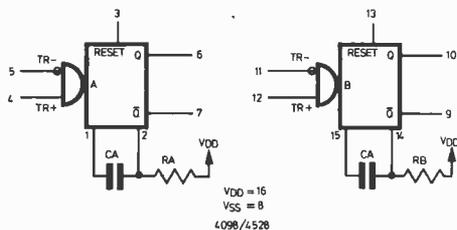


Fig. 6.1. Pin connections for the 4098 or 4528 dual retriggerable monostable. R_A and R_B can be between 5kΩ and 10MΩ. C_A and C_B can be any value, and the period is given approximately by T=RC seconds

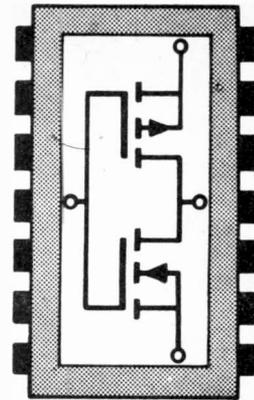

can be avoided by using the 4538, which incorporates linear circuitry to achieve a more accurately specified period.

DIGITAL FILTERS

From the waveforms of Fig. 6.2 (a) and (c) it is clear that in the retrigger mode the output will remain high as long as the period of the input is shorter than the period of the output pulse. These two circuits therefore act as digital low-pass filters,

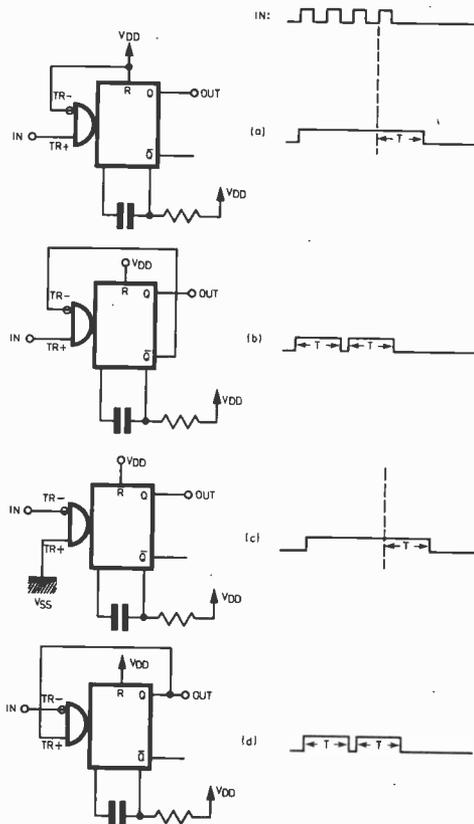


Fig. 6.2. The four possible modes of operation of the 4098/4528 monostable, and the four outputs obtained with the input shown

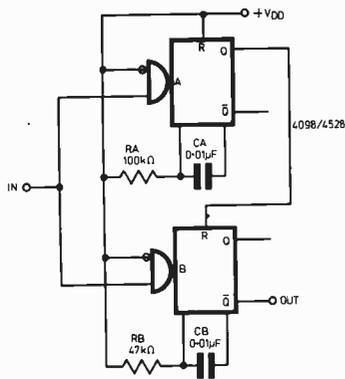


Fig. 6.3. Digital bandpass filter constructed from a single 4098/4528 package. If the input pulse interval lies between the periods of the monostables, the output follows the input. Otherwise the output is permanently held either high or low. With the values given only frequencies lying between 1kHz and 2kHz will be transmitted

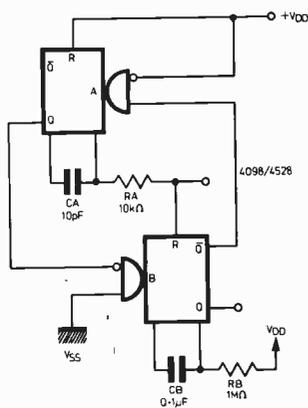


Fig. 6.4. Multivibrator using two monostables. With the values given the "on" and "off" times are about 0.1 secs and 0.1 μsecs respectively

admitting only frequencies of less than $1/T$. They can be used as envelope detectors, demodulation signals such as the pulse-modulated output of the gated oscillator described earlier. The values of R and C should be chosen to give a period just greater than that of the modulating frequency.

A bandpass filter can be built from a single package as shown in Fig. 6.3. This will only pass a pulse train whose pulse interval lies between the periods of the two monostables. The period T_A should be greater than the period T_B . The operation is as follows. If the pulse interval of the input is less than T_B , monostable B is repeatedly retriggered before it has a chance to deliver a full output pulse, and its output Q_B remains low. If the pulse interval is greater than T_A , monostable A delivers an output pulse for each input pulse, and these are fed to $RESET_B$. Therefore on the arrival of each pulse $RESET_B$ is low and monostable B remains untriggered with the output Q_B permanently high. In the third condition where the pulse interval lies between the periods T_A and T_B monostable A is repeatedly

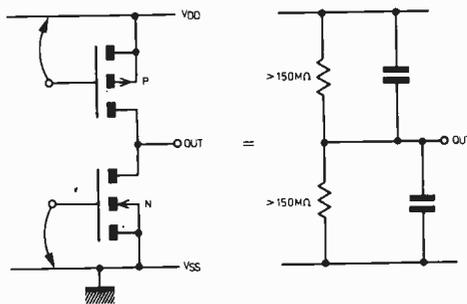


Fig. 6.5. Complementary pair with both devices biased "off" forms a disabled output which is floating with respect to the supply rails

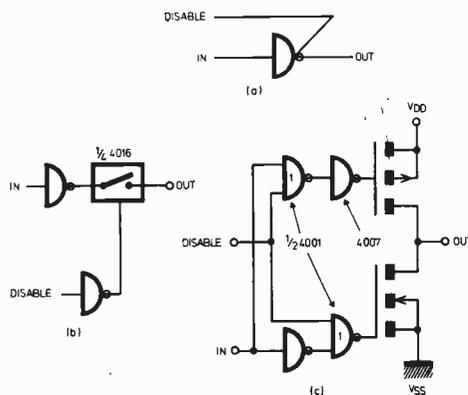


Fig. 6.6. (a) Symbol for an inverter with a three-state output. (b) Three-state output using a bilateral switch. The extra inverter is to make the disable input active when "high". (c) Three-state output using the connections to the gates of the individual MOSFETs, made available in the 4007

retriggered holding $RESET_B$ high, so that monostable B is free to give an output pulse for every input pulse.

Finally, two monostables can be arranged to trigger one another, forming a multivibrator in which the "on" and "off" periods can be varied independently. With the values given in Fig. 6.4 the mark-space ratio is 1 : 10⁷.

THREE-STATE OUTPUTS

In Part 1 of this series it was shown that the CMOS complementary pair output stage can be in one of two states; either the upper p -type is "on" holding the output to V_{DD} , or the lower n -type is "on" holding the output to V_{SS} . However, a third state can exist in which both devices are off, and this facility has several useful applications. Fig. 6.5 (a) shows a complementary pair in which both devices are "off", and (b) the equivalent electrical circuit shows that the output is floating with respect to both supply rails. Several CMOS parts are available with such three-state outputs. These usually have an "output disable" pin which, when taken to a logic "1" level puts all the outputs in the floating state; the 4502 strobed hex buffer inverter has already been mentioned.

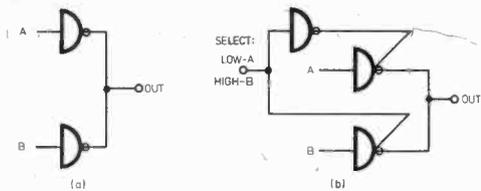


Fig. 6.7. (a) Inadvisable commoning of normal gate outputs. (b) Common bussing of two three-state outputs, where all but one are disabled at any time

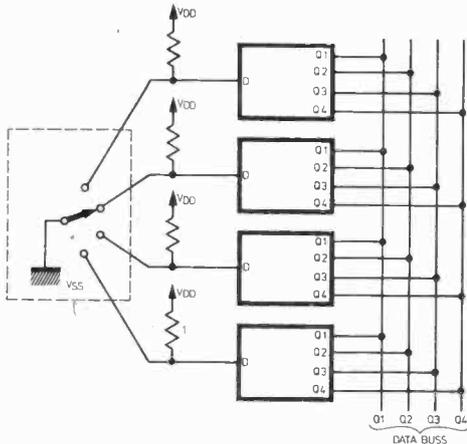


Fig. 6.8. Common bussing illustrated with hypothetical devices (such as the 4043) where only one set of outputs needs to be accessed at any time

It is also possible to build three-state outputs from discrete parts, and Fig. 6.6 shows two approaches. These are both inverters with three-state outputs, the symbol of which is shown in (a). In (b) a bilateral switch is added after the gate output. When the disable input is high, the switch is open leaving the output floating. Circuit (c) uses a 4007 package and two gates from a 4001 package to the same end. The disable input biases both output MOSFETs "off". The two inverters are formed from the remainder of the 4007 package.

OUTPUT SHARING

Three-state make possible 'common-bussing': the sharing of output lines between several outputs. In Fig. 6.7 (a) two normal outputs are commoned in an inadvisable arrangement. If the gates are in opposite states the output will be at around half the supply voltage, which is not a usable logic level. However, the arrangement is possible if the gates have three-state outputs, and all but one of the outputs are disabled as in (b). In this example the same result could be achieved using two 2-input gates, but in larger systems the gate saving becomes substantial. Fig. 6.8 shows four devices each with four three-state outputs sharing the same four buss. The switch ensures that all but one set of the outputs are disabled at any time, and would be replaced by control logic in an application.

Next month: More circuit variants and devices listed.

NEWS BRIEFS

Quad Achievements

FOR the first time exports of Quad equipment exceeded one million pounds in a year. This represents a contribution of more than £7,000 to the United Kingdom's balance of payments per employee.

This is a fine achievement in the highly competitive field of High Fidelity, which is widely regarded as being the exclusive domain of the Japanese.

Major overseas customers, each accounting for more than ten per cent of the total are United States, Japan, Canada and Benelux, with other European markets close behind.

Quad now looks to an even better year in 1976/77 thanks to the unprecedented success of the recently introduced Quad 405 current dumping amplifier, for which export orders of £400,000 have already been received.

A further achievement for Quad is the 405 amplifier winning a Consumer and Contracts award for good design, issued by the Design Council. This is the second Design Council award for Quad, the first was won in 1969 when their 33/303/FM3 system was selected.

Big Hit for Night Attack Missile

THE Navy's new Night Attack Missile scored a direct hit at night on a moving M48 tank, marking the second successful demonstration of the Night Attack Weapon System. The test took place at the Naval Weapons Center, China Lake, California.

The missile was launched from a Navy A-6 aircraft at the longest range yet recorded for any contemporary infrared air-to-surface weapon. The target was a standard, unaugmented M48 tank moving perpendicular to the aircraft flight path. Detection of the tank was accomplished using a forward looking infrared system (FLIR). Handoff from the FLIR to the missile seeker was accomplished automatically, without operator assistance, using the weapon system bresight computer.

The test was the second in a series whose purpose is to demonstrate that the weapon system technology is within the current state-of-the-art. In its first free-flight test, the system scored a direct hit on an M53 self-propelled gun in daylight. Night Attack programme objectives include clear day/night, fire-and-forget operation, minimum operator workload, and a low-cost expendable round.


Design objective of the Night Attack non-imaging Maverick system is to provide a first pass multiple launch capability at AAA standoff ranges against such tactical sea/land targets as tanks, trucks, and patrol boats. Test results to date have validated that capability.

New Electronic Exchange in Service

THE first of a new generation of electronic telephone exchanges forming the next phase in a major Post Office programme to modernise the nation's telephone service, has been successfully brought into operation.

The new exchange is in Birmingham. Of the type known as TXE4, it was brought into service when 3,000 customers previously connected to the Sutton Coldfield exchange were transferred to the new exchange.

The successful bringing into service of the new exchange, called Rectory, marks a positive step forward in Post Office plans for further improving the quality of Britain's automatic telephone service. Under this scheme, the present Strowger electro-mechanical telephone exchanges will be progressively replaced by modern electronic systems capable of giving improved service and reliability. Between now and March 1980 the Post Office expects on present plans to spend about £330M on electronic exchanges at current price levels.

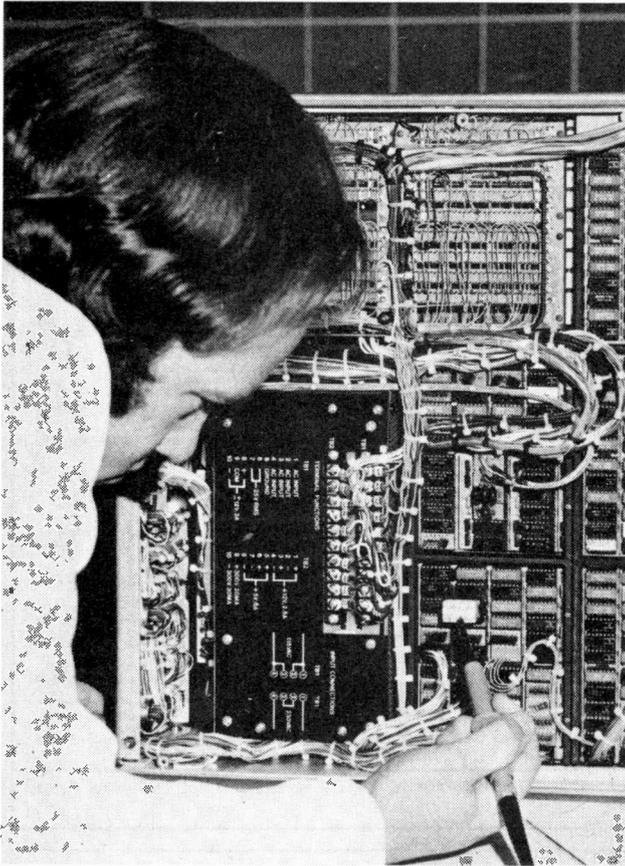

This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.



You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.


1

Build an oscilloscope.

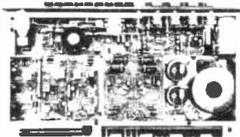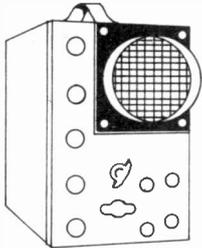As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.




2

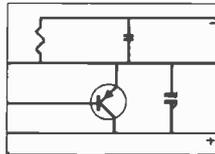

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

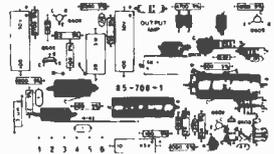

Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

PLUS FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSE RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. EL66
 P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

(Block caps please)

B. BAMBER ELECTRONICS

Dept PE, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

SPECIAL OFFER
FREE WELLER 25W (SP25) SOLDERING IRON (worth £2.72 inc. VAT) with all orders over £20. Limited period only. Send now.

ALU-SOL ALUMINIUM SOLDER (made by Mull-cox) Solders aluminium to itself or copper, brass, steel, nickel or tinplate. 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 30p pack. Large reel (approx. 12 metres) £2.75.

MIXED COMPONENT PACKS, containing resistors, capacitors, switches, pots, etc. All new (random sample bag revealed approx. 700 items), £2 per pack, while stocks last.

TUNED COILS, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance, many uses. Easily rewound, 3 for 50p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio Hi-Fi inputs, etc.) approx. 1in x 1 1/2in, 3 for 50p.

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108 MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx 8 1/2in x 1 1/2in, 2 for 35p. Multiturn Pots, 10 turn, 1in spindle (ex-equip), following values available: 2kohm, 5kohm, 10kohm, £1 each.

Lead suppressors (10kohm) for mobile plug leads, 4 for 50p.

1mA Meters, 2 in square, plastic fronts (these have a paper scale stuck over original markings) 0-1mA, which is easily peeled off and an internal 18K resistor which is easily removed, £1.75 each or 2 for £3.

TS Midget 3 pole 4 way, rotary switches, 40p each.

HIGH QUALITY SPEAKERS, 8in x 6in elliptical, only 2in deep, inverse magnet, 4ohms, rated up to 10W, £1.50 each or 2 for £2.75 (city discount available + 12 1/2% VAT).

TV PLUGS AND SOCKETS

TV Plugs (metal type), 5 for 50p.

TV Sockets (metal type), 4 for 50p.

TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12 1/2% VAT.

PLUGS AND SOCKETS

N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
N-Type Sockets (4-hole chassis mounting, 50 ohms (a small coax lead type), 50p each.
PL259 Plugs (PTFE), brand new, packed with reducers, 85p or 5 for £3.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 50p each or 5 for £2.25.
25-way ISEP Plugs and Sockets, 40p set (1 plug + 1skt)

Plugs and sockets sold separately at 25p each. Bulgin Round Free Scks 3 pin, for mains input on test equipment, etc. 25p each.

Mobile Converters, 24V DC input 13.8V at approx 3.4A DC output, fully stabilised, £3.50 each (ideal for running 12V car radio from 24V lorry battery).

Pkts of 2BA Nuts (the self-locking ones with the nylon insert) 100 for 50p.

We now stock Spiratux Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

1F. Cans, 1in square, suitable for rewind, 6 for 30p, + 12 1/2% VAT.
Miniature earphones with min. jack plug, 2 for 50p + 12 1/2% VAT.

TWIN 1F. CANS, approx. 1in x 1in x 1in high, around 3.5-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Duobiler Electrolytics, 500uF, 450V, 2 for 50p.
Duobiler Electrolytics, 100uF, 275V, 2 for 50p.
Pleassey Electrolytics, 470uF, 63V, 3 for 50p.
TCC Electrolytics, 1000uF, 30V, 3 for 60p.

Pleassey Electrolytics, 1000uF, 180V, 40p each (3 for £1).
Duobiler Electrolytics, 5000uF, 35V, 50p each.
Duobiler Electrolytics, 5000uF, 50V, 60p each.

ITT Electrolytics, 8800uF, 25V, high grade, screw terminals, with mounting clips, 50p each.

Pleassey Electrolytics, 10,000uF at 63V, 75p each.

Pleassey Cathodray Capacitors, 0-0.4uF at 12.5kV DC, Screw terminals, £1.50 each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. S.A.E. FOR LIST.

SPECIAL OFFER!

MAINS TRANSFORMER, TYPE 14/4, 14V at 4A, £2.50.

2-6pF, 10mm circular ceramic trimmers (for VHF/UHF work) 3 pin mounting, 5 for 50p.
T03 transistor insulator sets, 10 for 50p.
PC Board Withdrawal handles, mixed coils, 6 for 50p.

Solder, 20 SWG, 60/40 alloy, approx 8 yds for 25p.
MINIATURE 2 PIN PLUGS AND SOCKETS (fit into 1in hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors). Bargain pack of 3 plugs + 3 sockets + covers, 50p.

PROGRAMMERS (magnetic devices) Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable. Ideal for switching disco lights, displays, etc., or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 3 switch version £1.50, or 15 switch version £2.

HEAVY DUTY HEATSINK BLOCKS, undrilled, base area 2 1/2in x 2 1/2in, with 6 fins, total height 2 1/2in 50p each.

RUBBER MAGNETS 1in square, with mounting hole, 20 for 30p.
SPERRY 7-SEGMENT P.G.D. DISPLAYS, digit height 0.3in red, with decimal points, 150V to 120V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new, AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1 each, TYPE 333 (three digits on one mount) £1.50. (Sorry, no single digit available.) Data Supplied.

BSX20 (VHF Osc/Multi), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC 108 (plastic BC108), 5 for 50p.
OC200 Transistors, 6 for 50p.

BCY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type T05 Transistors, 12 for 25p.
BF152 (UHF amp mixer), 3 for 50p.

BA121 Varicap Diodes, 4 for 50p.
1N914 Diodes, 10 for 25p.

1in polythene chassis mounting fuseholders, 6 for 30p.
Mullard Tubular ceramic trimmers, 1-18pF, 5 for 50p.

I.C.s - some coded 14 DIL type, untested, mixed, 20 for 25p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

DIECAST BOXES (approx size in inches)
4.3 x 2.3 x 1.2 85p
4.8 x 2.3 x 1.5 75p
4.8 x 3.8 x 1 85p
4.8 x 3.8 x 2 £1.00
6.8 x 4.8 x 2 £1.45
4.8 x 3.8 x 3 £1.55
6.8 x 4.8 x 4 £2.25
8.8 x 5.8 x 2 £1.85
10.8 x 6.8 x 2 £2.25

Please add 8% VAT

WELLER SOLDERING IRONS

EXPERT, Built-in-spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN, £8.80 + VAT (54p)

EXPERT SOLDER GUN KIT (spare bits case, etc.), £8.80 + VAT (78p)

SPARE BITS, PAIR, 25p + VAT (2p)

MARKSMAN SOLDERING IRONS

SP150 15W £2.52 + VAT (20p)

SP250 25W £2.52 + VAT (20p)

SP250K 25W + bits, etc, kit £3.12 + VAT (25p)

SP400 40W £3.44 + VAT (28p)

BENCH STAND with spring for Marksmen Irons

£1.80 + VAT (14p)

SPARE BITS

MT8 for 25W, 42p + VAT (3p)

MT4 for 25W, 35p + VAT (3p)

MT10 for 40W, 40p + VAT (3p)

TCPI TEMPERATURE CONTROLLED IRON

Temperature controlled iron & PSU, £18.43 + VAT (£1.47)

SPARE TIPS

Type CC single flat, Type K double flat fine tip, 90p each + VAT (8p).

ALL SPARES AVAILABLE

MULTICORE SOLDER

Size 5 Savitl 18 s.w.g. in alloy dispenser, 32p + VAT (3p)

Size C15AV18 Savitl 18s w.g. 58p + VAT (4p)

Size 12 SAVBIT 18s w.g. on plastic reel £1.60 + VAT (15p)

MINIATURE PLIERS

High quality Crescent made in USA, £4.35 + VAT (35p)

SIDE CUTTERS, high quality Crescent, made in USA, £5.45 + VAT (44p)

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN.

SPRING MILDENHALL ROAD

	NORMAL PRICE	
F.M. Tuners, 8-transistor chassis with stereo decoder and L.E.D. Indicator	£16.60	£10.90
Aircraft-band Receiver. Just place near any radio	£5.97	£3.90
Echo-chamber (endless tape). Variable delay.	£5.00	£3.50
Field-strength indicators, 1-250MHz	£5.40	£3.30
Stereo Amplifiers complete, 3-watt, 8-ohm	£4.80	£2.75
10-watt Amplifiers, 12 volt d.c. 3/8/15-ohm.	£5.90	£3.90
Cartridges, Acos GP104. Ceramic/diamond	£2.32	£1.50
Cartridges, Acos GP101. Crystal/sapphire/compatible	£1.00	£0.50
Speakers, 2in, 8 ohm	£2.50	£0.35
Speakers, Car Stereo, 8 ohm, 5 watt, in cabinets	£3.90	£2.50
Dynamic Tape Mikas with remote-control facility	£1.30	£0.90
Crystal Tape Recorder Mikas	£1.00	£0.60
Crystal Mike Inserts with bracket	£0.30	£0.20
Indicators, 12 volt L.E.D. in chrome bezel	£0.48	£0.35
"Bargain Bags" 4lb caps/resistors/transistors/diodes	£5.00	£4.00
Controls, Volume/pre-set (rotary and slider). Assorted 100 Transistors, 20 npn/pnp. All new and marked	£1.00	£1.00
Transistors, 100 npn untested	£1.00	£1.00
Diodes, 100 germanium untested	£0.50	£0.50
Diodes, 100 silicon untested	£0.50	£0.50
Diodes, 100 zener untested	£1.00	£1.00
*Pack 1 —100 resistors, 100 ceramics, 100 diodes	£1.00	£1.00
*Pack 2 —100 resistors, 100 ceramics, 100 polystyrene	£1.00	£1.00
*Pack 3 —100 resistors, 100 s/mica ceramic, 100 polyester	£1.00	£1.00
Fluorescent 12-volt Camping Lights		
21in, 13 watt	£8.00	£4.90
12in, 8 watt	£7.00	£3.90
"Disco" Type 3-Channel Flashing Light Units. Built-in mike No connection needed to amp		
Multimeters—a.c. 0-1000V, d.c. 0-1000V, 0-100mA, 0-150kΩ	£19.95	£17.50
Multimeters:	£5.80	£3.50
a.c. 0-500V (10 ranges), d.c. 0-500V, (12 ranges)		
d.c. current 0-25uA to 0-10 amps (10 ranges)	£16.96	£11.30
Resistance 0-100 ohms to 0-16MΩ (4 ranges)	£8.50	£2.50
Panel Meters, 0-50uA, 2 1/2in x 1 1/2in	£1.58	£1.20
Soldering Irons, 15 watt, Pencil bit	£0.62	£0.50
Servisol Switch Cleaner (with snorkel)		
Copper-clad Fibre Glass Board		£1.00
Single-sided, Square foot		£1.25
Double-sided, Square foot		£1.20
Fototak Light Sensitive Spray for printed circuit making Developer for same		£0.30
Ferric Chloride for etching		£0.40
ALL ABOVE ITEMS PLUS 8% VAT		

G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Postage: Below £10—50p Above £10—Free

THE SOUND MATCHMAKER

Every month Practical Hi-Fi & Audio carries an updated matching hi-fi guide. With this detailed knowledge, you can now choose your components and assemble a quality system with confidence.

There is also regular coverage of hi-fi developments and commonsense advice on hi-fi problems.

A sound match of practical hi-fi and audio
PRACTICAL HI-FI & AUDIO
Every month 30p



BY FRANK W. HYDE

THE LARGE SPACE TELESCOPE

The long discussed space telescope which seemed until recently to be relegated to sometime in the future, is to be an international project. This telescope has the unanimous support of most astronomers. It is claimed that it could revolutionise present knowledge if it can be placed in orbit above the distorting layers of the Earth's atmosphere. Second thoughts on size have made it possible for the telescope to be in orbit as early as 1982.

To meet the request of the Congressional Committee to cut the cost, the size has been reduced from 3 metres to 2.4 metres for the mirror diameter. Restricting the effective diffraction diameter to 2 metres allows large savings in the cost of stabilisation. This decision satisfied the minimum standards but the advantages are still great.

A good comparison would be that it could be some 20 to 30 times better than a ground based telescope of equivalent size. The pointing accuracy of the instrument, better than 0.005 arc-seconds, will be achieved by star sensors and precision gyroscopes set at the rear end of the assembly. In addition its ability to concentrate the light accepted by the large aperture, to an image only 0.1 arc-second is unique.

This facility affords very considerable extension of the limits of observation particularly in the case of extra-galactic faint objects.

All this has enabled Congress to take a most unusual decision to

put the project back into the budget for this year. The cost of the modified design is of the order of 350 million dollars. The unit will weigh about 7.5 tonnes and will therefore be capable of being collected by the Space Shuttle when maintenance periods and the normal procedures of up-dating is required. The designed life is 15 years.

The European participation in this international project will not involve the capital cost of the telescope but rather the input of experiments and instrumentation.

SORE POINTS IN SPACE OCCUPATION

The launching of Russia's *Statsionar*, the first of its operational satellites, designated *Raduga*, is geostationary over the Indian Ocean at 80 degrees East $\pm 5^\circ$. It operates on the standard frequencies of 4 to 6 GHz. The USSR have announced that they will place two more in orbits at about 35° and 50° East. They further announce that they will be launching another seven over the Pacific, Atlantic and the Indian Oceans to establish a global network.

Since Indonesia has announced that she plans a communications system, and also the fact that one of the *Statsionar*'s is to be placed at 58° East (only 2° away from an operational *Intelstat 4*) interference could be a serious problem especially as the new *Intelstat 4As* is operational.

Is it possible that near space is to have traffic problems at this early stage?

THE NEW ERA OF SPACE ACTIVITY

At the Kennedy Space Centre great changes are taking place. By 1978 the scene must be set for the Shuttle programme. Already a runway 15,000 feet long and 300 feet wide has been started. This will be used as the landing strip for returning Orbiters from space. It will also accommodate the pickaback Boeing 747-Orbiter combination.

After returning from space the Orbiters will be towed from the runway to a processing area near the vehicle assembly such loads would include Spacelab. Other loads would be mounted on the Orbiters while on the launch pad.

There are plans for a double two man crew and selected astronauts will be trained to be ready for the first flight tests scheduled for mid

1977. The men selected have been named. The commander of the first crew is Fred W. Haise. He is the only crew man in the group to have flown in space. He was Lunar Module pilot for *Apollo 13* and back up commander for *Apollo 16*. Charles G. Fullerton will be pilot in the first crew. He was appointed to the NASA astronaut team in 1969. The second crew will be Joe H. Engle in command, and Richard H. Truly.

Approach and landing test-flights will be made. Drop tests will be made at the Edwards Air Force Base. The Orbiters will be carried up on specially designed Boeing 747 aircraft. The Orbiters will be released at 25,000 feet and make free flight landings.

ALSEP 14 SLEEPS FOR A MONTH

The operation of the Lunar Packages have been so constant and reliable that it was something of a shock when *ALSEP 14*, set up by the *Apollo 14* mission, suddenly ceased to function. The team at the Johnson Spaceflight Centre have not so far been able to explain the cessation of operation, and still less its recovery after a month.

Not only did all experiments and equipment come to life, but one worked even better than before.

This was the system which was concerned with the investigation of charged particles near to the surface of the Moon. Previously the experiment did not work during the Lunar day because of temperature conditions. Now it works continuously and more efficiently round the clock.

NOTE FOR POSTERITY

Things in the sky are a part of our composite memory and there now tends to be a somewhat blasé approach to it all. While it is still true that "what goes up must come down" the "come down" may take a very long time in terms of the length of civilisations.

For a specific set of "time stones" of the future there is the *Cosmos 761* with a life of 7,500 years. *Cosmos 765* will be expected to survive 10,000 years with replacement satellites, and whose rocket will remain for 20,000 years. Or take *Titan 3C* which will be around after many civilisations rise and fall, for more than a million years. In the not too distant future too, there is another with an estimated life of two million years.



AUDIO MILLIVOLTMETER

By R. A. PENFOLD

If one considers virtually any major audio amplifier parameter (noise level, distortion, frequency response voltage gain, etc.), it will be apparent that some form of sensitive a.c. voltmeter is required in its measurement. An a.f. millivoltmeter is thus an essential piece of test equipment for anyone involved in the design or testing of audio equipment.

The millivoltmeter described in this article covers seven ranges with full scale deflection sensitivities of 1mV, 3mV, 10mV, 30mV, 100mV, 300mV, and 1V. The -3dB frequency response is approximately 20Hz to better than 200kHz, and the response is virtually flat over the audio frequency spectrum. The input impedance is $1\text{M}\Omega$, which ensures a low level of loading on the equipment under test. A mains power unit is used to provide the stabilised supplies for the circuit, which is based on four inexpensive operational amplifiers.

FEEDBACK LOOP

A millivoltmeter does not merely consist of an amplifier driving a meter via a rectifier, as this would not give accurate results. The reason for this being that semiconductor diodes will not conduct heavily unless their forward conduction threshold voltage is exceeded.

This voltage varies with different types of diode, and with temperature, but is about 0.65V for a silicon diode and 0.2V for a germanium one. This voltage drop would obviously have a profoundly degrading effect upon the linearity of the circuit.

It is possible to overcome this forward voltage drop by including the meter and rectifier in a negative feedback loop connected in the output amplifier circuit. The basic arrangement for this is shown in Fig. 1a.

Until the diodes begin to conduct, there can obviously be no negative feedback, and the amplifier will have a high voltage gain. It will, in fact, have its open loop gain.

Any input signal, even a very small one, will cause the forward conduction threshold of the diodes to be quickly reached by the output of the amplifier.

As this threshold is reached and the diodes begin to conduct, an increasing level of negative feedback will be introduced into the circuit. The preset resistor sets the maximum available level of feedback, and hence also the effective voltage gain of the amplifier.

Fig. 1b shows the waveform which results at the output of the amplifier when a sine wave is fed into the input. The fast leading edge of the waveform overcomes the forward threshold voltage of the diodes

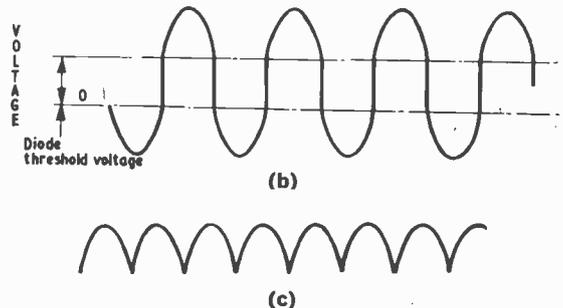
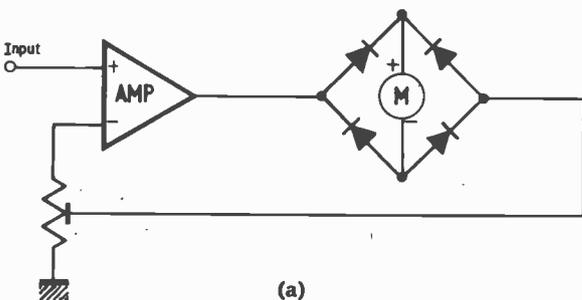


Fig. 1. (a) Overcoming diode forward voltage drop by placing them in the feedback loop of an amplifier. (b) The output waveform produced by the amplifier with a sine wave input. (c) Current waveform through meter

almost instantaneously, and then the relatively undistorted part of the waveform is fed to the meter, but is full wave rectified. A signal closely resembling a full wave rectified sine wave thus appears across the meter, as shown in Fig. 1c. This is, of course, exactly what is required.

Simply stated, the non-linearity of the diodes is cancelled out by the non-linearity of the voltage gain produced by including the diodes in the feedback loop.

PRACTICAL CIRCUIT

The circuit diagram of the audio millivoltmeter is shown in Fig. 2.

A 741 operational amplifier is used as the input stage. This is connected as a unity voltage gain buffer amplifier with a 100% negative feedback loop between its output and inverting input. R1 provides the bias voltage for this stage and sets the input impedance at 1MΩ. C1 provides d.c. blocking at the input. The output of this stage is taken to the attenuator via C2.

This simple arrangement provides a high input impedance and a low output impedance, and it also has a very low noise level. One slight disadvantage, however, is that at high frequencies (at about 100kHz and above) this stage may not be able to handle a signal of around 1 volt r.m.s. properly. This results in a reduced upper frequency response on the 1V range with readings approaching f.s.d.


ATTENUATOR

The attenuator section really consists of six separate attenuators, one for each range from 3mV to 1V. The lower resistor of each attenuator also forms the input bias resistor for the non-inverting input of IC2. In the 1mV position no attenuator is required, and R3 provides the input bias for IC2. The attenuator is connected in a low impedance part of the circuit so that stray capacitances have no significant effect on the unit's frequency response, and no frequency compensation is necessary.

IC2 is used as a non-inverting amplifier. Its closed loop voltage gain is controlled by the two feedback resistors, R15 and R16, and is approximately equal to $(R15 + R16) / R15$. This gives a voltage gain of about 10 times (20dB) with the values shown. C3 is the compensation capacitor.

IC3 is used in a virtually identical configuration to that adopted for IC2. The two stages are capacitively coupled via C4. R17 provides the bias for the non-inverting input. C5 is connected in parallel with feedback resistor R18, and at high frequencies where the impedance of this capacitor is low, it boosts the gain of this stage. This gives the millivoltmeter an improved high frequency response. IC3 is direct coupled to the output stage.

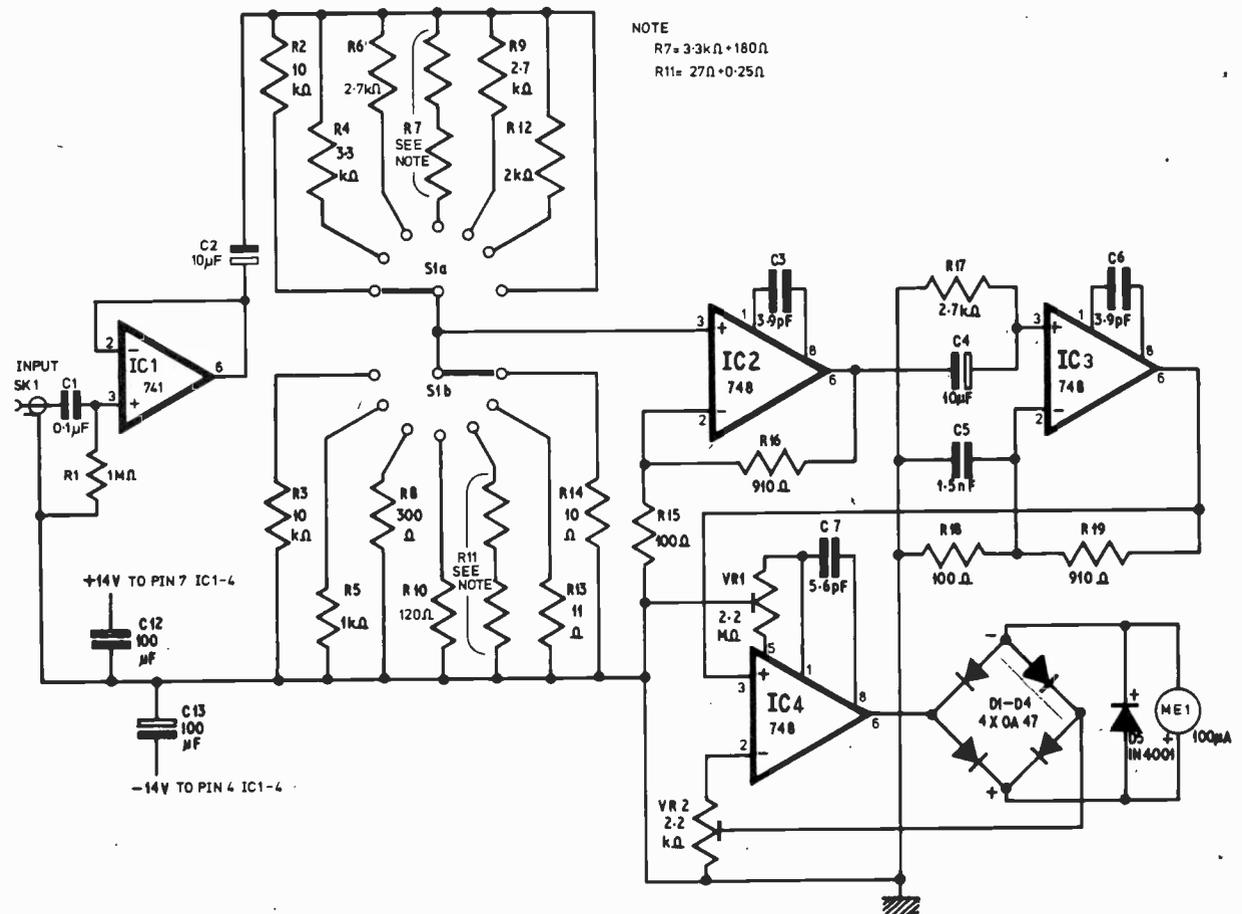This uses IC4 in the arrangement shown in Fig. 1, which was discussed earlier. As the meter and rectifier circuit is direct coupled to the output of the i.c., it is



NOTE
 R7 = 3.3kΩ + 180Ω
 R11 = 27Ω + 0.25Ω

Fig. 2. Circuit diagram of the Audio Millivoltmeter

necessary to have an offset null adjustment circuit. This is the function of VR1. VR2 permits adjustment of the sensitivity of the circuit, and allows the unit to be calibrated against an a.c. voltage of known value. Gold bonded diodes are used in the rectifier as these have a low forward conduction threshold voltage.

As the 748 i.c. is capable of giving a large enough output to damage a 100 μ A meter in the event of a fault or considerable overload, it is essential to have some form of overload protection for the meter. D5 has been included for this purpose, and it is used here as a sort of low voltage zener diode. This limits the voltage across the meter to about 0.5V, which is insufficient to damage most meters, even if sustained.

C12 and C13 are supply decoupling capacitors.

COMPONENTS . . .

Resistors

R1	1M Ω	R12	2k Ω 1%
R2	10k Ω 1%	R13	11 Ω 1%
R3	10k Ω 1%	R14	10 Ω 1%
R4	3.3k Ω 1%	R15	100 Ω
R5	1k Ω 1%	R16	910 Ω
R7	{ 180 Ω 1%	R17	2.7k Ω
	{ 3.3k Ω 1%	R18	100 Ω
R8	300 Ω 1%	R19	910 Ω
R9	2.7k Ω 1%	R20	2.7k Ω
R10	180 Ω 1%	R21	2.7k Ω
R11	27 Ω + 0.25 Ω 1%		

All resistors $\frac{1}{4}$ W 5% unless otherwise stated

Potentiometers

VR1	2.2M Ω
VR2	2.2k Ω

Capacitors

C1	100nF plastic
C2	10 μ F 10V elect.
C3	3.9pF ceramic
C4	10 μ F 10V elect.
C5	1.5nF disc ceramic
C6	3.9pF ceramic
C7	5.6pF ceramic
C8	400 μ F 25V elect.
C9	400 μ F 25V elect.
C10	100 μ F 16V elect.
C11	100 μ F 16V elect.
C12	100 μ F 16V elect.
C13	100 μ F 16V elect.

Semiconductors

IC1	741 8 pin d.i.l. (plus socket)
IC2, 3, 4	748 8 pin d.i.l. (3 off plus sockets)
TR1	BC148
TR2	BC158
D1-4	OA47 (4 off)
D5-7	1N4001 (3 off)
D8, 9	BZY88C15V (2 off)

Transformer

T1 Mains transformer with 6-0-6V at 100mA

Miscellaneous

Instrument case, approx. 215 x 215 x 85mm metal
100 μ A moving coil meter (see text).
D.P.S.T. mains rotary switch.
Mains panel neon with internal series resistor.
Miniature Maka-switch parts (see text).
Materials for p.c.b. manufacture.
20 s.w.g. aluminium for screen.
Two pointer knobs.
Sundry hardware.

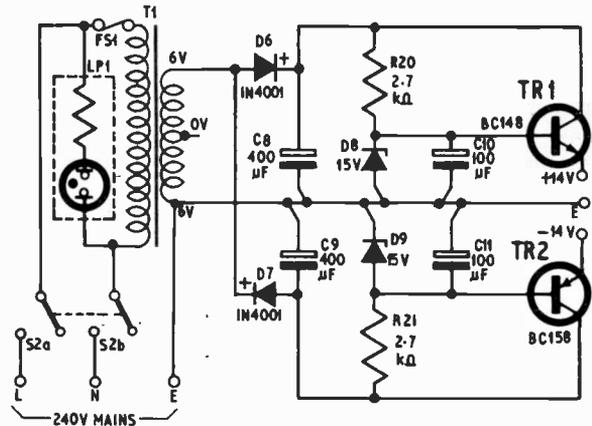


Fig. 3. Power supply circuit

POWER SUPPLY

Fig. 3 shows the circuit diagram of the mains power supply unit. Stabilised supplies are provided even though the gain of the millivoltmeter circuit is largely independent of the supply voltage. A stabilised supply ensures good stability of the direct coupled output stage. The p.s.u. fulfils the usual op. amp. requirement of equal positive and negative supplies with the central supply line being earthed.

The circuit consists of two halfwave supplies, one using D6 and C8 and providing a positive supply, and the other using D7 and C9 to provide a negative supply.

Electronic smoothing regulation of the positive supply are provided by R22, D8, C10, and TR1. These are connected in a well known configuration with TR1 operating as an emitter follower series regulator. An identical but complementary arrangement is used for the negative supply.

Although only half wave rectification is used, the outputs of the supply are well smoothed and regulated and provide about ± 14 V to the main circuit.

COMPONENTS

Any 100 μ A moving coil meter should work in the circuit, but as RS dual scaled 0-3 and 0-10 meter is most suitable. If an ordinary 100 μ A meter is used, it will be necessary to add a 0-3 scale by hand, which is not at all easy to do accurately.

In order to be sure of good accuracy on all ranges it is essential to use close tolerance resistors in the attenuator unit. 2% tolerance should be regarded as a minimum requirement for these components, and 1% types are preferable.

S1 is a seven way two pole rotary switch, and can be made from RS Miniature Maka-Switch parts. The parts required are one shafting assembly, two single pole wafers, and eighteen 3.2mm spacers. The adjustable end stop is set for seven-way operation, and the wafers are mounted one at the extreme front of the shafting assembly and one at the extreme rear.

R11 needs to have a value of about 0.27 ohms, but this value may be difficult to obtain in a low wattage. Four 1 ohm 1/8 watt resistors wired in parallel (0.25 ohms) were used for this component on the prototype.



Stirling Sound Products


FROM BI-PRE-PAK

AT £5.20 THIS SUPERB TRUE HI-FI POWER AMP. IS UNBEATABLE STIRLING SOUND SS125

OBTAINABLE ONLY FROM THE MAKERS, STIRLING SOUND/BI-PRE-PAK LTD.

Not only is this Stirling Sound's best audio amplifier yet; it rightfully qualifies as one of the best of its kind yet made available to constructors. Intended above all for high-fidelity, the characteristics of the SS125 are such that it can be used in many other applications where dependability is the prime consideration. The SS125 integrates well with other SS units as well as those of other manufacturers. Incorporates new circuitry using a complimentary long-tailed pair input and full complementary output circuits to give lab. standards of performance.

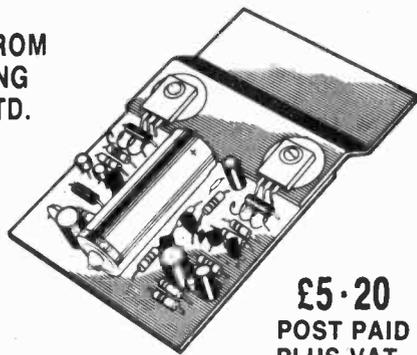- OUTPUT—25W R.M.S. into 8Ω using 50V.
- DISTORTION—Less than 0.05% at all power levels (from 10Hz to 10kHz).
- FREQUENCY RESPONSE—±1dB 15Hz to 30kHz (4Ω); ±1dB 10Hz to 30kHz (8Ω).
- HIGH Z INPUT—100kΩ (40dB gain/100x).
- INPUT SENSITIVITY—150mV for 25W R.M.D. out.
- SIZE—4½in x 3in x ½in high.




£5.20
POST PAID
PLUS VAT
(Total £5.85)

AT 12½% VAT BETTER VALUE THAN EVER MORE STIRLING SOUND MODULES

With easy to follow instructions


F.M. TUNER UNITS

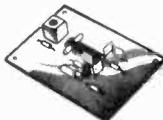- SS203** Stereo decoder for use with SS201 and SS202 or any good F.M. tuner. A L.E.D. beacon may be attached (3in x 2in) **£3.85**
- SS202** I.F. amp. A meter and/or A.F.C. can be connected (size 3in x 2in) **£2.65**




AUDIO MODULES

- SS105** 5 watt amplifier to run from 12V (3½ x 2in x ½in) **£2.25**
- SS110** Similar to SS105 but more powerful giving 10W into 4 ohms using 24V **£2.75**
- SS120** 20 watt module when used with 34 volts into 4 ohms **£3.00**
- SS140** Delivers 40 watts R.M.S. into 4 ohms using a 45V/2A supply such as our SS345. The power and quality of this unit are superb. Size 4in x 3in x ½in **£3.75***
- SS100** Active tone control, stereo ±15dB lift/cut bass-treble **£1.60**
- SS102** Pre-amp (stereo) inc. line feed back and RIAA correction **£2.25**
- SS101** Pre-amp for ceramic, etc. **£1.60**

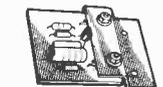

THE SENSATIONAL STIRLING SOUND POWER SUPPLY UNITS

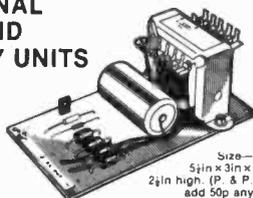Robustly designed units on each of which is a stabilised take-off point to provide power for tuner, pre-amp and control stages. All supplied with transformers.



Size—5½in x 3in x 2½in high. (P. & P. add 50p any model.)

- | | | | |
|------------------------|---------------|--|---------------|
| SS312
12V/1A | £3.75* | SS334
34V/2A | £5.20* |
| SS318
18V/1A | £4.15* | SS345
45V/4A | £6.25* |
| SS324
24V/1A | £4.60* | <i>SS334 and SS345 are supplied with separate transformers</i> | |

The "Super Spark" Mk. 5 Capacity Discharge Ignition Unit for all who own a car

Even better than the original B-P-P version, thousands of which are in use saving motorists appreciable time and money for petrol. Very easy to install. The "Super Spark" model incorporates switch for instant change to conventional ignition, easily adapted to pos. or neg. earth return; anti-burglar immobilising switch; pre-set control for rev. limitation. There are no exposed parts, the unit, on p.c.b., being housed in strong enclosed metal box. With instructions and leads. Size 7½in x 4½in x 2½in ex. switches.

KIT **£7.95*** BUILT AND TESTED **£10.05***

A USEFUL CATALOGUE—FREE

Send us a large S.A.E. with 10p stamp and we will send you back the latest Bi-Pre-Pak catalogue free by return. Packed with useful lines, it's a real money saver.

TERMS OF BUSINESS:

VAT at 12½% must be added to total value of order except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders unless marked otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

Order your Stirling Sound products from

BI-PRE-PAK LTD

Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHERN (0702) 46344

Make cheques/money orders payable to Bi-Pre-Pak Ltd

TO STIRLING SOUND (BI-PRE-PAK LTD), 220/222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send

..... for which I enclose £

Inc. V.A.T.

NAME

ADDRESS

PE6B

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE

1N21	0-17	AF181	0-50	BY213	0-25	OAZ205	0-45	Z8170	0-12
1N23	0-05	AF186	0-45	BY210	0-45	OAZ206	0-45	Z8271	0-20
1N85	0-08	AFZ11	1-15	BYZ11	0-40	OAZ207	0-45	ZT21	0-25
1N263	0-00	ASY26	0-25	BYZ12	0-40	OAZ208	0-40	ZT43	0-25
1N266	0-50	ASY29	0-45	BYZ13	0-42	OAZ209	0-40	ZTX107	0-12
1N645	0-16	ASY36	0-25	BYZ15	1-25	OAZ210	0-40	ZTX300	0-13
1N725A	0-20	ASY50	0-20	BYZ16	0-20	OAZ211	0-40	ZTX304	0-24
1N914	0-06	ASY51	0-40	BZY88	0-10	OAZ222	0-45	ZTX500	0-13
1N4007	0-12	ASY53	0-20	C111	0-55	OAZ223	0-45	ZTX503	0-18
18113	0-25	ASY62	0-25	CRS1/05	0-45	OAZ224	0-45	ZTX631	0-25
18202	0-23	ASY66	0-33	CRS1/40	0-65	OAZ241	0-25		
2G371	0-75	ASZ21	1-00	CS4B	1-90	OAZ242	0-15		
2G381	0-22	ASZ23	0-75	CS10B	3-50	OAZ244	0-25		
2G414	0-30	AU104	1-00	DD000	0-15	OAZ246	0-15	7400	0-16
2G417	0-25	AUY10	1-50	DD003	0-15	OAZ290	0-88	7401	0-18
2N404	0-22	BC107	0-14	DD006	0-25	OC16	1-00	7402	0-16
2N697	0-16	BC108	0-13	DD007	0-40	OC16T	1-00	7403	0-16
2N698	0-30	BC109	0-14	DD008	0-38	OC22	1-00	7404	0-26
2N705	0-12	BC113	0-15	GD3	0-33	OC24	1-10	7405	0-22
2N706A	0-12	BC115	0-20	GD4	0-10	OC25	0-40	7407	0-42
2N708	0-15	BC116	0-20	GD5	0-33	OC26	0-40	7408	0-28
2N709	0-40	BC118A	0-23	GD8	0-25	OC28	0-75	7409	0-28
2N1091	0-55	BC119	0-20	GD12	0-10	OC29	0-65	7410	0-16
2N1131	0-25	BC122	0-20	GET102	0-50	OC30	0-40	7411	0-16
2N1132	0-24	BC125	0-68	GET103	0-40	OC33	0-75	7412	0-80
2N1302	0-18	BC126	0-65	GET113	0-35	OC36	0-60	7413	0-86
2N1303	0-18	BC129	0-18	GET114	0-30	OC41	0-35	7416	0-88
2N1304	0-28	BC140	0-55	GET115	0-90	OC42	0-40	7417	0-86
2N1305	0-22	BC147	0-10	GET116	0-85	OC43	0-70	7420	0-18
2N1306	0-28	BC149	0-10	GET120	0-50	OC44	0-20	7422	0-25
2N1307	0-28	BC157	0-14	GET872	0-30	OC44M	0-17	7423	0-30
2N1308	0-28	BC158	0-12	GET880	0-60	OC45	0-40	7425	0-87
2N2148	0-60	BC160	0-63	GET881	0-25	OC45M	0-18	7427	0-87
2N2160	0-78	BC169	0-14	GET882	0-35	OC57	0-60	7428	0-40
2N2218	0-23	BCY31	0-45	GET885	0-40	OC58	0-60	7432	0-87
2N2219	0-25	BCY32	0-85	GEX44	0-08	OC59	0-60	7433	0-30
2N2369A	0-16	BCY33	0-38	GEX45/1	0-25	OC66	0-50	7437	0-87
2N2444	1-99	BCY34	0-45	GEX941	0-45	OC71	2-25	7440	0-22
2N2613	0-75	BCY36	1-00	GJ4M	0-50	OC72	0-25	7441AN	0-82
2N2646	0-50	BCY39	1-50	GJ5M	0-25	OC73	0-50	7442	0-79
2N2904	0-20	BCY40	0-80	GJ7M	0-25	OC74	0-30	7450	0-18
2N2906	0-20	BCY42	0-18	HG1005	0-50	OC75	0-30	7451	0-16
2N2907	0-23	BCY70	0-18	HG1009	0-20	OC76	0-30	7453	0-16
2N2924	0-13	BCY71	0-22	MAT100	0-20	OC77	0-50	7454	0-18
2N2925	0-15	BCZ10	0-80	MAT101	0-25	OC78	0-25	7460	0-16
2N2926	0-12	BD121	1-00	MAT120	0-20	OC79	0-30	7470	0-88
2N3054	0-48	BD123	1-00	MAT121	0-25	OC81	0-29	7472	0-88
2N3055	0-65	BD124	0-65	MJE340	0-47	OC81M	0-20	7473	0-42
2N3702	0-11	BFY11	0-10	MJE250	0-63	OC82	0-25	7474	0-48
2N3705	0-15	BF115	0-20	MJE2955	1-27	OC81DM	0-18	7475	0-69
2N3706	0-11	BF167	0-25	MJE3055	0-77	OC81Z	0-45	7476	0-45
2N3707	0-13	BF173	0-28	MFF102	0-40	OC82D	0-25	7480	0-60
2N3709	0-10	BF181	0-35	MFF103	0-36	OC83	0-60	7482	0-87
2N3710	0-11	BF184	0-22	MFF104	0-35	OC84	0-30	7483	1-10
2N3711	0-11	BF185	0-22	MFF105	0-36	OC114	0-38	7484	1-00
2N3819	0-38	BF186	0-22	NKT128	0-45	OC122	1-00	7490	0-55
2N4289	0-30	BF195	0-13	NKT129	0-20	OC123	1-10	7491	1-00
2N4927	0-53	BF196	0-15	NKT211	0-25	OC139	0-75	7492	0-70
2N3083	0-33	BF197	0-15	NKT212	0-25	OC140	1-14	7493	0-70
2N3091	0-59	BF861	0-25	NKT214	0-24	OC141	0-80	7494	0-80
28304	1-15	BF898	0-25	NKT216	0-40	OC169	0-20	7495	0-80
28501	0-75	BFX19	0-28	NKT217	0-45	OC170	0-30	7496	0-85
28703	1-00	BFX13	0-28	NKT218	0-45	OC171	0-30	7497	1-87
40250	0-84	BFX29	0-28	NKT219	0-38	OC200	1-00	74100	0-89
40251	0-81	BFX30	0-28	NKT220	0-30	OC201	1-50	74101	0-87
AA1129	0-50	BFX35	0-98	NKT224	0-25	OC202	1-50	74107	0-46
AAZ12	0-75	BFX63	0-50	NKT251	0-24	OC203	1-25	74110	0-58
AAZ13	0-12	BFX68	0-25	NKT271	0-20	OC204	1-50	74111	0-86
AAZ17	0-13	BFX84	0-25	NKT272	0-20	OC205	1-75	74118	0-90
AC107	0-51	BFX85	0-28	NKT373	0-20	OC206	1-10	74119	1-68
AC126	0-25	BFX86	0-25	NKT375	0-20	OC207	1-00	74121	0-50
AC127	0-25	BFX87	0-25	NKT378	0-25	OC208	1-00	74122	0-70
AC128	0-25	BFX88	0-24	NKT277	0-20	OC460	0-20	74123	1-00
AC187	0-21	BFY10	0-50	NKT278	0-25	OC470	0-30	74141	0-80
AC188	0-20	BFY11	0-50	NKT301	1-00	OC71	1-20	74145	1-26
ACY17	0-75	BFY17	0-40	NKT304	1-00	ORP12	0-60	74151	1-00
ACY18	0-35	BFY18	0-45	NKT403	1-00	ORP60	0-65	74154	2-00
ACY19	0-35	BFY19	0-45	NKT494	1-00	ORP61	0-48	74155	1-00
ACY20	0-35	BFY24	1-00	NKT678	0-30	SX68	0-20	74156	1-00
ACY21	0-35	BFY24	1-00	NKT713	0-30	SX691	0-45	74157	0-95
ACY22	0-35	BFY30	0-21	NKT773	0-25	SX635	0-55	74170	2-52
ACY27	0-25	BFY51	0-20	OA5	0-72	SX640	0-75	74174	1-57
ACY28	0-25	BFY52	0-20	OA6	0-12	SX641	0-75	74175	1-28
ACY29	0-25	BFY53	0-17	OA7	0-08	SX642	0-60	74176	1-28
ACY38	0-78	BFY64	0-30	OA71	0-20	SX645	0-85	74190	2-00
ACY40	0-22	BFY90	0-81	OA73	0-15	TIC44	0-29	74191	2-00
ACY44	0-22	BR100	0-40	OA74	0-15	V15/30P	0-75	74192	2-00
AD140	0-50	BSX27	0-50	OA79	0-10	V30/201P	0-75	74193	2-00
AD149	0-75	BSX60	0-98	OA81	0-18	V60/201P	0-75	74194	1-20
AD161	0-44	BSX76	0-18	OA85	0-15	V60/201P	0-75	74195	1-10
AD162	0-44	BSY26	0-17	OA86	0-15	XA101	0-10	74196	1-20
AF106	0-30	BSY27	0-20	OA90	0-07	XA102	0-18	74198	2-77
AF114	0-25	BSY31	0-10	OA91	0-07	XA151	0-15	74199	2-52
AF115	0-25	BSY95A	0-12	OA95	0-07	XA152	0-15		
AF116	0-25	BSY95	0-12	OA200	0-08	XA161	0-25		
AF117	0-24	BT102/300R	0-75	OA202	0-08	XA162	0-25		
AF118	0-57			OA210	0-20	XB101	0-43		
AF119	0-20	BTY42	0-92	OA211	0-35	XB102	0-30		
AF124	0-30	BTY79/100R	0-75	OA2200	0-50	XB103	0-35		
AF126	0-30	HTV79/400R	0-75	OAZ201	0-45	XB110	0-30		
AF127	0-30			OAZ202	0-45	XB113	0-30		
AF139	0-41	BY100	0-27	OAZ203	0-45	XB121	0-43		
AF178	0-55	BY126	0-14	OAZ204	0-45				
AF179	0-65	BY127	0-12						
AF180	0-55	BY182	0-85						

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only • Tel. 01-677 2424-7
Quotations for any types not listed.
Post and Packing 12p per order.
V.A.T. Plastic Transistors 12½%. Metal Can Transistors 8%. Integrated Circuits 8%.


Prices correct when going to press.

CLEARANCE OFFER!

PANEL METERS

AT GREATLY REDUCED PRICES
BAKELITE PANEL METERS—MODEL MR65

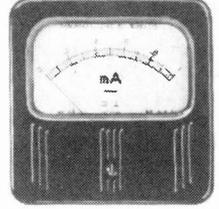Dimensions: Front 80mm x 80mm square
Panel Hole: 65mm diameter
Accuracy ± 2.5%




RANGES

100µA	5A d.c.	50V a.c.*
500µA	10A d.c.	150V a.c.*
50-0-50µA	15A d.c.	300V a.c.*
100-0-100µA	30A d.c.	300V a.c.*
500-0-500µA	50A d.c.	1A a.c.*
1mA	5V d.c.	5A a.c.*
1-0-1mA	10V d.c.	10A a.c.*
5mA	15V d.c.	20A a.c.*
10mA	20V d.c.	30A a.c.*
50mA	50V d.c.	50A a.c.*
100mA	150V d.c.	500mA a.c.
500mA	300V d.c.	50V a.c.
1A d.c.	30V a.c.*	100mV d.c.
2A d.c.		

£2.95 each
25µA 50µA 100µA VU Meter P. & P. + ins. 15p
£3.95 each £3.25 each £3.40 each

*Moving iron (all others are moving coil)

CLEAR PLASTIC PANEL METERS—MODEL MR85P

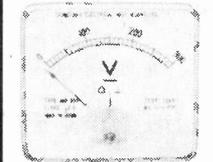

Dimensions: Front 110mm x 120mm wide
Panel Hole: 85mm
Accuracy ± 2.5%

RANGES

50µA	10mA	50V d.c.
100µA	50mA	150V d.c.
200µA	100mA	300V d.c.
500µA	500mA	15V d.c.
100-0-100µA	1A d.c.	300V a.c.
500-0-500µA	5A d.c.	1A a.c.*
1mA	15A d.c.	5A a.c.*
1-0-1mA	30A d.c.	10A a.c.*
5mA	10V d.c.	20A a.c.*
	20V d.c.	30A a.c.*

£3.95 each
S Meter 1mA £4.55 each VU Meter £4.55 each P. & P. + ins. 15p

*Moving iron (all others are moving coil)

EDUCATIONAL METERS—MODEL ED107

High quality moving coil meters ideal for school use and many other applications. Housed in strong black plastic cases. Clear view front. 3in mirror scale. Fully insulated terminals will accept either spade or 4mm plug. Dimensions: 100mm wide x 90mm deep x 105mm high overall. Accuracy ± 2%

METER CIRCUIT BOARD


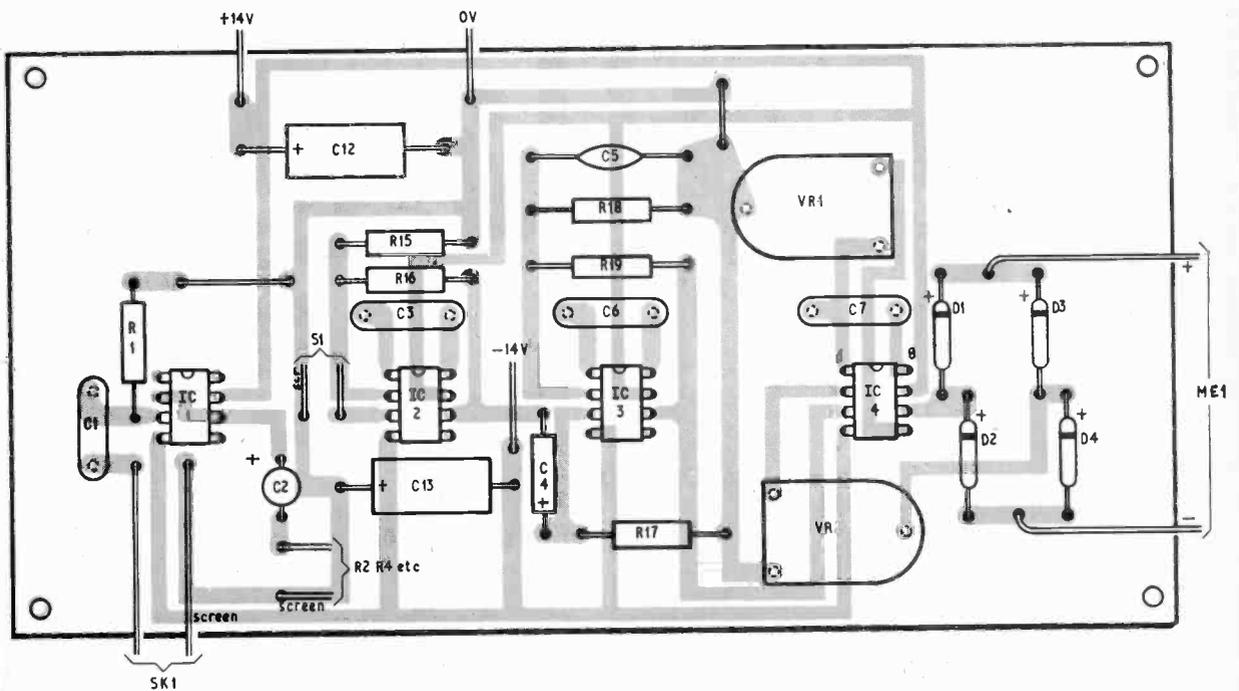
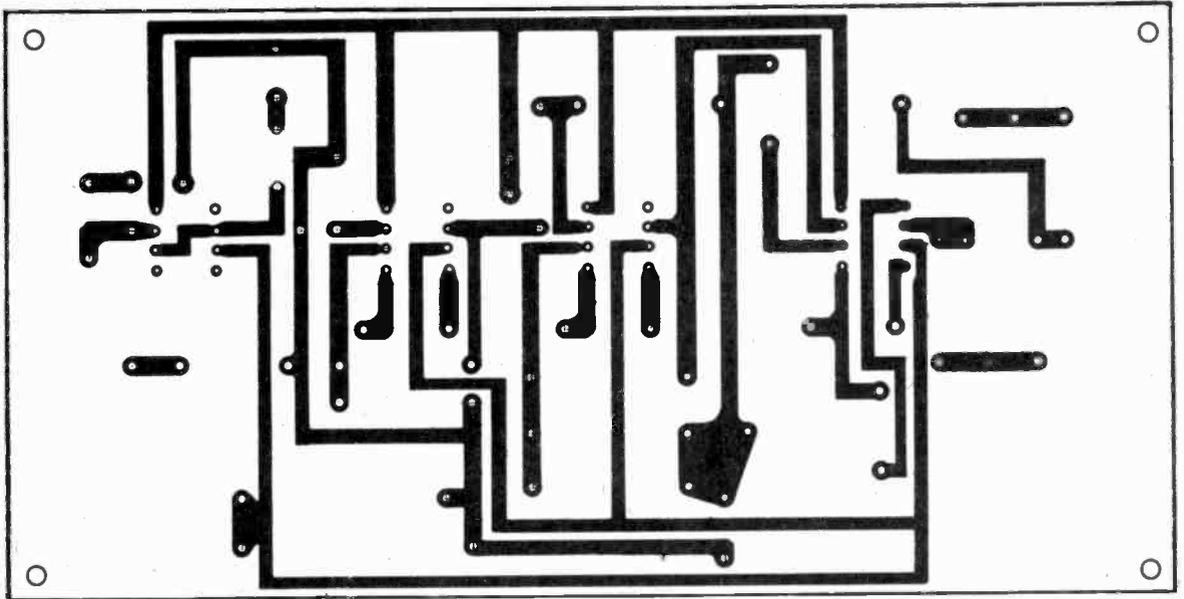


Fig. 4. Component layout and p.c.b. master for main board

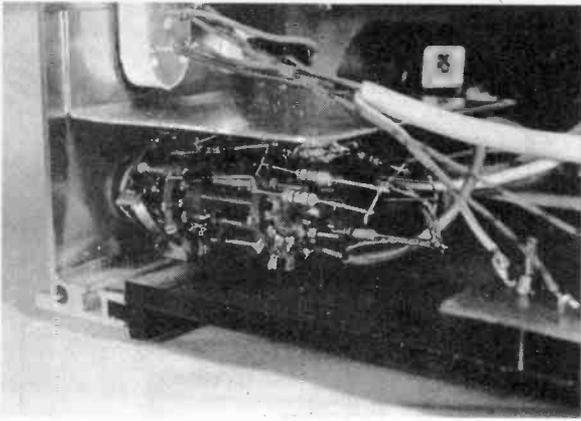

The input socket screen and attenuator resistors mounted on the selector switch

Any case which will comfortably accommodate the components can be used to house the unit, with the one proviso that it must be constructed of metal. The prototype is constructed in a "Swift Half Rack Width" case, and this can be obtained from West Hyde Developments Ltd.

CONSTRUCTION

Mechanically construction is quite straight forward, and the general layout of the prototype can be ascertained by reference to the accompanying photographs. It is strongly recommended that this layout is adhered to, as the circuit is very sensitive and stray pick-up of mains hum is the likely result of a careless layout.

An L-shaped 20 s.w.g. aluminium screen is used to isolate the attenuator unit and input socket from the mains wiring around the on/off switch. The screen is secured to the front panel by, in effect, being bolted to the panel using S2 and LP1. The large cutout for the meter can be made using a fretsaw.

The attenuator resistors and R3 are wired up on S1, the upper set of resistors (R2, R4, etc.) being mounted

POWER SUPPLY BOARD


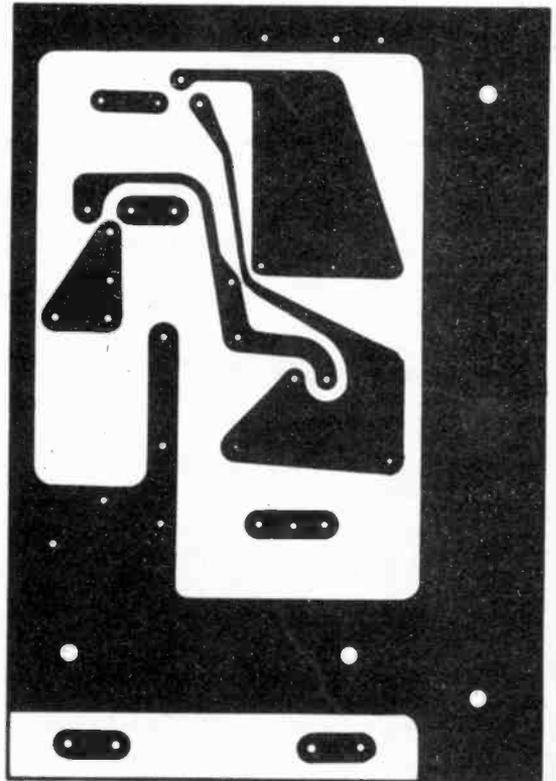
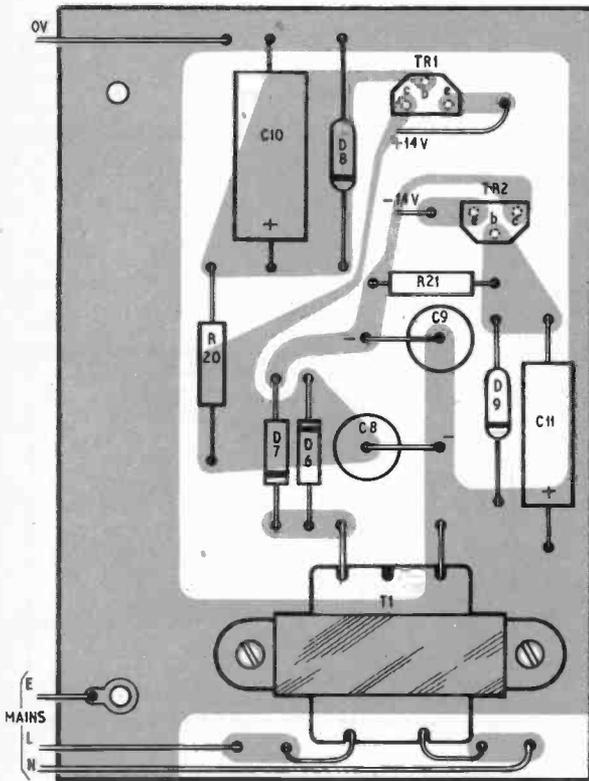


Fig. 5. Details of power supply p.c.b.

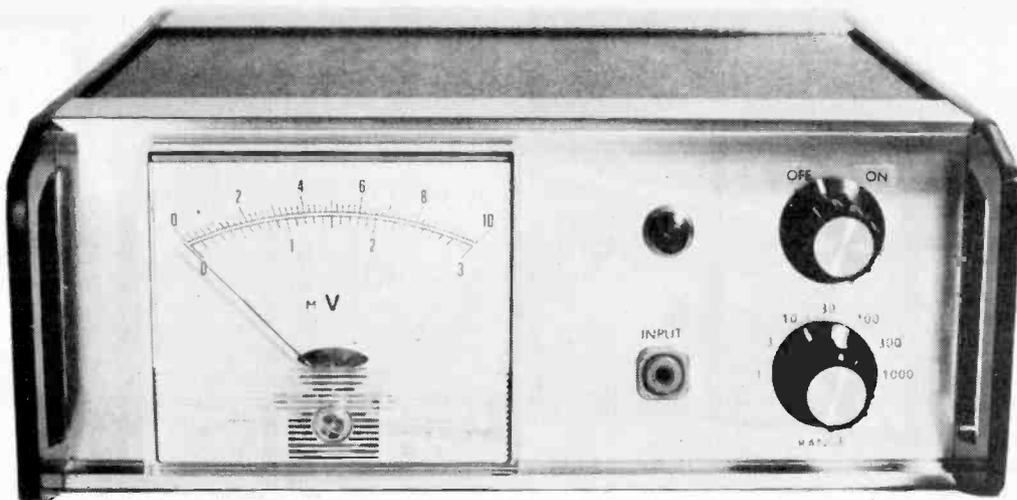

Front of the Audio Millivoltmeter showing the range switch and input socket

on the front wafer, and the lower set (R3, R5, etc.) being mounted on the rear one. This is not quite as simple as it may at first appear, as there is not a great deal of space for the resistors and their leads must be cut quite short. The resistors are wired up before the switch is mounted.

The main circuitry is contained on two printed circuit boards, one for the meter circuitry and the other for the p.s.u. The etching patterns and component layouts of these boards appear in Figs. 4 and 5 respectively. These have been kept as simple as possible and it should not be too difficult for the average constructor to produce his own p.c.b.s. It is not recommended that any other form of construction should be tried.

Veropins are used where leads will connect to the boards, so that when the boards have been mounted it will be a simple matter to wire up the unit. The two p.c.b.s. should be mounted as far apart as possible. Screened leads must be used at the three places specified in Fig. 4.

D5 is wired directly across the meter terminals.


CALIBRATION

Before switching on the finished unit, set VR1 and VR2 with their sliders at approximately the centres of their tracks and check that the meter is properly zeroed. Upon turning on, the meter should give a small positive indication, and VR1 is then used to zero the meter again.

For calibration an audio tone of around 250Hz to 2kHz with an amplitude between about 1mV and 1V r.m.s. is required. The precise amplitude of this signal must be known. Most signal generators have a calibrated output, but this can only be relied upon for a high degree of accuracy on the more expensive generators.

To calibrate the unit using such a signal generator it is merely necessary to set it for an output level which is the same as one of the full scale sensitivities of the millivoltmeter. With the millivoltmeter switched to the appropriate range it is then connected to the output of the signal generator. VR2 is then adjusted to give full scale deflection of the meter.

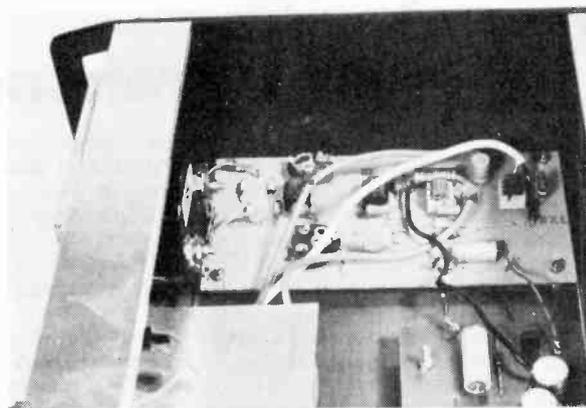It is possible to use a less sophisticated signal generator as a signal source, but in the interests of



Interior of the unit showing position and interwiring of boards

accuracy it is advisable to measure the output rather than rely upon the calibration of the generator.


For the average constructor the most practical method of calibrating the millivoltmeter is probably to use an ordinary multimeter set to a low a.c. volts range to enable the generator's output level to be accurately measured and set at 1V r.m.s. The millivoltmeter can then be measured on the 1V range.

One should aim to obtain a calibration signal which has its amplitude set with the highest possible accuracy, and great care should be taken to adjust VR2 with great precision since the accuracy of the finished unit largely depends upon these two factors.

INPUT IMPEDANCE

An input impedance of $1M\Omega$ should be more than adequate for virtually all tests, but if for some reason an increased input impedance should be required, this can be accomplished by merely increasing the value of R1 (up to a maximum of about $10M\Omega$).

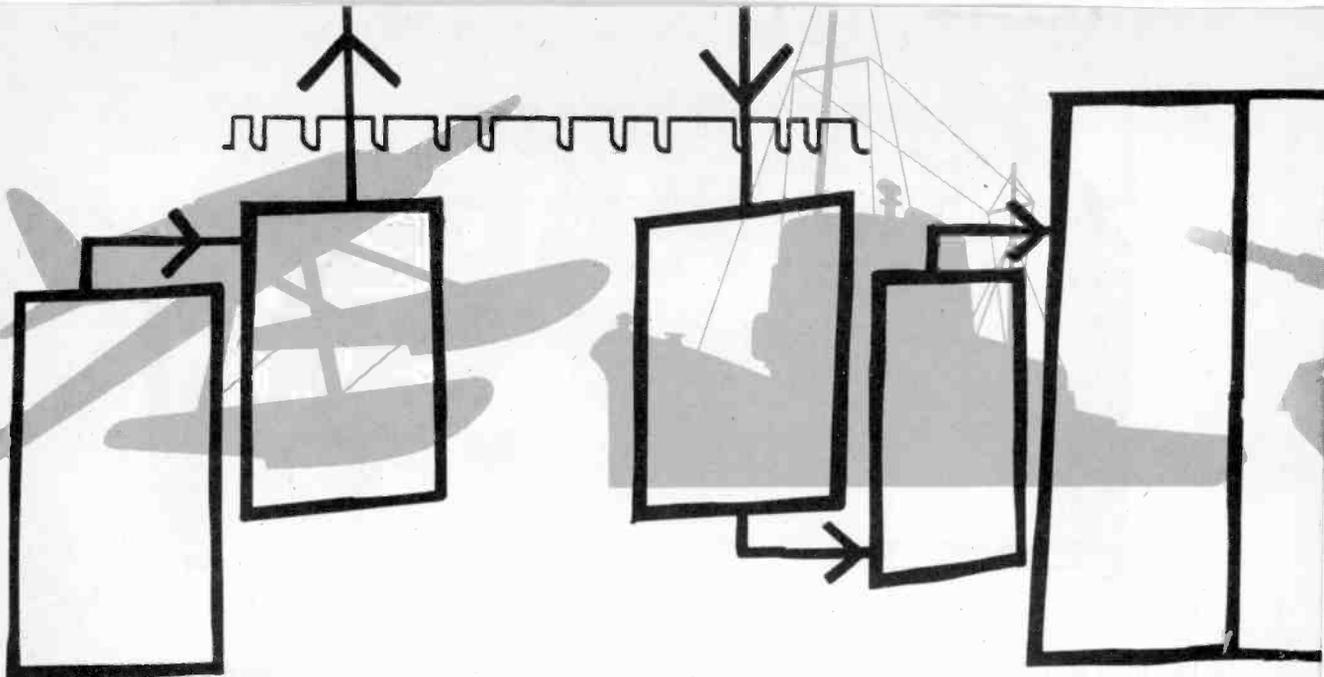Note, however, that increasing the input impedance also increases the risk of stray pick-up, and means that very careful screening of the input leads and circuitry would then be required. ★



PART 1 Transmitter and Coder

THIS series of articles describes the design and construction of a 9-channel radio control system, which operates at 27MHz, and has the option on each channel of either fully proportional control or on/off type switched control. All aspects of the system are covered: transmitter, receiver, coder, decoder, relay-drive and servo-drive. A block diagram is given in Fig. 1.

The system operates on a time-division multiplex principle whereby the outputs of each of the channels are scanned one after the other to form a pulse train of 9 comand pulses of varying length. These are

then followed by a sync pulse, the whole scan taking approximately 20ms. The proportional information is contained in the length of the pulse of each respective channel. In the case of the purely switching channels a pulse-width comparator is used to provide the on/off information, a short pulse denoting on, a long pulse: off.

At the receiver the pulses are first shaped and converted to t.t.l. operating levels, and then routed to the appropriate channels. A servo-system then controls a motor unit which provides the final mechanical output.

- ★ *9 Independent Channels*
- ★ *Fully Proportional Design*
- ★ *Option of Proportional or Relay Output On Each Channel*
- ★ *Suitable Servo System Included*

THE COMPLETE SYSTEM

Proportional RADIO CONTROL SYSTEM

By D. J. WHITELEY

The author has had a similar system operating in a model boat for some two years and finds it to be compatible with commercial equipment costing around £150.

The system will be described together with full constructional details section by section, commencing with the transmitter and coder.

CODER

The coder circuit diagram is shown in Fig. 2. This generates a repeating pulse train of a 0.5ms sync pulse followed by the 9 command pulses of widths set between 1-2ms depending on the setting of the resistors VR1-6 and R3-5, the sync pulse is sampled approximately every 20ms. This forms the basis of the coder, having 9 channels, each potentially fully proportional.

Transistors TR1-3 are connected as an astable multivibrator, the base of TR2 being connected to the open-collector outputs of the b.c.d. decoder IC2 via the control resistors (either potentiometers or

fixed resistors with switches across them). The discharge-time of C2 will therefore be determined by the setting of the potentiometers, the channel chosen being determined by the decoder. The decoder receives its b.c.d. input from the 7490 decade counter which in turn is clocked by the other "half" of the astable TR2/3. This half generates fixed duration spaces of shorter length (0.25ms).

When the count 0000 appears at the output of the counter a sync pulse is generated of approximately 0.5ms. At the receiver this is then detected and used to synchronise the receiver counter, thus allowing the command pulses to be routed to their respective channels.

An output is taken from the collector of TR3 to the modulator input of the transmitter.

CHANNEL OPTIONS

The circuit given for the coder shows 6 proportional channels and 3 switched. Any channel can be either proportional or switched, depending on

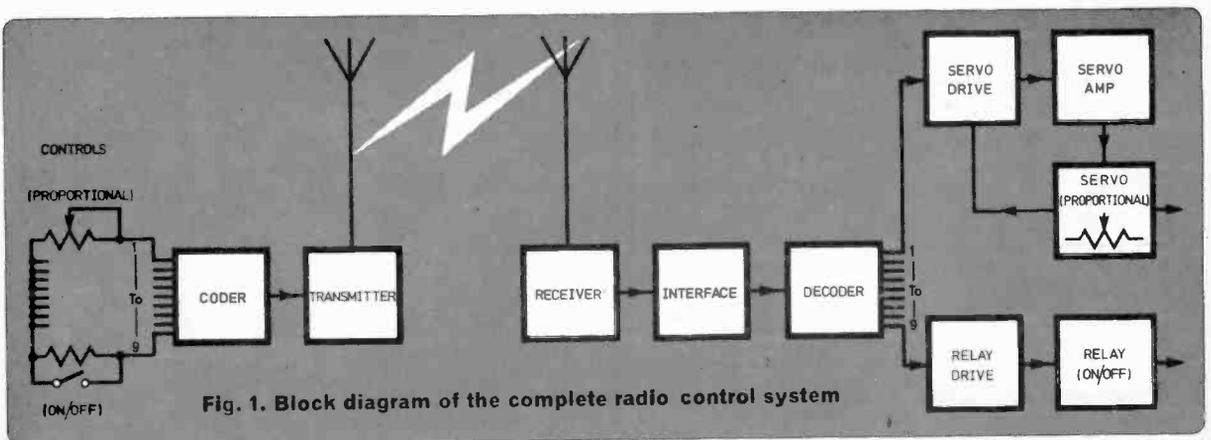


Fig. 1. Block diagram of the complete radio control system

CODER

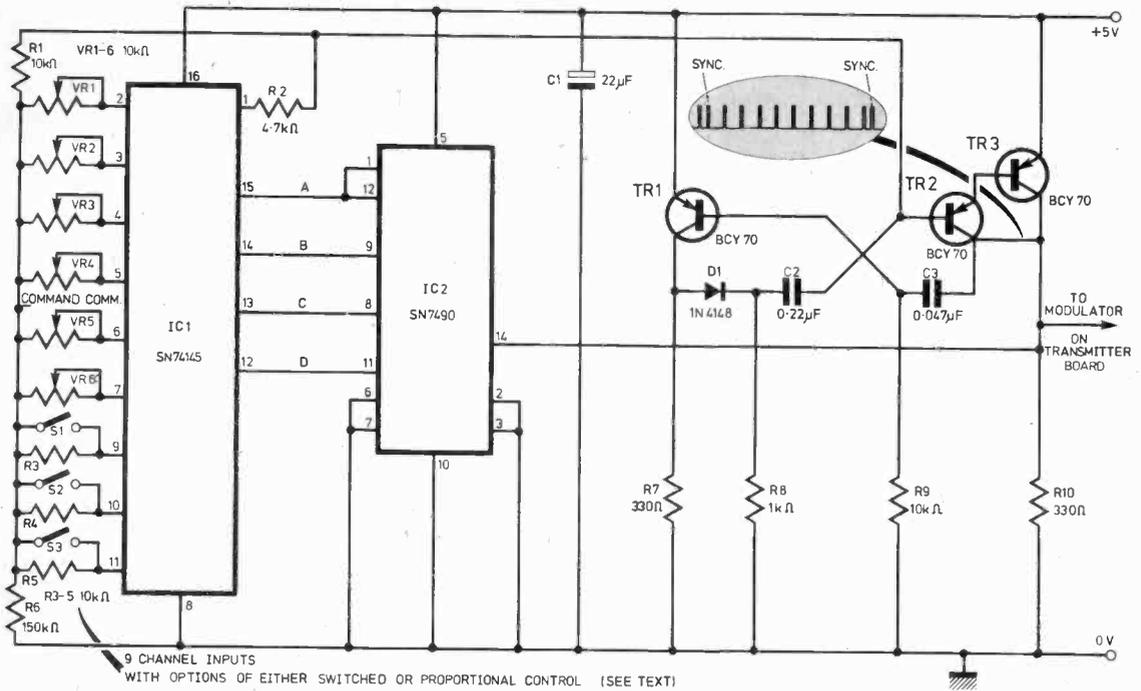


Fig. 2. Circuit diagram of the Coder

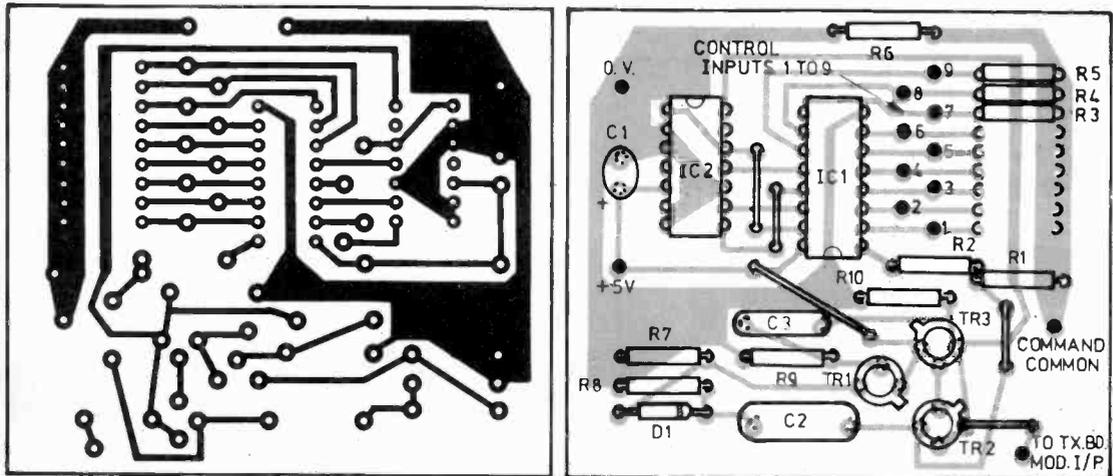


Fig. 3. Printed circuit master and component layout details for the Coder (full size)

TRANSMITTER

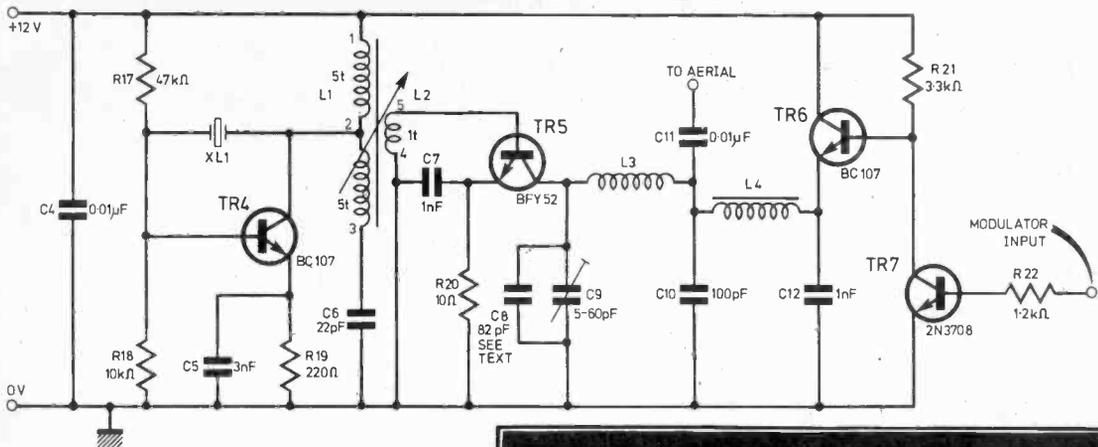


Fig. 5. Circuit diagram of the Transmitter

Fig. 6. Full size printed circuit master and component board layout for the transmitter. For coil details see text

COMPONENTS . . .

TRANSMITTER

Resistors

- R17 47kΩ
- R18 10kΩ
- R19 220Ω
- R20 10Ω
- R21 3.3kΩ
- R22 1.2kΩ

All resistors $\frac{1}{8}$ W 5%

Capacitors

- C4 0.01μF disc ceramic
- C5 0.003μF disc ceramic
- C6 22pF ceramic
- C7 1000pF ceramic
- C8 82pF ceramic
- C9 5/60pF trimmer (p.c.b. mounted type)
- C10 100pF ceramic
- C11 0.01μF ceramic
- C12 1000pF

Transistors



- TR4 BC107B
- TR5 BFY52
- TR6 BC107B
- TR7 2N3708

Crystal

- XL1 Crystal of the range 26.995–27.245MHz (to match with receiver crystal). These are sold in pairs.

Miscellaneous

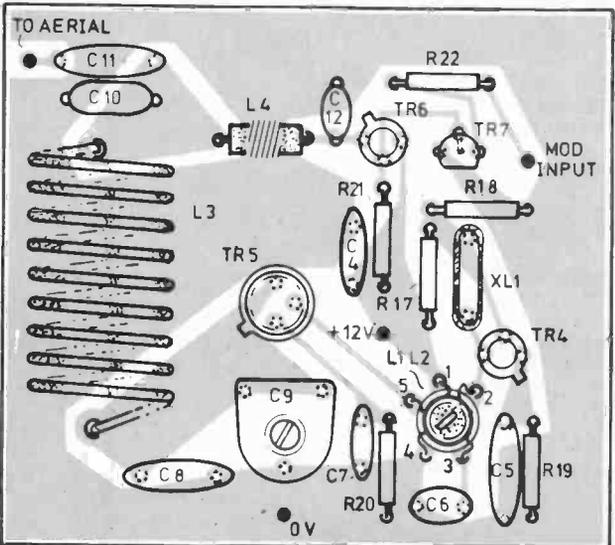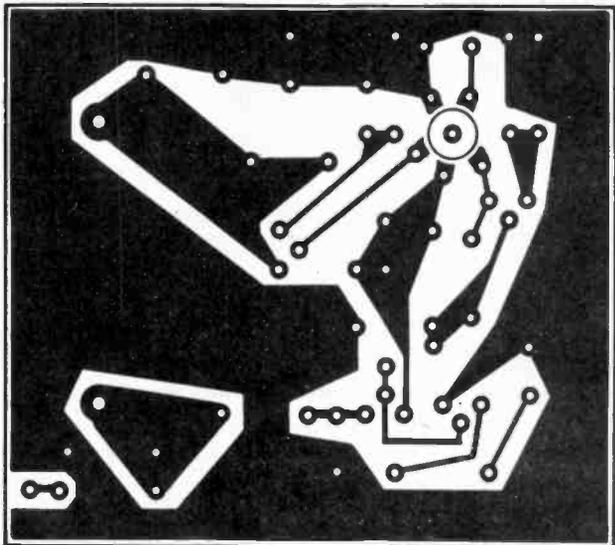- P.C.B. (70mm × 83mm) and etchant
- Circuit board pins
- 7mm Aladdin coil former
- Enamelled copper wire: 14 and 30 s.w.g.
- R.F. choke (L4) 20 to 40μH



SETTING UP

If an oscilloscope is available the output to the modulator can be viewed showing the inverted pulse train with the 0.25ms spaces at the top. When a command is operated, the corresponding pulse will reduce in width from 2ms to 1ms causing the pulse train to contract. The current drawn will be about 65mA at a supply of 5V, if a higher current than this is observed then the circuit must be checked again.

TRANSMITTER

The transmitter follows the design of a medium power 27MHz crystal controlled and t.t.l. modulated piece of equipment. The modulation is applied to a depth of 100 per cent on the r.f. carrier. From the circuit (Fig. 5) it will be seen that TR4 and the overtone crystal form the oscillator with L1 tuned to resonance.

The base of TR5 is coupled to the oscillator by L2, the collector is tuned by L3, C9, C12 to match the aerial loading. An r.f. choke prevents the r.f. from reaching the modulator stage TR6, TR7. The action of the modulator is that of a switch with TR6 turned hard on by R21, taking the base to the positive rail, and with TR5 connected to its emitter network r.f. is fed to the aerial. When TR7 base is driven positive by an incoming pulse, the base of TR6 is brought down, hence cutting off the transistor and switching off the output.

CONSTRUCTION AND COIL DETAILS

From the full size p.c.b. design shown in Fig. 6 a printed circuit board can be made. A hole is drilled in the board to accommodate a 7mm coil former on to which is wound L1/L2. L1 is a 10 turn centre tapped winding of 30 s.w.g. enamelled covered copper wire close wound with L2 a single turn of the same gauge wire on top of L1 at the positive end. L3 is an open winding consisting of 9 turns of 14 s.w.g. copper wire of 16mm inside diameter and the windings arranged to cover a length of 38mm.

SETTING UP THE TRANSMITTER

Before connecting the 12V supply, bring the core of L1/L2 to the top of the former and adjust C8 to minimum. Connect a voltmeter of about 3V f.s.d. across R20 then switch on the supply. Adjust the core L1/L2 for maximum reading on the voltmeter indicating that the oscillator is running, then adjust C8 to obtain a peak reading on the meter. Final tuning is best carried out when the equipment is housed and an aerial of 1m is connected, also the oscillator must be netted to the receiver in which case the "S-meter" connection can be used on the receiver and optimum power achieved. This is the method adopted by the author and is very fast and straightforward, providing the aerial is first removed from the receiver and a suitable distance separates the two pieces of equipment to allow a peak reading to be obtained. An ammeter connected to the supply should indicate a current of about 40mA when tuning is correct.

Acknowledgement: The coder, decoder, servo driver and servo amplifier used in this system are based on designs by M. F. Bessant and originally published in Wireless World.

Next month: the receiver, interface and decoder circuits will be described.

NEWS BRIEFS

Army on the Air

THE Ministry of Defence is to buy a unique mobile sound broadcasting facility which will enable the British Army deployed anywhere in the world to provide a local radio service of general interest and current news.

Under the terms of a £180,000 contract Marconi Communication Systems Limited is to supply two medium wave sound broadcasting transmitters, together with studio equipment, h.f. receivers, antenna arrays, a demountable mast, an aerial tuning unit and a range of associated test equipment for this facility. All of this equipment is to be mounted in two Army containers so that the resultant 'station' can be quickly air transported by Support Command to any destination and brought into operation at short notice.

One of the containers for the new facility will be fitted with two sound broadcast transmitters providing a full 2kW of power.

The second container will function as the sound broadcasting studio and will be fitted with a twelve channel sound mixer, microphones, disc reproducers, tape recorders and sound monitoring equipment. A separate compartment within this container will mount h.f. receivers operating in space diversity to enable overseas broadcasts to be received and re-transmitted as required. Additional ancillary equipment to provide a complete operational station is also included.

Delivery of this new facility to the Army is scheduled for mid-1977.

SPECIAL CALCULATOR SALE

New Texas Instruments SR56—10 + 2, 9 levels of brackets, 2 looping capabilities, 4 levels of sub-routine, 10 data memory register. £79.95; T.I. SR52. £248. CBM 4190R. Melcor SCP700 10 memory—algebraic programmable—S.A.E. for price. All subject to availability.

SC60 (Realtone)—10-digit mantissa, 2-digit exponent, algebraic logic, 3 user addressable memories which include Sum memory, Sum of Squares memory and Index memory plus index register. It has double bracketing as well as arithmetic mean, norm (sq. rt. of sum of squares) STANDARD deviation, factorial, binomial, co-efficient, permutation, function, normal distribution function, Gamma function, trig functions and their inverse, Logs and anti logs, group operation and group controls, flexible memory control, factor reversal, degree/radian selection, error detection and display. £46 plus £3.68 VAT. Total £49.68.

SC6010 (Realtone)—50 functions, 66 keyboard commands. As SC60 but with 10 memories which allow memory storage for up to 10 intermediate results or 10 constants at the user's option. The extra memories may be used to store a group of variables for repeated processing of the variables. £60 plus £4.80 VAT. Total £64.80.

SC44 (Realtone)—22 functions, 40 keys, 8 digit mantissa, 2 digit exponent, two levels of brackets, algebraic logic works to 10 rounds to 6 trig functions and their inverse, log and anti log, exponentiation (y^x), factorials, pi, ix, x², Vx (sq. rt. of x) degree/radian selection (trig or inverse trig) full feature memory STO, RCL, M+, exchange operation x-y, automatic error detection and display Clearing operation (CA, CE). £30 plus £2.40 VAT. Total £32.40.

All rechargeable with 220 240V adaptors. Size 3 1/2 x 3 1/2 x 1 1/2 in. Weight 330 grams. Realtone Calcs. New—10 + 2 green display cassette power supplier including rechargeable batteries and self-contained battery charger—LC40d. Memory + % green or red display calculators under £10 S.A.E.

S.A.E. for full details of our range. One year warranty. Send to:

KRAMER & CO.

Dept. PE, 9 October Place
Holders Hill Road, London NW4 1EJ
Telex 888941 (attn. Kramer); Tel. 01-203 2473
P. & P. 60p. C.W.O.

'HOW INVENTIVE ARE YOU' COMPETITION



These were your Inventions

FULL LIST OF PRIZE WINNERS



1st PRIZE £250

AWARDED TO

G. G. HUTCHIESON and B. RAY, PLYMOUTH (Group Entry)

for a HIGH INTENSITY BEACON

2nd PRIZE £100

AWARDED TO
S. CROFT, HITCHIN, HERTS.

for a PORTABLE
HEART START

WELL, you can now see the ideas which won prizes in our *How inventive are you?* competition. The entries submitted covered a very wide range of concepts so, it is not surprising that the major prize winning ideas were drawn from widely differing applications.

Our first prize goes to a High Intensity Beacon. The general idea on which this is based was the subject of several entries. Having established the principle that this idea was a potential prizewinner (based on the following facts: (1) the portable ignitor circuit can be modified very simply to drive a Xenon flash tube, so the technology is known; (2) market potential for a flashing warning beacon is good, so it is not difficult to generate a substantial list of applications in a wide range of market areas; and (3) the product could be manufactured at a cost which would be economically viable) the main problem for the judges was then to decide which particular entry or entries in this group had the greatest merit. The decision was in part based on the presentation of the entries (clarity of description and diagrams) and in part on the technical merit (use of minimum number of components, choice of component values, detailed circuit design, etc).

The eventual winner was the unanimous choice of the judges. This was a group entry so the prize money is shared equally between G. G. Hutchieson and B. Ray.

3rd PRIZE £50

AWARDED TO
R. CURRY, NEWTON AYCLIFFE,
CO. DURHAM

for a ALPHA/BETA
PARTICLE DETECTOR

RUNNERS-UP

The following 25 readers each receive a MAGISPARK GAS IGNITOR

A. R. Knight, Oxford	<i>Neon Ornament Circuit</i>
R. F. Fletcher, Lowestoft, Suffolk	<i>Neon Light Flasher</i>
G. Rochfort, Lymington, Hants.	<i>Distress Beacon</i>
A. Curry, Newton Aycliffe, Co. Durham	<i>H.V. Source For Physics Experiments</i>
D. W. Lloyd, Potton, Beds.	<i>Flasher Warning Buoy at Sea</i>
T. V. Mayhew, Poole, Dorset	<i>Flashing Beacon</i>
Q. A. Rice, Mitcham, Surrey	<i>Distress Signal</i>
R. Atkinson, Slaithwaite, Huddersfield	<i>Electric Fencer Unit</i>
R. Robertson, Chorley, Lancs.	<i>Muscle Stimulator</i>
B. Simpson, Mexborough, Yorks.	<i>Paraffin Heater Ignitor</i>
G. E. Dunning, Morden, Surrey	<i>Vacuum Leak Detector</i>
P. Smith, Barnsley, Yorks.	<i>Gas Detector</i>
J. P. Wilkinson, Alford, Lincolnshire	<i>Engine Combustion Improver</i>
R. W. Bleach, Durlieght, Somerset	<i>Plastic Weld Tester</i>
E. Jones, Corfe Mullen, Dorset	<i>Safety Tester</i>
G. T. Theasley, Riddlesden, West Yorks.	<i>Car Plug Tester</i>
J. A. Logue, Clondalkin, Ireland	<i>Spark Plug Tester</i>
M. J. B. Franklin, Eaglescliffe, Cleveland	<i>Fly Killer</i>
M. G. Wadlow, Ealing, W.5	<i>Electronic Record Cleaner</i>
G. S. Foreman, Denton, Sussex	<i>Multipurpose Welding Torch Lighter</i>
E. A. Ferrand, Fareham, Hants.	<i>Spark Plug Tester</i>
M. Woodman, Seaton, Cumbria	<i>Safe Ignitor for Chemical Apparatus</i>
C. Wolfe, Cambridge	<i>Paper Tape Puncher</i>
T. C. E. Probert, Penarth, Glamorgan	<i>Telephone Ringer</i>
H. V. Morris, Birmingham, 8	<i>Anti-Static Device</i>

The second prize—a Portable Heart Start—was a unique entry and proposed a kind of application Plessey had not themselves previously considered. Because of this it scored very highly on novelty alone, apart from the excellent and commendable social connotations behind the idea. Evaluation of the Heart Start idea required discussion and correspondence with authorities from the medical and medical electronics fields. Great concern was expressed over the use of such a device by people not fully instructed in its operation and although the entry was well detailed it was obvious that considerable further development would be required before the idea could be demonstrably effective, safe and viable. Nevertheless the judges were sufficiently impressed to award this idea the second prize.

The third prize was awarded for an Alpha/Beta Particle Detector. This was selected from a number of ideas for school laboratory or similar applications. The method of operation is very straight forward; for instance, the electrodes of the portable ignitor can be separated to the point at which breakdown just no longer takes place. The passage of beta particles through the air generates ions and if the particle passes within the vicinity of the electrodes ionization causes breakdown across the electrodes. Redesign of the mechanical side of the portable ignitor and some limited modification of the circuitry could provide a simple and cheaper high voltage source which would detect ionising radiation (alpha and beta particles, ultra violet light) and

The following 25 readers each receive a One-Year Subscription to PRACTICAL ELECTRONICS

C. A. Adamson, Osbaldwick, York.	<i>Record Cleaner</i>
G. A. Sergeant, Walton-on-Thames, Surrey	<i>Fluorescent Tube Starter</i>
C. I. Johnston, Malahide, Ireland	<i>Flashing Beacon</i>
P. J. Mann, Ampleforth College, York.	<i>General Purpose EHT Unit</i>
R. W. Whittaker, Bracknell, Berks.	<i>Emergency Beacon</i>
D. Huddart, Melksham, Wilts.	<i>Flashing Beacon</i>
G. M. Rossetti, West Alvington, S. Devon	<i>Emergency Lamp</i>
G. W. Rose, 20 Field-Workshop, R.E.M.E., BF PO 29	<i>Anti-theft Device (for suitcase)</i>
W. V. Legge, Tidworth, Hants.	<i>Touch Switch Electrical Fence</i>
R. Clarke, Clevedon, Avon.	<i>Electrostatic Spray Unit</i>
P. A. Turner, Heywood, Lancs.	<i>Electronic Dial Tester</i>
G. Cliff, Luton	<i>Explosive Gas Indicator</i>
J. G. Ransome, Southmoor, Oxon.	<i>Gas Detector</i>
J. Allesbrook, Stapleford, Notts.	<i>Engine Ignition</i>
W. A. L. Smith, Redhill, Surrey	<i>Car Lubricant Checker</i>
P. F. Walker, West Bridgford, Notts.	<i>Switched Output Insulation Tester</i>
B. A. Barnett, Hall Green, Birmingham	<i>Spark Plug Test</i>
N. J. Goddard, Tilehurst, Reading	<i>Insect Killer</i>
D. H. Dalby, Sholing, Southampton	<i>Anti-Static Device</i>
H. G. Taylor, Newbury, Berks.	<i>Arc Initiator Circuit</i>
C. H. Hughes, Ardley, Oxon.	<i>Animal Goad</i>
J. Grice, Gorleston, Norfolk	<i>Cattle Goad</i>
W. G. Clack, Annalong Newry, Northern Ireland	<i>Weed Killer</i>
K. Drake, Gosford, Staffs.	<i>Electric Organ</i>
G. T. Massey, Stockport, Cheshire	<i>Miniature Ozoniser</i>

flame ionisation, as well as serve as a general purpose high voltage source.

From the subjects included amongst the list of runners-up a good indication can be obtained of the very wide range of ideas proposed by the entrants to the competition. Some were highly original and reflect well on the inventive powers of their proposers.

As already mentioned in the *Initial Report from the Judges* (April 1976) all entries were initially grouped under applications and inevitably it was revealed that two or more, sometimes many, entrants had submitted the same or a very similar kind of idea. The next step was to place all entries of a grouping in some order of merit and then finally to select the winners, including the 50 runners-up. At least one award was made in each application grouping.

Finally, readers will be interested to know that many of the proposed circuits will be published in PRACTICAL ELECTRONICS during forthcoming months. We shall also be keeping readers up to date with the progress of selected ideas towards production and ultimate launch onto the market.

Our first three prizewinners will be given the opportunity to visit Plessey at Titchfield to see the portable ignitor and other products being manufactured.

The Plessey Company join with Practical Electronics in warmly congratulating all winners, and express thanks to all who participated in this really testing form of competition.

SEMICONDUCTOR UPDATE

By R.W. COLES

ZN425E MC14422
VMP-1 MC14423

GET CONVERTED

If you are used to thinking of Digital to Analogue and Analogue to Digital converters as exotic devices available only to a favoured band of professional engineers—then it's time you got converted!

A big breakthrough has been made by Ferranti who have introduced a new bipolar integrated circuit to their c.d.i. family which is about to make A to D and D to A converters about as run-of-the-mill as op-amps and NAND gates.

The new device, type **ZN425E**, contains an 8-bit binary counter, a precision resistor ladder, a set of logic controlled switches and even a 2.5V reference source, all crammed into a 16-pin plastic d.i.l. package with an extremely low price tag.

The **ZN425E** can be arranged to convert analogue voltages into an equivalent 8-bit binary word, or to convert an 8-bit binary word into an equivalent analogue voltage, with the minimum of ancillary components and with a very creditable degree of precision.

The secret of the new chip is its **R2R** resistance ladder which hitherto has been impossible to produce as part of a cheap monolithic circuit because of the close tolerances required of the resistors, traditionally a weak point with monolithic devices.

Don't go on thinking that D to A's and A to D's are only useful if you happen to have a computer, either, a cheap component like the **ZN425E** is ideal for use as a precision ramp generator for oscilloscope or display tube deflection, or as the heart of an analogue readout using the new bar-l.e.d.s.

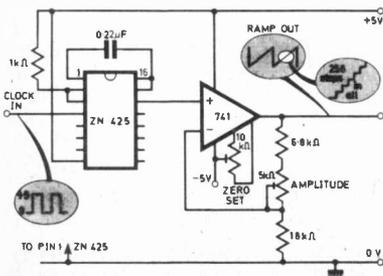


Fig. 1. Linear ramp generator

M.O.S. POWER

M.O.S.F.E.T. technology has always seemed a more reasonable way to conduct one's solid state affairs than the rather more mysterious bipolar approach. It's easy to understand, and one can think in terms of voltage rather than current, and without having to remember which are the minority carriers and which the majority variety either. Of course, it's not possible to turn one's back on BC107's and 2N3055's in the same way that you might have done with triodes and pentodes, because the m.o.s.f.e.t. ensemble still exhibits a few glaring shortcomings.

I suppose everyone knows about the dreaded "Nylon-knickers" effect which strikes down m.o.s.f.e.t.s in their prime when high voltage static charges punch holes in the vanishingly thin gate-oxide, requiring all those who come into contact with such devices to be securely earthed and conservative in their choice of underwear!

Well, cotton knickers you can learn to love, but if your electronic vocabulary includes the words amps or watts then m.o.s.f.e.t.s start to look a bit puny and it certainly seemed until recently as though 2N3055's would continue to kick sand in the faces of their m.o.s. rivals for a long time yet. The remedy for this sad state of affairs is just around the corner however, and it comes not from Charles Atlas but from Siliconix, champions of the underdog, and m.o.s.f.e.t. makers extraordinary who have just introduced a new device, the **VMP-1**, which actually lives in a TO3 can!

Appearances are not deceptive either, the **VMP-1** is a true power device, and although its maximum drain current of 2 amps is low by 2N3055 standards, its traditional m.o.s.f.e.t. characteristics make it extremely attractive.

The **VMP-1** is a 35W device which can switch 1A in 5 nanoseconds and can be driven directly by c.m.o.s. logic gates, all with a complete absence of the thermal-runaway and second-breakdown effects which plague their bipolar cousins. I won't make any promises, but the inherent linearity of the m.o.s.f.e.t. characteristic should make it ideal for high quality audio amplifiers too. And don't lose any sleep over your trendy nether-garments, the **VMP-1** has a Zener gate protection diode!

REMOTE CONTROL

Remote control of t.v. sets, Hi-Fi systems, light dimmers and other electronic home comforts has of course always been possible. Back in the 1950's t.v. sets were often fitted with a socket into which could be plugged a cable type remote control box, but these were not very popular for obvious reasons. Today, with a handful of phase-locked loop chips, a few op-amps and a PP9 or two, it is possible to build a remote control system which requires no cable and which relies on an Acoustic or Infra-Red carrier link for its operation.

Of course there is a problem, phase locked loops are not cheap, and this tends to restrict the control facilities available to the basic essentials. PP9's can set you back a few bob too, and it's all too easy to leave the remote unit switched on so that the batteries run down quickly. The march of electronic progress could not allow this state of affairs to continue for long, and, typically, it is Motorola c.m.o.s. expertise which has come to the rescue in the shape of the new **MC14422** and **MC14423** ultrasonic remote control transmitter chips which appear to offer the ideal solution to this control problem.

The two devices are similar but operate at different frequencies so that both could be used in the same domestic situation without interference. Each can provide no less than 22 separate control channels and include all the logic necessary to encode the correct command from a 22 switch keyboard. The key closures are used to produce a unique sequence of up to five acoustic tones between 34-688KHz and 42-755KHz with an output ready to drive a piezo-electric transducer via a single external transistor and transformer.


Power consumption of the c.m.o.s. circuit is very low, so low in fact that it is not necessary even to use an on-off switch!

With an 8V supply, current drain in the "Idling" condition is typically 0.4μA, which promises almost shelf-life from the batteries used. An n.m.o.s. receiver chip, the **MC6525**, will soon be available to complement the transmitter devices, but I have no data on this at present. The **MC14422** and **MC14423** are packaged in 16 pin d.i.l.'s and cost around £4.

NEXT MONTH!


P.E. DIGISCOPE

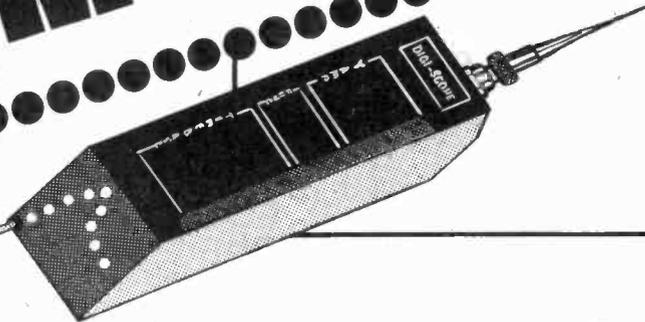An entirely new concept in oscilloscope design which puts many advantages of the traditional instrument into a pint sized package but uses an 8×10 i.e.d. matrix to form a flat screen display




AUTOSTOP for Model Railways...

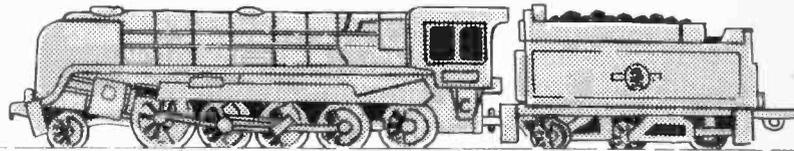A design to halt a model train for a pre-determined time at a station. Needs no external supplies and only two connections to the track



FLUORESCENT LIGHT INVERTER

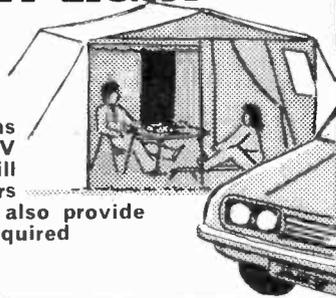Designed to drive a mains fluorescent lamp from a 12V supply this inverter will prove a boon to campers and caravanners and can also provide emergency lighting when required



RADIO CONTROL SYSTEM Part 2

Part two of this series describes the receiver, decoder and t.t.l. interface circuitry

PLEASE NOTE:

It is in your interest to place a firm order with your newsagent in advance. Back numbers are not available, so make sure of your copy now.

PRACTICAL

ELECTRONICS

JULY ISSUE ON SALE JUNE 11, 1976

TO AVOID DISAPPOINTMENT PLACE A REGULAR ORDER WITH YOUR NEWSAGENT — NOW!

INGENUITY UNLIMITED



A selection of readers suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

Please Note
Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

DIGITAL CALENDAR

THIS circuit is useful wherever a 24th-hour pulse is available. The pulse transferred to the input of the day's counter, IC1 and IC2, which can be reset after 28, 30 or 31 days; Mono 1 and OR gate G1, G2 ensure that the counter is reset to a binary count of 1 (i.e. the 1st of the month). The reset pulses are counted by a ÷ 12 counter IC3 which

provides a binary indication of the relevant month, Mono 2 and G3, G4 ensure the counter is reset to a count of 1 (since January is designated month number 1).

The 4-16 line decoder IC5 provides a decimal count of 12 from a binary input, which is used to determine where the day's counter resets. Inverter G7 gives a positive going output during February. G8 will only give an output when all

inputs are at logical one which only occurs on 29th Feb (a transient state). C13 is effectively a NOR gate since output pulse to LOGICALL occurs when logical 0 is applied to either of the inputs) and will reset the day's counter and increment the month's counter via G13. G9, G10 and G13 reset the day's counter after 30 days.

When the input to G9 is April, September, or November G10 of course being enabled by a transient input of 31. In the same way G11, G12 and G13 reset the counter after 31 days during the remaining months.

No facilities for leap years have been included, but since a yearly pulse is available at the output of G5, it would be a relatively simple matter to cater for 29 days in February, with the inclusion of a ÷ 4 counter and a few extra gates!

In the prototype the days were indicated by seven segment displays and their associated decoders. And the months by a binary readout of four lamps, mainly for the purpose of resetting. When resetting it is advisable to take the counters through all of their states to ensure that state 0 does not occur due to random outputs after switch on.

D. E. Clarke,
Colchester,
Essex.

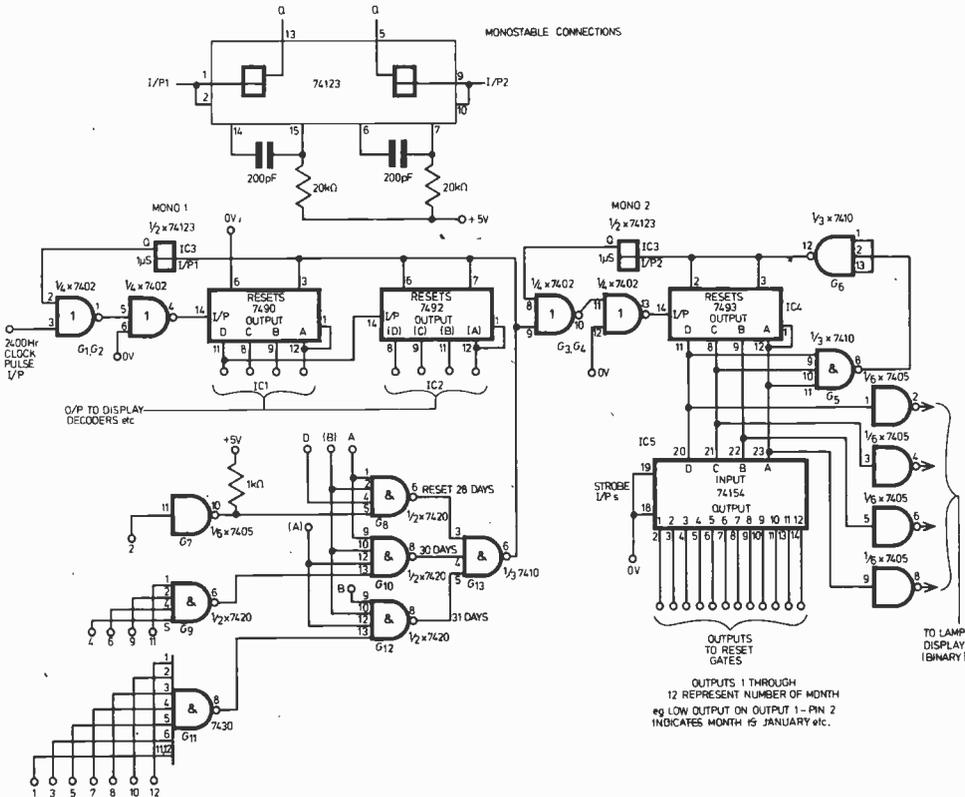


Fig. 1

ELECTRONIC DOORBELL

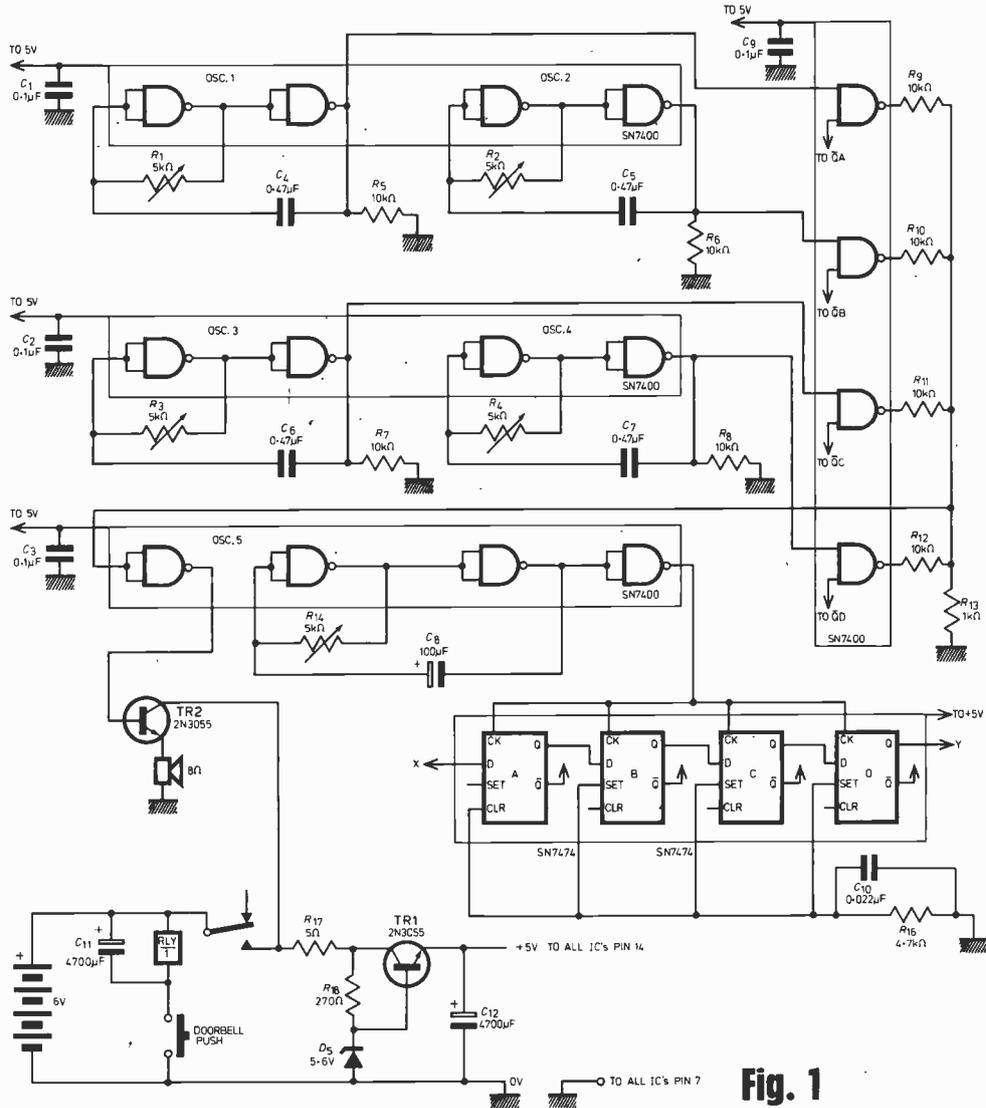


Fig. 1

THE electronic doorbell to be described uses five separate oscillators, one for each note of the tune, and one for the clock generator which governs the speed at which a four-note tune is played. Each oscillator uses two NAND gates, each gate generating the NOT function. These are arranged as shown in Fig. 1.

SN7400 quad dual input NAND gates are employed, and therefore one integrated circuit will form two oscillators. The frequency determining components are chosen to give a wide audio range control by the potentiometers of the note oscillators (1-4), and a rate of 0.5 to 5Hz of the clock oscillator (1).

The oscillators are sequentially switched to the output stage through four NAND gates. This is performed

by another SN7400. Each gate is opened by a gating pulse from a four bit shift register.

Each element of the shift register is a D type flip flop. Two SN7474 dual D type flip flops are used for this. The register is programmed on switch on with the binary number 0111 and the 0 is clocked along the shift register. The outputs from the register are taken from the \bar{Q} or inverted outputs - thus the binary number presented to the gates is 1000. As the 1 is clocked along, it opens each gate in turn. The four outputs from the gates are then mixed by summing resistors. Fig. 2 shows the shift register.

Programming is performed by taking the set or clear inputs to the flip flops to logic 0. If inputs are floating, they are normally high or

at logic 1. At the instant of switch on, C10 passes the switch on pulse and this programs the flip flops.

If X and Y are connected, the 0 clocked along the register will be reinserted at the input and thus the tune will be repeated. If, however, X & Y are left disconnected, the 0 will be lost when it reaches the end of the register. This means that all the gates will be left closed and the tune will only be played once.

The summed outputs from the gates are fed to a buffer which is in fact a spare gate in the SN7400 used for generating clock pulses. This output is connected directly to an emitter follower stage to drive the loudspeaker connected in the emitter of the output transistor.

N. C. Roberts,
Weymouth.

IRREGULAR WAVEFORM PRODUCTION

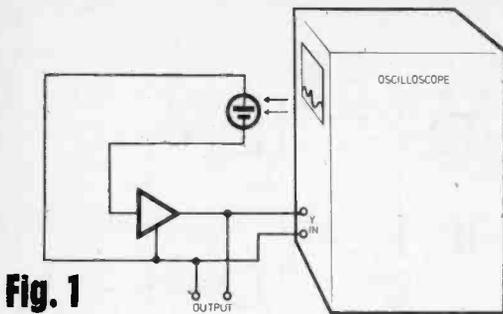


Fig. 1

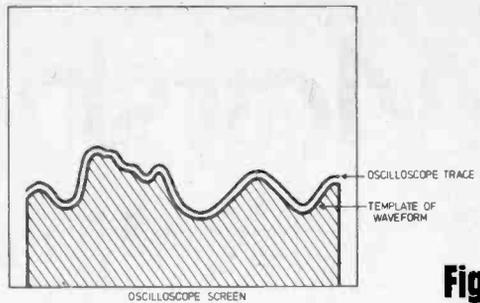


Fig. 2

WITH the use of an oscilloscope, a photovoltaic cell, an amplifier and a suitable template, any reasonably irregular waveform can be produced. The amplified output of the photocell is connected to the Y input of the oscilloscope with polarity such that an increase in illumination causes the oscilloscope trace to dip (Fig. 1). The photocell is placed facing the oscilloscope screen, whose brightness is turned up fully, so that the light from the spot itself causes the spot to dip. If an opaque template of a wave-

form is placed on the screen (Fig. 2), the spot will drop until it is partially obscured by the template, as the illumination of the photocell will then fall. Negative feedback causes the trace to follow the outline of the template closely. The amplifier output will therefore be the waveform of the template. If the waveform of a sound is traced from an oscilloscope screen, a template can be cut to reproduce it. This set-up will work in a dimly lit room. The oscilloscope should have a rapid flyback and short

persistence, and, if it has a graticule, this may be removed in order to fix the template closer to the screen to reduce parallax. The circuit for the amplifier will depend on the photocell and oscilloscope used; linearity is not essential if the gain is high enough, but the response must be fast enough for the time base frequency used for very low frequencies, an I.D.R. with a resistor and battery may be used in place of the photocell.

J. Samson,
Bishop's Stortford

SQUARE WAVE GENERATOR

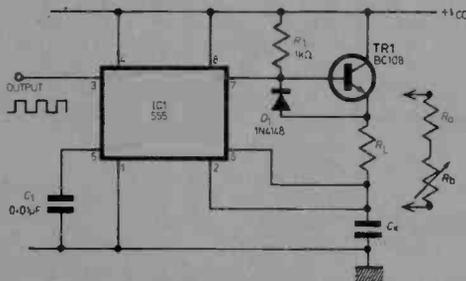


Fig. 1

THIS circuit basically produces a 1:1 mark space square wave from a standard 555 timer. The timing equation is as follows.

$$f_0 \text{ (frequency of oscillation)} = \frac{0.722 \text{ Hz}}{R_1 C_X} \text{ approx. the period}$$

$$\frac{1}{f_0} = 1.386 R_1 C_X \text{ sec.}$$

By making the resistor variable (R_1) with current limiting resistor (R_2) in place of R_1 , a frequency variation of 1,000:1 can be obtained with typical values of $1k\Omega$ for R_2 , $1m\Omega$ (variable) for R_1 . C_X charges via R_1 and TR1 which is turned fully on by the pull-up

resistor connected to pin 7. When the voltage at pin 6 (threshold) reaches $2/3 V_{cc}$ the internal discharge circuit is activated and pin 7 (which is the collector of the internal discharge transistor) is driven to earth potential. TR1 is now switched off and C_X now discharges through R_1 and D1. This continues until $1/3 V_{cc}$ is reached across C_X when the whole cycle is repeated.

This circuit with the resistor values given has been used to cover the entire audio range from 20Hz to 20kHz, all with one turn of the knob.

G. Sowersby,
Skipsea,
E. Yorks.

Readout

Sir—Referring to page 336 of PRACTICAL ELECTRONICS April 1976 I note the comments of Nexus concerning socialism, nationalised industry, competitive private enterprise, etc. I regard such comments as politically biased, and if you allow political discussion in your periodical, would offer my own humble opinion.

Was the first human venture into space achieved by competitive private enterprise? Was the first practical (though perhaps deplorable) use of atomic energy so achieved? Were the present availability of electronic components at favourable prices and the controlled quality of the same achieved solely by private enterprise without the support and the custom of national governments? Was the first manned mission to the Moon achieved by competitive private enterprise?

Finally, has not the present state of electronics industries been due to 25 years of major effort and a few billion pounds of taxes paid by World Citizens? *Verbum sapiente satis est!*

M. Knight,
London S.E.18

Get a great deal from

Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome

A Marshall (London) Ltd Dept: PE
 42 Cricklewood Broadway London NW2 3ET
 Tel: 01-452 0161/2 Telex: 21492
 & 85 West Regent St Glasgow G2 2OD
 Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272-654201/2
 & 27 Rue Danton Issy Les Moulineaux
 Paris 92

Catalogue price 30p

Top 500 Semiconductors from the Largest Range in the U.K.

2N456	0-80	Yellow	0-12	2N5190	0-92	AF106R	0-40	BC207	0-12	BF160	0-23	LM380	0-98	OC35	1-16
2N456A	0-85	Orange	0-12	2N5191	0-96	AF114	0-35	BC208	0-11	BF163	0-23	LM381	0-98	OC42	0-50
2N457A	1-20	2N3053	0-25	2N5192	1-24	AF115	0-35	BC212	0-16	BF166	0-40	LM702C	0-75	OC45	0-32
2N490	4-00	2N3054	0-60	2N5195	1-46	AF116	0-35	BC212L	0-16	BF167	0-25	LM709	0-48	OC71	0-17
2N491	4-38	2N3055	0-65	2N5245	0-29	AF117	0-35	BC214L	0-18	BF173	0-27	T099	0-48	OC72	0-25
2N492	5-00	2N3390	0-45	2N5295	0-48	AF118	0-35	BC237	0-16	BF177	0-29	8D1L	0-38	OC83	0-24
2N493	5-20	2N3391	0-28	2N5296	0-48	AF124	0-30	BC238	0-17	BF178	0-35	14D1L	0-40	ORP12	0-60
2N496	0-22	2N3391A	0-29	2N5296	0-48	AF125	0-30	BC239	0-15	BF179	0-43	LM710	0-47	R53	1-80
2N697	0-16	2N3392	0-15	2N5458	0-29	AF126	0-28	BC251	0-25	BF180	0-35	LM723C	0-66	SL1414A	1-80
2N698	0-82	2N3393	0-15	2N5457	0-29	AF127	0-28	BC253	0-25	BF181	0-36	LM741	0-40	SL610C	2-35
2N699	0-59	2N3394	0-15	2N5458	0-29	AF139	0-59	BC257	0-16	BF182	0-35	T099	0-40	SL611C	2-35
2N706	0-14	2N3402	0-18	2N5459	0-46	AF186	0-46	BC258	0-16	BF183	0-35	8D1L	0-40	SL612C	2-35
2N708	0-17	2N3414	0-18	2N5494	0-58	AF200	0-85	BC259	0-17	BF184	0-30	14D1L	0-38	SL620C	3-50
2N709	0-42	2N3415	0-21	2N5496	0-61	AF209	0-85	BC262	0-25	BF185	0-30	LM747	1-00	SL621C	3-50
2N711	0-50	2N3416	0-24	2N5776	0-45	AF240	0-90	BC262	0-25	BF194	0-12	LM748	0-40	SL623	5-75
2N718	0-23	2N3417	0-29	2N6027	0-45	AF279	0-70	BC263	0-25	BF195	0-12	8D1L	0-44	SL640C	4-00
2N718A	0-28	2N3440	0-59	3N128	0-73	AL102	1-00	BC300	0-38	BF196	0-13	14D1L	0-73	SL641C	4-00
2N720	0-57	2N3441	0-97	3N138	1-52	AL103	1-00	BC302	0-29	BF197	0-15	LM3900	0-61	SN76033N	2-92
2N914	0-22	2N3442	1-40	3N140	1-00	BC107	1-14	BC303	0-54	BF198	0-18	LM7805	2-50	SN76013N	1-95
2N916	0-28	2N3638A	0-15	3N200	2-49	BC109	0-15	BC307	0-17	BF200	0-40	LM7812	1-99	SN76023N	1-60
2N918	0-32	2N3638B	0-15	3N200	2-49	BC113	0-15	BC308A	0-15	BF225J	0-23	LM7815	1-99	SN76033N	2-92
2N929	0-25	2N3639	0-27	40361	0-40	BC115	0-15	BC309C	0-20	BF244	0-21	LM7824	1-99	ST2	0-20
2N930	0-26	2N3641	0-17	40362	0-45	BC115	0-17	BC317	0-12	BF246	0-45	MC1300	1-50	TAA263	1-20
2N1302	0-19	2N3702	0-12	40363	0-88	BC116	0-17	BC318	0-12	BF247	0-65	MC1300P	0-90	TAA300	1-84
2N1303	0-19	2N3703	0-13	40369	0-46	BC116A	0-18	BC337	0-20	BF248	0-58	MC1351P	0-80	TAA350	1-96
2N1304	0-26	2N3704	0-15	40395	0-56	BC117	0-21	BC338	0-20	BF254	0-19	MC1352P	0-80	TAA550	0-32
2N1305	0-24	2N3705	0-15	40395	0-65	BC118	0-14	BCY30	0-30	BF257	0-47	MC1468	3-50	TAA611C	2-18
2N1306	0-31	2N3706	0-15	40406	0-44	BC119	0-29	BCY31	0-85	BF258	0-53	MC1469	2-75	TAA621	2-03
2N1307	0-30	2N3707	0-18	40407	0-35	BC121	0-35	BCY32	1-15	BF259	0-55	ME0402	2-25	TAA661B	1-03
2N1308	0-47	2N3708	0-14	40408	0-50	BC125	0-16	BCY33	0-85	BF299	0-24	ME0404	0-13	TBA551	1-69
2N1309	0-47	2N3709	0-15	40409	0-52	BC126	0-23	BCY34	0-79	BF299	0-24	ME0412	0-18	TBA800	0-88
2N1671	1-54	2N3710	0-15	40411	2-00	BC132	0-30	BCY38	1-00	BF328A	2-30	ME4102	0-11	TBA820	0-98
2N1671A	1-57	2N3711	1-20	40594	0-74	BC135	0-13	BCY39	1-50	BF328	1-36	ME4104	0-11	TBA820	0-80
2N1671B	1-85	2N3712	1-20	40595	0-84	BC136	0-17	BCY42	0-28	BF329	0-25	MJ481	1-20	TIL209	0-35
2N1907	0-57	2N3714	1-38	40601	0-67	BC137	0-17	BCY56	0-30	BF329	0-35	MJ490	1-05	TI2P29A	0-49
2N2102	0-60	2N3715	1-50	40602	0-61	BC140	0-68	BCY59	0-32	BF330	0-35	MJ491	1-45	TI2P29C	0-80
2N2147	0-78	2N3716	1-80	40603	0-58	BC141	0-68	BCY70	0-17	BF384	0-30	MJ2955	1-00	TI3P0A	0-40
2N2148	0-94	2N3717	2-26	40604	0-58	BC142	0-23	BCY71	0-22	BF385	0-35	MJE340	0-48	TI3P30C	0-85
2N2180	0-47	2N3723	1-80	40636	1-10	BC143	0-28	BCY72	0-72	BF387	0-28	MJE2955	1-20	TI3P31A	0-62
2N2218A	0-47	2N3723	2-65	40669	1-00	BC147	0-10	BD115	0-75	BF388	0-30	MJE3055	0-75	TI3P31C	1-00
2N2219	0-42	2N3789	2-06	40673	0-73	BC148	0-09	BD116	0-75	BF389	0-90	MJE3070	0-65	TI3P32A	0-74
2N2219A	0-52	2N3790	2-40	AC126	0-20	BC149	0-13	BD121	1-00	BFY50	0-30	MJE317	0-75	TI3P32C	1-25
2N2220	0-25	2N3791	2-35	AC127	0-40	BC153	0-18	BD123	0-82	BFY51	0-28	MJE520	0-60	TI3P33A	1-01
2N2221	0-18	2N3792	2-60	AC128	0-35	BC154	0-18	BD124	0-67	BFY52	0-30	MJE521	0-70	TI3P33C	1-45
2N2222	0-20	2N3819	0-15	AC151TV	0-27	BC157	0-16	BD131	0-40	BFY53	0-18	MP8111	0-32	TI3P4A	1-01
2N2221A	0-21	2N3794	0-37	AC152V	0-49	BC158	0-16	BD132	0-50	BFY90	1-27	MP8112	0-40	TI3P4A	2-60
2N2222A	0-25	2N3820	0-29	AC153	0-35	BC160	0-78	BD135	0-21	BFY93	0-48	MP8113	0-47	TI3P5A	2-90
2N2368	0-17	2N3823	0-78	AC153K	0-40	BC167B	0-15	BD136	0-22	BSX20	0-28	MPF102	0-39	TI3P6A	3-70
2N2369	0-20	2N3904	0-19	AC154	0-25	BC168B	0-15	BD137	0-24	BSX21	0-30	MPSA05	0-25	TI414A	0-79
2N2369A	0-22	2N3906	0-19	AC176	0-40	BC168C	0-15	BD138	0-26	BU104	2-00	MPSA06	0-31	TI414C	1-40
2N2646	0-55	2N4036	0-67	AC176K	0-40	BC169B	0-15	BD139	0-71	BU115	2-25	MPSA12	0-35	TI4P2A	0-90
2N2647	0-48	2N4037	0-42	AC187K	0-35	BC169C	0-15	BD140	0-87	CI06D	0-65	MPSA55	0-21	TI4P2C	1-60
2N2904	0-95	2N4058	0-18	AC188K	0-40	BC170A	0-15	BD529	0-80	CA3020A	1-80	MPSA56	0-31	TI4P9C	0-70
2N2904A	0-45	2N4059	0-15	AC187	PR	BC171	0-16	BD530	0-80	CA3028A	0-79	MPSU05	0-65	TI2955	0-98
2N2905	0-47	2N4060	0-15	AC188	0-95	BC172	0-12	BDY20	1-05	CA3035	1-37	MPSU06	0-58	TI3055	0-50
2N2905A	0-50	2N4061	0-15	AD142	0-57	BC177	0-19	BF115	0-20	CA3046	0-70	MPSU55	0-63	TI543	0-28
2N2906	0-33	2N4062	0-15	AD143	0-58	BC178	0-18	BF117	0-55	CA3052	2-11	MPSU56	0-60	ZTX300	0-13
2N2906A	0-42	2N4126	0-21	AD149V	0-74	BC179	0-21	BF121	0-35	CA3089E	1-62	NE555V	0-70	ZTX301	0-13
2N2907	0-23	2N4289	0-34	AD150	1-15	BC182	0-12	BF123	0-33	CA3089A	1-08	NE556	1-30	ZTX302	0-20
2N2907A	0-24	2N4919	0-95	AD161	0-89	BY182L	0-12	BF125	0-35	CA3089E	1-96	NE560	4-48	ZTX500	0-15
2N2924	0-20	2N4920	1-10	AD162	0-89	BC183	0-12	BF152	0-20	CA3090Q	4-23	NE561	4-48	ZTX501	0-15
2N2925	0-20	2N4921	0-83	AD161	PR	BC183L	0-12	BF153	0-25	LM301A	0-48	NE565A	4-48	ZTX502	0-18
2N2926	0-19	2N4922	1-00	AD162	1-58	BC184	0-13	BF154	0-20	LM308	1-17	OC23	1-35	ZTX530	0-23
Green	0-12	2N4923	1-00	AF106	0-40	BC184L	0-13	BF159	0-27	LM309K	1-88	OC28	1-48	ZTX531	0-22

NEW RANGE TOOLS—HIGH QUALITY MINIATURE ELECTRONIC PLIERS INSULATED HANDLES

- Round nose box joint 4in long £2-50
- Diagonal cutters box joint 4in long £2-80
- Flat nose box joint 4in long £2-40
- Snipe nose box joint 4in long £2-40

P.C. MARKER PEN DALO 33PC, 87p. ZENER DIODES 400MW 11p, 1W 17p, 2-5W 35p.

- IC SOCKETS 8 DIL 12p, 14 DIL 14p, 16 DIL 16p.
- RESISTORS ½W 2p (100 per value 0-013p); ¼W 3p (100 per value 0-02p).
- SCORPIO CAR IGNITION KIT £12-75.
- JUMBO 7 SEGMENT DISPLAYS £2.
- DL 707 £1-75.
- MINITRON £1-50.
- LEDs Red, green and yellow, 20 dia. 32p.

SEE MARSHALL'S FOR CMOS

CD4000	0-18	CD4018	0-88	CD4042	0-70
CD4001	0-18	CD4019	0-82	CD4043	0-83
CD4002	0-18	CD4020	0-88	CD4044	0-77
CD4006	0-98	CD4021	0-88	CD4045	1-30
CD4007	0-18	CD4022	0-85	CD4046	1-20
CD4008	0-82	CD4023	0-18	CD4047	0-85
CD4009	0-52	CD4024	0-72	CD4048	0-45
CD4010	0-52	CD4025	0-19	CD4050	0-45
CD4011	0-18	CD4027	0-43	CD4051	1-25
CD4012	0-18	CD4028	0-83	CD4511	1-84
CD4013	0-88	CD4029	1-08	CD4516	1-28
CD4014	0-88	CD4030	0-82	CD4518	1-87
CD4016	0-88	CD4031	1-88	CD4520	1-87
CD4018	0-88	CD4037	0-88		
CD4017	0-45	CD4041	0-70		

Veroboard

Copper		Plain	
2.5 x 3½in	36p	25p	22p
2.5 x 5in	40p	39p	17p
3½ x			



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments.)

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a person who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 44 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE, DEPT CPE09 READING RG7 4PF CPE09
 Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-628 2721
 Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS

POSTCODE



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



FREE Brochure on New KITS

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

Send 15p S.A.E. (10in x 12in) to cover postage

PLEASE NOTE OUR NEW ADDRESS



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits—

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ "Mistral" Digital Clock Kit £12.50 (inc. VAT + 50p P. & P.); Built £18 + 50p P. & P.
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept. E, 35 Grosvenor Road, Twickenham, Middx. 01-891 1923

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
 (also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
 1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4J5
 Phone: 888-4474

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT
 Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 75p. P. & P. + 8%.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

- ★ Completely portable.
 - ★ Solders up to 150 joints per charge.
 - ★ Recharges in its own stand.
 - ★ Fine tip for all types of soldering.
 - ★ Only 8in long and weighs just 6 ozs.
- OUR PRICE £9.75 + 8%.**
 (Spare bits are available)

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Classic panels with metal front plate fitted with four screws (all supplied).
 An ideal box to give a small project a professional finish.
SIZE (internal) 81mm x 61mm x 28mm.
OUR PRICE 40p. + 8%.



"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE**
 170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ **THE PRE-AMP MODULE**
 Four control pre-amp, Vol, Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ **THE POWER SUPPLY**
 Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. £27.50, carr. £1.20. Send S.A.E. for further details on this or our ready built amplifiers. + 8%.

12-0-12V 500M/A

240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £1.20. + 8%.

TELESCOPIC AERIAL


Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended 43". Fully closed 7". Our Price 50p + P/P + VAT @ 12½%.

Low Voltage Stereo Amplifier

8 transistor stereo amplifier with volume, bass, balance and tone controls. Approx. 3W into 8 ohm per channel. Needs a 9/12V d.c. supply and is complete on a 2½in x 7½in P/c board. Ideal for domestic record players, etc.

A BARGAIN AT £5 + 12½% VAT

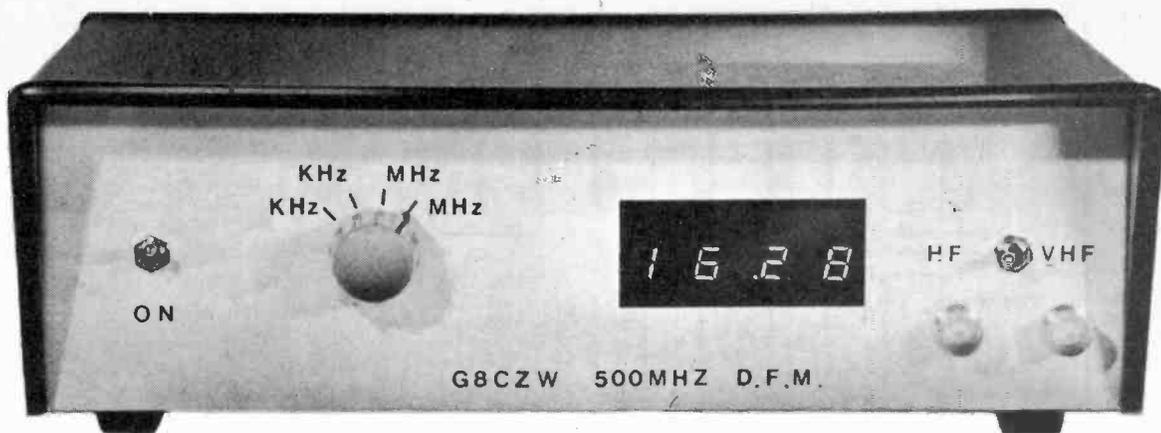U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
 VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.



DIGITAL FREQUENCY METER

By A. J. BUXTON

PART TWO

THIS concluding article deals with the construction of the main board, display board and details of the high impedance buffer and a v.h.f. prescaler.

CONSTRUCTION

The layout of the components on the main p.c.b. is shown in Fig. 7. A full size printed circuit master for this board is given in Fig. 8.

The layout of the components on the display board is shown in Fig. 9 and the printed circuit master in Fig. 10.

A ready-made case is used to house the instrument. A rectangular hole is needed in the front panel to show the display. This should be covered with a red filter to make the display more easily read.

Drilling details for the case are given in Fig. 11.

CIRCUIT BOARD ASSEMBLY

When the printed circuit boards have been obtained the components must be soldered in place. Start with the display board. First check that all holes including the 3mm fixing holes have been accurately drilled, then insert and solder the six wire links marked in Fig. 9. Insert and solder the components in the following order: resistors, i.c. sockets, transistors. The transistor leads need to be splayed out slightly; do not bend too close to the plastic.

Cut 15 70mm lengths of sleeved wire and strip 6mm from each end, tinning the bare wire. Insert these wires into the display board pads and solder in place. Check for solder bridges, then proceed to the main board.

After checking that all holes are present, solder in the 24 links shown on Fig. 7. If i.c. sockets are used, insert and solder these next. The socket for the


ZN1040E is 28 pins and can be made either by cutting two 14 pin sockets in half or by using strips of pins.

Insert and solder resistors, capacitors, transistors, diodes and the trimmer capacitor VC1. Insert integrated circuits.

Solder about 20cms of sleeved wire into the -9V and +5V pads (27 and 1) then the same length to pads 20, 21, 17, 18, 19, 22, 23, 24, 25, 26 and 28.

Short out pads 30 and 33 (W and Z) to give IC1 a gain of 100. Solder one end of the 6,800pF capacitor C1 to pad 29.

The main circuit board in position

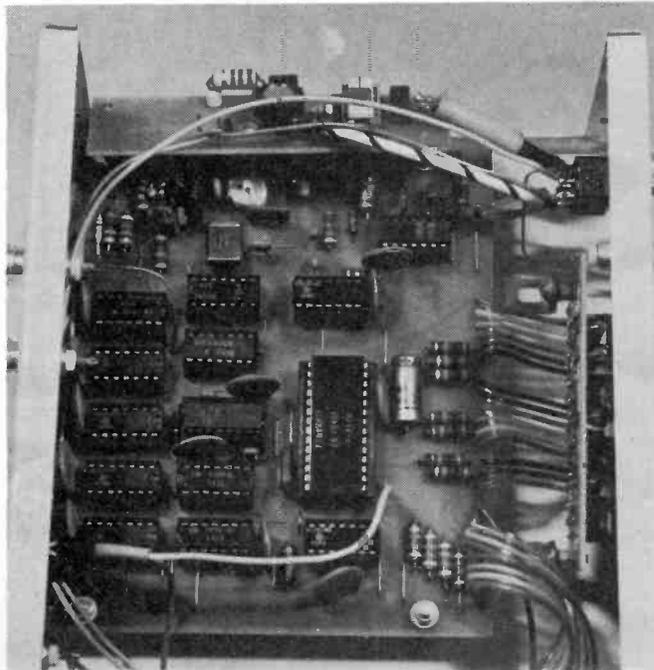

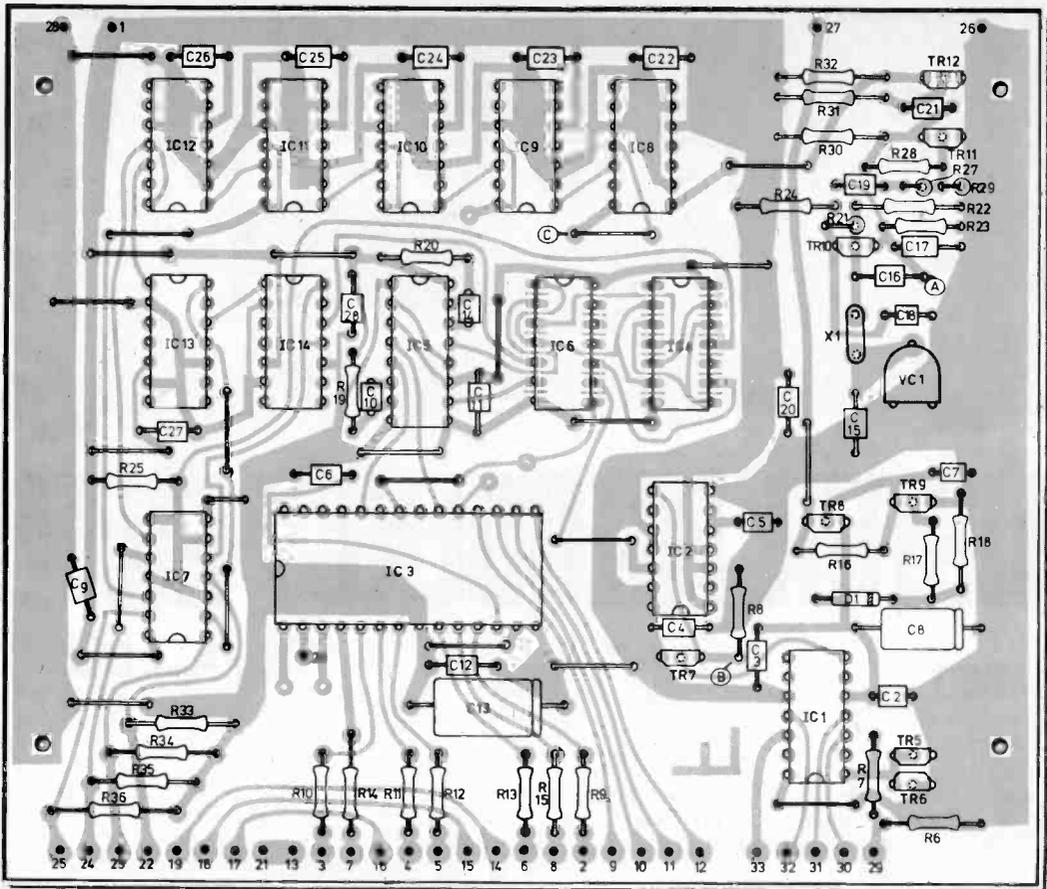


Fig. 7. Layout of the components on the main printed circuit board. Note that if the high impedance buffer is used then C1 and transistors TR5 and TR6 are not required. The three signal test points in Fig. 2 are marked as "A", "B" and "C". I.C. sockets should be used especially for IC3 as replacing a faulty i.c. is difficult

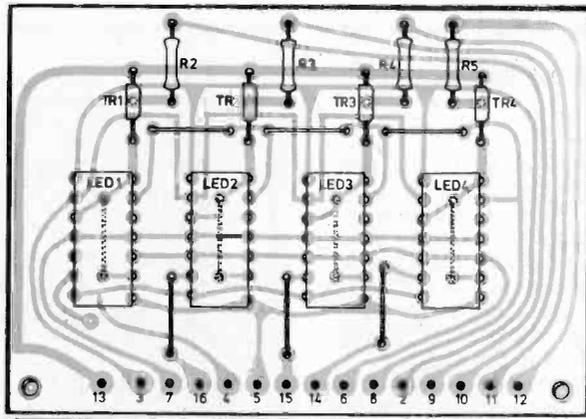


Fig. 9. Layout of the components on the display board. The 15 pads are wired to pads with the corresponding numbers on the main board

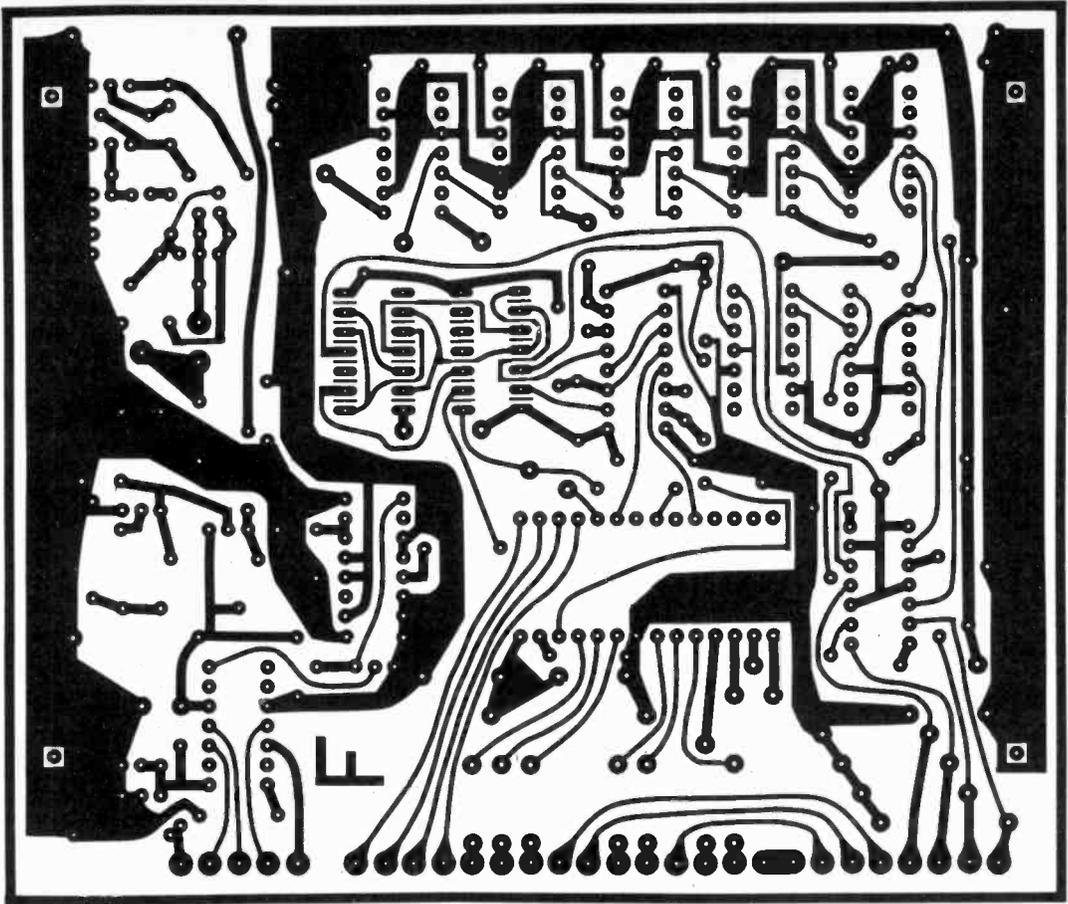


Fig. 8. Full size printed circuit master of the main board as viewed from the copper side

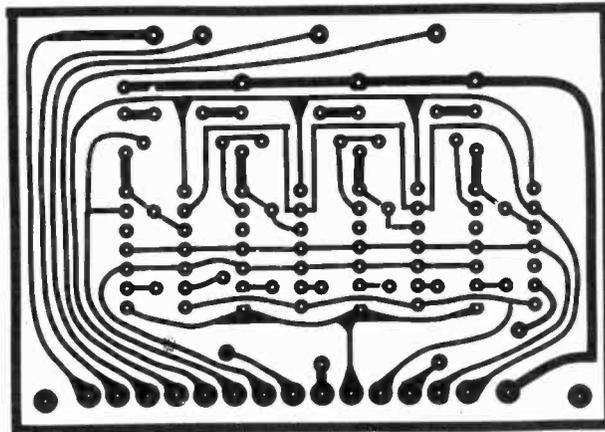


Fig. 10. Full size printed circuit master of the display board

Mount the display board onto its support brackets, check the main board for mistakes, then join the 15 wires from the display board to the main board.

Now insert and solder the crystal X1 leaving about 5mm of lead between can and board.

Glue filter onto inside of case, then mount input socket (SK1), range switch (S1), mains switch (S3), mains lead; fuse (FS1) and lamp test switch (S2).

The mains transformer should have flying leads soldered onto its mains, screen and 0V terminals. Mount the transformer using 4B.A. bolts with a solder tag on each. Take the transformer screen and 0V leads to these tags.

Mount the regulator IC15 using a 4B.A. nut and bolt, then the tag strip. Fig. 12 shows the general layout and interwiring.

Insert four 25mm 6B.A. bolts to hold the main board and fix with nuts. Then screw on another nut on each, leaving about 13mm between it and the case. The display board bolts are then fitted in a similar way, but 13mm bolts are used and 6mm is left between the second nut and the case.

The boards should then both be placed on their bolts and fixed with washers and nuts. The wires from pads 17, 18, 19 and 22, 23, 24, 25 are then soldered to the range switch.

The free end of C1 is soldered to the input socket. Wire up the power supply using Fig. 12.


Carefully check for mistakes, then switch the instrument on.

SETTING UP

The following tests should be made to check the correct operation of the instrument.

Measure the voltage on pin 5, IC1 (-5V) and pin 10 (+5V). If an oscilloscope is available the 5MHz

Fig. 11. Drilling details of the metal case. The oblong hole for the display is made by drilling along the perimeter or sawing with an Abrafile

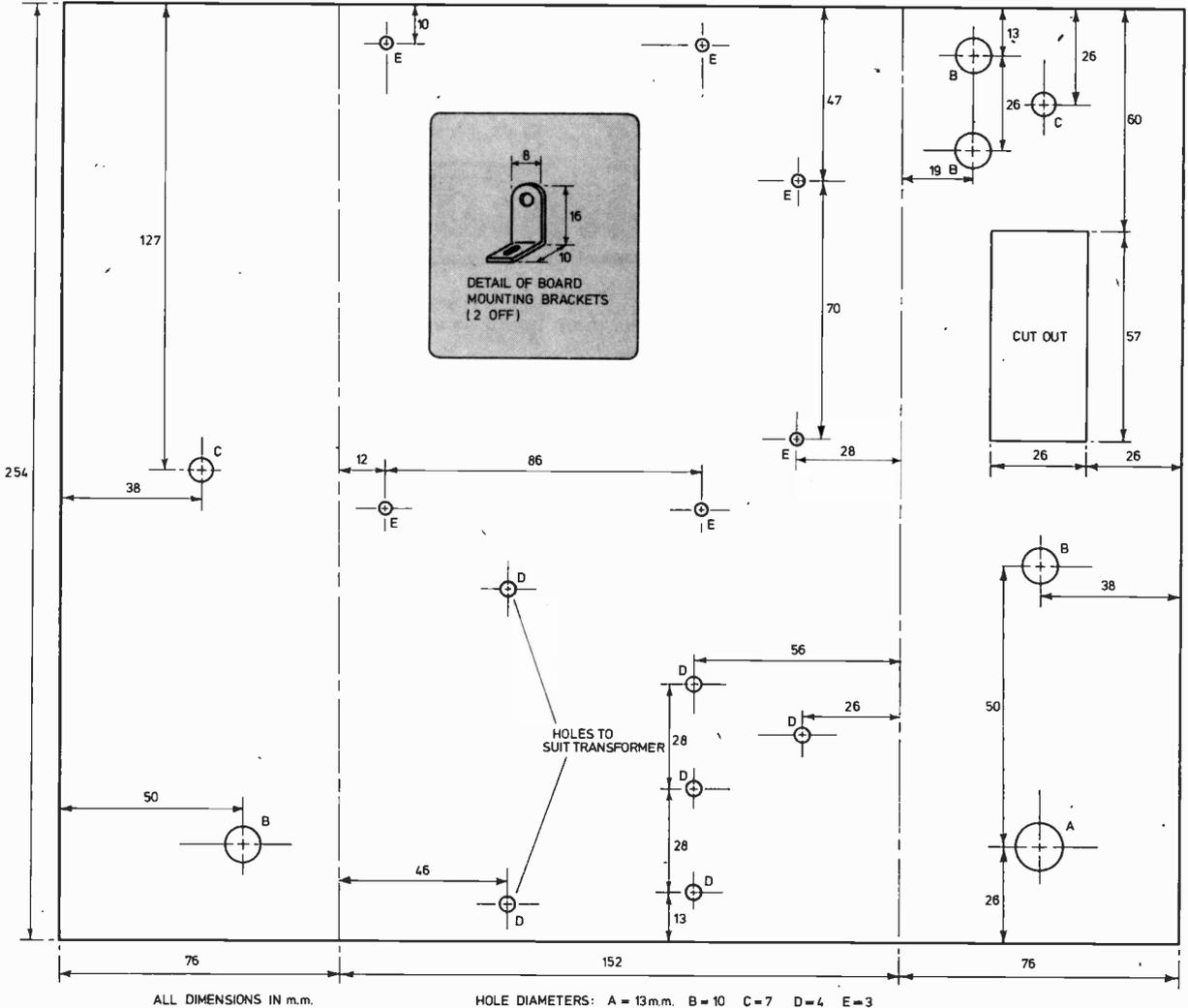


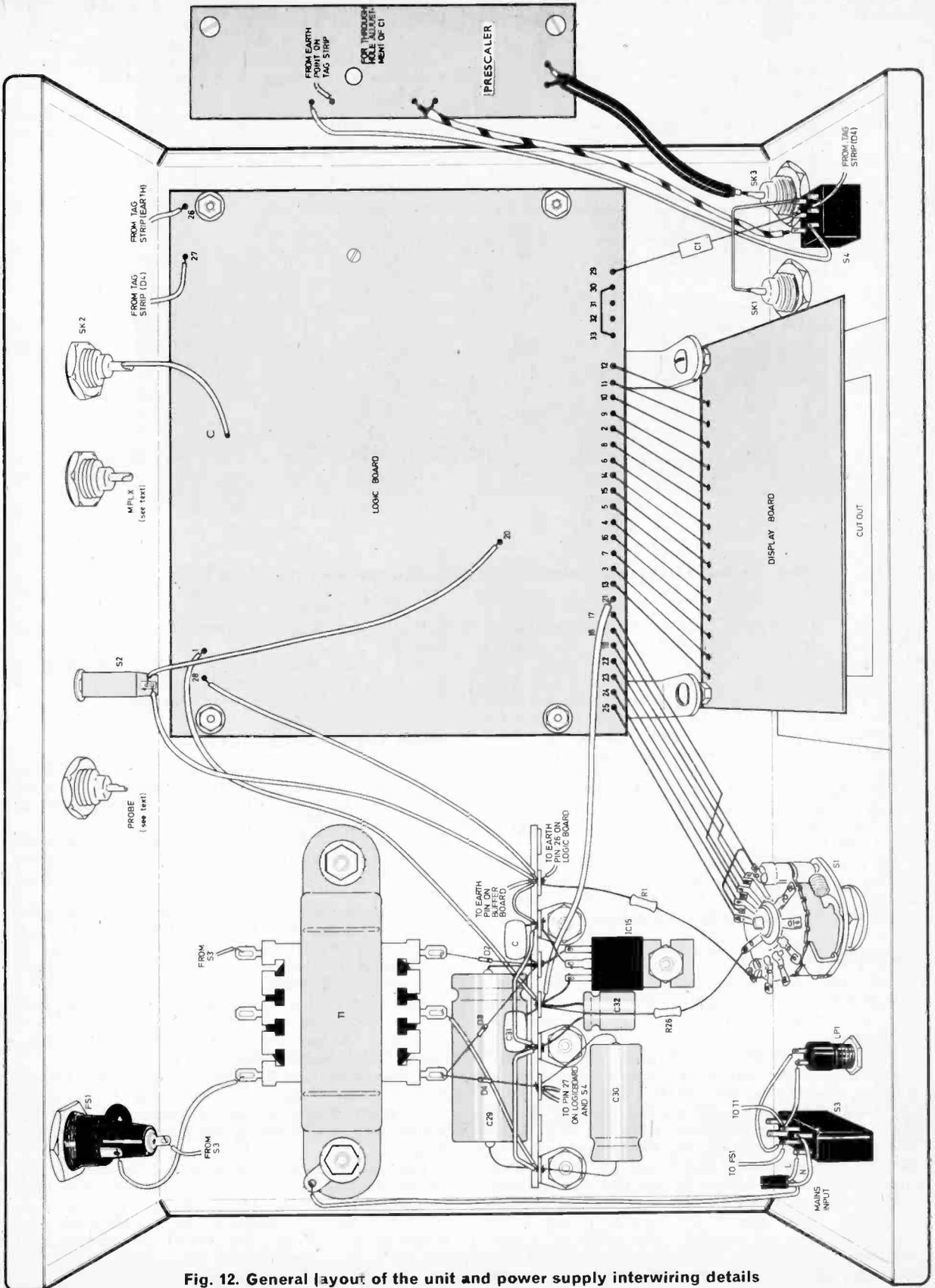


Fig. 12. General layout of the unit and power supply interwiring details

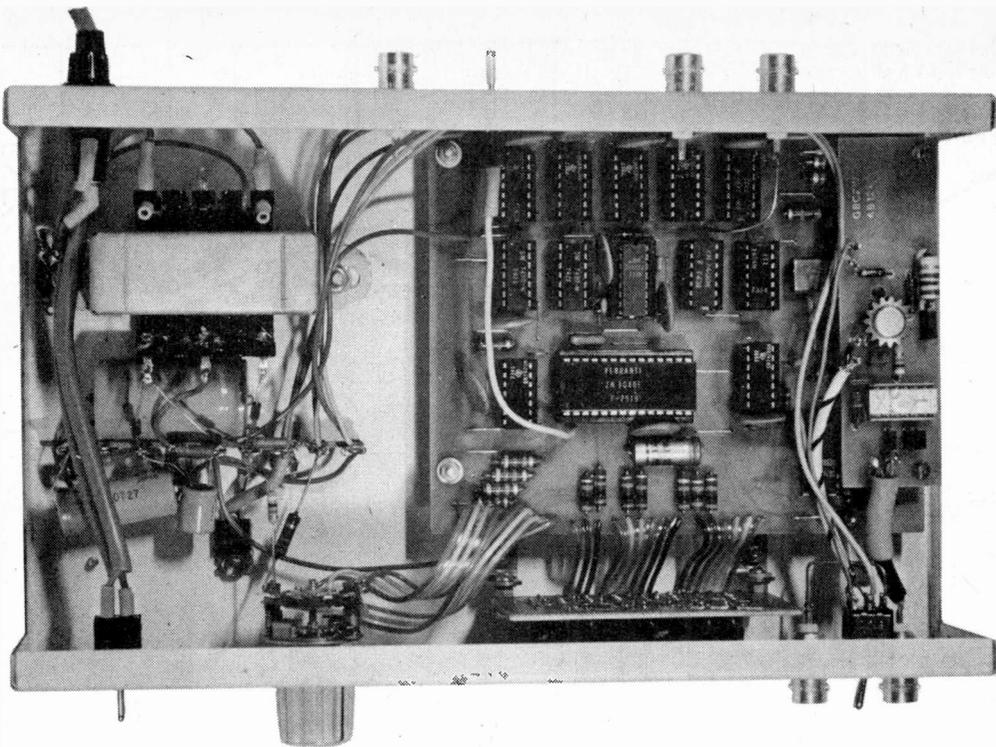

The completed frequency meter with the pre-scaler mounted in position on the right

frequency at point "A" should be checked. Then check the divider chain (IC8 to 14) for correct division.

If an oscilloscope or frequency meter is not available, a multimeter can give an indication of oscillation. Pin 12 of IC8 to 14 has a symmetrical waveform so at high frequencies about 2V or so will be registered. No output will register as either 0V or 4V.

Earthing pin 2 of IC3 with the lamp test switch causes the display to indicate all eights. If not, check that an oscillation of about 2.8kHz is present at pin 12, IC3.

On the lowest frequency range, pin 9 of IC4 should be high for one second and low for one second. The clear and transfer functions need a scope or timer to check their operation.

CALIBRATION

The only calibration required in this instrument is the setting of the oscillator frequency at 5MHz. The 3 to 60pF capacitor VC1 is used for this adjustment.

The most convenient calibration signal is that obtained from the long wave Radio 2 transmitter at 200kHz. By taking the 1MHz pulses from point "C" (IC8) through a capacitor and dividing this by five, one can obtain 200kHz from the D.F.M. A 7490 i.c. is quite suitable for this purpose and, in fact, the high impedance buffer board to be described later has provision for an i.c. for just this purpose.

The signal from the D.F.M. at 200kHz is coupled to a long wave receiver by draping a wire from this output over the receiver. The oscillator is then adjusted by means of VC1 until the audible beat frequency is very low. An "S" meter is a useful

indicator for this adjustment but ears are nearly as good.

The D.F.M. should be switched on for about an hour before this adjustment is made.

The instrument is now ready for use.

HIGH IMPEDANCE BUFFER

For general purpose use it is often important for the digital frequency meter to have a high input impedance so that it does not load the circuit to which it is connected.

The circuit of Fig. 13 (a) shows suitable buffer for use with this instrument. A field effect transistor (TR15) is used to give the required high input impedance.

The circuit gain is determined by the d.c. coupled amplifier formed by TR17 and TR18, as TR15 has unity gain. With resistor R48 having a value of 1.5 kilohm the gain is about four when the output is loaded by 50 ohms.

The two kilohm potentiometer VR1 is adjusted to give maximum gain. The input transistor TR15 is protected from voltage overload by the two diode-connected transistors TR13 and 14.

Also mounted on the buffer board is the 200kHz divider whose circuit is shown in Fig. 13 (b). Input and output should be via screened leads and the power lines should not be the same as those for the buffer.

The layout of the components on the printed circuit board and the p.c.b. master are shown in Figs. 14 and 15.

The wiring of the buffer board into the main unit is shown in Fig. 16. The board can be mounted on the same bolts holding the right-hand side of the main board, if these are made about 4cms.

COMPONENTS . . .

BUFFER BOARD

Resistors

R37	100k Ω
R38	47k Ω
R39	47k Ω
R40	470k Ω
R41, R42	100 Ω (2 off)
R43	180 Ω
R44	3.8k Ω
R45	6.3k Ω
R46	330 Ω
R47	180 Ω
R48	1.5k Ω
R49	470 Ω
All $\pm 5\%$ $\frac{1}{4}$ or $\frac{1}{2}$ W	

Potentiometer

VR1	2k Ω horizontal skeleton preset
-----	--

Capacitors

C33	0.047 μ F
C34	150pF polystyrene
C35-C40	0.01 μ F disc (6 off)
C41	10 μ F 63V elect
C42	0.1 μ F disc

Transistors

TR13, TR14	ZTX314 (2 off)
TR15	E300
TR16	ZTX302
TR17, TR18	ZTX313 (2 off)

Integrated Circuit

IC16	ZN54L90
------	---------

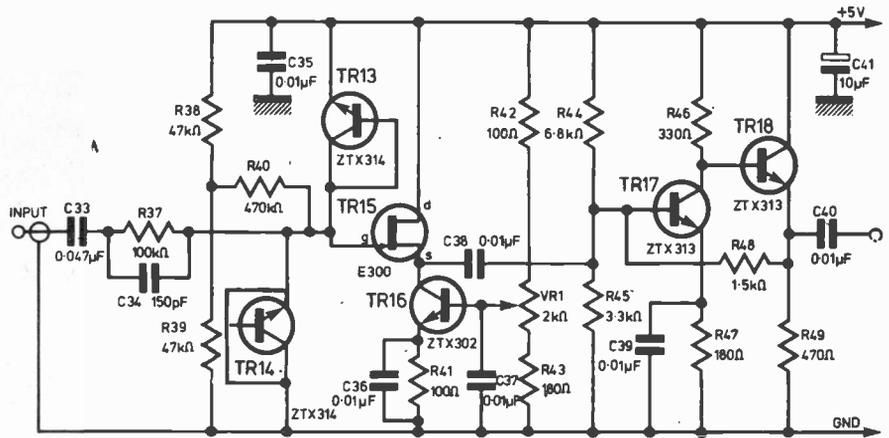


Fig. 13 (a). Circuit diagram of the high impedance buffer

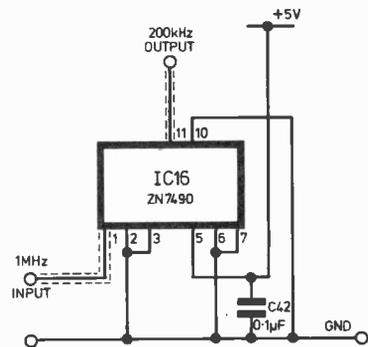


Fig. 13 (b). Circuit diagram of the divider to give the 200kHz calibration signal from the 1MHz available on the main board. Both circuits are mounted on the one board

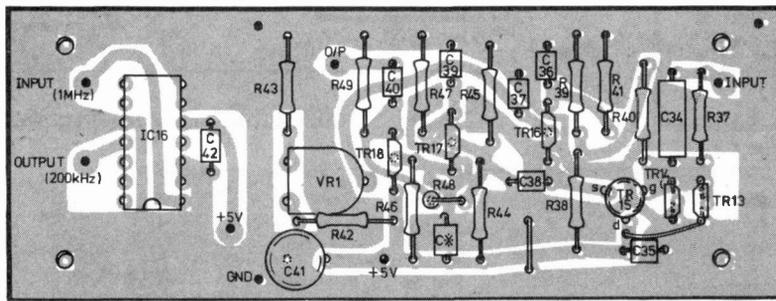


Fig. 14. Layout of the buffer and calibration circuits on the printed circuit board

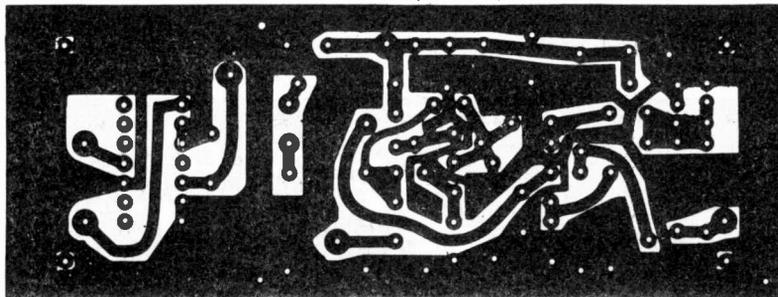


Fig. 15. Full size printed circuit master for the buffer and calibration board

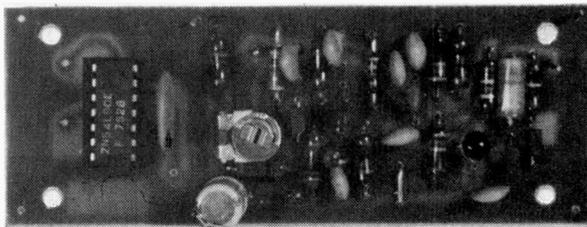
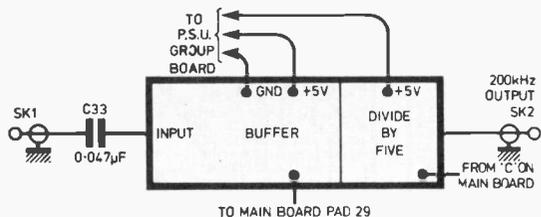


Fig. 16. Connections from the buffer and calibration board to the main unit

The high impedance buffer board

VHF PRESCALER

To enable the frequency meter to read frequencies up to 146MHz a pre-scaler is used. This pre-scaler uses Plessey UHF decade dividers. There are three devices in this family:

- SP630B 600MHz
- SP631B 500MHz
- SP632B 400MHz

The one used depends on one's frequency requirements.

The circuit (Fig. 17) shows the divider and a power supply regulator (TR19). The negative power supply can be taken from the same line that supplies the logic board. The shunt regulator maintains the supply of IC17 at -5.2 volts. It will cater for load current between 0 and 100mA. TR19 may be any silicon npn transistor of the 2N3053, 2N1711 type.

The value of R53 will depend on the input voltage V_{in} where

$$R_{53} = \frac{V_{in} - 5.2}{0.1} \text{ ohms}$$

COMPONENTS...

VHF PRE-SCALER	
Resistors	
R50	15kΩ
R51	450Ω
R52	100Ω
R53	100Ω
± 5% ¼W	
Capacitors	
C43-C47	1,000pF (5 off)
C48	0.1µF
Semiconductors	
D5	4.5V 400mW Zener
TR19	2N3053 with heatsink
IC17	SP630

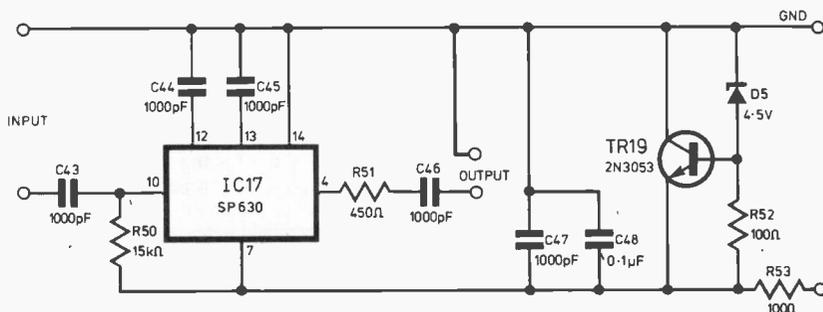


Fig. 17. Circuit diagram of the VHF Prescaler

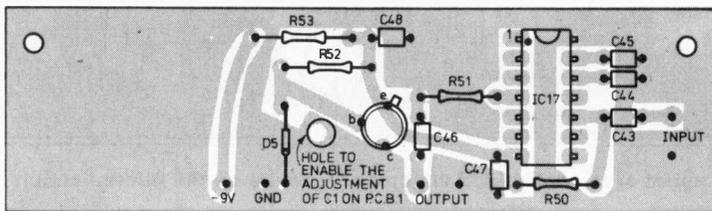


Fig. 18. Layout of the components on the VHF Prescaler board

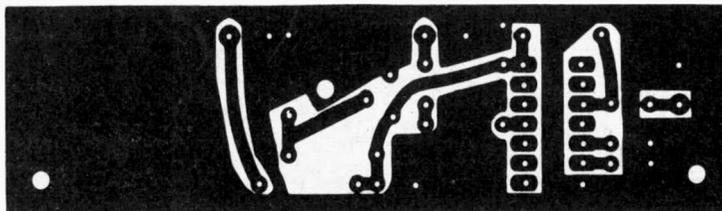


Fig. 19. Full size printed circuit master of the VHF Prescaler board

RETURN OF POST MAIL ORDER SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. A mono kit or a stereo kit. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors with printed front panel and volume, bass and treble controls. Spec. 10 watts output into 8 ohm, 7 watts into 15 ohms. Response 20 CPS to 30 K/C.S. input 100 M.V. high imp. Size 9 1/2 in. x 3 in. x 2 in.

Mono kit **£11.25** Stereo kit **£18** post 45p.
Easy to build. Full instructions supplied.



ELAC 10 inch

Dual cone plasticized roll sur-round. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts

£4.95

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12 in. For 12in. dia. **£11.25** Post Baker speaker. 75p

MODEL "B". 16 x 10 x 9 in. For 13 x 8 in. **£6.95** Post EMI speaker. 45p

LOUDSPEAKER CABINET WADDING 18in. wide. 25p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft. HI-FI CABINET £19.95 Carr. £2 each. Few only. Size 30 x 20 x 12in. Teak Finished Fluted Front.

TEAKWOOD LOUDSPEAKER FRONT GRILL Modernise your cabinets with the Grooved look. 10 1/2" x 7 1/2" 45p.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER Will mix Microphone, records, tape and tuner, with separate controls into single output 9 volt battery operated. **£5.20**

STEREO VERSION OF ABOVE £6.85.

R.C.S. STEREO FM TUNER



This completely cased mains powered Hi-Fi Tuner with brushed aluminium fascia is British made using the latest circuitry. Bargain **£30** Post 45p.


BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£3.95**

WAFER HEATING ELEMENTS T4H1M Size 10 1/2 x 8 1/2 x 1/2 in. Operating voltage 200-250V. a.c. 250 watts approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos. **ONLY 40p EACH (FOUR FOR £1.50)** ALL POST PAID—Discounts for quantity.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With flared tweeter cone and ceramic magnet. 10 watt. 8 ohm. Bass res. 45-50 cps. Flux 10,000 gauss. **£3.45** Post 45p

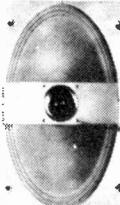With tweeter. And crossover. 10 watt. State 3 or 8 ohm. As illustrated. **£5.25** Post 45p
15 watt model 8 or 15 ohm £8.



BAKER MAJOR 12" £11.50



Post 50p
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14.50**
As illustrated. Post 80p
Please state 3 or 8 or 15 ohms.

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos Useful response 20-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8.95** Post 40p
12in. 30 watt
3, 8 or 15 ohms.

GROUP "35" **£10.50** Post 40p
12in. 40 watt
3, 8 or 15 ohms.

GROUP 50/12in. **£14.50** Post 80p
60 watt 8 or 15 ohms

GROUP "50" **£19.50** Post 80p
15in. 75 watt
8 or 15 ohms.

Group + PA Cabinets in stock Send for Leaflet.



BAKER 50 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 2 way mixing. Output 8/15 ohm. A.C. Mains. Separate treble and bass controls.

NEW 150 WATT MODEL 4 way mixing £68.
NEW 'DISCO 100 WATT' ALL PURPOSE AMPLIFIER CHASSIS £52 Carr. £1
2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis.




PW SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1000 watt channels. As featured in December Practical Wireless. **£12.50** CABINET extra £3.

GOODMANS CONE TWEETER

18,000 cps. 25 watts 8 ohm. Price **£3.60**

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS

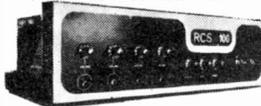

Professional model. Four inputs. Treble, Bass, Master-Volume Controls. Ideal disco, P.A. or groups. S.A.E. for details. 5 speaker outputs. **£85** plus £1.50 carr.
3 or 8 or 15 ohm or 100V line. Suitable carrying case £16.50.

E.M.I. GRAM MOTOR 120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. **£1.25** Post 30p

E.M.I. TAPE MOTOR 4 pole, 240v. 185 mA. 1400 rpm Spindle 1/2 in. diameter. 120v version £1. (illustrated). **£2.00** Post 30p
Size 3 1/2 x 2 1/2 in.



NEW BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 10" or 7" records Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in.

Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE **£10.95** Post 75p



PORTABLE PLAYER CABINET £4.50

Modern design. 8in. 18" x 15" x 7" rexine Post 50p. covered. Large front grille. Hinged Lid. Chrome fittings. Motor board cut for Garrard or BSR deck. Few only, in red and black.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/compat. cartridge. Base-plate. Size 11in. x 9 1/2 in. Turntable. Size 7in. diameter A/C mains. 220/250V.

3 speeds plays all size records. **£6.95** Post 45p
Two for £13. Post 75p

HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 x 7 1/2 in. **£5.95**
Model "B". Size 16 x 13 1/2 x 7 in. £6.50 Post 75p

TINTED PLASTIC COVERS ONLY

Sizes: 'A'—14 1/2 x 12 1/2 x 4 1/2, £2.50. 'B'—20 1/2 x 12 1/2 x 4 1/2, £2. 'C'—17 1/2 x 13 1/2 x 3 1/2, £3.25. 'D'—19 1/2 x 14 1/2 x 4 1/2, £3.50. Ideal for record decks, tape decks, etc. Post 75p.

BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

SUPERB
12in. 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps Flux Density 16,500gauss Useful response 20-17,000cps 8 or 15 ohms models.

£17.00 Post 80p

AUDITORIUM
12in. 35 watts



A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electronic organs. Ideal for Hi-Fi and Disco-theques. Bass Resonance 35cps Flux Density 16,000gauss Useful response 25-18,000cps 8 or 15 ohms models.

£15.50 Post 80p

AUDITORIUM
15in. 45 watts

Bass Resonance 35cps Flux Density 15,000 gauss Useful response 20-14,000 cps 8 or 15 ohms models.

£19.50 Post 80p

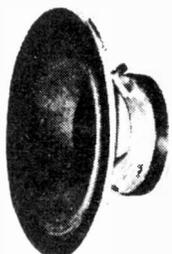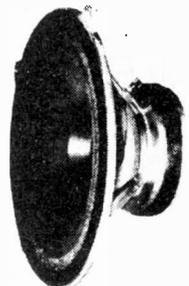

RADIO COMPONENT SPECIALISTS


Minimum post 30p. Access and Barclaycard Welcome. Radio Books & Components Lists 10p.

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Rail Selhurst. Tel. 01-684 1665

ELECTRONIC DIGITAL CLOCK

with alarm and snooze features

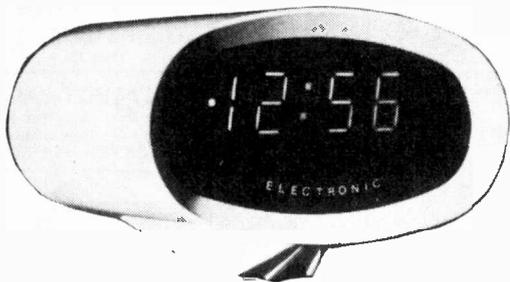

SPECIAL OFFER

£12.48

Plus 99p VAT

Features: ● 0-7 Inch High Digits ● Variable Intensity ● 24-hour Alarm ● 5-minute Repeating, Snooze Alarm ● Alarm Set Indicator ● Snooze Indicator ● Pulsing Second Indicator ● Power Interrupt Indicator ● Alarm Cancel Features—Tilt Operation ● Alarm Tone Output ● A.M.—P.M. Indicator

Size: 130mm x 90mm x 95mm. Weight: 10oz. Power supply: 110V a.c. ±10% 60Hz; 230V a.c. ±10% 50Hz.

Manufactured to high standards by a major American electronics corporation, this superbly styled solid-state timepiece is made available to all readers fully guaranteed.

Free trial in your home—Try out the clock in your home. If digital time is not for you return it in original condition within 10 days and we'll refund your money without question.

TIME MICROELECTRONICS

TM 33 Wateridge Road, Basingstoke, Hants
RG21 2RA.

Please send electronic clocks as illustrated. I enclose cheque postal order money order for £14.02 which includes P. & P.

Name

Address

Signature


ANNOUNCEMENT

P.W. RHYTHM GENERATOR.

SWING. WALTZ. ROCK. TANGO. CHA CHA. MARCH. MAMBA. FOX TROT. SHUFFLE.

ALL COMPONENT PARTS ARE AVAILABLE SEPARATELY S.A.E. FOR LISTS, OR FOR PRICING.

Tel. 0246-31475

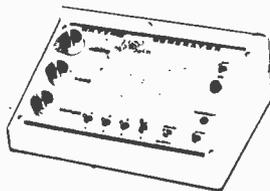

FULL KIT: £39.90 + £1.00 (includes V.A.T.)

KIT INCLUDES NEW UPDATED P.C.B.'s

With Printed layout for easy assembly, all components nice switches and knobs, case, in fact everything you need to complete this very exciting Project.

P.C.B.'s ARE AVAILABLE SEPARATELY

Set of NEW UPDATED P.C.B.'s with a printed layout, made in first class quality fibre-glass, by a well known national company.

Price on application to:



ASTRO
1 QUEEN STREET NORTH
WHITINGTON MOOR,
CHESTERFIELD,
DERBYSHIRE
Tel: 0246-31475



SPECIAL OFFER

CJL

CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT
ALL PRICES INCLUDE P&P AND V.A.T.

ANTEX SOLDERING IRONS

(with slide on & off bits)	
15W 'C' miniature irons	£2.30
3/32" 1/8" 3/16" bits—each	£0.45
'C' Elements	£1.10
18W 'G' miniature irons	£2.50
3/32" 1/8" 3/16" bits—each	£0.45
'G' Elements	£1.35
15W 'CCN' Low leakage irons	£2.70
3/32" 1/8" 3/16" bits—each	£0.45
'CCN' Elements	£1.50
25W 'X25' Low leakage irons	£2.30
3/32" 1/8" 3/16" bits—each	£0.47
'X25' Elements	£1.15
'SK1'; 'SK2'; Soldering Kits	£3.85
ST3 Stands—for all models	£1.10
SOLDER in Bib dispenser	£0.45

WIRE STRIPPER & CUTTER

£0.85	
HAND DRILLS Leytol precision, compact, 5/16" chuck	£3.99
AERIALS Extend 15-120cm	£1.50
CASSETTE 'Head Demagnetisers'	
Shaped pole—saves time	£3.65
EARPHONES Stethoscope	£1.25
Crystal earphone, lead & plug	£0.65
Headphone, 2,000 n.	£3.20
INTERCOMS 2-station	£6.35
MICROPHONES Dynamic	£2.15
PRINTED CIRCUIT KITS -All	
Items for producing p.c.'s	£3.99
SIGNAL INJECTOR -Audio through video signals, self contained	£4.25
STEREO HEADPHONES 8n	£4.85
SPEAKERS -75mm dia. 8n	£1.00


SPECIAL OFFER

	Price inc. VAT
Organ Keyboards—49 note C-C	£15.50
Organ Keyboards—61 note C-C	£20.00
Piano Keyboards—61 note F-F	£20.00
Master Tone Generator Unit: built and tested complete with transpose control; 12 tone outputs	£12.85
Master Tone Generator and Divider Unit: built and tested complete with transpose control; 72 tone outputs GD500/5	£25.00
I.C. Chips Master Frequency Generator: AY-1-0212 1-5MHz	£7.82
AY-1-0212A 2-5MHz	£8.75
AY-3-0214	£8.83
Rhythm Generator AY-5-1315	£8.18
Chord Generator AY-5-1317A	£8.66
Frequency Divider: Chips	
4 stage AY-1-5051	£1.85
5 stage AY-1-6721/5	£1.78
9 stage AY-1-6721/8	£2.00
7 stage AY-1-5050	£2.45

Supplied with Application/Data sheets

Elvins Electronic Musical Instruments

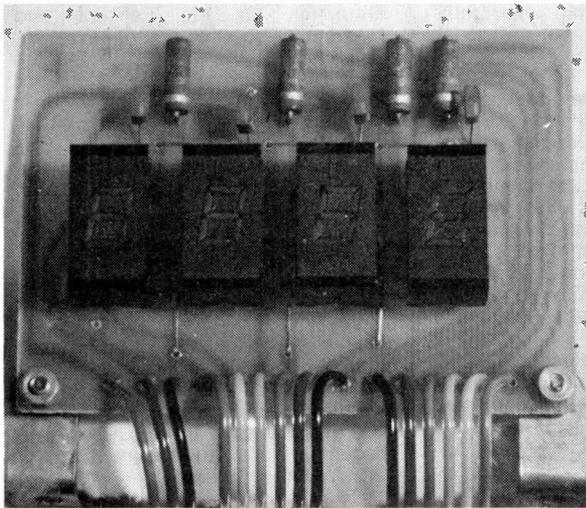40a Dalston Lane, London E8. Tel. 01-249 5624
(1 min. walk from Dalston Junction Station. Open 9 a.m. to 7 p.m.)



The display board

PRE-SCALER CONSTRUCTION

In this circuit a 100 ohm $\frac{1}{2}$ watt resistor is reasonable. It is advisable to use a socket to mount IC17. The SP632 costs about £16. The price of a socket does not compare to the price of a damaged circuit. The capacitors are all disc ceramic. All component leads should be kept short. Component layout is shown in Fig. 18 and p.c.b. master in Fig. 19.

The board is mounted on the oscillator side of the logic board. Two 13mm pillars are used to secure the logic board and the pre-scaler board mounts on top of these. The hole next to the 4.5V Zener is to adjust the oscillator trimmer capacitor VC1. The drawing (Fig. 12) shows how the prescaler is connected in circuit.

Test the power supply regulator before inserting IC17. Check that the voltage between pin 14 and pin 7 is about -5.2 volts. Plug a 68 ohm resistor between pin 7 and pin 14, check the voltage is still about -5.2 volts.

The input and output impedance is 50 ohms. The minimum drive voltage depends on frequency. The characteristics sheet should be consulted.

Note: The maximum peak input voltage must not exceed 5.2 volts.

APPLICATIONS

The digital frequency meter can be used to measure the frequency of any signal source. This ranges from transmitters, receiver oscillators, signal generators to function generator and pulse generator pulse repetition rates.

When using the 50 ohm input, care must be taken not to load the signal source in such a way that its frequency is changed. If the source is loaded then the D.F.M. may have to be left in circuit as the source is used.

The buffer amplifier will reduce the effect of this loading. When using large signal sources, a resistor in series with the D.F.M. input will further reduce the loading.

The buffer described has an input protection which starts to limit at an input voltage of 4.7V peak to peak. Before limiting the shunt capacitance is 5pF and after limiting 150pF. The limiting can be counteracted by using a variable resistor across the input to the D.F.M. (Fig. 20).

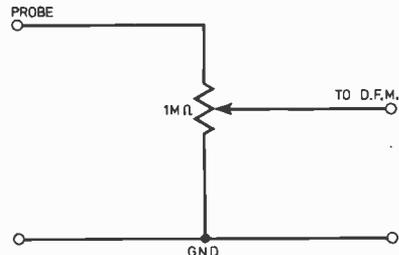


Fig. 20. A potentiometer across the input of the Digital Frequency Meter reduces the loading effects

High power transmitter frequencies can be measured by looping a piece of wire around the feeder. The D.F.M. input is connected to its ends.

If one wishes to measure, say, 35.01853MHz, one would measure the first four digits, then overrange the meter to read the following digits.

- Range 1 35.01
- Range 2 5.018
- Range 3 018.5
- Range 4 18.53

The D.F.M. can resolve down to 10Hz using this procedure. ★

PE

A VOLUME OF PRACTICAL KNOW-HOW

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At £2.10 incl. VAT and postage they are obtainable from:

Post Sales Department, IPC Magazines Ltd.
Carlton House, 66-68 Great Queen Street
London, W.C.2


I enclose P.O. cheque value for binders at £2.10 each for Practical Electronics Vol. No's.....

Name

Address

Date

PE

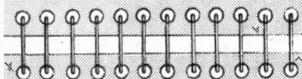

INDUSTRY NOTEBOOK

By Nexus



TOP OF THE POPS

Looking through back numbers of P.E., I find that in October 1974 I was commending the work of Godfrey Hounsfield, the bachelor boffin of EMI's Central Research Laboratories, who master-minded the EMI-Scanner brain X-ray equipment. At that time it had already clocked up £14 million of orders and was clearly going to be one of Britain's commercial as well as technical triumphs, which makes a change from the usual routine of British inventions being left for other nations to exploit.

What Hounsfield and his small team have now done for EMI emerged with startling clarity in the company's latest half-year results. The Scanner is generating profits on a scale unmatched since the days and following years when EMI had signed up the Liverpool Sound of the Beatles after John, Paul, George and Ringo had been rejected by Decca.

The EMI Group sales for the last half-year were £313 million, up 30 per cent, and profits (pre-tax) were £29.5 million, an increase of 81 per cent. But if we look closer at the figures we find that electronics as a separate activity in itself, had a 44 per cent increase in sales to £88 million and now, wait for it, profits had shot up to £10.6 million, an increase of 178 percent. Nice going in tough times!

But, said John Read, EMI Chairman, this is not a Scanner bonanza. Other sectors, too, had made big contributions and he cited defence electronics, industrial electronics and EMI's stake in TV transmission and studio equipment where the company had done particularly well in the Australian re-equipment programme in the switch-over to colour TV.

I didn't find Read's argument carrying much conviction. Profit on defence equipment is tightly controlled and TV and industrial electronics are, to say the least, highly competitive, which means that profit margins are necessarily restricted if you are to stay in business. The EMI-Scanner, however, was unique, technically and commercially, and could command in sales price what the market could afford. Although I disagree with John Read's comment, I don't argue with his reasons for making it which seem to have been intended to discourage potential competitors.

Total Scanner sales are now over £80 million and still rising fast. But note that the Scanner was unique. This is no longer the case with competitive models now appearing and there could be as many as 15 other manufacturers bringing similar equipment to the market in the next year or so. But, with a substantial lead in hand, EMI is still hopeful of remaining among the market leaders and a 20 per cent market share in 1980 could still represent sales of £100 million a year.

SALARIES

Last month I wrote at some length on the present salary structure for qualified engineers. My assessment was based on situations vacant notices in the national and technical press. Since then an authoritative survey has been published by the IEE as a result of a canvass among the membership. It more than confirmed my own general impression.

In the Associate Membership grade the greatest number is employed in non-managerial R & D where the median salary taking in all age groups is £3,700 although if those working in private industry are taken separately the median drops to £3,500 and the figure for the lower quartile (i.e., the figure below which 25 per cent of the sample falls) is £3,000. Non-managerial R & D is the most poorly paid.

Engineers working as salesmen or on maintenance and servicing earn more than the man in the laboratory. Fellows and Members, by definition, are people of greater maturity and experience and in general management in private industry enjoy a median income of £7,610 although a quarter get over £10,000.

It seems then, that the engineer whose main interest is income should switch as soon as possible to selling and marketing, and get a foothold on the managerial ladder.

What, to me, was a surprising finding in the survey is that engineers whose salaries are determined by collective bargaining do

less well than those whose salary is adjusted periodically by the employer. Of the Fellows and Members about one in nine enjoy, if that is the word, collective bargaining and get £1,000 a year less for it than the eight of their colleagues. Twenty-five per cent of Associate Members are in a collective bargaining situation and they run behind to the extent of £500.

MARINE RADAR

With shipbuilding in the doldrums at home one might expect marine radar to be taking a few knocks. Not so. Market leader Decca Radar took orders for nearly 200 installations in a single week recently, worth more than £700,000 and all from overseas.

The largest single order was from Yugoslavia for 93 sets, of which 67 are for fitting in a fleet of push-tugs under construction for Iraq. The second largest order came from Brazil, 35 sets for bulk carriers now being built as part of Brazil's maritime expansion programme. Another 37 sets were ordered by various navies, including those of Sweden and Chile.

Kelvin Hughes also appears to be doing very well in the world market and especially so with the KH Situation Display, a TV-type radar presentation which won the Queen's Award for Technological Innovation last year. KH engineers have been busy on further developments of the Situation Display and a new model, with improved definition, has just been released.

BELL CENTENARY

The 100th anniversary of the birth of the telephone provided the occasion for all manner of people to sound off about the virtues of instant person-to-person communication. Sir William Ryland, chairman of the Post Office and target of much impolite criticism over the past year, was well to the fore.

In an anniversary message to all his telecommunications staff he spoke of great achievement and said it was time the British people gave credit where it is due. He pointed out that the BPO installs 1,200 telephones an hour and invests at the rate of £1,700 a minute day and night.

But he didn't reveal how many people were asking for disconnection since the call charges went up, or that 9,000 workers are being made redundant in the manufacturing industry following cut-backs in orders. Sir William, however, remains optimistic that the BPO will make £80 million profit this year. I hope he is right. Last year the loss was £194.6 million.

SOUND DESIGN

A PRACTICAL ELECTRONICS PUBLICATION

THE MINISONIC MK2 SOUND SYNTHESISER

An up-dated version of the published Mk 1, the Mk 2 has an integral keyboard, two 250 mW monitoring channels and loudspeakers, and facilities for amplitude, frequency and harmonic modulation.



Available
Now
£1.20
POST PAID

*(Please allow at least 2 weeks for delivery)
If you do not wish to mutilate your copy of the magazine, please send
your order on a separate sheet.*

A SPECIAL
SELECTION
OF MUSICAL
PROJECTS
FROM PE

THE JOANNA ELECTRONIC PIANO

has realistic piano effect with touch-sensitive keyboard and additional choice of harpsichord or honky-tonk voicing.

THE ORION STEREO AMPLIFIER

A hi-fi amplifier with output of over 20+20 watts. Compact and complete in one unit, it measures only 14" x 6" x 2".

PLUS

Some great sound effects units for guitars, keyboard instruments and general recording.

To: Practical Electronics
IPC Magazines Ltd., Receiving Cashiers
Dept., King's Reach Tower,
Stamford Street, London SE1 9LS

Please send me copy (ies)
of "Sound Design". I enclose a Postal
Order/Cheque for £1.20 (post paid) or
(state amount for more than one copy)

(£2.35 post paid for 2 copies).

PLEASE WRITE IN BLOCK LETTERS

Name

Address

Post code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

Company registered in England. Regd. No 53626. A subsidiary of Reed International Limited.

PATENTS REVIEW...

AID FOR THE HANDICAPPED

Devices whereby a severely handicapped or paralysed person can control domestic equipment, such as a radio or television, are already known. These usually rely on a pressure-sensitive switch into which the patient blows. In BP 1 418 006, Signale und Automatik, of Bern, Switzerland, suggest an even more sensitive control switch.

It is suggested that even the most seriously handicapped persons can often still control tongue movement. Accordingly, a mouth-piece, generally similar to a microphone, carries two separate pairs of contacts, each embedded in insulating material.

These contacts, Fig. 1, are so spaced that the patient can bridge them easily with the tongue. One pair of contacts, *a, b*, is linked via cables to an excitation circuit, Fig. 2a. Terminal *a* connects to the collector of TR1, and terminal *b* to its base, with the emitter earthed. Transistor TR1 collector controls relay RLA via thyristor CSR1.

Contacts *c, d*, are linked to a de-excitation circuit Fig. 1b. Terminal *c* is connected to TR2 collector and terminal *d* is connected to its base, with the emitter earthed. Transistor TR2 collector controls relay RLB via thyristor CSR2. When closed, RLA1 connects the anode of CSR2 to earth.

To switch on load circuit *U*, the patient bridges contacts *a, b*, with

his tongue. This makes TR1 conductive, switches on CSR1, and energises RLA relay. Contact RLA2 closes to route power permanently to the circuit *U* and contact RLA1 closes to prepare Fig. 1b for de-excitation.

De-excitation is achieved by the patient bridging contacts *c, d*, to make TR2 conduct, switch CSR2 on and energise RLB.

Contact RLB1 is opened to switch off thyristor CSR1 and de-energise the relay RLA. Contacts RLA1 and 2 thus open, to isolate the load *U* and the relay RLB. Contact RLB1 now closes again to bring the device back to its rest state.

ELECTRIC FENCE

Farmers have for many years kept sheep and cattle within their fields by surrounding the area with a high voltage, low current wire. After a few shocks, the animals learn to keep clear of the wire, and the power need seldom be turned on. In BP 1 417 086, Richard Peck, of Pennsylvania, USA, describes a sophisticated version of the system, for use with domestic pets, for instance to prevent them from straying out of a house garden.

As shown in Fig. 1, a loop of wire defines the area in which the animal is to be confined. This loop can be buried under the ground.

BP 1 417 086

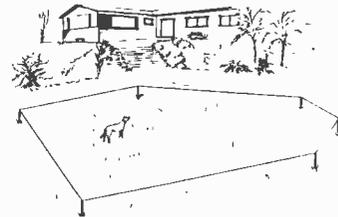


Fig. 1

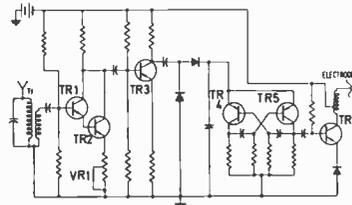


Fig. 2

The wire radiates, for instance at 560kHz, and the animal carries a small, battery-powered receiver on its collar.

The radiated signals are received at an aerial, Fig. 2, filtered and amplified by a Darlington pair TR1, TR2. Potentiometer VR1 serves as an adjustable feedback path for circuit stability and gain control. The output signal of the Darlington is fed via power amplifier TR3 to the rectifier pair and the following storage capacitor.

An astable multivibrator, TR4, TR5, is powered by the capacitor to produce a square wave signal which is amplified at TR6 and fed to induction coil. This produces a high voltage shock signal at the electrode which is in contact with the animal's skin. Alternatively the coil can power a loudspeaker close to the animal's ears. As soon as the animal strays too close to the wire, the multi-vibrator triggers a warning shock or sound in the animal's ear.

As an alternative arrangement, a transmitting aerial is located centrally within the confined area, and the circuit modified to trigger a shock when the animal moves too far from the aerial.

BP 1 418 006

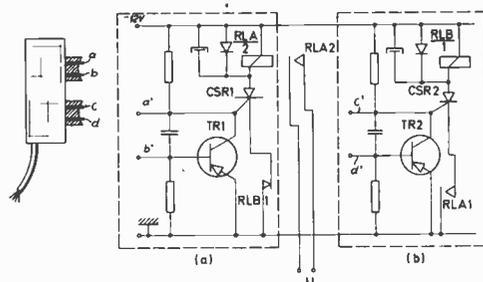


Fig. 1



COMPONENTS

Dept. P.E., WELLINGTON ROAD
LONDON COLNEY, ST. ALBANS
HERTS. AL2 1EZ

OPTO ELECTRONICS

TIL 209 Type 0-12in. LED 15p
MAN 3M 0-127in. Display 25p

LINEAR ICs

LM301AV Ext. comp. operational amplifier 36p
LM307V Int. comp. operational amplifier 45p
MC1458V Dual comp. operational amplifier 80p
NE510A Video amplifier £1.58
*NE540L Audio power driver £1.17
NE555V Timer 44p
NE556A Dual 555 14 pin 95p
NE561B Phase locked loop with A.M. demod. £2.70
NE562B Phase locked loop with V.C.O. £2.70
NE566V Phase locked loop function gen. £1.50
*PA239A Dual low noise stereo pre-amp. 95p
µA741CV Op. amp. 42p
µA747CA Dual op. amp. 90p
*MC1303L Dual stereo pre-amp. £1.47
*MC1306P 4W audio amp. £1.64
*MC1304P F.M. multiplex stereo demodulator £1.12
*MC1310P Stereo demodulator £1.92
*MC1312P } £1.94
*MC1314P } Quadrophonic decoder kit £3.31
*MC1315P } £3.59
*MC1330P Low level video detector 67p
*MC1496G Double balanced mixer 77p

MOS I.C.s

AY-5-1224 12/24 hour digital clock circuit £4.25
AY-3510 3 1/2 digit DVM circuit £6.10
*AY-1-0212 Master tone generator £5.55
*AY-1-5051 4 stage divider £1.20
*AY-1-6721/5 5 stage divider £1.30
*AY-1-6721/6 6 stage divider £1.45
*AY-1-5050 7 stage divider £1.75
C550 8 digit calculator chip £6.50
C500 8 digit calculator chip £3.25
2102B MOS 1024 bit static RAM £3.00

FERRANTI ICs

ZN1040E Universal counter/display cct £12.00
ZN1034E Precision timer cct £2.99
ZN414 A.M. radio circuit £1.00
Data and circuits on ZN414 10p

MULLARD AUDIO and RADIO MODULES

*LP1400 Stereo Decoder Module £8.02
*LP1162 5W Audio Amp. £5.46
*LP1173 10W Audio Amp. £7.54
*LP1181 RF-IF Module £4.46
*LP1182/2 Stereo pre-amp. £4.00
*LP1183/2 Stereo pre-amp. £4.92
*LP1184/2 Low distortion stereo pre-amp. £8.18
*LP1185 FM IF Amplifier £6.28
*LP1186 FM Tuner Module £7.78
*LP1194/40 Voltage Multiplier (EHT gen.) £8.10

SPECIAL OFFER

(1) 10 Watt stereo amplifier comprising:
1 LP1182/2 and 2 LP1173
*Normal price £19.08 *Offer Price £15.00
(2) FM tuner comprising:
1 LP1185 1 LP1186 1 LP1400
*Normal price £22.08 *Offer Price £18.00

I.C. SOCKETS

14 pin 12p 28 pin 27p
16 pin 15p 40 pin 30p
24 pin 26p

BOOKS

MOTOROLA

Diodes, Transistors, etc. over 3,500 pages £10.50
CMOS over 400 pages £1.50
Linear i.c. over 800 pages £2.00
Motorola M6800 Programming Manual £3.50
Motorola M6800 Applications Manual £7.00
From Minicomputers to Microprocessors £1.00

SIGNETICS

Data/Applications book over 1,600 pages £4.00
DMOS; 74LS; Consumer; shift registers;
RAM's; PROM's 20p each

FERRANTI

E-Line Applications 50p
Complete range of data and applications notes avail-
able 10p
No VAT this section

T.T.L.

N7400A 14p N7485B 117p
N7401A 14p N7490A 63p
N7402A 14p N7493A 48p
N7404A 18p N74121A 36p
N7405A 20p N74123B 90p
N7406A 41p N74132A 45p
N7410A 15p N74145B 90p
N7411A 21p N74147B 144p
N7412A 15p N74148B 126p
N7413A 25p N74153B 68p
N7414A 29p N74154B 144p
N7417A 27p N74155B 72p
N7420A 15p N74157B 68p
N7432A 25p N74174B 113p
N7440A 18p N74175B 81p
N7445B 135p N74181N 324p
N7460A 18p N74191B 144p
N7472A 24p N74192B 144p
N7473A 36p N74195B 90p
N7474A 30p N74196B 90p
N7475B 54p N74298B 128p
N7483B 99p

SPECIAL OFFERS

IN4148 Diodes:

12 for 50p.
30 for £1.00
1,000 for £25.00
5% Discount orders over £5.00
10% Discount orders over £10.00

Discount not applicable
to kits or special offers.

CAPACITORS

Electrolytic, paper, non-polar tant. Pack of 25 mixed (our
choice), 50p
Metal Tant:
6V—1, 3.3, 4.7, 56, 68, 180.
10V—150.
15V—4.7.
20V—0.1, 1, 39, 68.
35V—0.47, 0.56, 0.68, 0.82, 1.2, 1.8, 2.7, 3.3, 4.7, 10, 15, 33.
50V—3.3, 3.9, 10, 15, 22, 27, 50.
Plastic Tant: 6V—47.
Tubular:
20V—15.
35V—2.2, 3.3, 4.7, 6.8.
All values microfarads.
Your choice 10p each; pack of 20 mixed (our choice) £1.
Polystyrene—pack of 25 mixed 50p.

RESISTORS

1/2 watt carbon, Mullard CR37 10 for 20p
1/2 watt Metal Film, Welwyn MRS 10 for 50p
8 watt Wirewound, Welwyn W22 37p
12 watt Wirewound, Welwyn W23 39p
20 watt Wirewound, Welwyn W24 41p
CR37 and MRS. Min. quantity any one value 10 pcs.
E12 Series available to 1 MO except W23 and W24 up to
27k Ω only.

POTENTIOMETERS

Moulded Track—Panel Mounting
Lin—1W 250k Ω; 2M Ω.
Log—1/2W 10k, 500k Ω.
Min. Moulded Track Linear—Panel Mtg.
1/2W—22k Ω; 100k Ω; 220; 2M Ω
Open Min. Preset 1/2W Linear
100 Ω, 220 Ω, 250 Ω, 330 Ω, 470 Ω, 500 Ω, 1k Ω, 10k Ω,
25k Ω, 100 Ω, 500 Ω, 500k Ω, 1M Ω.
Sealed Min. Preset 1/2W Linear
33 Ω, 100 Ω, 220 Ω, 330 Ω, 500 Ω, 4k7, 5k Ω, 8k Ω, 22k Ω,
25k Ω, 50k Ω, 100k Ω, 500k Ω.
Your choice 10p each panel mtg., 5p each preset.
Pack of 10 (inc. 2 panel mtg.) 30p
Wirewound helical pots (10 turn) 100 Ω, 5 Ω, 50p each.

SOLDERING IRONS

Litesold 240V a.c.: 12 watt £3.16; 20 watt £3.22; 25 watt
£3.32.
Spare bits: 12 watt 10p; 20 watt 11p; 25 watt 14p.
Conqueror—light weight (35grm) high efficiency iron £3.15.
Spring stand for above irons £2.46.
Desoldering braid 5 foot reel 85p.

MULLARD TRANSISTORS—12 1/2% VAT

AC176/128 61p BC108 16p BD201 £1.30 BF337 42p
AD161/162 £1.20 BC108A 17p BD203 £1.30 BF338 47p
AC126 32p BC108B 13p BD232 £1.10 BFR90 £3.50
AC127 28p BC108C 21p BD233 60p BFR94 £7.00
AC128 19p BC109B 21p BD234 70p BFX84 41p
AC153 10p BC109C 28p BD235 68p BFX85 40p
AC176 25p BC147 9p BD237 70p BFY50 48p
AC176/181 25p BC148 7p BD238 80p BFY51 48p
AC187/188-01 95p BC148B 12p BF115 27p BFY90 £1.70
AC188 47p BC149 7p BF167 29p BR100 33p
ACY19 43p BC158 10p BF173 23p BR100-1 39p
ACY20 23p BC159 14p BF177 26p BR101 60p
ACY22 10p BV327 27p BF179 54p BR102 52p
ACY22D 10p BC328 25p BF180 47p BR103 50p
AD140 50p BC337 26p BF181 44p BR104 52p
AD149 69p BCY72 24p BF182 42p BSW67 96p
AF114 35p BD115 31p BF182 48p BSX19 32p
AF115 30p BD124 31p BF183 26p BSX20 42p
AF116 26p BD131 50p BF184 26p BSX20 42p
AF117 25p BD132 72p BF185 26p BSX20 42p
AF121 13p BD133 68p BF194 9p BSX20 42p
AF125 32p BD135 42p BF194B 14p BU126 £2.20
AF126 30p BD136 44p BF195 12p BU205 £3.00
AF139 42p BD138 59p BF196 13p BU206 £2.50
AF178 60p BD139 56p BF197 13p BU208 £4.00
AF239 90p BD140 68p BF200 30p GET103 6p
BAT10 £1.00 BD144 £1.80 BF240 20p GET887 6p
BAV10 11p BD160 £1.00 BF241 20p OC28 £1.00
BC107 18p BD181 £1.00 BF262 56p OC70 6p
BC107A 19p BD182 £1.00 BF263 56p OC75 6p
BC107B 15p BD183 £1.00 BF336 37p OC171 6p

MULLARD DIODES—12 1/2% VAT

AA119 11p BAX13 8p BY128 95p BYX36-600 p17
AA125 13p BAX17 19p BY164 41p BYX38-600 41p
AA213 10p BB105B 33p BY182 £1.10 BYX38-600R 59p
AA217 22p BB105G 29p BY184 41p BYX49-600R 43p
BA102 23p BR100 33p BY206 19p OA95 7p
BA154 10p BR100-1 39p BY207 27p OA200 13p
BA155 11p BR101 62p BYX10 23p OA202 9p
BA156 11p BY126 15p BYX36-150 23p OA2223 69p
BA182 23p BY127 13p

ZENERS—12 1/2% VAT

BZV10 59p BZX70C30 33p BZY91C15 £5.20 BZY95C15 68p
BZV15CR12 75p BZX79-4-7V-75V 10p BZY93C18 74p BZY95C18 68p
BZX61C27 10p BZY88C6V8 12p BZY93C20 74p BZY95C24 68p
BZX61C72 25p BZY88C13 12p BZY93C68 74p BZY95C68 68p
BZX70C11 33p

ALL PRICES EXCLUSIVE OF VAT WHICH MUST BE ADDED
VAT 8% EXCEPT ITEMS * 25% OR SPECIFIED CASH WITH ORDER
ADD 30p P. & P. U.K. £1 EEC COUNTRIES: NO OTHER EXPORT ORDERS ACCEPTABLE
CALLERS BY ARRANGEMENT ONLY

SYNTHESISERS AND KEYBOARDS

P.E. JOANNA

(P.E. May to Aug. 1975)

The new electronic piano that has switchable alternative voicing of Piano Honky-Tonk and Harpsichord. All PCB's are "as published".

Power Supply	£7.96
Tone Generator and Top C Envelope Shaper	£9.25
PCB for above	£1.30
Envelope Shapers	£32.16
12 sets (full requirement)	£15.00
Set of 12 PCB's (full requirement)	£8.37
Voicing and Pre-Amplifier Circuits	£1.84
PCB for above circuits	£14.50
Power Amplifier	95p
PCB for power amp	

KEYBOARDS

Kimber-Allen Keyboards as required for many published circuits, including the P.E. Joanna, P.E. Minisonic and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards made.


3 Octave Keyboard (37 notes C to C)	£20.50
4 Octave Keyboard (49 notes C to C)	£23.50
5 Octave Keyboard (61 notes C to C)	£27.00

Contact Assemblies for use with above keyboards: Single-pole change-over (SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (2P) as for P.E. Synthesiser. Special contact assembly (4PS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables the same keyboard to be used with the P.E. Synthesiser, P.E. Minisonic, and P.E. Synthesiser simultaneously thus avoiding the cost of more than one keyboard.

	3 Octave	4 Octave	5 Octave
Contact Each Set	Set	Set	Set
SP	20p	£7.40	£9.80
2P	24p	£8.88	£11.76
4PS	48p	£17.76	£23.52
			£29.28

Printed Circuit Boards for use with the above contacts and thus eliminating most of the inter-wiring required, are available—details in our lists.

PHONOSONICS

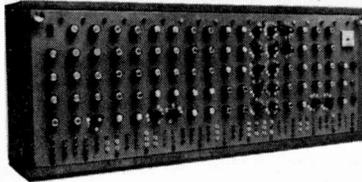

P.E. SYNTHESISER

(P.E. Feb. 1973 to Feb. 1974)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. All function circuits may be used independently, or interconnected. The greater the number of circuits, the greater the versatility. Other circuits in our lists may be used with the Synthesiser to good advantage.

THE MAIN SYNTHESISER

Stabilised Power Supply	£12.05
Two Linear Voltage Controlled Oscillators and one Inverter—all 3 circuits:	£16.38
PCB (2 are required)—each	£1.48
Two Ramp Generators and Two Input Amplifiers—all 4 circuits	£5.62
PCB (holds all 4 circuits)	£1.38
Sample-and-Hold and Noise Generator—PCB (holds both circuits)	£6.64
Tone Control, £2.43	PCB, 80p
Reverbation Amplifier	£6.36
Spring Line unit for Reverb Amp	£4.95
Ring Modulator	£3.75
Peak Level Meter Circuit	£1.50
100µA Panel Meter	
PCB for Rev., R-Mod. & Meter Ccts., Envelope Shaper, £5.33;	PCB, £1.46
Voltage Controlled Amp. and Diff. Amp.	£6.96
PCB (holds both circuits)	£1.32

THE SYNTHESISER KEYBOARD CIRCUITS	
Can be used without the Main Synthesiser to make an independent musical instrument)	
2 Log. Voltage Controlled Oscillators	£14.55
PCB for both log VCO's	£2.60
Divider, 2 Hold Circuits, 2 Modulation Amplifiers, Mixer and 2 Envelope Shapers	£19.64
PCB (Holds the first 6 circuits)	£1.80
PCB for both Envelope Shapers	£1.35
Keyboard Stabilised Power Supply	£7.30
Printed Circuit Board	94p



P.E. MINISONIC

(P.E. Nov. 1974 to March 1975)

A portable, battery or mains operated, miniature sound synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser, the functions offered by this design give it great scope and versatility.

Two Voltage Controlled Oscillators	£5.22
Voltage Controlled Filter	£3.41
and Voltage Reference Circuit	
Two Envelope Shapers and Two Voltage Controlled Amplifiers	£7.28
Keyboard Controller and Hold Circuits	£2.66
Keyboard Divider Resistors (select type to suit keyboard used, all are 2% tolerance), 2 Octave, £1; 3 Oct., £1.48; 4 Oct., £1.96; 5 Oct., £2.44.	
H.F. Oscillator and Detector	£1.66
Ring Mod., Noise Gen. & Env. Inverter	£5.27
Two Power Amplifiers and Two Mixers	£3.55
Battery Eliminator	£5.88
Temperature Stabiliser	£1.47
PCB to hold 2 VCOs, VCF and V-Ref	£2.02
PCB to hold 2 ESs, 2 VCAs, 2 Mixers, Ring Mod, Keyboard Control and Hold	£2.20
PCB to hold 2 Power Amps, Noise Gen, Envelope-Inverter, HF Osc. and Detector	£1.45
PCB for Battery Elim. & Temp. Stab.	£1.35

FOR ADDRESS, INFORMATION REGARDING POST AND PACKING VAT, LISTS, AND EXPORT TERMS SEE OUR ADVERTISEMENT ON OPPOSITE PAGE

Photos: 2 of our units containing some of the P.E. projects built from our kits and PCBs. (The cases were built by ourselves and are not for sale.)

HB ELECTRONICS

Mini Bulk Offers

All devices brand new and full spec. All prices include VAT.

1N4001/2	32p/10	BC108	85p/10
1N4003/4/5	48p/10	BC109	85p/10
1N4006/7	50p/10	BC212	95p/10
1N4148	20p/10	BFY50	£1.50/10
BC107	85p/10		£1.50/10

0-3 707 seven-seg. display	£5/4
Triac tab ended 8A 400V PIV	£3-10/3
741 op amp. 8 pin DIL.	£2-10/10
NE555 timer	£1-60/4
Red LED 0-2in	£1-00/10
Yellow LED 0-2in	£1-50/10
Green LED 0-2in	£1-50/10
Amber LED 0-2in	£1-50/10
Diode 6A 200V	£3-50/10
Jumbo display comm. anode	£2-75/2
Specials for June: mini slide switches £1.50/10; micro switches £1.50/5; MMS314 clock chip £3.50; MMS316 clock chip £5.50; SW power amp. I.C. from Sanyo (data supplied) £1.50.	

74 SERIES TTL

Type	Price	Type	Price	Type	Price
7401	12p	7441	62p	7482	45p
7402	12p	7442	55p	7493	40p
7403	12p	7445	71p	74100	89p
7404	13p	7447	78p	74121	28p
7405	15p	7474	26p	74122	39p
7406	15p	7476	26p	74141	83p
7408	15p	7483	75p	74145	58p
7410	13p	7486	26p	74174	83p
7413	31p	7490	40p	74177	£1-00
7432	25p	7491	55p	74196	£1-34

10% discount may be deducted from TTL prices for orders of 25 pieces or more

Large Stocks of Japanese transistors. Resistors (E12 values): ½W 2p each. Zeners: 400mW, 3V-30V 12p each. Submin. presets 12p.

HB ELECTRONICS

54 MONTAGU STREET, KETERING
NORTHANTS. Phone Kettering (0533) 83922
Shop open daily 9.30 a.m. to 6 p.m. (except Thursday, 9.30 a.m. to 2 p.m.)

Please add 30p for P. & P. to orders under £5, otherwise post free

MICROPROCESSORS

Provides general overview of the Technology, Design Ideas and Practical Applications.

by L. Altman. Price £9.25

NEWNES CONSTRUCTION GUIDE ELECTRONIC COMPONENTS Price £2.

NEWNES CONSTRUCTION GUIDE PRINTED CIRCUIT ASSEMBLY Price £2.

NEWNES CONSTRUCTION GUIDE ELECTRONIC DIAGRAMS Price £2.

ELECTRONICS POCKET BOOK by P. J. McGoldrick. Price £4.15.

T.T.L. COOKBOOK by D. Lancaster. Price £5.80.

WORLD RADIO TV HANDBOOK 1976 Price £5.

LINEAR I/C DATA AND COMPARISON TABLES Price £3.

THE POCKET CALCULATOR GAME BOOK by E. Schlossberg. Price £3.40.

THE RADIO AMATEUR'S HANDBOOK 1976 by A.R.R.L. Price £4.85.

RADIO VALVE AND SEMICONDUCTOR DATA by A. M. Ball. Price £2.50.

★ TOTAL PRICE INCLUDES POSTAGE ★


THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

INTERLOCKING PLASTIC STORAGE DRAWERS

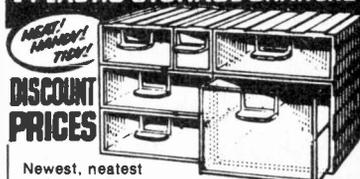

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

As supplied to Post Office, Industry and Government Dept.

SINGLE UNITS (1D) (5in x 2½in x 2½in). £2-40 DOZEN.

DOUBLE UNITS (2D) (5in x 4½in x 2½in). £4-20 DOZEN.

TREBLE (3D) £4-20 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £5-90 for 8.

EXTRA LARGE SIZE (6D1) £5-40 for 8.

PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%.
Orders over £60, less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES

Please add 8% V.A.T. to total remittance

FLAIRLINE SUPPLIES

(Dept. PE6)
24 Cricklewood Broadway, London NW2
Tel. 01-450 4844

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)
The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A MUST for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors) £13.05
8 channel component set (excl. thyristors) £22.56
Power supply component set £4.96
PCB for 4 frequency channels £3.32
PCB for power supply and 8 lamp drivers £1.56
1 Amp 400V thyristors (1 per chan. requ.) each 75p
Panel meter (1µA) (optional) £3.75

VOICE OPERATED FADER (P.E. Dec. 73)
For automatically reducing music volume during "talk-over" particularly useful for Disco work or for home-movie shows.

Component set incl. PCB £3.05

TAPE-NOISE LIMITER
Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB) £2.60
Regulated power supply (incl. PCB) £3.98

P.E. MINIMIX 6

DETAILS IN LIST

GUITAR EFFECTS PEDAL (P.E. July 75)
Will modify an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range.

Component set with special foot operated switches £6.25
Alternative component set with panel mounting switches £4.60
Printed Circuit Board £1.30

HI-FI TAPE-LINK (P.E. Mar./Apr. 73)
Designed for use with reasonable quality tape-decks, this high performance pre-amp includes record, playback and metering circuits. While stocks last.

Stereo component set (excl. panel meter) £24.25
Mono component set (excl. panel meter) £14.70
Power supply component set £5.93
Stereo main PCB £2.80
Stereo sub-assembly PCB 98p

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)
An independently designed VCF that can be used with the P.E. Synthesiser.

Component set £3.41
Printed circuit board £1.25

ENVELOPE SHAPER AND V.C.A.

The ADSR Envelope Shaper published in P.E. April 1976 and having its own voltage controlled amplifier and full manual control of its Attack, Release and Sustain functions.

Component set incl. PCB £5.43

AUTO WAH-WAH

Component Set and P.C.B. £2.99.

Transistors	BFY51	22p	2N3055	48p
AC128	20p	BFY52	24p	2N3702
AC176	20p	BSY95A	22p	2N3703
BC107	13p	MJE2955	110p	2N3704
BC108	13p	OC28	60p	2N3819
BC109	13p	OC71	14p	2N3822E
BC147	12p	OC72	14p	2N4871
BC148	12p	OC84	25p	2N5245
BC149	12p	ORP12	66p	2N5777
BC157	13p	ZTX107	12p	
BC158	13p	ZTX108	73p	
BC159	13p	ZTX501	13p	
BC182L	12p	ZTX503	15p	
BC184	12p	ZTX531	33p	
BC187	25p	2N4001	4p	
BC204	14p	2N706	13p	
BC209C	14p	2N914	22p	
BC212L	15p	2N1304	22p	
BC213	15p	2N2905	27p	
BC478	29p	2N2907	22p	
BCY71	22p	2N3053	18p	
BFY50	22p	2N3054	66p	
			Z5171	16p

RHYTHM GENERATOR

(P.E. Mar. Apr. 74)
Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and soft cymbal), and with variable time signatures and rhythm rates. Really fascinating and useful.
Tempo, Timing and Logic circuits £12.59
PCB for above circuits (double-sided) £2.94
Component set for all 8 effects circuits £10.49
Set of PCB's to hold all 8 effects £3.60
Simple mixer (no PCB available) £2.76
Alternative mixer with external volume controls and adjustable gain (independently designed), including PCB £9.93
Power Supply, including PCB £6.42

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.
Component set for above functions (excl. SWs) £6.58
Printed circuit board £1.58
Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.
Component set (incl. PCB) £2.55

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.
Component set (incl. PCB) £2.50

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.
Component set (incl. PCB) £3.75

ENVELOPE SHAPER

The ADSR Envelope Shaper published in P.E. October 1975 and having manual control of its Attack, Release and Sustain functions.
Component set incl. PCB £4.16

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.
Component set incl. PCB £2.83

POWER SUPPLIES

Sophisticated low-noise highly-stabilised power supply kits complete with PCB's and detailed information are now available. Details in list.

Other PCBs (all "as published") While stocks last
Bench Power Supply (P.E. Sept. 1974) 70p

CCTV:
Master Logic, Video Amp., Sync Mixer and Cathode Switch PCB (P.E. Oct. 1974) £2.20
PCB for remaining Circuits (P.E. Oct. 1974) £2.20
Digital Power Supply (P.E. Aug. 1972) 50p

Electronic Piano:
Pre-amp PCB (P.E. Oct. 1972) 85p
Power Supply PCB (P.E. Oct. 1972) 60p

Power Slaves: Power Supply PCB (P.E. Aug. 1974) 55p

Rondo:
Pre-Amp PCB (P.E. Oct. 1973) 60p
Tone, Balance and Volume Control PCB (P.E. Oct.) £1.40

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module £3.71
Component set and PCB

Basic Output Circuits
Combined component set with PCBs, for alphaphone cardiophone, frequency meter and visual feedback lamp driver circuits £5.39

Audio Amplifier Module £5.50
Type PC7

SINE AND SQUARE WAVE GENERATOR (P.E. July 75)

Suitable for audio, digital, or general purpose. Controllable through 4 decade ranges 10Hz to 100kHz. Switched attenuation through 10 ranges from 10V to 1mV peak-to-peak.
Component set £8.88
PCB for above components £1.60
Power Supply £5.70
PCB for Power Supply 96p

P.E. TUNING FORK

(P.E. NOVEMBER, 1975)
Main component set incl. PCB £13.50
Power supply set incl. PCB £6.57

REVERBERATION UNIT (P.V. Nov./Dec. 72)

A high quality unit having microphone and line input pre-amps, and providing full control over reverberation level.
Component set (excl. spring unit) £7.55
Printed circuit board £1.76
9 inch spring unit £4.95
Panel meter (50µA) (optional) £3.75

SEMI-CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.
Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB £8.44
Panel meter (500µA) £3.75

PHOTOPRINT PROCESS CONTROL (P.E. Jan./Feb. 72)

For colour and B & W, an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage. While stocks last.
Component set (excl. meter) £10.72
Printed Circuit Board £1.74
Panel meter (1mA) £3.75

P.E. SYNCHRONOME

(P.E. MARCH, 1976)
COMPONENT SET £10.20
PRINTED CIRCUIT BOARD £1.70

PHOTOCOPIES

Of P.E. texts for most of our kits are available. Prices in our lists.

SEE OUR LIST FOR OTHER GOODS STOCKED

Prices are correct at time of press. E. & O.E. deliveries subject to availability.

LIST
Send S.A.E. with all U.K. requests for free list giving fuller details of PCBs, kits, and other components.
Overseas enquiries for list: Europe—send 20p. Other countries—send 40p.

POST AND HANDLING
U.K. orders: under £15 add 25p. over £15 add 50p.
Optional: Fee for compensation against loss or damage in post (U.K., Eire & C.I. only): 35p.

VAT
Add 12½% (or current rate if different) to full total of goods, post and handling.
Overseas—VAT does not currently apply.

Overseas—will be charged extra. minimum charge 74p. Details of kit weights, and postage rates will be sent with list.
Eire and Channel Isles classify as overseas for posting purposes.

PHONOSONICS, DEPT. PE46, 22 HIGH STREET, SIDCUP, KENT DA14 6EH MAIL ORDER AND C.W.O. ONLY DON'T FORGET VAT!

Sparkrite mk2

Capacitive discharge
electronic ignition

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service — phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept. PE6,
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

	QUANTITY REQD.
Mk. 2 DIY Ass. Kit @ £11.80	
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's
for £

Cheque No.

Send SAE if brochure
only required.

Join the Digital Revolution

Understand the latest
developments in calculators,
computers, watches, telephones,
television, automotive instrumentation. . .

Each of the 6 volumes of this self-instruction course measures 11½" x 8½" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers. Design of Digital Systems.

£6 · 20

plus 80p packing and
surface post anywhere in
the world.

Payments may be made in
foreign currencies.

Quantity discounts available
on request.

VAT zero rated.



Also available—a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4 · 20

plus 80p P. & P.

Offer Order both courses for the
bargain price £9·70, plus 80p
P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises (Dept. ENG)
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me... set(s) of Design of Digital Systems at £7·00 each, p & p included

*or... set(s) of Digital Computer Logic and Electronics at £5·00 each, p & p included

*or... combined set(s) at £10·50 each, p & p included

Name

Address

*delete as applicable

No need to use a stamp—just print FREEPOST on the envelope. PE6


New Books on Electronics

MAIL ORDER SERVICE

EXPERIMENTS WITH OPERATIONAL AMPLIFIERS

George B. Clayton

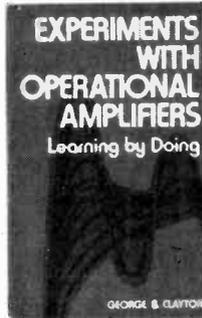This book covers a wide range of practical operational amplifier applications; it provides circuits which include component values, and suggests measurements that can be made in order to study circuit action. £3.35



LINEAR INTEGRATED CIRCUIT APPLICATIONS

George B. Clayton

This book is concerned with the newer circuits now available which find their main use in signal measurement and processing systems.

A practical approach is emphasised throughout and the reader is encouraged to try out the devices for himself. The applications of operational amplifiers as measurement amplifiers and in active filter circuits are dealt with. Subsequent chapters are concerned with the more recently introduced linear integrated circuits, including monolithic integrated circuit modulators, four quadrant multipliers, timers, waveform generators and phase locked loops. £4.90

Also available

ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRONIC ENGINEERS

Noel M. Morris

A handy reference book, A4 size for easy use, containing all the formulae necessary to the student and engineer in a wide variety of disciplines. It is up-to-date and includes a section on SI units as well as resistor colour codes and preferred values. £1.35

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS

Noel M. Morris

Using the example of the electronic calculator to illustrate many of the systems, this book begins with a description of basic logic functions, including a full coverage of boolean algebra and Karnaugh maps. It then goes on to describe high-speed switching elements, logic gates, calculating functions, asynchronous and synchronous counters, shift registers and display decoding circuits. £2.65

ELECTRONIC EQUIPMENT RELIABILITY

J. C. Cluley

The principles of assessing the reliability of electronic equipment, including the mathematical background, and methods to improve reliability are described and explained at a level suitable for degree and diploma students. £2.90

LINEAR ELECTRONIC CIRCUITS AND SYSTEMS

G. D. Bishop

This book covers linear electronic circuits from basic a.c. theory to modern integrated-circuit configurations, with the minimum of mathematics. It takes the 741 IC as a typical example, and illustrates the use of the operational amplifier in many different applications. £2.65

SEMICONDUCTOR ELECTRONICS BY WORKED EXAMPLE


F. Brogan

Intended for students taking Technician, Telecommunications and HNC/D courses, this large format, clearly laid-out text teaches the theory and practice of solid-state electronics by answering questions from past examination papers. All circuits, devices and systems discussed are related to today's technology, designs and developments. £2.90

MODERN COMMUNICATION SYSTEMS

R. F. W. Coates

This book presents a broad coverage of electronic communication systems. It emphasises the latest technical developments in the industry itself and provides a detailed and comprehensive treatment of the necessary Fourier transformed methods, which are also required in other areas of electronics. Also discussed are the various methods of modulating sinusoidal carrier waves. Modern circuit techniques are introduced wherever possible, particularly those suitable for integrated circuit fabrication. £6.35

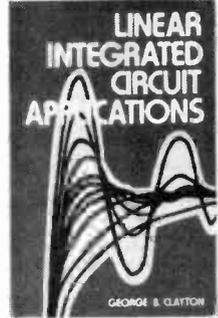

ELECTRONIC COMPONENT TESTING

W. F. Waller

Shows how to test the working parameters of electronic components. Contents include semi-conductors and integrated circuits. £1.35

ELECTRONIC MEASUREMENTS

W. F. Waller

A practical survey by specialist authors from industry of the methods and instrumentation necessary to obtain useful measurements of electrical quantities. £1.35

ELECTRICAL COMMUNICATIONS THEORY, WORKED EXAMPLES AND PROBLEMS

R. G. Meadows

This book provides degree, diploma and higher technician students with summarised notes, worked examples and exercise problems in electrical communications. £3.65

ELECTRONIC SYSTEMS FOR RADIO, T.V. AND ELECTRONICS MECHANICS

Rhys Lewis

This book covers, in non-mathematical terms, the fundamental theory and application of electronic systems, and includes work on fault-finding and system reliability. It meets the requirements of the 'systems' side of the CGLI Course 222, Radio, T.V. and Electronics Mechanics Parts I and II, and gives objective tests similar to those met in the examination. £2.80

AN INTRODUCTION TO ELECTRICAL INSTRUMENTATION

B. A. Gregory

A comprehensive introduction to the growing number of increasingly sophisticated instruments available for use by engineers and technicians. Coverage includes interference, calibration, accuracy, and a discussion on the selection criteria advisable when matching instruments to requirements. £4.35

COMING THIS AUTUMN!

Semi-Conductor Devices

Noel M. Morris

This book explains the principles of modern electronic devices. The function and use of each device is demonstrated in practical circuits and applications. Non-active and active semi-conductor devices are covered, including charge-coupled devices, and one chapter summarises the currently available range of optoelectronics. Tick here if you would like to be informed when this one is available.

All these are available from


Technical Book Services, 25 Court Close, Bray, Maidenhead, Berkshire SL6 2DL.

Please tick the titles you want and enclose cheque/P.O. for the correct remittance made payable to Technical Book Services. All prices include post and packing.

Name

Address

INVERTORS

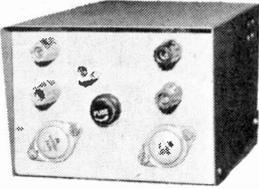

240v-50Hz from your 12v car battery.

25 watt—£4.75 300 watt (24v)—£26.45
40 watt—£8.27 400 watt (12v)—£39.05
75 watt—£12.03 500 watt (24v)—£48.10
150 watt—£21.27 1kW (50v)—£127.00
300 watt (12v)—£33.03 1.5kW (110v)—£140.00

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 + £1.70p. & p.


FLUORESCENT LIGHT INVERTOR KIT
8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.
12"-8 watt—£3.90 + 35p p. & p. Built up—£4.80 + 35p p. & p.
21"-13 watt—£4.20 + 52p p. & p. Built up—£5.80 + 52p p. & p.

TRANSFORMERS & COILS

Both high volume & small order capacity available.
Special offer. Miniature mains transformer 12-0-12v-6V.A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

P.E. ORION STEREO AMPLIFIER

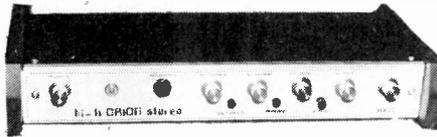

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response \pm 1dB 20 Hz to 20 kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.


Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £47.30 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

INSTRUMENT CASES

Bookend Amplifier and attractive styled Instrument Cases available. Send S. and A. envelope for Price List.

ASTRO IGNITION

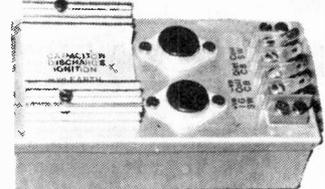

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 incl. VAT. Ready built with only two connections to alter £13.75 incl. VAT. Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS

Spring Bank Road, West Park
Chesterfield.

Random FLASHER UNIT
Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random
£18.95

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14 1/2 inches
BC Fitting **£9.55** EACH
ES Fitting **£10.35** EACH

Sound to Light MASTER UNIT
600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OF TWIN PLUGS AND MAINS INPUT SOCKET

TYPE A SPOT
(less lamp)
BC Fitting **£1.95** EACH
ES Fitting **£2.12** EACH

TYPE B 3 BANK UNIT
(Less Lamps)
BC Fitting **£6.90** EACH
ES Fitting **£7.26** EACH

TWIN BANK 12 LIGHT UNIT
(less lamps) Length 31 1/2
BC Fitting **£15.60** EACH
ES Fitting **£17.00** EACH

100 WATT SPOT LAMPS
RED, YELLOW, GREEN, BLUE, CLEAR
3 lamps
£1.18 each
B.C. or E.S. Fitting **£3.54**

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)
Send 20p for illustrated leaflet & price list.
ALBEN ENGINEERING CO LTD.
DEPT. PE THE CRESCENT, WORSTHORNE,
BURNLEY, LANCS. Tel Burnley 20940

ALWAYS SHELVES FULL OF ODD UNITS, CHASSIS, etc. Many bargains for callers. Lists also available S.A.E.

12in LONG PERSISTENCE CRT. New, boxed. Last few 100 to clear. Callers only. £1 each.

MIN. TRANSFORMER. 240V input. 3V 1A output. Brand new. Now only 25p each. P. & P. 50p.

WIDE RANGE WOBBLATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls. preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £8.75, P. & P. 35p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges, independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8.85 each. SINE WAVE only £8.85 each. P. & P. 35p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each. P. & P. 8p.

NEW—UPGRADED CONTENTS—FOR LESS MONEY. * 3lb electronic goodies, £1.60 post paid. * High value printed board pack—hundreds of components, transistors, etc.—no flat to the board transistors. £1.65 post paid.

GRATICULES 12 x 14cm high quality plastic 15p each. P. & P. 10p. * 1000pF feed thru capacitors 10 for 30p, P. & P. 15p. * CAPACITOR pack 50 brand new components only 50p, P. & P. 48p.

FIBREGLASS BOARD PACK. More board—less money. Larger pieces. Not less than 2.5 sq. ft for 95p, P. & P. 65p. Double or single sided cut to any size. New lower price 1p per sq.in. P. & P. extra.

***METER PACKS—**3 different meters £2, P. & P. £1.

SOME OSCILLOSCOPES ALWAYS AVAILABLE. S.A.E. stating specification and price range.

***TRIMMER PACK.** 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 15p.

***PHOTOCELL** equ. OCP71, 13p each.

***TELEPHONES.** Post Office Style 746. Black or two tone grey £8.50 each. Modern Style 706 Black or two tone grey £4.50 each. Modern Standard Style in grey or black with a place to put your fingers like the 746, £3 each. As above but discoloured grey only £2 each All telephones complete with standard dial and bells. P. & P. all styles 75p each.

HANDSETS complete with 2 inserts and lead £1.75 each. P. & P. 65p.

***CRYSTALS.** 4-43MHz. Brand new. Now at 25p each, P. & P. 15p.

***BEEHIVE TRIMMERS** 3/30pF. Brand new. 10 off 46p, P. & P. 15p; 100 off £3.50, P. & P. 75p; 500 off £15, P. & P. £1.25; 1,000 off £25, P. & P. 1.50.

MUFFIN FANS. 115V, size 5 x 5 x 1 1/2in. Superbly quiet and reliable. Ex eq. but tested. £1.50 each, P. & P. 75p.

***POT PACK.** All brand new modern. Single and ganged. Our choice. 7 for 25p, P. & P. 48p.

BNC PLUG TO BNC PLUG LEAD. Assembled ready to use 75p each. P. & P. 20p. Ex-eq. BNC socket 15p. BNC plug 20p. BNC Plug and Socket 30p, pair, P. & P. 15p.

Minimum Mail Order £2... excess postage refunded.
VAT NOT INCLUDED IN PRICE
Goods marked * 12 1/2% VAT, otherwise 8%
OPEN 9 a.m. to 5.30 p.m. ANY DAY

CHILTMHEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel. Reading 582805

barclay

ELECTRONICS

TECHNOLOGICAL
PRECISION PRODUCTS

DECIMO

VATMAN SCIENTIFIC (Illus.)—Large green display. 8-digits, 2 exponents, 4 trig log functions 10^{99} , radian degrees, exchange, memory, π , reciprocal, X^2 , etc. Single function keyboard. 20 hr battery life. **£27-50***



MINI-VATMAN—Green display, smaller and slimmer than 8-digits, % key. **£8-90***

MINI-VATMAN M—As above but with % and full-function memory. **£11-50***

VATMAN (Illus.)—8-digit, % key, green display. **£9-75***



SUPER-VATMAN—Similar to above but with full-function memory, X^2 , reciprocal, π , $\sqrt{\quad}$. **£12-75***

ROCKWELL

63R (Illus.)—8-digit, 2 exponent, 10^{99} memory, 2-level parentheses, all trig and log functions, degree radian, factorial, reciprocal, π , $\sqrt{\quad}$, etc. Rechargeable. **£27-95(R)**



61R—Green display, 8-digits, all trig and log functions. **£21-95(R)**

51R—8-digits, metric and currency converter. **£21-95(R)**

8R—8-digits, % key. **£8-75***

20R (Illus.)—8-digits, % key, full-function memory. **£10-95***



31R— $\sqrt{\quad}$, memory, memory exchange, reciprocal, X^2 . Rechargeable. **£15-95***

24RD—Green display, $\sqrt{\quad}$, 8-digit. **£13-75***

24K (Illus.)—Stainless-steel slimline, green display, beautiful leatherette wallet to hold pen, note-pad (all included) and credit cards. Full memory. $\sqrt{\quad}$, click-buttons. Rechargeable. **£21-95(R)**



CASIO

FX-20 (Illus.)—Full trig and log functions, 8-digit mantissa or 6-digit mantissa and 2-digit exponents; 10^{99} to 10^{-99} , bright green display, full sin, cos, tan, inverse sin, inverse cos, inverse tan; log X and ln x, e^x , X^x , $\sqrt{\quad}$, reciprocal degree radian conversion; memory and exponent key. **ONLY £16-85***



FX-15—As above but larger and including a larger display. X^2 key, π key, reciprocal key. **ONLY £20-85***

FX-101—De Luxe model with similar functions to the FX-15 but 8-digits + 2 exponents 10^{99} to 10^{-99} . **OUR PRICE £25-85***

8R—Memory, % key. **£8-95***

POCKET 8s—% key. **£7-95***

POCKET MINI-MEMORY—% key, bright green display. **£9-95***

ALL ITEMS CARRY A FULL YEAR'S GUARANTEE

* Free B.S.I. adaptor. (R) Free re-charger.

NOVUS

4520—8-digit, 2 exponent, 10^{99} RPN logic, full trig and log functions, 4-roll stack, memory, memory exchange, $\sqrt{\quad}$, degree and radian. Rechargeable. **£22-90(R)**



4525—Rechargeable. Programmable version of 4520. **£45-90(R)**

4510—8-digits, 3 level stack, all trig and log function, $\sqrt{\quad}$, π , reciprocal, memory, etc. **£14-90***

4515—100-step programmable version. **£37-90(R)**

6020—Financier **£17-95***

6025—Financier 100-step programmable. Rechargeable. **£45-90(R)**

2030—Statistician. **£17-80***

6035—100-step programmable Statistician. Rechargeable (inc. recharger) **£45-90(R)**

TEXAS

SR50A (Illus.)—10-digit, 2 exponent, all trig and log functions, hyperbolic, X to the root of Y, radian and degree, factorial, memory, etc. Rechargeable. **£35-90(R)**



SR51A—As above but with 3 independent memories, linear regression, mean, variance, standard deviation, permutation, random number generation plus 20 basic conversions and their inverse. Rechargeable. **£49-90(R)**

T1200 (Illus.)—8-digit, % key. **£8-95***




T1250—As above with memory. **£9-95***

JUST ARRIVED—THE NEW TEXAS SR56

100-step programmable—10-digit, 2 exponents, 10 independent memories, 2 loop control instructions, 4 additional and 3 unconditional branch instructions, plus 4 levels of subroutines, all log, trig and statistical functions! **£79-95**

Digital Watches

EXELAR

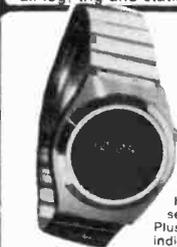

5-Function digital watch in stainless-steel finish with matching bracelet. Shows hrs, mins, date. Plus a.m. indicator and fade-out.

Gold finish **£23-90**

THE SUPERB 10-function PULSTRONIC



Shows date and month in correct order! Single button control. Display visible in pitch dark. Hrs, Mins, Secs. Date + Month. Day of Week, self-adjusting calendar. Auto hold and fade-out. A.M. setting. Indicator. P.M. setting. Indicator. Undoubtedly one of the most sophisticated watches available at this unbeatable price! Styled in finest solid Stainless-steel, satin finished with polished bevelled edges. Complete with adjustable matching stainless-steel bracelet AND a FREE presentation box.

LIMITED SUPPLIES
ONLY £37-40

ASTRA



3-Functions. Shows hrs, mins and secs. Single button operation. Limited supplies at this low price. **ONLY £13-95** with strap. **Gold finish £15-95**

ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS-THURS BETWEEN 2 and 5 p.m., SUNDAY 10 a.m. to 1 p.m. 01-458 4755.

To: BARCLAY ELECTRONICS Dept. PE7B, TEMPLE FORTUNE, 1115 FINCHLEY ROAD, LONDON N.W.11

Please send me
with/without optional mains adaptor. I enclose cheque/money order
total value £..... including 55p to cover P. & P.

NAME
ADDRESS

barclay

CBM

4148R (Illus.)—10-digits, 2 exponents Full log and trig functions. X^2 , Reciprocal, π , X root of Y. Polar rectangular co-ordinates. 2-store memory. Rechargeable. Mean and Standard deviation. **£32-50(R)**



S1800—Similar to the 4148R. Green display. Battery operated **£24-50***

7919D—Students Scientific. Full trig and logs, 8-digit or 5 + 2 exponents. Reciprocal, π , $\sqrt{\quad}$, memory. **£13-90**


796D—8-digits, % and store. **£6-75***

997R—Rechargeable % and full memory. **£12-50(R)**


ALL PRICES INCLUDE VAT.
Please add 55p P. & P.

PRECISION PETITE LTD. Dept. P.E.
119A HIGH STREET,
TEDDINGTON TW11 8HG
Tel. 01-977 0878

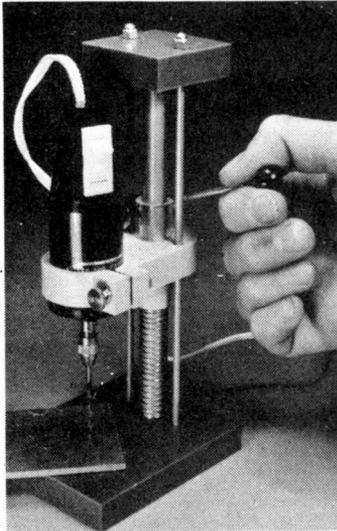**INTRODUCING A
MINIATURE
PRECISION 12V. D.C.
DRILL DESIGNED FOR
THE ELECTRONIC
ENGINEER**



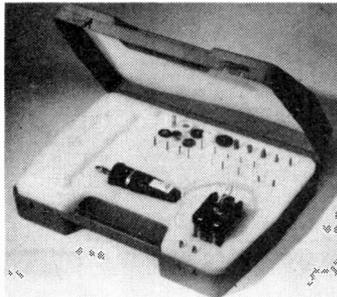Mk. II Drill only
£8.00 p.p. 35p
Stand £3.76 p.p. 58p




Complete kit as illustrated (less batts.) with a variety of 30 tools. Space for Stand and Transformer.

KIT 30 TOOLS £16.00 p.p. 75p
STAND £3.76 p.p. 35p
TRANSFORMER £5.50 p.p. 75p

**S.A.E. FOR
DETAILS**

FULL SPEC. LEDs

Packs of 5—Inc. clips and data

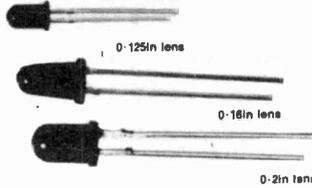

Red 75p; Green, Yellow, Orange £1.20.

ECONOMY QUALITY LEDs

Mixed bags. All colours of all sizes—ideal for experimenters: 50 for £5; 100 for £8.

**FULL SPEC. LED SEVEN
SEGMENT DISPLAYS**

0.3in common anode.
L.H. decimal.
Red, Green, Yellow, £1.35 each inc. data.



ECONOMY QUALITY
0.3in common anode. L.H. decimal.
Red, 73p each.

PLASTIC BOXES

COLOUR GREY



ABS—Ribbed inside on 5mm centres for 1.5mm PCB. Brass corner inserts for securing top with 3mm screws.

62mm x 112mm x 31mm, 1-9 52p each; 10 + 48p each.
120mm x 65mm x 40mm, 1-9 86p each; 10 + 82p each.
150mm x 80mm x 50mm, 1-9 75p each; 10 + 71p each.

POLYSTYRENE—Plain inside. Top secured by self-lapping screws. 61mm x 112mm x 31mm, 1-9 35p each; 10 + 32p each.

SPECIAL OFFER

Sample Pack, 4 boxes—1 of each size, £2.10.

NEON INDICATORS

240V (built-in resistance)—150mm lead out wires



Fit 8mm hole and include spire clip for fixing. Red, Amber, Clear, Opal—19p each; Green—23p each.
Type MP—Fits 6.4mm hole—nut fixing. Red, Amber, Clear, Opal, 22p each.

LAMPHOLDER DH

Takes either LES (with adaptor provided) or Midgast Flange Bulbs. Fits 13mm hole—nut fixing. Red, Blue, Green, Amber, Clear, Opal, Orange, 25p each (bulbs not provided).



Quotations for larger quantities on request. All prices include VAT at 8%. Please add 20p P. & P. on orders under £10. On orders for boxes please add 25p per £1, minimum 25p maximum £1.50.

**MICHAEL WILLIAMS
ELECTRONICS**
47 Vicarage Avenue
Cheadle Hulme, Cheshire SK8 7JP

GIRO NO 331 7056 Access and Barclay card accepted
C.W.O. only Terms of business as in our Catalogue
Export Order enquiries welcome (15 min.)
Official Orders accepted from Educational and Government Departments.
ALL PRICES include VAT and P. & P.
SHOP HOURS 9.12.30 - 1.30 - 5.00 - DAYS
CLOSED WEDNESDAY

1976 ISSUE 66 PAGES—3,000 ITEMS FULLY ILLUSTRATED
*20p CREDIT VOUCHERS
*ALL NEW STOCK
*SATISFACTION GUARANTEED
*DISCOUNTS
*NEW PRICE LIST FOR CAT. 4a S.A.E.

25p plus 19p postage

Boxes — Cases —
Kits — PC Materials —
Tools — Resistors — Test
Meters — Capacitors —
Hardware — Semiconductors —
Books — Pots — Coils —
Audio Accessories — Screws
Connectors — Audio — Modules
— Veroboard — Transformers —
Knobs — Calculators — Audio Leads
— Batteries — S dec Storage Units —
Heatsinks, etc. etc.

COMPONENTS
Catalogue 5
ORS LTD.

SPECIAL CAPACITOR KITS
C280 Kit—PC Mounting polyester 250V 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22uF, 2 of 0.47, 1uF, £1.98 net
C296 Kit—Tubular polyester, 400V, 5 of each value 0.01, 0.022, 0.047, 0.1, 0.22uF, 2 of 0.47uF, £2.87 net
Ceramic Kit—square plaques, 50V, 5 of each value, 22, 33, 47, 100, 220, 330, 470, 1000pF, 220, 4700pF, 0.01uF, £1.68 net.

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices include post & packing) 10E12 1W or 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 £5.29 net
25E12 1/4W or 1/8W KIT: 25 of each E12 value, 22ohms—1M, a total of 1425 £12.84 net

B. H. COMPONENT FACTORS LTD.

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—300mA in 5 ranges
Resistance—5Ω—1MΩ in 4 ranges
Accuracy—5% of F.S.D.
OSCILLATOR—1KHz and 485KHz (A.M.) at approx. 1 Volt.
Size—180 x 87 x 40mm
Supplied complete with carrying case, test leads and battery
PRICE £9.95 net P. & P. 75p

U4323

MULTIMETER U4324
34 Ranges. High sensitivity. 20,000Ω/Volt.
Vdc—0.6—1200V in 9 ranges
Vac—3—900V in 8 ranges
Idc—0.06—3A in 6 ranges
Iac—0.3—3A in 5 ranges
Resistance—25Ω—5MΩ in 5 ranges
Accuracy—dc and R—2% of F.S.D.
ac and db—4% of F.S.D.
Size—187 x 98 x 63mm
Supplied complete with storage case, test leads, spare diode and battery
PRICE £11.72 net P. & P. 75p

U4324

MULTIMETER U4341
27 Ranges plus Transistor Tester. 18,700Ω/Volt.
Vdc—0.3—900V in 8 ranges
Vac—1.5—750V in 6 ranges
Idc—0.06—600mA in 5 ranges
Iac—0.3—300mA in 4 ranges
Resistance—2KΩ—2MΩ in 4 ranges. Accuracy—dc—2%, ac—4% of F.S.D.
Ife—10—350 in 2 ranges
Size—115 x 215 x 90mm
Complete with carrying case, test leads, and battery.
PRICE £12.10 net P. & P. 75p

U4341

MULTIMETER U4313
33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy, mVdc—75mV.
Vdc—1.5—600V in 9 ranges
Vac—1.5—600V in 9 ranges
Idc—60—120 microamps in 2
Idc—0.6—1500mA in 6 ranges
Iac—0.6—1500mA in 6 ranges
Resistance—1KΩ—1MΩ in 4 ranges.
db scale—10 to +12db
Accuracy—dc—1%, ac—2%
Size—115 x 215 x 90mm
Complete with carrying case, test leads, and battery.
PRICE £16.09 net P. & P. 75p

U4313

(P.E.), LEIGHTON ELECTRONICS CENTRE,
59 NORTH STREET, LEIGHTON BUZZARD, LU7 7EQ.
Tel. Leighton Buzzard 2316 (Std. Code 05253)

Do Something Useful for a Change!

Do it in your spare time. And enjoy it. And, perhaps, you'll save yourself some money. The secret is to be practical about the way you spend your spare time.

These practical magazines show you how. Every month these six popular titles are packed with fascinating and constructive projects – full instructions for making your own furniture and fittings for the home as well as electronic gadgets for home, car or hobby.

See which 'practical' can widen your range of interests, whether in home-improvement, hi-fi or electronics – and on jobs you really could call useful.

everyday electronics

June issue : a waa waa pedal, an enlarger meter, a peak-level indicator and a continuity tester.

OUT MAY 21

30p

PRACTICAL WIRELESS

June issue : a digital frequency meter, talking transistors and a fault-finding guide.

OUT MAY 7

35p

PRACTICAL ELECTRONICS

June issue : a proportional radio-controlled system, an audio millivoltmeter and a rally milometer.

OUT MAY 14

35p

PRACTICAL HI-FI & AUDIO

June issue : 15 top pick-up cartridges compared, 12 pages of in-car entertainment and how an innocent fares on her first hi-fi shopping spree.

OUT MAY 14

30p

Television

June issue : a Decca 10/30 chassis service, a Pye 173 chassis service, a simple grey-scale generator and video-tape copying.

OUT MAY 17

40p

PRACTICAL WOOD WORKING

June issue : a pull-out booklet on hinges and fittings, a model traveller's van, a traditional-style spinster's chair and an ironing table.

OUT MAY 21

40p

Be Practical...Get a 'Practical' Today!

If you are unable to obtain a copy of any of the above titles from your newsagent, please contact :
Sales Manager, IPC Magazines Ltd., 66 Great Queen Street, London, WC2B 5DD

MIX PRICES	TTL		
	1-24	25-99	100+
7400	14p*	12p*	10p*
7401	14p*	12p*	10p*
7402	14p*	12p*	10p*
7403	15p*	12p*	10p*
7404	16p*	13p*	11p*
7408	16p*	13p*	11p*
7409	16p*	13p*	11p*
7410	16p*	13p*	11p*
7413	29p*	24p*	20p*
7417	27p*	22p*	20p*
7420	16p*	13p*	11p*
7427	27p*	22p*	18p*
7430	16p*	13p*	11p*
7432	27p*	22p*	18p*
7437	27p*	22p*	18p*
7441	75p*	62p*	50p*
7442	65p*	55p*	43p*
7445	85p*	71p*	57p*
7447	81p*	75p*	65p*
7448	75p*	62p*	50p*
7447A	95p*	83p*	67p*
7470	30p*	25p*	20p*
7472	25p*	21p*	17p*
7473	30p*	25p*	20p*
7474	32p*	26p*	21p*
7475	47p*	39p*	31p*
7476	37p*	26p*	21p*
7487	75p*	62p*	50p*
7485	£1.30*	£1.09*	87p*
7486	35p*	26p*	21p*
7489	£2.92*	£2.80*	£2.10*
7490	49p*	40p*	32p*
7491	65p*	55p*	45p*
7492	57p*	46p*	36p*
7493	45p*	40p*	32p*
7495	67p*	55p*	45p*
74100	£1.06*	89p*	73p*
74107	35p*	29p*	23p*
74121	34p*	28p*	23p*
74122	47p*	39p*	31p*
74141	78p*	63p*	51p*
74145	68p*	58p*	48p*
74154	£1.62*	£1.48*	86p*
74174	£1.00*	83p*	67p*
74180	£1.06*	89p*	71p*
74181	£3.20*	£2.50*	£1.90*
74192	£1.35*	£1.14*	90p*
74193	£1.35*	£1.14*	90p*
74196	£1.64*	£1.34*	99p*

LIGHT EMITTING DIODES

	0.125" dia. lens (TTL209)			0.16" dia. lens			0.2" dia. lens (MLED 650)		
	1"	10"	100"	1"	10"	100"	1"	10"	100"
Red	14p*	15p*	13p*	20p*	18p*	16p*	17p*	16p*	15p*
Green	26p*	24p*	22p*	26p*	24p*	22p*	26p*	24p*	22p*
Orange	26p*	24p*	22p*	26p*	24p*	22p*	26p*	24p*	22p*
Yellow	26p*	24p*	22p*	26p*	24p*	22p*	26p*	24p*	22p*

I.C. SOCKETS

Pin Sockets, pins in strips of 100. Just snip off what you need. 65p per strip.

Dual in line

8 pin 13p..	24 pin 26p.	10S
14 pin 15p	28 pin 30p.	8 pin 31p.
16 pin 15p	36 pin 39p.	10 pin 35p.

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p*(inc. VAT) (leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone CIVE for details.

LINE-O-LIGHT DISPLAYS

NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual in-line package. Ideal for solid state analogue meters or dials. Red and Green £3.25*. Check on Yellow, some in stock now.

0.33 Litronix DL 707 Series
 0.33 Monsanto MAN 50/70/80/3600
 0.33 Xciton XAN 70 Series
 0.43 Monsanto MAN 4000 Series
 0.63 Litronix DL747 'Jumbo' Series

PHOTO-DARLINGTON

V_{ceo} 25v 2N5777
 V_{ceo} 25v
 V_{zbo} 8v
 I_t 250 mA
 P_d 200 mW
 h_{fe} 2500

Low cost Red GeAsP Motorola MLED 500 in a T092 package

MULLARD MODULES

Still make the simplest, highly reliable F.M. tuner

LP1186 Varactor front end £7.74
 LP1185 I.F. Strip £6.25
 LP1400 Multiplex decoder £8.12

NOTE: MAN 4000 Series pin outs are 14 pin ditl the same as MAN 50, 70 and 80 series.

Our Bulk Buying Power enables a repeat of our Special Offer.

0.33" (LIT 707) 99p* (inc. VAT) Performance guaranteed.

3 1/2 DECADE DVM I.C.

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507


Short Form Catalogue

for your free copy send a S.A.E.

OPTO-ISOLATORS

ILI 4N25 or TIL116
 6 pin industry standard package
 2.5KV isolation £1.00*

C. Mos	Linear	Zenon	Regulators	Resistors	Switches
Audio I.C.'s	Memories	Rectifiers	Triacs	Pots	Boxes
Radio I.C.'s	Diodes	Heat Sinks	SCR's, SC'S	Vero	Tuning Cons.
TV I.C.'s	Transistors	Capacitors	Bridges	Coils	Connectors

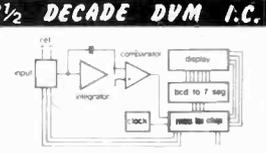

MAINS TRANSFORMERS

Secondaries	1A	1A	2A	4A
6-0-6V 100 mA 99p*	0-9-17V	-	£2.49*	£3.57*
9-0-9V 100 mA 99p*	0-12-15-20-74-30V	-	£3.47*	£4.65*
12-0-12V 100 mA 99p*	0-24-30-40-48-60V	-	£5.18*	£7.02*
20-0-20V 1 A £3.45*	0-19-25-33-40-50V	£3.47*	£4.65*	£7.24*
24-0-24V 0.5A £2.95*				
28-0-28V 1 A £3.95*				

P & P on transformers 20% of price, min. 25p.

OUR PRICE ONLY £6.59* (Data and Circuit Booklets alone 20p.)

VAT INC

Items followed by a * inc. VAT at 8% all others include 12 1/2%
 Overseas customers deduct 1/3% from items—1/3% from others
 Postage and Packing 25p Orders for over £8 post free. Except transformers
 Data Sheet and photocopy service available at 10p per page CALLERS ARE WELCOME

SYNTHESISER Modules by Dewtron®

The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p's; sample/hold/envelope module; 3-octave keyboards, contacts, special tuning-ladder resistors, etc. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 20p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown Dorset BH22 9AR

G8CZW DIGITAL FREQUENCY METER

COMPLETE KIT £54.00 inc. VAT and Post

ZN1040E Count/Display I.C.	£8.90	I.C. Sockets Pack	£2.30
Integrated Circuit Pack	£9.25	Switches, Knob, BNC Sockets, etc.	£4.15
DL707's and Filter	£7.28	Hardware and Wire Pack	£1.45
Semiconductor and Diode Pack	£2.38	Case—two-tone PVC-faced steel punched and lettered (+ 75p P & P.)	£5.75
Resistor and Capacitor Pack	£2.88	Spare min. BNC Sockets (50 ohm)	65p
Logic and Display P.C.B.s	£4.84	Spare min. BNC Plugs (50 ohm)	70p
5MHz Crystal	£3.45		
Transformer 8-0-8V (+ 40p P. & P.)	£2.48		

All prices inc. VAT at the standard rate Please add 20p P. & P. for packs. S.A.E. for lists.

abc Electronics (Oldham) Ltd.

83 Lees Road, Oldham OL4 1JW. Tel. 061-624 8812

Due to the time lag involved in publishing, readers are advised to check with advertisers about changes in prices, post Budget VAT rates, etc., before sending any money orders or cheques.

DESIGNED BY TEXAS



30,000 ALREADY SOLD
Texan Amplifier
 as featured by
PRACTICAL WIRELESS
 SOLE U.K. DISTRIBUTORS - HENRY'S

Build it yourself for only

£32 KIT PRICE INC. VAT + £1.00 p&p.
 Built and tested £42.00 inc. VAT + £1.00 p&p.

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.
Look at the Texan specification
 Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibre pcb; Gardeners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 8" x 2" overall. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

★ Can be built Stage by stage
 Ask for leaflet 5
 ★ Everything necessary supplied
 Full after sales service and guarantees.

TEXAN FM TUNER KIT **£23.50**
 inc. VAT + 50p p&p

Built and tested £28.50 inc. VAT + 50p p&p.
 Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.
THE NATURAL FOLLOW-ON

Henry's latest ELECTRONICS CATALOGUE

- ★ over 5000 items - many new
- ★ free 50p voucher inside every copy
- ★ virtually everything needed by amateurs and professionals
- ★ over 200 pages, complete alphabetical index
- ★ section index
- ★ everything at competitive prices

FREE to Educational Establishments when ordered on official headed notepaper

VIDEO SPORT



An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered. List Price £42.50

HENRY'S PRICE £25.00
 inc. VAT + 50p p&p
 ★ OVER 10,000 ALREADY SOLD
 ★ IDEAL GIFT

For this latest edition, we have made hundreds of changes and additions. Features now include:

TRANSISTOR & VALVE DISCOUNT PRICE LIST
 OVER 2000 TYPES SEND FOR YOUR FREE COPY



All mail to: Henry's Radio
 303 Edgware Rd. London W2

- LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381
- LONDON W1: 231 Tottenham Ct Rd. ^{lower sales floor} Tel: 01-636 6681
- * NOTTINGHAM: 94/96 Upper Parliament St. Tel: (0602) 40403
- * READING, BERKS: 130/131 Friar Street. Tel: (0734) 583230
- * HARROW: 190/4 Station Road. Tel: 01-863 7788
- * CROYDON: 110 North End. Tel: 01-681 3310

Please Note: Mail Order Customers **VAT DOWN** HENRY'S WILL CREDIT ANY VAT OVERPAYMENTS

NEW STORES

TRANSFORMERS

ALL EX-STOCK - SAME DAY DESPATCH. VAT 8%

MAINS ISOLATING
 Prim. 120/240V. Sec. 120/240V
 Centre tap with screen

Ref. No.	VA (Watts)	£	F & P
07*	20	3-77	58
149	60	4-69	72
150	100	5-33	85
151	200	8-54	12
152	250	10-32	41
153	350	12-47	41
154	500	14-33	61
155	750	21-84	BRS
156	1000	30-57	BRS
157	1500	34-89	BRS
158	2000	38-92	BRS
159	3000	61-48	BRS

115V or 240V sec. only*

30 VOLT RANGE
 Prim. 200/240V. Sec. 0-12-15-20-24-30V

Ref. No.	VA Amps.	£	F & P
112	0-5	1-90	58
113	1-0	2-52	72
3	2-0	3-77	72
20	3-0	4-70	85
21	4-0	5-58	85
51	5-0	6-75	97
117	6-0	7-52	-12
88	8-0	10-20	-25
89	10-0	10-36	-41

60 VOLT RANGE
 Prim. 200/240V. Sec. 0-24-30-40-48-60V

Ref. No.	VA Amps.	£	F & P
124	0-5	2-48	72
126	1-0	3-68	72
127	2-0	5-33	85
125	3-0	7-90	97
123	4-0	8-19	-41
40	5-0	10-24	-25
120	6-0	12-07	-41
121	8-0	15-75	BRS
122	10-0	19-40	BRS
189	12-0	20-25	BRS

SCREENED MINIATURES P & P

Ref. No.	VA	Voits	£	P
238	200	3-0-3	1-42	39
212	1A, 1A	0-5, 0-5	1-93	46
13	100	9-0-9	1-58	25
235	330, 330	0-3, 0-3	1-84	25
207	500, 500	0-8-0, 0-8-0	2-02	51
208	1A, 1A	0-8-0, 0-8-0	3-07	58
236	200, 200	0-15-0, 0-15-0	1-58	25
214	300, 300	0-20-0, 0-20-0	2-83	58
221	700 (d.c.)	20-12-0, 12-20	2-38	58
208	1A, 1A	0-15-20, 0-15-20	1-58	25
203	500, 500	0-15-27, 0-15-27	3-15	72
204	1A, 1A	0-15-27, 0-15-27	4-14	72
S112	500	12-15-20, 24-30	1-97	58

BRIDGE RECTIFIER

VA	2A	35p
100V	2A	40p
220V	1A	45p
400V	1A	65p
600V	2A	50p
500V	10A (PM 7A6)	£2-35

P & P 15p VAT 12 1/2%

TEST METERS

AVO 8 MK5	£5-88
AVO 72	£21-72
AVO MM5	£20-94
AVO TT169	£24-52

Cases and Accessories P & P £1-10. VAT 8%

ANEX ETHERING IRONS

15W £2-90, 18W £2-70, 25W £2-45
Kit £3-90
Stand for above £1-13.
P. & P. 25p. VAT 8%

MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR
 Operating voltage 20-45V
 only £2-65 P. & P. 18p. VAT 12 1/2%

BSR MINI-DECK
 4 Speed Autochanger £5 00
 P. & P. 72p. VAT 12 1/2%

NEW STEREO 30 COMPLETE STEREO CHASSIS INC:
 7 + 7W RMS AMP. Pre-amp, power supply, front panel, knobs (needs mains trans.). Stereo 30. £15-75. Mains trans. £2-45. Teak veneered cab. £3-85. P. & P. 85p. VAT 12 1/2%

PLEASE ADD VAT AFTER P & P
 Audio Accessories and Bargain Component Paks.
 Semi-Conductor stockists.
 Callers welcome (Mon-Fri) or send stamp for lists

Barrie Electronics Ltd.
 3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/8
 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

12 AND OR 24 VOLT PRIMARY 240-250 VOLTS P & P

Ref. No.	VA	12V	24V	£	P
111	0-5	0-25		1-54	58
213	1-0	0-5		1-86	58
71	2	1		2-41	58
18	4	2		2-97	72
70	6	3		4-43	72
108	8	4		5-09	85
72	10	5		5-50	85
116	12	6		5-80	97
17	16	8		7-48	97
115	20	10		10-91	1-61
187	30	15		14-20	1-41
226	60	30		17-67	BRS

50 VOLT RANGE
 Prim. 200/240V. Sec. 0-10-15-25-33-40-50V

Ref. No.	VA Amps.	£	F & P
102	0-5	2-71	58
103	1-0	3-55	72
104	2-0	4-95	85
105	3-0	6-10	97
106	4-0	7-98	1-12
107	6-0	12-71	1-25
118	8-0	13-63	1-61
119	10-0	17-75	BRS

AUTO TRANSFORMERS P & P

Ref. No.	VA	Auto Taps	£	P
113	20	0-115-210-240	1-75	51
84	75	0-115-210-240	3-05	72
4	150	0-115-200-220-240	4-33	72
86	300	0-115-200-220-240	6-11	85
87	500	0-115-200-220-240	9-38	1-25
84	1000	0-115-200-220-240	14-36	1-61
93	1500	0-115-200-220-240	18-92	BRS
95	2000	0-115-200-220-240	25-41	BRS
73	3000	0-115-200-220-240	38-84	BRS

CASED AUTO TRANSFORMERS
 240V mains lead input and U.S.A. 2-PIN outlets:

Ref. No.	VA	£	P & P
20VA	£3-20	P. & P. 72p	113W
150VA	£8-37	P. & P. 85p	4W
500VA	£10-97	P. & P. £1-25	87W
1000VA	£18-39	P. & P. BRS	84W
2000VA	£28-71	P. & P. BRS	95W

HIGH VOLTAGE MAINS ISOLATING
 Prim. 100/120V or 400/440V
 Sec. 100/120V or 200/240V

VA	Ref.	£	P & P
60	243	4-37	97
350	247	10-93	1-41
1000	250	28-31	BRS
2000	252	44-12	BRS

PLUS

POWER UNIT
 CC12-05 Output Switched
 3-4-5-6-7-5-9-12V at 500mA. £4-08. P & P 48p. VAT 12 1/2%

HIGH QUALITY MODULES

3 W RMS Amplifier	£2-30
5W RMS Amplifier	£2-85
10W RMS Amplifier	£3-95
25W RMS Amplifier	£3-95
Pre-Amp for 3-5-10W	£4-03
Pre-Amp for 25W	£13-20
Power Supplies 3-5-10W	84p
Power Supplies 25W	£3-00
Transformer 3W	£1-48
Transformer 10W	£2-13
Transformer 25W	£2-80
P. & P. Amps/Pre-Amps/Power Supplies 18p	
P. & P. Transformers 37p. VAT 12 1/2%	

ELECTROLIT METAL OXIDE RESISTORS

Style	Tol.	Omic Range	Price/per 100
TR4	2%	10Ω-300kΩ	£10-50
	5%	10Ω-300kΩ	£8-00
TR5	2%	10Ω-470kΩ	£2-50
	5%	510kΩ-1MΩ	£2-80
TR6	2%	10Ω-47Ω	£18-50
	2%	51Ω-510kΩ	£7-50
	2%	500Ω-2MΩ	£16-50
TR8	2%	10Ω-91Ω	£18-50
	2%	100Ω-100kΩ	£10-50
	2%	110kΩ-1MΩ	£17-50

QTY-P.O.A. P. & P. 25p/100

Practical Electronics Classified Advertisements

RATES: 13p per word (minimum 12 words). Box No. 35p extra. Semi-Display £10'00 per single column inch. Advertisements must be prepaid and addressed to GMG Classified Advertisement Manager, Room 2337, "Practical Electronics" IPC MAGAZINES LTD., Room 2337, King's Reach Tower, Stamford Street, London SE1 9LS. Tel. 01-261 5918

RECEIVERS AND COMPONENTS

MINIATURE CARBON FILM RESISTORS. 5%, 1W, 1/2W, E12 Series. 22ohm to 1MΩ. 10 for 15p, 50 for 50p, 100 for 85p, p. & p. 10p. Mixed values and wattages to your choice. OANDAR, Fréepost, Reading RG1 1BR.

LED	S	0-125	0-2	INFRA RED
	G/Y	15p	19p	550W Axial lead 40p
panel clip 1p	OR	27p	33p	1.5mW 11-55 6mW 11-55 ORP12 55p

OPTO-ISOLATORS		SCR's	50V	100V	400V
IL74	1.5kV, 150kHz	1	T05 1A	25p	27p
4350	2.5kV, 5MHz	£2-25	TR66 3A	27p	35p

Data free with all OPTO		TRAC	T05	2A	400V	80p
-------------------------	--	------	-----	----	------	-----

AC125/6/7/8	15p	2N2926(G)	12p	VOLTAGE REGS	
AD161/162	40p	2N3053	15p	5V 7805 Plastic	
AF117	20p	2N3054	45p	12V 7812 1 Amp	
AF124/5/6/7	34p	2N3055	41p	15V 7815 all	
BC107/8/9	9p	2N3702/3/4	12p	18V 7818 11-50	
BC109C	12p	2N3903/4/5/6	16p	723 DIP14	50p
BC147/8/9	10p	2N2846	35p		
BC157/8/9	11p	MPP102	40p	BRIDGE RECTS.	
BC167/8/9	11p	2N3819	25p	2A 50V	30p
BC169C	12p	2N3823	30p	2A 100V	36p
BC177/8/9	17p			2A 200V	41p
BC182/3/4/L	11p	BR100 Diac	21p	2A 400V	46p
BC186/7	30p	IN817	3p		
BC212/3/4/L	12p	IN4001	5p	ZENERS BZY88	
BC7Y07/17/2	13p	IN4002/3	6p	2-7-33V	9p
BF194/5	12p	IN4004/5	7p	NE555V	60p
BF196/7	14p	IN4006/7	8p	NE556	£1-10
BFY50/51	18p	IN4148	4p	LM380	£1-10
BFX29	30p	OA4	7p	ZN414	£1-10
BFK84	24p	OA70 OA79	7p	7400	16p
BK18/20	16p	OA81 OA95	6p	D.I.L. SOCKETS	
OC71	10p	OA200	6p	8-pin	12p
2N706	10p	OP.AMPS	7p	14-pin	13p
2N1711	20p			16-pin	14p
2N2219	20p			Mica + bushes	
2N2904/5/6/7	15p	709 all	25p	T03	T066
2N2905/6/8	18p	741 8-pin	29p	TO66	5p
2N2926(R)	17p	748 D.I.L.	36p	Dalo Pen	70p

PRICES INCLUSIVE + 15p P. & P. (1st class)

ISLAND DEVICES, P.O. Box 11, Margate, Kent

SEMI-CONDUCTOR CATALOGUE now ready, including data and applications, 15p, inc. post. **AUDIO-OPTICS**, 19 Middleway, Chinnor, Oxon.

250 WATTS

Power amplifier. 1 volt input. Output into 4 or 8 ohms.

Silicon transistors, all standard types.

Guitar or microphone two input preamp with level, bass, treble and extra high switch.

Microphone preamp 200 ohms to 50k, for stage use. Will take overload up to 300 mV without distortion. Level and gain controls.

Ready drilled circuit boards and all construction information.

Prices include tax and postage.

250 Power amp £2-25
Guitar preamp £1-20
High level preamp 90p

ALFA ELECTRONICS

96a Glengall Road, London, N.W.6
S.A.E. for more information. Mail order only

TURN YOUR SURPLUS capacitors, transistors, etc. into cash. Contact **COLES-HARDING & CO.** P.O. Box 5, Frome, Somerset. Immediate cash settlement.

A-MP 14 PIN DIL IC HOLDERS with non-rev's clip, 11p each; 10 for £1. Coupled Isolator 4N25 6 pin Dil, 90p; 10 for £8. Zener diodes. IN5341B 6-2 volts 5 watts, 8p each; 10 for 70p. BZX79 5-1 volts 400 mW, 8p each; 10 for 60p. 1Z15 15 volt 1 watt, 10p each; 10 for 90p. IN914 50 for £1. Motorola 2N3055, 50p each, 10 for £4-50. Liner Zener Diodes 6v, 7v, 8v, 9v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 35v, all 10p; 20p each. Bush for T.I.P. transistors, 10 for 20p; 100 for £1-75. MPS955 and MPS952, 30p each; 10 for £2-50. Minimum post 20p. All prices include VAT. All components full spec. **FIELD ELECTRIC LTD.**, 8 Shenley Road, Boreham Wood, Herts. 01-958 6009

£1 inc. VAT (plus 33p P. & P.) for the following:

1 Mains T/F 240V PRI/240V 20mA + 20V 50mA SEC
1 Pulse T/F
1 HV spark T/F
1 Di-charge tube Seimens KASO2
1 Motorola Uni Junction 2N4871
1 Ferranti transistor ZTX450 and heat sink
1 AC128 A7314 transistor
1 A fuse 250V 20mm x 5mm
1 20mm x 5mm P.C. MTG fuse holder
6 Diodes
13 Capacitors
12 Resistors

All the above are mounted on a P.C. board but guaranteed unused.

Some boards fitted with up to 3 continental cradle leads. These will be despatched to the early birds whose orders are received first, at no extra charge.

PAYLOR CONTROLS LTD.
1 Wellington Gardens
Bury, Lancs. BL8 2PQ

BRAND NEW COMPONENTS BY RETURN!

Electrolytic Capacitors 16V, 25V, 50V - 0.47, 1.0, 2.2, 4.7 and 10mF 5p; 22, 47 5p (50V 6p); 100 7p (50V 8p); 220 8p (50V 10p); 500 11p (50V 16p); 1,000 (16V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p. Subminiature Tantulum Bead Electrolytics - 0.1, 0.22, 0.47, 1.0, 2.2 at 30V, 4.7/25V 11p; 10/25V, 22/16V, 47/8V and 100/3V 12p.

Mullard Min. Ceramic E12 Series 63V 2% - 10-47pF 3p; 56-330pF 4p. Ceramic plate 50V E12 series 22-1,000pF and E6 series 1,500-47,000pF 2p.

Polystyrene E12 Series 63V Horizontal Mounting - 10-1,000pF 3p; 1,200-10,000pF 4p.

Mullard Polyester 250V Vertical Mounting E6 Series - 0.1-0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 8p; 0.68 11p; 1.0 13p; 1.5 20p; 2.2 22p.

Mylar (Polyester) Film 100V Vertical Mounting - 0.001, 0.002, 0.005 3p; 0.01, 0.02 3p; 0.04, 0.05 4p.

Miniature Resistors Highest. E12 Series 5% - Carbon Film 1/4W 10-10MΩ (10% 1M up) 1p; Metal Film 1/4W 10-2MΩ 1.5p; Metal Film 1/2W 10Ω-2MΩ 1.5p; Metal Film 1W 27Ω-10MΩ 1.75p.

1N4148 3p; 1N4002 3p; 1N4006 7p; 1N4007 8p; BC107/8/9, 147/8/9, 157/8/9, BF194/7 8p.

Fuses 20mm glass, 1/4in glass, 1in ceramic 3p. Post 10p (free over £4). Prices inclusive of VAT.

THE C.R. SUPPLY CO.
127 Chesterfield Road, Sheffield S8 0RN

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Tapped Auto Transformer, 240V-110V, 80 watts, £2 P.P. New.

Heat Sinks 5 x 4in, drilled for 2 T03 transistors. New 65p.

Transformer 240V primary 25 volts at 1 1/2 amps. New £2. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 x 1 1/2 in with circuit, £1-75 P.P.

Crouzet Geared Motors 240V. 5/6/15/20 r.p.m. New £1-75 P.P.

Panel with 3 l amp F/W bridge rect. 6 transistors, 5 pre set pots, etc., etc. Price 3 for £1-75 P.P.

Panel with 2 small Burrough's Nixie tubes, £1-65 P.P.

Panel with 220 approx. marked IC's only £4-50 inc. VAT. P.P.

Memory Array Panel. £1-50 inc. VAT. P.P.

Electrolytic Capacitors, 2,500 at 40V. Size 3 x 1 1/2in. 2 for £1 P.P. NEW.

Transformers, 12-0-12V, 100mA, £1-25 inc. P.P. 9-0-9V, 100mA, £1-25 inc. P.P. 6-0-6V, 100mA, £1-25 inc. P.P.

Transformer, 22 volt, 100mA, £1-25 P.P.

Transformer, 45 volt, 2 amp, £3-38 P.P.

P.C. Board, S/S, 5 1/2 x 5 1/2in, 10 for £1-10 P.P.

Power Unit Components Transformer, 18 volt 1 amp F/W bridge rectifier, 2 1/250 mfd capacitors, all new £1-60 per kit. P.P.

Mixed Pack of C280 series Mullard capacitors, 100 for £1-30 inc. P.P.

Tel. 061-236 1541
All prices include VAT and P.P.

500 COMPONENTS. Resistors, capacitors, diodes, transistors, pots, coils, etc. Identified, formed leads, fall-out and surplus. Good value at £1-60. All inclusive (U.K. postal rates only). C.W.O. please to: L. PENSENERY (PE), Bankhead Farm, South Queensferry, West Lothian.

Precision Polycarbonate Capacitors

All High Stability - extremely Low Leakage

440 V A.C. RANGE			63V D.C. RANGE		
Value (µF)	Dimen- sions (mm)	Price each	Value/µF	±%	±5%
0.1	27	12.7	0.01-0.2	±1-28	75p 50p
0.15	27	12.7	0.22-0.47	±1-32	75p 51p
0.22	33	16	0.68	±1-44	84p 56p
0.25	33	16	1.0	±1-56	91p 60p
0.33	33	16	1.5	±1-74	1.16 67p
0.33	33	16	2.2	±1-98	1.32 76p
0.47	33	19	3.3	±2-40	1.80 89p
0.5	33	19	4.7	±2-82	2.18 1.23
0.68	50	8	6.8	±3-48	2.82 1.47
1.0	50	8	10	±4-98	3.32 2.01
1.5	50	8	15	±7.14	4.76 2.68
2.0	50	8	22	±9.66	6.44 2.99

TANTALUM BEAD CAPACITORS - Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8µF at 15V/16V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. All at 15p each, 10 for £1-10, 50 for £5, 100 for £9.

TRANSISTORS & I.C.'s

BC107/8/9 9p *BC212/212L 12p 2N3055 60p
BC114 12p *BC213/213L 11p OC71/2 80p
BC147/8/9 10p *BC214/214L 11p *NE555Timer 61p
BC157/8/9 11p *BF194/5 7p *741C Spin DIL 18p
BC154/7/8/9 16p BFY60/1/2 80p
BC182/182L 11p AF178 40p ZN414 £1-15
BC183/183L 11p AF234 88p SN76013ND
BC184/184L 12p *2N3702/4 11p

POPULAR DIODES - 1N914 6p, 8 for 45p, 18 for 90p; 1N918 6p, 6 for 45p, 14 for 90p; 1844 6p, 11 for 80p, 26 for £1-00, 1N4148 5p, 6 for 27p, 12 for 45p; 1N4001 5p; 502 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p; 008 8p; 009 8p; 010 8p; 011 8p; 012 8p; 099 8p; 100 8p; 101 8p; 102 8p; 633 8p;

MAD, MAD PRICES FOR TTL!!

(All famous makes. Prices include VAT)

7400	0-09	7447A	0-71	74107	0-27
7401	0-10	7448	0-73	74109	0-54
7402	0-10	7450	0-11	74121	0-27
7403	0-10	7451	0-11	74122	0-43
7404	0-10	7453	0-11	74123	0-54
7405	0-10	7454	0-11	74141	0-65
7406	0-27	7460	0-11	74145	0-70
7408	0-11	7472	0-22	74150	1-05
7410	0-09	7473	0-24	74151	0-65
7411	0-20	7474	0-25	74153	0-65
7412	0-16	7475	0-44	74154	1-38
7413	0-27	7476	0-27	74155	0-65
7414	0-65	7480	0-38	74157	0-86
7417	0-26	7483	0-74	74160	1-05
7420	0-10	7484	0-87	74164	1-19
7422	0-20	7485	1-03	74174	0-97
7425	0-26	7486	0-27	74175	0-92
7427	0-26	7489	2-70	74181	1-94
7430	0-11	7490	0-35	74190	1-25
7432	0-24	7491	0-54	74191	1-25
7437	0-24	7492	0-38	74192	1-08
7440	0-11	7493	0-38	74193	1-08
7441	0-63	7495	0-54	74195	0-76
7442	0-57	7496	0-69	74196	1-03
7445	0-60	74100	0-97	IN4148	0-02
ZTX107	0-09	ZTX108	0-07	ZTX109	0-09
IN4001	0-04	IN4003	0-04	IN4004	0-04

Intel 2102 1k Memory £3

DL707E 0-3in. Display 0-69

Min. order £2. P. & P. 20p (1st class) C.W.O.

Send S.A.E. for full list

J. C. JONES (Dept. PE18)
46 Burstellars, St. Ives, Cambs.
PE17 4XX
(Mail Order only)

TAPES

TAPETALK

THE NATURAL WAY TO LEARN

Two C60 cassettes entitled

INTRODUCING TRANSISTORS

£5-44 plus 55p VAT/P. & P.

TAPETALK, P.O. Box 99 (PE)

Milton Keynes MK3 5BR

Tel.: Milton Keynes (0908) 77710

ELECTRICAL

STYLING AND CARTRIDGES. For the best at keenest prices send SAE for free illus. list to **FELSTEAD ELECTRONICS (PE)**, Longley Lane, Gatley, Cheshire, SK8 4EE.

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. **KINGS PATENT AGENCY LIMITED** (Est. 1886). B. T. King, Director, M.I.Mech.E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

TAPETALK

THE CLEVER WAY TO LEARN

TWO C60 Cassettes entitled

INTRODUCING ELECTRONICS

£5-44 plus 55p VAT/P. & P.

TAPETALK, P.O. Box 99 (PE)

Milton Keynes MK3 5BR

Tel.: Milton Keynes (0908) 77710

COLOUR TV SERVICING.

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from: **ICS SCHOOL OF ELECTRONICS, Dept.**

771T, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

BOOKS AND PUBLICATIONS

TV REPAIRS MADE EASY

Four easy to follow repair manuals cover the mono sets and three cover the colour sets from the early dual standards to date. Priced at only £3-50 each, you just send make/model no. (chassis type if possible) plus cost to receive manual covering the set by return. P. & P. 50p up to £3, £1 over 3.

British Colour TV Circuit Diagram Manuals in 2 vols, cross referenced to the above repair manuals at £8-50 (P. & P. £1) each. All mono sets circuits in 1 huge manual for same price.

TV TECHNIC, 76 Church St., Larkhall, Lanarks ML9 1HE
Tel. (0698) 883334

LOGIC. Reliable step-by-step design techniques for the non-specialist are described in a new Oxford book, "Problems and Solutions in Logic Design", by D. Zissos (1976). Over 50 problems with fully worked out solutions demonstrate the design steps. Obtainable from your bookseller, £3-50; paper covers £1-75.

START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience.

Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc., etc. A goldmine of information and knowledge. Only £3-65 plus 25p P. & P. From:

MAGNUM PUBLICATIONS, Dept. PES
Brinksway Trading Estate, Brinksway
Stockport SK3 0BZ

Overseas Distributors wanted.

SERVICE SHEETS

SERVICE SHEETS, radio, TV, etc. 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. **TELRAY,** 154 Brook Street, Preston, PR1 7HP.

BELL'S TELEVISION SERVICES for service sheets, manuals and books on Radio/TV, etc. Service sheets 50p plus S.A.E. Service sheet catalogue 25p. Back issues of magazines from April, '74 onwards. Cover price plus 12p post. Free booklists on request. S.A.E. with enquiries please to: **B.T.S. 190 Kings Road, Harrogate, Yorkshire.** Tel. Harrogate (0423) 55885.

SERVICE SHEETS for radio, TV, tape recorders, stereo, etc., with free fault-finding guide, 50p and S.A.E. **HAMILTON RADIO,** 47 Bohemia Road, St. Leonards, Sussex.

EDUCATIONAL

TECHNICAL TRAINING.

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from: **ICS SCHOOL OF ELECTRONICS, Dept.**

771T, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

CITY & GUILDS EXAMS.

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from: **ICS SCHOOL OF ELECTRONICS, Dept.**

771T, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

LADDERS

LADDERS, varnished 20' 9" extd. **£19-82.** Carr. £1-40. Leaflet. Also aluminium ext. and loft ladders. Tel. Telford 586644.

FOR SALE

OSCILLOSCOPE. Advance 1000 Dual Trace. Hardly used, **£150** o.n.o. Bradford (0274) 615082.

GENERAL PURPOSE TRANSISTORS—mixed lots of ME4003, BC108 and BC109—**£25** per 1,000. **G.R. INTERNATIONAL ELECTRONICS LTD.,** Almondbank, Perthshire, Scotland, PH1 3NQ.

WE HAVE 5 x QUAD CP 50E Power Amps in stock, which we would dearly like to clear. They are boxed, new. Will sell for **£55** each or **£250** all together. Phone 888 7487. Ask for **Remy.**

PRACTICAL ELECTRONICS. Complete set unbound. Nov. '64—May '76, except Dec. '73. Offers: **Mr. ANGEL.** 01-736 4057.

P.E. MAY 69. Electronic Organ, complete or sections. Reasonable offers to: **HILL, 14 Rothsay Terrace, Bedlington, Northumberland.**

AKAI TAPE RECORDER, minus electronics, suitable for P.E. Tape Link, **£12-50.** **SHEPPARD,** 17 Westbourne Avenue, Hull.

LIMITED OFFER, MM5314 clock chips, full spec. with data, **£2-65** inc. P. & P. L.B., 43 Westcott, Hayes, Middlesex, UB4 8AH.

CHEAP UNUSED COMPONENTS for sale, resistors, transistors, condensers, relays, switches, etc. Send for list to: **G. WATTS,** 236 Dill Hall Lane, Church, Nr. Accrington, Lancs.

FOR SALE. Home constructed 3-manual electronic organ; 95% complete, excellent buy for amateur electronics engineer. Only **£120** o.n.o., worth many more times this amount in components alone. Also large speaker cabinet **£150.** will sell separate if required—**RAVENS, THORPE UNITED REFORMED CHURCH (42),** c/o 18 Uplands Drive, Mirfield, WF14 9LY. Tel. 495149.

PRIVATE SELLER has seven, three octave keyboards c-c **£8** each. S.A.E. for details: **R. FOLLETT,** 26 Arbor Lane, Winnersh, Berks., RG11 5JD.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

MISCELLANEOUS

PRINTED CIRCUIT BOARDS. Supplied complete, glass fibre with a soldering varnish finish. (6p per sq. in. P. & P. 30p). **R. DARLISON,** 1 Valentine Drive, Oadby, Leicester. Tel. (0533) 716273.

ENAMELLED COPPER WIRE

S.W.G.	1/2 reel	1/2 reel
16 to 19	£2-40	£1-35
20 to 29	£2-45	£1-40
30 to 34	£2-60	£1-50
35 to 40	£2-85	£1-60

All the above prices are inclusive of postage and packing in the U.K.

COPPER SUPPLIES

102 Parrwood Road, Withington,
Manchester 20
Telephone 061-445 8753

MISCELLANEOUS

BUILD THE TREASURE TRACER MK III Metal Locator



- Variable tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete Kit **£12.50** Post 85p - £1.00 VAT (8%)
 Built and tested **£17.50** Post 85p - £1.40 VAT (8%)
MINIKITS ELECTRONICS, 66 CLEVELAND ROAD, LONDON E18 2AN (Mail Order Only)

SUPERB INSTRUMENT CASES by Bazell, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples, Width, Depth, Height, 8" x 5" x 3" **£1-55**; 10" x 6" x 3" **£2-20**; 12" x 6" x 3" **£2-70**; 14" x 6" x 3" **£2-95**; 10" x 8" x 3" **£2-75**; 12" x 8" x 3" **£3-20**; 14" x 8" x 3" **£3-60**; 12" x 10" x 3" **£3-60**; 8" x 4" x 4" **£1-80**; 10" x 6" x 4" **£2-70**; 12" x 6" x 4" **£2-85**; 14" x 6" x 4" **£3-25**; 12" x 8" x 4" **£3-60**; 14" x 8" x 4" **£3-80**; 7" x 7" x 5" **£2-65**; 8" x 10" x 6" **£3-60**; 12" x 8" x 7" **£4-24**; 14" x 8" x 7" **£4-80**; 12" x 10" x 7" **£4-25**; 12" x 12" x 7" **£4-40**; 14" x 10" x 7" **£5**; 12" x 10" x 8" **£5**; 14" x 10" x 8" **£5-30**; 14" x 12" x 7" **£5-20**; 12" x 12" x 8" **£5-50**; 14" x 12" x 8" **£5-60**. Plus 72p Carriage and 8% VAT. 16" x 8" x 8" **£7-60**; 16" x 10" x 8" **£8-40**; 18" x 8" x 8" **£9-50**; 18" x 10" x 8" **£10-30**; 19 1/2" x 8" x 8" **£11-50**; 19 1/2" x 10" x 8" **£12-30**. Plus £1-25 Carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). **BAZELLI, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.**

I.C. EXPERIMENTERS' KITS

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, L.E.D.s, and Instructions. Available at **£3.50** each (including P. & P.)
 Kit One—Gates Kit Two—Flip-Flops
 Kit Three—Shift Registers
 Kit Four—Counters Kit Five—Displays
 S.A.E. for further details to:
AUTOMATED HOMES
69 High Street, Ryton, Coventry CV8 3FJ (Mail Order Only)

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

12 VOLT FLUORESCENTS

35% OFF
RRP

Made by Thorn Lighting. Ideal for caravan, boat, tent, emergency lighting, etc. All lamps guaranteed for 12 months.



12in 8W
£4.00

21in 13W
£4.90

All lamps have on/off switch, wrong polarity protection device and diffuser.

C60 cassettes 32p
C90 cassettes 45p

All cassettes in plastic case with index and of screwed assembly

All prices include VAT. Add postage 5p in £1
 Quantity Discounts
 10 units 5%
 50 units 7%
 100 units 10%

SALOP ELECTRONICS
23 Wyle Cop. Shrewsbury
Tel 52306


BUILD YOUR OWN

YOU ARE INVITED TO SEND S.A.E. FOR LISTS ON OUR VERY EXTENSIVE RANGE OF HIGH QUALITY AMPLIFIERS, PRE-AMPS, F.M. TUNERS, INSTRUMENTS, RADIO CONTROL, IGNITION UNITS AND MANY OTHER KITS. STATE REQUIREMENTS.

TELERADIO ELECTRONICS
325 Fore St., Edmonton, London N9

ANYTHING REQUIRED from U.S.A., not readily available locally, send requests to POLTRONICS, One First Street, Los Altos, California 94022. Also taking application for mail order reps. to sell complete kits.

MINI ACCUMULATORS

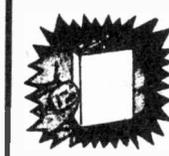

GARFIELDS, 295 Rye Lane, London SE15

2 volt **MULTI-USE**
Sealed Lead Acid Rechargeable Cells.

Size L450—1 1/4" x 1 1/4" x 0 1/4". 3 for **£2.15** inc. P. & P.

Size GA2—1 7/8" x 1 3/8" x 0 5/8". 3 for **£2.65** inc. P. & P.

Suits Fi-Cord

NICKEL CADMIUM fully sealed rechargeable batteries. Equivalent dry cell sizes. Discount. S.A.E. brings full details by return. Charges available. **SANDWELL PLANT LTD., 1 Denholm Road, Sutton Coldfield, West Midlands, B73 6PP. Tel. 021-354 9764.**

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
 Fretcloths, Coverings, Recess Handles, Strap Handles, Feet, Castors, Locks and Hinges, Corners, Trim, Speaker Bolts, etc., etc.
 Send 2 x 81p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)

Unit Q, Starline Works, Grainger Road
 Southend-on-Sea, Essex.

PRINTED CIRCUIT SERVICE. P.C.B. made to your design, give your projects a neat professional appearance. Estimates by return on receipt of design. Please enclose S.A.E. for reply. **MAX WALLS, 107 Boughton, Chester, CH3 5BH.**

PHOTOTECH (EUROPE)

New Optoelectronic Detectors

Type 1: Photodiode, 2 pin Configuration: Photosensitive area 0.85 x 10⁻³ square inches.
Type 2: Photoswitch, 4 pin Configuration, 20V-30V supply. Switching threshold set by external R.C.
Type 3: Photoswitch with automatic threshold adjustment. 6 pin Configuration 20V-30V supply.

LED: Gallium Arsenide Phosphide red emitting diode.
 Data and operating notes sent with each order.
 Prices: (including VAT, packaging and carriage)
 Type 1: 75p each Type 2: £1.00 each
 Type 3: £1.50 each
LED: 17p each, or free with each optoelectronic detector ordered.

Please send C.W.O. or S.A.E. for data only to:
Phototech (Europe), 21a Upper Elmers End Road, Beckenham, Kent

DIG THIS! Already over £500,000 worth of treasures have been uncovered with electronic metal detectors. C. SCOPE offer the best in BFO, IB and TR machines at competitive prices. Tel. Ashford 29141 for details.

CONSTRUCTORS SCREW PACKS

M2, 5—2.5mm pack—contents 120 pcs.
 M3 —3.0mm pack—contents 120 pcs.
 M4 —4.0mm pack—contents 72 pcs.
 M5 —5.0mm pack—contents 55 pcs.

Packs 75p each.

Each pack contains screws (3 lengths), nuts, plain and shakeproof washers.
 Add 8% V.A.T. and 20p P. & P.

C.W.O. only.

MULTUM HOLDINGS LIMITED
7 Churchyardside, Nantwich
 Cheshire CW5 5DE

TRANSMIT!

★ Unique **TRANSMITTER RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£7-95** plus 20p P. & P.

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's and parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send **£3.50** plus 20p P. & P.


(All prices include V.A.T.)

Send remittance to:

BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)
Or for more details, send 20p for lists

H.M. ELECTRONICS

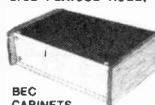275a Fulwood Road, Broomhill, Sheffield S10 3BD



BEC CABINETS

ORION cabinet still available punched or unpunched.

Give your project that professional looking finish. Build it in a BEC. Dry transfer lettering now available...

Send 15p (refundable) for leaflets.

LOW COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 60p, 7 and 8 hole plastic supports 50p pair. Quantity rates. S.A.E. details and sample. Trial pack 60p. (P. & P. 10p order). **P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.**

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs.

Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
Masons Road, Stratford on Avon
Warwicks. Tel. 4879

GLASS FIBRE P.C.B.s. 1:1 master and 7p per square inch tinned or 9p per square inch drilled and tinned Plus 30p per board. Send for quotation on double sided boards. Discount for quantity. **PROTO DESIGN, 4 Highcliffe Way, Wickford, Essex SS11 8LA.**

HELME
DO-IT-YOURSELF
HI-FI STEREO
SPEAKER KITS
The best value around!
Send for details
HELME AUDIO PRODUCTS LTD.
Dept. P.E.
SUMMERBRIDGE
HARROGATE YORKS
Tel. Darley 279 (Std Code 0423 72)

SINCLAIR IC20
IC20 10W+10W stereo IC amplifier kit with free booklet and printed circuit, £4-95.
P220 Power supply kit for the above, £3-95.
VP20 Volume, tone-control and preamp kit, £7-50.
SP7 10W 4 ohm speaker for ic20, £2-70.
CS20 11 x 6 x 3in attractive case for IC20 £2-95.

Send S.A.E. for free leaflet.

JC12 AMPLIFIER
6W IC audio amp with free data and printed circuit, £1-95*.

DELUXE KIT FOR JC12
Includes extra parts for the pcb and vol., bass and treble controls for mono version, £2-06. Stereo model with balance control, £4-46.

JC12 POWER KIT
Supplies 25V 1A, £3-25.

JC12 PREAMP KITS
Type 1 for magnetic pickups, mics and tuners. Mono £1-40 Stereo £2-80. Type 2 for ceramic or crystal pickups. Mono 78p. Stereo £1-56.

LOUDSPEAKERS FOR JC12
8in. x 5in. 8 ohms 5W £2-28.
Send S.A.E. for free leaflet on kits

FERRANTI ZN414
IC radio chip with data £1-34. Printed circuit and extra parts for radio £3-25. Case 80p extra. Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80
FM tuner £13-25. Q16 £10-95. P26 £8-70. P28 £9-10. Trans for P28 £5-60. Z40 £5-75. Stereo 80 £11-95. Project 80S0 £18-95. Quad decoder £14-95. Z60 no longer available, but we stock a similar 30W equivalent amp. £10-30.

PRINTED CIRCUIT KIT £3-95*
Make your own printed circuits. Contains etching dish, 200 sq. in. of copper clad board, 1lb ferric chloride, etch resist pen, small drill bit, laminate cutter and instructions.

MAINS TRANSFORMERS
6-0-6V 100mA 86p. 9-0-9V 100mA 86p. 18V 1A £1-65*.
0, 12, 20, 24, 30V 1A £2-95*. 12-0-12V 1A £1-85*.
0, 12, 15, 24, 30V 2A £4-20*. 20V 2A £2-00.
6V and 9V trans are d.c. rated, others are a.c. volts.

SINCLAIR BLACK WATCH
Fully assembled with black strap, £20-95*.
Bracelet, £2*.



SINCLAIR CALCULATORS*
Cambridge £7-95. Cambridge % £8-95. Scientific £11-95. Cam. Scientific £14-95. Oxford 100 £8-95. Oxford 300 £16-95. Programmable scientific £25-95. Mains adaptors for programmable and Oxfords £3-19; for Cambridge and Scientific £3-15.

CBM CALCULATORS*
776MD 7 digit, %, memory £5-95. 796MD 8 digit, %, memory £6-45. 897D 8 digit, %, 4 function memory £7-80. SR7919D 8 digit, memory, trig, log, pi, powers, scientific notation £13-20. SR1800 10 digit scientific £23-25. SR4148R 14 digit rechargeable scientific with charger £34-95. Mains adaptor for other machines £2-95.

CASIO CALCULATORS*
Personal mini 6 + 6 digits £5-95. Pocket 8S 8 digits, %, const. £8-95. Memory 8R 8 digits, %, memory, const. £8-95. FX20 £16-95. Mains adaptor for all models £3-95.

NOVUS CALCULATORS*
760 6 digit £5-45. 835 8 digit, %, const. sq root/4 function memory £7-60. 4525 10 digit programmable scientific calculator £47-95. 4510 £13-20. 4515 £39-95. 4520 £23-45. Mains adaptor £4-20.

24-HR. DIGITAL CLOCK KIT*
Includes pcb, mains power supply, attractive case, 0-5in. jumbo green display, clock chip, and all other parts. Displays hours and minutes separated by a pulsating colon. Kit £11-07. Built £13-50. Send S.A.E. for free leaflet.

S-DECS AND T-DECS*
S-DeC £2-24
T-DeC £4-05
µ-DeC A £4-45
µ-DeC B £7-85
N-DeC £10-45
IC carriers—
16 dill plain £1-07, with socket £2-21.
10 T05. plain 99p, with socket £1-95. SS11 60p, SSU1 60p, SSN1 80p.



SWANLEY ELECTRONICS
Dept. PE, PO Box 68, Swanley, Kent

Battery Eliminator Bargains

55 WAY SUPER
New switched model. 3 to 30V in 1/2V steps. Fully stabilized. 1A output. Kit £7-95. Assembled £10-95. 2 Amp model. Kit £9-95. Built £12-95.



6-WAY SPECIAL
Switched output of 3/4/6/7/9/12V at 500mA with 4-way multi-jack plug and free matching socket, £5-20.

6-WAY DOUBLE RADIO MODEL £6-20
Similar to above, but with press-stud battery connectors. 3+3/4+4+6+6.7+7+9+9.12+12V at 250mA. Also gives 15/18/24V single.

3-WAY MODEL
Switched output of 6/7/9V at 250mA with 4-way multi-jack plug and free matching socket, £2-95*.

RADIO MODELS
50mA with press-stud battery connectors for radios etc. 9V £3-25. 1.5V £3-45. 9 + 9V £4-45. 6 + 6V £4-45. 4 + 4V £4-45. ALC 9V 300mA £3-95.


CASSETTE MAINS UNITS
7 1/2V output to run cassette recorders from the mains. Complete with 5 pin DIN plug. 50 mA model £3-45. 300mA model £3-95.

CAR CONVERTORS
Input 12V DC. Output 6/7 1/2V DC 1A regulated, £3-95*.

BATTERY ELIMINATOR KITS
Send S.A.E. for free leaflet on range.
100mA radio type with press stud battery terminals. 4V £1-80. 6V £1-80. 9V £1-80.
50mA double radio type with press stud terminals. 4V + 4V £2-50. 6V + 6V £2-50. 9V + 9V £2-50.
100mA cassette type with 5 pin DIN plug. 7 1/2V £1-80.
Stabilized 8-way type with voltage stabilizer to give low hum. 3/4/6/7/9/12/15/18V 50mA, £2-95.
Heavy duty 12-way type. 4 1/2/6/7/8/11/13/14/17/21/28/34/42V. 1 amp £3-95. 2 amp £5-95.

Post 30p on orders under £2, otherwise free. Prices include VAT (Overseas customers deduct 7% on items marked *, otherwise 11%). Official orders from schools, government labs., etc., welcome.

4-STATION INTERCOM

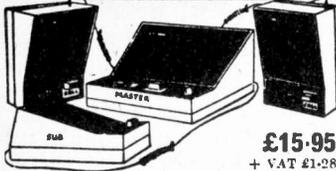

£15-95
+ VAT £1-28

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 75p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £28-12 per pair. P. & P. 75p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £12-95
+ VAT £1-04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. Volume. Direct tape recording model at £13-95 + VAT £1-12. P. & P. 70p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PE6)
169 KENSINGTON HIGH STREET, LONDON, W.8

OSMABET LTD We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS
Prim 200/240V a.c. 5V 1A 50p; 6 3V 1-5A £1-65; 3A £2-10; 6A CT £3-75; 12V 1-5A £2-10; 3A £3-75; 6A CT £5-25; 18V 1-5A CT £3-45; 24V 1-5A CT £3-75; 3A CT £5-25; 5A £8; 8A £11-25; 12A £18-50; 40V 3A CT £7-50; 50V 6A CT £18-75; 25V 2A + 25V 2A £7; 12V 4A + 12V 4A £7.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V 0-10-12-14-16-18V 2A, £4; 4A, £5-25. 0-10-15-20-24-30V 2A, £4-50; 4A, £8-75. 0-5-20-30-40-60V 1A, £4-85; 2A, £8-75. 0-40-50-80-80-100-110V 1A, £7.

MIDGET RECTIFIER TRANSFORMERS
For FW rect. 200/240V a.c. 6-0-6V 1-5A or 9-0-9V 1A £1-80 each. 12-0-12V 1A, or 20-0-20V 0-75A, or 9-0-9V 0-3A, or 12-0-12V 0-25A, or 20-0-20V 0-15A, or 6V 0-5A + 6V 0-5A, or 9V 0-35A + 9V 0-35A, or 12V 0-25A + 12V 0-25A, or 20V 0-15A + 20V 0-15A, all at £2 each.

LOUDSPEAKERS
2in 8 or 75Ω, 2 1/2in 8 or 25Ω, 3in 3, 8 or 35Ω, 3 1/2in 15 or 18Ω, £1 each. 8 x 5in 3, 8, 15 or 25Ω, £1-75; Goodmans 6 1/2in double cone 4Ω, £2-50; 7 x 4in, 3, 8, 15 or 25Ω, £1-50.

INSTANT* BULK TAPE/CASSETTE ERASER
Instant erasure any diameter; tape spool or cassette, demagnetises tape heads, 200/240V a.c., £3-75.

SYNCHRONOUS GEARED MOTORS 200/240V a.c.
Brand new Smiths, built in gear-box, 6 r.p.m., 75p each.

PAPER TUBULAR CONDENSERS
4-7mf. 180V, 30 x 20mm, 20p (10 for £10)

SPEAKER MATCHING AUTO TRANSFORMER
12W, 3 to 8 or 15Ω, up or down, £1-85.

G.E.C. MANUAL OF POWER AMPLIFIER COVERING VALVE AMPLIFIERS OF 30W TO 400W 35p.

CABLES — CABLES — CABLES

MICROPHONE TWIN H/DUTY, BRAIDED SCREEN
Professional cable for stage, studio, outdoor. PVC covered, grey, 20p per metre. Grey Single cable, black, 10p per metre

MULTI WAY SCREENED, PVC COVERED
36 way £1; 25 way 75p; 14 way 50p; 4 way 14p; 2 way 10p; 1 way 8p per metre

LOW COST CO-AXIAL CABLE 75Ω
UHF, white, 12p per metre. VHF, white, 9p per metre.

FLEXIBLE PVC MINI 3-CORE CABLE
19/010 100 metres 3-core for speakers, intercoms, etc., £3.

TWIN FIG. 8 CABLE
Polarised, £2-50 100 metres

ALL TYPES DOMESTIC AND COMMERCIAL CABLES.
ALL SIZES AND COLOURS CONNECTING WIRES. MULTI SCREENED AND UNSCREENED CABLE.

TRADE ENQUIRIES INVITED
Carriage and VAT extra on all orders
S.A.E. ENQUIRIES, LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

CLOCK MENU

Try the following recipe for a digital clock

Basic Ingredients

- MHI CLOCK KIT**
Comprises: clock chip, driver chip for common anode LEDs, PC board, and socket (if required). Types: basic clock, alarm clock, alarm clock with calendar, car clock, stop-clock, up/down counter.
- MHI DISPLAY KIT**
4 or 6 digit LEDs with PC board. Sizes: 0-3in, 0-5in, or 0-6in
- MHI CASE**
Size: 6 x 5 x 3in. White only.
- Transformer, resistors and transistors not supplied — all are stocked by most radio shops. With some kits we supply quartz crystals, trimmers or other components difficult to obtain.

Shipping List

	£
MHI5314 Basic clock	6-60
MHI5253 Alarm clock	8-35
MHI7001 Alarm and calendar	10-00
MHI5378 Car clock	15-10
MHI5399 Stop-clock	7-35
MHI5395 Up/down counter	10-50
MHI7074 (digit) 0-3in	6-60
MHI7076 (digit) 0-3in	9-50
MHI7274 (digit) 0-5in	8-50
MHI7276 (digit) 0-5in	12-00
MHI7474 (digit) 0-6in	9-60
MHI7476 (digit) 0-6in	14-70

MHI case £2-95 + 25p postage & packing

Please send S.A.E. for new catalogue.

Terms: CWO. Access. Barclaycard (simply quote your number and sign) Credit facilities to accredited account holders

VAT—All prices exclude VAT (8%). P. & P. 15p

BYWOOD

68 Ebbens Road, Hemel Hempstead
Herts. HP3 9ORB
Tel. 0442 62757

PRICES INCLUSIVE OF VAT

Add 20p P & P—NO OTHER EXTRAS

MAIL ORDER ONLY

Fully branded devices by RCA, TEXAS, MOTOROLA, MULLARD, etc.

TTL BY TEXAS		OP AMPS		VOLTAGE REGULATORS (PLASTIC)		TRANSISTORS						
7400	13p	7489	291p	301A	Ext. Comp. 8 pin DIL	40p	AC126/7	12p	BFY51	16p	2N2904/5	22p
7401	15p	7490	43p	709	Ext. Comp. 8/14 pin DIL	30p	723	12p	BFY52	17p	2N2928RB	9p
7402	15p	7491	81p	710	Diff. Comp. 14 pin DIL	55p	14 pin DIL 45p	1amp	BRV39	39p	2N29280	10p
7403	17p	7492	48p	741	Int. Comp. 8/14 pin DIL	25p	Data Sheets on	5V 7805	BSX19/20	20p	2N2926YG	11p
7404	17p	7493	43p	747	Dual 741 14 pin DIL	67p	Vol. Regs.	15V 7815	BU105	175p	2N3053	19p
7405	17p	7494	81p	748	Ext. Comp. 8 pin DIL	39p	10p each.	18V 7818	BU108	312p	2N3054	50p
7406	41p	7495	70p	776	Prog. Op. Amp. TO99	160p	10p each.	24V 7824	MJ2955	90p	2N3055	54p
7407	39p	7496	84p	CA3130S	CMOS Op. Amp. 8 pin DIL	108p	1488 Dual Vol. Reg. 300p.	Pre-set at ± 15V	AF114/5	18p	2N3442	151p
7408	17p	7497	295p	LM390L	Quad Op. Amp. 14 pin DIL	61p	Adjustable from ± 8V min. to ± 20V max.	AF116/7	MJE2955	107p	2N3702/3	14p
7409	22p	7498	116p	MC14500	Dual Op. Amp. 8 pin DIL	75p	OP/O ELECTRONICS	AF139	MJE3055	70p	2N3704/5	14p
7410	15p	7497	32p	NE536T	FET Op. Amp. TO99	300p	OCF70	AF239	MPSA06	37p	2N3706	12p
7411	25p	74110	64p	LINEAR ICs			OCF71	BC107/8	MPSA12	56p	2N3707	14p
7412	25p	74118	90p	CA3028	Diff. Cascade Amp.	112p	OCF72	BC149/8	MPSA12	56p	2N3708/9	11p
7413	34p	74121	32p	CA3046	5 Transistor Array	62p	OCF73	BC147/9	MPSA12	56p	2N3709	14p
7414	85p	74122	53p	CA3048	Quad Low Noise Amps.	250p	ORP60	BC149/8	MPSA12	56p	2N3866	90p
7415	32p	74123	79p	CA3089E	FM IF System 18 DIL	250p	ORP61	BC157	OC35	70p	2N3904	32p
7417	32p	74126	76p	CA3090AQ	FM Stereo Decoder	450p	2N5777	BC157	OC41/2	20p	2N3905/6	32p
7420	15p	74128	90p	ICL8038CC	VCO Funct. Gen.	300p	SCR-THYRISTORS	BC158/9	OC44/5	20p	2N4058	17p
7422	19p	74132	76p	LM380	2W Audio Amp	115p	1A 50V T05	BC169C	OC71	20p	2N4060	17p
7423	36p	74136	81p	LM381	Stereo Pre Amp.	200p	1A 100V T05	BC177	OC72	25p	40361	43p
7425	33p	74141	70p	MC1310P	FM Stereo Dec.	200p	1A 400V T05	BC178	OC83	35p	40360	40p
7427	40p	74145	76p	MC1495L	Multiplexer	360p	3A 100V Stud	BC182/3	OC28	85p	40361	41p
7430	15p	74148	17p	MC1498L	Bal Mod/Demod.	100p	3A 400V Stud	BC184	TIP29A	45p	40362	45p
7432	28p	74150	135p	MFC4000B	iW Audio Amp	75p	7A 400V	BC187	TIP30A	54p	40410	59p
7437	28p	74151	77p	MFC8040	Electronic Attenuator	140p	7A 400V	BC212	TIP31A	56p	40411	243p
7440	15p	74153	92p	NE555V	Timer 8 pin DIL	40p	T05 + HS	BC213	TIP32A	63p	40584	81p
7441	70p	74154	164p	NE556	Dual 555 14 pin DIL	108p	16A 100V Plastic	BC214	TIP33A	97p	40595	92p
7442	84p	74155	82p	NE561B	PLL with AM Demod.	350p	16A 400V Plastic	BC217	TIP34A	124p	FETA	
7443	130p	74156	82p	NE562B	PLL with VCO	350p	16A 800V Plastic	BCY70	TIP35A	243p	BF244	40p
7444	130p	74160	107p	NE565	PLL	216p	16A 800V Plastic	BCY71	TIP36A	297p	MPF102	34p
7445	100p	74162	107p	NE568V	PLL Function Gen.	200p	4A 100V	BD131	TIP41A	70p	MPF103/4	34p
7447	81p	74183	107p	NE567V	PLL Tone Decoder	200p	10 amp	BD132	TIP42A	78p	MPF105	34p
7448	75p	74164	130p	2567	Dual 567	400p	3 amp	BD135	ZTX108	11p	2N3819	25p
7450	16p	74166	136p	SN72733	Video Amp	150p	6 amp	BD139	ZTX300	15p	2N3820	50p
7451	16p	74174	130p	SN78013N	Pwr. Audio Amp + HS	175p	10 amp	BD140	ZTX500	17p	2N3823	54p
7453	17p	74175	92p	SN78023N	Pwr. Audio Amp + HS	175p	15 amp	BF115	ZTX504	54p	2N5457	34p
7454	18p	74176	130p	TBA491B	Audio Amp	275p	BR100	BF125	2N697	14p	2N5458/9	34p
7460	18p	74177	108p	TBA800	5W Audio Amp	112p	BRIDGE RECTIFIERS	BF173	2N698	32p	3N128	81p
7470	28p	74180	108p	TBA810	7W Audio Amp	125p	BY100	BF195	2N706	13p	3N140	92p
7472	27p	74181	322p	TBA820	2W Audio Amp	100p	1A 50V	BF196	2N708	19p	3N141	81p
7473	32p	74182	89p	TBA820	2W Audio Amp	100p	1A 100V	BF197	2N830	15p	3N187	28p
7474	32p	74185	146p	TDA2020	20W Audio Amp.	375p	1A 400V	BF200	2N1131/2	19p	3N202	130p
7475	48p	74190	155p	XR2240	Prog./Timer Counter	400p	1A 200V	BF220	2N1304/5	23p	40603	63p
7478	32p	74192	130p	ZN414	TRF Radio Receiver	140p	1A 800V	ZENERS	2N1306	30p	40673	63p
7480	54p	74193	130p	MM5314	Clock IC 24 pin DIL	460p	2A 50V	BF257/8	2N1363	34p	UJT	
7482	75p	74194	116p	LOW PROFILE SOCKETS BY TEXAS—8 pin			2A 100V	BF293/40	2N1711	22p	TIS43	32p
7483	86p	74195	83p	14p; 14 pin 15p; 15 pin 16p; 24 pin 54p.			2A 600V	BF297/80	2N1813	22p	2N2160	86p
7484	103p	74197	108p				4A 100V	BF384	2N1893	32p	2N2846	38p
7485	130p	74198	108p				6A 100V	BFX85/6	2N2219	22p	2N4871	34p
7486	32p	74198	214p				6A 100V	BFX87	2N2221/2	22p	2N6027	54p
							6A 100V	BFY50	2N2484	15p	(PUJT)	

GOVT DEPTS COLLEGES ETC ORDERS WELCOME

MINIMUM ORDER £2 (OFFICIAL ORDER £5) VAT INVOICE SUPPLIED

TECHNOMATIC LTD

Est. 1971. VAT No. 227 079263

54 SANDHURST ROAD LONDON NW9

Tel. 01-204 4333

INDEX TO ADVERTISERS

A.B.C. Electronics (Oldham) Ltd.	522	Field Electric Ltd.	524	Olson Electronics	446
Alben Engineering	518	Flairline Supplies	514	Orchard Electronics	458
Alfa Electronics	524			Osmab	527
Astro Electronics	508, 518	Garfield	526	Payler Controls	524
Automated Homes	526	Greenweid Electronics	448	Phononics	514, 515
				Phototech (Europe)	526
Bamber, B., Electronics	474	Harverson's Surplus	cover iii	Precision Petite	520
Barclay Electronics	519	H.B. Electronics	514	Pulse Electronics Ltd.	446
Barrie Electronics	523	Adam Hall	526	Radio Component Specialists	507
B.H. Components	520	Heathkit	452	Radio Exchange	cover ii
Bi-Pre-Pak	479	Helme Audio	526	P.F. Ralfe	448
Bi-Pak	444, 445	H.M. Electronics	526	Ramar Constructor Services	526
Birkett, J.	446	Henry's Radio	523	R.T. Services	524
Boffin Projects	526	Home Radio	462	R.S.T. Valve Mail Order Co.	480
British Institute of Engineering Technology	442, 454, 498			Radio & T.V. Components	460, 461
British National Radio & Electronics School	473	I.L.P. Electronics Ltd.	443	Salop Electronics	526
Butterworths	454	International Electronics Unlimited	449	Saxon Entertainments Ltd.	456, 457
Bywood Electronics	527	Intertext ICS	525	S.C.S. Components	513
		Island Devices	524	Service trading	447
Cambridge Learning	516	Jones, J. C.	525	Sintel	452
Chiltmead Ltd.	518	J.W.B. Radio	524	Swanley Electronics	527
Chromasonic Electronics	522				
C.J.L.	508	Kensington Supplies	525	Tapetalk	525
Copper Supplies	525	Kramer	489	Technomatic Ltd.	528
Crescent Radio Ltd.	498	Lasky's	480	Teleradio Electronics	526
Crofton Electronics	498	London College of Furniture	458	Time-Micro Electronics	508
C.R. Supply	524			Trampus Electronics	442
		Macmillan & Co.	517	TUAC	450, 451
Davian Electronics	452	Magnum Publications	525	T.V. Technic	525
Design Engineering	522	Maplin Electronics Supplies	cover iv		
Doram	453	Marco Trading	524	West London Direct Supplies	527
		Marshall, A., & Sons	497	Williams, Michael Electronics	520
Eaton Audio	458	G. F. Milward	474	Wilmslow Audio	455
Electronic Design Assocs.	516	Minikits Electronics	526		
Electrotime	459	Modern Book Co.	514	Young Electronics	442
Electrovalve Ltd.	448	Multum Holdings	526		
Elvins Electronics	508				

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz. 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Base Boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 4 1/2" high x 6" wide x 7 1/2" deep. AC 200/230V. PRICE £13.75. P. & P. 85p.

DE LUXE STEREO AMPLIFIER

A.C. mains 200-240 v. \pm 5% and a heavy duty fully isolated mains transformer with full wave rectification giving a quiet smoothing with negligible hum. Two dual triode pentodes 1 x E280 for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. £12.40. P. & P. 95p.

ALL PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched full smoothed D.C. outputs giving 6v, and 7.5v, and 9v, and 12v, at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finished metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. Price £5.75. P. & P. 85p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS apt. 54 in. wide. Our price £1.50 yd. length. P. & P. 30p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 85p. BARGAIN PRICE £5.00

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 15 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30, or 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.90 P. & P. 75p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 9-0-9 at 500 mA. £1.50. P. & P. 35p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.65. P. & P. 55p. Pri. 200/240V. Sec. 16-0-16 at 2 amp. £2.35. P. & P. 70p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 25dB. Solid encapsulation size 1 1/2" x 1 1/2" x 3/4". Brand new complete with instructions. Price £1.60 P. & P. 15p.

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.62 plus 20p P. & P. Stereo beacon light if required 40p extra.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. x 3in. deep x 6in. high. Ready built and tested. PRICE £20.00 P. & P. 100p.

ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £7.30. P. & P. £1.00.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match your 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to 'lock on' station and prevent drift. I.C. stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2in wide x 8in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed. AC mains 200/240V (not available in kit form).

Special Offer for 1 month only £22.50 + £1.20 P. & P.

LATEST ACOS GP91/15C mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.60. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £1.90. P. & P. 15p.

SONOTONE STACH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.38. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.88. P. & P. 15p.


LATEST CRYSTAL T/O STEREO COMPATIBLE CARTRIDGE for LP/LP/Stereo 78. £1.80. P. & P. 15p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.58. P. & P. 15p.

SPECIAL OFFERS

Mullard LP1159 RF-1F Double Tuned Amplifier Module for nominal 470KHz. Size approx. 2 1/2" x 1 1/2" x 3 1/2" 7.6V + earth. Brand new pre-aligned. Full specification and connection details supplied. £2.25 + P. & P. 12p.

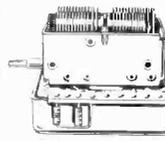Pye VHF/FM Tuner Head covering 88-108M/Hz. 10-7M/Hz IF output 7.8V + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-gear FM and 323 P1 + 323 P1 AM Tuning Gang only £3.15 + P. & P. 35p.



PRECISION MADE Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p C/O. Ov. all size 2 1/2" x 2 1/2" x 1 1/2". Supplied complete with chrome finished switch buttons 2 for £1.50 + 10p, P. & P.

HI-FI LOUDSPEAKER SYSTEM Mk II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which).

OUR PRICE £11.25 each. Carr. £1.60
Cabinet Available Separately £6.75. Carr. £1.20.
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £20.90. Carr. £1.60

LOUDSPEAKER BARGAINS

5in. 3ohm £1.45, P. & P. 35p. 7 x 4in. 3ohm £1.60, P. & P. 45p. 10 x 6in. 3 or 15 ohm £2.50, P. & P. 75p. E.M.I. 8 x 5in. 3ohm with high flux magnet £2.06, P. & P. 50p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £2.00 + 25p, P. & P.

"POLY PLANAR" WAFER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls. Send S.A.E. for details. Only £7.00 each. P. & P. 60p for one, 80p for two.


Now also available 8" x 8 ohm. 10 watts r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars. £4.70 + 40p P. & P.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass, boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. **AMPLIFIER KIT** £13.50. P. & P. 55p. **MAGNETIC INPUT COMPONENTS 33p extra** **POWER PACK KIT** £4.85 P. & P. 85p. **CABINET** £4.85 P. & P. 75p. **Special offer—only £22.50 if all 3 units ordered at one time including P. & P.**

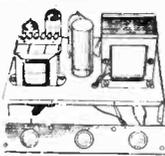Full after sales service. Also available ready built and tested £25.25. P. & P. £1.00. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporated ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 44 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7.80. P. & P. 85p.

H.S. 'FOUR' AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £7.00. P. & P. 85p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP85 and E280 rectifier. Simple instruction booklet 25p x S.A.E. (Free with parts). All parts sold separately. ONLY £11.25. P. & P. £1.25. Also available ready built and tested £15.20. P. & P. £1.20.

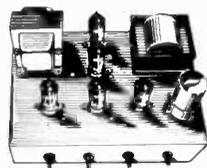

SPECIAL OFFER

Limited number of the latest BSR C1141Ri Auto/Manual changer de-luxe. Lightweight tubular arm cue-ing/leveler bias compensator £12.60 + £1.10 P. & P.

OUR PRICES INCLUDE VAT AT CURRENT RATES

(Please write clearly)

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4. Printed in England by Chapel River Press, Andover. Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd. Subscriptions not available at home or overseas. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee". Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

More than just a catalogue

Projects for you to build

READY MADE ALARM CLOCK MODULE!
* CAN CONTROL A RADIO, TOO!

- BRIGHT 4 DIGIT 0.5 INCH INCH DISPLAY
- FLASHING COLON (1Hz)
- SWITCH FOR DISPLAY SECONDS
- ALARM SET INDICATOR
- P.M. INDICATOR
- POWER FAILURE INDICATION
- SNOOZE TIMER
- AUTOMATIC DISPLAY BRIGHTNESS (NEEDS CDS CELL)
- TIME CAN BE SET ACCURATELY TO WITHIN ONE SECOND
- LEADING ZERO BLANKING

ONLY £8-60
INC. V.A.T. & P/P

Just add transformer and switches!



This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied with module shows how simple it is to connect an audible alarm, and your battery or mains radio. A smart case will be available shortly. Data sheet available separately. Please send s.a.e.

Simple clock kit £9.38. Alarm clock-radio kit £10.99. Alarm clock-radio case £11.99. Switching kit £11.51. All prices inc. V.A.T. and P. & P. Please note details in our catalogue




132 pages!
REALLY GOOD VALUE FOR MONEY AT JUST 40p.

MAPLIN ELECTRONIC SUPPLIES

SUPERSONIC SAME-DAY-SERVICE QUALITY COMPONENTS -FAST!

ELECTRONIC ORGAN

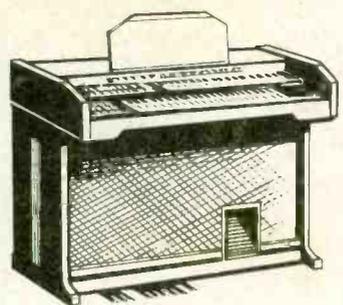

Build yourself an exciting Electronic Organ. Our leaflet MESS1, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops.

Leaflet MESS2, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MESS3, priced at 35p.

No more doubts about prices

Now our prices are **GUARANTEED** (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of **GUARANTEED** prices. Send us 30p and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next **GUARANTEED** period before the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your 30p when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.


Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Shop open 9 a.m.-5.30 p.m. Tuesday to Saturday (closed Mondays)

SYNTHESISER



A reprint of the complete article giving full construction details published by "Electronics Today International" between January-September '74 of the International Voltage Controlled Synthesiser, developed as a "state of the art", now available, price £1-50. S.A.E. please for detailed price list.

GRAPHIC EQUALISER

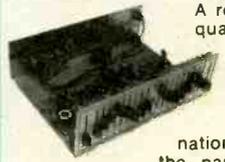

A really superior high quality stereo graphic equaliser as described in the January edition of "Electronics Today International". We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

MAPLIN ELECTRONIC SUPPLIES

please address all mail to
P.O. Box 3 Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101