

PRACTICAL



ELECTRONICS

JUNE 1977

40p

TV SPORTCENTRE

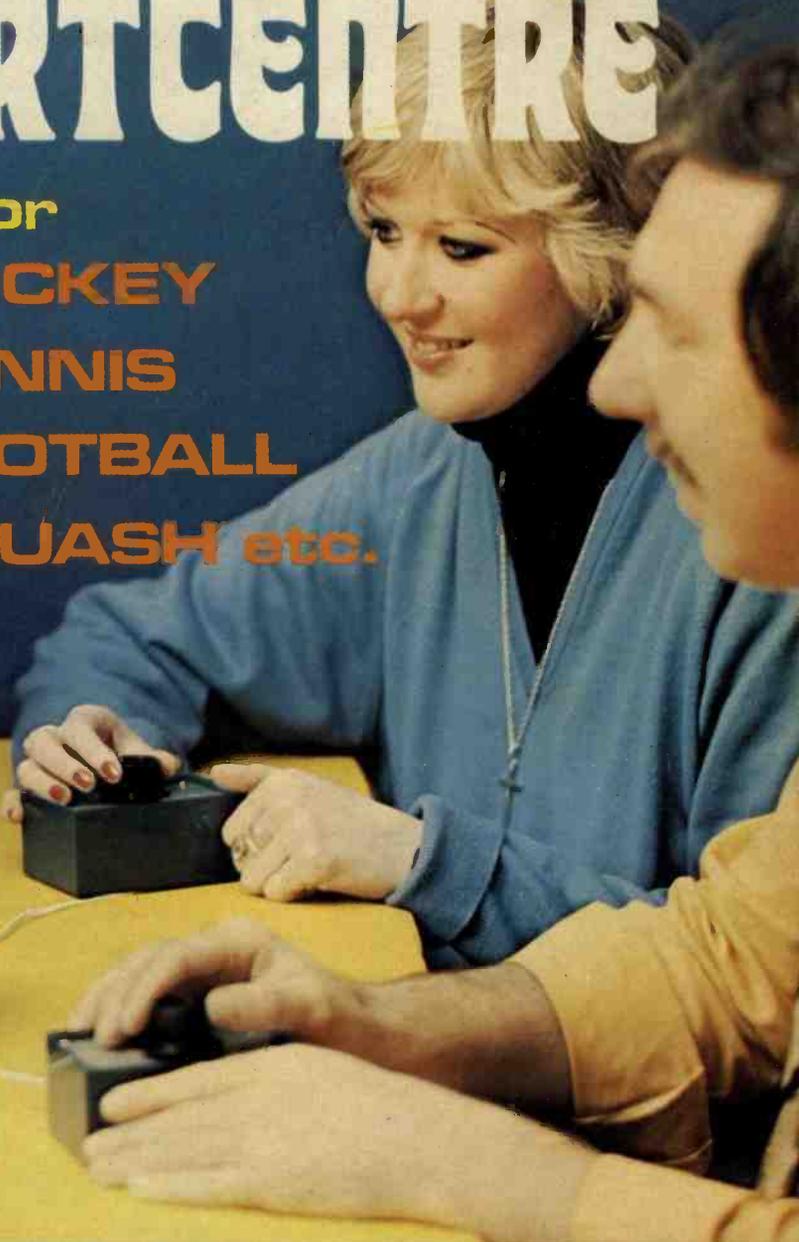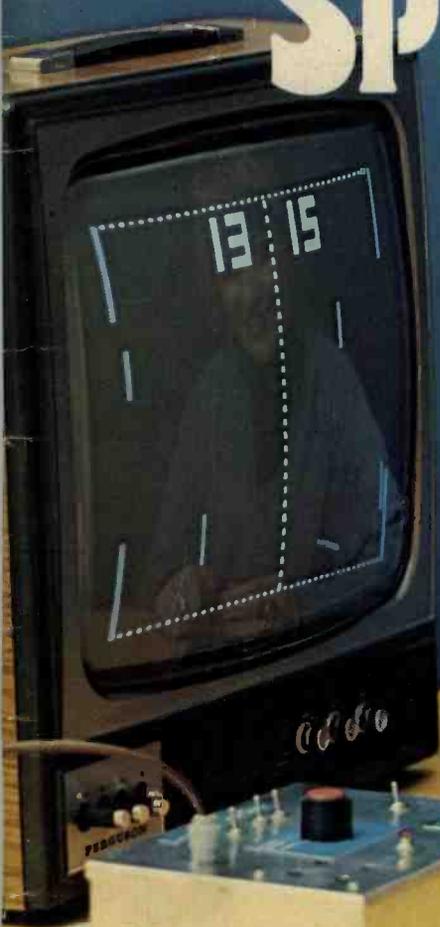...for
HOCKEY
TENNIS
FOOTBALL
SQUASH etc.



Also inside...

CAR LIGHTS REMINDER · SOUND to LIGHT CONVERTER

RETURN OF POST MAIL ORDER SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. A mono kit or a stereo kit. The mono kit uses 13 semiconductor. The stereo kit uses 22 semiconductors with printed front panel and volume, base and treble controls. Spec. 10W output into 8 ohms. 7W into 15 ohms. Response 20c/s to 30kc/s. Input 100M.V. high imp. Size 9 1/2in x 3in x 2in. A/C mains operated.

Mono kit **£11.25** Stereo kit **£18** post 46p
Easy to build. Full instructions supplied.



ELAC 10 inch

Ribbed cone. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 10W. 16 ohm impedance. **£4.50**

MAINS TRANSFORMERS ALL POST 50p each.

250-0-250V 70mA, 6-3, 2A **£2.95**
250-0-250 80mA, 6-3V 3.5A, 6-3V 1A or 5V 2A **£4.60**
350-0-350 80mA, 6-3V 3.5A, 6-3V 1A or 5V 2A **£5.80**
300-0-300 120mA, 6-3V 4A C.T., 6-3V 2A **£7.00**
220V 45mA, 6-3V 2A **£1.75p**
HEATER TRANS. 6-3V 3A. £1.45 1 amp. 85p
GENERAL PURPOSE LOW VOLTAGE.
Tapped outputs at 2A 3, 4, 6, 8, 9, 10, 12, 15, 18, 24 and 30V **£4.60**
1A 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£4.60**
2A, 6, 8, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£7.00**
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8.70**
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11.25**
5, 8, 10, 16V 1A £2, 6-0-6V 500mA £1, 9V 1A £1
12V 300mA £1, 12V 600mA £1, 12V 750mA £1
40V 2A tapped 10V or 30V **£2.85**, 20V 3A **£2.60**
20V 2A **£2.85**, 30V 5A + 34V 2A ct. **£3.75**
20-0-20V 1A £2, 30V 1A **£1.75**, 20V 1A **£1.80**
60V, 40V, 20V or 20-0-20V, 1A **£3.50**
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 160W £5, 250V £6, 400W £7, 500W £8.
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V 1A £2.75; 4A **£4.60**
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V output 1A 40p; 2A 55p; 4A 85p.

R.C.S. STABILISED POWER PACK KIT

All parts including printed circuit and instructions to build this unit. Packages available: 6V, 7.5V, 9V, 12V. Up to 100mA output. Post **£2.95** 46p.
Please state voltage required.

R.C.S. STEREO FM TUNER



This completely cased mains powered Hi-Fi Tuner with brushed aluminium fascia is British made using the latest circuitry. Bargain. Post 46p.
Kuba Stereo Tuner/Amplifier Chassis. Brand new **£33.50**.

BARGAIN 3W AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£3.95**

WAFER HEATING ELEMENTS THIN

Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.

ONLY **40p** EACH (FOUR FOR **£1.50**)
ALL POST PAID—Discounts for quantity.

E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. 10W. **£5.95**
State 3 or 8 ohm. Post 46p
As illustrated.

15W model **£8.50**
8 ohms. Post 65p

20W model **£9.50**
4 or 8 or 16 ohms. Post 65p



BAKER MAJOR 12 £14.95

Post £1.00



30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£18.95**
As illustrated.

Please state 4 or 8 or 16 ohms. Post £1.60

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s.

Bass Resonance 55 c/s.
GROUP "25" **£11.95**
12in 30V
4, 8 or 16 ohms. Post £1

GROUP "35" **£13.95**
12in 40V
4, 8 or 16 ohms. Post £1

GROUP 50/12in **£20.95**
60W 8 or 16 ohms with aluminium presence dome. Post £1.60

GROUP "50" **£24.95**
15in 75V
8 or 16 ohms. Post £1.60

Disco, Group + PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER

Ideal for Groups, Disco, P.A. and Musical Instruments. Output for speech and music. 4 way mixing. Output 4/8/16 ohm. a.c. Mains. Separate treble and bass controls. 50 watt model **£49**

NEW 'DISCO 100 WATT' **£52**
ALL TRANSISTOR AMPLIFIER CHASSIS 2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. BLACK CARRYING CABINET AVAILABLE £9.

Separate treble and bass controls. 50 watt model **£49**

PW SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1,000W channels. As featured in Practical Wireless. **£14.00** CABINET extra £3.

GOODMANS CONE TWEETER 18,000 c/s. 25W 8 ohm. Price **£3.25**
E.M.I. 5in. mid range 25W **£4.95**
E.M.I. 13 x 8 in. 25W Bass Unit **£8.50**

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model. Four inputs. Treble, Bass, Master Volume Controls. Ideal disco, P.A. or groups. S.A.E. for details. 5 speaker outputs. 4 or 8 or 15 ohm. 100V line to order. plus £2.50 carr. Suitable carrying case **£16.50**. **£85**

LOW VOLTAGE ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 6V 25p; 25V 42p; 50V 57p. 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p. 3000mF 100V £1.60. 4700mF 63V £1.20. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p.

COLLAR GRAM MOTOR 120V **75p**
GEAR BOX 5:1 95p.

PHILIPS GRAM MOTOR 6 VOLT A.C. **£1.50**

BSR HI-FI AUTOCHANGER

Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.c. 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE. Single Player version **£13.50**. All Post 75p
DE-LUXE AUTOCHANGER Balanced Arm **£17.50**
GARRARD MINICHANGER Size 12 x 8in **£8.95**
BSR P128 with Ceramic Cartridge **£19.50**



PORTABLE PLAYER CABINET £4.50

Modern design. Size 16in 1/2 x 7in 1/2 x 7in. Textured covered. Large front grille. Hinged lid. Chrome fittings. Motor board cut for Garrard or BSR deck. Post 50p.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/compat. cartridge. Baseplate. Size 11in x 8in. Turntable. Size 7in diameter. A.c. mains. 220/250V. 3 speeds plays all size records. **£6.95** Post 46p
Two for **£13**. Post 75p.

HEAVY METAL PLINTHS £6.50

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 in. Post 75p.
Model "B". Size 18 x 13 1/2 in. **£7.50**
Extra Large Plinth and Cover. For transcription decks. Size 20 x 17 1/2 x 9 in. uncut board. Callers only **£18.50**.

TINTED PLASTIC COVERS ONLY Sizes: 'A'—14 1/2 in x 12 1/2 in. **£2.50**. 'B'—20 1/2 in x 12 1/2 in. **£3.00**. 'C'—17 1/2 in x 13 1/2 in x 3 1/2 in. **£3.25**. 'D'—16 1/2 in x 14 in x 4 in. **£3.50**. 'E'—19 1/2 in x 14 1/2 in x 4 1/2 in. **£3.50**. Ideal for record decks, tape decks, etc. Post 75p.

BAKER HI-FI SPEAKERS HIGH QUALITY—BRITISH MADE SUPERB

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25 c/s
Flux Density 16,500 gauss
Useful response 20-17,000 c/s or 16 ohms models. **£21.95** Post £1.60



AUDITORIUM 12in 35 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques. Bass Resonance 35 c/s
Flux Density 15,000 gauss
Useful response 25-16,000 c/s or 16 ohms models. **£20.95** Post £1.60
15in model 45 watts **£24.95**. Post £1.60



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in sides, 6in x 4in, 70p; 8in x 6in, 90p; 10in x 7in, £1.15; 14in x 9in, £1.50; 16in x 6in, £1.45; 12in x 3in, 87p; 16in x 10in, £1.75; 12in x 8in, £1.35.

ALUMINIUM PANELS, 18 s.w.g. 6in x 4in, 15p; 8in x 6in, 25p; 10in x 7in, 30p; 12in x 5in, 30p; 12in x 8in, 40p; 16in x 6in, 45p; 14in x 9in, 50p; 12in x 12in, 55p; 16in x 10in, 75p.

ALUMINIUM ANGLE BRACKET, 6in x 3in x 3in, 15p.
ALUMINIUM BOXES, MANY SIZES IN STOCK.

RADIO COMPONENT SPECIALISTS

Minimum post 30p.

Access and Barclaycard Welcome.

Radio Books and Components Lists 10p.

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

Rail Selhurst.

Tel. 01-684 1665

PRACTICAL ELECTRONICS

VOLUME 13 No. 6 JUNE 1977

CONSTRUCTIONAL PROJECTS

- SOUND TO LIGHT CONVERTER** *by M. Hadley*
A three channel unit which is simple and cheap to build. Mains interference is negligible as zero voltage switching is used 418
- CAR LIGHTS REMINDER** *by D. J. Saunders*
Gives audible warning of lights left on 422
- TV SPORTCENTRE** *by A. M. Marshall*
A versatile games unit for your TV 434
- ELECTRONIC DIE** *by G. Jones*
Features touch operation, a novel counter and l.e.d. display 446 ✓

GENERAL FEATURES

- MICROPROCESSORS EXPLAINED—4** *by R. W. Coles*
Peripheral chips: memories 426
- HANDLING CMOS DEVICES** *by L. J. Gallace & H. L. Pujol*
The physics of breakdown in CMOS devices and simple rules on how to avoid it 452
- INGENUITY UNLIMITED**
Night Light Latch—Fluorescent Light Inverter—"Triumph" Warbler—
Seven Segment Weekdays 456 ✓

NEWS AND COMMENT

- EDITORIAL**—Not Totally Binding 417
- NEWS BRIEFS**
Bionic Voice—IERE Secretary 424
- SPACEWATCH** *by Frank W. Hyde*
Shuttle Trials—Uranus Rings—Jupiter—Black Cloud 433
- INTERCEPT JUNIOR REVIEWED** *by R. W. Coles*
A user's experience of this microprocessor development and tutorial system 442
- POINTS ARISING**
Low Cost Radio Control system—Autowah—Random Number Games Machine 445
- READOUT**
A selection of readers' letters 451
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 454
- PATENTS REVIEW**
Thought provoking ideas on file at the British Patents Office 455

Our July issue will be on sale Friday, June 10, 1977
(for details of contents see page 425)

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

SAXON ENTERTAINMENTS LTD

A FULL RANGE OF MODULES & READY-TO-USE EQUIPMENT TO PROFESSIONAL STANDARDS FOR THE PROFESSIONAL
SYSTEM 7000 COMPLETE & READY-FOR-USE EQUIPMENT

POWER AMPLIFIER MODULES 30—240 WATTS



- Fully tested & guaranteed.
- Full RMS Sine Wave output.
- Distortion typically 0.2%
- 10 Transistors, 4 Diodes.
- Response 30HZ-30KHZ
- Fully short & open circuit proof
- Sensitivity suits most mixers.
- Built-in surge suppression & compensation
- Twin D.C. & output fuses.
- Top-grade components throughout.

30 Watts rms	60 Watts rms		120 Watts rms		240W rms
SA308 30W rms/ 8 ohms £9-50	SA60v 60W rms/ 4 ohms £12-50	SA608 60W rms/ 8 ohms £12-50	SA1204 120W rms/ 4 ohms £14-50	SA1208 120W rms/ 8 ohms £21-00	SA2404 240W rms/ 4 ohms £25-50

POWER SUPPLIES FOR THE ABOVE MODULES—READY WIRED & FUSED ON GLASS FIBRE PCB

PM301	PM601/4	PM601/8	PM1201/4	PM1201/8	PM1202/4	PM1202/8	PM2404/1
For 1/2 SA308 £9-50	For 1/2 SA604 £12-50	For 1 SA608 £12-50	For 1/2 SA1204 £12-50	For 1 SA1208 £12-50	For 2 SA1204 £19-50	For 2 SA1208 £19-50	SA2404 £19-50

SYSTEM 7000 COMPLETE DISCO MIXERS (With Autofade)

Mono or Stereo



The choice of the professional D.J.

Controls: Mic volume, Bass, Treble, A/Fade Depth, B/Deck, R/Deck volumes, Bass, Treble, Master, Headphone volume, Selector & On/Off.

Mono 18v £37-50 Malns £43-50 Stereo 18v £53-50 Malns 59-50

IN MODULAR FORM—All you require is front panel (see below) knobs & sockets etc. All electronics are assembled & tested.

- Specification as for complete mixer
- All Potentiometers supplied & fitted
- Low cost do it yourself with step by step easy to follow instructions.

Mono £19-50 Stereo £29-50 Panel £3-50 Supply unit £8-50

SYSTEM 7000 LIGHTING CONTROL UNIT MK II (Four channel)



Has your light unit got?

- 4,000 W handling
- Sequence facility
- Smart 2 tone panel
- Advanced IC circuitry
- Top grade components
- All your needs in one superbly designed unit

- Integral dimmers
- Automatic audio level

OURS HAS!

ONLY £42-50

IN MODULAR FORM—THE QUADRAFACT

As with the mixers the Mk II L.C. unit may be purchased in module form with all controls, requiring only a panel, case & knobs etc. There are 13 simple connections

- 1-240w Audio
- 8A RCA tracs
- 0.5-20Hz Sequence
- Fully suppressed

CUSTOM MIXER MODULES (Complete or in printed circuit form only)

Make your own mixer, mono or stereo, up to 2 channels, with full monitoring facilities, and provision for echosend/return etc.

- Inputs for low and high 2 mic, ceramic & magnetic cartridge etc.
- Up to 20 input modules per single mixing module
- Feed most types of amplifier—accepts all inputs
- Professional low noise circuitry 20 Hz-30kHz
- Infinitely adaptable—Extremely economical



COMPLETE MODULES

With facia panel, Knobs & sockets, Monitor buttons, Ready wired & tested

Mono Input £8-50 Mono mixing stage £8-50
 Stereo Input £12-00 Stereo mixing stage £12-00

- 0.5W headphone circuit
- Full range bass/treble controls
- Noise—80dB

PRINTED CIRCUIT MODULES

With controls fitted, requires only sockets, facia & knobs

Mono Input £5-50 Mono mixing stage £5-50
 Stereo Input £9-00 Stereo mixing stage £9-00

Power supply for up to 20 channels—PPM18—£8-50.

SYSTEM 7000 SOUND—LITE (3-CHANNEL)

IN COMPLETE OR MODULAR FORM (Modular form illustrated)

- Complete unit similar to Mk II unit above
- Long established & proven design
- 3 Channels—100W per channel
- RCA 8A Tracs—Individual channel fuses
- 1-240 W input—master audio level plus Bass/Middle/Treble

COMPLETE UNIT—Fully cased with rear terminations—just plug in & go! £24-75

MODULAR FORM Facia & knobs etc. Needs only 11 simple connections

£16-50 (Panel £2-50)

CENTAUR—THE 100W RMS STEREO DISCO COMPLETE WITH SOUND-TO-LIGHT SEQUENCER & LIGHTS

ONLY £225 (+ £4-50 carr) or Low Interest terms Deposit £27-86
 12 months at £21-18 or 24 months at £12-01

- 100W RMS stereo output
- Twin heavy duty loudspeaker
- Four channel sound lite—sequencer complete with display
- Separate mic., music bass & treble controls
- Sturdy vynide cabinets with all leads
- Twin BSR decks with lift arm



NOW AVAILABLE
SUPER CENTAUR

200W Stereo output—other details as above £275 (carr. 4-50) or Deposit £31-06 12 months at £25-03 or 24 months at £14-20
 Cut-price condenser mic & headphones £15-00 (only with complete discos)

SAXON MINI-DISCO 50W RMS £139-50 (carr. £2-50)

- C/W Heavy duty loudspeaker 100W RMS £159-50
- 100W version has twin speakers
- Includes mic input & headphone monitor circuit
- Twin BSR decks with liftarm
- Tremendous value—just plug in & go
- Wide range bass & treble controls



Cut-price condenser mic & headphones £15-00 (only with complete discos)

10% DEPOSIT. LOW INTEREST CREDIT ON ORDERS OVER £150

SYSTEM 7000 MINOTAUR 100—All Purpose Wide Range Amplifier



- 100W rms — 1dB
- Standard 8 ohm output
- Twin mixed inputs accept a wide range of signals
- 30HZ-30KHZ ±2dB
- 23dB bass/treble

A four input, high power amplifier which will deliver up to 150 watts output. An absolute must where multiple mixing & power are required

- Four individually mixed inputs
- Wide range bass/treble-master

An extremely compact and versatile amplifier with full protection and a clean, attractive appearance. Ideal for all groups, disco's & clubs



£49-50

- Vynide covered case
- Fully short proof
- Superb value for money

SAXON 150 HEAVY DUTY AMPLIFIER £59-00

STROBES & PROJECTORS (We stock the full Pluto range) Send for details

SUPERSTROBE £19-75

- 2-3 Joules
- 80W Tube for long life
- Compact 4" x 4" x 4"

PRO-STROBE £32-50

- 6-8 Joules
- External trigger
- Long life tube timer circuit



150 WATT LIQUID WHEEL PROJECTOR

- Accepts all accessories
 - C/w with wheel & motor plate
 - Sturdy steel construction
- Remarkable value—Sold elsewhere at £39-50. Our price is only: £33-00

ACCESSORIES

Condenser mics ECM77 600 ohm £13-50
 ECM 81 Impedance £14-95 Crown headphones £8-75
 Heavy duty boomstand £14-50

All prices subject to VAT @ 8% except SA308/PM301, mics. & headphones (12½%)
 Add 50p post & packing on all orders except where already shown
 Ordering: By Telephone—Access, Barclay Card or COD Ring (01) 684 6385/0098
 By post —Send cheque or crossed P.O.'s or 60p for COD or send in your Access/Barclay card NUMBER ONLY

MAIL ORDERS & CALLERS TO: **CROYDON**

327-333 Whitehorse Road, Croydon Surrey CR0 2HS
 24 Hour Ansafone service (01) 684 6385

PIEZO HORNS!

Up to 150 watts handling, No X-over required £7-50 each

Exporters to 17 countries—enquiries welcomed
 Ring Sue Abegg on (01) 684 6385 for U.K. trade enquiries

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

AUTO TRANSFORMERS <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref</th> <th>VA (Watts)</th> <th>Taps</th> <th>£</th> </tr> </thead> <tbody> <tr><td>113</td><td>20</td><td>0-115-210-240</td><td>3-14</td></tr> <tr><td>64</td><td>75</td><td>0-115-210-240</td><td>4-73</td></tr> <tr><td>4</td><td>150</td><td>0-115-200-220-240</td><td>6-69</td></tr> <tr><td>66</td><td>300</td><td>0-115-200-220-240</td><td>8-82</td></tr> <tr><td>67</td><td>500</td><td>0-115-200-220-240</td><td>13-39</td></tr> <tr><td>84</td><td>1000</td><td>0-115-200-220-240</td><td>21-12</td></tr> <tr><td>93</td><td>1500</td><td>0-115-200-220-240</td><td>23-62†</td></tr> <tr><td>95</td><td>2000</td><td>0-115-200-220-240</td><td>34-17†</td></tr> <tr><td>73</td><td>3000</td><td>0-115-200-220-240</td><td>47-63†</td></tr> </tbody> </table>	Ref	VA (Watts)	Taps	£	113	20	0-115-210-240	3-14	64	75	0-115-210-240	4-73	4	150	0-115-200-220-240	6-69	66	300	0-115-200-220-240	8-82	67	500	0-115-200-220-240	13-39	84	1000	0-115-200-220-240	21-12	93	1500	0-115-200-220-240	23-62†	95	2000	0-115-200-220-240	34-17†	73	3000	0-115-200-220-240	47-63†	60 VOLT RANGE Prim. 220-240V Sec. 0-24-30-40-48-60V <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>Amps</th> <th>£</th> </tr> </thead> <tbody> <tr><td>124</td><td>0-5</td><td>4-69</td></tr> <tr><td>126</td><td>1-0</td><td>6-02</td></tr> <tr><td>127</td><td>2-0</td><td>8-36</td></tr> <tr><td>125</td><td>3-0</td><td>11-47</td></tr> <tr><td>123</td><td>4-0</td><td>13-92</td></tr> <tr><td>40</td><td>5-0</td><td>15-24</td></tr> <tr><td>120</td><td>6-0</td><td>17-86</td></tr> <tr><td>121</td><td>8-0</td><td>19-56†</td></tr> <tr><td>122</td><td>10-0</td><td>24-09†</td></tr> <tr><td>189</td><td>12-0</td><td>26-57†</td></tr> </tbody> </table>	Ref.	Amps	£	124	0-5	4-69	126	1-0	6-02	127	2-0	8-36	125	3-0	11-47	123	4-0	13-92	40	5-0	15-24	120	6-0	17-86	121	8-0	19-56†	122	10-0	24-09†	189	12-0	26-57†	SCREENED MINIATURES <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref mA</th> <th>Volts</th> <th>£</th> </tr> </thead> <tbody> <tr><td>238 200</td><td>3-0-3</td><td>2-74</td></tr> <tr><td>212 1A, 1A</td><td>0-6, 0-6</td><td>3-41</td></tr> <tr><td>13 100</td><td>9-0-9</td><td>2-45</td></tr> <tr><td>235 330, 330</td><td>0-9, 0-9</td><td>2-56</td></tr> <tr><td>207 500, 500†</td><td>0-9-9, 0-9-9</td><td>3-27</td></tr> <tr><td>208 1A, 1A</td><td>0-8-9, 0-8-9</td><td>2-65</td></tr> <tr><td>236 200, 200</td><td>0-15, 0-15</td><td>4-56</td></tr> <tr><td>214 300, 300</td><td>0-20, 0-20</td><td>3-36</td></tr> <tr><td>221 700 (DC)</td><td>20-12-0-12-20</td><td>4-04</td></tr> <tr><td>206 1A, 1A</td><td>0-15-20, 0-15-20</td><td>5-54</td></tr> <tr><td>203 500, 500</td><td>0-15-27, 0-15-27</td><td>4-95</td></tr> <tr><td>204 1A, 1A</td><td>0-15-27, 0-15-27</td><td>6-18</td></tr> <tr><td>S112 500</td><td>12, 15, 20, 24, 30</td><td>3-45</td></tr> </tbody> </table>	Ref mA	Volts	£	238 200	3-0-3	2-74	212 1A, 1A	0-6, 0-6	3-41	13 100	9-0-9	2-45	235 330, 330	0-9, 0-9	2-56	207 500, 500†	0-9-9, 0-9-9	3-27	208 1A, 1A	0-8-9, 0-8-9	2-65	236 200, 200	0-15, 0-15	4-56	214 300, 300	0-20, 0-20	3-36	221 700 (DC)	20-12-0-12-20	4-04	206 1A, 1A	0-15-20, 0-15-20	5-54	203 500, 500	0-15-27, 0-15-27	4-95	204 1A, 1A	0-15-27, 0-15-27	6-18	S112 500	12, 15, 20, 24, 30	3-45	MAINS ISOLATING SCREENED PRI. 120/240V SEC. 120/240V C.T. <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref</th> <th>VA (Watts)</th> <th>£</th> </tr> </thead> <tbody> <tr><td>07*</td><td>20</td><td>5-10</td></tr> <tr><td>149</td><td>60</td><td>7-11</td></tr> <tr><td>150</td><td>100</td><td>7-85</td></tr> <tr><td>151</td><td>200</td><td>12-59</td></tr> <tr><td>152</td><td>250</td><td>14-81</td></tr> <tr><td>153</td><td>350</td><td>18-08</td></tr> <tr><td>154</td><td>500</td><td>21-55</td></tr> <tr><td>155</td><td>750</td><td>28-20†</td></tr> <tr><td>156</td><td>1000</td><td>37-97†</td></tr> <tr><td>157</td><td>1500</td><td>45-51†</td></tr> <tr><td>158</td><td>2000</td><td>53-24†</td></tr> <tr><td>159</td><td>3000</td><td>80-78†</td></tr> </tbody> </table>	Ref	VA (Watts)	£	07*	20	5-10	149	60	7-11	150	100	7-85	151	200	12-59	152	250	14-81	153	350	18-08	154	500	21-55	155	750	28-20†	156	1000	37-97†	157	1500	45-51†	158	2000	53-24†	159	3000	80-78†	12 and or 24 Volt PRIMARY 220-240 VOLTS <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>12V</th> <th>24V</th> <th>£</th> </tr> </thead> <tbody> <tr><td>111</td><td>0-5</td><td>0-25</td><td>2-52</td></tr> <tr><td>213</td><td>1-0</td><td>0-5</td><td>3-24</td></tr> <tr><td>71</td><td>2</td><td>1</td><td>4-02</td></tr> <tr><td>68</td><td>3</td><td>—</td><td>5-43</td></tr> <tr><td>18</td><td>4</td><td>2</td><td>5-08</td></tr> <tr><td>85</td><td>5</td><td>—</td><td>5-79</td></tr> <tr><td>70</td><td>6</td><td>3</td><td>6-75</td></tr> <tr><td>108</td><td>8</td><td>4</td><td>8-04</td></tr> <tr><td>72</td><td>10</td><td>5</td><td>8-58</td></tr> <tr><td>116</td><td>12</td><td>6</td><td>9-89</td></tr> <tr><td>17</td><td>16</td><td>8</td><td>11-36</td></tr> <tr><td>115</td><td>20</td><td>10</td><td>15-80</td></tr> <tr><td>187</td><td>30</td><td>15</td><td>18-88</td></tr> <tr><td>226</td><td>60</td><td>30</td><td>24-78†</td></tr> </tbody> </table>	Ref.	12V	24V	£	111	0-5	0-25	2-52	213	1-0	0-5	3-24	71	2	1	4-02	68	3	—	5-43	18	4	2	5-08	85	5	—	5-79	70	6	3	6-75	108	8	4	8-04	72	10	5	8-58	116	12	6	9-89	17	16	8	11-36	115	20	10	15-80	187	30	15	18-88	226	60	30	24-78†
Ref	VA (Watts)	Taps	£																																																																																																																																																																																																																							
113	20	0-115-210-240	3-14																																																																																																																																																																																																																							
64	75	0-115-210-240	4-73																																																																																																																																																																																																																							
4	150	0-115-200-220-240	6-69																																																																																																																																																																																																																							
66	300	0-115-200-220-240	8-82																																																																																																																																																																																																																							
67	500	0-115-200-220-240	13-39																																																																																																																																																																																																																							
84	1000	0-115-200-220-240	21-12																																																																																																																																																																																																																							
93	1500	0-115-200-220-240	23-62†																																																																																																																																																																																																																							
95	2000	0-115-200-220-240	34-17†																																																																																																																																																																																																																							
73	3000	0-115-200-220-240	47-63†																																																																																																																																																																																																																							
Ref.	Amps	£																																																																																																																																																																																																																								
124	0-5	4-69																																																																																																																																																																																																																								
126	1-0	6-02																																																																																																																																																																																																																								
127	2-0	8-36																																																																																																																																																																																																																								
125	3-0	11-47																																																																																																																																																																																																																								
123	4-0	13-92																																																																																																																																																																																																																								
40	5-0	15-24																																																																																																																																																																																																																								
120	6-0	17-86																																																																																																																																																																																																																								
121	8-0	19-56†																																																																																																																																																																																																																								
122	10-0	24-09†																																																																																																																																																																																																																								
189	12-0	26-57†																																																																																																																																																																																																																								
Ref mA	Volts	£																																																																																																																																																																																																																								
238 200	3-0-3	2-74																																																																																																																																																																																																																								
212 1A, 1A	0-6, 0-6	3-41																																																																																																																																																																																																																								
13 100	9-0-9	2-45																																																																																																																																																																																																																								
235 330, 330	0-9, 0-9	2-56																																																																																																																																																																																																																								
207 500, 500†	0-9-9, 0-9-9	3-27																																																																																																																																																																																																																								
208 1A, 1A	0-8-9, 0-8-9	2-65																																																																																																																																																																																																																								
236 200, 200	0-15, 0-15	4-56																																																																																																																																																																																																																								
214 300, 300	0-20, 0-20	3-36																																																																																																																																																																																																																								
221 700 (DC)	20-12-0-12-20	4-04																																																																																																																																																																																																																								
206 1A, 1A	0-15-20, 0-15-20	5-54																																																																																																																																																																																																																								
203 500, 500	0-15-27, 0-15-27	4-95																																																																																																																																																																																																																								
204 1A, 1A	0-15-27, 0-15-27	6-18																																																																																																																																																																																																																								
S112 500	12, 15, 20, 24, 30	3-45																																																																																																																																																																																																																								
Ref	VA (Watts)	£																																																																																																																																																																																																																								
07*	20	5-10																																																																																																																																																																																																																								
149	60	7-11																																																																																																																																																																																																																								
150	100	7-85																																																																																																																																																																																																																								
151	200	12-59																																																																																																																																																																																																																								
152	250	14-81																																																																																																																																																																																																																								
153	350	18-08																																																																																																																																																																																																																								
154	500	21-55																																																																																																																																																																																																																								
155	750	28-20†																																																																																																																																																																																																																								
156	1000	37-97†																																																																																																																																																																																																																								
157	1500	45-51†																																																																																																																																																																																																																								
158	2000	53-24†																																																																																																																																																																																																																								
159	3000	80-78†																																																																																																																																																																																																																								
Ref.	12V	24V	£																																																																																																																																																																																																																							
111	0-5	0-25	2-52																																																																																																																																																																																																																							
213	1-0	0-5	3-24																																																																																																																																																																																																																							
71	2	1	4-02																																																																																																																																																																																																																							
68	3	—	5-43																																																																																																																																																																																																																							
18	4	2	5-08																																																																																																																																																																																																																							
85	5	—	5-79																																																																																																																																																																																																																							
70	6	3	6-75																																																																																																																																																																																																																							
108	8	4	8-04																																																																																																																																																																																																																							
72	10	5	8-58																																																																																																																																																																																																																							
116	12	6	9-89																																																																																																																																																																																																																							
17	16	8	11-36																																																																																																																																																																																																																							
115	20	10	15-80																																																																																																																																																																																																																							
187	30	15	18-88																																																																																																																																																																																																																							
226	60	30	24-78†																																																																																																																																																																																																																							
CASED AUTO TRANSFORMERS 240V cable in & 115V U.S.A. 2 pin outlet <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>VA</th> <th>£</th> </tr> </thead> <tbody> <tr><td>20VA</td><td>£5-67</td><td></td></tr> <tr><td>150VA</td><td>£9-30</td><td></td></tr> <tr><td>300VA</td><td>£11-93</td><td></td></tr> <tr><td>500VA</td><td>£14-32</td><td></td></tr> <tr><td>1000VA</td><td>£18-91</td><td></td></tr> <tr><td>2000VA</td><td>£22-84†</td><td></td></tr> <tr><td>3000VA</td><td>£37-82†</td><td></td></tr> </tbody> </table>	Ref.	VA	£	20VA	£5-67		150VA	£9-30		300VA	£11-93		500VA	£14-32		1000VA	£18-91		2000VA	£22-84†		3000VA	£37-82†		TEST METERS <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>£</th> </tr> </thead> <tbody> <tr><td>AVO 8 MK5</td><td>£76-33</td></tr> <tr><td>AVO 71</td><td>£31-48</td></tr> <tr><td>AVO 73</td><td>£42-07</td></tr> <tr><td>AVO MM5</td><td>£24-97</td></tr> </tbody> </table> AVO TT169 in circuit Transistor Tester £32-56 U4315 Inc steel case £17-52 <p style="text-align: center;">T.I. MINI-MULTIMETER D.C.—1,000V, A.C.—1,000V, 1,000Ω/V, D.C.—100mA, Res.—150kΩ. £8-39</p>	Ref.	£	AVO 8 MK5	£76-33	AVO 71	£31-48	AVO 73	£42-07	AVO MM5	£24-97	<h2 style="text-align: center;">PLUS</h2>	DECS SOLDERLESS BREAD-BOARDING S Dec 70 contacts £2-57 T Dec 208 contacts £4-35 U Dec "A" for I.C.s, etc. £4-75 U Dec "B" for I.C.s, etc. £7-98 <p style="text-align: center;">ELECTRONIC CONSTRUCTION KIT 10 projects (Including Electronic Organ). Ideal gift at £8-74 (no soldering needed)</p>	HIGH VOLTAGE Mains Isolating (screened) Prim. 100/220 or 400/440 Sec. 100/120 or 200/240 <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>VA</th> <th>Ref.</th> <th>£</th> </tr> </thead> <tbody> <tr><td>60</td><td>243</td><td>8-86</td></tr> <tr><td>350</td><td>247</td><td>16-59</td></tr> <tr><td>1000</td><td>250</td><td>25-92†</td></tr> <tr><td>2000</td><td>252</td><td>54-80†</td></tr> </tbody> </table>	VA	Ref.	£	60	243	8-86	350	247	16-59	1000	250	25-92†	2000	252	54-80†	50 VOLT RANGE Prim. 200-240V Sec. 0-19-25-33-40-50V <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>Amps</th> <th>£</th> </tr> </thead> <tbody> <tr><td>102</td><td>0-5</td><td>4-31</td></tr> <tr><td>103</td><td>1-0</td><td>5-55</td></tr> <tr><td>104</td><td>2-0</td><td>7-82</td></tr> <tr><td>105</td><td>3-0</td><td>9-86</td></tr> <tr><td>106</td><td>4-0</td><td>12-19</td></tr> <tr><td>107</td><td>6-0</td><td>17-56</td></tr> <tr><td>118</td><td>8-0</td><td>19-05</td></tr> <tr><td>119</td><td>10-0</td><td>22-04†</td></tr> </tbody> </table>	Ref.	Amps	£	102	0-5	4-31	103	1-0	5-55	104	2-0	7-82	105	3-0	9-86	106	4-0	12-19	107	6-0	17-56	118	8-0	19-05	119	10-0	22-04†																																																																																																																																									
Ref.	VA	£																																																																																																																																																																																																																								
20VA	£5-67																																																																																																																																																																																																																									
150VA	£9-30																																																																																																																																																																																																																									
300VA	£11-93																																																																																																																																																																																																																									
500VA	£14-32																																																																																																																																																																																																																									
1000VA	£18-91																																																																																																																																																																																																																									
2000VA	£22-84†																																																																																																																																																																																																																									
3000VA	£37-82†																																																																																																																																																																																																																									
Ref.	£																																																																																																																																																																																																																									
AVO 8 MK5	£76-33																																																																																																																																																																																																																									
AVO 71	£31-48																																																																																																																																																																																																																									
AVO 73	£42-07																																																																																																																																																																																																																									
AVO MM5	£24-97																																																																																																																																																																																																																									
VA	Ref.	£																																																																																																																																																																																																																								
60	243	8-86																																																																																																																																																																																																																								
350	247	16-59																																																																																																																																																																																																																								
1000	250	25-92†																																																																																																																																																																																																																								
2000	252	54-80†																																																																																																																																																																																																																								
Ref.	Amps	£																																																																																																																																																																																																																								
102	0-5	4-31																																																																																																																																																																																																																								
103	1-0	5-55																																																																																																																																																																																																																								
104	2-0	7-82																																																																																																																																																																																																																								
105	3-0	9-86																																																																																																																																																																																																																								
106	4-0	12-19																																																																																																																																																																																																																								
107	6-0	17-56																																																																																																																																																																																																																								
118	8-0	19-05																																																																																																																																																																																																																								
119	10-0	22-04†																																																																																																																																																																																																																								
30 VOLT RANGE Prim. 220-240V Sec. 0-12-15-20-24-30V <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>Amps</th> <th>£</th> </tr> </thead> <tbody> <tr><td>112</td><td>0-5</td><td>3-45</td></tr> <tr><td>79</td><td>1-0</td><td>4-37</td></tr> <tr><td>3</td><td>2-0</td><td>6-21</td></tr> <tr><td>20</td><td>3-0</td><td>7-51</td></tr> <tr><td>21</td><td>4-0</td><td>8-61</td></tr> <tr><td>51</td><td>5-0</td><td>9-99</td></tr> <tr><td>117</td><td>6-0</td><td>11-50</td></tr> <tr><td>88</td><td>8-0</td><td>14-44</td></tr> <tr><td>89</td><td>10-0</td><td>14-85</td></tr> </tbody> </table>	Ref.	Amps	£	112	0-5	3-45	79	1-0	4-37	3	2-0	6-21	20	3-0	7-51	21	4-0	8-61	51	5-0	9-99	117	6-0	11-50	88	8-0	14-44	89	10-0	14-85	BRIDGE RECTIFIERS £ <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>200V</th> <th>2A</th> <th>0-82</th> </tr> </thead> <tbody> <tr><td>400V</td><td>2A</td><td>0-93</td></tr> <tr><td>200V</td><td>4A</td><td>1-04</td></tr> <tr><td>400V</td><td>4A</td><td>1-21</td></tr> <tr><td>400V</td><td>6A</td><td>1-44</td></tr> <tr><td>500V</td><td>10A</td><td>2-97</td></tr> </tbody> </table>	200V	2A	0-82	400V	2A	0-93	200V	4A	1-04	400V	4A	1-21	400V	6A	1-44	500V	10A	2-97	POWER UNITS CC12-05, 3-4-5-6-7-5-9-12V at 500mA £5-40 STABILISED 3-6-7-5-9V at 400mA £7-24 3300 fits into 13A socket 6-7-5-9V 300mA (E4) £4-30 <p style="text-align: center;">TEAK AUDIO KIT 25W 2 + 25W Amplifiers, 1 + Pre-Amp 1 + Power supply, 1 + Transformer 1 + Front Panel 1 + Kit of parts to include on/off switch, neon ind. Stereo headphone socket. Plus instructions book £32-86.</p> <p style="text-align: center;">STEREO FM TUNER WITH PHASE-LOCK LOOP 4 Pre-selected stations supply 20-35V. 90mA Max. £23-44</p>	COMPONENT PACKS 200 Mixed value resistors (count by weight) 150 Mixed value capacitors (count by weight) 30 Mixed value precision resistors ½W 2 % 15 Assorted pots and pre-sets 10 Reed switches 3 Micro switches 15 Wire wound resistors—mixed wattage 1 Pack wire 50 metres, assorted colours STATE PACK REQUIRED £1-08 PER PACK <p style="text-align: center;">STEREO 30 Complete Stereo Chassis inc.: 7 + 7W RMS, Amp, Pre-amp, Power Supply, Front Panel, Knobs (Only needs Mains Trans.). Stereo 30 118-84 Mains Trans £3-89. Teak veneered cab. £5-91.</p>	HIGH QUALITY MODULES <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref.</th> <th>£</th> </tr> </thead> <tbody> <tr><td>5 Watt RMS AMPLIFIER</td><td>£3-70</td></tr> <tr><td>10 Watt RMS AMPLIFIER</td><td>£4-04</td></tr> <tr><td>25 Watt RMS AMPLIFIER</td><td>£5-27</td></tr> <tr><td>125W RMS AMPLIFIER</td><td>£18-50</td></tr> <tr><td>PRE-AMP for 5-10W</td><td>£7-92</td></tr> <tr><td>PRE-AMP for 25W</td><td>£15-90</td></tr> <tr><td>POWER SUPPLIES 5-10W</td><td>£1-84</td></tr> <tr><td>POWER SUPPLIES 25W</td><td>£4-60</td></tr> <tr><td>TRANSFORMER 5-10W</td><td>£4-50</td></tr> <tr><td>TRANSFORMER 25W</td><td>£6-43</td></tr> </tbody> </table>	Ref.	£	5 Watt RMS AMPLIFIER	£3-70	10 Watt RMS AMPLIFIER	£4-04	25 Watt RMS AMPLIFIER	£5-27	125W RMS AMPLIFIER	£18-50	PRE-AMP for 5-10W	£7-92	PRE-AMP for 25W	£15-90	POWER SUPPLIES 5-10W	£1-84	POWER SUPPLIES 25W	£4-60	TRANSFORMER 5-10W	£4-50	TRANSFORMER 25W	£6-43	CARTRIDGES <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Ref</th> <th>£</th> </tr> </thead> <tbody> <tr><td>AT55</td><td>£5-36</td></tr> <tr><td>SONOTONE</td><td></td></tr> <tr><td>V100</td><td>£5-95</td></tr> <tr><td>97AMC</td><td>£3-34</td></tr> <tr><td>ACOS</td><td></td></tr> <tr><td>GP93-1</td><td>£2-83</td></tr> <tr><td>GP96-1</td><td>£3-08</td></tr> <tr><td>B.S.R.</td><td></td></tr> <tr><td>SX6M</td><td>£2-91</td></tr> <tr><td>SC12M</td><td>£3-66</td></tr> <tr><td>GOLDRING</td><td></td></tr> <tr><td>G800</td><td>£5-71</td></tr> <tr><td>G850</td><td>£4-94</td></tr> <tr><td>SHURE</td><td></td></tr> <tr><td>M75-6S</td><td>£12-66</td></tr> <tr><td>M55E</td><td>£14-33</td></tr> </tbody> </table>	Ref	£	AT55	£5-36	SONOTONE		V100	£5-95	97AMC	£3-34	ACOS		GP93-1	£2-83	GP96-1	£3-08	B.S.R.		SX6M	£2-91	SC12M	£3-66	GOLDRING		G800	£5-71	G850	£4-94	SHURE		M75-6S	£12-66	M55E	£14-33																																																																																																													
Ref.	Amps	£																																																																																																																																																																																																																								
112	0-5	3-45																																																																																																																																																																																																																								
79	1-0	4-37																																																																																																																																																																																																																								
3	2-0	6-21																																																																																																																																																																																																																								
20	3-0	7-51																																																																																																																																																																																																																								
21	4-0	8-61																																																																																																																																																																																																																								
51	5-0	9-99																																																																																																																																																																																																																								
117	6-0	11-50																																																																																																																																																																																																																								
88	8-0	14-44																																																																																																																																																																																																																								
89	10-0	14-85																																																																																																																																																																																																																								
200V	2A	0-82																																																																																																																																																																																																																								
400V	2A	0-93																																																																																																																																																																																																																								
200V	4A	1-04																																																																																																																																																																																																																								
400V	4A	1-21																																																																																																																																																																																																																								
400V	6A	1-44																																																																																																																																																																																																																								
500V	10A	2-97																																																																																																																																																																																																																								
Ref.	£																																																																																																																																																																																																																									
5 Watt RMS AMPLIFIER	£3-70																																																																																																																																																																																																																									
10 Watt RMS AMPLIFIER	£4-04																																																																																																																																																																																																																									
25 Watt RMS AMPLIFIER	£5-27																																																																																																																																																																																																																									
125W RMS AMPLIFIER	£18-50																																																																																																																																																																																																																									
PRE-AMP for 5-10W	£7-92																																																																																																																																																																																																																									
PRE-AMP for 25W	£15-90																																																																																																																																																																																																																									
POWER SUPPLIES 5-10W	£1-84																																																																																																																																																																																																																									
POWER SUPPLIES 25W	£4-60																																																																																																																																																																																																																									
TRANSFORMER 5-10W	£4-50																																																																																																																																																																																																																									
TRANSFORMER 25W	£6-43																																																																																																																																																																																																																									
Ref	£																																																																																																																																																																																																																									
AT55	£5-36																																																																																																																																																																																																																									
SONOTONE																																																																																																																																																																																																																										
V100	£5-95																																																																																																																																																																																																																									
97AMC	£3-34																																																																																																																																																																																																																									
ACOS																																																																																																																																																																																																																										
GP93-1	£2-83																																																																																																																																																																																																																									
GP96-1	£3-08																																																																																																																																																																																																																									
B.S.R.																																																																																																																																																																																																																										
SX6M	£2-91																																																																																																																																																																																																																									
SC12M	£3-66																																																																																																																																																																																																																									
GOLDRING																																																																																																																																																																																																																										
G800	£5-71																																																																																																																																																																																																																									
G850	£4-94																																																																																																																																																																																																																									
SHURE																																																																																																																																																																																																																										
M75-6S	£12-66																																																																																																																																																																																																																									
M55E	£14-33																																																																																																																																																																																																																									

Hi
BUFFALO BOY!
What's
cooking?

I'm cooking up a new
electronic masterpiece!
I'm off to HOME RADIO now
to buy the components.

During the many years we've been serving the needs of radio and electronic constructors we've seen quite a few odd customers at our Mitcham shop, but we must admit we've not yet had a Chinese buffalo boy. However, even such a customer wouldn't really surprise us, for we get an amazing variety of characters, all having a common enthusiasm for this ever-growing hobby. They come to us knowing they can choose from a wonderful stock of components. They know too they'll get that extra bit of "service" that makes all the difference. Of course, apart from those who call at our shop we have thousands of faithful customers who order regularly by post, having chosen their components from our famous catalogue. Why not join them?

First of course you need our catalogue—all 200 pages of it! It's so packed with good things that it's known as the constructor's "Bible". It costs just £1 plus 40p for post and packing. With it comes a free Bargain List showing many items at such knock-down prices that the savings can pay for the catalogue several times over. Send for a catalogue today, using the coupon on the right.

A wise
move—
POST THE
COUPON
with cheque
or P.O. for
£1-40

Please write your Name and Address in block capitals


NAME

ADDRESS

HOME RADIO (Components) LTD, Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No
917984 London

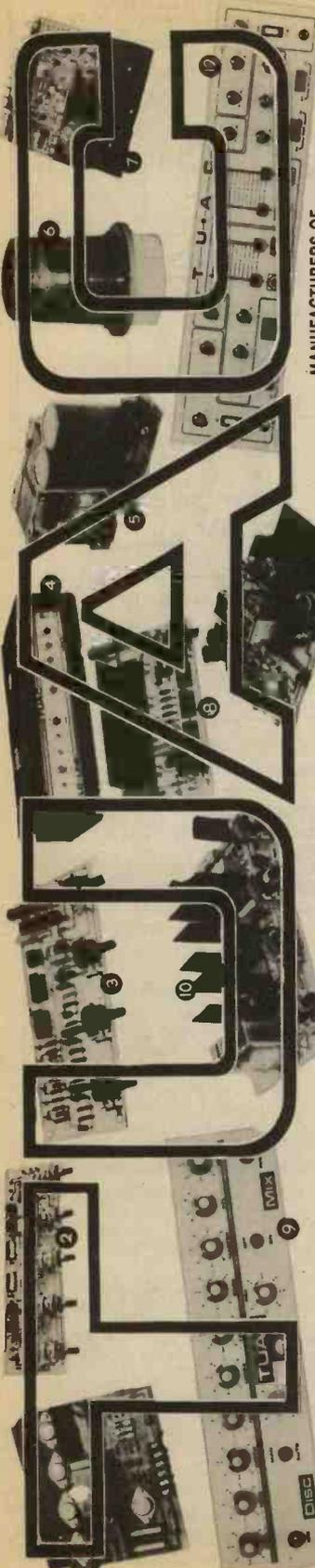HOME RADIO (Components) LTD Dept. PE 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422



TRANSISTOR UNIVERSAL AMPLIFICATION Co. Ltd. PHONE 01-672 3137/672 9080

9 MONO DISCO MIXER WITH AUTO FADE

Designed for the discerning D. J. of professional standard. Offering a vast variety of functions. Controls, Mic Vol., over-ride, depth, auto-manual, auto-off, R.F. Chorus, Volume, Treble and Bass, Tr. Phn Vol Selector, Master Vol On Off sw. Max output 3V RMS. Specification: Deck inputs—50mV into 1M Ω ; Deck Tone Controls—treble total range 36dB at 15kHz—Bass total range 36dB at 50Hz. Mic input—200 ohms upwards 2mV into 22k. Mic Tone Control—Total range 40dB at 15kHz. Tape input—100mV into 200 ohms. Power requirements: 20-50 volt/100mA at 50mA. R.I.A.A. comp mag inputs available 1sp extra. PANEL SIZE 10 x 4 1/2 in. DEPTH 3 in.

12 STEREO DISCO MIXER. T/S SWITCHING, etc. £115-00

4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER—4LSMI 8

- RCA 8A Triacs
- 1000W per channel
- Fully suppressor and fused
- Speed control for fixed rate sequence from 8 per minute to 25W per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections
- Patents applied for.

Model 501 500W per channel as above without sound triggering £12-25

10 3 CHANNEL LIGHT MODULATOR

- RCA 8A Triacs
- 1000W per channel
- Fully suppressor and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections

(Single Channel Version 1500 Watts £9-50)

3 ADD SEQUENCE CHASING AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR


- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel
- 12 easy connections

SEQUENCE DIMMER MODULE—3SDM1 £13-00

6 FUZZ LIGHTS RED GREEN BLUE AMBER £21-50

FRONT PANEL FOR LIGHTING EFFECT MODULES

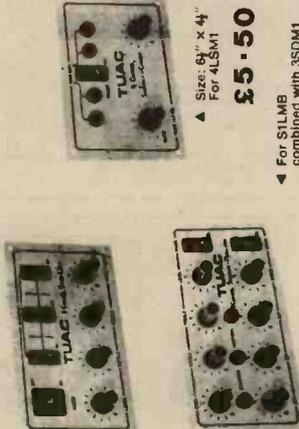(complete with switches, neons and knobs) as illustrated



▲ Size: 6 1/2" x 4 1/2"
For 4LSM1
£5-50

▲ For 3SDM1 combined with 3SDM1
£7-50

Size: 9" x 4 1/2"

ALL PRICES INCLUDE V.A.T.

POSTAGE AND PACKING stamped and addressed envelope with all enquiries for fully illustrated 12 page catalogue. Trade and Export Enquiries 01-672 9080

STOCKISTS—CALLERS ONLY

Geo. Mathews, 85 87 Hurst Street, Birmingham (Tel. 021 622 1941)
Arnold Salts Ltd, 28 Gardner Street, Tel. B. 656 656 (Birmingham)
Bristol (1956)
Sococod, 9 The Friars (Tel. Canterbury 60948)
Cooks Disco Centre, 136 West Street (Tel. Crewe 4739)
A1 Music Centre, 89 Oxford Street, Manchester (Tel. 061 236 0340)
C.B. Electronics, 54 Montagu Street (Tel. London 01 692 4412)
Damon Electronics, 88 Carrington Street (Tel. Nottingham 53880)
Luton Disco Centre, 88 Wellington Street, Luton (Tel. 411733)
Mitchell Electronics, 7 Queen Street (Tel. Salisbury 22589)
Seddon Music, 163 Mitcham Road, Wokingham (Tel. 0734 72143)
465, Stur 3 35 3 m 5 25 5 m Half Day West 9 30 a m 1 p m

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN G.T. BRITAIN FULLY TESTED AND GUARANTEED

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT

THE PIEZO SUPER HORN has all the features! ONLY £10-95

- NEEDS NO CROSS-OVER NETWORKS. FREQUENCY RESPONSE 4000-30,000HZ
- 5-10 WATT OUTPUT. PRINTING, NO VOICE COILS OR MAGNETS
- HIGH IMPEDANCE. ADAPTS TO ANY SYSTEM
- HIGH ACOUSTIC OUTPUT
- MANY CAN BE CONNECTED IN SERIES TO FORM AN ARRAY—INCREASED OUTPUT
- POWER HANDLING CAPACITY 25 volts RMS—see chart

POWER HANDLING GUIDE	
System Impedance	Capacity
2 ohms	312 watts
4 ohms	156 watts
8 ohms	78 watts
16 ohms	39 watts



COMPACT—3 1/2" x 3 1/2" x 2 1/2"

AMPLIFIER MODULES

- 7 TL30** D.C. COUPLED 5 x 5 x 1 1/2 in. **£12-50**
 - 30 watt R.M.S. continuous sine wave output
 - 8 transistors 4 diodes
- 11 TL60** 5 x 5 x 3 in. **£16-75**
 - 60 watt R.M.S. continuous sine wave output
 - 2 R.C.A. 110 watt 15 amp transistors
- 11 TL100** 5 x 5 x 3 in. **£18-75**
 - 100 watt R.M.S. continuous sine wave output
 - 2 R.C.A. 150 watt 15 amp transistors
- 1 TP125** 7 x 6 1/2 x 3 in. **£23-25**
 - 125 watt R.M.S. continuous sine wave output
 - 4 R.C.A. 150 watt 15 amp output transistors

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE 87) or quote Access/Barclaycard No. and post to TUAC LTD. (PE87), 119 Charlmont Road, London SW17 9AB. We accept phone orders from Access/Barclaycard Holders. Phone 01-672 9080.

How to support a SC/MP!

NEW SC/MP USERS START HERE

We make getting into microprocessors as painless as possible, with our range of SC/MP kits we can offer a start at virtually any level of experience or available finance.

SCRUMPI is our own SC/MP starter kit. It contains one SC/MP chip, two MM2112 RAM chips, two 74C173 four-bit I/O latches and a handful of other ICs, switches and LED lamps. The switches allow you to enter a program into the RAM and then execute that program, several operating modes allow for ease of testing. SCRUMPI can be extended to address up to 64K bytes and can be interfaced to ROM, PROM, RAM, EAROM or many types of I/O devices. SCRUMPI can also be used to replace a SC/MP in another circuit to give full in-circuit testing facilities. Kit contains PCB, IC sockets, cable, resistors, caps, etc. KIT PRICE £55.56

INTROKIT AND KBDKIT. Eurocard PCB with SC/MP chip, 256 bytes of RAM and 512 bytes of PROM containing KITBUG program, requires a TTY device as I/O. If you do not have access to a TTY then the NS KBDKIT allows you to replace the KITBUG PROM with another supplied, add a few other components (supplied) and you have a portable microprocessor

INTROKIT £66.33 KBDKIT £66.50

SCI SC/MP Control Card. Eurocard PCB with provision for 256 bytes of RAM and 1K bytes of PROM with basic I/O device address decoding. Similar in concept to the INTROKIT PCB but can be supplied with or without RAM or PROMs. PROMs can be supplied with any of our software programs listed below.

SCI PCB + decoding chips £13.89* SCI PCB + SC/MP + RAM + one PROM £60.19*
SCI PCB + second PROM £87.96*

LCDs. National's Low Cost Development Kit for SC/MP. Uses a hex keyboard and digital display or a TTY device to communicate with a 2K monitor program in ROM. The CPU application card plugs into one of the sockets on the main mother PCB. Additional PROM and RAM application cards are available to expand the system to its full 64K byte capacity. RUN/STEP/HALT modes allow for simple debugging. LCDs £349.30

EXISTING USERS START HERE

VDU SYSTEM. Two Eurocards which allow for interlace to a modified TV set (video not UHF) and ASCII keyboard. The TV display is in the form of 16 lines each of 64 characters (or 16x32 or 8x32 can be used), each character position can display any of 64 5x7 characters in black on white, black on grey, white on grey or white on black, any character set can also be flashed. Any keyboard giving parallel ASCII plus negative strobe output can be used. VDU SYSTEM £83.34*

CASSETTE INTERFACE. Eurocard PCB with interface to audio cassette recorder in format specified by National Semiconductors. Also includes a TTY interface as found on an INTROKIT together with a relay which can be used to switch a reader/punch or cassette recorder. Requires CASSETTY or CASSIO software (or similar as published by NS). CASS INTERFACE £16.67*

TTY INTERFACE. Convert your parallel I/O device to be TTY compatible and thus talk to your INTROKIT or LCDs (or 6800, 8080, 280, etc.). Parallel I/O is TTL or 5V CMOS compatible TTY INTERFACE £18.52*

4K PROM CARD. Eurocard PCB with sockets for up to eight MM5204 or MM5214 devices with address decoding for each device. Supplied with 2, 4, 6, or 8 blank or programmed PROMs from our selection below.

4K PROM CARD with 2 PROMs £54.82* 4K PROM CARD with 4 PROMs £120.38* 4K PROM CARD with 6 PROMs £160.87* 4K PROM CARD with 8 PROMs £204.34*

* These cards are all compatible with each other and with ETI SYSTEM 68.

SOFTWARE In MM5204 PROMs

Our range of software PROMs is small at present but new programs will become available every month.

VDUBUG. Uses a VDU and ASCII keyboard to give Memory Dump, Memory Change and Execute facilities.


CASSIO. Adds National's cassette interface to VDUBUG.

CASSETTY. National's cassette interface and TTY interface as executable sub-routines.

BLANK. MM5204C erased to logic '0'.

All above PROMs at £32.30 each

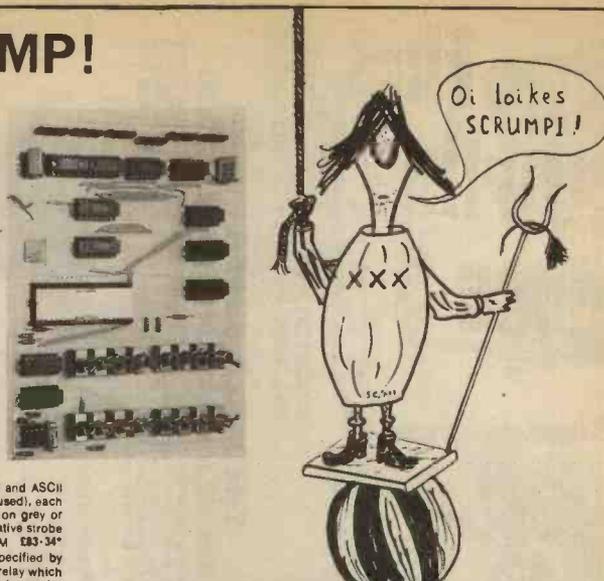We also stock a wide range of buffers, gates, RAMs, PROMs, data, etc. We have power supplies, cases, floppy discs, printers, etc. Send a S.A.E. for our microprocessor catalogue. (P.S. we still sell clock chips and kits.)



BYWOOD

BYWOOD ELECTRONICS
68 Ebbw Vale Road
Hemel Hempstead HP3 9QR
Tel. 0442 62757

Terms: C.W.O., Access or Barclaycard. Credit facilities to accredited accounts. 15% handling charge on cancellations after despatch. All prices exclude 8% VAT. Post and packing 30p.

PHILIPS



YOU & PHILIPS HI-FI KITS

The top sellers for home assembly in Europe - now available in the U.K.

Now - read all about the Philips range of quality kits for home assembly - mixers, amplifiers, speakers, etc, etc. Send today to S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London N17 0RN

Please send me, quickly, the new colour catalogue. PE 61

Name _____

Address _____

Postcode _____

PHILIPS

FOR THE FIRST TIME IN BRITAIN!
PHILIPS ELECTRONIC KITS
direct from S.S.T. Distributors

free SEND TODAY!


S.S.T. Distributors is a member of the Philips Group of Companies.

NOW AVAILABLE IN THE U.K!

CHINAGLIA



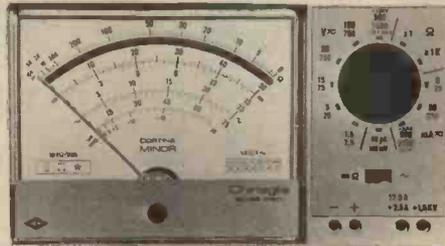ONE OF ITALY'S LEADING TEST EQUIPMENT MAKERS
PRESENT THE CORTINA MINOR



One of a range of professional quality instruments now available to U.K. users.

- SENSITIVITY 20,000 Ω/VOLT (D.C.), 4,000 Ω/VOLT (A.C.) ● ROBUST DIODE PROTECTED PRECISION MOVEMENT ● 33 RANGES D.C. VOLTS 0-100mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1,500V, D.C. CURRENT 0-50µA, 5mA, 50mA, 500mA, 2.5A, A.C. VOLTS, 0-7.5V, 25V, 75V, 250V, 750V, 1,500V, A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A, dB RANGES, -10 to + 69, RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100µF, IF F.S.D. ● ACCURACY-RESISTANCE, D.C. VOLTAGE AND CURRENT 2.5%, A.C. VOLTAGE AND CURRENT 3.5% ● OHMS RANGES POWERED BY INTERNAL BATTERIES ● COMPACT SIZE: 150 x 85 x 40mm 350g
 - CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR
 - PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT
 - FULLY GUARANTEED FOR 12 MONTHS ● AFTER SALES SERVICE AND SPARES FACILITIES ● SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET ● SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS OPTIONAL EXTRA.
- PRICE £35.10 (p & p £1) PROBE £12.85 inc. of VAT

For full details of the Chinaglia range contact:

ALCON Instruments Ltd.
19 MULBERRY WALK, LONDON SW3 6DZ TEL. 01-352 1897

This is Stirling Sound's price bombshell!

NO MORE V.A.T. & POSTAGE PROBLEMS

+ NEW DIRECT FROM FACTORY DELIVERY SPEED-UP

Another FIRST for Stirling Sound / B-P-P



THE FACTORY

Organised in the name of better service. Now our mail order dept. is right where the goods are made.

THE SHOPS

Really 3 shops—audio showroom, component bargains, modules, etc. Well worth a visit.



Why worry any more about working out VAT (12½% on £4.87 plus 8% on £3.39* plus 85p for p. & p., or should it be 54p?). We do it for you. Just send your order with the advertised prices—we attend to the rest. Buy at our shop in person and we deduct the postage charges automatically. *This is not all.* Now you send your orders direct to our factory (see below) where we make Stirling Sound products and we send back your order from there even quicker—real time saving that! AND STIRLING SOUND PRICES REMAIN KEENLY COMPETITIVE ALL THE TIME maintaining the lead we took in 1959 by being first to sell bargain component packs. We've come a long way since then—with our exciting programme for the seventies we're going even further!

YOU PAY THE PRICE YOU READ AND NOTHING MORE

subject only to (very rarely) there being a printing error or really vicious price rise in production costs. You're SAFE when you buy from Stirling Sound—the business that has grown on really understanding customers' needs and interests.

Special quotations to large quantity buyers. U.K. and overseas enquiries invited.

BEST SELLERS FROM OUR 1977 RANGE OF Q.V. MODULES

THE POWER AMPS

- SS.103 3 watt r.m.s. mono i.c. with short circuit protection £2.33
- SS.103-3 Stereo version of above using two i.c.s £4.33
- SS.105 5 watts r.m.s. into 3 ohms, using 12V supply £3.49
- SS.110 10 watts r.m.s. using 24V and 4 ohm load £4.05
- SS.120 20 watts r.m.s. into 4 ohms, using 34V supply £4.61
- SS.140 40 watts r.m.s. into 4 ohms using 45V. Ideal for small discos. Size 4" x 3" x 2" £4.99
- SS.1100 100 watts r.m.s. with heatsink type mounting bracket, short circuit protection £10.43
- SS.1100/H with full size heatsink (£11.39) (£11.82)

TONE CONTROL AND PRE-AMP MODULES

- SS.100 Active tone control, stereo, ±15dB on bass and on treble £3.00
- SS.101 Pre-amp for ceramic cartridges etc. Stereo. Passive tone control details supplied £2.33
- SS.102 Stereo pre-amp for low output magnetic P.U.s R.I.A.A. corrected £4.09

UNIT ONE

Combined pre-amp with active tone-control circuits. ±15dB at 10kHz treble and 30Hz bass. Stereo. Vol./balance/treble/bass controls. 200mV out for 50mV in. Operates from 10-16V £3.00

UNIT TWO

As Unit One, but for magnetic pick-ups. For inputs 1 to 5mV per channel. R.I.A.A. corrected. Adaptable to ceramic. Designed to genuine hi-fi standards. £12.43

THE BARGAIN THEY ALL WANT!

Your chance to lay the foundations of a really powerful disco or P.A. assembly at a marvellous price. This guaranteed Stirling Sound triumph is built for real hard work, so why pay more?

It's the SS.1100 100 watt R.M.S. amplifier (£10.45) together with SS.370 power unit (£14.63) plus full size heatsink for amp. (£1.39) yours for **£24.25** —A saving of £2.20!

(Items bought separately come to £26.45)

8 POWER UNITS

at very competitive prices

Firstly, the range covers well over 65% of all constructors' needs. Secondly, with 13-15 volt take off points on all models except SS.312, you get a valuable bonus; thirdly, the stabilised models with variable outputs complete a range to suit almost all requirements.

Complete with mains transformers and low volt take-off points.

SS.312	12V/1A	£6.35
SS.318	18V/1A	£6.54
SS.324	24V/1A	£7.27
SS.334	34V/2A	£8.31
SS.345	45V/2A	£9.98
SS.350	50V/2A	£10.38
SS.370	70V/2A	£14.63

SS.310/50 Complete stabilised power supply with variable output from 10 to 50V/2A. Built-in protection against shorting £16.69

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built-in protection against shorting £5.02

F.M. TUNING MODULES


- SS.201 Front end tuner, two gang, slow geared drive. A.F.C. facility. Tunes 88-108MHz £5.90
- SS.202 I.F. amplifier. Metering and A.F.C. facilities £3.46
- SS.203 Phase Lock Loop Stereo Decoder for use with the above or any other standard type FM mono tuners. A LED may be fitted £4.19
- SS.203-1 Coil type Stereo Decoder Neg. earth with I.C. £3.06
- SS.203-2 Pos. earth, transistor £2.50

MAIL ORDERS

STIRLING SOUND Dept. PE.6
37 Vanguard Way, Shoeburyness, Essex
Tel. Shoeburyness (0702-28) 5543

SHOP AND SHOWROOM
220-224 West Road, Westcliff-on-Sea,
Essex SS0 9DF

BI-PAK High quality audio

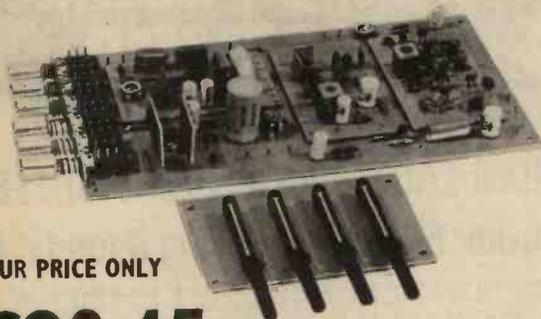

OUR PRICE ONLY

£20.45

The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

STEREO FM TUNER

Fitted with Phase Lock-loop

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v
at 90 Ma max.

STEREO PRE-AMPLIFIER

PA 100



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency Response + 1dB
20Hz-20KHz.
Sensitivity of inputs:
1. Tape Input 100mV into 100K ohms
2. Radio Tuner 100mV into 400K ohms
3. Magnetic P.U. 3mV into 50K ohms
P.U. Input equalises to R1AA curve within 1dB from 20Hz to 20KHz. Supply 20-35V at 20mA. Dimensions—299mm x 89mm x 35mm.

£13.75 p & p 45p

MK60 AUDIO KIT:

Comprising: 2 x AL60's 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £29.55 plus 62p postage.**

TEAK 60 AUDIO KIT:

Comprising: Teak veneered cabinet size 162" x 114" x 32", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £10.70 plus 62p postage.**

AL 60

25 Watts (RMS)

VAT
ADD
12½%

- Max Heat Sink temp. 90C.
- Frequency response 20Hz.
- Distortion better than 0.1 at 1kHz.
- Supply voltage 15-50v.
- Thermal Feedback.
- Latest Design Improvements.
- Load—3,4,5, or 16ohms.
- Signal to noise ratio 80db.
- Overall size 63mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

ONLY **£4.35**

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (r.m.s.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm, 105mm, 30mm. Incorporating short circuit protection.

INPUT VOLTAGE 33-40V. A.C.
OUTPUT VOLTAGE 33V. D.C. Nominal
OUTPUT CURRENT 10mA-1.5 amps **£3.75**
OVERLOAD CURRENT 1.7 amps approx.
DIMENSIONS 105mm x 63mm x 30mm
TRANSFORMER BMT80 £2.60 + 62p. postage

STEREO 30 COMPLETE AUDIO CHASSIS



7 + 7 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins.).

TRANSFORMER **£2.45** plus 62p p & p

TEAK CASE **£5.25** plus 62p p & p.

£16.25 P & P 45p.

equipment mono and other modules for Stereo

THE MEDIUM POWERED AL 80

35^{RMS} w power Amp!

ONLY £6.95

+ 8% VAT


A High Fidelity Power Amplifier with a maximum Power Output of 35 watt R.M.S., which has a maximum operating voltage of 60v. A MUST for all HI-FI users.

Maximum supply voltage	15-60v
Power output for 2% THD	35 watts R.M.S.
Harmonic distortion	0.1%
Load Impedance	3-8-16 ohm
Input Impedance	50K ohm
Frequency response +3dB	20Hz-40KHz
Sensitivity for 25 watts O/P	280mV R.M.S.
Max. Heat sink temperature	90°C
Dimensions	102mm x 64mm x 15mm
Mounting	2, 4BA fixing holes in heat sink
Fuse requirements	1.5A

AND for those who need more P-O-W-E-R

AL250

125^{RMS} w

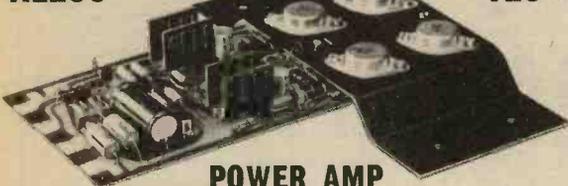

POWER AMP


Specially designed for use in—
Disco Units, P.A. Systems, high power Hi-Fi, Sound reinforcement systems

SPECIFICATION:

Output Power: 125 watt RMS	Total harmonic distortion
Continuous	50 watts into 4 ohms: 0.1%
Operating voltage: 50-80	50 watts into 8 ohms: 0.06%
Loads: 4-16 ohms	S/N ratio: better than 80dBs
Frequency response: 25Hz-20kHz Measured at 100 watts	Damping factor, 8 ohms: 65
Sensitivity for 100 watts output at 1kHz: 450mV	Semiconductor complement: 13 transistors 5 diodes
Input impedance: 33K ohms	Overall size: Heatsink width 190mm, length 205mm, height 40mm

ONLY £15.95 +8% VAT

MPA 30

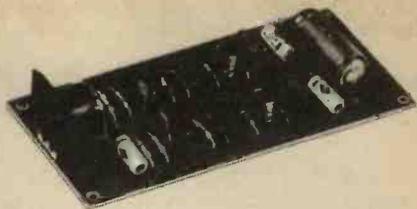

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new BI-Pak M.P.A. 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. Used in conjunction are 4 low noise high gain silicon transistors. It is provided with a standard DIN input socket for ease of connection. Supplied with full, easy-to-follow instructions.


£2.85

VAT ADD 12½%

POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

AL 20-30 AUDIO AMPLIFIER MODULES

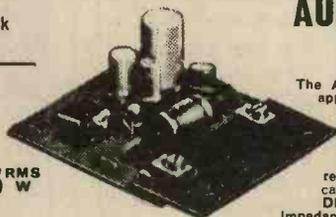

The AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 5 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home. Harmonic Distortion Po = 3 watts f = 0.25% Load Impedance 8-16 ohm

Frequency response ±3dB Po = 2 watts 50Hz-25KHz. Sensitivity for Rated O/P—Vs = 25v, RL = 80 ohm. f = 1kHz 75mV R.M.S. Size: 75mm x 63mm x 25mm.

AL20: 5w R.M.S. £2.95 AL30 10w R.M.S. £3.25

PA12 £6.70

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL20-30 Amplifier Modules. Features include on/off volume. Balance, Bass and Treble controls. Complete with tape output. Frequency Response 20Hz-20KHz (-3dB) Bass and Treble range ±12dB Input Impedance 1 meg ohm Input Sensitivity 300mV Supply requirements 24V. 5mA Size 152mm x 84mm x 33mm

PS12 Power supply for AL20-30, PA12, S450 etc. Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output Current 800 mA Max. Size 60mm x 43mm x 26mm. £1.30

Transformer T538 £2.30

BI-PAK

DEPT. P.W.5 P.O. BOX 6 WARE HERTS
COMPONENT SHOP: 18 BALDOCK STREET, WARE

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

£1.50 BARGAIN PACKS

Pack	No. Contents	Pack	No. Contents
K101	16 BC107	K140	30 2.2µF 25V capacitors
K102	17 BC108	K141	30 4.7µF 25V capacitors
K103	15 BC109	K142	28 10µF 25V capacitors
K104	35 IN4002	K143	26 22µF 25V capacitors
K105	30 IN4004	K144	24 33µF 25V capacitors
L106	25 IN4007	K145	22 47µF 25V capacitors
K107	50 IN4148	K146	20 100µF 25V capacitors
K108	12 AC127	K147	18 220µF 25V capacitors
K109	12 AC128	K148	10 1000µF 25V capacitors
K110	11 AC176	K149	24 1500µF 18V PC
K111	2 AD161/2	K150	30 Red and black croc. clips
K112	20 BC147	K151	11 ½in mono jack plugs
K113	20 BC148	K152	8 ½in stereo jack plugs
K114	20 BC149	K153	15 2.5mm jack plugs
K115	20 BC157	K154	15 3.5mm jack plugs
K116	20 BC158	K155	18 Red and black banana plugs
K117	20 BC159	K156	18 coax. plug, plastic
K118	20 BC348	K157	13 coax. plug, metal
K119	16 BCX33	K158	10 5-pin DIN plug
K120	12 BCY71	K159	15 2-pin DIN plug
K121	4 BD131	K160	11 ½in mono jack socket
K122	4 BD132	K161	8 ½in stereo jack socket
K123	16 BF194	K162	15 2.5mm socket
K124	16 BF195	K163	15 3.5mm socket
K125	16 BF196	K164	10 push-to-make switch
K126	14 BF197	K165	8 push-to-break switch
K127	12 BFY51	K166	10 sub-min DPCO slide switch
K128	20 2N2926		
K129	8 2N3053		
K130	4 2N3055		
K131	20 400mW Zener (state voltage required)	K167	12 assorted colours, insulating tape
K132	14 8-pin i.c. holders	K168	100 sq.in Vero off-cuts (0.1in)
K133	12 14-pin i.c. holders	K169	100 sq.in Vero off-cuts (0.15in)
K134	10 16-pin i.c. holders	K170	100 sq.in Vero off-cuts, mixed
K135	7 741	K171	100 sq.in Vero off-cuts, plain (0.1in)
K136	4 555		
K137	25 1 ohm 2W resistors		
K138	25 ½ ohm 2W resistors		
K139	30 1µF 25V capacitors		

ALL PACKS £1.50 EACH (including VAT and postage)

Buy 10 packs—get 1 (your choice) FREE! All goods in stock—no waiting, sent by return! ALL devices listed are new, full spec., and marked. Money back guarantee. The Greenweld Dragon is your Guardian of good value!

1977 Catalogue available very soon—much bigger and better than the '76 edition, 30p + 15p post, includes discount vouchers.



LEKTROPACKS

17 TURNHAM GREEN TERRACE, CHISWICK, LONDON W.4
Tel. 01-994 2784

MUSICAL EFFECTS EQUIPMENT

... NEW RANGE

- MC350E ECHO CHAMBER**—Top quality unit with endless play tape cartridge. Stationary play heads ensure good reproduction and echo is achieved by changing tape speed. Input imp. 50kΩ and 500 ohms. 240V a.c. operation. **£75.00**
- PS110 MINI FAZER**—Low priced "Phase Shifter" activated by on/off foot switch. 9V d.c. operation. **£27.00**
- RD10 RHYTHM MASTER**—Provides 10 Percussion Rhythms (Waltz, Foxtrot, Western, Polka, March, Rumba, Bossanova, Cha-Cha, Mamba, Rock 1, Rock 2) as accompaniment to other instruments. Has var. speed and tempo controls. 240V a.c. operation. **£79.00**
- GP5 GUITAR PICK-UP**—Easy to fit crystal unit complete with volume control. **£4.95**
- WFB FUZZ WAH PEDAL**—High quality professional standard unit, gives combined "Wah Wah" and "Fuzz" complete with "Fuzz Adjust", Tone, Volume controls and individual effect foot switches. 9V d.c. operation. **£32.00**
- FY2 FUZZ BOX**—Low priced "Fuzz" effect unit with variable speed and volume controls and on/off foot switch. 9V d.c. operation. **£18.50**
- EA45 ECHO REVERBERATION**—High quality combined reverb/erater/mixer amplifier. Has 4 inputs and separate control for reverb. section. 240V a.c. operation. **£39.00**
- RT18 RESLY TONE UNIT**—Basically a tremolo/phase shifter/verb. amp. all in one. A superb multi-effect unit from which an infinite variety of sounds can be obtained. 240V a.c. operation. **£78.00**

MICROPHONE MIXERS

- MM2 MIXER**—Mono/stereo 4 channel unit. Inputs 4 x 50kΩ. Gain 3dB. **£12.00**
- MM4 MIXER**—Mono 4 channel unit. 4 x 50kΩ inputs. Gain 3dB. **£8.00**
- MM3 MIXER**—Stereo 4 channel unit with 2 level control meters. 4 dual impedance (50kΩ or 600Ω) inputs. Gain 13 or 8dB. **£28.00**
- MPX12 MIXER**—Stereo 4 channel mixer/pre-amp. 4 dual impedance (600Ω or 50kΩ) inputs; stereo/phono (magnetic) inputs. Output. 250mV **£42.00**

MICROPHONES

- Suitable for P.A., singing, tape recording, groups, discos, musical instruments, etc.
- UD150 DYNAMIC CARDIOD**—Cardiod mic. with on/off switch. Supplied complete with jack plug/lead and plastic mic. holder. Dual Imp. 50kΩ + 600Ω. **£12.00**
- ECM97D ELECTRET CONDENSER**—Dual Impedance 50kΩ + 600Ω; detachable lead. Freq. response 20-25,000Hz + 2dB. Uni-Directional cardiod. cpl. with w/shield, mic-holder, battery. **£18.00**
- FLEXIBLE METAL GOOSENECKS**—200mm. **£2.50**; 330mm. **£3.50**; 550mm. **£5.00**.

All prices include VAT and U.K. postage

CMOS WITH DISCOUNTS!

Any mix: 10% for 25, 25% for 100, 33% for 1,000



Quartz Crystals
100kHz, MHz, 2-097152MHz, 3-2768MHz,
4-194304MHz, all same price £3.75.
32-768kHz TO5 can, £4.50.
50Hz time base kit for clocks, etc. £5-91
"Dalo" pen. 75p.

4000	0-20	4037	1-06	4075	0-24	14175	1-04	14526	1-22	'E' LED DISPLAYS	
4001	0-20	4038	1-20	4076	1-71	14194	1-17	14529	1-72	DL-704E D-3	70p
4002	0-20	4039	3-09	4077	0-65	14410	0-70	14530	0-95	DL-707E D-3	70p
4006	1-31	4040	1-19	4078	0-24	14411	0-54	14531	1-74	DL-728 2E x 0.5"	£1.80
4007	0-20	4041	0-83	4081	0-24	14412	17.07	14532	1-39	DL-727E 2E x 0.5"	£1.80
4008	1-07	4042	0-93	4082	0-24	14415	7-35	14534	0-15	DL-750E D-6"	£1.50
4009	0-60	4043	1-12	4085	0-80	14419	2-67	14536	4-00	DL-747E D-6"	£1.50
4010	0-60	4044	1-04	4086	0-80	14422	4-98	14537	13.17		
4011	0-20	4045	1-56	4089	1-74	14435	7-93	14539	1-24	RED LEOS	15p
4012	0-20	4046	1-48	4093	0-89	14440	11.58	14541	1.52	0.2"	15p
4013	0-60	4047	1-01	4094	2-08	14450	2-67	14543	1.92		
4014	1-12	4048	0-80	4095	1-16	14451	2-07	14549	4.10	CLOCK CHIPS	
4015	1-12	4049	0-80	4096	1-16	14450	6.51	14552	10.56	AY-5-1224A	£3.50
4016	0-60	4050	0-80	4097	6.13	14501	0.29	14553	4.68	MK 50253	£3.50
4017	1-12	4051	1-04	4098	1-22	14502	1.38	14554	1.67	MK 50382	£3.00
4018	1-12	4052	1-04	4099	2-03	14503	0.75	14555	1.01	(MK 50386 coming)	
4019	0-60	4053	1-64	4101	1-74	14505	6.38	14558	1.01		
4020	1-24	4054	1.28	4102	2.16	14506	0.57	14557	4.85	SOLDERCON PINS	
4021	1-12	4055	1.46	4103	2.16	14507	0.60	14558	1.25	100	80p
4022	1-12	4056	1.46	4104	2.26	14508	3.08	14559	4.10	1000	£4.00
4023	0.29	4057	29.81	4107	0.66	14510	1.51	14560	2.17	2500	£3.75
4024	0.87	4058	8.74	4108	1.45	14511	10.74	14561	3.77	10000 (half price)	£30.00
4025	0.29	4060	1.34	4109	2.21	14512	1.93	14562	5.59	DIL SOCKETS B/14/16 PIN	15p
4026	1.92	4061	25.80	4181	4.30	14514	3.47	14566	1.67	TIMER I.C.	
4027	0.60	4062	10.10	4182	1.73	14515	3.47	14568	3.15	NE555	45p
4028	1.00	4063	1.22	4194	2.26	14516	1.51	14569	3.72		
4029	1.27	4066	0.69	4257	2.26	14517	4.02	14572	2.07	PUSH SWITCHES	
4030	0.60	4067	4.13	4700	1.75	14518	1.39	14580	0.35	Type SW9	15p
4031	2.46	4068	0.24	7083	4.25	14519	0.37	14581	4.30	OP-AMPS	
4032	1.19	4069	0.24	14160	1.16	14520	1.39	14582	1.64	CA 3130 (COS/MOS)	£1.00
4033	1.55	4070	0.65	14161	1.18	14521	2.77	14583	0.84	CA 3140 (BIMOB)	95p
4034	2.11	4071	0.24	14182	1.18	14522	2.15	14584	7.1p	741 Minidip	25p
4035	1.31	4072	0.24	14183	1.18	14526	2.15	14585	1.10		
4036	3.09	4073	0.24	14174	1.08	14527	1.76				

Terms: C.W.O. Add VAT to all prices at 8%. Post, etc. U.K. 25p (+ 2p = 27p) per order. All orders processed same day. Official Govt., Varsity, Poly., etc. orders (written or telephoned) welcome.

GREENBANK ELECTRONICS (Dept. W6P)

94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG, England.
Tel: 051-645 3391

complete digital clock kits



REAL TEAK CASE

NON ALARM
£12.50 + £1 VAT

ALARM
£15.28 + £1.22 VAT
(including P. & P.)

Teak or Perspex case 6 x 2½ x 3in

FEATURES: 4 red ½in high LEDs. 12-hour display with a.m./p.m. indication. Power failure indicated by flashing display. Precise accuracy from mains frequency. Beautiful Burma Teak case or stylish Perspex (state first and second colour choice: white, red, blue, green, black).

NON ALARM: Complete Kit (including Teak case) £13.50 incl.; Module Kit (excluding case) £9.50 incl.

ALARM EXTRAS: Pulsed alarm tone. TIM operated "Snooze" period. Automatic brightness control. Simple setting.

ALARM: Complete Kit (including Teak case) £16.50 incl.; Module Kit (excluding case) £13 incl.

PERSPEX CASES: 50p less than Teak.

READY BUILT: Extra £1 on complete Clocks, extra 50p on Modules.

TIMER FACILITY: Count in seconds up to 9 min 59 sec, extra 50p.

"ALPHA" £12 incl.

Ready Built. Non Alarm. Perspex only.
4 digits phosphorescent green, ½in high, 12- or 24-hour display.



Discount on orders over 5 clocks or kits
Overseas: Add £2.50 for Airmail



Send payment with order. S.A.E. for details

Pulse Electronics Ltd

(PE1) 6 GOWER ROAD
ROYSTON, HERTFORDSHIRE


Telephone: Royston (0763) 43695



Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation. . .

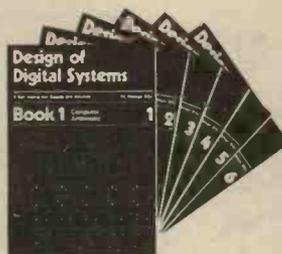Each of the 6 volumes of this self-instruction course measures 11½" x 8½" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers. Design of Digital Systems.



£6.20

plus 80p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4.20

plus 80p P. & P.

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

Cambridge Learning Enterprises (Dept. ENG),
Rivermill House, St. Ives, Huntingdon, Cambs. PE17 4BR

To: Cambridge Learning Enterprises (Dept. ENG)
FREEPOST, Rivermill House, St. Ives, Huntingdon, Cambs. PE17 4BR
*Please send me... set(s) of Design of Digital Systems at £7.00 each, p & p included
*or... set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included
*or... combined set(s) at £10.50 each, p & p included

Name
Address

*delete as applicable
No need to use a stamp—just print FREEPOST on the envelope. PE6

Random FLASHER UNIT
Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random. **£18.95**

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14½ inches
B.C. Fitting **£9.55**
E.S. Fitting **£10.35**

Sound to Light MASTER UNIT
600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INLET SOCKET

TYPE A SPOT
(less lamp)
B.C. Fitting **£1.95** each
E.S. Fitting **£2.12** each

TYPE B 3 BANK UNIT
(Less Lamps)
B.C. Fitting **£6.90** each
E.S. Fitting **£7.26** each

TWIN BANK 12 LIGHT UNIT
(less lamps) Length 31½
B.C. Fitting **£15.60** each
E.S. Fitting **£17.00** each

100 WATT SPOT LAMPS
RED, YELLOW, GREEN
BLUE
CLEAR **£1.40** each
3 lamps **£4.20**
B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. AND POST & PACKING
(These prices apply to the United Kingdom only)

(Send 20p for illustrated leaflet & price list)

ALBEN ENGINEERING CO. LTD.
DEPT. PE THE CRESCENT, WORSTHORNE,
BURNLEY, LANCs. Tel: Burnley 20940



MINI CONSOLES

Ideal for small desk control panels and consoles. Moulded in orange, blue, black and grey ABS. Incorporates slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of console and held by screws running into integral brass bushes.

MC 161 x 96 x 58mm £1.53 (1-9) £1.50 (10+)
 MC 216 x 130 x 75mm £2.20 (1-9) £2.17 (10+)
 Add 25p per £1 order value for Post & Packing

LIGHT EMITTING DIODES

Economy Quality 50 for £5 - 100 for £9
 Mixed bags, all sizes, various colours



Full Specification (In packs of 5 LED's)
 Red (specify size) 75p per pack
 Green, Yellow, Orange (specify size) £1.20 per pack
 (Mounting clips and data with Full Spec. LED's only)

TYPE A NEON INDICATORS

Supplied with resistor for 240 Volts operation
 Held in 8mm hole by plastic bezel
 150mm wire leads




Red, Amber, Clear, Opal 19p each
 Green 28p each

12 VOLTS MINI HAND DRILL

Ideal for drilling pcb, chassis etc as well as model making. Supplied with 2 collets that accept tools and drills with 3/32" and .050" dia. shanks. £7.56 (Includes VAT & P.P.)



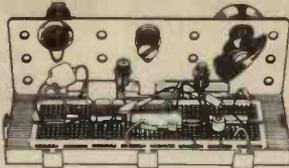Stop wasting time soldering
The NEW MW BREADBOARD accepts Transistors, LED's, Diodes, Resistors, Capacitors and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has over 400 individual sockets, plus Vcc and Ground Bus Strips
 Price £9.72 (includes VAT & P.P.)

TYPE MP NEON INDICATOR

Supplied with resistor for 240 Volts operation
 150mm leads, held in 6.4mm hole by nut



Red, Amber, Clear, Opal 20p each

SEVEN SEGMENT DISPLAYS

Economy Quality
 Common Anode - 0.3" - Left Decimal
 Red, Yellow and Green @ 45p each

Full Specification
 Common Anode - 0.3" - Left Decimal
 Red @ 98p each
 Green and Yellow @ £1.35 each
 (Data supplied with Full Spec. displays only)




Quantity quotations on request

P.P. Note Unless included in price add 25p Post & Packing for orders totalling under £10. All prices include VAT and are valid in UK only for 2 months from Journal issue date

Michael Williams Electronics
 47 Vicarage Av. Cheadle Hulme, Cheshire SK8 7JP

SC BOXES (square corners)

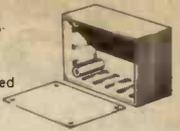
Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of the box and held by screws running into integral brass bushes.



SC 85 x 56 x 35mm 80p (1-9) 77p (10+)
 SC 111 x 71 x 48mm £1.07 (1-9) £1.04 (10+)
 SC 161 x 96 x 59mm £1.49 (1-9) £1.46 (10+)
 Add 25p per £1 order value for Post & Packing

240 VOLTS MINI HAND DRILLS

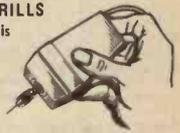Ideal for drilling pcb's, chassis etc as well as model making. Supplied with 3 collets that accept tools and drills with 1mm, 2mm and 1/8" dia shanks.



£9.72 (includes VAT & P.P.)
 Accessory tools... 6 Burs, 1mm, 2mm, 1/8th Drills, 3/32" Collet Price £1.75 (Includes VAT & P.P.)



RC BOXES (round corners)

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Close fitting flanged lids held by screws running into integral brass bushes.

RC 100 x 50 x 25mm 61p (1-9) 49p (10+)
 RC 112 x 62 x 31mm 59p (1-9) 52p (10+)
 RC 120 x 65 x 40mm 68p (1-9) 62p (10+)
 RC 150 x 80 x 50mm 77p (1-9) 74p (10+)
 RC 190 x 110 x 60mm £1.33 (1-9) £1.30 (10+)

Polystyrene version

in grey only with no slots, no integral brass bushes
 RC(P) 112 x 61 x 31mm 35p (1-9) 32p (10+)
 Add 25p per £1 order value for Post & Packing

A MINIATURE POWER TOOL

to speed your building

- Super 30 Kit (30 Tools) (incl. drill without stand) £17.62 plus P. & P. 85p
- Mk. II Drill Stand £4.40 plus P. & P. 35p
- Mk. II Drill only £8.79 plus P. & P. 35p
- Flexible Drive Shaft £5.46 plus P. & P. 25p
- Transformer 240V a.c./12V d.c. £6 plus P. & P. 70p
- Variable Speed Transformer £8.25 plus P. & P. 70p


Replacement drills, stones, burrs, etc. 40p each. Circular saw blades 50p each. £2 per set of 4 sizes. P. & P. any quantity 20p.

All VAT inclusive

PRECISION PETITE LTD.

119a High Street, Teddington, Middlesex TW11 8HG
 Tel. 01-977 0878 (24-hour answering service)

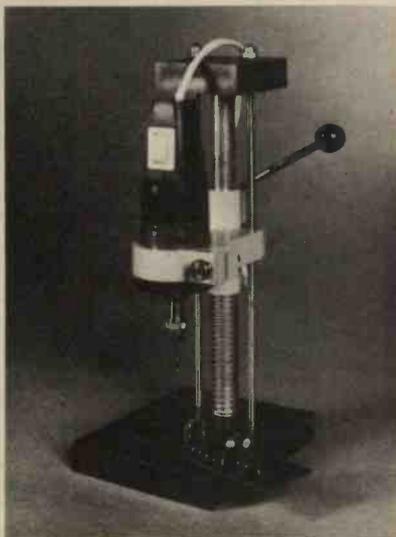9" x 4" S.A.E. please for leaflet and order form



★ TELEPHONES—Modern style 706 Black or two-tone grey £4.50 each. Older black style £1.50 each. P. & P. 75p. All with bells and dial.
 ★ SEMICONDUCTORS—All at 8p each*. P. & P. extra. Guaranteed all full spec. devices. Manufacturer's markings:
 BC147; BC158; 2N3707; BC107; BF197; BC327; 2N4403; BC172B; BC251B; BC251B; BC348B; BC171A/B; 2N3055CA 50p each. P. & P. 3p.
 2N5879 with 2N5881 Motorola 150 watt. Comp. pair £2 pair. P. & P. 15p.
 ★ Linear amp 709 25p each. P. & P. 8p.
 ★ BEEHIVE TRIMMERS 3/30pF. Brand new. 10 off 40p. P. & P. 15p.
 ★ TRIMMER PACKS. As previously advertised. 25p each. P. & P. 15p.
 ★ Meter PACKS—3 different meters £2, P. & P. £1. DON'T FORGET YOUR MANUALS, S.A.E. with requirements.
 GRATICULES 12 x 14 cm high quality plastic 15p each. P. & P. 10p.
 ★ CAPACITOR Pack. 50 Brand New components only 50p. P. & P. 48p.
 ★ 3lb Electronic Goodies £1.60, post paid.
 ★ High Value Printed Board Pack—hundreds of components, transistors, etc.—no flat to the board transistors £1.65 post paid.
 ★ 1000F Feed thru Capacitors 10 for 30p. P. & P. 15p.
 MIVAC Min Neons. Approx 60V Brand New. 10 off 20p. P. & P. extra.
 ★ POT PACK. All Brand New Modern. Single and Ganged. Our choice. 7 for 25p. P. & P. 48p.
 FIBREGLASS BOARD PACK. More board—less money. Larger pieces. Not less than 2.5 sq ft for 95p. P. & P. 65p.
 DON'T FORGET YOUR MANUALS—S.A.E. with your requirements.

TRANSFORMERS—All 240V 50HZ

Inputs
 Type A 17-0-17V 250mA; 7.5-0-7.5V 250mA 0-20V 5 amps; 0-4V 5 amps; 0-1-1.5V 5 amps. £2 each. P. & P. £1.25.
 Type B 17-0-17V 250mA; 8-0-8V 250mA; 0-12-5-13-5V 5 amps; 0-1-5-2V 5 amps. £1.50 each. P. & P. £1.
 Type C 19-0-19V 250mA; 8-0-8V 250mA; 0-7-5V 10p; 0-1-4V 5 amps; £1.25 each. P. & P. £1.25.

* VAT 12%, otherwise 8%

Minimum order £2. Excess postage refunded

CHILTMEAD LTD
 7/9 ARTHUR ROAD, READING, BERKS.
 (near Tech. College) Tel. Reading 582605



15-240 WATTS!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3–100mV; input impedance 47k Ω at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16–50V.

Price £5.22 + 65p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit; low distortion; short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz–16kHz –3dB.

Price £5.22 + 65p VAT. P. & P. free

AVAILABLE
EX STOCK

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; Integral heatsink; only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4–16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz–45kHz –3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price £6.82 + 85p VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; Integral heatsink; load line protection; thermal protection; five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4–16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz–45kHz –3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

Price £15.84 + £1.27 VAT. P. & P. free

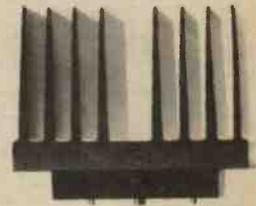

HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; Integral heatsink; no external components.

APPLICATIONS: hi-fi; disco; monitor; power slave; Industrial; public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4–16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz–45kHz –3dB. Supply Voltage— \pm 45V. Size—114 x 100 x 85mm.

Price £23.32 + £1.87 VAT. P. & P. free

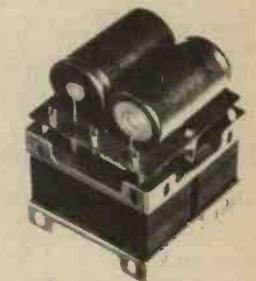

HY400 240W into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; Industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4–16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz–45kHz –3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price £32.17 + £2.75 VAT. P. & P. free

POWER SUPPLIES: PSU36—suitable for two HY30s £5.22 + 65p VAT. P. & P. free. PSU50—suitable for two HY50s £6.82 + 85p VAT. P. & P. free. PSU70—suitable for two HY120s £13.75 + 1.10 VAT. P. & P. free. PSU90—suitable for one HY200 £12.65 + £1.01 VAT. P. & P. free. PSU160—suitable for two HY200s or one HY400 £23.10 + £1.85 VAT. P. & P. free.

I.L.P. Electronics Ltd., Crossland House, Neckington, Canterbury, Kent CT4 7AD

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Neckington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

Registered office No. 1032630

SYNTHESISER AND SOUND EFFECT KITS

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs designed by Phonosonics.

PHOTOCOPIES of the P.E. texts for most of the kits are available—prices in our lists.



P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage, notably P.E. Minisonic Phasing Unit, Wind and Rain, Rhythm Generator, Sound Bender, Voltage Controlled Filter, Guitar Effects Pedal and Overdrive, Fuzz, Tremolo and Wah-Wah units.

The Main Synthesiser: PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp. Full details in lists.

Set of basic component kits £83.03
Set of printed circuit boards £11.45

The Synthesiser Keyboard Circuits (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and additional PSU. Full details in our lists.

Set of basic component kits £48.18
Set of printed circuit boards £7.66

P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, output amp and mixer, power supply.

Set of basic component kits from £64.25
Set of printed circuit boards £9.71

ELEKTOR "FORMANT" SYNTHESISER (Elektor Magazine 1977)

Details of component kits and PCBs are in our lists.

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.59

Alternative component set with panel mounting switches £4.96

Printed circuit board £11.43

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) £7.84

Printed circuit board £11.69

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

Component set (incl. PCB) £2.88

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2.87

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4.48

WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3.55

AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.27

Component set and PCB, with panel switches £4.83

POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £1.50 plus VAT.

Optional insurance for compensation against loss or damage in post, add 35p in addition to above post and handling.

Else, C.I., B.F.P.O., and other countries are subject to Export postage rates.

P.E. JOANNA (P.E. May/Sept. 75)

A five-octave electronic piano that has switchable alternative voicing of Honky-Tonk piano, ordinary piano, harpsichord, or a mixture of any of the three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The power amplifier typically delivers 24 watts into 8 ohms. The PCBs have been redesigned by ourselves making improved use of the space available.

Main power supply, tone generator, 61 envelope shapers, voicing and pre-amp circuits.

Set of basic component kits for above £75.29

Set of printed circuit boards for above £20.35

Power amplifier £15.97

Printed circuit board for power amp 95p

RHYTHM GENERATOR (P.E. Mar./Apr. 74)

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and soft cymbal), and with variable time signatures and rhythm rates. Really fascinating and useful.

Tempo, Timin, Logic, 8 Effects circuits, PSU.

Set of basic component kits for above £36.14

Set of printed circuit boards for above £7.03

REVERBERATION UNIT (P.W. Nov/Dec. 72)

A high quality unit having microphone and line input pre-amps, and providing full control over reverbation level.

Component set (excl. spring unit) £9.73

Printed circuit board £11.96

9in spring unit £6.50

Panel meter (50µA) (optional) £5.70

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £3.72

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit. Including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £8.86

Component set using dual rotary pot £6.20

Printed circuit board £11.62

FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £2.03

TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £3.64

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2.40

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4.58

ENVELOPE SHAPERS

Both of the kits below have manual control over their Attack, Decay, Sustain and Release functions. Kits include PCB (VCA means Voltage Controlled Amplifier)

Envelope Shaper and VCA (P.E. Apr. 76) £5.68

Envelope shaper (without VCA) (P.E. Oct. 75) £4.66

Transient generator (P.E. Apr. 77) £6.34

LIST—Send Stamped Addressed Envelope with all U.K. requests for free list giving fuller details of PCBs, kits, and other components.

OVERSEAS enquires for list: send 40p

DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

An independently designed VCF that can be used with the P.E. Synthesiser.

Component set £3.80

Printed circuit board £1.38

SOUND-TO-LIGHT (P.E. Aurora) (P.E. Apr.-Aug. 71)

Four channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensifiers.

Basic component set (excl. thyristors) £15.92

Printed circuit board for above £3.90

Power supply £5.78

PCB for power supply £1.79

3-CHANNEL SOUND-TO-LIGHT (P.E. Apr. 76)

A simple but effective sound-to-light controller capable of operating 3 lamps each of approximately 700 watts. Includes power supply, thyristors, and by-pass switches.

Component set (incl. PCB) £11.95

DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic component set £18.19

Printed circuit board £3.45

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. An LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic and electronic musical instruments alike.

Main component set (incl. PCB) £15.59

Power supply set (incl. PCB) £7.03

P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duplet, triplet and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.

Component set (incl. loudspeaker) £11.62.

Printed circuit board £2.04

PEAK LEVEL INDICATOR (P.E. Mar. 76)

A twin-channel visual display unit for monitoring the peak level of audio signals. Well suited for use when inter-coupling our many sound producing kits to help avoid signal over-loading.

Component set (incl. PCB) (as published) £3.88

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphascope, cardiophone etc.

Pre-Amp Module Component set (incl. PCB) £4.22

Basic Output Circuits—combined component set with PCBs, for alphascope, cardiophone, frequency meter and visual feedback lamp-driver circuits £6.59

Audio Amplifier Module Type PC7 £7.35

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

Standard tolerance set of components £2.96

Superior tolerance set of components £3.76

Regulated power supply (will drive 2 sets) £4.69

SEMI CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB £9.63

Panel meter (500µA) £5.70

MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl. PCB) £3.78

Prices are correct at time of press. E. & O.E. delivery subject to availability.

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 40p.

PHONOSONICS · DEPT. PE56 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

MAIL ORDER AND C.W.O. ONLY
SORRY BUT NO CALLERS PLEASE

The Finest . . .

KEYBOARDS

The "S.K.A." Plastic Keyboard was developed by Kimber Allen Ltd. in co-operation with a Swedish company and the manufacturers state that in their opinion it is the finest moulded plastic keyboard made and is not to be confused with cheaper keyboards available.

The keys are moulded in Acrylic plastic, a material chosen for its hard wearing properties and ideal feel to the touch. They are moulded in two parts, the key face, which has to be perfect in appearance and finish, and the action, which has to be strong and carry the mechanism. The strong section of aluminium extrusion upon which they are mounted is specially designed to take all the pressures of playing. Springs, felts, and contact actuators are supplied ready-fitted.



The contact assemblies are constructed of laminated bakelite, thus giving smooth slot walls and completely free movement of the gold-clad contact wires. Types available as follows (Contact pairs normally open):

GJ—SPCO	24p each	GH—5 pairs	57p each
GB—2 pairs	27p each	4PS—SPCO and 3 pairs	53p each
GC—3 pairs	36p each	Palladium Wire Bus Bars, 1 octave lengths	50p each
GE—4 pairs	45p each		

SEE OUR OTHER ADVERT FOR SYNTHESISER AND SOUND EFFECT KITS AND SEE OUR LISTS FOR OTHER COMPONENTS AND ACCESSORIES STOCKED. SEND S.A.E. FOR FULL LIST (OVERSEAS SEND 40p).



and CONTACTS

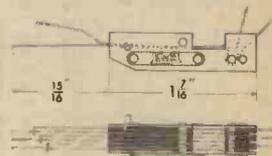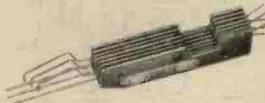

U.K. Post and Handling:

Keyboards: £1.50 each

Contacts: orders under £15: 25p;
orders over £15: 50p

37 Note C-C Keyboard
£25.50

49 Note C-C Keyboard
£32.25

61 Note C-C Keyboard
£39.75

VAT: Add 12 1/2% to final total on all U.K. orders

EXPORT ORDERS ARE WELCOME but please see our price list for Export Postage Rates. N.B. Eire, Channel Isles and B.F.P.O. classify as export.

Mall Order and C.W.O. only—Sorry but no callers please

Prices are correct at time of Press. E. & O.E. Delivery subject to availability

PHONOSONICS

DEPT. PE56, 22 HIGH STREET
SIDCUP, KENT DA14 6EH

INVERTORS



240v—50Hz from your 12v car battery.

25 watt—£4.75	300 watt (24v)—£26.45
40 watt—£8.27	400 watt (12v)—£39.05
75 watt—£12.03	500 watt (24v)—£48.18
150 watt—£21.27	1kW (50v)—£127.00
300 watt (12v)—£33.03	1.5kW (110v)—£140.80

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v—50Hz—150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 + £1.70p. & p.

DIGITAL WATCH

L.E.D. display giving hours, minutes, seconds and date. Design based on American technology, and fantastic value at £18 + 30p p. & p. One year guarantee.

TRANSFORMERS & COILS

Both high volume & small order capacity available. Special offer. Miniature mains transformer 6-0-6v—6V.A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

P.E. ORION STEREO



20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz—10kHz. Frequency response \pm 1dB 20 Hz to 20 kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £47.30 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

P.E. ORION TUNER

Full kit of parts for this superb tuner unit to complement the now well established amplifier. Parts may also be purchased separately. Send S.A.E.

ASTRO IGNITION



ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 incl. VAT. Ready built with only two connections to alter £13.75 incl. VAT. Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS

Spring Bank Road, West Park
Chesterfield.

INTERNATIONAL ELECTRONICS UNLIMITED

TTL	7400	7401	7402	7403	7404	7405	7406	7407	7408	7409	7410	7411	7412	7413	7414	7415	7416	7417	7418	7419	7420	7421	7422	7423	7424	7425	7426	7427	7428	7429	7430	
10-10	11	11	11	11	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	
10-13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	
74154	74155	74156	74157	74158	74159	74160	74161	74162	74163	74164	74165	74166	74167	74168	74169	74170	74171	74172	74173	74174	74175	74176	74177	74178	74179	74180	74181	74182	74183	74184	74185	74186

CMOS	4000A	4001A	4002A	4006A	4007A	4008A	4009A	4010A	4011A	4012A	4013A	4014A	4015A	4016A	4017A	74C00	74C01	74C02	74C04	74C08	74C10
21	21	21	1-10	22	1-46	47	48	48	22	22	1-17	1-22	1-22	1-22	1-19	26	26	1-25	68	35	
4018A	4019A	4020A	4021A	4022A	4023A	4024A	4025A	4026A	4027A	4028A	4029A	4030A	4031A	4032A	4033A	74C74	74C76	74C107	74C151	74C154	
89	89	1-22	1-11	90	21	72	41	48	81	17	1-04	99	1-21	48	1.04	1.36	1.13	2.62	3.15		
4066A	4068A	4069A	4071A	4072A	4073A	4074A	4075A	4078A	4082A	4518A	4528A	4585A	4901A		2.49	2.66	2.66	2.22	2.26		

**SHIPMENT MADE VIA AIR-POSTAGE PAID
3 DAYS FROM RECEIPT OF ORDER**

1702A
2048 bit static PROM elect.
prog. UV ears. 24 pin
£5-00

CENTRAL PROCESSING UNIT
8008 £12-95
8080A £12-95

2102
1024X1 STATIC RAM 16 PIN
£8-89

UART
AY51013A
£4-50

LED DISPLAYS DISCRETELEDS
MAN 1 £1-39 ME 4 £-20
MAN 2 2-79 MV 10 B -18
MAN 5 1-57 MV 50 -09
MAN 7 1-04 NSL100 -09
MAN 8 1-57
MAN 66 1-57 MV5020
FND 359 -63 RED -12
FND 500 1-33 CLEAR -12
FND 507 -75
DL10A 1-39

7489
64 bit ROM TTL 16 pin
£1-25

2518
HEX 32-bit STATIC SHIFT REGISTER
£2-00

2519
HEX 40-BIT STATIC SHIFT REGISTER
£2-00

10% OFF WITH £15 ORDER
15% OFF WITH £50 ORDER
THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED

MEMORIES
1101 256 bit static RAM -89
1103 1024 bit dynamic RAM -79
2102 1024 bit static RAM 1-50
5261 1024 bit dynamic RAM -79
F93410 256 bit bi-polar RAM 1-19
2513 ROM — character generator 7-00
82523 256 bit PROM 2-50

2708 1x 8k
EPROM
£20-00

IC SOCKETS - low profile
Solder tail - low profile
8 pin L-11 24 pin £-25
14 pin -12 28 pin -16
16 pin -13 40 pin -42
18 pin -19

LINEAR	101	102	104	105	107	108	109A	110	111	114	1201	1208	122
124	21	49	56	60	64	69	75	75	87	82	1-12	1-32	69
124	119	148	170	172	173	176	180	180	181	182	1-12	1-32	56
560	562	565	567	567	567	567	567	567	567	567	2-47	2-47	58
2-23	1-38	1-38	1-38	1-38	1-38	1-38	1-38	1-38	1-38	1-38	748	748	58
2-23	2-23	2-23	2-23	2-23	2-23	2-23	2-23	2-23	2-23	2-23	75491	75491	63

Date sheets on request. Add 20p ea. if item is priced below 50p each.

Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), international money order (include receipt) or bank cheque (make payable in U.S.).

Add 50p to cover shipping and handling if order is less than £5. The above prices do not include any taxes leviable by a purchaser's country of residence.

INTERNATIONAL ELECTRONICS UNLIMITED
VILLAGE SQUARE, P.O. BOX 449
CARMEL VALLEY, CA 93924 USA
PHONE (408) 659-3171

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of the many opportunities open to trained people. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

- City & Guilds Certificates:
- Telecommunications Technicians
- Radio, TV, Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- MPT Radio Communications Certificate

- Diploma Courses:
- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV, Audio Engineering and Servicing
- Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET.

To: International Correspondence Schools

ICS Dept. 771G Intertext House, London SW8 4UJ or telephone 01-622 9911

Subject of Interest.....

Name.....

Address.....

Tel.....

- SUB-MINIATURE 8 OHM LOUDSPEAKERS 1 1/4" dia., 75p each.
- 10 MULTI-TURN TRIM-POTS assorted for 60p.
- 1.000uF 40V.W. ELECTROLYTIC, size 1 1/2 x 1/4, 3 for 35p.
- TO39 5W NPN DARLINGTON TRANSISTORS, 20p each.
- 6 to 1 FRICTION SLOW MOTION DRIVES, 55p each.
- STANDARD 5K POT WITH SP SWITCH, 3 for £1.
- 2A WIRE ENDED CHOKES, 6 for 50p.
- 200 ASSORTED 1/2, 1W RESISTORS for 75p.
- 30 ASSORTED 10XAJ CRYSTALS, £1-10.
- AUDIBLE ALARM SYSTEM WITH TRANSISTORS and I.C. 12V, 75p.
- 20 PHOTO TRANSISTORS and PHOTO DARLINGTONS untested, £1.
- BRANDED TO92 PLASTIC BC108, BC212 types, 10 for 60p.
- 20 ASSORTED BRANDED 250mV ZENERS for 60p.
- EDGEWISE CENTRE ZERO 200uA METERS, 90p each.
- EDGEWISE LEVEL METERS 200uA, 90p each.
- PLASTIC TRACS 400 PIV 6A, 60p each.
- MULLARD C280 CAPACITORS 100 assorted for 57p.
- DUAL GATE MOS FET's like 40673, 33p, 4 for £1-10.
- 50 ASSORTED ELECTROLYTIC CAPACITORS for 57p.
- BOOKS. "Practical Test Equipment", 75p. "Simple Short Wave Receivers", 60p. "Practical Electronic Projects", 75p. The three books for £1-60.
- 50 BC107-8 TRANSISTORS untested for 57p.
- 800V 2A PLASTIC TO3 NPN TRANSISTOR, 50p, 3 for £1-10.
- TEXAS POWER PNP DARLINGTONS TYPE TIP 117, 35p each.
- STUD MOUNTING S.C.R.'s 10A type, 100 PIV, 25p, 400 PIV, 50p, 800 PIV, 60p.
- 60 ASSORTED WIRE WOUND RESISTORS 1 to 10W, 57p.
- AUDIO I.C.'s LM380, 80p. SN7601N, 50p.
- TRANSFORMERS 240V a.c. input. Type 1, 22V 1A, 88p. Type 2, 22V 300mA 7 1/2 1A, 99p. Type 3, 18V 500mA, 88p.
- 0-5V 5mA SILICON SOLAR CELLS, 35p.
- 30W PLASTIC POWER TRANSISTORS npn, 22p, pnp, 25p, 35p pair.
- 50 A.C. 120 TRANSISTORS branded but untested for 57p.
- 200 + 200 + 100uF 500V.W. ELECTROLYTIC 2 1/2 x 1 1/4, 25p each. 10 for £1-80.
- 100 SUB-MINIATURE 50V.W. DISC CERAMICS assorted for 57p.
- MINIATURE SILICON DIODES assorted PIV's for 57p.
- ELECTROLYTIC CAPACITORS 3300uF 16V.W. size 2 x 1/4, 25p, 4700uF 16V.W. size 2 x 1/4, 25p, 7500uF 16V.W. size 3/4 x 1 1/4, 55p.
- RADIO I.C. ZN414 with data, £1.
- 250pF SOLID DIELECTRIC VARIABLE CAPACITOR, 33p.
- B2087 PLASTIC POWER 90W TRANSISTORS, 55p each.
- SUB-MINIATURE TOGGLE SWITCHES SPST, 35p; DPDT, 45p.
- EMI HUGHES or TRANSITRON GOLD BONDED DIODES, 50 for 40p.

Please add 20p for post and packing on orders under £2. Overseas orders at cost.

J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln LN2 1JF
Tel. 20767

NOT TOTALLY BINDING

LARGE scale integration brings highly complex circuit systems within the ordinary constructor's reach. But at what cost to individual freedom and enterprise? The central LSI package rules the roost. It determines the overall pattern and personal designing is severely limited to a few peripheral trimmings, so far as the actual electronics is concerned. More scope is of course offered in the mechanical arrangement of the final working model for here personal preferences can be indulged in.

This somewhat pessimistic view is broadly true, although it does not apply totally in all cases. The general drift is at any rate discernible and is sufficient to suggest to some that the nature of project building is undergoing change, that a new era of "kit constructing" is dawning, an era reminiscent in many ways of the hey-day of the radio kits of the 20's and 30's. But the comparison is not quite fair since the present-day constructor has far more freedom of subject than the radio constructor of old who assembled kits strictly according to an unalterable plan. Today's electronics constructor has the advantage of the most advanced technology, in, moreover, a convenient miniaturised form. And not *all* LSI packages coming on the market are pre-ordained for some unique or exclusive electronic environment. Sometimes the options are open and true inventiveness has opportunity to shine outside the central star performer, the LSI chip.

Our Television Sportcentre is built around a well-known LSI chip and, naturally, individual initiative is rather restricted in this case. Even so, the opportunities are there, as a study of some of our contemporaries who have featured this same device will demonstrate. Each published design has its own individuality which shows through clearly. This provides good evidence that the construction of major projects based on the identical LSI chip need not necessarily become a drab uniform procedure, nor even just a kit assembly operation, as some might fear.

A greater danger to the hobby field comes from complete ready-made equipment. Television games again provide a good example at this very time. Maybe home constructed equipment of this kind will not be able to compete economically with the mass produced article, and TV games will join their honourable and distinguished predecessors the transistor radio, the pocket calculator, and the digital wristwatch as subjects generally abandoned after the initial experience in building one just for the sheer fun of the thing.

So this month's presentation of the Television Sportcentre may be a "one-appearance only". But who can really tell? Further innovations on the TV game theme are coming along from the i.c. manufacturers and it would be rash to predict any early closure of constructor activities in this particular field.

All users, commercial equipment makers and amateur constructors alike, have become dependent upon the device maker for the basic system design equally as for the actual device itself. Resourceful amateur designers will relish the challenge offered by every new LSI device that comes their way. Any successes in new adaptations for these devices will not go unmarked by the manufacturers and others on the professional side of the business, that is certain.

F.E.B.

Editor
F. E. BENNETT

Editorial
G. C. ARNOLD *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
M. ABBOTT

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4504

P. J. MEW
Phone: 01-634 4181

C. R. BROWN *Classified*
Phone: 01-261 5762

Make-up and Copy Dept.
Phone: 01-634 4372

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4504



A suitable transformer can be wound using 28 s.w.g. wire. The primary is 210 turns and the secondary 280. The core should be from a valve audio output transformer.

R6 prevents damage to the amplifier in use if T1 should short out, and to the 741s if very high signal levels are applied when the sensitivity is turned fully up. Its value depends on the power of the amplifier in use and is between 100 ohms and 4.7 kilohms. A value of 470 ohms is suitable for most applications.

The three filter outputs are taken via 1.2 kilohm resistors to the gates of CSRs 1 to 3.

MAINS SWITCHING

S.c.r.s are used to run the lamps on alternate half-cycles of the mains waveform. This reduces the cost and complexity of the circuit considerably, while scarcely affecting the display. The only effect is a reduction in overall brightness, which is generally welcomed at parties.

Zero-voltage switching is used instead of the more conventional "phase control" dimming: this offers several advantages. First, mains-borne interference is almost entirely eliminated, and no high voltage capacitors or bulky chokes are needed to filter it out. This reduces overall cost, more than offsetting the cost of the zero crossing detector. Second, a more rapid,

SOUND to LIGHT CONVERTER

By M. Hadley

THE Sound to Light Converter described in this article was developed to provide a simple, cheap, but effective unit for use at parties. It provides good channel separation while avoiding the most common failing of other cheap sound to light units, namely generating mains interference which produces an irritating buzz in the record player or sound system in use. As this is produced by the fast switching of large currents, the silicon controlled rectifiers (s.c.r.s) in this unit are only switched when the mains voltage is at or near zero volts in each cycle.

FILTER SECTION

The three channels are split by active filters using 741 op. amps. (IC1-3 in Fig. 1). The bass and treble filters are standard 12dB per octave Sallen and Key circuits, in low pass and high pass configurations, with breakpoints at 370Hz and 1kHz. These give very good channel separation which is vital for an attractive display when three channels are used.

The midrange channel has 6dB per octave filters with the same breakpoints. Since this channel only covers one octave or so, the filter characteristics are quite suitable.

Each filter input is taken via its own 10 kilohm logarithmic level control from the secondary of isolating transformer T1. This can consist of the output and feedback windings of a valve audio output transformer.

pulsating display is produced which most people find more pleasing than the slower effect. Finally, the dissipation in the s.c.r.s is reduced, cutting the size of the heatsinks needed.

The zero voltage switching circuit consists of TR1/2 and associated components. The mains voltage is attenuated by R1 and R2 and applied via C1 and R3 to the base of TR1. D1 removes negative half-cycles from the base, preventing reverse breakdown of the base emitter junction. The amplified pulses at the collector of TR1 hold TR2 off during positive half-cycles, except when the mains voltage is very low, holding the s.c.r. cathodes at about +9V. The gates are then reverse biased, and the s.c.r.s are held off. When TR2 is on, the s.c.r.s will turn on if the signal level at the filter output is above about 0.6V. Thus the s.c.r.s can only turn on when the mains voltage is passing through zero.

CONSTRUCTION AND POWER SUPPLIES

The prototype was built on 0.1in matrix Veroboard which carried all components except the transformers and level controls. The s.c.r.s used were 1A 400V types

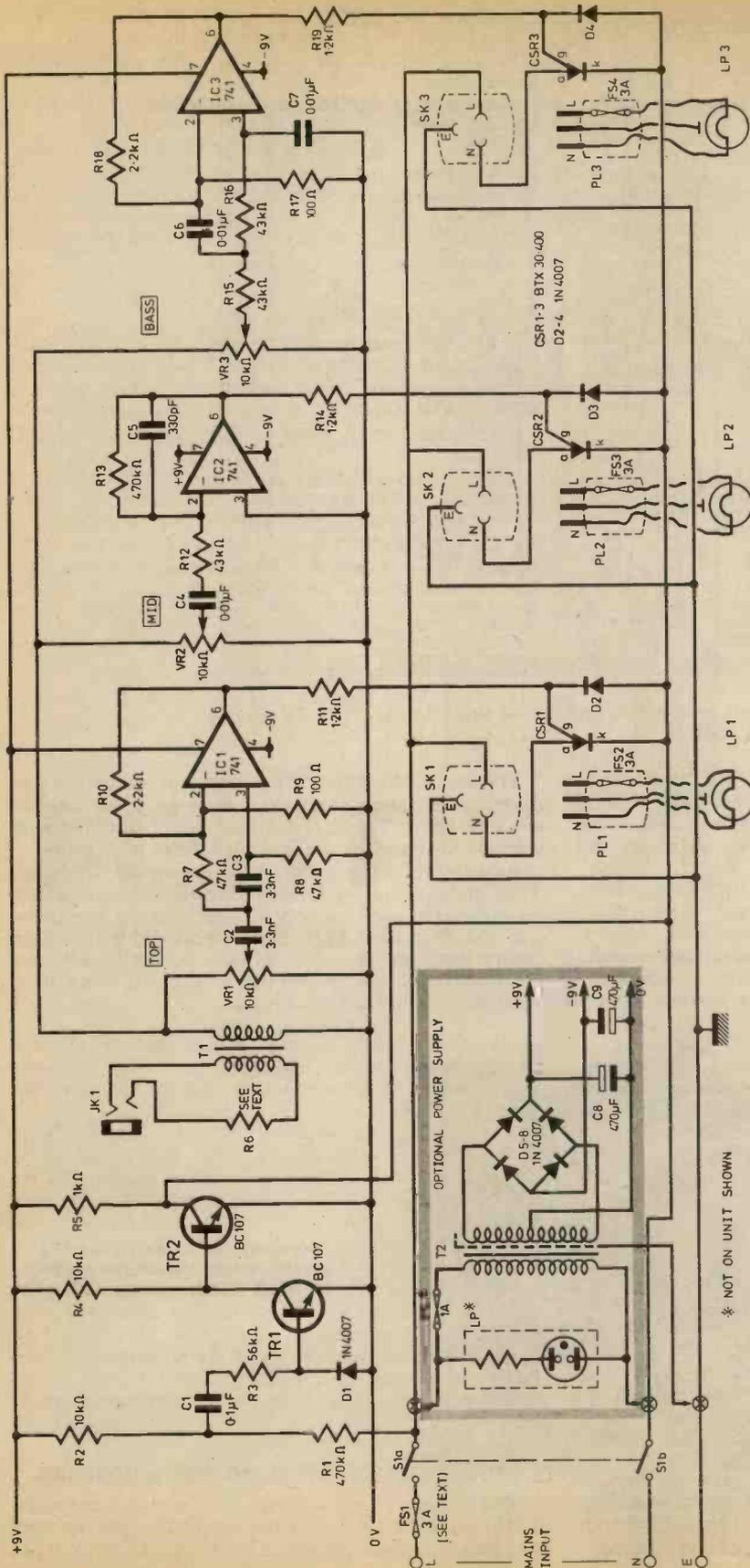


Fig. 1. Circuit of Sound to Light Converter. Each channel is suitable for lamps up to 150W

COMPONENTS . . .

Resistors

- R1 470 k Ω
- R2 10k Ω
- R3 56k Ω
- R4 10k Ω
- R5 1k Ω
- R6 See text
- R7 47k Ω
- R8 47k Ω
- R9 100 Ω
- R10 2.2k Ω
- R11 1.2k Ω
- R12 43k Ω
- R13 470k Ω
- R14 1.2k Ω
- R15, R16 which are 1W 5%
- R17 100 Ω
- R18 2.2k Ω
- R19 1.2k Ω

Potentiometers

- VR1-3 10k Ω log

Capacitors

- C1 0.1 μ F
- C2 3.3nF
- C3 3.3nF
- C4 0.01 μ F
- C5 330pF
- C6 0.01 μ F
- C7 0.01 μ F
- C8 470 μ F
- C9 470 μ F

Semiconductors

- TR1 & 2 BC107
- D1-8 1N4007
- IC1-3 741
- CSR1-3 BTX30-400V 1A or C106D 400V 3A

Miscellaneous

- T1 Valve audio output transformer (see text)
- T2 240V primary, 6-0.6V 1A transformer Type CT1 (Electrovalue)
- JK1 1/4-in jack or DIN loudspeaker socket
- FS1 3A (10A in high power version)
- FS2-4 3A
- S1 d.p.s.t. 13A mains toggle switch
- Metal case 228 x 152 x 101mm (Home Radio) control knobs, mains cable, SK1-3 13A sockets, PL1-3 plugs to suit.

* NOT ON UNIT SHOWN

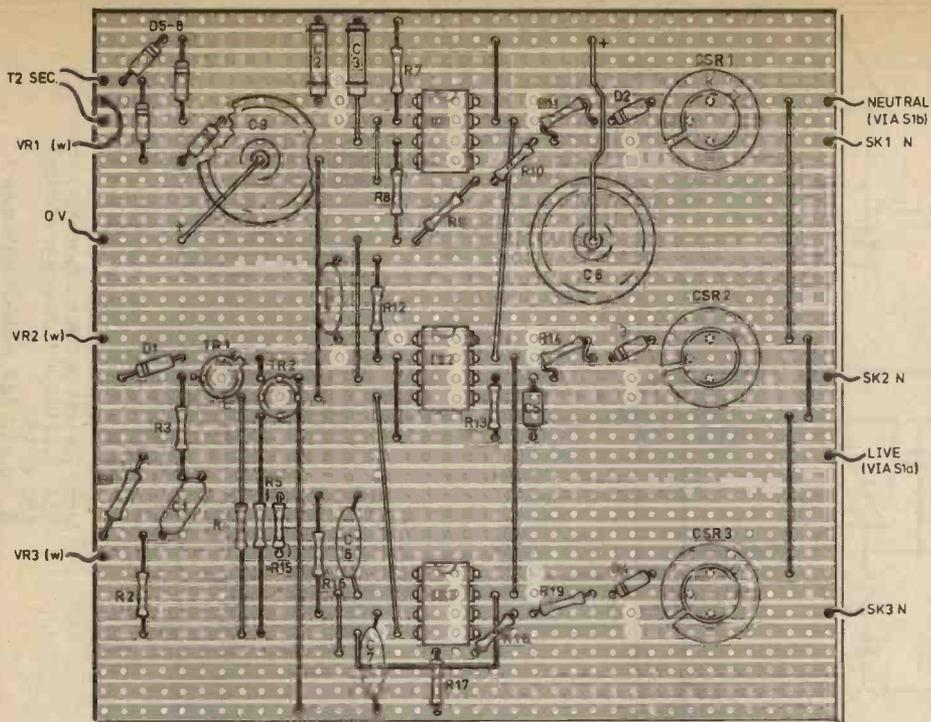


Fig. 2. Component and wiring details of main board. The 0V line is not connected to chassis


in TO5 cans which were mounted on the board and fitted with push-on "cog wheel" type heat sinks, which were found to be adequate, as they remained cool after several minutes running. A suitable Veroboard layout is shown in Fig. 2.

The unit was battery powered for simplicity and low cost, but for continuous use a power supply such as that shown in Fig. 1 is suitable.

The electronics is contained in a metal case which must be connected to mains earth. *It is, however, important that no part of the circuitry be earthed.*

The mains wiring should be done with standard p.v.c. mains cable, taking care that it does not chafe against any metal part. The level controls should be of the type with nylon shafts for the greatest safety.

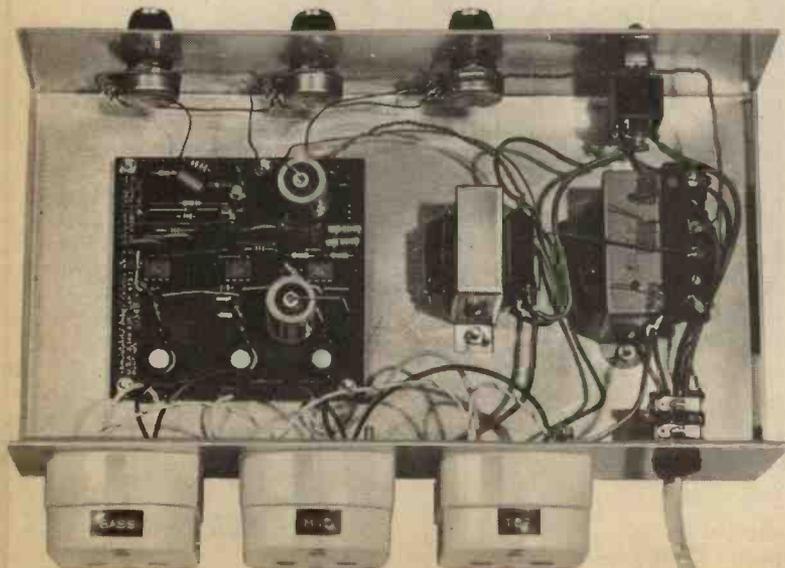A high standard of construction should be attempted when building any equipment which is to be connected directly to the mains supply, as mistakes can be expensive and dangerous. Particular care should be taken to ensure there are no solder bridges between tracks on the Veroboard, and that no part of the circuit board or heatsinks touches the metal case.



Showing the case assembly of the unit. Note the push fit heat sinks on the s.c.r.s

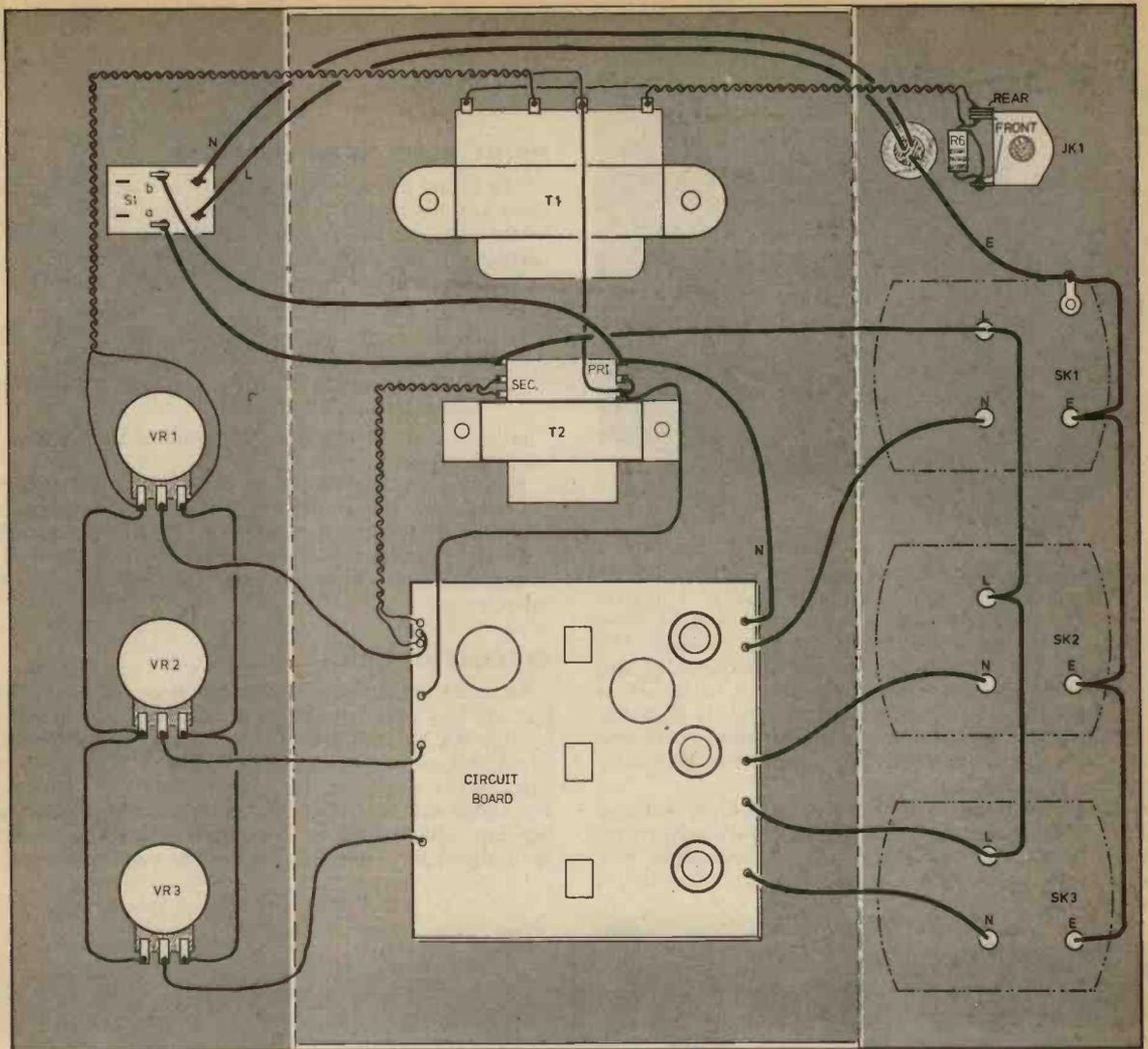


Fig. 3. Component interwiring to the board

The best form of lamp connector to use is the normal flat pin 13A socket, as this is both shuttered, for safety, and ensures that each lamp is fused. The sockets should be mounted on the rear of the unit and care taken to ensure that no "whiskers" of wire from the connecting cables touch each other or the case. These sockets are, however, expensive, and a suitable alternative is to build the lampholders into or onto the unit with the cables permanently wired in position.

The speaker input is isolated, and may be taken to a ½in jack socket, or a DIN speaker socket. These sockets must also be kept insulated from the case.

A professional finish can be given to the unit by labelling the controls with "Letraset" and finishing off with a coat of clear lacquer.

DISPLAYS


As it stands the unit is suitable for lamps of up to 150W per channel, which is about the most useful for a small private party. The circuit can be used without

other modification for 3A s.c.r.s giving a power handling of about 500W per channel which is suitable for a larger party or small disco.

In use, the unit is connected across the speaker output of the amplifier used, and adjusted to give a pleasing display with the music at the desired level. The bulbs used can be small 15-60W bulbs for a very rapid, "flashy" effect, or larger 100 or 150W coloured spot bulbs for a slower effect.

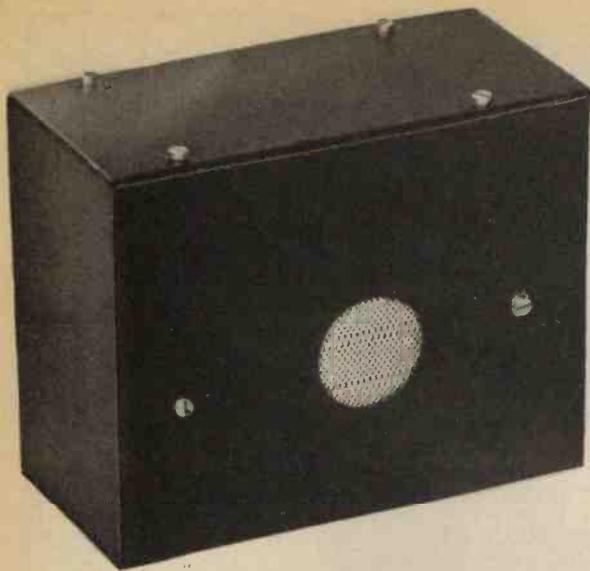As with the lamp connectors, this is an area where constructors can exercise their ingenuity to build a unit suitable for their own applications. ★





logic gates are used to ensure that the warning is sounded only when required. The circuit shown is suitable for negative-earth vehicles: amendments for positive-earth vehicles are given at the end of the article.

PRINCIPLES OF OPERATION

The circuit of this device is shown in Fig. 1. Connections are made to both the lighting and ignition feeds in the car, and the operation of the logic controls an oscillator. The oscillator is normally inhibited, and only starts working when the following sequence of events occurs:

1. Ignition and lighting supplies both on (driving with lights on);
2. Ignition supply is then switched off (driver leaves car with lights on).

The output of the oscillator is amplified and fed to a small loudspeaker.

By using this method, a warning is sounded only if the lights are left on after stopping. The warning is cancelled by turning the lights off. Nothing happens if the lights are turned on with the car already parked, so the deliberate use of parking lights will not set off the warning.

CIRCUIT DETAILS


Detailed operation of the circuit is as follows. The ignition and lighting voltages are filtered and stabilised by R1, R4, C2, D4 and R2, R3, C1, D3 respectively. The stabilised outputs are fed to IC1a. This is a NAND gate, so its output is zero only when both ignition and lights are on. IC1b and IC1c are arranged as a flip-flop, which is set by the output of IC1a and reset by a signal from the lighting supply passing through

Now that the Government has introduced regulations requiring drivers to use dipped headlights in daytime when visibility is poor, it is very easy to leave lights on accidentally when finishing a journey. The result of this can vary between embarrassment and considerable expense. A simple answer is to fit a warning light on the dashboard in parallel with the sidelights, but this is not usually satisfactory as the light will either dazzle the driver at night or be hardly noticeable during the day.

A better solution is to employ an audible warning system. This cannot, of course, be connected permanently to the car's lighting circuit. Instead, a few

Car Lights Reminder

By D. J. Saunders, M.A.

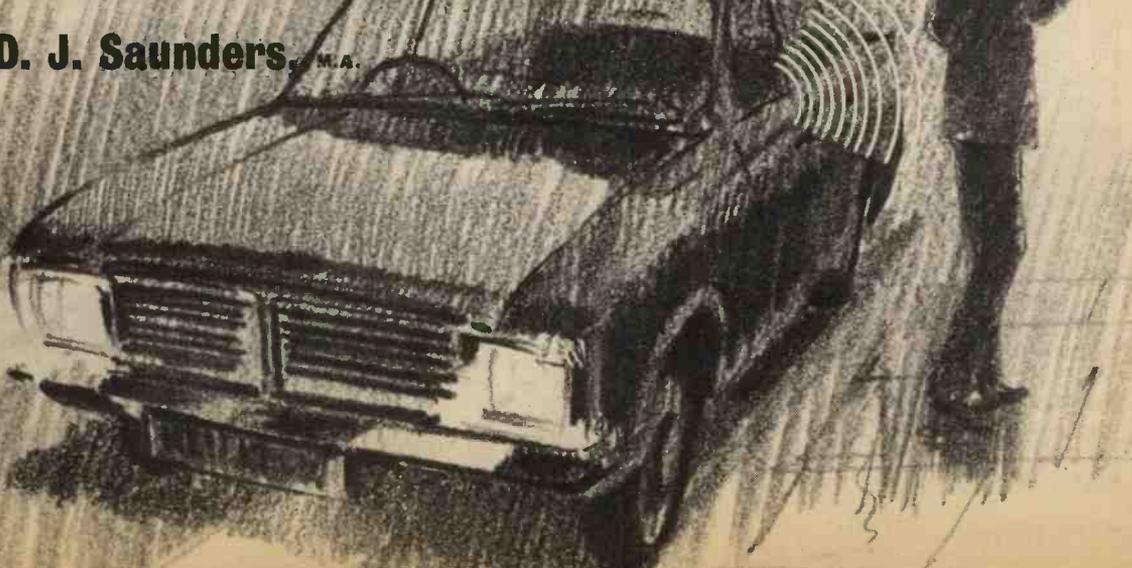

COMPONENTS . . .

Resistors

R1, R2, R7	1k Ω
R3, R4	47k Ω
R5, R6	1M Ω
All 10% $\frac{1}{4}$ W	

Capacitors

C1, C2, C4-C6	0.01 μ F polyester (5 off)
C3	4.7 μ F 15V tantalum


Semiconductors

IC1	CD4011AE
IC2	CD4001AE
TR1	BC108*
TR2	BFY51*
D1, D2	1N4001
D3, D4, D6	10V 400mW Zener
D5	1N914

Miscellaneous

Loudspeaker, 75 Ω miniature
Veroboard 0.1in pitch, 95 \times 64mm
Aluminium box, nuts, bolts, etc.

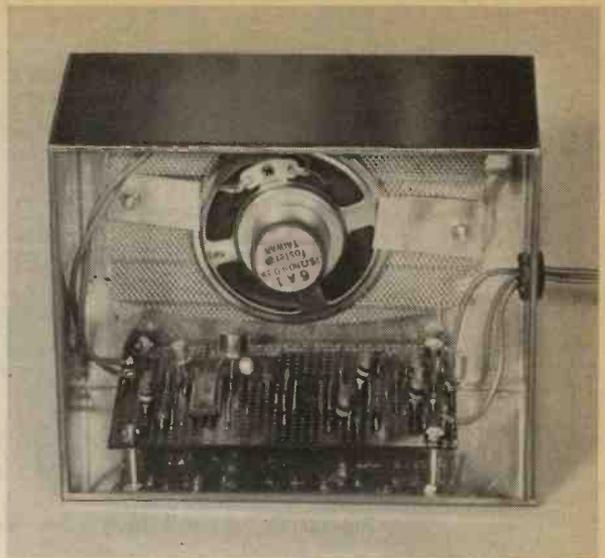*See text for types required for positive-earth version



Interior view of the prototype Car Lights Reminder

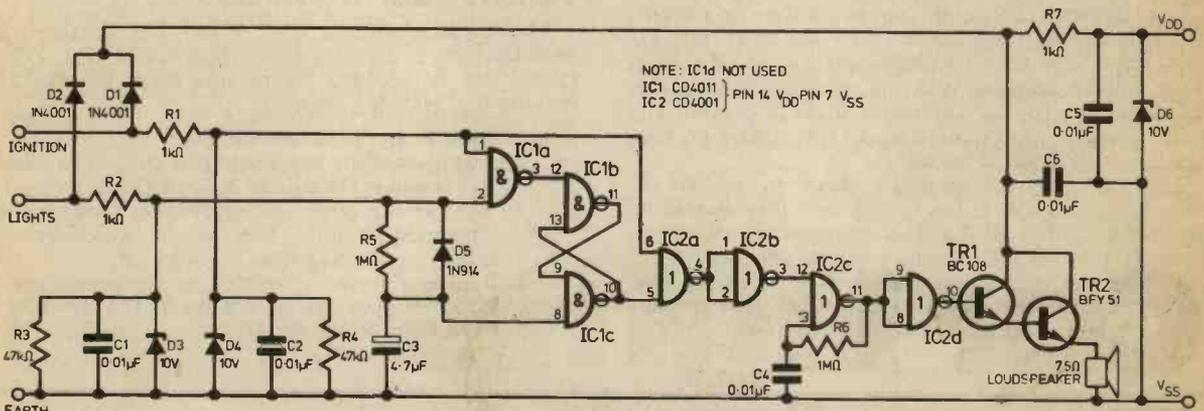


Fig. 1. Circuit diagram of the unit, negative earth version


the filter R5, D5, C3. The flip-flop "remembers" that the ignition and lights were both on together, and gives a zero output when this has occurred.

The output of the flip-flop and a signal from the ignition supply are both taken to IC2a. This is a NOR gate, so it gives a positive output only when both inputs are zero—that is, when the ignition is off and the flip-flop has remembered that both ignition and lights were previously on together.

The output of IC2a is inverted by IC2b and fed to IC2c, which is connected as a simple gated oscillator. The values shown for C4 and R6 produce a suitably unpleasant noise for the warning signal. Finally IC2d isolates the oscillator from the two transistors TR1 and TR2, which are connected as a Darlington pair for high current gain. The 75 Ω miniature loudspeaker is connected in the emitter circuit of TR2.

Power for the device is obtained from whichever of the ignition or lighting circuits is on, by means of the

two diodes D1 and D2. The supply is taken directly to the two transistors, but is stabilised before being used to power the integrated circuits.

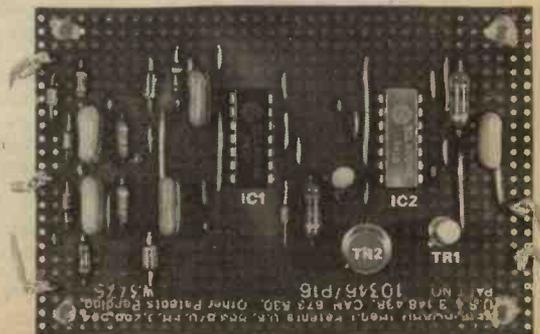

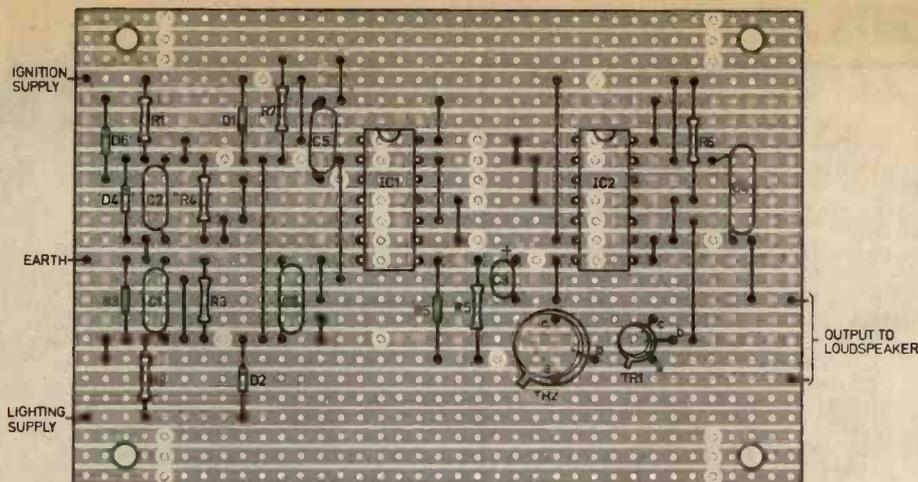


Fig. 2. Component layout on Veroboard, negative earth version

CONSTRUCTION

The unit may be built on a 95 × 64mm piece of 0.1in matrix Veroboard. The layout is not critical, and one possibility is shown in Fig. 2. A warning may be needed, however, concerning the two integrated circuits. These are CMOS types rather than the more familiar 7400 series, and they are electrically somewhat fragile. They will be supplied with the pins shorted together by aluminium foil or conductive foam to prevent any static charge from building up. They should be kept like this until required for use.

The i.c.s may be mounted either in sockets or directly on the board, but in any case they should be inserted last, after all the other components and wires. Insert IC1 before IC2. Avoid touching the pins, and if the integrated circuits are being soldered, ensure that the soldering iron is well earthed. If all these precautions are taken, there shouldn't be any trouble.

The completed board and the loudspeaker may be mounted in a small aluminium box and fixed at some convenient position inside the car.

POSITIVE-EARTH VEHICLES

The circuit shown in Figs. 1 and 2 is suitable for vehicles with a negative-earth electrical system. The circuit can be adapted for positive-earth vehicles by making the following changes:

1. Reverse all the diodes and C3.
2. Interchange the two integrated circuits (so that IC1 is now CD4001 and IC2 is CD4011).
3. Reverse the power supply connections to the integrated circuits. This can be accomplished simply by rotating them through 180°.
4. Replace the two transistors by *pnp* equivalents. Possible types are BC478 or BC158 for TR1, BC461 or 2N3134 for TR2. ★

NEWS BRIEFS

Bionic Voice

WHEN Mr Charles Lacey of Berinsfield, Oxford, began to relate his invention to a member of PE, nothing at first seemed very remarkable, until it was revealed that Mr Lacey has no larynx, and was using his invention there and then—an electronic voice!

For those, who after surgery, are told they can never speak again, here lies hope. For with Mr Lacey's bionic voice, audible oscillations are introduced orally by a circuit small enough to fit to the upper dental plate, whereupon the natural speaking action of the mouth modulates the sound into recognisable speech, even retaining most of the former accent.

Isolation inflicted on the voiceless has been tackled before, with gadgets producing a weak "Dalek" type speech, which on demonstration seem comparatively primitive. But with Mr Lacey's invention, an acoustically controlled feedback system produces floating frequency and amplitude, giving rise to artificial intonation and

automatic suppression when the mouth closes. However, with this and other of his aids for the handicapped, there are still obstacles to be overcome. The pioneering spirit of this self-taught electronics designer has so far been well supported and encouraged.

"Ideally", says Mr Lacey, "I should like to set up a viable but non-profit making workshop, producing aids to order. But for this I would need a sponsor." It would almost certainly be the first of its kind in the country!

His latest target is to raise £60 for a VDU in order to provide one of his Portable Keyboard Writers for a Speech Therapy patient at the Charing Cross Hospital.

Let us hope that Mr Lacey can find the backing, to reach those whom his inventions would undoubtedly benefit.


New Secretary for IERE

MR GRAHAM D. Clifford, C.M.G., C.Eng., F.I.E.R.E., F.C.I.S., retired as the secretary of the Institution of Electronic and Radio Engineers on March 31st, 1977. The Council has appointed Air Vice-Marshal Sinclair M. Davidson, C.B.E., C.Eng., F.I.E.R.E., F.R.Ae.S., RAF, as secretary. Mr Clifford will continue as the Director of the Institution with special responsibilities for a further year.


Make
NEXT MONTH
EVENT *feel with our*

DIGITAL STOPWATCH

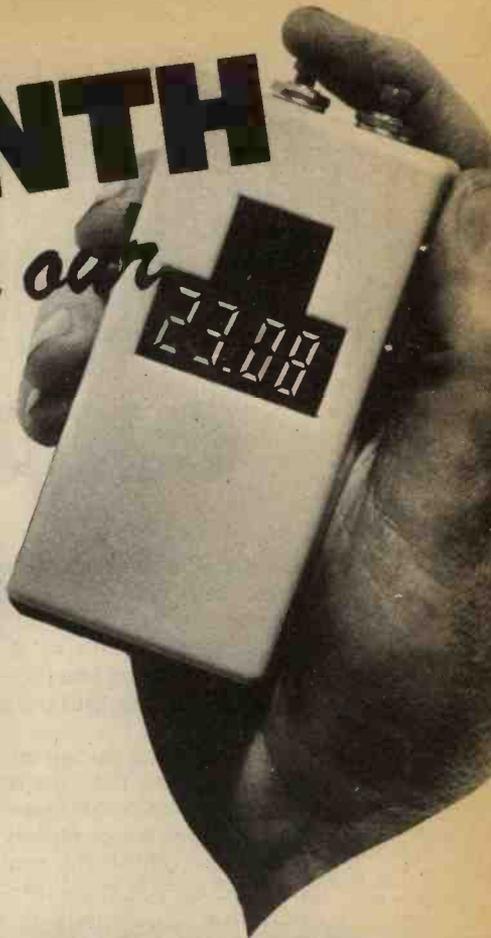This high accuracy digital stopwatch is based on the Intersil ICM 7205 chip, giving normal start-stop-reset operation, plus Taylor mode lap timing and cumulative timing. Clocking up to one hour is possible on the large six digit display. Other features include automatic reset at switch-on and a rechargeable power source with advanced warning (about 15 minutes) of low battery condition.



Also...

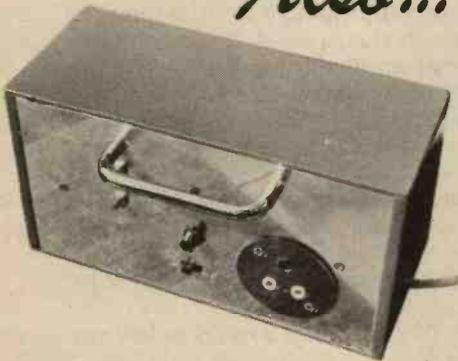

EARTH LEAKAGE CIRCUIT BREAKER

The effects of electric shocks can kill, either directly or indirectly. In many cases these are caused by faulty insulation or earthing so that dangerous leakage currents pass with skin contact. The only safe way to operate mains equipment is to monitor these fault currents and this is what this unit does simply and reliably.

TWIN TRACE DOUBLER

Four trace display for a double beam 'scope

PRACTICAL
ELECTRONICS

OUR JULY ISSUE WILL BE ON SALE FRIDAY, JUNE 10, 1977

MICROPROCESSORS

explained

By R.W. Coles



Up to now in this series we have concentrated our attention on the microprocessor chip itself, learning how it works, and what it can be instructed to do. There can be no doubt that the MPU chip is the Prima Donna of any system, but it's not much use at all on its own, and has to be supported by a variety of peripheral chips like the all important program and data memories, and of course the input and output ports which provide communication channels to the outside world.

Using the analogy of Part 2, a microprocessor system which consists of nothing more than an MPU chip is like a building site foreman complete with calculator and notebook, but without any building plans or any workforce, and consequently completely useless!

It is becoming the trend to incorporate as many of the necessary peripheral circuits as possible into the MPU package, but this is not a trend which can continue indefinitely if microprocessors are to retain their general-purpose nature, since it would eventually reduce user options regarding optimum memory size and number of input/output lines. However, in the special case of microprocessors used in large quantities for consumer applications, like the Texas TMS1000, the one chip MPU based system is already a reality. *Our* main concern is the use of the microprocessor as a general purpose problem solving tool, and so our interest in the one chip "Shoe-horn" jobs is necessarily limited.

An ideal system as far as we are concerned would use a capable MPU chip with external provision for data and program storage which can be expanded as necessary. Communication requirements vary from application to application, and so we would like to either have versatile parallel input-output devices available, or be able to put these together as required, from general purpose logic such as the TTL or CMOS families.

This month we shall be looking at the range of memories available for our use, and how these devices are used in practice.

To the uninitiated, the range of memory devices available must seem a little confusing, or perhaps to those with a well developed sense of the ridiculous, quite hilarious! Without great effort one can recall RAMS, ROMS, PROMS, EAROMS and EPROMS, but there *are* more, and you can quite enjoy yourself building up a list of your own. When you have gone as far as you can, try listing the semiconductor technologies involved as well; you can put down NMOS, PMOS, CMOS, FAMOS, AIM, and Fusable-Link to get started, but you'll find plenty more.

If this memory game is not your cup of tea, and you want to ignore everything which does not get you further along the road to switching on your very own microprocessor system, then don't despair because what you *need* to know is really quite simple.

READ/WRITE MEMORY

Easy storage and retrieval of data in a microprocessor system is of vital importance, and the read and write operations must take place at high speed if the speed of the microprocessor chip is to be utilised properly.

In the recent past all computer stores which were designed for rapid access used a matrix of ferrite rings, or cores, which could be magnetised in one of two directions to indicate whether a logic 1 or logic 0 was stored. These stores could be accessed in micro-seconds and had the advantage of random access to the data stored, and non-volatility when power was removed. Their disadvantages included high cost, large size, and the fact that data was destroyed when read out, so that a write-after-read cycle was necessary.

Stores of this type are called "core-stores", and this title is still sometimes applied to any memory system which provides a random access read and write storage facility, even that used in microprocessor systems.

Recently the true core stores have been replaced in computer designs by semiconductor memory chips called RAMs for Random Access Memory, and it was the ready availability of this high speed, low cost memory technology which helped to make the microprocessor a practical proposition. Semiconductor RAMs work on a totally different principle to the magnetic core stores because they use a matrix of transistor storage elements fabricated on an LSI chip using the same range of bipolar or MOS technologies as other semiconductor logic. This makes them easy to use, easy to drive, and very compact.

All microprocessor systems use read/write semiconductor RAM memory of one sort or another for data storage during calculations and stack operations. In some cases, it is used for program storage as well.

Semiconductor RAMs have the disadvantage that they are volatile, which means that their contents are destroyed when power is removed even if it only disappears briefly. This fact makes them unattractive for storing programs for dedicated systems, but in development systems, where programs are loaded and modified on a casual basis, they are used extensively for both data and program storage.

STATIC OR DYNAMIC?

Semiconductor RAMs can either be "static" or "dynamic" in operation and it is important to appreciate the trade-offs involved in choosing one or the other. Static RAMs use storage elements based on a conventional bistable flip-flop which can be set or reset by write operations, and which of course will *stay* set or reset until a new write operation takes place.

Information stored in a static RAM will remain inviolate providing power is applied, and the stored data does not have to be read or overwritten at any minimum rate to retain its integrity. Dynamic RAMs, on the other hand, do not use bistable flip-flops to store the data but rely on the storage of charge on the gate capacitor of an MOS transistor for their operation. The stored charge leaks away fairly quickly and this makes it necessary for the data to be "refreshed" at a regular rate to retain data integrity. This may sound a bit of a burden for the microprocessor system to bear, especially when one recalls that data must be refreshed about every 2 *milliseconds*, but you have to remember that many microprocessors can carry out several hundred program steps in that time and the use of dynamic RAMs does bring some useful advantages.

Because the storage element in a dynamic RAM consists of little more than a single MOSFET, larger numbers of these elements can be squeezed onto a given area of silicon, and power consumption is reduced into the bargain. Refreshing of the memory can be controlled by the microprocessor itself, or it can be carried out by external hardware which requires a few extra components but which makes the operation transparent to the programmer.

As far as amateur systems are concerned, for memory sizes up to 4K (4,096) words it is definitely better to use static RAMs, but beyond this size the cost-per-bit advantages of the dynamic types become increasingly attractive. At present, manufacturers are working on some giant dynamic RAMs with no less than 16K (16,384) bits in a 16-pin package!

RAM ORGANISATION

The typical RAM chip (static or dynamic) consists of a large array of storage elements, each of which will store a single binary bit. The chip can be "bit" or "word" organised, so that arrays of say 1,024 elements can be arranged as 1,024 separately addressable bits, or as 256 separately addressable words each of four bits.

The addressing of a particular bit or word inside the chip is achieved by the selection of a row and column line which intersect at the desired location(s) in the matrix. Since a 1K x 1 bit chip might have 32 rows and 32 columns in its matrix, some decoding of the

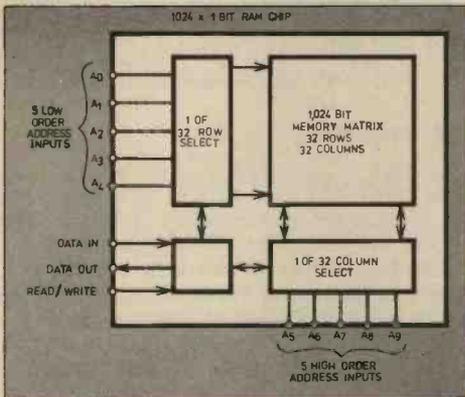


Fig. 4.1. Basic RAM organisation

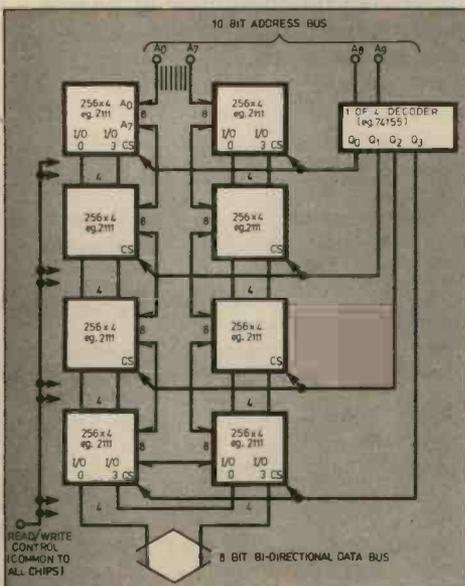


Fig. 4.2. Using the "Chip Select" inputs to build large memory arrays. This is a 1024 x 8 bit memory with Intel 2111 256 x 4 static RAMS

necessary ten-bit binary address code is required to produce the row and column select signals, and this is supplied "on-chip" in all currently manufactured RAM devices. See Fig. 4.1. Addressing a location causes the current state of its bit(s) to become available on the "data out" line(s). Overwriting the stored data can be achieved by setting up new data on the "data-in" lines and taking the "read/write" control line to the write state momentarily.

Memory arrays of any size can be constructed by using more than one chip. An eight-bit MPU requires an eight-bit word organised store, and this could be built by using eight $1K \times 1$ bit chips in parallel (1K word store) or by using two 256×4 bit chips in parallel (256 word store). If a larger store is required you can either use chips with a greater capacity (up to $4K \times 1$ bit at present) or you can take advantage of the "chip select" inputs, which can be found on most RAM chips, to build stores of unlimited size. The "chip select" input must be present before any read or write operation can take place, and by using an external address decoder to drive these inputs it is possible to extend the address range to any number of bits. See Fig. 4-2.

RAM TIPS

Random access memories of a certain size can be obtained with various "access times" of between about 50 nanoseconds and 1 microsecond. When choosing a RAM for a particular MPU system make sure you choose one fast enough, but *don't* overdo it, speed is expensive in both cash terms and in power dissipation!

CMOS RAMS are now available in sizes up to 1K bit. These devices are quite fast and have the overwhelming attraction of extremely low current drain during standby. Using CMOS static RAMS you can build non-volatile memories which will retain data for months with the aid of a small battery supply which takes over when the main supply is removed, an extremely useful facility in some situations. The only problem is that CMOS devices cost about four times as much as NMOS devices of the same size.

READ ONLY MEMORY

Read only memory is much cheaper than read/write memory on a cost per bit basis, and has the overwhelming advantage of complete non-volatility in normal usage. Information can be stored in a ROM chip either during manufacture, or, in the special case of PROM devices, at some time after manufacture with the aid of special programming equipment.

Read only memory is ideal for the storage of programs in a microprocessor system, and for those systems performing *dedicated* tasks it is by far the dominant form of memory used. A dedicated system might have many thousands of words of ROM store, and probably less than 1K word of RAM used as a "Scratch-pad" or "Jotter". Even MPU development systems and general purpose MPU based computers which use a lot of RAM memory need fixed ROM programs to enable them to do basic "house-keeping" jobs as soon as power is applied. Consider the National Semiconductor SC/MP Introkit for example: it uses a 512 word ROM store for the KITBUG program which enables the user to load *his* program into the 256 word RAM and subsequently execute and debug it.

INSIDE THE ROM

To the microprocessor, a ROM memory looks pretty much the same as a RAM memory. The MPU sends the ROM an address and gets back the data stored at that address via the data bus. The ROM usually shares the same address space as system RAM and so, if a programmer gets his knickers in a twist, the MPU *can* try to write into ROM locations by mistake. Since the ROM does not have inputs connected to the data bus and, of course, does not have a read/write control input, this would be a rather fruitless exercise which would fortunately not harm the ROM data already resident!

Internally, the ROM has an address decoder and a storage matrix rather like that of a RAM but in this case the matrix does not need bistables or dynamic storage elements and can make do with a simple "diode matrix" type of element where a connection is either present for a logic 1 or logic 0 stored.

Glossary of Terms

AIM—Avalanche Induced Migration. A PROM technology which relies on the *making* of links during the programming process, rather than the *blowing* of links which is perhaps a more common procedure.

EAROM—Electrically Alterable Read Only Memory. This is a PROM technology which uses MNOS (Metal Nitride Oxide Silicon) to form a memory which can be electrically erased and rewritten. This technology is in competition with ultra violet erasable EPROM devices, but is more expensive and apparently less popular.

EPROM—Erasable and re-Programmable Read Only Memory. A general name which is usually used to

refer specifically to ultra violet light erasable PROMS, like the popular 1702A which uses the FAMOS technology.

FAMOS—Floating gate Avalanche Metal Oxide Semiconductor. The ultra violet erasable PROM technology which is programmed by means of charge stored on the isolated poly silicon gate electrode of an MOS transistor via an avalanching junction. Erasure is achieved by neutralizing the charge with one of an opposite polarity produced by irradiation with ultra violet light.

PROM PROGRAMMER—A hardware facility for storing data or programs into PROM memory. The programming operation can involve "blowing" fuses, "making" links, or avalanching junctions with voltage or current pulses—the characteristics of which are specific to a particular device or family. Universal programmers are available which require the connection of a "personality" module to set up the system for a particular device type.

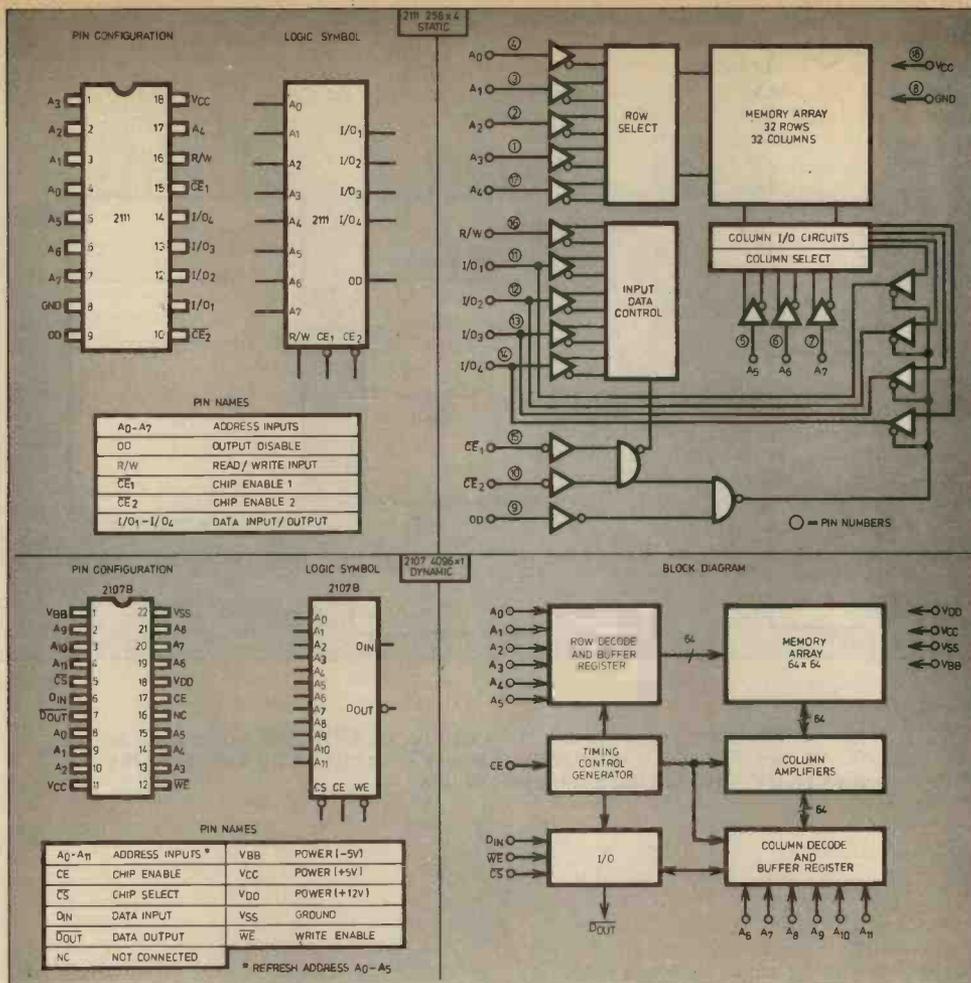


Fig. 4.3 Two useful NMOS RAMs suitable for MPU Systems. The 2111 is a 256 × 4 static device with common data in/out data lines controlled by the O.D. (Output Disable) Pin. The 2107 is a 4096 × 1 dynamic device with four times the capacity of the 2111

ROM TYPES

There are probably more variations on the read only memory theme than there are on the read/write memory theme, and this makes a basically simple device more difficult to get to grips with than should really be the case. For the purposes of this series we have chosen to look at ROMs from a less academic and more practical point of view, i.e. "What ROM types do we need to be familiar with to get our MPU systems operational?" To answer this question we need to consider just three types, the mask programmed ROM, the programmable ROM, or PROM, and the ERASEABLE AND RE-PROGRAMMABLE ROM or EPROM.

MASKED ROM

Mask programmed ROMs have their contents fixed by the final metallisation layer which is laid down on the semiconductor chip during the manufacturing process. This process yields the cheapest program store

available, but *only* if several thousand ROMs with the *same* contents are ordered together so that the high mask charge can be recovered. This may not sound of much use to *us*, but remember that development systems and prototyping cards often come with a set of system software, and masked ROM is sometimes used to house it.

PROM

Programmable ROMs have the great advantage that people like us can use them to store our programs *even* if our programs are only one-off. To program a PROM a PROGRAMMER is required, and you can pay over £1,000 for a really good one. Fortunately, there are a number of circuits around for simple programming that require little more than a few TTL monostables, some voltage regulator chips, and a row or two of toggle switches. Programming a PROM using a simple manual programmer of this sort is certainly a bit tedious for the larger PROMs, because data has to be entered in binary

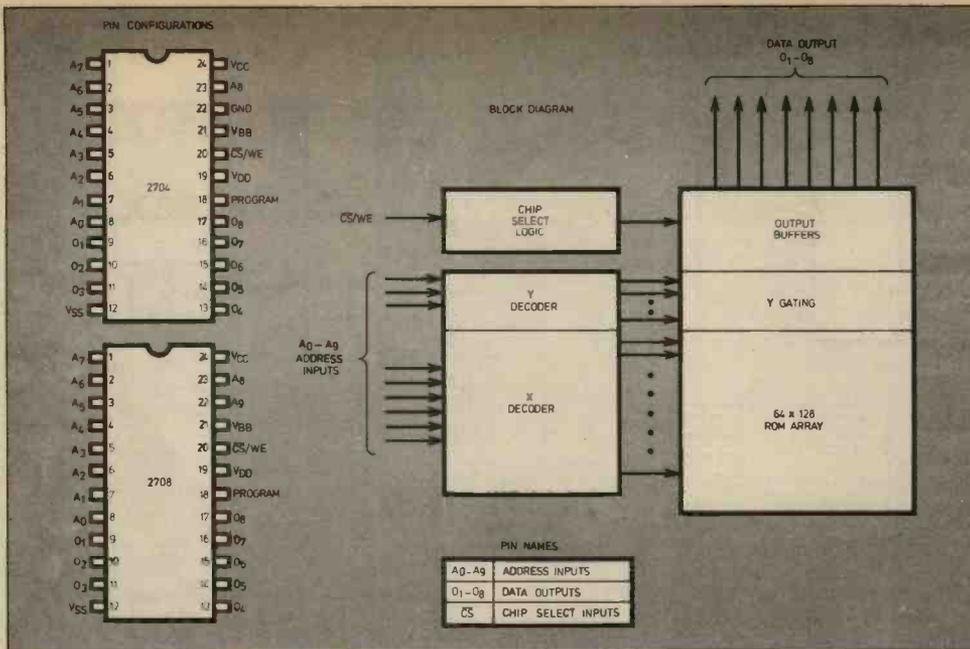


Fig. 4.4 The 2704 and 2708 are state of the art EPROMS organised as 512 × 8 and 1024 × 8 respectively. Erasure is achieved by exposing the chips to UV light via their transparent lids

form, but the tedium can be eased to some extent by thinking about all the money you are saving!

The PROM principle is implemented in a variety of different ways by different manufacturers, and each of them produce devices which require different programming voltages and currents so that it is not possible to build a low cost universal programmer. This means that you have to choose a PROM family and stick with it, even though, for our purposes, which family you choose is immaterial.

Most PROMS are fusible link devices which consist of arrays of nichrome or poly-crystalline silicon fuses which are "blown" during the programming operation. An alternative technique called AIM (Avalanche Induced Migration) relies on *making* links rather than breaking them.

Whatever type of PROM you use, there is one major drawback, and that of course is that *you have to get it right first time* unless you don't mind throwing away expensive PROMS and starting again!

EPROM

Everyone makes mistakes when writing programs, and during development work there is a need for a PROM which can be erased and reprogrammed over and over again. If that sounds like a RAM description to you, remember that *this* device must behave in circuit just like a mask programmed ROM except that at the end of the day it can be unplugged, erased, and reprogrammed. A range of devices which provide this useful

facility are available, and of all the ROM family, it is these which are of must use to the small micro-processor user.

The EPROMS we refer to are programmed with the aid of a PROGRAMMER which causes charge from an avalanching junction to be stored on the electrically isolated gate of a MOSFET device. Thanks to the high order of insulation provided for the floating gate electrode, the stored charge would take hundreds of years to leak away naturally but erasure is easily achieved by neutralising the stored charge with one of an opposite sign produced by irradiation with ultra-violet light. The chip is mounted in a standard 24-pin d.i.l. package with a glass window to permit erasure to be achieved. The ultra-violet light used has to be of short wavelength (2,537 Angstroms) which can be harmful to us humans, although simple and safe erasure boxes are easy to build. The EPROM chips are insensitive to daylight and any other type of light to which they might naturally be exposed during normal use, but erasure takes only about 15 minutes when light of the correct wavelength and intensity is used.

These devices are a bit more expensive than standard PROMS but they are very cost effective for most applications because of their reusability.

Three sizes are available, the 1702A 256 × 8 which was the first practical version on the market, the 2704 512 × 8 and the 2708 1K × 8 which are more recent and use an improved technology. See Fig. 4.4.

NEXT MONTH: Input/Output devices and Interrupts.

Unique full-function 8-digit wrist calculator... available only as a kit.

A wrist calculator is the ultimate in common-sense portable calculating power. Even a pocket calculator goes where your pocket goes – take your jacket off, and you're lost!


But a wrist-calculator is only worth having if it offers a genuinely comprehensive range of functions, with a full-size 8-digit display.

This one does. What's more, because it *is* a kit, supplied *direct* from the manufacturer, it costs only a very reasonable £9.95 (plus 8% VAT, P&P). And for that, you get not only a high-calibre calculator, but the fascination of building it yourself.

How to make 10 keys do the work of 27

The Sinclair Instrument wrist calculator offers the full range of arithmetic functions. It uses normal algebraic logic ('enter it as you write it'). But in addition, it offers a % key; plus the convenience functions \sqrt{x} , $1/x$, x^2 ; plus a full 5-function memory.

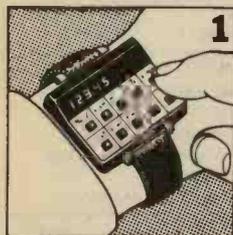All this, from just 10 keys! The secret? An ingenious, simple three-position switch. It works like this.




1. The switch in its normal, central position. With the switch centred, numbers – which make up the vast majority of key-strokes – are tapped in the normal way



2. Hold the switch to the left to use the functions to the left above the keys...

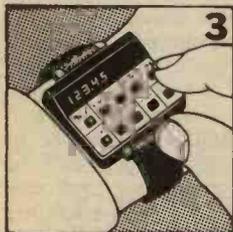3. and hold it to the right to use the functions to the right above the keys.



The display uses 8 full-size red LED digits, and the calculator runs on readily-available hearing-aid batteries to give weeks of normal use.

Dimensions:
 $1\frac{1}{8}$ " (46 mm) wide,
 $1\frac{1}{16}$ " (37 mm) deep.
Weight:
less than 1oz (28 g).

KIT ONLY
£9.95
PLUS VAT,
P&P

Sinclair Instrument Ltd,
6 Kings Parade, Cambridge,
Cams., CB2 1SN.
Tel: Cambridge (0223) 311488.

Assembling the Sinclair Instrument wrist calculator

The wrist calculator kit comes to you complete and ready for assembly. All you need is a reasonable degree of skill with a fine-point soldering iron.

It takes about three hours to assemble. If anything goes wrong, Sinclair Instrument will replace any damaged components *free*: we want you to enjoy assembling the kit, and to end up with a valuable and useful calculator.

Contents
Case and display window.
Strap.
Printed circuit board.
Switches.
Special direct-drive chip (no interface chip needed).
Display.
Batteries.

Everything is packaged in a neat plastic box, and is accompanied by full instructions.

The only thing you need is a fine-point soldering iron.

All components are fully guaranteed, and any which are damaged during assembly will be replaced free.

The wrist-calculator kit is available **only direct** from Sinclair Instrument. Take advantage of this 10-day money-back undertaking.

Send the coupon today.

To: Sinclair Instrument Ltd,
6 Kings Parade, Cambridge, Cams., CB2 1SN.

* Please send me... (qty) Sinclair Instrument wrist-calculator kits at £9.95 plus 80p VAT plus 25p P&P (Total £11).

* I enclose cheque/PO/money order for £

* Complete as applicable.

Name _____

Address _____

(Please print)
I understand that you will refund my money in full if I return the kit undamaged within 10 days of receipt.

PE/6

LYNX ELECTRONICS (LONDON) LTD

92 Broad Street, Chesham, Bucks. Tel. (02405) 75154

P. & P. 30p—Overseas 90p—Matching 20p per pair.
VAT 8% except * which are 12%. Prices correct at 31 March 1977.

RETURN
POST
SERVICE
ACCESS
WELCOME

Price list 20p

THYRISTORS

PVV	1A	3A	3A	4A	6A	8A	10A	15A	18A
(TO5)	(STUD)	(C106)	(TO220)	(TO220)	(TO220)	(TO220)	(TO220)	(TO49)	(TO220)
200	0-35	0-50	0-45	0-40	0-50	0-60	0-80	1-10	1-17
400	0-40	0-60	0-50	0-45	0-60	0-80	0-85	1-00	—
600	0-45	0-65	0-70	—	1-00	1-10	1-25	1-60	—

BT106 £1-00, BT107 £1-00, BT108 £1-00, BT109 £1-00, BT116 £1-00, 2N3525 £2-50

CLOCK CHIPS

MM5314	3-25	DISPLAYS	704	0-98
MM5316	3-85	707	1-95	
AA5-Y-1224A	3-25	704	0-98	
AA5-Y-4007D	9-95	727	1-95	
		728	1-95	
		747	1-80	
		750	1-80	

I.C. SOCKETS

8 PIN	0-13	L.E.D.	718	1-50
14 PIN	0-14	2 RED	0-13	
16 PIN	0-15	2 GREEN	0-20	
24 PIN	0-45	2 CLEAR	0-18	
40 PIN	0-80	TIL209	7918	1-50

REGULATORS

723	0-45	LM309K	0-95
7605	1-50	LM340-5	1-35
7812	1-50	LM340-12	1-35
7815	1-50	LM340-15	1-35
		LM340-18	1-35

TRIACS—Plastic TO-220 Package Isolated Tab

	4A	6-5A	6-5A	10A	15A
	(a) (b)				
100V	0-80	0-70	0-70	0-83	0-83
200V	0-84	0-64	0-75	0-87	0-87
400V	0-77	0-70	0-80	0-87	0-87
600V	0-80	0-80	1-81	1-10	1-10

N.B. Column (a) without internal trigger; (b) with internal trigger.

TTL 7400 SERIES

7400	0-16	7480	0-55
7401	0-16	7482	0-75
7402	0-16	7486	0-32
7403	0-16	7489	2-02
7404	0-18	7490AN	0-49
7405	0-18	7491AN	0-65
7408	0-18	7492	0-57
7409	0-18	7493	0-45
7410	0-16	7494	0-85
7412	0-25	7495	0-67
7413	0-40	7496	0-82
7414	0-72	74100	1-07
7417	0-43	74107	0-35
7420	0-16	74121	0-34
7425	0-30	74122	0-47
7427	0-30	74123	0-65
7430	0-16	74141	0-78
7432	0-28	74145	0-68
7437	0-30	74154	1-30
7441AN	0-76	74164	0-93
7442	0-65	74165	0-93
7445	0-90	74174	1-40
7447AN	0-81	74175	0-94
7448	0-81	74180	1-06
7470	0-32	74181	2-70
7472	0-26	74191	1-33
7473	0-30	74192	1-20
7474	0-42	74193	1-35
7475	0-47	74194	1-20
7476	0-36	74196	1-64

LINEAR I.C.s

301A	0-40*
307	0-55*
380	0-90*
381	1-60*
3900	0-70*
709	0-27
741	0-28
748	0-35
NE555	0-45
NE565	2-00*
NE566	1-50*
NE567	2-00*
CA3045	0-85*
CA3046	0-80*
CA3130	0-70
MC1304P	1-60*
MC1307P	0-85*
MC1310P	1-18*
MC1351P	0-75*
MC1352P	0-75*
MC1353P	0-75
MC1458P	0-77
MC1496L	0-82*
SAS580	2-25
SAS570	2-25
TAA300	1-61
TAA310A	1-38
TAA550	0-45*
TAA611B12	1-25*
TAA861	0-85
TBA530	1-85*
TBA530Q	1-90*
TBA560	2-20*
TBA570	0-98
TCA270SQ	1-95*



MEMORIES

2102A-6	3-60
2112A-4	4-75
6508	7-95
2102	2-50
2107	10-00
2112	4-50
2513	6-50
2602	2-50

SPECIAL OFFER SECTION


SG309K 1A TO 3 V	95p
NPN TO-3 POWER TRANSISTORS	
Fully tested but unmarked. Similar to 2N3055 except:	
BVCEO = 50+	
HFE (gain) = 20+ at 3A, VCE SAT < 1-3V at 3A	
5 pcs £1-00	25 pcs £4-00
50 pcs £7-50	100 pcs £13-00
TIL209 RED LED	18p
ITT BRANDED TRANSISTORS	
Medium voltage high gain type BSY65 similar to BC107B/9	
25 pcs £1-20	100 pcs £3-50
TO-3 HARDWARE. Mica, washers, solder tag, nuts, bolts, 50 sets for 65p.	
OC71	£1-15
RECTIFIERS DO-4 PACKAGE	
10A 50V 0-80 Please specify	
10A 100V 0-90 Polarity	
10A 200V 0-90 Stud Cathode or	
10A 400V 1-20 Stud Anode	
Ideal for Power Supplies, Inverters etc.	

DIODES

BA145	0-14*	BZX81 SERIES	0-28
BA148	0-13*	BZX85 SERIES	0-11
BA155	0-13	OAS	0-50*
BA156	0-12	OA10	0-40
BA157	0-22	OA85	0-12
BA158	0-22	OA90	0-08
BA159	0-25	OA91	0-08
BY206	0-15	OA200	0-09
BY207	0-20*	IN914	0-04*
BYX26-300	0-12	IN4001	0-04*
BYX26-600	0-15	IN4002	0-05*
BYX26-1200	0-18	IN4003	0-06*
BYX30-100	0-21	IN4004	0-07*
BYX30-500	0-50	IN4005	0-08*
BYX38-600	0-55	IN4006	0-09*
BYX38-900	0-60	IN4007	0-10*
BYX38-1200	0-65	IN4148	0-04*

TRANSISTORS

AC126	0-15	BC117	0-18*	BC300	0-34	BDY20	0-80	BFY40	0-50	OC71	0-35	2N2905	0-18
AC127	0-14	BC119	0-25	BC301	0-32	BDY38	0-40	BFY41	0-60	OC72	0-22	2N2905A	0-22
AC128	0-14	BC125	0-18*	BC302	0-40	BDY60	1-10	BFY50	0-20	OC84	0-40	2N2906	0-18
AC128B	0-25	BC126	0-20*	BC303	0-40	BDY61	1-85	BFY51	0-18	OC139	1-30	2N2925	0-14*
AC141	0-22	BC140	0-32	BCY30	0-55	BDY62	1-15	BFY52	0-10	OC140	1-30	2N2926	0-09*
AC141K	0-34	BC141	0-28	BCY31	0-55	BDY65	2-14	BFY53	0-25	OC170	0-23	2N2928P	0-18*
AC142	0-18	BC142	0-23	BCY32	0-60	BF121	0-50	BFY64	0-35	TP29A	0-44*	2N2929P	0-09*
AC142K	0-32	BC143	0-23	BCY33	0-55	BF123	0-50	BFY90	0-50	TP30A	0-52*	2N2929G	0-10*
AC176	0-16	BC144	0-30	BCY34	0-55	BF179	0-30	BSK19	0-16	TP31A	0-54	2N3053	0-20
AC176K	0-32	BC147	0-09*	BCY38	0-50	BF180	0-30	BSK20	0-18	TP32A	0-64	2N3055	0-50
AC187	0-18	BC148	0-09*	BCY39	0-55	BF181	0-30	BSK21	0-20	TP41A	0-68	2N3137	1-10
AC187K	0-30	BC149	0-09*	BCY40	0-75	BF182	0-30	BSY52	0-28	TP42A	0-72	2N3440	0-56
AC188	0-18	BC152	0-25*	BCY42	0-30	BF183	0-30	BSY53	0-38	2N404	0-40	2N3442	1-20
AC188K	0-32	BC153	0-18*	BCY54	0-60	BF184	0-20	BSY54	0-33	2N696	0-20	2N3570	3-60
AD149	0-45	BC157	0-09*	BCY70	0-12	BF185	0-20	BSY55	0-74	2N897	0-20	2N3702	0-18*
AD161	0-35	BC158	0-09*	BCY71	0-18	BF194	0-10*	BSY65	0-38	2N706	0-15	2N3703	0-18*
AD182	0-35	BC159	0-09*	BCY72	0-12	BF196	0-12*	BSY95A	0-16	2N718	0-22	2N3704	0-10*
AF114	0-20	BC160	0-32	BD115	0-55	BF197	0-12*	BU105	1-80*	2N929	0-16	2N3705	0-10*
AF115	0-20	BC161	0-30	BD131	0-30	BF224J	0-18*	BU105/02	1-90*	2N1131	0-15	2N3706	0-10*
AF116	0-20	BC168	0-00*	BD132	0-48	BF244	0-17*	BU108	3-00*	2N1132	0-18	2N3707	0-10*
AF117	0-20	BC169	0-12*	BD135	0-38*	BF257	0-38	BU109	3-00*	2N1302	0-40	2N3708	0-09*
AF118	0-20	BC169C	0-14*	BD136	0-38*	BF258	0-35	BU126	1-60*	2N1303	0-40	2N3709	0-09*
AF124	0-55	BC182	0-11*	BD137	0-40*	BF259	0-48	BU133	1-60*	2N1304	0-45	2N3710	0-10*
AF125	0-25	BC182L	0-11*	BD138	0-40*	BF259	0-35*	BU204	0-60*	2N1305	0-45	2N3711	0-10*
AF126	0-25	BC183	0-18*	BD139	0-40*	BF259	0-35*	BU205	1-90*	2N1306	0-50	2N3715	1-70
AF139	0-35	BC183L	0-10*	BD144	0-20	BF258	0-45*	BU206	2-40*	2N1307	0-50	2N3716	1-80
AF239	0-37	BC184	0-11*	BD157	0-60	BFW30	1-25	BU208	2-60*	2N1308	0-60	2N3717	1-60
AL102	1-45	BC184L	0-12*	BD181	0-60	BFW59	0-60	BU240	0-40	2N1309	0-60	2N3722	1-90
AL103	1-30	BC186	0-20*	BD182	0-92	BFW60	0-30	MJ481	1-05	2N1171	0-24	2N3773	2-10
AU107	3-30*	BC187	0-24*	BD183	0-87	BFX25	0-26	MJ490	0-90	2N1202	0-44	2N3819	0-28*
AU110	1-75*	BC207B	0-12*	BD184	1-20	BFX30	0-30	MJ491	1-15	2N2217	0-30	2N4047	1-10
AU113	1-60*	BC212	0-11*	BD232	0-60	BFX34	0-23	MJ530	0-40*	2N2369	0-14	2N4348	1-20
BC107	0-09	BC212L	0-12*	BD233	0-48	BFX35	0-25	MJ520	0-45	2N2369A	0-14	2N4870	0-35*
BC107B	0-09	BC213	0-12*	BD237	0-55	BFX36	0-25	MJ521	0-55				

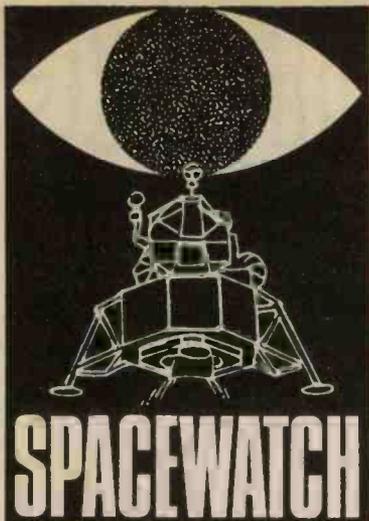

BY FRANK W. HYDE

SHUTTLE TRIALS

It is fifteen years since John Glenn circled the Earth in an epic four and a half hour mission. A milestone in American history made possible by the insistence of a young American President. In that period of half a generation the advance of science and technology has exceeded all expectations.

The advent of the Shuttle is also a landmark in the progress of technology, for the concept of the reusable vehicle is a radical departure from the expendable units and a final capsule return to Earth. The shuttle which after much testing for the validity of its aerodynamic design has successfully been through five unmanned test runs.

Space matters have moved at such a pace that even this new concept has its full recognition only among those with a special interest in the future. Just as the successive missions in space became commonplace news, often with but a passing reference by the media.

As has often happened in this sphere of activity time schedules have been improved so that the first vehicle *Orbiter 101* was available for tests in February. By March five test flights had proved that the Boeing 747-*OV101* ferry combination was successful. The drop tests were unmanned in this instance. *Orbiter 101* was rather different from the *OV 102* and the succeeding vehicles.

Since the tests did not require all the facilities of the final units the aerodynamics were settled in what could be described as a mock-up. One modification became necessary in the form of an air scoop above the crew cabin in order to supply air if the life support systems fail. Already a tail cone had been added to reduce

the buffeting of the tail section of the Boeing 747.

The *OV 102* tests will be with the final equipment and six manned flights due to be started in late May will be operative but no drops will be made. The first of the drop tests will begin in July.

The vehicle is 11m long, 6.7m high and 7.7m wide. There are three rocket engines in the tail section, two manoeuvring engines and forty-four attitude thrusters. The body will have heat resisting tiles over part of the surface with carbon/carbon-felt insulation for certain other parts. The final vehicle without crew and payload will be about 2,616kg.

BY JOVE, LIFE!

The possibility of life on Jupiter was presented in a paper by Carl Sagan and E. E. Salpeter. The paper points out quite boldly that the gaseous condition of the atmosphere of Jupiter is similar in structure to that of the Earth.

From the knowledge available about the chemistry of the atmosphere they are suggesting that the colours, especially the red tint, are the result of the activity of living organisms.

The two men believe that there are conditions which produce large floating organisms which could be visible to the cameras of the *Mariner 10* and *11* probes on the flyby mission later in the year. They suggest that an entry probe would be able to detect, with a mass spectrometer, such organisms. While this cannot be done on the mission scheduled for this year it will be possible to do this with the entry mission planned for 1982.

Sagan and Salpeter have compared the ecology of Jupiter's atmosphere. They say that the seas on Earth which have plankton at near surface levels on which the fish can feed is comparable with a condition on Jupiter where they suggest there are *creatures?* which they call floaters, sinkers and hunters. They are seen as gas bags, the hunters being up to many kilometres across. This would be within the limits of resolution of the *Mariner* space probe cameras.

Nothing like this was seen on the previous flypast. It is also salutary to remember that speculations of life on Mars had a somewhat similar direction of thought which, however, was not verified by the landers.

URANUS RINGS

It has been noted that Uranus, the planet which has an exceptional tilted axis, about 98° to the main plane of the Solar system, has rings around the equator. Observations of the occultation of the star SAO

158657 by Uranus, revealed that there were a series of occultations when the star was well clear of the planet itself.

This indicated that there were other obstructions to the light by some other bodies. The length of time that the star disappeared from sight is a measure of the size of the objects. From the observations it would seem that some of the bodies will be at least 100km across. If this is indeed the case then there could have been a satellite at about 20,000 km above the planet's surface.

There is a limit for the distance of a satellite from the centre of its parent which is critical. It is called the Roche limit. In the case of Uranus this limit is around 59,500km. The objects observed were between 44,000 km and 51,000km from the centre of the planet.

This is consistent with a disrupted satellite. However, the size of the parts is exceptionally large. This adds a new dimension to the odd planet that has many peculiarities. It lies almost on its side which means that the satellites move in a vertical direction with respect to the plane of the orbit. Undoubtedly more will be heard about this discovery.

It is not often that three independent groups observe the phenomenon together. The three groups were the observers in Kuiper Airborne Observatory, three astronomers at Perth, Australia, and two in the Indian Institute of Astrophysics.

THE BLACK CLOUD

Fred Hoyle wrote a science fiction story about a cloud that enveloped the Sun and appeared to have intelligence. Now this has become a point in his new excursion with Wickramasinghe into speculation that life exists between the stars.

These two outstanding men have now suggested that interstellar dust grains have accumulated skins of polymer and that evolution may already have begun. They take this idea a stage further and say that it is possible that proteins and even genes and the cells necessary for life on Earth may have formed on this medium. The idea was "sparked off" by the observation of an organic extract from a meteorite.

There is an ultra-violet spectral line which hitherto has not been identified and this new observation coincides with the position required. There is a broad absorption peak at a wavelength of 2,200 Angstroms. The line is about 300 Angstroms wide and is characteristic of such organic compounds. This is their story at the moment. It jumps ahead of all the other speculations now in vogue. They say "that they have a Darwinian type of evolution of a primitive gene as well as a primordial cell in interstellar space".

TV SPORTCENTRE

By A. M. MARSHALL

Mains-powered: no expensive batteries to replace!


THE TV SPORTCENTRE is based on the AY-3-8500 integrated circuit manufactured by General Instrument Microelectronics. This i.c. provides four basic games, plus two optional extras, with selectable bat size, and selectable ball angles and speed. Automatic scoring and on-screen display of scores are featured, while sound effects add realism to all the games, which are:

● *Tennis*—The picture on the television screen is as shown in Fig. 1 with a centre net, top and bottom boundaries and one bat per side. The scores for each side are counted up from 0-15 and displayed continuously.

After the RESET button has been pressed, the scores will be 0, 0 and the ball will serve arbitrarily from one side of the centre line at one of the angles. If the ball hits the top or bottom boundary it will be reflected and continue in play. The participant receiving service must move his bat to try to intercept the ball.

When a "hit" is detected by the logic, the ball will rebound at an angle determined solely by which part of the bat made the hit. Each bat is divided into four sections of equal length. When using the four-angle option, four different rebound angles are used, as the name implies. When using the two-angle option, the top and bottom pairs of sections are each summed together and only the two shallower angles are used.

The ball will traverse towards the other bat, reflecting from the top or bottom boundary as necessary. The action will repeat until one or other bat misses the ball, whereupon the logic detects a "score". The appropriate score counter is incremented and the new score displayed on the screen. The ball will then serve automatically from the centre line towards the side which had just missed. This sequence is repeated until one score reaches 15, whereupon the game stops. The ball will continue to bounce around the screen but no further hits or scores can be made. Pressing the RESET button zeroes the score counters and restarts the game.

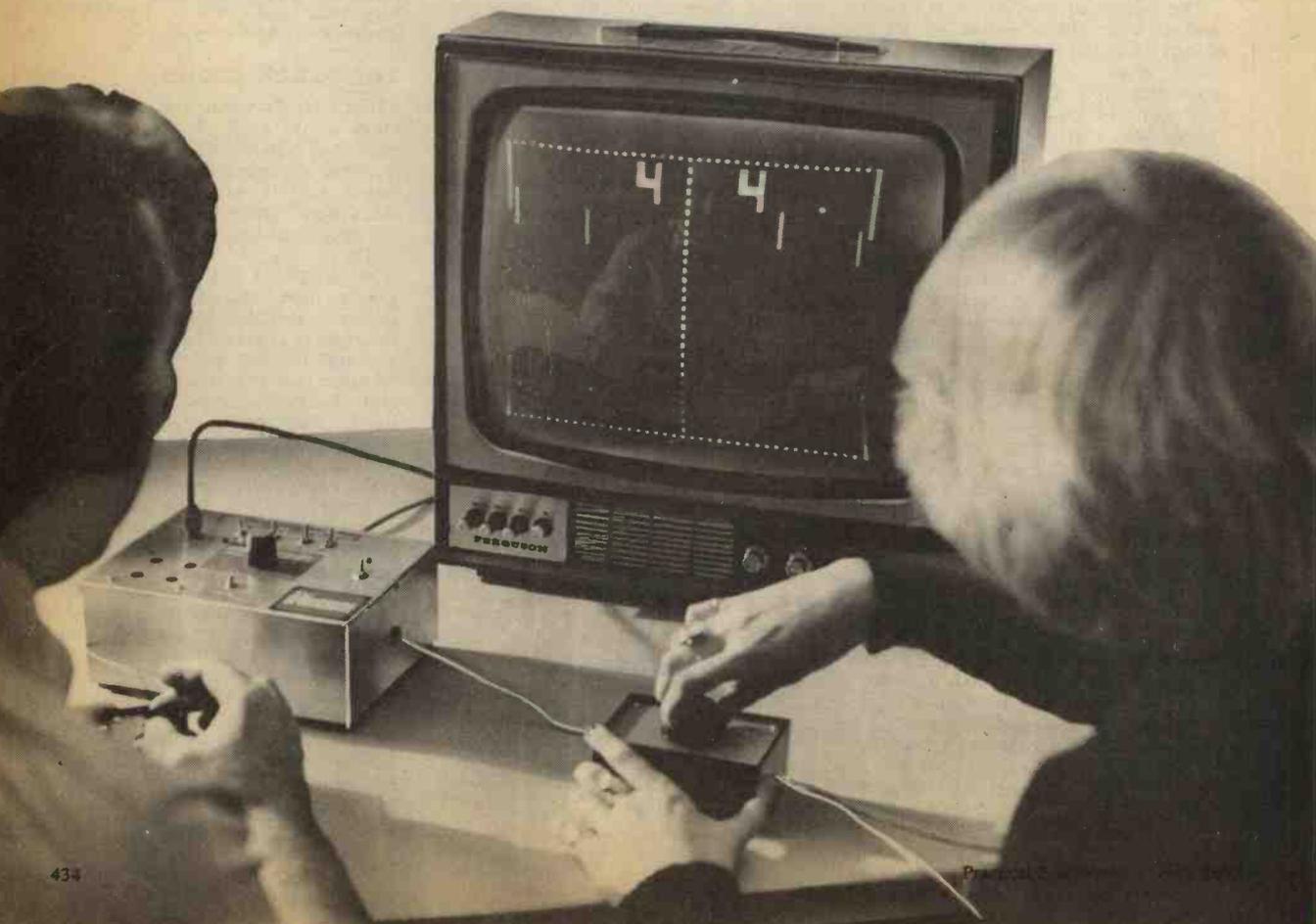

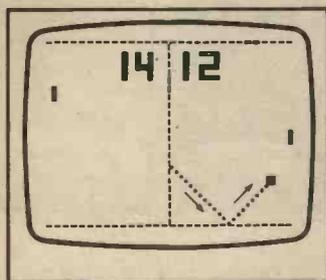
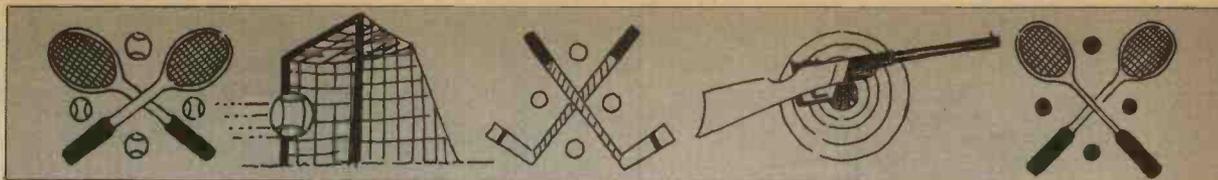


Fig. 1

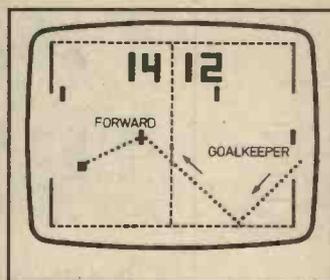


Fig. 2

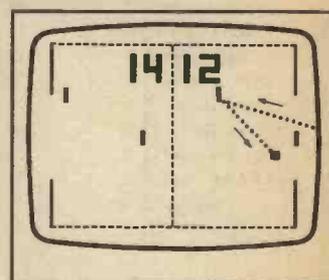


Fig. 3

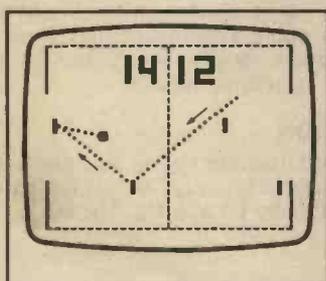


Fig. 4

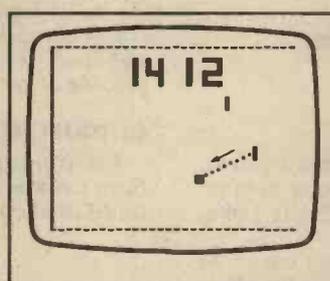


Fig. 5

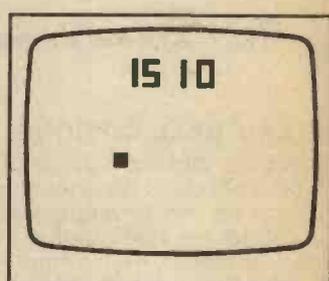


Fig. 6

While the game is in progress, three audio tones are produced to signify top and bottom reflections, bat hits and scores.

● **Soccer/Hockey**—The appearance of the game is shown in Fig. 2, where it will be seen that each participant has two players, a "goalkeeper" and a "forward". The goalkeeper is in his normal position and the forward is in the opponent's half.

When the game starts, the ball will appear travelling from one goal line towards the other side. If the opponent's forward can intercept the ball he can "shoot" it back towards the goal (Fig. 3). If the ball is missed it will travel to the other half of the field where the first team's forward can try to intercept the ball and redirect it forward at an angle determined by the player section used (Fig. 4). The players are subdivided in the same way as the bats in the tennis game. If the ball is reflected from the end boundary or "saved" by the goalkeeper, the same forward can intercept the outcoming ball and divert it back towards the goal.

A score is registered when the ball passes through one of the goal-mouths. Scoring and game control are similar to those of the tennis game, and the same sound effects are used.

● **Squash**—This game is illustrated in Fig. 5. There are two players who alternately hit the ball into the

court. The proper sequence of play is assured by enabling each player alternately, first the right-hand and then the left-hand.

● **Solo/Practice**—This game is similar to squash, except that there is only one player.

● **Rifle Shooting 1**—In this game (Fig. 6) a large target bounces randomly about the screen. A special rifle containing a lens and photocell is aimed at the target.

When the trigger is pulled, the shot counter is incremented. If the rifle is correctly aimed so that light from the target is reaching the photocell at that instant, the hit counter will be incremented and a hit sound generated. The target will then be blanked for a while. After 15 shots the score appears but the game can still continue.

● **Rifle Shooting 2**—This game is similar to the first shooting game except that the target traverses the screen from left to right under control of the manual serve switch.

RIFLE

As mentioned above, a special rifle is required to play the two shooting games. Such a rifle is presently under development, and we plan to publish full details in a future issue.

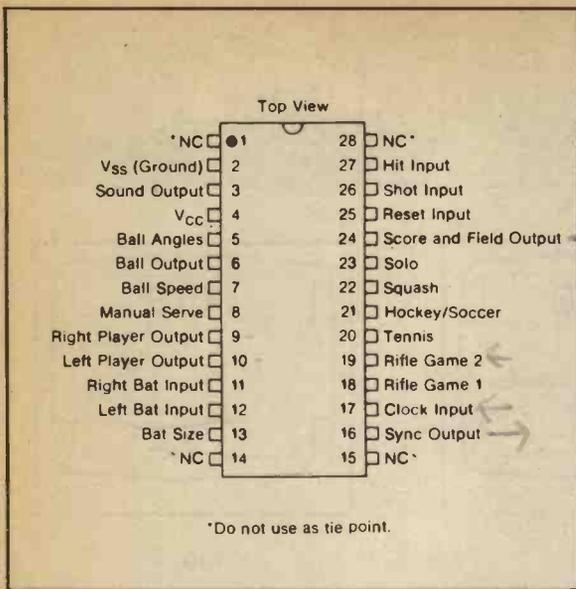


Fig. 7. AY-3-8500 pin configuration

BAT AND BALL OPTIONS

Apart from offering a choice of six different games, the AY-3-8500 chip allows the user to select a number of different options to vary the difficulty of any game. These are (see pin configuration Fig. 7):

● **Bat Size (pin 13)**—This input is left open circuit to select large bats and connected to 0V by S5 to select small bats. On a 19 in TV screen, large bats are 1.9 in high and small bats are 0.95 in high.

● **Ball Angles (pin 5)**—This input is left open circuit to select two rebound angles and connected by S2 to 0V to select four rebound angles. When two angles are selected they are $\pm 20^\circ$, when four angles are selected they are $\pm 20^\circ$ and $\pm 40^\circ$.


● **Ball Speeds (pin 7)**—This pin is left open circuit to select low speed (1.3 seconds for the ball to traverse the screen). When connected by S3 to 0V, high ball speed is selected (0.65 seconds for the ball to traverse the screen).

● **Manual Serve (pin 8)**—When this pin is left open circuit, the game stops after each score. The next serve is achieved by momentarily connecting the pin to 0V via S4. Leaving this pin connected to 0V gives automatic serving. The most convenient form for S4 is that of a push-to-break momentary switch. Alternatively a push-to-make switch can be connected in parallel with S4.

● **Sound Output (pin 3)**—Audio signals of three different frequencies appear on this pin. These are 976Hz for a hit, 488Hz for a boundary reflection and 1950Hz for a score.

BLOCK DIAGRAM

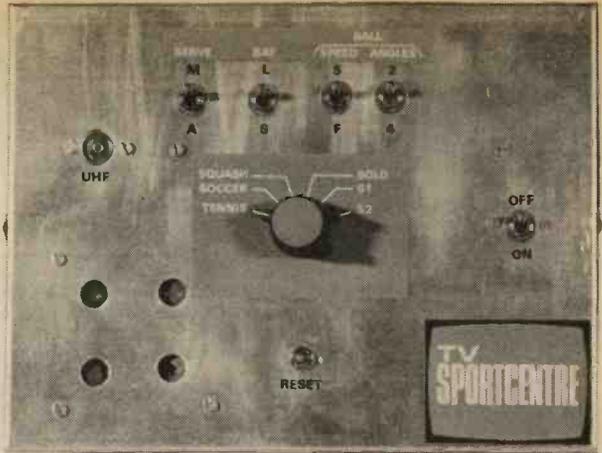The block diagram Fig. 8 shows the input, output and control requirements of the AY-3-8500 games integrated circuit. The master oscillator provides the clock signal for the i.c., from which its internal dividers produce the line and field sync pulses as well as the horizontal and vertical components of the video signals of the game.




These are combined in the video/sync mixer, the output of which modulates a simple u.h.f. oscillator.

The modulated signal is suitable for feeding into the aerial socket of a standard 625-line receiver tuned to around channel 50. A single transistor buffer enables the audio signals from the i.c. to drive a small moving coil loudspeaker. The whole system operates from a stabilised 9V d.c. power supply which should be capable of providing a current of 100mA.

CIRCUIT OPERATION

Referring to the circuit diagram Fig. 9, TR1 and TR2 form the master oscillator. TR1 is a Colpitts oscillator tuned to about 2.097MHz by L1 and C2. The output is

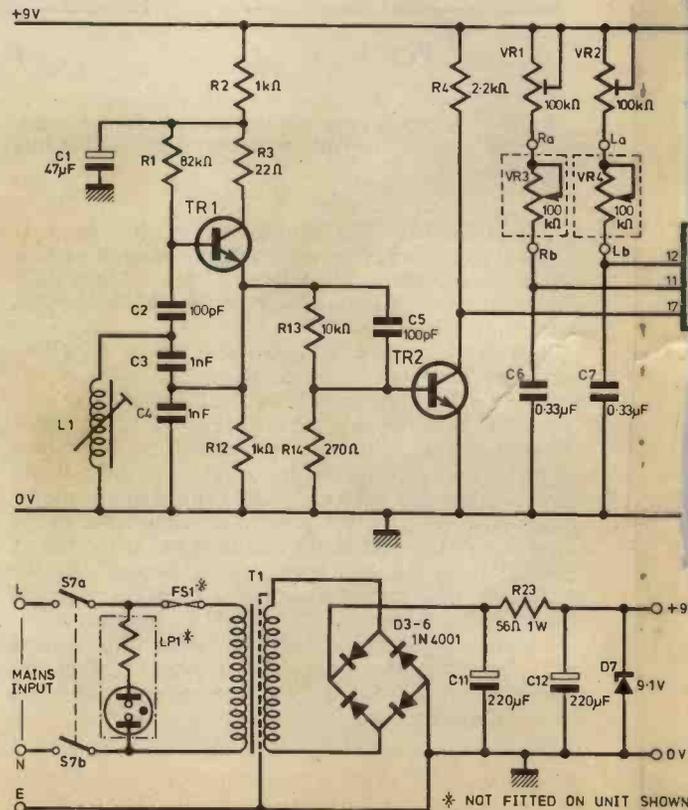

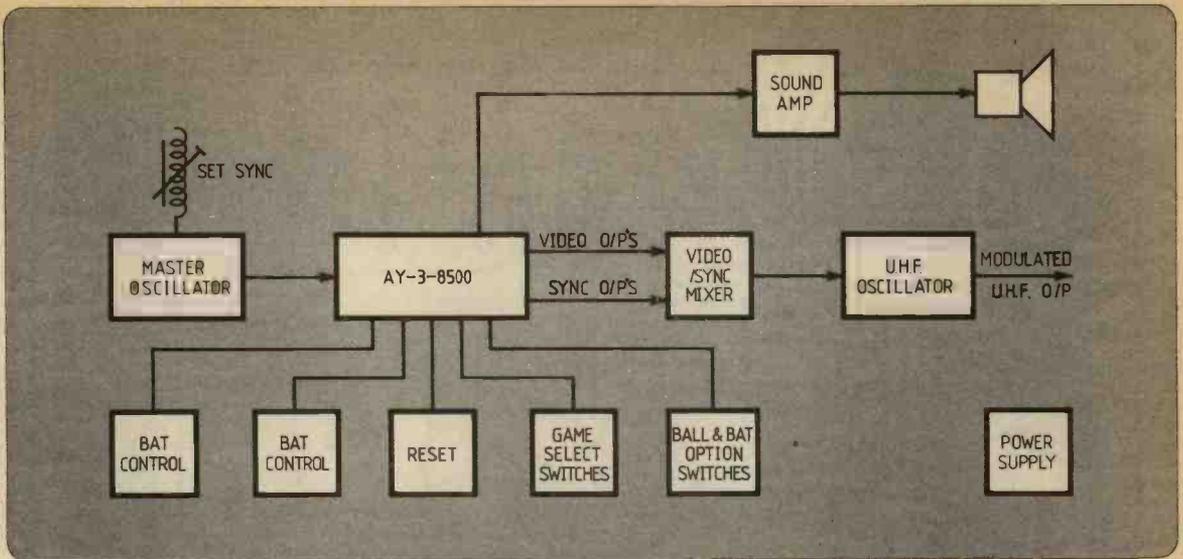


Fig. 8. Sportcentre block diagram

buffered by TR2 and feeds the clock pin of IC1. Variable resistors VR3 and VR4 are player controls for changing the bat positions. It was not found necessary to use screened lead to operate them remotely in the prototype. A 3m length of lightweight twin flex was used for each control. Preset controls VR1 and VR2 are for adjusting the bat displacement to cover the full height of the screen.

Transistor TR3 forms the video/sync mixer. The resistors connected to its base ensure that the video and sync levels are in the correct ratio. The composite video output is applied to the emitter of the u.h.f. oscillator TR5 to modulate it. The stripline inductors L2, L3 and L4 are part of the copper track of the printed circuit board. The frequency of the oscillator is set by C8.

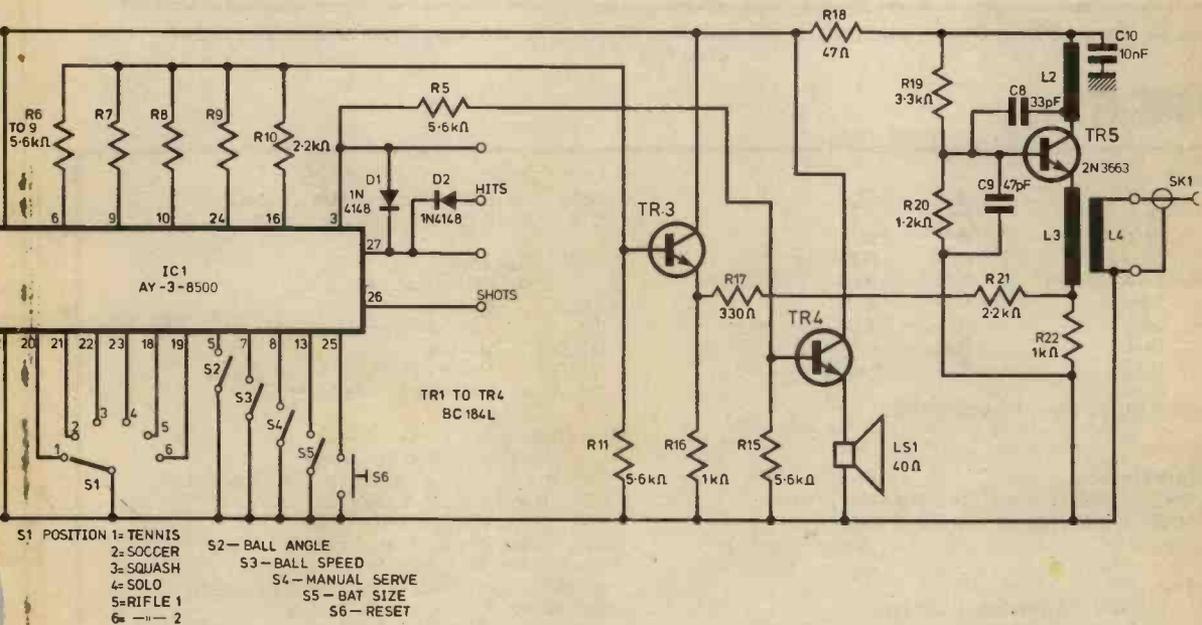


Fig. 9. Circuit diagram of the Sportcentre

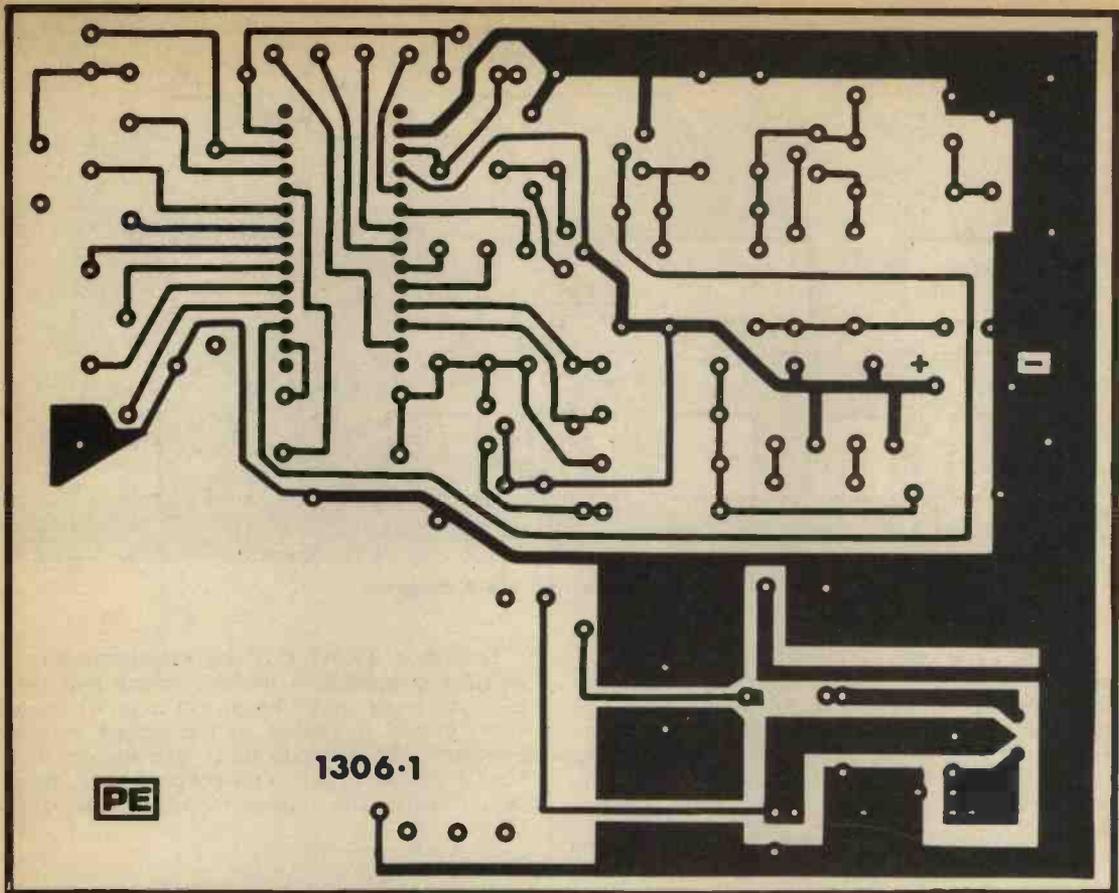


Fig. 10. Printed board track pattern, shown full size. Blank area at bottom left is reserved for rifle circuitry

COMPONENTS...

Resistors

R1	82k Ω	R15	5.6k Ω
R2	1k Ω	R16	1k Ω
R3	22 Ω	R17	330 Ω
R4	2.2k Ω	R18	47 Ω
R5-R9	5.6k Ω (5 off)	R19	3.3k Ω
R10	2.2k Ω	R20	1.2k Ω
R11	5.6k Ω	R21	2.2k Ω
R12	1k Ω	R22	1k Ω
R13	10k Ω	R23	56 Ω 1W
R14	270 Ω		

All $\frac{1}{4}$ watt 5% carbon film except R23

Potentiometers

VR1, VR2	100k Ω miniature horizontal presets
VR3, VR4	100k Ω linear moulded track

Capacitors

C1	47 μ F 16V	Tantalum bead type
C2	100pF	Polystyrene
C3	1nF	"
C4	1nF	"
C5	100pF	"
C6	0.33 μ F	MKM polycarbonate
C7	0.33 μ F	MKM polycarbonate
C8	33pF	sub-miniature plate ceramic
C9	47pF	sub-miniature plate ceramic

C10	10nF	disc ceramic
C11	220 μ F 25V	tubular electrolytic
C12	220 μ F 25V	tubular electrolytic

Semiconductors

TR1-TR4	BC184L (4 off)
TR5	2N3663
IC1	AY-3-8500 (GIM)
D1, D2	1N4148
D3-D6	1N4001 (4 off) or silicon bridge
D7	9.1V 400mW Zener diode

Miscellaneous

LS1	35/40 Ω 2.5in loudspeaker
T1	Min. mains transformer, 12V 6VA sec.
LP1	Neon indicator 240V a.c.
FS1	200mA 20mm with holder
S1	1-pole, 6-way rotary switch
S2-S5	S.P.D.T. min. toggle switch (4 off)*
S6	Min. push-to-make push-button switch
S7	D.P.S.T. min. toggle switch
	Printed circuit board. Aluminium box 200 x 150 x 75mm.
	Plastic moulded boxes 110 x 71 x 50mm (2 off).
	Coil former, 6mm diameter, with tuning slug.
	36s.w.g. enamelled copper wire. Knobs. Coaxial socket.
	Miniature group board.
	*See text regarding S4


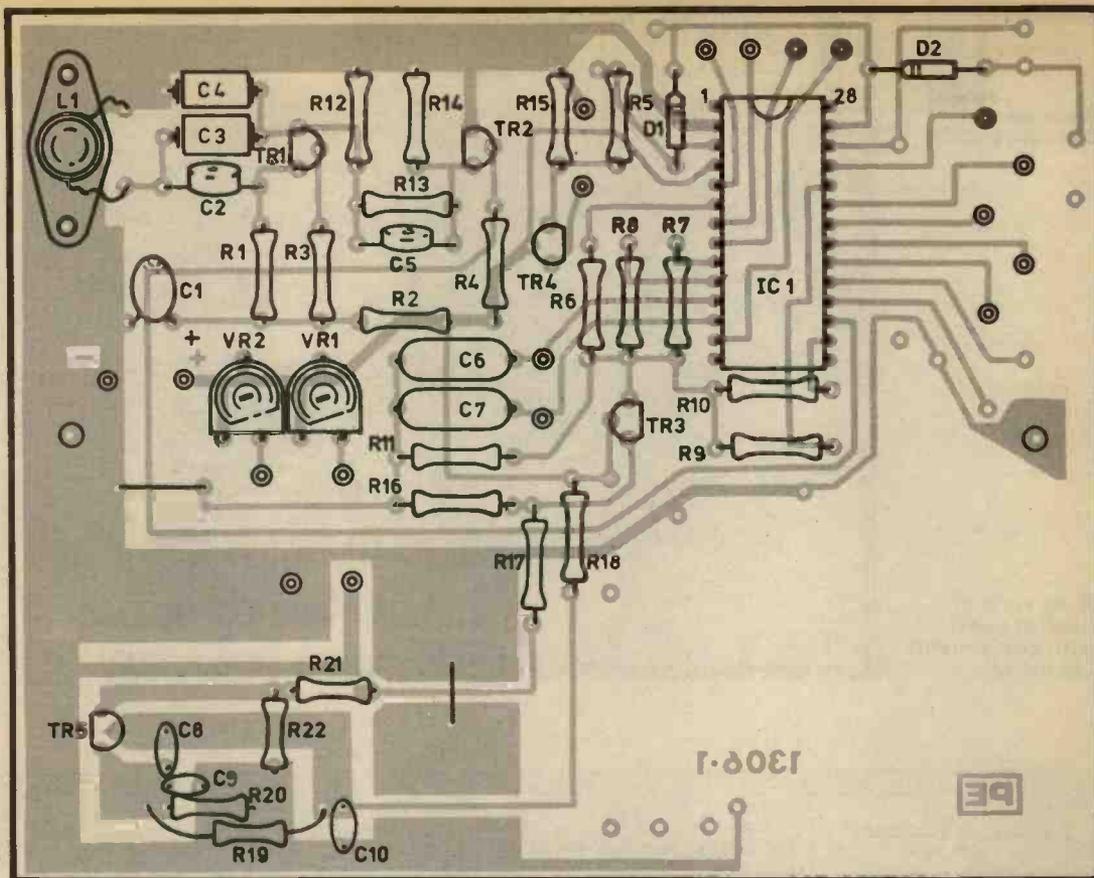


Fig. 11. Printed board component layout

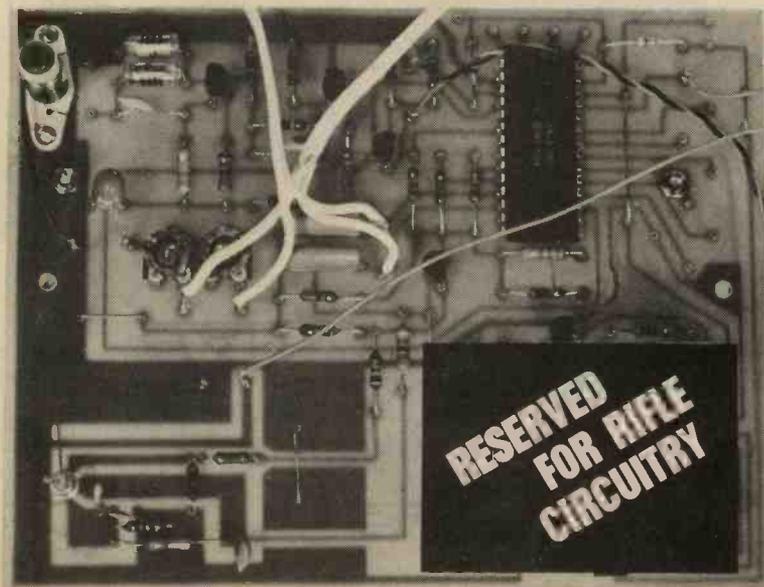

Prototype printed circuit board

**SPECIAL
OFFER
FROM**

MAPLIN

To P.E. Readers


**THE AY-3-8500
GAMES CHIP**

FOR ONLY


£8.99

UNTIL JUNE 15

(See back cover for address)

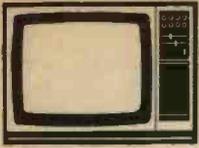

TV SPORTCENTRE

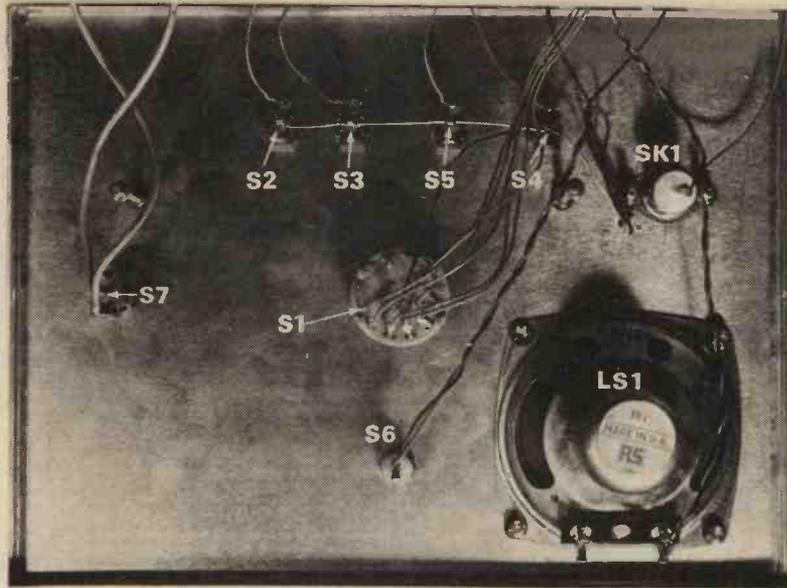

Rear view of control panel with components identified



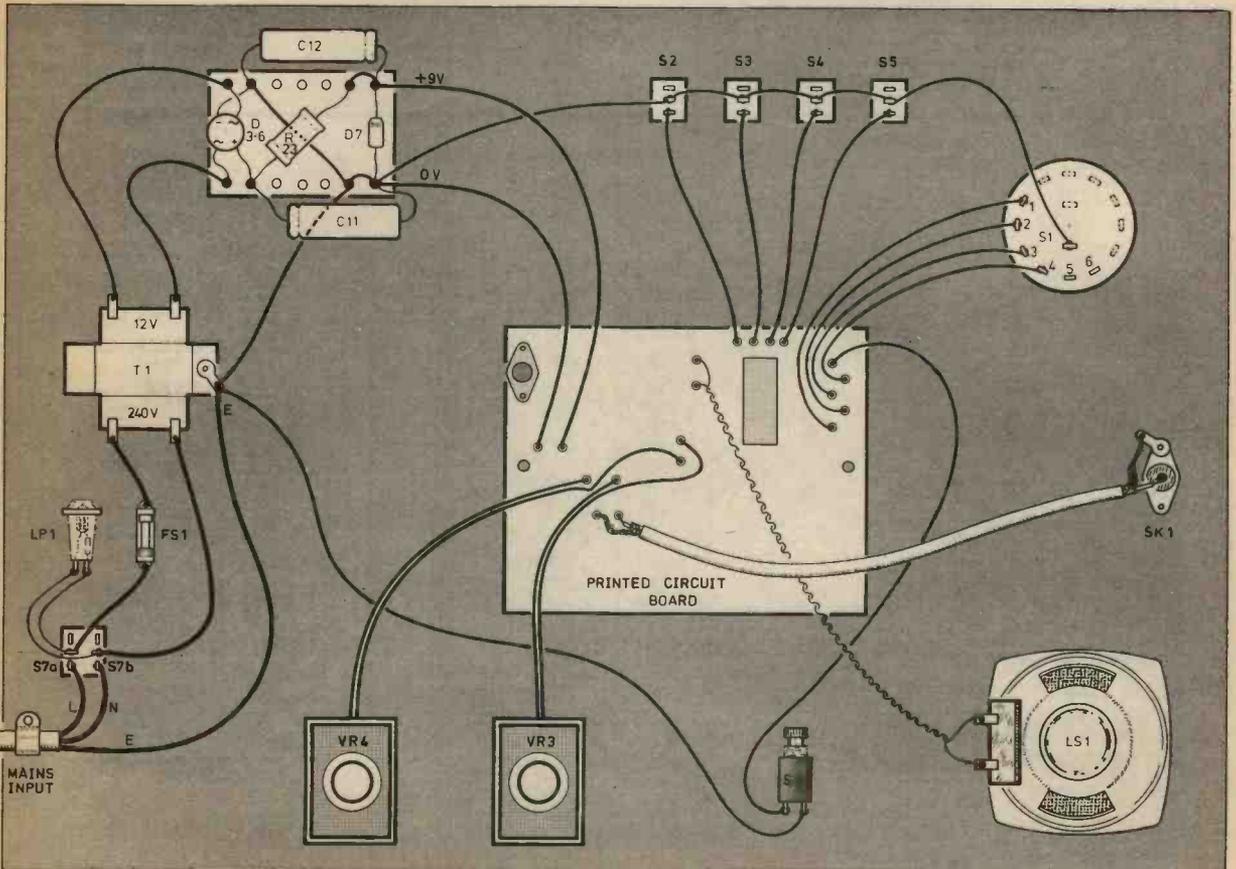


Fig. 12. Wiring diagram including power supply

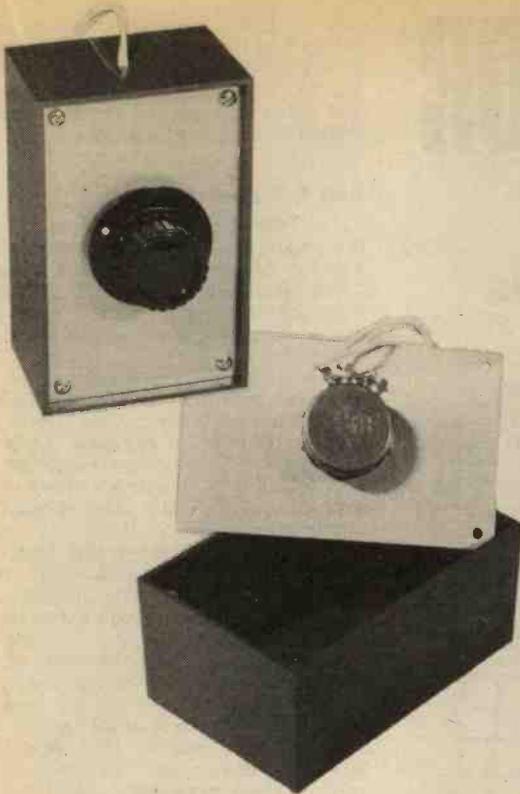

Remote controls

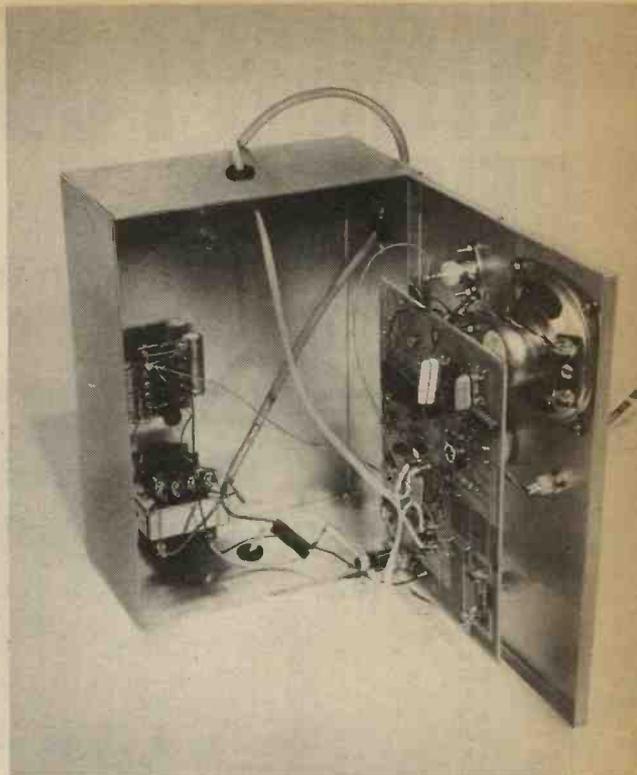

Interior view of prototype

CONSTRUCTION

The inductor L1 consists of 55 turns of 36 s.w.g. enamelled copper wire close wound on a 6mm (0.25in) diameter former. Two small holes (1mm dia.) should first be drilled in each side of the base of the former for anchoring the ends of the winding. A small amount of quick-setting adhesive should finally be applied to fix the turns of the coil.

The board (Figs. 10 & 11) can be assembled by fitting and soldering the links (tinned copper wire), resistors, diodes, capacitors, transistors, presets and coil. Carefully check the orientation of the transistors, diodes and electrolytics. The last component to be inserted is the integrated circuit, which should be retained in its packaging until required. This is an MOS i.c. and is thus susceptible to damage from static electricity until it has been soldered into the p.c.b. A properly earthed soldering iron must be used. If this precaution is observed it is not necessary to use a 28-pin i.c. socket, or Soldercon sockets.

The board is mounted behind the lid of the box, spaced off on long 6BA screws and nuts. Before attaching it, wires must be soldered to it for the switches, loudspeaker and power supply. The connection from the modulator to the coaxial socket can be made with a short length of screened lead.

The internal layout of the unit is shown in Fig. 12. The power supply components are mounted on a miniature group board which is fixed to the bottom of the main box by two 6BA screws and spacers. For D3-D6 use either four separate diodes or a bridge as preferred.

TESTING AND SETTING UP

Before switching on, carefully check the polarity of the connections to the power supply. Set the game selector switch to TENNIS and the serve switch to AUTOMATIC. After switching on, the tones for boundary reflections and scoring should be heard coming from the loudspeaker.


Connect a coaxial lead from the games unit to the aerial socket of a television receiver. A signal should be received at around channel 50. The core of L1 should now be adjusted for proper locking of the pattern. Fine adjustment of this core should stop any slow undulations in the pattern.

The capacitor C8 in the u.h.f. oscillator may have to be increased or decreased in value by 5 or 10pF if the signal does not tune in conveniently. Finally, the presets VR1 and VR2 should be adjusted so that the bats traverse the full height of the screen. ★



INTERCEPT JUNIOR REVIEWED

By R.W. COLES

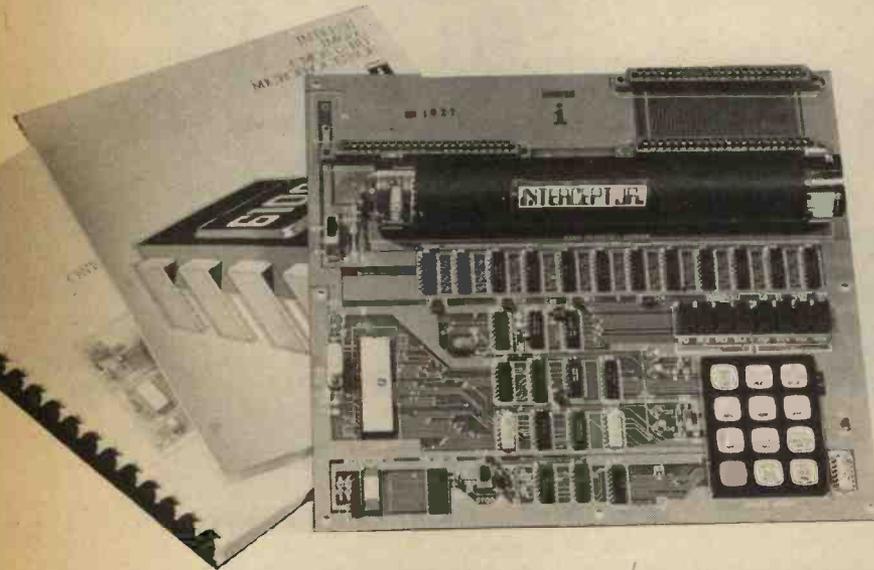

THE Intercept Junior is a "stripped down" microprocessor development and tutorial system which features the unique Intersil IM6100 CMOS microprocessor chip in a versatile and expandable "no frills" design.

The system is based on its big brother, Intercept itself, which is a cabinet mounted development and prototyping system with mains power supply, a comprehensive range of facilities, and needless to say, a price tag to match! Intercept Junior brings the undoubted power of the 12-bit IM6100 chip within the reach of the computer hobbyist and small industrial user.

COMPACT LAYOUT

As can be seen from the photograph, a very compact layout has been achieved where MPU, RAM, ROM chips, keyboard display and battery power source coexist on a single glass fibre printed circuit board measuring 28cm by 25cm, without appearing at all cramped. To keep the "Junior" as economical as possible, no case is provided, the rear of the board being protected by a hardboard cover with attached rubber feet.

The attractive component layout is laid bare to the probing oscilloscope or multimeter, as is the fashion with this type of system. At the rear of the

circuit board are three edge connector sockets which can be used for system expansion using either the RAM, PROM, and INPUT/OUTPUT cards available from Intersil, or suitable custom built alternatives which would be fairly simple to construct and probably cheaper.

THE IM6100 MICROPROCESSOR

Before delving further into the pros and cons of the Intercept Junior system it is as well to consider the chip which makes it all possible, the IM6100 itself. The feature which makes the IM6100 unique is the fact that it is configured to recognise the instruction set of the most popular range of minicomputers ever built, namely the PDP8's from Digital Equipment Corporation which are in use around the world in their tens of thousands controlling industrial plant, laboratory experiments, and almost anything else you care to name.

The PDP8 minicomputer has been around since the middle sixties, and not surprisingly, a comprehensive library of software routines has been established both by D.E.C. themselves, and by their customers, most of which could be run on systems using IM6100 microprocessors.

It's not just the availability of software which will guarantee success

for the IM6100 though, the simple fact is that there are more engineers in the business familiar with the PDP8E than with any other computer, and for these people, putting the IM6100 to work will be child's play.

CMOS TECHNOLOGY

The PDP8E connection is certainly the *biggest* gun in the Intersil arsenal, but the fact that the IM6100 uses CMOS technology which takes a mere 2.5mA from a five volt supply is a pretty potent sales weapon in its own right.

A silicon gate CMOS process is used and operation is fully static so that the system clock can be slowed, or even stopped, if required. Three versions of the chip are produced, the basic IM6100 which is characterised for operation at 5 volts at clock frequencies of up to 4MHz, the IM6100A which is a high-speed selection operating at up to 8MHz at 10 volts, and the economy IM6100C, which is a little slower with a 3.3MHz maximum clock rate at 5 volts. Intercept Junior uses the IM6100C which is adequate for the job; using the IM6100A at 10 volts can increase consumption to 10mA at 8MHz.

The chip is housed in a 40-pin ceramic package and includes an on-chip clock oscillator so that the external component count is minimised. At 5 volts, TTL compatibility is assured, though it seems more logical to use 4000 series or 74C series CMOS to save power.

A full complement of peripheral and support chips are supplied by Intersil (and others, incidentally) including CMOS RAMs and ROMs, a CMOS UART and a capable "Peripheral Interface Element" or PIE. One omission from the list is a CMOS PROM, but this I believe is in the pipeline, and, anyway, with a bunch of CMOS RAMs maintained for months by a couple of pen cells, who needs PROMs?

ARCHITECTURE

The IM6100, like its progenitor the PDP8E, employs 12-bit parallel-transfer operation, two's complement arithmetic, and single address instructions. The chip has six 12-bit registers, (Fig. 1) but only three of these are program accessible, namely the accumulator, the M.Q. register, and the program counter. When compared with other current microprocessors, the amount of on-chip storage provided seems limited, but against this must be set the fact that the first 128 words of RAM storage can be directly addressed and may be used as index registers, stack pointers and temporary data storage in the same way that on-chip registers are used in other designs.

Communication with memory and input/output ports etc. takes place on a single-bit bidirectional parallel bus

which carries address information, data inputs, and data outputs in time-multiplexed sequence.

This time-multiplexing means that the address outputs have to be latched externally, but this is not always a problem since the standard 6508 CMOS RAM has the necessary latches on chip. If other memory components are used, even standard bipolar PROMs for example, latches such as the SN74174 must be employed to store address information for use during memory read and write cycles.

The 12-bit address word gives a basic address range of 4096 locations, called a "field", and with extra external logic, up to eight fields can be accommodated. Each field is divided into 32 pages, with 128 words per page.

MICROINSTRUCTIONS

The IM6100 has the interesting distinction of a microcoded instruction capability, again like the PDP8. Microcoded instructions are instructions which may be designed by the programmer using combinations of simpler instructions (Microinstructions), in a single instruction word by

GROUP 1 MICROINSTRUCTION OPTIONS. A LARGE NUMBER OF BIT PERMUTATIONS ARE POSSIBLE.

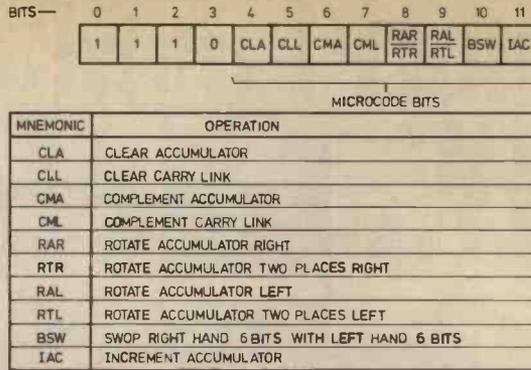


Fig. 2. An example of the IM6100 microcode format

setting appropriate word bits to a "One" or a "Zero" (See Fig. 2).

In practice, only certain combinations are normally used, and so lists of these "Popular" combinations are published in the IM6100 manuals in much the same way that other microprocessor instruction sets are laid out.


There is no doubt that a micro-coding capability can add flexibility

to a microprocessor, and the Intercept Junior makes full use of this as we shall see.

PROBLEMS

Subroutines can be a bit of a headache with the IM6100 if programs are stored in ROMs or PROMs, because a JMS (JUMP TO SUBROUTINE) instruction stores the

Fig. 1. Inside the IM6100 chip

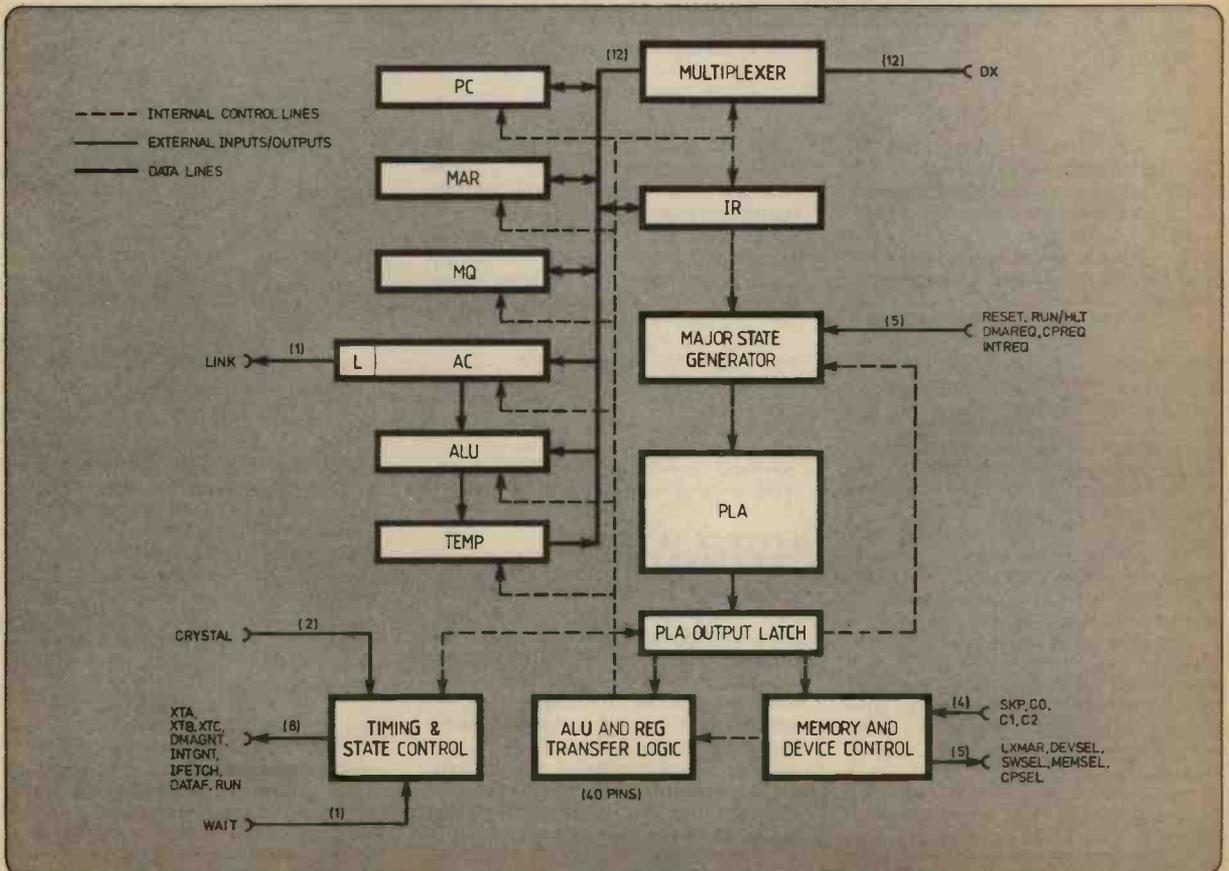

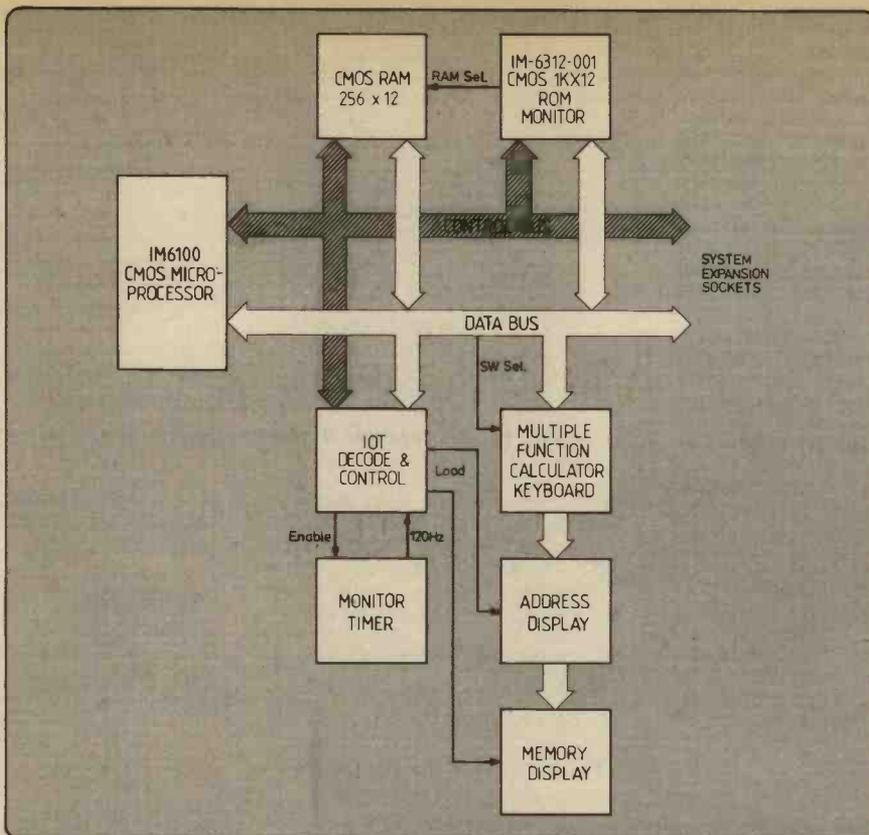


Fig. 3. The Intercept Junior system components

current contents of the program counter in the first *subroutine* address instead of using a separate stack area. If the subroutine is in, say, a ROM it is impossible to write the return address into what is, after all, a *read only* memory, and so we have a problem.

There is of course a way out, but it requires providing an entry point for each subroutine in RAM memory, and the contents of these entry points have to be "Initialised" at power-on by a part of the main program so as to load them with appropriate unconditional jump instructions. This is a programming anomaly which the IM6100 inherits from the PDP8 which would itself normally be used only with "Writable" program memory, and for the sake of that all important compatibility, it is something users will have to live with.

The only other complaint I think is worth voicing here is about the lack of BCD arithmetic instructions, though it could be argued that with a 12-bit machine there is every incentive to do all number-crunching in binary anyway.

CONTROL PANEL

A unique and very attractive feature of the IM6100 chip is the

provision for a dedicated and independent control panel which can utilise a completely separate memory to house test routines, loaders etc. This means that control panel functions such as those required by a general purpose microprocessor or development system can be provided on any IM6100 system without disturbing the main memory and its contents.

If appropriate, the control panel, complete with memory, can be a portable device which is plugged into dedicated systems only when it is required, for program loading, modifications, or debugging purposes.

INTERCEPT JUNIOR ORGANISATION

Intercept Junior has 256 words of RAM and 1,024 words of pre-programmed ROM, with a socket for another 1,024 words of ROM also on the main board (Fig. 3). Interaction with the system is achieved via the colourful multi-function keyboard and the eight-digit, seven-segment i.e.d. display which indicates the current program counter (P.C.) contents, and the contents of the address to which it points (E.A.). The binary contents of the P.C. and the E.A. are displayed in octal, using the character set 0 to 7

to represent a group of three binary bits, so that each bit word uses four characters.

The octal system for representing binary numbers is also used for keyboard entries, so that only the digits 0 to 7 appear on the keys. Those used to hexadecimal coding will probably not like having to use octal, but this is another inheritance from the PDP8 and in fact makes the Intercept Junior easier to use for those who are familiar with the D.E.C. machines.

The ROM supplied is a mask-programmed device which contains all the control panel monitor routines to provide keyboard encoding and debouncing, display driving, register saving and control of a teletype or tape reader when the appropriate interface card is fitted. The ROM occupies pages 24 to 31 at the high end of the 4096 word main memory area, while the RAM occupies the two lower pages, 0 and 1.

OPERATION

After switching on, the Intercept Junior can be loaded with user programs via the keyboard, although long programs would require the addition of extra memory, since half the 256 word RAM supplied is used

by the monitor routines, and this restricts user programs to only 128 steps in the basic system.

Program steps are entered not by looking up instructions in the manual and keying in their hex, or octal, equivalent as is usually the case with other systems, but by using the microcode mnemonics which appear directly on the keys. This means that after a little familiarity with the system, it is possible to enter program instructions directly through the keyboard without constant reference to coding lists.


With the basic system, the types of programs you can run are restricted to those which use the l.e.d. display for output, and the keyboard for input. Since the display is of the "decoded" type with no access via the program to individual segments, display is restricted to the 0-7 octal or 0-9 decimal set with no possibility of alphanumeric.

To take advantage of the D.E.C. PDP8E software such as the PAL III assembler, the 23-bit floating point math package, F.P.P., or the FOCAL 8 calculator package, it would be necessary to add an extra 4K of RAM memory and a teletype interface card. In principle at least, this is quite possible, although slots only exist for 1K of extra RAM if you use standard Intersil expansion cards.

HANDBOOK

One aspect of the Intercept Junior which deserves special mention is the excellent Owner's Handbook which comes with each system. We found this book easy to read and a mine of information on both the hardware and the software aspects of Intercept Junior.

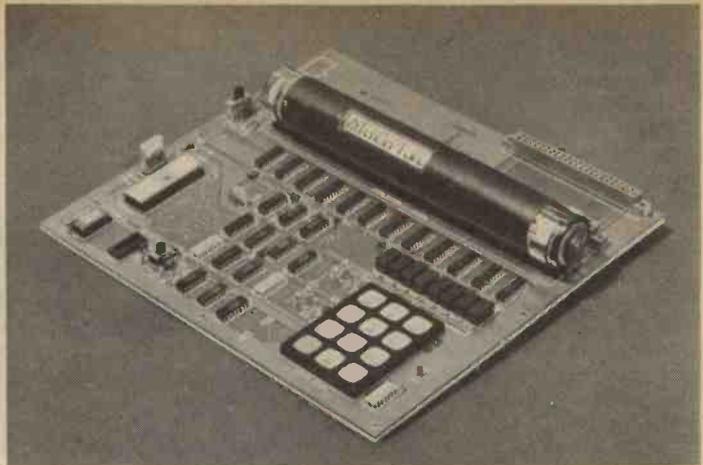Included as appendices are two very useful sections, one an introduction to logic, and the other a



comprehensive and concise glossary of all those microprocessor buzzwords like "Indirect Address" and "Data Break".

The book is written rather like a programmed learning course so that those with little or no knowledge of microprocessor techniques need not feel, (as is often the case) that they have been dumped in at the deep end. Programming is introduced by means of thirteen examples with easy to follow commentaries, and after working through these, most people would be ready to try some simple routines of their own. Full circuit details of the Intercept Junior and the optional plug-in cards are provided, and by studying these it should be possible to expand the system hardware without too much head-scratching.

VERDICT

Any assessment of the Intercept Junior must necessarily take account of the IM6100 microprocessor which

is such an essential part of it. We feel that for anyone with PDP8E experience or better still, access to PDP8E software, the IM6100 and the Intercept Junior are a very attractive proposition.

For people without either of these things, the Intercept Junior makes an excellent tutorial system which is reasonably priced if one considers that easy expansion is assured because of the on-board sockets.

The IM6100 is, of course, a powerful microprocessor and hardly the sort of thing you would want to invest in for the "low end" application such as, say, train set control. If, however, you long for the day when you can hook up your VDU and low-cost floppy-disc to a microprocessor-based home computer which will handle MasterMind and Chess programs, you may still have a couple of years to wait, but meanwhile the IM6100 and the Intercept Junior make a promising starting point!

POINTS ARISING

RANDOM NUMBER GAMES MACHINE (December 1976)

In Fig. 3, page 971, the TO-220 plastic package should have pins 2 and 3 transposed. In Fig. 4, page 973, pin 8 of IC6 should go to the 0V rail. There is an apparent discrepancy between circuit diagram and wiring diagram in the connections between the two counters IC3 and IC4 and IC9a/b. In fact both are correct as they are electrically equivalent.

The designation R5 and R6 in Fig. 4 should be transposed. Also, the point "T" (IC5 pin 6) should be linked to IC3 pin 11.

AUTOWAH (March 1977)

Note that the orientation of TR1 shown in Fig. 3, page 207, can be misleading. The correct leadout of the f.e.t. is shown above:



LOW COST RADIO CONTROL SYSTEM (January/February 1977)

In Fig. 3, page 105, two additional links are required on the printed board pattern. These are between R20/TR4 collector and C3/R21, and between the junction of R6/R9/R12/R24 and the 0V rail.



PUBLISHERS ANNOUNCEMENT

The current 1977 Binders will now only hold 8 issues as the September 1977 issue format will be increased in size.

A larger Binder to accommodate 16 issues from September 1977 to December 1978 will be introduced.

Remittances with overseas orders for binders: please add 60p to cover dispatch and postage.

ELECTRONIC DIE

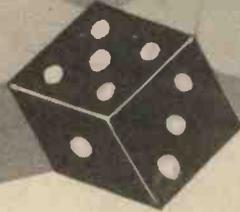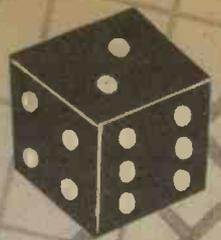

By G. Jones

This circuit illuminates l.e.d.s in the familiar die pattern, representing a number chosen at random on each "throw". Whilst the concept of such a device is not new, this design uses a novel counter which may be of interest.

OPERATION

The circuit shown in Fig. 1 consists of a gated clock driving a six-state counter which is stopped in a state chosen at random; this is then converted into a displayed pattern. The period for which the clock is operating is controlled by the length of time for which a finger bridges the strips of a touch plate. C3 charges

COMPONENTS . . .

Resistors

R1	100Ω
R2	1kΩ
R3-9	270Ω (7 off)
R10	390Ω
R11	120Ω
All ¼W carbon	

Capacitors

C1	0.33μF metal foil
C2	22μF 16V elect.
C3	10μF 16V elect.

Integrated Circuits

IC1	SN7413
IC2-3	SN7473 (2 off)
IC4	SN7400

Transistors

TR1	BFX88
TR2	BC107 or similar

Diodes

D1-7	T1L209 or similar
D8	1N914

Miscellaneous


6V supply/battery, Case, Veroboard, 1.8in x 3.5in (2 off) and off-cuts



The completed unit

through the skin resistance, saturating TR2 and sending the output of IC1a high. IC1b then acts as a simple multivibrator providing clock pulses to the counter.

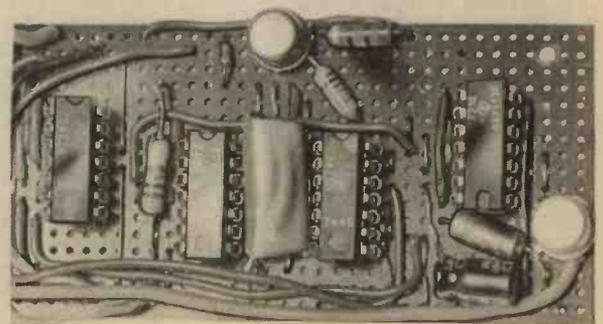When the touchplate is released, C3 discharges through TR2 allowing IC1a output to go low and



Circuit board component layout

turning on TR1. Then if any of points A, B, C, D are taken to ground (through the counter circuit) the appropriate l.e.d.s (D1-7) are lit. Thus the display is only on when the counter is stationary.

COUNTER

Previous designs have employed a three stage binary counter, forced into a short (6-state) cycle, and gate circuitry to decode the output into a form suitable for display. This type of circuit generally leaves a flip-flop unused as they are most conveniently available in pairs in the SN7473 i.c. By considering the face of a die it will be seen that only four independent display controls are necessary, labelled A-D in Fig. 1 and Fig. 2a.

As the counter uses four bistable elements, its state at any time can be represented by a four bit binary word DCBA; for example 0001 represents output A low, outputs B, C, D, all high. There are 2^4 , (16) of these states and on receipt of a clock pulse the counter will move from its present state into a new one, for example, from 0001, after one clock pulse, into 0111. This is represented by Fig. 2(b), where it will be seen that there are six states in a central "cycle".

No matter what the initial state of the counter, after one clock pulse it will rest in one of these states and after further clock pulses the counter will have moved into one of the six states. These six states are therefore chosen to represent the six states of the die and the number of spots illuminated is shown again each state thus: "4" is 0110 for example.

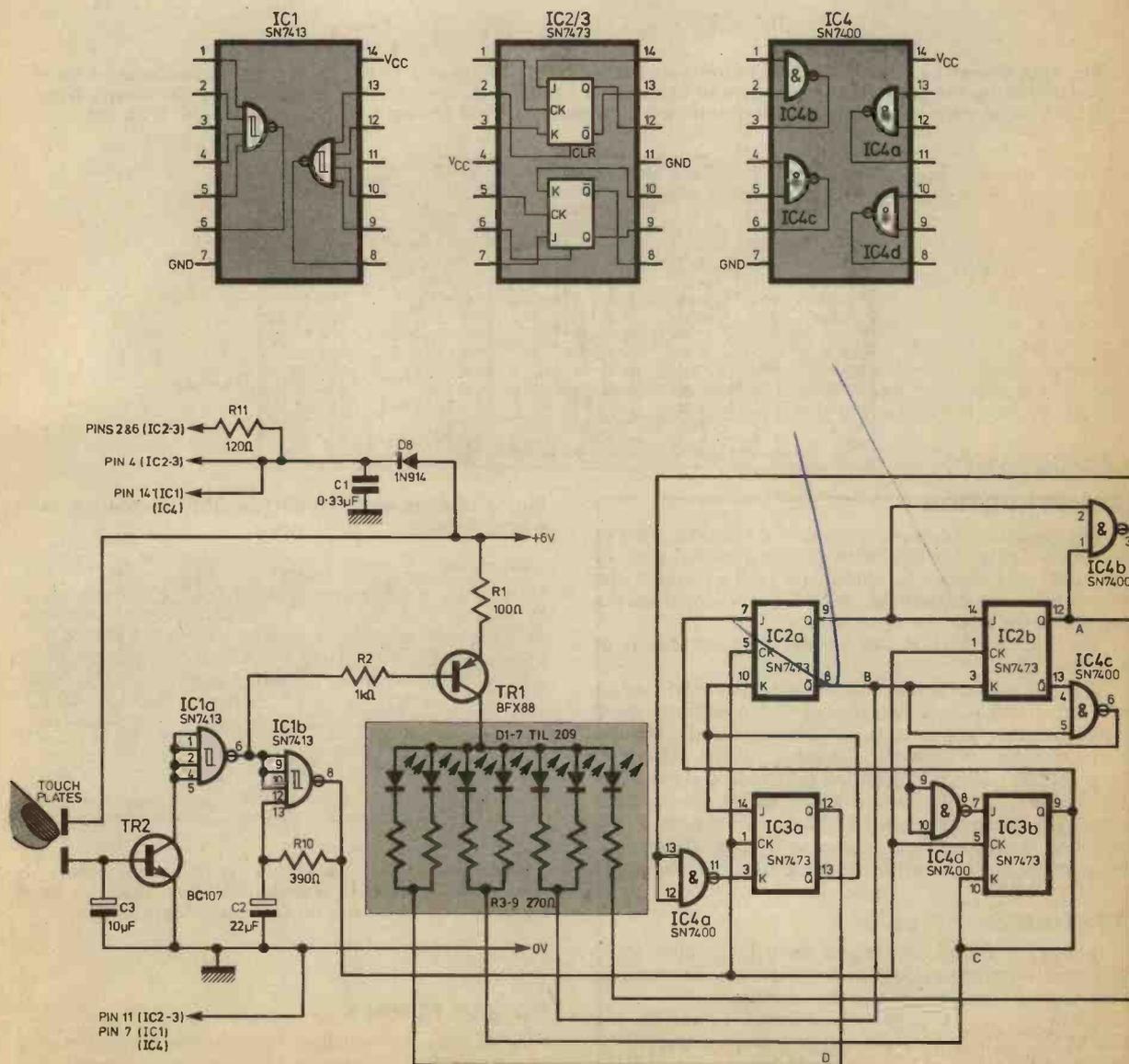


Fig. 1. Circuit of die and i.c. leadouts

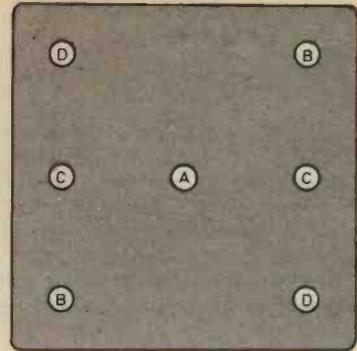
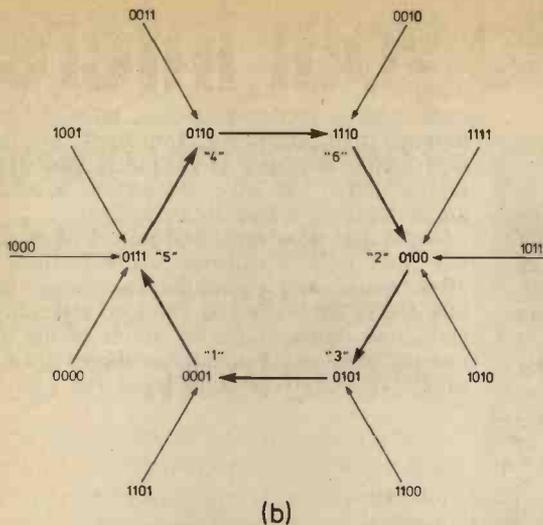


Fig. 2(a). Seven I.e.d.s are required to indicate the six states of the die. There are sixteen possible conditions presented by the four binary counters to the I.e.d.s. Each condition can be represented by the binary word DCBA. The words that relate to die 'number' configurations are shown in the central 'cycle' (Fig. 2b)

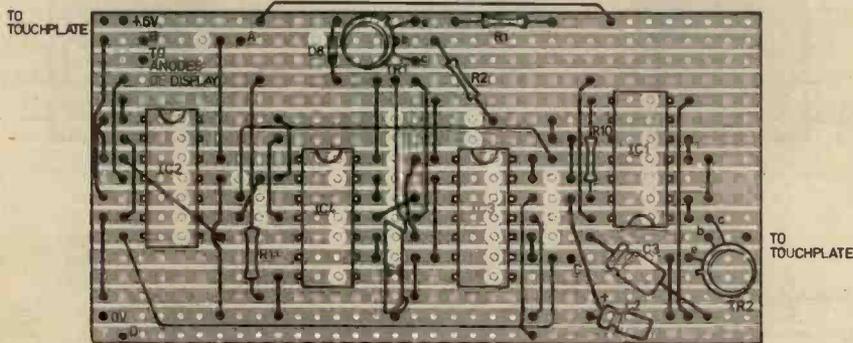


Fig. 3. Component layout for the Veroboard with wiring details

CONSTRUCTION

The majority of components are laid out on a piece of Veroboard (Fig. 3) with the display on a second piece of board. It was chosen to mount the I.e.d.s through the board from the copper side with R3-9 soldered on the copper strips from the same side.


The diodes are laid out in the manner shown in Fig. 2(a).

The touchplates in the prototype was constructed of two small offcuts of Veroboard (0.6in square) glued back-to-back (copper strips showing and running perpendicular to those on the other offcut). Alternate strips of the top board are then soldered by short wires to two strips on the bottom board which are the contacts. The plate can then be glued over a hole in the die case (insulated from the case if it is metal) and leadouts taken from within the case, through the hole.

TESTING

It may be found convenient initially to omit R10; IC1 will not then oscillate and the die can be made to step around the cycle to test the counter.

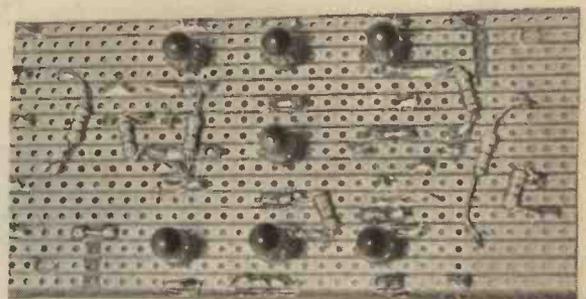Clock pulses are provided at about 100Hz by the circuit shown, and this rate can be greatly increased by lowering the value of C2. However, the fan out of IC1a is exceeded in this circuit and reliable operation may not be obtained if too low a value is selected.




The seven I.e.d. assembly with its resistors is mounted on its own Veroboard. The board is fixed by pushing the I.e.d.s through mounting clips

POWER SUPPLY

A 6V supply is specified because this is conveniently obtainable from batteries. However, as it exceeds the maximum safe V_{cc} for TTL i.c.s, D8 is included to lower V_{cc} by about 0.8V. ★

Bring 'scope' to your interest.



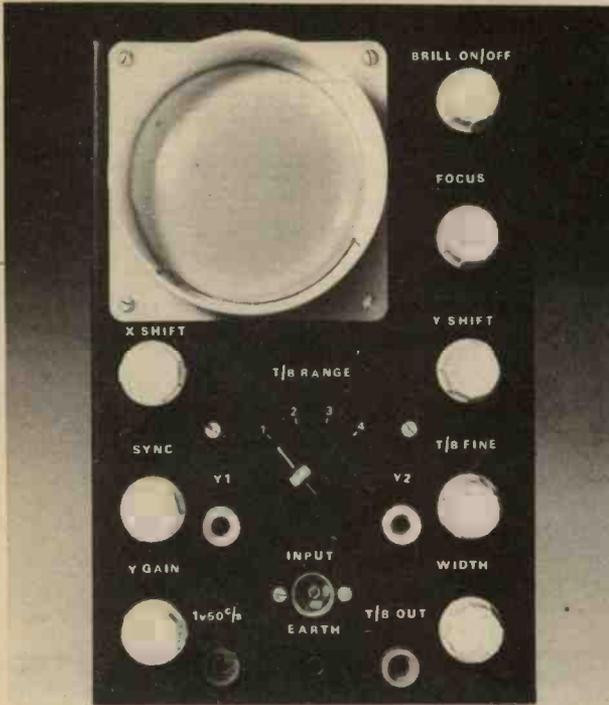


'There's only one way to master electronics... to see what is going on and learn by doing.'

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

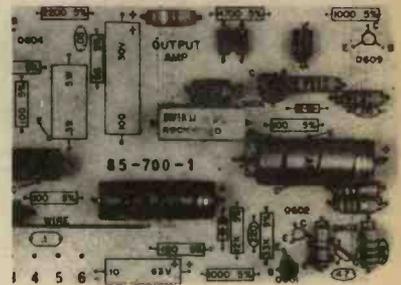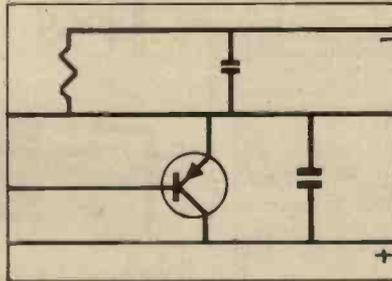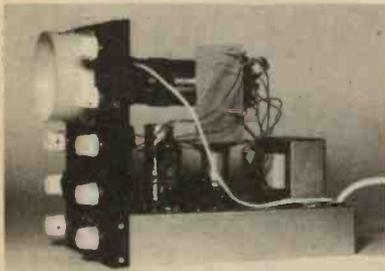All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

FREE GIFT



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronics School,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

PEB 6/7

B. BAMBER ELECTRONICS

Dept. PE, 5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

RED LEDs (Min. type) 5 for 70p.
VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6-80 each. Brand New.
FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK, S.A.E. FOR LIST.

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.
Type S (1/4in. square, dummy type).
Type SA 20 to 30MHz (when 33pf fitted in parallel).
Type SB 35 to 50MHz (with link winding).
Type SC 70 to 100MHz (with link winding).
Type SD 135 to 175MHz (with link winding).
Type M (1in. 1/4in. square types).
Type MA 19 to 28MHz (when 33pf fitted in parallel).
Type MB 22 to 32MHz (when 33pf fitted in parallel).
Type MC 25 to 35MHz (when 33pf fitted in parallel).
Type MD 38 to 50MHz (when 33pf fitted in parallel).
Type ME 45 to 60MHz (when 33pf fitted in parallel).
Type MF 100 to 200MHz (without slug) when 0 to 30pf variable fitted in parallel.
All the above coils available in packs of five only (same type) at 50p per pack of 5.

PLASTIC PROJECT BOXES with screw on lids (in Black ABS) with brass fixings.
TYPE N81 approx. 3in. x 2 1/2in. x 1 1/2in. 40p each.
TYPE N82 approx. 3 1/2in. x 2 1/2in. x 1 1/2in. 60p each.
TYPE N83 approx. 4 1/2in. x 3 1/2in. x 1 1/2in. 60p each.

MULLARD 85A2 85V STABILIZER VALVES (Brand New) 70p each or 2 for £1-20.

TO3 transistor insulator sets, 10 for 50p.

2N3055 type Transistors, O.K., but unmarked, 5 for £1.

110V NEONS, SCREW-IN-TYPE, 4 for 50p.

4MHz XTAL PACKS (10 assorted xtals between 4MHz and 5MHz), our selection only, £1 Pack.

MINIATURE PLIERS. High quality "Crescent", made in USA. £4-35 +VAT (38p).

SIDE CUTTERS. High quality, £3-70 + VAT 30p.

MAINS ISOLATION TRANSFORMERS. Tapped mains input 240V at 3A + 12V at 500mA output. New, boxed, made by Gardners, £12.

GARRARD 9V DC MINIATURE MOTORS. Type 318M, 3200 RPM governed, size approx. 1 1/4in. dia. x 1 1/2in. high, with 2mm spindle. Brand New. 60p each or 2 for £1.

SILICON HIGH VOLTAGE RECTIFIER STICKS. BY185 (new) 35kV 2.5mA £1 each. BY140 (test-equip) 12kV 2.5mA 45p each.

VARIABLE STABILISED POWER SUPPLY. mains input. 0-24V output, stabilised and current limiting at 500mA + 32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4in. complete with external 5K0 3-turn pot for voltage control. Connection data supplied. £7.

14 DIL REED RELAYS. 5 to 12V DC, 450 ohm coil. Designed to work directly from TTL Logic. Single Pole Change over. Contact ratings 28V 1/4A 3W. £1-75 each.

SPECIAL OFFER... STARPHONE HIGH BAND RF PCB BOARDS. with conversion data for making into a good 2M Converter. (All that is needed: 1 xal, 7 caps, 2 resistors, and 9V DC). PCB contains 2 Dual gate Mos Fet RF stages (3N140), Diode ring mixer, 3 stage Osc Multiplier. All on one PCB, approx. size 6" x 1 1/2", ext. connections, 9V DC supply, AGC (can be left fixed bias, or RF gain control) Ant. input, IF output (works from a few MHz to over 30MHz). All Brand New. £6-50 each, while stocks last.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 80p.
PNP audio type TO5 Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3819 Fet, 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 NPN SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.), approx. 1/2in. x 1 1/2in., 3 for 50p.

PERSPEX TUNER PANELS for FM Band 2 tuner) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/4in. x 1 1/2in., 2 for 35p.

PLUGS AND SOCKETS
N-Type Plugs 50 ohm, 60p each, 3 for £1-50.
PL259 Plugs (PTFE), brand new, packed with reducers, 65p or 5 for £3.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 50p each or 5 for £2-25.

SOLDER SUCKERS (Plunger Type), Standard Model, £4-50, Skirted Model, £4-95, Spare Nozzles 60p each.

WELLER SOLDERING IRONS
EXPERT. Built-in-spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN, £6-80 + VAT (54p).
EXPERT SOLDER GUN KIT (spare bits case, etc.), £9-80 +VAT (78p).

SPARE BITS, PAIR, 30p + VAT (2p).
MARKSMAN SOLDERING IRONS
SP15D 15W £3 + VAT (24p).
SP25D 25W £3 + VAT (24p).
SP25DK 25W + bits, etc. kit £3-85 + VAT (31p).
SP40D 40W £3-64 + VAT (28p).
BENCH STAND with spring Marksmen Irons, £2-22 + VAT (18p).

SPARE BITS
MT8 for 15W, 48p + VAT (4p).
MT4 for 25W, 38p + VAT (3p).
MT10 for 40W, 42p + VAT (3p).

TEMPERATURE CONTROLLED IRON. Temperature controlled Iron and PSU. £27 + VAT (£2-16).

SPARE TIPS
Type CC single flat, Type K double flat fine tip, Type P, very fine tip. £1 each + VAT (6p).

MOST SPARES AVAILABLE.

MULTICORE SOLDER
Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).
Size CISAV18 Savbit 18 s.w.g., 56p + VAT (4p).
Size 12 Savbit 18 s.w.g. on plastic reel £1-80 + VAT (15p).
1 Kg. (1-1lb) 60 x 40, 20 s.w.g. on plastic reel £3.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALL-SOL ALUMINIUM SOLDER (made by Mullard). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Large reel £2-75.

VARICAP TUNERS Mullard Type ELC1043/05. Brand New. £4-40 + 12 1/2% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Saebron Manufacture. Approx. 100. £1-60 per pack + 12 1/2% VAT.

Mobile Converters. 24V DC input 13-8V at approx. 3-4A DC output, fully stabilised. £3-80 each (ideal for running 12V car radio from 24V lorry battery).

We now stock Spirax Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

TWIN I.F. CANS, approx. 1in. x 1/2in. x 1in. high, around 3-5-6MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Duobiler Electrolytics 50µF, 450V, 2 for 50p.
Duobiler Electrolytics, 100µF, 275V, 2 for 50p.
Plessey Electrolytics, 470µF, 63V, 3 for 50p.
TCC Electrolytics, 1000µF, 30V, 3 for 60p.
Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).

Duobiler Electrolytics, 5000µF, 35V, 50p each.
Duobiler Electrolytics, 5000µF, 50V, 60p each.
ITT Electrolytics, 6800µF, 28V, high grade, screw terminals, with mounting clips, 50p each.
Plessey Electrolytics, 10,000µF at 63V, 75p each.
Plessey Cathodray Capacitors, 0-0-4µF at 12-5kV DC. Screw terminals, £1-50 each.
PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 5 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p.
Please add 12 1/2% VAT.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE WITH ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.

Doram kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

ELECTRONIC CAR IGNITION

£9.95 + VAT

£9.95 + 8% VAT
(Order code 997-005) Subject to availability

Avoid difficulty in starting your car on cold mornings with the Doram C.D. Ignition Unit. The complete kit incorporates features such as single switch reversion to the standard ignition system for servicing etc. and also an immobilisation facility. Improved performance and fuel consumption, along with reduced points erosion and longer plug life makes this unit a must for any 12V neg. earth car.

O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).

DORAM ELECTRONICS LTD.,
P.O. BOX TR8, WELLINGTON RD. IND. EST., LEEDS LS12 2UF.

An Electrocomponents Group Company

Test Equipment

Multimeters

The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment.

NAME _____

ADDRESS _____

Eagle International, Precision Centre, Heather Park Drive,
Wembley HA0 1SU Tel: (01)-902 8832



Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Solar Heating

Sir—With reference to the article "Electronic Control Unit for Solar Heating Systems" by G. I. Williams (PRACTICAL ELECTRONICS, February 1977), there are a number of points which I would like to make.

1. Under no circumstances use expanded polystyrene insulation in the collector. It will either melt or burst into flames, as temperatures inside a properly built collector can exceed 100°C.

2. Under no circumstances use a polythene cover, which will degrade due to the action of ultra-violet within about two months. Also, it will stretch when hot, touch the metal collector and melt. Planning permission is required for solar panels, and this will not be granted for sub-standard designs. If too many such designs appear, much of the hard work put in by manufacturers in overcoming the opposition of planning authorities will be undone.

3. In the arrangement of Fig. 1, an expansion tank should be included on the solar circuit.

4. In practice it is better to have a pump running time of seconds rather than minutes. Consider for example early morning; the collector heats up just enough to operate the pump, but the water in the pipework is usually very cold and will chill the collector, in theory sufficiently to switch off the pump.

However, on a nine-minute cycle, warm water will be drawn from the solar tank, passed through the collector where it will most likely be cooled by radiation to the sky, and returned to the tank to chill the water.

5. The thermal mass of the thermistors embedded in Araldite and copper tube will be so high that the response time will be very poor. I have found it to be very effective to Araldite the thermistors directly onto the back of the collector and tank.

D. D. Aylen-Baker,
Slough.

Sir—In his article on Solar Heating Controls, Mr. G. I. Williams states that the collector should be installed at an angle of 30° to the horizontal.

None of the other books on the subject which I have read agree with

each other as to any precise angle, but all seem to favour one at least twice that recommended by Mr. Williams.

To quote just one reference, *McLaughlin House of the Future* (TV Publications), "Taking the average elevation of the sun at different seasons and times of the day, the absorption of heat is most efficient if the collector is set up at an angle of $L + 13\frac{1}{2}^\circ$ to the horizontal, where L is the latitude in degrees of the site." This gives an angle of $65\frac{1}{2}^\circ$ to the horizontal for Bedford, for example.

K. J. Wilkinson,
Farnborough,
Hants.

The Author replies

Mr. Aylen-Baker is quite right to point out that polystyrene is a fire hazard. However, it is very debatable whether a hazard exists in this application. As far as I can ascertain it will not spontaneously ignite, though it will soften at around 104°C. Readers, if worried, may like to use alternative insulation.

I agree that glass is preferable to polythene. Some experimenters prefer glass with a low iron content, which is claimed to improve collector efficiency by about 10 per cent. A further improvement can be achieved by the use of a special black paint on the collectors, though this does not seem to be available on the retail market.

The position with regard to planning permission is confused. Some local authorities seem to require it, others I am told do not.

Readers who construct the control unit may wish to make R4 variable as suggested in the final paragraph, allowing the operate time to be shortened. Greater relay contact wear will result if the operate time is in seconds rather than minutes as Mr. Aylen-Baker suggests. Solid-state switching could be used instead of the relay, but this would make the unit less versatile.

The measured response time of the completed thermistor probes (0–100 per cent, in water) is 15 seconds for a 4°C change in temperature, the thermal conductivity of copper and Araldite being quite good.

In reply to Mr. Wilkinson, the optimum angle of the solar collector depends upon the time of year and time of day at which one wishes the collector to be most efficient. In *The Survival Handbook* by Michael Allenby (Pan Books), an angle of 30°–35° to the horizontal is quoted as being optimal for the six weeks of summer sun. I am of the opinion that October – March collection would be improved by a further 5° of inclination, without drastically degrading the summer performance.

Bright Ideas

Sir—Two small simple construction tips which may be of interest to your readers.

A "third hand" of a limited but convenient sort can be devised for use when soldering circuit boards by wrapping a broad elastic band several times round the workpiece. This acts as a "tyre" which holds the work to the table or bench by limiting the tendency for the work to skate around.

Cork tiles may be epoxied to metal chassis sides to provide an attractive finish, or to the bottom of a chassis in place of commercially available feet.

R. T. Third,
Aberdeenshire.


Simple Drilling

Sir—When designing my own printed circuit boards, in particular those which include integrated circuits, I always found it very difficult to drill holes at exactly 0.1in spacing and to keep the holes in a straight line.


However, I came up with this solution. By Sellotaping a piece of 0.1in Veroboard to the circuit board the holes in the Veroboard become an excellent guide for the drill, resulting in perfectly spaced holes.

It is a simple idea, but a very effective one.

J. M. Hayes,
Cononley.

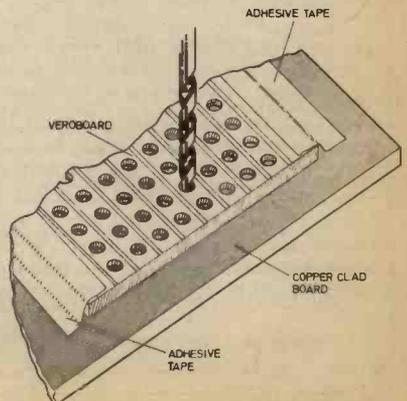

Handling

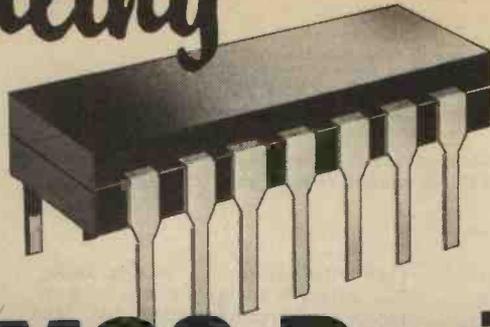

CMOS Devices

By L. J. Gallace & H. L. Pujol*

ALL metal-oxide semiconductor devices are susceptible to damage by electrostatic discharge of energy between any two pins. The gate input, for example, is equivalent to a small very low leakage capacitor which can be charged to a high voltage. The dielectric breakdown voltage is normally of the order of 80V, therefore, any discharge above this level could damage the gate oxide and result in a high leakage input.

Fig. 1 shows the standard RCA protection network incorporated in all CD4000A-series and some CD4000B-series COS/MOS integrated circuits. Diode D1 is a distributed resistor-diode network made up of $p+$ to $n-$ substrate material and having a voltage breakdown in the range of 30–50V. Diode D2 is a separate built-in diode of $n+$ to $p-$ well material and having breakdown in the range of 30–40V. This network can protect the gate oxide against electrostatic discharges of up to 1kV (worst case).

Fig. 2 shows an improved protection network used on new RCA COS/MOS devices which increases the worst-case protection to 4kV.

Fig. 3 shows the equivalent "body discharge" circuit used at RCA during all static test measurements. Improved protection can be obtained by adding series resistors or RC networks at the CMOS device inputs. In addition, Zener diodes at the output pins can clamp the voltage to safe levels. The Zener value should be above the expected maximum regulation excursion, but should not exceed 15V.

Operation above maximum ratings can force CMOS devices into a $p-n-p-n$ s.c.r. "latch up" mechanism which can be destructive. Care should be taken to suppress any transients and avoid any large loads during operation near the maximum rating.

"Latch-up" is considered to be the creation of a low-resistance path between the power supply and earth on a circuit during an electrical pulse, which then remains a low-resistance path after the pulse. In CMOS circuits, several parasitic bipolar transistors exist, as shown in Fig. 4.

The $p-n-p$ transistor is a wide-base lateral structure whose β is a function of device geometry, and is

normally less than 0.2. The conditions for s.c.r. turn-on are as follows:

- (1) $\beta_{n-p-n} \times \beta_{p-n-p} > 1$
- (2) The lateral $p-n-p$ and vertical $n-p-n$ base emitter junctions are forward biased.
- (3) The bias circuit which applies power to V_{DD} and to the input must be capable of supplying current equal to the holding current of potential s.c.r.s.

Fig. 5 shows the equivalent circuit for the s.c.r. structure present in CMOS circuits. Fig. 6 shows a curve of I_{DD} as a function of V_{DD} , which illustrates the effect of secondary breakdown and s.c.r. latch-up.

Table 1 shows typical values of breakdown voltage and sustaining voltage and current for COS/MOS A-series and B-series devices. The table shows that B-series devices are much harder to latch than A-series types because of the higher breakdown voltage.

Table 1

	A Series	B Series
$V_{BKDNmin}$	17V	25V
V_{sus}	15V	22V
I_{sus}	Type-Dependent 2–40mA	50–100mA

Observation of the following operating rules will enhance the life of any CMOS system:

- (1) When CMOS devices interface with external signal sources, the CMOS power supply should be turned on before the inputs are turned on. Similarly, the input should be turned off before the CMOS power supply is turned off. (In other words, $V_{SS} < V_{IN} < V_{DD}$.) This rule will avoid input-diode damage.
- (2) In the case of CD4009A and CD4010A devices, the diode between V_{CC} (pin 1) and V_{DD} (pin 16) should not be forward-biased. V_{DD} should always be greater than V_{CC} . This rule is especially important during power sequencing.
- (3) When series resistors are used on power supplies, it is wise to avoid biasing inputs to

*RCA Solid State

the non-limited side of the supply. This action will eliminate the potential hazard of forward biasing the input diodes.

- (4) The power-supply polarity should not be reversed (i.e. $V_{DD} - V_{SS} > -0.5V$). Such reversal could over-dissipate the substrate diode.
- (5) All inputs should be terminated. A floating input can force the CMOS inverter into a linear mode and cause faulty operation as a result of the large current.

- (6) When CMOS devices are interfaced in printed circuit cards, a pull-up or pull-down resistor should always be used if there is a possibility of an input becoming open.
- (7) CMOS outputs should not be "wire-OR-ed". Instead 3-state outputs or transmission gates should be used.
- (8) Output loads should not be returned to voltages greater than V_{DD} nor less than V_{SS} , otherwise the output diodes will be turned on. ★

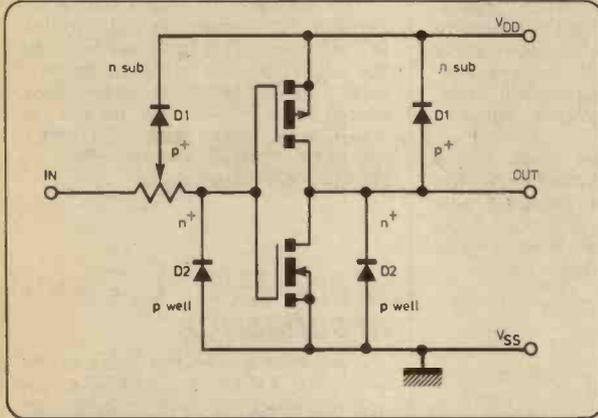


Fig. 1. Standard RCA protection network; used on all CD4000A and some CD4000B series devices

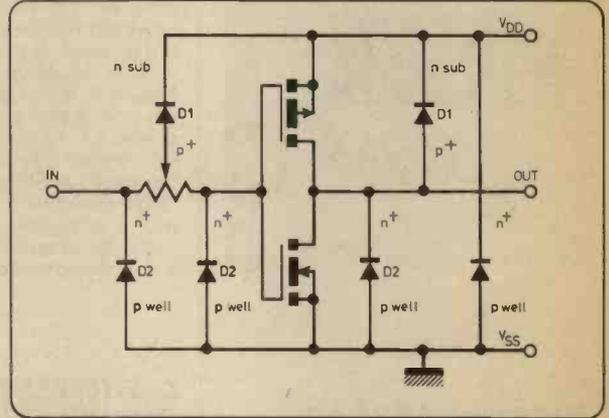


Fig. 2. Improved protection network used on new RCA CMOS devices

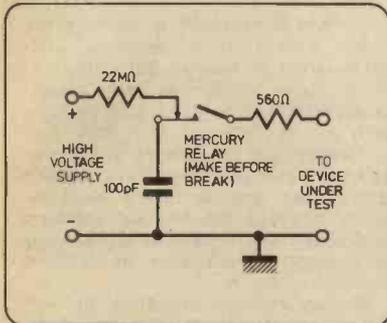


Fig. 3. Equivalent "body discharge" circuit used at RCA during all static test measurements

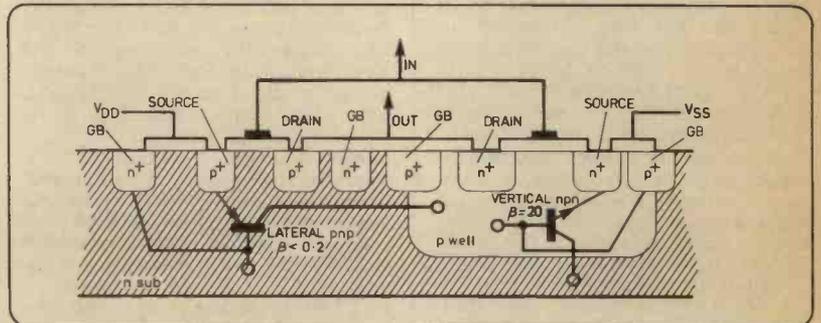


Fig. 4. Parasitic bipolar transistors in CMOS circuits

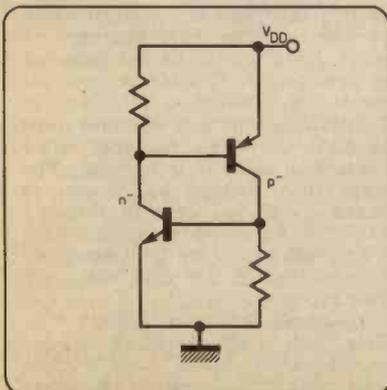


Fig. 5. Equivalent circuit for the s.c.r. structure present in CMOS circuits


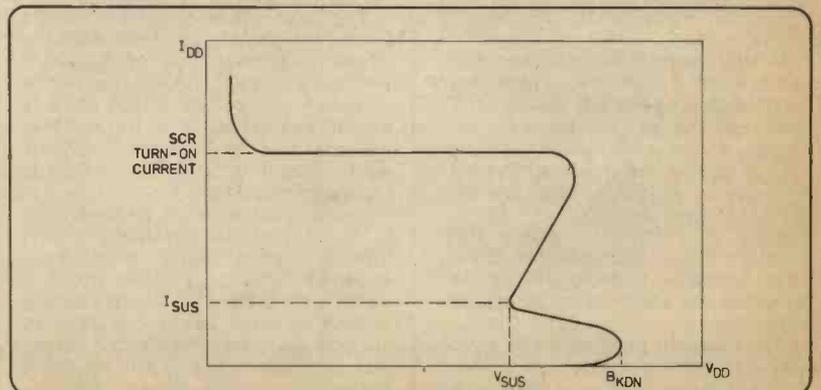


Fig. 6. Curve illustrating effect of secondary breakdown and s.c.r. latch-up

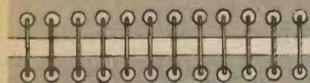

INDUSTRY NOTEBOOK

By Nexus

LOOKING ABROAD

Unstoppable Racal, after three months of cliff-hanging negotiations, finally won the battle for control of the Milgo Corporation. This single move has not only immensely increased Racal's stake in data communications with its great growth prospects but has also considerably strengthened Racal's status as a budding multinational organisation.

Bracknell-based Racal and Miami-based Milgo have had a long relationship through Racal-Milgo owned 50/50 whereby Racal-Milgo had marketing rights throughout the world except North America for Milgo products. Now Racal has full control of Milgo manufacturing as well. Previously Racal had only one manufacturing plant in the USA, that of the wholly-owned subsidiary Racal Communications Inc. at Rockville, Maryland, which makes top level communications receivers mainly used for surveillance by the US Government.

With stronger direct presence in the USA, Racal is now bidding for a share in re-equipping the US forces with a new generation of tactical field radios, a product in which Racal has proved successful in 130 armies with a range of products from low-cost simple-to-operate manpacks for the armies of emergent nations right through to the sophisticated Clansman equipment designed for the British Army and now in full production.

The US Army programme for which Racal is making a bid goes beyond anything Racal or anyone else has so far achieved in technology. But Racal could win in competition with US and other British suppliers like

Plessey and Marconi who are also expected to compete. For this programme the US authorities have waived the "Buy American" clause and will accept bids from the UK on equal terms.

Racal has teamed up with RCA Government Communications Systems at Camden, New Jersey, as a support company adding expertise on electronic counter-measures to Racal's proven performance on design, manufacture and delivery-on-time of tactical manpacks. Racal, however, will be the lead company of the two and, if the design contract is won, it could lead to huge manufacturing follow-on which will dwarf any of Racal's previous success stories.

It seems likely that Racal would have been bidding whether or not the Milgo deal had materialised but now with a strengthened American base and a tie-in with RCA, Racal clearly has a strengthened position.

DISHONESTY DIVIDENDS

The dividends coming to the electronics industry through criminal activities continue to increase as crime itself increases. And the dividends come not only from trying to counter the activities of the hardened wrong-doer. The "honest" citizen is not averse to a little fiddling, especially against authority, if he thinks he can get away with it.

A £1.8 million development contract for a prototype automated ticket inspection and barrier control system for British Rail has just been awarded to EMI Electronics with GEC-Elliott Automation as sub-contractors. The idea is dressed up as a help to passengers, saving time queuing up at ticket offices and at platform entrances and "allowing staff to provide a better service". Actually it is to plug the leak of £6 million a year estimated to be lost through dishonest commuters.

The pilot scheme will have trials for six months at five stations on the Waterloo-Staines line of Southern Region. If successful it is planned to establish the system at 600 stations on the busiest parts of the national network and the contract will be worth about £20 million. Further contracts could follow.

The system appears to be similar to that used on London's underground system using magnetically encoded tickets. I only hope it works a lot better. If you are carrying parcels in both hands the barriers are difficult to negotiate and it seems that an enormous staff of ticket collectors is still there, whether necessary or not is difficult to judge.

Petty pilfering is always a problem but one case recently reported was

not so petty. Perhaps it could only have happened in America but WOR, one of New York's broadcast stations, suffered the loss of 20,000 ft of above-ground copper wire earth radials from the aerial system. It seems incredible that such a quantity could be lifted without attracting attention and one wonders whether the thieves (there surely must have been more than one) sold it as having "fallen off the back of a lorry".

The dividend in this case didn't come to the electronics industry but to the ironmongery business because the whole lot was replaced by best quality galvanised steel barbed wire, much more difficult to handle by would-be pilferers and, apparently, without noticeably adverse effect on radiation efficiency.

RESURGENCE

After what seems like years in the doldrums, TV sales are showing an upturn, much to the delight of dealers, set manufacturers and the big component suppliers. Colour TV deliveries last January were up 30 per cent on the January 1976 figure.

Mullard is currently promoting the 20AX colour tube, already well-established in Europe but comparatively new to British set manufacturers. It is a fast warm-up tube with an in-line gun assembly and vertical striped phosphors which give superior colour registration. Major British set manufacturers have already adopted the Mullard solution and tubes and neckwear are already in quantity production at Mullard plants in the UK.

Mullard is also pressing on with Teletext components including dedicated i.c.s and remote control i.c.s for TV receivers. Samples of the i.c.s, all in the LSI class, are already with set manufacturers.

Mackintosh Consultants are forecasting 12 million UK Teletext users by 1985 so this new business is worth going for. Mullard is reported as having spent £350,000 on development and production facilities for Teletext i.c.s and this will have risen to £0.5 million by mid-year when production will start in earnest. The Mackintosh forecast, by the way, is based on 85 per cent of Britain's 20 million households having colour TV by 1985 and of the CTV-equipped households, 75 per cent will have Teletext.

Viewdata, accessed through P.O. lines, will have a much slower growth rate because, says Mackintosh, of the rising cost of telephone calls. No further comment is required from me, although I am sorely tempted.

PATENTS REVIEW . . .

TV AERIAL

In BP 1 458 006, Maxview Aerials Limited, of King's Lynn, Norfolk, discloses and claims the fine details of some improvements in aerial construction for TV reception.

The patent recapitulates on the standard techniques adopted, e.g. whereby a folded dipole is placed close to a linear-passive resonator to make the combined assembly resonant over a wider range of frequencies. The dipole-resonator combination is of course usually located between a reflector and sequence of directors.

The new patent claims are two-fold. First, it is proposed that the folded dipole be formed as an isosceles triangle (Fig. 1) with a base formed from the two end sections of the folded rod conductor, merging into two equal sides. This triangular dipole is arranged in a plane parallel to the plane of a resonator member, and within the angle defined between two reflectors.

The base of the isosceles triangle is approximately equal to half the wavelength of the signal to be received, and the included angle between the equal sides is about 90°.

The second aspect of the invention constitutes detailed data on the size and spacing to be adopted

for two forward passive members immediately ahead of the resonator, and twenty director elements mounted in a series ahead of the three members.

Size and spacing details are given for three specific types of aerial: one for reception in Group A (channels 21-34); one for reception in Group B (39-51) and one for reception in Groups C/D (49-68). It is claimed that the use of the isosceles triangle dipole in combination with passive members constructed and spaced exactly as described provides a useful increase in gain or bandwidth or both, in comparison to a similar aerial using a conventional folded dipole.

Also claimed is flatter impedance of the dipole over a wider band width.

MAGNETS

BP 1 457 145

In BP 1 457 145, Hitachi of Tokyo list most of the known permanent magnet alloys consisting of rare earth elements. Also discussed are their advantages (ability to produce an intense magnetic field from a light-weight, small-sized magnet) and their disadvantages (tendency of the magnetic characteristics to change with temperature).

They now claim to have improved the temperature-dependent characteristics of a powerful permanent magnet alloy by substituting part of the light rare earth elements in the alloy with heavy rare earth elements. The light rare earth element exhibiting the best permanent magnetic properties is samarium, which is often alloyed with cobalt.

According to the invention, it is beneficial if some of the samarium is substituted by the heavy rare earth elements, Ho, Er, Dy and Tb. Following such substitution, the reversible magnetisation temperature coefficient becomes lower than 0.03% in the temperature range from -50°C to +100°C. Other substitutions, for instance by Ce or Ce mischmetal, provide similarly beneficial results, at less cost. Indeed, good results are claimed up to 200°C.


Chemical details for the preparation of various specific magnetic mixes are given. For instance, a useful alloy consisting of 32.75% Sm, 3.99% Ho and 63.26% Co is prepared by arc melting and crushing to a fine powder under a pressure of 10 tons/centimetre² in an intense magnetic field. Further sintering and cooling produces a magnetic material with impressive characteristics and resistance to temperature effects.

IN BRIEF


BP 1 459 235—Matsushita Electric Industrial Co Ltd: *Switching Circuit*. Contains full circuit details for a touch switch giving mains control. Touching the switch alters the amplitude (rather than the frequency) of an oscillator output. The amplitude changes are detected and used as trigger pulses to govern the main control switch.

BP 1 460 003—EMI Ltd: *Television Game Apparatus*. A modification of the now familiar TV game. In a race, there is penalty override of the operator manual control. For instance, a blip on the screen depicting a car has its movement slowed down beyond the operator's control if it leaves an area depicting a race track.

BP 1 458 006

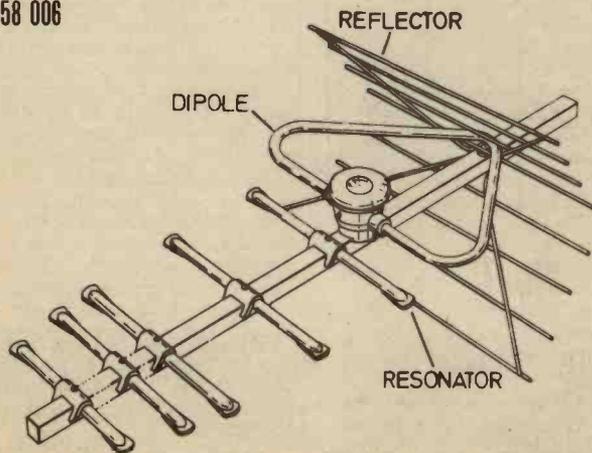

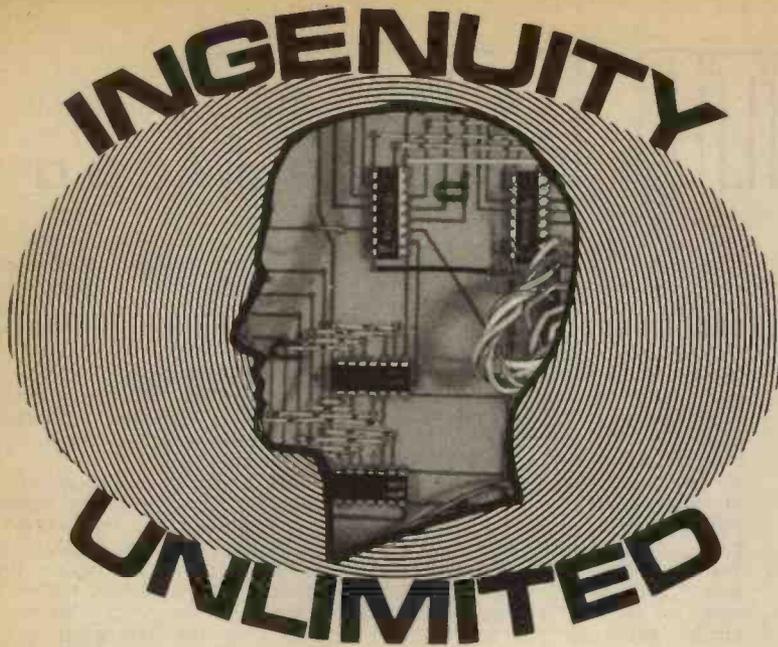Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each



A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.



NIGHT LIGHT LATCH

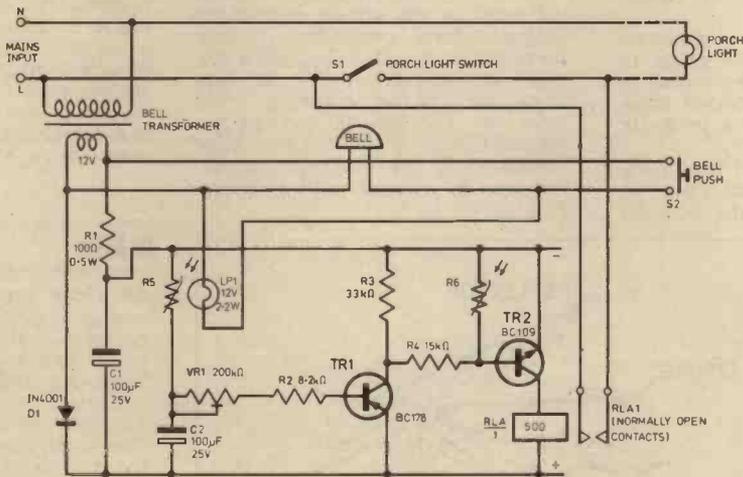


Fig. 1

THIS is a design for lighting a porch light from outside by using the bell push. This is particularly useful for when one is trying to find the keyhole in the dark. After a preset time the light switches off.

The porch light is lit from outside by pressing S2 which also rings the bell and LP1 lights lowering the

resistance of the l.d.r. R5 which in turn causes TR1/TR2 to turn on and hence the relay.

With RLA1 contacts closed the porch light comes on for a period determined by C2.

R6 acts as an effective short to TR2 b/e during the day so preventing the porch light being switched on.

VR1 varies the holding time of the relay between about 0.25—2 minutes.

LP1 and R5 should be juxtaposed and contained in a sealed, opaque plastic tube.

R. N. Johnson,
Coulsdon,
Surrey.

FLUORESCENT LIGHT INVERTOR

THE Fluorescent Light Invertor of P.E. July, 1976, incorporates no forward biasing for the transistors. I found this circuit reluctant to oscillate, and so produced an invertor with forward biasing, which oscillated readily (see Fig. 1), the circuit being a variant of the invertor of the P.E. Scorpio electronic ignition system.

The transformer primary is bifilar wound on a television e.h.t. transformer core, as in the original Fluorescent Light Invertor. The two 8 turn coils are wound first, and then covered by a layer of insulating tape. Next, the feedback coils are wound on top, and covered with tape. The beginning of each winding in Fig. 1 is indicated by a spot.

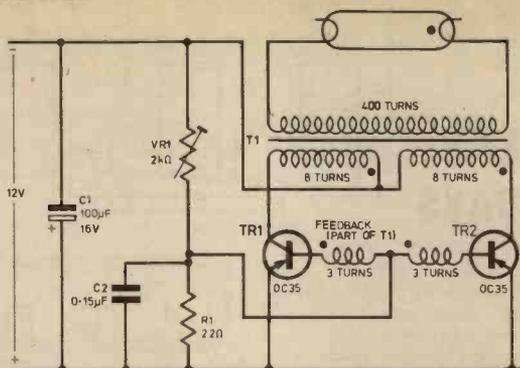


Fig. 1

Potentiometer VR1 determines the output power. This circuit can accommodate *npn* or *pnp* transis-

tors simply by changing the polarity of the supply and capacitor C1.

I. P. Kemp, Cowley, Oxford.

"TRIMPHONE" WARBLER

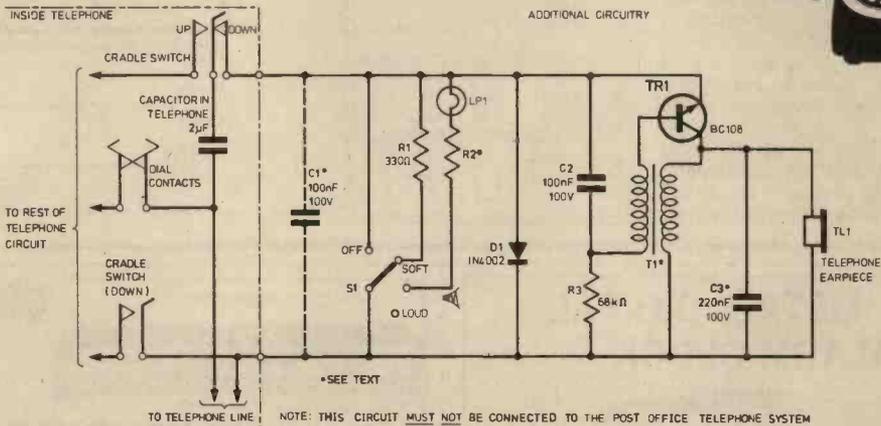


Fig. 1

MANY of the surplus telephones available through the second-hand market are sold without bells. The circuit in Fig. 1 will produce a "warbling ring" rather like a Trimphone, and can directly replace a conventional telephone bell, therefore being suitable for both these phones, and for situations where a different ringing sound is required to differentiate between an internal or Post Office telephone system.

The bell ringing current which alternates at about 17-25Hz, is halfwave rectified by D1 and then supplied to a simple oscillator formed by TR1, C2, C3, R3 and T1. This in turn drives a telephone earpiece (not the same one as in the handset). The oscillator is thus modulated at the ringing current frequency, producing the warbling tone. The oscillator circuit will also work on a d.c. supply, but of course the warbling effect will be lost.

To alter the volume, a shunt is

placed across the oscillator; the individual shunts being selected by switch S1. If the shunt selected is LP1 with R2, the bulb will take a few seconds to warm up, and so its resistance will slowly rise, giving a crescendo effect. The component values are not very critical, but some experimentation may be needed for optimum results.

The following points may be useful: T1 is a transistor radio type output transformer, tuned by C3, and so the frequency of oscillation may be adjusted by altering the value of C3. A frequency of around 2kHz is most suitable, as both the earpiece and ear are most sensitive at about this frequency. The connections to one side of the transformer may need reversing to produce oscillation. The combined resistance of R2 and LP1 should be around 200 ohms when cold, rising to about 500 ohms after approximately 10-20 seconds.

If an extension warbler is required, it will probably be necessary to include C1, and possibly also add series or parallel resistors to the circuit, so that both ring equally loud. Extension bells are usually connected in series to overcome this problem.

The changeover cradle switch can be replaced by a "make only" switch, with the ringer permanently connected across the line, provided that the line polarity during speech is always such as to bias the oscillator off. In this case the diode D1 must be omitted, and if d.c. is used for ringing a polarity reversal will turn the ringer off.

This circuit may not be connected to the Post Office telephone network, and should only be used on private systems.

A. J. V. and J. M. Yeomans,
Banstead,
Surrey.






SEVEN SEGMENT WEEKDAYS

The circuit in Fig. 1 provides a day of the week reading for digital clocks using three seven segment displays, and minimal circuitry. Although seven segment displays do not lend themselves to alphabetic display, the symbols produced are readable.

The circuit requires one pulse per 24 hours, but if one pulse per hour only is available, this can be divided down using a 7492 (divide by twelve), and the unused half of the second 7473 (divide by two).

The first half of the circuit consists of three JK flip-flops, being a counter which counts from 1 to 7, resetting to 1 again. This is decoded for the seven segment displays by the second part of the circuit. In order to keep costs low, only NAND and INVERT gates are used.

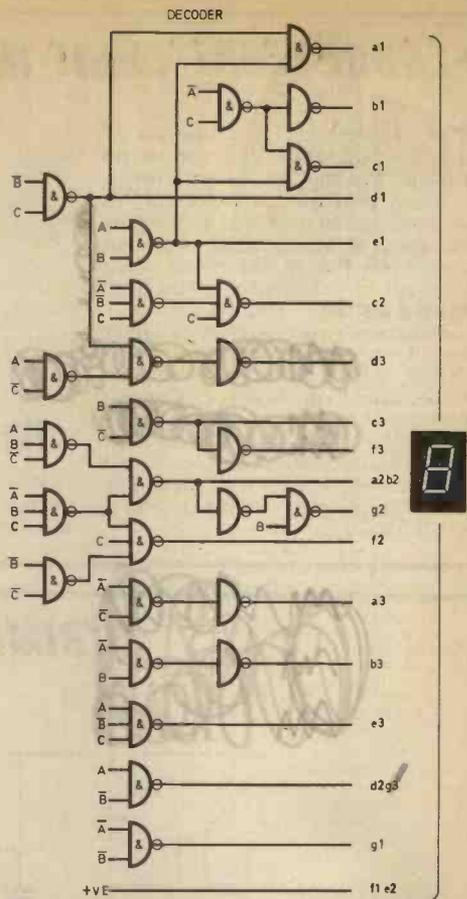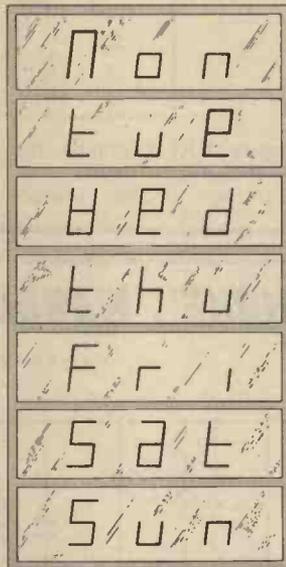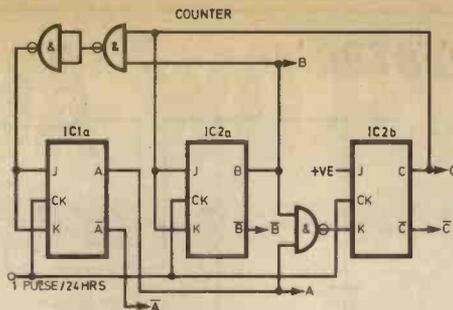The actual type of display and associated drive circuitry will depend upon the existing design of the clock. H. Pyman, Romford, Essex.



THE 'METAC' DIGITAL ALARM CLOCK



- Choice of Bright Orange 12 Hour Display, or Soft Green 24 Hour Display ● 24 Hour Alarm
- 10 Minute Repetition ● Alarm Set Indicator
- Accurate Silent Timekeeping ● British Designed and Built

SAME DAY DISPATCH orders received before 2 pm are posted same day

£12.99 + £1.04 VAT

Cash, Cheque or Postal Order or If you wish to use Barclaycard or Access, simply quote name, address and card number when ordering

Metac-Electronics and Time Centre



DAVENTRY
67 High Street
Daventry, Northants
Tel. (032-72) 76545

UXBRIDGE
3 The New Arcade,
High Street, Uxbridge,
Middx. Tel. (0895) 56961



Designer approved



STEREO TUNER

- Complete set of semiconductors £4.99
- Mullard LP1186 tuner head £7.75
- High quality glass fibre P.C.B. £2.45

ORION STEREO AMPLIFIER

- Complete set of semiconductors £9.40
- High quality glass fibre P.C.B. £2.99

Both the above PCBs are printed with component locations

PE DIGITAL VOLTMETER

ZNA116 *£6.00 with circuits and data

Complete set of all semiconductors for the P.E. DVM including I.C.'s, transistors, diodes, displays, regulator, etc. £20.50*

Set of two professional grade glass fibre P.C.B.'s printed with component locations £3.40*

Complete set of resistors, incl. attenuator resistors £1.00*

Complete set of capacitors incl. 2200uF power supply £1.60*

ZN424 E1, ZN423 E1, ZN744* E1-75, 78M05 regulator* 85p, ZN1034E* E1-80, ZN1040E* universal count/display i.c., with data £7.50

FERRANTI SEMICONDUCTORS—WE ARE THE EXPERTS!

BZV zeners 10p	BFS96 14p	ZTX107 11p	ZTX239 10p	MOTOROLA	
All types	MS4A* E1-35	ZTX108 9p	ZTX320 16p	BD695*	E1-14
BC415P 17p	ZS170 13p	ZTX109 11p	ZTX384 17p	BD708*	E1-28
BFS60 15p	ZS178 54p	ZTX212 15p	ZTX450 16p	MC1310P	E1-60
BFS61 15p	ZS271* 23p	ZTX213 15p	ZTX550 16p	MC1357PQ	E1-65
BFS97 15p	ZTXA20 10p	ZTX214 17p	ZTX4403 16p	SN7566ON	75p

We can supply any FERRANTI semiconductor device. S.A.E. for quotation. ZN1034E* E1-80, ZN1040E* universal count/display i.c., with data £7.50

PE TV SOUND SEPARATOR

Complete set of semiconductors £2.30, High quality glass fibre p.c.b. £1 POSTAGE AND PACKING 15p per order. Orders over £5 post free. All devices are top grade, brand new and to full manufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list. Prices do not include VAT—add 8% to items marked*, and 12½% to all others

DAVIAN ELECTRONICS (MAIL ORDER ONLY)
13 Deepdale Avenue, Royton, Oldham OL2 6XD



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£13-00
Baker Group 35, 3, 8 or 15 ohm	£14-50
Baker Group 50/12 8 or 15 ohm	£21-00
Baker Group 50/15 8 or 15 ohm	£25-75
Baker Deluxe 124, 8 or 15 ohm	£17-50
Baker Major 3, 8 or 15 ohm	£15-00
Baker Superb 8 or 15 ohm	£22-50
Baker Regent 12in 8 or 15 ohm	£12-50
Baker Auditorium 12in 8 or 15 ohm	£21-00
Baker Auditorium 15in 8 or 15 ohm	£25-75
Castle 8RS/DD 4 or 8 ohm	£9-95
Celestion G12M 8 or 15 ohm	£12-95
Celestion G12H 8 or 15 ohm	£15-95
Celestion G12/50 8 or 15 ohm	£18-00
Celestion G12/50TC 8 or 15 ohm	£20-00
Celestion G12/50 2236 w/cone	£18-00
Celestion G12/50 2239 s/cone, alum. dome	£18-50
Celestion G15C 8 or 15 ohm	£26-95
Celestion G18C 8 or 15 ohm	£39-95
Celestion HF1300 8 or 15 ohm	£7-50
Celestion HF2000 8 ohm	£8-55
Celestion HF4000 8 or 15 ohm	£13-50
Coles 4001G	£5-90
Coles 4001K	£5-90
Decca London ribbon horn	£31-50
Decca London CO/1000/8 crossover	£8-95
Decca DK30 ribbon horn	£20-50
Decca CO/1/8 crossover (DK30)	£4-75
EMI 14 x 9in bass 8 ohms, 14A770	£14-95
EMI 8 x 5in, 10W, d/cone, roll surr.	£3-95
EMI 6in d/cone, roll surr., 8 ohm	£3-95
EMI 8in roll surr. bass	£6-75
EMI 5in mid range	£3-50
EIac 59RM 109 (15 ohm), 59RM114 (8 ohm)	£3-50
EIac 6in d/cone, roll surr., 8 ohm	£3-95
EIac 10in 10RM239, 8 ohm	£3-95
Eagle FR4	£8-75
Eagle FR65	£11-95
Eagle FR8	£14-95
Eagle FR10	£18-50
Eagle HT15	£4-50
Eagle HT21	£5-50
Eagle MHT10	£5-25
Eagle FF28 Multicell. horn	£7-50
Fane Pop 15, 16 ohm	£5-75
Fane Pop 33T, 8 or 16 ohm	£9-95
Fane Pop 50, 8 or 16 ohm	£12-50
Fane Pop 55, 8 or 16 ohm	£16-95
Fane Pop 60, 8 or 16 ohm	£19-95
Fane Pop 70, 8 or 16 ohm	£21-75
Fane Pop 100, 8 or 16 ohm	£33-95
Fane Crescendo 12, 8 or 16 ohm	£42-95
Fane Crescendo 12BL, 8 or 16 ohm	£44-95
Fane Crescendo 15/100A, 8 or 16 ohm	£54-95
Fane Crescendo 15/125, 8 or 16 ohm	£64-95

SPEAKERS

Fane Crescendo 18, 8 or 16 ohm	£75-95
Fane 910 Mk II horn	£15-75
Fane 920 Mk II horn	£45-95
Fane HPX1 crossover 200W	£2-50
Fane 13C x 8in, 15W dual cone	£5-50
Fane 801T 8in d/c, roll surr.	£9-50
Gauss 12in	£15-00
Gauss 15in	£139-00
Gauss 18in	£165-00
Goodmans Axent 100	£8-50
Goodmans Audiom 200 8 ohm	£14-95
Goodmans Axiom 402 8 or 15 ohm	£16-00
Goodmans Twinaxiom 8, 8 or 15 ohm	£6-50
Goodmans 8P 8 or 15 ohm	£6-95
Goodmans 10P 8 or 15 ohm	£16-50
Goodmans 12P 8 or 15 ohm	£17-75
Goodmans 12PG 8 or 15 ohm	£18-75
Goodmans 12PD 8 or 15 ohm	£44-00
Goodmans 12AX 8 or 15 ohm	£49-00
Goodmans 15AX 8 or 15 ohm	£24-00
Goodmans 15P 8 or 15 ohm	£39-95
Goodmans 18P 8 or 15 ohm	£16-95
Goodmans Hifax 750P	£4-25
Goodmans 5in midrange 8 ohm	£16-25
Jordan Watts Module, 4, 8 or 15 ohm	£8-50
Kef T27	£10-75
Kef T15	£10-95
Kef B110	£11-95
Kef B200	£24-95
Kef B139	£2-75
Kef DN8	£7-25
Kef DN12	£4-95
Kef DN13 SP1015 or SP1017	£32-00
Lowther PM6	£35-00
Lowther PM6 Mk 1	£48-00
Lowther PM7	£8-25
Peerless KO10DT 4 or 8 ohm	£9-50
Peerless DT10HFC 8 ohm	£10-50
Peerless KO40MRF 8 ohm	£3-75
Peerless MT225HCF 8 ohm	£12-50
Richard Allan HP8B	£8-50
Richard Allan LP8B	£6-25
Richard Allan DT20	£16-95
Richard Allan CN8280	£3-15
Richard Allan CN820	£17-95
Richard Allan Super Disco 60W 12in	£28-50
Richard Allan CG15 15in bass	£13-25
Richard Allan Super Disco 8in 50 watt	£12-95
Richard Allan Super Disco 8in 50 watt	£26-95
Radford BD25	£12-95
Radford MD9	£17-95
Radford MD6	£8-25
Radford TD3	£16-95
Radford Cross Over Network	£78-75
Tannoy 10in Monitor HPD	

Tannoy 12in Monitor HPD	£85-00
Tannoy 15in Monitor HPD	£99-00

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohm	each	£18-00
Fane Mode Dne Mk II 15W	each	£10-35
Fane D40 Disco Kit	each	£19-95
Peerless DIN 20 4 or 8 ohm	each	£15-75
Goodmans Mezzo Twin Kit	pair	£51-95
Helme XLK 30	pair	£21-95
Helme XLK 35	pair	£26-75
Helme XLK 40.	pair	£38-50
Kefkit 1	pair	£59-50
Kefkit III	each	£56-00
Peerless 1060	pair	£61-50
Peerless 1070	each	£54-95
Peerless 1120	each	£61-50
Peerless 2050	pair	£43-95
Peerless 2060	pair	£58-50
Richard Allan Twin assembly	each	£13-95
Richard Allan Triple 8	each	£20-75
Richard Allan Triple 12	each	£25-95
Richard Allan Super Triple	each	£29-50
Richard Allan RA8 Kit	pair	£37-80
Richard Allan RA82 Kit	pair	£59-40
Richard Allan RA82L Kit	pair	£65-70
Wharfedale Denton 2XP kit	pair	£23-25
Wharfedale Linton 3XP kit	pair	£34-25
Wharfedale Glendale 3XP kit	pair	£49-50

HI-FI ON DEMONSTRATION in our showrooms:

Akal, Armstrong, Bowers & Wilkins, Castle, Celestion, Chartwell, Dalestord, Dual, IMF RAM, J.R. Formula 4, Kef, Leak, Linn Sondek, Neal, Ortolon, Pickering, Pioneer, Radford, Richard Allan, Rotel, Sansul, Stanton, Tandberg, Trio, Videotone, Wharfedale, etc.—ask for our Hi-Fi discount price list.

THIS MONTH'S SPECIALS! (Carr. £2-50)

Rotel RA312	£66-00
Sansul 331	£109-00
Trio KR2600	£109-00
Videotone Minimax II	£46-95
Sansul SC2000/2002	£145-00
Pioneer OTF2121	£136-00
Rotel RX152II	£91-00

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

ALL PRICES INCLUDE VAT

(PRICES CORRECT AT 9/3/77)

Send stamp for free 38 page booklet "Choosing a Speaker"

ALL UNITS GUARANTEED NEW AND PERFECT
Carriage and Insurance: Speakers up to 12in 60p;
12in £1; 15in £1.75; 18in £2.50. Kits £1 each (£2 per pair). Tweeters and Crossovers 33p each.

WILMSLOW AUDIO

Dept PE

Loudspeakers, mail order and export:
Swan Works, Bank Square, Wilmslow.

Hi-Fi, Radio and TV: Swift of Wilmslow,
5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi and Accessories: Wilmslow
Audio, 10 Swan Street, Wilmslow,
Cheshire.

Telephone: Loudspeakers, mail order and
export—Wilmslow 29599; Hi-Fi, Radio,
etc.—Wilmslow 26213.

Access and Barclaycard orders accepted by phone

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, Hi-Fi Answers Monitor (Rogers), Hi-Fi News No` Compromise (Frilsby), Hi-Fi News State of the Art, Wireless World Transmission Line (Bailey), Practical Hi-Fi and Audio Monitor (Giles), Practical Hi-Fi and Audio Triangle (Giles), Popular Hi-Fi (Colloms), etc.

On dem. Answers Monitor, State of Art, etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi Answers Monitor, free on request.

P.A. amplifiers, microphones, etc., by Shure, Linear, Eagle, Beyer, AKG, etc.

FREE with orders over £10—"Hi-Fi Loudspeaker Enclosures" book.



TRAMPUS ELECTRONICS LTD




58.60 GROVE RD.
WINDSOR, BERKS.
SL4 1HS.
TEL. 54525

ADD 8% VAT TO PRICES MARKED *
ADD 12% TO ALL OTHER PRICES.
OR AS CURRENT VAT LEGISLATION
SEND C.W.O. (EXCEPT GOV'T DEPT)
POST & PACKING 20P FOR THE U.K.
BARCLAYCARD & ACCESS BY POST
OR £5 MIN ON TELEPHONE ORDERS.
NEW CATALOGUE LIST FREE S.A.E.
MONEY BACK IF NOT SATISFIED.

FAST SERVICE



ON EX-STOCK ITEMS
NORMALLY 24 HOURS

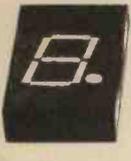

SEVEN SEGMENT LED DISPLAYS
BRIGHT DL707 COM ANODE &
DL704 COM CATH. 0.3" £1*
DL747 0.6" JUMBO CA £1.25*
DIGITAL CLOCK IC 51224 £4*
ZENON STROBE TUBES £4 & 17*

RED LEDS 10P.

RED LEDS 209 STYLE 0.125"
OR 0.2" DIA. NO CLIP 10p*

TIL209 RED LED & CLIP 12p*
BIG 0.2" RED LED & " 14p*
GREEN OR ORANGE LEDS 29p*
ORP12 54p* 2N5777/OC71 34p*

TRAMPUS
THE GREAT
BRITISH
DISTRIBUTOR



INDUSTRIAL, EDUCATIONAL, TRADE
& EXPORT SUPPLIED, SEND FOR
OUR FREE CATALOGUE LIST SAE
MANUFACTURERS EXCESS STOCKS
PURCHASED, DISCOUNTS 10% OFF
100 sp, 15% OFF 1000 sp....

TOP DISCOUNTS.

INTEGRATED CIRCUITS

555 TIMER	34p*	LM380(60745) £1	
556 2 x 555	89p*	LM381 Preamp £2	
703 RF/IF AMP	29p	LM3900 4xOPA 53p*	
709 T099 or DIL26p*		MC1303 2xPre £2	
710 DIL14	35p*	MC1310 stereo £2	
723 Regulator	44p*	MC1312P SQ £1.70	
741 DIL 8pin	21p*	MC1330	75p
741 DIL 14pin	31p*	MC1339 Preamp £2	
741 T099	33p*	MFC4000B 1W 72p	
747 DUAL 741	69p*	MFC6030	£1
748 DIL 8 pin	32p*	NES36 FETOPA £2*	
7805 5V1A+reg £1.35*		NES40 or 550 £2*	
7812 & 7815ea £1.40*		NES55 TIMER 34p*	
76013 6W AF	£1.50	NE556 2x555 90p*	
AVS1224 CLOCK £4 *		NE560/1/2/5/6/7/£13	
CA3046	54p*	SN72741 as 741	
ICL8038 Sigen £4 *		SN76660 IF 74p	
LM300H	£1 *	SN76611 IF £1	
LM301A D11 8	33p*	TBA800 5W AF 84p	
LM309K 5V reg £2 *		TBA810 7W AF 94p	
LM309H T05 can £1*		ZN414 Radio £1.19	
LM318 70vusOPA £3*		NEW 1466/69 £4	

CMOS TTL

4000 14p*	7400 12p*	7490 39p*
4001 15p*	7401 13p*	7491 75p*
4002 16p*	7402 15p*	7492/93 45p*
4007 16p*	7404 19p*	7495/96 72p*
4009 50p*	7408/10 18p*	74100 £1.25*
4011 16p*	7413 29p*	74107 32p*
4012 17p*	7440 16p*	74121 29p*
4049 50p*	7441 71p*	74123 69p*
4069 20p*	7442 72p*	74141 74p*
4501 26p*	7447 79p*	74145 85p*
4511f1.65*	7470/72 27p*	74147 £2.50*
4528 £1*	7473/74 31p*	74151 75p*
4543 £2*	7475/36 35p*	74154 £1.40*
4553 £5*	7486 35p*	74196 £1.50*

DIL SOCKETS PROFESSIONAL QUALITY
8pin, 14pin & 16pin ALL 12p ea *
SOLDERCONS 100 49p* 1000 £3.95*

NEW LOW PRICES.

TRANSISTORS AND DIODES

INS BUSB SET 5p ea*	TIP31/32.50p*
MATCHING 20p Pn*	TIP31c32c68p*
AC127/8 176 15p*	TIP41/42ea 86p*
AD161/162 ea36p*	TIP41c42c£1.50*
BC107 8p*	TIP2955 69p*
BC107B 13p*	TIP3055 65p*
BC108 8p*	TIS43 UJT 26p
BC108B or C 13p*	IN914/4148 4p
BC109 9p*	1N4001/2 4p*
BC109B or C 12p*	1N4004 5p*
BC147/8/9 8p	1N4007 7p*
BC157/8/9 11p	2N706/8 14p*
BC167/8/9 12p	2N2646 UJT 40p*
BC177/8/9 16p	2N2904/5pnp29p*
BC182/3/4a/110p	2N2925 ory 7p*
BC212/3/4a/112p	2N3053 37p*
BCY70/1/2 15p*	2N3055 90w 33p*
BD131/132ea 36p*	2N3055 115w45p*
BFY50/51 15p*	2N3614 T03 £1*
BFY52/53 16p*	2N3702/3/4 10p
BSX 19/20/2113p*	2N3705/6/7 9p
BZY88 ZENER 10p	2N3708/9 9p
C106D SCR 54p*	2N3710/11 15p
MJ2955 T03 99p*	2N3819 & 23e17p
MJE2955 99p*	2N3820 PFTT 40p
MJE3055 65p*	2N3904/5/6/8 15p
OA81/91 5p	2N5457 FET 32p
TIP29 & 30 40p*	BRIDGE1A50 20p*

BARGAIN PAKS FULL SPEC 1lea,

- PAK A: 11 RED LEDS full spec 11*
- PAK B: 5 741C 8 PIN OP AMP £1*
- PAK C: 4 2N3055 £1* D 12 BC109 £1*
- PAK E: 11 BC182 £1 F 11 2N3704 £1*
- PAK G: 7 BFY51 £1* H 8 2N3819 £1*
- PAK J: 6 2N3053 £1* K 4ox1N914 £1
- PAK M: 3 T099 3055 £1* N 25 OA91 £1*
- PAK P: 20 PLASTIC BC109 TYPEPnp £1

10-365PF TUNER, SINGLE GANG FOR
MED/SHORT WAVE, XTAL SET etc £1*
SET3/IF CANS 455/470KHZ TOKO £1*

Full spec devices

DALO pen 75p

PCB ETCH KIT 3 ITEMS £2*
ETCH RESIST PEN 2TIPS 75p*
FEC ETCH PAK TUB 600gm £1*
6x4" SRBP 45p* NYLON F/Gt £1*

SCR AND TRIACS BR100 25p*
TAG 1A400V 50p* 1A600V 65p*
1A50V 37p*, C106D 4A400 80p*
TRIACS: SC148D 10A400V £1*
DISCO TRIAC 15A400V £2*

AUDIBLE WARNING BLEEPER
12V35ma £1.20:30 off £1*

CAPACITORS 22pf -.01 5p
ELECTROLYTIC IN 10 & 25V
1/2/10/50/100 7p 50V 10p
200/500 10p. 1000/25 20p

POTENTIOMETERS A9 etc 20p
PRESETS 6p 3PRESISTORS 2p
HEATSINKS T05 or 18 7p
T03 16p, T03 4" 21inned 50p
DIN: PLUGS all 15p. Sockt 10p
SWITCHES SPST 20p dpdt 29p

GAS DETECTOR TGS 308etc £4*

vero

VERO 0.1" PITCH COPPERCLAD
21"x5" 40p* 31"x3" 45p*
21"x3" 36p* 31"x3" 40p*
31"x7" £2 FACE CUTTER 65p*
DIL BREADBOARD 2"x1" £1 or
6"x4" £2. VERO PINS 36 30p*

BLACK PLASTIC CASES 42mmx.
80x60 50p* 100x75 60p* 99p*
120 70p. DESOLDER BRAID 50p

PLAIN PAK STRIP

Patents applied for

The easiest way to make p/c boards without etching. Plain PAK STRIP is a very thin, flexible p/c board with a self adhesive backing. Cut out shapes with scissors or—lay a sheet on to paxolin—mark out design with a pencil—cut and lift unwanted copper sections with a scalpel or sharp model knife. It's so easy you can make a p/c board in minutes. 6in x 4in sheet of plain Paxolin, 10p. 6in x 4in PAK strip 39p inc. VAT, postage and instructions. S.A.E. for details or ask your local retailer.

Print-A-Kit Electronic Supplies

408 Sharrowvale Road, Sheffield, S11 8ZP

P.E. JOANNA

ELECTRONIC PIANO



ALL PARTS CAN BE SUPPLIED

Keyboard, Keyswitch, P.C.B.s.
Hardware, Semiconductors,
Resistors, Capacitors, Cabinets
Complete kits or easy stages

Send S.A.E. for details

Clef Products

21 Mountfield Road
Bramhall, Stockport, Cheshire SK7 1LY

THE OPEN DOOR TO QUALITY

THE COVER IS BLACK & WHITE

UP-DATED 4th EDITION

ELECTROVALUE
Catalogue No 8

4th ISSUE INCLUDES NEW METERS

as well as new switches and items from advanced opto-electronics to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts continue on many purchases; Semi and Barclaycard orders are accepted.

SEMI-CONDUCTORS • COMPONENTS • ACCESSORIES, ETC.

★ FREE POSTAGE on all C.W.O. mail orders over £2 list value (excluding VAT) in U.K. if under, add 15p handling charge.

144 pages

40p

post paid
inc. refund
voucher
worth 40p

ELECTROVALUE LTD

All communications to Head Office, Dept. PES 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 9HB. Phone Egham 3803. Telex 284475. Hours 9-5.30 daily; 1 pm Sat.
NORTHERN BRANCH: 580 Burnage Lane, Burnage, Manchester M19 1NA. Phone 061-432 4945. Hours 9-5.30 pm; 1 pm Sat.

ELECTRONICS

54 Montagu Street, Kettering, Northants. Phone Kettering 83922
shop open Monday to Saturday 9.00 to 6.00; early closing Thursday 1.00 p.m.

TRANSISTORS AND DIODES

AA117	10	BC556	17	E310	60
AA118	10	BB557	15	E420	180
AA133	10	BC557B	18	E430	120
AA144	10	BC558	15	ER900	30
AA217	30	BC559	20	IRL60	110
AC128	10	BC559C	20	IRL60	30
AC127	10	BCY38	85	MJE340	80
AC128	10	BCY59	27	MJE341	60
AC178	10	BCY70	22	MJE255	180
AC187	10	BCY71	22	MJE3055	110
AC188	10	BCY72	22	MPF102	30
AD149	50	BD106	140	OA47	30
AD161	45	BD131	40	OA90	9
AD162	45	BD132	40	OA91	9
AF114	25	BD133	42	OA200	10
AF115	25	BD135	38	OA202	10
AF116	25	BD136	50	OC28	75
AF117	25	BD137	38	OC35	50
AF118	45	BD138	40	OC44	18
AF238	50	BD139	40	OC45	16
BA127	11	BD140	42	OC71	15
BA145	18	BD181	145	OC171	30
BA148	16	BD240	70	OCPT71	75
BA200	16	BD241	70	TIL77	78
BAV61	28	BD242	75	TIL78	78
BB103	30	BF104	25	TI202A	50
BB104	30	BF167	24	TI32A	55
BB105	37	BF173	24	TI41A	60
BB106	35	BF178	30	TI42A	70
BB109	45	BF180	30	TI440	330
BB110	45	BF180	35	TI441	385
BB113	345	BF181	35	TI442	435
BC107	10	BF182	35	TI445	360
BC107B	13	BF183	30	TI446	415
BC108	10	BF185	45	TI447	495
BC108B	13	BF194	10	TI543	30
BC109	10	BF195	10	TI7X107	10
BC109C	15	BF196	10	TI7X108	10
BC139	27	BF197	10	TI7X109	10
BC140	42	BF198	12	TI7X300	18
BC141	25	BF199	15	TI7X500	15
BC142	25	BF200	30	IN194	5
BC143	25	BF201	30	IN4001	13
BC147	9	BF244	30	IN4002	5
BC147B	13	BF245	30	IN4003	5
BC148	9	BF254	30	IN4004	9
BC149	10	BF255	30	IN4005	9
BC157	10	BF282	40	IN4006	7
BC158	10	BF458	57	IN4007	7
BC159	10	BF494	25	IN5418	5
BC160	33	BF495	25	IN5419	13
BC161	33	BF499	28	IN5404	18
BC171	15	BF503	28	IN5408	23
BC177	15	BF534	140	IN1613	22
BC178	15	BFK41	45	IN2218	48
BC179	15	BFK54	27	IN2219	90
BC182L	12	BFK85	27	IN2646	55
BC183L	12	BFK86	27	IN2904	24
BC184L	12	BFK87	27	IN2905	24
BC186	25	BFK88	27	IN2906	10
BC187	25	BFK89	27	IN2908	10
BC205	18	BFY50	16	IN2926	10
BC212L	12	BFY51	16	IN2926Y	10
BC213L	12	BFY52	16	IN2926G	10
BC214L	12	BFY53	16	IN2926S	22
BC237	17	BP101	85	IN3054	50
BC238	17	BPW34	260	IN3055	55
BC239	17	BPW35	260	IN3056	55
BC261	20	BR101	30	IN3702	14
BC262	20	BRY39	40	IN3704	15
BC307	20	BRY56	50	IN3705	15
BC311	15	BS75	45	IN4706	28
BC337	15	BSY89	165	IN3819	25
BC338	15	BY103	38	IN3820	45
BC367	15	BY127	10	IN3823	40
BC481	40	E204	45	IN2904	15
BC482	40	BY167	135	IN3905	15
BC518	60	BYK10	30	IN5387	58
BC517	65	BYK36	5	IN5458	130
BC546	17	BYK55	7	IN5461	50
BC547	9	BY196	15	IN2027	32
BC548	14	E100	40	40603	80
BC548	12	E201	50	40673	85
BC549	12	E204	45		
BC549C	12	E300	45		

Zener diode 1W 3-3V to 220V E24 Series 30p
Zener diode 400 mW 2-7V to 47V E12 Series 12p
Large stock of Japanese Transistors

TTL

SN74 Series TTL Integrated Circuits					
7400	18	7438	27	7490	39
7401	18	7439	27	7491	70
7402	16	7440	16	7492	45
7403	18	7441	68	7493	45
7404	16	7442	68	7494	60
7405	18	7443	100	7495	70
7406	30	7444	100	7496	75
7407	39	7445	100	74100	110
7408	18	7446	100	74107	35
7409	22	7447	72	74109	65
7410	18	7448	75	74110	50
7411	24	7450	16	74118	85
7412	26	7451	18	74121	30
7413	30	7452	18	74122	50
7414	70	7453	18	74123	70
7415	34	7460	18	74125	45
7416	32	7470	30	74126	70
7417	30	7472	28	74128	45
7420	18	7473	28	74132	70
7421	40	7474	28	74136	75
7422	20	7475	47	74137	90
7423	38	7476	30	74141	70
7424	30	7480	45	74145	70
7425	30	7481	100	74147	172
7426	24	7482	85	74148	165
7427	36	7483	100	74150	150
7428	40	7484	120	74151	75
7430	18	7485	120	74153	60
7432	27	7486	34	74154	135
7437	27	7489	290	74155	80

ELEKTRONIKS

Kits include all the components described in the original article together with any additional items specified in subsequent Missing Link columns. Kits come complete with the EPS printed circuit board(s) where published and suitable power supplies can also be provided on request if not included in the original design.

TV SOUND (E2) The audio output stage of many domestic TV receivers is rarely Hi-Fi. This project allows the high quality transmitted F.M. sound signal to be fed into a domestic Hi-Fi system. 950p

VERSATILE LOGIC PROBE (E1) A seven segment display indicates the logic states of the TTL circuits under test. 350p

LED LIGHT SHOW (E14) A sound to light modulator using light emitting diodes, which could however be replaced with 1L74 opto isolators to fire flash controlled filament bulbs. 820p

SIMPLE MW RECEIVERS (E8) A straightforward receiver design with no alignment problems. 715p

DIGIBELL (E14) A novel electronic doorbell which produces the Westminster Chime. 715p

POLAROID TIMER (E12) The timer incorporates a sensor to compensate for temperature induced variations in the development times of polaroid films. 430p

LOUD MOUTH (E18) The Loud Mouth enables outputs of up to 40W to be achieved from a 12V vehicle supply. 1450p

SENSITIVE METAL DETECTOR (E19) A fresh approach to an old problem which allows rapid and accurate location of even small articles. 830p

ALARM (E18) The ultrasonic movement detector can be utilised as an intruder alarm. 1530p

SIGNAL HORN (E18) Although utilising inexpensive components this unit generates an intense sound 550p

SIRENS (E20) A striking sound effect unit which simulates both european and american police sirens, for application to an audio amplifier. 450p

DRILL CONTROL (E20) This design utilised a feed back system to allow the drill to operate at lower speeds without a reduction of torque. 900p

ELEKTROSCOPE (E20/21) A separate kit is to be supplied for each module, and further details are available on request.

AUDIO IC'S (E21) 3 related projects describe easily assembled medium power audio amplifiers. 940p

STR 025 950p STR 036 1150p TDA 2020 700p

MARBLES (E21) The nostalgic childrens game re-visited with TTL. 940p

NOISE GENERATOR (E21) The white and pink noise produced by this unit can be utilised in test equipment and in many types of sound effect units. 630p

LOCAL RADIO (E22) An easily assembled FM receiver with no alignment problems which comes in four sections: Front End (EPS 9512A) 600p IF Stage (EPS 9609) 440p Power Supply (EPS 9499-2) 340p

HI-FI DYNAMIC RANGE COMPRESSOR (E22) As a supplement to a volume control a compressor allows an amplification system to accept large variations in input signal while maintaining a relatively constant output. 1030p

Stereo version 1030p

IC POWER SUPPLY (E22) This practical 25V 2A supply comes complete with transformer and meters. 2850p

VARIOTUNER 1 (E23) A quality novel FM tuner incorporating a phase locked loop which has been designed for ease of construction and alignment. The kit includes the Variometer tuning coil and drive accessories. 7110p

RUN RABBIT, RUN (E23) An electronic novelty to test your wit! 1350p

RESISTORS

Values available to E3 series (1, 2, 4 and 7) and multiples			
Single gang 100R to 2M2	log 1K to 2M2	30	
Single gang + DPDT Switch	log 4-7K to 1M	50	
Tandem	log 1K to 1M	80	
Tandem + DPDT Switch	log 100K to 470K	95	

HARDWARE

HEATSINKS	20	SOLDER	50
TO126/220	35	3 core "SAVBIT" 18 swg 80/40 200g	160
TO18	20	SILVER PLATED COPPER WIRE	60/mtr
TO218	20	22 swg	50/mtr
TO247	20	24 swg	45/mtr
TO263	20	ENAMELLED COPPER WIRE	50
TO270	20	18 swg	35
TO286	20	19 swg	30
TO292	20	20 swg	30
TO300	20	21 swg	30
TO310	20	22 swg	30
TO320	20	23 swg	30
TO330	20	24 swg	30
TO340	20	25 swg	30
TO350	20	26 swg	30
TO360	20	27 swg	30
TO370	20	28 swg	30
TO380	20	29 swg	30
TO390	20	30 swg	30
TO400	20	31 swg	30
TO410	20	32 swg	30
TO420	20	33 swg	30
TO430	20	34 swg	30
TO440	20	35 swg	30
TO450	20	36 swg	30
TO460	20	37 swg	30
TO470	20	38 swg	30
TO480	20	39 swg	30
TO490	20	40 swg	30
TO500	20	41 swg	30
TO510	20	42 swg	30
TO520	20	43 swg	30
TO530	20	44 swg	30
TO540	20	45 swg	30
TO550	20	46 swg	30
TO560	20	47 swg	30
TO570	20	48 swg	30
TO580	20	49 swg	30
TO590	20	50 swg	30

IC'S

3817	clock	40 dli	750
AY-1402Q	master generator	16 dli	830
CA3080	OTA	16 dli	830
CA3086	transistor array	14 dli	70
CA3090AQ	decoder	14 dli	520
CA3130T	regulator	TO5	120
F2H 141	dual 5 input NAND	16 dli	305
F2H 241	dual 4 input NAND	16 dli	540
F2H 251	quad 2 input AND	16 dli	415
FZU 181	4 bit shift register	16 dli	845
H2405	Quad opamp	18 dli	1600
ICM7038A	clock time base	18 dli	470
L129	5V regulator	flapback	2400
LM205	stop watch	TO220	125
LM705	5V regulator	TO220	125
L130	12V regulator	TO220	125
L131	15V regulator	TO220	125
LF350	Bi Fet opamp	TO5	390
LD130	3 digit DVM 1%	18 dli	1385
LM301AN	opamp	8 dli	85
LM308N	opamp	8 dli	85
LM309	5V regulator	TO3	180
LM317K	adjust reg.	TO3	385
LM318	voltage comparator	TO5	245
LM319N	opamp	14 dli	385
LM324N	quad opamp	TO5	245
LM325N	15V regulator	TO5	340
LM326H	12V regulator	TO5	340
LM327H	+5 to +12V regulator	TO5	340
LM380N	audio amp	14 dli	1600
LM381N	dual audio pre amp	14 dli	220
LM555N	timer	8 dli	45
LM556N	dual timer	14 dli	140
LM5568N	voltage detector	14 dli	170
LM7033LH	r amp	TO5	100
LM709CN	opamp	8 dli	50
LM723CH	voltage regulator	TO5	56
LM723CN	voltage reg.	14 dli	71
LM740	fet input opamp	TO5	820
LM741CN	opamp	8 dli	30
LM746CN	opamp	8 dli	90
LM1812N	ultra sonic transceiver	14 dli	695
LM3909N	clock Norton amp	16 dli	90
LM3909N	led flasher	8 dli	90
LM3909N	temperature transducer	TO46	410
M252	rhythm generator	16 dli	950
M253	rhythm generator	24 dli	1350
MC1310P	decoder	14 dli	220
MC1312P	matrix SQ	14 dli	250
MC1314P	vca SQ	16 dli	400
MC1315P	logic control SQ	16 dli	600
MC1488CP1	dual opamp	14 dli	90
MC1488L	dual regulator	14 dli	420
MC1440Z	watch LED	40 dli	2100
MC14543CP	watch LED	16 dli	1600
MC14533CP	LCD driver	16 dli	275
MC14553P	3 digit counter	16 dli	640
MC14566P	time base	16 dli	230
MM5313N	clock	40 dli	450
MM5316N	clock	40 dli	550
MM5318N	clock T.V.	40 dli	740
MM5330	4 1/2 digit DVM -02%	16 dli	1155
MM5841N	TV display driver	28 dli	1200
MM74C14	hex trigger	14 dli	200
MM74C48	BCD to 7 seg	16 dli	345
RG194TC	dual regulator	TO66	870
SG3501T	dual regulator	TO5	575
SN7413N	audio	16 dli	150
SN76131N			

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE

- ★ 30A power transistors
- ★ Glass fibre P.C.B
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S

TAM1000 100W 4 ohms 65V	£9-80
TAM500 50W 4 ohms 45V	£7-50
TAM250 25W 8 ohms 45V.	£4-75

POWER SUPPLIES	
For 1 or 2 TAM250/500	£7-50
For 1 or 2 TAM1000	£9-80
(Carriage 50p on supplies)	

- Suits loads 4-16 ohms
- 20-20,000 Hz \pm 1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

High grade components used throughout: Texas, Mullard, R.C.A., Plessey, etc.



- Low distortion (0-1%)
- Low profile (1in high 3½in x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections



ALL PURPOSE MIXER/PRE-AMP.

(with 60mm slider volume)

- Suitable for multiple input systems
 - High and low impedance inputs
 - High sensitivity
 - Built-in supply smoothing
 - 20-20,000 Hz \pm 1dB
 - -80dB noise level
 - Accepts a wide variety of inputs
 - Wide range bass and treble controls
- Use up to 10 PRE-AMPS with 1 power

Printed circuit board assembly with treble and bass controls plus slider volume control **£6-50**

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W units and at 12½% for 25W units.

Hours, 9.30 a.m.—5 p.m.
Monday — Saturday.
Callers welcome.
Tel: (01) 684 0098

TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS
8-3V 1-5A £2; 3A £2-50; 6A CT £4-25; 12V 1-55A £2-40; 3A CT £4-25; 6A CT £8; 18V 1-5A CT £4-25; 24V 1-5A CT £4-25; 3A CT £2; 5A £3-75; 8A £18; 12A £21-50; 40V 3A CT £3-75; 50V 8A CT £21; 15V 0-5A + 15V 0-5A £3-75; 15V 1A + 15V 1A £4-85; 18V 0-5A + 18V 0-5A £4-50; 18V 1A + 18V 1A £5-65; 20V 1A + 20V 1A £3-60; 12V 4A + 12V 4A £7-50; 25V 2A + 25V 2A £7-50.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V 0-10-12-14-16-18V 2A £4; 4A £5-25; 0-12-15-20-24-30V 2A £4-50; 4A £7-50; 0-5-20-30-40-60V 1A £3-25; 2A £7-50; 0-40-50-60-80-100-110V 1A £7-50.

MIDGET RECTIFIER TRANSFORMERS
For FW recs. 200/240V a.c.: 6-0-6V 1-5A or 9-0-9V 1A £2-25 each; 12-0-12V 1A or 20-0-20V 0-75A, or 9-0-9V 0-3A, or 12-0-12V 0-25A, or 20-0-20V 0-15A or 9V 0-5A + 9V 0-5A, or 9V 0-35A + 9V 0-35A, or 12V 0-25A + 12V 0-25A, or 20V 0-15A + 20V 0-15A, all at £2-65 each.

LOUDSPEAKERS
2½in 8Ω, 2½in 8 or 25Ω, 3in 8 or 35Ω, 3½in 15Ω, all at £1 each; 8 x 5in 4, 8 or 25Ω, £2 each; 7 x 4in 3, 8, 15 or 25Ω, £1-50 each 8in 8Ω £2.

"INSTANT" BULK CASSETTE/TAPE ERASER
Instant erasure of cassettes and tape spools. demagnetises tape heads. 200/240V a.c. £3-75.

SYNCHRONOUS GEARED MOTORS 200/240V a.c.
Brand new Smiths, built-in gearbox, 8 f.p.h., £1-25.

EDGWISE LEVEL METER. FSD 200.
Size 19 x 18 x 20mm. 800Ω, 65p each.

SPEAKER MATCHING AUTO TRANSFORMERS
12V, 3 to 8 or 15Ω, up or down, £2.

AUTO TRANSFORMERS
110/240V a.c. 20 watts. £1-25.

CABLES—CABLES—CABLES
MICROPHONE TWIN H/DUTY, BRAIDED SCREEN
Professional cable for stage studio, outdoor. PVC covered. 20p per metre.

MULTI WAY SCREENED, PVC COVERED
36-way, £1; 25-way 75p; 14-way 50p; 6-way 25p; 4-way 20p; 2-way 10p; 1-way 8p per metre.

LOW LOSS CO-AXIAL CABLE 75Ω
UHF 18p per metre; VHF 10p per metre.

BALANCED TWIN FLAT FEEDER 300Ω
50p per 10 metres.

MINI 3-CORE CABLE, 16/6.10mm
Ideal for speakers, intercoms, etc., £3-50 per 100 metres.

TWIN FIG 8 CABLE
Polarised. 100m/£2; screened stereo. 15m/£1.

ALL TYPES DOMESTIC AND COMMERCIAL CABLE
MULTI SCREENED AND UNSCREENED CABLE
ALL SIZES AND COLOURS CONNECTING WIRES
TRADE ENQUIRIES INVITED
Carriage and VAT on all orders
S.A.E. ENQUIRIES, LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx HA8 8YG
Tel. 01-958 9314

Towers' International

Transistor Selector

by T. D. Towers Price £5-00

WORLD RADIO TV HANDBOOK
by J. M. Frost Price £5-50

THE RADIO AMATEUR'S HANDBOOK 1977
by A. R. R. L. Price £6-50

THE MEMORY & MICROPROCESSOR DATA BOOK FOR DESIGN ENGINEERS
by Texas Price £3-50

UNDERSTANDING MICROPROCESSORS
by Motorola Price £3-75

THE OSCILLOSCOPE IN USE
by I. R. Sinclair Price £2-85

ELECTRONIC CLOCKS & WATCHES
by M. S. Robbins Price £5-10

OP-AMP CIRCUIT DESIGN & APPLICATIONS
by J. Carr Price £4-00

TTL COOKBOOK
by D. Lancaster Price £6-65

MICROELECTRONICS
by C. L. Hallmark Price £3-90

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

INTERLOCKING PLASTIC STORAGE DRAWERS



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2½in x 2½in). £2-90 DOZEN.

DOUBLE UNITS (2D) (5in x 4½in x 2½in). £4-90 DOZEN.

TREBLE (3D) £4-90 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £7-25 for 8.

EXTRA LARGE SIZE (6D1) £6-25 for 8.

PLUS QUANTITY DISCOUNTS
Orders over £20, less 5%.
Orders over £60, less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance
All prices correct at time of going to press

FLAIRLINE SUPPLIES
(Dept. PE6)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

Get a great deal from

Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat Trade and export enquiries welcome

A. MARSHALL (LONDON) LTD. DEPT. P.E.
LONDON—40-42 Criklewood Broadway NW2 3ET
Tel: 01-452 0161. Telex: 21492
GLASGOW—85 West Regent Street G2 2QD
Tel: 041-332 4133
BRISTOL—1 Stratts Parade, Fishponds Rd BS16 2LX
Tel: 0272 654201

NEW CATALOGUE 77

168 page catalogue with 500 new lines. 55p post paid (40p to callers)

TOP 400 SEMICONDUCTORS FROM THE LARGEST RANGE IN THE U.K.

EXPRESS M.O. SERVICE BY RETURN POST—all orders received despatched same day on stock items

2N696	0-35	2N6103	0-15	2N6126	0-45	BC158	0-11	BD115	1-20	BFX30	0-40
2N697	0-30	2N6104	0-15	40361	0-45	BC159	0-14	BD116	1-20	BFX85	0-40
2N698	0-52	2N6105	0-15	40362	0-48	BC160	0-50	BD131	0-51	BFX87	0-40
2N699	0-55	2N6106	0-16	40363	1-20	BC161	0-50	BD132	0-54	BFX89	0-40
2N706	0-24	2N6107	0-16	40406	0-58	BC187	0-12	BD135	0-37	BFY50	0-34
2N706A	0-12	2N6108	0-16	40407	0-45	BC168	0-12	BD136	0-37	BFY51	0-38
2N708	0-21	2N6109	0-16	40408	0-65	BC169	0-12	BD137	0-35	BFY52	0-36
2N709	0-50	2N6110	0-16	40409	0-65	BC170	0-16	BD138	0-38	BFY53	0-34
2N718	0-27	2N6111	0-18	40410	0-65	BC171	0-14	BD139	0-40	BFY59	1-37
2N718A	0-30	2N6112	1-20	40411	2-65	BC172	0-12	BD140	0-40	BFY39	0-50
2N720A	0-80	2N6113	2-30	40594	0-75	BC177	0-20	BD239	0-40	BSX20	0-21
2N810A	0-35	2N6114	2-40	40595	0-65	BC178	0-20	BD240	0-45	BSX21	0-32
2N816	0-30	2N6115	2-55	40673	0-73	BC179	0-23	BD241	0-45	BU105	1-50
2N816	0-30	2N6116	2-55	40673	0-73	BC182	0-11	BD242	0-47	BU205	2-20
2N829	0-25	2N6117	1-65	AC124	0-44	BC182L	0-14	BD243	0-62	MEC402	2-20
2N830	0-26	2N6118	2-20	AC126	0-37	BC183	0-11	BD244	0-62	MEC404	0-15
2N1131	0-60	2N6119	2-90	AC151V	0-35	BC183L	0-14	BD245	0-65	MEC412	2-20
2N1132	0-60	2N6120	2-90	AC152V	0-50	BC184	0-12	BD246	0-66	MEC410	0-10
2N1613	0-35	2N6121	3-10	AC153	0-49	BC184L	0-14	BD249	0-42	ME104	0-10
2N1711	0-37	2N6122	3-10	AC153K	0-35	BC207	0-12	BD530	0-47	MJ480	1-35
2N1893	0-38	2N6123	3-50	AC175	0-40	BC208	0-11	BDY20	1-10	MJ481	1-55
2N2102	0-60	2N6124	0-30	AC176	0-65	BC212	0-14	BDY23	0-65	MJ301N	0-44
2N2119	0-37	2N6125	0-38	AC187K	0-55	BC212L	0-17	BF117	0-70	MJ493	1-85
2N218A	0-33	2N6126	0-28	AC188K	0-55	BC213	0-14	BF121	0-55	MJ2955	1-25
2N2219	0-30	2N6127	0-30	AD161	0-85	BC213L	0-16	BF123	0-55	MJE340	0-58
2N2219A	0-32	2N6128	0-21	AD162	0-85	BC214	0-16	BF125	0-25	MJE370	0-58
2N2220	0-35	2N6129	0-22	AF106	0-55	BC214L	0-17	BF153	0-25	MJE371	0-60
2N2221	0-22	2N6130	0-67	AF109	0-75	BC237	0-17	BF154	0-25	MJE520	0-45
2N221A	0-26	2N6131	0-55	AF124	0-65	BC238	0-12	BF159	0-35	MJE521	0-65
2N2222	0-25	2N6132	0-55	AF125	0-65	BC239	0-16	BF160	0-30	MJE2955	1-42
2N222A	0-25	2N6133	0-20	AF126	0-65	BC251	0-15	BF161	0-60	MJE3055	0-85
2N2368	0-25	2N6134	0-20	AF127	0-65	BC253	0-22	BF166	0-40	MP811	0-35
2N2369	0-25	2N6135	0-17	AF139	0-69	BC257A	0-17	BF167	0-38	MP812	0-40
2N2369A	0-29	2N6136	0-18	AF186	0-50	BC258A	0-17	BF173	0-38	MP813	0-45
2N2646	0-75	2N6137	0-17	AF200	0-70	BC259B	0-18	BF177	0-30	MPF102	0-30
2N2647	1-40	2N6138	0-20	AF239	0-74	BC261A	0-21	BF178	0-35	MPS105	0-23
2N2904A	0-37	2N6139	0-65	AF240	0-98	BC262B	0-19	BF179	0-35	MPSA06	0-24
2N2905	0-37	2N6140	0-60	AF279	0-80	BC263C	0-30	BF180	0-40	MPSA12	0-35
2N2905A	0-38	2N6141	0-53	AF280	0-85	BC300	0-45	BF181	0-40	MPSA55	0-24
2N2906	0-28	2N6142	0-53	BC107	0-15	BC301	0-45	BF182	0-45	MPSA56	0-24
2N2906	0-28	2N6143	0-53	BC108	0-15	BC303	0-45	BF183	0-45	MPSU05	0-50
2N2906A	0-25	2N6144	0-60	BC109	0-15	BC307	0-20	BF184	0-38	MPSU06	0-56
2N2907	0-21	2N6145	0-70	BC113	0-17	BC308	0-18	BF185	0-30	MPSU55	0-55
2N2907A	0-22	2N6146	0-75	BC115	0-19	BC309C	0-25	BF194	0-14	MPSU56	0-60
2N2924	0-15	2N6147	0-80	BC116	0-19	BC317	0-14	BF195	0-13	TP29A	0-45
2N2925	0-17	2N6148	0-35	BC116A	0-20	BC318	0-13	BF196	0-14	TP29C	0-80
2N3019	0-55	2N6149	0-40	BC117	0-22	BC327	0-20	BF197	0-17	TP30A	0-49
2N3053	0-30	2N6150	0-40	BC118	0-16	BC328	0-19	BF198	0-18	TP30C	0-65
2N3054	0-60	2N6151	0-40	BC119	0-30	BC337	0-19	BF200	0-35	TP31A	0-50
2N3055	0-70	2N6152	0-40	BC121	0-45	BC338	0-21	BF225J	0-25	TP31C	0-66
2N3390	0-25	2N6153	0-15	BC132	0-30	BC547	0-12	BF244	0-35	TP32A	0-50
2N3391	0-25	2N6154	0-15	BC134	0-15	BC548	0-12	BF245	0-34	TP32C	0-75
2N3391A	0-25	2N6155	0-19	BC135	0-15	BC549	0-13	BF246	0-75	TP33A	0-80
2N3392	0-16	2N6156	0-32	BC136	0-19	BCY30	1-03	BF254	0-24	TP33C	1-10
2N3393	0-16	2N6157	0-32	BC137	0-14	BCY31	1-05	BF255	0-24	TP34A	0-50
2N3394	0-15	2N6158	0-29	BC140	0-40	BCY32	1-70	BF257	0-37	TP34C	1-20
2N3439	0-88	2N6159	0-34	BC141	0-45	BCY33	1-00	BF258	0-45	TP35A	2-50
2N3440	0-64	2N6160	0-38	BC142	0-30	BCY34	1-20	BF259	0-49	TP36A	3-35
2N3441	0-85	2N6161	0-53	BC143	0-30	BCY38	2-00	BF259	0-45	TP11A	0-70
2N3442	1-35	2N6162	0-65	BC147	0-12	BCY42	0-60	BF260	0-38	LM741C	0-85
2N3638	0-16	2N6163	0-43	BC146	0-32	BCY58	2-50	BF261	0-80	LM741D	1-05
2N3638A	0-16	2N6164	0-42	BC149	0-13	BCY59	2-50	BF262	0-80	LM741E	1-23
2N3639	0-30	2N6165	0-38	BC153	0-27	BCY70	2-25	BF263	0-30	LM741F	0-50
2N3641	0-20	2N6166	0-41	BC154	0-27	BCY71	2-25	BF264	0-27	LM741G	0-50
2N3702	0-17	2N6167	0-43	BC157	0-12	BCY72	0-24	BF265	0-38	LM741H	1-76

INTEGRATED CIRCUITS

CA3020	1-70	LM1806	1-92	TA4550	0-60
CA3020A	2-29	LM1829	1-78	TA4560	1-50
CA3028B	1-01	LM3301N	0-85	TA4570	1-85
CA3028A	1-29	LM3302N	1-40	TA4610	2-30
CA3030	1-24	LM3401	0-70	TA4621	2-15
CA3030A	1-89	LM3900	0-75	TA4661A	1-32
CA3045	1-40	LM3905	1-60	TA4661B	1-32
CA3046	2-23	MC1302	0-88	TA4700	3-91
CA3048	2-23	MC1035	1-75	TA4830A	2-30
CA3049	1-66	MC1303	1-47	TA4830B	1-05
CA3052	1-62	MC1304	1-65	TA4910	1-95
CA3053	0-60	MC1305	1-85	TBA120	0-65
CA3060	0-68	MC1306	1-00	TBA400	1-50
CA3080A	1-88	MC1310	1-91	TBA500	2-21
CA3086	0-51	MC1312	1-98	TBA500A	2-36
CA3088	1-59	MC1327	1-54	TBA520	2-21
CA3089	2-52	MC1330	0-92	TBA520C	2-30
CA3090	3-80	MC1350	0-75	TBA520	2-21
CA3130	0-94	MC1351	1-20	TBA520C	2-30
LM301A	0-65	MC1352	0-97	TBA530	1-98
LM301N	0-44	MC1357	1-45	TBA530C	2-07
LM307A	2-45	MC1452	0-60	TBA5700	1-38
LM307N	0-65	NE555	0-53	TBA5700C	2-50
LM308C	1-92	NE556	1-05	TBA5700	1-52
LM308N	1-17	NE565	1-30	TBA700C	0-81
LM309K	0-20	NE566	1-65	TBA720C	2-50
LM317K	3-00	NE567	1-80	TBA750	1-98
LM318N	2-25	SAS560	2-50	TA4500	2-07
LM323K	6-40	SAS570	2-50	TBA810	1-20
LM339N	1-75	S042P	2-50	TBA810	1-16
LM348N	1-91	76001N	1-57	TBA820	1-03
LM360N	2-75	76003N	2-55	TBA820	1-79
LM370N	3-00	76008K	2-50	TBA920	2-99
LM371N	2-25	76013N	1-70	TBA940	1-62
LM372N	2-15	76018ND	1-87	TBA1600	1-20
LM373N	2-25	76019K	1-70	TBA1600	1-16
LM374N	2-25	76023N	1-70	TBA810	1-16
LM377N	1-75	76023ND	1-57	TBA820	1-03
LM378N	2-25	76033N	2-55	TBA820	1-79
LM379S	3-95	76110N	1-48	TBA920	2-99
LM380-8	0-90	76115N	1-87	TBA940	1-62
LM380N	0-95	76116N	2-06	TCA1600	1-20
LM381A	2-45	76131N	1-30	TCA160B	1-85
LM381N	1-60	76226N	1-94	TCA270	2-25
LM382N	1-25	76227N	1-51	TCA280A	1-30
LM384N	1-45	76228N	1-75	TCA290A	3-13
LM386N	0-65	76530N	0-31	TCA420A	1-84
LM387N	1-05	76532N	1-50	TCA730	3-22
LM388N	1-00	76533N	1-30	TCA740	2-76
LM389N	1-00	76544N	1-44	TCA750	2-30
LM702C	0-75	76545N	2-09	TCA760	1-38
LM709C	0-65	76546N	1-44	TCA870	3-13
LM709N	1-10	76550N	0-41	UA4170	2-00
LM741C	0-85	76552N	1-50	UA4180	2-00
LM741D	1-05	76553N	2-08		
LM741E	1-23	76554N	1-50		
LM741F	0-50	76555N	1-10		
LM741G	0-50	76666N	0-60		
LM741H	1-85	74163	1-41		
LM741I	1-11	74164	1-41		
LM741J	1-11	7417			

Sparkrite mk2

Capacitive discharge electronic ignition kit

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE
OCT. 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.
Improve performance & economy NOW

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing

ELECTRONICS DESIGN ASSOCIATES, 82 Bath St., Walsall, WS1 3DE

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept. PE6
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

	QUANTITY REQUIRED
Mk. 2 DIY Ass. Kit @ £11.80	
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's
for **£**

Cheque No.

Send SAE if brochure
only required.

CRESCENT RADIO LTD.

164-166 HIGH ROAD, WOOD GREEN, N22 888-3206
(also) 13 SOUTH MALL, EDMONTON, N.9 803-1685

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4J3
Phone: 888-4474

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 200V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 70p. P. & P. + 8%.

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed 1lb poly packs. Our Price 65p + P/P + VAT at 8% per lb.

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied). Size (internal) 81mm x 61mm x 28mm. Our Price 60p + 8%.

EFFECTS PROJECTOR "150"

No disco should be without our new effects projector, we believe that this is the most versatile machine for projecting coloured images to supplement your music. Spec.: Volts—220/240, a.c., 50 Hz, Lamp—A1/187 150W, Standard Lens—60 mm. A sturdy metal construction and takes a range of lenses and accessories. Comes complete with 6in wheel and ready to use. A bargain at £27 + VAT 8%.



"C100" 100 WATT AMPLIFIER

All built and tested, mounted on a plain aluminium chassis which measures 18 x 9 1/2 x 4in, and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls, S/C protected output. 100W clean into 8 ohm L/S. Ideal for disco, music groups, P.A. and clubs. A bargain at £48 + £1 carr. + 8% VAT.

GOODMANS 8in. LOUDSPEAKER

Goodmans "Audium 8PA" Bass L/speaker, impedance 8 ohm, power handling 15W nominal. Our price £4.20 + 12 1/2% VAT per pair.

HEADPHONES (MONO)

Standard Type G1105, impedance 2,000 ohms each earphone. Price £1.50 + 12 1/2% VAT per pair.

PPI POWER SUPPLY UNIT

Switched 3, 4 1/2, 6, 7 1/2, 9 and 12V at 500 mA. With on/off switch and pilot light. Size: 130 x 55 x 75 mm. Only £5.60 + 8% VAT.



AUDIO LEADS + 12 1/2% VAT

Good quality audio connecting leads at moderate prices: L1 6-pin DIN plug 180° to 5-pin DIN plug 180°, length approx. 1.2m, 80p; L12 5-pin DIN plug 180° to open end, length approx. 1.2m, 65p; L14 2-pin DIN plug to 2-pin DIN line socket, length approx. 3m, 80p; L16 2-pin DIN plug to 2-pin DIN line socket, length approx. 7m, 75p; L11 5-pin DIN plug 180° to four phono plugs, length approx. 1.2m, £1.10p; L10 5-pin DIN plug 180° to four phono line sockets, length approx. 1.2m, £1.20; L21 stereo headphone extension lead (curly type), length approx. 20 ft., £1.50; L22 guitar lead (curly type), length approx. 20 ft., £1.60. Various other combinations stocked. Prices on request.

ACCESS AND BARCLAYCARD ACCEPTED
U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

Doram kits

DORAM KITS CONTAIN
EVERYTHING DOWN TO
THE LAST NUT!



50W PA/Guitar AMP

£29.95
+ VAT

£29.95 + 12 1/2% VAT
(Order code 997-011)

Subject to availability

Especially designed for general purpose use with guitars, PA systems etc. This amp will provide 50 Watts RMS into 8 ohms with harmonic distortion level as low as 0.15%. Robust case and load fault protection contribute to the rugged design, which incorporates an IC mixer/pre-amp (giving 2 separate inputs) and a thermally compensated power amplifier. Overall freq. response (-3dB) is 15Hz to 100KHz with sensitivity 30mV for full output and 52dB sig. to noise ratio.

Overseas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).

DORAM ELECTRONICS LTD.
P.O. BOX TR8, WELLINGTON RD. IND. EST., LEEDS LS12 2UF.

An Electrocomponents Group Company

REVERSIBLE ASSEMBLY FRAME FOR PRINTED CIRCUITS

Simply assemble, turn over and solder



This apparatus allows fast, neat assembly of single circuit boards, or several smaller boards at a time.

You just insert the circuit boards between the holding bars, assemble components, clamp down the foam cover, invert the frame, then cut and solder connections. Our special magnetic locking system ensures that components stay firmly in place.

Indispensable for any circuitry laboratory, repair shop, or production line use.

Available in three sizes
Max area:
JA 500-220 by 170 mm
JA 1100-350 by 230 mm
JA 1100S-500 by 400 mm.

- ★ Takes one or more circuit boards
- ★ Fully adjustable foam cover
- ★ Also ideal for repairs and retouching

For full details, please contact:
Special Products Distributors Ltd.,
81 Piccadilly, London W1V 0HL.
Telephone: 01-629 9556.

NEWS FROM JOSTY KIT

JOSTYKIT—a product from Denmark

HF 61-2 DIODE MEDIUM WAVE RECEIVER



By means of a very simple technique a reasonable reception is attained. HF 61-2 is built on a small circuit board of the same size as the general purpose amplifier AF 380. The two assemblies should be connected to produce power for a loudspeaker. HF 61-2 is especially useful for beginners, who have not tried to assemble electronic kits before.

£4-30

HF 305 VHF RADIO-CONVERTER

Extend the range of your transistor radio. Listen to Amateurs (2 metre band), Aircraft, Trawlers, etc. Two transistor circuit with printed circuit coils, varactor diodes and superior circuit design. Converts radio signals in the 100-200MHz range to output signal at 100MHz. Pipe this into your VHF receiver and you're in a new dimension.

£6-70



AT 365 3-CHANNEL DISCO LIGHT




A new concept in psychedelic lighting. Uses built-in microphone. Avoids awkward connections to amplifiers. Position light-show to best advantage without long trailing leads—just plug in to nearest power point. Circuit combines latest integrated circuit techniques with solid-state power control. Quasi op. amp. makes selection of bass, midrange and treble frequencies easy. Three thyristors (SCRs) control three separate lampbanks. Kit includes fused dc power supply and FET zero light adjustment. **WARNING:** Only experienced persons should attempt the interconnection of mains equipment.

£17-00


HF 385-2 VHF/UHF AERIAL AMPLIFIER

A quality, printed circuit, no trimming, aerial amplifier. Fantastic frequency range due to use of printed coils, 21dB amplification at 400MHz. Two separate inputs for UHF and VHF. No loss of signal or intercommunication problems.

£5-80

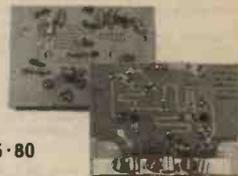

NT 410 AERIAL AMPLIFIER CURRENT SUPPLY

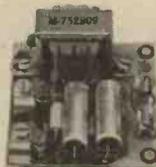

NT 410 is a current supply, specially built for aerial amplifiers, such as HF 385-2, but can also be used for other aerial amplifiers. NT 410 is supplied with input and output clamps for 75 ohm or 50 ohm aerial cables. It is therefore not necessary to solder—just cut and strip the aerial cable and attach to NT 410. The aerial signal from the aerial amplifier to the receiver passes without complications and the current to the aerial amplifier

passes through the same cable. NT 410 describes how to use NT 410 together with HF 395 and HF 385-2.

£4-50

CHINAGLIA DINO—ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

PRESENT THE

DOLOMITI

20k Ω /V a.c. and d.c.

A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED



Accuracy: D.C. ranges, $\pm 2.0\%$, A.C. & Ω ranges $\pm 2.5\%$.
39 ranges: d.c. V, 0-150mV, 500mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1-5kV; d.c. I, 0-50 μ A, 500 μ A, 5mA, 50mA, 0-5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1-5kV; a.c. I, 5mA, 50mA, 0-5A, 5A; dB -10 to +65 in 6 ranges; Ω 0-0.05k Ω , 5k Ω , 50k Ω , 500k Ω , 5M Ω , 50M Ω , pF 50kpf, 500kpf.

Automatic overload protection and high current range fusing. Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £45-90 incl. VAT (£1 P. & P.)
30kV Probe £12-85 incl. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

ALCON

19 MULBERRY WALK, LONDON SW3 6DZ TEL: 01-352 1877



JOSTY KIT (U.K.) LTD


MAIL ORDER DIVISION
P.O. BOX 68, MIDDLESBROUGH,
CLEVELAND, ENGLAND B1 5CQ

SEND FOR OUR FREE CATALOGUE

ELECTRONI-KIT

Proclaimed "... educational kits of exceptional quality" in extensive survey by AUDIO mag. Also many other first class Press reports.

EDUCATIONAL ELECTRONIC KIT

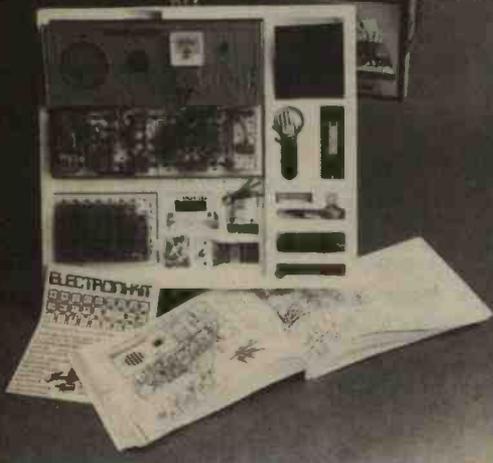

The Famous DENSHI kits —now even better value

The kits are suitable both for the beginner to gain a wide practical understanding of electronics and for the more experienced to carry out many advanced experiments not available elsewhere.

Illustrated is the SR-4ADX kit—over 150 different actual working projects can be built, dismantled and rebuilt any number of times, plus any circuits of your own design.

Each component is beautifully encapsulated in transparent plastic, engraved with its electronic symbol. No soldering is involved with any kit and yet this fantastic versatility is provided. The kits are complete in every respect, including educational manuals and batteries. NOTHING ELSE NEEDED.

This is the most practical and effective way to learn about electronics—the kits are also first-class testing kits for laying-out and testing new circuits quickly. There is no danger whatsoever in the use of these kits.

Add-on kits and spares are available too, to increase the scope of each kit if required.

SR-3A—over 100 experiments—radio receivers, transmitters, amplifiers, microphones, alarms, morse code, electronic birds, cats, sirens, organs, intercoms, metronomes, photoelectric cell, high voltage generator, circuits demonstrating Amps, Ohms, Watts, etc., etc. £26-45 COMPLETE

SR-3ADX—over 105 experiments—similar to SR-3A plus sophisticated control panel and solar cell circuits, etc., etc. £33-45 COMPLETE

SR-4ADX—over 150 experiments—similar to SR-3ADX plus Relay and Multi-meter circuits—ammeter, voltmeter, resistance meter, water purity —, ion concentration —, volume —, output —, field intensity meter, illuminometer, etc., etc. £41-45 COMPLETE

PRICES INCLUDE VAT, P. & P., MANUALS, BATTERIES, etc. NOTHING ELSE TO PAY—FANTASTIC VALUE for MONEY.

Educational and Trade enquiries welcomed.

Personal callers welcome.

CHEQUE/P.O. (or 11p for illustrated literature) to: DEPT. PE

Satisfaction guaranteed
ELECTRONI-KIT LTD.

20 Bride Lane, Ludgate Circus, London EC4Y 8DX
Tel. 353 6430. Cables: Tronikit London

VALVE BARGAINS

Any 5-64p, 10-£1-20, 50-£5-00.
Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL-14, 6F28.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested.
35p each.

Aerial Splitters—2 way, 75 OHMS, Inside Type, £1-50

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11—For TH stereo and standard VHF/FM radio.

B12—For the older VHF television—Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs and sockets. Next to the set fitting.
£3-80

250,000

Capacitor Clearance Sale

ALL MULLARD C280 AND C281 RANGE OF POLYESTER FILM CAPACITORS 250 AND 400 VOLTS WORKING. VERY GOOD MIXED SELECTION OF VALUES FROM 0.01μ TO 1.5μ f.

PRICE 100 - £1-50, 500 - £7-00, 1000 - £12-00

ALL PRICES INCLUDE VAT. P&P 20p PER ORDER. PLEASE SEND UNCROSSED P.O. OR CHEQUES FOR RETURNING IF WE ARE OUT OF STOCK OF CAPACITOR BARGAIN PACKS. EXPORTS WELCOME AT COST.

ELECTRONIC MAILORDER LTD.

62 BRIDGE STREET, RAMSBOTTOM, BURY, LANCS.
Telephone: RAMS (070 682) 3036



CROFTON FOR USED VIDEO EQUIPMENT



Used Video Equipment bought and sold daily. If we do not have what you want, we enter your requirements on our register and advise you when it is available. U.H.F. Modulators supplied for connecting a camera directly to a domestic TV or Phillips V.C.R. Camera Kits for the enthusiast also in stock.

Fujinon Lens available.

Repairs of all types of Video equipment undertaken.


WHATEVER YOUR VIDEO REQUIREMENTS
FIRST CONTACT CROFTON

CROFTON ELECTRONICS LTD

Dept. E, 35 Grosvenor Road, Twickenham, Middx. Tel. 01-891 1923


SUPERSOUND 13 HI-FI MONO AMPLIFIER

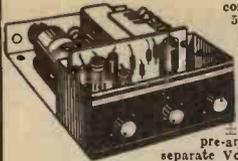A superb solid state audio amplifier. Brand new components throughout.




3 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz $\pm 3\text{dB}$. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 5" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £12-75. P. & P. £1-00.

DE LUXE STEREO AMPLIFIER

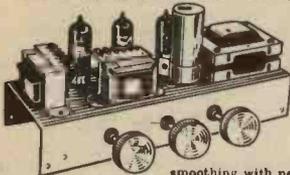

A.C. mains 200-240 v. Using heavy duty fully isolated transformer mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes, 1 x E230 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. £12-40. P. & P. £1-30.

HARVERSON STEREO 44

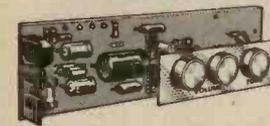

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume control, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" x 2 1/2" x 1" max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically), at only £29-00 plus 50p P. & P. Mains transformer with an output of 17V a/c at 500 mA can be supplied at £1-50 plus 40p P. & P. if required. Full connection details supplied.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-240-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-40v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2-90. P. & P. 90p.

MAINS TRANSFORMER. For power supplies. Fri. 200/240v. Sec. 9-0-9 at 500 mA. £1-50. P. & P. 60p. Fri. 200/240v. Sec. 12-0-12 at 1 amp. £1-65. P. & P. 60p. Fri. 200/240v. Sec. 10-0-10 at 2 amp. £2-35. P. & P. 90p. Fri. 200/240v. Sec. 23v. at 1.5 amp, 6v at 6 amp, 8v at 50 ma. £2-00 + 60p P. & P.

ALL PURPOSE POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 9v, and 12v, at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finlab metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. Price £6-75. P. & P. 85p.

STEREO-DECODER SIZE 2" x 3" x 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of brass and tips) supplied. £5-65 plus 20p P. & P. Stereo beacon light if required 40p extra.



QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £7-90. P. & P. 90p. ALSO AVAILABLE mounted on board with output transformer and speaker. Price £3-00. P. & P. £1-00.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State A/M F/M Stereo Tuner. Covering M.W. A.M. 540-1605 KHz, VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600 mV RMS into 30K. Simulated teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w. x 4" h. x 9 1/2" d. approx. LIMITED NUMBER ONLY at £28 + £1-30 P. & P.

SPECIAL OFFERS

Mullard LP1169 RF-IF Double Tuned Amplifier Module for nominal 470kHz. Size approx. 2 1/2" x 1 1/2" x 2 1/2" 7-6v + earth. Brand new e-aligned. Full specification and connection details supplied. £2-25 + P. & P. 12p.

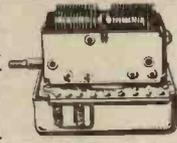Five VHF/FM Tuner 1 and covering 88-108MHz. 107MHz IF output 7-6v + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-ganged FM Gang and 323 Pf + 323 Pf AM Tuning Gang only £3-15 + P. & P. 35p.



PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O Interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/2" x 1". Supplied complete with chrome finished switch buttons 2 for £1-50 + 20p. P. & P.

HI-FI LOUSPEAKER SYSTEM Mk II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 8" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which). Handling power 10 watts R.M.S.

OUR PRICE £12-80 each. Carr. £1-90

Cabinet Available Separately £7-60 each. Carr. £1-40. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £11-10 each. Carr. £1-90.

LOUDSPEAKER BARGAINS

5in. 3 ohm £2-00. P. & P. 35p. 7 x 4in. 3 ohm £2-35. P. & P. 45p. 10 x 6in. 3 or 16 ohm £3-20. P. & P. 75p. 8 x 5in. 3 ohm with high flux magnet £3-00. P. & P. 50p. Tweeter. Approx. 21". Available 3 or 8 or 15 ohms. £2-00 + 25p. P. & P.

2" PLASTIC CONE HF TWEETER 4 ohm, £3-50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 ohm Dome Tweeter. 1" voice coil. Magnet size 3" dia. Suitable for use in up to 50 watt systems. £4-50 each + 60p P. & P.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS approx. 54 in. wide. Our price £1-80 yd. length. P. & P. 60p per yd. (min. 1 yd.). S.A.E. for samples.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, etc. and used with or without baffle. Send S.A.E. for details. Only £3-40 each. P. & P. 75p for one, 90p for two.

Now also available 8"-8 ohm. 10 watts r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1". Ideal for Hi-Fi or for use in cars. £5-10 + P. & P. (one 30p, two 65p).

LATEST ACOS GP1/180 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1-60. P. & P. 18p.


CERAMIC CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £1-90. P. & P. 18p.

SONOTONE 9TAH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Saphire 78. ONLY £2-36. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-86. P. & P. 18p.

LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1-90. P. & P. 18p.

LATEST T/MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-58. P. & P. 18p.

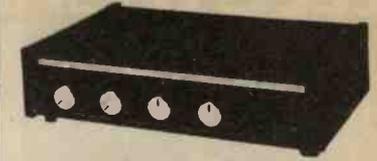HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Use 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response $\pm 3\text{dB}$ 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: $\pm 3\text{dB}$ 12-15,000 Hz. Bass, boost approx. to $\pm 12\text{dB}$. Treble cut approx. to -16dB . Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £13-50 P. & P. 65p (Magnetic input components 23p extra)
POWER PACK KIT £5-50 P. & P. 35p
CABINET £5-50 P. & P. 85p

Special offer—only £23-75 if all 3 units ordered at one time plus £1-00 P. & P.

Full after sales service
Also available ready built and tested £31-25. P. & P. £1-00.



3-VALVE AUDIO AMPLIFIER HA34 MK II


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates EOC83, EL84, E230 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4j watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £8-20. P. & P. £1-00.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £7-60. P. & P. £1-00.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.

Fully braced section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC83, EP86 and E230 rectifier. Simple instruction booklet 25p x SAE (Free with parts). All parts sold separately. ONLY £12-00. P. & P. £1-35. Also available ready built and tested £16-50. P. & P. £1-35.

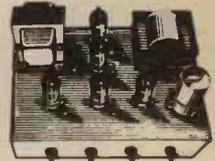

SPECIAL LINES OFFERED SUBJECT TO STOCK AVAILABILITY

Limited number of British Manufacturer's Surplus Professional 100 watt RMS Slave amplifiers. Special features: 2 separate power modules, 1 for Bass response, and 1 for mid. range/tweeter. 5 stage LED display for power o/p indication. A/c mains 1/p switchable for 110 or 240V. Can easily be converted to stereo. AVAILABLE TO PERSONAL CALLERS ONLY—PLEASE PHONE TO CONFIRM AVAILABILITY. Brand new and tested only £38-75.

OUR PRICES INCLUDE VAT AT CURRENT RATES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W. 19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



RECEIVERS AND COMPONENTS

Power Electrolytics, 800µF, 450V (value not stamped on can). Single end connections with screw terminals, 2 1/2 in dia. x 4 1/2 in high, including studs. Min. order, 4 for £2 inc. VAT (add 60p P. & P.). Sub-min. mains transformer, 12-0-12V, 50mA/22p. Mains transformer 0-12V, 100mA/45p. Bridge rectifier 2A/100V 40p. Phono plug to phono plug (6ft lead) 16p. Items 2, 3, 4 and 5, prices include VAT (add 20p P. & P.).

LINWAY ELECTRONICS

843 Uxbridge Road, Hayes End, Mddx., UB4 8HZ. Tel. 01-573 3677
Offers of company surpluses always welcomed. Cash settlement.

UP TO 50% discount on new components. SN-7486N 28p, 74107N 25p, 74121N 25p, 74366N 60p, 74174N 97p, 74175N 75p, 74180 75p, 74181N £2.30, 74190N £1.20, TMS 4030JL £4.50. List on request, other components available, orders under £5 50p P. & P. MALLEY ASSOC., 428 Staines Road, Bedford, MK15X.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V—0.47, 1.0, 2.2, 4.7 and 10µF 5p; 22, 47 5p (50V 6p); 100 7p (50V 8p); 220 8p (50V 10p); 470 11p (50V 16p); 1,000 (16V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p. Subminiature Bead Tantalum Electrolytic—0.1, 0.22, 0.47, 1.0, 2.2 at 35V, 4.7/25V 11p; 10/25V 13p, 22/16V, 47/6V and 100/35V 15p. Mullard Min. Ceramic E12 Series 63V 2%—10pF to 47pF—3p; 56pF to 330pF 4p. Vertical Mounting Ceramic Plate 50V—E12 series 22-1,000pF and E6 series 1,500-47,000pF 2p. Polystyrene E12 Series 63V Horizontal Mounting—10-1,000pF 3p; 1,200-10,000pF 4p. Mullard Polyester 250V Vertical Mounting E8 Series—0.01-0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 8p; 0.68 11p; 1.0 13p; 1.5 20p; 2.2 22p. Mrlar (Polyester) Film 100V Vertical Mounting—0.001, 0.002, 0.005 3p; 0.01, 0.02 4p; 0.04, 0.05 4p. Miniature Resistors Highest E12 Series 5%. Carbon Film 0.25W 10Ω to 10MΩ. (10% over 1M) 1p. Metal Film 0.125W, 0.25W and 0.5W 10Ω to 2MΩ 1p. Metal Film 1W 27Ω to 10MΩ 2p. 1N4148 3p; 1N4001 5p; 1N4006 7p; 1N4007 8p; BC107/8/9, BC147/5/9, BF157/8/9, BF194, 197 8p. Fuses 20mm glass, 2 1/2 in glass, 1 in ceramic 2 1/2 p. Post 10p (free over £4). Prices include VAT.

THE C.R. SUPPLY CO.

127 Chesterfield Road, Sheffield S8 0RN

P. E. GEMINI: transformers £11. 10-piece 16 s.w.g. metalwork systems, £15. Transistors £12.40, assorted new components, £20 value for £6 (including hardware and metalwork). Post paid. M. EVANS, 7 Shop Road, Worcester.

P.C.Bs Paxolin 5 1/2 in x 5 1/2 in, 6 for £1. 12 in x 9 in 70p. 17 1/2 in x 9 1/2 in, £1. Fibre glass 13 in x 5 1/2 in, £1. 13 in x 1 1/2 in, £1.75. D.S. 7 in x 8 in, 80p. Bank of 10 Neons with 10 x C407 transistors £1. Five figure Resettable Counter 18/22V works on 12V £3.10. P.S.U. panel 2 x 2N3702, 2 x AC153, bridge rect. electrolytics, etc 55p. Three assorted meters £2.10. 7 lb assorted components £2.75. List 15p. Refund on purchase. Over £1 post paid; under add 20p; insurance add 10p.

J. W. B. RADIO

2 Barnfield Crescent, Sale, Cheshire, M33 1NL

RESISTORS, capacitors, semiconductors, ics, potentiometers DIN sockets, plugs, cabinets, hardware. S.A.E. price list. R.B. ELECTRONICS, 24 Springfield Park, Hollyport, Maidenhead (Tel. 39798).

SMALL ADS

The prepaid rate for classified advertisements is 15 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £12.00 per single column inch (2.5cm). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IFC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

RESISTORS: AEL2 type carbon film high stab. 5% (E12 range). Sold in units of 10. 1/4W (4E7 to 2M2), 8p per 10; 1/2W (1E to 10M), 9p per 10. Also transistors BC108/9, 75p per 10. LEDs red, 12p; green and yellow, 20p. Type TIL200/FLV11 0.2in: potentiometers (Phillips/Egen) 1k, 4k7, 10k, 100k, 220k, 470k, 1M, 2M2. Lin/Log at 21p each + VAT (high rate) 12 1/2p, plus 20p postage. S.A.E. for more details to: GW ELECTRONICS, Dept. PE, 10 Kingsley Path, Britwell Estate, Slough, Berkshire. We also have a trade and export dept.

Precision Polycarbonate Capacitors

All High Stability—extremely Low Leakage

440 V C.R. RANGE				63V D.O. RANGE			
Value (µF)	Dimens (mm)	each	Price	Value (µF)	±1%	±2%	±5%
L	D						
0-1	27	12-7	88p	0-01-0-2	£1-28	75p	50p
0-15	27	12-7	80p	0-22-0-47	£1-32	77p	51p
0-22	33	16	86p	1-0	£1-56	91p	60p
0-25	33	16	92p	1-5	£1-74	116p	67p
0-33	33	16	99p	2-2	£1-98	132p	75p
0-47	33	19	£1-10	3-3	£2-40	£1-60	98p
0-5	33	19	£1-16	4-7	£2-82	£1-88	£1-23
0-68	50-8	19	£1-25	6-8	£3-48	£2-32	£1-47
1-0	50-8	19	£1-37	10	£4-98	£3-32	£2-01
1-5	50-8	25-4	£1-84	15	£7-14	£4-76	£2-88
2-0	50-8	25-4	£1-95	22	£9-68	£4-44	£3-90

TANTALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8µF at 15V/25V or 35V; 10-0µF at 16V/20V or 25V; 22-0µF at 6V/10V or 16V; 33-0µF at 6V or 10V; 47-0µF at 3V or 6V; 100-0µF at 3V. All at 12pF each, 10 for £1.10*, 50 for £5*, 100 for £9*.

TRANSISTORS & I.C.'s
BC107/8/9 8p *BC212/212L 22p 2N3055 50p
*BC114 12p *BC213/213L 11p OC71/2 20p
*BC147/8/9 10p *BC214/214L 10p *NF555Timer: 61p
*BC153 16p *BF194/5 12p *741C 8pin DIL 32p
*BC154/7/8/9 12p BF501/2 20p
*BC182/182L 11p AF178 40p ZN414 £1-15
*BC185/185L 11p AF239 38p SN76013ND
*BC184/184L 22p *2N3702/4 11p £1-50

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N915 8p, 6 for 45p, 14 for 90p; 184 6p, 11 for 50p, 26 for £1.00, 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p. LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. 3V; 3V3; 3V6; 4V7; 6V1; 5V6; 6V2; 6V8; 7V5; 8V2; 9V1; 10V; 11V; 12V; 13V; 13-6V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each, 5 for 33p, 10 for 65p, 50 for £3-12. SPECIAL OFFER: 100 Zeners (may be mixed) for £6-00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C, 1/2W at 70°C. E12 series only—from 2-2Ω to 2-2MΩ. ALL at 1p each, 8p* for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK; 10 of each value 2-2Ω to 2-2MΩ (730 resistors) 55*

SILICON PLASTIC RECTIFIERS—1-5 amp, wire-ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p). BRIDGE RECTIFIERS—2 1/2 amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0-1W only: All at 5p* each; 50; 100; 220; 470; 680 ohm; 1k; 2k; 4k7; 6k8; 10k; 15k; 22k; 47k; 100k; 320k; 680k; 1M; 2M5; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with * which are 12 1/2p. Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies. MARCO TRADING (Dept. P.3) The Old School, Edlaston, Wem, Shropshire. Tel: Whixall 464/465 (STD 094 872) (Proprs. Minicost Trading Ltd.)

VALVES—Radio, TV, industrial, transmitting. We dispatch to any part of the world by return of post, Air or Sea Mail. 2,700 types in stock. 1930 to 1970 obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers. Mon. to Sat. 9.30-5.00, closed Wed. 1.00. We purchase all types of new and boxed valves. COX RADIO (Sussex) Ltd., Dept. P.E., The Parade, East Wittering, Sussex, PO20 8BN. West Wittering 2023. (STD code 024366).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

COMPLETE COMPONENT SERVICE. Second to none, suppliers to D.O.E., A.E.R.E., U.K.A.E.A., Government departments, universities, schools and equipment manufacturers. All orders are despatched on day of receipt. Are you being served? Join the professionals and get this best service at the right prices. Stock list free, send S.A.E. Big catalogue 50p (includes 2 vouchers worth 50p). Discounts for the big spender, its all here! For the fastest friendly service—ORCHARD ELECTRONICS, Flint House, High Street, Wallingford, Oxon (0491-35529).

Brand New Components

Semiconductors			
Part No.	Value	Price	Part No.
AC126/7/8	14 BF194/5	11	2N1711
AD161/2	35 BF196/7	13	2N2219
BC107/8/9	8 BFY50/51	15	2N2904/5/6
BC147/8/9	8 BFX29	25	2N2926(R)
BC157/8/9	10 BFX24	20	2N2926(G)
BC167/8/9	10 M1255	96	2N3053
BC177	11 MPF102	33	2N3054
BC178/9	12 1N4001/2	3	2N3055
BC182/3/4L	11 1N4003/4	4	2N5459
BC212/3/4L	11 1N4005/6	6	NE555
BC170/71/72	13 1N4148	3	µA741 DIL
BD139	35 2N697	12	LM380
BD140	37 2N706	9	

Electrolytic Capacitors				
Value	25V	50V	50V	50V
25V	25V	50V	50V	50V
10	22	100	10	4-7
47	100	2-2	10	47
4p	5p	6p	4p	5p

Polyester Capacitors. 250V PC mounting. 0-01, 0-022, 0-033, 0-047, 3p; 0-068, 0-1, 4p; 0-15, 0-22, 5p; 0-33, 0-47, 8p; 0-68, 11p; 1-0, 13p; 1-5, 19p; 2-2µF, 22p.

Carbon Film Resistors. 0.33W 5% Hi-stability. E12 series 470-1M. Any selection. 0.9p each, 0.8p 100+; 0.75p 1000+.

Return of post service. Prices include VAT. Allow 15p for carriage. Mail order only. Export enquiries welcome.

C. N. Stevenson (PE)

304 Avery Hill Road, London SE9 2JN

SUPERSCOOP. Fully marked brand new semiconductors and goodies at bargain prices. Send S.A.E. for details and prices: DALESOUND, 15 Balcombe Road, Horley, Surrey, RH6 7JR.

R. T. SERVICES (MAIL ORDER ONLY)

75 Hayfield Rd., Salford 6, Lancs.

BRAND NEW S/S P.C. BOARD. 8 1/2 in. x 7 in. 5 pieces, £12 0/0.

PANEL with 6 2N3055 transistors plus 6 N.P.N. and 6 P.N.P. transistors £17 5 inc.

FM TUNER with R.F. Stage and A.G.C. 3 transistors, neg. earth 2 1/2 x 2 1/2 in with circuit, £17.5.

MAINS INPUT TRANSFORMERS 20V-0-20V at 2amp, £3.95. New. 6V at 1 amp, £1.45. New. 12V at 1/2 amp, £1.45. New.

Mixed Pack of C280 series Mullard capacitors, 100 for £1-15 inc., P. & P. Send S.A.E. for our list prices.

Tel. 061-236 1541
All prices include VAT and P. & P.

CARBON FILM RESISTORS. 5% E12 Series, 1/4W, 1/2W. Mixed to your choice, 100 for 90p. Microprocessors SC/MP £15, introtik £77, keyboard kit £74, MM6800 £27. P. & P. 15p. Mail order only. CANDAR, 8 Almond Drive, Caversham Park, Reading.

LEDs	Red	Green	Yellow	Orange	INFRA RED
0-125"	15p	27p	27p	27p	8mw £1-55
0-2"	19p	33p	33p	33p	ORP12 55p
					DCP71 40p
OPTO-ISOLATOR Ttl L1 LED + clip + 1p					
AC125/6/7/8	15p	SCR's	50V	100V	400V TRIACS
AD161/162	40p	TOS 1A	25p	27p	2A TOS 80p
AF117	20p	T066 3A	27p	35p	BR100 Diac 21p
AF124/5/6/7	34p	Stud 7A	50p	55p	10ATO220 £1-50
AF139/239	40p	2N3055	41p		
BC107/8/9	9p	2N3070/3/4	12p		
BC109C	12p	2N3903/4/5/6	16p		
BC147/8/9	10p	2N2646	45p		
BC157/8/9	11p	TIS43	25p		
BC167/19	11p	BF244	35p		
BC169C	12p	MPF102	40p		
BC177/8/9	17p	2N3819	25p		
BC182/3/4/L	11p	2N3823E	30p		
BC1887	30p	2N5450	40p		
BC212/3/4/L	12p	IN914	3p		
BC370/7/17/2	13p	IN918	3p		
BD131/32	40p	IN918	3p		
BD139/140	60p	IN4001	5p		
BF194/5	12p	IN4002/3	5p		
BF196/7	14p	IN4004/5	7p		
BF198/5/1	15p	IN4006/7	8p		
BF208	15p	IN4148	4p		
BFX84	24p	3A/50V	14p		
BSX19/20	16p	3A/100V	15p		
MJE2955	15p	3A/60V	22p		
MJE3055	15p	BA100	10p		
OC71	10p	BA156	12p		
2N697	15p	BAX12	9p		
2N706	10p	BY127	16p		
2N119	20p	OA47	5p		
2N1271	20p	OA70 OA79	9p		
2N1271	20p	OA81 OA90	7p		
2N2904/5/6/7	18p	OA91 OA95	6p		
2N2904/5/6/A	18p	OA200	6p		
2N2925(R)	7p	OA202	7p		
2N2925(G)	12p	ZENERS 2 7-33V	5p		
2N3053	15p	BZY88 or sim	3p		
2N3054	45p	Avdelbond 2gm	65p		

ISLAND DEVICES, P.O. Box 11, 19 Carraways Place, Margate, Kent. Morder only. Prices inc. + 15p P. & P.

FULL SPEC. TTL (Prices include VAT)					
7400	14p	7450/3/4	15p	74121	31p
7401/2/3	14p	7460	15p	74122	43p
7404/5	16p	7472	22p	74123	59p
7406	36p	7473/4/6	29p	74141	66p
7408	18p	7475	46p	74145	72p
7410/20	14p	7480	44p	74150	£1-10
7411/2	20p	7483	73p	74153	65p
7413	30p	7484	97p	74154	£1-10
7414	67p	7485	£1-03	74155	69p
7417	30p	7486	29p	74157	68p
7422	18p	7489	£2-40	74160	99p
7425/7	28p	7490	43p	74164	£1-10
7430/40	14p	7491	60p	74174	97p
7432	28p	7492/3	46p	74175	85p
7437	29p	7495	60p	74181	£2-40
7441	66p	7496	69p	74190	£1-25
7442	59p	74100	97p	74193	£1-08
7445/7/8	78p	74109	45p	74195	88p
DL707E 0-3In. displays 69p. IN4148 2p. Intel 2102A-6 (650ns) 1K Memories £3. Mullard OC28 (ex equip.) 20p, S/90, 50/£8. S.A.E. for full list. P. & P. (1st class) 20p. C.W.O. J. C. JONES (PE24) Mail order only 46 Burstellars, St. Ives, Cambs., PE17 4XX					

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 4188. Immediate settlement.

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains re-wiring required. Insulated Touch Plates. All with easy to follow instructions.

NEW! TSD300K—TOUCHSWITCH and DIMMER combined. ONE touch plate to switch light on or off. Brightness controlled by small knob. ONLY—£5-95.

TS300K—TOUCHSWITCH. TWO touch plates ON and OFF. ONLY—£3-67.

TSA300K—AUTOMATIC. One touch plate. Light turns off after preset delay. ONLY—£3-67.

LD300K LIGHT DIMMER KIT £2-45

SPECIAL OFFER
3-555 TIMER ICs for ONLY £1-00

CMOS (Motorola)

4000	16p	4013	51p	4040	97p
4001	16p	4015	91p	4049	48p
4002	16p	4016	51p	4077	45p
4007	16p	4017	91p	4501	20p
4011	16p	4023	17p	4519	56p
4012	17p	4025	19p	4566	155p

TRIACS 400V T0220	NE555 8 pin dil	36p
Case Isolated Tab	741 8 pin dil	24p
6-5A 80p 8-5A 85p	2N6027 (PUT)	34p
Diac 21p	2N3055	36p

QUANTITY DISCOUNTS ON REQUEST

Add 8% VAT + 25p. P. & P.

Mail order only to:

T. K. ELECTRONICS (PE)
106 Studley Grange Road, London W7 2LX

EIGHT-CHANNEL TRACE SPLITTER, converts single beam oscilloscope into 8-channel instrument. Accepts TTL or CMOS logic inputs up to 15V. Range d.c. to 5MHz, battery powered. Ready built £11-50, kit £9-25 inclusive. S.A.E. for leaflet. J. PAWSON, 4 Kalm Crescent, Bathgate, W. Lothian.

SPECIAL OFFER. 74H00 22p, 7490A 30p, 7474A 28p, 75450 50p, MJE3055 50p. ITT 58 70ST nixl + data 50p, 555 45p, Sperry SP425-09 9 digit 7 seg + data £1, SKT 50p, BYX49 1200V 2-5A 35p, R5 Fuse holder 1 1/2 in panel mnt 20p, TTL209 + clip 15p, 741 20p, IN4148 3p, BC108C 10p. P. & P. 10p. List S.A.E. L.B. ELECTRONICS, 43 Westacott, Hayes, Middx. UB4 8AH (PE).

VHF POCKET PORTABLE RADIO, tuning 108 to 138MHz. Very sensitive, easily adjusted to tune 144MHz band, £16-50 (inc. post and VAT). ROMAK LTD., 10 Hibel Road, Macclesfield, Cheshire.

LADDERS

LADDERS, varnished, 25 1/2 ft. extd., £30-41. Carr. £1-90. Leaflet. Immed. despatch. THE LADDER CENTRE (PEE3), Halesfield (1), Telford, Salop. Tel. 586644.

EDUCATIONAL

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 771G, Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 771G, Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 771G, Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

SITUATIONS VACANT

TECHNICAL AUTHORS. Small progressive company located in North London requires persons able to write functional English text from notes and drawings on a variety of digital equipment. Write to box No. 68.

SERVICE SHEETS

SERVICE SHEETS, radio, TV, etc. 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

SERVICE SHEETS, Radio, TV, etc. 50p and S.A.E. Catalogue 20p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for service sheets on radio, TV, etc., 75p plus S.A.E. Colour TV service manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55385.

FOR SALE

P.E. KEYBOARD SYNTHESIZER, 61-note Kimber-Alen keyboard, heavy duty power supply will take more circuits. Working, only requires case, £85 o.n.o. Mr. ALLINSON, 15 Shadforth Drive, Billingham, Cleveland. Tel. Stockton 561452.

NEW 188UES of "Practical Electronics" available from April 1974 edition up to date. Price 55p each—BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

FULLY BUILT large synthesiser. Perfect working order, based on ET1 4600. Plus extras, £550 o.n.o. Student hard up so must sell. Details: 101 Village Road, Bromham, Bedford.

MINISONIC Mk II. Fully built. 3 octave Kimber Allen keyboard. Eaton Audio P.C.B., £225 o.n.o. Tel. Brampton 2632 (Cumbria).

TWO MANUAL ORGAN. Working order, un-completed modifications, £55. Tel. 051-924 0988.

ORGAN CABINET. Dual keyboard, foot pedals—Unfinished Project. £60 o.n.o. Tel. Prestatyn 5605.

BARGAIN! APPROX. 150 copies P.E. & P.W. 1965-75 Mint condition—at least 5 complete volumes. Offer over £20 secure. Buyer collects. YEATS, 34 Woolmer Green, Basildon, Essex.

WANTED

WANTED. P.E. Synthesiser and P.E. Minisonic or other synthesisers. H. REEVES, 138 Blandford Avenue, Castle Bromwich, Birmingham 36 (021-747 8489).

TURN YOUR surplus components into cash. Tel. 0491-35529 (Oxon).

WANTED, NEW VALVES, TRANSISTORS, top prices, popular types—KENSINGTON SUPPLIES (B), 367 Kensington Street, Bradford 8, Yorkshire.

ELECTRICAL

8TYLI, CARTRIDGES AND AUDIO LEADS, etc. For the best at keenest prices send S.A.E. for free illustrated list to: FELSTREAD ELECTRONICS (PE), Longley Lane, Gatley, Cheadle, Cheshire, SK8 4EE.

MISCELLANEOUS

A UNIQUE OPPORTUNITY

We can show you how to earn a lot of money working part or full time from home. We are the ONLY company in the U.K. offering this unique information.

A basic interest in electrical engineering is necessary. Government Departments are making use of our system, why don't you? For complete return of post details send a large stamped addressed envelope to:

MAGNUM

Dept. PE

Brinksway Trading Estate
Brinksway, Stockport SK3 0BZ

NOW AVAILABLE for D.I.Y. Burglar Alarm Systems. The Lawrence Electronics Solid State Control Module, £6-50 inc. VAT, P. & P. or S.A.E. for full details on security equipment available. LAWRENCE ELECTRONICS, 78 Manningham Lane, Bradford, Yorkshire.

ARMATURE AND COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied.

All orders despatched within 24 hours.

S.W.G.	1 1/2 reel	1 1/2 reel
10 to 19	£2-95	£1-60
20 to 29	£3-15	£1-80
30 to 34	£3-45	£1-90
35 to 40	£3-65	£2-10

All prices inclusive of P. & P. In U.K.

COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20 Telephone 061-445 8753

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy-duty pvc faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 82p. Examples: width, depth, height, 8in. x 5in x 3in, £1.70; 10in x 6in x 3in, £2.42; 10in x 8in x 3in, £3.02; 12in x 10in x 3in, £3.96; 8in x 4in x 4in, £1.98; 10in x 6in x 4in, £2.97; 12in x 8in x 4in, £3.96; 7in x 7in x 5in, £2.91; 8in x 10in x 6in, £3.96; 12in x 8in x 7in, £4.40; 12in x 10in x 7in, £4.84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated): **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state **TRANSMITTER RECEIVER** kit. Only £8.25 plus 20p P. & P.

'Brain-freeze' 'em with a **MINI-STROBE** kit, pocket-sized 'lightning flashes', variable, for disco's and parties. A mere £3.80 plus 20p P. & P.

Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher: ready-made multi-function modules: £5 plus 20p P. & P. **LOTS MORE!** Send 20p for lists.

(Prices include VAT).
(Mail Order U.K. only).

BOFFIN PROJECTS

4 Cunliffe Road
Stoneleigh, Ewell, Surrey (P.E.)

CITIZEN'S BAND. British Campaign for Public 2-Way Radio. **CITIZEN'S BAND ASSOCIATION**, 16 Church Road, St. Marks, Cheltenham, Gloucs.

H.M. ELECTRONICS

275a Fulwood Road, Broomhill, Sheffield S10 3BD



BEC CABINETS

ORION cabinet still available punched or unpunched. Send 15p (refundable) for leaflets.

Give your project that professional looking finish. Build it in a BEC. Dry transfer lettering now available.

DO-IT-YOURSELF LOUDSPEAKERS for hi-fi are our speciality. Full range of components and accessories including chassis speakers, cross-overs, sound absorbent, grille fabrics, etc., always available. We stock the fabulous value Helms speaker kits (complete with full and easy instructions), also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 84p stamp for bargain list to: **AUDIOSCAN**, Dept. PE-677, 4 Princes Square, Harrogate, North Yorkshire.

ENAMELLED COPPER WIRE

SWG	1 lb	8oz	4oz	2oz
14-19	2.40	1.20	0.60	0.50
20-29	2.45	1.60	0.82	0.59
30-34	2.60	1.70	0.89	0.64
35-40	2.85	1.90	1.04	0.75

Inclusive of P. & P. and VAT.
S.A.E. brings catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY
P.O. Box 30, London, E4 9BW
Reg. Office: 22 Coningsby Gardens

PRINTED CIRCUIT BOARDS supplied in glass fibre drilled, tinned or varnished from your own or published designs. Send S.A.E. for quotations. **R. F. DARLISON**, 12 Whiteoaks Road, Oadby, Leicesters.

MAKE YOUR OWN PRINTED CIRCUITS

RUB-ON TRANSFERS—starter pack (5 sheets, lines, pads, I.C. pads) £1.30, spare sheets 27p. **FERRIC CHLORIDE**—1lb bags 70p (P. & P. 30p). **SOLDERCON SOCKETS**—100 65p (quantity rates). **PLASTIC SUPPORTS**—7 or 8 hole 6p/pair.

S.A.E. lists, sample. P. & P. 15p/order.

P.K.G. ELECTRONICS
Oak Lodge, Tansley, Derbyshire

Musical Miracles!

by **Dewtron** ®

Build your own synthesiser or musical effects using some of the huge range of **DEWTRON** modules. Or, build fuzz or waa-waa at budget prices using special kits.

Send 25p for Catalogue from:

D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AB.

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, L.E.D.s, and Instructions.

Available at £4.00 each (including P. & P.)
Kit One—Gates Kit Two—Flip-Flops
Kit Three—Shift Registers

Kit Four—Counters Kit Five—Displays
S.A.E. for further details to:
AUTOMATED HOMES

69 High Street, Ryton, Coventry CV8 3FJ
(Mail Order Only)

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

BUILD THE TREASURE TRACER

MK III Metal Locator



- Versicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and telephone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and nuts
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete Kit £14.75 Post £1 + £1.18 VAT
Built and tested Post £1 + £1.58 VAT

MINIKITS ELECTRONICS, 6c CLEVELAND ROAD
LONDON E18 2AN (Mail Order Only)

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fratcloths, Coverings, Recess Handles, Strap Handles, Feet, Castors, Locks and Hinges, Corners, Trim, Speaker Bolts, etc., etc.
Send 2 x 84p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)

Unit G, Starline Works, Grainger Road
Southend-on-Sea, Essex.

RECHARGEABLE NICAD BATTERIES "AA" (HP7), £1.26; Sub. "C" £1.28; "D" (HP1) £2.38; "D" (HP2) £2.92; PP3 £4.98. Matching chargers, respectively, £4.48, £4.48, £5.24, £5.24, £3.98. All prices include VAT. Add 10% P. & P. S.A.E. for full list, plus, if wanted, 50p for "Nickel Cadmium Power" booklet. **SANDWELL PLANT LTD.**, 1 Denholm Road, Sutton Coldfield, West Midlands, B73 6PP. Tel. 021-354 9764.

MORSE CODE TUITION AIDS

Cassette 3-1-12 w.p.m. for amateur radio examination.
Cassette 5-12-24 w.p.m. for professional examination preparation.

Morse by light system available. Morse Key and Buzzer Unit for sending practice. Prices: Cassettes (including booklets) £4; Morse Key and Buzzer £4. Prices include VAT, postage, etc., overseas £1 extra.

MHEL ELECTRONICS (PE)
12 Longshore Way, Milton, Portsmouth PO4 8LS

GLASS FIBRE P.C.B.'s

From your own tape, film or ink master.

Send S.A.E. for quotation.

PRACTICAL ELECTRONICS P.C.B.'s in glass fibre, tinned and drilled.

May 76 Digital Frequency Meter (GBCZW). Complete set of 4 boards £4.85.

June 76 Transmitter 98p, Coder 94p.

July 76 Receiver 98p, Decoder 79p.

Interface 58p, August 76 Servodrive 74p.

Servo Amp 58p, Relay Drive 68p.

Complete set of above boards £5.80.

Sept. 76 Tone Generator 71p, Tone Decoder 78p.

Cross-Hatch Generator £2.85.

Nov. 76 Hazard Warning Flasher 68p.

Dec. 76 Orion Tuner £2.48. Feb. 77 Decoder (1302-1) £1.32.

April 77 Digital Volt Meter (GBCZW) Complete set of two boards (£104-3/4) £2.55.

Send S.A.E. for information on current boards. C.W.O. please.

R.S. Components. All of this well known supplier's components available.

PROTO DESIGN

4 Highcliffe Way, Wickford, Essex SS11 8LA

SALVAGED TTL ICs from 7p. Good quality. S.A.E. for lists and samples. **BEUERER**, 17 Heald Close, Shawlough, Rochdale, Lancs.

WIRE THREADING KIT

WIRE DISTRIBUTION SYSTEM INTRO-KIT

£3.95 inc. of VAT and P. & P. (Mail order only)

KIT CONSISTS: WIRE DISTRIBUTION PENCIL, W-D BOARD, W-D STRIPS, SPARE SPOOL OF WIRE, IC LEG DEFORMER, COMPREHENSIVE INSTRUCTIONS.

Or for further details please send a S.A.E. Trade and overseas enquiries welcome.

ZARTRONIX 115 Lion Lane, Haslemere, Surrey GU27 1JL

METER REPAIRS. Ammeters, voltmeters, multi-meters, etc., contact: **METER REPAIRS**, 21 Mount Road, Benfleet, Essex, SS7 1HA.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs.

Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES

Masons Road, Stratford on Avon Warwick. Tel. 4879

RELAYS, PROGRAMMERS, etc. Send S.A.E. for list. Mr. D. HIPKIN, 194 Long Drive, Ruislip, Middx. (01-845 9065).

P.O.B.'s—FAST SERVICE FROM YOUR MASTER

1.6mm glass fibre + 1 oz copper + solder varnish £1.35 + 4p/sq.in. (VAT and P. & P. inc.). ±100 volt sweep amplifiers, £5.90 (VAT and P. & P. inc.). 10 cpw PCB with BUSS lines (24in x 14in)—DIP and TOS IC to 0.1in. edge conn adaptors—30p each, 10 up 25p each (add P. & P. 15p). S.A.E. for quantity discounts/specials, prototype service—circuit design, layouts, assay and test.

MICROINICS ELECTRONICS ENG. SERVICES
13a Olive Road, Birkdale, Southport, Merseyside, PR8 4RZ. Tel.: Southport (0704) 64855.

BURGLAR ALARM COMPONENTS. White oblong reed and magnet, 65p pair, minimum 10. Flush circular and magnet, 60p pair, minimum 10. 12V sirens, £4.88. Key Pass switches, £2.25. All prices inclusive. **COLIN WHITELEY**, 11 Denbrook Walk, Bradford, W. Yorkshire, BD4 0QS.

BOOKS AND PUBLICATIONS

SIMPLIFIED TV REPAIRS. Full repair instructions, individual British sets, £4.50; request free circuit diagram. Stamp brings details unique TV Publications. **AUSEPE**, 78 Church Street, Larkhall, Lanarkshire.

TLAs by TEXAS		C-MOS ICs		OP AMPS		Linear ICs		AC125 20p		BF200 40p		TIP42C 96p		2N3904/5 22p		VOLTAGE REGULATORS (Plastic) Fixed			
7400	18p	4000	21p	1458	75p	AY-1-0212	850p	AC126/7	20p	BF244/B	40p	TIP2955	76p	2N3906	22p	1Amp +ve			
74H00	30p	4001	21p	301A	40p	CA3028A	115p	AC128	20p	BF257/B	36p	TIS43	40p	2N4080	12p	5V 7805	130p		
74LS00	32p	4002	21p	3130	100p	CA3040	85p	AC141/2	20p	BFR39/40	34p	TIS93	30p	2N4123/4	22p	12V 7815	130p		
74S00	48p	4006	120p	3140	108p	CA3048	85p	AC176	20p	BFR41	34p	ZTX108	12p	2N4125/6	32p	15V 7815	130p		
7401	18p	4012	21p	324	225p	CA3053	75p	AC187/8	20p	BFR79/80	34p	ZTX300	16p	2N4401/3	24p	18V 7818	150p		
7402	18p	4017	21p	339	225p	CA3080	87p	AC187K	25p	BFR81	34p	ZTX500	20p	2N4427	97p	24V 7824	150p		
7403	18p	4018	21p	3800	78p	CA3089E	250p	AC188K	25p	BFR88	40p	2N697	25p	2N4471	60p	LM309K (TO3)	5V 1A, 160p; LM323K (TO3)	5V 3A, 700p; TBA625B (TO5)	12V 0.5A 120p; 7805 (TO3), 150p; 1468 Dual Preset ±15V
7404	24p	4019	21p	3900	78p	CA3090AQ	500p	AD149	85p	BFX29/30	34p	2N698	40p	2N5296	85p	16 pin DIL, 300p; LM327N Dual Polarity +ve, -12V 100mA 14 pin DIL	300p	LM317 1A 2V-37V TO220	340p
7404A	40p	4020	21p	4000	40p	ICL8038C	400p	AD181/2	39p	BFX84/85	34p	2N708/8	22p	2N5457/8	40p				
7405	25p	4021	21p	4001	40p	LM318N	250p	AF114/5	22p	BFY51	16p	2N918	43p	2N5459	40p				
7407	45p	4022	21p	4002	40p	LM380N	115p	AF116/7	22p	BFY52	16p	2N930	19p	2N6027	80p				
7408	25p	4023	21p	4003	40p	LM381N	190p	AF124	36p	BFY51	16p	2N1304/5	75p	2N6247	20p				
7409	27p	4024	85p	4004	40p	LM383N	150p	AF127	36p	BRY39	45p	2N1306/7	75p	2N6254	140p				
7410	18p	4025	21p	4005	40p	LM389N	150p	AF139	43p	BRY39	45p	2N1613	22p	2N6292	70p				
74H10	30p	4026	220p	4006	40p	LM390N	115p	AF239	48p	BRY39	45p	2N1613	22p	2N6292	70p				
7411	28p	4027	81p	4007	40p	LM391N	150p	BC107/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7412	28p	4028	152p	4008	40p	LM392N	150p	BC108/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7413	36p	4029	120p	4009	40p	LM393N	150p	BC109/C	11p	BRY39	45p	2N1613	22p	2N6292	70p				
7414	96p	4030	59p	4010	40p	LM394N	150p	BC110/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7418	35p	4031	110p	4011	40p	LM395N	150p	BC111/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7417	40p	4032	110p	4012	40p	LM396N	150p	BC112/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7420	18p	4033	55p	4013	40p	LM397N	150p	BC113/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7421	43p	4034	100p	4014	40p	LM398N	150p	BC114/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7422	27p	4035	150p	4015	40p	LM399N	150p	BC115/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7423	38p	4036	150p	4016	40p	LM399N	150p	BC116/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7425	33p	4037	110p	4017	40p	LM399N	150p	BC117/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7427	40p	4038	100p	4018	40p	LM399N	150p	BC118/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7430	18p	4039	150p	4019	40p	LM399N	150p	BC119/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7432	34p	4040	110p	4020	40p	LM399N	150p	BC120/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7437	37p	4041	80p	4021	40p	LM399N	150p	BC121/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7438	27p	4042	54p	4022	40p	LM399N	150p	BC122/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7440	18p	4043	100p	4023	40p	LM399N	150p	BC123/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7441	85p	4044	110p	4024	40p	LM399N	150p	BC124/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7446	75p	4045	140p	4025	40p	LM399N	150p	BC125/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7443	130p	4046	120p	4026	40p	LM399N	150p	BC126/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7444	130p	4047	29p	4027	40p	LM399N	150p	BC127/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7445	108p	4048	25p	4028	40p	LM399N	150p	BC128/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7446	108p	4049	80p	4029	40p	LM399N	150p	BC129/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7448	80p	4050	54p	4030	40p	LM399N	150p	BC130/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7450	20p	4051	180p	4031	40p	LM399N	150p	BC131/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7451	20p	4052	140p	4032	40p	LM399N	150p	BC132/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7452	20p	4053	140p	4033	40p	LM399N	150p	BC133/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7453	20p	4054	140p	4034	40p	LM399N	150p	BC134/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7454	20p	4055	140p	4035	40p	LM399N	150p	BC135/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7455	20p	4056	140p	4036	40p	LM399N	150p	BC136/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7456	20p	4057	140p	4037	40p	LM399N	150p	BC137/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7457	36p	4058	140p	4038	40p	LM399N	150p	BC138/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7458	36p	4059	140p	4039	40p	LM399N	150p	BC139/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7459	36p	4060	120p	4040	40p	LM399N	150p	BC140/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7460	20p	4061	25p	4041	40p	LM399N	150p	BC141/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7461	20p	4062	25p	4042	40p	LM399N	150p	BC142/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7462	20p	4063	25p	4043	40p	LM399N	150p	BC143/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7463	15p	4064	25p	4044	40p	LM399N	150p	BC144/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7464	15p	4065	25p	4045	40p	LM399N	150p	BC145/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7465	15p	4066	25p	4046	40p	LM399N	150p	BC146/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7466	36p	4067	25p	4047	40p	LM399N	150p	BC147/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7469	340p	4068	25p	4048	40p	LM399N	150p	BC148/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7480	43p	4069	25p	4049	40p	LM399N	150p	BC149/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7481	108p	4070	25p	4050	40p	LM399N	150p	BC150/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7482	85p	4071	25p	4051	40p	LM399N	150p	BC151/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7483	85p	4072	25p	4052	40p	LM399N	150p	BC152/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7484	103p	4073	25p	4053	40p	LM399N	150p	BC153/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7485	130p	4074	25p	4054	40p	LM399N	150p	BC154/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7486	36p	4075	25p	4055	40p	LM399N	150p	BC155/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7489	340p	4076	25p	4056	40p	LM399N	150p	BC156/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7490	43p	4077	25p	4057	40p	LM399N	150p	BC157/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7491	81p	4078	25p	4058	40p	LM399N	150p	BC158/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7492	55p	4079	25p	4059	40p	LM399N	150p	BC159/B	10p	BRY39	45p	2N1613	22p	2N6292	70p				
7493	43p	4080	25p	406															



THE "Manta" CAPACITIVE DISCHARGE ELECTRONIC IGNITION UNIT

THE NEW, HIGHER RELIABILITY VERSION OF THE P.E. "SCORPIO MK II" IS NOW AVAILABLE IN KIT FORM!! Our thousands of satisfied customers report:

More miles per gallon (customers reports give 10%-25% saving—letters available)

An increase in overall performance—your 4 cylinder car feels like a 6 cylinder

No more cold morning splutters—saves you even more petrol through much less use of choke.

The price? A snip at only £16.50, fully inclusive of all parts, instructions, postage/packing and V.A.T. (ready built unit available—£19.85 fully inclusive)

All parts to high specification, first quality and brand new

Construct this invaluable accessory, following our easy step by step instructions (also available separately, price 30p post paid). Send for our free interesting six page brochure—"Electronic Ignition—How it Works" (S.A.E. Please) to:

ELECTRO SPARES

Dept. P.E., 187a Sheffield Road, Chesterfield, Derbyshire
S41 7JQ. Telephone: Chesterfield (0246) 36638

G8CZW Digital Frequency Meter



Complete 50MHz
kit £54.00 inc.
VAT, post free
(U.K.)

	£		£
ZN1040E Count/Display I.C.	8-10	Hardware and Wire Pack	1-45
Integrated Circuit Pack	9-25	Case, Two-tone p.v.c.-faced steel, punched and lettered (+95p P. & P.)	5-75
Displays and Filter Pack	7-78	Min BNC Sockets (50 ohm)	0-85
Semiconductor and Diode Pack	2-38	Min BNC Plugs (50 ohm)	0-70
Resistor and Capacitor Pack	2-98	500MHz Prescaler Kit	1-78
Logic and Display P.C.B.s	4-84	SP8631B 500MHz I.C.	8-96
5MHz Crystal	3-45	NE592 Wideband Video Amp	1-43
Transformer 8-0-0V 0-5A (+75p P. & P.)	2-48	Hi-Z Buffer Kit	3-62
Switches, Knob, BNC's etc.	4-15	D.F.M. Reprint (post free)	0-50

G8CZW Digital Voltmeter



Complete kit
£44.30 inc. VAT,
post free (U.K.)

	£		£
ZNA116E 3 1/2 Digit I.C.	6-48	Hardware and Wire Pack	1-20
Integrated Circuit Pack	5-24	Case, Two-tone p.v.c.-faced steel, punched and lettered (+95p P. & P.)	5-75
Displays and Filter Pack	7-78	I.C. Sockets Pack	1-08
Semiconductor and Diode Pack	2-60	Transformer (+75p P. & P.)	2-48
Resistor Pack Inc. cermet	4-64	5V Reg., 2 Rect., 2,000µF Cap., Mains SW., Fuse and Holder	3-75
Capacitor Pack	1-58	D.V.M. Reprint (post free)	0-35
Logic and Display P.C.B.s	2-05		
Voltage Attenuator Pack	0-68		
Range Switch 6P. 4-way	2-38		

All prices inc. VAT at the standard rate. Please add 20p P. & P. for packs. S.A.E. for full lists. Overseas—Deduct 8% off these prices.

Designer
approved



ELECTRONICS (OLDHAM) LTD.
83 Lees Road, Oldham OL4 1JW
Tel. 061-624 8812

INDEX TO ADVERTISERS

A.B.C. Electronics	472	Electrospares	472	Osmabet	462
Adam Hall (P.E. Supplies)	470	Electrovalue	460	Phonosonics	414, 415
Alben Engineering	411	Flairline Supplies	462	PKG Electronics	470
Alcon Instruments Ltd.	406, 465	Greenbank Electronics	410	Precision Petite Ltd.	412
Astro Electronics	415	Greenweld Electronics	410	Proto Design	470
Automated Homes	470	Harversons	467	Pulse Electronics	411
Bamber, B., Electronics	434	H.B. Electronics	461	Radio Component Specialists	cover ii
Barrie Electronics	404	H.M. Electronics	470	Ramar Constructor Services	470
Bi-Pak	408, 409	Home Radio	404	RST Valve Mail Order Co.	402
Bi-Pre-Pak	407	I.L.P. Electronics Ltd.	413	R.T. Services	468
Birkett, J.	416	International Electronics Unlimited	416	Saxon Entertainments	403
Boffin Projects	470	Intertext ICS	416, 469	Scientific Wire Co.	470
British National Radio & Electronics School	433	Island Devices	469	Service Trading Co.	cover iii
Bywood	406	Jones, J. C.	469	Sinclair Instruments Ltd.	429
Cambridge Learning	411	Josty Kit (UK) Ltd.	465	Special Products Distributors Ltd.	465
Chillmead Ltd.	412	J.W.B. Radio	468	S.S.T. Distributors	406
Clef Products	460	Lektropaks	410	Stevenson, C. N.	468
Copper Supplies	469	Linway Electronics	468	Swanley Electronics	430
Crescent Radio Ltd.	464	Lynx Electronics	430	Tamba Electronics	462
Crimson Elektrik	471	Magnum Publications	469	Technomatic Ltd.	471
Crofton Electronics	466	Maplin Electronic Supplies	cover iv	Tempus	402
C.R. Supply Co.	468	Marco Trading	468	T.K. Electronics	469
Davian Electronics	458	Marshall, A., & Sons	463	Trampus Electronics Ltd.	460
D.E.W. Ltd.	470	Metac Electronics	458	T.U.A.C.	405
Doram	402, 434, 464, 471	MHEL Electronics	470	Williams, Michael	412
Eagle International	434	Microics Electronics Eng. Services	470	Wilmslow Audio	459
Eaton Audio	471	Minikits Electronics	470	Zartronix	470
Electronic Design Assoc.	464	Modern Book Co.	462		
Electronic Mail Order	466				
Electronic Supplies	460				
Electron-kit	466				

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock, phone or write in your enquiries.

FT3 NEON FLASH TUBE

High intensity multi turn, high voltage, neon glow, discharge flash tube. Design for ignition timing, etc. £1.50. P. & P. 25p. 3 for £3.00. P. & P. 50p.




NI-CAD BATTERIES

	Height (mm)	Width (mm)	Length (mm)
16AH Metal £3	163	55	27
23AH Plastic Case £4	214	79	27
35AH Metal £6.50	219	75	29
40AH 1.2V Plastic Case £8	275	80	35

21 WAY SELECTOR SWITCH WITH RESET COIL. The ingenious electro mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil. 230/240V a.c. operation. Unit is mounted on strong chassis, complete with cover. Price £5.50. P. & P. 75p.

NEW HEAVY DUTY SOLENOID.

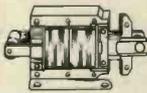mfg. by Magnetic Devices. 240V a.c. operation approx. 20lb pull at 1.25in. Price £7. P. & P. 75p. Similar to above approx. 10lb pull £3.50 P. & P. 60p.



UNISELECTOR SWITCHES

4 bank, 25 way 75 ohm. Coil, 36-48V d.c. operation. Ex. New equipment £4.25. P. & P. 75p. Total price inc. VAT £5.40.



MINIATURE UNISELECTOR

12 volt 11-way, 4 bank (3 non-bridging, 1 homing). £2.50, p.p. 35p.

RODENE UNISET TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding, mixing, etc. Price £6 P. & P. 60p.



MICRO SWITCH

Sub miniature Burgess Button Type V.A.T.I. 10 for £2.50, 50 for £10. Post paid. Sub min Honeywell roller m/s type 3115m 90¢, 10 for £2.50 post paid. BF LEVER OPERATED 20amp, C/O. Mfg. by Unimax USA, 10 for £4. P. & P. 50p (min. order 10).



24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two x approx. 1lb pull ½ inch travel. 6 x approx. 4oz. pull ½ inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £3.00. Post £1. ABSOLUTE BARGAIN.

VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max. air delivery of 1.5 cubic metres per min. Max. static pressure 600mm W.G. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions: length 22cm x width 25cm x height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12 + £1.50 P. & P. Suitable transformer for 230/240V a.c. £6 + £1 P. & P.



INSULATION TESTERS

NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 500V, 500 megohms, £40. Post 80p. 1,000V, 1,000MΩ, £46. Post 80p.



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

- 200 watt (1 amp) inc. AC voltmeter £11.50
- 0.5 KVA (2½ amp) (MAX) £14.00
- 1 KVA (5 amp) (MAX) £18.00
- 2 KVA (10 amp) (MAX) £30.00
- 3 KVA (15 amp) (MAX) £38.00
- 4 KVA (20 amp) (MAX) £60.00



L.T. TRANSFORMERS

- 0-12V/24V at 1 amp, £2.50 (P. & P. 50p).
- 0-15V at 1 amp + 0-15V at 1 amp (30V 1 amp), £2.50 (P. & P. 50p).
- 25-0-25V at 2½ amp, £4.50 (P. & P. 75p).
- 0-12V/24V 10 amp, £12.35 (P. & P. £1.50).
- 0-4V/6V/24V/32V at 12 amp, £13 (P. & P. £1.50).
- 0-12V at 20 amp or 0-24V at 10 amp, £12.40 (P. & P. £1.50).
- 0-6V/12V/17V/18V/20V at 20 amp, £14 (P. & P. £1.50).
- 0-6V/12V at 20 amp, £11.85 (P. & P. £1).

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes £18. Post 75p. Specially designed case and reflector for Hy-Light £8.25. P. & P. £1.

XENON FLASHGUN TUBES

Range available from stock. S.A.E. for details.



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt, £7.00 (callers only). 2ft 20 watt, £5.00. Post 60p. (For use in standard bi-pin). MINI. 12in 8 watt, £1.75. Post 25p. 9in 6 watt, £1.40. Post 25p. 6in 4 watt, £1.40. Post 25p. Complete ballast unit and holders for 6in, 9in and 12in tube, £3.50. Post 40p. Also available for 12V d.c. operation, £3.50 plus P. & P. 40p.

GALVANOMETER

50 micro mirror galvo. Calibrated 50-0-50 and 0-100. Mfg. by Griffon & George Ltd. Offered at a fraction of maker's price, in original ministry packing. £12. P. & P. 60p.




WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (Footscap) for details.

CONTACTOR

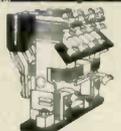mfg by Hendrey Relays type C2839 220/250 AC ops. Contact 4C/O at 20 amp at 440 volts AC price £6.00. P. & P. 75p.



RESET COUNTER

230 volt AC 3 digits mfg Veeder Root type LL/1441 £1.75. P. & P. 25p.



BIG INCH

Tiny precision built 3RPM USA motor size only 1 x 1 100 volt AC op supplied with resistor for 230 volt AC price £2.00. P. & P. 20p. 4 for £5.00 post paid.



VAT

AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

GEARED MOTORS

100 r.p.m. 115 lb.in. 110V, 50Hz. 2-8A, single phase, split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250 mm. Dia. 135 mm. Spindle dia. 15.5 mm. Length 145 mm. Ex-equipment tested £12. Post £1.50. Suitable transformer 230/240V operation £8. Post 75p.



CITENCO

FHP motor type C 7333/15 220/240 volts AC 19RPM reversible motor, torque 14.5 kg gear ratio 144-1 brand new incl. compactors, our price £14.25. P. & P. £1.25.



BODY TYPE N.C.I.

(Type J) 71 r.p.m. torque 10 lb.in. Reversible 1/70th h.p. 50Hz. The above precision made U.S.A. motor is offered in 'as new' condition. Input voltage of motor 115V A.C. Supplied complete with transformer for 230/240V A.C. input. Price, either type £6.25. Post 75p or less transformer £3.75. Post 60p. (Type J) 71 r.p.m. 4 lb.in. 230V a.c. Continuously rated. Reversible. £6.50. Post 75p.

15 R.P.M.

Type SD48 80 lb. in. Input 100/200 volt A.C. Length incl. gearbox 270 mm. Height 135 mm. Width 150 mm. drive shaft 16 mm. Weight 8.5 Kilos. BRAND NEW. Price £10. Carr. £1. Suitable transformer for use on 220/240 volt A.C. £3.85. Post 50p.

24 R.P.M. 230V a.c. Continuously rated. Mfg. Mycalex. Ex-equip. Fully tested, £3.85. Post 75p.

1 R.P.M. 230/240V A.C. SYNCHRONOUS! Ex-equipment. Thoroughly tested and guaranteed. ONLY £1.50. Post 20p.

20 R.P.M. 230/240 volt a.c. miniature motor. Price £1. Post 20p.

PROGRAMME TIMERS

230V operations c. 15 or 20 r.p.m. 6 cam model £5. Post 60p. 12 cam model £7.50. Post 60p. Also available for 50V operation. Prices as above.



METERS NEW—90 mm Diameter

Type: 65CS D.C. M/C 2, 5, 10, 20, 50 amp. £3. 100 amp £3.25. 20p. Type: 62T2 A.C. M/I 1, 10, 50 amp. £3. Post 20p. 0-150 volt. A.C. M/I £3.25 and 300 volt A.C. R/M/C. £3. P. & P. 30p.



WHY PAY MORE?!

MULTI RANGE METER. A.C. volts 2.5-500. D.C. volts 2.5-500 (Sensitivity 3000Ω/V D.C. and A.C.) D.C. current 0/1/10/100 mA. Ohms range. Sturdy compact moving coil instrument with 21 ranges, dimensions 120 x 80 x 44 mm. Weight 0.32 kg. SERVICE TRADING CO. Price £5.50. incl. leads and battery. Post 50p. (Total price incl. VAT and Post £6.48).



TIME SWITCH

'Horstmann' Type V Mk. II Time switch. 200/250 volt A.C. Two on/two off every 24 hours, at any manually preset time. 30 amp contacts. 36 hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board Spec. Individually tested. Price £7.75. Post 50p. (Total inc. VAT £8.91)



Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated. 25 WATT 10/25/50/100/150/250/500/1k/1.5k ohm. £1.90. Post 20p. 50 WATT 100/250/500/1k ohm. £2.40. Post 25p. 100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £3.70. Post 35p. Black Silver, Skirted knob calibrated in Nos. 1-9 1½in. dia. brass bush. Ideal for above 22p each.



Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

All Mail Orders—Callers—Ample Parking
Dept. PE11, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

MAPLIN



The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet—they're coming soon), but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.




This high quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us (except woodwork) including drilled and printed metalwork. Construction details in our leaflet: 15p.

We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system, which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches—there are dozens to choose from, but it's only a tiny part of our fantastic range.

A completely self-contained pedal unit. 13-note, 2-octave range, 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!

Play fascinating games NOW on your own TV in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets—anyone could win—with Maplin's prices everyone can win. All parts at remarkably low prices (I.C. alone £11.99). Send for our latest newsletter for details. All prices include VAT and P. & P. Complete kit £24.50. Please add 35p to kit price for copy of constructional details.

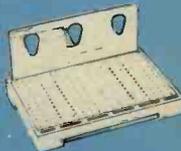

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller! **DON'T MISS OUT! SEND 50p NOW!**

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 50p

Please rush me a copy of your 216 page catalogue by return of post. I enclose 50p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 50p refunded immediately.

NAME _____

ADDRESS _____



MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 47379