

PRACTICAL

# ELECTRONICS

DECEMBER 1977

45p



*Also inside... Your INDEX for Volume 13*



# PRACTICAL ELECTRONICS

VOLUME 14 No. 4 DECEMBER 1977

---

## CONSTRUCTIONAL PROJECTS

- CAR BURGLAR ALARM** *by M. J. O'Leary*  
Easy to install system which triggers the horn and lights 242
- 128 NOTE SEQUENCER** *by D. G. Evans*  
Final construction and use of the unit 246
- P.E. CHAMP—4** *by R. W. Coles and B. Cullen*  
Constructional details of CHAMP board and plinth 268
- P.E. MASTERMIND—5** *by P. F. Turney*  
Final section of the scoring logic is covered, together with the display logic 278

## GENERAL FEATURES

- INGENUITY UNLIMITED**  
Leading Zero Suppression—Polarity Protector—"True" Snap—Car Lights Alarm—  
Lamp Failure Indicator—Battery Condition Indicator 275

## NEWS AND COMMENT

- EDITORIAL**—The Way Things Go—Non-Crystal Ball—Switching Off 241
- MICRO-BUS** *by DJD*  
Real-time from the air, chess computer and cheap D/A converter 250
- NEWS BRIEFS**  
Infrared Sound—Home TV Terminal—SERT Symposium 252, 260, 266
- SPACEWATCH** *by Frank W. Hyde*  
Sails In The Sunset, Space Shuttle, Jupiter 253
- MARKET PLACE**  
Interesting new products 254
- SEMINAR**  
Two day course on MPU systems design 255
- INDUSTRY NOTEBOOK** *by Nexus*  
What's happening inside industry 256
- HOME ENTERTAINMENT SHOW**  
Some of the attractions at this new exhibition 259
- BOOK REVIEWS**  
Selected new books we have received 260, 267
- POINTS ARISING**  
Digital Reaction Timer 286
- INDEX FOR VOLUME 13** 263

Our January issue will be on sale Friday, 9 December, 1977  
(for contents see page 245)


---

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



# LOOK! Here's how you master electronics




... the practical way

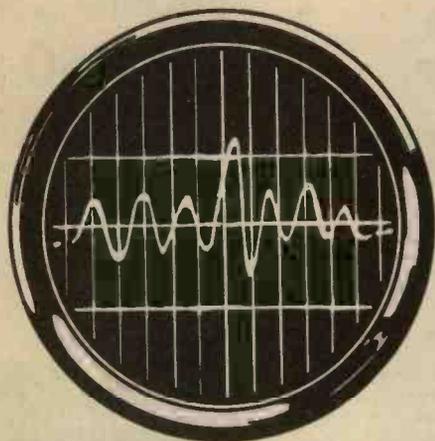

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

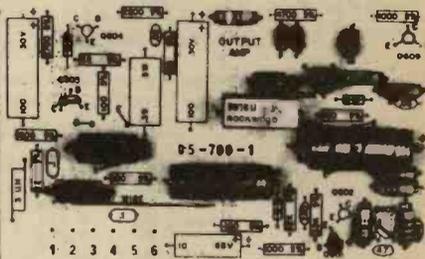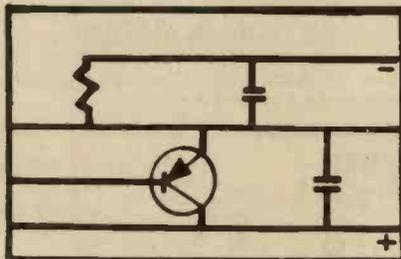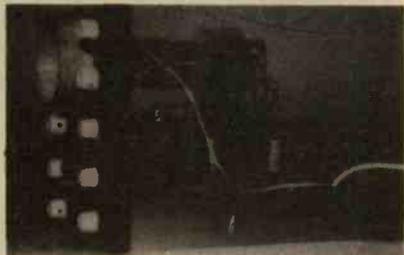All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



## 1 Build an oscilloscope

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

## 2 Read, draw and understand circuit diagrams

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

## 3 Carry out over 40 experiments on basic circuits

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

**Free!**

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

### British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME .....

ADDRESS .....

PEB12

Block caps please

# SAXON ENTERTAINMENTS LTD

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT  
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

## CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,  
TWIN SPEAKERS & LEADS

### Standard 100W

**£225** or Deposit **£28.80**  
12 Months @ £21.38 or 24 Months @ £12.01

### Super 200W

**£275** or Deposit **£32.80**  
12 Months @ £26.13 or 24 Months @ £14.67

### GXL 200W (with twin 200 watt cabinets)

**£349** or Deposit **£42.72**  
12 Months @ £32.78 or 24 Months @ £18.40

BSR Decks - 17,000 Line Loudspeakers - Rugged Aluminium Trimmed Cabinets - Cue Light And Phones  
Output - Slave Output - Deck Lights/Motor Starts (GXL)

COMPLETE STEREO  
ROADSHOWS - BUILT IN  
SOUND TO LIGHT/SEQUENCER  
& DISPLAY

TWO YEAR  
GUARANTEE

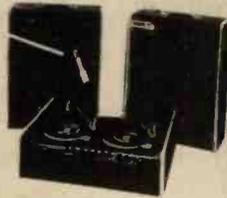


Illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & mic with monitoring facilities - override and are supplied complete with sound to light + sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

## MINI DISCO 100 WATT MONO SYSTEM

**£159.50** Deposit **£22.66**

12 Months @ **£14.73**  
or 24 Months @ **£8.27**

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system	£7.50
EM507 Electret Mic	£15.00
ECM 81 Electret Mic	£19.95
Boom Stand	£15.50
Carriage on all disco systems	£10.00
(Included in H.P. Prices)	

**10% Deposit Terms  
On All Orders  
Over £150 - 12 or 24  
Months - Low Interest**

### D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS

SA308 30W 8 ohms 45V	£9.95*	SUPPLY FOR TWO MODULES	£10.90*
SA604 60W 4 ohms 50V	£13.25	SUPPLY FOR TWO MODULES	£13.50
SA608 60W 8 ohms 65V	£14.25	SUPPLY FOR TWO MODULES	
SA1204 120W 4 ohms 75V	£15.95	SUPPLY FOR ONE MODULE	£22.50
SA1208 120W 8 ohms 95V	£21.00	SUPPLY FOR TWO MODULES	
SA2404 240W 4 ohms 95V	£29.50	SUPPLY FOR ONE MODULE	

0.2% Distortion, 30Hz-20, KHz ± 2dB, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers - D.C. & Output Fuses fitted.

TOP QUALITY COMPONENTS THROUGHOUT



### DISCO MIXERS - COMPLETE OR MODULAR



MONO OR STEREO  
WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE:  
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.


MODULES	
Mono module	£22.50
Stereo module	£33.50
Panel	£3.95
Kit of knobs/sockets etc	£5.50
COMPLETE MIXERS (with case)	
Mono 18V	£39.50
Stereo 18V	£57.50
Mono mains	£45.75
Stereo mains	£63.75
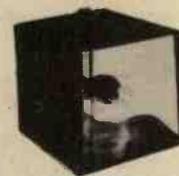
### COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!



Lighting Control Unit Mk II £44.50  
4kW Sequencer + Sound Light + Dimmers  
+ Automatic Level Integrated Logic Module £32.50  
Circuitry Panel £2.95

Three Channel Sound to Light £26.75  
3kW 1-240W input - master Module £19.75  
Plus channel controls Panel £2.95



### STROBE UNITS

Pro-Strobe 4-6 Joules £37.50  
Super Strobe 2-3 Joules £22.50  
(Pro-Strobe has external trigger facility).

### SPARES & ACCESSORIES - LOUDSPEAKERS & CABINETS

Rope Lights - Red or Multicolour	£22.00	Melos Echo Chomber	£59.00
per 12 ft.		Headphones	£7.50*
Rope Light Controller for up to 120 ft	£30.00	Sirens: English Police, USA Police,	
Fuzz Lights - Red/Blue/Yellow/Green	£22.80	Destroyer	£8.90
Magnetic Cartridge Equalisers	£3.50*	Bulgin 8 way lighting plug/socket	£1.90

### PROJECTORS - PLUTO -

### CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten	£37.50	Liquid wheels	£7.50
P500 100W Q.I.	£79.50	Cassettes	£8.00
P500 250W Q.I.	£89.50	Picture wheels from	£5.00
		(Wide choice available)	

100 Watt Chassis Loudspeakers 12" £23.50 18" £47.50 (Add £1.50 corr.)  
Empty Loudspeaker Cabinets: Small 12" £14 Large 12" £18 Small 2 x 12" £22  
Large 2 x 12" £28 1 x 18" £28

Projector lamps: A1167 £2.90. M6 £5.65.  
100W Spot lamps Red/Blue/Yellow/Green  
£1.50 ea £13.50 for 10  
Spot banks: 3 way £7.50 6 way £11.50  
12 way £18.50  
Bubble machines (optokinetics) £36.50


Strobe tubes 80W £8.50  
ICI Vynide 50" wide £3.50 Metre  
Kickproof Grille 24" wide £3.25 Metre  
Kick Resistant Grill 50" wide £3.25 Metre.  
FULL RANGE OF RE-AN PRODUCTS IN STOCK  
SEND FOR OUR BROCHURE NOW!!

### PIEZO HORNS only £7.50 YES! - only £7.50

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an  
UNBEATABLE PRICE

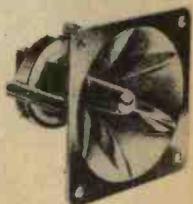No crossover required 4kHz - 30kHz rated  
75W/8 ohms 150W/4 ohms use two per 100W  
amplifier - Full instructions supplied.





# BD 103 - The Connoisseur's Professional Choice

An exceptional transcription unit that performs to truly professional standards. Fitted with a new specially designed arm, the BD 103 will form the start, or an integral part, of a system for those who never believed they could achieve this level of quality at a reasonable price, simply compare specifications. \*Low voltage DC servo controlled motor with electronic speed variation on all 3 speeds - 33 $\frac{1}{3}$ , 45 and 78 rpm. \*Externally housed power source, thereby eliminating hum fields, convertible for 120 or 230v mains supply. \*Belt drive with precision ground natural rubber moulded belt of round cross section. \*Neon illuminated stroboscope underneath 12" aluminium turntable is viewed through a mirror in the platform; available with either 50 or 60Hz stroboscope. \*Pick-up arm automatically raises at the end of the playing section of the record. Automatic lift-off can be overridden for non-standard records. \*Low friction pick-up bearings - unipivot for horizontal motion, knife edges for vertical motion - with a unique system of magnetic stabilization on the unipivot bearings. \*Playing weight adjusted by sliding weight on arm tube, which is calibrated. Additional counter weights provided for accommodation of a full range of cartridges. Adjustable magnetic bias, calibrated for varying playing weights. \*Inter-changeable lightweight plug in head shell accepts cartridges with  $\frac{1}{2}$ " mounting centres. The turntable unit is solidly mounted on to a walnut plinth, which stands on a sprung and damped anti-vibration suspension system, thereby using maximum

mass to improve performance, and fitted with a hinged acrylic dust cover with lid stay.

Dimensions: 15" x 18" x 5 $\frac{1}{4}$ ".

An alternative version is available without the pick-up arm and lifting device, incorporating a larger walnut/plastic cover, enabling most high quality pick-up arms to be used.

Dimensions: 15" x 18" x 7".

BD 103 Alternative unit without arm and lifting device.



The BD 103 Transcription turntable and External Power unit

## Connoisseur

Write for further details to:

A. R. Sugden & Co. (Engineers) Ltd.

Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road,

Brighouse, West Yorkshire HD6 1ES


Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden G,

Telegrams & Cables: Connoisseur Brighouse.

# V-Q
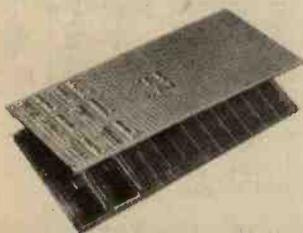
## WAS MADE FOR YOU

VERO QUAD BOARD was designed to provide a simple circuit board capable of accepting nearly all types of integrated circuits, plus transistors, resistors, capacitors and many other components.



ASK FOR V-Q - IT WAS MADE FOR YOU

No track cutting. 1,624 holes on 0.1" x 0.1" matrix. Packed complete with layout sheet. Fits Vero Plastic Cases 1237, 1238 and 1239. Costs about 90p from your local shop or mail order company.

Send for our booklet describing many other products made for you, S.A.E. 7" x 9" plus 10p to:

VERO ELECTRONICS LTD. RETAIL DEPT.  
INDUSTRIAL ESTATE, CHANDLERS FORD,  
HANTS. SO5 3ZR.

# VERO

## PE SUSTAIN UNIT



BUILD A SUSTAIN UNIT EQUAL TO THE BEST COMMERCIAL MODELS.

COMPLETE KIT - £7.95

ALL HIGH QUALITY COMPONENTS AS SPECIFIED.

DESIGNER APPROVED.



**ORION**  
tuner

Complete set of semiconductors

£4.99

LP1186 Tuner Head

£9.60

Gloss fibre PCB, printed with component locations

£2.45

**ORION**  
amplifier

Complete set of semiconductors

£9.40

Glass fibre PCB, printed with component locations

£2.99

## PE DIGITAL VOLTMETER (APRIL 1977)

ZNA116 \*£6.00 with circuits and data

Complete set of all semiconductors for the P.E. DVM including I.C.'s, transistors, diodes, displays, regulator, etc. Set of two professional grade glass fibre P.C.B.'s printed with component locations

£20.50\*

£3.40\*

Complete set of resistors, incl. attenuator resistors

£1.00\*

Complete set of capacitors incl. 2200µF power supply

£1.60\*

## PE TV SOUND SEPARATOR

Complete set of semiconductors £2.30, High quality glass fibre p.c.b. £1 POSTAGE AND PACKING 15p per order. Orders over £5 post free. All devices are top grade, brand new and to full manufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list. Prices do not include VAT—add 8% to items marked\*, and 12½% to all others

DAVIAN ELECTRONICS (MAIL ORDER ONLY)

13 Deepdale Avenue, Royton, Oldham OL2 6XD

# 15-240 WATTS!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

**APPLICATIONS:** hi-fi; mixers; disco; guitar and organ; public address.

**SPECIFICATION:** Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; input impedance 47k $\Omega$  at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble  $\pm$ 12dB at 10kHz; bass  $\pm$ 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— $\pm$ 16-50V.

Price  $\pounds$ 5.22 + 65p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



## HY30 15W into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

**FEATURES:** complete kit; low distortion; short, open and thermal protection; easy to build.

**APPLICATIONS:** updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

**SPECIFICATION:** Output Power—15W R.M.S. into 8 $\Omega$ . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price  $\pounds$ 5.22 + 65p VAT. P. & P. free

## HY50 25W into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

**APPLICATIONS:** medium power hi-fi systems; low power disco; guitar amplifier.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 25V. Size—105 x 50 x 25mm.

Price  $\pounds$ 6.82 + 85p VAT. P. & P. free



## HY120 60W into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

**APPLICATIONS:** hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 35V. Size—114 x 50 x 85mm.

Price  $\pounds$ 15.84 +  $\pounds$ 1.27 VAT. P. & P. free

## HY200 120W into 8 $\Omega$


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

**FEATURES:** thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

**APPLICATIONS:** hi-fi; disco; monitor; power slave; industrial; public address.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 45V. Size—114 x 50 x 85mm.

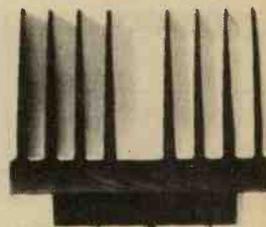Price  $\pounds$ 23.32 +  $\pounds$ 1.87 VAT. P. & P. free



## HY400 240W into 4 $\Omega$


The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** thermal shutdown; very low distortion; load line protection; no external components.

**APPLICATIONS:** public address; disco; power slave; industrial.

**SPECIFICATION:** Output Power—240W R.M.S. into 4 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

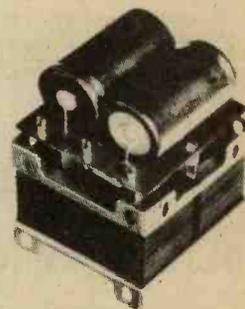Price  $\pounds$ 32.17 +  $\pounds$ 2.75 VAT. P. & P. free



**POWER SUPPLIES:** PSU36—suitable for two HY30s  $\pounds$ 5.22 + 65p VAT. P. & P. free. PSU50—suitable for two HY50s  $\pounds$ 6.82 + 85p VAT. P. & P. free. PSU70—suitable for two HY120s  $\pounds$ 13.75 + 1.10 VAT. P. & P. free. PSU90—suitable for one HY200  $\pounds$ 12.85 +  $\pounds$ 1.01 VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400  $\pounds$ 23.10 +  $\pounds$ 1.85 VAT. P. & P. free.

I.L.P. Electronics Ltd., Crossland House, Nackington, Canterbury, Kent CT4 7AD

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

**I.L.P. Electronics Ltd.**  
Crossland House,  
Nackington, Canterbury  
Kent CT4 7AD  
Tel (0227) 63218

Please supply .....

Total Purchase price .....

I Enclose: Cheque  Postal Orders  Money Order

Please debit my Access account  Barclaycard account

Account number .....

Name and Address .....

Signature .....

Registered office No. 1032630







Do-it-Yourself Kits Or Factory Assembled

- WERSI Organs
- WERSI Pianos
- WERSI String Ensembles
- WERSI MATIC Rhythm
- WERSI MATIC Accompaniment
- WERSI VOICE Rotor Sound-String Choir
- WERSI Professional Series
- WERSI Audio Mixer 2004
- WERSI TONE Rotating Baffles
- WERSI Speaker Cabinets

Send for our 104 page full-colour catalogue and 16-page price list, for £2.00, which is refunded against your first order value £25.00.

**AURA SOUNDS (P2),**  
Cophthorne Bank, Crawley, W. Sussex.

IC's 	TRANSISTORS 	RESISTORS 
DESPATCHED ON DAY ORDER RECEIVED		
SWITCHES 	LAMPS 	PLUGS/SOCKETS 



**ORDERING IS EASY WITH THE UNIQUE COMBINED CATALOGUE/ORDER FORM**

ACE MAILTRONIX LTD  
Dept. PE, Tootal Street  
Wakefield, W. Yorkshire WF1 5JR

SEND STAMP ADDRESSED ENVELOPE NOW FOR THE EASY TO USE ACE ORDER FORM CONTAINING 500 TOP QUALITY POPULAR ELECTRONIC COMPONENTS AT PRICES YOU CAN AFFORD. P&P FREE ON ORDERS OVER £2, OTHERWISE 20p. ALL PRODUCTS GUARANTEED ONE YEAR IF CORRECTLY USED. SOME EXAMPLES FROM THE COMPETITIVE ACE RANGE WITH VAT INCLUSIVE PRICES ARE SHOWN BELOW

BC107/108/109 Metal	13p	1/4W Resistors CF ±5%	3for 6p
BC207/208/209 Plastic	11p	Minpresets Horiz./vert.	8p
2N3055	65p	Electrolytic 100µF 25v	10p
741 Op Amp - 8pin	30p	Polyester C280 0.1F	8p
555 Timer	50p	LED Red 0.2"	15p
W04 1A Bridge	31p	Phono plugs	8p
7400 TTL	15p	Mintoggle SPST	80p
IN4148 Diode	4p	Wire - PVC Stranded 10m	25p
IN4001 Rec	5p	Veroboard 0.1-2.5x3-75	50p
BZY88 Zeners	12p	S-DEC Breadboard	216p

**Get an ACE up your sleeve!**

# Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 1/2 in x 8 1/2 in and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

*Design of Digital Systems.*



**£7.10**

plus 90p packing and surface post anywhere in the world.

Overseas customers should send for proforma invoice

Quantity discounts available on request. VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic.

*Digital Computer Logic and Electronics*

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

**£4.60**

plus 90p P. & P.

Offer Order both courses for the bargain price £11.10, plus 90p P. & P.—a saving of £1.50.

**Designer  
Manager  
Enthusiast  
Scientist  
Engineer  
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

**NEW** from Cambridge Learning Enterprises:  
**FLOW CHARTS AND ALGORITHMS**—use, design and layout; vital for computing, training, wall charts, etc. **£2.95** plus 45p P. & P.

**Guarantee**—If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, FREEPOST, Unit 2, Rivermill Lodge, St. Ives, Huntingdon, Cambs. PE17 4BR

To: Cambridge Learning Enterprises, FREEPOST, Unit 2, Rivermill Lodge, St. Ives, Huntingdon, Cambs. PE17 4BR

\*Please send me . . . set(s) of Design of Digital Systems at £8.00 each, P. & P. included

\*or . . . set(s) of Digital Computer Logic and Electronics at £5.50 each, P. & P. included

\*or . . . combined set(s) at £12.00 each, P. & P. included

\*or . . . the Algorithm Writers Guide at £3.40 each, P. & P. included

Name .....

Address .....

\*delete as applicable

No need to use a stamp—just print FREEPOST on the envelope.

PE12

# KITS FOR SYNTHESISERS, SOUND EFFECTS



**COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

**CIRCUIT AND LAYOUT DIAGRAMS** are supplied free with all PCBs designed by Phonosonics.

**PHOTOCOPIES** of the P.E. texts for most of the kits are available—prices in our lists.

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

## P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, output amp and mixer, power supply.

Set of basic component kits from £64.25  
Set of printed circuit boards £9.71

## P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser Complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage, notably P.E. Minisonic, Phasing Unit, Wind and Rain, Rhythm Generator, Sound Bender, Voltage Controlled Filter, Guitar Effects Pedal and Overdrive, Fuzz, Tremolo and Wah-Wah units.

**The Main Synthesiser:** PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp. Full details in lists.

Set of basic component kits £83.03  
Set of printed circuit boards £13.20

**The Synthesiser Keyboard Circuits** (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and additional PSU. Full details in our lists.

Set of basic component kits £48.18  
Set of printed circuit boards £7.66

## GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £5.59  
Alternative component set with panel mounting switches £4.96  
Printed circuit board £1.43

## SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include: envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) £7.84  
Printed circuit board £1.81

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

Component set (incl. PCB) £2.88

## PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2.87

## PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4.48

## SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektron", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set £17.69  
Printed circuit board £2.33

## WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3.55

## AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.27  
Component set and PCB, with panel switches £4.83

## P.E. JOANNA (P.E. May/Sept. 75)

A five-octave electronic piano that has switchable alternative voicing of Honky-Tonk piano, ordinary piano, harpsichord, or a mixture of any of the three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The power amplifier typically delivers 24 watts into 8 ohms. The PCBs have been redesigned by ourselves making improved use of the space available.

Main power supply, tone generator, 61 envelope shapers, voicing and pre-amp circuits.

Set of basic component kits for above £75.29  
Set of printed circuit boards for above £20.35  
Power amplifier £15.97  
Printed circuit board for power amp 95p

## ELECTRONIC ORGAN

5-octave electronic organ with 5 basic voices that can be used individually or together, 5 pitches (2ft, 4ft, 8ft, 16ft, 32ft), variable attack, tremolo, vibrato, phasing, and variable sustain. Details in our list.

## ORGAN CONVERSION KIT

Converts the P.E. Joanna electronic piano to also provide most of the facilities offered by the above electronic organ.

Basic component set and PCB £12.34

## SYNTHESISER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl. sw.) £7.45

## GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Details in list.

SEE OTHER PAGE FOR KEYBOARDS, AND OUR LISTS FOR OTHER COMPONENTS AND ACCESSORIES STOCKED

## WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £3.72

## GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £6.86  
Component set using dual rotary pot £6.20  
Printed circuit board £1.62

## FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £2.03

## TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £3.64

## TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2.40

## P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic and electronic musical instruments alike.

Main component set (incl. PCB) £15.59  
Power supply set (incl. PCB) £7.03

## P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duple, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.

Component set (incl. loudspeaker) £11.62  
Printed circuit board £2.04

## TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

Standard tolerance set of components £2.96  
Superior tolerance set of components £3.78  
Regulated power supply (will drive 2 sets) £4.69

## ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) £4.66

## ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6.68

## TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set £4.52  
Printed circuit board £1.82

## WAVEFORM CONVERTER

Slightly modified from a circuit published in a German edition of "Elektron". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw's) £8.19

## VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 65-1) £8.22

## RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 59-1) £5.50

## NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 60-1) £3.35

## SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

## MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl. PCB) £3.78

## VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

## DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4.58

## POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £2.00 plus VAT.

Optional insurance for compensation against loss or damage in post, add 35p in addition to above post and handling.

Else, C.I., B.F.P.O., and other countries are subject to Export postage rates.

## DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

**EXPORT ORDERS** are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 40p.

PHONOSONICS · DEPT. PE5N · 22 HIGH STREET · SIDCUP · KENT DA14 6EH MAIL ORDER AND C.W.O. ONLY SORRY BUT NO CALLERS PLEASE



**NEW**

8th EDITION

# BEGINNER'S GUIDE TO RADIO

GORDON J. KING



Introduces the reader in easy step-by-step stages to all aspects of radio technology, from simple electromagnetic theory to the full range of radio components and circuits.

Completely rewritten and updated, the 8th edition contains all the latest developments in radio technology.

Written in a non-technical style with a minimum of mathematics, this new edition will develop the reader's knowledge and interest and enable him to use radio equipment with confidence and skill.

- \* **CONTENTS:** Electricity and magnetism. Radio signals. Signal propagation and reception. Transmitter principles. Receiver principles. Radio components. Valves, solid-state devices and transistors: Integrated circuits. Microphone, pickup and loudspeaker. Modern radio receivers. Index.

\* Sept. 1977 . 240 pages . £2.75



Order now from your local bookseller or from:

**NEWNES TECHNICAL BOOKS**  
Borough Green, Sevenoaks, Kent TN15 8PH

ANOTHER RECENT TITLE  
**Beginner's Guide to Integrated Circuits**  
I.R. Sinclair

**CONTENTS:**  
What is an Integrated Circuit?  
Production of i.c.s.  
Simple Voltage Amplifier i.c.s.  
Simple Digital i.c.s.  
MOS i.c.s.  
Domestic Uses of i.c.s.  
Other Specialised i.c.s.  
Practical Construction  
Index  
1977 192 pages  
£2.75

# PHILIPS



**NEW!**

The latest catalogue from S.S.T. includes even more Philips electronic home assembly kits - mixers, amplifiers, speakers, etc. etc. Plus P.B. Electronics Dec and Blob-Boards for circuit proving and construction. Send today to: S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London, N17 0RN.

**ELECTRONIC KITS**  
direct from S.S.T. Distributors

Plus BREADBOARD, BLOB-BOARDS and ACCESSORIES

# free

**SEND TODAY!**

Please send me, quickly, the new S.S.T. Catalogue.

S.S.T. Distributors is a member of the Philips Group of Companies.

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Postcode \_\_\_\_\_

PE/A/12/77



# Wilmslow Audio


**THE firm for speakers!**

**SEND 10p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST**

ACT ● AUDAX ● BAKER  
 BOWERS & WILKINS ● CASTLE ● CELESTION  
 CHARTWELL ● COLES ● DALESFORD  
 DECCA ● EMI ● EAGLE ● ELAC ● FANE  
 GAUSS ● GOODMANS ● HELME ● I.M.F.  
 ISOPHON ● JR ● JORDON WATTS  
 KEF ● LEAK ● LOWTHER ● MCKENZIE  
 MONITOR AUDIO ● PEERLESS ● RADFORD  
 RAM ● RICHARD ALLAN ● SEAS  
 TANNOY ● VIDEOTONE ● WHARFEDALE

**WILMSLOW AUDIO (Dept. P.E. 8)**  
**SWAN WORKS, BANK SQUARE, WILMSLOW,**  
**CHESHIRE SK9 1HF**

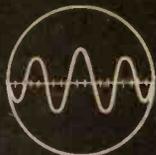Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street  
Tel.: Wilmslow 29599 for Speakers Tel.: Wilmslow 26213 for Hi-Fi



# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING  
CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE  
correct at 1/9/77

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE127) or quote  
Access/Barclaycard No. and post to TUAC LTD. (PE127) 119  
Charlmont Road, London SW17 9AB. We accept phone orders  
from Access/Barclaycard Holders. Phone 01-672 9080.

## PRE AMPLIFIERS

Designed for use with TUAC power amplifier modules.



### VA08

Vol. Treb. Mid. and Bass controls. HI. IMP. FET. I/P suitable Mid.  
Guitar, Radio Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at  
16kHz. Mid +20 -15dB at 1kHz. Bass +20 -10dB at 40Hz.

£9.00

### VA06

Vol Treb. and Bass controls. Sensitivity 8mV. Treb +28 -15dB at  
12kHz. Bass ±18dB and 40Hz.


£7.75

### SVA08 STEREO PRE AMP

Vol. Treb. Mid and Bass controls. I/P suitable Guitar, Radio,  
Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +  
20 -7dB at 4kHz. Bass +20 -18dB at 30Hz Plus Full Balance Control.  
Fully I/C operation supply voltage ±25VDC.

£15.00


## POWER SUPPLIES

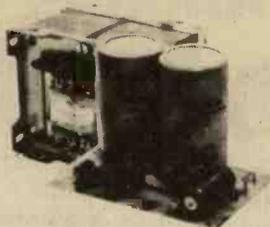

Vacuum varnish impregnated. Transformers  
with supply board incorporating pre-amp supply:

PS250 for supplying 2 TP125s	£28.50
PS200 for supplying 2 TP100s	£28.50
PS60/60 for supplying 2 TL60s	£25.00
PS125 ±45 volts for TP125	£17.75
PS100 ±43 volts for TL100	£16.25
PS60 ±38 volts for TL60	£15.25
PS30 ±25 volts for TL30	£11.75
PSU 2 for supplying disco mixer	£7.50

## AMPLIFIER MODULES

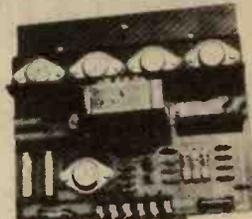

### TL30 D.C. COUPLED 5 x 5 1/4 in.

- 35 watt R.M.S. continuous sine wave output
- 8 transistors 4 diodes

£12.75

### TL60 5 x 5 3/4 in

- 60 watt R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£18.25

### TL100

- 100 watt R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors


£20.75

### TP125 7 x 6 1/2 x 3 in

- 125 watt R.M.S. continuous sine wave output
- 4 R.C.A. 150 watt 15 amp output transistors

£25.75
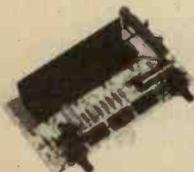
## 4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSMI



- Full wave control
- RCA BA Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/4W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£20.75

Model 501 500W per channel as above without  
sound triggering

£12.25

## FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)  
as illustrated



For S1LMB £6.50  
Size 8" x 4 1/2"




4LSM1 £5.50  
Size 6 1/2" x 4 1/2"



FUZZ LIGHTS  
Red, Green, Blue,  
Amber. £23.50



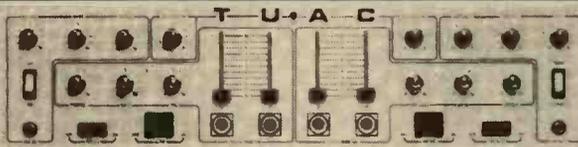S1LMB £7.50  
Combined with 3SDM1  
Size 9" x 4 1/2"



## STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls ±18dB at 60Hz. Treble controls ±18dB at 15kHz.

OUTPUT: Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz ± dB.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.


Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions

Size: 25in long x 6in high x 3in deep.

Mono Disco Mixer with autofade £45.00

£129.00

## 3 CHANNEL LIGHT MODULATOR SILMB

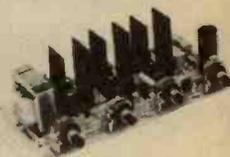

## new from TUAC... ULTRA QUALITY HIGH POWER TD 500 POWER AMPLIFIER New DC coupled design

Output power using PS250

300w into 2 Ohms

220w into 4 Ohms

140w into 8 Ohms

75w into 15 Ohms

RMS continuous sine wave

output

INPUT Sensitivity 0.775V

RMS (ODB) at 25 KOHMS

Hum and Noise - 100dB

Relative full output

THD = at Full Power 0.1%



7" x 9" x 1 3/4" £45

## PIEZO SUPER HORN . . . . £10.95

### STOCKISTS - CALLERS ONLY

- A1 Music, 88 Oxford Street, Manchester (Tel. 061-236 0340)
- Geo Mathews, 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)
- Bristol Disco Centre, 25 The Promenade, Gloucester Road (Tel. Bristol 41666)
- Socodi, 9 The Friars (Tel. Canterbury 60948)
- Cookies Disco Centre, 132 West Street (Tel. Crewe 4739)
- Garland Bros. Ltd., Deptford Broadway, London 01-692 4412
- Luton Disco Centre, 88 Wellington Street, Luton (Tel. Luton 411733)
- Mitchell Electronics, 7 Queen Street (Tel. Salisbury 23689)

Session Music, 163 Mitcham Road, Tooting (Tel. 01-672 3413).  
Mon-Sat 10 a.m. - 6 p.m. Closed Wed.

- RCA BA Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.25

Single Channel Version 1500 Watts

£9.75

## ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel


3SDMI

£14.50

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED  
SEND NOW FOR OUR FREE 20 PAGE ILLUSTRATED CATALOGUE. S.A.E. STAMPED PLEASE
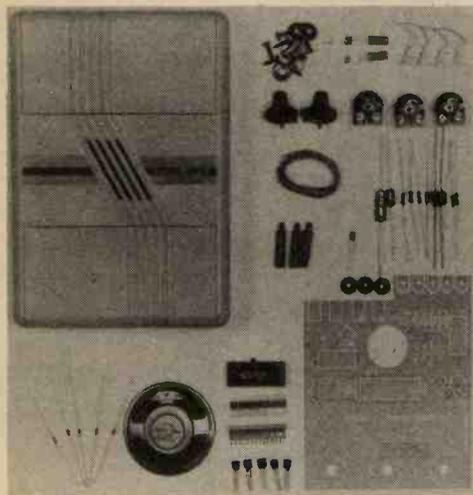
# Build a microprocessor electronic musical door chime which can play 24 different tunes!

*A complete Chroma-Chime Kit for only £18 inc. p.&p. & VAT.*



- \* A great introduction to the fascinating world of microcomputers.
- \* Save pounds on normal retail price by building yourself.

Plays:

Greensleeves  
God Save the Queen  
Rule Britannia  
Land of Hope and Glory  
Oh Come All Ye Faithful  
Oranges and Lemons  
Westminster Chimes  
Sailor's Hornpipe  
Beethoven's "Fate Knocking"  
The Marseillaise  
Mozart  
Wedding March

Cook House Door  
The Stars & Stripes  
Beethoven's Ode to Joy  
William Tell Overture  
Soldier's Chorus  
Twinkle, Twinkle Little Star  
Great Gate of Kiev  
Maryland  
Deutschland uber Alles  
Bach  
Colonel Bogie  
The Loralie

\*These tunes play longer if the push button is kept pressed.

- \* Handsome purpose built ABS cabinet
- \* Easy to build and install
- \* Uses Texas Instruments TMS1000 microcomputer
- \* Absolutely all parts supplied including I.C. socket
- \* Ready drilled and legended PCB included
- \* Comprehensive kit manual with full circuit details
- \* No previous microcomputer experience necessary
- \* All programming permanently retained is on chip ROM
- \* Can be built in about 3 hours!
- \* Runs off 2 PP3 type batteries.
- \* Fully Guaranteed

The Chroma-Chime is the world's first electronic musical door chime which uses a pre-programmed microcomputer chip to generate tunes. Instead of boring old buzzes, dings or dongs, the Chroma-Chime will play one of its 24 well known tunes from its memory using its tiny 'brain' to all the music synthesizing! Since everything is done by precise mathematics, it cannot play the notes out of tune.

The unit has comprehensive built-in controls so that you can not only select the 'tune of the day' but the volume, tempo and envelope decay rate to change the sound according to taste.

Not only visitors to the front door will be amazed, if you like you can connect an additional push button for a back door which plays a different tune!

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

The CHROMA-CHIME is exclusively designed by

## CHROMATRONICS

River Way, Harlow, Essex.

To CHROMATRONICS, River Way, Harlow, Essex, U.K.

Please send  Chroma-Chime Kits at £18.00 each including VAT and post and packing

PLEASE USE BLOCK CAPITALS

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I enclose cheque/PO value £ \_\_\_\_\_  
or debit my ACCESS/BARCLAYCARD account No. \_\_\_\_\_

Signature \_\_\_\_\_

N.B. The CHROMA-CHIME is also available, fully assembled, price £24.95 inc VAT and post and packing.

Please allow 7-21 days for delivery.

## THE WAY THINGS GO

As the year approaches its end a little ruminating may not be amiss. Around 1967 PRACTICAL ELECTRONICS was but a few years old and we were all still busily engaged in exploring the uses of the transistor, when the integrated circuit became generally available and started to alter the pattern of circuit design. Today we find ourselves in a somewhat parallel situation to the late 1960s, with the microprocessor now marking the latest revolution in the far from placid history of electronics.

As would be expected, microprocessors have made their initial impact in the industrial and the Service areas, and only just now are these devices beginning to appear in consumer products. Amongst the very first of this kind is a 24-tune door chime. (The designer is in fact a past contributor to this magazine.) To follow, we are promised intelligent toys and combination door locks, according to one speaker at a recent Texas Instruments Seminar. *Hurrah for technology!* Yes, we will not be surprised if some eyebrow-raising greets these disclosures.

We can also make a disclosure. Amateur-inspired combination lock circuits have been an editor's embarrassment ever since TTL chips became cheap and abundant. Like several other popular circuit ideas, they had more worth as design than in any real-life use.

Looking back, it is amusing to recall that P.E. has in the past been accused by a few individuals of encouraging the alleged "frivolous" use of electronics.

Evidently, if this is done on a large enough scale and turns into profitable business, the frivolity can be overlooked! The real truth is that, paradoxically, the more advanced the technology the easier it becomes to apply it to what some might consider trivial or frivolous purposes. Thus does electronics perform as a major conditioner of all our affairs.

At this particular moment one certainly gets the impression that microprocessor makers are still groping around for ways to use their latest wonder devices. Large and potentially valuable areas have indeed been marked out for attention. One such is the motor car industry, but to fully implement the use of the latest in electronics in a non-electronic industry is bound to take time.

Various smaller-scale developments are happening of course, often on a modest budget, perhaps in rather unpretentious laboratories. Some examples came to light during the SERT Symposium last September. It became clear that cash constraints and the inability to purchase the very latest in MPUs are no deterrent to enthusiasm among dedicated workers, especially if the goal is something really worthwhile and of likely benefit to mankind, as for example in the medical field.

Serious amateur experimenters are kindred spirits to these professional "loners" and will also have their contributions to make in this latest area of our technology. Here it might be pertinent to say that the biggest memory and the fastest MPU are not necessarily the best for every purpose. The Mini has not been rendered obsolescent by the TR7.

## NON-CRYSTAL BALL

From the present, a peep into the future. What will be the next milestone in electronics?

The award of the Nobel Prize for Physics to Sir Nevill Mott (shared with two American physicists) for work on amorphous materials at Cambridge naturally reawakens interest in the use of non-crystalline materials, particularly glass, as the basis for a new generation of semiconductor devices. Low cost is the chief virtue of glass as a semiconductor and one possible application relates to solar cells. It is being suggested that amorphous solar cells could change the whole situation making direct generation of electricity from solar radiation a perfectly economic operation.

## SWITCHING OFF

At this point our crystal gazing must stop: quite finally unfortunately, so far as the present writer is concerned. To explain this a change to the first person now seems in order.

After guiding the destiny of PE since its inception I now have reluctantly to relinquish my editorship. This is due to the relocation of our editorial offices to Poole, Dorset. It is especially sad to part at this very time since PE has now become number one in its field in the UK.

These thirteen years have been exciting, stimulating and rewarding. A great number of contacts have been made with members of all sections of the industry, with advertisers, and with contributors. I have been fortunate in that many of these have become more than just business associations; friendships have been made which I greatly value.

There is of course that far larger band of readers with whom I have always felt a strong rapport despite no direct personal contact. To these unseen tens of thousands who have supported PRACTICAL ELECTRONICS throughout the years (including the critics) I am conscious of my indebtedness. For it is in the end the readers who make a magazine. Our task is to try and meet their needs. I can only hope that in the aggregate we have succeeded.

Also leaving PRACTICAL ELECTRONICS will be colleague David Barrington who has worked with me continuously since the pre-launch period in early 1964. He has been a key figure in the compilation of every issue, and his varied feature writing responsibilities included *Market Place*. Dave will join our associate publication EVERYDAY ELECTRONICS which I will continue to edit from our London Offices.

So now, cheerio. PRED BENNETT.

## EDITORIAL

### Editor

F.E. BENNETT

D. BARRINGTON Production Editor  
G. GODBOLD Technical Editor  
M. ABBOTT Technical Sub Editor

J.D. POUNTNEY Art Editor  
D.J. GOODING Technical Illustrator  
R.J. GOODMAN Technical Illustrator  
K.A. WOODRUFF General Artist

Editorial Offices:  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191  
Telex: 915748 MAGDIV-G

## ADVERTISEMENTS

### Advertisement Manager

D.W.B. TILLEARD

P.J. MEW Representative

C.R. BROWN Classified Manager

MAKE-UP and COPY DEPT.  
Phone: 01-261 5000

Advertising Offices:  
King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Phone: Advertisements 01-261 5000  
Telex: 915748 MAGDIV-G

If you've ever had to leave your car in a "shady" area of town, and you are only too aware of how little opposition the average car lock presents to a thief, then you probably will have promised yourself a burglar alarm one day. It's not just a question of your car being stolen, but you could come back to find your "in-car" music centre missing, and even a simple system is a good deterrent while there are still other vehicles around without protection.

This automobile burglar alarm is triggered by the door operated courtesy light switches, causing pulsation of the horn and headlights, and features exit and entry time delays with the ON/OFF switch hidden somewhere to hand inside the car. The alarm unit itself is fixed in a convenient location somewhere under the bonnet.

### CIRCUIT OPERATION

The circuit diagram of the alarm is shown in Fig. 1. With the latch (TR1 and TR2) in the "off" state (TR2 collector low), Timer A is disabled via D2, and the relay is not energised so that the car headlights and horn are off. When the latch is in the "on" state, Timer A is allowed to oscillate, thereby repetitively energising and de-energising the relay, and thus the horn and headlights.

The latch toggles from the "off" to the "on" state when triggered by any of the door switches, except for a short interval after power is applied to the circuit via the hidden switch, when Timer B holds the latch off while the driver vacates the vehicle.

When S1 is closed, C1 begins to charge through R6, at which time the output of Timer B is high, biasing TR2 on, irrespective of the state of all door switches. While TR2 is on, C4 is prevented from charging, and the output

of Timer A is high, de-energising the relay. During this interval, the warning light mounted on the dashboard is illuminated to indicate that it is safe to open the car door.

After about 17 seconds ( $1.1 \times C1 \times R6$ ), the voltage across C1 reaches the threshold level of Timer B, and the output goes low, releasing the latch and turning off the warning light to indicate that opening the car door will now trigger the alarm.


When one of the door switches is operated (closed) by opening the door, even momentarily, the latch toggles from "off" to "on", so that TR2 collector is high. This allows C4 to charge through R7 and R8. After about 18 seconds ( $1.1C4 [R7 + R8]$ ), the voltage across C4 reaches the threshold level of Timer A and the output goes low, energising the relay.


At the same time, C4 begins to discharge through R8 and the timer pin 13. The discharge period lasts for about 11 seconds ( $0.7 \times C4 \times R8$ ), until the voltage across C4 falls to the trigger level of Timer A. At this point the timer output goes high, de-energising the relay. Also, the timer discharge pin (pin 13) is now disabled, so that C4 begins to charge once more through R7 and R8.

The charging period this time lasts for about 12 seconds ( $0.7C4 [R7 + R8]$ ) before discharging proceeds as before, so that from now on, the relay is repeatedly energised and de-energised for periods of 11 and 12 seconds respectively.

During the 18 second interval, between the latch being triggered by the door switch and the relay first being energised, the circuit can be de-activated by opening S1. This allows the car owner to enter the vehicle and turn off the power before the horn and headlights operate.

The capacitors C1 and C4 must be low leakage types, otherwise the threshold levels of the timers will not be reached. The remaining components are not critical.

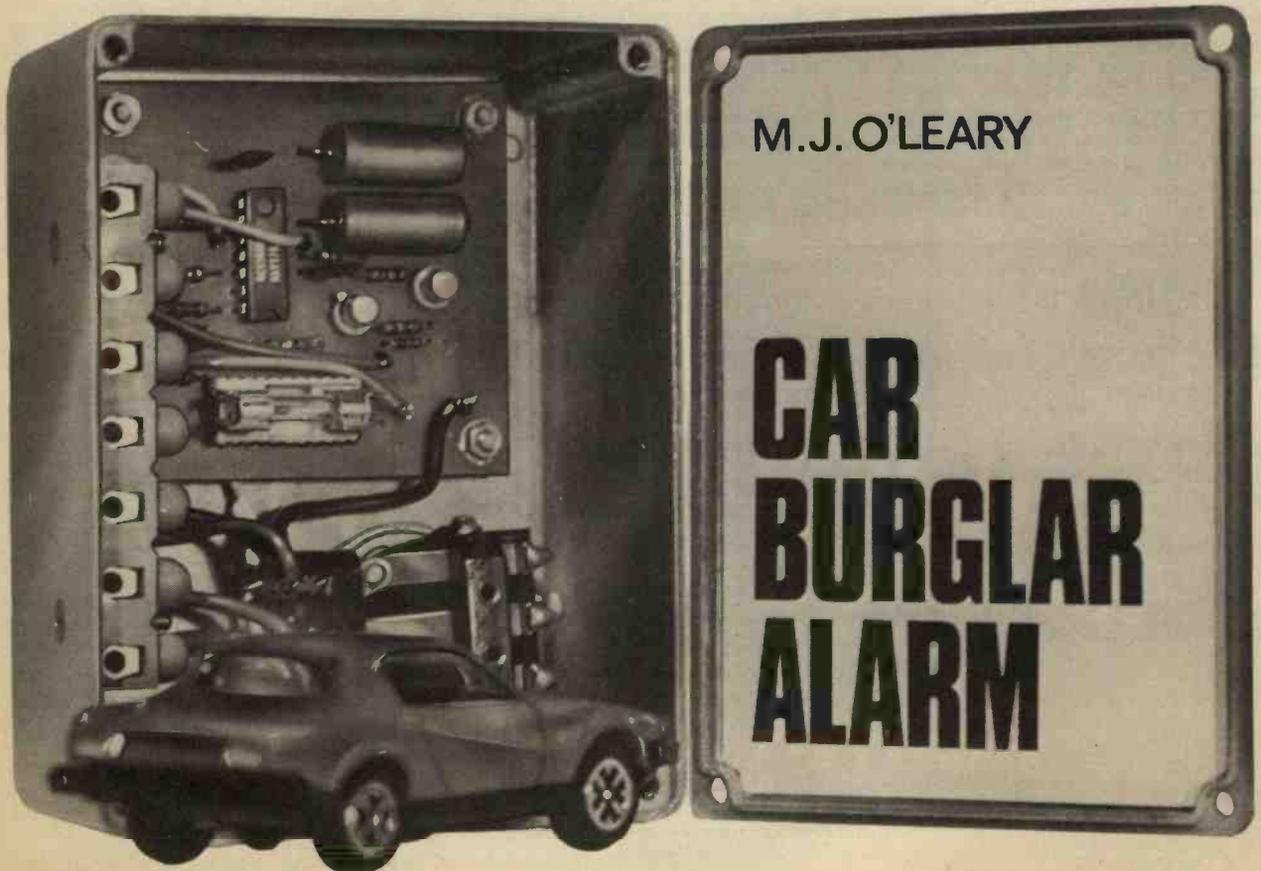

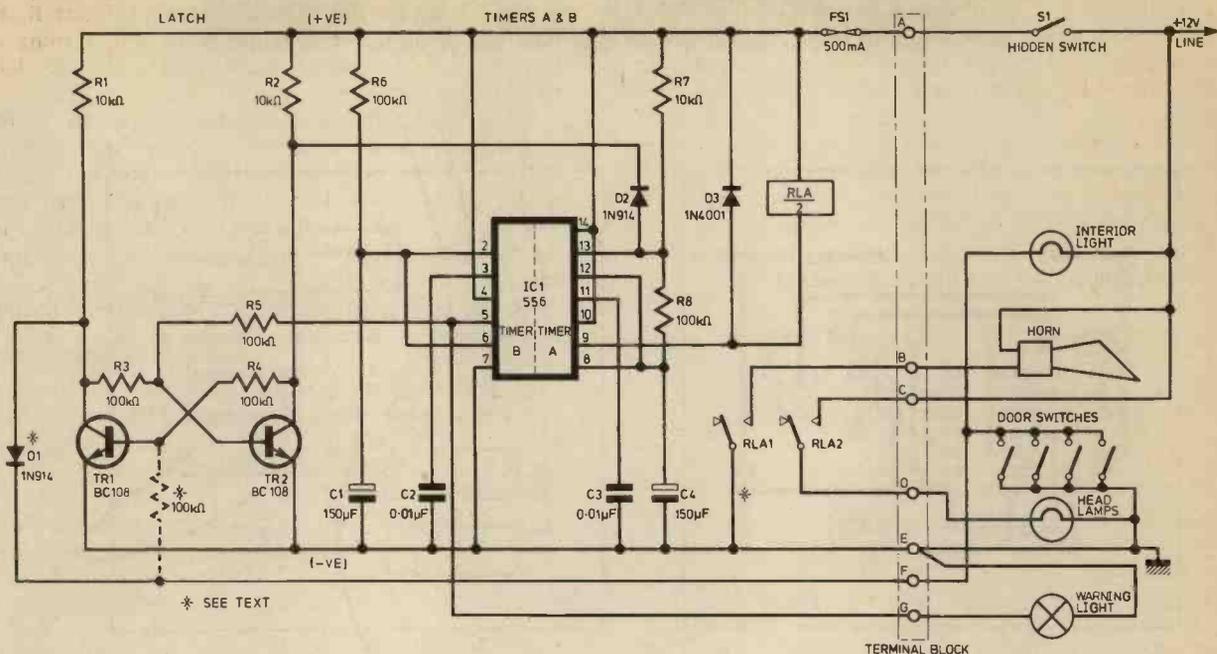

**Fig. 1. Burglar Alarm circuit diagram. For positive earth vehicles, D1 is replaced by a 100kΩ resistor which goes to the base of TR1**

## COMPONENTS . . .

### Resistors

R1, R2, R7 10kΩ (3 off)  
 R3, R4, R5, R6, R8 100kΩ (5 off)  
 All resistors ½W min carbon

### Capacitors

C1, C4 150μF/15V solid tantalum (2 off)  
 C2, C3 0.01μF ceramic (2 off)  
 The tant' capacitors must be low leakage (<0.01μA/μFV)

### Transistors

TR1, TR2 BC108 (2 off)

### Integrated Circuits


IC1 556 Timer

### Diodes

D1, D2 1N914 (2 off)  
 D3 1N4001

### Miscellaneous

Single sided p.c.b. 58 × 66mm  
 P.c.b. pins  
 S1 on/off toggle switch  
 FS1 500mA fuse and 20mm holder  
 Relay, 12V/110Ω, 2 pole c/o, 10A contacts (Doram)  
 Diecast box 114 × 55 × 89mm  
 Terminal block, 7-way  
 Grommet, 6mm (¼in)  
 P-clip, size N2  
 Warning lamp, 12V/2.2W. (An l.e.d. could be used in series with a 680Ω resistor)

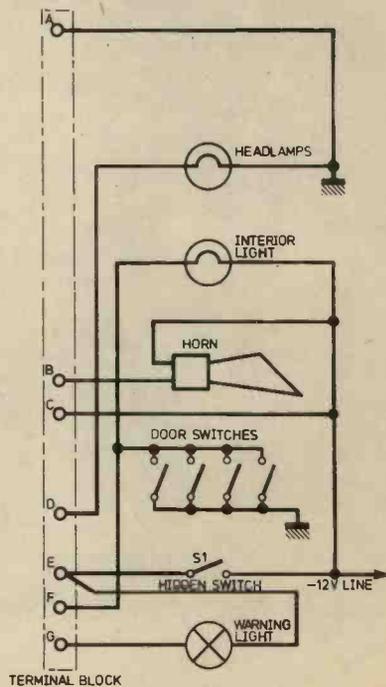

**Fig. 2. External wiring arrangement for positive earth vehicles**

# CAR BURGLAR ALARM

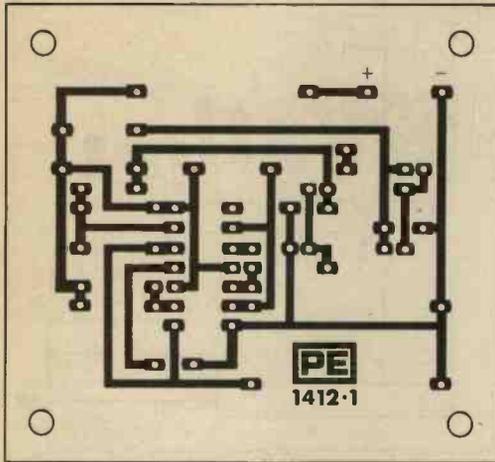


Fig. 3. Printed circuit for Car Burglar Alarm


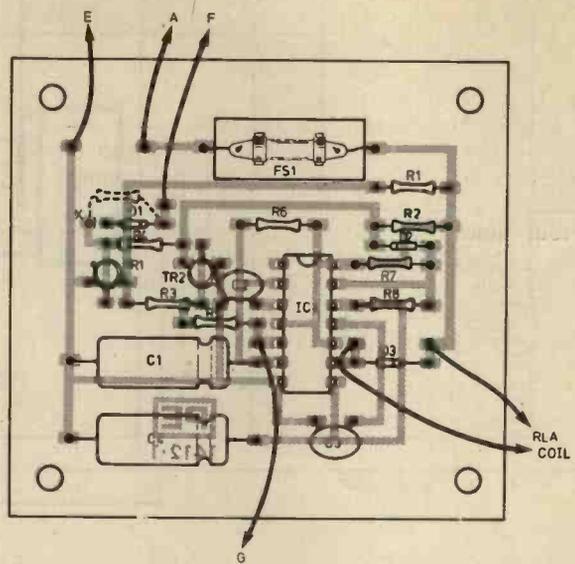
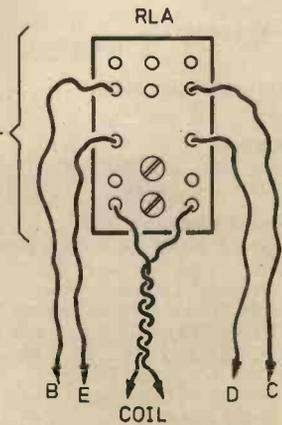


Fig. 4. Component layout of Burglar Alarm board. The spare pad (marked X) is for the "positive earth" modification

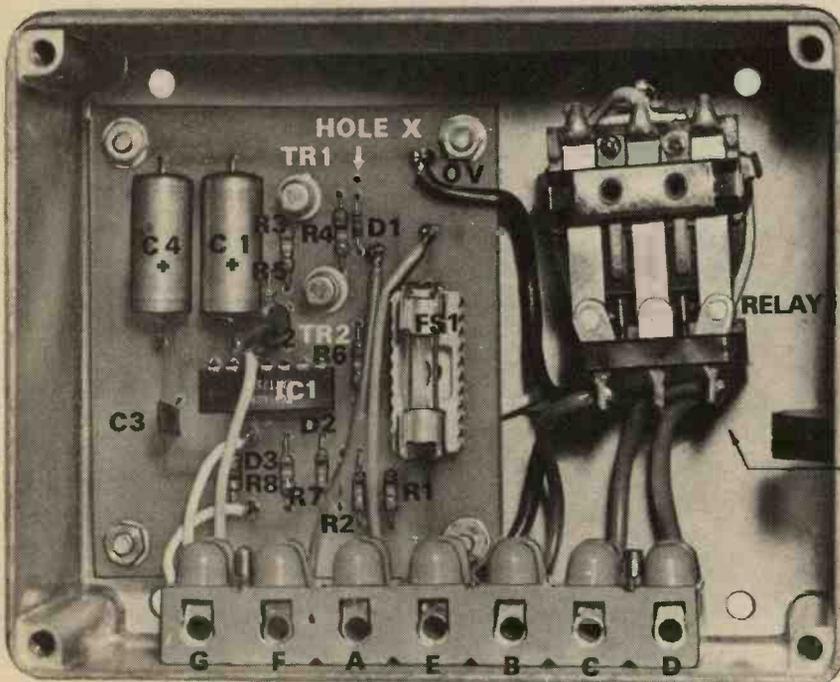

The details shown for wiring up RLA are only correct for the Doram type 72-722-0 relay

## CONSTRUCTION

The unit comprises a small p.c.b. (which is shown in Fig. 3), a suitable relay, and a seven way terminal block, all housed in a diecast aluminium box which is mounted under the car bonnet. Firstly the p.c.b. should be assembled following the diagram of Fig. 4, and then the metalwork should be carried out.

Four holes are drilled through the base of the box to accommodate the p.c.b. mounting screws. These screws will be independently fastened with nuts to form studs over which the p.c.b. can be placed. They will also act as spacers to separate the board from the base of the box. Fixing holes for the relay should be drilled, and also for the terminal block, and one further hole for the grommet through which the interconnecting leads will enter.

A final four holes are necessary for the self tapping screws which will secure the whole unit to the car. This means that the unit has to be screwed down with the lid off, and the lid subsequently replaced. Make sure that these drillings are situated where there will be plenty of room to introduce a screwdriver once the "bits and pieces" are installed inside the box.

A robust case with tight fitting lid was chosen in preference to a plastics type because the environment inside an engine compartment is pretty hostile. The box will have to stand up to vibration, corrosive elements, and severe heat variations. The unit should be screwed together tightly, using shakeproof washers wherever possible. Good soldering is also necessary.

## CONVERSION TO POSITIVE EARTH

The unit as shown in Fig. 1 is designed for negative earth cars, but it can readily be adapted for positive earth vehicles. See Fig. 2.

In this case the positive terminal of the unit (A) is connected directly to earth, instead of S1, and the negative terminal of the unit (E) is now connected to S1, which continues on to -12 volts.

The same p.c.b. and components are used, with the exception that D1 is replaced by a 100k $\Omega$  resistor, and an extended pad (marked X in Fig. 4) is provided for this larger component, which goes to the base of TR1 instead of its collector. This is so that the latch can still be triggered by the door switches which are generally connected to earth, and which will give a positive voltage in this case.

The horn and headlight relay contact connections are similar to those for a negative earth system, except that now the horn connection inside the unit (RLA1 pole) is connected to the positive rail instead of the negative one, and the headlights (terminal block C) are connected to negative supply instead of the original +12 volts.


The warning light will still be connected between terminal block points G and E, but since point E is no longer earth, all wiring relating to this lamp will need to be insulated from the car chassis.

## POINTS TO CHECK

The wiring details given in this article are based on certain assumptions, but the following points should be verified before wiring up the unit: That the headlamp bulbs, and door switches return directly to the car chassis, irrespective of the polarity of the system; and that the horn returns to "Line" and *not* chassis, i.e. +ve for a negative earth vehicle, or -ve for a positive earth vehicle.

These checks can be made with a simple multimeter, or even a small 12 volt bulb, and the internal relay can be rewired to compensate for any variations encountered. ★

# ...NEXT MONTH

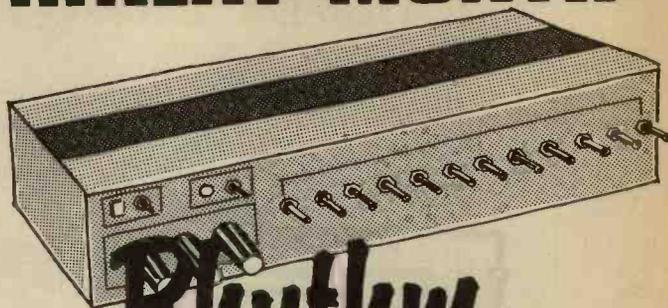

## Rhythm GENERATOR

### For the Musician

An attractive low profile, low cost rhythm unit with 12 popular rhythms which can be individually switch selected or mixed and varied in tempo as required. A 'downbeat' i.e.d. indicator gives an 'easy-to-follow' visual indication of this bar measure.

### For the Motorist

## Battery Condition Indicator

Keep an eye on your battery charge level using our 'tri-state' voltage indicator; simple to build, it could save you from being underpowered or even stranded. One i.e.d. warns of low voltage, and the other warns of overcharging. Both off means everything is okay.

## 9v Stabilised P.S.U

A simple converter for driving expensive 9V battery operated radios or recorders from a 12V supply. Ideal for the motorist or caravanners as it will supply up to 0.25A and can be easily altered to provide 6V.

## NEW SERIES... Electronic Fault Diagnosis

To the newcomer to electronics causes of failure in equipment can be baffling and frustrating without an awareness of troubleshooting procedures. This series affords an opportunity to acquire skills to remedy.

## PRACTICAL ELECTRONICS

OUR JANUARY ISSUE WILL BE ON SALE  
FRIDAY, DECEMBER 9

## PART 2



# 128 NOTE

# SEQUENCER

D. G. EVANS

In this second and final part describing the 128 note sequencer, details will be given for constructing the three sub-assemblies making up the unit together with testing procedures and patching examples for use with a synthesiser.

### POWER SUPPLY

The power requirements for the sequencer are positive five volts at about 200mA and five volts negative at a very low current for the 741 op amp. The circuit for this is given in Fig. 7 and provides both regulation and stabilisation for the two lines.

Constructional details for realising this are given in Fig. 8 which shows the majority of components mounted on a 76 × 54mm printed circuit board. When assembled both this and the transformer are mounted on a simple angled aluminium sub-frame. The p.s.u., main and counter display boards should be mounted on the baseboard adjacent to the control panel.

### MAIN BOARD

The p.c.b. and component layout for the circuit of Fig. 2 is given in Fig. 8. Here i.c. sockets are used throughout to obviate the possibility of chip damage in assembly. They also facilitate the replacement of i.c.s.

When this board is assembled all i.c.s apart from the RAM should be inserted. This will enable the clock oscillator, counter and D-A converter to be checked for correct functioning.

First the control panel is made up from a piece of 135 × 235mm aluminium. This should be drilled and cleared to suit the components shown annotated in the photograph.

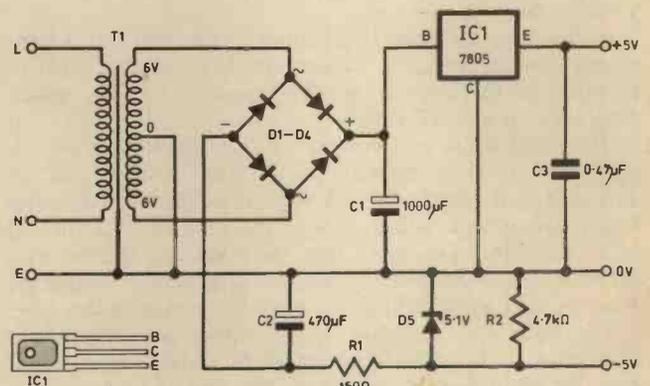


Fig. 7. Circuit of power unit

The Letraset legends were laid on a black paint background and then secured with a clear polyurethane spray.

After this preparation and finishing the control components should be fitted and wired according to Fig. 10 to the main board.

### DIGITAL READOUT OF COUNTER

It was found when operating the prototype sequencer that it was often helpful to know what position in the memory had been reached when writing in a tune. It was considered that a full numerical display of the counter state was not necessary, and should greatly increase the cost of the unit. Fig. 9 shows an alternative arrangement which was used in the prototype. In this the binary number at the memory address inputs of IC3 is displayed on seven l.e.d.s, driven via buffer transistors.

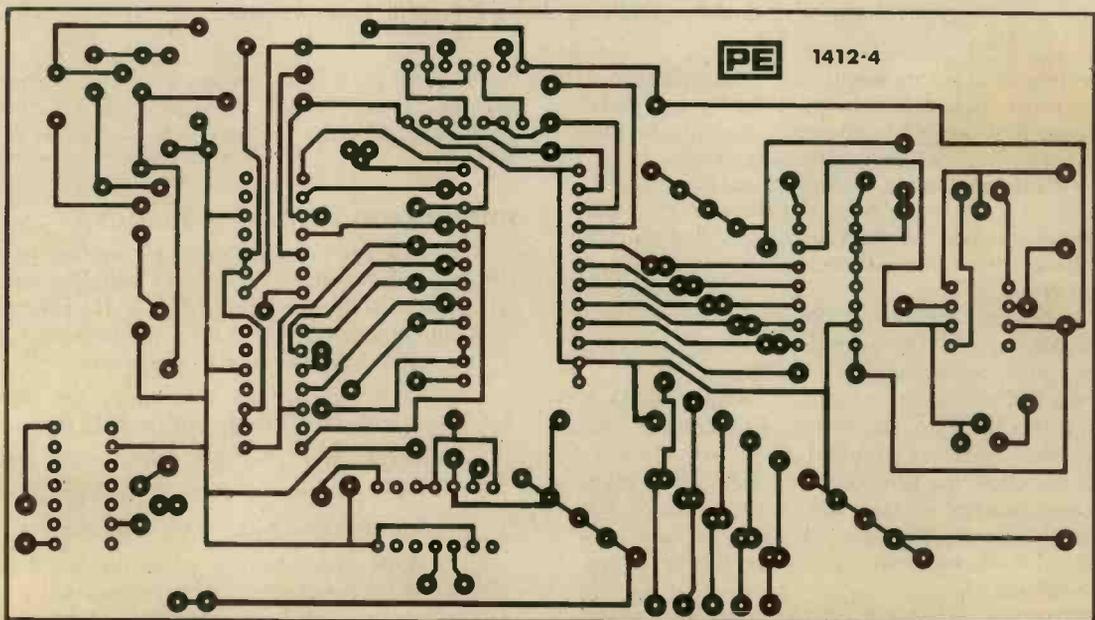
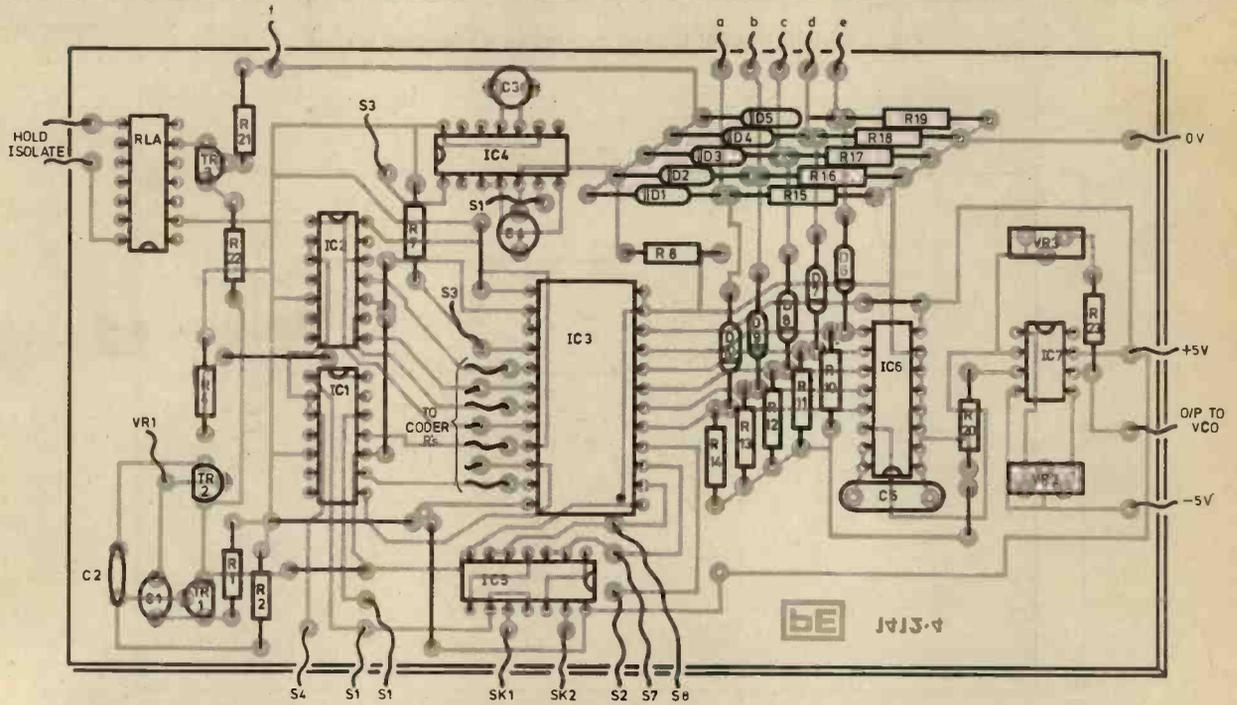
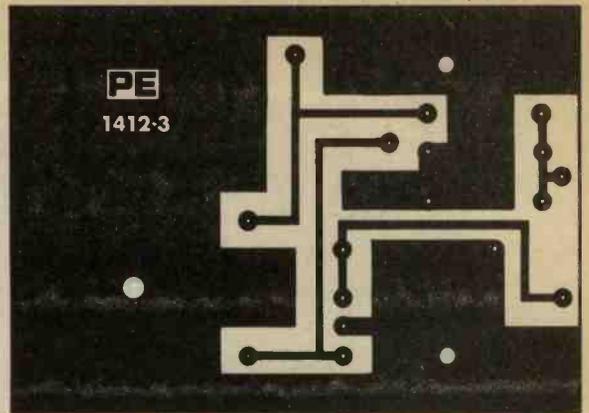
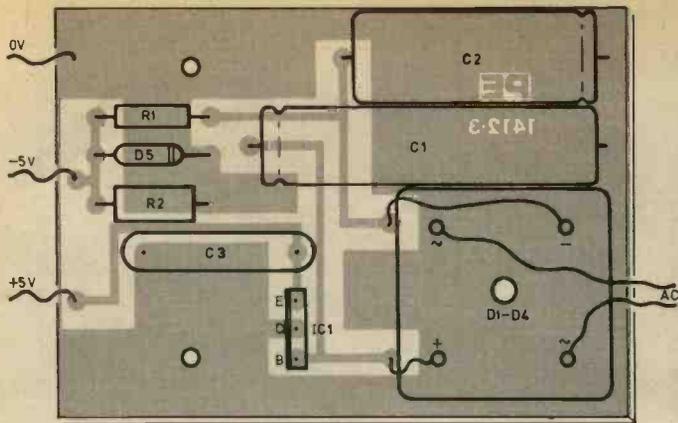


Fig. 8 (top). Showing component layout and p.c.b. for main components of power unit and (below) component board and etching details for the main circuit (Fig. 2)

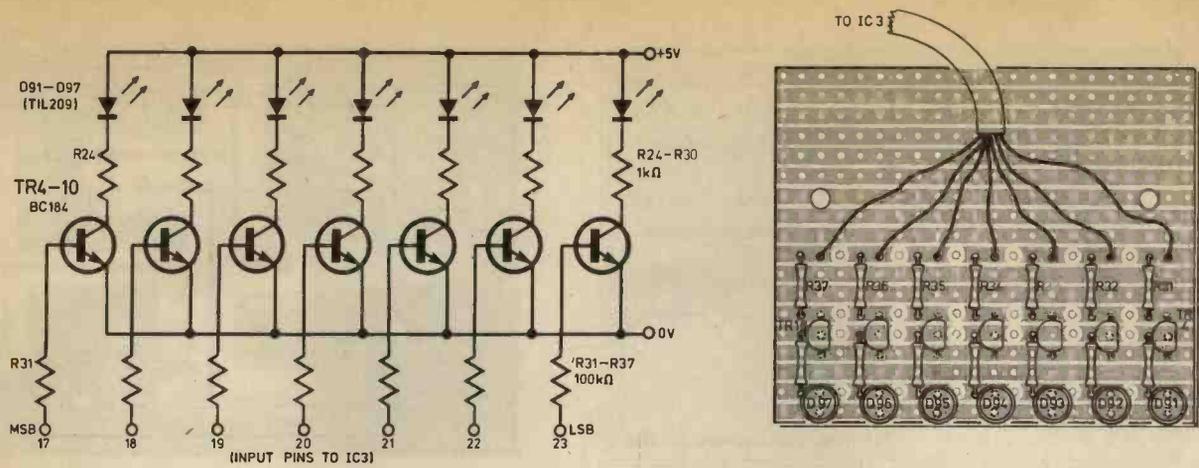


Fig. 9. Circuit of counter and prototype Veroboard layout

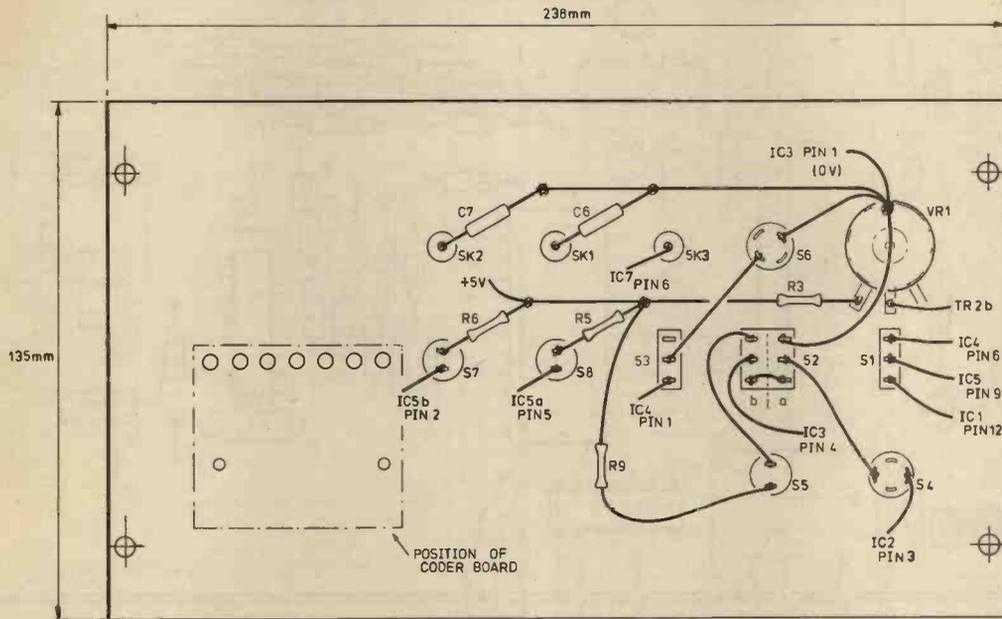


Fig. 10. Interwiring and component layout for control panel

On the prototype unit this circuit was assembled on a 45 × 55mm 0.1in matrix Veroboard (Fig. 9) and fixed with two screws and bushes to the control panel so that all the l.e.d.s are visible via cut-outs from the front.

To check circuit functioning set the "Stop/Run" switch to "Run" and apply power. With a voltmeter or oscilloscope examine whether the clock oscillator is producing pulses and the correct binary count appears at the l.e.d. "Count" display.

Set the "Stop/Run" switch to "Stop" and check that depressing a key causes the counter to step, and also that it causes a pulse to appear at pin 1 of IC4.

Still with the MCM6810 out of circuit, connect the D-A output to a synthesiser v.c.o. Adjust the offset control VR2 (Fig. 2) until the sequencer output is zero with no keys depressed. Now adjust the gain control VR3 so that playing consecutive octaves on the keyboard produces the correct pitch change in the v.c.o. (It may be necessary to adjust the value of the feedback resistor R23 to obtain the correct pitch span.)

If all is correct so far, switch off the power and insert the MCM6810.

On reapplying power, a random series of notes should

be sounded by the v.c.o. when the clock is running. Pressing the "Erase" switch while running the clock at a fast speed will clear the memory. The sequencer is now ready for use.

### PROGRAMMING THE SEQUENCER

A certain amount of practice is needed to programme the sequencer correctly, the user should familiarise himself fully with the working of the device before attempting to write complicated tunes into the memory.

The operating procedure is as follows:

- (1) Clear the memory by running the clock at a fast speed with the "Erase" button held down.
- (2) Select "Stop" with the "Stop/Run" switch.
- (3) Press the counter "Reset" button.
- (4) Set the "Reset Read/Write" switch to "Write".
- (5) Write the required notes in by depressing the appropriate keys (go fairly slowly to avoid mistrigging the circuit). If a note is to be held for more than one beat, the key should be pressed more than once.

If the envelope trigger outputs are being used, the trigger button (1 or 2) should be pressed at the same time as a key whenever a trigger pulse is required.

(6) When the last note of the tune has been written in, hold the "Reset Write" button, and press the last key again.

(7) The tune is now ready to be played. Reset the counter, put the "Reset Read/Write" switch to "Read" and select "Run". The tune should now be played through the synthesiser v.c.o.

## USING THE SEQUENCER

Even when used with fairly simple synthesisers, the sequencer is capable of producing quite startling results.

Some typical patching arrangements are shown in Fig. 11. The sounds produced by Fig. 11(d) are extremely entertaining if the two v.c.o.s are tuned to a musically related interval.



Fig. 12. Demonstrating a simple tune for the sequencer

## COMPONENTS . . .

### P.S.U.

#### Resistors

R1 150Ω ½W  
R2 4.7kΩ ½W

#### Capacitors

C1 1,000μF 25V elect  
C2 470μF 25V elect  
C3 0.47μF

#### Semiconductors

D1-D4 Bridge rectifier (2A, 200V) (R.S. Components)  
D5 BZX85-5.1 5.1V, 1.3W Zener (R.S. Components)  
IC1 7805 5V, 1A regulator (R.S. Components)

#### Transformer

T1 6-0-6V 250mA mains transformer

### L.E.D. COUNTER (Optional to main board)

#### Resistors

R24-R30 1kΩ (7 off)  
R31-R37 100kΩ (7 off)

#### Semiconductors

TR4-TR10 BC184 (7 off)  
D91-D97 TIL209 (7 off)

### KEYBOARD

49 note keyboard C to C  
4 s.r.b.p. strips 169 × 51mm for mounting contact blocks  
Contact blocks type GB2 (49 off)  
(All keyboard items available from Maplin Supplies)

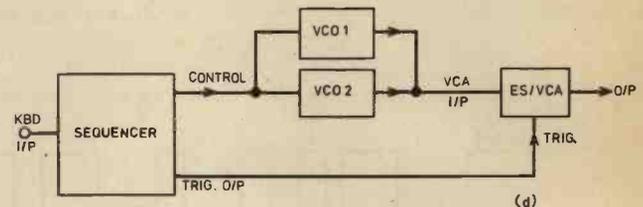
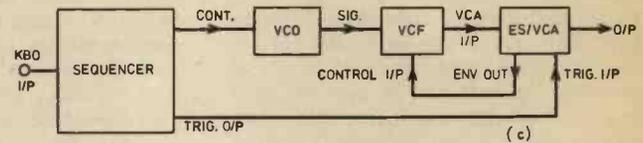
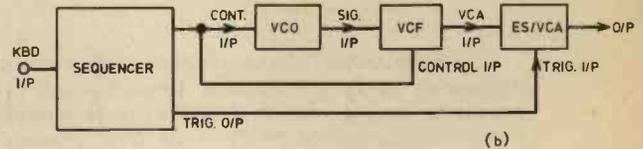
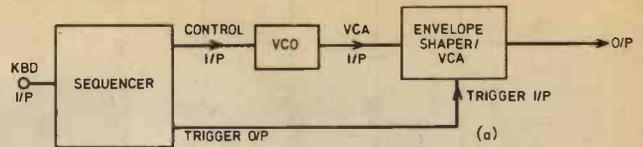


Fig. 11. Some typical patching arrangements with a synthesiser

Fig. 12 demonstrates how a simple tune can be played. Here each bar is divided into 12 beats, a close approximation of the dotted notes is given by using the 1st, 3rd, 4th, 6th, 7th, 9th, 10th and 12th beats only. By writing trigger pulses only on the accented beats the impression is given of a separate bass and melody line being produced by only one oscillator!

It is interesting to note that this tune only uses 25 positions in the memory, less than a fifth of the unit's capacity!

It must be realised that this is a very simple example; the full capabilities of the sequencer are really only limited by the imagination of the user.

## EXPANSION

More ambitious constructors should have no difficulty expanding the unit in a number of ways, for example, two or more memories could be connected in series to give longer sequences. Alternatively, two memories could be paralleled to provide more outputs (two tunes could be played at once!).

Even in its basic form, the 128 note sequencer is a very useful addition to a synthesiser, making possible effects and sounds that are very difficult to produce manually. ★

# MICRO-BUS

Compiled by DJD.

This is the second of a new regular feature covering all aspects of microprocessors and minicomputers. Appearing every two months, Micro-Bus will present ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas will probably come from readers working on their own microcomputer systems, and payment will be made for any contribution featured here. This is also the place to air your views, in general, on this new technology, so let's be hearing from you!

## TIME-CODE CLOCK

In the past the only type of clock which did not need to be set to the correct time was the sundial; other clocks are at best only as accurate as the last time they were set. However since 1974 when the National Physical Laboratory started transmitting a high-accuracy time code, it has been possible to design an electronic clock which automatically sets itself to the correct time within a minute of switching it on!

amplifier which brings the signal up to the 25mV needed to drive the PLL. The aerial should be placed at least 2ft away from the receiver to minimise pick up from the PLL, and the wire connecting them should be screened.

In the prototype the front-end was built from a kit supplied by D. W. R. Higginson Limited, Bristol Road, Sherborne, Dorset, DT9 4EF, for £14.08 (inc. VAT), and this included a pre-aligned aerial (available separately).

The output from the PLL drives an l.e.d. which should flash at 1Hz when a signal is being received, and the two inputs to the MC6820 Peripheral Interface Adapter (PIA) in the microprocessor system. One input is a conventional input and the other is a latched control unit.

The clock was tested on a Motorola D2 kit, which uses a 6800 MPU, and the complete program is shown in Fig. 3. This could easily be modified for use

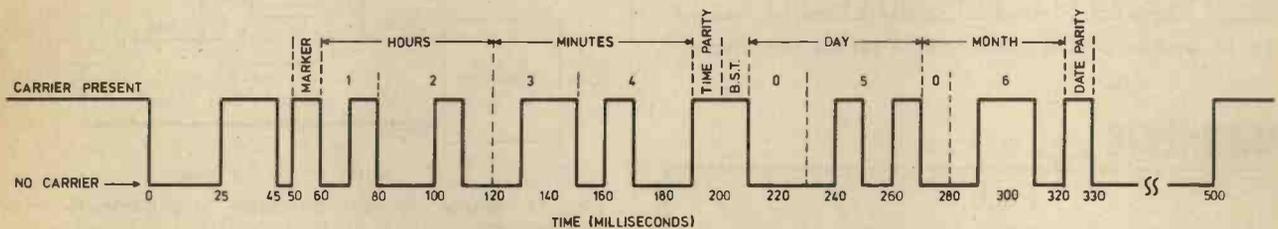


Fig. 1. Format of the encoded time and date information transmitted at the start of each minute

The signal is transmitted from Rugby on M.S.F. 60kHz. A 100-millisecond break in the carrier occurs every second (and on some half-seconds), and each minute the time and date are transmitted in a binary coded decimal format, see Fig. 1. Designs have appeared which used logic gates to read and decode the information but these needed a large number of integrated circuits and much wiring.

An alternative approach presented here is to do all the decoding by software using a circuit based on a microprocessor; in this case the only parts needed, apart from the microprocessor system, are the receiver section and interface as in Fig. 2. This would therefore make an ideal system clock for a microcomputer.

The receiver is built around an NE567 phase-locked loop (PLL) tone decoder whose frequency is set to 60kHz by VR1. When a frequency within about 14 per cent of this is present at its input, it drives the output low. A ferrite-rod aerial tuned to 60kHz feeds a two-stage


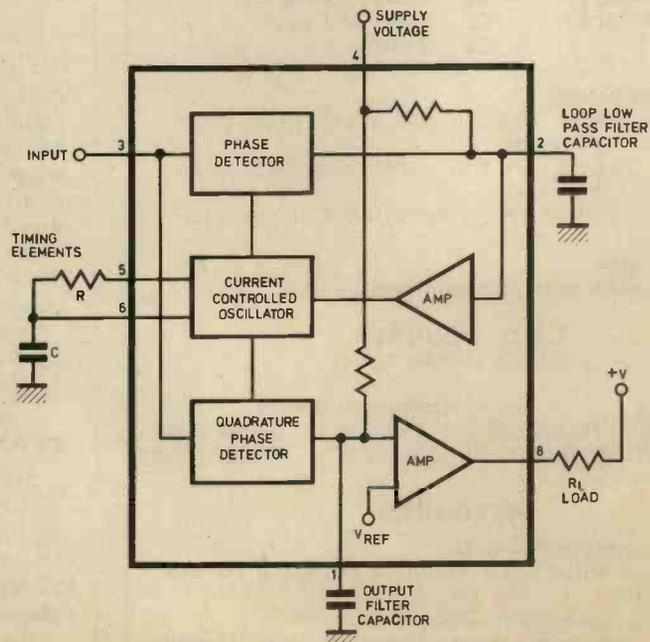


Fig. 2. (a) Block diagram of the NE567 phase locked loop tone-decoder integrated circuit used in the receiver

**Fig. 2 (b).** Circuit diagram of a suitable 60kHz receiver. The PIA interfaces the circuit to the micro-processor system, and these connections are not shown

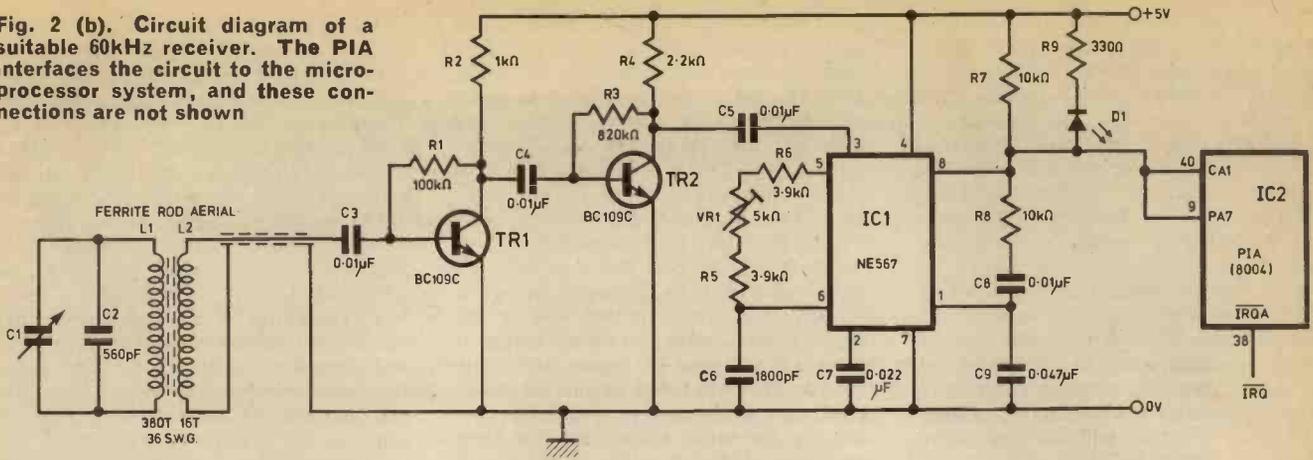

```

NAM      CLOCK
*** RUGBY TIME CLOCK ***
*
0004     PIA      EQU      $8004
E0FE     OUTDS   EQU      $E0FE      IN JBUG
A000     IRQ      EQU      $A000
*
0000 0002 XTEMP  RMB  2
0002 0001 DATA  RMB  1      HOURS
0003 0001     RMB  1      MINUTES
0004 0001     RMB  1      TIME PARITY BIT
0005 0001     RMB  1      B.S.T. BIT
0006 0001     RMB  1      DAY
0007 0001     RMB  1      MONTH
0008 0001     RMB  1      DATE PARITY BIT
0009 0006     BITS  FCB  6,7,1,1,6,5,1
000A 07
000B 01
000C 01
000D 06
000E 05
000F 01

*** MAIN PROGRAM ***
*
0010 06 07 BEGIN  LDA  A  $20000111
0012 07 0005     STA  A  PIA+1      CONTROL WORD
0015 CE 0022     LDX  X
0018 0F A000     STX  IRQ      INTERRUPT VECTOR
0019 06 0004     LDA  A  PIA      CLEAR INTERRUPTS
001E 0E         CLI
001F 7E E0FE     JMP  OUTDS   OR MAIN PROGRAM

*** INTERRUPT SERVICE ROUTINE ***
*
0022 CE 0903 ISR  LDX  $30000/13 (30 HSEC.)
0025 0D 39     ESR  DELAY
0027 06 0004     LDA  A  PIA
002A 2B 33     BMI  RETURN  NOT MINUTE PULSE
002C CE 0A04 MINUTE LDX  $35000/13 (35 HSEC.)
002F 0D 2F     BSR  DELAY
0031 CE 0002     LDX  $DATA
0034 DF 00     NDIGIT STX  XTEMP
0036 E6 07     LDA  B  7,X
0038 4F 00     CLR  0,X
003A 06 0004 NEXTIN LDA  A  PIA
003D 43     COM  A
003E 49     ROL  A
003F 49 00     ROL  0,X
0041 CE 0301     LOX  $10000/13 (10 HSEC.)
0044 8D 1A     BSR  DELAY
0046 DE 00     LDX  XTEMP
0048 5A     DEC  B
0049 26 EF     BNE  NEXTIN
004E 08     INX
004C BC 0009 CPX  $DATA+7  ALL IN?
004F 26 E3     BNE  NDIGIT YES
*** SUMMERTIME CORRECTION ***
0051 96 02     LDA  A  DATA  HOURS
0053 98 05     ADD  A  DATA+3  B.S.T.
0055 19     DAA
0056 81 24     CMP  A  $424
0058 26 01     BNE  FINE
005A 4F     CLR  A      CHANGE 24 TO 00
005B 97 02     FINE  STA  A  DATA
*** DISPLAY DATA **
005D 8D 05     BSR  UPDATE
005F 3B     RETURN RTI

**** DELAY APPROX. X*13 USEC. ****
*
0060 09     DELAY  DEX
0061 26 FD     BNE  DELAY
0063 39     RTS

**** UPDATE DISPLAY BUFFER ****
*
E0C4     CLRDS  EQU  $E0C4
E31C     DIS01 EQU  $E31C
E327     DIS23 EQU  $E327
*
0064 8D E0C4 UPDATE JSR  CLRDS
0067 76 02     LDA  A  DATA
0069 8D E31C     JSR  DIS01
006C 96 03     LDA  A  DATA+1
006E 8D E327     JSR  DIS23
0071 39     RTS

```

**Fig. 3** Program for the 6800 which reads and decodes the time and date information from the receiver section, and displays the time on the displays in the D2 kit

with other micros. As it stands the program uses the display routine in the D2 kit JBUG monitor to display the time; when executed the program first causes an arbitrary number to be displayed (and this flickers at one-second intervals due to the time taken by the interrupt service routine), and then each minute the display is updated to the new correct time as the time code is received.

The program is entered at BEGIN, and this first section initialises the PIA, making CA1 an interrupt input, and puts the address of the interrupt-service routine ISR into the pseudo interrupt-vector at A000; on interrupts this is picked up by the monitor and used as a jump address.

The interrupt mask is then cleared, and control transferred to the main program; in this case OUTDS, the display routine which refreshes the 7-segment displays in the D2 kit.

On the rising edge of every pulse from the receiver an interrupt is generated and the routine ISR is called. This routine is only concerned with minute pulses, so it reads the input line after 30 milliseconds and returns to the main program if it is still high. Otherwise the ISR updates the seven locations at DATA with the decoded information, and it does this as follows:

The program delays a further 35 milliseconds to the centre of the first data bit and then reads bits at 10 millisecond intervals into the correct location at DATA. The number of bits to be shifted into each location is different (see Fig. 1) and is given by the number in the corresponding element of the array BITS. All the delays are generated by the subroutine DELAY which counts down the index register X, and in systems with different clock rates the delay parameters will have to be altered accordingly.

To convert from G.M.T. to the more familiar B.S.T. the program adds the summertime bit to the number of hours. Finally, for testing purposes, the routine UPDATE uses subroutines in JBUG to

clear the displays and load the new hour and minute counts into the display buffer. Note that although the date and parity information are not displayed they are available in the array.


**DATA**

As well as making an ideal source of the time and date in an existing micro-computer system, a time-code clock could be constructed using a dedicated microprocessor with the program stored in ROM. It would be a simple matter to extend the program to give date display, error-checking (using the parity bits), seconds, an alarm, and time-controlled switching of circuits. All things considered, the sundial does not have much going for it any longer!

**MICRO PLAYS CHESS**

The "Chess Challenger" pictured below is a new microprocessor-based game that is being imported from the States, and it is currently on sale here for about £150. It is a remarkable example of how micros have crept up on us, and most people who have played against it are amazed that such a serene-looking wooden case contains a machine that can produce strong opposition to their moves.

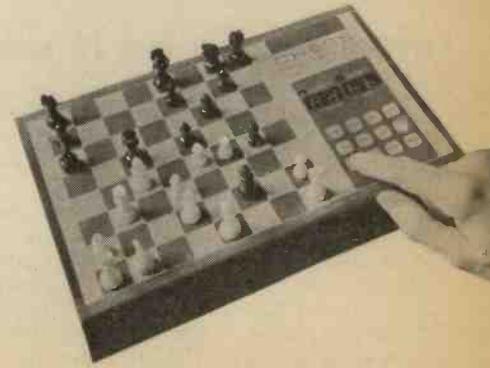**The Chess Challenger microprocessor-based chess playing game**



The player enters his move at a keyboard to the right of the chess-board, and the machine gives its reply on a four-digit seven-segment display. The moves are entered as the co-ordinates of the two squares involved (in what is unfortunately the opposite of standard algebraic notation): e.g. FROM 4b TO 4d. The "EN" key then enters the move and the machine replies in about two seconds.

It is worth noting that the machine performs no move checking, so any piece may be moved to any square that is either unoccupied or else occupied by an enemy piece; it is up to you not to cheat! This has the side-effect of making it possible to set up mid-game positions, albeit in a rather tedious way.

### AN EXCELLENT PARTNER

The special moves of castling and en-passant captures are dealt with by means of the "DM" double-move key. This prevents the machine from replying to the next move entered, so it enables you to move more than one piece in one turn. The machine will castle at the first opportunity and it sometimes castles through check; in this event it is necessary to move its king and rook back and ask it to move again, and it will not attempt another castling. It does not capture en-passant. If a player's pawn reaches the back line it is promoted into a queen and you cannot ask for an under-promotion. However, it neglects to promote its own pawns, and in one game played against it where it could have forced a victory it left its pawn unpromoted on the last line.

The machine announces "check" by an l.e.d., and when mated says "I lose" with an other. A useful additional feature is the possibility of interrogating for the current board position piece by piece to verify that the pieces are set up correctly.

At first sight the machine plays a good game, and it certainly never misses a trick if one is immediately possible. However, it only performs a static evaluation of the current position and does not look ahead at all. In other words it will fail to spot a mate in two, unless it happens to choose the key move for other reasons. Despite this the algorithm it uses to choose what it considers to be the best move is well designed so that nine times out of ten it actually does come up with one of the better moves. When for some reason it gives a bad move its opponent usually remarks that "it failed to see what was going on"; it cannot spot long-term plans and, by the same token, does not form long-term plans. This is a common failing of all but the most sophisticated of chess programs.

Out of a number of games played against it by players of ordinary to club standard it won about one-third. The shortest mates are spectacular if unrepresentative, but they illustrate the machine's blind spots and two are given below:

*Pete Christian*

White

1. 5b-5d
2. 4a-8e
3. 7a-6c
4. 6cN5e (xP)
5. 8e-6g (xP)

*Geoff Walker*

White

1. 5b-5d
2. 2a-3c
3. 6b-6d
4. 4b-4d
5. 4b-4d
6. 6a-3d
7. 6c-5e
8. 4a-8e (ch)
9. 8e-6g

*Chess Challenger*

Black

- 5g-5e
- 7g-7e
- 8g-8f
- 7h-6f
- I LOSE

*Chess Challenger*

Black

- 5g-5e
- 2g-2f
- 5e-6d (xP)
- 3h-2g
- 7g-7e
- 6h-5g
- 6g-6f (??)
- 5h-6h
- I LOSE

The game is based on the 8080A micro, the Intel-designed 8-bit device descended from their 8008 and currently the most widely used microprocessor. The program and keyboard/display interface routines are stored in a 2K byte ROM, and for the board position and other variables there are 1/2K bytes of RAM. As the photograph shows, it forms a very compact unit, this being made possible by supplying the transformer as a separate unit.

This machine is an excellent partner for average players who want some rapid and accurate opposition to help them improve their game, and it will certainly get one past the stage of leaving pieces unprotected. Unfortunately, while you are improving, the machine stays at the same level making the same mistakes. Perhaps with this in mind the makers offer to upgrade the game for an additional £50 by replacing the program chip. The upgraded game can be set to play at one of three strengths, and at level 3 it searches to a greater depth and takes up to 30 seconds per move. For those who do not play chess the makers say that a "Backgammon Challenger" is in the pipeline, and who can guess what else may be on the way?

### FERRANTI D/A CONVERTER

The ZN425E is the cheapest monolithic 8-bit D/A converter currently available despite its excellent specifications, and as an added bonus it contains an 8-bit binary counter so that it can be used as the basis of a simple A/D converter. It was specified for the digital waveform generator in the previous *Micro-Bus*, and can be obtained from S.D.S. Components Ltd., Hilslea Industrial Estate, Gunstore Road, Portsmouth for £3.78 (inc. VAT) plus 65p postage.

A few tapes of the program for a "Bulls and Cows" game are still available from P.E. (see October issue).

## NEWS BRIEFS

### Program Cassettes for Home TV Terminal

GENERAL Instrument Microelectronics Ltd and EMI Tape Ltd have jointly developed an inexpensive method of storing computer data for home use, using conventional audio cassette tapes and a standard audio cassette mechanism or deck.

The technique, for which patents have been obtained, permits the storage of 1.6 million bits of data on each side of a conventional C-60, 30-minute per side cassette and offers one hundredfold increase in storage capacity in comparison with ROM microcircuit cartridges, at one quarter of the price. Moreover the technique allows voice and digital data to be stored on the same cassette.

The widespread availability of inexpensive hardware for the storage and playback of computer programs is seen as a key requirement in the development of the domestic television receiver into a computer system for use by all the family as a TV games centre and programmed learning and information terminal.

The possible range of programs is unlimited. By plugging a suitable cassette program into the cassette deck contained in the TV Game, the linked television could be transformed into a scientific or business calculator display in which every stage of calculation is displayed on the TV screen. Alternatively, language tapes could be made available combining on-screen text with the spoken word.

General Instrument Microelectronics have in an advanced state of development a set of compatible MOS microcircuits for interfacing the television to its CP1600 microprocessor family. Modular in concept, these interface circuits can be used by the manufacturer to offer a wide range of optional extras on the standard TV, culminating in a complete home computer system. These interface circuits allow the reception of the Viewdata and Teletext services.



# SPACEWATCH

FRANK W. HYDE

## SAILS IN THE SUNSET

The now rejected system of photon propulsion for the spacecraft which will be used to rendezvous with Halley's comet has caused some people difficulty. In fact the same principles apply to this system, which uses photon wind for the propulsive medium, as to the normal sailing dinghy. The incident radiation would be reflected by the sail and the resultant energy would urge the vehicle in the same manner as the wind on Earth. It is, of course, necessary to take into account the action of gravitational and centrifugal forces.

However, it could be intriguing to plot a course with its necessary tacking when moving towards the sun. It might not be so facetious if it was suggested that the variations in the medium and the strength of the radiation might lead to the use of the planets as buoys.

## SPACE SHUTTLE

Now that the space shuttle has entered both the vocabulary of the public at large and the world as a whole, it is to be hoped that a new look will appear on the space scene. Since there will be much that other countries can aim for at a much lower budget, it is foreseeable that many more missions will be required than envisaged in the first plans.

The rate at which mission time has already been taken up, it would seem that the second and third shuttles are already justified. Indeed, the natural reaction to the September disaster for the second *Voyager* may accelerate this.

It must be very apparent now that the way to economic stability in the space

programmes is via a maximum use of these new methods. The horizons are so wide that the accusation of "money wasted on wrong things" can be easily disposed.

The implications for industry and further employment is very considerable particularly in light metal raw materials. These are to be thought of in terms of millions of tons. So much indeed is required that every country in the world can benefit where process industries are working.

## CHEAP SOLAR CELLS

One of the greatest needs of solar development is the requirement of cheap solar cells. It would not require any more money spent on development to increase efficiency for the quantities needed would be so great that a very rapid lowering of price would result.

While the last little fraction of efficiency is required for space missions, this does not apply to earth based equipment. The difference in cost for a low grade cell is very great and other alternatives of basic materials could now be investigated.

The same reasoning applies to space projects where the shuttle is used. The weight that can be raised to orbit is so great in comparison to a single launch, that larger quantities of solar cells can be used. Here again the economic law applies. It is better and cheaper to use a large number of less efficient units which will in the end exceed the installed equivalent power.

## THERMOELECTRIC DEVICES

So far as earth based units are concerned, attention might also be given to thermoelectric devices. Used in cylindrical reflectors the area of activity is of sufficient extent for continuous lines of such devices to be used without overheating.

For example, a two metre by one metre sheet of aluminium will give a very high concentration of heat over a plane of 500 centimetres. For the "do it yourself" enthusiast it may be extended cheaply using simple angles instead of a parabola-cum-cylinder arrangement. A simple corner reflector will serve very well if slightly modified. Two sheets of aluminium, two metres by one metre, set longways will provide one square metre of concentration with a gain of four to one. In fact a complete unit such as this, with preheating from the distributed "lost heat", can make a very efficient garden unit to supplement the household heating.

The last few sentences may be thought to be far removed from space, but is it really so? Does not the new space age offer such spin-off facilities? The same techniques can be moved from one discipline to another to make the maximum

use of resources. Many years ago it was suggested that a large reflector arranged in orbit could not only supplement the heating of the Earth but that also it could be arranged to act as a second moon. Such a project is well within the compass of present technology.

The moving of the large gravity pulled structures and the associated equipment into space would reduce many costs and enable many devices on Earth to be reduced considerably in dimensions. Is it so fanciful to see the Earth controlled from its outer environs?

Certainly, if all nations took part in such a future programme there would be automatic control of attitudes. There would be so much for everyone to do that common interest could lead to common citizenship. Such a situation would indeed make horizons boundless. Not least of the benefits would be a wrist telephone which put everyone in touch with everyone else. Perhaps it is better to leave the subject there for the moment.

## JUPITER

There seems to be a number of people who have been somewhat dismayed by the interpretation of Prof. McNally's report about the Jovian planet. Within the last several weeks there have been many questions as to whether Jupiter is to be a second Sun. It is unfortunate that when these ideas take hold of public imagination a whole crop of pseudo science appears.

It has been known for a very long time that Jupiter gives out more heat than it receives. This in no way justifies a statement that it will grow hotter and hotter to reach a state of concentrated gravity condition to raise temperatures to fission level. Indeed, application of the inverse square law will settle any fears of a new "Sun" within the lifetime of the one already sustaining the Earth and its people.

At the distance of Jupiter from the Sun, nearly 500 million miles, a much smaller fraction of the Sun's heat per square mile of the planet is received than that received on the Earth.

The *Pioneer* results, in any case, have established the reigning temperature very definitely. A great deal of heating up would be required to bring it to a hospitable level. The projected mission into the atmosphere of the planet will bring forward much needed data to enable assessments to be made in these matters.

That Jupiter is a remnant of the original nova is gaining ground now. This would seem to be a logical explanation of Jupiter's size and effect in the solar system. Its effect on the Sun is considerable because the centre of rotation of the Sun and Jupiter is some 30,000 miles outside the photosphere. The inevitable result is a disturbance of the atmosphere of the Sun.

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

## POCKET MULTIMETER

A new, high accuracy, personal digital multimeter from **Sinclair Radionics** is now available in the UK at £29.95 plus VAT.

Claimed to be less than one-third the price of existing  $3\frac{1}{2}$  digit meters, the PDM35 fits easily into a coat pocket, brief case or tool kit.

Using an adaption of the old Oxford calculator cases (to save cost), the PDM35 will measure a.c. and d.c. voltage to an accuracy of 1 per cent of reading. Also d.c. current can be measured to the same accuracy. The resistance range is up to 20 megohms. Range selection is by a slide switch as against the usual rotary type.

There is no provision for a.c. current measurement as Sinclair claim their investigations show little demand for this facility.

A brief technical specification is as follows: D.C. Volts (4 ranges) 1mV to 1,000V at 1 per cent  $\pm 1$  count, 10M $\Omega$  input impedance; A.C. Volts (40Hz–5kHz) 1V to 500V at 1 per cent  $\pm 2$  count, mean reading r.m.s. (calibrated); D.C. Current (6 ranges) 1nA to 200mA at 1 per cent  $\pm 1$  count, maximum resolution 0.1nA; Resistance (5 ranges) 1 $\Omega$  to 20M $\Omega$  at 1.5 per cent  $\pm 1$  count, also provides 5 junction-test ranges.


Additional extras include an a.c. adaptor for 117V 60Hz or 220/240V 50Hz, carry case and a 30kV probe.

For addresses of nearest stockists of the PDM35 digital multimeter readers should write to **Sinclair Radionics Ltd., Dept P.E., London Road, St. Ives, Huntingdon, Cambs, PE17 4HJ**, although most good component shops and some stores will have stocks.
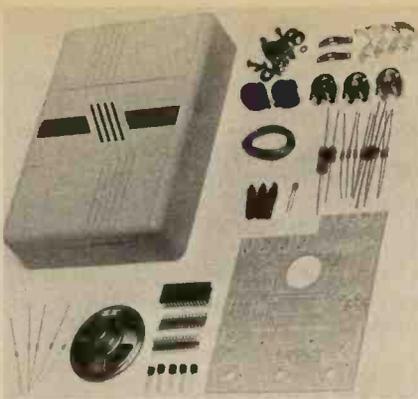
## MUSICAL DOORBELL

No doubt most readers will have already heard of the Chroma-Chime, claimed to be the world's first microprocessor controlled electronic doorbell manufactured by **Chromatronics**.

This product is now available in kit form for the enthusiasts who want to build their own units. The kit comes complete with all parts including the



**Chroma-Chime kit from Chromatronics**

microprocessor chip, printed circuit board and a comprehensive assembly manual.

At £18 inclusive of VAT and postage the Chroma-Chime will certainly make a novel gift to add to the Christmas shopping list. Further details and kits can be obtained from **Chromatronics, Dept P.E., Coachworks House, River Way, Harlow, Essex**.

We hope to give a more in-depth report on the Chroma-Chime kit in the near future.

## TAPE/RECORD CARE

With the price of tapes and records on the increase each month, it would seem that **BASF** have taken the ideal opportunity to launch their Checkpoint record and tape care accessories.

Being their first venture into record accessories, they have produced special gift packs containing such items as cleaning fluid, record cleaning arm and strobe speed check discs. For the cassette recorder there's a cassette tape head cleaner and even an inspection mirror.


Apart from complete record and tape care kits all Checkpoint accessories are available separately in special bubble packs.

Prices of the **BASF** Checkpoint accessories vary from £7.94 for a complete record and cassette case kit to 30p for a record cleaning cloth. All units are available from most audio shops and some big stores.
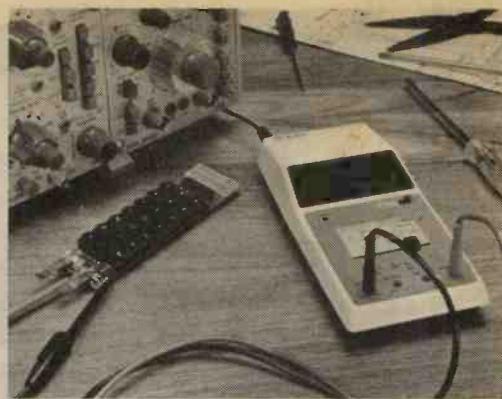
## DIFFICULT COMPONENTS

Readers who are experiencing difficulty in obtaining the Radiospares switches for the "Digital Multimeter", published in our October issue, will be pleased to know that **Sparks Developments** are able to meet their requirements.

They are also able to offer a low cost alternative to the 1 per cent high stability resistors required for the input divider chain. By using two resistors for each of R20–R26 allows the use of preferred resistance values from the E12 range.



**Sinclair PDM35 digital multimeter**

Also, by utilising the spread in values of a sample of components, a pair of resistors can be selected by measurement to obtain a final value very close to the ideal value.

They are prepared to supply a complete set of resistors R20–R27 to make up the input divider chain to an accuracy of 1 per cent. In addition they will supply printed circuit boards for the project with the necessary modifications to accommodate the extra resistors.

All enquiries should be addressed to **Sparks Developments, Dept P.E., 53 North Street, Melbourne, Derbys, DE7 1FZ**. A stamped addressed envelope should be enclosed with any enquiry.

## GOOD-BYE

*This is a very sad occasion for me to have to say goodbye to all readers of P.E., having been responsible for "Market Place" since the first issue.*

*This is due to a management decision that the magazine would benefit by a move to Poole, Dorset. Even though the Editor and myself, who first started Practical Electronics way back in 1964, feel that this is a bad move for the magazine.*

*Not being able to make this move West the Editor, Fred Bennett, and myself are having to relinquish our positions on Practical Electronics at a time when the efforts of all the P.E. Team have now made it No. 1 in its field in the U.K.*

*For myself it is particularly sad as I am the sole Editorial staff member of the Practical Group of magazines who worked with and was trained by the late F. J. Camm, the originator of the "Practicals".*

*I should like to take this opportunity to thank all my friends at our Printers, my colleagues on P.E. (particularly Dave Tilleard and Peter Mew of Advertising), our Advertisers and my close friend Gordon Godbold for an exciting and rewarding 13 years.*

*Finally, I hope that all readers of P.E. will continue to give the magazine the support it deserves.*

*Dave Barington*

...TWO-DAY COURSE

Sponsored by **PE**

# SYSTEM DESIGN with MICROPROCESSORS

Organised by INTERPROJECTS Limited  
Technical Services

**JANUARY 6 and 7 1978**  
9 a.m. to 5 p.m.

at the **INSTITUTION of ELECTRICAL ENGINEERS**  
**SAVOY PLACE LONDON W.C.2**

Conducted by **D. ZISSOS**  
Professor of Computer Science University of Calgary Canada

An intensive two-day course aimed to enable practising engineers, technical managers and hobbyists to design and implement their own microprocessor systems using methods that require no specialist knowhow of electronics or programming other than a basic knowledge of logic.

Professor D. Zissos is an established authority on logic design, on both sides of the Atlantic. He has written numerous books and articles on the subject. Professor Zissos is also a practising design consultant known for his pragmatic approach, with several projects to his credit.

#### Registration

The course is of limited enrolment and applicants will be dealt with strictly in order of receipt of completed coupon and remittance.

**Fee: £45 (plus £3.60 VAT)** includes a book "Problems and Solutions in Logic Design" by D. Zissos and comprehensive lecture notes.

*The proceedings will be opened by Professor C. Turner, King's College, London.*

Please use **BLOCK CAPITALS**

To INTERPROJECTS LTD.,  
29, Church Street, Edmonton, London N9 9DY

Please make the following reservations for the 2-day course System Design with Microprocessors.

Signature .....

Name .....

Address Home/Company .....

Delegates name


1.....

2.....

3.....

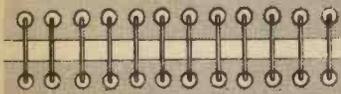4.....

Enclose cheque/PO £..... at £45 plus £3.60 VAT each. Payable to Interprojects Ltd.



# INDUSTRY NOTEBOOK

*By Nexus*



## MAIL BAG

The most distressing feature of being a columnist in 1977 is the occasional mail which arrives from young people seeking an entry into the electronics industry. The writers are generally out of work or in some dead-end job. Can I help? Would I please supply names and addresses of firms who have vacancies, give introductions. They are sad letters to receive, reflecting the high level of unemployment in our society, especially among school leavers.

Regretfully, I have to point out that while sympathising with the plight of my correspondents, it is no function of PE to act as an employment agency although, of course, we are always glad to receive letters from readers and give what advice we can.

It seems to me that career expectations are much higher today than they used to be. Young people are encouraged to believe that jobs will be found for them, whereas, we of an older generation were brought up to help ourselves and be far more self-reliant. We had to be prepared to work long hours for very little pay if this meant getting experience and a foothold on the bottom rung of the ladder.

Any sort of job would do to get a start and provide a chance to prove yourself. But if you fell down on the job, then it was a week's notice and out you went. My first job in electronics was as a junior service engineer at a local radio dealer for which I got £1.25 for a 48-hour week and no extra pay for overtime. It was a start on the road to becoming a qualified engineer.

Those were the bad old days of hire and fire, long hours and low wages,

but those days offered the opportunity of getting a start, however humble. Today there are so many rules and regulations that employers are much more reluctant to take on any but the obviously best youngsters. Greater job security would seem to have limited the job opportunities.

The other great change is in the electronics industry itself. It is still a great growth industry but not in the numbers of people employed. If we look back to the first generation of electronic computers we find that the original ENIAC computer developed in the United States and completed just over 30 years ago used 18,000 valves and consumed 100kW of power.

It seems laughable today but just think of the employment it provided. All those valves, valveholders, resistors, capacitors, the millions of interconnections all wired by hand and laboriously soldered, joint by joint. Even when they got it going it needed an army of trouble-shooters to keep it on stream.

The fact is that today an unskilled operator pushes an I.S.I. module in to a printed circuit board and passes it to a flow-soldering machine and in less than a minute has wired up as many as 5,000 components and the board works first time and keeps on working. And today, the chances are that even the testing of the board after assembly will be done on automatic test equipment by a semi-skilled operator.

This hard fact was brought home forcibly to me when I was looking over the last set of GEC accounts. This year's record profits and turnover were achieved with less people employed. The UK work-force in 1976 was 166,000 people. Today it is 10,000 less.

By no means is this reduction entirely due to things like I.S.I. but it does show the trend resulting from mechanisation and automation and modernisation.

If we look at Racal Electronics Group we find turnover in 1975 of £50 million generated by 4,187 people. 1976 saw a huge leap forward to £79 million generated by 5,028 people. This year's turnover was £122 million with 5,373 people. Note that turnover has more than doubled with only a 25 per cent increase in employment in the past two years. In the past year alone, turnover was up 53 per cent and yet the Group employed only just over 300 more people.

All is not lost however for the bright young person. Technology-based companies are hungry for talent. Last year GEC spent £150 million on R and D. So my advice to keen youngsters is to get qualifications as quickly as they can. An ONC or HNC won't guarantee a job but it will impress an employer that the applicant is career-minded and not just a job-hunter.

## PRICE BREAKTHROUGH

After the National Enterprise Board took a big stake in Sinclair Radionics everything seemed to go quiet, unusual for such a publicity-conscious concern. Then there was that sudden spate of press advertising for Sinclair calculators and now the big breakthrough in instruments.

To market a digital multimeter with a price tag of under £30 was a bold move. But such a price is only possible if the instrument can be produced in great volume. The DM2 had done well with over 25,000 units sold but the new smaller and cheaper PDM35 will do even better as it started off with firm orders for 20,000 from the USA alone.

Among the cost-cutting economies to get price down without sacrificing performance were the use of an adaptation of the Oxford calculator case as a housing, thus saving on tooling costs, and a precision resistor network on a single thick film circuit.

The designer of the DM2, John T. Nicholls, has also designed the PDM35. As head of Sinclair's Instrument Division he is already looking ahead to a range of instruments to be introduced to the international market in 1978. I understand that an up-market model will be an auto-ranging 4½ digit instrument but it is also hinted that there will be some down-market instruments as well. Sinclair Radionics is aiming to be the world's largest manufacturer of digital multimeters, at least in volume of instruments, by mid-1978.

Meantime, I can reveal that production of Sinclair's tiny t.v. set is rapidly expanding and although the bulk of production is ear-marked for the United States market it is expected to be available in the UK by Christmas.

## SIGNS OF THE TIMES

Selling information can be just as profitable and far less risky than selling products. But while some people talk, others get out and sell. Oil-rich Libya has just given Marconi Communications Systems Ltd its biggest ever single order, worth £9 million, for updating the radio facilities at Benghazi and Tripoli airports.

The capacitor manufacturers, Advance Filmcap, has changed its name to Gould Components Ltd., reflecting its change of ownership to the US Gould Corporation. I think it unlikely that the Advance name will be dropped from instruments but one never knows.

The Co-op has signed up for another £4 million worth of ICL main-frame computers. This is the biggest single commercial order that ICL has ever taken and raises Co-op purchases from ICL in the past 18 months to £6 million.

# Logic Probe LP-1

It's compact.  
It's versatile.  
It's beautifully designed.  
It identifies High, Low,  
or Intermediate levels,  
open circuits, and  
pulsing  
nodes.



It enables you to trace logic levels, pulses and logic sequences through complex digital circuits. It detects pulses as short as 50nsec and stretches them to  $\frac{1}{3}$  sec for easy observation.

**Try the LP-1 and you won't know how you ever managed without it!**

## How it works

You just clip the probe leads to the circuit power supply, setting the 'Logic Family' switch to DTL, TTL or CMOS. (CMOS position also covers HTL.)

Touch the probe's tip on the node you're investigating and the LP-1 lights up to show you exactly what you've got. The LED marked 'HI' comes on for logic state 1 (High) and 'LO' comes on for logic state 0 (Low).

The third LED, marked 'PULSE', shows the dynamic signal activity at the node under test. Set the switch to 'PULSE' and pulses as narrow as 50 nanoseconds are stretched to  $\frac{1}{3}$  second. Single-shot and low rep. rate pulses are clearly shown—you can't do that even with a fast CRO! High frequency pulses up to 10MHz will make the 'PULSE' LED blink continuously at 3Hz; and with asymmetric signals the 'LO' LED will come on for duty cycles under 30%, and 'HI' for those over 70%.

Another useful feature is 'Pulse Memory'.

Put the probe tip on to a node, switch to 'MEM' and the next logic change—positive or negative—or the next pulse edge, will cause the 'PULSE' LED to come on and stay on, until reset. Meanwhile, 'HI' and 'LO' LEDs continue to function as usual. No other probe or logic checking device gives you all that!

**ONLY £29.00**

Complete with instruction book, leads, and including VAT (8%) and post and packing.

It's easy to order

Telephone 01-890 0782 and give us your Access, Barclaycard or American Express number. Your Probe is in the post same day!

Or, write your order, enclosing cheque, postal order, or stating credit card number and expiry date. (Don't post the card!)

Alternatively, ask for our latest catalogue, showing all CSC time-and-cost-saving products for the engineer and the home hobbyist.

## Brief Specification:

Input Impedance: 100,000 Ohms, constant for all functions.

DTL/TTL Thresholds:

logic 1, 2.25V  $\pm$  0.15

logic 0, 0.80V  $\pm$  0.10

HTL/CMOS Thresholds:

logic 1, 1.70% Vcc

logic 0, 0.30% Vcc

Min. detectable pulse:

50 nanoseconds

Max. input signal frequency: 10MHz

Power requirements:

5 Volt Vcc, 30mA

15 Volt Vcc, 40mA


36 Volts max.

Size: 6.1 x 1.0 x 0.7 inches

(155 x 25 x 18mm)

Weight: 3oz (85g)

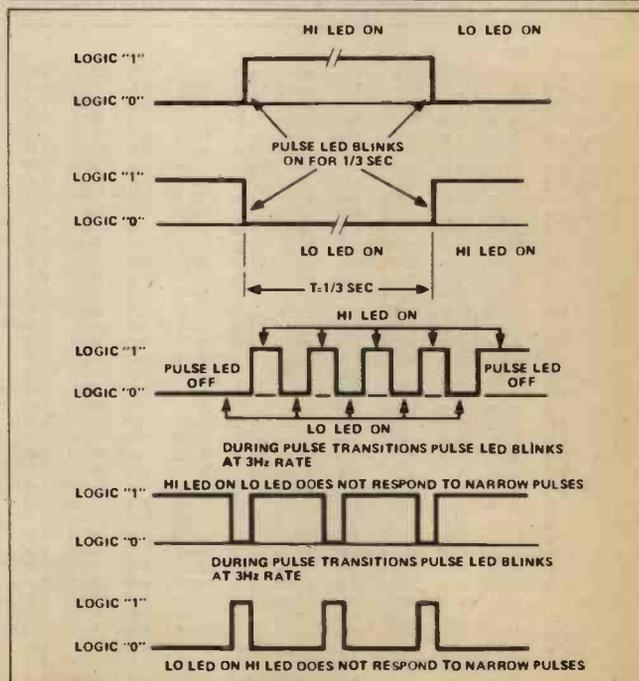
Power leads: 24 inches (610mm), colour coded.



CONTINENTAL SPECIALTIES CORPORATION





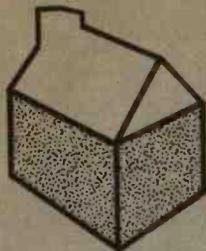

# Home Entertainment Show

M. Abbott

THE balconies remained empty in the Grand Hall of Olympia for what used to be called the Audio Fair, where just under ninety stands barely filled the main floor.

The exhibition ran from September 12 to 18, and giving lectures during that period at the *Wireless World* stand was John Logie Baird himself! This lifesize model of the inventor, with his blank wax face animated by a sound synchronised movie projector, was chillingly convincing, as he (it?) told of his early experiments in television.

Although numerous big names in hi-fi were present at the exhibition, their interest rating seemed "pushed over" in favour of such things as calculators, alternative uses for television, digital watches and clocks, including an *l.e.d.* clock radio from SI Electronic (UK) for under £20. The show was of no real interest to organ or synthesiser fans.

## INTELLIGENT TURNTABLE

There was a chance to see and operate the new ADC Accutrak +6 Turntable, and this gave a good example of the subservient microprocessor's ability to please, because this deck, which is expected to retail at around £150 inclusive of cordless remote control, can play up to six l.p.s using touch-switch activated "hands off" servo mechanisms which *really do* treat the records with loving care. There can be no mishaps, and the records are not dropped brutally on to the platter.

What is more, the system can be instructed to play any combination of tracks in any order. The micro-processor stroboscopically controls the turntable speed, and seeks out the selected recordings with an infra-red "eye" mounted in the cartridge, which counts the smooth unmodulated gaps between tracks. ADC are keen to point out that this is a *true* hi-fi class deck, and not a mere gimmick. The circuit blueprint for the Accutrak +6 measures nearly 5m by 6m, most of which is on a 2.5mm MOS chip!

## CORDLESS HEADPHONES

Listening to recordings with headphones is generally accepted as being more satisfying than using loudspeakers,

but nobody likes tripping over wires. For this reason Beyer Dynamic developed their infra-red cordless system. The ISS 76 Stereo Transmitter (there is also a mono version), along with the DT444S headphones incorporating infra-red receiver, will set you back about £190, but if you have your own headphones, you can buy a discrete plug-in type receiver for about £30.

The transmitter can take an audio signal from any source, and the infra-red output is semi-directional, therefore needing some walls around to "bounce" the signal.

## INFORMATION BY TV

Much activity was centred on television, providing an opportunity to try out the CEEFAX and ORACLE teletext systems for one's self, but by far the most impressive t.v. data service to use was that of Viewdata, both from simplicity of operation and the potential usefulness point of view.

Unlike other systems, the PO's Viewdata communicates via telephone lines and is completely user interactive. If the required page number is not known, you simply call up the general index, and select a suitable heading by entering its number. A more appropriate index will then appear, and further selection through this "family tree" of pages will bring you to anything from a Which Report on a particular freezer to an airline ticket booking facility. You could find the nearest golf course to your Summer holiday location, complete with fees and opening hours.

The services possible are endless; it simply depends upon which organisations feed their information into the system. For example, a motoring organisation could provide a diagnostic service. If your car will not start on a cold morning, by answering "yes/no" type questions, the most likely fault would be displayed.

As yet there is only a pilot service, and a full public service is not envisaged until the early 1980s. Because of this, there are no conversion modules which will instantly give your t.v. Viewdata capability, and a set designed for this additional facility would probably cost an extra £80

## MARKSMANSHIP BY TV

Anyone expecting to hear the roar of tank battles and dog fights at the t.v. games stands would have been disappointed, for with the odd uninspiring exception, only the "blipping" of the usual ball games could be heard.

Along with these games, Interton Electronic were showing the rifle range option of their Video 3001 multi-games (colour) unit, with which, for an extra £20 on top of a basic £52, you can plug in the V300 Rifle and aim at a spot of light bouncing around the screen, or call for the target to fly past in clay pigeon style. No scores appear on the screen (for obvious reasons) and the plastics "shooting iron" gets flooded by daylight, so the game has to be played in a darkened room.

## OTHER INTERESTS

The show was by no means all about hardware, and among the other activities were live music performances at the theatre, with an open invitation to make private recordings, and which included a demonstration by the BBC Radiophonic Workshop. There were lectures by various hi-fi experts too!

A cinema showed films of all kinds, one of which, produced by the BBC, gave an insight to local radio behind the scenes. The London Broadcasting Company (LBC), local radio, were indeed present, and transmitting live from Olympia throughout the show, whilst a few stands away, the BBC were busily receiving experimental transmissions of Proms concert music for live demonstration in Matrix H Quadraphony.

The new base of this exhibition may not please the hi-fi buff, but will undoubtedly provide greater scope for imagination in the future.



Beyer ISS 76 infra-red stereo transmitter and DT444S stereophone.



The ADC Accutrak +6 turntable.

# NEWS BRIEFS

## SERT MICROPROCESSOR SYSTEMS and SOFTWARE SYMPOSIUM

**M**ORE than 140 delegates attended the Society of Electronic and Radio Technicians three-day symposium held at the University of Kent last September. Twenty papers were delivered during the five sessions of this wide ranging programme. Overall the Symposium embraced a broad spectrum of user experience with contributions from active participants in this new technology from universities, technical colleges, semiconductor makers, industry, the Health Service, the Post Office and the National Institute of Agricultural Engineering.

The opening session covered introductory and basic matters. Software is a subject that makes many strong electronics men blanche, whereas the hardware side of the business is reasonably easy to digest. Papers dealing with machine codes and structure and language in software specification and design must have cleared points of doubt or confusion among those without much experience in program compiling.

### SOFTWARE SENSE

A point stressed during the fourth paper was the importance of consulting fully with the user at the initial planning stage and defining precisely the problem to be solved before attempting to construct a flow chart. Subsequent alteration or additions to the software can only be made at considerable expense and trouble. Whereas hardware costs have fallen dramatically, software tends to become more expensive and is the major cost factor in current computer systems. All this indicates a need to organise a method for examining programmes in detail at different steps. Here a leaf could be taken from the hardware engineer's book, for something analogous to circuit fault finding is the obvious answer.

### THINGS TO COME

Looking ahead, the same speaker ventured the view that soon microprocessor will speak to microprocessor—and that might spell doom for the human programmer. Software could be available on the shelf in the form of standard modules to be selected and plugged in just like hardware units.

In the meanwhile, however, the electronics designer has to face reality and get to grips with development systems, programmers, languages, editors, and compilers—subjects which received attention during Session 2 entitled Programming and System Design.

## LOW COST MICROPROCESSOR APPLICATIONS

The Third Session included papers dealing with Low Cost Storage on Audio Cassettes, an MPU System for the Enthusiast or Small Laboratory, and Microprocessors in Education. The presenter of the last paper enthused over US minicomputers, which are available in this country either as complete machines or in kit form, recommending these for students and hobbyists alike.

## COMMERCIAL APPLICATIONS

Session 4 was devoted to commercial applications; these included a microprocessor system which has replaced a conventional pneumatic logic control system in a factory air conditioning plant with a claimed 70 per cent energy saving; a system for monitoring and controlling commercial greenhouse environments; and a microprocessor control system for telephone coin boxes. The latter has been developed by Post Office Research to replace existing relay logic systems. The tremendous scaling-down of hardware (and of the circuit diagrams) was demonstrated with illustrations of the existing relay equipment and its probable successor. It is of interest to learn that the Post Office started on this project in 1972 before the first commercial microprocessor had become available.

## SOPHISTICATED SYSTEMS

Session 5 was devoted to advanced and unusual uses of microprocessors and included two papers relating to medical applications. Assuredly there is an exciting and socially important role for microprocessors in the Health Services. One example is a microprocessor-based foetal monitoring system devised to overcome the disadvantages of the normal chart recording bedside monitor which has been in use for many years. The system described has been used successfully for monitoring patients in the labour ward of a maternity hospital, and has been well received by medical staff.

The second medical application provided an example of computer assisted learning, a technique which has become well established for education and training in a wide range of subjects. The project described is a training equipment for patients undergoing haemodialysis treatment with artificial kidney machines. The haemodialysis Simulator/Trainer incorporates an Intel 4040 together with an alphanumeric display unit.

## SYMPOSIUM PAPERS

Reprints of all the papers presented at this symposium are available in a single volume comprising some 200 pages. This publication is available to Practical Electronics readers at the specially reduced price of £7.00 which is inclusive of postage and packing. Orders, with remittance, should be sent to the Secretary, 1977 MPU Symposium (Dept P.E.), S.E.R.T. 8-10 Charing Cross Road, London WC2H 0HP.

This reviewer for example was disappointed to find no mention of Messrs. Colpitts, Hartley, Cockcroft or Walton, Foster or Seely, or Wien in the List of Inventors. Truly an unfortunate slight to these gentlemen and their contributions to classic circuitry.

Under Transistors and Semiconductor Devices we find Esaki and the tunnel diode, also Ovshinsky and the amorphous semiconductor. But absent is Dr. Carl Zener.

What is an electronic invention? The author himself discusses this tricky definition in the Preface. One could also enquire exactly what is entitled to be referred to as "electronic". Surely not the Phonograph or Gramophone? Yet this invention of Mr. Edison's in 1877 is given a place. There are further examples of equipment or devices which taken on their own have no claim to be considered electronic, yet they are commonly accepted as so nowadays because in their modern form they are an integral part of some electronic amplifying or control system.

These points of criticism are in fact a kind of compliment to this book, for they demonstrate the fascinating nature of its contents and the thoughts they set going in the reader. The author invites additional data, for possible inclusion in a further edition. It is to be hoped that this work undergoes further research and expansion for it could be the basis of a badly needed central reference source in the field of electronics. But it will require revising and expanding at least once a year!

F.E.B



## BOOK REVIEWS

### ELECTRONIC INVENTIONS 1745-1976

By G. W. A. Dummer

Published by Pergamon Press

158 pages, 190 x 275mm. Price £5.50

**T**HIS is an unusual, if not unique, book. A source of reference for serious student work, but also an enticing volume for browsers, perhaps even a bedside book for electronics enthusiasts to dip into.

Brief descriptions of inventions with source reference are given in chronological order. Ample cross reference is provided through separate listings of subjects and inventors, plus an index.

The concept is excellent. The subject is so immense, the task therefore colossal. So the courage of the compiler is to be admired. This kind of reference book courts trouble—since spot the omissions is a game all can play!


# SOC20.


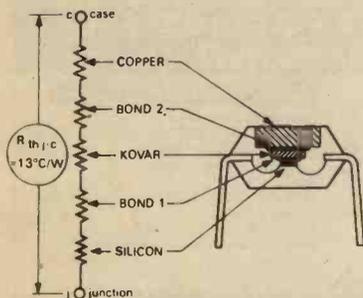
## The most powerful Monolithic IC amplifier in the world.

20 watts output (continuous sine wave) . . .  
 Less than 0.2% total harmonic distortion at *all* powers,  
*all* frequencies . . .  
 And totally electronically indestructible!


Until recently, all monolithic IC chips suffered from two basic design weaknesses. First, thermal runaway causing heat to build up as current increased; and second, short circuiting.



Standard plastic package with copper slug.

Until the SOC20 IC chip! This extraordinary new power amplifier chip is uniquely designed to improve thermal dissipation. It also has two separate built-in circuits, one of which measures on-chip temperature. If this should rise above 150°C the output transistors are switched off thus preventing thermal runaway.

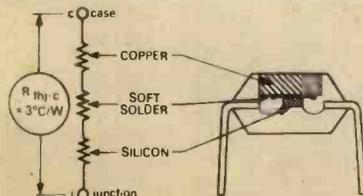And short circuits? The other circuit continuously monitors both current and voltage. If the product of current and voltage rises above a critical level, the



SOC20 plastic package with chip directly soft-soldered to copper slug.

drive is adjusted to bring the transistors within safe operating limits.

The amplifier can drive speakers of any impedance – maximum power will only fall outside the recommended 4 Ω – 8 Ω range.

And *any* pin on the chip may be shorted to *any* voltage in the system for *any* length of time . . . and *no* damage will occur!

### Superb quality . . . extraordinary power

The SOC20 isn't only safe . . . it's also extraordinarily sophisticated. Total harmonic distortion is less than 0.2% at all powers and all frequencies – and in normal use is well below 0.1%.

If power is at a premium, use two SOC20 amplifiers in 'Full Bridge' to give over 40 watts continuous into 8 Ω speakers.

The SOC20 is naturally guaranteed unconditionally for one year. Although with the SOC20's unique patented design, we think you'll have little cause to make use of any guarantee!

### Specification

- Maximum supply voltage ± 22 V (44 V total)
- Output power 20 watts continuous 4 Ω or 8 Ω
- Open loop gain 100 dB
- Supply voltage rejection 50 dB
- Input noise voltage 4 nV
- Number of transistors 18

Supplied with free printed circuit board, heat sink mounting bracket, comprehensive instructions, and suggested applications.

The SOC20 will work on any supply from 12-44 volts and therefore can be used for in-car as well as domestic applications. Apart from its obvious audio uses the fact that it is DC coupled throughout makes it ideally suited for servo systems – in radio-controlled models for example.

### Incorporate the SOC20 in your equipment today!

SOC20's cost £4.95 each, or £7.95 a pair for, say, stereo applications. Only a few readily-available components are needed to build a full amplifier unit.

Of course, the SOC20 comes with a 10-day money-back guarantee.

Science of Cambridge Ltd,  
 6 Kings Parade,  
 Cambridge, Cambs., CB2 1SN.  
 Tel: Cambridge (0223) 311488.

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me \_\_\_\_\_ (qty)  
 SOC20 Monolithic IC Amplifiers  
 (£4.95 each or £7.95 per pair,  
 inclusive of p&tp and VAT at 8%).

I enclose cheque/money order/  
 postal order for £ \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

(PLEASE PRINT).

PE/12



# PRACTICAL ELECTRONICS

## INDEX

**JANUARY 1977 TO AUGUST 1977**

(eight issues prior to new format)

PAGES	ISSUE	PAGES	ISSUE
1-80	January	321-400	May
81-160	February	401-472	June
161-240	March	473-544	July
241-320	April	545-616	August

IPC Magazines Ltd., Fleetway House, Farringdon St., London EC4A 4AD Reg. No. 53626

# VOLUME 13

# CONSTRUCTIONAL PROJECTS

Acid Meter .. .. .	178, 288, 382	Leakage Detector .. .. .	488
Alarm, Burglar .. .. .	342	Leslie Effect Circuit .. .. .	338
Alkali Meter .. .. .	178, 288, 382	Light Show .. .. .	418
Amplifier Power Meter .. .. .	46	Lights Reminder, Car .. .. .	422
Anti-theft Alarm .. .. .	342	Mastermind-I (5 parts) by P. F. Turney .. .. .	562
Auto-display Dimmer .. .. .	586	Meter, C/R .. .. .	580
Autowah by P. J. Goodwin .. .. .	206, 445	Meter, Millivolt .. .. .	120
Ballgame, TV .. .. .	434	Meter, pH .. .. .	178, 288, 382
Bandit, One Arm .. .. .	359	Meter, Power .. .. .	46
Beam Doubler for Oscilloscopes .. .. .	496	Meter, Volts .. .. .	258, 382
Breaker, Earth Leakage .. .. .	488	Microphone Mixer by R. S. Wilson .. .. .	36
Burglar Alarm by P. J. Fasoli .. .. .	342	Millivolt Meter by D. W. Easterling .. .. .	120
Capacitor Meter .. .. .	580	Mixer, Microphone .. .. .	36
Car Exhaust Monitor by E. Ball & R. A. Crane .. .. .	21, 306	Model, Pelican Crossing .. .. .	590
Car Lights Reminder by D. J. Saunders .. .. .	422	Model, Radio Control System .. .. .	18, 102
Car Systems Monitor by J. P. Seymour .. .. .	210	Monitor, Car Exhaust .. .. .	21, 306
Character Generator, Video .. .. .	126	Monitor, Car Systems .. .. .	210
Checker, C/R .. .. .	580	One Arm Bandit by K. Amor .. .. .	359
Chemical Meter, Acid .. .. .	178, 288, 382	Organ Tremolo Unit by L. F. Reeve .. .. .	338
Circuit Breaker, Earth Leakage .. .. .	488	Oscilloscope 7 Segment Display .. .. .	126
Clock Auto-Dimmer by E. B. Eves .. .. .	586	Oscilloscope Trace Doubler .. .. .	496
Constant Volume Intercom by R. A. Penfold .. .. .	184	Output Meter, Power .. .. .	46
Controller, Solar Heating .. .. .	98	Pelican Crossing by D. Edwards .. .. .	590
Control, Radio .. .. .	18, 102	pH Meter by K. E. Langford .. .. .	178, 288, 382
Converter, Sound to Light .. .. .	418	Photographic Timer .. .. .	366
C/R Meter by R. A. Penfold .. .. .	580	Pocket Stopwatch by M. W. Headington .. .. .	508
Crossing, Model, Pelican .. .. .	590	Power Output Meter by H. T. Kitchen .. .. .	46
Darkroom Timer by A. Koltai & G. S. Brimble .. .. .	366	Radio Control System by G. D. Southern .. .. .	18, 102
Day Indicator by M. H. George .. .. .	266	Reminder, Car Lights .. .. .	422
Detector, Leakage .. .. .	488	Resistor Meter .. .. .	580
Dice, Electronic .. .. .	446	Seven Segment Display For Oscilloscopes by L. M. Newell .. .. .	126
Digital Clock Dimmer .. .. .	586	Shaper, Envelope .. .. .	296
Digital Stopwatch .. .. .	508	Side-lights Reminder .. .. .	422
Digital Voltmeter by A. J. Buxton .. .. .	258, 382	Snap, Electronic Game .. .. .	132
Dimmer for Digital Clocks .. .. .	586	Solar Heating Controller by G. I. Williams .. .. .	98, 306, 382
Disco Light Show .. .. .	418	Sound effects, "Wah" .. .. .	206, 445
Display Auto-dimmer .. .. .	586	Sound To Light Converter by M. Hadley .. .. .	418
Display (7 seg) for Oscilloscopes .. .. .	126	Stopwatch, Digital .. .. .	508
Doubler, Oscilloscope Trace .. .. .	496	Synthesiser Tuning Indicator by C. Yallop .. .. .	522
Earth Leakage Circuit Breaker by K. A. Smith .. .. .	488	Systems Monitor, Car .. .. .	210
Electronic Die by G. Jones .. .. .	446	Timer, Darkroom .. .. .	366
Envelope Shaper .. .. .	296	Timer, Stopwatch .. .. .	508
Exhaust Monitor, Car .. .. .	21, 306	Trace Doubler for Oscilloscopes .. .. .	496
Fruit Machine, Electronic Version .. .. .	359	Transient Generator by R. Gwinn .. .. .	296
Game, Code-breaking (Mastermind part I) .. .. .	562	Tremolo, Organ .. .. .	338
Game, I.C. Snap .. .. .	132	Tuning Reference for Synthesisers .. .. .	522
Game, One Arm Bandit .. .. .	359	TV Sportcentre by A. M. Marshall .. .. .	434
Games, TV Sportcentre .. .. .	434	Twin Trace Doubler by R. A. Penfold .. .. .	496
Generator, Transient .. .. .	296	Video Games .. .. .	434
Guitar Autowah .. .. .	206, 445	Voltmeter, Digital .. .. .	258, 382
Headlights Reminder .. .. .	422	Voltmeter, Millivolts .. .. .	120
House Burglar Alarm .. .. .	342	Wah Effects Unit .. .. .	206, 445
I.C. Snap by P. D. Scargill .. .. .	132	Wattage Meter .. .. .	46
Indicator, Day .. .. .	266	Weekday Indicator .. .. .	266
Intercom, Constant Volume .. .. .	184		

# GENERAL FEATURES


Handling CMOS Devices by L. J. Gallace and H. L. Pujol .. .. .	452	Side-light Controller J. W. Willis .. .. .	535
INGENUITY UNLIMITED .. 54, 136, 217, 279, 376, 456, 531, 598		Simple Compressor Q. A. Rice .. .. .	141
Acoustic Relay T. Robinson .. .. .	218	Simple Logic Probe S. G. Bailey .. .. .	602
Active Crossover J. Macauley .. .. .	58	Simple Position Servo J. C. Hardman .. .. .	218
Automatic Car Aerial R. J. Darling .. .. .	137	Simple Power Supply Regulator R. Scott .. .. .	225
Bench Power Supply A. R. Winstanley .. .. .	217	Simple Tuning Fork Pek Yaw Kee .. .. .	221
Bistable Touch Switch P. S. Robinson .. .. .	279	Simplified Clock Display N. Coxhead .. .. .	142
Cheap Overvoltage Protector A. Damper .. .. .	138	Solar Panel Controller P. R. Williams .. .. .	531
Computer Voice Oscillator W. H. Montgomery .. .. .	221	Sound Operated Flash Trigger R. A. Dix .. .. .	57
Cycle Lighting A. Chadwick .. .. .	61	Thermal A.G.C. For Transistor Power Amplifiers R. Walsh .. .. .	226
DC Motor Controller J. Lidster .. .. .	279	Touch Switch N. Nazo A-Ruiz .. .. .	532
Digital Analogue Converter J. P. Fitzgerald .. .. .	225	"Trimphone" Warbler A. & J. Yeomans .. .. .	457
Digital Logic Checker P. D. Maddison .. .. .	138	TV Tennis Score Unit D. E. Launchbury .. .. .	376
Dual Power Supply N. Croucher .. .. .	54	Warning System Z. Najam .. .. .	599
Economical Relay A. A. Farman .. .. .	222	Memories by A. Briar .. .. .	26, 108
Fluorescent Light Invertor I. P. Kemp .. .. .	457	1—General account of memory devices .. .. .	26
Graphic Level Display L. Robinson .. .. .	57	2—Read Only Memories and Charge Coupled Devices .. .. .	108
Guitar Frequency Doubler P. G. Ludgate .. .. .	598	Microprocessors Explained by R. W. Coles .. .. .	199, 280, 346, 426, 515, 570
Guitar Fuzz Unit J. White .. .. .	61	1—Introduction to microprocessors .. .. .	199
Guitar Tuning Reference W. P. Bond .. .. .	600	2—The m.p.u. chip .. .. .	280
Heads Or Tails P. Chambers .. .. .	142	3—The instruction set and programming .. .. .	346
Initial Reset E. V. Dias .. .. .	279	4—Peripheral chips and memories .. .. .	426
Joanna Modification D. A. Boyd .. .. .	381	5—Input/output devices .. .. .	515
Ladder Oscillator With CMOS C. J. Collins .. .. .	58	6—A buyers' guide to m.p.u. chips .. .. .	570
Light Control System M. Whyte .. .. .	600	Mobile Disco Techniques by N. McCleod .. .. .	270, 372
Logic Probe J. Froggatt .. .. .	222	1—Equipment and operating techniques .. .. .	270
Low Cost VCA M. Bryant .. .. .	602	2—Monitoring systems, speakers, and ancillaries .. .. .	372
Modified Squarewave Oscillator A. Glover .. .. .	61	Noise Sources by D. Maynard .. .. .	134
Motor Driver A. P. Wilkinson .. .. .	378	Programming A Microprocessor by D. B. Johnson-Davies .. .. .	299
Night Light Latch R. N. Johnson .. .. .	456	SEMICONDUCTOR UPDATE by R. W. Coles .. .. .	35, 119, 192, 265, 355, 495, 568
Overheat Indicator J. W. Cheshire .. .. .	137	RCA 3140 BI MOS op amp, Siliconix LD130 DVM chip .. .. .	35
Percussion Effects L. Robinson .. .. .	141	Zilog Z80 microprocessor chip, National DM71, LS95, LS96, LS97, LS98 tristate buffers, ITT DITAL dot matrix display .. .. .	119
Polyphonic Keyboard System E. F. Flint .. .. .	136	GIM AY-3-8500 TV games chip, Siliconix VMP2 power MOS, Raytheon 4151 v to f converter .. .. .	265
Programmable Melody Generator J. R. Skeels .. .. .	382	Siliconix T100 & T300 j.f.e.t. Texas TL430 programmable Zener, Ferranti F100L microprocessor .. .. .	355
Random Light Display P. R. G. Reynolds .. .. .	599	LM3911 thermometer chip, Reticon SAD1024 delay .. .. .	495
Sawtooth Triangle Converter D. F. Bowers .. .. .	226	Texas TL497 switching regulator, Texas TBMO101 bubble memory, RCA CD40107BE CMOS driver .. .. .	568
Sensitive Burglar Alarm I. Musa .. .. .	54	Thermal Resistance And Derating Of Devices by C. Rudd .. .. .	30
Sequential Timer P. R. G. Reynolds .. .. .	532		
Seven Segment Weekdays H. Pyman .. .. .	458		

# NEWS AND COMMENT

BOOK REVIEWS .. .. .	24, 106, 191, 567	Motorola D2 Kit Reviewed <i>D. B. Johnson-Davies</i> ..	500
Computer Hobbies In The US <i>Roger Woolnough</i> ..	115	NEWS BRIEFS .. .. .	53, 116, 195, 298, 306, 345, 424, 524, 588
EDITORIAL .. .. .	17, 97, 177, 257, 337, 417, 487, 561	PATENTS REVIEW .. .. .	65, 145, 214, 386, 455, 527, 596
INDUSTRY NOTEBOOK <i>Nexus</i> .. .. .	45, 130, 209, 286, 385, 454, 514, 584	POINTS ARISING .. .. .	30, 101, 306, 382, 445
Intercept Junior Reviewed <i>R. W. Coles</i> .. .. .	442	READOUT .. .. .	66, 146, 451, 566, 585
MARKET PLACE .. .. .	32, 124, 370, 528, 589	SC/MP Reviewed <i>R. W. Coles</i> .. .. .	196
Microprocessor Competition .. .. .	507	Scrumpi Kit Reviewed <i>D. B. Johnson-Davies</i> ..	577
Microprocessor Forum .. .. .	195	Selling Microprocessors .. .. .	191
Microprocessor Report .. .. .	356	SPACEWATCH <i>Frank W. Hyde</i> .. .. .	25, 107, 188, 269, 352, 433, 597
Microvision TV .. .. .	198	STRICTLY INSTRUMENTAL <i>K. Lenton-Smith</i> ..	371

# SPECIAL SUPPLEMENTS

Diode Identichart .. .. .	March 1977	COMPETITION	
PE Transistor Guide 77 .. .. .	May 1977	Microprocessor Competition .. .. .	31
Putting It Together .. .. .	April 1977	FORUM	
ANNOUNCEMENT		Microprocessor Forum .. .. .	131
Back Numbers .. .. .	585		

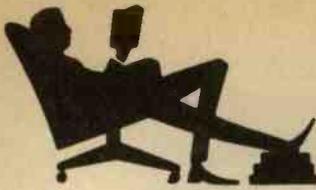

# BOOK REVIEWS

## EDISON THE MAN WHO MADE THE FUTURE

By Ronald W. Clark

Published by Macdonald and Jane's  
256 pages, 240 × 165mm. Price £6.95

THE Edison story is perhaps the most romantic of all in the realm of invention. From his earliest years Thomas Alva Edison had an enquiring mind that could be satisfied only by intense experimentation. Throughout his life a relentless physical drive coupled to a great creative mind bore a prolific crop of inventions such as no one else has equalled, as evidenced by the vast number of patents in his name.

The talking machine (phonograph), the electric light bulb, and electricity generation and distribution are his most memorable achievements, but there were many others. Not a scientist, but essentially a practical experimenter and innovator, Edison nevertheless was an instigator of research and development, his Menlo Park "invention factory" being the forerunner of the modern R and D Department.

*Edison, the man who made the future* is the latest addition to a long list of published biographies. Published this October no doubt to coincide with the centenary of the gramophone, Ronald Clark's book is a good introduction to the great man. There are obvious difficulties in treating adequately this subject within a mere 250 pages; however Edison's life, his inventions and the (often tempestuous) commercial affairs that formed a large part of the Edison story are described in sufficient detail for this purpose. Another feature that will ensure this book's popularity is the historically interesting photographic record presented in 48 pages of sepia prints. This colour, used also for the text, intensifies the sense of history, and plays its part in making this an attractive volume. F.E.B.

## PROBLEMS AND SOLUTIONS IN LOGIC DESIGN

By D. Zissos

Published by Oxford University Press

146 pages, 155 × 230mm. Price £1.75 Paperback;  
£3.50 Hardback

MOST elementary books on logic design show how, using Boolean algebra, a minimal logic circuit can be derived from the truth-table. However in practice theoretically correct circuits may not work, due to race-hazards (spikes caused by gate delays), or may need modification to allow for fan-in restrictions (the maximum number of inputs available on each gate).

Previously these aspects of the design had to be worked out empirically, but in this book Professor Zissos shows how these factors can be taken into account in the design stages by using some elegant methods derived by him. Furthermore he shows how sequential logic circuits too can be systematically designed, using his sequential equations which give the new states of the circuit in terms of its previous states.

Most of the book is taken up with, as its title suggests, worked problems illustrating the various techniques. These fifty-one problems fall under four headings:

Unlocked sequential circuits; e.g. traffic lights, pump controller, panel game, electronic dice.

Clocked sequential circuits, using flip/flops; e.g. word scanner, paper-tape reader, parity circuit.

Counters; e.g. programmable counter, self-locking counter, 24-hour clock.

Combinational circuits; e.g. seven-segment display, binary-to-gray converter.

As can be seen from the above examples the problems chosen are practical and entertaining, and where the techniques are not explained in quite enough detail the problems provide the necessary supplement. The book assumes no specialist knowledge and should provide anyone with the necessary tools for designing practical digital circuits. D.J.D.

## AN INTRODUCTION TO MICROCOMPUTERS: VOLUME 1—BASIC CONCEPTS

By Adam Osborne

THIS is an expanded version of the chapters forming the first half of an earlier edition of *An Introduction to Microcomputers* which sold 30,000 copies in the USA. The book deals with microcomputers on two levels. Firstly it contains a very clear description of the fundamental concepts of computing—binary arithmetic and boolean algebra—and explains how a typical microprocessor operates. It comes into its own, however, in the later chapters which cover such subjects as input/output and memory addressing, and provide answers to questions like "what is the difference between cycle stealing and simultaneous DMA?" and "why do few microprocessors provide indirect memory addressing?". In dealing with the internal logic of the microprocessor the chip slice is explained, and the book concludes with the compilation and discussion of a hypothetical instruction set.

The book is well illustrated with diagrams clearly drawn and in a uniform style (not just extracted from manufacturers' data as is unfortunately sometimes seen), and a novel technique of dividing the text into sections of boldface type, for fundamental facts, and lightface, for explanations in greater depth. makes the book useful as a reference source. All in all it provides well written, authoritative, and very readable explanations of most aspects of microcomputer design. D.J.D.

## A PRACTICAL INTRODUCTION TO ELECTRONIC CIRCUITS

By M. H. Jones

Published by Cambridge University Press

237 pages, 175 × 255mm. Price £9.50 Hardcover  
£3.95 Paperback

AN excellent up-to-date text book practically orientated and using well-known circuit devices as illustrations throughout. Explanations are clear and to the point, uncluttered by unnecessary delving into non-essentials. There is no excessive recourse to mathematics. Component values and pin connections are given in the circuit diagrams so that the readers can follow out the author's recommendation to prove by practise. For Dr. Jones is, as he tells us in the Preface, a staunch believer in learning by constructing and experimenting.

One chapter is devoted to thermionic valves and the cathode ray tube otherwise the book concentrates on solid state devices. The function of bi-polar, field-effect, power and other discrete devices is explained and such devices are then shown in typical applications. Integrated circuits received full attention. The 741 is the most frequently used linear example. One chapter on logic, counters and timers introduces digital i.c.s—TTL, the 555 timer and alternative forms of logic such as MOS and CMOS.

All the well-known circuit building blocks seem to be covered including one of fairly recent introduction, the bucket brigade. This makes the book a good work of reference apart from its main purpose as a textbook for those who have already some knowledge of simple circuits and who wish to progress with a serious study of the subject. *A Practical Introduction to Electronic Circuits* deserves to become a standard work for the hobbyist and student. F.E.B.

## STARTING AND RUNNING A SMALL BUSINESS



By Alan Sproxtton

Published by United Writers

130 pages, 210 × 130mm. Price £3.95

THE component retailing business offers plenty of examples of "The Small Business". It is appropriate therefore that a book on this subject should come from the pen of one who has established his own highly successful component business, well-known in the constructor field. Mr. Sproxtton's experiences as an entrepreneur have not been limited to electronic components but he has in the past been involved in several different business ventures.

Drawing freely upon all of this wide background the author has written a book that is enjoyable to read and imparts helpful information to the would-be proprietor. The author explains the problems every small owner faces and from personal experience offers sound and valuable advice, interlacing the hard facts of business life with amusing anecdotes and humorous asides. In this free and entertaining approach he has been aided and abetted by Jack Pountney, Art Editor Practical Electronics, who has provided this book with amusing illustrations. F.E.B.

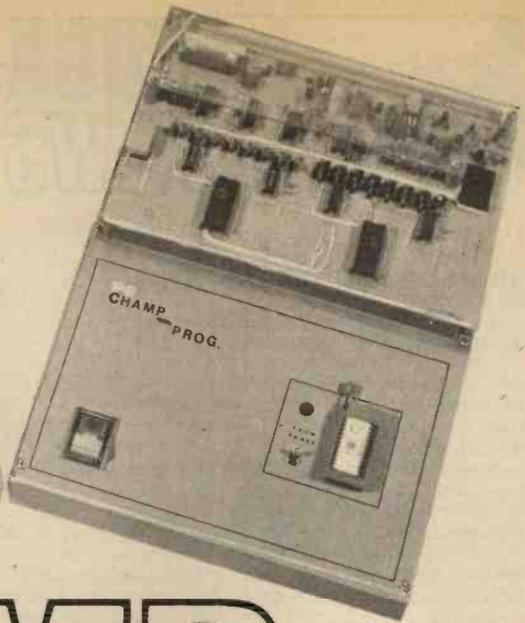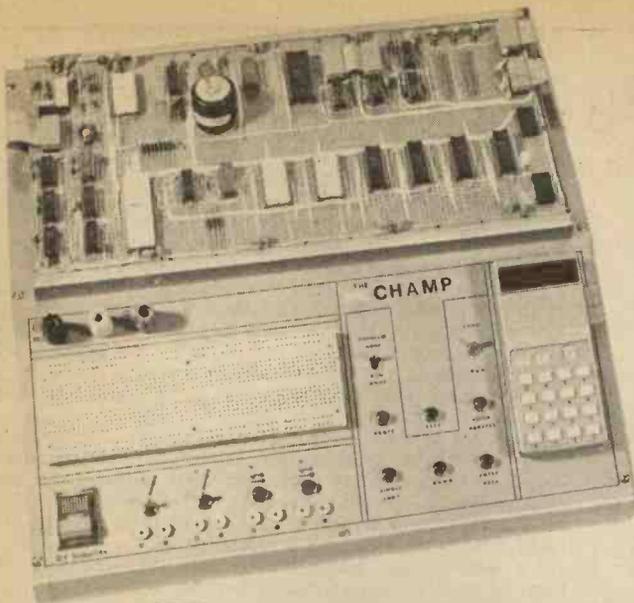

# PE CHAMP

R. W. COLES  
B. CULLEN

## PART FOUR

Now that we have examined the circuitry of the CHAMP main board, and the details of its interface with the control panel and keyboard, we are in a position to move into the construction phase. This month we will consider the assembly of the main board, the design and construction of the power supply module, and the assembly of the plinth which supports the main board, and houses the power supply module.

### STRIPBOARD LAYOUT

The CHAMP main board consists of a piece of 0.1in matrix Veroboard measuring 304.6 × 165mm (12 × 6.5in). This is an unusually large size for Veroboard, and if you intend to build CHAMP PROG it may be wise to buy two sheets at the same time, because of course CHAMP PROG uses the same type of board.

The board layout and the required track breaks are shown in Fig. 4.1 and Table 4.1. Before working on the board we would recommend chamfering the edges where they slide into the self adhesive card guides, because these guides grip very firmly and this can hamper board removal later.

As far as possible, the Veroboard component geography is similar to the circuit layout of Fig. 2.3, and although there are some differences, constructors should have no difficulty in finding their way around. Notice in particular that the program memory data and address buses, and the four bit m.p.u. bus are each represented by parallel runs of Veroboard copper track. This arrangement is costly in board space, but is more than made up for by the added convenience when wiring up and trouble shooting, and it provides a layout which can be related to the circuit diagram very easily.

### SOCKETS

On the prototype board all i.c.s were mounted using Soldercon socket strips. This technique is strongly recommended for three reasons:

- (a) Sockets are essential in MOS systems because of the damage which can occur if an LSI chip ever has to be removed.
- (b) Soldercon pins are the cheapest way of providing sockets.
- (c) Soldercon pins have the advantage that wiring up can take place *between* the i.c. pins instead of *just outside* the i.c. pins, as would be necessary with "raft" type sockets. This is a big help when using 0.6in wide chips, and allows maximum use of available board space.

The *disadvantage* of Soldercon pins is that they are not much good when repeated insertions or withdrawals of the chip is necessary.


This is not a problem with the CHAMP integrated circuits, but the interfacing sockets (SK1-8) certainly will get well used, and consequently conventional low profile 16-way d.i.l. sockets should be used in these positions. It is also possible that constructors of CHAMP PROG will find themselves regularly swapping 4702A chips around on the CHAMP board, and in this case 24-way low profile sockets could be substituted in the IC18 and IC19 positions, although this has not yet been found necessary on the prototype.

You may have noticed that the prototype board sports an extra 28-way Soldercon i.c. socket in the top right-hand corner. This was installed in the prototype to allow

**TABLE 4.1.**

**Track cut positions to be made on CHAMP Veroboard**

Row	Positions
5	BN-BF, BB-AV, AR-AJ, T
6	AD-W
9	BN-BE, BB-AU, AR-AJ, T, R-H
11	AD-W
14	BN-BF, BB-AV, AR-AJ
15	V-H
18	BN-AS, AE-AB, D, E
19	AR-AJ, AA-X
20	W
23	V-H
24	BP-AT
29	BP-BD, V-H
31	BA-AT, Y
35	P-H
36	BC-AT
38	P-H
39	BC
40	BB-AT, BD
41	BC
43	R-H
45	BD-AT, AH, AF
46	V, T
48	R-H
49	BA-AT
53	R-H
55	BE-AT
57	X-H
61	BE-AT
66	X-H
67	BE-AT
69	AA-U, R-H
72	AA-H
73	BD-AT
76	AA-H, AB
78	BD-AT
81	R-H
82	AA-T
83	BD-AT
86	AA-T, R-H
87	S
88	BD-AT
91	AA-U, S-H
93	BD-AT
94	F, E, D
95	AA-L
96	K, J, H
98	BD-AT
100	H, D,
101	AA-L, E
103	BD-AT
105	H, D,
108	BD-AT, E
109	AA, U
111	BP-BF, T-N
112	AB-U, M-D
115	BN-BF, AS-AJ
116	BP, AB-U, N-D

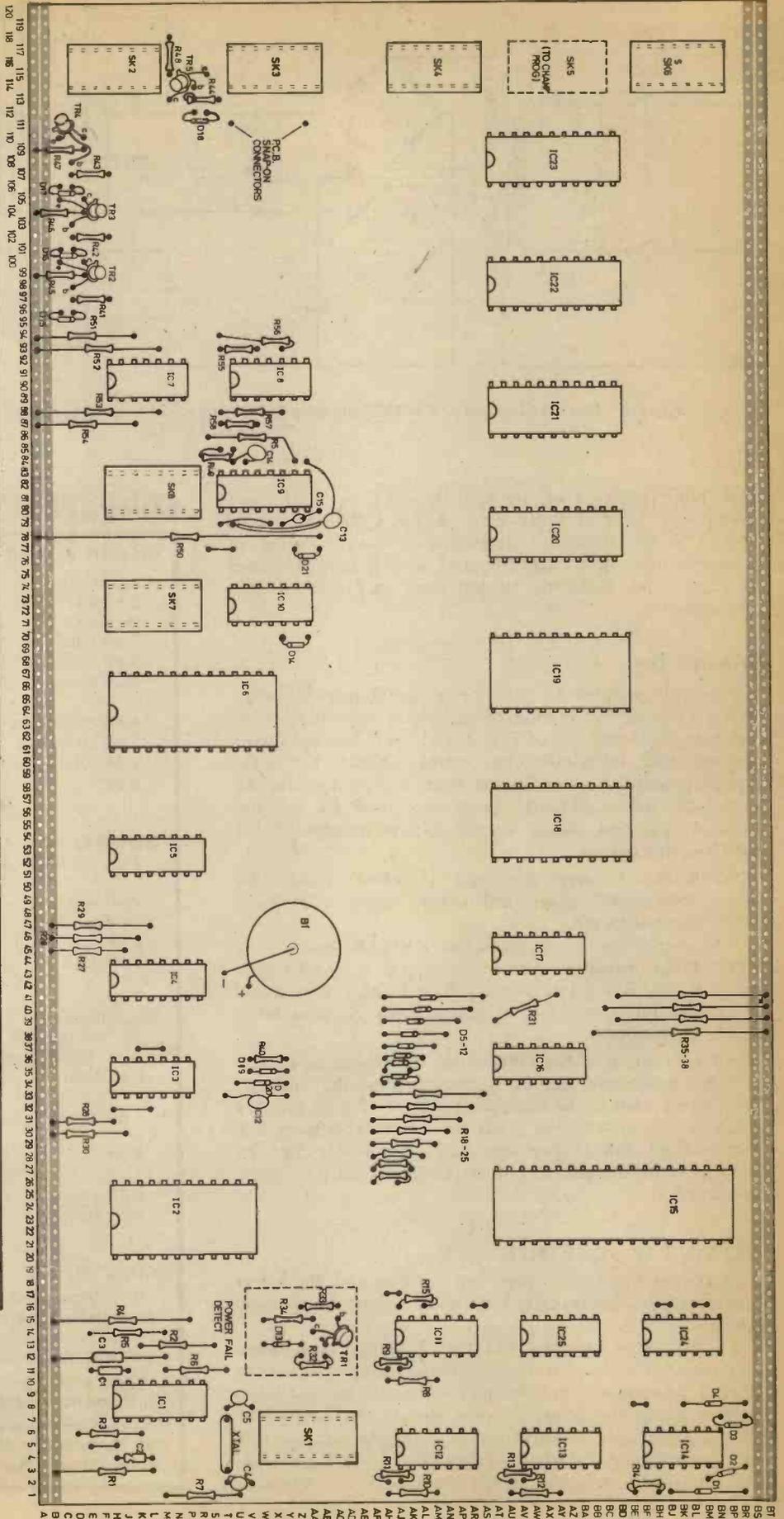

**Fig. 4.1. Basic CHAMP board layout. Wiring details of CHAMP complexity cannot be superimposed on this diagram and so for full assembly of this board reference to Fig. 2.3 should be made**

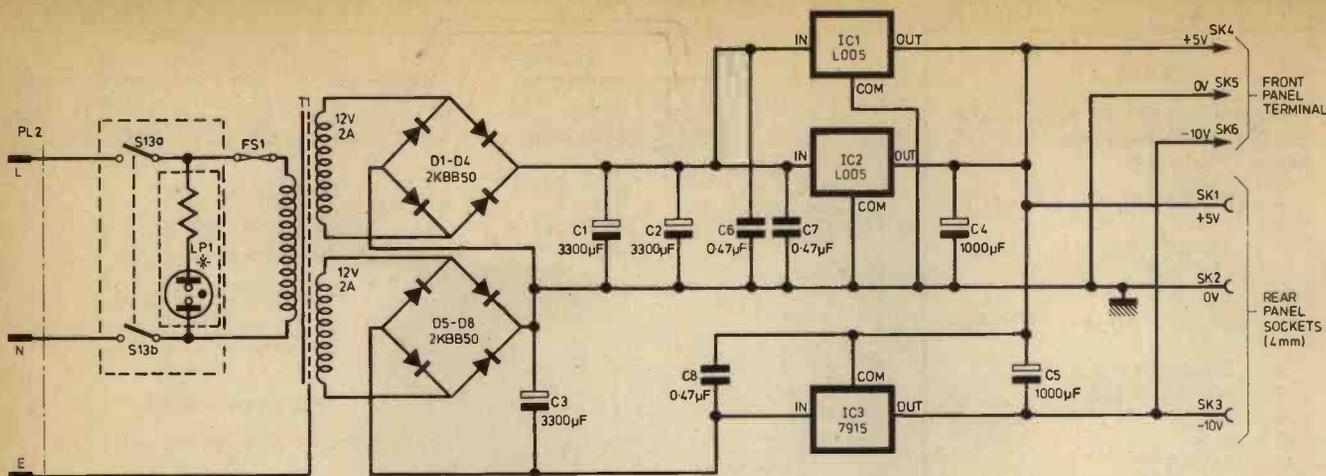


Fig. 4.2. Circuit diagram of CHAMP power supply. Fuse FS1 is only essential if a fused mains plug is not used and should be 2A

the future addition of an 8251 USART or 8253 programmable interval timer chip to the CHAMP board, should it be desirable. With hindsight we consider it unlikely that most constructors would require these facilities, and therefore suggest that this area is left uncommitted.

### WIRING UP

It is not possible to produce a comprehensive inter-wiring diagram for Veroboard circuits of this complexity, but with combined use of Fig. 2.3, Fig. 4.1, and the board photographs, interconnection wiring should be fairly straightforward for the experienced constructor. In the prototype yellow KYNAR wire was used for all the logic wiring, and this is very highly recommended for the following reasons:

- Kynar is very fine and therefore avoids the "Spaghetti" effect which can occur with p.v.c. insulated wire.
- Despite its small diameter, KYNAR has a very tough insulation which is nevertheless easy to strip.
- KYNAR is silver plated which helps you to avoid dry joints and assures you of high integrity interconnections.

The *disadvantage* of KYNAR is that it seems to be difficult to find in amateur suppliers' catalogues at the moment. It is widely used in the electronics industry for its primary purpose of wire-wrapped joints and is available from R.S. Components, but if you are unable to secure any, be sure to substitute the very finest single strand p.v.c. wire you can find.

### GETTING IT TOGETHER

Once the board has been cut to size and the edges chamfered, track breaks can be made, which conform to Table 4.1.

The Soldercon pins and d.i.l. sockets should be soldered in position first, to provide a reference framework for the discrete components and the interwiring, but the bandolier strip to which the Soldercon pins are attached should be left in place until construction is complete, as this will help prevent any distortion or loss of pins during soldering. The exact order in which the discrete components

## COMPONENTS . . .

### CHAMP POWER SUPPLY & MAINFRAME

#### Capacitors

2 off 0.1µF	30V ceramic disc	C9, C10
3 off 0.47µF	Ceramic disc	C6, C7, C8
2 off 100µF	35V tant bead	C11, C12
2 off 1,000µF	25V electrolytic	C4, C5
3 off 3,300µF	25V electrolytic	C1, C2, C3

#### Semiconductors

2 off L005	Regulator	IC1, IC2
1 off 7915	Regulator (Technomatic)	IC3
2 off	Bridge rectifier	B1, B2
	2 Amp (I.R. 2KBB50)	

#### Switches

4 off s.p.d.t.	Doram type sub min	S1, S2, S11, S12
4 off c/o	Doram type min push	S5, S6-S8
2 off n.c.	Doram type min push	S3, S4
2 off n.o.	Doram type min push	S9, S10
1 off d.p.s.t.	Doram type illuminating rocker switch	S13

#### Miscellaneous

T1	0-12 0-12V, 25VA winding	
PL2	Mains chassis mounting plug	
3 off 4mm	Socket/terminal post	SK4, SK5, SK6
1 off 16-pin	d.i.l. socket (or other connector)	SK7
1 off	Experimenter 300 Breadboard	
8 off 2mm	Sockets	SK8-SK15
3 off 4mm	Sockets	SK1, SK2, SK3

#### CONSTRUCTOR'S NOTE

The large sheets of Veroboard can be obtained from **A. Marshall (London) Ltd.** A suitable transformer for T1 can be obtained from **Doram**, order code: 66-150-6, or **RS Components**, order code: 207-251.

Card guides for the CHAMP main board may also be obtained from **Doram**, order code: 68-337-1.

The breadboard (EXP300) is available from **Continental Specialties Corporation (UK) Ltd.**, Spur Road, North Feltham Trading Estate, TW14 0TJ.

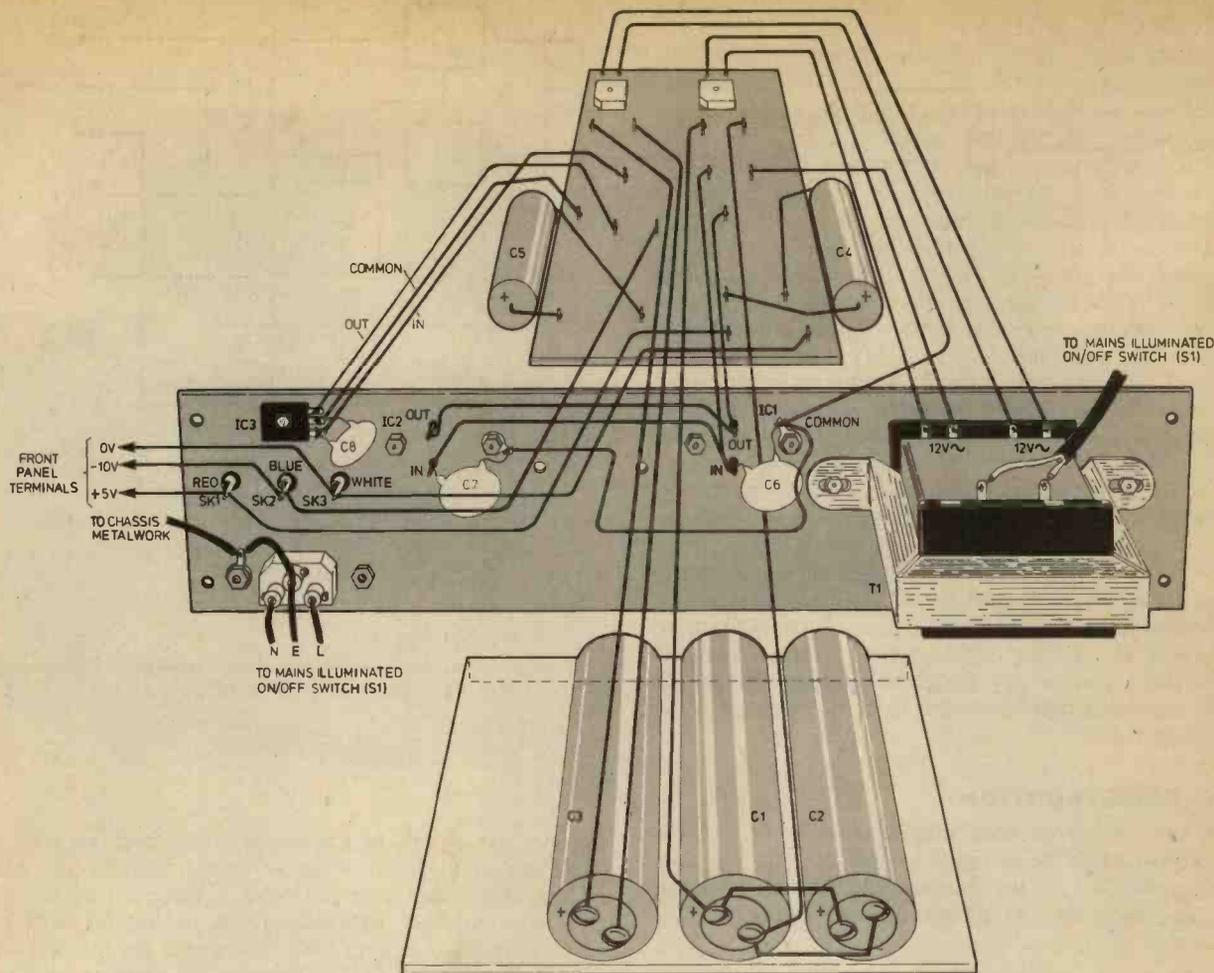


Fig. 4.3. Exploded view and wiring layout of CHAMP power supply. The p.c.b. and the large electrolytic support plate are both mounted on the CHAMP back-plate

and the interwiring are added, is best left to individual preference, but of course, the MOS chips should *not* be plugged into their places until construction is complete, to prevent accidental damage. The last component to be mounted should be the DEAC stack, and in fact it might be wise to add this only after the circuit has been checked with power applied.

The power connections to the board are made via three wander plug terminated flying leads, and these are made with p.v.c. insulated flexible wire soldered to terminal pins inserted in the CHAMP board power bus tracks. Terminal pins are also used to provide the keyboard power, and two are situated adjacent to SK3 for this purpose, wired to +5V and 0V respectively.

The 16-way interconnection jumpers from SK7 to SK8, and from SK1 to the front panel socket can ideally be made up using ribbon cable, and 16-way plugs of the penetrating "no solder" variety such as those made by T & B Ansley, which was the method used in the prototype. The main problem with these components is availability; putting them together was found to be easy even without the special tools made for the purpose, and much more convenient than making soldered connections. An alternative to the ribbon cable system is to use d.i.l. "header plugs" with soldered multiway cable, a more tedious but perfectly sound solution.

## POWER SUPPLY CIRCUIT

The CHAMP power supply is designed to provide sufficient current to power the main board, the CHAMP-PROG board, and any reasonable combination of interface circuitry on the breadboard socket. The specification therefore calls for a +5V supply at 1A, and a -10V supply at 750mA. In practice these current specifications have been comfortably exceeded.

The circuit of the power supply module is shown in Fig. 4.2, and as can be seen, the design is fairly conventional, using fixed voltage regulators to set the output potential and provide the necessary high quality regulation. The positive supply uses two L005 devices in parallel to meet the current requirement, but there is no reason why LM309Ks should not be substituted directly if available. The LM309K will also provide a higher current capability if this should be necessary, although to take full advantage of this, the bridge rectifier would have to be changed to a 4 amp unit to prevent overheating.

A negative regulator from the 79' series i.c.s is used to provide -10V but since -10V units are not available, a 15V device (the 7915), is used with its common terminal referenced not to zero volts, but to the +5V output from the L005s.

This configuration works well with no compromise of the short circuit protection provided in the regulator.

## POWER SUPPLY LAYOUT

The power supply is built as a module which can be tested independently of the other CHAMP components, and which can be removed easily from the plinth as and when necessary. The module uses the aluminium back panel of the plinth as its main structural component and also as a heat sink for the regulators and transformer. The large electrolytic smoothing capacitors are supported by an aluminium tray which rests on the bottom panel of the plinth for stability, and for the sake of neatness, some of the circuit interconnections are provided by a printed circuit board which mounts on a bracket also attached to the back panel.

Figure 4.3 shows the overall arrangement and the connections required, and this should be compared with the photograph of the unit assembled in the plinth. The printed circuit board layout is shown in Fig. 4.4, although 0.15in matrix Veroboard or even pin-board could be used instead if p.c.b. making is not your area of interest.

The only thing to remember when wiring up the unit, is that wire of sufficient diameter to handle the currents involved should be used, and that all terminals conducting mains voltage should be properly insulated. It is of course *essential* that all exterior metalwork be connected to the mains earth to prevent any danger of electric shock, and CHAMP should always be used with a 13 amp plug fitted with a 2 amp fuse.

## PLINTH CONSTRUCTION

The plinth design has been simplified as far as possible so that construction is straightforward, but as you can see, the appearance of the finished unit is very pleasing to the eye. Materials and dimensions are given in Figs. 4.5 and 4.6.


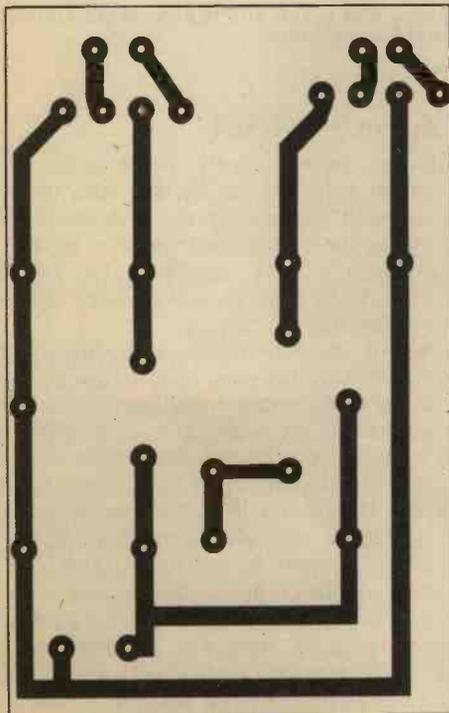



Fig. 4.4. Printed circuit layout of CHAMP power supply, p.c.b.

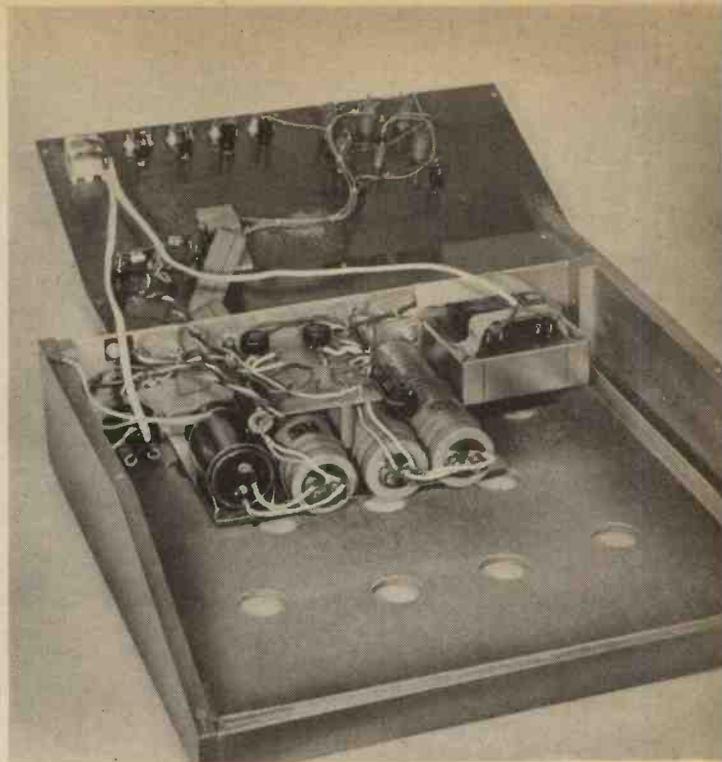

The first step is to cut the plywood parts to size, and it is important at this stage to ensure that the two plinth side members are identical. This is achieved by clamping the sides together with G clamps, or binding with tape before finally trimming both to size. On the inside bottom edge of the sides, mark a line equivalent to the thickness of the bottom panel, and similarly on the inside rear edge, mark a line equivalent to the thickness of the back panel, and finally, on the front edge draw a line equivalent to the thickness of the front edging strip.

The plywood runners should be cut to fit inside these marks, and then pinned and glued in position with a woodworking adhesive such as Evostick Resin W. If a large illuminated mains on/off rocker switch like the one in the prototype is used, it will probably be necessary to truncate the left-hand plywood runner to provide the necessary clearance for the switch body. The bottom panel, when cut to size, should have a number of air holes drilled in it to allow for convection cooling of the power supply module, whereupon it can be primed and glued to the sides and the front edging strip.

It is a good idea to temporarily attach the aluminium back panel at this stage, so that the plinth is properly aligned while the glue hardens. The aluminium top panel or cover should be carefully cut to size, and all the

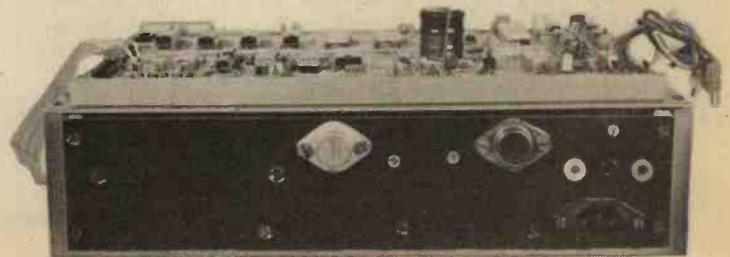


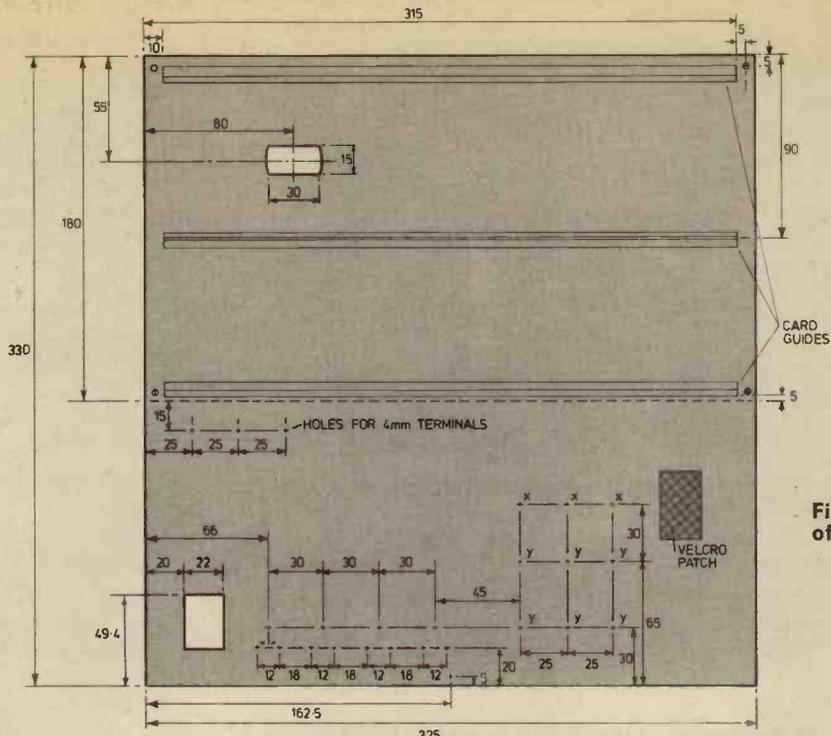


Fig. 4.5. Top/front panel of CHAMP unit

"x" HOLES • 6.6mm DIA.  
 "y" HOLES • 7.13mm DIA.


TOP/FRONT PANEL

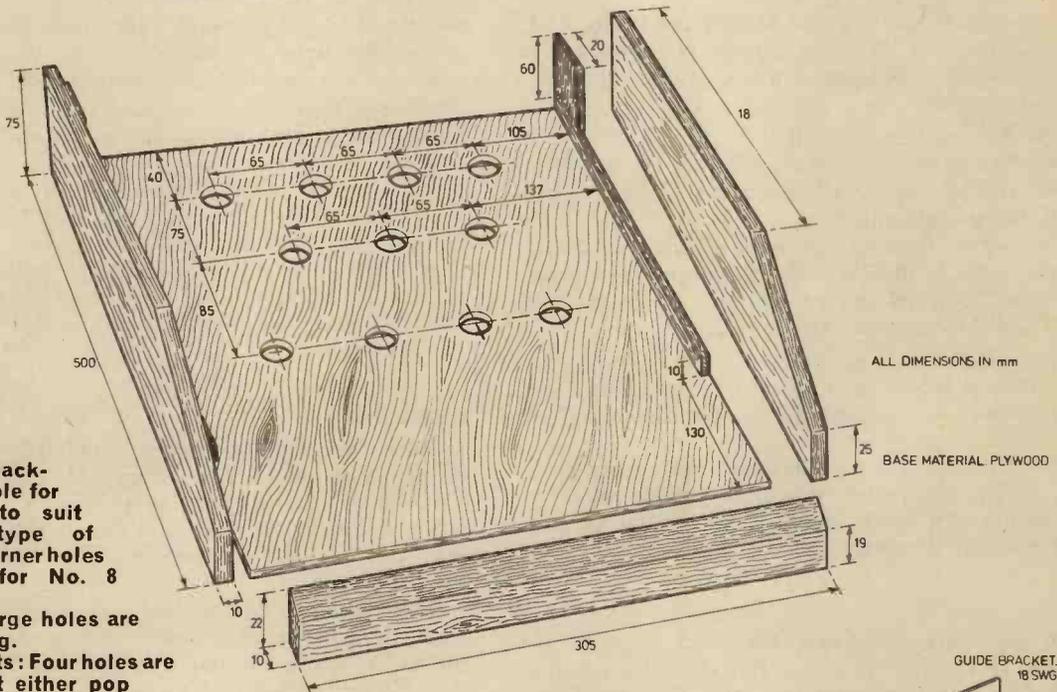

ALL DIMENSIONS IN mm

BASE MATERIAL PLYWOOD

**Fig. 4.6. Back-plate:** The hole for P1 is cut to suit whichever type of plug used. Corner holes are drilled for No. 8 woodscrews.  
**Base:** The large holes are for air cooling.  
**Guide brackets:** Four holes are drilled to suit either pop rivets or screws

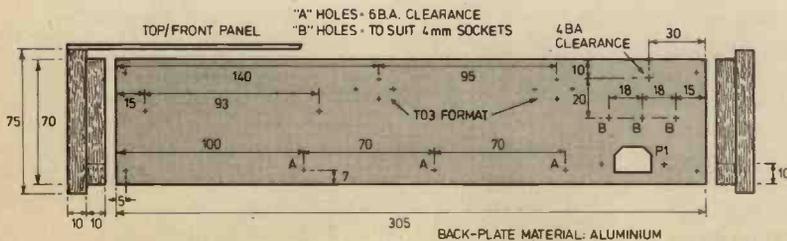


"A" HOLES - 6BA CLEARANCE

"B" HOLES - TO SUIT 4mm SOCKETS

4BA CLEARANCE

30

BACK-PLATE MATERIAL: ALUMINIUM

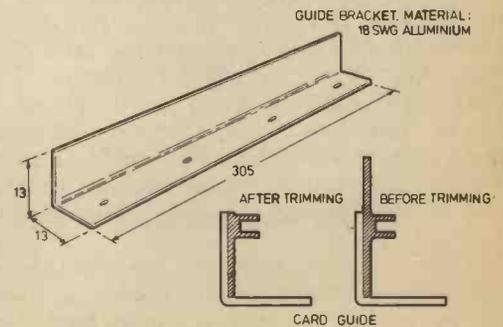

GUIDE BRACKET MATERIAL: 18 SWG ALUMINIUM

AFTER TRIMMING

BEFORE TRIMMING

CARD GUIDE

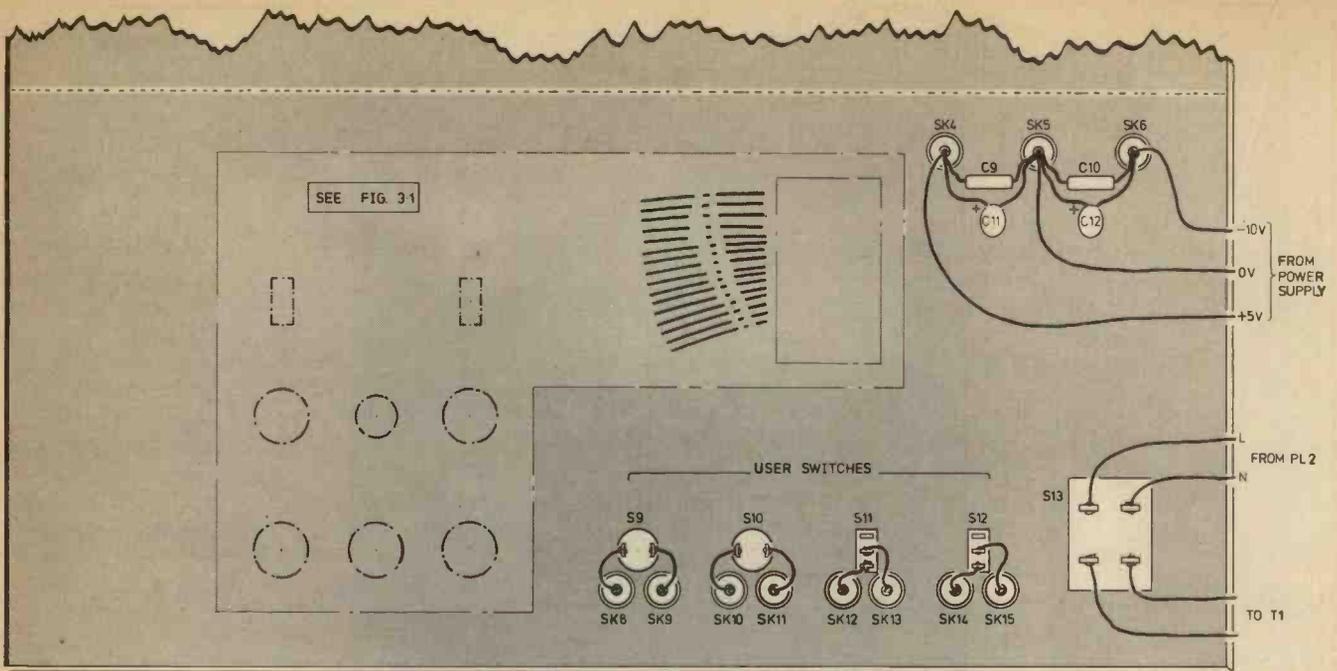


Fig. 4.7. Rear view of front panel wiring. A 16-way connector (d.i.l. socket in the prototype) enables all leads from the CHAMP board to be disconnected at once. Details given match Doram type pushbutton switches

necessary component locating and fixing holes drilled and deburred. The bend in the cover can be produced fairly easily, even without a bending machine, if the following procedure is followed:

- (i) Mark the bend line in pencil.
- (ii) Clamp the panel to a workbench with the aid of a stout straight edge, with the pencil mark aligned with the straight edge.
- (iii) With another stout straight edge press evenly down on the panel, bending it only a few degrees at a time.
- (iv) Remove the panel often and check it against the plinth until the desired angle is obtained.

The cover should now be screwed to the plinth and the edges trimmed before the L shaped brackets and card guides are bolted (or pop-riveted) into position (see Fig. 4.6).

It is a good idea to use the CHAMP main board as a jig while finally positioning the card guides prior to fixing, to ensure that the board is not too loose or too tight when assembly is complete.

#### FINISH

A lot of care was taken over the finish imparted to the CHAMP prototype, and we feel that the results achieved, justify the small amount of extra effort involved. When the "fit" of the plinth components is satisfactory, the cover should be removed and the plywood base given two or three coats of aerosol primer. Allow the primer to dry and sand down to a fine surface between coats. A top coat of a suitable colour can then be applied; in the case of the prototype, a metallic cellulose paint was used, with attractive results.

The cover should be rubbed down all over with wet and dry paper or fine Emery to provide a good "key" for the primer which is applied, and as before, apply two or three coats. A contrasting metallic finish was chosen as

the top coat, and several light coats should be applied until a good finish is achieved.

Before the outlines and lettering are applied to the cover, the paint should be allowed at least two days to harden off to prevent damage to the finish. The outlines are first pencilled in with the aid of a soft pencil, then inked over with either drawing ink or a spirit based felt tipped pen. (Do not use a water based ink, or the lines will run when varnish is applied.)

All necessary lettering is applied with Letraset, or a similar dry transfer technique, before the application of a coat of clear polyurethane varnish to give a durable protective finish.


#### ASSEMBLY

When the plinth is complete, the front panel components can be fitted and wired up as in Fig. 4.7. The use of a 16-pin d.i.l. socket as a termination adds to the modularity of the design, but is not strictly necessary. Terminal pins and soldered connections could be used instead if desired.

The ribbon cable, or loom, from the front panel is taken through the large hole in the cover to appear under the main board, so that it can be unobtrusively mated with the appropriate d.i.l. socket.

The power supply module should be thoroughly tested in isolation before the main board is plugged in, and it is wise to do comprehensive voltage checks on the main board before any chips are plugged in. It will not be possible to get CHAMP to run properly at this stage because the keyboard has not been described, and the CHAMP firmware will not be available, but if desired, the clock chip can be plugged in and the clock and reset waveforms checked with an oscilloscope, as can the SYNC pulses emanating from the 4040 CPU chip.

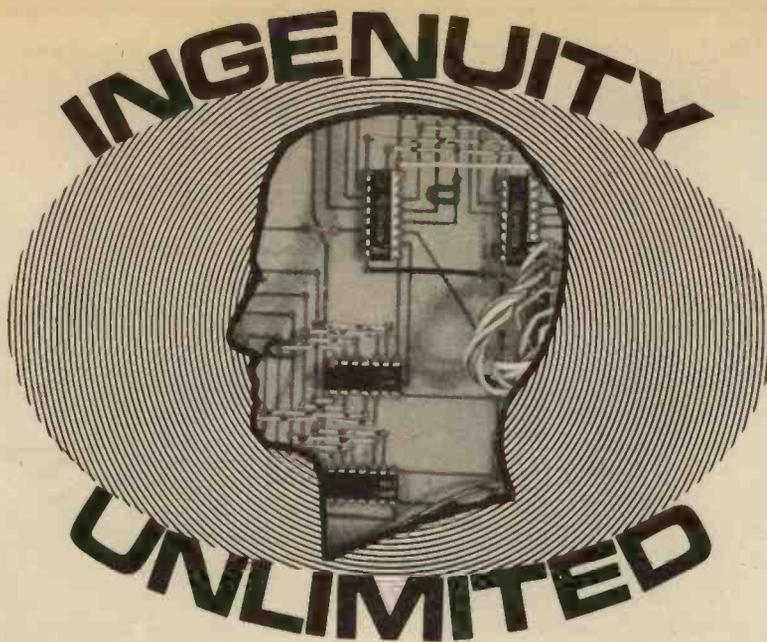**NEXT MONTH: Keyboard design and construction**



A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

## CAR LIGHTS ALARM

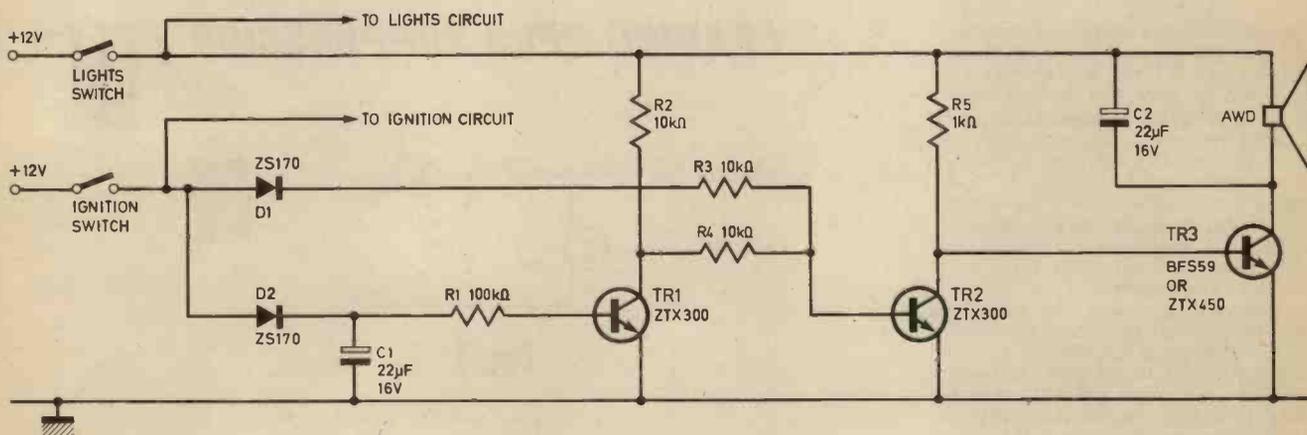


Fig. 1

THE alarm circuit shown in Fig. 1 can save the embarrassment of a flat battery due to forgetting to turn off the side lights. The alarm will sound for about five seconds after the ignition is switched off, so if the lights are needed for parking the alarm is eventually silent. This circuit is designed for negative earth cars. For positive earth vehicles, p.n.p. transistors would have to be used, and the capacitors and ZS170 diodes reversed.

The circuit can be built on a piece of stripboard. It is then connected to the car earth, and to the lighting and ignition switches as indicated in Fig. 1.

If the RS Components type audio alarm is used, which has an average current of 60mA and peaks of 1A, then a high current transistor should be used for TR3.

When both lights and ignition are on, TR2 is on, which holds TR3 off. Also TR1 is on because C1 is charged

up. When the ignition is turned off, TR2 turns off, and is temporarily kept off by TR1 being on for five seconds by the charge on C1. When this charge decays, TR1 goes off and TR2 switches back on, thus inhibiting the alarm.

The circuit works very well, and gives a short sharp reminder to turn off the lights.


A. J. Buxton,  
Stockport,  
Cheshire.

**T**HE circuit in Fig. 1 was intended as a rear light bulb failure indicator for cars, but could be used for any light source monitoring. Numerous designs for this purpose have appeared over the years, but this is probably the simplest method possible (and should therefore be the most reliable!), having only three components.

The l.d.r. (R2) is mounted in a convenient position within the lamp housing, with the active face directed towards the filament. When the bulb is illuminated, R2 has a low resistance thereby short circuiting the l.e.d. which consequently remains off. If, however, the bulb blows, the resistance of the l.d.r. rises causing the voltage across D1 to increase sufficiently for it to light up.

The circuit as shown, is for a 12V negative earth system. For positive earth vehicles, reverse the l.e.d., and for 6V systems reduce R1 to 470Ω. In any case, the warning circuit should be wired on the correct side

## LAMP FAILURE INDICATOR

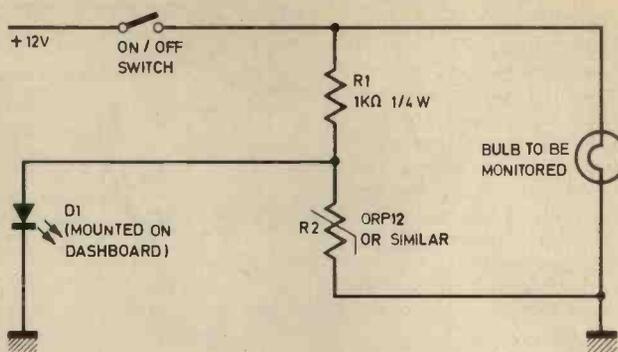

**Fig. 1**

of the on/off switch to ensure that no current consumption takes place while the lights are turned off.

If there is insufficient room within the lamp housing for the l.d.r., a

small hole can be drilled through the reflector, angled towards the filament, and the l.d.r. mounted behind it.

G. H. Lucas,  
Leicester.

**A**LTHOUGH this circuit was designed for the six digit common anode display of a CT7001 digital clock i.e. it could be modified for use with other types of seven segment display.

Zero blanking in the tens-of-hours digit is normally achieved by using the circuit shown in Fig. 1. The count here is either 1 or 2, depending upon whether a 12 or 24 hour display is used. At segment *f* it is possible to detect the presence of a zero, and suppress the display.


However, to blank the zeros in tens-of-minutes and tens-of-seconds where the count climbs to 5, two segments have to be used, and segments *c* and *e* are selected, as it is only in a zero format that both of these segments are active at the same time.

In Fig. 2, a 7432 OR gate is used to detect a zero. The output of the gate connected to the digit driver will only be low when the inputs connected to segments *c* and *e* are both low. As this only happens when a zero is present, all other figures from 1 to 5 will be displayed, while a zero which requires both segments, will be inhibited.


Only one gate is required, as the output is fed via diodes to the tens-of-minutes and tens-of-seconds digit drivers.

G. Ballantyne,  
Clydebank,  
Dunbartonshire.

## LEADING ZERO SUPPRESSION

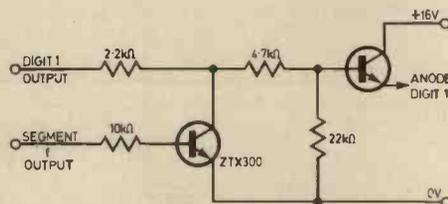

**Fig. 1**

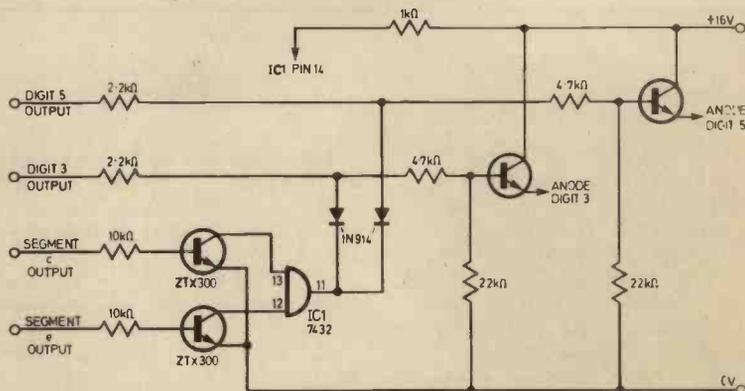

**Fig. 2.**



## POLARITY PROTECTOR

THE home experimenter can all too easily destroy expensive components at the anxious moment of trying out a circuit, by hastily applying reversed polarity to the supply input.

Time and money can be saved by simply fitting a bridge rectifier to the circuit, as shown in Fig. 1. Polarity of the applied power is now unimportant. The sacrifice made for the benefit of this precaution is that a volt or more will be lost across the rectifying diodes, but more often than not, this voltage loss will be inconsequential.

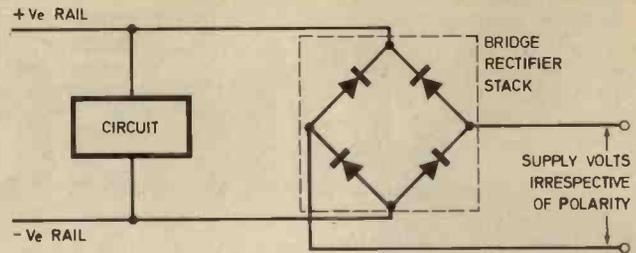


Fig. 1

This idea is particularly suitable for car radios and cassette players, where the vehicle may have a positive

or negative earth electrical system.

P. M. Freeman,  
Nottingham.

## LOGIC PROBE

HAVING seen many different types of TTL logic probes advertised in magazines varying in price from £5-£25, I was prompted to design this circuit which has many of the features of a probe in the £9-£12 range, yet it only costs about £1 to build.

The circuit (Fig. 1) was built onto an old "fat" ball point pen tube, which had flying leads for +5V and 0V connections.

When A is at 0 the output of IC1a is at 1, so i.e.d. D3 is on, indicating the "low" state.

When A is at 1, because of the inverter, IC1 pin 5 is at 0, so the

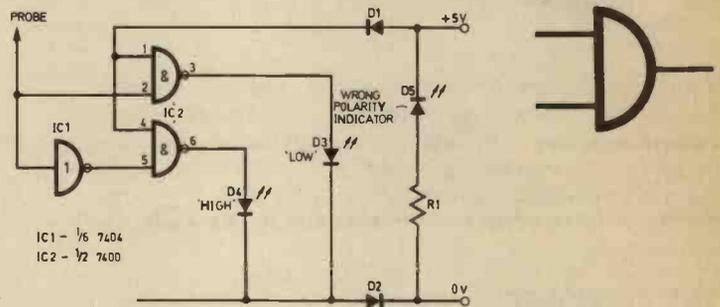


Fig. 1

output of IC1b is at 1 and D4 is on, indicating a "high" state.

D1 and D2 are included to protect the circuit against wrong polarity

R1 is chosen to give correct operating current for D5.

J. Scott Patterson,  
East Lothian.

THIS circuit was built to replace an expensive meter in a radio control transmitter.

The NiCad battery used is nominally 12 volts, with a maximum of nearly 14V when fully charged. When discharged, the cell voltage should not fall below 1 volt; that is, 10 volts for the battery.

The circuit of Fig. 1 is a Schmitt trigger operating an i.e.d. indicator. The reference voltage is provided by the 5.6V Zener diode, and hysteresis is set by the ratio of R4 and R5 to about 1 volt. The trip voltage is set by the ratio of the potential divider resistors, R2 and R3. For accurate setting, R3 could be replaced by a variable resistor. When the battery falls to 10 volts the output of IC1 goes low and turns off the i.e.d., which remains off until the battery rises to at least 12 volts again. The total cost is very much less than the cheapest meter.

A. Langton,  
Aberdeen.

## BATTERY CONDITION INDICATOR


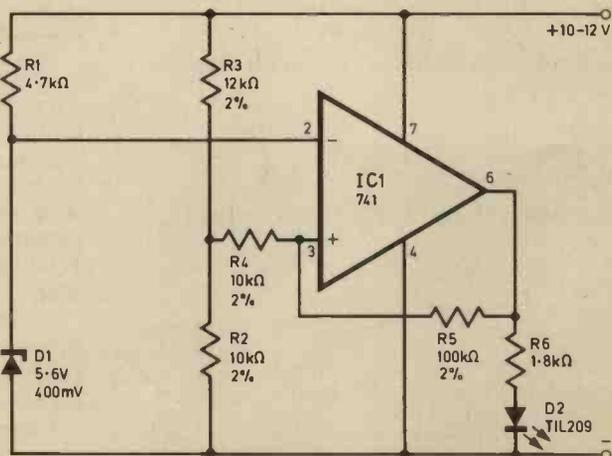


Fig. 1

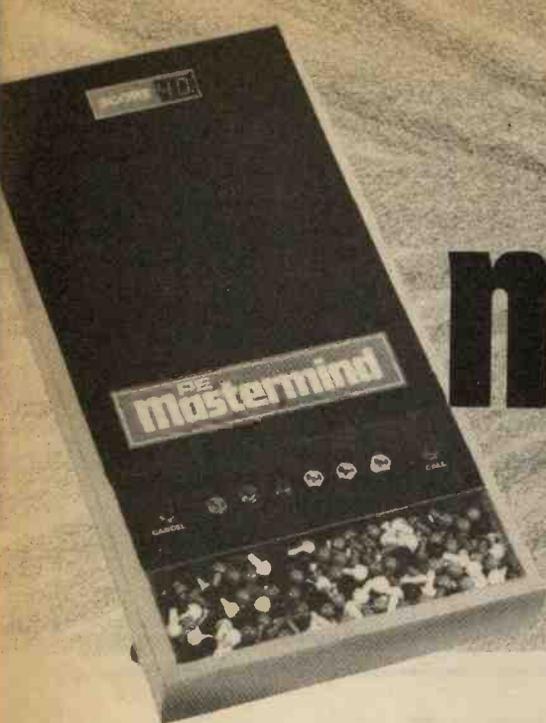

# PE Mastermind\*

P. F. TURNEY

## Part Five

LAST month it was seen how the position indicator signal handled the situation of repeated internal colours with both "P" and "I" correct entries. The final section of the scoring logic, dealing with the cases where there are repeated internal colours with only "I" correct entries, is to be considered this month, together with the display logic.

### THE RESET LOGIC

The existence of this logic was mentioned last month and rather than to now undertake a full operational description the approach will be to illustrate its action with a series of actual examples.

The basic function of this logic is highlighted by the example shown in Fig. 5.1. Below is shown a sequence of events executed by the machine in response to the colours of this example.

(1) Enter First Red	$K = 1$
$C_1\bar{C}$ $E = 0$	$I_1, S_1, P_1 = 0$
$C_2\bar{C}$ $E = 1$	$I_2, S_2 = 1$
$C_3\bar{C}$ $E = 1$	$I_3, S_3 = 1$
$C_4\bar{C}$ $E = 1$	$I_4, S_4 = 1$

(2)-(4) no further change of status (except for clearing of "S"s).

Fig. 5.1. Example showing the need for the reset logic

		X CODE			
		B	R	R	R
ENTRIES	R	0	1	1	1
	W	0	0	0	0
	W	0	0	0	0
	W	0	0	0	0

Table 5.1  
TRUTH TABLE FOR THE RESET LOGIC


Slave Status				Reset functions				A Flip Flop I/P's			
$S_1$	$S_2$	$S_3$	$S_4$	$R_1$	$R_2$	$R_3$	$R_4$	$J_{A3}$	$J_{A4}$		
0	0	0	0	0	0	0	0	0	0		
0	0	0	1	0	0	0	0	0	0		
0	0	1	0	0	0	0	0	0	0		
0	0	1	1	0	0	0	1	0	1		
0	1	0	0	0	0	0	0	0	0		
0	1	0	1	0	0	0	1	0	K		
0	1	1	0	0	0	1	0	K	0		
0	1	1	1	0	0	1	1	1	0		
1	0	0	0	0	0	0	0	0	0		
1	0	0	1	0	0	0	1	0	0		
1	0	1	0	0	0	1	0	0	0		
1	0	1	1	0	0	1	1	0	0		
1	1	0	0	0	1	0	0	0	0		
1	1	0	1	0	1	0	1	0	0		
1	1	1	0	0	1	1	0	0	0		
1	1	1	1	Don't care condition							

It is seen that  $I_2, I_3$  and  $I_4$  are all set, giving an incorrect score of three white key pegs. It is the function of the reset logic to reset two of these flip flops and produce the correct score of one white key peg. By convention  $I_3$  and  $I_4$  are reset with  $I_2$  retained. The truth table for this and all other examples of reset logic operation is shown in Table 5.1. The final two columns of this table will be discussed a little later.

In the example just considered "S" flip flops  $S_2, S_3$  and  $S_4$  were all set by a single entry, corresponding to a slave status of 0111 in the truth table, which shows that  $I_3$  and  $I_4$  are to be reset to logical zero ( $R_3 = R_4 = 1$ ).

These resets are enabled by clock pulse  $C_5\bar{C}$  from the comparison counter, and there are two reasons why this must be so. Firstly, by the time  $C_5\bar{C}$  appears all flip flops will have been clocked and given time to set, and secondly,

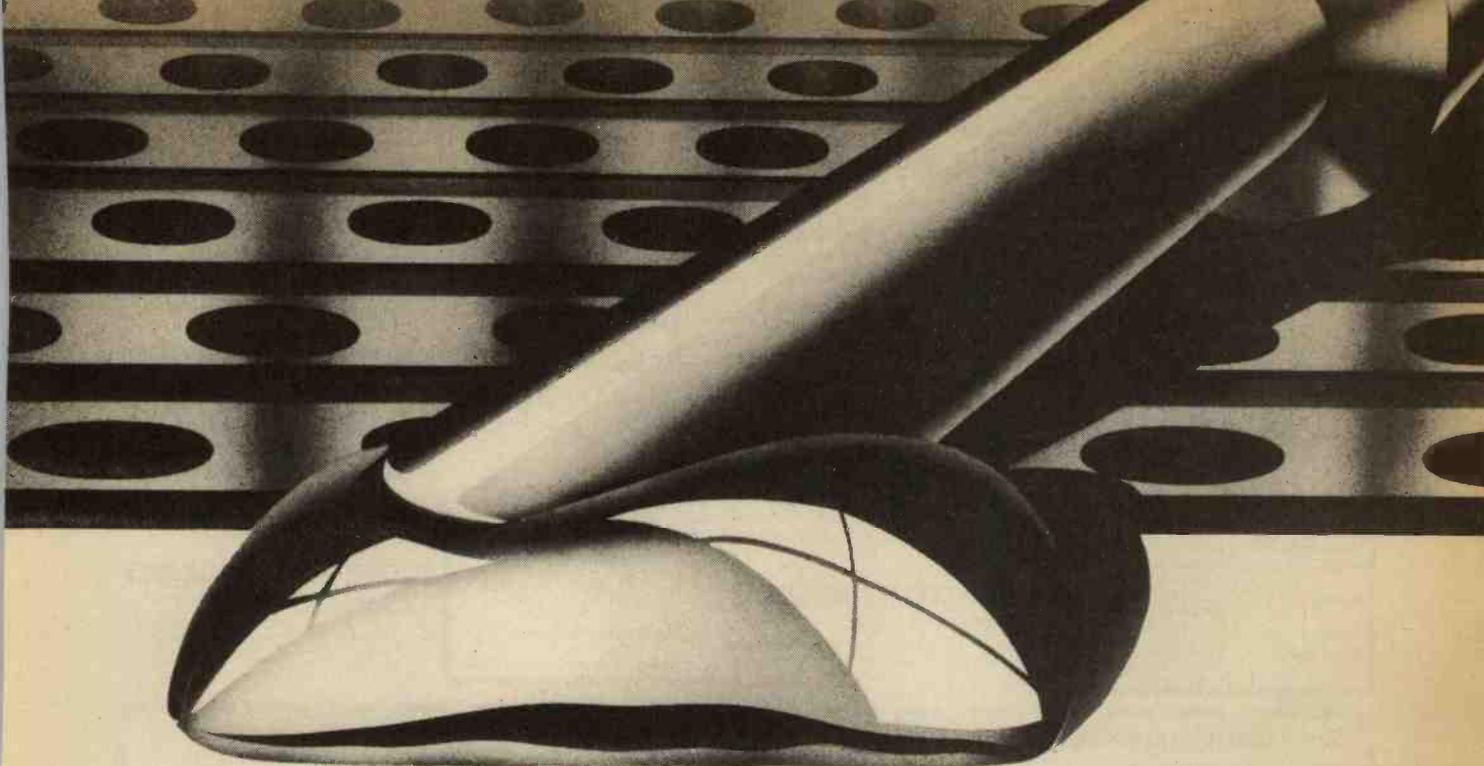\* Mastermind is the registered trade mark of Invicta Plastics Ltd



# The Blob Story.

Yes, they have got a funny name:  
Blob Boards.

And if you've never heard of them,  
you might wonder what on earth they're for.

After all they sound more like sci fi  
than practical electronics.

But in fact there is a good reason for  
the name.

It actually describes the way these  
printed circuit boards work. You just put a tiny  
blob of solder onto circuit board and  
component and you've made a perfect  
contact.

Every time.

There are of course a few other  
printed circuit boards around.

But we think the prices are a bit shocking.

Our prices, we think you'll agree, are  
more down to earth.

These Blob Boards are about half the  
price of the few comparable alternatives.

And unlike those alternatives, on most  
Bandridge Blob Boards you won't have to  
break the contact rails to make your circuit.  
So you'll be able to use them again and again.

The roller tinned copper on Blob Board  
makes soldering easy, and it won't corrode, so


they'll work for as long as you want them to.

You'll find a Bandridge Blob Board for  
every circuit you'll ever want to make, from  
the simplest to the most complex.

And if you're using Bandridge  
solderless DEC's for your prototypes you'll be  
pleased to learn that there's a Blob Board that  
exactly matches every DEC.

So when you're looking for a circuit  
board it'll be worth your while remembering  
Blob Boards.

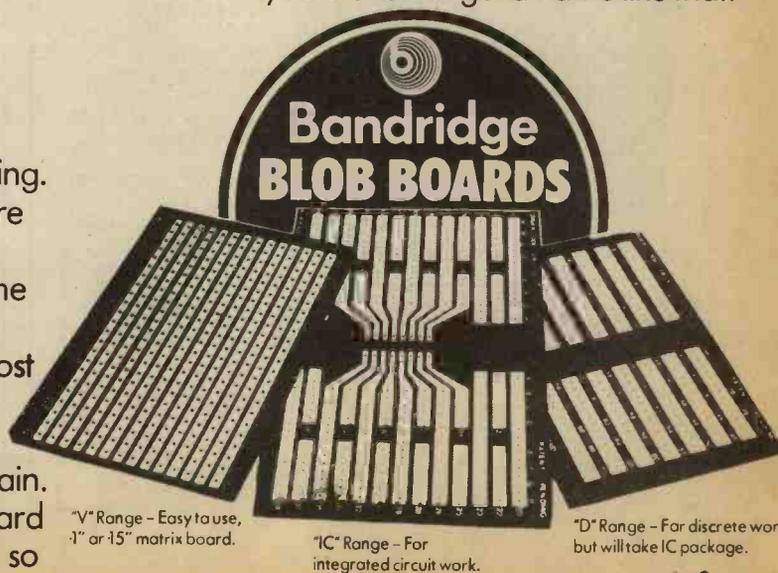As if you'd ever forget a name like that.



"V" Range - Easy to use,  
1" or 1.5" matrix board.

"IC" Range - For  
integrated circuit work.

"D" Range - For discrete work  
but will take IC package.

Are you receiving us? NEW Doram

# DIGITAL FREQUENCY METER YOURS FOR ONLY £54.50+ £4.36 VAT



The DFM you must have at a price that could save you up to £25. It's easy to see how accurate this new Doram meter is thanks to 4 digit display with extra shift left to check 5 digits for even greater accuracy!

You can see the well-designed shatterproof case with its built-in handle/display tilt-foot looks so much more expensive than many a kit product.

But Doram kits always give you the best for less. This complete kit with case, printed circuit boards, all components and instructions is yours for only £54.50 + £4.36 VAT.

The meter covers 20Hz to 50MHz with prescaler (additional purchase) provision allowing you to measure up to 500MHz. Input impedance and sensitivity are very high with read-out accurate to ± 0.01%!

So the message comes through loud and clear—don't miss this latest Doram digital bargain.

## DEPEND ON DORAM

Thousands of kit makers do for top value and modern technology.

Doram Electronics Ltd, PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds, West Yorkshire LS12 2UF.  
Registered in London No. 1155856. Directors: R. A. Marier, D. I. Turner, F. Chabie.

### KEY DATA

Frequency range	20Hz to 50MHz in 3 steps
Sensitivity	20mV r.m.s
Input Impedance	1M $\Omega$ in parallel with 30pF
Input Coupling	AC
Maximum Input	10V r.m.s.
Frequency Standard	1MHz, 0.01% calibration tolerance
Display	4 Digit LED display with shift left for 5 digit readout
Accuracy	± 1 digit (0.1%)
Supply Voltage	220-240V ac with 12V dc 100mA output for prescaler supply

Big saving, good looking, fast checking NEW Doram

# DIGITAL MULTIMETER— BUILD IT YOURSELF AND SAVE UP TO £40!



A clear, functional multimeter, featuring extremely accurate digital display, in superbly styled shatterproof carry-case. It could cost £100! But the complete Doram kit with case, printed circuit board, leads and all components is yours for just £54.50 plus £4.36 VAT.

Based on Ferranti technology with accuracy  $\pm 0.6\%$ , the new Doram Multimeter is an indispensable tool at a terrific saving. Measurement is indicated by a 3 $\frac{1}{2}$  digit display updated twice per second—display flashes to indicate overload.

### KEY DATA

Volts DC	200mV, 2V, 20V, 200V, 1000V. Input impedance 4.2M $\Omega$ . Maximum sensitivity 100 $\mu$ V.
Volts AC	200mV, 2V, 20V, 200V, 500V. Input impedance 4.2M $\Omega$ . Maximum sensitivity 100 $\mu$ V.
Current AC/DC	200 $\mu$ A, 2mA, 20mA, 200mA, 2A.
Resistance	200 $\Omega$ , 2K $\Omega$ , 20K $\Omega$ , 200K $\Omega$ , 2M $\Omega$ .

And it saves you money before it's even built!

## DEPEND ON DORAM

Thousands of kit makers do for top value and modern technology.

Doram Electronics Ltd, PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds, West Yorkshire LS12 2UF.  
Registered in London No. 1155856. Directors: R. A. Marier, D. I. Turner, F. Chabie.

### Yes, I want to save up to £25

Please send me (subject to availability) ... complete kit(s) for DORAM DIGITAL FREQUENCY METER at (£54.50 + £4.36 VAT inc p & p) total £58.86. I understand I can return unused kit(s) within 7 days and claim my money back if kit(s) returned in the form received and ready for re-sale.

Please send me ... complete DORAM KITS CATALOGUE(s) showing an additional 25 kits at 25p each. I enclose cheque/PO value.

NAME (BLOCK CAPITALS)

ADDRESS

TOWN

COUNTY

POST TO: DORAM ELECTRONICS LTD, DEPT P&M 1 PO BOX TR8, LEEDS WEST YORKSHIRE LS12 2UF

### Yes, I want to save up to £40

Please send me (subject to availability) ... complete kit(s) for DORAM DIGITAL MULTIMETER at (£54.50 + £4.36 VAT incl. p & p) total £58.86. I understand I can return the unused kit(s) within 7 days and claim my money back if kit(s) returned undamaged in the form received and ready for re-sale.

Please send me..... complete DORAM KITS CATALOGUE(s) showing an additional 25 kits, at 25p each.

I enclose cheque/PO value

NAME (BLOCK CAPITALS)


ADDRESS

TOWN

COUNTY

POST TO: DORAM ELECTRONICS LTD, DEPT P&F 1 PO BOX TR8, LEEDS WEST YORKSHIRE LS12 2UF

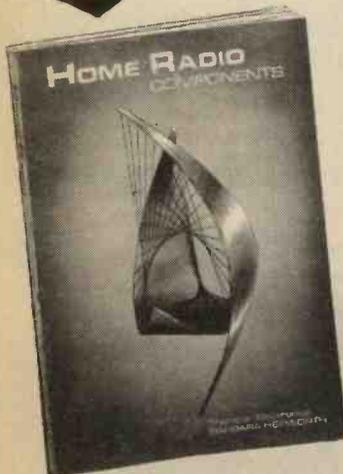**THIS is the Catalogue you need to solve your component buying problems!**



- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., 234-240 London Road, Mitcham, Surrey CR4 3HD

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD Dept PE  
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No 917986 London

## ORCHARD ELECTRONICS ! SERVICE SECOND TO NONE - TRY US AND SEE ! SUPPLIERS TO U.K.A.E.A. D.O.E. UNIVERSITIES. ETC.

ARE YOU GETTING THE BEST SERVICE?

TRANSISTORS + 200 OTHER TYPES IN STOCK	ORP12	85p	C/MDS	BARCLAYCARD
AC128 20p BC147A 9p* BC 262A 19p	47p	4000	0.19	<p>TRANS-FORMERS 6-0-6-100mA 1.20 9-0-9-75mA 1.20 9-0-9-4A 3.20 12-0-12-50mA 1.30 12-0-12-1A 2.75 min Q/P for OC712 use 0.25 8-0-6-280mA 2.40 12-0-12 150mA 2.40 MOT 700 0P P-1K2 8.00 200 MW 0-50</p> <p>OFFER RED LED's 125 10 for £1 RED LED's 2 100 for £1 BC 108C 11 for £1 2N 3702 100 for £9 3704 100 for £9</p> <p>SK 1122 TV 0.30 Game Kit Colour Sound Incl Semi Cond. Caps. Res. XTAL PCB, Data £21</p> <p>ZENERS (400mw) B2X 83 3V, 3V3, 5V1, 5V6, 7V5, 9V1, 10V, 12V, 18V, 22V, 30V, All at 12p* each.</p> <p>S.A.E. for free Stock List. Orders out by 4.00pm every day. £5.00 V.A.R.I.C.A.P. TUNER</p>
176 22p 147B 10p* 287 28p 31A 87p	30A	56p*	4001 0.19	
AD161 52p 148 9p* 300 35p 41A 87p	42A	80p	4002 0.19	
162 52p 148B 10p* 301 34p	42A	80p	4006 1.45	
MCH/PR 149B 11p* 303 35p	TIS43	35p	4007 0.19	
AF117 28p 154 18p* 557 15p*	ZTC30	13p*	4011 0.19	
BC107 11p 157B 12p* BCY71 18p	502	13p*	4012 0.19	
107A 12p 177 17p 72 14p	502	13p*	4013 0.58	
108 10p 178B 18p BFY50 25p	1N914	5p	4014 1.42	
CIL108 8p 179B 19p 51 25p	1N4001	5p	4015 1.16	
8C108B 11p 184B 12p* 52 25p	4002	6p	4016 0.52	
108C 12p 184L 11p* MPF102 40p*	4005	9p	4017 1.12	
109 12p 187 26p OA47 14p	4006	10p	4023 0.19	
109B 13p 212A 13p* 90 7p	4148	5p	4024 0.75	
109C 13p 212L 15p* 91 8p	2N2219	30p	4029 1.95	
117 18p* 213B 12p 200 10p	2646	66p	4050 0.54	
142 24p 214 15p* OC44 45p	29260	13p*	4511 1.94	
143 24p 214L 17p* 72 35p	2926G	15p*		
THYRISTORS 60V 1A 9.28	7400	0.15	400V 1A 0.28	
100V 1A 0.38 TAG 1 100	7401	0.20	400V 2 1/2A 0.65	
200V 1A 0.60 TAG 1 200	7402	0.18	7428 0.50	
600V 1A 0.80 TAG 1 600	7403	0.18	7430 0.18	
700V 1A 1.40 BT 106	7404	0.23	7432 0.28	
400V 4A 0.85 C108D1	7407	0.40	7437 0.42	
500V 8 1/2A 1.85 BT 108	7408	0.24	7440 0.18	
	7410	0.18	7442 1.00	
	7411	0.24	7443 1.00	
	7412	0.25	7446 1.00	
	7413	0.27	7447 0.98	
	7414	0.72	7448 1.00	
	7416	0.36	7451 0.18	
	7417	0.36	7460 0.18	
	7420	0.18	7470 0.32	
	7421	0.32	7472 0.30	
	7427	1.90*	7473 0.35	
	TBA530Q	1.90*	7474 0.48	
	NE568	2.70	7475 0.32	
	NE567	2.80	7476 0.32	
	SN76003N	1.80	7480 0.65	
	SN76013ND	1.78	7481 1.00	
	SN76023N	1.78		
	SN76023ND	1.60		
	SN76033N	2.75		
	SN76660	0.90		
	TAA550	0.60		
	TBA120ASQ	1.30		
	TBA480Q	1.25		
	TBA520Q	1.70*		
	TTL DIGITAL			
	LED Tri 209/0.125"	0.2"		
	Red	20p		
	Green	29p		
	Clips for above	3p		
	RESISTORS			
	1/4 WATT 5%	2p* each		
	10 of 1 value	15p*		
	20 mixed values	30p*		
	POTENTIOMETERS			
	Lin/Lin			
	5K 10K 25K 50K 100K 250K			
	500K 1M 2M 25p* each.			

POST THIS COUPON with cheque or P.O. for £1.40

had a "P" correct entry been made the PI signal would have gated clears to any "I" and "S" flip flops also set by the entry, prior to the appearance of  $C_5\bar{C}$ . If more than one "S" flip flop has remained set by the time  $C_5\bar{C}$  appears, it is known that only "I" correct entries have been made and the reset logic can therefore be enabled.

The slave status 1111 can never occur, since in this situation one entry would be "P" correct (1111 means that the entry is correct for colour with all internal colours and so must be correct for position with one of them), and all slaves would be cleared prior to  $C_5\bar{C}$ .

IC48 and 49, shown in Fig. 5.2, are used to implement these reset functions.

### THE "A" FLIP FLOPS

The example of Fig. 5.3 will be used to demonstrate the requirement for two more flip flops. The sequence of events is summarised below.

- (1) Enter Red      K high  
 $C_2\bar{C} - C_4\bar{C}$        $I_2, S_2; I_3, S_3$  and  $I_4, S_4$  set  
 $C_5\bar{C}$                $I_3$  and  $I_4$  reset by reset logic
- (2) Enter Red      L high  
 $C_0$                 Slaves cleared  
 $C_2\bar{C}$                $P_2$  sets -  $I_2, S_2$  therefore cleared and inhibited via gate 2 of reset level 1. PI goes high  
 $C_3\bar{C} - C_4\bar{C}$        $S_3, I_3$  and  $S_4, I_4$  set and promptly cleared by PI  
 $C_5\bar{C}$               No action (no slaves remaining set)
- (3)-(4) No change

Only  $P_2$  remains set and an incorrect score would be indicated. What has happened is that  $P_2$  in (2) clears  $I_2$  which was retained in (1) by the reset logic, reducing the score by one white key peg. Had the reset logic been organised to clear  $I_2$  and  $I_3$  and retain  $I_4$  instead there would still be input combinations that would be wrongly scored.

The solution to this dilemma is to use conditional deletions or clears, and the "A" flip flops are used to indicate whether or not a clear is conditional. No detailed description of these flip flops is to be given and their operation is illustrated by way of example, see Fig. 5.3 and the sequence of events below.

- (1) Enter Red      K high  
 $C_2\bar{C} - C_4\bar{C}$        $S_2, I_2; I_3, S_3$  and  $S_4, I_4$  set  
 $C_5\bar{C}$                $I_3$  and  $I_4$  reset by reset logic.  $A_3$  set to indicate that  $I_3$  was conditionally reset
- (2) Enter Red      L high  
 $C_0$                 Slaves cleared  
 $C_2\bar{C}$                $P_2$  sets and clears and inhibits  $I_2$  and  $S_2$ . PI high  
 $C_3\bar{C}$                $S_3, I_3$  set. PI line is inhibited from clearing  $S_3$  and  $I_3$  by  $\bar{A}_3 = 0$  at input to gate 3 of reset level 2 (see Fig 4.1)  
 $C_4\bar{C}$                $I_4, S_4$  set and promptly cleared by PI  
 $C_5\bar{C}$               No action (only  $S_3$  set)
- (3)-(4) No change

The score is now the correct score of one black and one white key peg. Flip flop  $A_4$  serves for  $I_4$  in a similar fashion, no example is to be given for this case.

The set conditions for the "A" flip flops are shown in the last two columns of Table 5.1. The entries of K (from

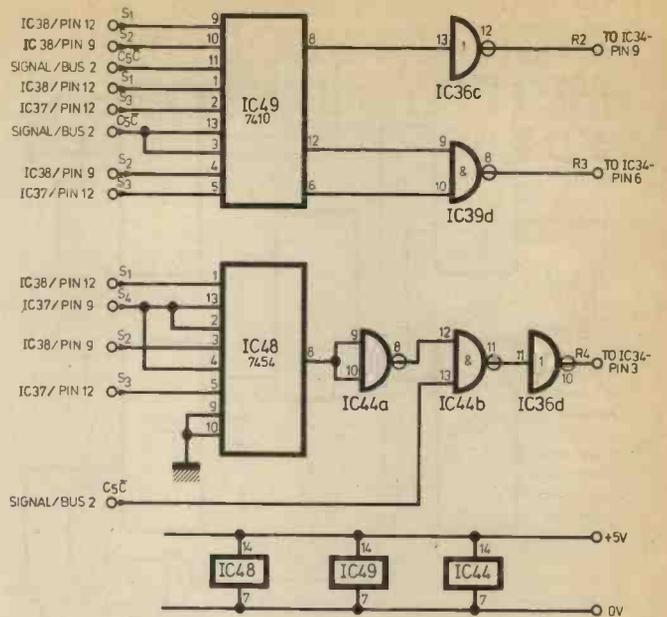


Fig. 5.2. The reset logic circuitry

the entry counter) in these columns indicate that only if the corresponding slave status arises in response to a first entry is a conditional reset necessary. Note that the status 0101, for example, can arise only if an entry is made in position 1 or in position 3 (otherwise it would be "P" correct), and only in position 1 is the retained "I" flip flop  $I_2$  subject to a possible reset by the occurrence of a "P" correct entry in position two.

### 0111 GATE


This is a two input NAND gate (IC39c) that acts to inhibit the PI line from resetting  $I_4$  when the 0111 status arises, which can only be in response to a first entry. A full discussion of its role is somewhat involved and is for this reason not included here.

Fig. 5.3. Example illustrating three reset modes of the scoring logic

		X CODE			
		B	R	R	R
ENTRIES	R	0	$I_B$	$I_A$	$I_A$
	R	0	P	$I_C$	$I_C$
	W	0	0	0	0
	W	0	0	0	0

The reset modes are as follows:—(a)  $I_A$ —cleared by "reset logic"; (b)  $I_B$ —cleared by  $P_2$  (clear and inhibit function); (c)  $I_C$ —cleared by PI enabling "Reset Level 2".

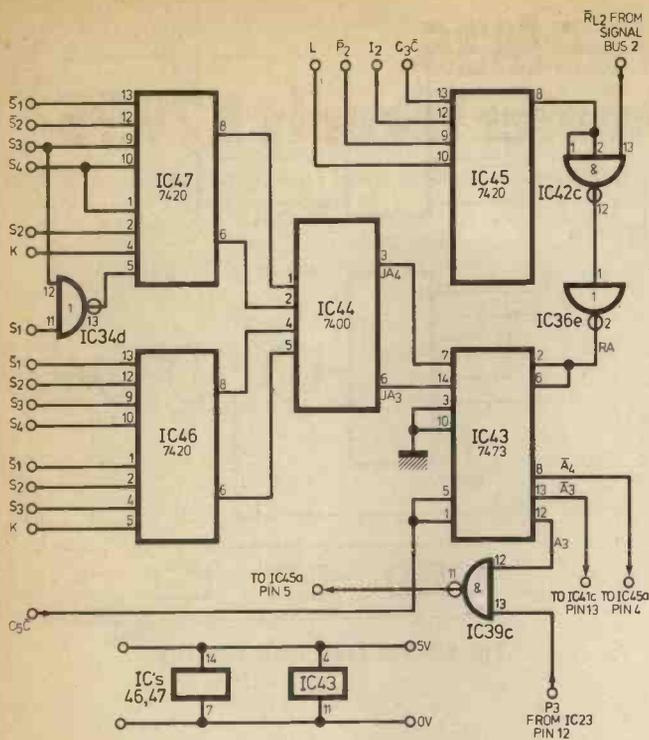As explained in the text, the score given here is incorrect, and so necessitating the use of the "A" flip flops.



$S_1$  from IC38/pin 12  
 $\bar{S}_1$  from IC38/pin 13  
 $S_2$  from IC38/pin 9  
 $\bar{S}_2$  from IC3/pin 8  
 $S_3$  from IC37/pin 12  
 $S_4$  from IC37/pin 9  
 $C_3\bar{C}$  from Signal Bus 2  
 K from Signal Bus 1

$L$  from Signal Bus 1  
 $\bar{P}_2$  from IC22/pin 8  
 $I_2$  from IC31/pin 9  
 $C_3\bar{C}$  from Signal Bus 2

**Fig. 5.4. The "A" flip flop and associated logic. Locations for i.c. pin outs are also listed**


### CLEARING THE "A" FLIP FLOPS

Both these flip flops are cleared by the reset signal  $R_{L2}$ , but  $A_3$  is additionally cleared via IC45. The reason for this is that unless  $A_3$  is cleared as soon as it has served its purpose it can in certain circumstances incorrectly inhibit the PI line from clearing  $I_3$ .

A type SN7473N dual JK flip flop is used for  $A_3$  and  $A_4$ , shown in Fig. 5.4 together with the set and reset logic, ICs 43; 44, 46 and 47; and 45b respectively.

### DISPLAY LOGIC

Conventional display logic is employed using two SN7447N seven segment decoder drivers coupled to a type DL727 dual seven segment i.e.d. display (see Fig. 5.5). This display must only be enabled when the final results are available from the scoring logic. For this reason signal N from IC20, the entry counter, is taken to the BI/RBO (Blanking input/Ripple blanking output) of both drivers, so that these are only enabled following the fourth entry made, and until such time as a subsequent deduction is commenced. Signal N is buffered by IC19 and 27 before being taken from board one to board two.

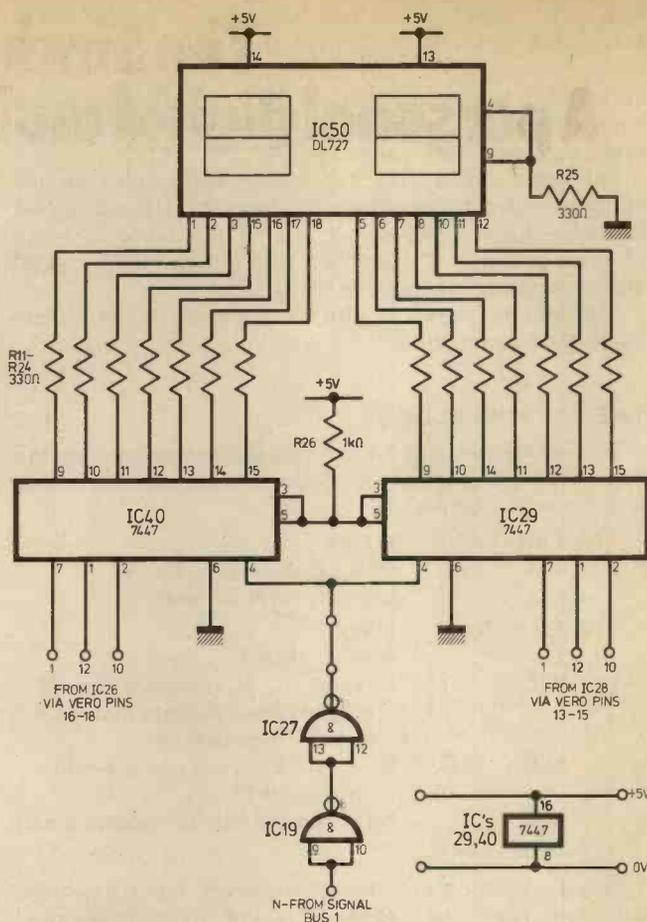

**Fig. 5.5. Circuitry for the display logic**

Strictly the BI/RBO should be used in conjunction with an open collector gate, but in this application the internal output is disabled by ensuring that the RBI never assumes the value of logical zero.

Limiter resistors are necessary between the decoder and the displays. Do not use values of resistance below approximately 180 ohms in an effort to achieve greater brightness from the displays. (A value of 330 ohms, as given in the list of components, was used for these resistors in the prototype).

### CONSTRUCTION

The remaining section of the scoring logic is wired on the main board (Board 1), with i.c. positions as shown in Fig. 5.6. As usual, all wiring is carried out using single cored wire on the top side of the board, reference being made to the circuit diagrams of Fig. 5.2 and 5.4 as appropriate.


Remember that an i.c. should be carefully positioned and orientated on the board before any of the copper tracks are broken and any connections made.

The display circuits are wired onto Board 2. The details of this board are given in Fig. 5.6. One important point to remember here is that the DL727 display is viewed through the cut-out on the peg board. It is therefore a very wise precaution to check that the final position of this display on Board 2 lines up exactly with this cut-out when the board is mounted in the casing. The display itself should be mounted using, for example, solder-con pins.

# The Sinclair PDM35.

## A personal digital multimeter for only £29.95

(+8% VAT)

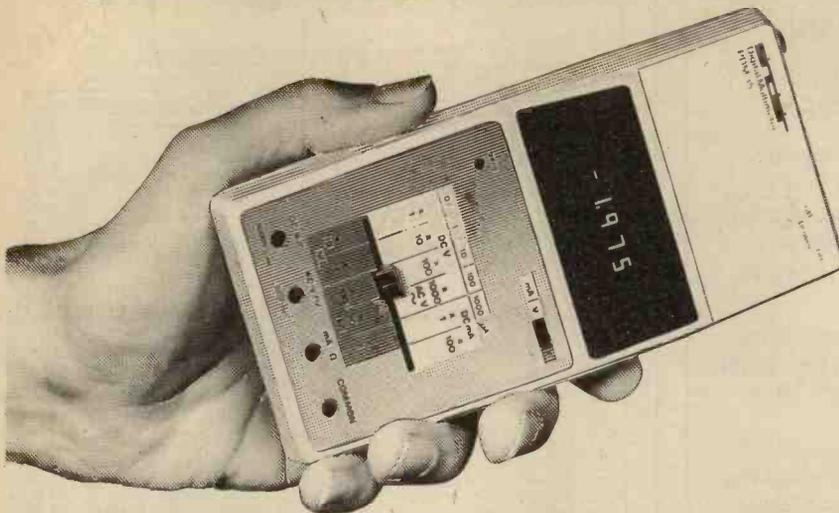

### Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

### What you get with a PDM35

3½ digit resolution.

Sharp, bright, easily read LED display, reading to ±1.999.

Automatic polarity selection.

Resolution of 1 mV and 0.1 nA (0.0001 µA).

Direct reading of semiconductor forward voltages at 5 different currents.  
Resistance measured up to 20 MΩ.  
1% of reading accuracy.

Operation from replaceable battery or AC adaptor.

Industry standard 10 MΩ input impedance.

### Compare it with an analogue meter!

The PDM 35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

### Technical specification

#### DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading 1.0% ± 1 count.

Note: 10 MΩ input impedance.

#### AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

#### DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

#### Resistance (5 ranges)

Range: 1 Ω to 20 MΩ.

Accuracy of reading: 1.5% ± 1 count.

Also provides 5 junction-test ranges.

**Dimensions:** 6 in x 3 in x 1½ in.

**Weight:** 6½ oz.

**Power supply:** 9 V battery or Sinclair AC adaptor.

**Sockets:** Standard 4 mm for resilient plugs.

**Options:** AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

### The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

### Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

We'll mail your PDM35 by return!  
Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdon, Cambs., PE17 4HJ,  
England. Regd No: 699483.

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs, PE17 4HJ.

Please send me \_\_\_\_\_ (qty) PDM35(s)

@ £33.00 (inc £2.40 VAT and 65p P&P)

each: \_\_\_\_\_ £ \_\_\_\_\_

\_\_\_\_\_ (qty) De-luxe padded

carrying case(s) @ £3.00 (inc VAT

and P&P) each: \_\_\_\_\_ £ \_\_\_\_\_

\_\_\_\_\_ (qty) AC adaptor(s) for

240 V 50 Hz power @ £3.00

(inc VAT and P&P) each: \_\_\_\_\_ £ \_\_\_\_\_

I enclose cheque/PO made payable

to Sinclair Radionics Ltd for

(indicate total amount): \_\_\_\_\_ £ \_\_\_\_\_

I understand that if I am not completely

satisfied with my PDM35, I may return it

within ten days for a full cash refund.

Name: \_\_\_\_\_

Address: \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

PE/12



# sinclair

World leaders in fingertip electronics



## SUPER TOUCH—SENSITIVE PIANO

**ALL THE CHARACTERISTICS OF A REAL PIANO HAVE BEEN POSSIBLE WITH ELECTRONICS**

- ★ Featuring:— Pianissimo and Fortissimo playing technique.
- ★ Natural speaking time – higher notes have shorter sound and the lower notes have longer sound.
- ★ Higher notes have slightly louder sound than the lower notes.
- ★ Perfect key up and key down effect of a real piano. When a key is depressed and held down the sound decays slowly, and when the key is released the sound decays rapidly.
- ★ Loud and Soft Pedal:— When the loud pedal is depressed and the note is played and released the sound decays slowly, but when the loud pedal is released the sound decays instantly.

ALL THIS MAKES OUR ELECTRONIC TOUCH-SENSITIVE PIANO THE FINEST IN THE WORLD. Complete kit price **£199.00** carr. £6, plus £25.62 VAT.



## MAYFAIR MK11 ELECTRONIC ORGAN

Specification: 11 voices, 4 pitches, sustain, split keyboard.  
Complete kit price **£175.00** carr. £6, plus 12½% VAT.

### THE ORGAN MANIACS WILL BE AROUND FOR 100 YEARS!

To enable us to keep our prices low our advertisement will not be appearing as regularly. We are the only London stockists for keyboards, pedal boards, consoles, key-contacts, stop switches, organ i.c.'s and all specialised components for electronic music.

**ORGAN AND PIANO KITS:** To maintain our success we will only sell professionally designed and 100% proven kits.

Our organs and pianos can be purchased from most music stores as we are now supplying to the trade. Sorry no catalogue at present, if you are keen visit our showroom, without obligation.



**ELECTRONIC MUSICAL INSTRUMENTS**  
12 Brett Road, Hackney, London E8 1JP  
Tel: 01-986 8455/5063

Component Shop,  
40a Dalston Lane, E8 2AZ Tel: 01-249 5624


## G8CZW Digital Frequency Meter



Complete 50MHz kit **£54.00** inc. VAT, post free (U.K.)

ZN1040E Count/Display I.C.	8.10	Hardware and Wire Pack	1.45
Integrated Circuit Pack	9.25	Case, Two-tone p.v.c. faced steel, punched and lettered (+95p P. & P.)	5.75
Displays and Filter Pack	7.78	Min BNC Sockets (50 ohm)	0.65
Semiconductor and Diode Pack	2.47	Min BNC Plugs (50 ohm)	0.70
Resistor and Capacitor Pack	3.10	500MHz Prescaler Kit	1.78
Logic and Display P.C.B.s	4.84	SP8631B 500MHz I.C.	8.96
5MHz Crystal	3.45	NES92 Wideband Video Amp	1.43
Transformer 8-0-0V 0.5A (+75p P. & P.)	2.48	Hi-Z Buffer Kit	3.62
Switches, Knob, BNC's etc.	4.15	D.F.M. Reprint (post free)	0.50

## G8CZW Digital Voltmeter

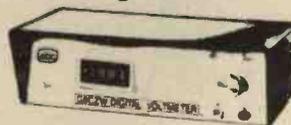

Complete kit **£44.30** inc. VAT, post free (U.K.)

ZNA116E 3½ Digit I.C.	6.48	Hardware and Wire Pack	1.20
Integrated Circuit Pack	5.24	Case, Two-tone p.v.c. faced steel, punched and lettered (+95p P. & P.)	5.75
Displays and Filter Pack	7.78	I.C. Sockets Pack	1.68
Semiconductor and Diode Pack	2.60	Transformer (+75p P. & P.)	2.48
Resistor Pack inc. cermet	4.84	5V Reg., 2 Rect., 2,000µF Cap., Mains SW., Fuse and Holder	3.75
Capacitor Pack	1.58	D.V.M. Reprint (post free)	0.35
Logic and Display P.C.B.s	2.05		
Voltage Attenuator Pack	0.68		
Range Switch 6P. 4-way	2.38		

All prices inc. VAT at the standard rate. Please add 20p P. & P. for packs. S.A.E. for full lists. Overseas—Deduct 8% off these prices.

Designer approved



**ELECTRONICS (OLDHAM) LTD.**

83 Lees Road, Oldham OL4 1JW

Tel. 061-624 8812

## BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs – £4.95; 14lbs – £7.95; 28 lbs – £12.00; 56lbs – £20.00; 112 lbs – £30.00.

### Handy Packs

4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. £1.00  
Self fluxing enamelled copper wire 18 & 22 swg on 2 oz reels. 2 for £1.10  
100 miniature reed switches ideal for burglar alarms, model railways, etc. £2.20  
15 2-pole reed relays on board operate at 12 volts £2.45  
6 6-pole 12 volt reed relays on board £2.45  
High quality capacitor panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95

### BARGAIN PACKS

New U.H.F. transistor TV tuners 4 pushbutton type £2.50  
Rotary type with slow motion drive £2.50  
Aluminium TV coax plugs. 10 for £1.00

Hardware Packs each containing 100's of items including: BA nuts and bolts, Nylon, Self-tapping, Posidrive, "P" clips. Cable clamps, Fuse holders, Spire nuts etc. £1 per pound. 100 assorted "P" clips £1.  
Belling Lee outdoor Triplexers, U.H.F., Band 1, Band 2, 50p each, 3 for £1.

### DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1 lb ferric chloride, 1 dolu etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions / only £5.30

### REFILL PACKS FOR ABOVE

150 sq. in. fibre glass board	£1.50	5 lbs ferric chloride to mil spec	£4.00
Dolu pen	90p	Instruction sheet	20p
1 lb ferric chloride to mil spec	£1.00		

### TV SURPLUS

Brand New ITT C.T.V. Triplers, fit Decca "Bradford" chassis £2.50 each; 5 for £10.  
Pye and Philips "GB" C.T.V. panels, various types. All incomplete but invaluable for spares or completing. 6 assorted panels for £7.50.  
Thorn B & W T.V. bottom panel "950" series, manufacturers surplus £1.50 each.  
Pye 114 contrast controls. 10 for £1.  
Thorn tape motors mains £1.20 each.  
Pye EHT bases, DY51 etc. 10 for £1.  
Ceramic P/C mounting valve bases PL509, PL508 etc. 10 for £1.

### Semiconductor Bargains

100 new & marked silicon and germanium transistors including BC148, BF194, BC183, etc. £3.95  
200 new & marked transistors, including 2N3055, AC128, BFY50, BD131, etc. £6.95  
100 mixed diodes IN4148, etc. £1.20  
100 mixed diodes including zener, power and bridge types £3.30

200 unmarked mixed transistors, lots of interesting types including power. Send 60p for samples £4.50

25 New & marked integrated circuits including 555, 741, 7400, 7490, TBA 800, CD4001, etc. £4.70

BR 101 full spec. 5 for £1.00

DY 51 EHT Rectifier £1.00

TBA 120A 50p each

20 mm anti-surge fuses your selection 500mA to 3.15A. 12 for £1.00.

### Component Bargains

300 mixed resistors & watt £1.00  
200 modern mixed caps most types £3.30  
100 mixed polyester caps £1.40  
100 mixed modern miniature ceramic plate caps, most values to 10000 PF £2.20  
100 mixed polystyrene caps to 5000 PF £2.20  
100 mixed electrolytics £2.20  
100 mixed wirewounds £1.00  
200 printed circuit resistors £1.00  
25 mixed pots & presets £1.00

30p P & P ON ALL ABOVE ITEMS. SEND CHECK OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PE, 20A WADDON ROAD, CROYDON, SURREY.

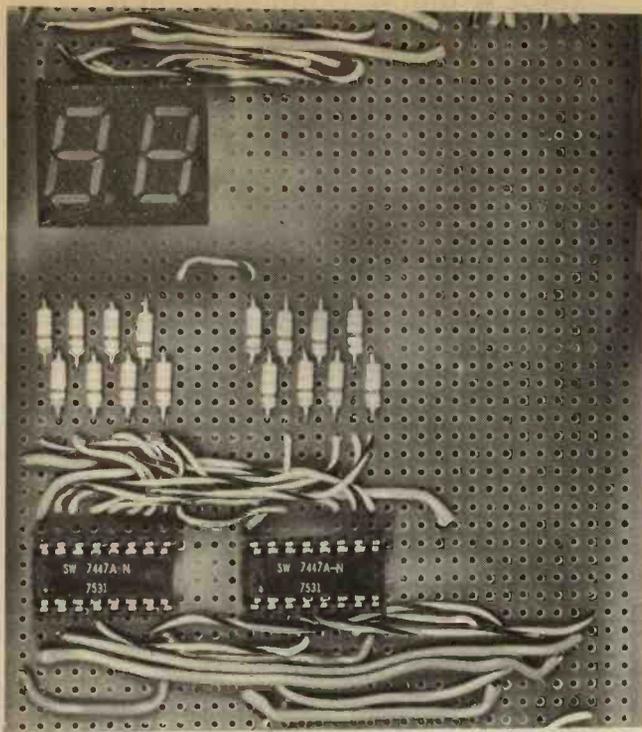


Fig. 5.6. Component layout for the display logic. A photo of the prototype is shown above. For assembly details Fig. 5.3 should be referred to

In the test schedule last month it was suggested that temporary connections be made between pins 9, 6 and 3 of IC34 and 0V in order to perform worthwhile testing. Do remember to remove any such connections before proceeding with this month's construction!

### FINAL TESTING

The ultimate test of any piece of equipment is to connect it up and try it! The scoring may be checked by monitoring the internal X codes and comparing the achieved scores with those expected from appropriately chosen combinations of inputs. Advantage may be taken of any occurrences of repeated X codes to verify that the reset logic and "A" flip flops are performing correctly.

Remember that fault tracing may be expedited by slowing down the internal clock as described in part three. To help those who do meet with problems a list of likely oversights is given below.

- (a) Check i.c. power connections—these are easily missed!
- (b) Make sure that you have not forgotten to solder in any i.c. pins.
- (c) Check for shorting Veroboard tracks.
- (d) Forgotten any Veroboard breaks?

Finally, it may be mentioned that there is a golden rule with non-operative TTL built systems: Always suspect your wiring first and the IC last! ★

## COMPONENTS . . .

### Semiconductors


IC43	SN7473N
IC44	7400
IC46-47	7420 (2 off)
IC48	7454
IC49	7410
IC40-29	7447 (2 off)
IC50	DL727 l.e.d. display (Litronix)

### Resistors

R11-R25	330Ω
R26	1kΩ
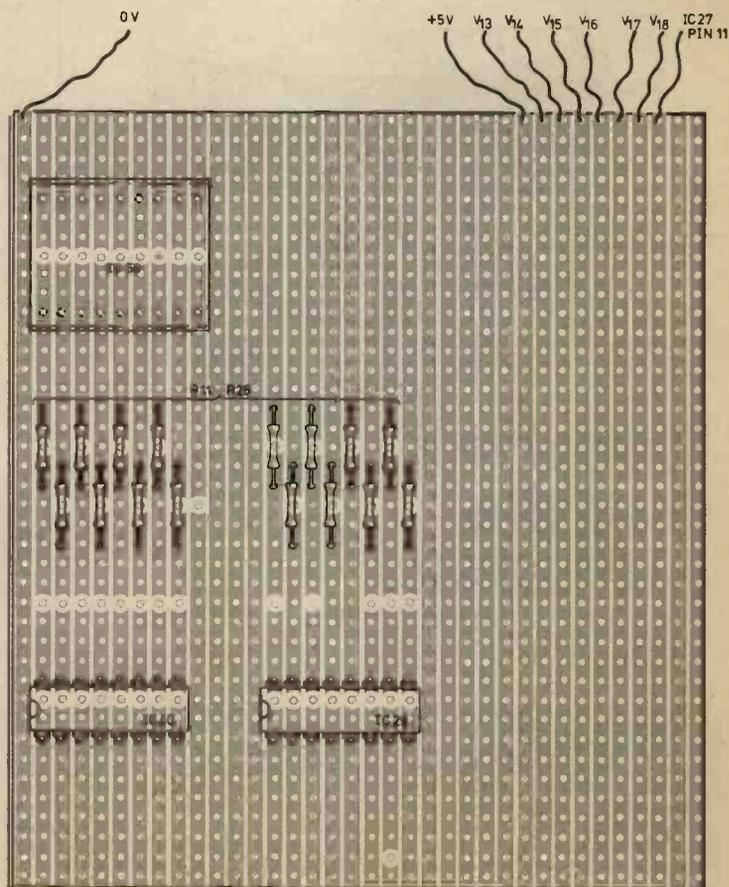
### Miscellaneous

Veroboard 0.1in matrix  
coppered size 3½in by 4in  
(Board 2)





# PHOENIX ELECTRONICS

(SOLENT) LTD

46 Osborne Road, Southsea, Hants

All prices include VAT  
Include 20p extra for carriage

### SOME SEMICONDUCTORS

BC107/8/9	11p
BC177/8/9	15p
BC204/5/6	14p
BC207/8/9	9p
BDY56	£1.72
1N4001	7p
1N4004	10p
1N4148	5p
2N2218/19/21/22	22p
2N2904/5/6/7	24p
2N3442	88p
2N3702-11	12p

### RESISTORS

½W carbon film (10)	18p
½W metal film (5)	18p

### CAPACITORS

Disc ceramic. Aluminium electrolytic. Tantalum bead.

### PANEL HARDWARE

Connectors, lampholders, switches, fuses, knobs.

### MISCELLANEOUS

Hand tools, instrument cases, Veroboard, relays, transformers.

### SOLDERING EQUIPMENT

Weller and Adcola irons, tips, desoldering tools, instant-heat guns.

### INTEGRATED CIRCUITS


DTL 930 series.  
TTL 74 series.  
Linear series.  
Consumer circuits.

**Buy More for Less Outlay with Our Bargain Packs**

Please send your 1977 catalogue—free!

Name .....

Address .....

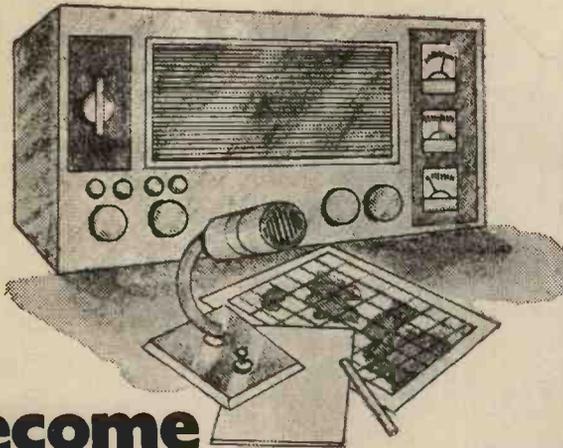

## Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA  
PEK12

Free!

Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O.Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_ (Block caps please)

# NEWS BRIEFS

## Sound Transmission by Infra-red Light

A NEW multi-channel infra-red sound transmission system has recently been demonstrated in this country. The Sennheiser Intraport System designed and manufactured in West Germany by Sennheiser is a large-scale development from the cordless headphones system for domestic hi-fi equipment first introduced at the Berlin Audio Fair 1975. Equipment is available for up to nine channel operation.

The demonstration was arranged by Hayden Laboratories Limited, of Chalfont St. Peter, Bucks, the U.K. distributors, and took place at Shepperton Film Studios. The whole of one stage area was saturated at high intensity from a number of strategically placed i.r. radiators (aerials). Each infra-red power radiator contains a bank of diodes and the power stage electronics. An automatic level setting amplifier ensures a low distortion radiation at maximum power.

The transmitter contains the exciter circuits of the multi-channel unit and the power supply for up to eight power radiators. A high frequency carrier is frequency-modulated by the audio signal. The transmitter output feeds the active radiators, where the emitted infra-red light is amplitude-modulated by the carrier. A special connection cable contains a coaxial lead for the r.f. signal and two d.c. supply leads for the power radiators.

The receiver is incorporated in the headset. This is fitted with a channel selector switch and houses standard batteries. Mounted on the headset, facing forward, is the infra-red receiving diode.

Reception is not entirely dependent upon direct line-of-sight with the radiators, since the i.r. radiation is reflected from light-coloured walls and objects, and so a strong field can be built-up within the room or hall. The number of radiators required depends upon the area to be covered and the reflection nature of the surrounding surfaces. The system's only limitation is that it cannot function in bright environments (over 300ft candles).

Using the standard headset PE's representative found that excellent reception was obtainable anywhere within the stage area, a fall-off in signal and increase in background noise being experienced when the wearer closely approached the dull-coloured distant walls, but a sheet of polystyrene of about 1 metre square was sufficient to restore the reception to normal.

The system is stated to be ideal for conference halls, factories and other large, moderately well-lit areas. Since solid surfaces are opaque to infra-red no radiation "leaks" out of the enclosed area, thus the infra-red system has great possibilities for "security sensitive" applications.

No licence is required for this type of wire-less communication.


# POINTS ARISING

## DIGITAL REACTION TIMER (November 1977)

The p.c.b. conductor layout in Fig. 2 does not show the necessary copper cladding extension around the fixing holes, which allow the stiff copper wire p.c.b. anchors to be soldered. This omission should be catered for. Also, the fixing holes themselves need not be as large as indicated in Fig. 3.

**ALL PRICES  
INCLUDE VAT**
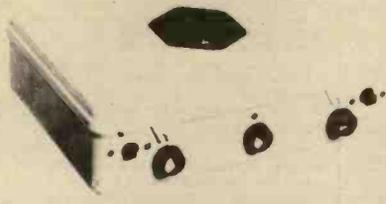
## NEW EDU-KIT MAJOR COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN -PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 5" x 3" Loudspeaker
- 3 12-way Connectors
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 6½ yards of wire
- 1 yard of sleeving, etc.
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier.
- Earpiece
- Mica

Complete kit of parts including construction plans  
**Total building costs £9.00 P.P. and Ins. £11.00**


### V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the long wave band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. All parts including case and plans  
**£3.95 P.P. & Ins. 60p**


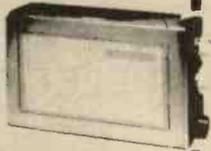
### POCKET FIVE

Now with 3in Loudspeaker 3 tuneable wavebands. MW, LW and trawler band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½in x 1½in x 3½ in approx. Complete kit of parts including construction plans.  
**Total Building Costs: £3.60 P.P. and Ins. 80p**




### NEW ROAMER TEN MODEL R.K. 3

MULTIBAND V.H.F. AND A.M. RECEIVER. 13 TRANSISTORS AND FIVE DIODES. QUALITY 5" x 3" LOUDSPEAKERS.

WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9—9 volt Battery.

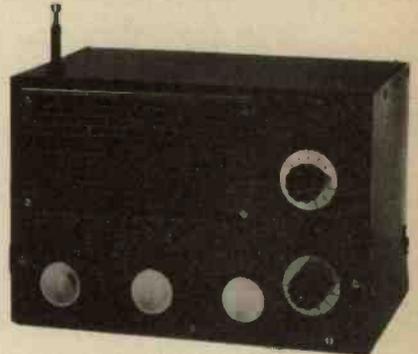Complete kit of parts including carrying strap, Building Instructions and operating Manuals. **£13.99** Inc. P. & P. Case enclosure kit (if required), £1.90 inc. P. P. and Ins.



### NEW Everyday Series




Build this exciting new series of designs. E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.  
**Total Building costs £4.30 P. & P. + Ins. 80p**

E.V.6. Case and looks as above. 6 Transistors 3 diodes. Powered by 9V battery. Ferrite rod aerial. 3in. loudspeaker, etc. MW/LW coverage. Push/Pull output. All parts including Case and Plans.  
**Total Building costs £4.95 P. & P. + Ins. 90p**

E.V.7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9V battery. Push pull output. Telescopic aerial for short waves. 3in. Loudspeaker. All parts including Case and Plans.  
**Total Building Costs £6.95 P. & P. + Ins. 90p**

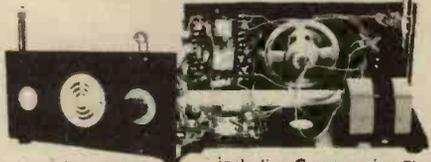
## ELECTRONIC CONSTRUCTION KITS

**E.C.K. 2** Self Contained Multi-Band V.H.F. Receiver Kit. 8 transistors and 3 diodes. Push pull output. 3in loudspeaker, gain control, 7 section chrome plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).  
**Complete kit of parts £7.95 P.P. and Ins. 90p**



including Construction Plans

**E.C.K. 4** 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band. 3 Short Wave Bands. Receiver Kit. With 5in x 3in loudspeaker. Push pull output stage, gain control, and rotary switch. 7 transistors and 4 diodes. 6 section chrome-plated telescopic aerial. 5in sensitive ready wound ferrite rod aerial, tuning capacitor, resistors, capacitors, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).  
**Complete kit of parts £7.25 P.P. and Ins. 90p**

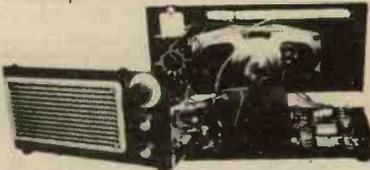


including Construction Plans

### EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

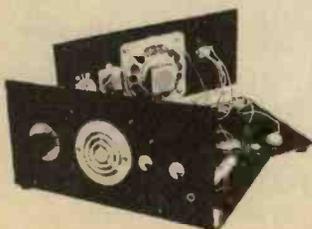All parts including loudspeaker, earpiece, MW ferrite rod aerial, capacitors, resistors, transistors, etc.  
**Complete kit of parts £6.55 P. & P. including construction plans + Ins. 80p**




To: RADIO EXCHANGE LTD.  
 61A High Street  
 Bedford MK40 1SA  
 Tel.: 0234 52387  
 REG NO. 788372

- Callers side entrance "Lavelis" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

I enclose £..... for.....  
 Name.....  
 Address.....  
 PE/1277

## SUPERSOUND 13 HI-FI MONO AMPLIFIER

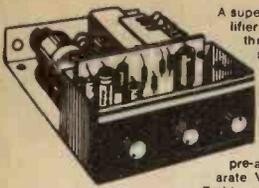

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz - 30KHz  $\pm$  3dB. Fully integrated pre-amplifier stage with separate Volume, Bass Boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, esutchcon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. AC 200/250V. PRICE £15.00 P. & P. £1.20.

## HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1-5mV into 47k. Input 2-5mV into 47k (suitable for use with mic. or guitar etc.). Input 3 100mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front esutchcon. For ac mains operation 200/240 volts. Size approx. 12in. wide x 5in high x 7in deep.

Special introductory price £28.00 + £2.50 carriage and packing.

### SPECIAL OFFERS

Mullard LP1159 RF-IF module 470 kHz £2.25 + P. & P. 20p. Full specification and connection details supplied. Pye VHF/FM Tuner Head covering 88-108 MHz. 10.7 MHz I.F. output. 7.8V  $\pm$  earth. Supplied pre-aligned, with full circuit diagram with precision-gear F.M. gang and 323PF  $\pm$  323PF A.M. Tuning gang only £3.15 + P. & P. 35p.

STILL AVAILABLE  
3 Valve Audio Amp. 4w, output £8.50 + £1.40 P. & P. Also HSL 'FOUR' amplifier kit £8.00 - £1.40 P. & P.

## MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State F.M. A.M. Stereo Tuner. Covering M.W. A.M. 540-1605KHz V.H.F. F.M. 88-108MHz.

Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/v Voltage 600mV R.M.S. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8in wide x 4in high x 9in deep approx.

Limited number only at £28.00 + £1.50 P. & P.

### PRECISION MADE

Push Button Switch bank, 8 buttons giving 16 S/P C/O Interlocked switches plus 1 Cancel Button plus 3 D/P C/O. Overall size 5in x 2in x 1in. Supplied complete with chrome finished switch buttons 2 for £1.60 + 20p P. & P.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC83, EF86 and E280 rectifier. Simple instruction booklet 25p + S.A.E. (Free with parts). All parts sold separately. ONLY £13.50 P. & P. £1.40. Also available ready built and tested £18.00 P. & P. £1.40.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11in x 14in x 1in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + P. & P. (one 90p, two £1.10). Now available in either 8 ohm round version or 4 1/2 x 8in rectangular. 100 watts R.M.S. 60Hz-20KHz £5.25 + P. & P. (one 85p, two 75p).

SPECIAL OFFER. 6in long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for HI.FI. £3.95 + 75p P. & P.

2in PLASTIC COME HF TWEEETER 4 ohm. £3.50 per matched pair + 50p P. & P.

## HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors. In the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design. All parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wires, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts R.M.S. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A overall size 12in wide x 8in deep x 2in high.

Fully detailed 7 page construction manual and parts list free with kit or sent 25p plus large S.A.E.

AMPLIFIER KIT £13.50 P. & P. 80p  
(Magnetic input components 33p extra)

POWER PACK KIT £5.50 P. & P. 95p

CABINET £5.50 P. & P. 95p

SPECIAL OFFER—only £23.75 if all 3 items ordered at one time plus £1.25 P. & P.

Full retail sales service  
Also available ready built and tested £31.25 P. & P. £1.50

## HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel. Size approx. 9in x 2in x 1in max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way esutchcon (to allow the amplifier to be mounted horizontally or vertically) at only £9.00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

### STEREO DECODER

SIZE 2' x 3' x 1' ready built. Pre-aligned and tested for 9-15V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday, 9.30-5 Saturday  
Closed Wednesday.  
Prices and specifications correct at time of press. Subject to alteration without notice

# HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY  
P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

C-MOS	4066	60p	7410	20p	7492	54p	74172	880p	
	4069	27p	7411	30p	7493	44p	74173	187p	
4000	20p	4070	50p	7412	20p	7494	88p	74174	100p
4001	20p	4071	25p	7413	38p	7495	65p	74175	98p
4002	20p	4072	25p	7414	98p	7496	90p	74176	123p
4006	114p	4073	26p	7415	35p	7497	35p	74177	123p
4007	20p	4076	118p	7417	40p	74100	120p	74178	110p
4008	99p	4077	48p	7420	20p	74104	73p	74179	138p
4009	57p	4081	20p	7421	40p	74105	73p	74180	106p
4010	57p	4082	25p	7422	26p	74107	36p	74181	282p
4011	20p	4083	95p	7423	32p	74109	75p	74182	83p
4012	20p	4502	123p	7425	32p	74110	50p	74184	234p
4019	62p	4510	139p	7426	107p	74111	86p	74185	187p
4014	107p	4511	150p	7427	89p	74116	251p	74190	134p
4015	114p	4512	81p	7428	81p	74120	155p	74191	134p
4016	51p	4514	264p	7430	20p	74121	35p	74192	115p
4017	114p	4515	264p	7432	29p	74122	53p	74193	115p
4018	110p	4516	123p	7433	118p	74123	81p	74194	107p
4020	115p	4520	123p	7437	38p	74125	59p	74195	102p
4021	101p	4520	123p	7438	38p	74128	59p	74196	134p
4022	99p	4526	122p	7440	20p	74128	98p	74197	130p
4023	20p	4527	140p	7443	130p	74132	75p	74198	124p
4024	79p	4528	115p	7444	130p	74143	346p	74221	109p
4025	20p	4531	115p	7445	105p	74144	346p	74246	205p
4026	155p	4543	115p	7447	90p	74145	90p	74247	195p
4027	60p	4555	115p	7448	90p	74147	148p	74248	171p
4028	95p	4556	115p	7450	20p	74148	150p	74249	171p
4029	123p	4581	348p	7451	20p	74150	150p	74251	170p
4030	55p	4582	140p	7453	20p	74151	78p	74265	94p
4033	155p	4584	99p	7454	20p	74153	78p	74278	311p
4034	347p	4585	108p	7460	20p	74154	138p	74279	75p
4035	118p			7470	33p	74155	90p	74283	94p
4040	132p	TTL		7472	30p	74156	90p	74284	712p
4041	84p			7473	33p	74157	82p	74285	712p
4042	89p			7474	33p	74158	140p	74290	122p
4043	99p			7475	46p	74159	265p	74293	122p
4044	91p			7481	125p	74160	102p	74298	173p
4046	137p			7483	95p	74161	102p	74365	93p
4049	55p			7484	119p	74162	102p	74366	93p
4050	55p			7485	128p	74163	102p	74367	93p
4051	140p			7496	33p	74164	119p	74368	93p
4052	140p			7489	340p	74165	115p	74390	189p
4053	140p			7490	43p	74167	358p	74393	189p
4060	140p			7491	77p	74170	213p	74490	254p

Full price list of linears, discretes, capacitors, resistors, potentiometers, tools, soldering irons and accessories available. Send 20p or large S.A.E. This list is sent free with the first order.

Prices correct June 1977.

Terms C.W.O. Add VAT to prices at 8%. Post, etc.: U.K. 25p, overseas 75p. Access and Barclaycard. And all convertible currencies accepted.

# TRIRO ELECTRONICS

Grenfell Place, Maidenhead, Berks.

Tel. (0628) 36229

Mail order division of RITRO Electronics UK Ltd.

## PINNER ELECTRONICS

S-DEC	1.99	TRANSFORMERS	£
T-DEC	3.51	8-0-8 100 MA	92*
U-DEC A	3.51	8-0-8 175 MA	92*
U-DEC B	5.99	12-0-12 50 MA	98*
ANTEX IRON C240 - 15W	3.30	6-0-6 1.5 A	2.66
ANTEX IRON CCN240 - 15W	3.54	9-0-9 1 A	2.25
ANTEX IRON CX240 - 17W	3.30	12-0-20-24-30V 1 A	2.84
ANTEX ST3 STAND	1.50		4.24
ANTEX C240 ELEMENT	1.43	DIE CAST BOXES	
TOWERS TRANSISTOR DATA & EQUIV. BOOK	4.36(Z)	3 1/2 x 1 1/2	1.08
TOWERS FEET DATA & EQUIV. BOOK	3.40(Z)	4 1/2 x 2 1/2	1.25
SERVISOL SWITCH CLEANER Box.	.89	4 1/2 x 2 1/2	1.15
SERVISOL FREEZER Box.	.69	4 3/4 x 2 1/2	1.99
TKM500 M/METER 30,000 O.P.V.	24.30	6 1/2 x 4 1/2	2.41
TKM500 CARRY CASE	5.00		
SP25 MK. III MOTORS	8.62*		
SP25 MK. IV MOTORS	10.64*		
DE SOLDA BRAID	.86		

PLEASE ADD 8% V.A.T. except those marked \* when you should add 12 1/2% V.A.T. (Z) = Zero V.A.T. All prices include postage and packing. Ten of any individual item - less 10% CASH WITH ORDER TO:

PINNER ELECTRONICS, 4 Village Way East, Rayners Lane, Harrow, Middlesex. Telephone: 01-868-5500

## BURGLAR ALARM

EQUIPMENT SUPPLIES (TRADE)

Bell boxes plastic coated steel	£5.25	Heavy duty 6in bell 12V	£7.75
Magnetically operated door switch surface type	£0.65	Siren 12V	£6.00
Magnetically operated door switch flush type	£0.60	3in bell	£2.25
Vibro sensitive switch	£2.75	Key switch two pole + chrome plate	£3.00
Pressure pads large 29in x 15in 4 wires	£1.75	Battery for above large HP1	£2.50
Pressure pads stair tread size 4 wires	£1.50	Kojak horn	£16.00

CONTROL UNITS			
Aluminium window foil 100th self adhesive	£3.00	Battery operated model	£14.00
Take off blocks for window foil per pair	£0.40	Battery and mains model	£19.00
		B.S. 4737 model battery + mains	£32.00
		D.I.Y. battery model	£11.00
		D.I.Y. battery and mains	£15.00

ALL PRICES + 12 1/2% VAT. NO VAT EXPORTS. POST FREE DISCOUNTS PER ITEM: £ + 10%; 25 + 15%; 100 + 20%. S.A.E. FOR FREE LIST OF SPECIAL EQUIPMENT


## ASTRO ALARMS

25 STOCKTON ROAD, SUNDERLAND

TYNE AND WEAR, ENGLAND.

TEL. 0783 77825

# THE DYNAMIC DUO

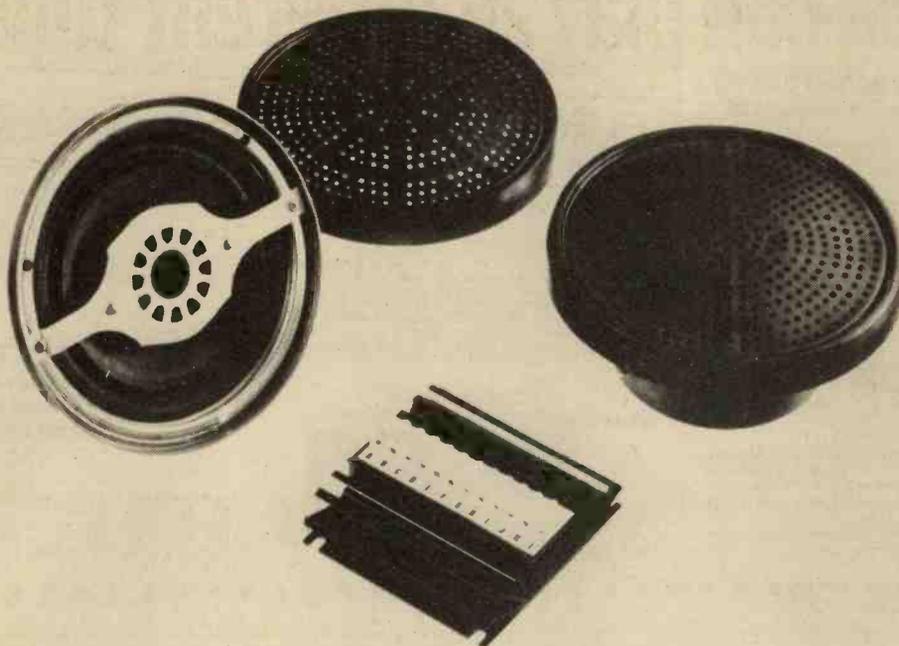

The C15/15 is a unique Power Amplifier providing Stereo 15 watts per channel or 30 watts Mono and can be used with any car radio/tape unit. It is simply wired in series with the existing speaker leads and in conjunction with our speakers S15 produces a system of incredible performance.

A novel feature is that the amplifier is automatically switched on or off by sensing the power line of the radio/tape unit hence alleviating the need for an on/off switch.

The amplifier is sealed into an integral heatsink and is terminated by screw connectors making installation a very easy process.

The S15 has been specially designed for car use and produces performance equal to domestic speakers yet retaining high power handling and compact size.

#### C15/15

15 watts per channel into 4Ω  
 Distortion 0.2% at 1kHz at 15 watts  
 Frequency response 50Hz-30kHz  
 Input Impedance 8Ω nominal  
 Input sensitivity 2V R.M.S. for 15 watts output  
 Power line 10-18V  
 Open and Short circuit protection  
 Thermal protection  
 Size 4 x 4 x 1 inches

#### Data on S15

6in Diameter  
 5½in air Suspension  
 2in Active Tweeter  
 20oz Ceramic magnet  
 15 watts R.M.S. handling  
 50Hz-15kHz frequency response  
 4Ω Impedance

C15/15 Price £17.74 + £2.21 VAT. P. & P. free

S15 Price per pair £17.74 + £2.21 VAT. P. & P. free

**TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS**

**I.L.P. Electronics Ltd**  
**Crossland House**  
**Nackington, Canterbury**  
**Kent CT4 7AD**  
**Tel. (0227) 63218**

Please Supply .....

Total Purchase Price .....

I Enclose Cheque  Postal Orders  Money Order

Please debit my Access account  Barclaycard account


Account number .....

Name and Address .....

Signature .....

## INVERTERS

KIT FORM or BUILT UP.

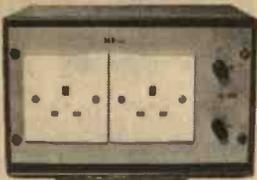

240V-50Hz from your 12v car battery.

O/P Powers available. 25W-40W-75W-150W-300W-400W-500W-1kW-1.5kW. Various battery I/P voltages available.

## AUTOMATIC INVERTORS

These units have built-in battery charger which functions whilst mains are healthy. Upon mains failure unit automatically switches to inverter operation ensuring no interruption of supply. Send S.A.E. for price lists.

## RHYTHM GENERATOR



15 different rhythms, 9 percussion instruments. Tempo range 15 to 100 bars/min. Full kit of parts available at £39.50 + £1.20 P. & P. + VAT at 8%. Price assembled and tested add £12. Parts available separately, send S.A.E.

We reserve the right to alter published prices in the event of component or postal increases.

## P.E. ORION STEREO AMPLIFIER & TUNER



May be mounted slim line or stacked as above. Parts available separately for both units.

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.1% 100Hz-10kHz. Frequency response  $\pm$  1dB 20Hz to 20kHz. Hum level virtually nil with volume full on. This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

## TUNER UNIT

May be purchased separately in matching slim line case. As full kit or individual parts. Send S.A.E. for price list and specification sheets.



## LOUDSPEAKERS

8 inch system

This system is designed for use with above amplifiers rated up to 25W r.m.s. per channel at 8 $\Omega$ . May be incorporated in an enclosure 295 x 490 x 295mm (11.5 x 19.3 x 11.5in) approx. external, constructional details of which are given with each bass unit, to provide an overall frequency response of 50Hz to 22kHz. Four-element cross-over, ready constructed on p.c.b. Output leads have push-on receptacles to suit speaker tags. Cross-over frequency is 2.8kHz approx.

## POWER UNIT

Regulated



Voltage adjustable from 1-35v at 2 amps. Short circuit protected. Voltage and current meters incorporated. Full Kit of parts £48 + 8% VAT or assembled and tested £58 + 8% VAT.

## ASTRO IGNITION



SAVE FUEL

Complete kit of parts for this proven and tested system. (£11.90 + 60p P. & P.) + 8% VAT or ready built with only two connections to alter.

(£14.90 + 60p P. & P.) + 8% VAT.

Consider the advantages:

Fuel economy. Faster acceleration. More power. Excellent cold starting. Smoother running. No contact breaker burning. Less exhaust gases.

## TRANSFORMERS

### SPECIAL OFFER

Miniature Mains Trans.

6-0-6v-6VA.

12-0-12v-6VA.

(£1.29 + 25p P. & P.) + 8% VAT

Transformer and coils manufactured to customer specifications both in High Volume and Small Order capacity.

TRADE AND EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS:

## ASTRO ELECTRONICS

Springbank Road  
Chesterfield (S1475)  
Derbyshire

N.B.—DELIVERIES ON ALL ITEMS MAY TAKE UP TO 28 DAYS, DEPENDING ON AVAILABILITY AND DEMAND. CASH IN REGISTERED ENVELOPE OR POSTAL ORDERS CAN REDUCE TIME BY NOT HAVING TO CLEAR CHEQUES

# CMOS COOKBOOK

by D. Lancaster

Price £7.50

OPTOELECTRONICS THEORY AND PRACTICE by A. Chappell (Texas ins.) Price £8.00

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS by I. R. Sinclair Price £3.20

INTRODUCTION TO MICRO-PROCESSORS by D. Aspinall Price £5.40

PROBLEMS IN ELECTRONICS WITH SOLUTIONS by F. A. Benson Price £4.50

PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos Price £4.50

ELECTRONICS FAULT DIAGNOSIS by I. R. Sinclair Price £3.00

FOUNDATIONS OF WIRELESS AND ELECTRONICS by M. G. Scroggie Price £4.25

110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price £3.30

NEWNES TAPE RECORDER SERVICING MANUAL VOL. I by J. Gardner Price £8.40

VOL. II Price £8.40

TOWERS' INTERNATIONAL TRANSISTOR SELECTOR by T. D. Towers Price £5.00

\* ALL PRICES INCLUDE POSTAGE \*

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books

19-21 PRAED STREET  
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

## INTER-LOCKING PLASTIC STORAGE DRAWERS



NEAREST NEIGHBOUR! TRY!

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2½in x 2½in). £2.90 DOZEN.

DOUBLE UNITS (2D) (5in x 4½in x 2½in). £4.90 DOZEN.

TREBLE (3D) £4.90 for 8.

DOUBLE TREBLE 2 drawers. In one outer case (6D2), £7.25 for 8.

EXTRA LARGE SIZE (6D1) £6.25 for 8.

### PLUS QUANTITY DISCOUNTS

Orders over £20. less 5%.

Orders over £60. less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage

QUOTATIONS FOR LARGE QUANTITIES  
Please add 8% V.A.T. to total remittance  
All prices correct at time of going to press

## FLAIRLINE SUPPLIES

(Dept. PE12)

124 Cricklewood Broadway, London NW2

Tel. 01-450 4844

## OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V a.c.  
6-3V 1-5A £2; 3A £3; 6A CT £4.25; 12V 1-5A £2.50; 3A £4.25; 6A CT £8; 18V 1-5A CT £4.25; 24V 1-5A CT £4.25; 3A CT £8; 5A CT £10; 6A CT £15; 12A CT £21; 40V 3A CT £10; 50V 6A CT £21.

TWIN SEC TRANSFORMERS: Prim 240V a.c.  
6V 0-6A + 6V 0-6A; 9V 0-4A + 9V 0-6A; 12V 0-25A + 12V 0-25A; 20V 0-15A + 12V 0-15A all at £2.85 each; 15V 0-75A + 15V 0-75A £4; 15V 1-5A + 15V 1-5A £5; 18V 1A + 18V 1A £4.50; 18V 1-5A + 18V 1-5A £5.75; 20V 1-5A + 20V 1-5A £5.75; 12V 4A + 12V 4A £7.50; 25V 2A + 25V 2A £7.50.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V a.c.  
6-0-6V 1-5A or 0-9V 1A £2.25 each; 12-0-12V 1A or 20-0-20V 0-75A £2.85 each; 9-0-9V 0-3A or 12-0-12V 0-25A or 20-0-20V 0-15A £2 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V a.c.  
0-10-12-14-16-18V 2A £4; 4A £5.25; 0-12-15-20-24-30V 2A £4.50; 4A £7.50; 0-5-20-30-60V 1A £5.25; 2A £7.50; 0-40-50-60-80-100-110V 1A £7.50.

MAINS TRANSFORMERS: Prim 240V a.c.  
250-0-250V 60mA 6-3V 1A £1.85 inc. P. & P. and VAT  
250V 100mA 6-3V 2A £2.50 inc. P. & P. and VAT  
23V 0-5A £1.50 inc. P. & P. and VAT

110/240V a.c. Auto 20W  
SPEAKER MATCHING AUTO TRANSFORMERS  
12W, 3 to 8 or 15, up or down, £2.25 inc. P. & P. and VAT

LOUDSPEAKERS  
2½in 8 $\Omega$ , 2½in 8 or 25 $\Omega$ , 2½in 8 or 80 $\Omega$ ; 3in 35 $\Omega$ , 3½in 3, 16 or 80 $\Omega$ , all at £1.80 each; 7 x 4in 3, 16, 25 or 80 $\Omega$ , £2 each; 8 x 5in 4, 8 or 25 $\Omega$ , £2.70; 8in 8 $\Omega$  £2.70 inc. P. & P. and VAT.

"INSTANT" BULK CASSETTE/TAPE ERASER  
Instant erasure of cassettes and tape spool, any diameter, demagnetises tape heads, 200/240V a.c. £8 inc. P. & P. and VAT.

POWER SUPPLY, TWIN OUTPUT: Prim 240V a.c.  
New, ex British manufacture. Smoother d.c. output 20V 1-5A, plus stabilised 15V 100mA, plus 12V a.c. 0-5A, with diagram, £4.75 inc. P. & P. and VAT.

CONDENSERS  
Electrolytic, W.E. 1000-50V 30p; 4700/40V 60p; Paper tubular, W.E. 47/500V, 2-2/400V, 4-7/160V all 25p each (£15 per 1000).  
Electrolytic screw terminal 1200/75V 50p.

EDGEMILE LEVEL METER FSD 200A  
Size, 19 x 18 x 20mm, 800, £1.35 inc. P. & P. and VAT

PRINTED CIRCUITS ETCHING KIT  
Make your own PC Boards: Comprehensive commercial kit, instructions, £4 inc. P. & P. and VAT.

MULTI WAY CABLE, SCREENED PVC COVERED  
36 way £1; 25 way 75p; 14 way 50p; 8 way 25p; 4 way 20p; 2 way 10p; 1 way 5p per metre. Fig. 8 stereo twin, £1.25 15 metres.

MINI 3-CORE CABLE, 19/0, 10mm  
Ideal for speakers, intercoms, etc. £4.85 inc. P. & P. and VAT.

TWIN FIG. 8 CABLE  
Polarised, 100m, £5.00 inc. P. & P. and VAT.  
All types domestic and commercial cables. Enquiries invited.

Carriage and VAT EXTRA on all orders

except where otherwise stated.

Callers by appointment only  
S.A.E. Enquiries, lists.

46 Kenilworth Road, Edgware, Middx HA8 9YG  
Tel. 01-958 8314

# STRIKE YOUR OWN BARGAIN WITH

**NO EXTRAS TO PAY FOR POSTAGE OR V.A.T.**

# Stirling Sound

## Britain's most go-ahead module manufacturers

CHOOSE THE ITEMS YOU WANT AND BUY THEM THE STIRLING SOUND BARGAIN WAY whether for a new system, to up-grade what you use now, to build a disco or P.A. outfit, a domestic intercom or any other device where an amplifier might be used. Whatever it be, there's a Stirling Sound power amp for it up to 100 watts R.M.S., together with a choice of stereo tone control/pre-amps. Build with Stirling Sound now! See what you save and hear how good it sounds.

### THE SCHEME

Choose from any of the 9 power amplifier modules shown in our ad. and then the Stirling Sound power supply unit best likely to suit the job. Refer to the published prices (which already include V.A.T. and post free in U.K.). When you send the money

**DEDUCT 5% FROM THE TOTAL PRICE OF THE TWO ITEMS**

If you order UNIT ONE at the same time that you order a power amp. and power unit as above

**DEDUCT A FURTHER £1.00 FROM THE TOTAL PRICE**

If you order UNIT TWO at the same time that you order a power amp. and power unit as above

**DEDUCT A FURTHER £1.18 FROM THE TOTAL PRICE**

### UNIT ONE

Combined stereo pre-amp & active tone control unit. Input sensitivity 50mV for 200mV out. 10-16V operation. Bass  $\pm 15$ dB at 30Hz; Treble  $\pm 15$ dB at 10KHz; Balance control; Volume control. For ceramic p.u., radio or tape inputs. WITH FREE CONTROL PANEL FASCIA. £9.00



### UNIT TWO

With control facilities similar to UNIT ONE but for magnetic cartridge input. Input sensitivity - 5mV for 200mV out (can be varied). WITH FREE CONTROL PANEL FASCIA £12.43 CONTROL PANEL FASCIA available separately 50p

SS.100 Basic active stereo tone control module to provide  $\pm 15$ dB on bass at 30Hz and on treble at 10KHz. £3.00

SS.101 Stereo pre-amp suitable for ceramics, tape, radio, etc. £2.75

SS.102 Stereo pre-amp for mag. pick-ups. £4.45

F.M. STEREO DECODER, phase lock loop type, with LED indicator showing when a stereo transmission is being received. £5.25


WHEN ORDERING ALL PRICES QUOTED INCLUDE V.A.T. AND GOODS ARE SENT POST FREE IN U.K. Owing to time between sending our ad. to this journal and the time it appears, prices may be subject to alteration without notice. E.&O.E. ORDER BY ACCESS OR BARCLAYCARD - SIMPLY LET US HAVE YOUR NUMBER.

## Stirling Sound

Dept. PE1277

37 VANGUARD WAY, SHOE BURYNESS, ESSEX.  
Telephone (03708) 5543.


Shop - 220-224 West Rd., Westcliff-on-Sea, Essex.  
Telephone Southend (0702) 351048.

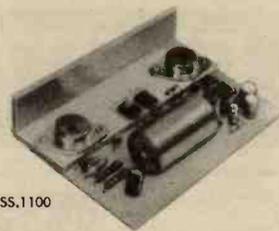

SS.1100

Made in our own U.K. factory and sold direct to you, the user

**SATISFACTION GUARANTEED**

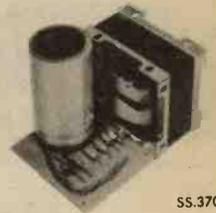

SS.370

### AMPLIFIERS 3 to 100 WATTS R.M.S.

Ready assembled on P.C.B.s, tested and guaranteed. Easy to connect. With instructions. Output ratings  $\pm 1$ dB.

- SS.103 I.C. amp. 3 watts R.M.S. using 20V/8Q or 14V/4Q. Input 100mV. £2-85
- SS.103-3 Stereo version of above, 2 I.C.s. £5-00
- SS.105 5 watts R.M.S. into 3Q using 13.5V. Sensitivity - 30mV. THD - 0.3%.  $3\frac{1}{2}'' \times 2'' \times 1''$ . £3-95
- SS.110 10 watts R.M.S. into 4Q using 24V. Sensitivity - 60mV. THD - 0.3%.  $3\frac{1}{2}'' \times 2'' \times 1''$ . £4-65
- SS.120 20 watts R.M.S. into 4Q using 34V. Sensitivity - 80mV. THD - 0.3%.  $3\frac{1}{2}'' \times 2'' \times 1''$ . £5-15
- SS.125 25 watts R.M.S. into 8Q using 50V. Sensitivity - 140mV. Distortion - Less than 0.05% into 8. S/N better than 70dB. £7-25
- SS.140 40 watts R.M.S. into 4Q using 45V. Sensitivity - 300mV. Distortion typically 0.1%.  $5'' \times 3\frac{1}{2}'' \times 1\frac{1}{2}''$ . £6-50
- SS.160 64 watts R.M.S. into 4Q using 50V. Sensitivity - 350mV. Distortion typically 0.1%.  $5'' \times 3\frac{1}{2}'' \times 1\frac{1}{2}''$ . £8-50
- SS.1100 100 watts R.M.S. into 4Q using 70V/2A. Input sensitivity - 500mV. Distortion at half-power, typically 0.1%.  $5'' \times 3\frac{1}{2}'' \times 1\frac{1}{2}''$ . £10-50
- HS.160 Multi-finned heatsink for SS.140 or SS.160. 75p
- HS.1100 Dito for SS.1100 £1-50

### POWER UNITS

Every Stirling Sound Power Unit is tested and guaranteed under working conditions before despatch. All units except SS.312 include a stabilised low voltage take-off point (13-15V) for pre-amp, tone control, radio tuner, etc. Outputs quoted minimal unloaded ratings.

SS.312	12V/1A	£6-60
SS.318	18V/1A	£6-95
SS.324	24V/1A	£7-65
SS.334	34V/2A	£8-75
SS.345	45V/2A	£10-75
SS.350	50V/2A	£11-75
SS.360	60V/2A	£12-75
SS.370	70V/2A	£14-75

SS.310/50 Stabilised power supply unit with variable output from 10V to 50V/2A. Short circuit protected £17-75

SS.300 Power stabilising unit variable from 10 to 50V/8A for adding to un-stabilised supply units £5-50

Improved circuitry and performance standards. More to choose from.

To STIRLING SOUND	
Please supply.....	NAME .....
.....	ADDRESS .....
.....	.....
.....	.....
for which I enclose £.....	My Access or Barclaycard No. is.....
	PE1277

**BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:**

**DOES IT HAVE**

- ★ 30A power transistors
- ★ 2-year guarantee
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S

TAM1000 100W 4 ohms 65V	£9.80
TAM500 50W 4 ohms 45V	£7.50
TAM250 25W 8 ohms 45V	£5.75

<b>POWER SUPPLIES</b>	
For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carriage 50p on supplies)	

- Suits loads 4–16 ohms
- 20–20,000 Hz  $\pm 1$ dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

High grade components used throughout: Texas, Mullard, R.C.A., Plessey, etc.



- Low distortion (0.1%)
- Low profile (1in high 3½in x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections



**ALL PURPOSE MIXER/PRE-AMP.**  
(with 60mm slider volume)

- Suitable for multiple input systems
- High and low impedance inputs
- High sensitivity
- Built-in supply smoothing
- 20–20,000 Hz  $\pm 1$ dB
- –80dB noise level
- Accepts a wide variety of inputs
- Wide range bass and treble controls

Use up to 10 PRE-AMPS with 1 power supply

Printed circuit board assembly with treble and bass controls plus slider volume control

**£6.50**

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W systems and at 12½% for 25W systems (including preamp if ordered at same time).

Hours, 9.30 a.m.–5 p.m.  
Monday — Saturday.  
Callers welcome. Tel. (01) 684 0098

# TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

## AITKEN BROS.

**35, High Bridge, Newcastle upon Tyne**

Tel: 0632 26729

### S-DEC

This, the most popular Board is designed solely for the use of discrete components and is particularly useful for basic educational purposes.  
(No. of Contacts: 70)  
PRICE £2.13 Inc. VAT

### T-DEC

This Board allows 2 TO5 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC application where considerable numbers of discrete components may be required.  
(No. of Contacts: 208)  
PRICE £3.93 Inc. VAT.

### μ-DEC 'A'

The μ-DEC 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used but will accommodate discrete components with equal facility.  
(No. of Contacts: 208)  
PRICE £4.31 Inc. VAT.

### μ-DEC 'B'

The μ-DEC 'B' is for similar uses as μ-DEC 'A', but has two 16 lead IC sockets as part of the Board.  
(No. of Contacts: 208)  
PRICE £7.55 Inc. VAT.

### PANEL METERS

Dims: 60mm x 45mm.  
50μ amp, 100μ amp, 500μ amp, 1MA, 5MA, 10MA, 50MA, 100MA, 500MA. 1 amp, 2 amp, 25V dc, 30V dc, 50V ac, 300V ac, "S", "VU", 50-0-50μA, 100-0-100μA, 500-0-500 μA.  
PRICE £4.13 Inc. VAT.

POTS\* CAPACITORS, BOXES, INST. CASES, DIN PLUGS, RESISTORS, ETC., ALWAYS IN STOCK. POSTAGE AND PACKING 20p EXTRA. 1978 CAT. AVAILABLE JAN. PLEASE SEND 40p.

## WIRE THREADING INTROKIT

**£6.60**

Spare bobbins—Blue, Green, Pink, Copper	0.40
Oryx temp. cont. iron and stand	£11.05
Microshear cutters (with safety clip)	£2.84
Quality tweezers	0.90
Conductive paint 3g tube "Elecolit 340"	£2.30

### COMPARE OUR PRICES!

**TERMS:** Add 35p P. & P. per order (Oryx iron and stand 45p P. & P.). Add 8% VAT to all orders—Overseas—Allow £1 extra for P. & P.

**MAIL ORDER ONLY:** Access available. Trade enquiries welcome.

**ZARTRONIX, 115 Lion Lane, Haslemere  
Surrey GU27 1JL**

## YOUR OWN COMPUTER WHY NOT!

The Microprocessor Users Group can help you build it, with a regular magazine of circuits and software, plus free use of our software library, free technical and programming assistance and discounts on all components systems and services sold by us. For full details write with S.A.E. to Computabits Ltd, 41 Vincent Street, Yeovil, Somerset. Tel. (0935) 26522.

Get a great deal from

# Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome

A. MARSHALL (LONDON) LTD. DEPT. P.E.  
 LONDON—40-42 Cricklewood Broadway NW2 3ET  
 Tel.: 01-452 0161. Telex: 21492  
 LONDON—325 Edgware Rd W2. Tel: 01-723 4242/3  
 GLASGOW—85 West Regent Street G2 2QD  
 Tel.: 041-332 4133  
 BRISTOL—1 Straits Parade, Fishponds Rd BS16 2LX  
 Tel: 0272 654201

**CATALOGUE** NEW 1977 AUTUMN ★  
 COMPLETE BUYERS GUIDE TO ELECTRONICS COMPONENTS  
 PRICE 35p POST PAID. 25p FOR CALLERS

### TOP 400 SEMICONDUCTORS FROM THE LARGEST RANGE IN THE U.K.

EXPRESS M.O. SERVICE BY RETURN POST—all orders received despatched same day on stock items

Please add VAT to your order. P. & P. 40p

2N696	0-35	2N3703	0-15	2N6126	0-45	BC159	0-16	BD116	1-20	BFX85	0-35
2N697	0-30	2N3704	0-15	40361	0-50	BC160	0-35	BD131	0-51	BFX87	0-30
2N698	0-62	2N3705	0-15	40362	0-55	BC161	0-35	BD132	0-54	BFX88	0-30
2N699	0-55	2N3706	0-16	40363	1-30	BC167	0-12	BD135	0-37	BFY69	1-20
2N706	0-28	2N3707	0-18	40406	0-60	BC168	0-12	BD136	0-37	BFY50	0-25
2N706A	0-28	2N3708	0-13	40407	0-52	BC169	0-12	BD137	0-38	BFY51	0-25
2N708	0-28	2N3709	0-15	40408	0-75	BC170	0-18	BD138	0-38	BFY52	0-25
2N709	0-50	2N3710	0-16	40409	0-75	BC171	0-18	BD243	0-60	BFY53	0-34
2N718	0-27	2N3711	0-16	40410	0-75	BC172	0-14	BD140	0-40	BFY50	0-20
2N718A	0-50	2N3712	1-20	40411	2-85	BC177	0-20	BD239	0-40	BFY39	0-50
2N720A	0-80	2N3713	2-30	40594	0-80	BC178	0-20	BD240	0-45	BXY20	0-33
2N814	0-35	2N3714	2-45	40595	0-90	BC179	0-23	BD241	0-45	BXS21	1-32
2N816	0-30	2N3715	2-55	40573	0-75	BC182	0-21	BD242	0-50	BU105	1-40
2N818	0-38	2N3716	3-00	40126	0-45	BC182L	0-14	BD243	0-60	BU205	2-20
2N825	0-25	2N3717	1-95	AC127	0-45	BC183	0-14	BD244	0-65	ME042	0-20
2N830	0-26	2N3722	2-00	AC128	0-45	BC183L	0-14	BD245	0-65	ME040	0-15
2N1131	0-30	2N3773	2-90	AC151V	0-40	BC184	0-12	BD246	0-66	ME042	0-20
2N1132	0-37	2N3789	2-90	AC152V	0-50	BC184L	0-14	BD246	0-66	ME042	0-10
2N1613	0-30	2N3790	3-10	AC153	0-55	BC207	0-18	BD350	0-38	ME104	1-10
2N1711	0-30	2N3791	3-10	AC153K	0-55	BC208	0-16	BDY20	1-10	MU481	1-50
2N1893	0-38	2N3792	3-50	AC156	0-50	BC212	0-14	BF115	0-38	MU490	1-35
2N2102	0-98	2N3794	2-00	AC176K	0-65	BC212L	0-17	BF121	0-55	MU491	1-45
2N2216	0-33	2N3819	0-36	AC187K	0-60	BC213	0-14	BF123	0-55	MU2955	1-20
2N2218A	0-37	2N3820	0-38	AC188K	0-60	BC213L	0-16	BF152	0-25	MU304	0-58
2N2219	0-35	2N3823	0-80	AD161	1-00	BC214	0-16	BF153	0-25	MUE370	0-58
2N2219A	0-36	2N3904	0-21	AD162	1-00	BC214L	0-17	BF154	0-25	MUES31	0-60
2N2220	0-35	2N3906	0-22	AF106	0-55	BC237	0-14	BF155	0-25	MUE20	0-45
2N2221	0-25	2N4036	0-67	AF109	0-75	BC238	0-18	BF160	0-30	MUE521	0-60
2N2221A	0-26	2N4037	0-55	AF124	0-65	BC238	0-15	BF161	0-40	MUE2955	1-50
2N2222	0-25	2N4058	0-20	AF125	0-65	BC251	0-18	BF166	0-60	MUE3055	1-50
2N2222A	0-25	2N4059	0-15	AF126	0-65	BC253	0-22	BF167	0-35	MP8111	0-35
2N2368	0-25	2N4060	0-20	AF139	0-69	BC257A	0-17	BF173	0-35	MP8112	0-35
2N2369	0-25	2N4061	0-21	AF166	0-55	BC258A	0-17	BF175	0-25	MP8113	0-45
2N2369A	0-25	2N4062	0-18	AF167	0-55	BC259	0-18	BF178	0-25	MPP102	0-20
2N2646	0-75	2N4126	0-17	AF239	0-65	BC281A	0-24	BF179	0-30	MPSA05	0-25
2N2647	1-40	2N4289	0-20	AF240	1-14	BC262B	0-24	BF180	0-35	MPSA06	0-25
2N2904	0-36	2N4919	0-65	AF279	0-80	BC263C	0-30	BF181	0-35	MPSA12	0-40
2N2904A	0-37	2N4920	0-75	AF280	0-85	BC300	0-40	BF182	0-35	MPSA55	0-25
2N2905	0-37	2N4921	0-50	BC107	0-15	BC301	0-40	BF183	0-40	MPSA56	0-25
2N2905A	0-38	2N4922	0-55	BC108	0-15	BC303	0-50	BF184	0-38	MPSU05	0-50
2N2906	0-28	2N4923	0-70	BC109	0-15	BC307	0-15	BF185	0-35	MPSU06	0-58
2N2906A	0-28	2N4929	0-60	BC113	0-20	BC308	0-15	BF194	0-15	MPSU55	0-55
2N2907	0-25	2N5191	0-70	BC115	0-20	BC309C	0-15	BF195	0-15	MPSU56	0-60
2N2907A	0-25	2N5192	0-75	BC116	0-19	BC317	0-14	BF196	0-16	TP29A	0-40
2N2924	0-15	2N5195	0-90	BC116A	0-20	BC318	0-13	BF197	0-17	TP29C	0-60
2N2925	0-17	2N5245	0-34	BC117	0-22	BC327	0-20	BF199	0-18	TP30A	0-40
2N3019	0-55	2N5294	0-40	BC118	0-20	BC328	0-19	BF200	0-35	TP30C	0-65
2N3053	0-26	2N5295	0-40	BC119	0-30	BC337	0-19	BF225J	0-25	TP31A	0-50
2N3054	0-60	2N5296	0-40	BC121	0-45	BC338	0-21	BF244	0-35	TP31C	0-66
2N3055	0-70	2N5298	0-40	BC132	0-30	BC347	0-12	BF245	0-40	TP32A	0-75
2N3390	0-20	2N5447	0-15	BC134	0-20	BC348	0-12	BF246	0-75	TP32C	0-55
2N3391	0-20	2N5448	0-15	BC135	0-20	BC349	0-13	BF254	0-24	TP33A	0-80
2N3391A	0-20	2N5449	0-19	BC136	0-19	BC350	0-10	BF255	0-24	TP33B	1-10
2N3392	0-16	2N5457	0-32	BC137	0-20	BCY31	1-00	BF257	0-37	TP34A	0-80
2N3393	0-15	2N5458	0-33	BC140	0-35	BCY32	1-00	BF258	0-45	TP34C	1-20
2N3394	0-15	2N5459	0-29	BC141	0-40	BCY33	1-00	BF259	0-48	TP35A	2-50
2N3439	0-88	2N5486	0-34	BC142	0-30	BCY34	1-00	BF459	0-50	TP36A	0-80
2N3440	0-64	2N5486	0-38	BC143	0-30	BCY38	2-00	BF459	0-50	TP41A	2-70
2N3441	0-61	2N6027	0-60	BC147	0-12	BCY40	1-00	BF459	0-50	TP41C	0-90
2N3442	1-15	2N6101	0-45	BC148	0-12	BCY59	2-25	BF528	1-38	TP42A	0-80
2N3638	0-16	2N6107	0-42	BC149	0-14	BCY59	2-25	BF561	0-30	TP42C	1-00
2N3638A	0-16	2N6109	0-50	BC153	0-27	BCY70	0-25	BF598	0-38	TP2955	0-65
2N3639	0-30	2N6121	0-38	BC154	0-27	BCY71	0-26	BF729	0-35	TP3055	0-55
2N3641	0-20	2N6122	0-41	BC157	0-14	BCY72	0-24	BFX30	0-35	TIS43	0-43
2N3702	0-13	2N6123	0-43	BC158	0-14	BD115	0-80	BFX84	0-35	LM748	0-55
										LM748B	0-55
										LM748C	0-60
										LM748D	0-75
										LM748E	0-60
										LM748F	0-60
										LM748G	0-60
										LM748H	0-60

### INTEGRATED CIRCUITS

CA3020	2-20	LM1600	1-76	TA570	2-30
CA3020A	2-20	LM1608	1-92	TAA611B	1-85
CA3028	1-10	LM1828	1-75	TAA621	2-15
CA3028A	1-01	LM3301N	0-85	TAA651A	1-50
CA3030	1-35	LM3302N	1-40	TAA700	3-91
CA3030A	2-00	LM3301	0-70	TAA900A	1-30
CA3045	1-40	LM3900	0-75	TAA930B	1-30
CA3046	0-88	LM3905	1-60	TAA930B	1-30
CA3048	2-23	LM3909	0-68	TAD100	1-95
CA3049	1-80	MC1035	1-75	TBA120	0-75
CA3050	2-42	MC1303	1-03	TBA160	2-30
CA3052	1-52	MC1304	1-40	TBA500	2-21
CA3080	0-75	MC1305	1-40	TBA500Q	2-30
CA3080A	1-88	MC1310	1-91	TBA510	2-21
CA3086	0-80	MC1327	1-54	TBA510Q	2-21
CA3088	1-70	MC1330	1-00	TBA520	2-21
CA3089	2-92	MC1350	0-90	TBA520Q	2-21
CA3090	0-80	MC1351	1-20	TBA530	2-30
CA3130	0-58	MC1351	1-10	TBA530Q	2-30
LM301A	0-67	MC1458	1-91	TBA540	2-21
LM301N	0-40	NE555	0-40	TBA540Q	2-30
LM304	2-45	NE556	1-10	TBA550	3-13
LM307N	0-65	NE565	1-30	TBA550Q	3-22
LM309C	1-82	NE566	1-65	TBA560Q	3-22
LM309B	0-85	NE567	1-80	TBA570	1-29
LM309K	1-85	SA5560	2-50	TBA570Q	1-38
LM317K	3-00	SA5570	2-50	TBA641B	2-70
LM318N	2-26	SA02P	1-25	TBA651	2-70
LM323K	6-46	76001N	1-30	TBA700	1-52
LM339N	1-40	76033N	2-20	TBA700Q	1-51
LM348N	1-50	76034N	1-50	TBA720Q	2-30
LM350N	2-75	76131N	1-50	TBA750	1-98
LM370N	2-50	76130ND	1-30	TBA750Q	2-07
LM371N	1-70	76101K	1-50	TBA800	1-25
LM372N	1-70	761023N	1-45	TBA810	1-25
LM373N	2-80	76023ND	1-26	TBA820	1-25
LM374N	3-10	76133N	2-20	TBA920	2-90
LM378N	2-25	76115N	1-51	TBA940	1-62
LM379S	3-95	76116N	1-66	TCA160C	1-85
LM380	0-90	76131N	1-20	TCA160B	1-61
LM380N	0-98	76226N	1-56	TCA270	2-25
LM381A	2-45	76227N	1-20	TCA280A	1-30
LM381B	1-60	76228N	1-41	TCA290A	1-13
LM382N	1-25	76530N	0-75	TCA420A	1-84
LM384N	1-45	76532N	1-40	TCA730	3-22
LM386N	0-80	76533N	1-20	TCA740	2-76
LM387N	1-05	76544N	1-44	TCA750	2-30
LM388N	0-75	76545N	1-65	TCA760	1-38
LM389N	1-00	76546N	1-40	TCA800	2-00
LM702C	2-75	76550N	0-55	UA1170	2-00
LM709C	0-65	76552N	0-35	UA1180	2-00
LM709N	0-45	76570N	1-68		
LM710C	0-60	76570N	0-90		
LM710N	0-60	76650N	1-10		
LM739C	0-85	76660N	0-60		
LM739N	0-75	76662N	0-82		
LM741C	0-65	TAA320A	2-48		
LM741N	0-40	TAA521	1-90		

# BUILD YOUR OWN HI-FI SYSTEM

*Satisfaction! Economy! Pleasure!*

Enjoy the satisfaction of building your own hi-fi system and save your money into the bargain.

Starting with this issue, Practical Hi-Fi & Audio shows you how to construct an amplifier, bookshelf loudspeakers and a record turntable, all from readily available components.

Inside this issue: building a pair of bookshelf loudspeakers.

## SPECIAL SUPPLEMENT

What was new at the Harrogate Audio Show, the Audio Fair at Olympia and the High Fidelity 77 Autumn Exhibition.

**SPECIAL CHRISTMAS OFFER**  
**A third BASF LH Super Cassette FREE!**  
**When you buy two!**  
**ALSO 100 BASF Checkpoint Cassette Care Kits to be won!**

**PRACTICAL HI-FI & AUDIO**

December issue 40p  
 On sale Friday, November 18



LOW PROFILE DIL SOCKETS - TIN PLATED				READY DRILLED BLACK ANODISED HEAT SINKS				
PRICE PER	1	5	10	25	TO 3	1 @ 40p	5 @ £1.80	
8 PIN	10p	45p	85p	£2.00	TO 66	1 @ 40p	5 @ £1.80	
14 PIN	12p	55p	£1.05	£2.50	TO 3 x 2	1 @ 70p	5 @ £3.20	
16 PIN	13p	60p	£1.15	£2.75	HEAT SINK COOLERS, FITTING TO 5.			
28 PIN	25p	£1.20	£2.30	£5.50	NF 204	1 @ 14p	5 @ 65p	
40 PIN	40p	£1.80	£3.50	£8.25	NF 205	1 @ 12p	5 @ 55p	
STANDARD PROFILE DOUBLE-SIDED DIL - SOCKETS					NF 207	1 @ 13p	5 @ 60p	
14 PIN	14p	65p	£1.25	£3.00	NF 209	1 @ 15p	5 @ 75p	
16 PIN	15p	70p	£1.35	£3.25	INSULATING KITS, 5 WASHERS TO BUSHES.			
MOUNTING PADS						MELINEX	MICA	
TO 5 4 HOLE	9p	40p			TO 3	@ 28p/KIT	@ 30p/KIT	
TO 18 4 HOLE	9p	40p			TO 66	@ 28p/KIT	@ 30p/KIT	
CONVERTERS						BUSH SHANK LENGTH REQ. .205, .153, .125, .05, .025, .125, .05, .025. For TO 3 only.		
TO 99 TO DIL	55p	£2.50			TRANSISTOR INSULATION COVERS			
TO 100 TO DIL	55p	£2.50			TO 3	5 @ 35p	10 @ 70p	
TO 92/98 TO TOS	9p	40p			TO 5	5 @ 15p	10 @ 25p	
TO 18 TO TOS	9p	40p			TO 66	5 @ 35p	10 @ 70p	
TO 98 TO TOS	9p	40p			POWER SOCKETS			
DIODE CRADLES	10p	45p			TO 3	1 @ 14p	5 @ 65p	
LARGER RANGE OF TRANSISTOR PADS AND INSULATING BUSHES IN CATALOGUE. ALL PRICES INCLUDE V.A.T.						TO 66	1 @ 16p	5 @ 75p
						TO 220 INSULATING KITS 5 Washer 5 Bushes MELINEX 20p/KIT MICA 25p/KIT.		

POST AND PACKING 15p KITS/PADS/SOCKETS/COOLERS. 45p FOR ANODISED HEAT SINKS

FULL ILLUSTRATED CATALOGUE - SEND 30p FOR POST AND PACKING.

FROM \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_


**MOULDED ELECTRONIC COMPONENTS INT. LTD.**  
 34d QUARRY HILL ROAD  
 TONBRIDGE, KENT.  
 Telephone: 0732 365910

## AUDIBLY SUPERIOR AMPLIFICATION

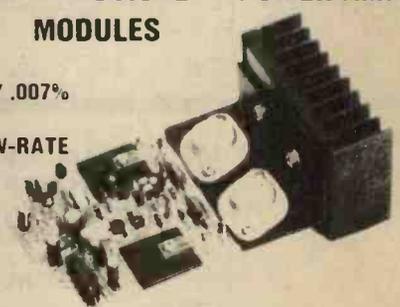**HIGH DEFINITION - 'MUSICAL' - POWER AMP MODULES**

- ★ T.H.D. TYPICALLY .007% @ 10W, 500Hz
- ★ ZERO T.I.D. (SLEW-RATE LIMIT 16 V/μS)

Module size: 120 x 80 x 25 mm, using glass fibre pcb with ident and solder resist. Illustrated with light duty heatsink.



CRIMSON ELEKTRIK power amplifier modules are fast gaining a reputation as the best sounding, most musical modules available. Perhaps the most important features of this design are exceptional freedom from crossover distortion (due to the use of output triodes) and zero T.I.D. The amplifier is protected against open and short circuit loads and yet will drive a highly reactive lower impedance load which is more representative of a real loudspeaker. Square waves maintain their rise times up to full power whilst simulated electrostatic loads are easily handled with negligible overshoot and a settling time of 12μS. Other specs S/N > 110dB. Rise time 10μS. Sensitivity 775mV. DC coupled. 5Hz-35kHz (-3dB). THO < -015%. 100mW clipping, 500Hz.

CRIMSON ELEKTRIK power supplies are in kit form for maximum flexibility and feature a low field slimline toroidal transformer with a 120-240v primary and screen, two large capacitors bridge rectifier and all fixings. Heatsinks are attractive black anodised extrusions, 80mm wide.

POWER AMP MODULES	HOME	EUROPE
CE 608 60Wrms 8 ohms 35v dc	£16.30	£16.30
CE 1004 100Wrms 3 ohms 35v dc	£19.22	£19.00
CE 1008 100Wrms 8 ohms 35v dc	£23.22	£22.70
POWER SUPPLIES		
CPS 1 For 2xCE608 or 1xCE1004	£12.85	£14.20
CPS 2 For 2xCE1004 or 2 or 3xCE1008	£14.55	£17.90
CPS 3 For 2xCE1008	£15.85	£19.20
HEATSINKS		
Light Duty 50mm 2 C/W	90	£1.30
High power 100mm 1.4 C/W	£1.60	£2.40
Disc group 150mm 1.1 C/W	£2.30	£3.65

**CRIMSON ELEKTRIK (PE)**  
 74 STATION ROAD  
 RATBY  
 LEICESTER, LE6 0JN  
 TEL: (0533) 386211

Home prices include VAT and carriage. Payment by cheque. PO COD 60p (£50 limit). Export no problem. European prices include carriage, insurance and handling payment in Sterling by bank draft, PO, International Giro or Money Order. Outside Europe please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price list on request. Suitable pre-amp circuit 20p.

# TRAMPUS



**A SEMICONDUCTOR POWER HOUSE**  
**TRAMPUS ELECTRONICS LTD., 58-60 GROVE ROAD, WINDSOR**  
 BERKS. SL4 1HS. (Trade, export & retail.)

Tel: Windsor (07535) 54525. Callers welcome. Mon-Sat. 9 am-5 pm.  
 Fast service. On ex stock product same day despatch normally. Quality  
 devices, manufacturers specifications, lowest prices. Barclay Card and  
 Access by post or telephone £5 minimum. VAT: add 8% to prices marked \*.  
 Add 12% VAT to all other prices. Post and packing 20p U.K. Send C.W.O.  
 except Gov. Dept. etc. Money back if not satisfied. Catalogue sale list  
 free, send S.A.E.

IC's	All price each	BC109B or C	15p*	Pak N: 25 x OA81/91	£1*
555 DIL 8 Timer	37p*	BC147/8/9	12p	Pak M: 3 x 2 amp, PNP/NPN	
723 TO99 Reg.	47p*	BC167/8/9	10p	Pairs 60V (Total 6)	£1*
723 DIL 14 pin	69p*	BC177/8/9	20p	Pak W: 20K mixed 10V	
741 DIL 8 pin op. amp.	25p*	BC182/3/4 A or L	10p	electrolytic 2-100µF	£1
741 DIL 14 or TO99	36p*	BC123/3/4 A or L	14p	More Paks in free lists	
747 Dual 741	89p*	BC770/71/72	20p*	SCR and TRIACS: ST2 25p*; BR100 40p*; C106 4A 400V 55p*; 1A 400V 50p*; 1A 600V 89p*.	
748 DIL 14 pin	29p*	BD131 or 132 each	39p*	DISCO TRIAC 10A 400V 80p* VERO. All stocked i.e. 0-1in. 2 1/2 x 3 1/2in 42p*; 3 1/2 x 5in 56p*; 3 1/2 x 17in £2-50*; 2 x 4in DIL 75p*; 6 x 4in DIL Bread Board £2-44* Pois 25p; Presets 9p; Resistors 2p.	
748 DIL 8 pin	49p*	BFY50, 51 or 52	20p*	CAPACITORS: Ceramic 5p; Electrolytic 1µF-100µF 7p; Heatsinks: TO18/TO5 5p*; TO3 29p. Solder Dispenser 18 S.W.G. 35p*.	
7805 plastic or TO3	£1*	MJ2955 (PNP 3055)	£1-50*	Soldercon 100 45p*; 1,000 1£4* DIL Sockets £. 14 or 16 15p* CMOS. Many stocked i.e. 4001 or 2 23p*; 4009 10 59p*; 4011 20p*; 4049 or 69 23p*.	
7812 or 15 plastic	£1-50*	MJE2955	£1-40*	TTL 7400N SERIES	
78019 or 78023	£1-69	MJE3055	55p*	7400 14p* 7485/86 10p*	
8038 Sig. Gen.	£5*	ORP12	50p*	7401 9p* 7490 49p*	
AY5124 Clock	£2-50*	TIP29, 30, 31, 32C	60p*	7404 20p* 7491 50p*	
LM340	50p*	TIP41A or 42A	65p*	7408/9 10p* 7493/5 50p*	
LM301 DIL 14 pin	29p*	TIP41C or 42C	£1*	7413 39p* 74107 20p*	
LM301 DIL 8 pin	59p*	TIP2955	65p*	7417/20 29p* 74121 33p*	
LM309K TO3 5V	£1*	TIP3055	55p*	7430 8p* 74123 39p*	
LM318 70V U.S.	£2-25*	TS43 UJT	39p	7440 15p* 74141 89p*	
LM3800 2W A.F.	£1	2N2546 UJT	50p*	7441 79p* 74157 50p*	
LM3900 Quad op. amp.	75p*	2N2904 ORS	30p*	7447 84p* 74193 50p*	
MC1310 V5 only	75p*	2N2926 YG	15p*	7448 60p*	
NE555 Timer	37p*	2N3053	24p*	7470/72 29p* ad. for 7473/74 35p* ad. for 7475 40p* special 7476 39p* prices 7480/2/3 10p* shown.	
NE556 2 x 555	£1*	2N3055 115W	45p*		
SN75611 and 60 IF	£1-25	2N342 120V 3055	39p		
TBA810 7W A.F.	£1	2N3702/3/5/6	10p		
LEDs 1/4in and 0-2in dia.		2N3704	9p		
Red no clip	11p*	2N3819e or 23e	18p		
0-2in Red and clip	15p*	2N3904/5/6	20p		
Colour LEDs	29p*	2N5457 FET	50p		
DISPLAYS (Red LED)		INS Bush Sets	each 10p*		
0-3in DL704/2	65p*	Matching, add	20p*		
0-3in DL707/2	65p*				
0-6in DL747/2	£1*	DIODES OA81/91	5p		
TGS308 Gas Detector	£5*	IN4148 and IN914, silicon	4p*		
390pF Med./Short Tuner	£1*	IN4001	5p		
Audible warning bleeper		IN4004	7p*		
12V 100mA	£1-40*	B2788 Zeners, 400mW	10p*		
Dato PCB Pen, 2 tips	74p*	Bridge: 1A 50V	25p*		
SRBP 6 x 4in	60p*	6A	£1*		
FEC	£1*				
PCB Etching Kit	£2*	FULL SPEC PAKS			
TRANSISTORS		Pak A: 10 x LEDs	£1*		
BC107, 108 or 109 all	9p*	Pak B: 4 x 741C	£1*		
BC107B	15p*	Pak C: 3 x 2N3055	£1*		
BC108B or C	15p*	Pak H: 6 x 2N3819e	£1*		
		Pak K: 4 x IN914	£1*		

# Sparkrite mk2

## Capacitive discharge electronic ignition kit

VOTED BEST  
 OF 8 SYSTEMS  
 TESTED BY  
 'POPULAR  
 MOTORING'  
 MAGAZINE  
 OCT. 74



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

### OPTIONAL EXTRAS

Electronic/conventional ignition switch.  
 Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

**CALLERS WELCOME.** For Crypton tuning and fitting service - phone (0922) 33008.

**PRICES INCLUDE VAT, POST AND PACKING.**  
**Improve performance & economy NOW**

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing  
 ELECTRONICS DESIGN ASSOCIATES, 82 Bath St., Walsall, WS1 3DE

**POST TODAY!**

**Quick installation**  
 No engine modification required

Electronics Design Associates, Dept. PE11  
 82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....

Address .....

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		Cheque No.
		Send SAE if brochure only required.

## THE IDEAL CHRISTMAS PRESENT

S O L D E R

# MINIATURE SOLDERING IRON

for HOBBY or TRADE

PRICES: (including VAT and P and P)

**Irons £3-70** each

**Bits 41p** each

(Bit type 20 fitted as standard).

Stands  
 £3.90 each

Solder 28p & 56p

18 watts of power  
 at 240 v. straight to the bit

BIT SIZES:  
 19 (1.5 mm) 20 (3.0 mm)  
 21 (4.5 mm) 22 (6.0 mm)

Trade Enquiries Welcome

From your Local Dealer or Direct from the Manufacturers:  
**S. & R. BREWSTER Ltd.**  
 86-88 UNION ST. PLYMOUTH Tel 0752-65011

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

**A MERRY XMAS  
TO ALL OUR CUSTOMERS  
PLUS A XMAS PRESENT FROM US  
IN THE FORM OF A**

**10% DISCOUNT  
ON ALL ORDERS RECEIVED  
FROM 1st to 31st DECEMBER**

For items in our current  
ads and lists only

**THIS OFFER IS FOR 1 MONTH ONLY**

Slider Switches, 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

**A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.**

Aluminium Boxes with Lids.		
AB10	5 1/2 x 4 x 1 1/2	60p
AB13	6 x 4 x 2	80p
AB14	7 x 5 x 2 1/2	£1-00
AB15	8 x 6 x 3	£1-30
AB16	10 x 7 x 3	£1-50
AB17	10 x 4 1/2 x 3	£1-30
AB25	6 x 4 x 3	£1-00

**Vinyl Coated Instrument Cases**  
Light Blue tops and White lower sections. Very smart finish.

WB1	5 x 2 1/2 x 2 1/2	60p
WB2	6 x 4 1/2 x 1 1/2	£1-10
WB3	8 x 5 x 2	£1-60
WB4	9 x 5 1/2 x 2 1/2	£1-80
WB5	11 x 6 1/2 x 3	£2-00
WB6	11 x 7 1/2 x 3 1/2	£2-25
WB7	12 x 6 1/2 x 5 1/2	£2-60
WB853	8 x 5 1/2 x 3 1/2	£2-00

**MAINS TRANSFORMERS.** Type 60/2. Mains input 200-210-220-230-240-250V a.c., output 0-20-40-60V at 2A, in Metal and Plastic case, approx. 7 1/2 x 4 x 4, fully fused (ideal for PSU) £3-00 each.

**MAINS TRANSFORMERS.** Type 15/300 240V input, 15V at 300mA output, £1-50 each.

**MAINS TRANSFORMERS.** Type 45/100, 240, 220, 110, 20, 0V input, 45V at 100mA output, £1-50 each.

**MAGNETIC DEVICES PROGRAMMERS.** Contain 9 fully adjustable cams and 9 change over micro-switches (rated approx. 1A at 240VAC). Needs slow-motion motor to drive (not supplied). Ideal for disco lights, sequence switching, etc. ex equipment £1-50 each.

**VIDICON SCAN COILS** (Transistor type, but no data) complete with vidicon base £6-50 each. Brand New.

**FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK.** S.A.E. FOR LIST.

**NEW FOR THE VHF CONSTRUCTOR.** A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.

Type S (jin. square, dummy type).  
Type SA 20 to 30MHz (when 33pF fitted in parallel).  
Type SB 20 to 30MHz (with link winding).  
Type SC 70 to 100MHz (with link winding).  
Type SD 135 to 175MHz (with link winding).  
Type M (Min. jin. square types)  
Type MA 19 to 28MHz (when 33pF fitted in parallel).  
Type MB 22 to 32MHz (when 33pF fitted in parallel).  
Type MC 25 to 35MHz (when 33pF fitted in parallel).  
Type MD 38 to 50MHz (when 33pF fitted in parallel).  
Type ME 45 to 60MHz (when 33pF fitted in parallel).  
Type MF 100 to 200MHz (without slug) when 0 to 30pF variable fitted in parallel.  
All the above coils available in packs of five only (same type) at 50p per pack of 5.

**SEMICONDUCTORS**

BSX20 (VHF Osc/Mult). 3 for 50p.  
BC108 (metal can). 4 for 50p.  
PBC108 (plastic BC108). 5 for 50p.  
BFY51 Transistors. 4 for 60p.  
BCY72 Transistors. 4 for 50p.  
PNP audio type TO5 Transistors. 12 for 25p.  
BF152 (UHF amp/mixer). 3 for 50p.  
2N3819 Fet., 3 for 60p.  
BC148 NPN SILICON. 4 for 50p.  
BC158 PNP SILICON. 4 for 50p.  
6AY1 Signal Diodes. 10 for 25p.  
BAV21 Varicap Diodes. 4 for 50p.

741CG op amps by RCA. 4 for £1

RED LEDs (Min. type) 5 for 70p.

**PLASTIC PROJECT BOXES** with screw on lids (in black ABS) with brass inserts.  
Type NB1 approx 3in. x 2 1/2in. x 1 1/2in. 40p each.  
Type NB2 approx. 3 1/2in. x 2 1/2in. x 1 1/2in. 50p each.  
Type NB3 approx. 4 1/2in. x 3 1/2in. x 1 1/2in. 60p each.

**MULLARD 05A2 85V STABILISER VALVES** (Brand New) 70p each or 2 for £1-20.

TO3 transistor insulator sets. 10 for 50p

**PERSPEX TUNER PANELS** (for FM Band 2 tuners) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2in x 1 1/2in., 2 for 35p.

**PLUGS AND SOCKETS**

N-Type Plugs 50 ohm, 60p each, 3 for £1-50.  
PL259 Plugs (PTFE), brand new, packed with reducers, 65p each.  
SO239 Sockets (PTFE), brand new (4-hole fixing type). 50p each

**SOLDER SUCKERS** (Plunger type). Standard Model. £5. Skirted Model £5-50. Spare Nozzles 60p each.

**NEW MARKSMAN RANGE OF SOLDERING IRONS.**

SI25D 25W 240V £3-80.  
SI40D 40W 240V £4-20.  
SI25OK 25W 240V + bits etc.. KIT £4-90.

**BENCH STAND** with spring and sponge for Marksman Irons £2-38.

Spare bits MT9 (for 15W) 50p, MT5 (for 25W) 45p, MT10 (for 40W) 50p.

ALL PRICES + 8% VAT.

**TCP2 TEMPERATURE CONTROLLED IRON.** Temperature controlled Iron and PSU. £30 + VAT (£2 40).

**SPARE TIPS**

Type CC single flat. Type K double flat fine tip. Type P, very fine tip. £1 each + VAT (8p).

**MOST SPARES AVAILABLE.**

**MULTICORE SOLDER**

Size 5 Savbit 18 s.w.g. in alloy dispenser. 32p + VAT (3p).  
Size GTSAV18 Savbit 18 s.w.g., 56p + VAT (4p).  
£ Kg. (1-1lb) 60 x 40, 20 s.w.g. on plastic reel £3 + VAT (24p).

**WELLER SOLDERING IRONS**  
EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.  
EXPERT SOLDER GUN 81000 £9-90.  
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £12-90.  
Spare bits 35p pair.

**A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.**

**MIXED COMPONENT PACKS**, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

**ALU-90L ALUMINIUM SOLDER** (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 s.w.g. with multicore flux, with instructions, Approx. 1 metre coil 40p pack. Large reel £2-75.

**VARICAP TUNERS** Mullard type ELC1043/05. Brand New. £4-40 + 12 1/2% VAT.

**BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS.** Up to 50V working. Seatronic Manufacture. Approx. 100. £1-50 per pack + 12 1/2% VAT.

**OSMOR REED RELAY COILS** (for reed relays up to 1/2in dia., not supplied) 12V, 500 ohm coil, 2 for 50p.

We now stock Spiralux Tools for the electronic enthusiast. Screwdrivers, Nut spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.


Dubilier Electrolytics, 50µF, 450V, 2 for 50p.  
Dubilier Electrolytics, 100µF, 275V, 2 for 50p.  
Plessey Electrolytics, 470µF, 63V, 3 for 50p.  
TCC Electrolytics, 1000µF, 30V, 3 for 60p.  
Dubilier Electrolytics, 5000µF, 35V, 50p each.  
Dubilier Electrolytics, 5000µF, 50V, 60p each.  
ITT Electrolytics, 6800µF, 25V, high grade, screw terminals, with mounting clips, 50p each.

**PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.**

**TV PLUGS AND SOCKETS**

TV Plugs (metal type), 4 for 50p.  
TV Sockets (metal type), 4 for 50p.  
TV Line Connectors (back-to-back sockets), 4 for 50p.  
Please add 12 1/2% VAT.

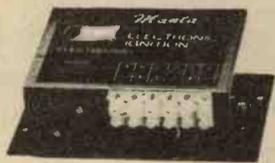**Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE WITH ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY**



**THE "Manta"  
CAPACITIVE DISCHARGE ELECTRONIC  
IGNITION UNIT**

**FITS ALL CARS—IMPROVES  
PERFORMANCE—SAVES PETROL**

Specifically designed for the Home Constructor, this top quality, high output unit incorporates the latest sophisticated electronic circuitry for the best consistent performance.

Developed from the popular P.E. "Scorpio Mk 11" (designed by Messrs. Gibbs and Shaw), but improved to give highest reliability. Uses only top quality components.

PRICE OF COMPLETE KIT NOW ONLY £15-50 (inclusive of VAT, P. & P.). After sales service available.

READY MADE UNIT ALSO AVAILABLE NOW ONLY £17-50 (inclusive of VAT and P. & P.). Full two year guarantee.

Do not confuse with cheaper electronic ignition units.

Send 7p stamp for full details and our six page explanatory brochure "Electronic Ignition—How it Works".

**ELECTRO SPARES**

Dept. P.E., 187a Sheffield Road, Chesterfield, Derbys.  
S41 7JQ. Telephone: Chesterfield (0246) 36638

**TECHNICAL TRAINING  
IN ELECTRONICS AND  
TELECOMMUNICATIONS**

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of the many opportunities open to trained people. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

**City & Guilds Certificates:**  
Telecommunications Technicians  
Radio, TV, Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
MPT Radio Communications Certificate

**Diploma Courses:**  
Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting

**POST OR PHONE TODAY FOR FREE BOOKLET**

To: International Correspondence Schools

**ICS** Dept. 772A Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_ Tel. \_\_\_\_\_ Age \_\_\_\_\_

## DIY SPEAKER KITS

**15-WATT KIT IN CHASSIS FORM**  
When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the enclosures illustrated below. Size 13" x 8" (approx.) woofer (EMI), tweeter, and matching crossover components. Power handling capacity 15 watts rms. 30 watts peak.  
**£17.00 PER STEREO PAIR**  
+ P & P £3.40

## EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak, each unit.  
**£28.00 PER STEREO PAIR**  
(approx.) + P & P £5.50

## COMPACT FOR TOP VALUE

Now about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only **£8.50** — just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready milled and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.  
**£8.50 per stereo pair**  
+ P & P £2.20

**SPEAKERS** Two models — Duo IIb, teak veneer, 12 watts rms, 24 watts peak. 18 1/2" x 13 1/2" x 7 1/2" (approx.).

**★ £34 PER PAIR**  
+ P & P £8.50

Duo III, 20 watts rms, 40 watts peak. 27" x 13" x 11 1/2" (approx.).

**★ £52 PER PAIR**  
+ P & P £7.50


## EASY TO BUILD RECORD PLAYER KIT

Ideally suited for the constructor who requires a complete stereo unit at a budget price, comprising ready assembled stereo amp, module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phono socket and record/replay socket.  
**£26.95**  
+ P & P £4.05
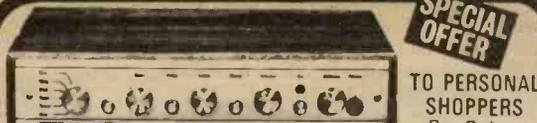
## CAR RADIO KIT

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control. The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. Size approx. 7" x 2" x 4 1/2". 12 volts pos or neg earth (altered internally) P & P £1.50  
**£12.50**  
Output 4 watts into 4 ohms.

● **FREE TO PERSONAL SHOPPERS BUYING CAR RADIO KIT** ELECTROMATE Rear window heater modern line element all wiring and switch worth **£3.00**



**SPECIAL OFFER**

**TO PERSONAL SHOPPERS**  
See Below

## 20 x 20 WATT STEREO AMPLIFIER

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. **£29.90**  
Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak. P & P £2.50

● **FREE** To cash or cheque personal shoppers  
A 4 channel Stereo Adaptor to all buyers of the Viscount 20 x 20 Amplifier at **£29.90** limited offer. Available separately at **£3.95**  
+ £1.00 P & P

## SPECIAL OFFER

For example  
Duo speaker system II or III  
Viscount Amplifier,  
MP60 type turntable complete

**DEDUCT 10% DEDUCT 15%**

★ on complete stereo systems using ★  
starred Products

## ADD-ON STEREO CASSETTE TAPE DECK KIT

Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control ready for mating together with the mechanism.

Specifications: Sensitivity — Mic. 0.85mV ± 20K OHMS;  
Din. 40mV ± 400K OHMS; Output — 300mV RMS per channel → 1KHz from 2K OHMS source; Cross Talk — -30db;  
Tape Counter — 3 Digit - Resettable; Frequency Response — 40Hz — 8KHz ± 6db; Deck Motor — 9 Volt DC with electronic speed regulations; Key Functions — Record, Rewind, Fast Forward, Play, Stop & Eject. P & P £2.50

Pair of Dynamic microphones **£3.95** + £1.00 P & P.  
Optional extras: Mains transformer **£2.50** + £1.00 P & P.

**STEREO CASSETTE RECORD/REPLAY** fully built P.C.B. board incorporating 4 I.C.s. **£2.75**  
**GRUNDIG 5 1/2"** tape 1800 ft. **£1.20** each. 5 for **£5.00**  
**PAIR STEREO 8 WATT SPEAKERS**  
8" bass units with 3 1/2" approx. tweeters power handling 8 watts imp 8 ohms. Size 16 1/2" x 11" x 8 1/2" approx. **£12.95**  
**SLIMLINE RECORD PLAYER PLINTH** Accepts B.S.R. turntable **95p**  
**GOODMAN 5"** approx. 7 watt bass speaker **£2.70**  
**AM. FM. TUNER P.C.B.** with Mullard L.P. 1186, 1185, 1181 modules **£9.50**  
**100K** Multiturn Varicap tuning pots 6 for **£1.00**  
**HEAVY DUTY FIBRE GLASS COPPER CLAD BOARD** **£1.90**  
**25" x 17"** approx. per sheet only **£2.95**  
**DECCA DC1000 Stereo Cassette Record deck P.C.B.** complete with switch oscillator coils and tape heads and circuit diagrams. **£36.00**  
**AM. FM. STEREO MULTIPLEX CAR RADIO/CASSETTE** player in dash fixing Negative earth 5 watts output **£18.95**  
I.C. Stereo 8 Track to Cassette adaptor converts any 8 track player to cassette player.

## BSR TURNTABLES

**BSR MP60 TYPE**  
Single play record player (Chassis form) **£15.95**  
less cartridge. P & P £2.55

Cartridges to suit above  
**ACOS MAGNETIC STEREO** £4.95  
**CERAMIC STEREO** £1.95

**BSR automatic record player deck (Chassis form)** with cueing device and stereo ceramic head. P & P £2.55 **£9.95**

**TURNTABLE illus.** diamond stylus, and de luxe plinth and cover. **£29**  
Popular BSR MP 60 type, complete with magnetic cartridge. Ready wired **★ P & P £4.50**

## 30 x 30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed. Cabinet is finished in teak veneer. Silver fascia and easy-to-handle aluminium knobs: **£29.00**  
Output 30 + 30 watts rms, 60 + 60 peak. **£35.00** + P & P £2.50

## DECCA 20 WATTS STEREO SPEAKER

This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters comp with crossover networks. **£20.00**  
£4.00 P & P stereo pair

(Order giving your credit card number ONLY)

**ALL PRICES INC. VAT AT 12 1/2%**  
GOODS NOT DESPATCHED OUTSIDE UK  
All items subject to availability. Price current 1/29/77 and subject to change without notice.  
We are unable to show all our products so

Send stamped addressed envelope for further details.

**RTVC**

323 EDGWARE ROAD, LONDON W2  
Personal Shoppers EDGWARE ROAD 3 30am - 5 30pm, Half Day Thurs  
21D HIGH STREET, ACTON, LONDON W3 6NG  
ACTON: Mail Order only No callers

## PORTABLE MONO DISCO



with built-in pre-amplifiers  
Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. P & P £6.50  
Simply connects into your existing slave or external amplifier. **£64.00**

## 45 WATT MONO DISCO AMP

**£35.00**

+ P & P £2.50

Size approx. 13 1/2" x 5 1/2" x 6 1/2"

Here's the mono unit you need to start off with. Gives you a good solid 45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. **£57**  
lets YOU hear next disc before fading 70 watt it in. VU meter monitors output level. 100 watt Output 100 watts RMS 200 watts peak. P & P £4.00 **£65**

## 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"

Sloping fascia, you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth acting, vertically mounted slide controls — master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading 70 watt it in. VU meter monitors output level. 100 watt Output 100 watts RMS 200 watts peak. P & P £4.00 **£57**

## BSR BDS95 TYPE

Belt drive turntable unit. 2 speed, semi automatic operation **£24.95**  
+ P & P £2.55

## PRACTICE GUITAR AMPLIFIER WITH BUILT-IN SPEAKER

This budget practice amplifier, has been specially designed for the amateur, who requires a quality self-contained unit with all facilities. 2 inputs — 1 for mic or guitar, the 2nd for record player or cassette deck, it also can be used for cine-sound amplification. 2 volume controls, 1 for each input, also base and treble controls. Power output with internal speaker, 10 watts RMS, with remote speaker (not supplied) 20 watts **£32.50**  
RMS. Size approx. 17" x 9" x 11" + P & P £3.00

## HOME 8 TRACK CARTRIDGE PLAYER

Automatically switches programmes monitored by indicators, with manual override track selection. This unit will match with the Unisound modules and is compatible with the Viscount IV amplifier with Sim teak cabinet, approx. 9" x 8" x 3 1/2". P & P £2.50 **£16.50**  
Output 125 Mw

## PYE STEREO GRAM CHASSIS

(Complete with circuit diagrams)  
Complete ready to install — Wave bands LM, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S. per channel 14 watts peak 8 ohms. 2" x 8" approx chassis speakers and BSR auto record player deck. **PERSONAL SHOPPERS ONLY £35.00**

# V.D.U./MACRO COMPUTER - With so many features

Look at these features

- \* Rock Steady Pictures
- \* Crystal Controlled
- \* Expandable Number of Lines
- \* Telephone Interface
- \* Tape Programmable
- \* Software Available
- \* Ideal for Education
- \* Expandable Memory
- \* Games and Things on Tape
- \* Ready-Built or in Kit Form
- \* Video or UHF Output
- \* Selectable Flashing Characters
- \* Forward and Reverse Typing Mode
- \* Repeat Facility
- \* Tab Key
- \* Automatic Tape Stop/Start



COME ALONG AND PLAY MASTERMIND or S.A.E. FOR INFORMATION

## Crofton Electronics Limited

35 GROSVENOR ROAD, TWICKENHAM  
MIDDLESEX  
Tel: 01-891 1923

### PROGRESSIVE RADIO

**MM5316 Clock Chips £3.50**  
200 pf twin solid dielectric variable caps 1/2 spindle 35p  
Grundig electret mike inserts with F.E.T. preamp £1.50  
**PL259 plugs with reducer 55p**  
S0239 sockets single hole or standard mtg 40p  
12 volt reed relay 4 make 20p  
12 volt sealed relay 3 pole n/o 1 pole n/c 1 pole c/o 2 amp contacts 1300 coil 65p  
Bulgin roller micro 15p  
Toko 465 KHz AM I.F. panels new 30p  
12 VDC 6 pole motor, 35p  
Savitt 500 gram cored solder per reel £2.80 + 35p P&P  
Stereo preamp chassis with controls ceramic input with circuit £3.80 + 50p P&P  
1 pole 20 way 2 bank stud winker switches, adj. stop 75p  
300 KHz HCGU crystals 40p  
500 mtr reels twin solid core connecting wire £4.00 + 85p P&P  
CV2184 2 1/2" C.R.T. with P.D.A. £1.95 + 80p P&P  
1:1 triac pulse transformers 30p  
6 MH 3 amp smoothing chokes 30p  
6-12v DC G.P.O. buzzers 30p  
6-12 volt hooters 50p  
Board with 6 volt change over reed relay £1.75  
G.P.O. board with 64 BC107 type transistors, 2 reed and 1 mercury relays, diodes, etc. £2.00 + 75p P&P  
Newmarket power supply 240v AC input 8 volts DC output at 250mA £1.35  
Crystal microphone insert 37 m/m 60p  
Bridge rectifier 500v 600mA ex. equip. 10 m/m cube 25p  
Long + medium wave serials 1/2" x 8" 40p  
240v AC solenoid 45p  
12v DC solenoid heavy duty 75p  
Tung Hal. bulbs 24 volts 250 watts, ex. equip. 30p  
100-0-100vA level meters 75p  
Stereo tuning meters 100  $\mu$ A per movement £2.75  
4-43 MHz Colour TV crystals 45p  
Veeeder root 3 digit reset counter 240v AC. £1.95  
Adj. table humidity switch, 80p  
Curly leads 7 core heavy duty, 8 foot max. 30p  
50v AC geared motor driving 24 way stud contact switch 85p  
Connecting wire 5 x 5 yard lengths multi colours 30p  
**B.S.R. 3" TAPE HEADS**  
MN1330 1/2 track dual imp record/playback 60p  
SRP90 1/4 track stereo record playback £1.95  
TD10 dual head assemblies 1/4 track record playback staggered stereo with built in erase, per head £1.20  
45E and 1/4 track erase heads 30p  
Mono cassette heads Jap 90p  
Postage 25p on orders under £2.00, 35p postage and packing on orders over £2. Unless otherwise shown V.A.T. included in all prices.

ORDER ADDRESS: PROGRESSIVE RADIO, 31 CHEAPSIDE, LIVERPOOL 2.

### CRESCENT RADIO LTD.

MAIL ORDER DEPT.

1 ST. MICHAELS TERRACE, WOOD GREEN,  
LONDON N22 4SJ  
PHONE: 888-4474

**POPULAR HIGH POWER AMPLIFIER**  
70 watts R.M.S continuous into 8 ohms. Ready to use. S.A.E. for further details. Size: 540mm x 250mm x 145mm approx. Cost: £71 + 8% V.A.T.

#### PIEZO ELECTRIC HORN UNITS

New High Quality. High Power tweeter (100 watts). No Xover required. Freq. response: 3-8kHz to 28kHz. Spec. sheet sent on receipt of S.A.E.  
Our price: £9.75 each + 8% V.A.T.



#### CLEAR PLASTIC PANEL METERS (FULL SCALE)

Size: 50 x 46 x 35mm. These meters require a 38mm dia. hole for mounting.  
ME 6 = 0-50uA ME13 = 0-100mA  
ME 7 = 0-100uA ME14 = 0-500mA  
ME 8 = 0-500uA ME16 = 0-50V DC  
ME 9 = 0-1mA ME17 = 0-300V AC  
ME10 = 0-5mA ME18 = 'S' METER  
ME11 = 0-10mA ME19 = 'VU' METER  
ME12 = 0-50mA

Our Price: £5.00 + 8% V.A.T.

#### "CRESCENT" 100 WATT R.M.S. AMPLIFIER KIT

This kit consists of three modules, power amp. module, pre-amp. module and power supply module including mains transformer. Requires no technical knowledge as full instructions are supplied. S.A.E. for further details.  
Limited Stock—Buy Now While Stocks Last. Cost: £30 + 8% V.A.T.

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E. WITH ALL ENQUIRIES PLEASE

Personal callers welcome at: 164-166 High Road, Wood Green, N22. Phone: 888 3206 and 13 South Mall, Edmonton N9. Phone: 803 1685

#### EFFECTS PROJECTOR "150" (150 watt)

Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6in. Liquid Wheel. Ready to use.

A bargain at £34 + 8% V.A.T.

#### 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT (1000 Watt per channel)

Three channel: Bass, Middle, Treble. The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display.  
Full instructions supplied or S.A.E. for details.  
Fantastic Value at £20.00 + 8% V.A.T.

#### LOUDSPEAKER SELECTION + 12 1/2% V.A.T.

2 1/2in. 8, 40, and 75 ohm at £1.10 (please state which impedance is required)  
5in. 8 ohm Ceramic at £1.70  
8in. Goodmans "Audiom 8PA" 8 ohm 15W £5.25.  
10in. "ELAC" Dual Cone 8 ohm 10 watt at £4.75

### For Semi-Conductors

including  
Small Signal Transistors  
Power Semi-conductors  
TTL, CMOS, I.C.s  
Linear I.C.s  
Signal and Power Diodes  
Zener Diodes  
Magneto Resistors  
Hall-effect devices  
Magnetic Proximity Switches  
Opto-electronic devices

Go to

**ELECTROVALUE**

TO MAKE THE BEST OF

### For passive components

including  
Plastic Film Capacitors  
Electrolytics  
Semi-precision capacitors  
Transformers  
Pot Cores  
R. M. Cores  
Ring Cores, etc.

Go to

**ELECTROVALUE**

THE PROJECTS YOU BUILD

### The Open Door to Quality

It's the Electrovalue Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated. 40p post free with 40p voucher usable on orders for £5 or more. Send for yours now and order in confidence.  
**GOODS SENT POST FREE IN U.K. FOR C.W.O. ORDERS.** Keenly competitive prices plus **ATTRACTIVE DISCOUNTS** and only best quality goods.

**ELECTROVALUE LTD**

(Dept. PE11) 28 St. Jude's Road, Englefield Green,  
Egham, Surrey TW20 0HB.  
Tel. Egham 3603. Telex 264475.  
North: 680 Burnage Lane, Burnage, Manchester.  
Tel. (061) 432 5945

# You can work wonders with your free time.

There's immense satisfaction in making your own equipment. And you'll get excellent results with Heathkit.

Every kit is absolutely complete down to the last nut and bolt. The quality is the best. And each kit has an easy to follow instruction manual that explains exactly what to do at each step.

So you enjoy assembling your kit and you finish with first-class equipment every time.

That's why Heathkit are so successful. And that's why the range is the biggest in the world.

It's all in the new edition of the free Heathkit catalogue. Everything from the simplest to the most sophisticated. Alarms, digital clocks, testers, transceivers and lots more... even the tools are there!

See for yourself. Send the coupon now.


## NEW CATALOGUE

## NEW TEST INSTRUMENTS

## NEW DIGITAL BATHROOM SCALES

## NEW AMATEUR RADIO EQUIPMENT
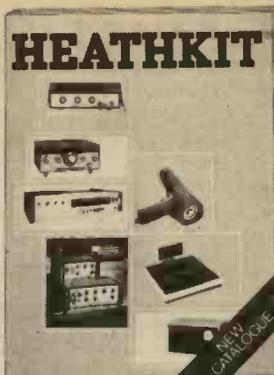
## NEW AUDIO SYSTEMS AND MANY OTHER NEW ITEMS



**The new Heathkit catalogue. Out now FREE.**

To: Heath (Gloucester) Ltd., Dept. PE 127, Gloucester, GL2 6EE. Please send me my Heathkit catalogue. I enclose an 11p stamp for postage.



Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

**ACCESS AND  
BARCLAY CARD  
WELCOMED**

Showrooms at 233 Tottenham Court Road, London (Phone 01-636 7349) and Bristol Road, Gloucester (Phone Gloucester 29451).

### T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD etc

7400 14p	7426 25p	7473 30p	74121 25p	74151 65p	74179 140p
7401 14p	7427 25p	7474 30p	74122 40p	74153 65p	74180 100p
7402 14p	7428 40p	7475 30p	74123 60p	74154 120p	74181 200p
7403 14p	7430 15p	7476 30p	74125 50p	74155 70p	74182 75p
7404 14p	7432 25p	7483 85p	74126 50p	74156 70p	74184 150p
7405 14p	7437 25p	7485 100p	74130 130p	74157 70p	74185 150p
7406 40p	7438 25p	7486 30p	74131 100p	74160 90p	74188 350p
7407 40p	7440 15p	7489 250p	74132 65p	74161 90p	74189 350p
7408 20p	7441 85p	7490 35p	74135 100p	74162 90p	74190 140p
7409 20p	7442 65p	7491 75p	74136 60p	74163 90p	74191 140p
7410 15p	7445 80p	7492 45p	74137 100p	74164 125p	74192 120p
7411 20p	7446 85p	7493 40p	74138 125p	74165 125p	74193 120p
7412 20p	7447 75p	7495 60p	74139 100p	74166 125p	74194 100p
7413 30p	7448 70p	7496 70p	74141 60p	74167 325p	74195 100p
7414 60p	7450 15p	74100 95p	74142 270p	74170 200p	74196 100p
7416 30p	7451 15p	74104 40p	74143 270p	74173 150p	74197 100p
7417 30p	7453 15p	74105 40p	74144 270p	74174 100p	74198 185p
7420 15p	7454 15p	74107 30p	74145 75p	74175 75p	74199 185p
7422 20p	7460 15p	74109 50p	74147 230p	74176 100p	
7423 25p	7470 30p	74118 90p	74148 160p	74177 100p	
7425 25p	7472 25p	74120 90p	74150 120p	74178 140p	

### CMOS

4000 20p	4030 60p
4001 20p	4032 150p
4002 20p	4043 220p
4006 120p	4046 150p
4007 20p	4047 115p
4009 70p	4049 70p
4011 20p	4050 50p
4012 20p	4054 130p
4013 55p	4055 140p
4015 90p	4056 145p
4016 55p	4060 130p
4017 110p	4066 55p
4018 250p	4069 30p
4020 140p	4071 30p
4022 180p	4072 30p
4023 20p	4081 20p
4024 100p	4082 30p
4025 20p	4510 145p
4026 200p	4511 200p
4027 85p	4516 140p
4028 155p	4518 110p
4029 130p	4528 130p

### SPECIAL OFFERS

IN4148 100 for £1-50  
555 Timers 35p each (100 for £30-00)  
741 op. amps. 25p each (100 for £20-00)  
7410 I.C.'s 10 for £1-00 (100 for £9-00)

PLEASE NOTE ALL PRICES INCLUDE POSTAGE AND VAT AT 8 OR 12% AS APPROPRIATE

### MULLARD POT CORES

LA3 100-500kHz 75p  
LA4 10-30kHz 100p  
LA5 30-100kHz 100p  
LA7 8 10kHz 100p  
LA13 for W.W. Oscilloscope 200p

### WIRE WOUND RESISTORS BY VTM

5K 9 Watts  
10 for £1-00  
100 for £6-00  
1,000 for £50-00  
10,000 for £400-00

## NEW FROM CASIOTRON

Casiotron watches are probably the success story of the decade and rightly so! We proudly announce a new range of these superb quality watches at lowest ever prices. They all have a constant liquid crystal display of hours, minutes, seconds, AM-PM/day, date and month, with night illumination and automatic 28, 30 and 31 day calendar. In new ultra slim Stainless Steel cases, with mineral glass face, they are anti-magnetic, shock-resistant and water resistant to 100 feet. Most have a Stopwatch (ST) from 1 second to 13 hours and some also have Dual Time Zone (TM), second time memory. Display life expectancy of over 6 years. Can be easily changed at low cost.



LADIES MODEL 27CL-10B £49-95. Available soon; ALARM WATCH with stopwatch.

Many other digital and quartz analogue watches. Stopwatches, clocks, car clock, T/V games, Casio scientific calculators. Accurist, Citizen, Ibcico, N-S, Fairchild Timeband etc. Send 15p for our illustrated catalogue. Lowest discount prices. Prices include VAT, P & P. Send cheque, P.O. or phone your credit card number to:-

Dept. P.E.  
19/21 Fitzroy Street  
Cambridge CB1 1EH  
Telephone (0223) 312866

# TEMPUS

## XEROZA RADIO

306 ST. PAUL'S ROAD,  
HIGHBURY CORNER, LONDON N.1

Telephone: 01-226 1489

Easy access to Highbury via Victoria Line (London Transport) British Rail



# SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.00 per single column centimetre. All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

## NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## RECEIVERS AND COMPONENTS

### TTL at NEW LOW PRICES INCLUDING VAT!

All full spec. by famous manufacturers

7400	13p	7460	15p	74141	58p
7401/2/3	14p	7472	22p	74145	69p
7404/5	16p	7473/4/6	27p	74150	£1.09
7406	32p	7475	43p	74151	64p
7408	18p	7480	38p	74153	63p
7410/20	14p	7483	70p	74154	£1.08
7411	18p	7484	90p	74155	67p
7412	26p	7485	£1.00	74157	64p
7413	30p	7486	27p	74160	75p
7414	64p	7489	£2.20	74164	£1.06
7417	27p	7490/2/3	44p	74174	94p
7422	18p	7491	58p	74175	75p
7425/7	27p	7495	60p	74181	£2.56
7430	15p	7496	73p	74190	£1.24
7432	24p	74100	97p	74191	£1.06
7437	27p	74107	31p	74192/3	£1.00
7440	14p	74109	40p	74195	67p
7441	61p	74121	31p	74196	84p
7442	54p	74122	40p	IN4148	2p
7445/7/8	75p	74123	53p	DL707E	69p
7450/3/4	15p	74125/6	44p	2102A-6	£2.50

S.A.E. for full lists. P. & P. (1st class) 20p. C.W.O.

J. C. JONES (PE28) Mail Order only.

46 Burstellars, St. Ives, Cambs., PE17 4XX.

**DECEMBER ONLY** MJE3055, 40p; TIL209, 9p; 2102 (500NS), £1.50; 8080A, £16; MM5314, £2.95; BF195, 9p; BC213, 9p; BC183, 9p; CCP70, 16p, 7 way DIL switches 50p; 74H00 20p. Timers in 11 pin relay case, 13-5 secs-5 mins approx + PCB Base 65p, P & P. 10p. LB ELECTRONICS, 43 Westcott, Hayes, Middx UB4 8AH.



## SPECIAL OFFERS.

Buy NOW while stocks last. PRICES INCLUDE V.A.T.

RESISTORS 1/2W 5% carbon film E24 range 10R-1M.			
2p each, 100 of one value £1.05, 1000 of mixed 100's		£8.95	
E12 series pack 10R-1M, 10 of each value (610 resistors)		£6.40	
E24 series pack 10R-1M, 10 of each value (1210 resistors)		£12.70	
E12-E24 expansion packs 10 of each value (600 resistors)		£6.30	
TRANSISTORS			
BC107/8/9C	10p	BC182/184L	12p
BCY71	15p	BC212L	12p
2N2926Y	10p	2N2926G	11p
2N3054	48p	2N3055	48p
INTEGRATED CIRCUITS			
CA3089E IF System	£1.99	CA3090AQ Sier. Decoder	£3.99
741 8 pin DIL Op Amp	26p	748 LN Op Amp	38p
709 8 pin DIL Op Amp	27p	723 Voltage Regulator	34p
LM3900 Quad Amp	76p	LM380 2W Amp	99p
LED's Red 3 or 5mm	13p	Pack 10 LED's (seconds)	89p
RECTIFIERS IN4001	5p	1A/50V Bridge	29p
POLYESTER CAPACITORS (250V)			
0.1uF 3p, 0.22uF 4p, 0.47uF 7p, 1.0uF 12p.			

Please add 15p for Postage. Send 2 stamps for Catalogue. BARCLAYCARD phone service available. Tel. 0473 50975.

FRASER-MANNING LTD.,  
26 HERVEY STREET, IPSWICH, IP4 2ES.

BC132 10p, BC348 8p, BC351 11p, ME1075 9p, XK1152 7p. Diode 1S940 3p. Capacitors 0-1/600V 4p. Bridge 1A/50V 16p. Wirewound Resistors 0.5 OHM to 27K, 5W, 5p, 10W 6p, 15W 7p, 20W 8p. Min order £2. P & P 20p. HEWITT'S, 9 St. Peter's St., Syston, Leics.

Power Electrolytics, 800uF, 450V (Value not stamped on can), Single end connections with screw terminals. 2 1/2" dia. x 4 1/2" high inc. studs. Min. order 4 for £2 inc. VAT (add 80p P & P). Sub-Min D.I.L. Switch, 7-S.P.S.T., 0.1 Pitch ..... 50p  
Op. Amp. Motorola MC 1530G ..... 65p  
Dual Transistor, 2N 2643 ..... 50p  
Bridge Rectifier, 2A/100V, 34mm x 34mm ..... 40p  
Culet Knobs For 4mm Spindles, Black with Red Caps, 10 for £1  
Transistors. C407. NPN, High Voltage Nixie Driver..... 5 for 50p (Items 2-6, Prices include VAT. Add 20p P & P)

**LINWAY ELECTRONICS**  
843 Uxbridge Road, Hayes End, Middx. UB4 8HZ.  
Tel: 01-573-3677  
VISIT OUR SELF-SERVE RETAIL PREMISES AT THE ABOVE ADDRESS (9.45 to 6.00, Closed Weds.)

**VALVES** - Radio, TV, industrial, transmitting. We dispatch to any part of the world by return of post, Air or Sea Mail. 2,700 types in stock. 1930 to 1976 obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers. Mon to Sat. 9.30-5.00, closed Wed. 1.00. We purchase all types of new and boxed valves. COX RADIO (Sussex) Ltd., Dept. P.E., The Parade, East Wittering, Sussex, PO20 8BN. West Wittering 2023. (STD code 024366).

## TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains wiring required. Insulated Touch Plates. Easy to follow instructions. TSD300K—TOUCHSWITCH and DIMMER combined. ONE touch plate to switch light on or off. Brightness controlled by small knob—£5.20. TS300K—TOUCHSWITCH. TWO touch plates ON and OFF—£4.00. TSA300K—AUTOMATIC. One touch plate. Light turns off after preset delay—£4.00. LD300K LIGHT DIMMER KIT £2.80.

### SPECIAL OFFER

3 TRIACS 8A/400V Isolated Tab, ONLY—£2.25

TRIACS 400V Plastic	CMOS - LOW PRICES	TRANSFORMERS Miniature Mains	
3A	4001	250V 100mA	
8.5A	4007	18p	
12A	4011	18p	
16A	4013	51p	
20A	4015	91p	
6.5A with trigger	4017	91p	
Diac	81p	4040	97p
	20p	4049	50p
		C106D 5A/400V	48p

Clock 1kW Appliance Timer KIT inc. AY-5-1230, 0.5" LED, display, triac, switches, box, pcb's, etc. £16.25  
AY-5-1230 Clock/Appliance Timer IC £4.85

### QUANTITY DISCOUNTS ON REQUEST

Add 8% VAT + 25p, P. & P.

Mail order only to:

**T. K. ELECTRONICS (PE)**

106 Studley Gate Road, London W7 2LX

**TURN YOUR SURPLUS** capacitors, transistors, etc. into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 4188. Immediate settlement.

## ORCHARD ELECTRONICS

I.C.s. TTL, C/MOS. Linear. Capacitors, Resistors (E12). SIL/Rectifiers. Diodes. LED. Thyristors. Zeners. Voltage Reg. DIL Sockets. Bridge Rectifiers. Potentiometers. Presets. Triacs. Diac. Plugs. Sockets. Cable. Verob. Carefully selected range, excellent despatch service. Same day turn round. S.A.E. List. Suppliers to A.E.R.E. U.K.A.E.A. Government Depts. Schools. Universities. Manufacturers. Accounts opened for trade and amateur. Join the professionals. Phone by 4 p.m. Goods out 1st class by 5 p.m. Try us and prove it!

### ORCHARD ELECTRONICS

Flint House, High Street, Wallingford, Oxon  
Telephone 0491-3529

**COMPONENTS AND HARDWARE.** Wide range. Fast service. CATALOGUE—2 x 9p stamps. MAGENTA, PJ10, 61 Newton Leys, Burton on Trent, Staffs. DE15 0DW.

P.C.Bs Paxolin 9 1/2in x 7in, 45p. 12in x 9in 70p. 17 1/2in x 9 1/2in, £1. Fibre glass double sided 7in x 8in. 80p. 12in x 6in, £1, 12in x 12in, £1.90. 20 wire ended nets, £1-50. Five figure Resetttable Counter 18/22V, works on 12V £3.20. 20 assorted 74 series I.C.s on panel(s), £1-35. Three assorted meters £2.20. 7 lb assorted components £2-95. List 15p. Refund on purchase. Over £10 post paid; under add 20p; insurance add 15p.

J. W. B. RADIO

2 Barnfield Crescent, Sale, Cheshire, M33 1NL

**MAINS TRANSFORMERS** 240V Pri two separate secs each. 7V at 500mA. £1.30 each + 35p P & P. Two for £2.40 + 55p P & P. NF ELECTRONICS, Church Lane, Flax Bourton, Bristol.

## BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V—0.47, 1.0, 2.2, 4.7 and 10mF 5p; 22, 47 51p (50V 8p); 100 7p (50V 8p); 220 8p (50V 10p); 470 11p (50V 16p); 1,000 (16V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p. Subminiature Bead Tantalum Electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 at 35V, 4-7/25V 11p; 10/25V 13p; 22/16V, 47/6V and 100/3V 15p. Mullard Min. Ceramic E12 Series 63V 2%—10pF to 47pF—3p; 50pF to 330pF 4p. Vertical Mounting Ceramic Plate 50V—E12 series 22-1,000pF and 1/8 series 47,000pF 2p. Polystyrene E12 Series 63V Horizontal Mounting—10-1,000pF 3p; 1,200-10,000pF 4p. Mullard Polyester 250V Vertical Mounting E8 Series—0.01-0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 8p; 0.68 11p; 1.0-13p; 15 20p; 2-2 22p. Mylar (Polyester) Film 100V Vertical Mounting—0.001-0.002, 0.002 3p; 0.01, 0.02 4p; 0.04, 0.05 4p. Miniature Resistors Highstab E12 Series 5%. Carbon Film 0-25W 1Ω to 10M Ω (0.2% over 1M) 1p. Metal Film 0-125W, 0-25W and 0-5W 10 Ω to 20M Ω 1/4p. Metal Film 1W 27 Ω to 10M Ω 2p. 1N4148 3p; 1N4002 5p; 1N4006 7p; 1N4007 8p; BC107/8/9, BC147/8/9, BF157/8/9, BF194, 197 8p. Fuses 20mm glass, 1 1/2in glass, 1in ceramic 21p. Post 10p (free over £4). Prices inclusive of VAT.

**THE C.R. SUPPLY CO.**

127 Chesterfield Road, Sheffield S8 0RM

**CARBON FILM RESISTORS** 5% E12 1/4W, 1/2W, 1W. Your mix, 90p per 100. Metal Film 1/2W, £1.10/100. Mail Order Only. CANDAR, 9 Galloway Close, Bletchley.

## SOLAR CELLS

2-2 1/2" Dia. 250mW at 0.5V—£8.00  
1-00" Dia. 35mW at 0.5V—£4.50  
5-3 x 6-3mm 2-5mW at 0.5V—£1.25

Cells are supplied with leads attached and are coated with varnish. "Solar Cells" booklet 75p. Data sheets on above devices 20p. Mail Order only. Speedy service.

**EDENCOMBE LIMITED**

16 Princes Avenue, Kingsbury, London NW9 9JB

## BOOKS AND PUBLICATIONS

**YOU CAN'T HELP BUT MAKE MONEY.** If you follow the planned and detailed information on how to start your own business rewinding ARMATURES, set out in the new manual which is profusely illustrated and leads you through easily understood stages of fault diagnosis, taking data, test procedures, laying down new windings, where to obtain work, how to cost jobs etc. NO PREVIOUS ELECTRICAL KNOWLEDGE REQUIRED. Complete instruction manual £4.00 plus 30p P & P CWO. Copper Supplies, 102 Parnwood Road, Withington, Manchester 20. DEPT PEB.

**SIMPLIFIED TV Repairs.** Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique. TV PUBLICATIONS (Ausepp), 76 Church Street, Larkhall, Lanarkshire.

## LADDERS

**LADDERS.** Varnished 25 1/2ft extd. £30-41. Carr. £1-00. Leaflet. Immed. despatch. THE LADDER CENTRE (PEE), Halesfield (1), Telford, Salop. Tel. £82644.

## EDUCATIONAL

### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

#### ICS SCHOOL OF ELECTRONICS

Dept. 771A Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

#### ICS SCHOOL OF ELECTRONICS

Dept. 771A Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

#### ICS SCHOOL OF ELECTRONICS

Dept. 771A Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### COURSES—RADIO AMATEURS EXAMINATION.

City and Guilds. Pass this important examination, and obtain your G8 licence, with an RRC Home Study Course. For details of this, and other courses (GCE, Professional Examinations etc) write or phone THE RAPID RESULTS COLLEGE, Dept. J.S.1, Tuition House, London SW19 4DS. Tel. 01-947 7272 (Careers Advisory Service) or for a prospectus only ring 01-946 1102. (24hr recording service).

## FOR SALE

**NEW ISSUES** of "Practical Electronics" available from April 1974 edition up to date. Price 65p each. Post free. **BELLS TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

**SC/MP** Introkit and Keyboard Kit with power supply in case £160. Tel: Stoke on Trent 84507.

## P. E. MULTIMETER

P.C. BOARD SET £2.65 inc.  
LD130 £5.50 inc., E501's from stock.  
Complets Kits £42.50.

S.A.E. for details:  
**SPARKS DEVELOPMENTS**  
53 North Street, Melbourne, Derby.

**PRACTICAL ELECTRONICS** complete from first issue to present date. Vols. 1 to 9 in binders. Offers over £30 considered. Buyer collects. **CLOUGH**, Crawley 28669. Evenings or weekends.

**OSCILLOSCOPE** — 10MHz, Double-Beam, Full Working Order. £35. Tel: 01-472 6212.

## SERVICE SHEETS

**SERVICE SHEETS** for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, TV, etc. 70p plus S.A.E. Colour TV Service Manuals on request, S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

## WANTED

**WANTED-NEW VALVES**, Transistors. Top Prices, popular types. **KENINGTON SUPPLIES**, (B) 367 Kensington Street, Bradford 8, Yorkshire.

**WANTED FOR HARTLEY**. 13A. Oscilloscope HT Transformer. **POOLE**, Pixley, Hinstock, Market Drayton, Shropshire.

## AERIALS

**AERIALS FOR FM & TV** Types for all Bands I to V available.

**TV UHF**  
Fuba XC 391 £38.90 DX 87 Ch21-60 £22.75  
DX43 Ch21-68 £14.50 Exa08 Panel Ch21-68 £11.25  
**FM**  
Fuba Uka St. 8 £33.33 DX8-H £22.75  
DX7-H £19.00 DX5-H £12.50  
All above have anodised alloy finish. Cables, Rotators, Masts, Lashings, M/H Amps, Dist Amps etc., Carriage free mainland UK orders above £25. Carr. £1 otherwise. **Audio Workshops Ltd.** 33 London Road, Southborough, Tunbridge Wells, Kent, TN4 0PB. Tel: Tun. Wells (0892) 39222. Access/Barclaycard.

## ELECTRICAL

**STYLI, CARTRIDGES, AUDIO LEADS** etc. For keenest prices send S.A.E. for free list to: **FELSTEAD ELECTRONICS (PE)**, Longley Lane, Gatley Cheadle, Cheshire, SK8 4EE.

## MISCELLANEOUS

## BURGLAR ALARMS SUPPLIES AND EQUIPMENT



S.A.E. FOR FREE CATALOGUE

**INFRA-RED BEAMS, 36ft.**  
12V DC MODULATED BEAM  
BLACK LIGHT TRANSMITTER & RECEIVER  
ONLY £32.00 + 12½% VAT. POST FREE  
**BELLS SIRENS ALARM-UNITS CABLE**  
**BELL COVERS WINDOW FOIL VIBRATION**  
**CONTACTS ULTRASONIC AND INFRA-RED**  
**DETECTORS INERTIA SWITCHES.**

**A. D. ELECTRONICS**

217 Warbreck Moor, Aintree  
Liverpool L9 0HU. Tel. 051-525 3440

**CLEARING LABORATORY.** Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Tel. Lower Beeding 236.

## SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1-80, MOT CMOS Databk 3-50, 6800 Appl Man 12-95, 6800 Prog Man 5-35, SC/MP Introkit Man 0-75, NS TTL Databk 2-10, RCA CMOS Databk 5-45, 8085 User's Man 5-15, Z80 Ass Lang Prog Man 7-50, Z80-CPU Man 5-60, Z80-CTC Spec 0-80, Z80-P10 Man 3-30. Also a full range of CMOS—send for free catalogue. MPUs: MEK6800D2 190-00, MC6820 8-02, Z80 28-44, Z80A 36-98, Z80-CTC 12-80, Z80-P10 12-80. Memories: 2102A-6 2-36, 2112A-4 2-90. Displays: FND500 1-30, TIL321 1-50, TIL322 1-49, 5LTO1 4-90. Crystals: 32.768KHz 3-50, 5.12MHz 3-60. Clock ICs: AY51202 3-10, AY51224 3-50, MK50253 5-60. Soldercon Pins: 100 0-50, 1000 4-00, 3000 10-50. Free catalogue by return. All items CWO (Books-No VAT) add 8% VAT & 35p p&p. **SINTEL, P.O. Box 75B, 209 Cowley Road, Oxford. Tel. (0865) 49791.**

2102 memory chips. £1.60 (including Data, VAT, P & P). 10 or more £1.50 each. C.W.O. Research Resources Ltd., P.O. Box 160, Barn Close, Welwyn Garden City, Herts.

## RECHARGEABLE BATTERIES

'AA' pencil (HP7) £1.32; sub 'C' £1.64; 'C' (HP11) £2.43; 'D' (HP2) £3.92; PP3 £4.98. Matching chargers £5.91 each except PP3 charger £4.99. Charging holders for 2, 3, 4, 5 or 6 pencils 50p. 'C' and 'D' size holders, 4 cell only, 80p. 250/12 volt inverters now available.

Prices include VAT. Add 10% post, package and insurance orders under £20. PP3 £4.98. S.A.E. for full details plus 75p for 'Nickel Cadmium Power' booklet. Mail orders to:

**DEPT. PR. EL., SANDWELL PLANT LTD.**

201 Monmouth Drive, Sutton Coldfield, West Midlands. Tel. 021-354 9764  
Callers to T.L.C., 32 Craven Street, Choring Cross, London, WC2.

**8TICKIES ARE NEW** High quality IC-size self-adhesive labels printed with pin-outs for the 61 most popular 16- and 14-pin 7400-series IC's. Each pin identified immediately. For design, construction and de-bugging. Also ideal for students. Introductory offer Set of 450 £2.80 inclusive. **CONCEPT ELECTRONICS (A2)**, 8 Bayham Road, Sevenoaks, Kent.

## H. M. ELECTRONICS

275a Fulwood Road, Broomhill, Sheffield S10 3BD



Give your project that professional looking finish. Build it in a BEC. Dry transfer lettering now available...

ORION cabinet still available punched or unpunched. Send 15p (refundable) for leaflets.

**OUTSTANDING HI-FI FM TUNER.** Comprises 7 transistors superhet design with varicap tuning, AFC. Latest silicon circuitry, full coverage 88-102 MHz. Supplies built and tested with metal front panel and instruction sheet, only £9.95 + 30p P. & P. **GREGG ELECTRONICS**, 86-88 Parchmore Road, Thornton Heath, Surrey.

## THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA.

Featuring \*24 key keyboard \*Seven segment display \*Cassette interface \*Erom & Ram Expandable \*Interface Capability \*Full Documentation \*5 Volt power supply Required \*One years FREE membership of The Amateur Computer Club with every purchase\*. £176 + £1.50 P & P + 8% VAT.

## ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
14-19	2.60	1.40	.66	.55
20-29	2.80	1.60	.85	.65
30-34	3.00	1.70	.95	.70
35-40	3.35	1.90	1.10	.79
40-43	4.50	2.50	1.90	1.25
44-46	5.00	3.00	2.10	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb. Multicore 60/40 Solder 18SWG £3.24 per lb. Prices include P & P and VAT.

SAE brings list of copper and resistance Wires.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30 London E.4.

Reg. Office, 22 Coningsby Gdns.

## CABINET FITTINGS

FOR Stage Loudspeakers and Amplifier Cabs  
Fretcloths, Coverings, Recess Handles, Strap Handles, Feet, Castors, Locks and Hinges, Corners, Trim, Speaker Bolts, etc., etc.

Send 2 x 9p Stamps for samples and list.

**ADAM HALL (P.E. SUPPLIES)**

Unit Q, Starline Works, Grainger Road Southend-on-Sea, Essex.

**SUPERB INSTRUMENT CASES BY BAZELLI**, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

## MAKE YOUR OWN PRINTED CIRCUITS

**RUB-ON TRANSFERS** — Starter pack (5 sheets, lines, pads, I.C. pads) £1.30, Single Sheets 27p. **FERRIC CHLORIDE** — 1 lb bags 70p (P. & P. 40p).  
**SOLDERCON SOCKETS** — 100 65p. (quantity rates). **PLASTIC SUPPORTS** — 7 or 8 hole 6p./pair. S.A.E. lists sample, P. & P. 15p/order except\*.

**P.K.G. ELECTRONICS**

**OK LODGE, TANSLEY, DERBYSHIRE**

## BUILD YOUR OWN TV CAMERA



ONLY KNOWN HIGH PERFORMANCE SOLID STATE CAMERA IN KIT FORM. Also available factory assembled. Ideal for experimenters, industry security, education etc. \*Will work with most other CCTV equipment. \*Fully guaranteed. \*Completely self-contained. With our modulator will connect to any domestic TV set. Model C1 complete with Vidicon £99. Less Vidicon £82.35. (Lens available as optional extra). SAE for info or phone your order through using your Barclay or Access Card.

**CROFTON ELECTRONICS LIMITED**  
35 Grosvenor Road, Twickenham, Middlesex. 01-891 1923

**INVENTORS.** "Profit from Your Invention". Sources of Finance and other assistance. Details: Large S.A.E. DELTA (PE), 15 St. Mary Street, Southampton, Hants.

### GAS-SMOKE SENSORS COMPLETE CIRCULAR UNITS

Brand New uses TGS 105 sensor runs from 24V DC supply. Can be modified to 12 volt identical unit described in P/E Sept '76 complete with Data + Mod Sheets £12.96. IC's 555 Timer 45p. 5-za 739 dual preamp ceramic 14 pin DIL. IC's £1.50. 5-TILL 116 Opto isolator 6 pin DIL £1.50.

TRANSISTORS 10 AC128 £1.50 10 AC176 £1.50 10 AC188 £1.50 any mixture. All devices are full spec and guaranteed.

No remarks. Quantity discounts available on request. Also a few C/MOSS CD4001 in packs of 25 for £3 per pack in antistatic tube unsealed. PROMPT DELIVERY. All prices include VAT + P & P. TO: RF SERVICES, 50-51 Deptford Broadway, London SE8. Telephone 01-692 4284.

100 WATT GUITAR/PA/Music Amplifier superb treble bass overdrive slimline solidstate 12 months guarantee unbeatable offer at £39. Money returned if not absolutely delighted within 7 days. Send cheque or P.O. to: WILLIAMSON AMPLIFICATION, 62 Thorncliffe Avenue, Dukinfield, Cheshire.

#### ARMATURE AND COIL WINDING

ENAMELLED COPPER WIRE  
Only top quality materials supplied.  
All orders despatched within 24 hours.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices inclusive of P. & P. in U.K.

#### COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20 Telephone 061-445 8753

### GLASS FIBRE P.C.B.'s

From your own tape, film or ink master. Send S.A.E. for quotation.

PRACTICAL ELECTRONICS P.C.B.'s in glass fibre, tinned and drilled. Complete set of Radio Control boards, June to Aug. 76 £5.80p. Cross Hatch Generator £2.85p.

April 77 Digital Volt Meter (G8CZW). Complete set of two boards (1304-3/4) £1.75. May 77 Burglar Alarm (1305-1) £1.68. June 77 Sports Centre (1306-1) and power supply p.c.b. £2.66. July 77 Digital Stopwatch (1307-1) £1. Oscilloscope trace doubler 95p. Earth Leakage C.B. (1307-2) £1.96p. Aug. 77 C/R Meter (1308-1) 97p. Sept. 77 Freq. Counter Timer (1309-2/3) £3.98 set of two boards. Scope Probe (1309-1) 56p. Oct. 77 Digital Multimeter (1401-1/2) £2.94. set of two boards. Guitar Sustain (1410-3) 55p. Send S.A.E. for information on current boards and a full list. C.W.O. please.

### PROTO DESIGN

4 Highcliffe Way, Wickford, Essex SS11 8LA

**BURGLAR ALARM** equipment, safes, trade supplies. ASTRO-ALARMS, 25 Stockton Rd., Sunderland. Tyne and Wear. Tel.: 77825. Free list S.A.E.

### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

### BOFFIN PROJECTS

Cunliffe Road, Stoneleigh Ewell, Surrey (P.E.)

PRINTED CIRCUIT BOARDS supplied in glass fibre, drilled, tinned or varnished, from your own or published designs. Send S.A.E. for quotations. UNIVERSAL APPLICATIONS, 12 Whiteoaks Road, Oadby, Leicester.

## BUILD THE TREASURE TRACER



### MK III Metal Locator

- Variable tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete Kit £15.95 Built and tested £20.95  
Post £1.20 - £1.37 VAT Post £1.20 - £1.77 VAT

MINIKITS ELECTRONICS 6g CLEVELAND ROAD LONDON E18 2AN (Mail Order Only)

## NOTICE TO READERS

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.*

### ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for ..... insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager

PRACTICAL ELECTRONICS

GMG, Classified Advertisement Dept., Room 2337,

King's Reach Tower, Stamford Street,


London SE1 9LS.

Telephone 01-261 5846

Rate:

18p per word, minimum 12 words. Box No. 60p extra.

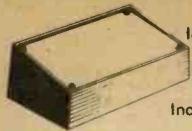Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.



### MINI CONSOLES

Ideal for small desk control panels and consoles. Moulded in orange, blue, black and grey ABS. Incorporates slots for holding 1.5mm thick pcb's

Aluminium panel sits recessed into front of console and held by screws running into integral brass bushes.

MC 161 x 96 x 58mm £1.53 (1-9) £1.50 (10+)

MC 215 x 130 x 75mm £2.20 (1-9) £2.17 (10+)

Add 25p per £1 order value for Post & Packing

### ECONOMY QUALITY LED's

50 for only £5 - 100 for only £9  
Mixed bags, all sizes, various colours

### FULL SPECIFICATION LED's



Red (specify size) 75p per pack

Green, Yellow, Orange (specify size) £1.20 per pack

(Each pack contains 5 LED's, Mounting Clips and Data)

### TYPE A NEON INDICATORS


Supplied with resistor for 240 Volts operation  
Held in 8mm hole by plastic bezel  
150mm wire leads




Red, Amber, Clear, Opal 19p each  
Green 28p each
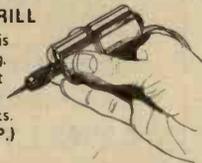
### 12 VOLTS MINI HAND DRILL

Ideal for drilling pcb, chassis etc as well as model making. Supplied with 2 collets that accept tools and drills with 3/32" and .050" dia. shanks. £7.56 (Includes VAT & P.P.)



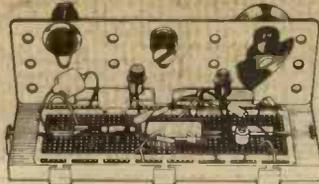Stop wasting time soldering  
The NEW MW BREADBOARD accepts Transistors, LED's, Diodes, Resistors, Capacitors and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has over 400 individual sockets, plus Vcc and Ground Bus Strips  
Price £9.72 (includes VAT & P.P.)

### TYPE MP NEON INDICATOR

Supplied with resistor for 240 Volts operation  
150mm leads, held in 6.4mm hole by nut



Red, Amber, Clear, Opal 20p each

### SEVEN SEGMENT DISPLAYS

Economy Quality  
Common Anode - 0.3" - Left Decimal  
Red, Yellow and Green @ 45p each

Full Specification  
Common Anode - 0.3" - Left Decimal  
Red @ 98p each  
Green and Yellow @ £1.35 each  
(Data supplied with Full Spec. displays only)



### Quantity quotations on request


P.P. Note Unless included in price add 25p Post & Packing for orders totalling under £10. All prices include VAT and are valid in UK only for 2 months from journal issue date

## Michael Williams Electronics

47 Vicarage Av. Cheadle Hulme, Cheshire SK8 7JP
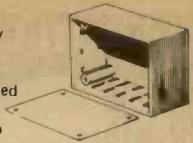
### SC BDXES (square corners)

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of the box and held by screws running into integral brass bushes.



SC 85 x 56 x 35mm 80p (1-9) 77p (10+)


SC 111 x 71 x 48mm £1.07 (1-9) £1.04 (10+)

SC 161 x 96 x 59mm £1.49 (1-9) £1.46 (10+)

Add 25p per £1 order value for Post & Packing
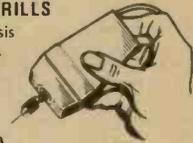
### 240 VOLTS MINI HAND DRILLS

Ideal for drilling pcb's, chassis etc as well as model making. Supplied with 3 collets that accept tools and drills with 1mm, 2mm and 1/8" dia shanks.




£9.72 (includes VAT & P.P.)

Accessory tools... 5 Burrs, 1mm, 2mm, 1/8th Drills, 3/32" Collet Price £1.75 (Includes VAT & P.P.)
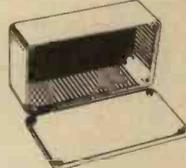
### RC BOXES (round corners)

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Close fitting flanged lids held by screws running into integral brass bushes.



RC 100 x 50 x 25mm 51p (1-9) 49p (10+)

RC 112 x 62 x 31mm 59p (1-9) 52p (10+)

RC 120 x 65 x 40mm 68p (1-9) 62p (10+)

RC 150 x 80 x 50mm 77p (1-9) 74p (10+)

RC 190 x 110 x 60mm £1.33 (1-9) £1.30 (10+)

### Polystyrene version

in grey only with no slots, no integral brass bushes  
RC(P) 112 x 61 x 31mm 35p (1-9) 32p (10+)

Add 25p per £1 order value for Post & Packing

# P.E. JOANNA

## ELECTRONIC PIANO



### ALL PARTS CAN BE SUPPLIED

Keyboard, Keyswitch, P.C.B.s, Hardware, Semiconductors, Resistors, Capacitors, Cabinets  
Complete kits or easy stages  
Send S.A.E. for details

## Clef Products

16 Mayfield Road  
Bramhall, Stockport, Cheshire SK7 1LY


## CHINAGLIA DINO—ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

### PRESENT THE
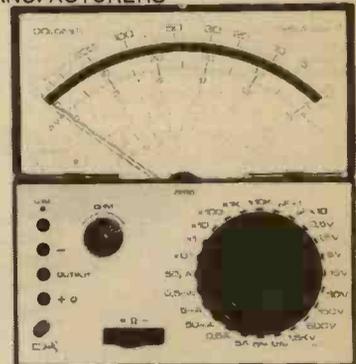
## DOLOMITI

20kΩ/V a.c. and d.c.

A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED



Accuracy: D.C. ranges, ± 2.0%, A.C. & Ω ranges ± 2.5%

39 ranges: d.c. V, 0-150mV, 500mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1-5kV;  
d.c.I, 0-50μA, 500μA, 5mA, 50mA, 0-5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1-5kV; a.c.I, 5mA, 50mA, 0-5A, 5A; dB - 10 to + 65 in 6 ranges; Ω 0-0.05kΩ, 5kΩ, 50kΩ, 500kΩ, 5MΩ, 50MΩ, pF 50kpF, 500kpF.

Automatic overload protection and high current range fusing.

Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £45.90 incl. VAT (£1 P. & P.)

30kV Probe £12.85 incl. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

# ALCON Instruments Ltd.

19 MULBERRY WALK. LONDON SW3 6DZ TEL: 01-352 1897

PLEASE MENTION  
**PRACTICAL ELECTRONICS**  
WHEN REPLYING  
TO ADVERTISEMENTS

<b>TTLs by TEXAS</b>	<b>CMOS I.C.s.</b>	<b>OP. AMPS.</b>	<b>MEMORY I.C.s.</b>	<b>LOW PROFILE DIL SOCKETS BY TEXAS</b>	<b>TRANSISTORS</b>	<b>DIODES</b>	<b>BRIDGE RECTIFIERS</b>
7400 14p 7411 80p 7401 14p 7412 216p 7402 18p 7418 180p 7403 18p 7419 225p 7404 24p 7420 130p 7405 25p 7421 32p 7406 43p 7422 52p 7407 43p 7423 75p 7408 22p 7424 75p 7409 22p 7425 85p 7410 18p 7428 82p 7411 28p 7432 82p 7412 25p 7436 81p 7413 40p 7437 81p 7414 88p 7442 300p 7416 40p 7445 95p 7417 40p 7447 205p 7420 18p 7450 130p 7421 43p 7451 81p 7422 28p 7452 80p 7423 38p 7453 81p 7425 33p 7454 80p 7426 43p 7456 97p 7427 40p 7457 97p 7428 40p 7458 97p 7430 18p 7460 90p 7432 37p 7461 130p 7433 43p 7462 130p 7437 37p 7463 130p 7438 37p 7464 130p 7440 18p 7465 150p 7441 85p 7466 160p 7442 75p 7467 320p 7443 120p 7470 260p 7444 120p 7472 75p 7445 108p 7473 130p 7446 108p 7474 130p 7447 75p 7475 97p 7448 85p 7476 130p 7450 18p 7477 100p 7451 18p 7480 160p 7453 18p 7481 320p 7454 18p 7482 150p 7460 15p 7484 250p 7470 38p 7485 190p 7472 32p 7486 130p 7473 36p 7490 140p 7474 37p 7491 140p 7475 43p 7492 120p 7476 37p 7493 100p 7480 54p 7494 160p 7481 108p 7495 110p 7482 90p 7496 130p 7483 99p 7497 130p 7484 108p 7498 270p 7485 102p 7499 210p 7486 36p 7501 175p 7489 34p 7502 150p 7490 36p 7505 97p 7491 90p 7507 320p 7492 58p 7509 30p 7493 36p 7510 220p 7494 30p 7511 175p 7495 75p 7512 250p 7496 90p 7513 84p 7497 200p 7514 160p 74100 140p 7516 220p 74104 75p 7517 160p 74105 75p 7518 160p 74107 36p 7519 160p 74109 80p 7520 220p 74110 80p 7521 220p 74111 75p 7522 250p	7400 14p 7411 80p 7401 14p 7412 216p 7402 18p 7418 180p 7403 18p 7419 225p 7404 24p 7420 130p 7405 25p 7421 32p 7406 43p 7422 52p 7407 43p 7423 75p 7408 22p 7424 75p 7409 22p 7425 85p 7410 18p 7428 82p 7411 28p 7432 82p 7412 25p 7436 81p 7413 40p 7437 81p 7414 88p 7442 300p 7416 40p 7445 95p 7417 40p 7447 205p 7420 18p 7450 130p 7421 43p 7451 81p 7422 28p 7452 80p 7423 38p 7453 81p 7425 33p 7454 80p 7426 43p 7456 97p 7427 40p 7457 97p 7428 40p 7458 97p 7430 18p 7460 90p 7432 37p 7461 130p 7433 43p 7462 130p 7437 37p 7463 130p 7438 37p 7464 130p 7440 18p 7465 150p 7441 85p 7466 160p 7442 75p 7467 320p 7443 120p 7470 260p 7444 120p 7472 75p 7445 108p 7473 130p 7446 108p 7474 130p 7447 75p 7475 97p 7448 85p 7476 130p 7450 18p 7477 100p 7451 18p 7480 160p 7453 18p 7481 320p 7454 18p 7482 150p 7460 15p 7484 250p 7470 38p 7485 190p 7472 32p 7486 130p 7473 36p 7490 140p 7474 37p 7491 140p 7475 43p 7492 120p 7476 37p 7493 100p 7480 54p 7494 160p 7481 108p 7495 110p 7482 90p 7496 130p 7483 99p 7497 130p 7484 108p 7498 270p 7485 102p 7499 210p 7486 36p 7501 175p 7489 34p 7502 150p 7490 36p 7505 97p 7491 90p 7507 320p 7492 58p 7509 30p 7493 36p 7510 220p 7494 30p 7511 175p 7495 75p 7512 250p 7496 90p 7513 84p 7497 200p 7514 160p 74100 140p 7516 220p 74104 75p 7517 160p 74105 75p 7518 160p 74107 36p 7519 160p 74109 80p 7520 220p 74110 80p 7521 220p 74111 75p 7522 250p	OP310 100p 709 CA3140 100p 733 CA3160 120p 741 LM301A 40p 747 LM318 175p 748 LM324N 130p 776 MC1458P 75p 3900	NE540 140p NE550 40p NE560 150p NE562B 25p NE565 75p NE568 85p NE567 250p RC4151N 75p SN72710N 200p SN7603N 87p SN7608 250p SN7613N 425p SN7613DN 400p SN7618 175p SN76023N 112p LM3801N 190p TAA621A 310p TAA651A 150p TBA120 97p TBA21B 190p TBA51 110p TBA80 490p TBA81 112p TDA2020 180p TDA14 160p ZNA25E 420p	AC125-6 20p AC127-8 20p AC176 20p AC187-8 20p AD149 80p AD161 45p AC162 30p AF114/5 30p AF116/7 20p AF127 40p AF139 40p AF238 40p BC107/B 10p BC108/B 10p BC109 10p BC109C 11p BC147 9p BC148 8p BC156 11p BC169C 15p BC172 11p BC177 20p BC178 17p BC179 20p BC182/3 12p BC184 14p BC187 12p BC212 14p BC213 12p BC214 14p BC167 12p BC478 32p BCY70 20p BCY71 20p BD134 140p BD135/6 54p BD139 36p BD140 60p	BDY56 225p BF115 24p BF181 25p BF170 50p BF173 27p BF178 30p BF190 35p BF180-1 30p BF184/5 24p BF194 13p BF195 11p BF196 17p BF197 19p BF200 40p BF248 40p BF258 80p BF257 34p BF258 39p BF259 44p BF337 32p BF339 34p BF340 34p BF341 34p BF342 34p BF1000 34p	2N2928B 11p 2N2928B 11p 2N3053 12p 2N3054 12p 2N3055 12p 2N3056 12p 2N3187 12p 2N31	

### R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductor components. The stereo kit uses 22 semiconductor components. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms, 7W into 15 ohms. Response 20c/s to 30kc/s. Input 100mV. High Imp. Size 8 1/2 x 3 x 3 in. A/C mains operated.

Mono kit **£11.25** Stereo kit **£18** post 45p  
Easy to build. Full instructions supplied.

### MONO PRE-AMPLIFIER

A mains operated solid state pre-amplifier unit designed to compliment amplifiers without low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket input and output are rear located. AC mains 240V.



**£4.50 ea. - 2 for £8.** Post 50p.

### BAKER MAJOR 12 INCH £15



30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W.  
NOTE: 4 or 8 or 16 ohms available.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle, 19 x 12 1/2 in. instructions. As illustrated. **£19** Post £1.60

### "BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s. Bass Resonance 55 c/s.

GROUP "25" 12in 30W **£12** Post £1

GROUP "35" 12in 40W **£14** Post £1

GROUP 50/12in 12in 60W **£21** Post £1.60

GROUP 50/15in 15in 75W **£26** Post £1.60

Disco, Group + PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.

### BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music. 4 way mixing. Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£72** Carr. £1.50

NEW "DISCO 100 WATT" **£59** Carr. £1  
ALL TRANSISTOR AMPLIFIER CHASSIS. 2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. Made by Jennings BLACK CARRYING CABINET AVAILABLE. £9.

### PW SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1,000W channels. As featured in Practical Wireless. **£14.00**  
CABINET extra £3.

### GOODMANS CONE TWEETER

18,000 c/s. 25W 8 ohm. Price **£3.25**  
E.M.I. 5in. mid range 25W £4.95.  
E.M.I. 13 x 8in. 25W Bass Unit £10.50

### R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model. Four inputs. Treble, Bass, Master, Volume Controls. Ideal disco, P.A. or groups. S.A.E. for **£94** details. 5 speaker outputs. 3 or 8 or 15 ohm. 100V line to order. Suitable carrying case £16.50. plus £2.50 carr.

### LOW VOLTAGE ELECTROLYTICS

1 1/2, 2, 4, 5, 8, 16, 25, 30, 50, 100mF 15V 10p, 500mF 12V 15p; 25V 20p; 50V 30p; 100mF 12V 17p; 25V 25p; 50V 47p; 100V 70p; 2000mF 6V 25p; 25V 42p; 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p; 3900mF 100V £1.60; 4700mF 63V £1.20; 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.60.

### R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required. **£2.95** Post 45p

### R.C.S. POWER PACK KIT

12V, 750mA. Complete with printed circuit board and assembly instructions. **£3.35** Post 30p  
12V 300mA KIT. £3.15.

### R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE £1.45

Ideal for Mike, Tape, P.U., Guitar. Battery 9-12V or H.T. line 200-300V d.c. operation. Size 1 1/2 x 1 1/2 x 1/2 in. 25 c/s to 25 kc/s. 26 dB gain. For valve or transistor equipment. Instructions supplied.

### ELECTRO MAGNETIC PENDULUM MECHANISM 95p

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays. Teaching electro magnetism or for metronome, strobe, etc. Post 30p


### BSR HI-FI AUTOCHANGER

Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. a.c. 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE. **£12.95** All Post 75p

Single Player version **£13.50**  
BSR P128 with Magnetic Cartridge **£24.50**  
GARBARO MINI-HANDED plays all records **£9.95**  
BSR P163 BELT DRIVE DECK, less cartridge **£30**
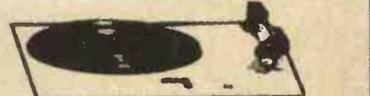
### BSR DE LUXE AUTOCHANGER

Features balanced arm. Cueing device, stylus pressure gauge. 3 speed plays all size records. Fitted with stereo ceramic cartridge. Size 13 x 12 in. **£17.50** Post £1



### R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo compatible cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable. Size 7in diameter. a.c. mains. 220/250V. 3 speeds plays all size records **£6.95** Post 45p

### HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A": Size 12 1/2 x 14 1/2 x 7 1/2 in. **£6.50** Post £1.30  
Model "B": Size 16 x 13 1/2 x 7 in. £7.50. Extra Large Plinth and Cover. For transcription decks Size 20 x 17 1/2 x 9 in. uncut board. Cutters only £18.50.

TINTED PLASTIC COVERS ONLY  
SIZES: "A"—14 1/2 x 12 1/2 x 4 1/2 in. £3. "B"—14 x 12 1/2 x 2 1/2 in. £3.50.  
"C"—16 1/2 x 14 1/2 x 3 in. £3.75. "D"—16 1/2 x 14 x 4 in. £4.  
"E"—19 x 14 1/2 x 4 1/2 in. £4. 15 x 13 1/2 x 3 in. £3.50.  
Ideal for record decks, tape decks, etc. Post 75p.

### BAKER HI-FI SPEAKERS

HIGH QUALITY—BRITISH MADE

### SUPERB 22

12in 25 watt Post £1.60

Quality loudspeaker. low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register.  
Bass Resonance 25 c/s  
Flux Density 16,500 gauss  
Useful response 20-17,000 c/s  
8 or 16 ohms models.

### AUDITORIUM 21

12in 35 watt Post £1.60

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.  
Bass Resonance 35 c/s  
Flux Density 15,000 gauss  
Useful response 25-16,000 c/s  
8 or 16 ohms models.

### AUDITORIUM 26

15in 45 watt Post £1.60

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in sides. 6 x 4 in. 70p; 8 x 6 in. 90p; 10 x 7 in. £1.15; 14 x 9 in. £1.50; 16 x 6 in. £1.45; 12 x 3 in. 87p; 16 x 10 in. £1.70; 12 x 8 in. £1.35.  
ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in. 15p; 8 x 6 in. 25p; 10 x 7 in. 30p; 12 x 5 in. 30p; 12 x 8 in. 40p; 16 x 6 in. 45p; 14 x 9 in. 50p; 12 x 12 in. 55p; 16 x 10 in. 75p.  
ALUMINIUM ANGLE BRACKET, 6 x 1/2 x 1/2 in. 15p.  
ALUMINIUM BOXES, MANY SIZES IN STOCK.  
4 x 2 x 2 in. 55p; 3 x 2 x 1 in. 55p; 6 x 4 x 2 in. 65p; 8 x 6 x 3 in. £1; 9 x 4 x 4 in. £1.20; 12 x 4 x 4 in. £1.80

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. a.c. mains 200/240V Leaflet S.A.E. **£4.95** Post 40p

### ELAC HI-FI SPEAKER 8in TWIN CONE

Dual cone plastic roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 40 c/s. 8 ohm impedance. 15 watts. RMS. **£5.95** Post 35p

### MAINS TRANSFORMERS

ALL POST 50p each  
250-0-250V 70mA. 6.3. 2A **£3.45**  
250-0-250 80mA. 6.3V 3.5A. 6.3V 1A or 5V 2A **£4.60**  
350-0-350 80mA. 6.3V 3.5A. 6.3V 1A or 5V 2A **£5.80**  
300-0-300 120mA 2 x 6.3V 2A C.T. 6.3V 2A **£8.50**  
220V 45mA. 6.3V 2A **£1.75**  
HEATER TRANS. 6.3V 3A. £1.45. 1 amp. £1.00  
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2A 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V **£5.30**  
1A. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5.30**  
2A. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8.50**  
3A. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11.00**  
5, 8, 10, 15V 1A £2.12V 100mA £1. 12V 300mA £1. 12V 750mA £1.30. 40V 2A tapped 10V or 30V £2.95. 20V 3A £2. 40V 2A £2.95. 30V 5A + 34V 2A ct. £3.75. 2 x 18V 6A £11.  
20-0-20V 1A £2.95. 30V 1 1/2A £2.75 20V 1A £2.20. 60V. 40V. 20V or 20-0-20V. 1A £3.50  
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5; 250W £6; 400W £7; 500W £8.  
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V 1 1/2A £2.75; 4A £5.20.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs 1 1/2A 40p; 2A 55p; 4A 85p. HALF WAVE 12V 1 1/2A 25p

### GOODMAN'S COMPACT 12in BASS WOOFER

Standard 12in diameter fixing with cut sides 10 1/2 in square. 14,000 gauss magnet. 30 watt r.m.s. 4 ohm impedance. Bass resonance: 30 c.p.s. Frequency response: 30-8,000 c.p.s. £10.95 each. Post £1.00.

### ADASTRA 3-3W STEREO AMPLIFIER.

10 Transistor Push-Pull Ready built with volume, treble and bass controls. 240V operated.

Size 8 x 3 x 6 in. **£10.95**

### HEATING ELEMENTS WAFER THIN

Size 10 1/2 x 8 1/2 x 1/8 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity

### E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. State 4 or 8 ohm.  
10W Model **£7.95** Post 45p  
15W model **£10.50** Post 65p  
20W model **£11.50** Post 65p

### TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in. For 12in. dia. or 10in. speaker. Illustrated. **£14.50** Post £1.60  
MODEL "B". BOOKSHELF For 13 x 8in. or 8in. speaker. **£8.50** Post £1  
R.C.S. BOOKSHELF SPEAKERS Size 14 x 9 x 6in. approx. Response 50 to 14,000 cps 6 watt rms 8 ohms. **£16 pair** Post £1.30  
ACOUSTIC WADDING 18in. wide. 20p ft.

## RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

Published approximately on the 15th of each month by IPC Magazines Ltd. Fleetway House, Farringdon Street, London EC4. Printed in England by Chapel River Press, Andover. Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/asia) Ltd. South Africa—Central News Agency Ltd. Subscriptions not available at home or overseas. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee" Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Hire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# MAPLIN

in a modern world of electronics

## AUDIO MIXER

A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request



## 10 CHANNEL

### STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top flight hi-fi class. All this for less than £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 40p.




## INTEGRATED CIRCUITS

Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build. Post the coupon now!


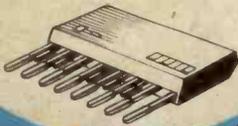
## PEDAL UNIT

A completely self-contained pedal unit. 13-note, 2-Octave range. 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!



## SYNTHESISER

The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart teak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request, full construction details in our construction book £1.50.



Who says the Maplin Catalogue's worth having?

"in our 'musts' for readers-to-collect list"—P.E.

"contains . . . just about everything the DIY electronic enthusiast requires"—P.W.

"probably the most comprehensive catalogue we have ever come across"—E.E.

"has been carefully prepared and is very well presented"—R.E.C.

"makes the job of ordering components an easy, accurate and enjoyable pastime"—P.W.

"Only one word describes the publication—superb!"—E.T.I.

OVER 60,000 COPIES SOLD. DON'T MISS OUT!  
SEND 60p NOW

## MAPLIN ELECTRONIC SUPPLIES

P.O. Box 3, Rayleigh, Essex SS6 8LR  
Telephone: Southend (0702) 715155  
Shop: 284 London Road, Westcliff-on-Sea,  
Essex. (Closed on Monday). Telephone: Southend (0702) 715157.

Our bi-Monthly newsletter keeps you up to date with latest guaranteed prices—our latest special offers—details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

POST THIS COUPON  
NOW FOR YOUR COPY OF  
OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

Name \_\_\_\_\_

Address \_\_\_\_\_

