


PRACTICAL

ELECTRONICS

FEBRUARY 1978

45p

AUTO RANGING VOLTMETER

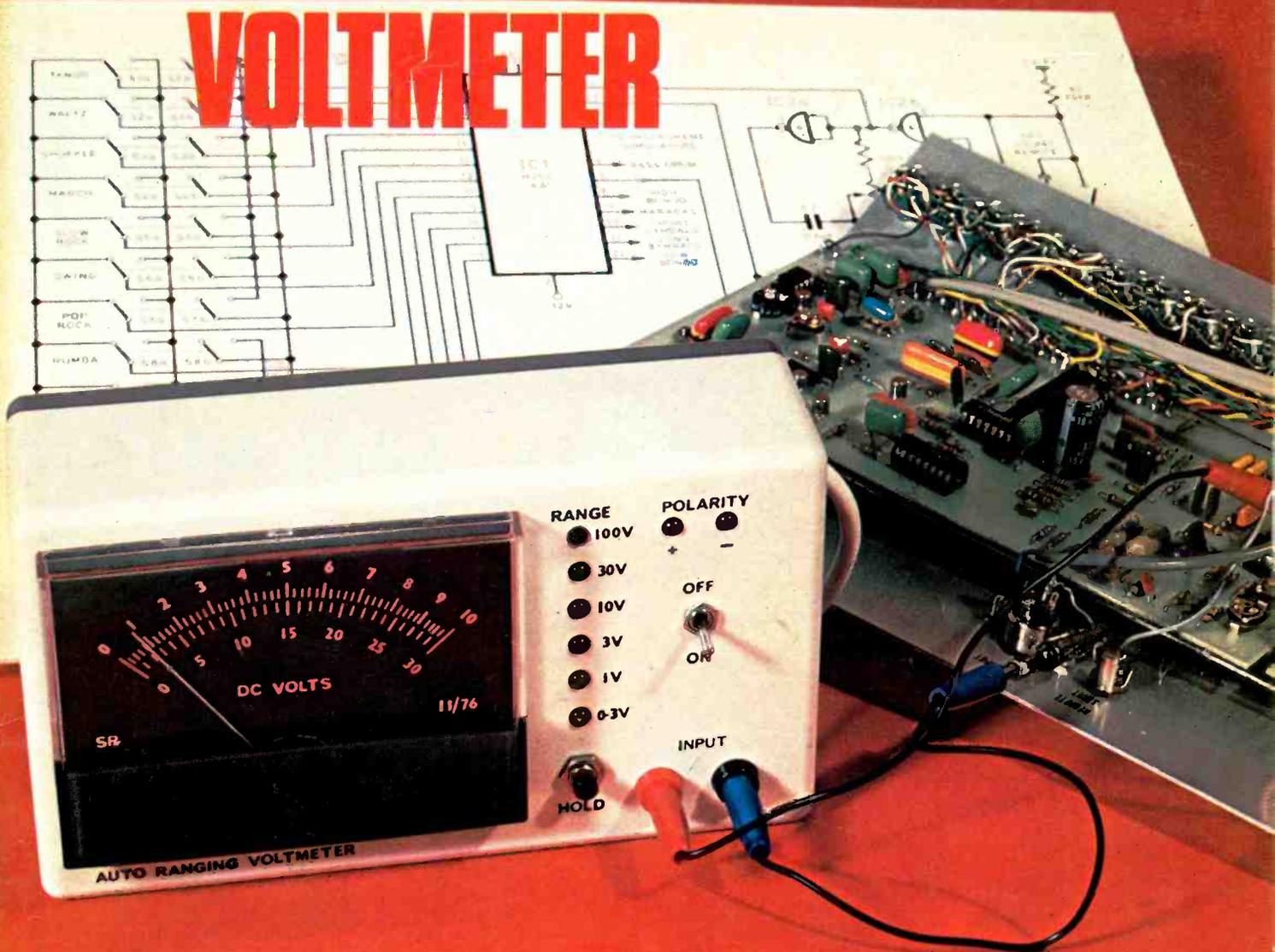

ALSO INSIDE...

KIM Hobby Computer Review

Part 2 of our New FAULT FINDING Series

WATFORD ELECTRONICS

33 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 37774

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P add 25p* to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. SEND LARGE S.A.E. FOR OUR FREE LIST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12½%. We stock many more items. Send S.A.E. for our free list. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in µF)
400V: 0.001, 0.0015, 0.0022, 0.0033 8p; 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 10p; 0.047, 0.068 14p; 0.10 15p; 0.15, 0.22 22p; 0.33, 0.47 33p; 0.68, 45p.
160V: 0.039, 0.15, 0.22 13p; 0.33, 0.47 22p; 0.68, 1.0 22p; 1.5 33p; 2.2 39p; 4.7 47p.
DUBILIER: 1000V: 0.01, 0.015 16p; 0.022 18p; 0.047 16p; 0.1 34p; 0.47 43p.

POLYESTER RADIAL LEAD (Values in µF) 250V:
0-01 0.015 6p; 0-022 0.027 7p; 0-033, 0.047, 0.068, 0.1 8p; 0-15 12p; 0-22, 0.33 14p; 0-47 16p; 0-68 20p; 1-0 24p; 1-5 27p; 2-2 31p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF)
63V: 0.47 1.0 1.5 2.2 2.5 3.3 4.7 5.6 8.0 10 15 22 29p; 47 32 50 12p; 63 100 27p; 50V: 100 7p; 50 100 22p 25p; 470 50p; 1000 2200 68p; 40V: 22 33 9p; 100 12 3300 62p; 4700 64p; 35V: 10 33 7p; 330 47 32p; 1000 49p; 25V: 10 22 47 6p; 80 100 160 8p; 220 250 13p; 470 640 25p; 1000 27p; 1500 30p; 2000 34p; 3300 52p; 4700 54p; 16V: 10 40 47 68 7p; 100 125 8p; 220 16p; 1000 1500 20p; 2200 34p; 10V: 4 100 6p; 640 10p; 1000 14p.
TAG-END TYPE: 70V: 2000 98p; 4700 121p; 50V: 3000 75p; 40V: 4000 70p; 2500 65p; 25V: 4700 48p; 2000 37p; 40V: 2000 - 2000 55p; 325V: 200 + 100 + 50 + 100 190p.

TANTALUM BEAD CAPACITORS
35V: 0.1µF, 0.22, 0.33, 0.47, 0.68 1p
1.0 2.2µF, 3.3, 4.7 68 25V: 1.5, 1.0 20V: 1.5 16V: 10µF 13p each
10V: 22µF, 33 47 68: 47 68 100 3V: 68, 100µF 20p each

POTENTIOMETERS (AB or EGEN)
Carbon Track, 1/8W Log & 1/8W Linear values
1KΩ & 2KΩ (lin only) Single gang 28p
5KΩ-20KΩ single gang 55p
5KΩ-20KΩ single gang D/P switch 26p
5KΩ-20KΩ dual gang stereo 70p

FEED THROUGH CAPACITORS
100µF 350V 8p

MYLAR FILM CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01µF 5p
0.015, 0.02, 0.04, 0.05, 0.056µF 6p
0.1µF 0.15, 0.22 7p 50V: 0.47µF 10p

SLIDER POTENTIOMETERS
0.25W Log and linear values 60mm
5KΩ-50KΩ single gang 70p
10KΩ-50KΩ dual gang 80p
Self Stick Dialed Bezels 20p

OPTO ELECTRONICS*
LEDs - chip
TIL209 Red 13
TIL211 Gm 27
ORP12 Yellow 27
T110 2M
2 Red 17
2 Yellow Green 21
OCF10 46
2N5777 54
7 Seg Displays
TIL312 C An 3 125
TIL313 C Ch 3 125
TIL321 C An 5 130
TIL322 C Ch 5 130
DL704 C A 99
DL707 C A 99
DL747 C A 180
FND 357 140
DR ZERS
75491 75492 85

CERAMIC CAPACITORS
0.5pF to 10nF
15nF 22nF 33nF 47nF
0.1µF

PRESET POTENTIOMETERS
0.1W 50Ω - 50MΩ Miniature
Vertical & Horizontal
0.25W 100Ω - 3MΩ Horiz
0.25W 200Ω - 4.7MΩ Vert

RESISTORS - Eric make 5% Carbon
Miniature High Stability Low noise

CERAMIC TRIMMER CAPACITORS
2.7pF 4.15pF 6.25pF 8.30pF 20p

FREE STOCK LIST
We stock thousands more items. Please send a large SAE for our free list.

SWITCHES*
TOGGLE 2A 250V
SPST 26p
DPDT 34p
4 pole on/off 58p
SP - MIN TOGGLE
SP changeover 59p
SPST on/off 54p
DPDT Centre off 92p
DPDT Biased 115p
SLIDE 250V
1A DPO 14p
1A DP C/over 16p
1A DPDT 13p
4 pole on/off 24p
PUSH BUTTON
Spring loaded
SPST on/off 55p
SPDT on/off 65p
DPDT 6 Tag 85p

MINIATURE TYPE TRIMMERS
2.5-6pF 3-10pF 10-40pF
5-25pF 5-45pF 60pF 88pF

JACK PLUGS
Screened chrome Plastic body open metal moulded with ferric chloride*
2.5mm 12p 8p 8p 8p
3.5mm 15p 10p 8p 10p
MONO 23p 15p 10p 24p
STEREO 31p 18p 15p 24p

SOCKETS
In Line
2 Pin Loudspeaker 13p
2.5 Pin Audio 8p
CO-AXIAL (TV) 14p
PHONO assorted colours 9p
Metal Screened 10p
BANANA 4mm 12p
2mm 10p
1mm 8p
WANDER 3mm 9p

CO-AXIAL (TV) 14p

SWITCHES * Miniature Non-Locking
Push to Make 15p
ROCKER (white) 10A 250V 28p
SP changeover centre off
ROCKER (black) on/off 10A 250V 23p
ROCKER (illuminated) (white) Lights when on 3A 240V 52p
ROTARY: (ADJUSTABLE STOP) 1 pole / 2-12 way 2p/2.6W 3p/2.4W 4p/2.3W 41p
ROTARY: Mains 250V AC, 4 Amp 42p

DIL SOCKETS* (Low Profile - Texas)
8 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 20p; 20 pin 26p; 24 pin 30p; 28 pin 42p; 40 pin 58p.

PHONO assorted colours 9p
Metal Screened 10p

DIAGRAM
DALO ETCH Resist Pen Spare Tip 75p*

COPPER BOARDS*
Fibre Glass Single Sided 6x6 78p
6x12 130p
S R B P
8 x 10 70p

BANANA 4mm 12p
2mm 10p
1mm 8p
WANDER 3mm 9p

VOLTAGE REGULATORS
723C 48p
TA6258 95p
TO3 Can
1A 5V 170p
1A 12V 180p
1A 15V 190p
1A 18V 210p
LM323K 625p
1A - 5V 220p
1A - 12V 220p

PLASTIC
1A 5V 118p
1A 12V 118p
1A 15V 120p
1A 18V 125p
1A 24V 130p
0.1A 5V 51p
0.1A 6V 51p
0.1A 8V 51p
0.1A 12V 51p
0.1A 15V 51p

SPECIAL OFFER

TV GAMES
"Olympic Kit" £20.80*
"Olympic" Colour Kit £28.50* (p&p insured add 95p)
EconoGame Kit £8.99*
COLOUR ADAPTOR for existing Black & White Games £8.85*
"Sure Fire Rifle" Kit for "Olympic" Game £8.50*
"Sure Fire Rifle" Kit for other makes £9.25* (p&p insured add 48p)
"Joy Stick" £1.95*
IC AY-3-8500 £4.50*
IC AY-3-8550 £7.50*
IC AY-3-8600 £9.00*
(TV Games & Rhythm Gen. Demonstration on at our shop)

RHYTHM GENERATOR
Build this PE (Jan. '78) Easy-build Low cost Rhythm Generator. We are the sole suppliers of the complete Kit including the case, pre-drilled printed front panel and the printed Circuit Boards.
Complete Kit price incl. VAT £49.95 only. P & P £1.10 insured. Send S.A.E. for descriptive leaflet.



SPECIAL ADDITIONAL DISCOUNTS ON OUR LOW PRICED TEXAS TTL - MOTOROLA CMOS. Due to massive purchases we are now able to offer the following discounts on published prices.
LESS 5% 10- mixed
LESS 7½% 25- mixed
LESS 10% 50- mixed
LESS 15% 75- mixed
LESS 20% 100- mixed
even more discount on larger quantities.

TTL 74*		CMOS*		LINEAR IC'S		M253AA*	
7400	7483 95	75491	75 4053 89	4450	295 4512	98 4527	152
7401	14 7484 95	75492	80 4054 120	4451	295 4512	98 4527	152
7402	16 7485 110		4055 134	4490F	695 4514	265 4529	165
7403	16 7486 320		4056 2570	4490V	625 4515	299 4530	85
7404	20 7490 36		4000 15 4057 480	4501	17 4516	125 4531	165
7405	22 7492 53		4002 17 4060 115	4502	120 4517	382 4532	127
7406	38 7493 35		4006 105 4061 2380	4503	69 4518	102 4534	788
7407	38 7495 85		4008 92 4062 999	4506	51 4519	59 4536	20
7408	20 7496 82		4009 58 4063 110	4507	55 4520	108 4538	160
7409	20 7497 125		4010 15 4064 21	4508	298 4521	268 4539	110
7410	15 7498 262		4012 9 4065 22	4510	136 4522	199 4545	101
7411	24 7499 402		4013 55 4066 22	4511	168 4526	199	
7412	37 7499 62		4014 99 4067 22				
7413	37 7499 62		4015 93 4068 22				
7414	74 74105 84		4016 92 4069 22				
7415	35 74110 70		4017 95 4070 32				
7416	35 74110 70		4018 99 4071 40				
7417	39 74116 198		4019 60 4072 21				
7420	16 74118 90		4020 102 4073 21				
7421	33 74127 111		4021 99 4074 21				
7422	24 74121 28		4022 96 4075 23				
7423	32 74122 48		4023 20 4076 129				
7425	30 74123 70		4024 96 4077 21				
7426	36 74125 65		4025 109 4078 21				
7427	36 74126 60		4026 98 4079 21				
7428	38 74128 60		4027 98 4080 21				
7430	18 74136 73		4028 98 4081 21				
7432	32 74141 72		4029 98 4082 21				
7433	40 74143 314		4030 58 4083 21				
7437	30 74144 314		4031 230 4084 21				
7438	33 74145 85		4032 90 4085 21				
7439	17 74147 175		4033 145 4086 21				
7441	74 74148 143		4034 105 4087 21				
7442	68 74150 118		4035 120 4088 21				
7443	115 74153 75		4036 325 4089 21				
7444	112 74154 140		4037 109 4090 21				
7445	94 74155 82		4038 109 4091 21				
7446	94 74156 80		4039 109 4092 21				
7447	82 74159 225		4040 109 4093 21				
7448	78 74160 116		4041 98 4094 190				
7450	17 74162 118		4042 98 4095 105				
7451	17 74166 141		4043 98 4096 105				
7452	32 74185 146		4044 98 4097 105				
7454	17 74170 240		4045 98 4098 105				
7460	17 74172 625		4046 98 4099 105				
7470	30 74173 175		4047 98 4100 105				
7472	28 74177 116		4048 98 4101 105				
7473	32 74186 146		4049 98 4102 105				
7474	32 74188 65		4050 98 4103 105				
7475	42 74190 140		4051 98 4104 105				
7476	30 74194 140		4052 89 4440 1275				
7480	50 74195 95						
7481	48 74198 248						
7482	82 75150 110						

TRANSISTORS

AC117	35	BC168C	12	BF198	18	OC46*	35	ZTX504	25	2N3702	10
AC125*	19	BC169C	14	BF200	18	OC70*	30	ZTX531	25	2N3703	11
AC126*	15	BC170	14	BF224A	18	OC71*	30	ZTX550	25	2N3704	10
AC127*	18	BC171	11	BF256*	50	OC72*	30	ZN526*	58	2N3705	11
AC128*	18	BC172	11	BF257*	29	OC77*	76	ZN696*	35	2N3706	10
AC141*	24	BC177*	18	BF258*	29	OC79*	76	ZN697*	21	2N3707	10
AC141K*	38	BC178*	16	BF259*	30	OC81*	28	ZN698*	20	2N3708	10
AC142*	38	BC179*	16	BF294	22	OC82*	45	ZN699*	50	2N3709	11
AC142K*	38	BC182	10	BF594	22	OC83*	35	ZN706A*	19	2N3710	16
AC176*	18	BC181	13	BF595	38	OC83*	48	ZN707*	50	2N3711	12
AC187*	20	BC183	10	BF596	25	OC84*	44	ZN708*	19	2N3715*	250
AC188*	20	BC183L	12	BF620	25	OC85*	115	ZN712*	32	2N3724*	80
AC191*	35	BC184	11	BF679	28	OC85*	140	ZN713*	26	2N3731*	268
AC198*	40	BC184L	14	BF680	28	OC140	125	ZN918*	30	2N3819	22
AC199*	40	BC186	24	BFX29	28	OC141*	157	ZN920*	51	2N3820	38
AC20*	35	BC187*	28	BFX81*	130	OC170*	40	ZN930*	18	2N3823*	65
AC21*	35	BC212	11	BFX85*	24	OC171*	40	ZN961*	61	2N3824*	70
AC222*	40	BC212L	13	BFX86*	28	OC202*	140	ZN1132*	25	2N3903	20
AC23*	40	BC213	11	BFX87*	23	OC203*	150	ZN1302*	35	2N3904	18
AC239*	78	BC213L	14	BFX88*	26	OC204*	150	ZN1303*	50	2N3905	18
AC240*	48	BC214	14	BFY18	50	OT29*	43	ZN1304*	50	2N3906	17
AC244	39	BC241L	15	BFY50	17	OT29A	44	ZN1305*	28	2N4037*	52
AD140	69	BC307B	20	BFY51*	17	OT29C	50	ZN1306*	20	2N4058	17
AD149*	70	BC328	15	BFY52*	17	OT30	52	ZN1307*	50	2N4061	17
AD151*	48	BC329	15	BFY53*	17	OT30A	52	ZN1308*	46	2N4064*	120
AD162*	42	BC441*	45	BFY71	47	OT30B	64	ZN1613*	20	2N4236*	145
AF114*	20	BC461*	38	BSX20	18	OT30C	70	ZN1671*	190	2N4289	20
AF115*	20	BC462*	45	BSX20*	18	OT31*	50	ZN1671B*	195	2N4859	65
AF116*	20										

PRACTICAL ELECTRONICS

VOLUME 14 No. 6 FEBRUARY 1978

CONSTRUCTIONAL PROJECTS

- AUTO-RANGING VOLTMETER** *by S. Roberts* 400
A useful piece of test gear that leaves your hands free
- STRENGTH METER** *by N. Riddiford* 412
A game to test your grip
- P.E. CHAMP-6** *by R. W. Coles and B. Cullen* 422
CHOMP firmware put under the microscope
- RHYTHM GENERATOR** *by N. A. Cooke* 432
Construction and final setting up

GENERAL FEATURES

- SEMICONDUCTOR UPDATE** *by R. W. Coles* 411
A look at some recently released devices
- INGENUITY UNLIMITED** 437
Telephone Monitor
- FAULT FINDING—2** *by G. Loveday* 445
Trouble shooting complete systems

NEWS AND COMMENT

- EDITORIAL** 399
- KIM 1 REVIEW** 408
Report on another new microprocessor
- NEWS BRIEFS** 417
Microcomputer Kit—Watts On The Road—Exhibition
- MARKET PLACE** 418
Interesting new products
- SPACEWATCH** *by Frank W. Hyde* 421
U.F.O.s, Life And Death From Outer Space, Landsat
- MICRO-BUS** *by DJD* 429
A bimonthly focus on micro's for the home constructor
- INDUSTRY NOTEBOOK** *by Nexus* 438
What's happening inside industry
- PATENTS REVIEW** 441
The history of the gramophone
- BOOK REVIEWS** 448
Selected new books we have received

Our March issue will be on sale Friday, 10 February, 1978
(for contents see page 407)

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

EASY BUILD SPEAKER DIY KITS

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers.

£2800
STEREO PAIR Input 15 watts rms, 30 watts peak, each unit, + p & p £5.50 Cabinet size 20" x 11" x 9 1/2" (approx.).

SPEAKERS AVAILABLE WITHOUT CABINETS.
It's the units which we supply with the enclosures illustrated. Size 13" x 8" (approx.) woofer. (EMI), 2 1/2" app. **£1700** per tweeter, and matching crossover components. stereo pair Power handling 15 watts rms, 30 watts peak, + p & p £3.40

COMPACT FOR TOP VALUE These infinite baffle enclosures come to you ready mitred and professionally finished. Each cabinet measures approx. per stereo pair 12" x 9" x 5" deep, and is in wood simulate. Complete with two 8" (approx.) speakers for a maximum power handling of 7 watts. 8Ω. **£850** + p & p £2.20

SPEAKERS Two models - Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.). Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" app. Duo IIb **£17** PER PAIR Duo III **£52** PER PAIR p & p £6.50 p & p £7.50

DECCA 20 WATTS STEREO SPEAKER stereo pair This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters complete with crossover networks. 8Ω. **£4.00 p & p. £20.00**

PERSONAL SHOPPERS

STEREO CASSETTE record/replay fully built P.C. board **£275**

AM. FM. TUNER P.C.B. with Mullard L.P. 1186, 1185, 1181 modules. **£950**

100K Multiturn Varicap tuning pots, 6 for **£1.00**

PAIR STEREO 8 WATT SPEAKERS 8" bass units with 3 1/2" approx. tweeters Size 16 1/2" x 11" x 8 1/2". **£12.95**

Plinth & cover BSR or Garrard teak finish **£6.00**

DECCA DCI000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads **£2.95**

AM. FM. Stereo Multiplex Car Radio/cassette player in dash fixing Negative earth 5 watts output **£36.00**

I.C. Stereo 8 Track to Cassette adaptor converts, any 8 track player to cassette player. **£18.95**



20 x 20 WATT STEREO AMPLIFIER **£2990**

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets, OIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

30 x 30 WATT AMPLIFIER KIT Specially designed by RT-VC for the experienced constructor, complete in every detail. Same facilities as Viscount IV amplifier. 60 + 60 peak, p & p £2.50 **£2900**

NOW AVAILABLE fully built and tested. **£3500** Output 30 + 30 watts rms, 60 + 60 peak. p & p £2.50

FREE To cash or cheque personal shoppers A 4 channel Stereo Adaptor to all buyers of the Viscount 20 x 20 **£2900** Available separately **£395** Amplifier at + £1.00 p & p.

ADD-ON STEREO CASSETTE TAPE DECK KIT

Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control for mating with mechanism. Specifications: Sensitivity - Mic. 0.85 mV @ 20K OHMS; Din. 40mV @ 400K OHMS; Output - 300mV RMS per channel @ 1KHz from 2K OHMS source; Cross Talk - 30db; Tape Counter - 3 Digit, Resettable; Frequency Response - 40Hz - 8KHz ± 6db; Deck Motor - 9 Volt DC with electronic speed regulations; Key Functions - Record, Rewind, Mains Transformer **£19.95** Fast Forward, Play, Stop & Eject. **£2.50** + £1 p & p & p £2.50. Opt. extras: Pair of Dynamic microphones **£3.95** + £1.00 p & p.



323 EDGWARE ROAD, LONDON W2
210 HIGH STREET, ACTON W3 6NG
ALL PRICES INCLUDE VAT AT 12 1/2%
All items subject to availability. Price correct at 1.11.77 and subject to change without notice.



45 WATT MONO DISCO AMP

£3500 p & p £2.50
Size approx. 13 1/2" x 5 1/2" x 6 1/2"
45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"
Brushed aluminium fascia and rotary controls. Five vertical slide controls - master volume, tape level, mic level, deck level, PLUS INTER-DECK FAOER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control 70 watt (PFL) lets YOU hear next disc before fading 140 watt peak in. VU meter monitors output level. 100 watt **£65**



CHASSIS RECORD PLAYER DECKS

BSR BD S 95 TYPE II ILLUS. **£24.95**
Belt drive turntable unit, 2 speed, semi automatic p & p £2.55
BSR MP60 TYPE Single play record deck less cartridge. p & p £2.55
Cartridges to suit above
Acos. magnetic stereo **£4.95**
Ceramic stereo **£1.95**
BSR automatic record player deck cueing device and stereo ceramic head, p & p £2.55 **£9.95**

BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. p & p £4.50
Home 8 Track cartridge player. This unit will match with the Viscount IV 9" x 8" x 3 1/2". p & p £2.50 **£16.50**

Tourist IV CAR RADIO KIT

For the experienced constructor only
Output 4 watts into 4 ohms.
12 volts pos or neg (altered internally) **£12.50** p & p £1.50
FREE TO PERSONAL SHOPPERS BUYING CAR RADIO KIT worth **ELECTROMATE** Rear window heater, modern line element, **£3.00**



Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



Free! Brochure, without obligation to: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,** P.O.Box 156, Jersey, Channel Islands.


NAME _____

ADDRESS _____ (Block caps please)

PE SUSTAIN UNIT



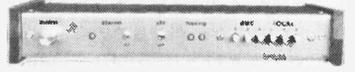BUILD A SUSTAIN UNIT EQUAL TO THE BEST COMMERCIAL MODELS.
COMPLETE KIT - £7.95
ALL HIGH QUALITY COMPONENTS AS SPECIFIED.
DESIGNER APPROVED.



ORION Complete set of semiconductors **£4.99**
tuner LP1186 Tuner Head **£9.60**
Glass fibre PCB, printed with component locations **£2.45**

ORION Complete set of semiconductors **£9.40**
amplifier Glass fibre PCB, printed with component locations **£2.99**

PE DIGITAL VOLTMETER (APRIL 1977) ZNA116 *£6.00 with circuits and data


Complete set of all semiconductors for the P.E. DVM including I.C.'s, transistors, diodes, displays, regulator, etc. **£20.50***
Set of two professional grade glass fibre P.C.B.'s printed with component locations **£3.40***
Complete set of resistors, incl. attenuator resistors **£1.00***
Complete set of capacitors incl. 2200µF power supply **£1.60***

PE TV SOUND SEPARATOR

Complete set of semiconductors £2.30, High quality glass fibre p.c.b. £1
POSTAGE AND PACKING 15p per order. Orders over £5 post free. All devices are top grade, brand new and to full manufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list.
Prices do not include VAT—add 8% to items marked*, and 12 1/2% to all others

DAVIAN ELECTRONICS (MAIL ORDER ONLY)
13 Deepdale Avenue, Royton, Oldham OL2 6XD

BD1-The Connoisseur's Budget Choice

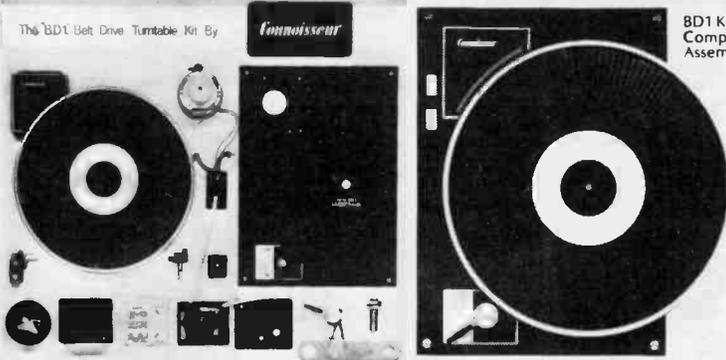

BD1 Kit & Completed BD1 Assembly



BD1 with Plinth, Cover & SME Arm.

The Connoisseur BD1 transcription turntable is a precision engineered product designed to provide top grade performance at a moderate cost. Simplicity is the main feature of this unit giving excellent performance and reliability. A slow speed synchronous motor is used and because of its construction the hum field is very low, so that even the most sensitive of pickups can be used, including the Connoisseur SAU2 or the SME 3009 Series II.

Speed change is achieved by a press button unit at the rear of the platform which automatically moves the drive belt from one pulley groove to the other whilst the turntable is turning. The BD1 turntable kit can be assembled by the home constructor within the hour and when completed will give top quality performance. No soldering is required. Complete the unit with a modern BD1 plinth and cover. The plinth is finished in walnut veneer and fitted with spherical, anti-vibration feet. Add to this a strong Acrylic, bronze cover, hinged with 2-position lid stay and you have a first class turntable at a budget price!

Connoisseur

Write for further details to:

A. R. Sugden & Co. (Engineers) Ltd.
Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES
Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden Crighouse,
Telegrams & Cables: Connoisseur Brighouse.

B. BAMBER ELECTRONICS

Dept. P.E. 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

A RANGE OF DRAPER TOOLS FOR THE ELECTRONICS ENTHUSIAST
MAINS TESTER SCREWDRIVERS 100 to 500V Standard size 50p, Large 70p
RADIO PLIERS 5 $\frac{1}{2}$ " £1.60, 6 $\frac{1}{2}$ " £1.80.
DIAGONAL SIDE CUTTERS 6 $\frac{1}{2}$ " £1.90.
SMALL SIDE CUTTERS L2, Standard £3.70, L17 (with wire holding device) £4.10.
MIDGET OPEN ENDED SPANNER SETS
0-1 2-2 3-5 4-6 6-8BA SIZES £2.85 set of 5.
4-4.5 5-5.5 4-6 6-7 8-9 10-11 mm SIZES £3.50 set of 6.
MINIATURE FILE SETS. Set of 6 £1.90. Set of 10 £3.25 (Round, flat, etc.).
TAP AND DIE SETS (18 piece) contain 1 each of 0, 2, 4, 6, 8, BA SIZES in Dies, Plug Taps, Taper Taps + American type tap wrench, T type tap wrench, Die Holder. £11.80.

LARGE ELECTROLYTIC CAPCS. Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces, £3.00 per pack (+12½% VAT).

Slider Switches, 2 pole make and break (or can be used as a 1 pole change-over by linking the two centre pins), 4 for 50p.

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.

Aluminium Boxes with Lids.	60p
AB10 5 $\frac{1}{2}$ x 4 x 1 $\frac{1}{2}$	80p
AB13 6 x 4 x 2	£1.00
AB14 7 x 5 x 2 $\frac{1}{2}$	£1.00
AB15 8 x 6 x 3	£1.30
AB16 10 x 7 x 3	£1.50
AB17 10 x 4 $\frac{1}{2}$ x 3	£1.30
AB25 8 x 4 x 3	£1.00

Vinyl Coated Instrument Cases

Light Blue tops and White lower sections. Very smart finish.	60p
WB1 5 x 2 $\frac{1}{2}$ x 2 $\frac{1}{2}$	£1.10
WB2 6 x 4 $\frac{1}{2}$ x 1 $\frac{1}{2}$	£1.10
WB3 8 x 5 x 2	£1.60
WB4 9 x 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$	£1.80
WB5 11 x 6 $\frac{1}{2}$ x 3	£2.00
WB6 11 x 7 $\frac{1}{2}$ x 3 $\frac{1}{2}$	£2.25
WB7 12 x 6 $\frac{1}{2}$ x 5 $\frac{1}{2}$	£2.60
WB853 8 x 5 $\frac{1}{2}$ x 3 $\frac{1}{2}$	£2.00

MAINS TRANSFORMERS. Type 20/2. Mains input 200-210-220-230-240-250V a.c., output 0-20-40-80V at 2A, in Metal and Plastic case, approx. 7 $\frac{1}{2}$ x 4 $\frac{1}{2}$ x 4, fully fused (ideal for PSU) £3.00 each.

MAINS TRANSFORMERS. Type 15/300 240V input, 15V at 300mA output. £1.50 each.

MAINS TRANSFORMERS. Type 45/100, 240, 220, 110, 20, 0V input, 45V at 100mA output. £1.50 each.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6.50 each. Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits for formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.
Type S ($\frac{1}{2}$ in. square, dummy type).
Type SA 20 to 30MHz (when 33pF fitted in parallel).
Type SB 35 to 50MHz (with link winding).
Type SC 70 to 100MHz (with link winding).
Type SD 135 to 175MHz (with link winding).
Type M (Min. $\frac{1}{2}$ in. square types).
Type MA 19 to 28MHz (when 33pF fitted in parallel).
Type MB 22 to 32MHz (when 33pF fitted in parallel).
Type MC 25 to 35MHz (when 33pF fitted in parallel).
Type MD 38 to 50MHz (when 33pF fitted in parallel).
Type ME 45 to 60MHz (when 33pF fitted in parallel).
Type MF 100 to 200MHz (without slug) when 0 to 30pF variable fitted in parallel.
All the above coils available in packs of five only (same type) at 50p per pack of 5.

SEMICONDUCTORS

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TO5 Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3619 Fets, 3 for 80p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.

741CG op amps by RCA, 4 for £1

RED LEDs (Min. type) 5 for 70p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts.
Type NB1 approx 3in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. 40p each.
Type NB2 approx. 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. 50p each.
Type NB3 approx. 4 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. 60p each.

MULLARD 85A2 85V STABILISER VALVES (Brand New) 70p each or 2 for £1.20.

TO3 transistor insulator sets, 10 for 50p

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 $\frac{1}{2}$ in x 1 $\frac{1}{2}$ in., 2 for 35p.

PLUGS AND SOCKETS
N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
PL259 Plugs (PTFE), brand new, packed with reducers, 65p each
SO239 Sockets (PTFE), brand new (4-hole fixing type), 50p each

SOLDER SUCKERS (Plunger type). Standard Model, £5. Skirted Model £5.50. Spare Nozzles 60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS.

S125D 25W 240V £3.60.
S140D 40W 240V £4.20.
S125DK 25W 240V + bits etc., KIT £4.90.

BENCH STAND with spring and sponge for Marksmen Irons £2.38.
Spare bits MT9 (for 15W) 50p, MT5 (for 25W) 45p, MT10 (for 40W) 50p.
ALL PRICES + 8% VAT.

TEMPERATURE CONTROLLED IRON.

Temperature controlled iron and PSU £30 + VAT (£2.40)

SPARE TIPS

Type CC single flat, Type K double flat fine tip, Type P, very fine tip, £1 each + VAT (8p).

MOST SPARES AVAILABLE.

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).
Size C15A18 Savbit 18 s.w.g., 56p + VAT (4p).
 $\frac{1}{2}$ Kg. (1.1lb) 60 x 40, 20 s.w.g. on plastic reel £3 + VAT (24p).

WELLER SOLDERING IRONS
EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN #1000 £9.90.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £12.90.
Spare bits 35p pair.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALU-BOL ALUMINIUM SOLDER (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 s.w.g. with multicore flux, with Instructions, Approx. 1 metre coil 40p pack. Large reel £2.75.

VARICAP TUNERS Mullard type ELC1043/05. Brand New, £4.40 + 12½% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working, Saeonic Manufacture. Approx. 100. £1.50 per pack + 12½% VAT.

OSMOR REED RELAY COILS (for reed relays up to 5in dia., not supplied) 12V, 500 ohm coil, 2 for 50p.


We now stock Spiralux Tools for the electronic enthusiast. Screwdrivers, Nut spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

Dubilier Electrolytics, 50 μ F, 450V, 2 for 50p.
Dubilier Electrolytics, 100 μ F, 275V, 2 for 50p.
Plessey Electrolytics, 470 μ F, 63V, 3 for 50p.
TCC Electrolytics, 1000 μ F, 30V, 3 for 80p.
Dubilier Electrolytics, 5000 μ F, 35V, 50p each.
Dubilier Electrolytics, 5000 μ F, 50V, 60p each.
ITT Electrolytics, 6800 μ F, 25V, high grade, screw terminals, with mounting clips, 50p each.

PLEASE ADD 12½% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p.
Please add 12½% VAT.

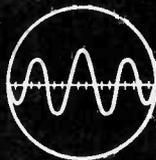Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY) SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN CALLERS WELCOME BY APPOINTMENT ONLY



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS


PRICES INCLUDE VAT. P & P FREE
correct at 1/9/77

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE28) or quote
Access/Barclaycard No. and post to TUAC LTD. (PE28), 119
Charlmount Road, London SW17 9AB. We accept phone orders
from Access/Barclaycard Holders. Phone 01-672 9080.

PRE AMPLIFIERS

Designed for use with TUAC power amplifier modules

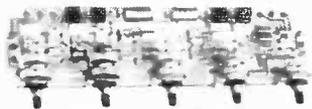

VA08

Vol. Treb. Mid. and Bass controls. HI. IMP. FET. I/P suitable Mid. Guitar. Radio Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1kHz. Bass +20 -10dB at 40Hz.

£9.00

VA06

Vol. Treb. and Bass controls. Sensitivity 8mV. Treb +28 -15dB at 12kHz. Bass +18dB and 40Hz.


£7.75

SVA08 STEREO PRE AMP

Vol. Treb. Mid. and Bass controls. I/P suitable Guitar. Radio. Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -7dB at 4kHz. Bass +20 -18dB at 30Hz Plus Full Balance Control. Fully I/C operation supply voltage $\pm 25VDC$.

£15.00


POWER SUPPLIES

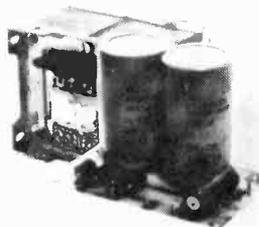

Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply:

PS250 for supplying 2 TP125s	£28.50
PS200 for supplying 2 TP100s	£28.50
PS60/60 for supplying 2 TL60s	£25.00
PS125 ± 45 volts for TP125	£17.75
PS100 ± 43 volts for TL100	£16.25
PS60 ± 38 volts for TL60	£15.25
PS30 ± 25 volts for TL30	£11.75
PSU 2 for supplying disco mixer	£7.50

AMPLIFIER MODULES

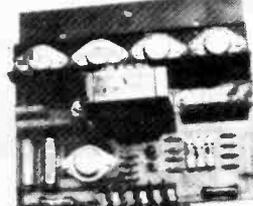

TL30 D.C. COUPLED 5 x 5 1/4 in.

- 35 watt R.M.S. continuous sine wave output
- 8 transistors 4 diodes

£12.75

TL60 5 x 5 3/4 in.

- 60 watt R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£18.25

TL100

- 100 watt R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors


£20.75

TP125 7 x 6 1/2 x 3 in.

- 125 watt R.M.S. continuous sine wave output
- 4 R.C.A. 150 watt 15 amp output transistors

£25.75

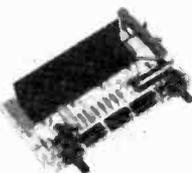4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSMI



- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£20.75

Model 501 500W per channel as above without sound triggering

£12.25

FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs) as illustrated




For S1LMB £6.50
Size 8" x 4 1/2"




4LSM1 £5.50
Size 6 1/2" x 4 1/2"



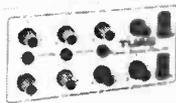FUZZ LIGHTS
Red, Green, Blue,
Amber. £23.50



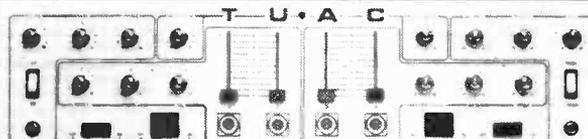S1LMB £7.50
Combined with 3SDM1
Size 9" x 4 1/2"



STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls $\pm 18dB$ at 60Hz. Treble controls $\pm 18dB$ at 15kHz.

OUTPUT: Up to 3 volts ($\pm 12dB$) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz $\pm dB$.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.


Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions

Size: 25in long x 6in high x 3in deep

Mono Disco Mixer with autofade £45.00

£129.00

3 CHANNEL LIGHT MODULATOR SILMB

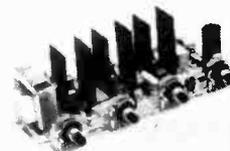

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.25

Single Channel Version 1500 Watts

£9.75

ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1

£14.50

new from TUAC... ULTRA QUALITY HIGH POWER TD 500 POWER AMPLIFIER New DC coupled design

Output power using PS250
300w into 2 Ohms
220w into 4 Ohms
140w into 8 Ohms
75w into 15 Ohms



RMS continuous sine wave output
INPUT Sensitivity 0.775V
RMS (ODB) at 25 KOHMS
Hum and Noise - 100dB
Relative full output
THD = at Full Power 0.1%

7" x 9" x 1 3/4" £45

PIEZO SUPER HORN £10.95

STOCKISTS - CALLERS ONLY

A1 Music, 88 Oxford Street, Manchester (Tel. 061-236 0340)
Geo Mathews, 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)
Bristol Disco Centre, 25 The Promenade, Gloucester Road (Tel. Bristol 41666).

Soccodi, 9 The Friars (Tel. Canterbury 60948)

Cookies Disco Centre, 132 West Street (Tel. Crawley 4739).

Garland Bros. Ltd., Deptford Broadway, London 01-692 4412

Luton Disco Centre, 88 Wellington Street, Luton (Tel. Luton 411733)

Mitchell Electronics, 7 Queen Street (Tel. Salisbury 23689).

Session Music, 163 Mitcham Road, Tooting (Tel. 01-672 3413).
Mon-Sat 10 a.m. - 6 p.m. Closed Wed.

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 20 PAGE ILLUSTRATED CATALOGUE. S.A.E. STAMPED PLEASE

Sparkrite mk2

Capacitive discharge electronic ignition kit

VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE OCT. 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service — phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING. Improve performance & economy NOW

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing
ELECTRONICS DESIGN ASSOCIATES, 82 Bath St., Walsall, WS1 3DE

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept. PE1
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass Kit @ £11.80	QUANTITY REQ.
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's for **£**

Cheque No.

Send SAE if brochure only required.

Random FLASHER UNIT
Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random. **£18.95**

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14 1/2 inches
BC Fitting **£9.55**
ES Fitting **£10.35**

Sound to Light MASTER UNIT
600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS WIRE SOCKET

TYPE A SPOT
(less lamp)
BC Fitting **£1.95** each
ES Fitting **£2.12** each

TYPE B 3 BANK UNIT
(Less Lamps)
BC Fitting **£6.90** each
ES Fitting **£7.26** each
100 WATT SPOT LAMPS RED, YELLOW, GREEN, BLUE, CLEAR **£1.50** each
Maximum 3 lamps B.C. or E.S. Fitting **£4.50**

TWIN BANK 12 LIGHT UNIT
Length 31 1/2 (less lamps)
BC Fitting **£15.60** each
ES Fitting **£17.00** each

ALL PRICES INCLUDE V.A.T. and POST & PACKING (these prices apply to the United Kingdom only)
ALBEN ENGINEERING CO. LTD., DEPT. PE THE CRESCENT, WORSTHORNE, BURNLEY, LANCs. Tel: Burnley 20940

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs - £4.95; 14lbs - £7.95; 28 lbs - £12.00; 56lbs - £20.00; 112 lbs - £30.00.

BARGAIN PACKS

- Handy Packs**
4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. £1.00
Self fluxing enamelled copper wire 18 & 22 swg on 2 oz reels. 2 for £1.10
100 miniature reed switches ideal for burglar alarms, model railways, etc. £2.20
15 x 2-pole reed relays on board operate at 12 volts £2.45
6 x 6-pole 12 volt reed relays on board £2.45
High quality computer panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95
- New U.H.F. transistor TV tuners** 4 pushbutton type £2.50
Rotary type with slow motion drive £2.50
Aluminium TV coax plugs. 10 for £1.00
Miniature 5K log pots with s/p switch. 4 for £1.
Hardware Packs each containing 100's of items including: BA nuts and bolts, Nylon, Self-topping, Posidrive "P" clips, Cable clamps, Fuse holders, Spire nuts etc, etc. £1 per pound. 100 assorted "P" clips £1.
Selling Lee outdoor Triplexers, U.H.F., Band 1, Band 2, 50p each, 3 for £1.

DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1 lb ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions / only £5.30

REFILL PACKS FOR ABOVE

- 150 sq. in fibre glass board £2
Dalo pen 90p
1 lb ferric chloride to mil spec £1.25

TV SURPLUS

- Brand New ITT C.T.V. Triplers, fit Deca "Bradford" chassis £2.50 each. 5 for £10.
Pye and Philips "G8" C.T.V. panels, various types. All incomplete but invaluable for spares or completing. 6 assorted panels for £7.50.
Thorn B & W T.V. bottom panel "950" series, manufacturers surplus £1.50 each.
Pye 11U contrast controls. 10 for £1.
Thorn tape motors mains £1.20 each.
Pye EHT bases, DY51 etc. 10 for £1.
Ceramic P/C mounting valve bases. For PL509, PL508, etc. 10 for £1.

- Semiconductor Bargains**
TH3 Thermistors. 10 for £1.
100 new & marked silicon and germanium transistors including BC148, 8F194, BC183, etc. £3.95
200 new & marked transistors, including 2N3055, AC128, BFY50, BD131, etc. £6.95
100 mixed diodes IN4148, etc. £1.20
100 mixed diodes including zener, power and bridge types £3.30
- Bridge rectifier 100v 2.5 amp. 4 for £1.
5 lbs ferric chloride to mil spec **£4.00**
Instruction sheet **20p**
200 unmarked mixed transistors, lots of interesting types including power. Send 60p for samples £4.50
25 New & marked integrated circuits including 555, 741, 7400, 7490, TBA 800, CD4001, etc. £4.70
BR 101 full spec. 5 for £1.00
DY 51 EHT Rectifier £1.00
TBA 120A 50p each
20 mm anti-surge fuses your selection 500mA to 3.15A. 12 for £1.00
- Component Bargains**
300 mixed resistors 1/2 & 3/4 watt £1.00
200 modern mixed caps most types £3.30
125 mixed resistors, mostly 1 & 2 watt £1.
100 mixed polyester caps £1.40
100 mixed modern miniature ceramic plate caps, most values to 1000 PF £3.30
100 mixed polystyrene caps to 5000 PF £2.20
100 mixed electrolytics £2.20
100 mixed wirewounds £1.00
200 printed circuit resistors £1.00
25 mixed pots & presets £1.00

40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PE, 20A WADDON ROAD, CROYDON, SURREY.

G8CZW Digital Frequency Meter




Complete 50MHz kit £54.00 inc. VAT, post free (U.K.)

ZN1040E Count/Display I.C.	£ 8.10	Hardware and Wire Pack	£ 1.45
Integrated Circuit Pack	9.25	Case, Two-tone p.v.c.-faced steel, punched and lettered (+95p P. & P.)	5.75
Displays and Filter Pack	7.78	Min BNC Sockets (50 ohm)	0.65
Semiconductor and Diode Pack	2.47	Min BNC Plugs (50 ohm)	0.70
Resistor and Capacitor Pack	3.10	500MHz Prescaler Kit	1.78
Logic and Display P.C.B.s	4.84	SP8631B 500MHz I.C.	8.96
5MHz Crystal	3.45	NE592 Wideband Video Amp	1.43
Transformer 8-0.8V 0.5A (+75p P. & P.)	2.48	D.F.M. Reprint (post free)	0.50
Switches, Knob, BNC's etc.	4.15		

NEW! Hi-Z Buffer Kit enables D.F.M. to count below 100Hz £6.50 (inc. P & P)

G8CZW Digital Voltmeter

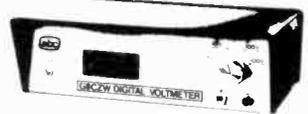

Complete kit £44.30 inc. VAT, post free (U.K.)

ZNA116E 3 $\frac{1}{2}$ Digit I.C.	£ 6.48	Hardware and Wire Pack	£ 1.20
Integrated Circuit Pack	5.24	Case, Two-tone p.v.c.-faced steel, punched and lettered (+95p P. & P.)	5.75
Displays and Filter Pack	7.78	I.C. Sockets Pack	1.08
Semiconductor and Diode Pack	2.60	Transformer (+75p P. & P.)	2.48
Resistor Pack inc. cermet	4.64	5V Reg., 2 Rect., 2,000 μ F Cap., Mains SW., Fuse and Holder	3.75
Capacitor Pack	1.58	D.V.M. Reprint (post free)	0.35
Logic and Display P.C.B.s	2.05		
Voltage Attenuator Pack	0.68		
Range Switch 6P, 4-way	2.38		

All prices inc. VAT at the standard rate. Please add 20p P. & P. for packs. S.A.E. for full lists. Overseas—Deduct 8% off these prices.

Designer approved




ELECTRONICS (OLDHAM) LTD.
83 Lees Road, Oldham OL4 1JW
Tel. 061-624 8812

AUDIBLY SUPERIOR AMPLIFICATION

HIGH DEFINITION — 'MUSICAL' — POWER AMP MODULES

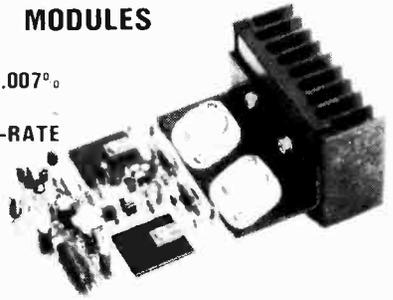- ★ T.H.D. TYPICALLY .007%
- ★ ZERO T.I.D. (SLEW-RATE LIMIT 16 V / -S)



Module size: 120 x 80 x 25 mm, using glass fibre pcb with ident and solder resist. Illustrated with light duty heatsink.

CRIMSON ELEKTRIK power amplifier modules are fast gaining a reputation as the best sounding, most musical modules available. Perhaps the most important features of this design are exceptional freedom from crossover distortion (due to the use of output triodes) and zero T.I.D. The amplifier is protected against open and short circuit loads and yet will drive a highly reactive lower impedance load which is more representative of a real loudspeaker. Square waves maintain their rise times up to full power whilst simulated electrostatic loads are easily handled with negligible overshoot and a settling time of 12 μ s. Other specs: S/N > 110dB. Rise time 10 μ s. Sensitivity 775mV. DC coupling. 5Hz-35kHz (-3dB) THD < 0.15%. 100mW clipping, 500Hz.

CRIMSON ELEKTRIK power supplies are in kit form for maximum flexibility and feature a low field silicone toroidal transformer with a 120-240V primary and screen, two large capacitors bridge rectifier and all fixings. Heatsinks are attractive black anodised extrusions, 80mm wide.

POWER AMP MODULES	HOME	EUROPE
CE 508 50W/8ms 8 ohms 35v dc	£16.30	£16.30
CE 1004 100W/8ms 3 ohms 35v dc	£19.22	£19.00
CE 1008 100W/8ms 8 ohms 35v dc	£23.22	£22.70

POWER SUPPLIES	HOME	EUROPE
CPS 1 For 24CE508 or 14CF1004	£12.85	£14.20
CPS 2 For 24CE1004 or 2 or 34CE608	£14.55	£17.90
CPS 3 For 24CE1008	£15.85	£19.20

HEATSINKS	Home	EUROPE
Light Duty 50mm x 2 C W	90	£2.40
High power 100mm x 1.3 C W	£1.60	£2.40
Disc group 150mm x 1.1 C W	£2.30	£3.85

CRIMSON ELEKTRIK (PE)
1A STAMFORD STREET, LEICESTER LE1 6NL.
Telephone: (0533) 537722.

Home prices include VAT and carriage. Payment by cheque. PO COD 60p (£50 limit). Export no problem. European prices include carriage, insurance and handling payment in Sterling by bank draft, PO, International Giro or Money Order. Outside Europe please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price list on request. Suitable pre-amp circuit 20p.

SPECIAL OFFER

NO EXTRA CHARGES FOR THIS MONTH
TOP SPEC IN 914 Packet of 10 25p.
All Prices Inc. VAT and P. & P. U.K. only

TTL	74 Series	7494	83p	CMOS	R.C.A.	CD4050	80p	CD4082	23p
7400 13p	7441 74p	7495 77p	7495 77p	CD4000 18p	CD4022 84p	CD4054 120p		CD4086 24p	
7401 15p	7442 74p	7496 77p	7496 77p	CD4001 18p	CD4023 21p	CD4055 180p		CD4088 10p	CD4088 10p
7402 18p	7443 123p	7497 130p	7497 130p	CD4002 18p	CD4024 83p	CD4056 180p		CD4090 117p	CD4090 117p
7403 18p	7444 123p	7498 130p	7498 130p	CD4003 18p	CD4025 29p	CD4057 180p		CD4091 117p	CD4091 117p
7404 22p	7447 182p	7499 130p	7499 130p	CD4004 18p	CD4026 190p	CD4058 180p		CD4092 117p	CD4092 117p
7405 22p	7448 130p	7499 130p	7499 130p	CD4005 18p	CD4027 50p	CD4059 180p		CD4093 117p	CD4093 117p
7406 44p	7454 18p	7499 130p	7499 130p	CD4006 18p	CD4028 82p	CD4060 22p		CD4094 117p	CD4094 117p
7407 44p	7470 20p	7499 130p	7499 130p	CD4007 18p	CD4029 82p	CD4061 110p		CD4095 117p	CD4095 117p
7408 23p	7472 20p	7499 130p	7499 130p	CD4008 18p	CD4030 82p	CD4062 22p		CD4096 117p	CD4096 117p
7409 23p	7473 20p	7499 130p	7499 130p	CD4009 18p	CD4031 130p	CD4063 22p		CD4097 117p	CD4097 117p
7410 15p	7475 20p	7499 130p	7499 130p	CD4010 18p	CD4032 82p	CD4064 110p		CD4098 117p	CD4098 117p
7411 24p	7475 40p	7499 130p	7499 130p	CD4011 18p	CD4033 130p	CD4065 110p		CD4099 117p	CD4099 117p
7412 24p	7476 40p	7499 130p	7499 130p	CD4012 20p	CD4034 130p	CD4066 110p		CD4100 117p	CD4100 117p
7413 30p	7480 40p	7499 130p	7499 130p	CD4013 50p	CD4035 130p	CD4067 110p		CD4101 117p	CD4101 117p
7414 41p	7482 81p	7499 130p	7499 130p	CD4014 50p	CD4036 130p	CD4068 110p		CD4102 117p	CD4102 117p
7418 33p	7483 90p	7499 130p	7499 130p	CD4015 67p	CD4037 130p	CD4069 110p		CD4103 117p	CD4103 117p
7417 33p	7485 100p	7499 130p	7499 130p	CD4016 50p	CD4038 130p	CD4070 117p		CD4104 117p	CD4104 117p
7420 18p	7486 30p	7499 130p	7499 130p	CD4017 110p	CD4039 130p	CD4071 117p		CD4105 117p	CD4105 117p
7425 20p	7489 30p	7499 130p	7499 130p	CD4018 85p	CD4040 130p	CD4072 117p		CD4106 117p	CD4106 117p
7427 20p	7490 37p	7499 130p	7499 130p	CD4019 85p	CD4041 130p	CD4073 117p		CD4107 117p	CD4107 117p
7430 20p	7491 82p	7499 130p	7499 130p	CD4020 110p	CD4042 130p	CD4074 117p		CD4108 117p	CD4108 117p
7432 20p	7492 57p	7499 130p	7499 130p	CD4021 90p	CD4043 130p	CD4075 117p		CD4109 117p	CD4109 117p
7437 20p	7493 57p	7499 130p	7499 130p		CD4044 130p	CD4076 117p		CD4110 117p	CD4110 117p
					CD4045 150p	CD4077 117p		CD4111 117p	CD4111 117p
					CD4046 131p	CD4078 24p		CD4112 117p	CD4112 117p
					CD4047 85p	CD4079 24p		CD4113 117p	CD4113 117p
					CD4048 65p	CD4080 23p		CD4114 117p	CD4114 117p

DIODES	TRANSISTORS
CA3028 85p	BC148 10p
CA3046 90p	BC149 10p
CA3052 152p	BC151 10p
CA3078 136p	BC158 10p
CA3080 57p	BC159 10p
CA3089 230p	BC162 10p
CA3090 327p	BC169 12p
CA3130 133p	BC171 12p
CA3140 74p	BC172 12p
CA3160 140p	BC173 12p
LM301 39p	BC177 18p
LM308 54p	BC178 18p
LM380 100p	BC179 18p
LM391 100p	BC182L 13p
LM471 10p	BC183L 13p
LM474 24p	BC184L 13p
LM474 24p	BC185 13p
LM474 24p	BC186 13p
LM474 24p	BC187 13p
LM474 24p	BC300 13p

SWITCHES	ROTARY SWITCHES	TRANSFORMERS (Mains prim 220-240V)
Toggle	1 Pole 12 way 46p	L744 60p
Large DPST 27p	2 Pole 2 way 46p	LT700 60p
DPDT 35p	2 Pole 4 way 46p	6-0-6 100MA 83p
SDT SPST 86p	2 Pole 6 way 46p	9-0-9 74MA 87p
DPDT 75p	3 Pole 2 way 46p	12-0-12 100MA 96p

SAXON ENTERTAINMENTS LTD

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,
TWIN SPEAKERS & LEADS

Standard 100W

£225 or Deposit **£28.80**
12 Months @ £21.18 or 24 Months @ £11.81

Super 200W

£275 or Deposit **£32.80**
12 Months @ £25.89 or 24 Months @ £14.44

GXL 200W (with twin 200 watt cabinets)

£349 or Deposit **£42.72**
12 Months @ £32.49 or 24 Months @ £18.11

BSR Decks – 17,000 Line Loudspeakers – Rugged Aluminium Trimmed Cabinets – Cue Light And Phones Output – Slave Output – Deck Lights/Motor Starts (GXL)

COMPLETE STEREO
ROADSHOWS – BUILT IN
SOUND TO LIGHT/SEQUENCER
& DISPLAY
TWO YEAR GUARANTEE

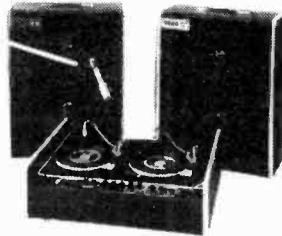


illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & iiiiic with monitoring facilities – override and are supplied complete with sound to light + sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

MINI DISCO 100 WATT MONO SYSTEM

£159.50 Deposit **£22.66**

12 Months @ £14.60
or 24 Months @ £8.14

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system **£7.50**
EM507 Electret Mic **£15.00**
ECM 81 Electret Mic **£19.95**
Boom Stand **£15.50**
Carriage on all disco systems **£10.00**
(Included in H.P. Prices)

**10% Deposit Terms
On All Orders
Over £150 – 12 or 24
Months – Low Interest**

D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS

SA308 30W 8 ohms 45V	£9.95*	SUPPLY FOR TWO MODULES	£10.90*
SA604 60W 4 ohms 50V	£13.25	SUPPLY FOR TWO MODULES	£13.50
SA608 60W 8 ohms 65V	£14.25	SUPPLY FOR TWO MODULES	
SA1204 120W 4 ohms 75V	£15.95	SUPPLY FOR ONE MODULE	£22.50
SA1208 120W 8 ohms 95V	£21.00	SUPPLY FOR TWO MODULES	
SA2404 240W 4 ohms 95V	£29.50	SUPPLY FOR ONE MODULE	

0.2% Distortion, 30Hz-20, KHz ± 2dB, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers – D.C. & Output Fuses fitted.

TOP QUALITY COMPONENTS THROUGHOUT



DISCO MIXERS – COMPLETE OR MODULAR



MONO OR STEREO
WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted – full instructions supplied.

FEATURES INCLUDE:


Twin Deck – Mic & Tape Inputs – Wide range bass & treble controls – Full headphone monitoring – Crossfade – Professional standard performance.

MODULES	
Mono module	£22.50
Stereo module	£33.50
Panel	£3.95
Kit of knobs/sockets etc	£5.50
COMPLETE MIXERS (with case)	
Mono 18V	£39.50
Stereo 18V	£57.50
Mono mains	£45.75
Stereo mains	£63.75

COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!



Lighting Control Unit Mk II	£44.50
4kW Sequencer + Sound Light + Dimmers	
+ Automatic Level Integrated Logic	Module £32.50
Circuitry	Panel £2.95
Three Channel Sound to Light	£26.75
3kW 1-240W input – master	Module £19.75
Plus channel controls	Panel £2.95

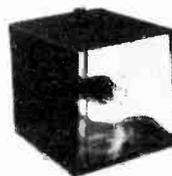

STROBE UNITS

Pro-Strobe 4-6 Joules **£37.50**
Super Strobe 2-3 Joules **£22.50**
(Pro-Strobe has external trigger facility).

SPARES & ACCESSORIES – LOUDSPEAKERS & CABINETS

Rope Lights – Red or Multicolour	£22.00	Melos Echo Chamber	£59.00
per 12 ft.		Headphones	£7.50*
Rope Light Controller for up to 120 ft	£30.00	Sirens: English Police, USA Police,	
Fuzz Lights–Red/Blue/Yellow/Green	£22.80	Destroyer, Alien Voice Simulator	£7.50
Magnetic Cartridge Equalisers	£3.50*	Bulgin 8 way lighting plug/socket	£1.90

PROJECTORS – PLUTO – NEW LOW PRICES!!! CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten	£34.00	Liquid wheels	£7.50
P500 100W Q.I.	£69.50	Cassettes	£8.00
P500 250W Q.I.	£79.50	Picture wheels from	£4.75
		(Wide choice available)	

100 Watt Chassis Loudspeakers 12"	£23.50	18"	£47.50	(Add £1.50 corr.)
Empty Loudspeaker Cabinets: Small 12"		Large 12"	£21.50	Small 2 x 12"
	£15.50, Large 2 x 12"		£28	£22.50

Projector lamps: A1167 **£2.90**, M6 **£5.65**.
100W Spot lamps Red/Blue/Yellow/Green
£1.50 ea £13.50 for 10
MD Spot Banks: 3-way 300W **£19.50**,
4-way 400W **£22.50**.
Bubble machines (optikinetics) **£36.50**


Strobe tubes 80W **£8.50**
ICI Vynide 50" wide **£3.50** Metre
Kickproof Grille 24" wide **£3.25** Metre
Kick Resistant Grill 50" wide **£3.25** Metre.
FULL RANGE OF RE-AN PRODUCTS IN STOCK
SEND FOR OUR BROCHURE NOW!!

PIEZO HORNS only £7.50 YES! – only £7.50

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an
UNBEATABLE PRICE

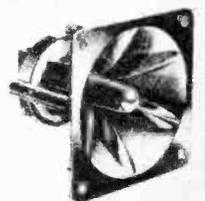No crossover required 4kHz – 30kHz rated
75W/8 ohms 150W/4 ohms use two per 100W
amplifier – Full instructions supplied.





PACKAGE P.A. SYSTEMS (2 Year Guarantee)

Complete with PIEZO horn columns fitted with 100 watt units (100 watt system illustrated)


100 Watt £145
Deposit £19.70

12 Months @ £13.66 or 24 Months @ £7.61

200 Watt £225
Deposit £28.80

12 Months @ £21.18
24 Months @ £11.81

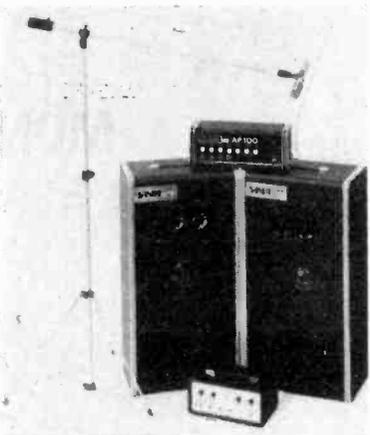These systems come complete with a Four Channel Amplifier, Leads etc. The 200 Watt system features Twin 100 Watt drive units in each cabinet.




ALSO ILLUSTRATED:

Melos Echo Unit £59.00 Boom Stand £15.50 Electret Mic ECM81 £19.95* Floor Stands £9.90 EM507 Mic* £15.00 Phasers £19.80

D.I.Y. MODULES FOR P.A. SYSTEMS Mono or Stereo

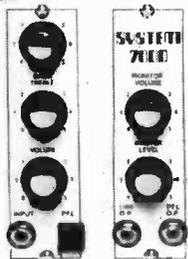Make your own mixer - Mono/Stereo - up to 20 channels with these, easy to wire modules - Available as PCB's or assembled on panels.



Input Stages Up to 20	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Mixer/Monitor (One only per system)	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Power supply for up to 20 channels		£9.50	Blank panel	£1.00


Send for free brochure for complete specification

Saxon AP100 Amplifier £45

Four mixing inputs - 100W into 4 ohms
Wide range bass & treble controls
+ master - Twin outputs

Saxon 150 Amplifier £59

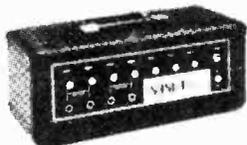Four mixing inputs - 100W into 8 ohms
150W into 4 ohms - wide range bass & treble controls + master



All prices subject to 8% VAT except where asterisked (12 1/2%)
Shop premises open Mon to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm
Mail order dept open Mon to Fri 10 am - 4 pm - Ring 01-684 6385

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclay Card Number NOT THE CARD.

By Phone You may order COD, Access or Barclay Card.

Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS LTD.

327 Whitehorse Road, Croydon, Surrey.
All Enquiries Large SAE Please Brochures on request

WHAT'S NEW?

ME, semiconductor teaching kit



the most MODERN, RAPID, ECONOMIC way to master space age electronics. Starting even from ZERO, by performing over,

100 EXPERIMENTS
and creating more than 20 practical applications

You learn all about the most up to date electronic circuits: how to calculate, repair, and design them, while pursuing your favorite hobby. Start from scratch, or improve your present knowledge. Train and earn money in your spare time turn your pastime into valuable job opportunities. Compare our price: you receive the entire course, "mini laboratory" and components for LESS than the price of the components alone.

COMPLETE KIT: nothing else to buy*

you get:

- instruction manual : over 200 pages of detailed step-by-step instructions -starting from scratch, explains basic laws and physics of Electricity, semiconductor principles and operation electronic circuits : from diodes (including diac, zener) transistors, triacs to integrated circuits (C.MOS, operational amplifiers) etc...
 - Over 200 Electronic components : aerospace technologic printed circuit experiment board, phototransistor, triac, thyristor I.C.S Transistors (including FET, MOSFET) LEDS + résistors , capacitors, speaker, milliammeter, potentiometers, variable capacitor, etc... etc... etc...
 - measuring instruments (you assemble yourself from among components furnished in kit.)
- ELECTRONIC VOLTMETER, LOW FREQUENCY MEASURING AMPLIFIER, LOGIC INDICATORS, REGULATED POWER SUPPLY, MILLIAMMETER.


you perform:

- over 100 DIFFERENT EXPERIMENTS : from the most basic voltage measurements to radio transmitter circuits and including HI FI, Flip Flops, Ic applications, triac use, etc... etc... etc...

you construct

- more than 20 complete functional systems : light modulator, high fidelity amplifier, radio control set, radio receiver and transmitter, electronic gadgets and games and many, many more.

* Hand tools not furnished.

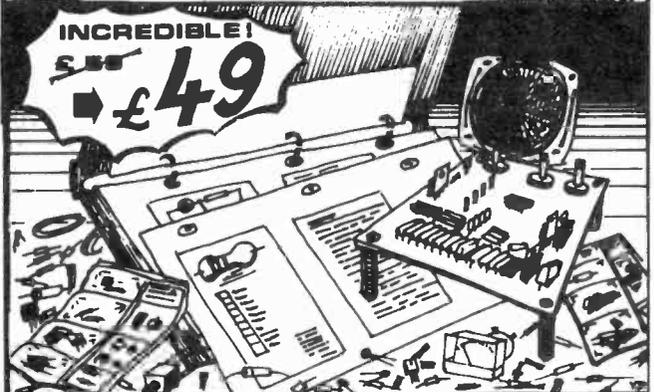

INCREDIBLE!

£49

SAVE £10 mail coupon today - SAVE £10

SAGA ENGLAND: P.O. Box 401
Kingsmead, Kings Lane, Chipperfield,
Nr. King's Langley, Herts. WD4 9PB

Please send me (QTY) IK2 teaching Kit(s)
I enclose Cheque/Postal order for £

NAME _____
ADDRESS _____

SAGA FRANCE !! SEE PROMPT HELPAD POST CODE
DELCO RECORDS FRANCE.

AUDIO MODULES - ALL REDUCED! TRANSISTOR PRICES SLASHED! MANY PAKS 33% OFF

BI-PAK GREAT SPACE

WE NEED THE SPACE

SPECIAL OFFER!

THYRISTORS

No. THY1A/50	1 Amp.	50 volt	T05	18p
No. THY1A/400	1 Amp.	400 volt	T05	32p
No. THY3A/50	3 Amp.	50 volt	T064	25p
No. THY3A/200	3 Amp.	200 volt	T064	32p
No. THY3A/400	3 Amp.	400 volt	T064	40p
No. THY5A/50	5 Amp.	50 volt	T066	25p
No. THY5A/400	5 Amp.	400 volt	T066	40p
No. THY5A/600	5 Amp.	600 volt	T066	50p
No. C106/4	6 Amp.	400 volt	T0220	42p

TRIAC

SB4	8 Amp.	400 volt	T0220 Plastic (Non Isolated Tab)	80p
-----	--------	----------	----------------------------------	-----

DIACS

BR100				15p
D32				15p

SWITCHES

No. 16178	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF - 10µF	
16202	18 Electrolytics	10µF - 100µF	
16203	18 Electrolytics	100µF - 680µF	
All 3 at SPECIAL PRICE of £1.20*			
16160	24 Ceramic Caps	22pF - 82pF	
16161	24 Ceramic Caps	100pF - 390pF	
16162	24 Ceramic Caps	470pF - 3300	
16163	21 Ceramic Caps	4700pF - 0.047µF	
All 4 at SPECIAL PRICE of £1.60			

RESISTOR PAKS

Order No.				
16213	60½W.	100 ohm - 820 ohm		
16214	60½W.	1K - 8.2K		
16215	60½W.	10K - 82K		
16216	60½W.	100K - 820K		
All 4 at SPECIAL PRICE of £1.60*				
16217	40½W.	100 ohm - 820 ohm		
16218	40½W.	1W - 8.2K		
16219	40½W.	1K - 8.2K		
16220	40½W.	100K - 820K		
All 4 at SPECIAL PRICE of £1.60*				

TRANSISTOR FALL-OUT PAK, GERM, SILICON, POWER, NPN, PNP. ALL MIXED. YOURS TO SORT AND TEST.

Approx. 500 Pieces.
Order No. S23
£1.25 per pack.

VOLTAGE REGULATORS

Positive			
No. MVR7805	µA7805	T0220	85p
No. MVR7812	µA7812	T0220	85p
No. MVR7815	µA7815	T0220	85p
No. MVR7818	µA7818	T0220	85p
No. MVR7824	µA7824	T0220	85p
Negative			
No. MVR7905	µA7905	T0220	£1.10
No. MVR7912	µA7912	T0220	£1.10
No. MVR7915	µA7915	T0220	£1.10
No. MVR7918	µA7918	T0220	£1.10
No. MVR7924	µA7924	T0220	£1.10

µA723C T099	38p	72723 14 pin Dil	38p
LM309K T03	£1.20		

MICROPHONES

DYNAMIC DUAL IMPEDANCE UNI DIRECTIONAL CARDIOID MICROPHONE
Impedance 600 ohms and 50K. Response 50-14,000 Hz. Sensitivity 54db at 50K.
Size 1½" Dia. x 6½" Long
Order No. 1328 £7.50*

DYNAMIC CASSETTE MIC

Fitted with On/Off switch. 1 metre of tough lead with floating 2.5 and 3.5 mm plugs.
Impedance 200 ohms. Sensitivity 90db.
Frequency 90-10,000 Hz.
Size 20mm Dia. x 120mm Long
Order No. 1326 £1.15*

LOGIC PROBE

A pocket size instrument capable of detecting T.T.L., D.T.L. Flip Flop and other pulse circuits. It is easy to use and operates from the 5V. D.C. supply of the circuit under test. The logic levels are indicated by 2 red LED's one for High and the other for Low. There is also a green LED for the Pulse Mode of the unit.
No. S69 Our Special Price £15.95.

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	9p	TIP32C	36p	2N1893	25p
AC128	16p	BC182	9p	BF197	12p	TIP41A	34p	2N2218	18p
AC128K	24p	BC182L	9p	BF200	25p	TIP41B	35p	2N2218A	18p
AC176	16p	BC183	9p	BF229	22p	TIP41C	36p	2N2219	18p
AC176K	24p	BC183L	9p	BFX84	18p	TIP42A	36p	2N2219A	18p
AC187	16p	BC184	9p	BFY50	12p	TIP42B	37p	2N2221	15p
AC187K	26p	BC184L	9p	BFY51	12p	TIP42C	38p	2N2221A	16p
AC188	16p	BC212	10p	BFY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	BC212L	10p	MPSA05	22p	TIP3055	62p	2N2222A	16p
AD161/162 MP	80p	BC213	10p	MPSA06	22p	ZTX107	6p	2N2369	10p
AF139	30p	BC214	10p	MPSA55	22p	ZTX108	6p	2N2904	14p
AF239	30p	BC214L	10p	MPSA56	22p	ZTX109	7p	2N2904A	15p
8C107	6p	BC251	10p	OC44	12p	ZTX300	7p	2N2905	14p
8C108	6p	BCY70	12p	OC45	12p	ZTX301	7p	2N2905A	15p
8C109	6p	BCY71	12p	OC71	9p	ZTX302	9p	2N2906	12p
8C118	10p	BCY72	12p	OC72	12p	ZTX501	10p	2N2907	12p
8C147	8p	BD115	40p	OC75	10p	ZTX502	12p	2N2907A	13p
8C148	8p	BD131	37p	OC81	14p	2N696	10p	2N2926G	8p
8C149	8p	BD132	37p	TIP29A	35p	2N706	7p	2N3053	12p
8C154	8p	BF115	17p	TIP29B	36p	2N708	8p	2N3055	35p
8C157	9p	BF167	19p	TIP29C	38p	2N708	8p	2N3072	7p
8C158	9p	BF173	20p	TIP30A	36p	2N1302	12p	2N3703	7p
8C159	9p	BF180	25p	TIP30B	37p	2N1303	15p	2N3704	6p
8C169C	9p	BF181	25p	TIP30C	38p	2N1304	15p	2N3903	11p
8C170	6p	BF182	25p	TIP31A	32p	2N1307	18p	2N3904	11p
8C171	6p	BF183	25p	TIP31B	33p	2N1309	22p	2N3905	11p
8C172	6p	BF184	25p	TIP31C	34p	2N1309	22p	2N3906	11p
8C173	7p	BF185	25p						

DIODES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	8AX16/		BY216	30p	OA85	7p	IS44	3p
AAZ13	4p	OA202	5p	BY217	28p	OA90	6p		
BA100	6p			BY218	28p	OA91	7p	IN5400	10p
BA115	5p	BY100	15p	BY219	28p	OA95	7p	IN5401	11p
BA144	5p	BY127	10p					IN5402	12p
BA148	10p	BY210	32p	OA47	5p	IN34	5p	IN5404	13p
BA173	10p	BY211	32p	OA70	5p	IN60	6p	IN5406	16p
BAX13/		BY212	32p	OA79	7p	IN94	4p	IN5407	17p
OA200	5p	BY213	30p	OA81	7p	IN4148	4p	IN5408	19p

LINEAR I.C.'s

TBA800	12 pin QIL	*75p	UA711C T099	25p	UA748 T099	28p
TBA810	12 pin QIL	*£1.00	UA703 T099 (Plastic)	20p	72558 (Dual 748) T099	45p
TBA820	14 pin QIL	*80p	741P 8 pin DIL	18p	MC1310P 14 pin DIL	*£1.25
LM380	14 pin DIL	*80p	7274 14 pin DIL	20p	76115 14 pin QIL	*£1.25
LM381	14 pin DIL	*£1.35	UA741C T099	20p	NE555 8 pin DIL	32p
72709	14 pin DIL	28p	72747 14 pin DIL	55p	NE556 14 pin DIL	60p
UA709 T099	28p		748P 8 pin DIL	28p	SL414A 10 pin	*£1.80

NEW CONSIGNMENT ZN 414 RADN CHIP 75p*

OPTOELECTRONICS

Displays		2nd QUALITY LED PAKS			
No. 1510	707 LED Display	70p each	No. 1507	10 x LED's Assorted	75p
No. 1511	747 LED Display	£1.50 each	LED CLIPS		
No. S53	DL33 Triple 7 Segment LED Display Character height .11" Common Cathode 12 pin DIL	30p each	No. 150B/125	.125	5 for 12p
			No. 150B/2	.2	5 for 15p
LED's		SPECIAL REDUCTIONS			
No. S51	Red TIL209 (5 x .125")	50p	No. 1514	NORP 12	45p each
No. S52	Red FLV117 (5 x .2")	50p	No. S76	OC71	5 for £1.00
No. 1502	Green .125"	18p each	No. S83 5	NIXIE Tubes ITT 5870 ST	£2.00 (including Data)
No. 1505	Green .2"	18p each	No. S77	Neon Indicator Lamps 230V A.C. State Colour (Red, Amber and Green.)	25p each
No. 1503	Yellow .125"	18p each			
No. 1506	Yellow .2"	18p each			
No. S82	Clear .2" (illuminating red)	12p			

D.I.Y. PRINTED CIRCUIT KIT

Contains 6 pieces of copper laminate board, box of etchant powder, measure, tweezers, marker pen, high quality pump drill, Stanley knife and blades and 6 in. metal rule.
Full easy to follow instructions.
Order No. S64 Sale Price £5.50

P.C.B. BOARDS

S61	8 pieces B" x 3½" (approx.) single sided paper	50p
S62	4 pieces B" x 3½" (approx.) single sided fibreglass	50p
S63	3 pieces 7" x 3½" (approx.) double sided fibreglass	50p

ETCH RESIST PENS

Order No. 1609 50p each

SOLDER

5m of 18 sw Multi-core Solder.
Order No. S60 50p

I.C. INSERTION EXTRACTION TOOL

Order No. 2015 30p

MAMMOTH I.C. PAK

Approx. 200 Pieces. Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked - you to identify.
Order No. 16223 £1.00

POWER SUPPLY STABILIZER BOARD

Unused ex-equipment stabilizer board, Input 30V. D.C. Output 20V. Complete with circuit diagram.
Order No. S81 £1.25

P.O. RELAYS

S85 - 2 Off Post Office relays 40p

BATTERY HOLDERS

to take 6 x HP7's
Order No. 202 10p each

EX. G.P.O. MICROSWITCHES

Order No. S51 4 for 50p

CABLE CLIPS

S84 - 50 2.5mm round single pin fixing 30p

UNTESTED SEMICONDUCTOR PAKS

Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/B1	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like IN4148	40p
No. 16134	50 750mA Sil. top hat Rects. like OA70/B1	40p
No. 16135	20 3 amp Sil. stud Rect.	40p
No. 16136	50 400mw Zeners D.O.7 case	40p
No. 16137	30 PNP Plastic trans. like BC107/8	40p*
No. 16138	30 PNP Plastic trans. like 8C177/8	40p*
No. 16139	25 PNP trans. like 2N697/2N1711 T039	40p
No. 16140	25 PNP trans. like 2N2905 T039	40p
No. 16141	30 NPN trans. like 2N706 T018	40p
No. 16143	30 PNP Plastic trans. like 2N3906 40p*	
No. 16144	30 PNP Plastic trans. like 2N3906 40p*	
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN to 3 Power trans. like 2N3055	80p

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 24 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

TRANSISTOR SOCKETS

No. S71	15 x T018 Sockets	£1.00
No. S72	10 x T05 Sockets	£1.00

MOUNTING PADS

No. S73	50 Mixed Transistor Pads T018 and T05	40p
---------	---------------------------------------	-----

TRANSISTOR HEATSINK PAK

20 Assorted types. T01, T05, T018, T092
Our Mix
Order No. S75 60p

TRANSISTOR INSULATING KITS

Mica washers and bushes assorted types i.e. T0220, T066, T03 etc. Approx. 100 pieces. (Approx. 40 sets).
Order No. S74 50p

DARLINGTON POWER TRANSISTORS

70 watt 8 amp NPN and PNP in plastic case 199 High Voltage (Typ. 80V). High gain. 10 pieces 5 NPN and 5 PNP. Data Sheet supplied.
Order No. S78 £1.00 per Pak

MATCHED PAIRS OF PNP GERMANIUM MED. POWER TRANS

SAVING SALE BI-PAK

YOU MAKE THE SAVING!

OPT FOR OPTOELECTRONICS! PRINTED CIRCUIT KITS, BOARDS & PENS.

SILICON RECTIFIERS - 1/2 AMP. G.E.

No. S48	40 x 50V	60p
No. S49	30 x 200V	60p
No. S50	20 x 700V	60p

G.E. HIGH VOLTAGE SILICON RECTIFIERS

GR559	10mA 14KV (14,000)	20p each
GA432	1 AMP. 2 KV (2,000)	20p each
FD025	2.5 KV Voltage Doubler	20p each

POTENTIOMETERS

Slider 40mm TRAVEL		
Order No.	Description	Price
16191	6 x 470 Ohm LIN Single	40p*
S24	6 x 1 K LIN Single	40p*
S25	6 x 5 K LIN Single	40p*
16192	6 x 10 K LIN Single	40p*
S26	6 x 10 K LOG Single	40p*
16193	6 x 22 K LIN Single	40p*
16195	6 x 47 K LOG Single	40p*
16194	6 x 47 K LIN Single	40p*
S27	6 x 100 K LIN Single	40p*
S28	6 x 100 K LOG Single	40p*
S29	6 x 500 K LOG Single	40p*
Slider 60mm TRAVEL		
S30	6 x 2.5 K LOG Single	40p*
S31	6 x 10 K LIN Single	40p*
S32	6 x 50 K LIN Single	40p*
S33	6 x 250 K LOG Single	40p*
S34	4 x 5 K LOG Dual	40p*
S35	4 x 10 K LIN Dual	40p*
S36	4 x 100 K LOG Dual	40p*
S37	4 x 1.3 MEG LOG Dual	40p*
S38 MIXED SLIDER POTS - VARIOUS VALUES AND SIZES - OUR MIX ONLY £1.00*		
S39 6 x CHROME SLIDER KNOBS 40p*		

WIREWOUND

A range of wirewound single gang pots. with linear tracks of 1 watt rating.

Order No.	Value	Order No.	Value
1891	10 ohms	1894	100 ohms
1893	47 ohms	1895	220 ohms
1896	470 ohms	1898	2K2
1897	1K	1899	4K7

NOW 35p* each

16173	15 Rotary Potentiometers. Assorted values and types.	40p*
16186	25 Pre-sets Assorted Values and types	40p*

MULTI-TURN PRE-SETS

S40 3 x 100 K LIN ONLY 50p*

AUDIO PLUG AND SOCKET PAKS

Order No.	Description	Price
S1	5 x 3.5 mm Plastic Jack Plugs	40p*
S2	5 x 2.5 mm Plastic Jack Plugs	40p*
S3	4 x Std. Plastic Jack Plugs	50p*
S4	2 x Stereo Jack Plugs	30p*
S5	5 x 5 Pin 180° DIN Plugs	50p*
S6	8 x 2 Pin Loudspeaker Plugs	50p*
S7	6 x Phono Plugs Plastic	50p*
S8	5 x 3.5 mm Chassis Sockets (Switched)	25p*
S9	5 x 2.5 mm Chassis Sockets (Switched)	25p*
S10	4 x Metal Std. Chassis Switched Jack Sockets	50p*
S11	2 x Stereo Jack Sockets with instruction leaflet for H/Phone connection.	50p*
S12	5 x 5 Pin 180° DIN Chassis Sockets	40p*
S13	8 x 2 Pin DIN Chassis Sockets	50p*
S14	6 x Single Phono Sockets	40p*

AUDIO LEADS

Order No.	Description	Price
117	A.C. Mains connecting lead for cassette recorders and radios Telefunken type	45p*
118	5 pin DIN headphone plug to stereo socket	78p*
119	2 x 2 pin plug to inline stereo socket for headphones	60p*
123	20 ft. of coiled guitar lead	£1.15*
124	3 pin to 3 pin DIN plug	50p*
125	Audio lead 5 pin plug to 5 pin DIN plug	50p*
126	Audio lead 5 pin DIN plug to tinned open ends	50p*
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug - Mirror Image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p*
132	10 metre lead 2 pin DIN plug	65p*

HEAVY GAUGE BLACK PLASTIC BOX

With aluminium lid and fixing screws. Size 6 1/2" x 3 1/2" x 2" Order No. S16 Only 75p

74 SERIES TTL ICs

TYPE	QUANTITY		TYPE	QUANTITY		TYPE	QUANTITY	
	1	100		1	100		1	100
	Ep	Ep		Ep	Ep		Ep	Ep
7400	0.09	0.08	7448	0.70	0.68	74122	0.45	0.42
7401	0.11	0.10	7450	0.12	0.10	74123	0.65	0.62
7402	0.11	0.10	7451	0.12	0.10	74141	0.68	0.65
7403	0.11	0.10	7453	0.12	0.10	74145	0.75	0.72
7404	0.11	0.10	7454	0.12	0.10	74150	1.10	1.05
7405	0.11	0.10	7460	0.12	0.10	74151	0.65	0.60
7406	0.28	0.25	7470	0.24	0.23	74153	0.70	0.68
7407	0.28	0.25	7472	0.20	0.19	74154	1.20	1.10
7408	0.28	0.25	7473	0.26	0.22	74155	0.70	0.68
7409	0.12	0.11	7474	0.24	0.23	74156	0.70	0.68
7410	0.09	0.08	7475	0.44	0.40	74157	0.70	0.68
7411	0.22	0.20	7476	0.26	0.25	74160	0.95	0.85
7412	0.22	0.20	7480	0.45	0.42	74161	0.95	0.85
7413	0.26	0.25	7481	0.90	0.88	74162	0.95	0.85
7416	0.28	0.25	7482	0.75	0.73	74163	0.95	0.85
7417	0.26	0.25	7483	0.88	0.82	74164	1.20	1.10
7420	0.11	0.10	7484	0.85	0.80	74165	1.20	1.10
7422	0.19	0.18	7485	1.10	1.00	74166	1.20	1.10
7423	0.21	0.20	7486	0.28	0.26	74174	1.10	1.00
7425	0.25	0.23	7489	2.70	2.50	74175	0.85	0.82
7426	0.25	0.23	7490	0.38	0.32	74176	1.10	1.00
7427	0.25	0.23	7491	0.65	0.62	74177	1.10	1.00
7428	0.36	0.34	7492	0.43	0.35	74180	1.10	1.00
7430	0.12	0.10	7493	0.38	0.35	74181	1.90	1.80
7432	0.20	0.19	7494	0.70	0.68	74182	0.80	0.78
7433	0.38	0.36	7495	0.60	0.58	74184	1.50	1.40
7437	0.26	0.25	7496	0.70	0.68	74190	1.40	1.30
7438	0.26	0.25	74100	0.95	0.90	74191	1.40	1.30
7440	0.12	0.10	74104	0.40	0.35	74192	1.10	1.00
7441	0.60	0.57	74105	0.30	0.25	74193	1.05	1.00
7442	0.80	0.70	74107	0.30	0.25	74194	1.05	1.00
7443	0.95	0.90	74110	0.48	0.45	74195	0.80	0.75
7444	0.95	0.90	74111	0.75	0.72	74196	0.90	0.85
7445	0.80	0.75	74118	0.85	0.82	74197	0.90	0.85
7446	0.80	0.75	74119	1.30	1.20	74198	1.90	1.80
7447	0.70	0.68	74121	0.28	0.26	74199	1.80	1.70

Devices may be mixed to qualify for quantity price. Data is available for the above series of ICs in booklet form price 35p.

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.14	CD4018	£0.85	CD4035	£1.40	CD4056	£1.15
CD4001	£0.16	CD4019	£0.45	CD4037	£0.78	CD4069	£0.32
CD4002	£0.16	CD4020	£0.95	CD4040	£0.78	CD4070	£0.32
CD4006	£0.80	CD4021	£0.85	CD4041	£0.68	CD4071	£0.20
CD4007	£0.17	CD4022	£0.80	CD4042	£0.68	CD4072	£0.20
CD4008	£0.80	CD4023	£0.18	CD4043	£0.78	CD4081	£0.20
CD4009	£0.90	CD4024	£0.64	CD4044	£0.78	CD4082	£0.20
CD4010	£0.90	CD4025	£1.18	CD4045	£1.15	CD4510	£1.10
CD4011	£0.18	CD4026	£1.85	CD4046	£0.95	CD4511	£1.25
CD4012	£0.17	CD4027	£0.48	CD4047	£0.75	CD4516	£1.10
CD4013	£0.42	CD4028	£0.80	CD4049	£0.46	CD4518	£1.10
CD4015	£0.80	CD4029	£0.95	CD4050	£0.46	CD4520	£1.10
CD4016	£0.42	CD4030	£0.46	CD4054	£0.95		
CD4017	£0.80	CD4031	£1.80	CD4055	£1.60		

AUDIO MODULE SALE

Type	Description	Normal Price	Sale Price
AL30A	10W RMS Power Amp	£3.65*	£2.95*
AL60	25W RMS Power Amp	£4.95*	£3.55*
AL80	35W RMS Power Amp	£6.95*	£5.95
AL250	125 W RMS Power Amp	£15.95*	£14.45
SPM80	35V Power Supply	£3.75*	£3.10*
PS12	20-30V Power Supply for AL30A	£1.30*	£1.15*
PA12	Stereo Pre-Amp for AL30A	£6.70*	£5.95*
PA100	Stereo Pre-Amp for AL60/AL80	£13.75*	£12.45*
S450	Stereo F.M. Tuner	£20.45*	£18.65*
MPA30	Magnetic-Ceramic Pre-Amp	£2.85*	£2.55*
Stereo 30	Complete Audio Chassis 7W x 7W RMS	£16.25*	£14.95*

LOOK & LISTEN

GE 100 NINE CHANNEL MONO-GRAPHIC EQUALIZER MODULE

The GE100 has nine 1 octave adjustments using integrated circuit active filters. Boost and Cut limits are ±12db, Max. Voltage handling 2 V RMS, T.H.D., 0.5%, input impedance 100 K, output impedance less than 10 K. Frequency response 20 Hz-20 KHz (3db). The nine gain controls are centred at 50, 100, 200, 400, 800, 1600, 3,200, 6,400 and 12,800 Hz. The suggested gain controls are 10 K LIN sliders. (Not supplied with the module). See Paks S31 and 16192.

ONLY £19.50

SG30 Power supply board for GE100 15-0-15 Volt **£4.50**

SEND SAE FOR TECHNICAL DATA ON ANY OF THE AUDIO MODULES.


SPECIAL OFFER! COMPONENT PAKS

Order No.	Quantity	Price
16164	200 approx. Resistors mixed values. (Count by weight)	40p*
16165	150 approx. Capacitors mixed values. (Count by weight)	40p*
16167	80 1/2W Resistors mixed values	40p*
16168	5 pieces Assorted Ferrite rods	40p*
16169	2 pieces Tuning gangs MW/LW	40p*
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p*
16172	3 Micro switches	40p*
16176	20 Assorted electrolytics Trans types	40p*
16177	1 pack Assorted hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p*
16184	15 Assorted Fuses 100mA - 5 amp	40p*
16188	60 1/2W resistors mixed values	40p*
16187	30 metres stranded wire assorted colours	40p

1/2 PRICE BARGAIN!

£4 worth (Min. Value) of Electronic Project Books, Technical, Semiconductor Data and Equivs - Books of Assorted Titles. **OUR CLEARANCE PRICE £2 per bundle**

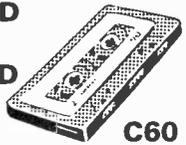SUPER SOUND SAVING METRO SOUND LOW NOISE CASSETTES



Order No. S53 **10 for £2.50***

BIB GROOVE CLEAN

Model 60. Chrome Finish Plastic Order No. 829 **£1.40***

HOT OFFER

ANTEX SOLDERING IRONS

Order No. 1931 X25 15 watt. LOW LEAKAGE **Usually £3.40 SALE PRICE £2.95**

PLUS FREE Heatshunt

1948 Model C 15 watt General purpose **Usually £3.40 SALE PRICE £2.95**

PLUS FREE Heatshunt

1939 ST3 Soldering Iron Stand suitable for either Iron. **£1.20**

NEW Siren Alarm Module

American Police screamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown, and other security purposes.

Order No. S15 **£3.50**

AVDEL BOND

Cyanocrylate adhesive bonds - plastic, rubber, transistors, components in seconds. Order No. 143 **55p per 2 gm. phial**

ORDERING

Please word your orders exactly as printed, not forgetting to include our part number.

VAT


Add 12 1/2% to prices marked* Add 8% to others excepting those marked †. These are zero.

BI-PAK

Dept. PE2, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

FOR RELIABLE JOINTS - ANTEX IRONS!

KITS FOR SYNTHESISERS, SOUND EFFECTS

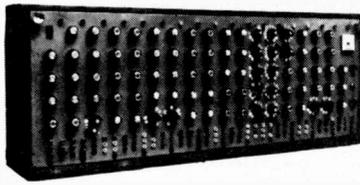

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs designed by Phonosonics.

PHOTOCOPIES of the P.E. texts for most of the kits are available—prices in our lists.

P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, output amp and mixer, power supply.

Set of basic component kits £64.25
Set of printed circuit boards £9.71

P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage, notably P.E. Minisonic, Phasing Unit, Wind and Rain, Rhythm Generator, Sound Bender, Voltage Controlled Filter, Guitar Effects Pedal and Overdrive, Fuzz, Tremolo and Wah-Wah units. The Main Synthesiser: PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp. Full details in lists.

Set of basic component kits £83.03
Set of printed circuit boards £13.20

The Synthesiser Keyboard Circuits (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and additional PSU. Full details in our lists.

Set of basic component kits £48.18
Set of printed circuit boards £7.66

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.59
Alternative component set with panel mounting switches £4.96
Printed circuit board £1.43

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) £7.84
Printed circuit board £1.81

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

Component set (incl. PCB) £2.88

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2.87

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4.48

SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektron", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set £17.69
Printed circuit board £2.33

WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3.55

AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.27
Component set and PCB, with panel switches £4.83

P.E. JOANNA (P.E. May/Sept. 75)

A five-octave electronic piano that has switchable alternative voicing of Honky-Tonk piano, ordinary piano, harpsichord, or a mixture of any of the three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The power amplifier typically delivers 24 watts into 8 ohms. The PCBs have been redesigned by ourselves making improved use of the space available.

Main power supply, tone generator, 61 envelope shapers, voicing and pre-amp circuits.

Set of basic component kits for above £75.29
Set of printed circuit boards for above £20.35
Power amplifier £15.97
Printed circuit board for power amp 95p

ELECTRONIC ORGAN

5-octave electronic organ with 5 basic voices that can be used individually or together, 5 pitches (2ft, 4ft, 8ft, 16ft, 32ft), variable attack, tremolo, vibrato, phasing, and variable sustain. Details in our list.

ORGAN CONVERSION KIT

Converts the P.E. Joanna electronic piano to also provide most of the facilities offered by the above electronic organ.

Basic component set and PCB £12.34

SYNTHESIZER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl. sw.) £7.45

GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Details in list.

SEE OTHER PAGE FOR KEYBOARDS, AND OUR LISTS FOR OTHER COMPONENTS AND ACCESSORIES STOCKED

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £3.72

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £6.86
Component set using dual rotary pot £6.20
Printed circuit board £1.62

FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £2.03

TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £3.64

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2.40

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic and electronic musical instruments alike.

Main component set (incl. PCB) £15.59
Power supply set (incl. PCB) £7.03

P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duplo, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.

Component set (incl. loudspeaker) £11.62
Printed circuit board £2.04

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs.

Standard tolerance set of components £2.96
Superior tolerance set of components £3.76
Regulated power supply (will drive 2 sets) £4.69

ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) £4.66

ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6.68

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set £4.52
Printed circuit board £1.82

WAVEFORM CONVERTER

Slightly modified from a circuit published in a German edition of "Elektron". Converts a saw-tooth waveform into four different waveforms sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw's) £8.19

VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 65-1) £8.22

RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 59-1) £5.50

NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 60-1) £3.35

SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl. PCB) £3.78

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4.58

POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £2.00 plus VAT. Optional insurance for compensation against loss or damage in post, add 35p in addition to above post and handling. Eire, C.I., B.F.P.O., and other countries are subject to Export postage rates.

DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 40p.

PHONOSONICS · DEPT. PE5N · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

MAIL ORDER AND C.W.O. ONLY
SORRY BUT NO CALLERS PLEASE

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list: Europe—send 20p, other countries—send 40p.



KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits, including the P.E. Joanna, P.E. Minisonic, and P.E. Synthesizer. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C. The keys are plastic, spring-loaded and mounted on a robust aluminium frame.

3 Octave (37 notes) £25-50, 4 Oct (49 notes) £32-25, 5 Oct (61 notes) £39-75.
Contact Assemblies for use with above keyboards: Single-pole change-over (type SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (type DP) as for P.E. Synthesizer. Special contact assembly (type 4PS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables THE SAME KEYBOARD to be used with the P.E. Synthesizer, P.E. Minisonic and the P.E. Joanna simultaneously thus avoiding the cost of more than one keyboard. See our list for other contacts.

Contact	Each	3 Octave Set	4 Octave Set	5 Octave Set
SP	£ 8-88	£11-76	£14-64	
DP	£ 9-99	£13-23	£16-47	
4PS	£ 5-30	£10-61	£25-97	£32-33

PRINTED CIRCUIT BOARDS for use with the above contacts and thus eliminating most of the inter-wiring required, are available. Details in our lists.

MORE NEW KITS!

NEW RHYTHM GENERATOR

Redesigned, improved and extended version of the PE 1974 design and including new automatic rhythm programme selector.

TUNE-PROGRAMMABLE SEQUENCER

(PE Nov. 77) The new music unit currently being published.

FORMANT SYNTHESIZER

(Elektr Magazine 1977). Very sophisticated music synthesiser for the advanced constructor and for whom cost is secondary to performance.

GUITAR SUSTAIN UNIT

(PE Oct. 77).
 Details in lists. Please send S.A.E.

SOUND-TO-LIGHT (P.E. Aurora) (P.E. Apr.-Aug. 71)

Four channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities.

Basic component set (excl. thyristors)	£15-92
Printed circuit board for above	£3-90
Power supply	£5-78
PCB for power supply	£1-79

3-CHANNEL SOUND-TO-LIGHT (P.E. Apr. 76)

A simple but effective sound-to-light controller capable of operating 3 lamps each of approximately 700 watts. Includes power supply, thyristors, and by-pass switches.
 Component set (incl. PCB) £11-95

DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.
 Basic component set £18-19
 Printed circuit board £3-45

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

Pra-Amp Module Component set (incl. PCB)	£4-22
Basic Output Circuits—combined component set with PCBs for alphaphone, cardiophone, frequency meter and visual feedback lampdriver circuits	£6-59
Audio Amplifier Module Type PC7	£7-35

SEMI CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.
 Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB Panel meter (500µA) £9-63
 £5-70

TRANSISTORS

AC128	26p
AC176	26p
BC107	14p
BC108	14p
BC109	14p
BC147	12p
BC148	12p
BC149	12p
BC157	13p
BC158	13p
BC159	13p
BC182L	12p
BC184	12p
BC187	25p
BC204	14p
BC209C	14p
BC212L	15p
BC213	15p
BC478	29p
BCY71	22p
BD131	44p
BD132	54p
BFY50	22p
BFY51	22p
BFY52	24p
BSY95A	22p
MD8001	172p
OC28	60p
OC71	20p
OC72	25p
OC84	25p
ORP12	79p
ZTX107	12p
ZTX108	9p
ZTX501	13p
ZTX503	15p
ZTX531	23p
2N706	13p
2N914	22p
2N1304	22p
2N2219	27p
2N2905	35p
2N2905A	36p
2N2907	22p
2N3053	18p
2N3054	66p
2N3055	48p
2N3702	12p
2N3703	12p
2N3704	12p
2N3819	35p
2N3820	64p
2N3823E	39p
2N4060	12p
2N5245	51p
2N5459	33p
2N5777	45p

INTEGRATED CIRTS.

318	230p	
718	TO5	40p
709	8-pin DIL	48p
723	TO5	105p
741	8-pin DIL	32p
748	TO5	63p
748	8-pin DIL	63p
µA7805	TO220	205p
µA7808	TO220	205p
µA7812	TO220	205p
µA7815	TO220	205p
µA7818	TO220	205p
AY-1-0212		650p
AY-1-6721/6		185p
CA3046		90p
MC3340		150p
SG3402N		282p

GREENWELD

443 Millbrook Road Southampton
 SO1 0HX Tel:(0703) 772501

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

* **SAVE ON TIME** - No delays in waiting for parts to come or shops to open!

* **SAVE ON MONEY** - Bulk buying means lowest prices - just compare with others!

* **HAVE THE RIGHT PART** - No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES - SENT BY RETURN OF POST. VAT INCLUSIVE PRICES

K001 50V ceramic plate capacitors, 5% . 10 of each value 22pF to 100pF. Total 210, £3.35

K002 Extended range, 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75
K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2, 2.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for £14.20

K007 Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M. E12 series. Total 610 resistors, £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mW 5%. BZY88 etc. 10 of each value from 27V to 36V, E24 series. Total 280 for £15.30
K042 As above but 5 of each value £8.70

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15.

FERRIC CHLORIDE

Anhydrous technical quality, 1lb double sealed packs. 1lb £1.00; 3lb £2.18; 10lb £5.60; 100lb £39.00

SIRENS

Work off 4 x HP7 batteries, emit very loud noise. Overall size 110 x 75 x 60mm. Use as Burglar Alarm in car, house, workshop etc. ONLY £1.95.

VERO OFFCUTS

Pack A, All 0.1"; Pack B, All 0.15"; Pack C, Mixed; Pack D, All 0.1" plain
 Each pack contains 7 or 8 pieces with a total area of 100 sq. in. Each pack is £1.30. Also available by weight, 1lb £3.45, 10lb £31.
 17 x 3 1/2" strips: 0.1" £2.20, 10 for £15; 0.15" £1.96; 0.1" plain £1.83.

TEXAS 741
8 PIN DIL
FULL SPEC.
100 off £19.50
25 off £5.50

TRANSFORMERS

Special - 12V 8A for only £4.00. 6-0-6V 100mA 85p; 9-0-9V 75mA 85p; 12-0-12V 50mA 85p; 100mA 95p; 12-0-12V 1A £2.90; 20-0-20V 2A £4.70; 20V 2.75A £4.

VERO PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type		
2518 120	65 x 40mm	£2.24
2520 150	80 x 50mm	£2.68
2522 188	110 x 60mm	£3.72

Sloping front versions:
 Type
 2523 220 174 x 100/52mm £6.90
 1798 171 x 121 x 75/37.5mm £4.65
 Gen. purpose plastic potting box 71 x 49 x 24, in black or white 40p.
 Hand controller box, shaped for ease of use in the hand, 94 x 61 x 23mm 64p.

S-DECS & T-DECS

S-DEC Breadboard £2.25
 T-DEC Breadboard £3.95

RELAYS AND SOLENOIDS

12V DC enclosed, 2 10A c/o contacts £1.00

Open construction relay with 2 10A c/o contacts, coil rated 24V AC, but works well on 6V DC 60p

240V AC enclosed, 11 pin plug in base, 3 10A c/o contacts, £1.20

240V AC open, 2 15A c/o contacts £1.50

6V miniature low profile for PC mounting, 0.1" pitch 2 pole c/o 137R coil - RS price £2.71 - our price £1.00

Solenoid, rated 48V DC, but work on 24V, 10mm push or pull action. Single hole fixing. Size 27 x 18 x 15mm. Made by Varley. Only 40p.

1977/8 CATALOGUE NOW AVAILABLE - MUCH BIGGER AND BETTER, WITH 50p DISCOUNT VOUCHERS. ONLY 30p plus 15p POST.

WIRE AND FLEX

Flex pack - 5m of 5 diff colours, thick or thin, 25m for 30p. 25 way (14/0076) cable with braided overall screen and PVC sheath, 40p/m.

POWER PACK

Wood grained metal case 90 x 80 x 75mm containing mains transformer giving 6V at 200mA, 2 co-ax sockets, PC board with 1 1/2 fuseholder R's C's etc. Only £1.

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold plated connectors enables us to offer them at less than 1/3rd their original list price! 18 way 41p 21 way 47p 32 way 72p 40 way 90p 43 way 97p 49 way 111p

SOLAR CELLS

As used on space labs etc., these tiny cells give 50µA at 0.5V in sunlight. Ideal for powering small C-MOS projects etc. Can be banked for greater power output. Size 19 x 6.5mm. 3 for £1; 10 for £3; 25 for £7; 100 for £25.

SCR PANEL

Has 12 60V 0.8A thyristors (gate current only 200µA!), MEU21, 2N3904, 1N4004 x 14, R's C's etc. Only £1.00.

MISCELLANEOUS IC'S

All supplied with data.
 MC3302 Quad comparator £1.20.
 ITT7105 LED Digit driver, 8 for £1.
 710 TO99 case Diff. comparator 40p.
 MC1469R Voltage reg. £1.50.
 ZN1034E Precision timer £2.25.
 LM1303 Dual stereo preamp £1.40.
 7M3 Diff. video amp £1.20.
 LM301 Op amp 40p.
 ITT326 2 x 2.8 x 2 x 3 1/2" TTL NAND gate, 10 for £1.
 SLD2128 Dual 128 bit static shift reg. £1.50.


Our retail shops at 21 Deptford Broadway, London, SE8 (01-692 2009) and 38 Lower Addiscombe Road, Croydon (01-688 2950) stock some of the advertised goods for personal callers only. Ring them for details.

All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

PRICES ARE CORRECT AT TIME OF PRESS.
 E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONONICS

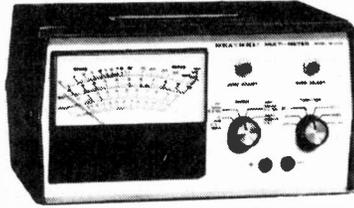
Over 200 kits in the free Heathkit Catalogue



NEW 4 Function Solid State Multimeter — One of a whole range of test equipment




NEW Digital Clock — with repeater alarm

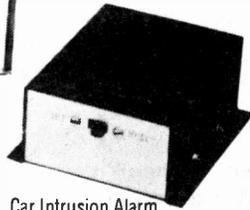

Car Intrusion Alarm — Gives a distinctive 'yelping' sound-signal the moment your car is tampered with

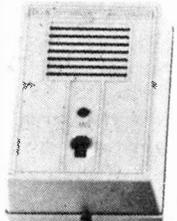Freezer Alarm — Gives audible signal if freezer temperature rises to -6°C for any reason



NEW Electronic Chess Game

Right now, there's a brand new edition of the Heathkit Catalogue — packed with hundreds of practical and fascinating items which you can build yourself.

Send for your copy now!

To Heath (Gloucester) Ltd.
Department PE 28
Bristol Road, Gloucester, GL2 6EE.

Please send a copy of the Heathkit Catalogue. I enclose 11p in stamps to cover postage only.

Name

Address



Soldering iron offer FREE

When you receive your catalogue you'll get details of this free offer worth approximately £4.75.

HEATH
Schlumberger
The world's biggest producers of electronic kits.

ACCESS AND BARCLAYCARD WELCOMED

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).



PHOENIX ELECTRONICS

(SOLENT) LTD

46 Osborne Road, Southsea, Hants

All prices include VAT
Include 20p extra for carriage

SOME SEMICONDUCTORS

BC107/8/9	11p
BC177/8/9	15p
BC204/5/6	14p
BC207/8/9	9p
BDY56	£1.72
1N4001	7p
1N4004	10p
1N4148	5p
2N2218/19/21/22	22p
2N2904/5/6/7	24p
2N3442	88p
2N3702-11	12p

RESISTORS

$\frac{1}{2}$ W carbon film (10)	18p
$\frac{1}{2}$ W metal film (5)	18p

CAPACITORS

Disc ceramic. Aluminium electrolytic. Tantalum bead.

PANEL HARDWARE

Connectors, lampholders, switches, fuses, knobs.

MISCELLANEOUS

Hand tools, instrument cases, Veroboard, relays, transformers.

SOLDERING EQUIPMENT

Weller and Adcola irons, tips, desoldering tools, instant-heat guns.

INTEGRATED CIRCUITS

DTL 930 series.
TTL 74 series.
Linear series.
Consumer circuits.

Buy More for Less Outlay with Our Bargain Packs

Please send your 1977 catalogue—free!

Name

Address

.....

C-MOS	4066	60p	7410	20p	7492	54p	74172	860p	
	4069	27p	7411	30p	7493	44p	74173	187p	
4000	20p	4070	50p	7412	20p	7494	88p	74174	100p
4001	20p	4071	25p	7413	38p	7495	65p	74175	98p
4002	20p	4072	25p	7414	96p	7496	90p	74176	123p
4006	114p	4073	26p	7416	35p	7497	35p	74177	123p
4007	20p	4076	118p	7417	40p	74100	120p	74178	110p
4008	99p	4077	48p	7420	20p	74104	73p	74179	138p
4009	57p	4081	20p	7421	40p	74105	73p	74180	106p
4010	57p	4082	25p	7422	26p	74107	39p	74181	262p
4011	20p	4083	95p	7423	32p	74109	75p	74182	83p
4012	20p	4502	123p	7425	32p	74110	50p	74184	234p
4013	51p	4510	139p	7428	107p	74111	86p	74185	187p
4014	107p	4511	150p	7427	89p	74116	251p	74190	134p
4015	114p	4512	81p	7428	81p	74120	155p	74191	134p
4016	51p	4514	264p	7430	20p	74121	38p	74192	115p
4017	114p	4515	264p	7432	29p	74122	53p	74193	115p
4018	110p	4516	123p	7433	118p	74123	61p	74194	107p
4019	62p	4518	123p	7437	39p	74125	59p	74195	102p
4020	115p	4520	123p	7438	38p	74126	59p	74196	134p
4021	101p	4522	122p	7440	20p	74128	98p	74197	130p
4022	99p	4526	122p	7442	69p	74132	75p	74198	124p
4023	20p	4527	140p	7443	130p	74142	302p	74199	199p
4024	79p	4528	115p	7444	130p	74143	348p	74221	109p
4025	20p	4531	115p	7445	105p	74144	348p	74246	205p
4026	158p	4543	115p	7447	90p	74145	90p	74247	195p
4027	60p	4555	115p	7448	90p	74147	148p	74248	171p
4028	95p	4556	115p	7450	20p	74148	150p	74249	171p
4029	123p	4581	348p	7451	20p	74150	150p	74251	170p
4030	59p	4582	140p	7453	20p	74151	78p	74265	94p
4033	155p	4584	99p	7454	20p	74153	78p	74278	331p
4034	347p	4585	108p	7460	20p	74154	138p	74279	75p
4035	118p			7470	33p	74155	90p	74283	9p
4040	132p			7472	30p	74156	90p	74284	712p
4041	84p			7473	33p	74157	82p	74285	712p
4042	89p	7400	18p	7474	33p	74158	140p	74290	122p
4043	89p	7401	18p	7475	48p	74159	285p	74293	122p
4044	91p	7402	18p	7481	125p	74160	102p	74298	173p
4046	137p	7403	20p	7483	95p	74161	102p	74365	93p
4049	55p	7404	24p	7484	119p	74162	102p	74368	93p
4050	55p	7405	24p	7485	128p	74163	102p	74367	93p
4051	140p	7406	42p	7486	33p	74164	118p	74368	93p
4052	140p	7407	58p	7489	340p	74165	115p	74390	189p
4053	140p	7408	25p	7490	43p	74167	358p	74393	189p
4060	140p	7409	25p	7491	77p	74170	213p	74490	254p

Full price list of linears, discretes, capacitors, resistors, potentiometers, tools, soldering irons and accessories available. Send 20p or large S.A.E. This list is sent free with the first order.

Prices correct December 1977.

Terms C.W.O. Add VAT to prices at 8%. Post. etc.: U.K. 25p, overseas 75p. Access and Barclaycard, and all convertible currencies accepted.

TIRRO ELECTRONICS

Grenfell Place, Maidenhead, Berks.

Tel: (0628) 36229

Mail order division of RITRO Electronics UK Ltd.

CHIPS UP!

CHIPS could be going up in the next few months! There have been various guarded comments about the cost of i.c.s, and the more popular l.s.i. devices, over the last few months; some time ago at least one of the larger manufacturers rationalised their range and increased the price of a number of items—some by very large factors.

It is not the cost of production which is likely to send prices up, since it is well known that the production cost of each item is an insignificant part of the total price. However, manufacturers have followed a policy of price reduction and this must soon (and is now in some cases) come to an end, since the major part of the cost of each item is the marketing, distribution and back up which all the devices require.

Unfortunately this price factor will probably not affect the multinational concerns that can buy tens or even hundreds of thousands of devices but it will affect the smaller companies and, of course, the hobbyist since neither he nor the component supplier is

able to purchase in vast quantities. Admittedly some suppliers are connected with distribution houses and the advantage that they already have appears likely to be increased.

MADE IN SPACE

Looking ahead rather further, it seems likely that some devices may be manufactured in space and will thus be coming down an even greater path to us! It has been muted that the space (area?) availability on some space shuttle flights could be used for the manufacture of integrated devices with the obvious advantages of clean "air" etc. The technology would obviously add to the 5,000 pounds (weight) of electronics which will be a permanent part of each shuttle.

HOBBY COMPUTERS

Having indicated that we may well be in for some cost increases in devices, we must hasten to add that we fully expect to see the cost of many complete systems to continue in a downward direction. The major one—and obviously the one that many are watching at the present time—being the microprocessor based systems and

the "hobby computer". You will find a review of the KIM I system in this issue and also mention of a British designed system in kit form which is now available (NASCOM I).

NEW TECHNOLOGY

We do not intend to "bury our (editorial) head in the sand" when it comes to any new technology and its possible use by the hobbyist. In fact we believe that it is part of our job to help the introduction of new systems and devices to your home and workbench. This policy is borne out by the use of modern phasing devices—c.c.d.s. or bucket brigade, call them what you will—in the *P.E. String Ensemble* to be featured in next month's issue. Even if the actual unit does not interest you as a constructional project, the use of these devices and the circuitry must.

In addition to the use of delay line technology to produce a rich orchestral string sound, the unit employs CMOS i.c.s. throughout the divider circuit and unique CMOS chorus drive circuitry.

Mike Kenward.

EDITORIAL

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland TECHNICAL SUB EDITOR

Jack Pountney ART EDITOR

Keith Woodruff SENIOR ARTIST

George Dilkes TECHNICAL ILLUSTRATOR

Editorial Offices:
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

ADVERTISEMENTS

ADVERTISEMENT MANAGER

D. W. B. Tilleard

P. J. Mew REPRESENTATIVE

C. R. Brown CLASSIFIED MANAGER

Make Up and Copy Dept.

Phone: 01-261 5000

Advertising Offices:
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Phone: Advertisements 01-261 5000
Telex: 915748 MAGDIV-G

Back Numbers and Binders

Copies of our June 1977 and subsequent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 65p each including Inland/Overseas p & p.

Binders for PE are available from the same address at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Cheques and postal orders should be made payable to IPC Magazines Limited.

Letters

Queries regarding articles published in PE should be addressed to the Editor, at the Editorial Offices, and a stamped, addressed envelope enclosed. We cannot undertake to answer questions regarding other items, nor to answer technical queries over the telephone.

AUTO-RANGING VOLTMETER

STEVE ROBERTS



TO ANYONE concerned with practical work with electronic circuits, the type of measurement most frequently required is undoubtedly voltage. Many instruments are available today which enable voltages to be measured with various degrees of accuracy, clarity or ambiguity, and which present the information on one of two types of readout—linear or digital.

The cost effective digital meter is relatively new upon the scene, but is felt by many people to have disadvantages over its analogue counterpart. One problem is its tendency to create false confidence; 1.32 volts displayed probably means 1.32 ± 0.015 volts. The analogue meter, by its very nature, serves as a constant reminder that the reading is not an absolutely indisputable value. Needle width and parallax effects are two sources of reminder. Another shortcoming of the digital display is its inability to provide qualitative information. A meter needle spinning wildly up to the top end of the scale, or vibrating about a reading, is much more evocative than a simple overrange indication, or a number that keeps changing.

It may also appear to be something of a paradox that when it is required to measure a voltage (implying that the voltage is initially unknown), it is first necessary to select the meter range appropriate to the measurement, for which it is required to know the voltage. This is of course not normally a problem, since the approximate voltage can usually be anticipated, and confirmation or greater accuracy is all that is required.

Much more of a problem is that of remembering to change the meter range for each measurement, or even changing the test leads over when the polarity is reversed. An auto-ranging facility overcomes these problems, and in doing so aids continuity of mental effort, not to mention prevention of damage to meters!

SPECIFICATION

Input resistance	10M Ω
Ranges	0.3V, 1V, 3V, 10V, 30V, 100V automatically selected
Polarity	Either + or - accepted and indicated
Accuracy	2% attainable
Power requirements	Optional mains supply, or $\pm 6V$ batteries
Size	110mm \times 188mm \times 60mm (mains option)

The design to be described is therefore a combination of the best features of analogue and digital instrumentation. It is adequate for all the more usual voltage measurements, and takes up no more room on the bench than the average multimeter.

DESIGN CRITERIA

The instrument was designed with the following points in mind:

- Accuracy comparable with better quality analogue meters.
- High input resistance.
- As clear a display as possible.
- As few controls as possible to leave hands free.
- Total measurement range to cover all normal d.c. voltage reading requirements for i.c. and transistor work.
- Foolproof in use.

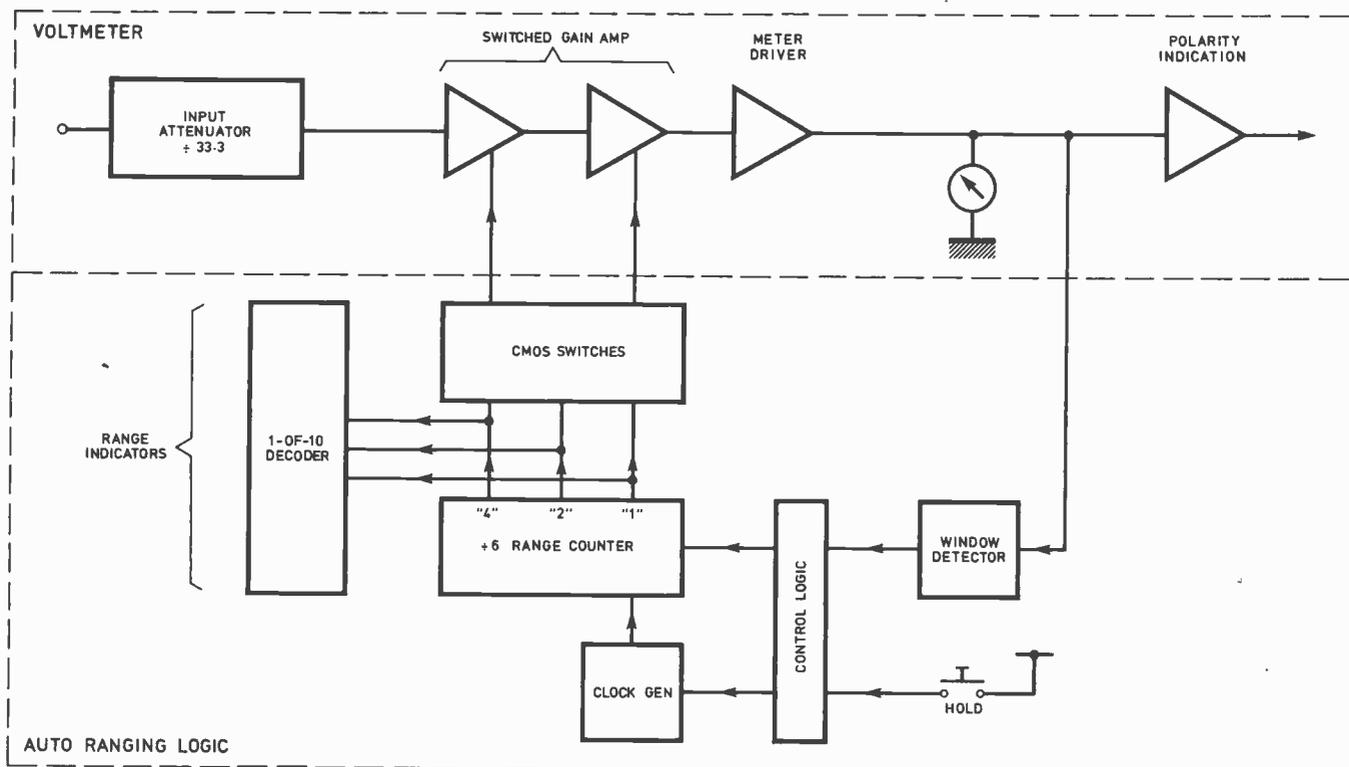


Fig. 1. Block diagram of Auto-Ranging D.C. Voltmeter



CIRCUIT DESCRIPTION

Referring initially to the block diagram of Fig. 1, the voltmeter section consists of an input attenuator, a two stage amplifier and a rectifier/meter driver.

Referring to the auto-ranging logic section, if the voltage present at the moving-coil meter does not fall within a predetermined window (between 20 per cent and 90 per cent of full scale), the output of the window detector enables the range counter on the next pulse of the clock oscillator. The range counter output controls the status

of the CMOS range selector switches, and thus the gains of the voltmeter amplifiers are changed. The whole process is repeated until a gain has been selected which causes the voltage being displayed to fall within the range of the window detector, at which time the range counter is inhibited and the range remains selected. A decoder is provided which decodes the output of the range counter and drives the range indicating i.e.d.s.

For the detailed circuit description, we must now refer to the full circuit diagram, Fig. 2.

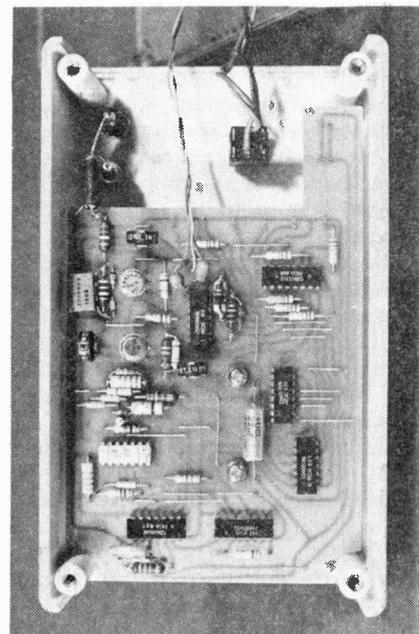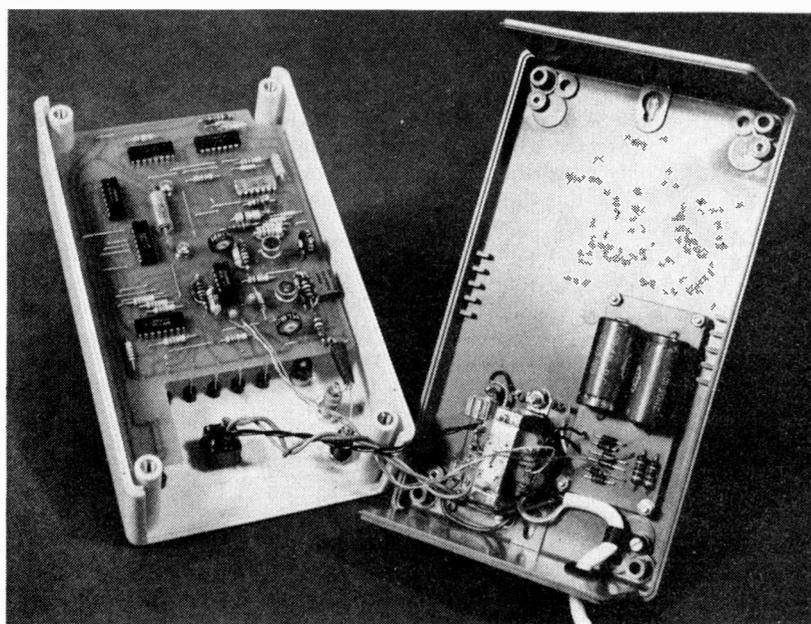

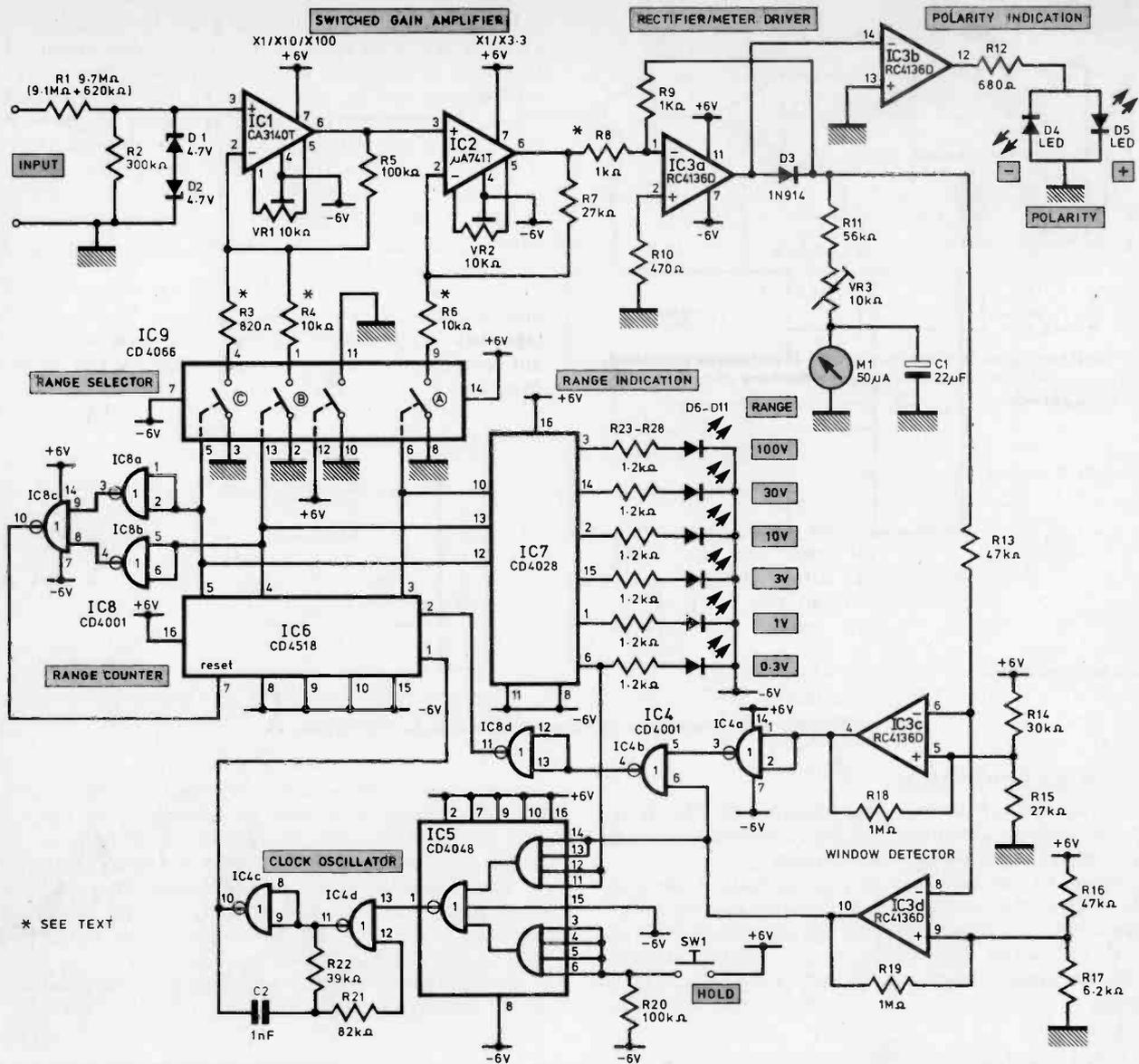


Fig. 2. Full circuit diagram of Voltmeter unit. Although the circuit contains a rectifier, it will not give the conventional true r.m.s. reading for an a.c. input

The input attenuator, R1 and R2, determines the input resistance of the instrument, and reduces the highest possible voltage presented for measurement to a level that can be handled by the input circuitry. Diodes D1 and D2 prevent damage to the circuit should a very high input voltage be applied inadvertently.

The switched-gain amplifier is formed by IC1 and IC2. Op amp IC1 is a very high input resistance device, which is necessary to preserve the integrity of the input attenuator. The gain of the amplifier is adjusted by changing the degree of negative feedback through the CMOS switches.

A conventional full-wave rectifier circuit is formed by IC3a, which presents about +3V at the cathode of D3 for full scale deflection of the meter. The polarity of the voltage at IC3 pin 3 is monitored by IC3b, and this in turn causes the appropriate polarity indicator to be illuminated.

The meter drive voltage is also presented to IC3c and IC3d, which are connected as voltage comparators. If the meter drive voltage is higher than the reference voltage provided by R16 and R17, the pin 10 output is "Low". Similarly, if the voltage is lower than the reference

voltage from R14 and R15, the pin 4 output is "High", and IC4 pin 3 is therefore "Low". The two low inputs presented to IC4b produce a high output, which is present *only* when the two inputs are both low. After inversion by IC8d, this output is used to inhibit the range counter IC6. Note the hysteresis resistors R18 and R19 (giving slight positive feedback) which eliminate any tendency to indecision around the comparison voltage.

NOR gates IC4c and IC4d form an oscillator of around 10kHz. The actual frequency is uncritical as it only affects the search rate of the instrument. The oscillator may be disabled by a high input from IC5, to which reference will be made later.

The dual 4-bit binary counter (IC6), has only half in use. IC8a, b and c, cause the counter to reset on a count of six, thus preventing the selection of invalid gain settings occurring. The binary outputs of the counter are used to activate the CMOS switches, thus selecting the different gain values. See Table 1 under "Test And Calibration".

The binary-to-decimal decoder IC7 provides a "1 of 10" output, which is used to drive directly the range i.e.d.s.

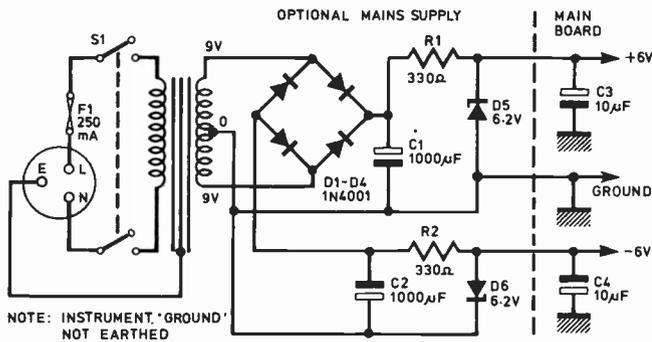


Fig. 3. Optional power supply circuit. If batteries are used, a larger case will be necessary, and a battery check facility would be advisable

LOW READING STABILITY

A problem could occur when the meter has a zero or near-zero input. The window detector would see a voltage too low for the 0.3V range, and would therefore change scales in an attempt to locate the correct range. As there is no more sensitive range, the circuit would search continuously and prevent very low voltage measurements from being made.

The output from pin 6 of IC7, which is high when the most sensitive range is selected, is monitored by IC5, as is the output of IC3d. If the lowest range is selected now, and if the measured voltage falls below the magnitude window, the clock oscillator is inhibited, thus preventing further searching.

Occasions may arise when it is desirable that the range does not automatically change; for example, when examining a voltage that is fluctuating between 8.5 and 9.5 volts. As these figures embrace a range change, meter indications would largely be meaningless unless the range is "held" at, say, 10V. The exact behaviour of the input may then be observed as long as the Hold button is pressed. Pressing this button has the effect of inhibiting the clock oscillator as before.

CONSTRUCTION

The prototype was built in a Type 103 Verobox which provided an attractive and durable housing.

Constructors should decide, before choosing a case, whether the mains, or a battery supply is to be used. As there is no 6V battery of modest dimension readily available, a somewhat larger case than the suggested Verobox would be required. This factor, and the cost of replacement batteries, led to the author's choice of a mains power supply for the prototype. See Fig. 3.

The main printed circuit board (Fig. 4) was secured by means of the meter terminals only; a method found to be quite satisfactory. With the depth of meter body used, the leads of the eight l.e.d.s were found to be just long enough to allow them to protrude through the front panel (see photograph). Mounting clips were not used as these would have made assembly and subsequent removal very difficult, and with the correct size holes a more attractive appearance is presented. Note from the photograph that the l.e.d.s are mounted on the *copper* side of the p.c.b. See Fig. 5 for assembly of the p.c.b.

Use of the suggested printed circuit board layout is to be recommended due to the complexity of the design. There is, however, no reason why other forms of construction may not be used.


If a mains supply is decided upon, note that the mains earth is *not* connected to the instrument ground. It is desirable, therefore, to use a transformer with an earthed interwinding screen, and to ensure that the instrument is connected particularly carefully where the mains wiring is concerned. Care should also be taken to ensure that this mains wiring is kept as far away as possible from the high impedance input components, as this area is susceptible to hum pick-up. Because of the rectifying action of the meter driver, any a.c. signal present at the input will register as a d.c. voltage on the meter.

The resistors used to select the amplifier gains (R3, R4 and R6) and the \pm balance resistor R8 might advantageously be mounted on extension pins which would aid component changing if required during the calibration procedure.


As most of the i.c.s use MOS technology, the appropriate handling precautions should be taken.

The CA3140 was chosen for IC1 as it requires no phase compensation. If this fairly new device is not readily available, a CA3130 may be used instead, with a 47pF ceramic capacitor connected between pins 1 and 8 on the copper side of the board.

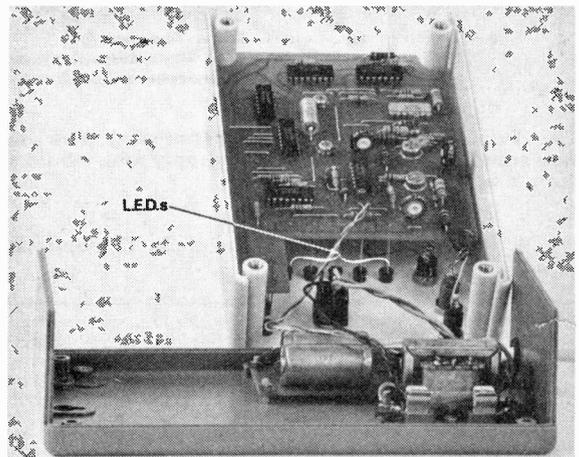If the recommended meter is used, it will need to be re-scaled as shown in Fig. 6.



Note the cut out power supply section from the main p.c.b. Also that the l.e.d.s are mounted at maximum length from the board on the conductor side

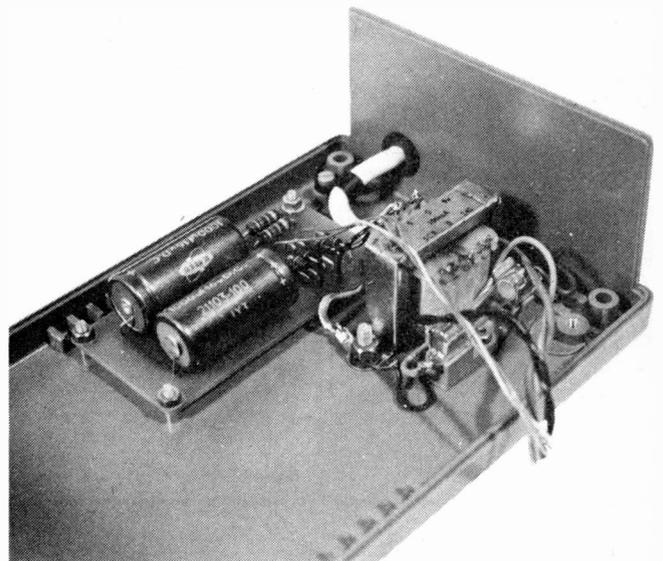


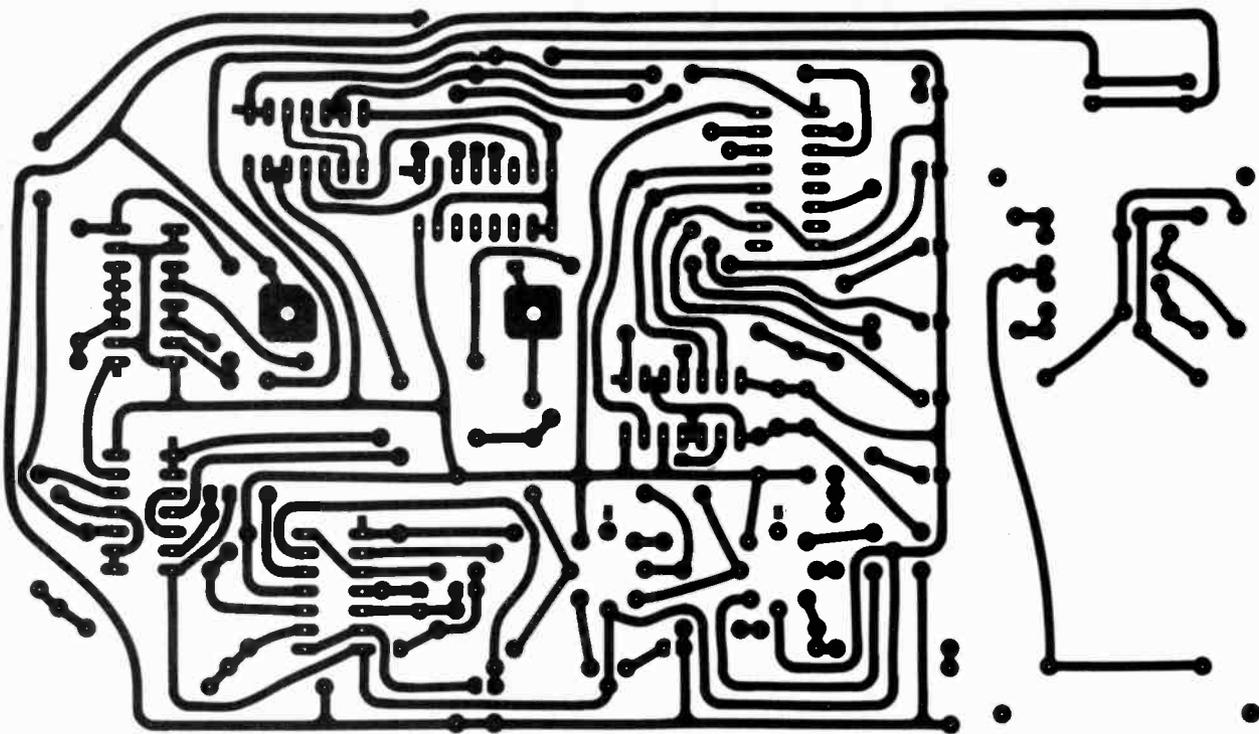


Fig. 4. Printed circuit board layout (full size). The power supply board is included on the same layout so that both can be etched simultaneously. The power supply area would still need to be cut out even if batteries are to be used. Note the shape of the p.c.b. in the photographs

Fig. 5. Component layout of the p.c.b. The optional power supply portion of the circuit board is shown by dotted line

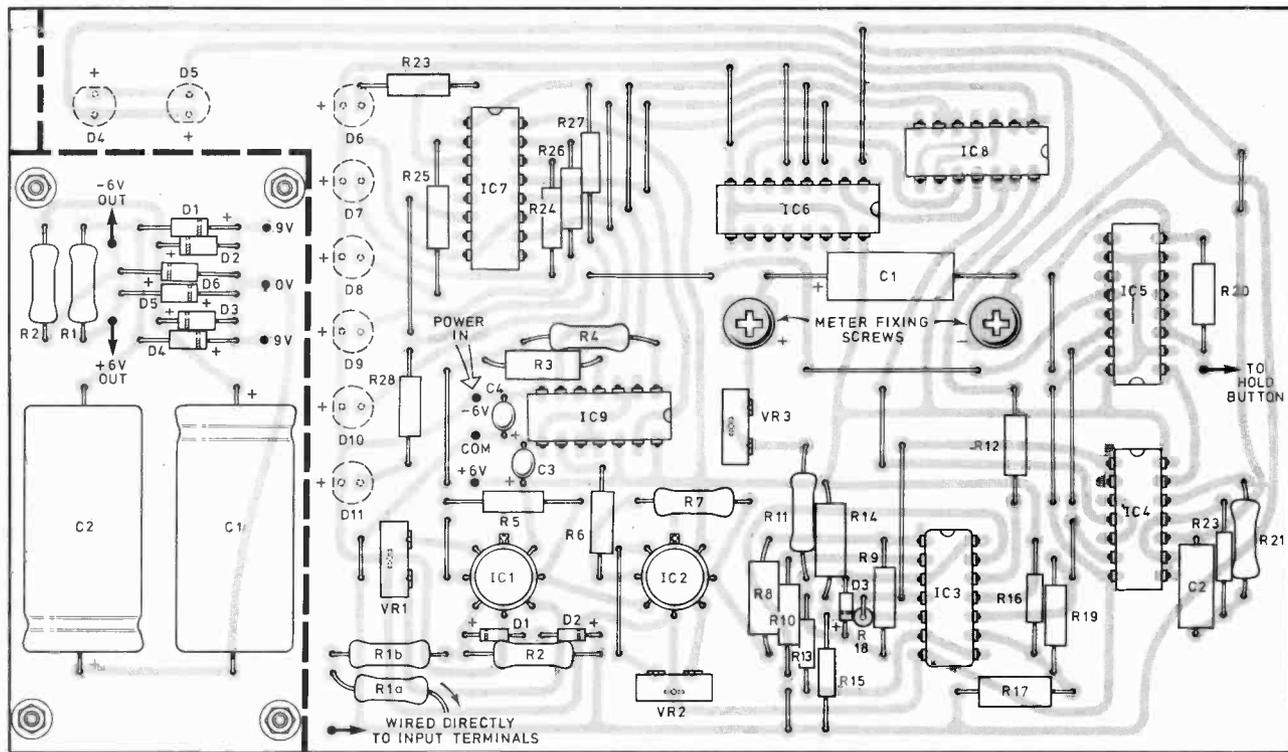

AUTO-RANGING

D.C. VOLTMETER



COMPONENTS . . .

BASIC AUTO-RANGING D.C. VOLTMETER

Resistors

R1	9.1M Ω + 620k Ω in series
R2	300k Ω
R3	820 Ω *
R4	10k Ω *
R5	100k Ω
R6	10k Ω *
R7	27k Ω
R8	1k Ω *
R9	1k Ω
R10	470 Ω
R11	56k Ω
R12	680 Ω
R13	47k Ω
R14	30k Ω
R15	27k Ω
R16	47k Ω
R17	6.2k Ω
R18, R19	1M Ω (2 off)
R20	100k Ω
R21	82k Ω
R22	39k Ω
R23-28	1.2k Ω (6 off)

All resistors are $\frac{1}{4}$ W 5% carbon.

*Resistors to be selected on test, see text.

Potentiometers

VR1-VR3 10k Ω vertical preset (sub min)

Capacitors

C1 1000pF polyester
C2 22 μ F 25V
C3, C4 10 μ F 10V tant (2 off)

Diodes

D1, D2 BZY88C4V7 zener (2 off)
D3 1N914
D4-D11 0.2" red l.e.d. (8 off)

Integrated Circuits

IC1 CA3140T
IC2 μ A741T
IC3 RC4136D
IC4 CD4001
IC5 CD4048
IC6 CD4518
IC7 CD4028
IC8 CD4001
IC9 CD4066

Miscellaneous

S1 Single pole, push-to-make
Case 110mm \times 188mm \times 60mm
M1 50 μ A panel meter (with scale recalibrated)
P.c.b.
4mm plugs and sockets, wire, and prods for probes

COMPONENTS . . .

OPTIONAL MAINS SUPPLY

Resistors

R1, R2 330 $\frac{1}{4}$ W carbon (2 off)

Capacitors

C1, C2 1000 μ F 25V (2 off)
C3, C4 10 μ F 10V (2 off)

Diodes

D1-D4 1N4001 (4 off)
D5, D6 BZY88C6V2 Zener (2 off)

Miscellaneous

S1 Sub min d.p.s.t.
F1 250mA and suitable holder
T1 9-0-9V mains transformer with screen
P.c.b. to design given

CONSTRUCTOR'S NOTE

If the recommended p.c.b. design is used, the CA3140T type should be ordered for IC1 (T stands for 8-lead TO5 package).

Since P.E. does not operate a p.c.b. service we cannot quote a supplier of ready made boards for those who do not wish to make their own, but we can advise that readers keep an eye on P.E. advertisers who specialise in p.c.b. manufacture, and have in the past generally followed up with a service.

The "Large Moving Coil Meter" is available from **Maplin Electronic Supplies** (see advertisers' index for address).

The RC4136D (IC3) is made by Raytheon, and available from **Distronic Ltd., 50/51 Burnt Mill, Elizabeth Way, Harlow, Essex.** Tel: Harlow 32947. Type RC4136DP may be used (D stands for d.i.l. and P for plastic).

The estimated cost to build this unit using all new parts, is in the region of £25.


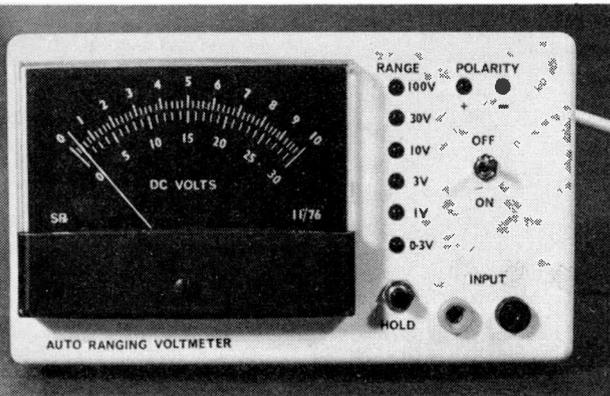


Fig. 6. Meter scale required by the Auto-Ranging D.C. Voltmeter

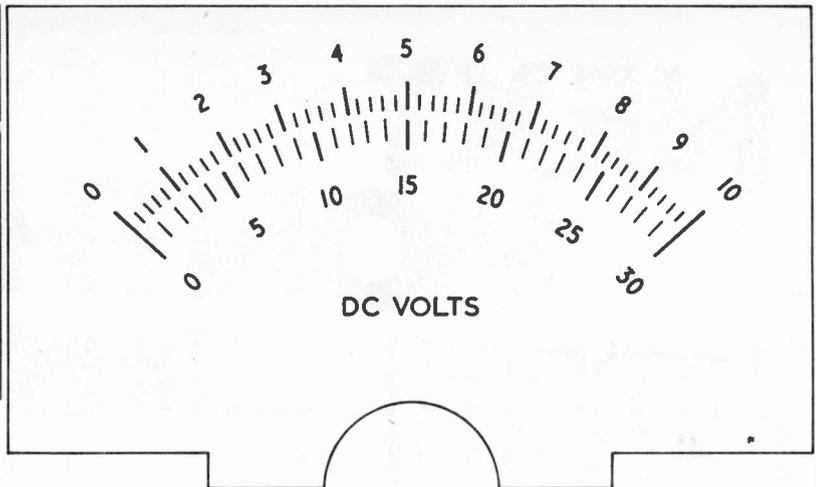

TEST AND CALIBRATION

Before first switch-on, all preset pots should be at approximately mid-range. Any meter reading should be ignored for the present, although a large offset in IC1 may cause a range change, necessitating adjustment of VR1 to cancel this effect.

Odd combinations of RANGE l.e.d.s, or "searching" should be resolved during calibration, and this procedure is as follows:

(A) Set zero

- (1) With the power off, set the meter mechanically to zero.
- (2) Switch on. Check that the 0.3V range is indicated, and allow a few minutes for thermal stabilisation.
- (3) Short IC2 pin 3 to the zero volt rail. Adjust VR2 for minimum reading on the meter. Remove short.
- (4) Short input. Adjust VR1 for minimum reading. The meter should now read zero.

(B) Set positive/negative balance

- (1) Apply an input to the meter and adjust for a convenient reading.
- (2) Reverse the connections to the meter and check that exactly the same reading is displayed. If not, adjust R8 as necessary.

Table 1. Should a fault exist, this table may be used to check the switching functions. Check all supply voltages first

COUNTER CONTENT	SWITCHES CLOSED	IC 1 GAIN	IC 2 GAIN	TOTAL GAIN	RANGE
0	-	x1	x1	x1	100V
1	A	x1	x3.3	x3.3	30V
2	B	x10	x1	x10	10V
3	A,B	x10	x3.3	x33	3V
4	C	x100	x1	x100	1V
5	A,C	x100	3.3	x333	0.3V
6	B,C	INVALID SETTINGS WHICH DO NOT APPEAR - COUNTER RESETS AT 6			
7	A,B,C				

(C) Set meter calibration

This adjustment compensates for any small inaccuracy in the input attenuator.

- (1) Apply about 50V to the meter input, thereby selecting the 100V range.
- (2) Check meter reading against a known good meter.
- (3) Adjust VR3 for correct reading.

(D) Check $\times 100$ amp gain

- (1) Apply about 0.5V to input, thereby selecting 1V range.
- (2) PRESS HOLD. Adjust input voltage to 1V exactly
- (3) Check that meter reads 1V. If not, adjust R3 for an acceptable result.

(E) Check $\times 10$ amp gain

- (1) Apply about 5V to input, thereby selecting 10V range.
- (2) Press HOLD. Adjust input to 10V exactly.
- (3) Check that the meter reads 10V. If not, adjust R4 for an acceptable result.

(F) Check $\times 3.3$ amp gain

- (1) Apply about 15V to input thereby selecting 30V range.
- (2) Press HOLD. Adjust input voltage to 30V exactly.
- (3) Check that the meter reads 30V. If not, adjust R6 for an acceptable result.

(G) Check upper range-change point

- (1) The range should change to the next highest at about 90 per cent of full-scale reading. If not, adjust R14/R15 as necessary.

(H) Check lower range-change point

- (1) The range should change to the next lower at about 20 per cent of full scale. Adjust R16/R17 if necessary.

This completes the calibration, and the instrument, if correctly set up, should conform to the figures in the specification.

Acknowledgement

The author would like to thank Mr. D. Bowers for his helpful comments and suggestions during this project. ★

NEXT MONTH...

FREE! COVER-MOUNTED GIFT matrix marker

...a useful tool for constructors

PE STRING ENSEMBLE




Employing modern delay line technology this instrument produces rich reverberant orchestral string sounds. Additional time and variable envelope controls can be mixed to produce a wide spectrum of sound. Features include:

- * Split keyboard with register variance in both hands
- * Four selectable pitches to match accompanying musical instruments
- * Single contact electronic keyswitch action
- * CMOS i.c.s throughout divider circuitry
- * Unique CMOS chorus drive circuitry
- * Third cost of equivalent commercial instrument

DIGITAL LAP COUNTER

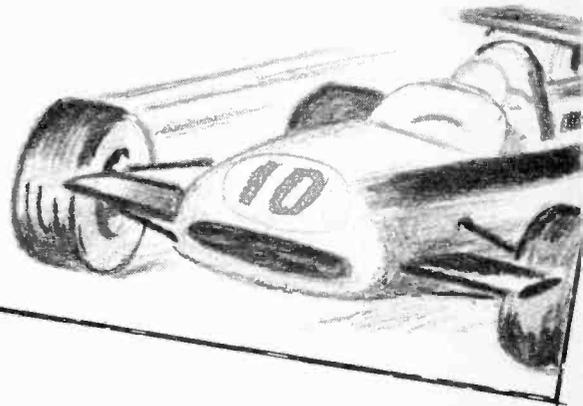Eliminates any argument when staging a model car race. This system does not impede the cars in any way and can be used to turn off the power after a preset number of laps.



PRACTICAL ELECTRONICS

OUR MARCH ISSUE WILL BE ON SALE FRIDAY, FEBRUARY 10, 1978

KIM HOBBY COMPUTER REVIEW

R.W. COLES

THE LAST twelve months have been very exciting for anyone interested in microprocessors and their application.

Of course, these fascinating and powerful devices have been around for several years now and have already taken the professional electronics industry by storm, but it is really only in the last year or so that microprocessor manufacturers have turned their attention squarely towards the needs of the electronic and computer hobbyist, with some very interesting results.

The hobby market trail blazer (in terms of wide availability anyway) was the National Introkkit which featured the SC/MP microprocessor. The Introkkit was of course reviewed within these pages earlier in the year, and reviews of other units like the Intercept Junior, featuring the IM6100 MPU chip, and the Motorola D2 kit featuring the M6800, were soon to follow.

To start with, manufacturers were a little lazy about just *who* they were aiming their "small system" designs at. Their cautious approach was obvious from the way systems were described as "Prototyping systems", "Introductory systems", and "Tutorial systems" with manuals written, it seemed, for professional engineers who were expected to rapidly move on to bigger and better things, with their loyalty to a particular MPU chip already established! With the unexpected mushrooming of the hobby computer market in the U.S.A. manufacturers soon realised that a huge new market had arisen, and also that this new breed of hobbyist was *not* going to be satisfied with a cheap system which had a limited usefulness and future. The average amateur was not likely to move on to a de-luxe development system with floppy discs and a teletype; he wanted a low cost system which nevertheless could be used to do practical things, a system which had inputs and outputs available for his use, a system with a self-contained keyboard and display, a system with a reasonable RAM memory capacity, a system which could use *low cost* peripherals such as cassette tape recorders, and of course, above all, a system which he could expand when he felt the need for more performance.

HOBBY COMPUTER

KIM-1 is the result of a deeper understanding of the requirements of hobbyists, and is a successful attempt to provide the amateur with the things he needs at a realistic price. KIM-1 is a design from M.O.S. TECHNOLOGY, INC. and uses their own 6502 microprocessor array in a ready built system which arrives

tested and guaranteed for 90 days. The cost of KIM-1 is around the £200 mark, but for this you get a well made micro-computer circuit board which includes a hexadecimal keyboard and 8 digit l.e.d. display, an audio cassette interface, 1,024 words of RAM storage, a comprehensive monitor program in 2,048 words of ROM and 15 input/output lines available on an edge connector. In addition to the KIM-1 board itself, you get a User Manual, a Programming Manual, a Hardware Manual, a system wall chart and a programmer's reference card. The three manuals together are no less than 4cm thick, and even at first glance these appeared to be *very* comprehensive to us!

With a full 1k of user RAM available from the start, a KIM-1 owner is unlikely to feel cramped for space for quite a while, especially since programs can be stored on, and retrieved


from, conventional cassette tapes with the simple addition to the system of a low cost audio cassette recorder. As a user becomes more ambitious however, the KIM-1 board can be augmented with the KIM-2, 3, 4, or 5 boards which will provide sufficient extra RAM memory to run sophisticated high level software, like BASIC for example, when this becomes available.

The 6502 microprocessor and associated circuits require only a single 5 volt supply which can be easily put together using a fixed voltage LM309K regulator. When a cassette recorder is used, an additional low current 12 volt supply is required to power the interface circuitry.

THE MPU CHIP FAMILY

The MCS6502 chip used as the heart of KIM-1 is one member of a large family of microprocessor chips produced

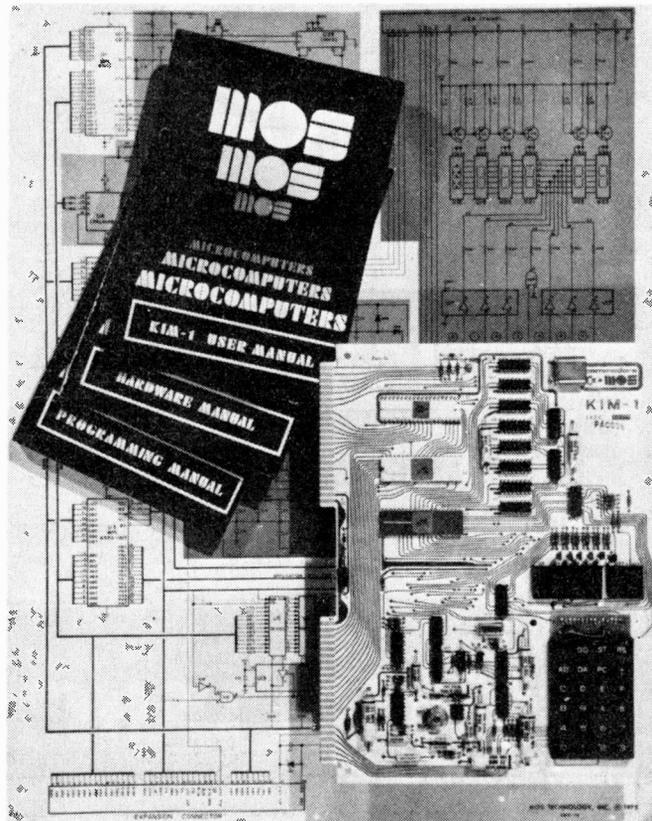At a price of £199 upwards, the KIM-1 is supplied as an assembled and tested microcomputer with keyboard, display and full documentation. Available from GR Electronics Ltd., Newport, Gwent



V _{ss}	1	40	RES
RDY	2	39	θ ₂ (DUT)
φ ₁ (OUT)	3	38	S.O.
IRQ	4	37	θ ₀ (IN)
N.C.	5	36	N.C.
NMT	6	35	N.C.
SYNC	7	34	R/W
V _{cc}	8	33	DB0
AB0	9	32	DB1
AB1	10	31	DB2
AB2	11	30	DB3
AB3	12	29	DB4
AB4	13	28	DB5
AB5	14	27	DB6
AB6	15	26	DB7
AB7	16	25	AB15
AB8	17	24	AB14
AB9	18	23	AB13
AB10	19	22	AB12
AB11	20	21	V _{ss}

MCS6502

The MCS6502 microprocessor chip used in KIM-1.

by M.O.S. TECHNOLOGY, INC. Many readers may be unfamiliar with this manufacturer and the MCS 65XX series of MPU chips, although they are fairly well known in the U.S.A. The family is described by M.O.S. as "Third generation" and it is certainly true to say that several advanced features are available within the family, which obviously owes a lot of its basic design to the Motorola M6800 chip with which its members are bus compatible.

There are nine microprocessors in the family and these offer complete software compatibility (the same instruction set) but differing hardware features such as 28 or 40 pin package, on or off chip clocks, varying address range from 4k to 65k words, and choice of interrupt facilities. All members of this family offer NMOS high speed (2MHz maximum) operation and a very efficient in-

struction set with 56 basic instructions. The MCS6502 is an on chip clock, 40 pin package version with an address range of 65k words, making it a very sophisticated device with lots of potential.

PERIPHERAL CHIPS

Also on the KIM-1 board are two MCS6530 chips, and these devices are not microprocessors but a powerful combination of a ROM array, a RAM array, an Interval timer and two eight bit input/output ports, all in a single 40 pin package! It is probably the availability of these devices which makes the KIM-1 possible at such a low price, because providing these facilities separately would certainly be expensive!

Each MCS6530 contains 1,024 words of mask programmed ROM normally used to hold programs, and 64 words of RAM which can be used for scratch pad storage, stacks, etc. The interval timer is a down counter which can be preset under program control, and which will interrupt the MPU chip when a count of zero is reached. Under program control the MCS6530 timer can be used to generate a wide variety of timing functions which allows this important system task to be unloaded from the microprocessor itself, promoting software efficiency.

The sixteen input/output lines are individually programmable as either inputs or outputs under software control, and they can source 3mA at 1.5 volts when used as outputs, making interfacing straightforward.

CAUTION

One word of caution on the MCS6530; its ROM section, being mask programmable, is unsuitable for use in any "homebrew" system, although of course,

it is ideal for the KIM-1 itself where the monitor program is loaded during manufacture by M.O.S. themselves. A homebrew system *would* be possible using external EPROM chips such as the 2708 or 1702A, if required.


User program storage on the KIM-1 board is provided by eight 1024 by 1 bit 2102 type NMOS RAM chips, although as you will have gathered from the description of the MCS6530 chip, a further 128 words is available if required. The basic address range of KIM-1 is 8k words, with the MCS6530 ROM, RAM I/O and TIMERS mapped into the upper three 1k pages, and the user RAM mapped as the lower 1k page. Expansion to the full 65k words can be carried out externally at a later date if desired.

OUR EXPERIENCES

With the system up and running with the aid of a bench 5 volt supply, we tried out the simple program on page 9 of the User Manual. The method of program entry is, in our opinion, better than the MEM, TERM system used on the SC/MP Introkit, because it is much simpler. To set an address you press the AD key followed by *four* HEX digits. To enter instructions or data you press the DA key followed by *two* HEX digits, and to increment to further locations for further entries you press the + key followed by the next two HEX digits and so on. To run a program you enter its start address using the AD mode, and press the GO key.

The other keys available are RS, which causes system reset, ST which terminates the current program and PC which allows you to display the value of the program counter at the time that an interrupt occurred or the ST key was pressed. Execution can be continued from where it was stopped by the ST key by pressing

KIM-1 block diagram.

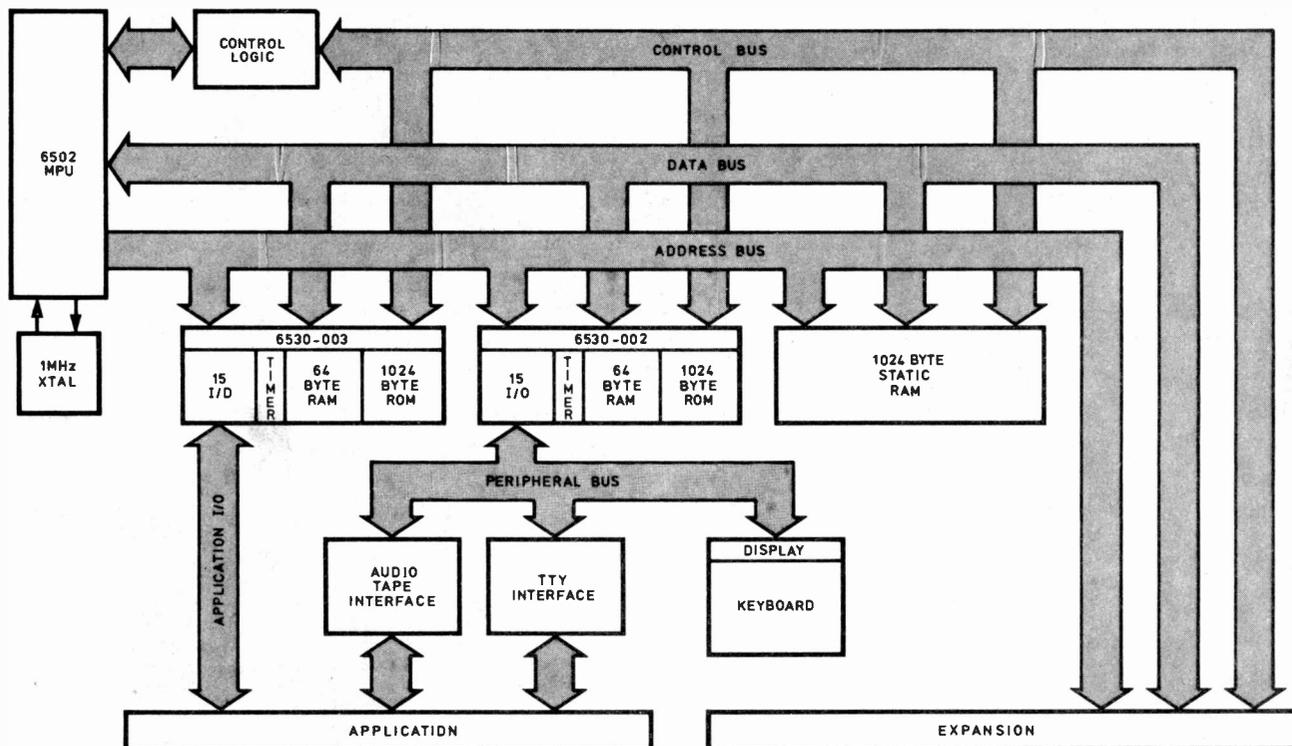

the GO key. A slide switch on the keyboard allows you to enter the "single-step" mode so that single instructions are executed for each press of the GO key.

With a feeling of "So far so good", we hooked up a 12 volt supply in addition to the 5 volts already connected then blew the dust off of our portable cassette recorder and connected it up, too, following the simple diagram in the manual.

CASSETTE


The KIM-1 monitor program controls the storage and retrieval of data on the cassette, and when recording a program a checksum is added in at the end so that verification is possible during replay into KIM-1 RAM. Each program must be given a unique "name" before recording takes place, and this "name" (actually a two digit HEX code) is used to identify the required program on replay. We dumped the simple trial program from RAM onto a cassette, switched off the power, and then attempted to reload it into RAM—failure!

After a lot of experimentation we discovered that it was necessary to use different volume control settings for record and replay to get the system to work. Now this might have been the fault of our cassette recorder, which was not new but seemed perfectly serviceable, but the manual certainly led us to understand that a unit of the type we used would be quite satisfactory, and that no adjustment of the controls would be required.

After some practice the record and replay functions were operating correctly most of the time, and we began to realise the enormous advantages of the cassette system compared with the pencil and paper method of storing programs! By hooking up a microphone to the recorder it is also possible to cue programs verbally on the tape, so that both you and your KIM-1 know what's going on! (Voice signals are ignored by the monitor routines on replay.)

KIM-1 also comes with a routine for handling teletypes or VDUs of any standard baud rate, and is equipped with a 20mA current loop interface for this purpose. We were unable to try out this particular aspect of system operation however.

Suitable power supply for KIM-1

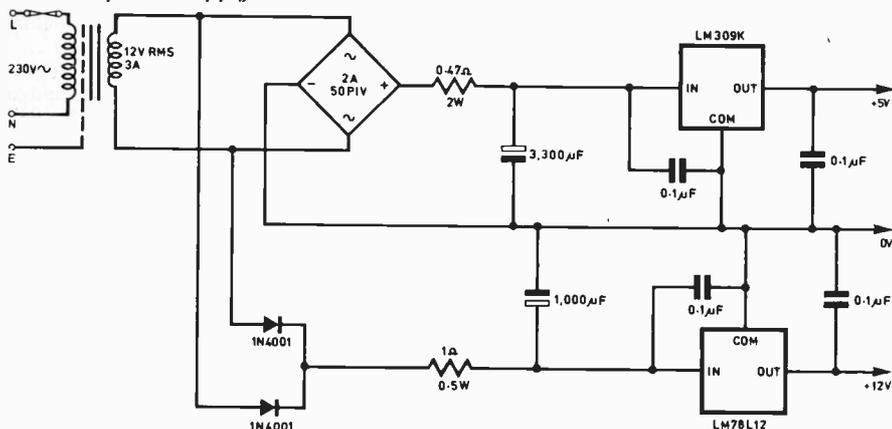

MCS6502 MICROPROCESSOR INSTRUCTION SET—ALPHABETIC SEQUENCE

ADC	Add Memory to Accumulator with Carry	JSR	Jump to New Location Saving Return Address
AND	"AND" Memory with Accumulator	LDA	Load Accumulator with Memory
ASL	Shift Left One Bit (Memory or Accumulator)	LDX	Load Index X with Memory
BCC	Branch on Carry Clear	LDY	Load Index Y with Memory
BCS	Branch on Carry Set	LSR	Shift One Bit Right (Memory or Accumulator)
BEQ	Branch on Result Zero	NOP	No Operation
BIT	Test Bits in Memory with Accumulator	ORA	"OR" Memory with Accumulator
BMI	Branch on Result Minus	PHA	Push Accumulator on Stack
BNE	Branch on Result not Zero	PHP	Push Processor Status on Stack
BPL	Branch on Result Plus	PLA	Pull Accumulator from Stack
BRK	Force Break	PLP	Pull Processor Status from Stack
BVC	Branch on Overflow Clear	RORL	Rotate One Bit Left (Memory or Accumulator)
BVS	Branch on Overflow Set	RORR	Rotate One Bit Right (Memory or Accumulator)
CLC	Clear Carry Flag	RTI	Return From Interrupt
CLD	Clear Decimal Mode	RTS	Return From Subroutine
CLI	Clear Interrupt Disable Bit	SBC	Subtract Memory from Accumulator with Borrow
CLV	Clear Overflow Flag	SEC	Set Carry Flag
CMP	Compare Memory and Accumulator	SED	Set Decimal Mode
CPX	Compare Memory and Index X	SEI	Set Interrupt Disable Status
CPY	Compare Memory and Index Y	STA	Store Accumulator in Memory
DEC	Decrement Memory by One	STX	Store Index X in Memory
DEX	Decrement Index X by One	STY	Store Index Y in Memory
DEY	Decrement Index Y by One	TAX	Transfer Accumulator to Index X
EOR	"Exclusive-or" Memory with Accumulator	TAY	Transfer Accumulator to Index Y
INC	Increment Memory by One	TSX	Transfer Stack Pointer to Index X
INX	Increment X by One	TXA	Transfer Index X to Accumulator
INY	Increment Y by One	TXS	Transfer Index X to Stack Pointer
JMP	Jump to New Location	TYA	Transfer Index Y to Accumulator

VERDICT

The thing which impressed us most about the KIM-1 system was the provision of the three excellent manuals which between them covered all aspects of system operation and programming in minute detail. Anyone with a basic knowledge of microprocessors, or computers in general, should be able to find their way around easily with the aid of these books. The User Manual is written in a chatty informal style which puts the reader at ease right from the word "go". Following this book in step-by-step fashion is rather like taking a programmed learning course, and most KIM-1 owners will find themselves eager to delve into the other two manuals, which are rather more formal, once they have mastered its contents.

On the hardware side, the powerful MCS6502 chip, the full 1k of user RAM and the cassette interface, speak for themselves.

KIM-1 also has that magic ingredient "expendability" so that owners need not feel boxed in. Expansion can be carried out *without* a soldering iron, and those who look forward to a powerful "Home computer" have every chance of achieving this later if a VDU or teletype is added to the system, and the manufacturers start to provide software on cassette (which is likely). As it is, the basic KIM-1 can be programmed easily in machine code, and can of course be connected up directly to external gadgetry by means of the input output lines, if required.

The instruction set of the MCS6502 has some powerful features, like I3 addressing modes, and the ability to set the arithmetic unit to "Decimal mode" for the duration of a B.C.D. calculation rather than having to use "Decimal adjust" instructions as is the case with other devices. The mnemonics looked easy to learn to us, although they are different to those used with the 8080, or the 6800 its two major competitors.

The construction and component quality looked good. We noticed that the cassette recording format is not of the "Kansas City" type, which means a black mark, although the system used *is* self clocking which is to its credit. The seven segment displays were a little difficult to decipher in high ambient lighting, but we soon cured this by adding a piece of red filter material.

All in all then, the KIM-1 seems a good buy for all low-budget micronuts, and a useful step nearer that impossible dream, the "perfect" system.

ANYONE looking for a simple and novel project to build, just for fun, may be interested in the Strength Meter described in this article.

The power of the contestant's grip is displayed on a row of l.e.d.s while he squeezes two cannisters as tight as he can. However, the indicator is not to be treated with scientific reverence since it *really* works by measuring the resistance between the hand-grips.

CIRCUIT DESCRIPTION

The circuit shown in Fig. 1 is designed so that the number of l.e.d.s which illuminate along the row comprising D1 to D4, increases as the resistance between the hand-grips falls; which of course happens when the contestant squeezes harder.

A potential divider is produced between 0V and +9V by R1 and R2, and since their resistance ratio is 1:1, the voltage at point "B" will be half the supply, which is +4.5V. The differential amplifier formed by IC1 uses this voltage as a reference, so that it amplifies the difference between points "A" and "B".

Voltage "A" however, is produced by a potential divider of variable ratio, which is dependent on the hand-grip resistance. This voltage, for any given degree of hand-grip squeeze, can be set using VR1, but the voltage generated by zero squeeze (no hand-grip contact at all) always starts off from 0V. This "slope" setting will also determine the amount of grip necessary to pull up all four l.e.d.s.

After amplification in the non-inverting amplifier IC1, the generated voltage is fed to the base of TR1. This stage has no voltage gain (some voltage will in fact be

lost across the base-emitter junction), but simply multiplies the output current capability of the 741 by the gain figure of the BC107, a figure which of course will vary from one such transistor to another due to production spread. But in any case TR1 will add sufficient current drive to take the load consisting of the resistor chain R5 to R9.

The point of the resistor chain is to divide the voltage produced at point "C" into five equally spaced potentials. This way, as the voltage at "C" increases, the voltage at "D" will eventually become sufficient to overcome the base-emitter junction potential of TR2, plus a little more to push some current through R10. When this happens D1 will illuminate as TR2 switches into conduction.


If the voltage at "C" continues to increase, then the voltage at "E" will become sufficient to bias TR3 into conduction, and so on, until all the l.e.d.s are illuminated. Just as R10 to R13 limit the base current to their respective transistors, resistors R14 to R17 limit the l.e.d. currents to around 17mA.

CONSTRUCTION

The circuit was built on a piece of 0.1 inch matrix stripboard and the layout, shown in Fig. 2, will accommodate either an 8-pin d.i.l. or the 14-pin version of the 741 amplifier. Care should be taken to ensure that the appropriate breaks are made to the copper tracks, and that no blobs of solder or shavings of copper form a bridge between conductors.


A simple aluminium box was used for the prototype, and this could be formed from a sheet of metal if a

STRENGTH

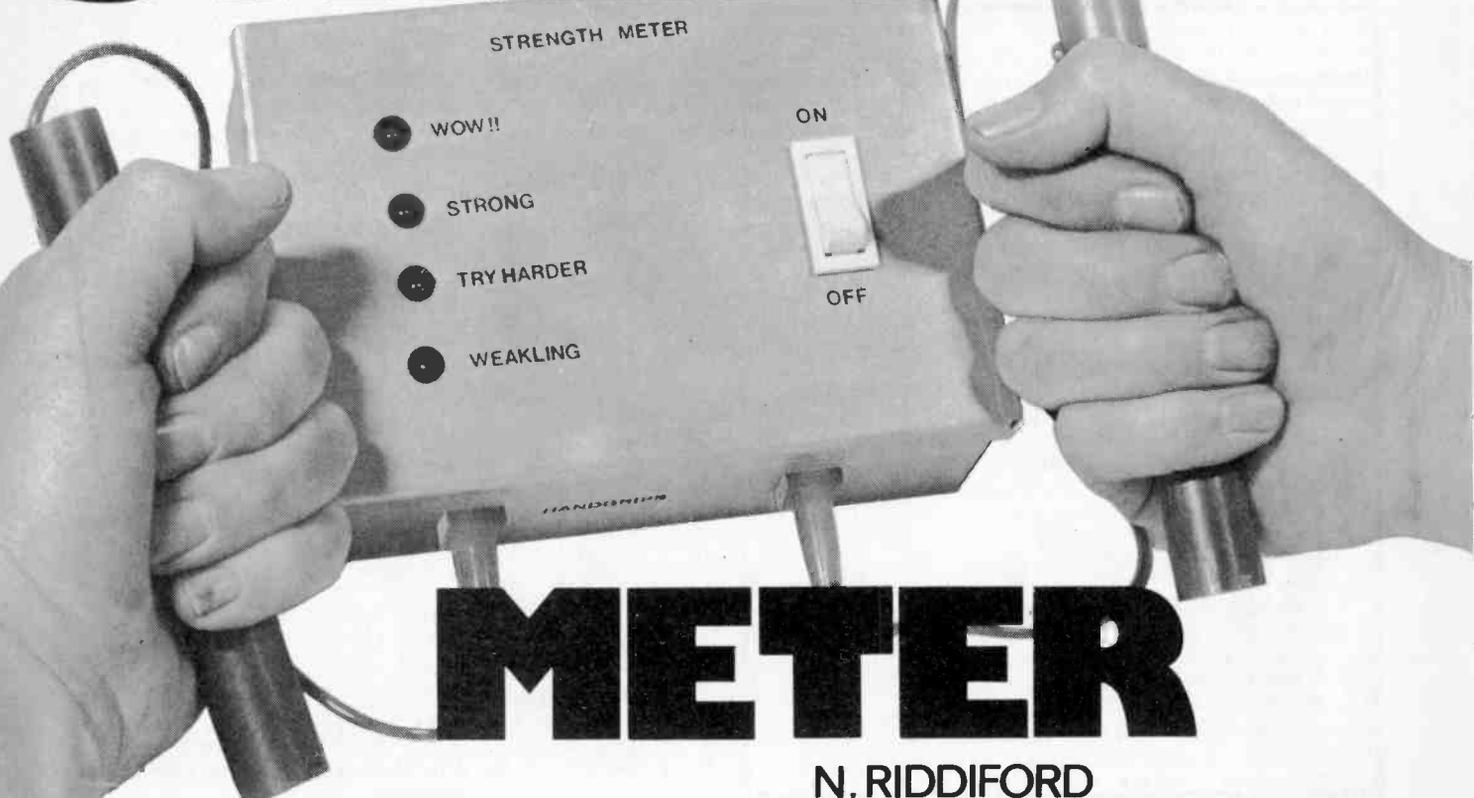

N. RIDDIFORD

Fig. 1. Complete circuit diagram of Strength Meter. The diode D5 protects TR1 from a negative voltage swing at IC1 output. Although the photographs show a single-pole on/off switch, the arrangement detailed in this circuit diagram is recommended, and uses a two-pole rocker for total switch-off

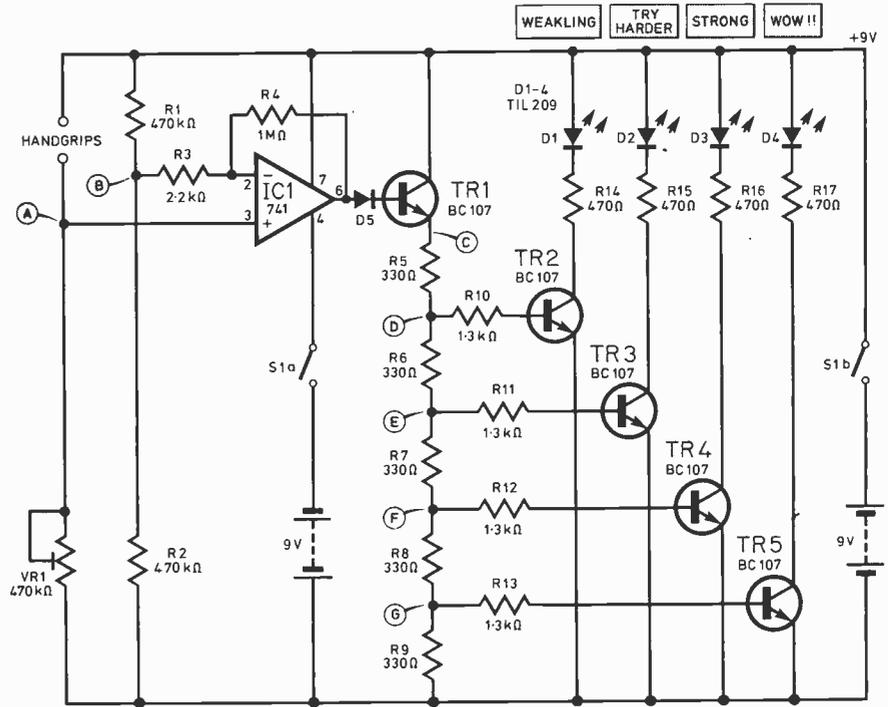

COMPONENTS . . .

Resistors

R1, R2	470kΩ
R3	2.2kΩ
R4	1MΩ
R5-R9	330Ω (5 off)
R10-R13	1.3kΩ (4 off)
R14-R17	470Ω (4 off)
All resistors ½W 5% carbon film	

Potentiometers

VR1 470kΩ horizontal preset

Semiconductors


IC1	741 8- or 14-pin d.i.l.
TR1-TR5	BC107 or similar (5 off)
D1-D4	0.2 inch red l.e.d. (4 off)
D5	1N4148 or similar

Miscellaneous

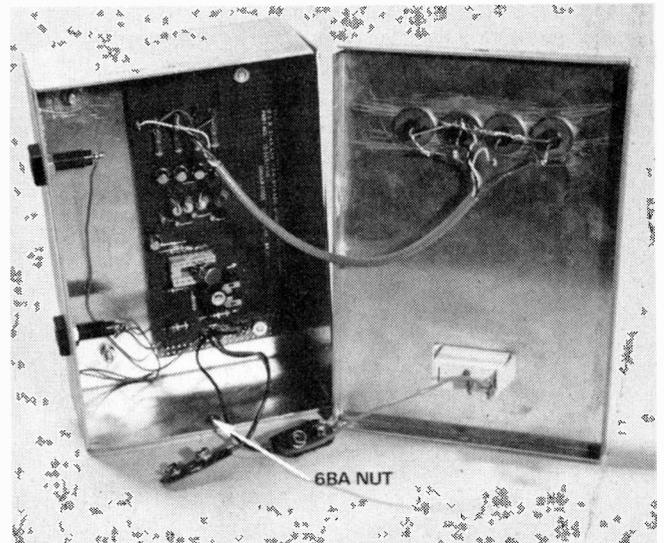0.1 inch stripboard 127 × 63mm
 14-pin i.c. socket (optional)
 4mm plugs and sockets (2 of each)
 PP3 batteries (2 off)
 Case: 155 × 105 × 53mm, or sheet alloy to form
 Suitable battery studs (2 off)
 Plastics l.e.d. bezels (4 off)
 Rocker type on/off switch D.P.C.O.
 Tubing for handgrips

suitable size cannot be found ready made. Four holes should be drilled in the base to accommodate 4BA screws for fixing rubber feet to the unit. Two of these screws should be long enough to take spacers, the stripboard and fastening nuts. Two holes need to be drilled to mount the 4mm sockets, and a further four in the lid to house the l.e.d. bezels. Finally an oblong hole should be cut out (using an Abrafile) if the R.S. type switch is used for the ON/OFF function.

The prototype box which was "home made" had 6BA nuts held in place on the side of the base, by an epoxy resin glue, to take the lid retaining screws (see photograph).




The 741 op amp in this photograph is a TO5 type, which is not the recommended i.c. package. If the box is "home made", 6BA nuts to take the lid retaining screws can be fixed to the case using Araldite Rapid or similar resin based adhesive.

Mini-priced breadboards for maxi-sized projects.

Experimenter® low-cost solderless breadboards are the first in the world specially designed for 0.3" and 0.6" pitch DIP's.

They clip together by an exclusive interlocking system in any configuration, (just like dominoes), so you arrange the breadboards to suit your circuit, not vice-versa.

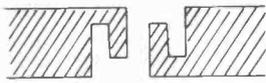
They are precision moulded from durable, flame-retardant plastic, and feature alphanumeric coding for easy circuit building, and non-corrosive, pre-stressed nickel-silver alloy contacts—reliable for well over 10,000 insertions.



EXCLUSIVE INTERLOCKING SYSTEM.




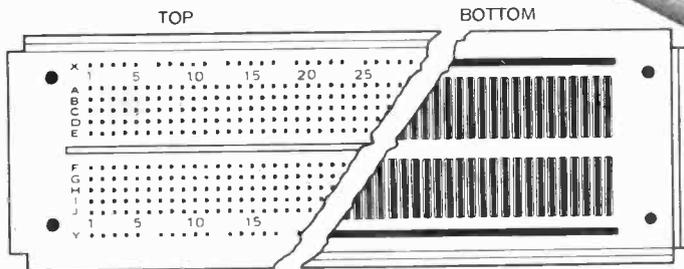Get your hands on an Experimenter and stop wasting time!



Contact resistance is a mere 0.4 mΩ and interterminal capacitance is typically less than 5 pF. The **Experimenter** is usable to over 100 MHz.

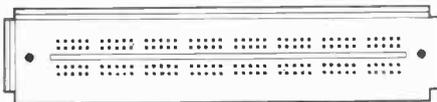Experimenter 600 and 650 models are ideal for RAM's ROM's and PROM's (0.6" centre IC's) while the 300 and 350 models are for smaller DIP's (0.3" centres). All four models, of course, also take all standard components, the 0.1" grid being compatible with transistors, diodes, LED's, capacitors, resistors, pots—in fact any component with lead sizes between 0.015" and 0.032"



A useful quad bus strip (EXP4B) further

Model	Length"	Width"	Centre channel"	5-way tie points	Bus	Price
EXP300	6.0	2.1	0.3	94(470)	2(80)	£6.77
EXP350	3.6	2.1	0.3	46(230)	2(40)	£3.69
EXP600	6.0	2.4	0.6	94(470)	2(80)	£7.35
EXP650	3.6	2.4	0.6	46(230)	2(40)	£3.99
EXP4B	6.0	1.0	N/A	N/A	4(160)	£2.83

All units are 0.330" deep. Prices include VAT (8%) and p&p for UK Orders. Add 5% to all orders outside UK. All prices and specifications correct at the time of going to press.

expands the versatility of the system for the MPU user.

Experimenter breadboards can be used alone or mounted on any convenient flat surface, thanks to moulded-in mounting holes and vinyl insulation backing that prevents short circuits. Mount them from the front with 4-40 flathead screws or from the rear with 6-32 self tapping screws.

But however you use them, **Experimenter** breadboards are the quickest and easiest way to build and test circuits. If you're working on IC's, MPU's, memories,

displays or any other circuits, buy the breadboards that are designed for you.

Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night.

Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days.

Otherwise ask for our complete catalogue.





ELECTRONICS (London) Ltd.

NASCOM I

Microcomputer for the Hobbyist

HARDWARE FEATURES:

- ☆ SUPPLIED IN KIT FORM FOR SELF-ASSEMBLY.
- ☆ FULL DOCUMENTATION SUPPLIED.
- ☆ INCLUDES PRINTED CIRCUIT BOARD.
- ☆ FULL KEYBOARD INCLUDED.
- ☆ INTERFACES TO KEYBOARD, CASSETTE RECORDER & T.V.
- ☆ 2K x 8 RAM
- ☆ 1K x 8 EPROM MONITOR PROGRAM
- ☆ POWERFUL Z80 CPU.
- ☆ 16 LINE x 48 CHARACTER DISPLAY INTERFACE TO STANDARD, UNMODIFIED T.V. SET.
- ☆ ON BOARD EXPANSION FACILITY FOR ADDITIONAL 16 LINES I/O.
- ☆ TOTAL EXPANSION TO 64K x 8 MEMORY.
- ☆ TOTAL EXPANSION TO 256 INPUT PORTS AND 256 OUTPUT PORTS.

SOFTWARE FEATURES:

- ☆ 1K x 8 'NASBUG' PROGRAM IN EPROM.
- ☆ PROVIDES 8 BASIC OPERATOR COMMANDS INCLUDING SINGLE STEP.
- ☆ EXPANDABLE SOFTWARE SYSTEM VIA ADDITIONAL USER PROGRAMS IN RAM OR EPROM.


COST £197.50 PLUS 8% VAT.

Phone or write for details to:

92 BROADSTREET, CHESHAM, BUCKS.
TELEPHONE: (02405) 75154.



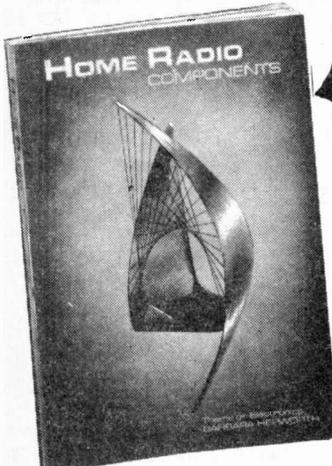*Start the New Year well
by treating yourself to this
famous
Components
Catalogue*



- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

POST THIS COUPON
with cheque or P.O. for £1.40


Please write your Name and Address in block capitals

NAME _____

ADDRESS _____

HOME RADIO (Components) LTD. Dept PE
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No
917965 London

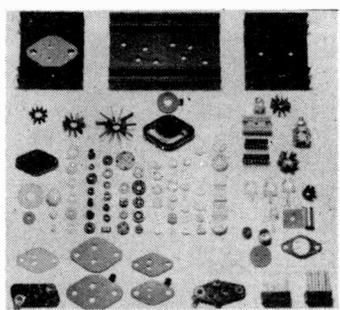


LOW PROFILE DIL SOCKETS - TIN PLATED				READY DRILLED BLACK ANODISED HEAT SINKS			
PRICE PER	1	5	10	25	TO 3	1 @ 40p	5 @ £1.80
8 PIN	10p	45p	85p	£2.00	TO 66	1 @ 40p	5 @ £1.80
14 PIN	12p	55p	£1.05	£2.50	TO 3 x 2	1 @ 70p	5 @ £3.20
16 PIN	13p	60p	£1.15	£2.75	HEAT SINK COOLERS. FITTING TO 5.		
28 PIN	25p	£1.20	£2.30	£5.50	NF 204	1 @ 14p	5 @ 65p
40 PIN	40p	£1.80	£3.50	£8.25	NF 205	1 @ 12p	5 @ 55p
STANDARD PROFILE DOUBLE-SIDED DIL - SOCKETS					NF 207	1 @ 13p	5 @ 60p
14 PIN	14p	65p	£1.25	£3.00	NF 209	1 @ 15p	5 @ 75p
16 PIN	15p	70p	£1.35	£3.25	INSULATING KITS. 5 WASHERS 10 BUSHES.		
MOUNTING PADS				10/PACK	50/PACK	MELINEX MICA	
TO 5 4 HOLE	9p	40p			TO 3	@ 28p/KIT	@ 30p/KIT
TO 18 4 HOLE	9p	40p			TO 66	@ 28p/KIT	@ 30p/KIT
CONVERTERS					BUSH SHANK LENGTH REQ. -.205, -.153, -.125, -.05, -.025-125, -.05, -.025. For TO 3 only.		
TO 99 TO DIL	55p	£2.50			TRANSISTOR INSULATION COVERS		
TO 100 TO DIL	55p	£2.50			TO 3	5 @ 35p	10 @ 70p
TO 92/98 TO TOS	9p	40p			TO 5	5 @ 15p	10 @ 25p
TO 18 TO TOS	9p	40p			TO 66	5 @ 35p	10 @ 70p
TO 98 TO TOS	9p	40p			POWER SOCKETS		
DIOLE CRADLES	10p	45p			TO 3	1 @ 14p	5 @ 65p
					TO 66	1 @ 16p	5 @ 75p
LARGER RANGE OF TRANSISTOR PADS AND INSULATING BUSHES IN CATALOGUE. ALL PRICES INCLUDE V.A.T.					TO 220 INSULATING KITS 5 Washer 5 Bushes MELINEX 20p/KIT MICA 25p/KIT.		
					POST AND PACKING 15p KITS/PADS/SOCKETS/COOLERS. 45p FOR ANODISED HEAT SINKS		

FULL ILLUSTRATED CATALOGUE - SEND 30p FOR POST AND PACKING.

FROM _____

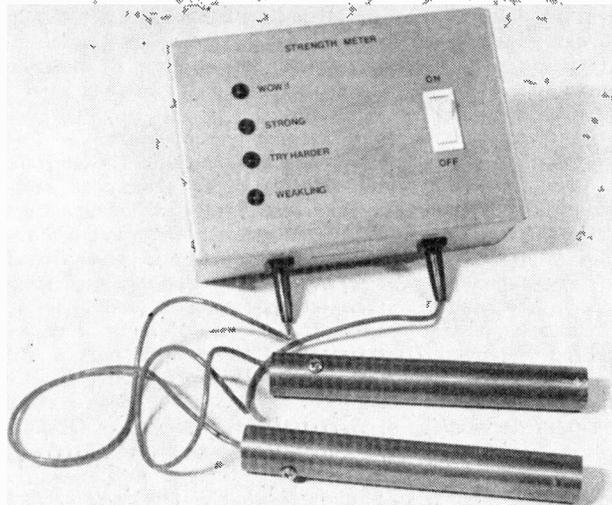MOULDED ELECTRONIC COMPONENTS INT. LTD.
34d QUARRY HILL ROAD
TONBRIDGE, KENT.
Telephone: 0732 365910



HAND-GRIPS

The hand-grips can be made from a number of things such as curtain or stair rod, or as in the prototype, 18mm diameter brass tubing. To connect wires to these it is necessary to drill a hole in each, so that a 6BA nut and bolt can be passed through to clamp a solder tag. The wires should be soldered to the tags *before* clamping them, as objects showing thermal inertia of this magnitude will not solder readily without a very large soldering iron indeed.

The prototype used 4mm plugs and sockets to terminate the hand-grips, so that they can be disconnected, wrapped in something soft, and then stored inside the case. If the recommended size is used, there will be ample room for this.

SETTING UP

The potentiometer VR1 should be adjusted so that a gentle hold on the hand-grips will just illuminate D1, the WEAKLING light. ★

NEWS BRIEFS

Exhibition

THE 1978 IEA (Instruments, Electronics and Automation) Exhibition will be held at the National Exhibition Centre, Birmingham, from March 13-17.

A computerised visitor registration and enquiry system will be operating in four languages, and this will give specific information on product categories and exhibitors to the visitor, thus providing a mutually beneficial two-way service.

The exhibitors will be of a highly international mixture, consisting of manufacturers ranging from passive components right through to computerised machine automation, and they will occupy the largest hall at the centre.

The exhibition is claimed to be the only recognised trade fair of 1978 in the U.K. covering the electronic instruments industries, and will again be held alongside ELEC-TREX, following their successful coming together in 1976.

Watts On The Road

THE first three of a planned 62 strong fleet of electric delivery vans hit the roads of London in November last year, as part of a three year plan to assess the performance of electric vehicles in urban conditions.

The machines are confined to the 0.75-1.75 tonne range, with high acceleration, regenerative braking, top speeds of around 50 m.p.h., and a realistic range of up to 60 miles per charge-up.

Under the scheme the Department of Industry is contributing in all, up to £400,000 to users of these vehicles to offset the cost over that of conventional vans.

Co-operation between the DoI, the manufacturers, the operators, the Department of Transport and the GLC, has led to the use of three types of electric vehicle being used in the scheme: 12 vehicles from Crompton Electriccars, 25 "Silent Karriers" from a consortium of Chloride Technical, Chrysler Motors and the National Freight Corporation,

and 25 "Bedford CF Vans" from Joseph Lucas Ltd. in association with Vauxhall Motors.

The GLC will collect data from such operators as Initial Services and National Carriers for collating, and a final report will be published by the DoI upon conclusion of the scheme.

Microcomputer Kit

IN the face of much criticism concerning the potential usefulness of microcomputers in the home, Lynx Electronics have launched the NASCOM 1 microcomputer kit which carries a basic price tag of £197.50 plus VAT. The launch came as part of a seminar entitled Home Microcomputer Symposium which was attended by some 550 people. Over 300 kits were sold in the two weeks following the launch.

The concepts of NASCOM 1, as described by Mr K. Borland of Lynx, were: "To produce for sale a complete microprocessor system that is of intelligent use to the home users and is priced around £200.00.

By using the best available product on the market, within our price range, to design the maximum possible system. This is an advantage that an independent design has over an in-house design by a manufacturer with his own product range.

To design for maximum control by software. By the choice of components it should be possible to totally minimise the constrictions of hardware.

To design a system that offers major future expansion. Either expansion by the user to his own design, or by additional Lynx products.

These were the four main ideas. It followed on that certain other details were going to be necessary.

Firstly, it would be essential in providing an intelligently usable system, to have a full keyboard. The limitations of a calculator type keyboard are now well known. Also any major expansion would make a full keyboard essential.

Secondly, there must be sufficient memory for the user to load and execute reasonably sized programs.

Thirdly, incorporate a fixed command program to allow easy user communication with the system.

We are delighted that it has been possible to achieve all these goals in the NASCOM 1."

For full details write to Lynx Electronics (London) Ltd., 92 Broad Street, Chesham, Bucks.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

DESK CALCULATOR

The newest calculator to be added to the Sinclair range is a desk top machine, the Sinclair President. This calculator has been specifically designed for the businessman whatever the task, be it balancing the yearly budget or working out the week's expense account. The President is exactly suited to the needs of the executive.

In style, the calculator strikes a well proportioned balance—not too heavy, yet not too light to serve as a genuine desk top model—the President will fit comfortably into a slimline briefcase.


Sinclair commissioned a consumer research programme among leading executives, and found that what was required was: a battery powered unit, but with mains option, a six function memory, a bright easy to read display, and single function keys. The President incorporates all of these!

The keyboard has a split layout. On the left are found the standard numerical and arithmetical functions, % key and six function memory. To the right are located functions specifically for business use, parenthesis, $+/-$, $x < > y$, \sqrt{x} , $1/x$, x^2 , and π .

Reflecting its desk top role, the elegant satin silver President has a large bright blue angled display, and rubber feet which keep it stable during use.

Priced at £17.95 + VAT the President is available at all leading stores, and carries the usual Sinclair 12 month unconditional guarantee.

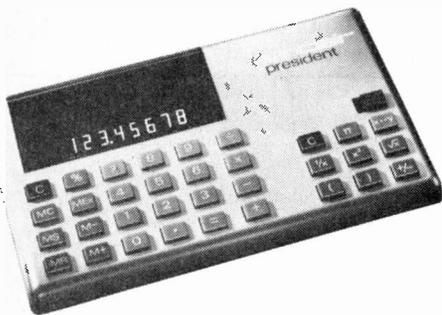Sinclair Radionics Ltd., London Road, St Ives, Huntingdon, Cambs, PE17 4HJ.



Sinclair President desk top calculator

STOPWATCH

One of the pities of metrication is that it does not extend to time measurement. With a stopwatch you can assess quite accurately the length of one cycle in hours, minutes and seconds. But you can't immediately tell how long 100 cycles will take simply by shifting the decimal point two places. You have to work instead in sexagesimal arithmetic.

To the rescue come Casio Electronics Co with their new ST-1 stopwatch/calculator. It will time any operation up to a maximum of about ten hours, to an accuracy of a tenth of a second, and then its calculator section will perform any of the four arithmetic functions you like, on that, or any other time. It can yield an answer in decimal hours and/or conventional hours, minutes and seconds.

Alternatively, the Casio ST-1 will handle ordinary decimal arithmetic, complete with independent memory, per cent and square root keys.

As a stopwatch, this instrument offers a choice of four modes: standard start/stop with automatic reset at every start, time-out or net timing where a restart carries on from the previous stop time, and lap timing with or without reset at each start. There is also a totalling feature whereby in standard stop timing, it tells you the total of say, a series of separately timed operations (from which the average can be calculated on the same machine). In the time-out mode it can indicate time loss during stoppages, and in split lap timing it adds the "splits" to give an overall time.

The calculation capacity is eight digits, or one second short of 100 hours, and there is a clip-on hood for increasing readout contrast in strong ambient light.

Measuring approximately 127mm x 76mm x 25.4mm and weighing under 5 ounces complete with AA size battery, Casio ST-1 sits neatly in the hand. Supplied with security wrist strap, this amazing little instrument has a recommended retail price of only £29.95.

Casio Electronics Co. Ltd., 28 Scrutton Street, London, EC2A 4TY.



SCRUMPI 2

Following the microprocessor development kit Scrumpi 1, comes Scrumpi 2 which has all the facilities of the former system plus additional PROM and RAM.

The new kit is still mounted on a single p.c.b. but increased in size to include two edge connectors for interfacing with extender cards. Developed around the new NMOS National Semiconductor SC/MP2 microprocessor, Scrumpi 2 from Bywood Electronics Ltd gives reduced power consumption and increased speed.

The memory consists of 768 bytes of RAM and 512 bytes of PROM. Two 4-bit latches act as an 8-bit I/O port in which each set of four can be wired as either inputs or outputs. The various functions of the kit are controlled by a flip-flop, a 555 Timer, and NAND gates, all of which are selected by eight toggle switches: RESET, SLOW, STOP, PROTECT, SENSE-A, SENSE-B, ROM/RAM START and LOAD. Programming can only be carried out during a read cycle, since during a write cycle the microprocessor is putting data on the data bus.


Interfacing facilities on Scrumpi 2 are suitable for either 4-bits or 8-bits and simple VDUs.

Scrumpi 2 will also drive several MM2112 RAM chips and/or PROM on EAROM chips without further buffering.

The basic kit (without RAM and ROM i.c.s) costs £55.56 and with the extra memory facilities £74.07. The PROM can be supplied blank or programmed by Bywood to customer specification for an extra £20.

All parts are supplied in the kit, including sockets for all i.c.s. The switches are soldered directly to the board, and the circuit needs supplies of +5V, -7V and -12V (which could be derived from a 17V supply with a 5V Zener diode).

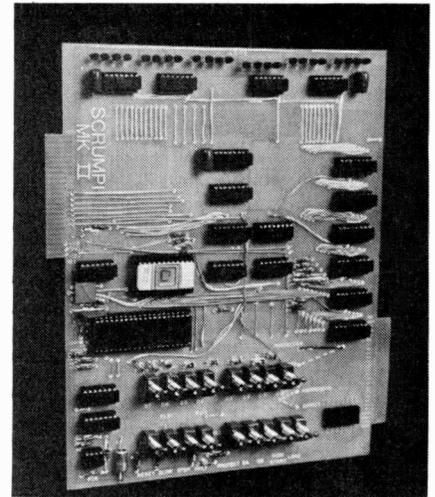Further information from Bywood Electronics Ltd, 68 Ebbens Road, Hemel Hempstead, Herts, HP3 9QR.




Scrumpi 2 from Bywood

The Sinclair PDM35.

A personal digital multimeter for only £29.95

(+8% VAT)

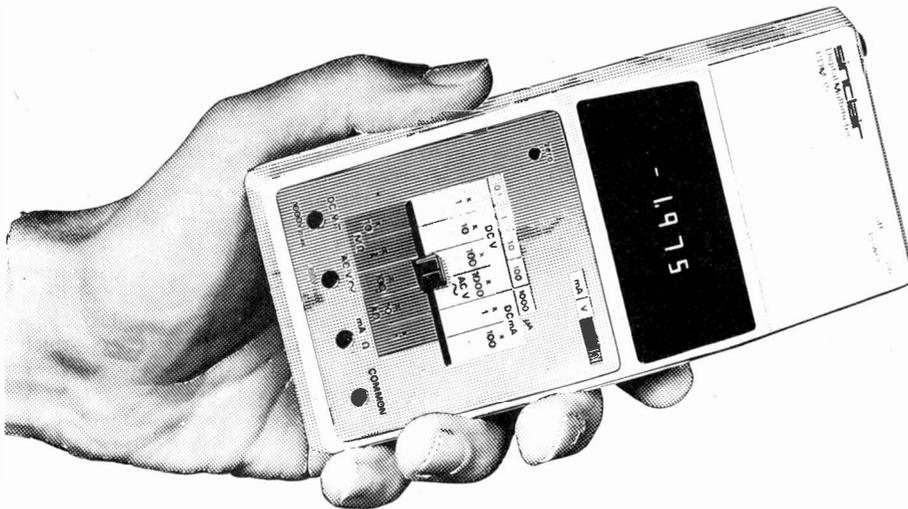

Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

What you get with a PDM35

- 3½ digit resolution.
- Sharp, bright, easily read LED display, reading to ±1.999.
- Automatic polarity selection.
- Resolution of 1 mV and 0.1 nA (0.0001 μA).
- Direct reading of semiconductor forward voltages at 5 different currents.
- Resistance measured up to 20 MΩ.
- 1% of reading accuracy.

Operation from replaceable battery or AC adaptor.
Industry standard 10 MΩ input impedance.

Compare it with an analogue meter!

The PDM 35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

Technical specification

DC Volts (4 ranges)

Range: 1 mV to 1000 V.
Accuracy of reading: 1.0% ± 1 count.
Note: 10 MΩ input impedance.

AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.
Accuracy of reading: 1.0% ± 2 counts.

DC Current (6 ranges)

Range: 1 nA to 200 mA.
Accuracy of reading: 1.0% ± 1 count.
Note: Max. resolution 0.1 nA.

Resistance (5 ranges)

Range: 1 Ω to 20 MΩ.
Accuracy of reading: 1.5% ± 1 count.
Also provides 5 junction-test ranges.

Dimensions: 6 in x 3 in x 1½ in.

Weight: 6½ oz.

Power supply: 9 V battery or Sinclair AC adaptor.

Sockets: Standard 4 mm for resilient plugs.

Options: AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ. PE/2

Please send me..... (qty) PDM35(s)
 @ £33.00 (inc £2.40 VAT and 65p P&P) each:..... £.....

..... (qty) De-luxe padded carrying case(s) @ £3.00 (inc VAT and P&P) each:..... £.....

..... (qty) AC adaptor(s) for 240 V 50 Hz power @ £3.00 (inc VAT and P&P) each:..... £.....

I enclose cheque/PO made payable to Sinclair Radionics Ltd for (indicate total amount):..... £.....

I understand that if I am not completely satisfied with my PDM35, I may return it within ten days for a full cash refund.

Name.....

Address.....


sinclair
 World leaders in fingertip electronics

All prices include V.A.T. Carriage & packing add 25p (U.K.). Add extra for overseas. C.W.O. only. Discounts over £5 less 5%, over £10 less 10%, over £25 less 15%, over £50 less 20%.

ASTRA-PAK

92 GODSTONE ROAD
WHYTELEAF SURREY CR3 0EB

★ NEW ★ FULLY GUARANTEED COMPONENTS ★
FULL SPEC SEMICONDUCTORS ★ QUANTITY
DISCOUNTS ★ SEND S.A.E. FOR COMPLETE LIST ★

BEAD TANTALUM		ELECTROLYTICS	
.1 22 33 47 .68 1µF 35V all values	1p	16V 25V 40V 63V	
11p; 2.2 3.3 4.7 6.8µF 35V all values	1.5	04p 05p 05p 06p	
14p; 10µF 25V 22µF 18V both values	2	04p 05p 05p 06p	
13p; 33µF 10V 14p; 47µF 6.3V	2.2	04p 05p 05p 06p	
58 and 100µF 3V all values 18p; 47µF	3	04p 05p 05p 06p	
16V 20p; 100µF 10V 48p	4	04p 05p 05p 06p	
CARBON FILM RESISTORS		POLYESTER 100V Radial lead	
1/2 Watt 10 10MG—E12 Series 1p	6.8	001 0012 0015 0018 0022	
each .9p for 10 of any one value.	10	0027 0033 0039 0047 0056	
75p for 100 of any one value.	22	0068 0082 01 .045 012 015	
I.C. SOCKETS		018 022 05 027 033 039	
8 pin 11p	33	047 055 056 068 07 082	
14 pin 15p	47	1 12 15 075 18 22 27 09	
18 pin 24p	68	33 10 39 11 47 12	
22 pin 38p	88		
24 pin 40p	100		
28 pin 52p	150		
40 pin 70p	220		
	4700		
S.C.R.s		LEDs	
1Amp 200V 30p	100	0 125m 0 2in	
4Amp 200V 40p	150	11p 13p 18p 26p	
4Amp 400V 50p	220	11p 15p 20p 28p	
7Amp 100V 50p	330	12p 16p 22p 32p	
7Amp 200V 65p	470	14p 18p 26p 36p	
10Amp 400V 80p	680	18p 24p 35p 48p	
16Amp 100V 75p	1000	20p 29p 40p	
	2200	24p 32p 60p	
	4700	39p 52p 85p	
400mW ZENER		DIODES	
1Amp 200V 30p	2 7V .33V	4Amp 200V 40p	
4Amp 200V 40p	each	4Amp 400V 50p	
7Amp 100V 50p	80p for 10	7Amp 100V 50p	
7Amp 200V 65p	(Any)	10Amp 400V 80p	
10Amp 400V 80p	£3.50 for 50	16Amp 100V 75p	
16Amp 100V 75p	£8.25 for 100		
1 WATT ZENER DIODES			
3.3V-100V	18p		

AC128 .14	BC212 .12	BSX19 .18	OC35 .95
AD161 pr.80	BC212L .11	BSX21 .20	OC36 .96
AD162 .80	BC213 .11	BSY25 .38	OC71 .25
8AX13 .04	BC213L .11	BYX10 .14	OC84 .65
8AX16 .05	BC214 .13	BYX36-150 .08	TIL31 1.70
8C107 .085	BC214L .13	CI06D .60	TIL33 1.70
8C107B .085	BC2618 .15	ME3001 .12	TIL111 1.00
8C108 .085	BC549 .12	NJE340 .65	TIP29A .46
8C109 .09	BCY42 .25	NJE371 .66	TIP29B .50
8C142 .25	BCY70 .17	MJE521 .80	TIP29C .60
8C143 .26	BCY71 .18	MJE2955 .92	TIP30A .52
8C147 .09	BCY72 .16	MJE3055 .65	TIP30B .55
8C148 .09	BD131 .40	MPP102 .38	TIP30C .66
8C149 .09	BD132 .41	MPS5172 .14	TIP31A .50
8C157 .10	BD133 .50	MPS6522 .20	TIP31B .55
8C158 .11	BD139 .46	MPSA-06 .22	TIP31C .64
8C159 .11	BD140 .48	MPSA-13 .24	TIP32A .61
8C171 .10	BF241 .25	MPSA-56 .22	TIP32B .61
8C172B .11	BF258 .24	MPSU-01 .35	TIP32C .70
8C177 .16	BFX85 .23	MPSU-51 .38	TIP41A .67
8C182 .11	BFX86 .23	OA47 .08	TIP41B .70
8C182L .11	BFX87 .22	OA79 .08	TIP41C .82
8C183 .11	BFX88 .22	OA81 .08	TIP42A .75
8C183L .11	BFY50 .16	OA90 .07	TIP42B .80
8C184 .11	BFY51 .16	OA91 .075	TIP42C .90
8C184L .11	BPY52 .16	OA202 .085	TIP3055 .50
8C187 .18	BR100 .26	OC20 1.80	TIS43 .30
8C208 .12	BRY39 .46	OC28 .95	Z781 .50

ZTX107 .10	2N1306 .20	2N4126 .16	ELECTROLYTIC PAK
ZTX304 .20	2N1307 .36	2N5133 .16	1lb. in weight.
ZTX450 .20	2N1513 .21	2N5136 .16	Approximately
ZTX502 .20	2N2219 .20	2N5142 .18	50 capacitors
ZTX604 .26	2N2221 .17	2N5458 .28	Mixed values of
ZTX550 .20	2N2222 .18		capacitance and
1N914 .06	2N2222A .20	voltages.	
1N916 .07	2N2368 .20	RECTIFIERS	
1N918 .07	2N2368B .20	25 Amp Cathode	
1N4001 .06	2N2389 .22	case Press fit type	
1N4002 .06	2N2646 .42	50V .32	
1N4003 .06	2N2904 .20	100V .40	
1N4004 .075	2N2904A .22	200V .50	
1N4005 .09	2N2906 .18	400V .62	
1N4006 .095	2N3053 .17	600V .75	
1N4007 .10	2N3054 .42	1000V 1.00	
1N4148 .08	2N3055 .42	35A 30V Anode case	
1N5400 .13	2N3440 .50	Press fit type .15	
1N5402 .16	2N3702 .08	40A 100V Stud .70	
1S44 .05	2N3704 .07	StateAnode/Cathode	
1S020 .11	2N3705 .07	BRIDGE	
1S920 .06	2N3706 .08	RECTIFIERS	
1S921 .07	2N3707 .08	ceramic,	
1S922 .08	2N3710 .07	polycarbonate,	
1S923 .09	2N3771 2.20	mica, electrolytic,	
1S951 .10	2N3773 3.10	etc.	
1S951 .10	2N3773 3.10	40A 100V 1.80	
1S951 .10	2N3773 3.10	25 Amp 100V 1.80	
1S951 .10	2N3773 3.10	Full list of linears,	
1S951 .10	2N3773 3.10	CMOS, 7400 TTL & BOOKS	
1S951 .10	2N3773 3.10	AVAILABLE	

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE

- ★ 30A power transistors
- ★ 2-year guarantee
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S

TAM1000 100W 4 ohms 65V	£9-80
TAM500 50W 4 ohms 45V	£7-50
TAM250 25W 8 ohms 45V	£5-75


POWER SUPPLIES

For 1 or 2 TAM250/500	£7-50
For 1 or 2 TAM1000	£9-80

(Carriage 50p on supplies)

- Suits loads 4-16 ohms
- 20-20,000 Hz ± 1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

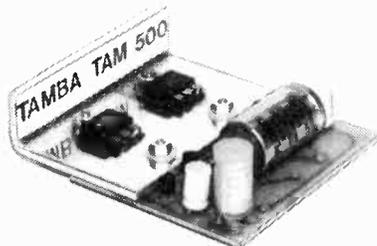High grade components used throughout: Texas, Mullard, R.C.A., Plessey, etc.



- Low distortion (0.1%)
- Low profile (1in high 3½in x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections

NEW

ALL PURPOSE MIXER/PRE-AMP.

(with 60mm slider volume)

- Suitable for multiple input systems
- High and low impedance inputs
- High sensitivity
- Built-in supply smoothing
- 20-20,000 Hz ± 1dB
- -80dB noise level
- Accepts a wide variety of inputs
- Wide range bass and treble controls

Use up to 10 PRE-AMPS with 1 power supply

Printed circuit board assembly with treble and bass controls plus slider volume control

£6-50

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W systems and at 12½% for 25W systems (including preamp if ordered at same time).

Hours, 9.30 a.m.—5 p.m.
Monday — Saturday.
Callers welcome. Tel. (01) 684 0098

TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

For Semi-Conductors

including
Small Signal Transistors
Power Semi-conductors
TTL, CMOS, I.C.s
Linear I.C.s
Signal and Power Diodes
Zener Diodes
Magneto Resistors
Hall-effect devices
Magnetic Proximity Switches
Opto-electronic devices

Go to
ELECTROVALUE
TO MAKE THE BEST OF

For passive components

including
Plastic Film Capacitors
Electrolytics
Semi-precision capacitors
Transformers
Pot Cores
R. M. Cores
Ring Cores, etc.


Go to
ELECTROVALUE
THE PROJECTS YOU BUILD

For Service & Quality

It's the Electrovalue Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated. 40p post free with 40p voucher usable on orders for £5 or more. Send for yours now and order in confidence.
GOODS SENT POST FREE IN U.K. FOR C.W.O. ORDERS £5.00 or more. If under, add 25p handling charge. Keenly competitive prices plus **ATTRACTIVE DISCOUNTS** and only best quality goods.

ELECTROVALUE LTD

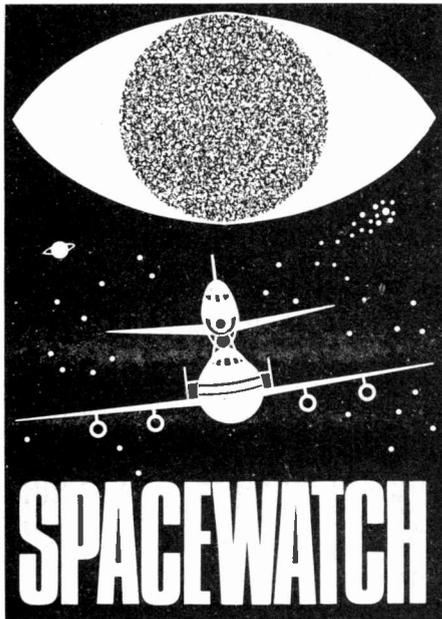(Dept. PE28) 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. Tel. Egham 3603. Telex 264475. North: 680 Burnage Lane, Burnage, Manchester. Tel. (061) 432 4945



FRANK W. HYDE

UN-IDENTIFIED FLYING OBJECT

Now that the excitement of a possible new planet has died down it is perhaps a good time to look at the facts that are available. The suggested size is between 100 and 400 miles in diameter, that the orbit is near circular and that the orbit lies between Saturn and Uranus.

From these data it can be deduced that the object is not a comet because a comet has a highly eccentric orbit. The orbit was determined by sequential photographs so that the circular orbit is now confirmed. The probable distance from the Sun is about 1,500 million miles. It is possible that this "Object Kowal" is the first of a new swarm of asteroids. If a regular watch is kept, it could well be possible that the computation of the orbit, would show that Voyager I might observe it after leaving the vicinity of Saturn and on its way to Uranus.

Many of these small bodies are now on record and Charles Kowal now has the right to choose a name for his discovery. The number of the planetoid is 2042. It is interesting to record that by about 1890 some three hundred of these small planetary bodies were known. A year later another of those new applications of technology which open up new vistas took place. This time it was the advent of photographic methods which widened the horizons. Very quickly many hundreds of faint objects were identified as coming from the asteroid belt which lies between the orbits of Mars and Jupiter.

Another spurt was given when computers appeared and now over 2,000 are numbered, and at least a similar figure covering those lost or not yet determined

exactly. Since they can be accurately timed both into the future and back into the past their behaviour in relation to other planets in the solar system can be examined; even so, many of these bodies are just accidental discovery.

So scarce is time on the world's telescopes that searches for those lost is not economically possible. This emphasises the value of orbiting telescopes with continuous operation. In fact technically there is a great advantage, for only small telescopes are required in space for purposes of this kind. That there is very great scientific interest in knowing about these bodies is shown by the fact that already there are a number of projects for sending probes to land on or take samples from them. A great deal is already known and it would need a lengthy article to describe the present state of the art.

LIFE AND DEATH FROM OUTER SPACE

Whenever something unusual occurs in the environment or in space, outside agencies are postulated as being concerned with the welfare of the human race. Scarcely a week passes without some past happening being brought out as support for unknown origins of events. It is not surprising therefore that from science fiction and "new thought" a new look at data takes place. Much of it may be discarded at once but always there is left a glimpse of what might be. If it stirs someone or some team to relook at past happenings and link them with new possibilities then it is worth while as an exercise. In the dissemination of knowledge the negative results often have the greatest impact.

The sensational situation has arisen about the star Sirius and its "companions". On the strength of some "evidence" from religious beliefs a whole edifice of presumed happenings has been raised. Many people are now convinced that the skills and ills were brought by someone from outer space. Diagrams and pictures are produced in support of the idea mostly without careful examination and indeed in some cases manipulation to support the theory. On this particular theory great claims have been made that scientists are actively, and keenly supporting the theory. In fact this is not so.

To set the scene for this Sirius mystery, the first point of importance is that Sirius is an extremely unlikely candidate for the support of a planetary system. It is true that some very eminent astronomers have indeed been active in their examination of certain data. However, no evidence has been found to support the claims as made. There is the existence of the folk lore, which at first sight is difficult to evaluate. However, this is not really the field of astronomy or space science, still less can it be justified when more specialised branches of science engage in such matters.

Two radio observatories have just released information of their previously unpublished activities. One of these in Canada used a 46 metre radio telescope with entirely negative results. No intelligible signals were received. The other observatory is that of Ohio State University where Dr. R. S. Dixon used the 21 centimetre hydrogen line frequency. Over a period of search, carried out each day, there were no detectable transmissions. The publications from the sensational media do not take into account these tests. Indeed two British scientists found it necessary to insist on a disclaimer that they supported the theories. This particular case has been cited because it is concerned with space. It follows then that the less fanciful but certainly more tenable cases should be in the same area. Both are concerned with life on earth as well as in space.


A number of disciplines have been concerned with the possibility of life having begun outside the earth and found its way to the planet. It is so frequent for the work of some individuals and groups to be quoted out of context in support of sensation, yet in the cases now to be detailed there are sensational features. It has often been put forward that cometary bodies could be carriers of some form of life. The earth passing through a tenuous medium would not, except by the use of highly sophisticated techniques, show any indication that anything had happened.

Scientists Sir Fred Hoyle and Chandra Wickelmaier announced that they favour the theory that in the centres of comets there exist the building blocks of life and disease. As the comets travel through the solar system changes take place which lead to the formation of new viruses and bacteria. When a comet brushes the Earth these are released. The two scientists suggest that this is a far more plausible account of new epidemics.

A number of groups are investigating the possibilities of life being brought to Earth by means of meteorites and other interplanetary debris. In Russia V. I. Goldanski of the Institute of Chemical Physics of the Academy of Sciences in Moscow is known to be working in this area. Certain changes take place near absolute zero temperature and interstellar clouds could be a source of the grains of cold life. A new planetary system rich in dust would be an ideal situation for this kind of evolution.

LANDSAT

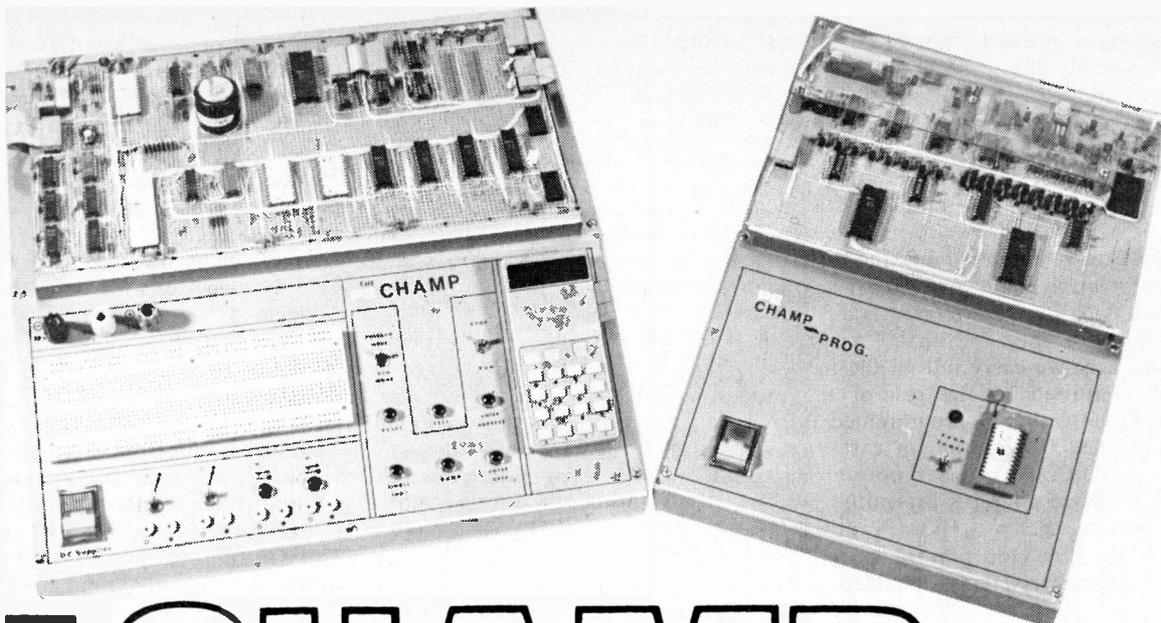The Landsat vehicle is to help the Navajo Indians to assess the resources of their 16 million acres of reservation, the volume of timber and its condition. This is the first time a private company has had this kind of co-operation with NASA. The activity will eventually range over five states. A great deal of headway has been made with this satellite which has justified the project.



PE CHAMP

R.W. COLES
B. CULLEN

PART SIX

Now that the "hardware" description of CHAMP is complete, we can move on to consider that magic new ingredient, "software". As you will no doubt recall, the program which makes CHAMP work is called CHOMP (CHamp Operating system and Monitor Program), and this month we shall examine the program.

COMMERCIAL KITS

Most commercial microprocessor development kits provide the user with only a simple listing of their operating programs, and ploughing through these listings to gain an understanding of how the system operates can be a painful experience.

CHAMP is for hardware oriented people; not the software genius; so we have done more than just provide a simple listing of the code you will need in PROM chip zero to get CHAMP to work. We cannot, for space reasons, give an intimate description of every line in the program, but we will be discussing the overall program flow chart. As an introduction to programming techniques, we will be showing how segments of the overall flow chart are converted first into more detailed flow charts, and then into hexadecimal code. In this way we hope to use CHOMP not only as an essential part of CHAMP, but also as a sort of software training ground for fledgling CHAMP programmers!

Constructors are advised to spend some time developing a familiarity with this program, and also of course with the 4040 instruction set which it uses.

4702A PROM

CHOMP should, strictly speaking, be called a firmware program, because it resides not on paper tape or magnetic cassette, but in a ROM or Read Only Memory. The type of ROM used is in fact an erasable and reprogrammable type using the FAMOS technology, and these devices are

more properly described as EPROMS, or just PROM for short. The actual device used is the 4702A chip which contains 256 eight bit words, has supply requirements compatible with the 4040, and can be erased by means of exposure to short wave ultra violet light. The 4702A is a selection from the 1702A family, characterised to work on +5V and -10V supplies over the full temperature range, instead of the usual +5V and -9V of the 1702A. The 4702A is also a less speedy device than the 1702A, having a 1.7 μ s maximum access time. The only extra requirement the 4702A has, is for that extra volt on the supply rails, and in fact it is virtually certain that any 1702A chip will work well in the CHAMP circuit, at least over the usual domestic temperature range. This has been tried on the prototype with complete success, and opens up the possibility of using the low cost 1702As now being advertised. Of course, it is not possible for us to *guarantee* success with anything other than the 4040 manufacturers' recommended 4702A devices.

CHOMP uses 248 locations out of the 256 available in a 4702A, and the PROM containing CHOMP has to be plugged into the CHIP ZERO location, i.e. the left hand PROM socket.

MAIN FLOW CHART

Figure 6.1 shows the main flow chart of CHOMP, and this is in effect an overview of the whole program in a much simplified form. We have chosen to use just four symbols to draw the flow chart:

- Circles represent the beginning and end of events.
- Oblong boxes represent actions to be performed.
- Diamonds represent decision points with two possible exits.
- Square arrows represent "Jumps" to other pages of memory.

When power is first applied to CHAMP, or when the

RESET button is pressed, the 4040 address counter is cleared to address 000H, and it fetches its next instruction from this address, which is of course the first location in chip zero, and the beginning of CHOMP. The flow chart can be traced from this RESET point which is located at the top left of Fig. 6.1.

The first box is not very exciting; it simply tells us that we must jump past address 003H, because this is the program location which contains the first instruction of the Interrupt routine, and we only want to go to *that* address when a hardware interrupt is acknowledged.

Box three represents the first "meaty" part of the program, and here we carry out all the preliminary house-keeping jobs required by the rest of the program. The 4265 INPUT/OUTPUT chip is programmed into mode 9; the switch flag latches are cleared (in case any were already indicating a switch closure when power was applied), and the various software counters are initialised to a required starting condition (i.e. the CHOMP address counter is set to point to the first location in program RAM, 200H). Finally, the interrupt system is enabled so that any interrupt signal from now on will cause the 4040 to save the current address on its internal stack, and jump to 003H, the interrupt vector. The only source of interrupt recognised by CHOMP itself is the keyboard, but for the moment let's assume that no interrupt has been received and continue on to box 4.

After initialisation, the CHOMP address counter holds 200H, and this box is present to load that address value into the display buffer register, so that we can see it on the right hand three display digits. Notice that box 4 is also entered via LOOP 2, and in this case the current address value (whatever it is) will be displayed.

Box 5 performs the vital job of refreshing the l.e.d. display. Each time this box is entered, a new eight bit word is presented to the segment lines and the display shift register is stepped on one position. Eight entries are required to refresh the complete display, and to ensure regular use, box 5 is made part of LOOP 1, through which the 4040 cycles continuously as long as no control switches are pressed.

Box 6 is also part of LOOP 1, and the main purpose of this box is to read into the 4040 accumulator register the state of the four control switches, so that the state of these may be checked and appropriate action taken. The interrupt system is again disabled at this point to prevent interference with switch responses. The INTERRUPTS RECOGNISED zone is quite extensive enough for a prompt response to any key press, and making the rest of the program interruptible would be an unnecessary complication.

Box 7 is a decision based not upon the switch flags, but upon the separate 4040 TEST input. If the TEST button is pressed, box 7 ensures a jump to the start of Chip 1, address 100H. Chip 7 is normally used for the PROMPT programmer software of course, but if the programmer is not in use, any 4702A resident program can be started by pressing TEST.


Boxes 8, 9, 10 and 11, check each of the switch flag bits in the accumulator in turn, by shifting them into the carry flip-flop and performing a JCN instruction. If no switches are pressed at box 6 time, then LOOP 1 is completed, and is in fact repeated indefinitely, refreshing the display and checking the switches on each pass. Needless to say, CHAMP spends most of its time in this loop when CHOMP is running, only leaving it intermittently, to respond to control switch closures.

If the ENTER DATA switch is pressed then CHAMP exits from LOOP 1 at box 8. Box 12 represents a routine which takes data previously entered via the keyboard and stores that data (8 bits) in the program RAM location pointed to by the CHOMP address counter, before passing on to box 16 to increment to the next address in sequence. The new address is displayed by means of box 4, and then LOOP 1 is re-entered.

If the ENTER ADDRESS switch is pressed, then LOOP 1 is left at box 9. Box 13 is then executed, and this loads the three digit hexadecimal data previously entered via the keyboard into the CHOMP address counter to replace the previous contents. In this case there is no need to increment the address counter, and so LOOP 1 is re-entered via LOOP 2.

When the DUMP switch is pressed, a sequence of operations similar to those for ENTER DATA takes place, although in this case box 14 represents a routine which reads data (8 bits) from the program RAM location pointed to by the CHOMP address counter, and loads it into the display buffer for examination. When the PROGRAM MODE/RUN MODE switch is in the RUN position box 15 is entered, and a routine is executed to cause an unconditional jump to the start of the user program RAM at address 200H. From this point onwards of course, CHOMP has relinquished its control of CHAMP facilities to whatever user program is resident in RAM.

Fig. 6.1. CHOMP main flow chart. The complete CHOMP program, taken from a larger computer print-out, is shown on the centre pages

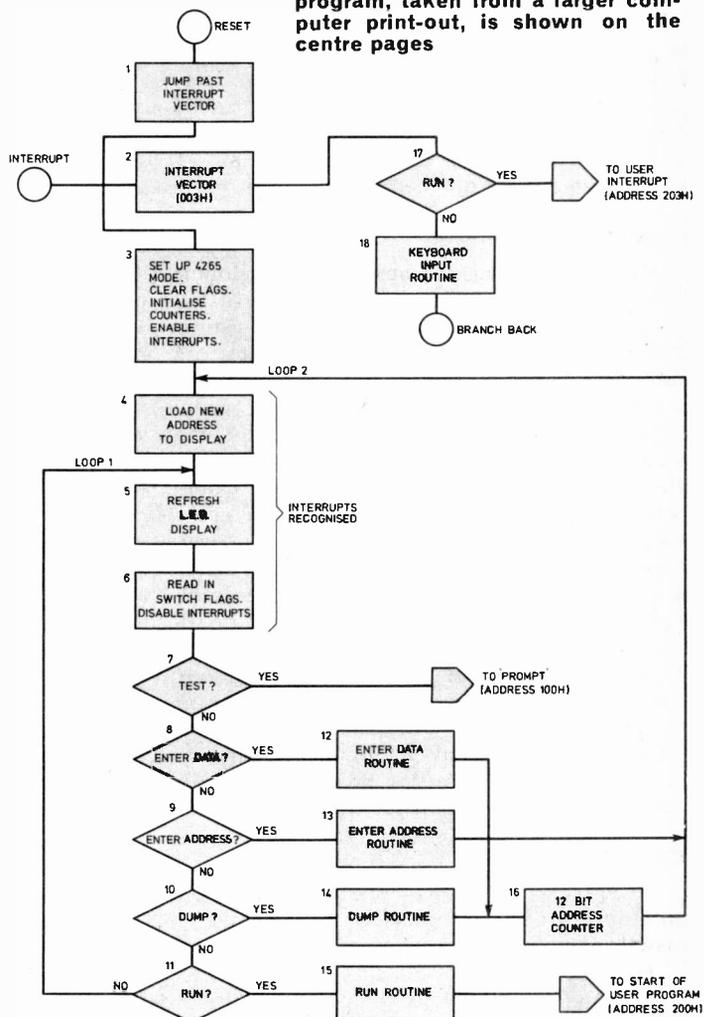

0042	AC	LD 0CH	
0043	B2	XCH 2	
0044	AE	LD 0EH	
0045	B4	XCH 4;	RELOAD COUNTER WITH 12 BIT ADDRESS CLEAR SWITCH FLAGS
0046	5097	JMS CLRFI;	
0048	400E	JUN LOOP 2	
004A	2C00	DUMP: FIM 0CH, 00H	
004C	2800	FIM 8, 00H	
004E	29	SRC 8	
004F	A4	LD 4	
0050	E1	WMP;	SELECT RAM CHIP
0051	23	SRC 2;	ADDRESS BYTE
0052	0E	RPM;	GET LS NIBBLE
0053	BC	XCH 0CH	
0054	0E	RPM;	GET MS NIBBLE
0055	BE	XCH 0EH	
0056	2A00	FIM 0AH, 00H;	CLEAR KBD COUNT
0058	2850	FIM 8, 50H	
005A	29	SRC 8	
005B	E2	WRR;	CLEAR FLAGS BUT NOT KBD DISPLAY DUMP BYTE
005C	50CE	JMS LOKY	
005E	730E	COUNT: ISZ 3, LOOP 2	
0060	720E	ISZ 2, LOOP 2	
0062	740E	ISZ 4, LOOP 2	
0064	400E	JUN LOOP 2;	ADDRESS COUNTER
0066	0B	INTER: SB1	
0067	B6	XCH 6	
0068	F7	TCC;	SAVE AC AND CARRY
0069	B7	XCH 7	
006A	2240	FIM 2, 40H	
006C	23	SRC 2	
006D	EA	RDR;	GET PROG/RUN SWITCH
006E	F5	RAL;	PUT IN CY
006F	1276	JC PROMO;	ARE WE IN PROG MODE?
0071	A7	LD 7;	USER IR SO RESTORE STATUS
0072	F6	RAR	
0073	A6	LD 6	
0074	4203	JUN 203H;	GO TO USER IR
0076	2480	PROMO: FIM 4, 80H;	SELECT 4265
0078	25	SRC 4	
0079	EC	RDO;	GET KBD BCD
007A	BF	XCH 0FH;	PUT IN KBD TEMP
007B	6B	INC 0BH;	BUMP TABLE INDEX
007C	6B	INC 0BH	
007D	D8	LDM 8	
007E	BA	XCH 0AH;	MS TABLE INDEX NIBBLE
007F	AF	LD 0FH;	PUT KBD IN ACC
0080	3B	JIN 0AH;	BRANCH VIA TABLE
0082		ORG 082H	
0082	4088	TABLE: JUN FIRST	
0084	408B	JUN SECON	
0086	408E	JUN THIRD	
0088	BE	FIRST: XCH 0EH;	FIRST KBD DIGIT INRE
0089	4091	JUN TERM	
008B	BC	SECON: XCH 0CH;	SECOND TO RC
008C	4091	JUN TERM	

00C9	78C9	LOOP 3: ISZ 8, LOOP 3	
00CB	79C9	ISZ 9, LOOP 3	
00CD	C0	BBL 0H	
00CE	2800	LOKY: FIM 8, 00H;	SET UP ADDRESS
00D0	AE	LD 0EH	
00D1	B1	XCH 1;	GET LOW FOUR
00D2	50DD	JMS HEXL;	CONVERT TO SEVEN SEG CODE
00D4	AC	LD 0CH	
00D5	B1	XCH 1;	
00D6	50DD	JMS HEXL;	CONVERT TO SEVEN SEG CODE
00D8	AD	LD 0DH	
00D9	B1	XCH 1	
00DA	50DD	JMS HEXL;	CONVERT TO SEVEN SEG CODE
00DC	C0	BBL 0H	
00DD	DF	HEXL: LDM 0FH;	SEVEN SEG TABLE LOOKUP
00DE	B0	XCH 0;	TABLE BASE IN RP 0
00DF	30	FIN 0;	GET SEG CODE FROM TABLE
00E0	29	SRC 8	
00E1	A1	LD 1;	FIRST FOUR TO 4002
00E2	E0	WRM;	
00E3	69	INC 9;	BUMP NIBBLE POINTER
00E4	29	SRC 8	
00E5	A0	LD 0;	LAST FOUR TO 4002
00E6	E0	WRM;	
00E7	69	INC 9;	BUMP NIBBLE POINTER
00E8	C0	BBL 0	
00F0		ORG 0F0H	
00F0	7E	DB 07EH	
00F1	0C	DB 00CH;	LOOKUP TABLE
00F2	B6	DB 0B6H	
00F3	9E	DB 09EH	
00F4	CC	DB 0CCH	
00F5	DA	DB 0DAH	
00F6	FA	DB 0FAH	
00F7	0E	DB 00EH	
00F8	FE	DB 0FEH	
00F9	DE	DB 0DEH	
00FA	EE	DB 0EEH	
00FB	F8	DB 0F8H	
00FC	72	DB 072H	
00FD	BC	DB 0BCH	
00FE	F2	DB 0F2H	
00FF	E2	DB 0E2H	

SYMBOL TABLE

CLRF	0097	COUNT	005E	DATO	00C5	DDRV	00B1
DUMP	004A	ENTAD	0040	ENTDA	0032	FIRST	0088
HEXL	00DD	INTER	0066	LADR	00A2	LOKY	00CE
LOOP 1	0010	LOOP 2	000E	LOOP 3	00C9	PASS	00C7
PROMO	0076	RUN	0028*	SECON	008B	SKIP	001D
TABLE	0082*	TERM	0091	THIRD	008E		

Fig. 6.2. Complete CHOMP program

```

000 00 NOP
0001 4005 JUN $ + 4;
0003 4066 JUN INTER;
0005 2880 FIM 8, 80H
0007 29 SRC 8
0008 D9 LDM 9
0009 E1 WPM;
000A 5097 JMS CLRF;
000C 2428 FIM 4, 28H;

000E 50A2 LOOP 2; JMS LADR;
0010 0C LOOP 1; EIN;
0011 50B1 JMS DDRV;
0013 2840 FIM 8, 40H
0015 29 SRC 8
0016 EA RDR;
0017 0D DIN;
0018 F6 RAR;
0019 111D JNT SKIP;
001B 4100 JUN 100H
001D 1A32 SKIP: JNC ENTDA;
001F F6 RAR;
0020 1A40 JNC ENTAD;
0022 F6 RAR;
0023 1A44A JNC DUMP;
0025 F6 RAR;
0026 1210 JC LOOP 1;
0028 5097 RUN: JMS CLRF
002A 2880 FIM 8, 80H
002C 29 SRC 8
002D F0 CLB
002E E5 WR1;
002F E6 WR2
0030 4200 JUN 200H;

0032 2800 ENTDA: FIM 8, 00H
0034 29 SRC 8
0035 A4 LD 4
0036 E1 WPM;
0037 23 SRC 2;
0038 AC LD 0CH
0039 E3 WPM;

003A AE LD 0EH
003B E3 WPM;
003C 5097 JMS CLRF;
003E 405E JUN COUNT;
0040 AD ENTAD: LD 0DH;
0041 B3 XCH 3

```

```

SKIP INTERRUPT
INTERRUPT VECTOR

SET UP 4265 MODE
CLEAR SWITCH FLAGS
SET MS ADDR. COUNT AND
DDRV COUNT
LOAD ADDRESS TO DISPLAY
ENABLE INTERRUPTS
DISPLAY DRIVER

READ IN SWITCHES
DISABLE INTERRUPTS
FIRST FLAG TO CY
JUMP TO CHIP 1 IF TEST SET

ENTER DATA?
NEXT FLAG TO CY
ENTER ADDRESS
NEXT FLAG TO CY
DUMP?
LAST FLAG TO CY
RUN OR BACK AGAIN

BLANK DISPLAY

JUMP TO USER PROG IN
CHIP 2

SELECT PROGRAM RAM CHIP
ADDRESS BYTE

WRITE LEAST SIG NIBBLE
TO RAM

WRITE MOST SIG NIBBLE
CLEAR SWITCH FLAGS
BUMP ADDRESS COUNT
PUT KBD IN COUNTER

```

```

008E BD THIRD: XCH 0DH;
008F 2A00 FIM 0AH, 00H;
0091 50CE TERM: JMS LOKY;
0093 A7 LD 7
0094 F6 RAR;
0095 A6 LD 6
0096 02 BBS
0097 2850 CLRF: FIM 8, 50H;
0099 29 SRC 8
009A E2 WRR;
009B 2A00 FIM 0AH, 00H;
009D 2C00 FIM 0CH, 00H
009F 2E00 FIM 0EH, 00H
00A1 C0 BBL 0H
00A2 280A LADR: FIM 8, 0AH;
00A4 A4 LD 4
00A5 B1 XCH 1
00A6 50DD JMS HEXL;

00A8 A2 LD 2
00A9 B1 XCH 1
00AA 50DD JMS HEXL;

00AC A3 LD 3
00AD B1 XCH 1
00AE 50DD JMS HEXL;

00B0 C0 BBL 0H
00B1 27 DDRV: SRC 6;
00B2 E9 RDM;
00B3 2880 FIM 8, 80H
00B5 29 SRC 8;
00B6 E5 WR1
00B7 67 INC 7;
00B8 27 SRC 6
00B9 E9 RDM;
00BA 29 SRC 8
00BB E6 WR2;
00BD 67 INC 7;
00BE 75C5 ISZ 5, DATO;
00BF DF LDM 0FH;
00C0 E0 WRM;
00C1 D8 LDM 08H;
00C2 B5 XCH 5
00C3 40C7 JUN PASS
00C5 DE DATO: LDM 0EH;
00C6 E0 WRM;
00C7 2880 PASS: FIM 8, 080H;

THIRD IN RD
CLEAR KBD CHAR COUNT
PUT NEW KBD DIGIT IN 4002
RESTORE STATUS

SELECT ROM O.P. PORT 5
CLEAR SWITCH FLAGS
CLEAR KBD REGISTERS

FETCH 4002 SRC START ADD
CODE

CONVERT TO SEVEN SEG
CODE

CONVERT TO SEVEN SEG
CODE

CONVERT TO SEVEN SEG
CODE

DISPLAY DRIVER ROUTINE
LOW FOUR FROM 4002

LOW FOUR TO 4265 PORT X
BUMP NIBBLE POINTER

HIGH FOUR FROM 4002

LOW FOUR TO 4265 PORT Y
BUMP NIBBLE POINTER
INCREMENT SHIFT COUNTER
FETCH WRM CODE
BIT SET 4265 Z3 HIGH
PRESET SHIFT COUNTER

FETCH WRM CODE
BIT SET Z3 LOW
SLOW DOWN MULTIPLEX
RATE

```

INTERRUPT

If CHOMP is running and a keyboard switch is pressed, one interrupt is latched by IC10 and CHOMP responds (from the INTERRUPTS RECOGNISED zone) with a jump to box 2 (address 003H) which is called the interrupt vector.

Box 2 contains another jump to the start of the interrupt routine proper, which just happens to be elsewhere in chip zero (actually at address 066H). Before the keyboard handler routine is entered, CHOMP makes a check to see whether it is actually in PROGRAM MODE. Interrupts to RUN MODE user programs are also vectored to address 003H, so this check is essential, and is represented by box 17. If PROGRAM MODE is current, then box 18 is entered and a routine executed to read-in a single four bit hexadecimal digit from the keyboard, and store it away in a 4040 register. The keyboard routine also updates the display buffer so that each digit appears on the left hand side of the display as it is entered.

User interrupts are re-vectored to address 203H, so that the RAM resident program can define how a response is to be made. If you want to use the keyboard interrupt routine in your own program, simply carry out a JUN (Jump UNconditional) to address 066H from address 203H. Remember to use a BBS (Branch back and SRC) at the end of any "custom" interrupt routines you write!

CHOMP LISTING

Figure 6.2 is a complete listing of the CHOMP program, showing hexadecimal address data (column 1), hexadecimal instruction code data (column 2), mnemonic instruction codes (column 3) and comment lines (column 4).

The listing of Fig. 6.2 is the output of an assembler program which runs not on CHAMP, but on a much larger computer. Before anyone cries *cheat!* let me hasten to point out that CHOMP was originally written without the benefit of any such sophisticated facilities, directly in hexadecimal code. The reasons for eventually putting CHOMP into this form are simple:

- The assembler program does produce nice neat output listings which are useful for publication purposes.
- Since we are indeed saying that you do not need assembler programs when writing CHAMP software, we thought it only fair to show you what you are doing without!

When entering programs into an assembler, you have to enter columns 3 and 4 of Fig. 6.2 via a teletype terminal. From these the assembler produces columns 1 and 2 which tell you *what* hexadecimal code to enter *where* in program memory. The advantages of using an assembler program are firstly that the mnemonic instruction codes are all you have to remember, and that is fairly easy; and secondly, that instead of having to specify addresses in hexadecimal code you can use labels (i.e. names) instead. The assembler program will turn instruction mnemonics and address labels directly into hexadecimal code, and produce neat listings like the one shown here.

These sort of facilities sound very useful of course, and we would be the first to agree that with more complicated micros such as the Z80 or the 6800 they are very helpful indeed. The disadvantages are of course that you have to have lots of RAM available to store all those useful comments, and you also need a teletype or a V.D.U. The authors have assembler facilities available to them, but even so we prefer to write our 4040 programs directly in hex, with a pencil and paper: an exercise which is quite simple after a little practice!

Before leaving the subject of assemblies, let me explain a few things about the output listing shown in Fig. 6.2 which may be puzzling some readers:

- ORG and END are pseudo instructions, nothing to do with the 4040 but understood by the assembler.
- Some lines in column 2 have four hexadecimal digits. These involve two line instructions such as JUN, and will of course occupy two consecutive bytes in program memory.
- Some lines are field separators required by the assembler program.
- Notation. The assembler requires hexadecimal data to start with a decimal digit (don't ask us why!), and to be followed by an H. This means that FF hex is written 0FFH, while 2F hex is written 2FH.
- Register references can be made in a variety of ways, but we referred to them using hexadecimal, or decimal where this was equivalent.

Putting this information together, refer to Fig. 6.3 which explains how a complete assembler line is made up.

To get a CHOMP PROM from Fig. 6.2, all you have to do is step through the PROM addresses (column 1) entering the hexadecimal instruction codes from column 2. To do this you need a PROM programmer of course, and since most constructors will not have access to such a unit, arrangements have been made for the provision of a CHAMP programming service which will carry out the programming for you. Details next month.

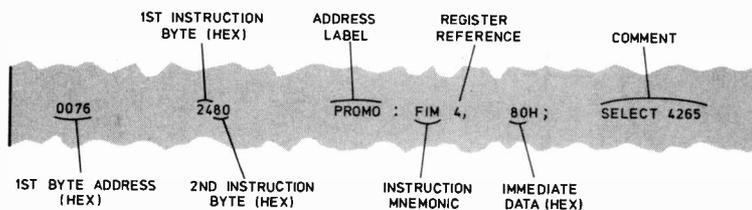


Fig. 6.3. One assembler output line and what it means

DETAILED FLOW CHARTS

No doubt many readers who felt reasonably happy with the overall flow chart in Fig. 6.1 had second thoughts when they tried to relate it to the program listing of 6.2. This is inevitable, because there is a missing link between the two, namely the detailed flow charts of each separate section of the program. Figures 6.4 to 6.8 show some of the detailed flow charts needed, but lack of space makes it impossible to reproduce all of them, so a certain amount of "unravelling" will still be necessary if any reader wishes to trace the operation of the complete program.

Let us start off with something easy, and have a look at how box 16 of Fig. 6.1 is turned into a 4040 program segment. Box 16 is a software implemented 12 bit binary counter routine which is updated each time the ENTER DATA or DUMP switches are pressed. The current count value is used during the ENTER DATA or DUMP program segments as a program memory address, and is displayed on the rightmost three display digits in hexadecimal.

Counters are implemented in 4040 software by using the ISZ (Increment and Skip if Zero) instruction which has the effect of incrementing the value of an internal four bit 4040 register by one, and jumping to a specified address if the contents of the register are not zero. If they are zero, the jump does not take place, and the next instruction in sequence is fetched. Figure 6.4 shows the implementation of the 12 bit address counter using ISZ,

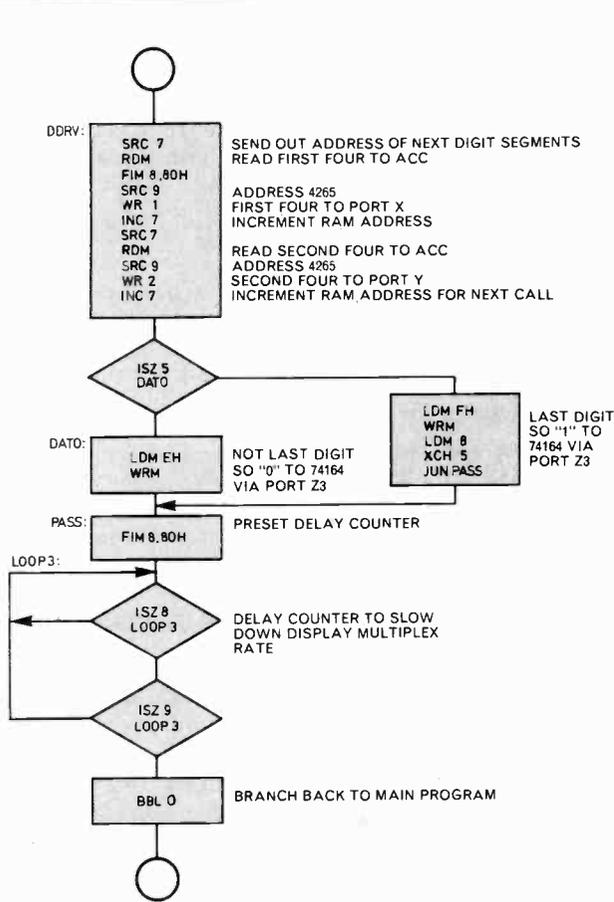


Fig. 6.5. Display driver subroutine. Refer to box 5 in CHOMP main flow chart, and address 00B1H on CHOMP program listing

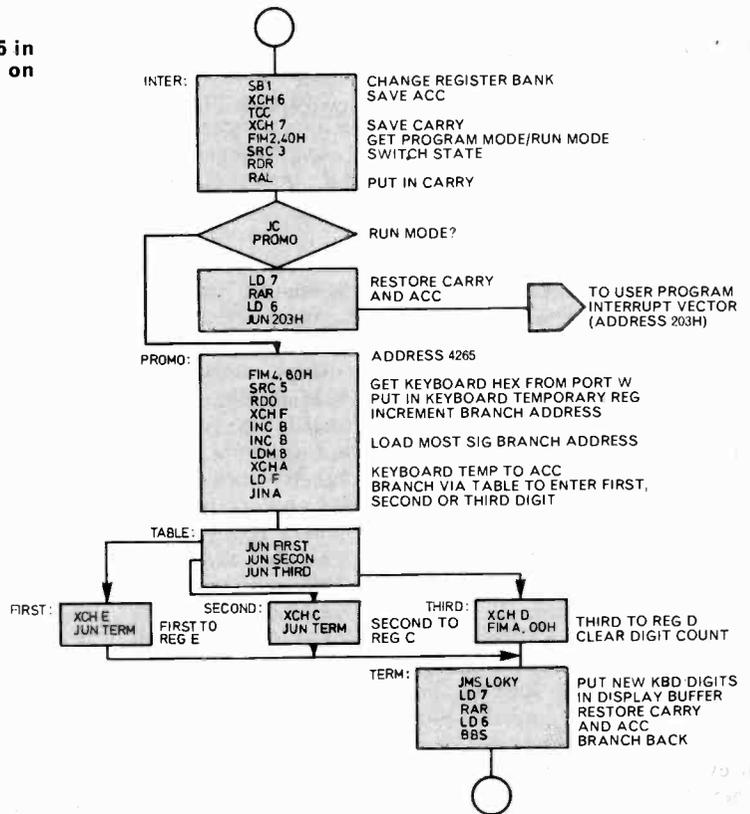


Fig. 6.6. Interrupt routine. Refer to boxes 17 and 18 in CHOMP main flow chart, and address 066H in CHOMP program listing

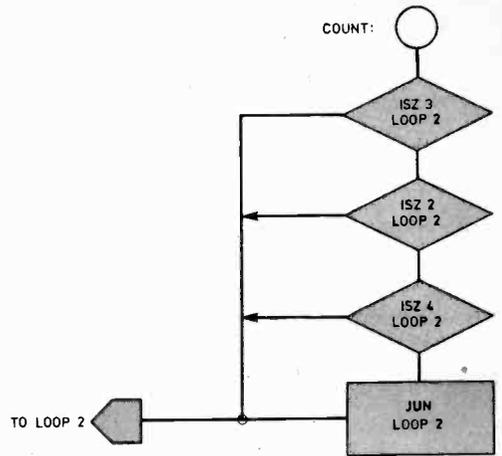


Fig. 6.4. Twelve bit address counter flow chart. Refer to box 16 in CHOMP main flow chart, and address 005EH. The CHAMP address counter should not be confused with the 4040 address counter

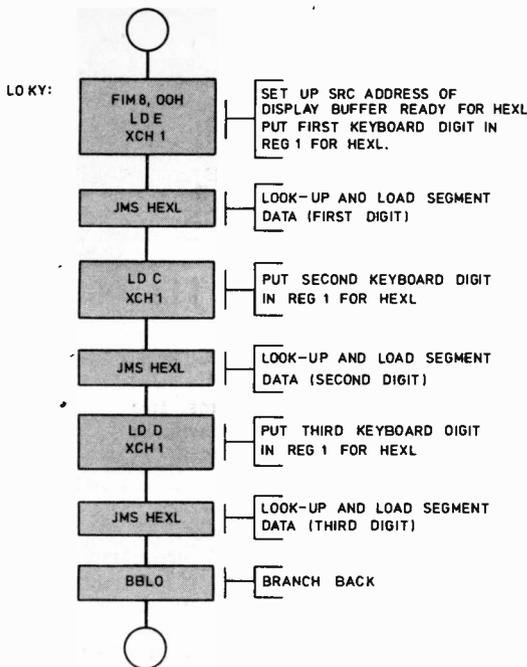


Fig. 6.7. Load keyboard subroutine. Refer to address 00CEH in CHOMP program

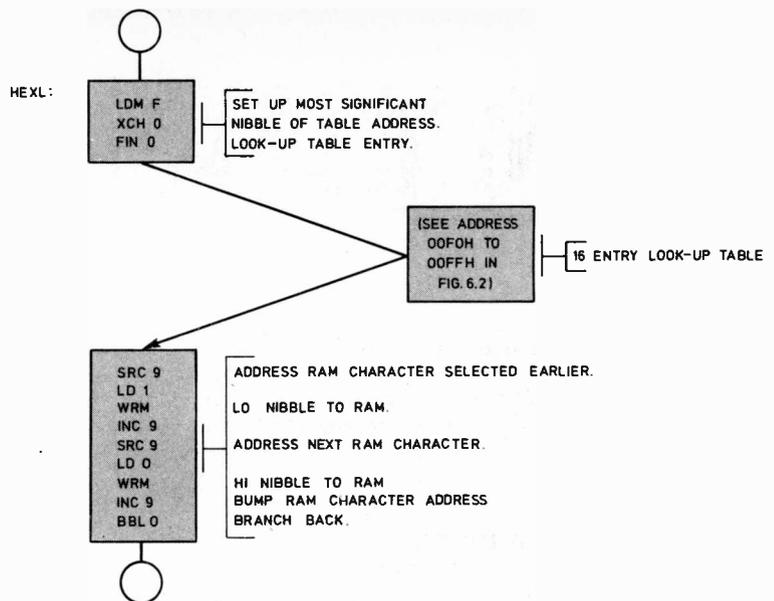


Fig. 6.8. Seven segment from hex look-up subroutine. Refer to address 00DDH in CHOMP program

the registers used being 3, 2, and 4 in that order. (The order is important because the high order address bits during an SRC instruction are taken from the lower register of a pair, and of course we use the lower eight bits of the counter as a SRC value when addressing program memory, before using RPM or WPM instructions.) The required 12 bit length of the counter is arranged by using three cascaded ISZ instructions, each with a common jump address, namely LOOP 2. You can probably see that Register 3 is incremented 16 times more often than Register 2, which itself is incremented 16 times more often than Register 4, in traditional binary counter fashion.

DISPLAY DRIVER

The subroutine DDRV is the full version of box 5 in Fig. 6.1, and its detailed flow chart is shown in Fig. 6.5.

This subroutine increments a counter (Register 7) twice each time it is called, and uses the counter contents as part of a SRC address to the data RAM display buffer (RAM chip 0, register 0). On each call it reads two four bit locations from the 4002, and sends their contents to the 4265 output ports X and Y which control the display segment lines. After doing this it increments another counter (Register 5) which it uses as a digit counter. This counter is preset to 8 hex (using LDM) when it reaches zero, and a logic one is placed on the 74164 shift register DATA INPUT via 4265 output Z3, using the WRM command. If this counter does not reach zero during a call then a logic zero is placed on the shift register data input.

You can probably see how this subroutine displays eight digits, one per call; and how it recycles to repeat the process over and over again. On seven out of eight calls it shifts a logic zero into the register, but on the eighth it generates a new "digit strobe" for the display, to replace the one which has just "dropped off the end" of the 74164.

INTERRUPT ROUTINE

Figure 6.6 shows the interrupt routine, INTER, which is boxes 17 and 18 on the overall flow chart of Fig. 6.1. The main thing of interest here is the use of a "Branch Table" accessed using the JIN (Jump Indirect) instruction to route the program flow to the correct segment depending on whether the current keyboard digit entry is the first, second, or third in sequence. Notice also that at the start of the routine the current accumulator and carry flip-flop contents are saved in registers 6 and 7 of Bank 1, to be restored at the end of the routine so that the main program flow can continue normally. A subroutine LOKY is used to enter the newly entered keyboard data into the display buffer.

The subroutine LOKY is itself shown in Fig. 6.7. It takes the contents of the three keyboard registers (E, C, and D) and converts their hexadecimal data into seven segment code using another subroutine HEXL.

HEXL itself is shown in Fig. 6.8, and as you can see it uses a FIN (Fetch Indirect) instruction to access a look-up table with sixteen entries. To convert hex to seven segment code, the hex is used as part of an indirect address so that the correct segment data can be "looked up" in the table. Table look-up is a powerful and simple technique which is very useful when converting data from one format to another. HEXL also loads the seven segment data into the 4002 RAM buffer register, at the appropriate address passed to it in registers 8 and 9 by the subroutine LOKY.

There are several other detailed flow charts required for a full understanding of CHOMP, and it would be excellent practice for CHAMP users to try and draw these up for themselves using Figs. 6.1 and 6.2 for reference. Don't be discouraged if it takes a while for the flash of inspiration to arrive, programming a microprocessor takes some getting used to, and is invariably a frustrating business at first, particularly for us "hardware people".

NEXT MONTH: Putting CHAMP to work

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus will present ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas will probably come from readers working on their own microcomputer systems, and payment will be made for any contribution featured here. This is also the place to air your views, in general, on this new technology, so let's be hearing from you!

CALCULATING ON A MICRO

SINCE microprocessors are designed as controllers rather than as computers they do not lend themselves to arithmetic work, and most instruction sets do not even include multiply and divide operations. There are two ways to add the capability of a scientific calculator to a micro. One is to add a floating-point package: a collection of programs to handle calculations involving floating-point numbers, and providing trigonometrical and logarithmic functions in addition to the arithmetic operations. The disadvantage is the extra memory required—typically 1½k.

The alternative is to add a hardware "arithmetic processing unit" which performs the calculations independently of the main micro. One such device is National Semiconductor's MM57109 "Number Cruncher Unit" or NCU. This chip offers the functions of a programmable calculator (see Table 1), a four-element stack and a memory, and floating-point arithmetic to 8-digit accuracy.

NUMBER CRUNCHER UNIT

The NCU is similar in operation to a calculator; 6-bit instructions correspond to key-presses, and these are presented to it on six input lines, I1-I6. Numbers are entered digit by digit as in a calculator.

A summary of the instructions is given in Table 1. The NCU shows that it has finished executing an instruction by pulsing its RDY output high. When RDY is high you must either send it another instruction or else put HOLD high to halt it until you are ready.

The result of a calculation is obtained by presenting the OUT instruction. The NCU then puts the digits out on DO1-DO4 at regular intervals and pulses R/W low when each digit is valid. There are some test instructions, such as TX=O, and these cause the BR output to be pulsed low if the result is true.

The NCU is not directly compatible with a microprocessor bus but fortunately all the necessary logic is provided within a single device, the Motorola MC6820 Peripheral Interface Adapter or PIA, also manufactured by MOS Technology in their 6500 series as the MCS6520. The PIA is a versatile general purpose input/output circuit whose particular mode of operation is determined by numbers loaded into its two control registers. It consists of two similar halves, A and B, each with an 8-bit I/O port PA0-PA7 (or PB0-PB7) and two control lines CA1 and CA2 (or CB1 and CB2).

In the present application the PIA is configured to operate as represented in Fig. 1: DO1-DO4 input to location 0400;

R/W and BR are latched inputs which set the top two bits of control register A at location 0401; I1-I6 are fed by latched outputs from location 0402; and RDY and HOLD are in "handshake mode" with RDY setting the top bit of control register B at location 0403. In handshake mode HOLD is taken high when RDY goes high, halting the NCU, and goes low when an instruction is written to the NCU, thus releasing the NCU to execute the instruction. This handshaking makes it unnecessary for the micro to respond immediately to the RDY pulse from the NCU.

INTERFACE

The complete interface circuit is shown in Fig. 2. The NCU is a PMOS device requiring a 9V supply (at 20mA) and to make it compatible with the microprocessor system supplies of +5V and -4V are used. The PIA side A inputs PA0-PA7 and CA2 presents one TTL load, and so pull-down resistors to the -4V rail are needed on the DO1-DO4 outputs, and BR needs a buffer transistor. The CA1 and CB1 inputs are high impedance so a pull-down resistor to 0V is needed on the R/W and RDY outputs.

The HOLD and POR (Power-On Reset) inputs to the NCU must be driven between its supply rails and so transistor

Table 1. Summary of the instructions available in the MM57109.

I ₄ -I ₁	I ₆ I ₅			
	00	01	10	11
0000	0	TJC*	INV	XEY
0001	1	TX=0*	EN	EX
0010	2	TXLT0*	TOGM	10X
0011	3	TXF*	ROLL	SQ
0100	4	TERR*	SIN(SIN ⁻¹)	SQRT
0101	5	JMP*	COS(COS ⁻¹)	LN
0110	6	OUT*	TAN(TAN ⁻¹)	LOG
0111	7	IN*	SFI	1/X
1000	8	SMDC*	PF1	YX
1001	9	IBNZ*	SF2	+(M+)
1010	DP	DBNZ*	PF2	-(M-)
1011	EE	XEM	ECLR	×(M×)
1100	CS	MS	RTD	/(M/)
1101	PI	MR	DTR	PRW1
1110	AIN	LSH	POP	PRW2
1111	HALT	RSH	MCLR	NOP

*indicates a two-word instruction.


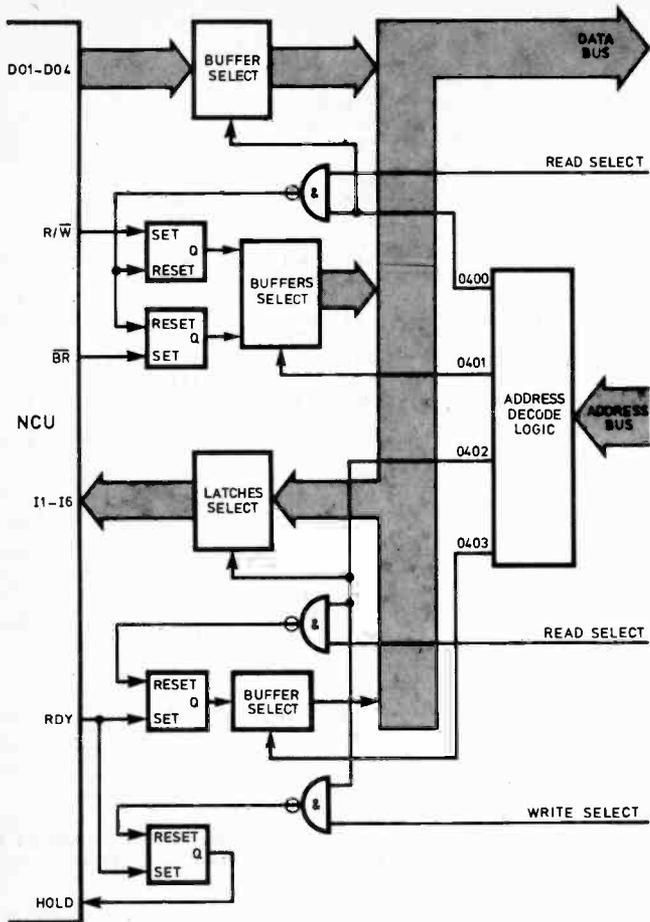


Fig. 1. Block diagram showing the logic needed to interface the Number Cruncher Unit with a micro as described. This logic is all provided in the PIA

Fig. 2. Circuit using a PIA to interface the Number Cruncher Unit with a microprocessor system such as KIM

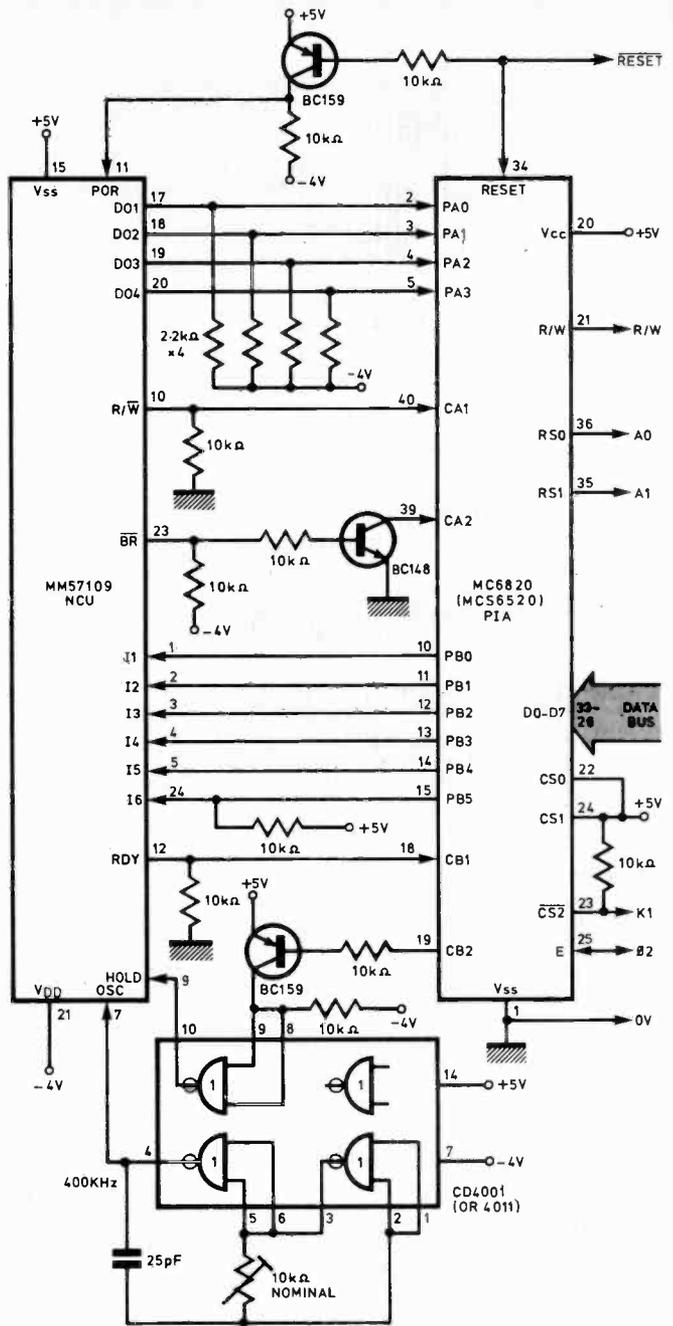

drivers are needed, and a CMOS inverter re-inverts HOLD to active high. Two other gates in the CMOS package form a simple 400kHz oscillator to drive the OSC input. Finally, a resistor is required from I6 to +5V as shown. The circuit was constructed on a plain matrix board using wire-threading (see Fig. 3) and connected to the microprocessor system by a 16-way ribbon cable.

PROGRAM

The Number Cruncher Unit circuit was used with the MOS Technology KIM development system (see review elsewhere in this issue), which is based on their 6502 micro, and the interface program is given in Fig. 4. The 6502 is similar in some respects to the 6800 and converting the program for the latter should present few problems. The 6502 has two 8-bit index registers, X and Y, and one accumulator. In the program the X register is used to point to the next

instruction to be sent to the NCU, and the Y register points to the address at which digits output by the OUT instruction are to be stored.

The program first configures the PIA, and points X to the first instruction for the NCU. It then waits in a loop testing for a signal on one of the control inputs. The BIT instruction in the 6502 loads the top two bits of the memory word—the control register A in this case—into the N and V status flags. If R/W has gone low, bit 7 will be set and a branch to the label RW is called for. If BR has gone low bit 6 will be set and a branch

to BR is required. Finally, bit 7 of control register B will be set by RDY going high, and an instruction should be sent. If not set the program continues to wait.

The NCU's test instructions and OUT, each generate two RDY pulses; i.e. they are effectively two-word instructions. The second word is used by this program as the address (in page zero) for the jump or for the output of digits, and is ignored by the NCU. The OUT instruction causes one digit to be stored per byte, although the program could be modified to pack two per byte.

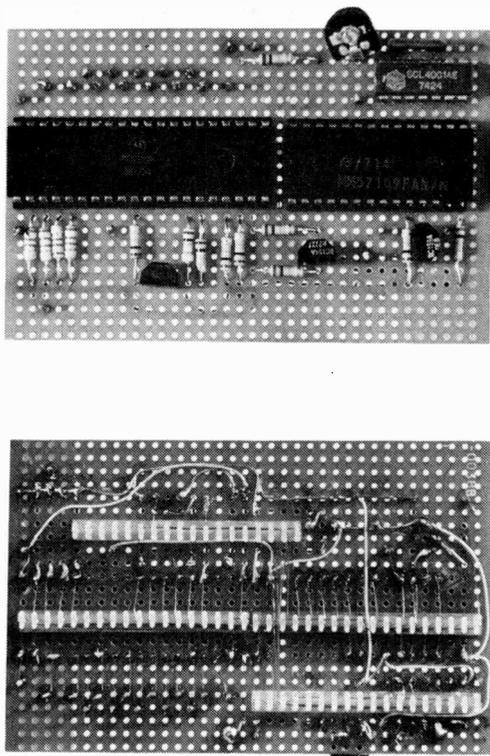


Fig. 3. The Number Cruncher Unit and interface circuits described in this article. Top and underside view

A sequence of instructions for the NCU is shown in Table 2. This finds the sum of the terms of the series $1/M^2$ for $M = 1$ to 100 and gives the result 1.6349839 (close to $\pi^2/6$, the infinite sum). The program takes 9 seconds. The NCU is slow by computer standards; the slowest instruction X^Y takes up to 1 second, and multiply takes 32 milliseconds.

One advantage of a hardware arithmetic processor over the software equivalent is that while instructions are being executed the micro is free to go away and do something else. In the program described it waits in a loop, but with a trivial modification the three inputs RDY, R/\bar{W} , and \bar{BR} could cause interrupts so that a negligible time would be taken up in servicing the NCU. Perhaps someone may be inspired to write a BASIC interpreter which uses an arithmetic processor working in parallel with the micro in this way.

GENERATING SINE WAVES

The program for generating sine waves in October's Micro-Bus used a look-up table for the values. Mr. T. Froggatt of York University has shown how this can be dispensed with:

"The problem is not to generate the sine of a given angle, but to generate the sine of an angle having just generated the sine of a nearby angle. So remembering that the rate of change of a sine wave is a cosine wave, and that the rate

of change of a cosine wave is an inverted sine wave, the following program is all we need:

Cosine = 0.0
Sine = 1.0

Loop: Output (Sine)

Cosine = Cosine - Delta x Sine
Sine = Sine + Delta x Cosine
Go to Loop.

To make this program work on an 8-bit micro the sine and cosine should each be held as two-byte items, and each time round the loop the upper byte of the sine subtracted from the cosine and the upper byte of the cosine added to the sine. This avoids the need for multi-

```

; NUMBER-CRUNCHER (MMS7109)
; INTERFACE PROGRAM
;
; PIA ADDRESSES:
AREG = $0400
ACON = $0401
BREG = $0402
BCON = $0403
;
0000          *=$0200
0200 A9 14          LDA #$04          CONFIGURE PIA:
0202 8D 01 04      STA ACON          CA1 & CA2 INPUTS,
0205 A9 FF          LDA #$FF
0207 8D 02 04      STA BREG          PB0 - PB7 OUTPUTS,
020A A9 26          LDA #$26
020C 8D 03 04      STA BCON          B HANDSHAKE MODE.
020F A2 00          LDX #0          FIRST INSTRUCTION
0211 2C 01 04      WAIT BIT ACON      GET BITS 6 & 7
0214 30 17          BMI RW          IRQA1 SET?
0216 70 1F          BVS BR          IRQA2 SET?
0218 AD 03 04      LDA BCON
021B 10 F4          BPL WAIT          IRQB1 CLEAR?
021D AD 02 04      LDA BREG          NO - CLEAR IRQB1
0220 E4 00          LDY 0,X          LOAD INSTRUCTION
0222 EB            INX              POINT TO NEXT
0223 8C 02 04      STY BREG          SEND TO NCU
0226 C0 0F          CFY #$0F        HALT INSTRUCTION
0228 D0 E7          BNE WAIT
022A 4C 4F 1C      JMP MAIN          RETURN TO MONITOR
;
; READ AND STORE DIGITS
022D AD 00 04      RW LDA AREG          CLEARS IRQA1 TOO
0230 99 00 00      STA 0,Y          STORE DIGIT
0233 C8            INY
0234 4C 11 02      JMP WAIT
;
; BRANCH INSTRUCTION
0237 98            BR TYA          GET ADDRESS
0238 AA            TAX              POINT X TO IT
0239 AD 00 04      LDA AREG          CLEAR IRQA2
023C 4C 11 02      JMP WAIT

```

Fig. 4. Complete program for the 6502 micro which sends a sequence of instructions to the Number Cruncher Unit and stores the answers received back into memory

plication and effectively fixes Delta as $1/256$."

The period of the sine wave produced is about $2\pi/\text{Delta}$ iterations of the loop. Mr. Froggatt described a program he has written which uses this method of generating a sine wave to sing Christmas carols, using a table to give the value of Delta for each note.

ADDENDUM

In December's Micro-Bus the second Chess Challenger game contained an error. The fourth move should have read:
4. 7a-6c 3h-2g

Table 2. Example of a sequence of instructions for the Number Cruncher Unit. This calculates the sum of the first 100 terms of the series $1/M^2$.

Address	Code	Mnemonic	Comments
00	3F	NOP	First 3 instructions are
01	3F	NOP	ignored by the NCU after
02	3F	NOP	a Power-on Reset
03	01	'1'	Digit input
04	0B	EE	Enter exponent
05	02	'2'	X = 100; push stack
06	1C	MS	Store X in memory
07	00	'0'	X = 0; push stack
08	1D	MR	Recall memory to stack
09	33	SQ	X = X ²
0A	37	1/X	X = 1/X
0B	39	+	X = X + Y
0C	1A	DBNZ	Decrement memory and go
0D	08		to 08 if non-zero
0E	16	OUT	Output X starting at
0F	40		40 (i.e. 0040)
10	0F	HALT	Return to monitor



PART 2

GENERATOR

N.A. COOKE

THIS month the second and final part will deal with constructional details and setting up procedures.

CONSTRUCTION

Construction is very straightforward as all components are mounted on two p.c.b.s with the exception of the three potentiometers, the switches, fuse holder, socket and indicators which are mounted on either the front or back panels.

Figs. 10 and 11 show the etching details and component layout of the main board.

It is advisable when assembling the p.c.b.s to fit the components of smallest dimensions first. Bending their leads to an angle of 45 degrees after insertion will prevent them from falling out when the board is turned over for soldering. Figs. 12 and 13 gives p.s.u. board assembly details.

Care should be taken to make sure diodes and radial lead electrolytic capacitors are fitted the right way round. With the general purpose 1N4148 the larger width band indicates the positive end of the diode. Positive or negative markings will be printed on the electrolytic capacitors.

The polyester radial lead capacitors should fit the p.c.b. exactly. They are very fragile and the leads will break off if the capacitor is forced into position.

If lead adjustment is necessary this should be carried out with the use of a small pair of pliers while firmly gripping each end of the capacitor.

SOCKETS

It is advisable to use sockets to fit the four CMOS i.c.s. These devices are supplied in a conductive foam or wrapped in tin foil and should not be removed until immediately prior to insertion. Although the devices are internally protected they are still vulnerable to high static charges and it is worth earthing oneself when handling them.

Another point to remember is that they should not be inserted or removed from their sockets while the power is switched on.

The p.c.b. should be visually checked upon completion of assembly to ensure that components are in their correct positions and the track side inspected for any dry joints or solder bridging. Figs. 14 and 15 show the positions of the components mounted to the front and back panels.

SWITCH MOUNTING

The subminiature switches used on the control panel must be tightened from the back of the panel otherwise severe scratching of the anodised finish and the legend will result. The potentiometer spindles should be cut to approximately $\frac{1}{16}$ in before fitting to the panel. The three knots used have a very fine taper on the internal $\frac{1}{16}$ in fixing bore and once pushed on and rotated into place may be difficult to remove.

The DIN socket with the 3.5mm jack socket, fuse holder and grommet are mounted to the back panel as indicated in Fig. 15.

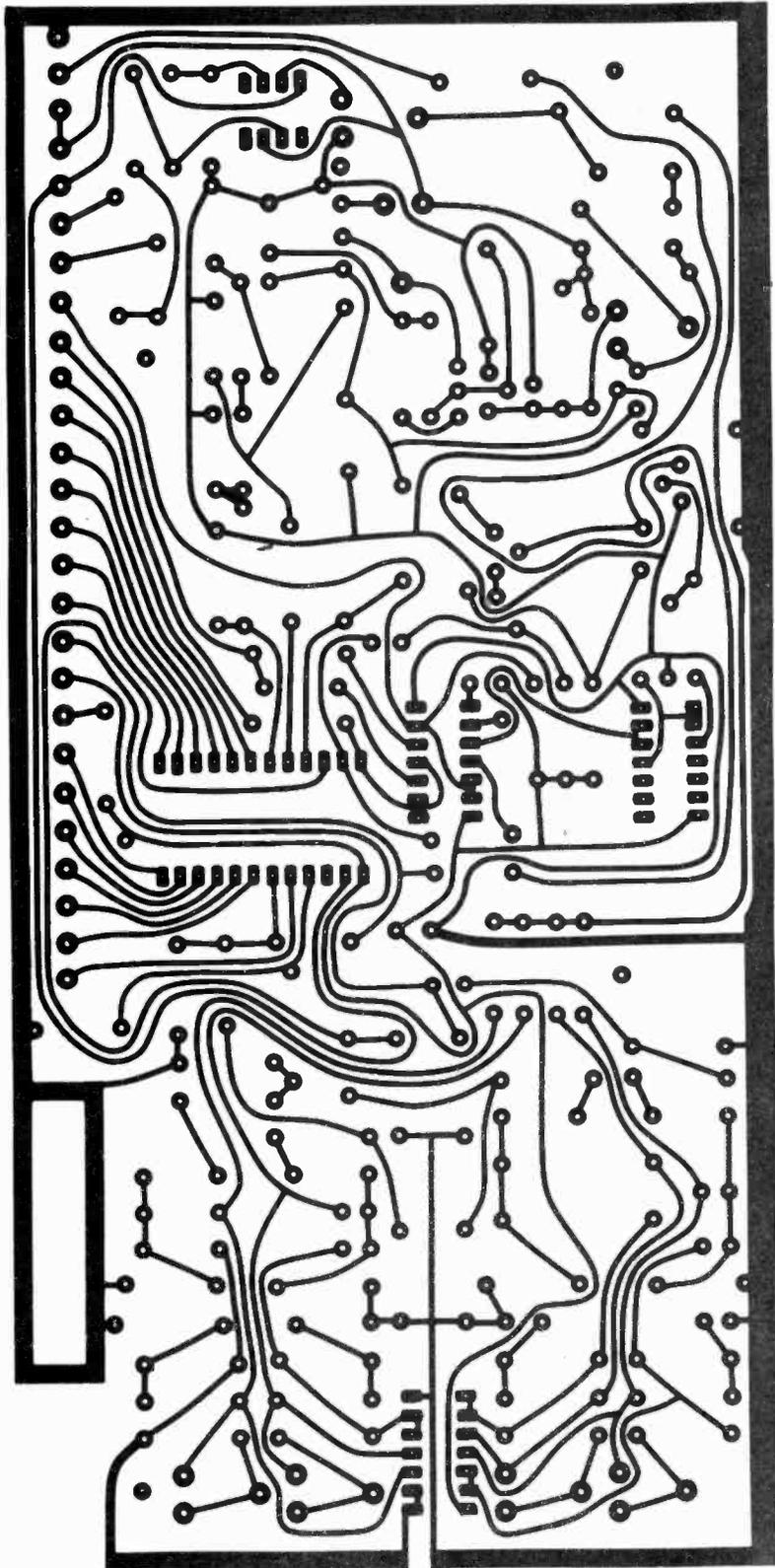


Fig. 10. Printed circuit layout of main board


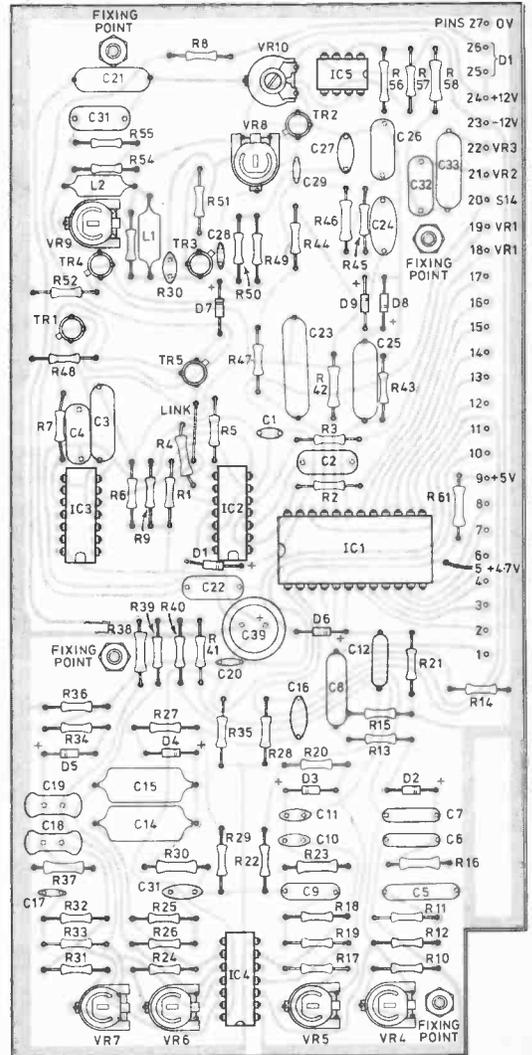


Fig. 11. Component layout on main board

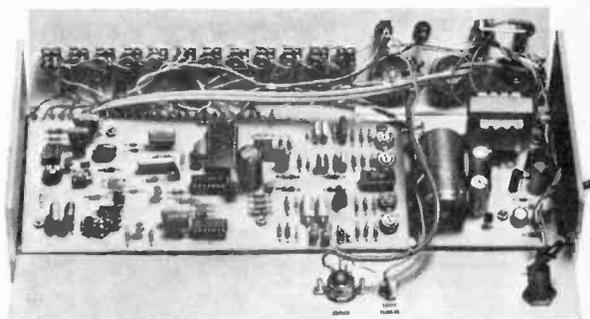

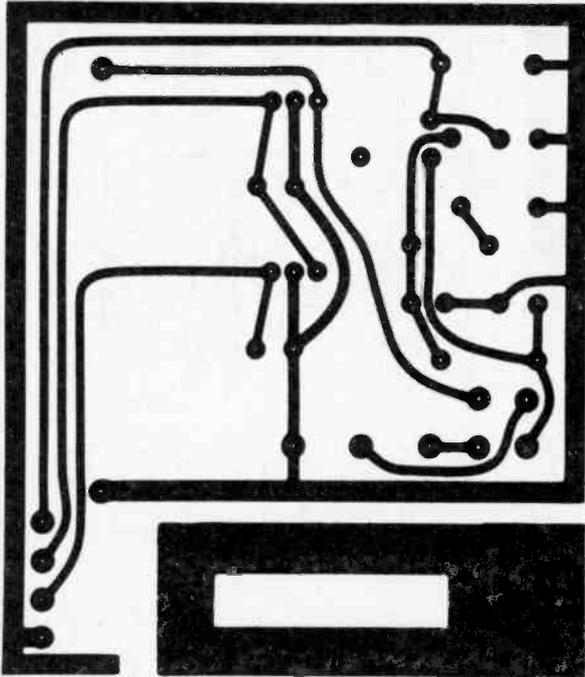


Fig. 12. Power supply board etching details


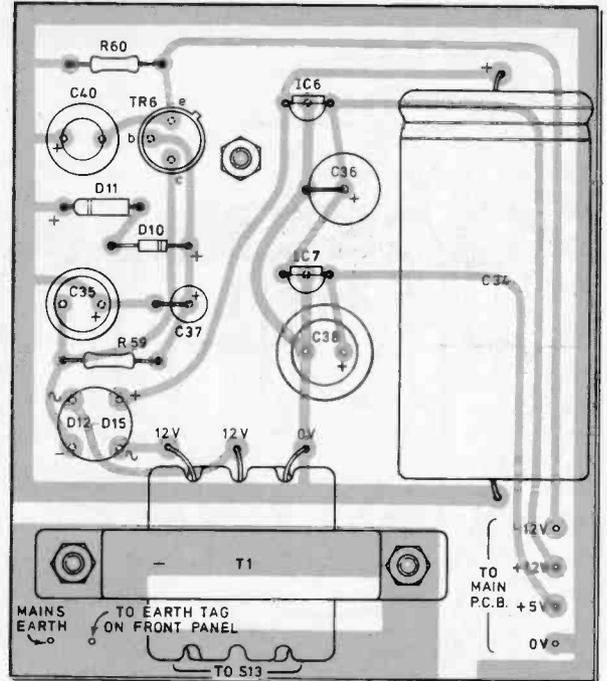


Fig. 13. Component layout of power supply board

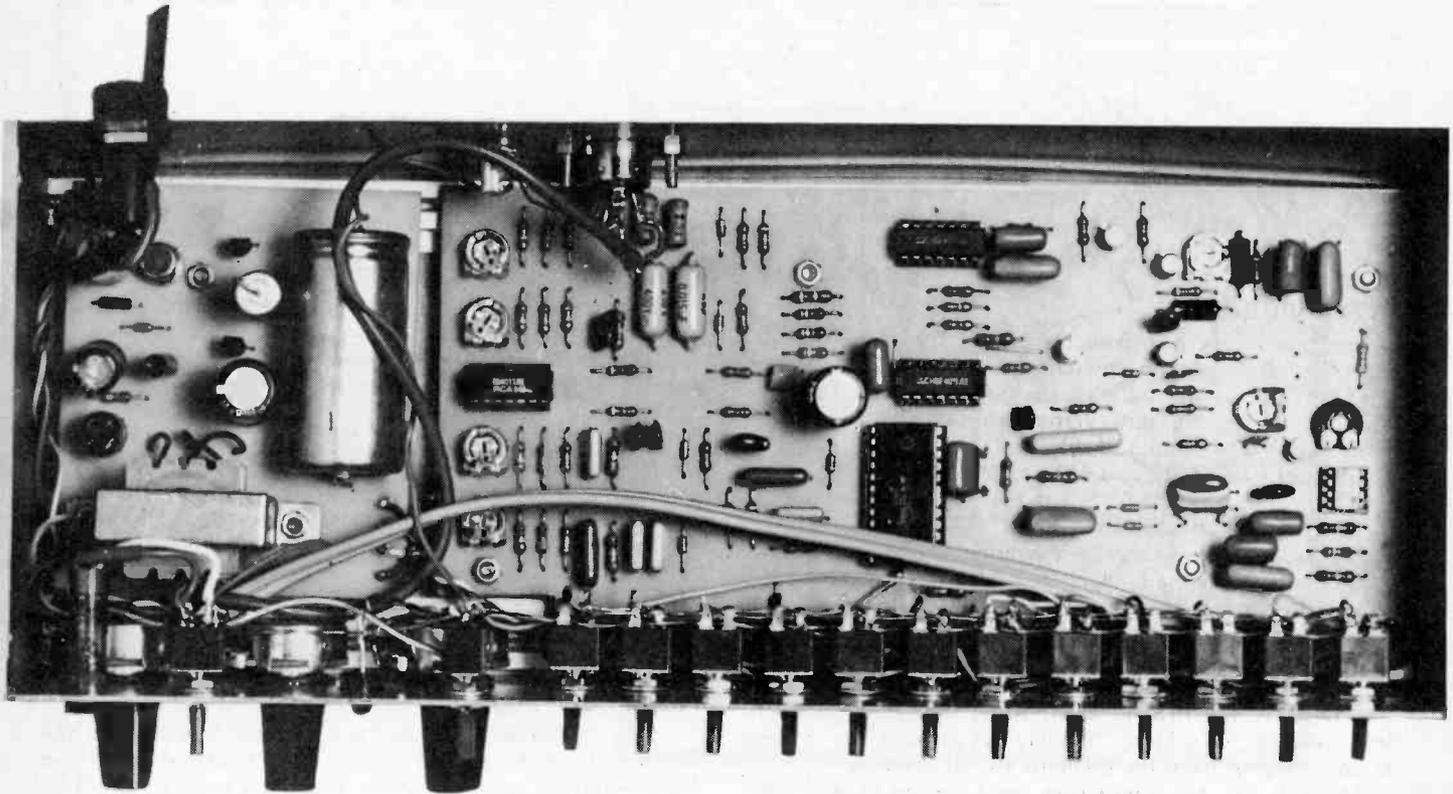

Plan view of Generator interior

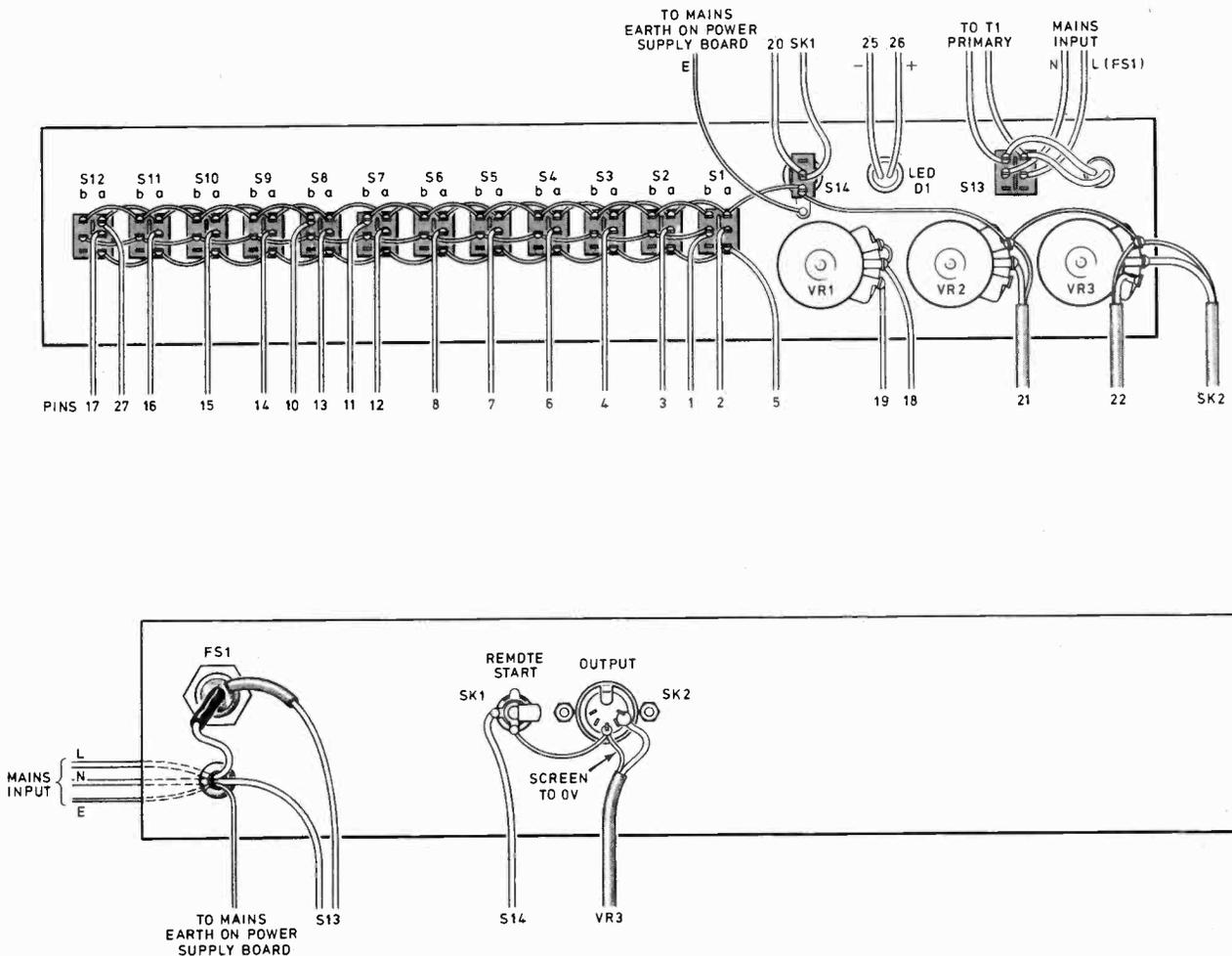


Fig. 15. Back panel wiring

INTERWIRING

The interwiring is reasonably straightforward with the exception of the selection switch wiring.

Fig. 14 shows the back of the control panel. The five common connecting rails across the switches should be fitted first. The common 0V rail not only links the switches but also VR2 and VR3 and the stop/start switch. It is suggested as this 0V rail is the most complicated of the five that this should be fitted first.

For each of the five rails a length of 22 s.w.g. tinned copper wire should be used.

Start at one end of the line of switches and terminate the wire by wrapping and soldering it into position. The wire is then wrapped over a screwdriver which spaces the bridging link to the next switch. It is not necessary to wrap the wire around each switch tag however—each joint should be soldered quickly to prevent the wiring from springing from the previous switch contacts.

The rest of this interwiring must be made with the front panel, p.c.b. and back panel lying horizontally. The front and back panels must be arranged either side of the p.c.b.

The row of Veropins should be nearest the front panel and two gaps of 30mm each should be left between the p.c.b. and front and back panel. If this gap is not left all the wires will be too short when the assembly is fitted into the case framework.

The connections from the common rails and individual switches can now be made to the p.c.b. It is worthwhile to check every joint after making it as it is possible to forget a connection and be left with one extra Veropin at the end!

SAFETY FIRST

Whenever a metal case is used to house mains operated equipment, it is advisable to take extra care with the mains wiring connections. Each joint should be inspected to ensure a good mechanical and soldering bond.

It is advisable to scrape away a small section of the anodised finish on the internal surfaces of the four aluminium extrusions and the front and back panels. This should be done to ensure a good earth contact throughout the case, as unfortunately the anodised surfaces act as an insulator.

FINAL CHECK

Apply mains voltage (without any i.c.s in place). The neon should light. Check the voltage across pin 1 (positive) and 2 (negative) of the M253AA socket. The reading should be $17 \pm 1V$. Also check that the outputs from the power supply board are +12, +5 and -12V.

If the voltages check out, again isolate the supply and carefully fit the i.c.s taking the necessary precautions described earlier with the four CMOS devices.

Check that all the chips are fitted in their correct positions, but do not turn on until you have completed the initial setting up procedures.

INITIAL SETTING UP

Set all the internal preset controls as follows:

Identification	Adjustment	Control Description
VR4	Midway	Oscillator damping
VR5	Midway	Oscillator damping
VR6	Midway	Oscillator damping
VR7	Midway	Oscillator damping
VR8	Fully anti-clockwise	white noise generation level
VR9	Midway	Balance of noise to Snare Drum simulators
VR10	Midway	Output attenuation

Set the front panel controls as follows:

VR1	Midway	Tempo
VR2	Fully clockwise	Tone
VR3	Fully anti-clockwise	Volume

S13
S3 to S14

Start
Bossa Nova on

Stop/Start Switch
"Rhythm Select"

CONNECT UP

Connect the DIN output to the radio socket of an external amplifier and turn on.

The downbeat lamp should light and by advancing VR3 a rhythmic beat should be heard. The tempo control should be adjusted to suit the rhythm. Continuous oscillations may be heard as well and will be corrected in the final setting procedure.


FINAL SETTING UP

With the unit operating the four presets VR4-VR7 should be adjusted just to prevent continuous oscillation. VR9 should be set to give a realistic balance between the white noise simulators and the Snare Drum. VR8 may be backed off from full anticlockwise slightly to reduce harshness of the white noise effect if necessary.

In combination with the adjustment of VR8, switch to the March rhythm and adjust VR9 to achieve the best setting for a realistic Snare Drum sound and correct Cymbals level.

VR10 controlling the output attenuation should be adjusted to suit the amplifier being used. Re-adjustment, using the prescribed procedure may be repeated once or twice to obtain the most balanced and realistic sound. ★

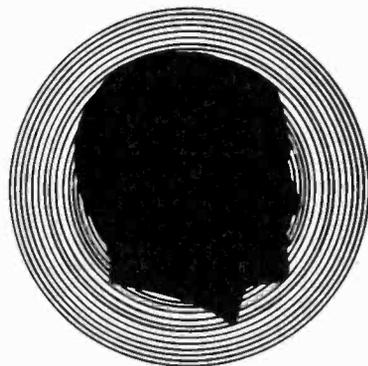NOTE: In the Components List R61 is 33Ω , VR2— $25k\Omega$ logarithmic, C31— $0.1\mu F$ polyrad and ICI—M253AA. *Watford Electronics, 33-35 Cardiff Road, Watford, Herts.* can supply a complete kit of parts for £49.95 including VAT & P. & P. £1.25 (insured).




INGENUITY UNLIMITED

It is often useful to know if your telephone has been ringing while you have been away. This circuit will light an l.e.d. when it detects the magnetic field of a telephone bell. The l.e.d. remains on until it is later reset by the telephone user.

A TELEPHONE MEMORY

Fig. 1

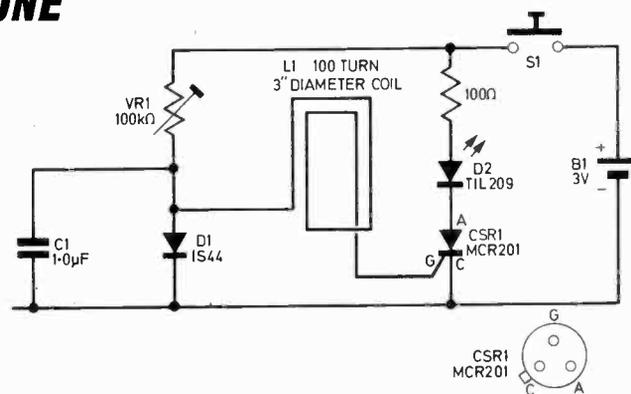


In Fig. 1 a 100-turn 3in. diameter coil of 30 s.w.g. enamelled copper wire is positioned on the underside of the telephone in a position (approximately dead centre where the bell magnetic field can be picked up. Voltage induced in the coil appears across the gate/cathode of thyristor MCR201 which is already biased close to conduction by the voltage across diode D1. This additional voltage, caused by the bell, triggers the thyristor and lights the l.e.d.

To reset the circuit a normally-closed push button is pressed to temporarily interrupt the supply to the circuit.

As the value of VR1 is reduced, a point will be reached where the thyristor will spontaneously trigger. The value of VR1 should be increased a small amount from this point to set the circuit at its most sensitive.

This circuit draws approximately $60\mu A$ when the l.e.d. is not lit, and 7mA when it is, therefore dry batteries will give quite a good life.

A. Russell,
Whinmoor,
Leeds

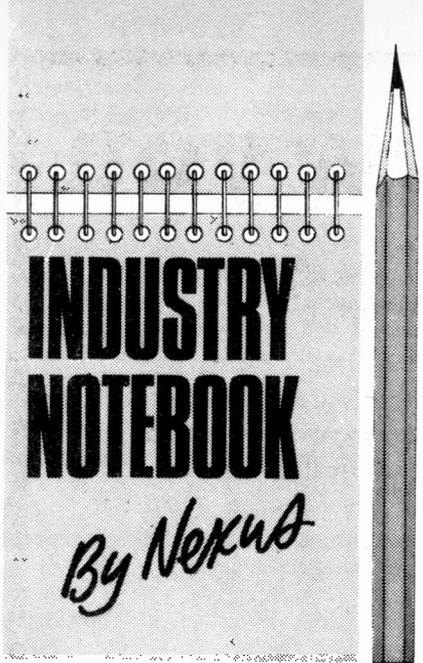

INDUSTRY NOTEBOOK

By Nexus

MARINE ELECTRONICS

The slump in the shipping industry and in particular in the fishing industry has gravely affected a few companies, notably Redifon now phasing out their Cwmbran, South Wales, manufacturing plant with 250 redundancies. But some companies in the marine business continue to prosper. Prime example is Decca Radar, currently selling over 5,000 marine radars a year. Starting from nothing in 1950 the grand total is 75,000 radars sold, 15,000 in the last three years of difficult trading conditions.

Another boom sector is in the North Sea drilling rigs where the chief beneficiary is Marconi with multi-channel over-the-horizon troposcatter systems coupled into the UK telephone network. The investment by the Post Office in such systems is £5 million.

Finally, there is the VLF global navigation system code-named Omega which will get its final validation for accuracy in 1982, the aim being one nautical mile accuracy in daylight and two miles at night. The market for ship-borne Omega as a master navigation system is already established but is clearly capable of enormous growth.

BIGGEST DATA BANK

Disk storage of 2,800 million bytes, all of it on-line and said to be equivalent of 10,000 books of novel length, is now available at Aberdeen University through its recently commissioned Honeywell 66/60 computer. University departments can interrogate the system through 100 remote terminals, most of them VDUs.

Of topical interest is the work of the Department of Arts and Social Science using the computer to analyse trade union bargaining and wage rounds.

How sensible it would be to feed in workers' demands on the one hand and employer's ability to pay on the other, the length of time a strike could last without the employer (or the country) collapsing, or workers starving, overall cash loss to the country (there is never a gain), damage to trade both in short and long term etc., and let the computer work out the compromise solution which is invariably arrived at. If every dispute were to be solved by computer there would be no need for strikes. I doubt if the Aberdeen researchers are thinking along these lines. I offer the idea free of charge but with little hope of its adoption. Far too many trade union officials and industrial relations officers have a vested interest in interminable argument to accept the impartial and practically instantaneous solution that the computer can and should be allowed to provide. And where could such people, if made redundant, find alternative employment?

INVENTOR'S CHANCE

Odd phenomenon of 1977 was the National Research Development Corporation's inability to attract new joint venture schemes to exploit inventions and ideas. With a pre-tax surplus of over £10 million for the year 1976-77, up from £3.7 million the previous year, NRDC has plenty of cash to back new projects but few takers. NRDC holds some 5,000 patents in the UK and overseas and is currently co-operating with nearly 1,000 companies.

Should 1978 prove to be a vintage year for inventions, NRDC has the cash but any schemes put forward needs to have originality and the prospect of profitable exploitation in the market place. Perpetual motion machines are not encouraged. In its life-time, NRDC has examined schemes from over 28,000 companies and only 7,000 have qualified for a second look.

PLESSEY STAYS FIRM

Plessey, hard hit by the Post Office cut-backs in orders, shows great underlying strength. Pre-tax profits for the quarter to last September totalled £9.6 million against £8.1 million on world sales nine per cent up at £149.7 million. Exports over a half year have increased by 51 per cent.

The weakness of being over-dependent on a single large customer, in this case the British Post Office, is illustrated by the labour force of 20,000 (slimmed down from 23,600) on telecommunications which contributed only 30 per cent of sales in the last half year. Contrast this with the 8,800 people in Plessey Electronic Systems who accounted for 37 per cent of sales and 40 per cent of the pre-tax profit.

The big breakthrough for Plessey may come next April when the International Civil Aviation Organisation (ICAO) is meeting in Montreal to decide on the next generation of instrument landing systems for airports. Plessey's doppler microwave system has a good chance of succeeding in the competition and if it does it will create work for years ahead and good profits from manufacturing and licence agreements.

Meantime, an example of Plessey's advanced technology is the recently announced PR2250 professional communications receiver which includes a microprocessor for programmed surveillance of spot frequencies and a memory module which allows instant tuning to 16 pre-set frequencies at the touch of a button. Real state-of-the-art, but it also costs real money, about £6,500 each says Plessey but you might be able to negotiate a quantity discount!

RACAL EXPANDS

It's still action all the way in the Racal Electronics Group with expansion at home and overseas. Dana Laboratories in Irvine, California is the latest acquisition together with the Dana sales affiliates in the UK and France. The Dana range of digital instruments is now added to the complementary range from Racal Instruments Ltd and the combined instrument operations will soon be trading with the new name of Racal-Dana Instruments Ltd under the overall direction of John Ceresa who heads up Racal Instruments in the UK.


The new acquisition immediately bumps up Racal turnover in instruments by £5 million and the combined Racal-Dana is targeted for £13.8 million turnover in its first full year of operation. So Racal-Dana is now pressing hard on the heels of Marconi Instruments, at present the largest of the British-owned companies in electronic test and measuring instruments.

British Physical Laboratories, the specialist analogue panel meter company in the Racal Group has now established West Germany as its largest single export market. Among recent successes is a five-year contract for the supply of meters to Robert Bosch GmbH. Also in Germany, Racal-Redac the CAD company has opened a new sales office at Bensberg near Cologne, supplementing the Munich office which was opened in January 1977.

Of course anyone can build turnover by buying companies or selling products at give-away prices. What counts in the end is profitability and here Racal cannot be faulted, having achieved the number one spot in the profitability league table of 200 British companies published by "Management Today", topping even ICI and Shell.

LOOK! Here's how you master electronics




... the practical way

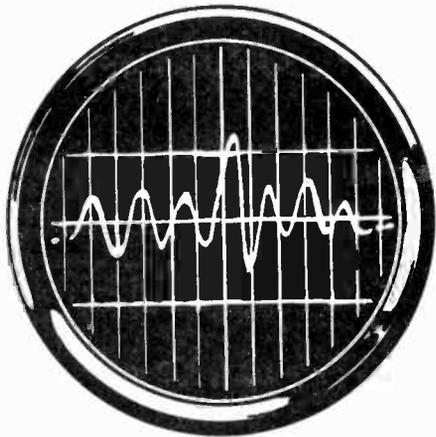

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

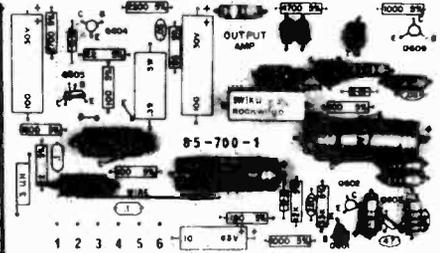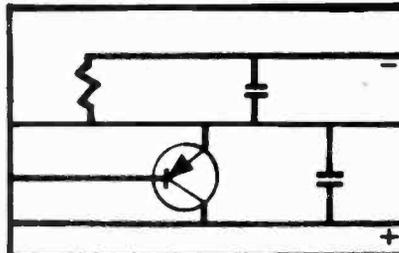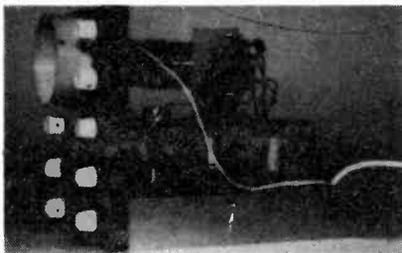All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2 Read, draw and understand circuit diagrams

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

FREE GIFT

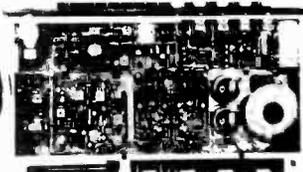

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME


ADDRESS

Block caps please

Free!

PEB2

SUPER SOUND 13 HI-FI MONO AMPLIFIER

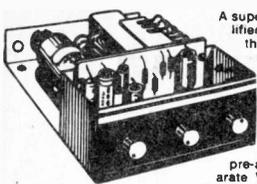

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz ± 3 db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal. Suitable for Sensitivity approx 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. AC 200/250V. PRICE £15.00 P. & P. £1.20.

8-15 ohm speakers. Input for ceramic or crystal. Suitable for Sensitivity approx 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. AC 200/250V. PRICE £15.00 P. & P. £1.20.

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Oiac, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1 5mV into 47k. Input 2 5mV into 47k (suitable for use with mic. or guitar etc.). Input 3 100mV into 1 meg. suitable for gram. tuner. or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12in. wide x 5in high x 7in deep. Special introductory price £28.00 + £2.50 carriage and packing.



Mullard LP1159 RF-IF module 470 kHz £2.25 + P. & P. 20p Full specification and connection details supplied. Pye VHF FM Tuner Head covering 88-108 MHz. 10.7 MHz 1 F output 7.8V - earth. Supplied pre-aligned, with full circuit diagram with precision-gear F.M. gang and 323PF A.M. Tuning gang only £3.15 + P. & P. 35p. STILL AVAILABLE HA34 3 Valve Audio Amp. 4 1/2w o/p. Ready built and tested £6.50 + £1.40 P. & P. Also HSL 'Four' Amp. Similar to above but in kit form. £8.00 + £1.40 P. & P.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State F.M. A.M. Stereo Tuner. Covering M.W. A.M. 540-1605kHz V.H.F. F.M. 88-108MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator. Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV R.M.S. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 6 1/2in wide x 4in high x 9 1/2in deep approx. Limited number only at £28.00 + £1.50 P. & P.

Push Button Switch bank. 8 buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button plus 3 Dip C/O. Overall size 5in x 2 1/2in x 1in. Supplied complete with chrome finished switch buttons 2 for £1.60 + 20p P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished mono amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + S.A.E. (Free with parts). All parts sold separately. ONLY £13.50 P. & P. £1.40. Also available ready built and tested £18.00 P. & P. £1.40.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2in x 1 1/4in x 1 1/4in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffles. Send S.A.E. for full details. Only £8.40 each + P. & P. (one 90p, two £1.90). Now available in either 8in round version or 4 1/2 x 8 1/2in rectangular. 10 watts R.M.S. 60Hz-20kHz £5.25 + P. & P. (one 65p, two 75p.).

SPECIAL OFFER. 6in long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for HI FI. £3.95 + 75p P. & P.

2in SLIP CONE HF TWEETER 4 ohm, £3.50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 ohm Ome Tweeter. 1in voice coil. Magnet size 3in dia. Suitable for use in up to 50 watt systems. £4.50 each + 60p P. & P.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts R.M.S. per channel into 5 ohms. Frequency response ± 3 dB 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth: ± 3 dB 12-15,000Hz. Bass boost approx. to ± 12 dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A overall size 12in wide x 8in deep x 2 1/2in high.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £13.50 P. & P. 80p (Magnetic input components 33p extra)

POWER PACK KIT £5.50 P. & P. 95p

CABINET £5.50 P. & P. 95p

SPECIAL OFFER—only £23.75 if all 3 items ordered at one time plus £1.25 P. & P. Full after sales service. Also available ready built and tested £31.25 P. & P. £1.50

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec. play socket are mounted on the printed circuit panel. Size approx. 9in x 2 1/2in x 1in max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £9.00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

STEREO DECODER

SIZE 2" x 3" x 1" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 9385

A few minutes from South Wimbledon Tube Station


(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

AITKEN BROS.

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729

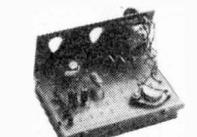

S-DEC

This, the most popular Board is designed solely for the use of discrete components and is particularly useful for basic educational purposes. (No. of Contacts: 70) PRICE £2.43 inc. VAT.



T-DEC

This Board allows 2 TO5 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC application where considerable numbers of discrete components may be required. (No. of Contacts: 208) PRICE £4.30 inc. VAT.



U-DEC 'A'

The μ -Dec 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used but will accommodate discrete components with equal facility. (No. of Contacts: 208) PRICE £4.31 inc. VAT.



U-DEC 'B'

The μ -Dec 'B' is for similar uses as μ -DEC 'A', but has two 16 lead IC sockets as part of the Board. (No. of Contacts: 208) PRICE £7.55 inc. VAT.



PANEL METERS

Dims: 60mm x 45mm. 50 μ amp, 100 μ amp, 500 μ amp, 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25v dc, 30v dc, 50v ac, 300v ac, "S", "VU", 50-0-50 μ A, 100-0-100 μ A, 500-0-500 μ A. PRICE £4.13 inc. VAT.

POTS* CAPACITORS, BOXES, INST. CASES, DIN PLUGS, RESISTORS, ETC., ALWAYS IN STOCK. POSTAGE AND PACKING 20p EXTRA. 1978 CAT. AVAILABLE JAN. PLEASE SEND 40p.

TRAMPUS



A SEMICONDUCTOR POWER HOUSE. TRAMPUS ELECTRONICS LTD., 58-80 GROVE ROAD, WINDSOR, BERKS SL4 1HS. TELEPHONE WINDSOR (07533) 54252. CALLERS WELCOME MON-SAT 9AM-5PM. Fast service, on ex stock product, normally 24 hour turn around. Quality devices to manufacturers specifications. Barclay Card & Access by post or telephone. £5 minimum. Send C.W.O. Add 20p Post and Packing plus 8% VAT to items marked*. 12% VAT to unmarked items. No minimum order charge for cheque or postal orders. Government Depts, Schools, N.M.A. £5 min. order. Free catalogue sale list. Send SAE. Money back if not satisfied. (Prices may change.)

IC's	All price each	TRANSISTORS	DIL SPEC PAKS £1
555 DIL 8 Timer	34p	BC107, 108	PAK A: 10 x Red LED £1*
723 Regulator	68p	BC109	PAK B: 4 x 741 DIL 8 £1*
741 DIL 8 pin	25p	BC107, 108, 109 B	PAK C: 3 x 2N3055 £1*
741 DIL14/TO99	38p	BC108 or 109 C	PAK H: 6 x 2N3819 £1*
747 Dual 741	69p	BC147/8/9	PAK K: 4 x 1N814 £1*
748 DIL 14 pin	29p	BC167/8/9	PAK N: 25 x OA81/91 £1
748 DIL 8 pin	49p	BC177/8/9	PAK T: 4 x LM301 £1*
7805 plastic or TO3	£1	BC182/3/4 A or L	PAK W: 20 x Electrolytics £1*
7812 or 15 A	£1.50*	BC212/3/4 A or L	MORE PAKS IN LISTS.
78013 or 78023	£1.49	BCY70/71/72	CAPACITORS: Ceramic 5p
8038 Sig. Gen.	£5*	BD131 or 132 each	Electrolytic 1v-200v 7p
AY51224 Clock	£2.25*	BFY 50, 51 or 52	HEATSINKS TO18/TO5 5p*
LM301 DIL 14	29p	MJ2955 (PNP)	TO3 Small 29p*
LM301 DIL 8	59p	MJE2955	Big 89p*
LM309K TO3, 5V	£1*	MJE 3055	DIL SOCKETS
LM382 (LM381)	£2	ORP 12 plastic	Low Profile 8 pin 12p*
LM380/60745	89	TIP29, 30, 31, 32C	14 or 16 pin 15p*
LM3130/CA3130	95p*	TIP41 or 42A	VERO All 0.1 in. stocked
LM3900	75p	TIP41C or 42C	2 1/2 x 3 1/2 42p*
MC1310 MPX DR	75p	TIP2955	3 1/2 x 5 56p*
NE555 Timer	34p	TIP3055	3 1/2 x 17 22.50
NE555 2 x 555	£1*	T1843 or 2N2846	2 1/2 x 5 50p*
TBA 810 or 820	£1	2N2904 & 2905	DIL Board 6" x 4" £2.44*
LEDs 1/2" x 2" dia.		2N2922 1G	POTS 25p PRESETS 2p
Red no clip	11p*	2N3053	RESISTORS 2p
2" or 208 & clip	19p*	2N3055 115W	CMOS: Range in Lists
Colour LEDs all	19p*	2N3442/472 120V	4001 or 2 23p*
NEW 6x6z LED Cover Clip	10p*	2N3819e & 23e	4009/10 59p*
		2N3820 FT	4011 20p* 4049/89 23p*
		2N5457 low noise	TTL 7400N SERIES
DISPLAYS (Red LED)		INS BUSH SETS	7400 14p* 7485/8610p*
0.3" DL704/2	59p*	MA CHING	7401 10p* 7490 49p*
0.3" DL707/2	£1*	DIVIDER/OA81/91	7404/5 20p* 7491/2 50p*
0.6" DL747/2 No DP	£1*	IN814 & 4148 all	7408/1017p* 7493/5 50p*
TGS 308 GAS D	£5*	IN4001 5p* 4004 7p*	7413 39p* 74107 59p*
390PF Tuning Cap	£1	BRIDGE 1A 50V	7417/2025p* 74121 33p*
Bleeder RS type	£1.48*	BZ788 400mW	7430 15p* 74123 39p*
DIAL POS PEN	69p*	ZENERs 5-30V	7440 15p* 74141 80p*
SRP 8" x 4"	69p*	SCR & TRIAC'S	7441 79p* 74157 50p*
JKG FERRIC TUB	£1*	DISCO TRIAC 10A 400V 21*	7445 48p* 74193 50p*
PCB etch KIT	£2*	DISCO SCR C108 4A 400V	7447 84p*
VU METERS	£1.50*	SCR 1A400V	7470/7229p* QUOTE
		1A 800V	7473/438p* THIS
		DIAC - ST2	7475 40p* AD FOR
		BR100	7476 39p* SPECIAL
		STEREO 7w AMP	7480/2/5 PRICES
			10p* SHOWN.



PATENTS REVIEW...

Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

The centenary year of recorded sound has now passed; so it seems fitting to mention briefly some of the most important patents relating to sound reproduction which have been granted over the past hundred years. All the patent specifications mentioned can be referred to, free of charge, at the Science Reference Library attached to the Patent Office, just off Chancery Lane in London, during Civil Service working hours. Where possible British rather than foreign specifications have been cited because many of these will also be available for reference in the two dozen public libraries in cities around the UK that hold patents.

INVENTOR

There is a dispute over who should be credited with the invention of the gramophone. One school of thought argues in favour of Frenchman Charles Cros, who, in April, 1877, deposited a sealed packet of documents at the Academy of Sciences, with instructions that it should not be opened until December 1877. The packet described a photo-mechanical process of recording sound on a disc, but it was never put into practice by Cros. Meanwhile, Thomas Alva Edison was working on improvements to the basic telephone and telegraph system.

In July 1877, Edison filed a British Patent (BP 2927/1877) for a scheme to make a permanent record of a telegraph message by making impressions in paper on a disc or cylinder backing. In the same month, Edison patented (BP 2909/1877) a microphone system which enabled the human voice to be transmitted over telegraph wires. The electrical resistance of a point of contact on a diaphragm varied as the diaphragm vibrated, so as to modulate a d.c. current. Although this patent appears to contain details for producing the first gramophone, or phonograph as Edison called it (by teaching how to use the vibrating diaphragm to cut a groove in a cylinder), the filing date for the relevant drawings and description is, in fact, much later—January, 1878. By this time Edison had


already filed what is the master patent on the Phonograph, USA Patent 200521.

This patent described a cylinder recording system for the human voice. Its filing date, December 24, 1877, is regarded by many as the birth-date of recorded sound.

LATERAL CUT

In 1887 Emile Berliner patented lateral-cut recording (USA Patent 372786) as the solution to the mass reproduction of recordings, and although Edison had already patented similar suggestions (even in the 1877 Christmas patent), Berliner's claims are regarded as the birth-date of the modern pressed disc record. Interestingly, Berliner's patent refers to a "gramophone", rather than the "phonograph" referred to by Edison.

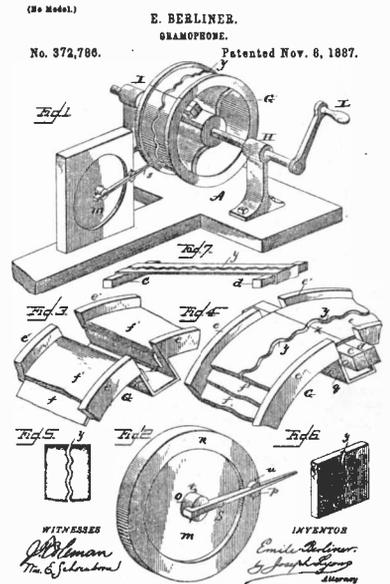Two years before Berliner (in 1885) Sumner Tainter had patented the basic



Edison phonograph, Home Model A, American 1898 (*Science Museum Photograph*).



concept of magnetic recording. He proposed a disc with a groove cut in its surface to induce electric currents in a coil when tracked by a needle, with the currents transduced into sound by a telephone diaphragm (USA Patent 341287). In 1899 Valdemar Poulsen of Denmark patented (BP 8961/1899) a magnetic recorder designed to function as a phonograph or a telephone answering machine. Poulsen was probably the first man actually to make a reliable magnetic recording, and at the Paris Exposition of 1900 he won the Grand Prix. In the same year, Guglielmo Marconi patented the first tunable wireless system (BP 7777/1900).

VALVE

In 1904 John Ambrose Fleming of University College, London, patented (BP 24850/1904) "a vacuum vessel having in it two conductors . . . one of them heated" and the diode valve was born. In 1907 Lee de Forest, of New York, patented (BP 1427/1908) a modified "evacuated vessel" which contained an extra electrode to make it a triode. Although de Forest is rightly credited with inventing the audion, as it was then called, it is important to note this valve really only found a valuable use, and fame, when Edwin Howard Armstrong in the USA invented and patented the feedback principle. The relevant patent is USA 1,113,149 which dates back to a notarised document of January, 1913.

It is also interesting to recall that in 1882 Edison had almost patented the valve! His USA patent No. 273,486 related to an early form of electric light bulb and described the phenomenon whereby material gradually disperses from the filament and accumulates on the inside surface of the glass envelope, blackening it and leaving the filament weak. Edison's answer, buried in the patent as an afterthought amongst other suggestions, was to use a second filament in the same envelope electrically connected to one side of the d.c. supply. This attracted or repelled the particles leaving the filament and thus prevented them from reaching the glass. In other words Edison had patented a diode, nearly twenty years before it was invented.

Incidentally, Edison as far back as 1878, had also patented disc and cylinder machines with facilities for electro-magnetic cutting and reproduction (British Patent 1644/1878). Oliver Lodge, of University College, Liverpool, in 1898, was almost certainly the first worker to invent and patent (BP 9712/1898) a moving coil microphone or speaker system.

Everything had so far, of course, been in mono, or single channel. In 1920, a Washington inventor, Samuel Waters, filed a patent (USA Patent 1520378) for a two-channel disc reproducer. The object of the exercise was

to improve signal to noise ratio rather than to create true stereo, as was interesting other workers at the same time, especially in the cinema. As early as 1911 Augustus Rosenberg of High Holborn, London, had patented a two-channel optical film recording system (BP 23620/1911). Incidentally, it was in 1925 (in British Patent 258 864) that the word "stereophonic" was used almost certainly for the first time.

STEREO

In 1927, W. Bartlett Jones, of Chicago, patented (USA Patent 1855149) the first binaural, or dummy head, stereo system. And in 1931 Alan Blumlein of EMI patented loudspeaker stereo and the 45 degrees double modulation of a 90 degrees groove, as used today (BP 394 325).

In 1936, Bell Telephone Laboratories filed a patent (USA Patent 2137032) which, buried in amongst its other disclosures, taught how the apparent direction of a sound source could be manipulated by altering volume levels to the loudspeakers—the way in which modern pan-potted recordings are made and stereo balance controls function.

Earlier, in 1929, Arthur Keller of Bell Telephone Laboratories in New York had patented the basis of modern multiplexing (USA Patent 1910254), by describing how two separate channels of sound could be recorded in a single record groove by division into two separate frequency bands.



Modern multi-channel discs of discrete multiplex type (as marketed by JVC for the CD-4 system) find their origin there and in a 1946 invention made by EMI engineer William Livy (BP 612 163). The system relied on a recorded carrier to lock a demodulation oscillator to the rotational speed of the record.

Meanwhile, there was considerable invention in other closely associated areas. As early as 1900 Joseph Poliakoff of Moscow had patented (BP 18046/1900) an optical film recording system using a selenium photo-cell. The idea was taken several stages further by Eugene Lauste of London in 1906 (18057/1906). In 1924, Paul Voigt of London patented (BP 231 972) a feedback circuit for an amplifier to compensate for distortion introduced by the loudspeaker—i.e. motional feedback. In 1933, Maj. Edwin Armstrong of New York, USA, patented the basis of modern f.m. radio (USA Patent 1941069).

F.E.T.

In 1934 in Berlin, Oskar Heil invented a solid-state amplifier of semi-conductive material and patented it in Britain (BP 439 457). Oskar Heil is better known for the air-motion transformer loudspeakers sold today by ESS, but his 1934 invention was the first f.e.t.!

A workable system of video recording

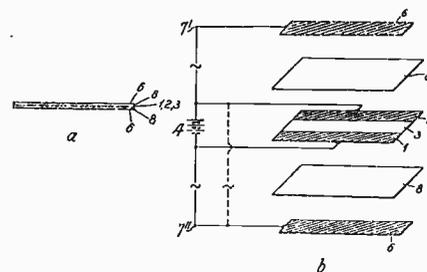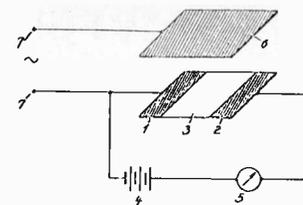

Paul Voigt patent illustration of 1924

was first patented in 1955, by the Ampex Corporation of California (BP 798 927), one of the named inventors being Ray Dolby. BP 1 120 541, of 1965, is in the name of Ray Dolby alone, and constitutes the first patent disclosure of the now well known Dolby noise reduction system. Over recent years much audio patenting activity has centred around surround sound or quadraphonics, the first major matrixing patent being that filed in 1969 by Peter Scheiber of New York (BP 1 328 141 and 1 328 142). The current resurgence of interest in surround sound and the lack to-date of any standardisation on an agreed world system, suggests that the next few years will see this trend of interest continuing. Most recently, and in a slightly lighter vein perhaps, the cinema sound development, Sensurround, which enables audiences to be literally shaken in their seats by very low frequency sound waves generated by high power "effects" circuits is patented in USA Pat. No. 3 973 839. This lengthy patent and ten sheets of circuit diagrams give very full details of how the effects are generated and handled.


Readers who are particularly interested in the history and development of sound may find the current exhibition of over a hundred instruments from the EMI collection of vintage phonographs and gramophones, at the Science Museum, South Kensington, London, of particular interest.

Included in the display is an example of the gramophone that appears in the famous "dog-and-trumpet" trademark and an instrument that could be folded up and pocketed. The exhibited instruments illustrate developments from 1877 to about 1935 but a further display of posters, record sleeves and photographs covers the full 100 years.

The exhibition is located in gallery 1, and is open daily until April.

Understanding Digital Electronics

New teach-yourself courses

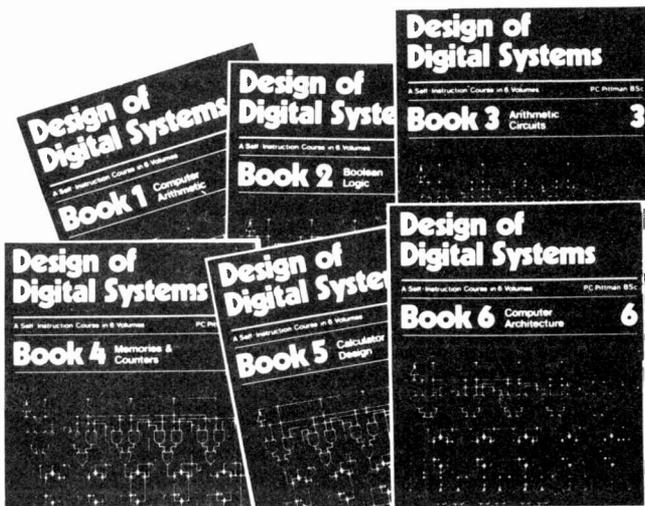

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, Unit 2, Freepost, RIVERMILL LODGE, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. Giro Ac. No. 278 9159. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only:

£7.10

And the four volumes of Digital Computer Logic and Electronics cost only:

£4.60

But if you buy both courses, the total cost is only:

£11.10

+ 90p post & packing by surface mail anywhere in the world. Airmail extra.

Flow Charts & Algorithms

The Algorithm Writer's Guide is a practical book on how to write flow charts and algorithms. Nothing is assumed, though the student should have an aptitude for analytical and logical thought. One volume, A5 size, 130 pages.

Contents: construction, content, form, use, layout of algorithms and flow charts.

£2.95

+ 45p post and packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Unit 2, Freepost, Rivermill Lodge, St. Ives, Huntingdon, Cambs, PE17 4BR, England.

Please send me the following books:

.....sets Digital Computer Logic & Electronics @ £5.50, p & p included

.....sets Design of Digital Systems @ £8.00, p & p included

.....Combined sets @ £12.00, p & p included

.....The Algorithm Writer's guide @ £3.40, p & p included (PE2)

Name


Address

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number

Signature*delete as appropriate

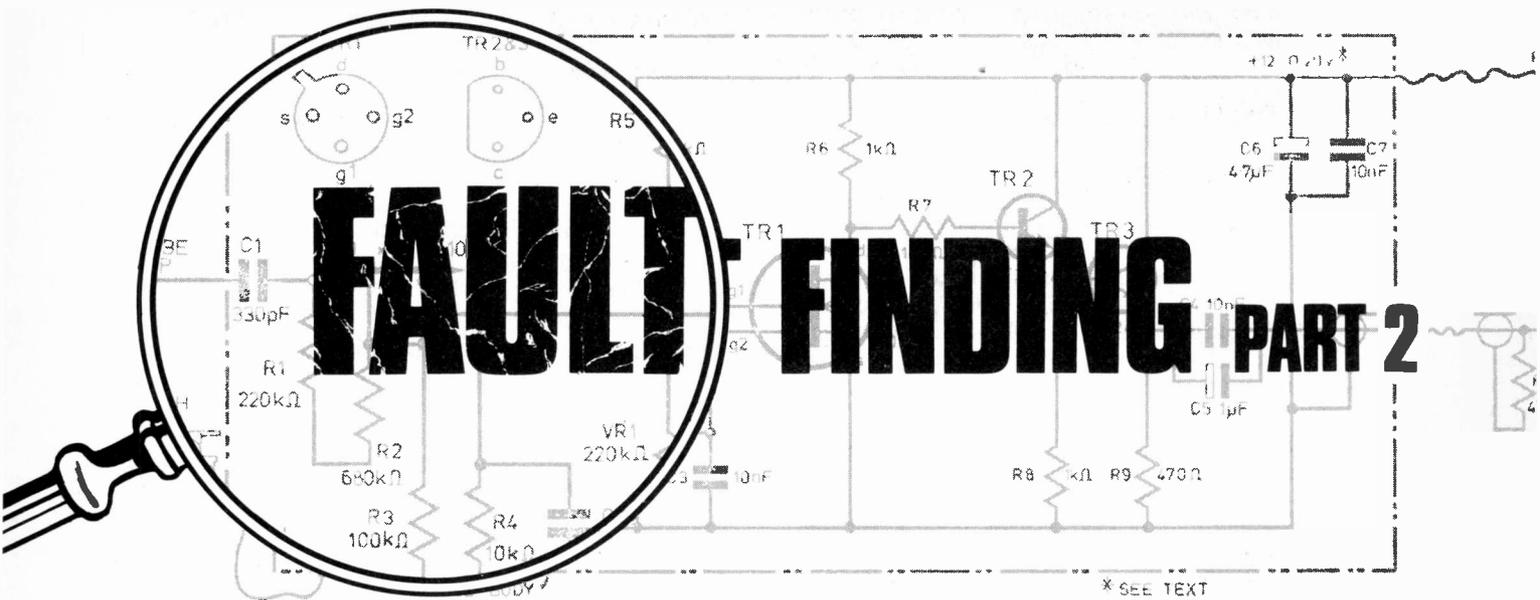Telephone orders from credit card holders accepted on 0480-67446 (ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank.



G. LOVEDAY

Fault Finding on Systems

THE first part of this series dealt with faults caused in an electronic circuit by one component failure. It was shown that when a component fails; goes open or short circuit, then a certain set of symptoms result, and by using these symptoms it is possible to pinpoint the faulty component. The symptoms are any changes in the circuit operation, such as low output signal with distortion, and changes in the d.c. bias voltages. However, when it comes to fault finding on a complete electronic instrument, or system, the situation is made more difficult because of the size and complexity of the system. One component failure will often cause the whole system to fail, but the total number of components may number several hundred. Since time, in the service situation, is of prime importance, it's not acceptable to sit down and methodically measure every voltage and waveform until the faulty component is found. Another technique must be used.

Luckily nearly all electronic instruments can be divided up into several functioning circuit blocks and the quickest way to find the faulty component is by measuring to first of all locate which portion or block of the system has failed, then to work on that block to find the actual component.

THE BLOCK DIAGRAM

This is a really valuable aid in servicing and in helping to understand the operation of a complex piece of equipment. For example, let's look at the block diagram of a basic r.f. signal generator shown in Fig. 2.1. It is made up of six blocks, each of these performing a separate circuit function.

A variable r.f. oscillator feeds a sine wave signal to an amplifier and the output of this amplifier can either be amplitude modulated at 400Hz or constant wave (c.w.) depending upon the setting of the switch.

Since these are two output signals and two possible output conditions for the r.f. output, we can use the states of the outputs as symptoms to fault find the generator. If, for example, there were no outputs at all the fault would most probably lie in the power supply, since it would be unlikely (although possible) that both oscillators had failed. Suppose, however, that the r.f. output was correct in both the modulation and c.w. switch positions but no a.f. output could be obtained. The fault lies in the a.f. attenuator or its connections. These examples show the sort of logical approach

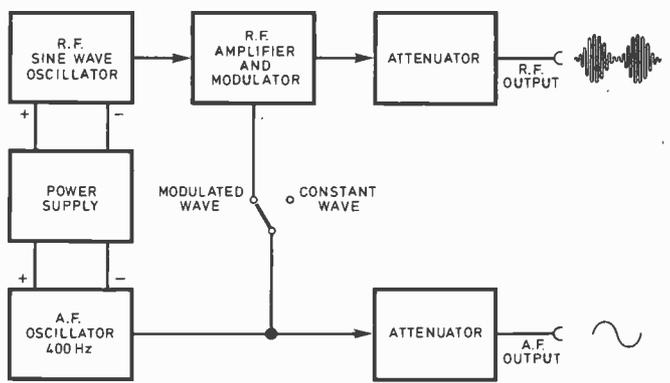


Fig. 2.1. Block diagram of r.f. generator

that's required. The various methods for system fault finding will be shown later in this article. What would be the symptoms for (a) an a.f. oscillator failure or (b) a modulator failure.

INTERPRETING IT

Now let's look at the way in which a block diagram can help in understanding how a unit operates. A switched mode power unit has a full circuit diagram that can look rather forbidding, but when it is drawn out in block form (Fig. 2.2) the operation can be more clearly understood and fault diagnosis is made much easier. Switch power supplies are used in relatively high power applications (e.g. 5 volts at 20 amps) because they have high efficiency, low heat loss and therefore use up less space than a conventional stabilised power unit. The mains voltage is itself rectified and smoothed giving about 340 volts d.c. This voltage is switched at a frequency above audio, usually 20kHz, by high voltage transistors to provide an alternating waveform to the transformer primary.

Since a fairly high frequency is used the transformer need not be so bulky as a 50Hz type. The a.c. voltage at the secondary is rectified and smoothed to give a d.c. voltage across the load. The output is stabilised by comparing it with a reference supply (usually a Zener) and using the different signal to alter the duty cycle of the switching signal to the transistors. If the d.c. output should fall when the load is increased the comparator gives a signal to the pulse width modulator that switches the transistors on for a longer time than they are off during the 20kHz switching period. This provides more power via the transformer to the load and the output voltage rises. The opposite occurs if the load current is reduced.

METHODS FOR SYSTEM FAULT FINDING

One of the first jobs when fault finding on a system is to accurately define the fault. To do this a functional check must be made and the exact symptoms noted. This usually entails making measurements and comparing the performance with the actual specification. In a service department

the engineer would need the up-to-date figures for the performance specification plus the circuits and service manuals and also the necessary test gear. In any project work we should follow the same procedure.

At this stage, depending on the symptoms, it is wise to check that the power supply rails are at their correct voltage levels before proceeding to make measurements to narrow down the search for the faulty component to one part of the block diagram.

It's possible of course to use a completely random approach to find which block is faulty, checking the circuits in any order, but usually a systematic logical approach yields the quickest results. The three methods are called:

- (1) Input to output (or beginning to end)
- (2) Output to input (or end to beginning)
- (3) Half-split.

Here we are considering actual measurements, but don't forget that a visual inspection for broken wires, dry joints, burnt components, damaged copper track, etc., can also be worthwhile. This is especially the case when a system that you have just assembled refuses to function at all.

METHODS ANALYSED

The first two methods listed above are fairly obvious and most of us used input to output checking before we knew that somebody had given it a name! A suitable input signal (if required) is injected into the first block and then measurements are made sequentially at the output of each block in turn until the faulty block is located. Output to input is the reverse; leaving the input to block (1) measurements are made from output block towards the input. This presupposes that the units are all in series, but this is rarely the case. The s.m.p.u. for example cannot be fully checked using a straightforward sequence of tests. Suppose the unit fails with the symptom of zero output. The fault could be in almost any block. One sequence of checks to find that fault could be the following:

- (a) Measure d.c. voltage from mains rectifier block (1)
- (b) Measure output of 20kHz oscillator block (2)

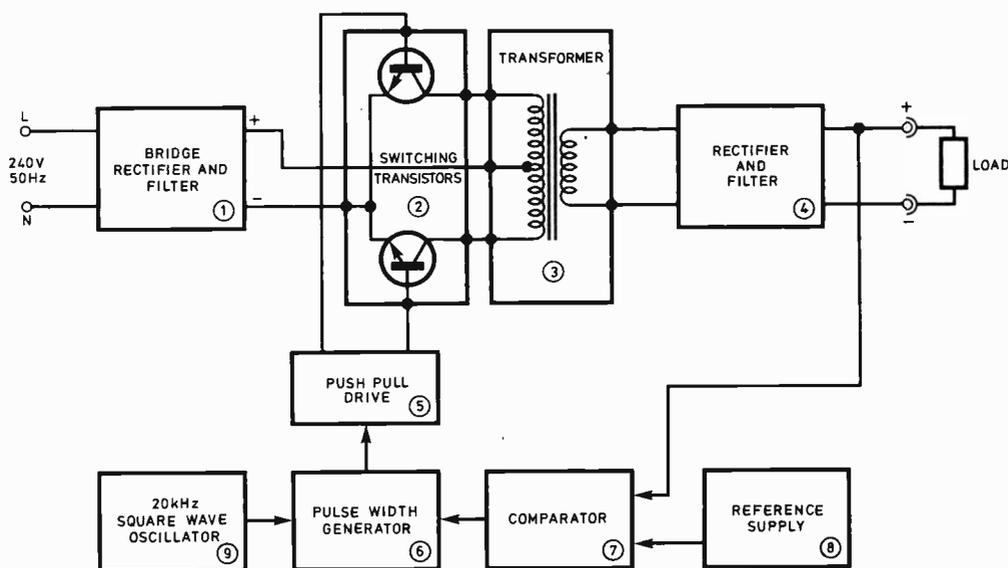


Fig. 2.2. Block diagram of switched mode power unit

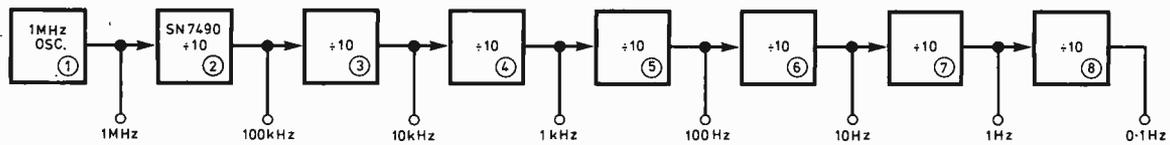


Fig. 2.3. Frequency divider chain

By doing these checks first we verify the two primary conditions for an output across the load. Assuming both these blocks are functioning correctly we can then use output to input by measuring (4), (3), (2) and then (5), (6), (7), (8) or input to output measuring from (8), (7), (6), (5), (2), (3), (4). Either method is satisfactory, but the first is probably the best as it checks early on through the circuits that probably have the highest failure rate (namely the switching transistors). Using this criterion the sequence of test could be (1), (9), then (2), (3), (4), and finally (5), (6), (7), (8). The important thing to realise is that the tests ought to follow some logical sequence.

Imagine now a fault with the symptoms of high un-stabilised output voltage. From this we can conclude that blocks (1), (2), (3), (4) and (9) are all operating. The fault is somewhere in blocks (5), (6), (7), (8). Here a good start would be to measure the output of (8) since an open circuit reference supply would give these particular symptoms.

HALF-SPLIT METHOD

The half-split method for system fault location is really useful when the instrument or system is made up of a large number of blocks in series. A good example is fault finding on the frequency divider chain of a digital frequency meter (Fig. 2.3). Here the frequency of a 1MHz crystal oscillator is divided down by decade counters to give the required timing pulses. Since eight blocks are used it is possible to divide the unit into two equal parts, test to decide

which half is working correctly, then split the non-working section into half again to locate the fault. Let's assume that block (6) has failed; the sequence of tests would be as follows:

1. Split whole unit into half by measuring output from block (4). This will be alright showing that the fault lies somewhere in blocks (5) to (8).
2. Split blocks (5) to (8) in half checking output of block (6). There will be no output.
3. Check output of block (5). This will be all right proving that the fault is in block (6).

Now try the method for yourself by assuming that block (3) or block (8) has failed, and you will find that the number of checks necessary to locate the fault is always three. On average more tests would be required using any other method. Unfortunately many instruments are not made up of many blocks in series. More often than not a system has feedback loops that are necessary for operation and which cannot be split. Also convergence, where two inputs are required to make a circuit block operate correctly, and divergence, where an output from a block feeds two or more other blocks are quite common. These situations complicate the use of the half split. When fault finding try and use the method, or a combination of methods that will locate the faulty block in the shortest possible time. This isn't always achieved with the minimum number of test measurements. A common sense logical approach to the problem is the basic requirement.

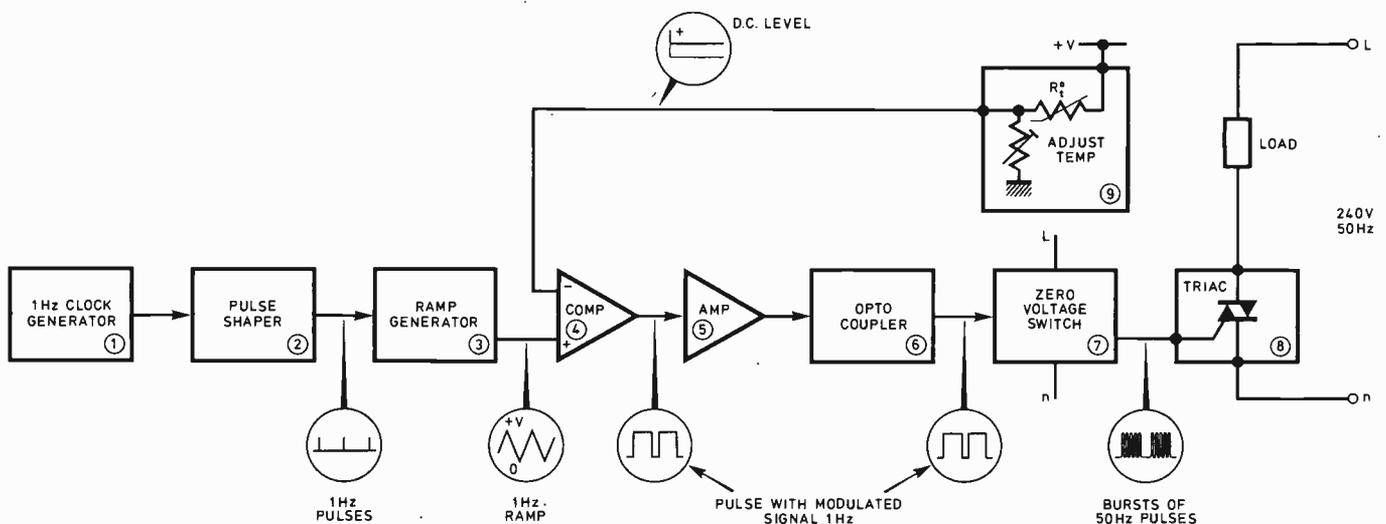


Fig. 2.4. Block diagram of temperature controller

TEMPERATURE CONTROLLER FAULT DIAGNOSIS

As a final exercise we are going to look at the block diagram of an oven temperature controller. This is a nice series type of circuit but with the added complication of feedback from the temperature sensor. The unit uses burst cycle firing of a triac to control the power dissipated in a heating element. With this type of control, power is applied for a few cycles of the mains at a time, say 40 out of 50 cycles when the temperature is lower than required, reducing to maybe 5 out of 50 cycles when the oven temperature has stabilised. A zero voltage switch ensures that the triac is only pulsed on when the mains voltage is near zero thus eliminating the generation of r.f. interference.

The operation is fairly straightforward. A clock generator gives pulses via a shaping circuit of 1Hz to a ramp generator. This ramp is compared with the d.c. level from the temperature sensor. When the temperature inside the oven is lower than required this d.c. level is also low so the output of the comparator is high. The ramp goes from a positive voltage towards zero. While the ramp voltage exceeds the d.c. voltage from the sensor the output is high. This level is amplified and then applied via an opto-coupler to the zero voltage switch. The opto-coupler ensures that the mains side of the system is isolated from the low voltage portion. While the comparator output is high the zero voltage switch delivers pulses to gate on the triac and so power is applied to the heater. As the temperature in the oven rises so does the d.c. voltage from the temperature sensor and this means that the comparator output is high for a shorter time during the 1 second clock period.

A FEW QUESTIONS

The feedback could complicate fault diagnosis but since

all the rest of the circuit blocks are in series it is possible to use any of the methods described. We just have to ensure that a reasonable d.c. level is present on the inverting terminal (-) of the comparator. Assuming that the temperature sensor is o.k. a meter could be used to monitor this d.c. voltage or alternatively the feedback line could be broken and an adjustable d.c. voltage applied in its place.

If you are still with it, try your hand at answering a few questions:

- (1) Which fault finding method should theoretically get the quickest results?
- (2) What would be symptoms for the following faults?
 - (a) Short circuit triac.
 - (b) Temperature sensor open circuit.
 - (c) No output from 1Hz unit.
 - (d) Ramp output failed with output permanently low.
 - (e) Ramp failed with reduced amplitude (lower starting voltage).

ANSWERS

- (1) Half split.
- (2) (a) Oven overheating, no control. Few pulses at the output of the zero voltage switch.
(b) Oven overheating, no control. Many pulses at the output of the zero voltage switch.
(c) Ramp output will remain at +V therefore full power will be applied to the load. Many pulses at the output of the zero voltage switch.
(d) No heating. Low d.c. level from temperature sensor. Output of comparator remaining low however.
(e) Slow response to changes in temperature control.

Next month: Fault diagnosis of thyristor and triac circuits.



BOOK REVIEWS

MODERN ELECTRONICS MADE SIMPLE

By G. H. Olsen

Published by W. H. Allen & Co Ltd
306 pages, 130 × 215mm. Price £1.75

THIS book is good value indeed! It covers a wide variety of fields, and would serve as an excellent reference to have around for those whose memories occasionally require refreshment (most of us), or for the student of "A" Levels or an ONC Course, or C&G, at college.

The author has gauged the contents so that no prior knowledge of electronics is needed, other than basic electricity, and each new device covered is explained in terms of its physics before commencing with applications and design theory. The explanations are fairly thorough; for instance, the chapter entitled "Power Supplies" starts with batteries and their very chemical structure. Questions are posed at the end of each chapter, which you should be able to answer correctly before advancing to the next section.

The final chapter, "Projects", gives a number of circuits to play around with—just to satisfy yourself that what you've learned really works! These are by no means constructional projects in the sense that P.E. presents them, but if reading is the way to learn, then this is the way to remember.

My only criticism would be against the title, in that it's not so much a case of *Modern Electronics Made Simple* as just modern electronics set out clearly; but perhaps this is a trivial point since clarity is half the battle.

M.A.

TV TECHNICIAN'S BENCH MANUAL

By G. R. Wilding

Published by Argus Books Ltd.

217 pages, 143 × 224mm. Price £4.50

IT is the objective of this hardback, to present in a handy form adequate information for the service technician or enthusiastic amateur to locate television receiver faults of all kinds, fairly promptly.

Each chapter gives a brief run-down of all important aspects of the receiver section it covers, followed by the recommended servicing procedure to break down the most likely cause of trouble in order of probability.

Circuit diagrams for *specific* television receivers are present throughout, extracted from various manufacturers, but not too many circuit diagrams from Japanese sets are given.

There are 13 chapters, covering just about all the aspects of television receivers, and the last four chapters form a section devoted to colour.

This book gives fairly thorough coverage of its subject, but assumes a certain amount of prior knowledge, and therefore is not suitable for anyone seeking to understand television for the first time. As the name suggests, it is for the technician who already understands the overall functioning of a television, but perhaps needs a reference source for the more subtle variations he may encounter with different sets, and the appropriate servicing routines.

M.A.

15-240 WATTS!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.


FEATURES: complete pre-amplifier in single pack; multi-function equalisation, low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV, auxiliary 3-100mV, input impedance 47k Ω at 1kHz. Outputs—tape 100mV, main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16-50V.

Price **£5.22** + 65p VAT. P. & P. free

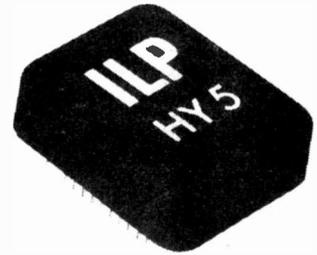HY5 mounting board B.1. **40p** + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit, low distortion; short, open and thermal protection, easy to build

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price **£5.22** + 65p VAT. P. & P. free

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink, only five connections, 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems, low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price **£6.82** + 85p VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion, integral heatsink, load line protection, thermal protection, five connections; no external components.

APPLICATIONS: hi-fi; high quality disco, public address, monitor amplifier, guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

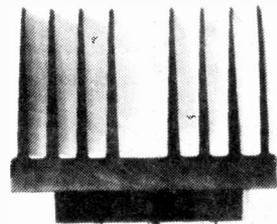Price **£15.84** + £1.27 VAT. P. & P. free



HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown, very low distortion; load line protection, integral heatsink, no external components.

APPLICATIONS: hi-fi, disco, monitor; power slave, industrial, public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Size—114 x 100 x 85mm.

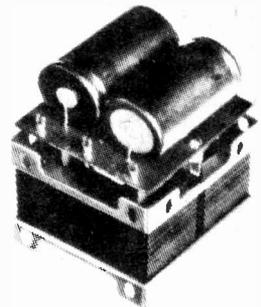Price **£23.32** + £1.87 VAT. P. & P. free



HY400 240W into 4 Ω

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown, very low distortion; load line protection, no external components

APPLICATIONS: public address, disco, power slave, industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price **£32.17** + £2.75 VAT. P. & P. free

POWER SUPPLIES: **PSU36**—suitable for two HY30s **£5.22** + 65p VAT. P. & P. free. **PSU50**—suitable for two HY50s **£6.82** + 85p VAT. P. & P. free. **PSU70**—suitable for two HY120s **£13.75** + 1.10 VAT. P. & P. free. **PSU90**—suitable for one HY200 **£12.65** + £1.01 VAT. P. & P. free. **PSU100**—suitable for two HY200s or one HY400 **£23.10** + £1.85 VAT. P. & P. free.

I.L.P. Electronics Ltd., Crossland House, Nackington, Canterbury, Kent CT4 7AD

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

Registered office No. 1032630



MINI CONSOLES

Ideal for small desk control panels and consoles. Moulded in orange, blue, black and grey ABS. Incorporates slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of console and held by screws running into integral brass bushes.

MC 161 x 96 x 58mm £1.53 (1-9) £1.50 (10+)
MC 215 x 130 x 75mm £2.20 (1-9) £2.17 (10+)
Add 25p per £1 order value for Post & Packing

ECONOMY QUALITY LEO'S

50 for only £5 - 100 for only £9
Mixed bags, all sizes, various colours

FULL SPECIFICATION LEO'S


Red (specify size) 75p per pack
Green, Yellow, Orange (specify size) £1.20 per pack
(Each pack contains 5 LED's, Mounting Clips and Data)


TYPE A NEON INDICATORS

Supplied with resistor for 240 Volts operation
Held in 8mm hole by plastic bezel
150mm wire leads



Red, Amber, Clear, Opal 19p each
Green 28p each

12 VOLTS MINI HAND DRILL

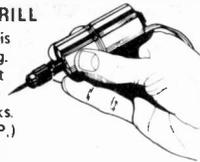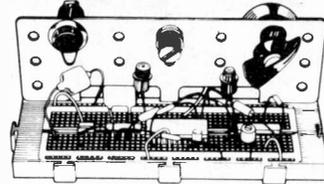Ideal for drilling pcb, chassis etc as well as model making. Supplied with 2 collets that accept tools and drills with 3/32" and .050" dia. shanks. £7.56 (Includes VAT & P.P.)



Stop wasting time soldering
The NEW MW BREADBOARD accepts Transistors, LED's, Diodes, Resistors, Capacitors and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has over 400 individual sockets, plus Vcc and Ground Bus Strips
Price £9.72 (includes VAT & P.P.)

TYPE MP NEON INDICATOR

Supplied with resistor for 240 Volts operation
150mm leads, held in 6.4mm hole by nut



Red, Amber, Clear, Opal 20p each

SEVEN SEGMENT DISPLAYS

Economy Quality
Common Anode - 0.3" - Left Decimal
Red, Yellow and Green @ 45p each

Full Specification
Common Anode - 0.3" - Left Decimal
Red @ 98p each
Green and Yellow @ £1.35 each
(Data supplied with Full Spec. displays only)




Quantity quotations on request

P.P. Note Unless included in price add 25p Post & Packing for orders totalling under £10. All prices include VAT and are valid in UK only for 2 months from journal issue date

Michael Williams Electronics
47 Vicarage Av. Cheadle Hulme, Cheshire SK8 7JP

SC BOXES (square corners)

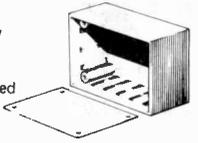Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of the box and held by screws running into integral brass bushes.



SC 85 x 56 x 35mm 80p (1-9) 77p (10+)
SC 111 x 71 x 48mm £1.07 (1-9) £1.04 (10+)
SC 161 x 96 x 59mm £1.49 (1-9) £1.46 (10+)
Add 25p per £1 order value for Post & Packing

240 VOLTS MINI HAND DRILLS

Ideal for drilling pcb's, chassis etc as well as model making. Supplied with 3 collets that accept tools and drills with 1mm, 2mm and 1/8" dia shanks.



£9.72 (includes VAT & P.P.)
Accessory tools... 5 Burrs, 1mm, 2mm, 1/8th Drills, 3/32" Collet Price £1.75 (Includes VAT & P.P.)

RC BOXES (round corners)



Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Close fitting flanged lids held by screws running into integral brass bushes.

RC 100 x 50 x 25mm 51p (1-9) 49p (10+)
RC 112 x 62 x 31mm 59p (1-9) 52p (10+)
RC 120 x 65 x 40mm 68p (1-9) 62p (10+)
RC 150 x 80 x 50mm 77p (1-9) 74p (10+)
RC 190 x 110 x 60mm £1.33 (1-9) £1.30 (10+)

Polystyrene version

in grey only with no slots, no integral brass bushes
RC(P) 112 x 61 x 31mm 35p (1-9) 32p (10+)
Add 25p per £1 order value for Post & Packing

SEMICONDUCTOR OFFERS ALL FULL SPEC

BC212, BC182, BC237, BF197, BC159, ALL 8p each. RCA 2015 TO3 POWER TRANSISTOR (SIM TO 2N3055) 35p. ACY18 18p. BF200 20p. MOTOROLA MRD 3051 PHOTO TRANSISTORS 35p. N. CHANNEL F.E.T.S SIMILAR TO 2N3819 18p. MOSFET SIM. TO 40673 35p. 3N140 MOSFETS 50p. M203 DUAL MATCHED PAIRS MOSFETS SINGLE GATE PER F.E.T. 40p. S1301 DUAL MATCHED PAIR SIL. N.P.N. POWER TRANSISTORS FT 300MHz 30p. INTEL 1024 BIT MOS RAMS 95p. MULLARD BB113 TRIPLE VARICAP DIODE 35p. MC1310 STEREO DECODER I.C.s £1.20. TB800 I.C. AMPS 90p. CD4051 CMOS 50p. MC1303N ST. PREAMP I.C. £1.30. 741 8 PIN D.I.L. 23p. MM5316 CLOCK CHIPS £3.50. 400v 15 amp STUD S.C.R. 75p. 500v 600mA BRIDGE RECS. (EX. EQUIP.) 25p. 1N4002 100v 1A DIODES 4p. 1A005 800v 1A DIODES 7p. 200 volt 5 amp SIL. BRIDGES EX. EQUIP. 40p. CV7556 200v 150 amp STUD RECS. £1.25. E.H.T. SIL. REC. 15kV 2.5 mA, 15mm x 5mm 85p. 7812 1A PLASTIC V. REGS. 95p. MIN. NIXIES ITT 5870ST 13 x 6mm FIG SIZE 85p. NIXIES ITT CN/9A 13 x 8mm 65p. 0.2" OR 0.125" RED LEDs 12p each. MAN3A 3mm LED DISPLAYS 50p. MONSANTO 4640A 0.3" 7 SEG. C. CATH. DISPLAYS 95p. MICROPHONES—GRUNDIG ELECTRET INSERTS WITH BUILT IN F.E.T. PREAMP £1.50. CRYSTAL MIKE INSERTS 37mm 50p. ELECTRET CONDENSER MIKES 1K0 IMP. WITH STD JACK PLUG £2.85. CASSETTE CONDENSER MIKES WITH 2.5 AND 3.5 JACK PLUGS £2.85. STANDARD CASSETTE MIKES 200 OHM IMPED. WITH 2.5 AND 3.5 JACK PLUGS £1.20. P.A. MIKES MOBILE TYPE 50K0, THUMB SWITCH £4.20. MORSE KEYS—PLASTIC TYPE 95p. HI-SPEED TYPE ALL METAL £2.25. HI-IMP. PHONES 2K0 £1.65. AERIAL COAX SWITCH 3 POSITION, 3 OUTPUTS, 0-30MHz, 150 watts MAX. USES SO239 SOCKETS £4.95. LOW PASS IN-LINE FILTERS, 30MHz CUT OFF, 50 OHM IMP. £3.30. S.W.R. METER, 50 OHM IMP. WITH POWER SCALE £10.50. XTAL MARKER GEN. 300kHz WITH STAPS TO 60MHz, SUPPLIED WITH XTAL FOR THIS COVERAGE £7.90. CRYSTALS 300kHz HC60 40p. 4.43MHz C.T.V. XTALS 45p. 0.1" EDGE CONNECTORS 64 Way 65p. 32 Way 40p. RELAYS—MIN. SEALED RELAYS ALL 4 POLE CHANGE OVER, 360 (6v DC) 45p. 7000 (24v DC) 55p. MIN. 220v AC SEALED RELAY 2 POLE C/O 45p. 240v AC SEALED RELAY 3 POLE C/O 5 AMP CONTACTS 11 PIN BASE 80p. 12 VOLT 4 POLE N.O. REED RELAY 20p. MOTORS—1.5 TO 6v DC MODEL 20p. 115v AC MIN. 3 R.P.M. WITH GEARBOX 30p. 240v AC SYNCH. MOTOR 1/5TH R.P.M. 65p. 240v AC SYNCH. MOTOR 1/24TH R.P.M. 65p. BOXES—BLACK A.B.S. PLASTIC WITH BRASS INSERTS AND LID, 75 x 56 x 35mm 40p. 95 x 71 x 35mm 49p. 115 x 95 x 36mm 57p. GREY POTTING BOXES WITH LUGS, 23 x 48 x 23mm 11p. 38 x 52 x 25mm 13p. 60 x 80 x 42mm 28p.

TRANSFORMERS—0-0-6v 100mA, 9-0-9v 75mA, 12-0-12v 50 mA 75p each. 12-0-12v 100mA 95p. 12v 500mA 95p. 35v 2A AND 2.5v 2A TOROID £2.75 + 35p P & P. 18v 1 amp RECTIFIED £1.95 + 35p P & P. 25v 2 amp £1.75p + 35p P & P. 0-12-15-20-24-30v 1 amp £3.25 + 35p P & P (2 amp VERSION £4.45 + 35p P & P). 30-0-30v 1A £3.00 + 35p P & P. 25-0-25v 2A £3.95 + 35p P & P. 100 volt LINE TRANSFORMER 15 watts MAX - 0-8-15 £1.80 + 35p P & P. 1:1 TRIAC XENON PULSE TRANSFORMER 30p. 6MH 3 amp CHOKES 30p. SWITCHES—MIN. TOGGLE, SPST 12 x 6 x 9mm 54p. D. P.DT 12 x 11 x 9mm 60p. DPDT CENTRE OFF 12 x 11 x 9mm 75p. 4P 2W SLIDERS 20p. 6P 3W SLIDERS 30p. DPDT C/O SLIDERS 20p. SPST 10 amp ROCKERS 12p. R.S. SINGLE POLE C/O PUSH-BUTTONS 45p. ROLLER MICRO SWITCHES 15p. MIN. MICRO SWITCHES 13 x 10 x 4mm 20p. G.P.O. KEYSWITCH ASSY. 3 SWITCHES 2-3 WAY, 1-2 WAY MULTIPLE 35p. MIN. PUSH TO MAKE OR PUSH TO BREAK SWITCHES 16 x 6mm 15p. PLESSEY WINKLER STUD SWITCHES 2 BANK, 1 POLE 30 WAY ADJ. STOP 75p. DE-SOLDERING TOOLS, PLUNGER TYPE £4.95. TAPE HEADS—JAP. CASSETTE MONO 90p. CASSETTE STEREO £3.00. BSR MN1330 3 TRACK DUAL IMPEDANCE REC/PLAYBACK 50p. BSR SR990 3 TRACK STEREO REC/PLAYBACK £1.95. TD10 ASSEMBLES TWO HEADS 3 TRACK REC/PLAYBACK STAGGERED STEREO WITH BUILT IN ERASE PER HEAD £1.20. TAPE HEAD DEMAG 240v AC £1.95. BUZZERS—GPO TYPE 6-12v 30p. 6-12v HOOTERS 50p. MIN. SOLID STATE BUZZERS 6-9-12 OR 24v 15MA 75p. U.H.F. T.V. TRANSISTORISED PUSH BUTTON TUNERS (NOT VARICAP), NEW AND BOXED £2.50. POT CORES—ADJ. VINKOR 250-370 MICRO H 20p. 260 OR 500 MILLI HENRY CORES 10p each. METERS—100-0-100µA LEVEL METERS 7.75. STEREO TUNING METERS 100µA PER MOVEMENT £2.75. GRUNDIG BATT. LEVEL METER 1mA 40 x 40mm £1.10. MIN. LEVEL METER 200µA 25 x 15mm 75p. FERRANTI 1mA PANEL METER 55 x 70mm £2.95. FERRANTI PANEL METER 100µA 55 x 70mm £3.50. FERRANTI 600v AC METER £3.95. BOARDS—G.P.O. BOARD WITH 64, BC107 TYPE TRANSISTORS, 2 REED, 1 MERCURY RELAY ETC. £2.00. + 55p P & P. SINGLE STAGE STEREO PRE-AMP BOARDS MAX 1/2 700 M/V (HI-Z) GAIN 26 DB 40p. 465kHz I.F. PANELS. 6 I.F.T.'s 30p. BOARD WITH 14 12v N.O. REED RELAYS £2.40. BOARD WITH 6v C/O REED RELAY £1.20. AEROSOLS—SERVISOL SWITCH CLEANER + LUBRICANT Gearz 55p. FREEZER 60sz 50p. GEAR CLEANER + TAR REMOVER 14ozs 85p. SOLENOIDS—240v AC 45p. 12v DC H DUTY 75p. 240v AC LARGE 25lbs PULL 4" TRAVEL £3.25 + 50p P & P. POSTAGE 30p UNLESS OTHERWISE SHOWN (EXCESS POSTAGE REFUNDED WITH ORDER). OVERSEAS POST AT COST. VAT INCLUDED IN ALL PRICES.

'COMPUTER CHESS CHALLENGER'



— IT'S YOU AGAINST THE COMPUTER (IN YOUR OWN HOME!)

A Microcomputer, programmed to challenge you at one of THREE levels to match and improve your game. With this unique game, there is no need to find an opponent! You simply enter your moves, then 5-40 seconds later, after analysing the new position, the computer will respond!
This amazing microprocessor computer is supplied complete with Chessmen, comprehensive instructions, and mains adaptor; and is fully guaranteed. You can now play chess when you are ready, day or night, without the bother of finding a chess partner.
The 'COMPUTER CHESS CHALLENGER' has many other features to intrigue and excite the chess enthusiast, whether young or old, including: Casting and en passant, position verification by computer memory recall. You can even set up chess problems on the board!
Available by mail order post free. Price: £185.00 (SINGLE level model available at £135.00).
Write or telephone now for full colour literature and data sheets.
COMPUTER BACKGAMMON GAME NOW AVAILABLE - Write or 'phone for full details.
Sinclair Microvision Pocket Television - Write or 'phone for full details.
We offer SEIKO watches at discount prices - SAE.
We accept company purchase orders by telephone. Scientific calculators - all brands - supplied at discount prices - SAE.

GEMINI ELECTRONICS
3 Branksome Avenue, Prestwich,
Manchester M25 5AG.
Tel: 061-773 4467.
EXPORT ORDERS WELCOME

ORDER ADDRESS:

PROGRESSIVE RADIO 31 CHEAPSIDE, LIVERPOOL 2. 051-236 0982.

Get a great deal from

Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome

A. MARSHALL (LONDON) LTD. DEPT. P.E.
 LONDON—40-42 Cricklewood Broadway NW2 3ET
 Tel: 01-452 0161 Telex: 21492
 LONDON—325 Edgware Rd W2 Tel: 01-723 4242/3
 GLASGOW—85 West Regent Street G2 2OD
 Tel: 041-332 4133
 BRISTOL—1 Straits Parade, Fishponds Rd BS16 2LX
 Tel: 0272 854201

CATALOGUE NEW 1977 AUTUMN ★
 COMPLETE BUYERS GUIDE TO
 ELECTRONICS COMPONENTS
 PRICE 35p POST PAID. 25p FOR CALLERS

TOP 400 SEMICONDUCTORS FROM THE LARGEST RANGE IN THE U.K.

EXPRESS M.O. SERVICE BY RETURN POST—all

Please add VAT to your order. P. & P. 40p

orders received despatched same day on stock items

2N696	0-65	2N3703	0-45	2N6126	0-45	BC159	0-16	BD116	1-20	BFX88	0-35
2N697	0-20	2N3704	0-15	40361	0-50	BC160	0-35	BD131	0-51	BFK87	0-30
2N698	0-65	2N3705	0-15	40362	0-55	BC161	0-35	BD132	0-54	BFK88	0-30
2N699	0-55	2N3706	0-16	40363	1-30	BC167	0-12	BD135	0-37	BFK89	1-25
2N700	0-28	2N3707	0-18	40406	0-60	BC168	0-12	BD136	0-37	BFV50	0-25
2N706A	0-28	2N3708	0-13	40407	0-52	BC169	0-12	BD137	0-38	BFV51	0-25
2N708	0-28	2N3709	0-15	40408	0-75	BC170	0-18	BD138	0-38	BFV52	0-25
2N709	0-50	2N3710	0-16	40409	0-75	BC171	0-18	BD139	0-40	BFV53	0-34
2N718	0-27	2N3711	0-16	40410	0-75	BC172	0-14	BD140	0-40	BFV90	1-20
2N718A	0-20	2N3712	1-20	40411	2-85	BC177	0-20	BD239	0-40	BRV39	0-50
2N720A	0-30	2N3713	2-30	40594	0-80	BC178	0-20	BD240	0-40	BSK20	0-33
2N914	0-35	2N3714	2-45	40595	0-90	BC179	0-23	BD241	0-45	BSK21	0-32
2N916	0-30	2N3715	2-55	40773	0-75	BC182	0-11	BD242	0-50	BU105	1-40
2N918	0-38	2N3716	3-00	AC128	0-45	BC182L	0-14	BD243	0-60	BU205	2-20
2N920	0-25	2N3717	1-95	AC127	0-48	BC183	0-11	BD244	0-65	ME0402	2-00
2N930	0-26	2N3717	2-00	AC128	0-45	BC183L	0-14	BD245	0-65	ME0404	1-15
2N1131	0-30	2N3773	2-90	AC151V	0-40	BC184	0-12	BD246	0-66	ME0412	2-00
2N1132	0-37	2N3789	2-90	AC152V	0-50	BC184L	0-14	BD529	0-45	ME4102	1-10
2N1613	0-30	2N3790	3-10	AC153	0-55	BC206	0-16	BD530	0-50	ME4104	1-10
2N1711	0-30	2N3791	3-10	AC153K	0-55	BC206	0-16	BD531	1-00	ME4104	1-10
2N1893	0-30	2N3792	3-50	AC176	0-50	BC207	0-16	BF115	0-38	MJ490	1-35
2N2102	0-98	2N3794	2-00	AC176K	0-65	BC212L	0-17	BF121	0-55	MJ491	1-85
2N2218	0-33	2N3819	0-36	AC187K	0-60	BC213	0-14	BF123	0-55	MJ2955	1-25
2N2218A	0-37	2N3820	0-38	AC188K	0-60	BC213L	0-16	BF152	0-25	MJE340	0-58
2N2219	0-35	2N3823	0-80	AD161	1-00	BC214	0-16	BF153	0-25	MJE370	0-58
2N2219A	0-36	2N3824	0-80	AD162	1-00	BC214L	0-17	BF154	0-25	MJE371	0-58
2N2230	0-35	2N3806	0-22	AF106	0-55	BC237	0-14	BF159	0-35	MJE520	1-50
2N2221	0-25	2N4036	0-67	AF109	0-75	BC238	0-12	BF160	0-30	MJE521	0-65
2N2221A	0-26	2N4037	0-55	AF124	0-65	BC239	0-15	BF166	0-40	MJE3055	0-95
2N2222	0-25	2N4058	0-50	AF125	0-65	BC251	0-10	BF167	0-40	MJE3055	0-95
2N2222A	0-25	2N4059	0-15	AF126	0-65	BC251	0-22	BF167	0-40	MJE3055	0-95
2N2366	0-25	2N4920	0-20	AF139	0-59	BC257A	0-17	BF173	0-35	MPR112	0-40
2N2369	0-25	2N4061	0-17	AF186	0-50	BC258A	0-17	BF177	0-25	MPR113	0-45
2N2369A	0-25	2N4062	0-18	AF200	1-20	BC259B	0-18	BF178	0-25	MPP102	3-00
2N2646	0-75	2N4126	0-17	AF239	0-65	BC261A	0-24	BF179	0-30	MPSA05	0-25
2N2647	1-40	2N4289	0-20	AF240	1-14	BC262B	0-24	BF180	0-35	MPSA06	0-25
2N2904	0-36	2N4919	0-65	AF279	0-80	BC263C	0-30	BF181	0-35	MPSA12	0-40
2N2904A	0-37	2N4920	0-75	BC180	0-85	BC260	0-40	BF182	0-35	MPSA15	0-45
2N2905	0-37	2N4921	0-50	BC107	0-15	BC301	0-40	BF183	0-40	MPSA56	0-25
2N2905A	0-38	2N4922	0-55	BC108	0-15	BC303	0-50	BF184	0-38	MPSU05	0-50
2N2906	0-28	2N4923	0-70	BC109	0-15	BC307	0-15	BF185	0-35	MPSU06	0-56
2N2906A	0-35	2N5190	0-60	BC113	0-20	BC308	0-15	BF194	0-15	MPSU55	0-55
2N2907	0-25	2N5191	0-70	BC115	0-20	BC309C	0-15	BF195	0-15	MPSU56	0-60
2N2907A	0-25	2N5192	0-75	BC116	0-20	BC317	0-16	BF196	0-15	MPSA58	0-60
2N2924	0-15	2N5195	0-90	BC116A	0-20	BC318	0-13	BF197	0-17	TIP28C	0-60
2N2925	0-17	2N5245	0-34	BC117	0-22	BC327	0-20	BF198	0-16	TIP30A	0-49
2N3019	0-55	2N5294	0-40	BC118	0-20	BC328	0-19	BF200	0-35	TIP30C	0-65
2N3053	0-26	2N5295	0-40	BC119	0-30	BC337	0-19	BF225J	0-25	TIP31A	0-50
2N3054	0-30	2N5296	0-40	BC121	0-45	BC338	0-21	BF244	0-35	TIP31C	0-66
2N3055	0-70	2N5298	0-40	BC132	0-30	BC347	0-12	BF245	0-45	TIP32A	0-65
2N3390	0-20	2N5447	0-15	BC134	0-20	BC348	0-12	BF246	0-75	TIP32C	0-75
2N3391	0-20	2N5448	0-15	BC135	0-20	BC349	0-13	BF254	0-24	TIP33A	0-80
2N3391A	0-20	2N5449	0-19	BC136	0-19	BCY30	1-00	BF255	0-24	TIP33C	1-10
2N3392	0-16	2N5457	0-32	BC137	0-20	BCY31	1-00	BF257	0-37	TIP34A	0-90
2N3393	0-15	2N5458	0-33	BC140	0-35	BCY32	1-00	BF258	0-45	TIP34C	1-20
2N3394	0-15	2N5459	0-29	BC141	0-40	BCY33	1-00	BF259	0-49	TIP35A	0-80
2N3394A	0-16	2N5460	0-34	BC142	0-40	BCY34	1-00	BF259	0-49	TIP35A	0-80
2N3440	0-85	2N5485	0-38	BC143	0-30	BCY38	2-00	BF459	0-50	TIP36A	2-80
2N3441	0-81	2N6027	0-50	BC147	0-12	BCY42	0-60	BF493	0-28	TIP41A	0-70
2N3442	1-35	2N6101	0-45	BC148	0-12	BCY58	0-25	BF528	1-38	TIP41C	0-90
2N3638	0-16	2N6107	0-42	BC149	0-14	BCY59	0-25	BF528	1-38	TIP42A	0-80
2N3638A	0-16	2N6109	0-50	BC153	0-27	BCY70	0-25	BF528	1-38	TIP42C	1-00
2N3639	0-30	2N5121	0-38	BC154	0-27	BCY71	0-26	BF529	0-30	TIP2955	0-65
2N3641	0-10	2N6122	0-41	BC157	0-14	BCY72	0-24	BFX30	0-35	TIP3055	0-55
2N3702	0-23	2N6123	0-43	BC158	0-14	BD115	0-80	BFX84	0-35	TIS43	0-43

INTEGRATED CIRCUITS

CA3020	2-00	LM1800	1-76	TAA570	2-30
CA3028	2-29	LM1808	1-92	TAA611B	1-85
CA3028B	1-29	LM1828	1-75	TAA621	2-15
CA3028A	1-01	LM3301N	0-85	TAA651A	1-50
CA3030	1-35	LM3302N	1-40	TAA661B	1-50
CA3034	1-40	LM3901	0-70	TAA700	3-91
CA3046	0-89	LM3905	0-60	TAA930A	1-30
CA3048	2-23	LM3909	0-68	TAD100	1-30
CA3049	1-80	LM3035	1-75	TBA120	0-75
CA3051	2-42	MC1303	1-03	TBA120	0-75
CA3052	1-62	MC1304	1-40	TBA500	2-21
CA3080	0-75	MC1305	1-40	TBA500Q	2-30
CA3080A	1-88	MC1310	1-91	TBA510	2-21
CA3086	0-80	MC1327	1-54	TBA510Q	2-21
CA3088	1-70	MC1330	1-00	TBA520	2-21
CA3089	0-53	MC1350	1-90	TBA520Q	2-21
CA3090	4-00	MC1351	2-20	TBA530	1-98
CA3130	0-98	MC1352	1-10	TBA530Q	2-07
LM301A	0-67	MC1458	1-91	TBA540	2-21
LM301N	0-40	NE555	0-40	TBA540Q	2-30
LM304	2-45	NE556	1-10	TBA540Q	2-30
LM307N	0-65	NE557	1-65	TBA550	3-13
LM308C	0-82	NE556	1-65	TBA560	3-22
LM308N	0-85	NE567	1-80	TBA570	1-29
LM309K	1-85	SAS560	2-50	TBA570Q	1-38
LM317K	3-00	SAS570	2-50	TBA61B	2-70
LM318N	2-26	S042P	1-25	TBA651	2-20
LM323K	6-46	76011N	1-30	TBA700	1-62
LM339N	1-40	76013N	1-50	TBA700Q	1-51
LM348N	1-50	76008K	1-50	TBA720Q	2-30
LM360N	2-75	76013N	1-50	TBA750	1-98
LM370N	2-50	76013ND	1-50	TBA750Q	2-07
LM371N	1-70	76018K	1-50	TBA800	1-25
LM372N	1-70	76023N	1-45	TBA810	1-25
LM373N	2-80	76023ND	1-26	TBA820	1-25
LM374N	3-00	76033N	2-20	TBA920	2-90
LM377N	1-75	76110N	1-18	TBA920Q	2-99
LM378N	2-25	76115N	1-51	TBA940	1-62
LM379S	3-95	76116N	1-66	TCA160B	1-61
LM380B	0-90	76120N	1-56	TCA160C	1-85
LM380N	0-98	76225N	1-56	TCA270	2-25
LM381A	2-45	76227N	1-40	TCA280A	1-30
LM381N	1-60	76228N	1-21	TCA290A	3-13
LM382N	1-25	76530N	0-75	TCA420A	1-84
LM384N	1-45	76532N	1-40	TCA730	3-22
LM386N	0-80	76533N	1-65	TCA740	2-76
LM387N	0-85	76534N	1-44	TCA750	2-30
LM389N	1-00	76546N	1-44	TCA760	1-38
LM702C	0-75	76550N	0-35	TCA800	3-13
LM709C	0-65	76552N	0-95	UA170	2-00
LM709N	0-65	76570N	0-50	UA180	2-00
LM710C	0-50	76520N	0-60		
LM714N	0-40	76550N	0-60		
LM741-8	4-00	76650N	1-10		
LM742-8	4-00	76660N	1-60		
LM747N	0-90	TAA522	1-90		
LM748-8	0-55	TAA520	1-60		
LM748N	0-55	TAA560	0-75		

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2	1	3.41	0.78
18	4	2	4.03	0.96
70	6	3	5.35	0.96
108	8	4	6.98	1.14
72	10	5	7.67	1.14
116	12	6	8.99	1.32
17	16	8	10.39	1.32
115	20	10	13.18	2.08
187	30	15	17.85	2.08
226	60	30	26.82	0A

30 VOLT RANGE

Prim 220/240V Sec 0-12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30, 36, 48, 60V or 24-0-24V or 30-0-30V

Ref	Amps	£	P & P
112	0.5	2.44	0.78
79	1.0	3.57	0.96
3	2.0	5.27	0.96
20	3.0	6.20	1.14
21	4.0	7.60	1.14
51	5.0	8.37	1.32
117	6.0	9.92	1.45
88	8.0	11.73	1.64
89	10.0	13.33	1.84

60 VOLT RANGE

Prim 220/240V Sec 0-24-30-40-48-60V
Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24-0-24V or 30-0-30V

Ref	Amps	£	P & P
124	0.5	3.88	0.96
126	1.0	5.58	0.96
121	2.0	7.60	1.14
125	3.0	10.54	1.32
123	4.0	12.23	1.84
40	5.0	13.95	1.64
120	6.0	15.66	1.84
121	8.0	20.15	0A
122	10.0	24.83	0A
189	12.0	27.13	0A

50 VOLT RANGE

Prim 220/240V Sec 0-20-25-33-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40, 25-0-25 or 20-0-20V

Ref	Amps	£	P & P
102	0.5	3.41	0.78
103	1.0	4.57	0.96
104	2.0	6.98	1.14
105	3.0	8.45	1.32
106	4.0	10.60	1.50
107	6.0	14.62	1.64
118	8.0	17.85	2.08
119	10.0	21.70	0A

MAINS ISOLATING (SCREENED)

PRIM 120/240 SEC 120/240 CT

Ref	VA (Watts)	£	P & P
07*	20	4.40	0.79
149	60	6.20	0.96
150	100	7.13	1.14
151	200	11.16	1.50
152	250	12.79	1.84
153	350	16.28	1.84
154	500	19.15	2.15
155	750	29.06	0A
156	1000	37.20	0A
157	1500	45.60	0A
158	2000	54.80	0A
159	3000	71.05	0A

*This model 115 or 240V only.

HIGH VOLTAGE MAINS ISOLATING

Prim 200/220V or 400/440V
Sec 100/120V or 200/240V

Ref	Va	£	P & P
60	243	5.89	1.32
350	247	14.11	1.84
1000	250	35.65	0A
2000	252	54.25	0A

30 VOLT RANGE

Prim 220/240V Sec 0-12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30, 36, 48, 60V or 24-0-24V or 30-0-30V

Ref	Amps	£	P & P
124	0.5	3.88	0.96
126	1.0	5.58	0.96
121	2.0	7.60	1.14
125	3.0	10.54	1.32
123	4.0	12.23	1.84
40	5.0	13.95	1.64
120	6.0	15.66	1.84
121	8.0	20.15	0A
122	10.0	24.83	0A
189	12.0	27.13	0A

AUTO TRANSFORMERS

240V cable in & 115V USA 2 pin outlet

Ref	VA (Watts) Volts	£	P & P
113	15 0-115-210-240	2.48	0.71
64	75 0-115-210-240	3.95	0.96
4	150 0-115-200-220-240	5.35	0.96
67	500 0-115-200-220-240	10.99	1.64
84	1000 0-115-200-220-240	18.76	2.08
93	1500 0-115-200-220-240	23.36	0A
95	2000 0-115-200-220-240	34.82	0A
73	3000 0-115-200-220-240	48.00	0A

CASED AUTO TRANSFORMERS

240V cable in & 115V USA 2 pin outlet

Ref	VA (Watts) Volts	£	P & P
15	4 96	0.96	113W
150	150	1.14	4W
200	9 92	1.45	65W
250	10 49	1.45	69W
350	12 53	1.64	53W
500	15 73	1.64	67W
750	18 55	1.76	83W
1000	22 88	0A	84W
1500VA	26 02	0A	93W
2000	37 65	0A	95W

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	1.99	0.55
212	1A, 1A	0-6, 0-6	2.85	0.78
13	100	9-0-9	2.14	0.38
203	330, 330	0-9, 0-9	1.99	0.38
207	500, 500	0-8.9, 0-8.9	2.59	0.71
208	1A, 1A	0-8.9, 0-8.9	3.53	0.78
236	200, 200	0-15, 0-15	1.99	0.38
214	300, 300	0-20, 0-20	2.56	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-15-20	4.63	0.96
203	500, 500	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	5.38	0.96
S112	500	12-15-20-24-30	2.64	0.78
239	50	12-0-12	1.99	0.38

TEST METERS

AVO 8 MK5	£71.00
AVO 71	£28.00
AVO 73	£39.10
AVO MMS	£24.00
AVO TT169 In circuit Transistor Tester	£30.00
U4315 Budget Meter 20kΩ/VDC 2kVAC 1000V AC/DC 2.5A AC/DC 500k res. in.	£14.95
Robust steel case & lead	£14.95
VAT 8% P & P E1.15.	
AVO cases and accessories.	
See Megger	£58.80

BRIDGE RECTIFIERS

200V	2A	£0.45
400V	2A	£0.55
200V	4A	£0.65
400V	4A	£0.80
400V	6A	£1.05
500V	10A	£2.35
VAT 12½% VAT 8% 15p P & P		

Audio Kit 25W - 25W. Complete with instructions £27.55. Teak cabinet mounting hardware £9.20. P & P £1.73 VAT 12½%

Magnetic to Ceramic Cartridge Converter operating voltages 20-45V only £3.50. VAT 12½% P & P 35p

PLUS

HIGH QUALITY MODULES	£3.66
10 WATT RMS AMPLIFIER	£4.57
25 WATT RMS AMPLIFIER	£6.95
35 WATT RMS AMPLIFIER	£15.95
125 WATT RMS AMPLIFIER	£6.70
PRE-AMP for 5-10 WATT	£13.88
POWER SUPPLIES 5-10 WATT	£1.30
POWER SUPPLIES 25 WATT	£3.75
TRANSFORMER 5-10 WATT	£3.09
*TRANSFORMER 25 WATT	£4.79
P & P Modules 35p. Trans. 96p. VAT 12½%	

STEREO 30 - Complete chassis in 7.7W rms amp, pre amp, power supply front panel knobs. (Need Trans.) £19.05. Trans. £3.57. Teak cabinet. £25. P & P £1.02. VAT 12½%

BLOB BOARD (Pack of 3)
2 5" x 5 1/2" or 2 5/8" x 5 1/2" 15" £0.75
3 7/8" x 5 1/2" or 3 7/8" x 5 1/2" 15" £1.14
10" x 6 1/8" or 10" x 6 1/8" 15" £3.78

IC Range
4 8" x 3 2" £0.96. 4 7 5/8" x 7 5/8" £2.13
P & P 35p. VAT 8%

ELECTRONIC CONSTRUCTION KIT
10 projects (including electronic organ). No soldering needed £7.29. VAT 8% P & P 40p

COMPONENT PACKS
200 Mixed value resistors (count by weight)
150 Mixed value capacitors (count by weight)
30 Mixed value precision resistors 1W 2%

15 Assorted pots
10 Reed switches
15 Wire wound resistors—mixed wattage
1 Pack wire 50 metres assorted colours
25 Pre-sorted assorted types and values
Please state pack required.
60p per pack. VAT 12½% P & P 40p

Prices correct 7/11/77. Please add VAT after P & P. PE1

MUSIC CENTRE CHASSIS

FM (STEREO) MW LW 15 - 15W
Music Power Inc Tran
Price £22.50 inc VAT P & P £1.50
VAT 8%

BATTERY ELIMINATORS

"Save on Batteries"
Stabilised 3-6-7-9V/400mA
multiplug outlet £5.95
3000 rls into 13A socket 6-7-9V
300mA multiplug outlet. £3.30
812: 3, 4, 5, 6, 7.5, 9, 12V 500mA
DC plug outlet £6.32
VAT 12½% P & P 55p

DECS SOLDERLESS BREAD-BOARDING

S Dec 70 contacts £1.98
T Dec 208 contacts £3.63
U Dec "A" for I.C.s etc £3.99
U Dec "B" for I.C.s etc £6.99
VAT 8% P & P 40p

ANTEX SOLDERING IRONS

15W £3.75 18W £3.75
25W £3.40 Stand £1.40
P & P 46p VAT 8%

MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA
Res-150kΩ 1000Ω/V Bargain £5.86
P & P 62p VAT 8%

STEREO FM TUNER WITH PHASE-LOCK LOOP

4 Pre-selected stations, varicap tuning, switched AFC, LED Beacon £20.45
VAT 12½% P & P 40p.

TRANSFORMERS SPECIAL OFFER (Limited Stocks)

BE1 Prim 0-120-0-120V (120 or 240V) Sec 24V 10A	£5.50	P & P £1.66
BE2 Prim 0-90-110-200-220-240V Sec 0-110V 0-20-24V. 2A £2.25 P & P 96p. VAT 8%		
BE3 100V line to 4Ω 7/10W £2.05 P & P 66p		
BE4 SCREENED 0-120 x 0-120-0-9 1A £2.40 P & P 71p		
BE5 15W matching trans sec 150V suit 5L89 £1.50 P & P 50p		
BE6 PR1 0-220V sec 4500V 10 MA £4.50 P & P £1.00		
Ref 30 240-240 Isolators 200VA £4.20 P & P 96p		
Ref 62 240-240 Isolators 250VA £5.20 P & P 96p		

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

ORCHARD ELECTRONICS

Flint House, St. Martins Street, Wallingford, Oxon (Tel. 0491 35529)


SERVICE SECOND TO NONE
TRY US AND SEE
NEW BIG CAT 50p+ Refundable Vouchers

SUPPLIERS TO D.O.E., A.E.R.E., U.K.A.E.A.
Government Depts., Universities, Schools and equipment manufacturers.
Stock list FREE with S.A.E.
Post & Packing 25p. Discounts £5=5%, £10=7½%, £15=10%. VAT * add 12½%. Rest at 8%

TRANSISTORS

AA119	0-08	BC178B	0-18	BF167	0-21	OC71	0-35	2N3703	0-14*
AC125	0-25	BC179B	0-18	BF173	0-24	OC72	0-45	2N3704	0-13*
AC126	0-28	BC182B	0-18*	BF179	0-24	OC74	0-45	2N3705	0-14*
AC127	0-28	BC182B	0-18*	BF179	0-24	OC81	0-50	2N3707	0-14*
AC128	0-20	BC183B	0-10*	BF183	0-34	OC82	0-70	2N3708	0-12*
AC151	0-35	BC183L	0-10*	BF184	0-25	ORP12	0-68	2N3709	0-14*
AC153	0-35	BC184B	0-12*	BF185	0-28	TIP29A	0-47*	2N3710	0-11*
AC176	0-22	BC184L	0-11*	BF194	0-10*	TIP30A	0-58*	2N3711	0-11*
AC178	0-22	BC185	0-23	BF195	0-10*	TIP31A	0-57	2N3819E	0-25*
AC188	0-20	BC187	0-26	BF196	0-12*	TIP32A	0-47	2N3820	0-45*
AC187/188		BC204A	0-16*	BF197	0-12*	TIP33A	0-84	2N3823E	0-25*
AD149	0-68	BC204B	0-16*	BF199	0-15*	TIP34A	1-13	2N4036	0-40
AD161	0-52	BC212A	0-13*	BF200	0-38	TIP41A	0-67	2N4058	0-18*
AD182	0-52	BC212L	0-15*	BFX29	0-20	TIP42A	0-80	2N4059	0-10*
BC107	0-11	BC213B	0-12*	BFX30	0-25	TIP295S	0-87	2N4061	0-12*
BC107A	0-12	BC213L	0-14*	BFX40	0-28	TIP305S	0-60	2N4124	0-20*
BC107B	0-13	BC214	0-15*	BFX88	0-22	TIS43	0-35*	2N4126	0-30*
BC108	0-16	BC214A	0-17*	BFY50	0-25	ZTX109	0-14*	2N5298	0-50*
BC108/08		BC237A	0-16*	BFY51	0-25	ZTX300	0-13*	2N5457	0-50*
BC108B	0-11	BC300	0-35	BFY52	0-25	ZTX301	0-13*	2N5458	0-40*
BC108C	0-12	BC301	0-34	ME040	0-18*	ZTX302	0-18*	2N5459	0-40*
BC109	0-12	BC303	0-35	ME041	0-18*				

SAVE POUNDS

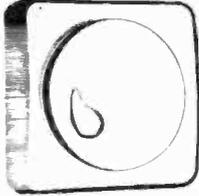

WITH THIS UNBEATABLE OFFER
from Britain's Largest Dimmer Makers

Complete Kit of Parts for our VCL500M, 500W Dimmer Switch, only £1.85, plus p&p 25p. (inc. Vat.) Full Instructions supplied.

BARGAIN COMPONENTS

ELECTROLYTIC CAPACITORS

470 MFD - 6.3V	15p.	1000 MFD - 16V	30p.
150 MFD - 6.3V	17p.	330 MFD - 63V	29p.
470 MFD - 10V	18p.	68 MFD - 6.3V	12p.

POLYESTER CAPACITORS

0.01 MFD - 400V 9p.

THYRISTORS

C106.01 70p. 41 RCS60 £4.50

B.L. 12-WAY TERMINAL BLOCK

P.C.B. MOUNTING 39p.

POTENTIOMETERS

Pre-set 1MΩ Linear	11p.	Pre-set 4.7KΩ Linear	12p.
Pre-set 220KΩ Linear	11p.	Pre-set 25KΩ Linear	19p.
A. B. 2 Gang 25 + 25KΩ	82p.	A. B. 1 Gang 220KΩ	26p.

All prices include VAT. Postage & packing included on all orders over 50p. Under 50p. please add postage. For quick delivery please send cheque or P/O to: — Dept. PE1.

Stirling Sound

OUR UNIQUE BARGAIN PLAN CLOSES JAN. 31st


STIRLING POLICY means specs. and prices you can rely on — no hidden extras — nothing to misunderstand. Until Jan. 31st, when ordering a power amp. and power supply unit together.

DEDUCT	<i>If ordered with</i>	DEDUCT A FURTHER	<i>If ordered with</i>	DEDUCT A FURTHER
5%	UNIT ONE	£1	UNIT TWO	£1.18

AMPLIFIERS 3 to 100 WATTS R.M.S.

Ready assembled on P.C.B.s., tested and guaranteed. Easy to connect. With instructions. Output ratings ± 1db.

SS.103 i.c. amp. 3 watts R.M.S. using 20V/80 or 14V/40. Input 100mV	£2.85
SS.103-3 Stereo version of above, 2 i.c.s	£5.00
SS.105 5 watts R.M.S. into 3Ω using 13.5V. Sensitivity — 30mV. THD — 0.3%. 3½" x 2" x 1"	£3.95
SS.110 10 watts R.M.S. into 4Ω using 24V. Sensitivity — 60mV. THD — 0.3%. 3½" x 2" x 1"	£4.65
SS.120 20 watts R.M.S. into 4Ω using 34V. Sensitivity — 80mV. THD — 0.3%. 3½" x 2" x 1"	£5.15
SS.125 25 watts R.M.S. into 8Ω using 50V. Sensitivity — 140mV. Distortion — Less than 0.05% into 8Ω 5/N better than 70db	£7.25
SS.140 40 watts R.M.S. into 4Ω using 45V. Sensitivity — 300mV. Distortion typically 0.1%. 5" x 3½" x 1½"	£6.50

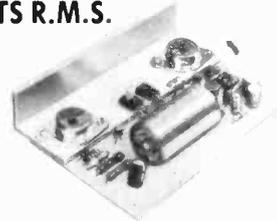

SS.160 64 watts R.M.S. into 4Ω using 50V. Sensitivity — 350mV. Distortion typically 0.1%. 5" x 3½" x 1½"	£8.50
SS.1100 100 watts R.M.S. into 4Ω using 70V/2A. Input sensitivity — 500mV. Distortion at half-power, typically 0.1%. 5" x 3½" x 1½"	£10.50
MS.160 Multi-finned heatsink for SS.140 or SS.160.	75p
MS.1100 Dimo for SS.1100	£1.50

THE CONTROL AND PRE-AMP MODULES

UNIT ONE

Combined stereo pre-amp and active tone control unit. Input sensitivity 50mV for 200mV out, 10 16V operation. Bass + 15db at 30Hz; Treble + 15db of 10KHz; Balance control; Volume control. For ceramic P.U., radio or tape inputs. WITH FREE CONTROL PANEL FASCIA

£9.00

UNIT TWO

With control facilities similar to UNIT ONE but for magnetic cartridge input. R.I.A.A. corrected. Input sensitivity — 5mV for 200mV out (can be varied). WITH FREE CONTROL PANEL FASCIA


£12.43

■ CONTROL PANEL FASCIA available separately 50p

■ SS.100

Basic active stereo tone control module to provide ± 15db on bass or 30Hz and on treble at 10KHz


£3.00

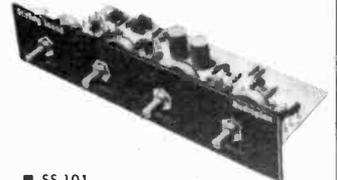

■ SS.101	Stereo pre-amp suitable for ceramics, tape, radio, etc.	£2.75
■ SS.102	Stereo pre-amp for mag. pick ups. R.I.A.A. corrected	£4.45
■ F.M. STEREO DECODER	phase lock loop type, with LED indicator showing when stereo transmission is being received.	£5.25

POWER SUPPLY UNITS

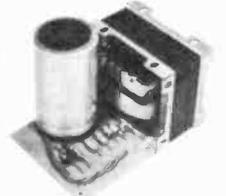Every Stirling Sound Power Unit is tested and guaranteed under working conditions before despatch. All units except SS.312 include a stabilised low voltage take-off point (13-15V) for pre-amp, tone control, radio tuner, etc. Outputs quoted minimal unloaded ratings.



SS.312	12V/1A	£6.60
SS.318	18V/1A	£6.95
SS.324	24V/1A	£7.65
SS.334	34V/2A	£8.75
SS.345	45V/2A	£10.75
SS.350	50V/2A	£11.75
SS.360	60V/2A	£12.75
SS.370	70V/2A	£14.75

SS.310/50 Stabilised power supply with variable output 10V to 50V/2A. Short circuit protected. £17.75
SS.300 Add-on power stabilising unit variable from 10 to 50V/8A £5.50

ALL GOODS POST FREE IN U.K. ALL PRICES INCLUDE VAT

Prices subject to alteration without notice. Order to Dept. PE28A.

STIRLING SOUND, 37 VANGUARD WAY, SHOEBOURNESS ESSEX

Phone (03708) 5543

Shop & Showroom 220/224 West Rd., Westcliff-on-Sea. Phone Southend

(0702) 351048

ACCESS OR BARCLAYCARD CUSTOMERS — JUST TELL US YOUR NUMBER

STIRLING SOUND, 37 VANGUARD WAY, SHOEBOURNESS, ESSEX

Please send.....

(or as attached list) for which I enclose £.....

NAME.....

ADDRESS.....

PE28A

Fotherby, Willis Electronics Ltd.

GLADSTONE TERRACE, STANNINGLEY, LEEDS, LS28 6NE.
Telephone: Leeds (STD 0532) 563373 Telex: 557111

24 HR. CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1kW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display/drivers, switches, LEDs, trac, complete with PCBs and full instructions. £14.85
Special white box (56 x 131 x 71mm) with red Acrylic window — undrilled £2.38
drilled £2.70

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated touch plates. Complete with easy to follow instructions.

TS300K — TOUCHSWITCH and DIMER combined. ONE touchplate to switch light on or off. Brightness controlled by small knob. £5.62

TS300K — TOUCHSWITCH. TWO touch plates. One for ON one for OFF. £4.32

TSA300K — AUTOMATIC TOUCHSWITCH. ONE touch plate. Touch for ON and light stays on for preset time (variable from 2 secs. to 3½ mins.). Ideal for stairs and hall. £4.32

LD300K — 300W LIGHT DIMMER KIT. Replaces conventional light switches. £3.02

AY-5-1230 Clock/Appliance Timer I.C. £5.24

LM3911 Thermometer/Temperature Control IC (with data) £1.08

NE555 Timer I.C. 8 pin dil 39p (3 for £1.08)

741 Op. Amp. I.C. 8 pin dil 26p (5 for £1.08)

BC147 9p BFY50 16p 2N6027 PUT 37p

BC148 9p 2N3055 43p TIS43 UJT 26p

BC158 11p TIP31A 54p 1N4148 5p

BC182L 9p TIP32 54p 1N4004 5p

CMOS LOW PRICES

4000 19p 4012 19p 4023 19p 4077 49p

4001 19p 4013 55p 4025 19p 4501 22p

4002 19p 4015 98p 4040 105p 4510 162p

4007 19p 4016 55p 4049 54p 4516 162p

4011 19p 4017 98p 4050 54p 4519 61p

TRIAC BARGAINS

400V Plastic **isolated tob

3A 68p

6.5A with trigger** 85p

8.5A** 85p

12A 91p

16A 112p

20A 178p

25A 192p

DIAC 23p

C106D 5A/400V 54p

MINI MAINS TRANSFORMERS

6-0.6V 100mA 92p

12-0.12V 100mA 103p

OPTO ELECTRONICS

0.2" Red LED 11p

0.2" Green LED 23p

0.2" Yellow LED 27p

DL727 Dual 0.5" Display £1.62

C280 Polyester Capacitors 250V d.c. (values in µF)

01 5p; 022, 033, 047, 0.68 6p; 01 7p; .5 8p; .22 9p;

33 12p; 47 13p; 68 19p; 1.0 22p; 2.2 39p.

RESISTORS. 33W 5% 22 ohm to 10M ohm

Push Button, push to make 2p

23p

QUANTITY DISCOUNTS ON REQUEST

PRICES VAT INCLUSIVE. ADD 25p P&P. MAIL ORDER ONLY TO:

T. K. ELECTRONICS

106 STUDLEY GRANGE ROAD, LONDON, W7 2LX.

RST

VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS
MAIL ORDER SERVICE**

Ep	Ep	Ep	Ep	Ep	Ep	Ep			
AA119	0-20	BCY71	0-22	*MPSU01	0-32	*ZTX550	0-16	7403	Ep
AAV30	0-13	BCY72	0-17	*MPSU08	0-40	1N914	0-07	7404	0-26
AAV32	0-13	BCZ11	1-50	*MPSU56	0-45	1N916	0-07	7405	0-26
AZ13	0-25	BD115	0-60	NKT401	2-00	1N4001	0-06	7406	0-55
AAZ15	0-31	BD121	1-50	NKT403	1-73	1N4002	0-07	7407	0-55
AAZ17	0-25	BD123	1-50	NKT404	1-73	1N4003	0-08	7408	0-28
AC107	0-75	BD124	1-00	NE555	0-45	1N4004	0-09	7409	0-28
AC125	0-30	BD131	0-51	OA5	0-75	1N4005	0-13	7410	0-20
AC126	0-25	BD132	0-54	OA7	0-55	1N4006	0-15	7412	0-26
AC127	0-25	*BD135	0-35	OA10	0-55	1N4007	0-15	7413	0-45
AC128	0-25	*BD136	0-36	OA47	0-14	1N4009	0-15	7416	0-40
AC141	0-20	*BD137	0-37	OA70	0-30	1N4148	0-07	7417	0-40
AC141K	0-30	*BD138	0-40	OA79	0-30	1N5400	0-14	7420	0-20
AC142	0-20	*BD139	0-43	OA81	0-30	1N5401	0-16	7422	0-25
AC142K	0-25	BD144	2-00	OA85	0-30	1S44	0-06	7423	0-35
AC176	0-25	BD144	2-00	OA90	0-00	1S920	0-08	7425	0-35
AC187	0-25	BD181	1-38	OA91	0-00	1S921	0-08	7427	0-35
AC188	0-25	BD182	1-48	OA95	0-08	2G301	1-00	7428	0-50
ACY17	0-65	BD237	0-80	OA200	0-10	2G302	1-00	7430	0-20
ACY18	0-65	BD238	0-80	OA202	0-11	2G306	1-10	7432	0-36
ACY19	0-65	BDX10	0-75	OA210	0-75	2N404	0-60	7433	0-37
ACY20	0-65	BDX32	2-25	OA211	0-75	2N696	0-25	7437	0-42
ACY21	0-65	BDY20	1-42	OA2200	0-65	2N697	0-16	7438	0-37
ADY39	1-25	BDY60	0-75	OA2201	0-65	2N698	0-30	7440	0-22
AD149	0-70	BF115	0-39	OA2206	0-65	2N705	0-90	7441AN	0-92
AD161	0-75	BF152	0-25	OA2207	0-65	2N706	0-12	7442	0-78
AD162	0-75	BF153	0-25	OC16	1-25	2N708	0-21	7447AN	1-20
AF106	0-46	BF255	0-45	OC20	2-00	2N930	0-20	7450	0-20
AF114	0-25	BF159	0-35	OC22	2-50	2N1131	0-26	7451	0-20
AF115	0-25	BF160	0-30	OC23	2-75	2N1132	0-26	7453	0-20
AF116	0-25	BF167	0-39	OC24	3-50	2N1302	0-37	7454	0-20
AF117	0-25	BF173	0-39	OC25	0-90	2N1303	0-37	7460	0-20
AF139	0-40	BF177	0-38	OC26	0-90	2N1304	0-45	7470	0-35
AF186	1-50	BF178	0-48	OC28	2-00	2N1305	0-45	7472	0-36
AF239	0-45	BF179	0-48	OC29	2-00	2N1306	0-50	7473	0-36
AFZ11	2-75	BF180	0-45	OC35	1-50	2N1307	0-50	7474	0-40
AFZ12	2-75	BF181	0-45	OC36	1-50	2N1308	0-60	7475	0-59
ASV26	0-45	BF182	0-45	OC41	0-50	2N1309	0-60	7476	0-42
ASV27	0-50	BF183	0-45	OC42	0-50	2N1613	0-33	7480	0-60
ASZ15	1-25	BF184	0-38	OC43	1-50	2N1671	1-50	7482	0-85
ASZ16	1-25	BF185	0-37	OC44	0-50	2N1893	0-33	7483	1-00
ASZ17	1-25	*BF194	0-12	OC45	0-50	2N2147	1-40	7484	1-00
ASZ20	0-75	*BF195	0-11	OC71	0-45	2N2148	1-65	7486	0-40
ASZ21	1-50	*BF196	0-13	OC72	0-45	2N2218	0-33	7490	0-52
AU113	1-70	BF200	0-32	OC73	1-00	2N2219	0-42	7491AN	0-85
AU110	1-10	BF200	0-32	OC74	0-75	2N2220	0-35	7492	0-60
BA145	0-15	*BF224	0-20	OC75	0-60	2N2221	0-22	7493	0-70
BA146	0-15	*BF244	0-35	OC76	0-50	2N2222	0-25	7494	0-80
BA154	0-10	BF257	0-37	OC77	1-20	2N2223	2-75	7495	0-80
BA155	0-12	BF258	0-42	OC81	0-75	2N2368	0-17	7496	0-60
BA156	0-13	BF259	0-45	OC81Z	1-00	2N2369A	0-21	7497	0-87
BAW62	0-85	*BF336	0-50	OC82	0-75	2N2484	0-21	74100	1-75
BAX13	0-07	*BF337	0-53	OC83	0-55	2N2646	0-50	74107	0-45
BAX16	0-07	*BF338	0-55	OC84	0-60	2N2904	0-35	74109	0-86
BC107	0-12	BFS21	2-27	OC122	1-50	2N2905	0-35	74110	0-57
BC108	0-12	BFS28	1-38	OC123	1-50	2N2906	0-25	74111	0-86
BC109	0-10	*BFS61	0-25	OC130	2-25	2N2907	0-21	74116	1-89
*BC113	0-15	*BFS98	0-25	OC140	1-85	*2N2924	0-15	74118	0-85
*BC114	0-18	BFW10	0-90	OC141	2-25	*2N2925	0-17	74119	2-00
*BC115	0-18	BFW11	0-90	OC170	0-75	*2N2926	0-13	74120	1-10
*BC116	0-18	BFX84	0-38	OC171	0-75	2N3053	0-25	74121	0-45
*BC117	0-22	BFX85	0-41	OC200	1-00	2N3054	0-50	74122	0-60
*BC118	0-18	BFX87	0-32	OC201	1-50	2N3055	0-65	74123	1-00
*BC125	0-18	BFX88	0-32	OC202	1-25	2N3440	0-25	74125	0-90
*BC126	0-25	BFY50	0-28	OC203	1-25	2N3441	0-60	74126	0-80
*BC135	0-15	BFY51	0-26	OC204	1-25	2N3442	1-20	74128	0-80
*BC136	0-19	BFY52	0-26	OC205	1-75	2N3525	0-90	74132	0-80
*BC137	0-16	BFY64	0-30	OC206	1-75	2N3614	1-20	74136	0-68
*BC147	0-10	BFY90	0-32	OC207	1-25	*2N3702	0-15	74141	0-85
*BC148	0-10	BSX19	0-34	OC211	1-25	*2N3703	0-15	74142	0-90
*BC149	0-13	BSX20	0-34	ORP12	0-63	*2N3704	0-15	74143	3-00
*BC157	0-12	BSX21	0-32	*R2008B	2-25	*2N3705	0-15	74144	3-00
*BC158	0-11	BT106	1-25	*R2009	2-25	*2N3706	0-14	74145	1-00
*BC159	0-13	BT178/400R	3-19	*R2010B	2-25	*2N3707	0-18	74147	2-45
*BC167	0-07	*BU205	2-25	T1C4	0-38	*2N3708	0-15	74148	2-00
*BC170	0-16	*BU206	2-25	T1C226D	1-30	*2N3709	0-14	74150	1-75
*BC171	0-14	*BU208	2-50	T1L209	0-25	*2N3710	0-14	74151	0-90
*BC172	0-13	BY100	0-45	*T1P29A	0-50	*2N3711	0-15	74154	2-00
*BC173	0-15	BY126	0-14	*T1P30A	0-60	2N3771	1-80	74155	0-90
*BC177	0-18	BY127	0-15	T1P31A	0-62	2N3772	1-70	74156	0-80
*BC178	0-18	BZK61	0-20	T1P32A	0-75	2N3773	2-65	74157	0-90
BC179	0-20	Series		T1P33A	1-00	*2N3819	0-36	74159	2-50
*BC182	0-11	BZY88	0-13	T1P34A	1-20	*2N3820	0-46	74170	0-80
*BC183	0-11	Series		T1P41A	0-70	*2N3823	0-60	74172	5-00
*BC184	0-12	CRS1/05	0-45	T1P42A	0-90	2N3866	1-00	74173	1-75
*BC212	0-14	CRS1/40	0-60	T1P2955	1-00	*2N3904	0-21	74174	1-57
*BC213	0-14	CRS3/05	0-45	T1P3055	0-50	*2N3905	0-22	74175	1-00
*BC214	0-17	CRS3/40	0-75	*T1S43	0-35	*2N3906	0-22	74176	1-10
*BC237	0-17	CRS3/60	0-90	*ZS140	0-25	*2N4058	0-20	74178	1-85
*BC238	0-12	GEX66	1-50	*ZS170	0-12	*2N4059	0-15	74179	1-85
BC301	0-45	GEX541	1-75	*ZS178	0-54	*2N4060	0-20	74180	1-85
BC303	0-60	GJSM	0-75	*ZS271	0-22	*2N4061	0-17	74181	1-48
*BC307	0-18	GJSM	0-75	*ZS278	0-58	*2S278	0-18	74181	1-48
*BC308	0-18	GMO378A	1-90	*ZTX107	0-11	*2N4124	0-17	74192	1-25
*BC327	0-22	*KS100A	0-50	*ZTX108	0-10	*2N4126	0-17	74193	1-25
*BC328	0-18	MJE340	0-59	*ZTX109	0-12	*2N4286	0-20	74194	1-25
*BC337	0-19	MJE370	0-65	*ZTX300	0-12	*2N4288	0-25	74195	1-10
*BC338	0-18	MJE371	0-65	*ZTX301	0-13	*2N4289	0-25	74196	1-20
BCY30	1-00	MJE520	0-65	*ZTX302	0-17	*2N5457	0-36	74197	1-00
BCY31	1-00	MJE521	0-75	*ZTX303	0-17	*2N5458	0-35	74198	2-25
BCY32	1-00	MJE2955	1-25	*ZTX304	0-18	*2N5459	0-35	74199	2-25
BCY33	0-90	MJE3055	0-75	*ZTX311	0-12	3N125	1-75	*76013N	1-75
BCY34	0-90	*MPF102	0-30	*ZTX314	0-20	3N141	0-85		
BCY39	3-00	*MPF103	0-30	*ZTX314	0-20				
BCY40	1-25	*MPF104	0-30	*ZTX500	0-13				
BCY42	0-30	*MPF105	0-30	*ZTX501	0-14				
BCY43	0-30	*MPF106	0-30	*ZTX502	0-17				
BCY58	0-23	*MPSA08	0-25	*ZTX503	0-18				
BCY59	0-23	*MPSA56	0-25	*ZTX504	0-20				
BCY70	0-18			*ZTX505	0-20				

Do-it-Yourself Kits Or Factory Assembled

- WERSI Organs
- WERSI Pianos
- WERSI String Ensembles
- WERSI MATIC Rhythm
- WERSI MATIC Accompaniment
- WERSI VOICE Rotor Sound String Choir
- WERSI Professional Series
- WERSI Audio Mixer 2004
- WERSI TONE Rotating Baffles
- WERSI Speaker Cabinets

Send for our 104 page full-colour catalogue and 16-page price list, for £2.00, which is refunded against your first order value £25.00.

AURA SOUNDS (P2),
Cophthorne Bank, Crawley, W. Sussex.




**FROM CASIO, OF COURSE
POCKET WATCH, CALCULATOR
TWO WAY TIMER, ALARM**

Ultra slim pocket calculator.
LCD display 6 digit clock.
Daily (10 second) Alarm, Timer
up to 12 hours, or Repeat Timer
(for example, can be set to buzz
every three hours). Calculator
four key memory, percentage,
square roots etc. Battery life
2000 hours plus. Leatherette case.

AQ 810 An incredible £19.95

Fairchild Timeband

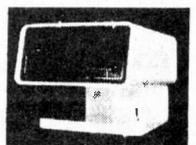

CASIO
21QS-108 (ST, TM) 9.6 mm
£34.95

CASIO
31QR-128 (ST) 8.5 mm thick
£29.95

C500 Alarm
Black or white
£14.35

Superb CASIO LCD watches. Seven functions, Light, Auto Calendar. STOPWATCH (ST) DUAL TIME ZONE (TM). All Stainless steel, Mineral glass, WATER RESISTANT to 100 feet. AVAILABLE JANUARY: CASIO Chronograph £59.95 and £64.95. ALARM watch (ST) £59.95

Send 15p for our illustrated catalogue. Lowest discount prices.
Prices include VAT, P & P. Send cheque, P.O. or phone your credit card number to—

TEMPUS
Dept. P.E.
19/21 Fitzroy Street
Cambridge CB1 1EH
Telephone (0223) 312866

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7
Quotations for any types not listed S.A.E.
Post and Packing 25p per order + 8% V.A.T.
Items marked * 12½%

Prices correct when going to press


CHINAGLIA DINO—ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

PRESENT THE

DOLOMITI

20k Ω /V a.c. and d.c.

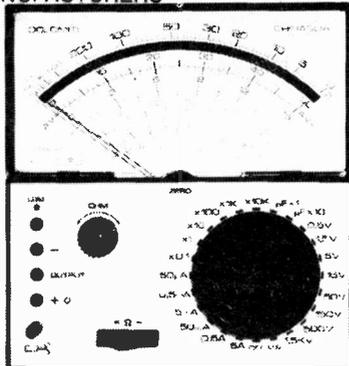A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED



Accuracy: D.C. ranges, $\pm 2.0\%$, A.C. & Ω ranges $\pm 2.5\%$.
39 ranges: d.c. V, 0-150mV, 500mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1-5kV; d.c.I, 0-50 μ A, 500 μ A, 5mA, 50mA, 0-5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1-5kV; a.c.I, 5mA, 50mA, 0-5A, 5A; dB -10 to +65 in 6 ranges; Ω 0-0.05k Ω , 5k Ω , 50k Ω , 500k Ω , 5M Ω , 50M Ω , pF 50kPF, 500kPF.

Automatic overload protection and high current range fusing. Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £45.90 incl. VAT (£1 P. & P.)
 30kV Probe £12.85 incl. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

ALCON Instruments Ltd.

19 MULBERRY WALK. LONDON SW3 6DZ TEL: 01-352 1897

We can help you See and Solve your problems

HONELIGHT

Universal Portable Inspection Light

The shadowless Honelight utilises the principle of optical fibres, in a tube of virtually unbreakable material, insulated, transparent and resistant to alcohol.

It gives all-round illumination to otherwise inaccessible confined spaces and corners. Simple, lightweight and practical (weight with batteries 40 grammes approx.). Suitable for all professions—Electronics, Radio/TV—machines of all types.

Also useful in the realm of Medicine: general and specialised, Dentistry, Veterinary etc.
 (Operates from 2-1.5 volt batteries).



Desoldering Tool "SPECIPROD"

High precision manufacture de-soldering pump. Available three sizes for all de-soldering requirements.

Chromed interior, nickel pump, teflon nozzle.

Three Sizes.

"Maxi Super" length 37cm, nozzle diameter 2mm.


"Maxi Mini" length 22cm, nozzle diameter 1.5 mm.

"Maxi Micro" length 16cm (diameter body 12mm, nozzle diameter 1.5mm).

(The smallest de-soldering pump available).

Literature and general catalogue available on request from:

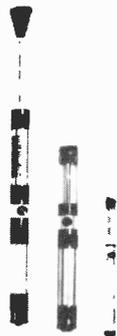Special Products Distributors Limited, 81 Piccadilly, London W1V 0HL
 Tel: 01-629 9556 Cables: Speciprod London W1



TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry. ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work

Also MPT Radio Communications Certificate

Diploma Courses

Colour T.V. Servicing
 Electronic Engineering & Maintenance
 Computer Engineering and Programming
 Radio, T.V. and Audio, Engineering & Servicing
 Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. 273M, Intertext House, London SW8 4UJ
 or telephone 01-622 9911 (all hours)

All you need for listening!



Listen with the complete hi-fi magazine

PRACTICAL HI-FI & AUDIO

Every month 40p

50 ASSORTED TANTALUM BEAD CAPACITORS for £1.50.
 12 BRANDED F.E.T's Assorted @ £1.
 DIE CAST ALLOY BOXES sizes 4" x 2" x 1" @ 65p, 4 1/2" x 2 1/2" x 1 1/2" @ 65p.
 4 1/2" x 2 1/2" x 1 1/2" @ 85p, 6" x 3 1/2" x 2" @ £1.15.
 1N4148 SILICON DIODES 20 for 50p.
 AUDIO I.C's TAA611B @ 65p, SN 76001N @ 50p, SL 414 @ £1.60.
 VERNITRON 10.7 MHz CERAMIC FILTERS @ 50p.
 TBA 1205 FM I.C's Untested with data @ 6 for 60p.
 50 VARI-CAP DIODES Assorted Untested for 57p.
 BOOKS. By G. Dobbs. "Practical Test Equipment" @ 75p, "Simple Transistor Short Wave Receiver" @ 60p, "Practical Electronic Projects" @ 75p. The Three Books for £1.60.
 STANDARD 2 AMP TV CHOKES @ 10p, 6 for 50p.
 MINIATURE 8uf 300v.w. ELECTROLYTICS @ 10 for 57p.
 SWITCHED STEREO SOCKETS @ 4 for 60p.
 2 GHz NPN STRIPLINE TRANSISTORS @ £1 each.
 10 AMP 2 POLE MAKE TOGGLE SWITCHES @ 40p each.
 POSTAGE STAMP TRIMMERS 10pf, 30pf, 50pf, 1000pf. All @ 6p each.
 100 ASSORTED DISC CERAMICS for 57p.
 200 ASSORTED 1/2, 1/4 watt RESISTORS for 75p.
 50 ASSORTED PLASTIC BC 107-8-9 TRANSISTORS 85% Good @ 57p.
 5 WATT NPN TO39 DARLINGTON TRANSISTORS @ 20p each.
 10 MULTI TURN TRIMPOTS Assorted Values @ 57p.
 50, AC 128 TRANSISTORS Branded but Untested @ 57p.
 8F 451 SILICON PNP 300 MHz TRANSISTORS @ 6 for 35p.
 LARGE HEAT SINKS suitable for two TO3 Transistors 60p (20p P&P).
 NUT FIXING 1000pf FEEDTHRU's 500v.w. @ 15p each.
 1.2K WIRE WOUND POTENTIOMETERS 6 watt @ 22p.
 5.5MHz CERAMIC FILTERS @ 27p each.
 JACKSON TYPE C804 VARIABLE CAPACITORS 5pf @ 75p.
 IFT TRANSISTORS NPN TYPE TM 11 300 MHz @ 24 for 60p.
 DAU TRIMMERS 2 To 9pf @ 10p, 5 To 38pf @ 10p, 6 To 45pf @ 10p, 8 To 125pf @ 12p, 8 To 140pf @ 15p.
 COIL FORMERS Sub-Miniature 6/8 x 1/2" with core @ 5p, 6 for 25p.
 WIRE ENDED CRYSTALS 28 KHz, 28.5 KHz. Both 50p each.
 UNMARKED GOOD 400mW ZENERS 6.8v, 10v, 11v, 12v, 13v, 16v, 24v, 30v, 33v, 36v. All @ 10 for 40p.
 6 To 1 FRICTION SLOW MOTION DRIVES @ 55p.
 MINIATURE 8uf 300v.w. ELECTROLYTICS @ 10 for 57p.
 12 BRANDED ASSORTED F.E.T's for £1.
 30 ASSORTED 10XAJ CRYSTALS Between 5100 To 7900 KHz @ £1.10.
 SUB-MINIATURE 10 x 10pf DIFFERENTIAL PRE-SET CAPACITORS @ 22p.
 100 MULLARD C280 CAPACITORS Assorted @ 57p.
 TRANSFORMER 240v Input, Output 24v Tapped at 14v 1 amp @ £1.25 (20p P&P).

Please add 20p for post and packing on UK orders under £2, unless otherwise stated. Overseas orders at cost.

J. BIRKETT
RADIO COMPONENT SUPPLIERS
 25 The Strait, Lincoln LN2 1JF
 Tel. 20767.

P.E. JOANNA

ELECTRONIC PIANO



ALL PARTS CAN BE SUPPLIED

Keyboard, Keyswitch, P.C.B.s, Hardware, Semiconductors, Resistors, Capacitors, Cabinets, Complete kits or easy stages
 Send S.A.E. for details

Clef Products
 16 Mayfield Road
 Bramhall, Stockport, Cheshire SK7 1LY

FREE CATALOGUE/ORDER FORM SEND S.A.E.

500+ Top quality Transistors, I.C's, Resistors, Capacitors, Plugs/Sockets, Veroboard/cases, Indicators, Knobs, Switches, Wire and Books at prices you can afford.

741 ONLY 30p

555 ONLY 50p

TIL209 ONLY 15p

IN4001 ONLY 5p

All prices include VAT. P&P FREE over £2.

Name _____


Address _____

ACE

Get an ACE up your sleeve!

ACE MAILTRONIX LTD
 Dept. P.E. Tootal Street
 Wakefield, W. Yorkshire WF1 5JR

THE DYNAMIC DUO

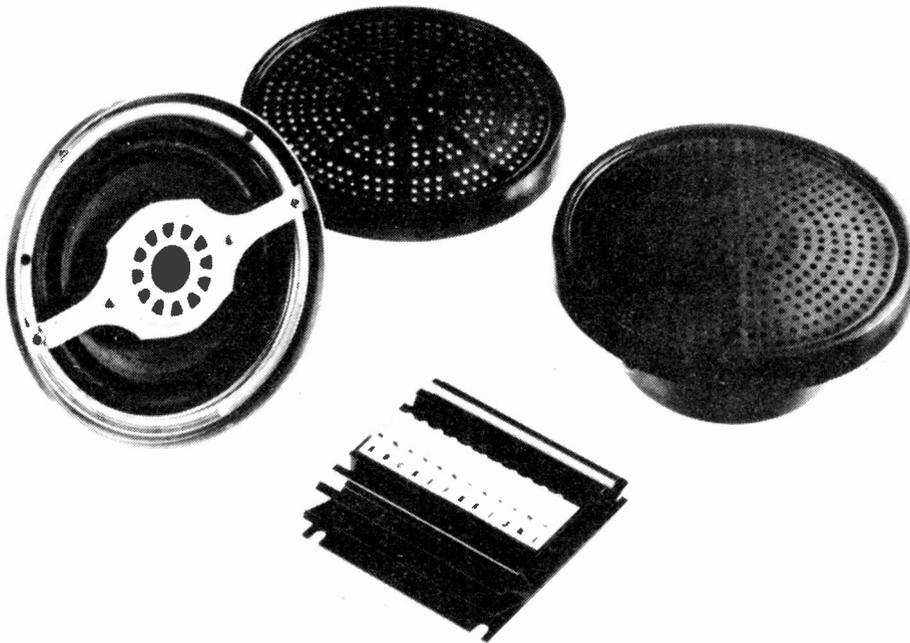

The C15/15 is a unique Power Amplifier providing Stereo 15 watts per channel or 30 watts Mono and can be used with any car radio/tape unit. It is simply wired in series with the existing speaker leads and in conjunction with our speakers S15 produces a system of incredible performance. A novel feature is that the amplifier is automatically switched on or off by sensing the power line of the radio/tape unit hence alleviating the need for an on/off switch. The amplifier is sealed into an integral heatsink and is terminated by screw connectors making installation a very easy process. The S15 has been specially designed for car use and produces performance equal to domestic speakers yet retaining high power handling and compact size.

C15/15
 15 watts per channel into 4Ω
 Distortion 0.2% at 1kHz at 15 watts
 Frequency response 50Hz-30kHz
 Input Impedance 8Ω nominal
 Input sensitivity 2V R.M.S. for 15 watts output
 Power line 10-18V
 Open and Short circuit protection
 Thermal protection
 Size 4 × 4 × 1 inches

Data on S15
 6in Diameter
 5½in air Suspension
 2in Active Tweeter
 20oz Ceramic magnet
 15 watts R.M.S. handling
 50Hz-15kHz frequency response
 4Ω Impedance

C15/15 Price £17.74 + £2.21 VAT. P. & P. free

S15 Price per pair £17.74 + £2.21 VAT. P. & P. free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 63218


Please Supply
 Total Purchase Price
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number
 Name and Address
 Signature

Registered office No. 1032630.

A VIDEO NEW YEAR

Impress the neighbours with A game they haven't seen yet and proudly tell them you made it yourself.

NEW

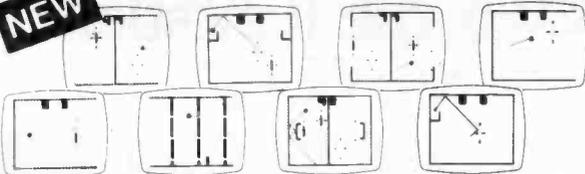

8 GAME T.V. PROJECT

BASED ON AY-3-8600


- * Basket-ball * Grid-Ball * Hockey * Tennis * Squash * Football + Two - One-Player Games. * Horizontal and Vertical Bat Coverage
- * Automatic Ball Speed-Up * Players Colour Coded
- * Three Tone Sound-Effects * Sound from T.V.
- * Ball Colour Coded to indicate turn in Squash-Game
- * All Components supplied guaranteed including sound and vision modulator C.H. 36 UHF.
- * Power requirement 9v battery * Just add controls and case.

Basic AY-3-8600 Paddle II Kit B + W £21.00 only £15.00
Colour £29.00 only £20.90

B+W Mini-Pack Chip + P.C.B. only £12.90
COLOUR Mini-Pack Chip + P.C.B. only £13.90

POPULAR AY-3-8500 PADDLE I

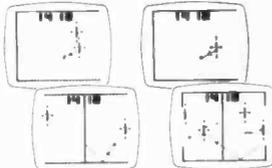
- * Three Tone Sound Effects
- * All components supplied guaranteed just add controls, speaker and case
- * UHF varicap modulator (B+W)
- * Power requirement - 9v battery
- * Stock clearance price down



Black + White £10.50 £9.90 Colour CH36 £16.50 £15.90
Mini-Pack P.C.B. + chip B+W £6.90 Colour £7.90

NEW JOY STICK CONTROLS

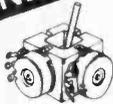DESIGNED FOR T.V. GAMES
(AY-3-8550-AY-3-8600) Subminiature Size



UNBEATABLE LOW PRICE
One off £1.90 Two off £3.50

COLOUR CONVERTER KIT

- * Easily connects to all b+w games using AY-3-8500 - AY-3-8550
- * Green background—Red boundaries—Yellow and Blue bats—White ball
- * No extra parts * No special equipment needed
- * New even lower price £8.50 complete

NEW VISION MODULATOR UHF-CH36

BUILT & TESTED £2.90 Order both together- £5.50

SOUND MODULATOR

CONNECTS WITH ABOVE £2.90

TELETEXT DECODER SAVE OVER £50.00

TEXAS TIFAX - XM11

Tested and Guaranteed Only £99.90

Full Colour Display ORACLE AND CEEFAX
Simple to interface with most TV's.
Keyboard and power supply extra.

Also in stock NEW Colour TV's complete with Teletext FROM £399.00



All Projects supplied with easy to follow assembly instructions.
All prices include VAT + Postage. Orders under £10.00 - Add 20p p & p.
Make all Cheques or Postal Orders payable to

TELECRAFT

A Dedicated Visual Display-Company

Mail Orders: 53 Warwick Road, New Barnet, Herts, EN5 5EQ.

Retail Shop and Demonstrations - 14 Station Road, New Barnet, Herts.

For further Details and Technical Help - Phone 01-440 7033

(French and German spoken)

Quantity discount negotiable.

For extra speed phone your order on Barclay-or-Access Cards.



Wilmslow Audio

THE firm for speakers!

SEND 10p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

ACT ● AUDAX ● BAKER
BOWERS & WILKINS ● CASTLE ● CELESTION
CHARTWELL ● COLES ● DALESFORD
DECCA ● EMI ● EAGLE ● ELAC ● FANE
GAUSS ● GOODMAN'S ● HELME ● I.M.F.
ISOPHON ● JR ● JORDON WATTS
KEF ● LEAK ● LOWTHER ● MCKENZIE
MONITOR AUDIO ● PEERLESS ● RADFORD
RAM ● RICHARD ALLAN ● SEAS
TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO (Dept. P.E. 8)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street
Tel.: Wilmslow 29599 for Speakers Tel.: Wilmslow 26213 for Hi-Fi

complete digital clock kits



TEAK OR PERSPEX CASE

NON ALARM £12.50

ALARM £15.50

“DELTA”
6in x 2½in x 3in

All prices include P. & P. and VAT

FEATURES: 4 LED digits ½in high. Red. ● 12 hour display with a.m./p.m. indication. ● Mains frequency accuracy. ● Easy to build: all components included. ● Beautiful real wood case or perspex: White, Black, Red, Blue and Green. ● Flashes to indicate power cuts.

NON ALARM: Complete kit including case, £12.50. Ready built, £14.50.

Module kit excluding case, £9.50. Ready built, £10.00.

ALARM: Pulsed alarm tone. Automatic brightness control. 9 minute "Snooze".

Simple setting. Complete kit including case, £15.50. Ready built, £17.00.

Module kit excluding case, £13.00. Ready built, £13.50.

TIMER FACILITY: Stopwatch use to 9 min. 59 sec. extra 50p.

EXCELLENT VALUE - GUARANTEED NOVUS

● LCD Gent's Watch. 5 function. Back light. Chrome case. Black strap. £15.95
● 4 Function Calculator. £3.78

DISPLAYS: FND500 ½in LED, £1.19 each: 6 for £6.48. NSB 5430, ½in Red LED stick of 4 £4.32. 5LTO2, ½in Green Phosphor stick of 4 £5.40.

CLOCK CHIPS: 50253N Alarm 12/24 hour 4/6 digit, £5.67.

50362N Calendar clock, £7.75. MM5385N 12hr 4 digit Alarm

£4.32. 6 Decade up/down counters, 50395/6/7 £13.10.

MICROPROCESSOR: Z80 CPU, £22.68. Z80 CTC, £15.70.

1702A UV Erasable PROM, £11.35. Z80 PIO £15.70. 2102NA, 1K Static RAM

£2.70. UV PROM Eraser, £103 plus £5 P. & P. 4KX1 16 pin Dyn. RAM £7.05.

RECHARGEABLE BATTERY SET: Super Value £8.10. Includes 4 AA (1.2V) Nickel Cadmium batteries (separately £1.08 each), 3/6/9V switched Universal Mains Adaptor with 4 plug connector for most calculators (separately £3.78), plus battery holder.

payment with order to:

BARON

(PE)

Southview House, 6 Gower Road
Royston, Hertfordshire

Telephone: Royston (0763) 43695



A SPECIAL FREE OFFER FROM DORAM

The revolutionary new 'Cyalume' lightstick as featured in 'Tomorrow's World'


The lightstick is a safe, easy-to-use emergency liquid lighting device. Quickly activated by bending, the lightstick will illuminate an average room giving sufficient light for reading. It's ideal for camping and boating and floats on water.

To obtain your free lightstick order £15 worth of goods from the Doram Edition 4 catalogue, issued in September, attaching this advertisement to your order.

The catalogue contains a complete range of kits, test equipment and high-quality components.

If you don't have the Doram catalogue, send 20p to cover post and packing with the coupon. We will despatch it by return to enable you to take advantage of this offer.

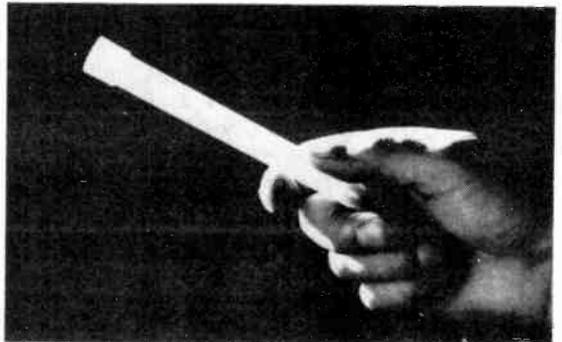Check out your Doram catalogue today and send your order to:
Doram Electronics Limited, PO Box TR8, Leeds LS12 2UF.
Offer closes March 10th, 1978.(PEF)



Please send a copy of the Doram catalogue by return. I enclose 20p to cover post and packing.

Name

Address

Doram Electronics Limited, PO Box TR8,
Leeds LS12 2UF. (PEF)



DORAM

Electronics you can depend on.

GREAT SOUND – GREAT VALUE!

**Stirling Sound
Disco 2
Mixer Control unit
+ power supply**



£39.95
inc. V.A.T. &
post free
in U.K.

By designing and manufacturing in our own Essex factory, with strict material control and stage by stage checking and then selling direct to YOU, the customer, we can save you pounds, offer better service and guarantee satisfaction. Our latest modular assembly, Disco 2, has already been thoroughly field tested and is ready for immediate service under the toughest working conditions.

- **INPUTS** – Left deck, right deck, mic. and aux.
- **INPUT IMPEDANCE** – 47K ohms
- **POWER SOURCE** – 220-240V. A.C. Mains
- **CONTROLS** – Mains on-off, master volume, bass ± 15 db, treble ± 15 db, L and R mixing, L and R motor switches, selector switch for P.F.L. (Pre-Fade Listening), headphone volume, mic. vol., aux. vol., LED indicators on mains and decks on/off switches.
- **HEADPHONE AMPLIFIER** – Powerful 2 watts into 8 ohms; separate vol. control.
- **TERMINATIONS** – Five $\frac{1}{4}$ " jack sockets – 2 input, 2 output, headphones.
- **SIZE** – $23\frac{3}{4}$ " x $3\frac{3}{4}$ " x $2\frac{1}{2}$ " max. depth to rear (plus separate power unit). Panel in matt black with controls sensibly grouped for easy handling.

■ **PRICE** – Post free, with power unit and inc. V.A.T. **£39.95**
Delivery ex-stock.

Suitable Stirling Sound power amps with heat sinks and power supply units – 140PH £18. 160PH £22. 1100PH £26.75.

OTHER STIRLING SOUND DISCO/P.A. ITEMS

- **BASIC CONSTRUCTIONAL MODULES**
 - SS.104/2 Two channel mixer stage £3.75
 - SS.104/4 Four channel mixer stage £7.00
 - SS.DTM Output control stage 30db variation on both treble and bass. Master vol. control. 3mV in for 2V out. 18V working voltage. £6.75
- **INTEGRATED POWER AMPLIFIERS**
 - Ready built in cases, tested and guaranteed – 60 watts R.M.S. into 4 ohms.
 - POWER AMP 60/with two channel mixer £48.00
 - POWER AMP 40 – 40 watts R.M.S. into 4 ohms with two channel mixer £43.00
 - POWER AMP 100 – 100 watts R.M.S. into 4 ohms with 4 channel mixer £85.00
 - 100 watt SLAVE AMP £50.00
- **READY BUILT ITEMS TESTED AND GUARANTEED**
 - SSTL3/250B Sound to light unit 3 channels, 250 w. each £23.95
 - SSTL3/1000B Sound to light unit 3 channels, 1000 w. each £25.95
- **STIRLING SOUND-LIGHT MODULES**
 - SSTL3/250 Three channels, each 250 watts output £9.25
 - SSTL3/1000 Three channels, each 1,000 watts £11.50

TO ORDER BY ACCESS OR BARCLAYCARD JUST WRITE OR PHONE IN YOUR NUMBER

ALL PRICES QUOTED INCLUDE VAT AND GOODS SEND POST FREE IN U.K. with C.W.O. orders. Owing to length of time between preparing this ad. and its appearance to the public, prices are subject to amendment without notice.



Mail Orders to Dept. PE28

STIRLING SOUND, 37 VANGUARD WAY, SHOEBOURNESS, ESSEX (03708) 5543. Shop & Showroom 220/224 West Rd., Westcliff-on-Sea (0372) 351048



SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

ORCHARD ELECTRONICS

I.C.s. TTL, C/MOS, Linear, Capacitors, Resistors (E12), SIL/Rectifiers, Diodes, LED, Thyristors, Zeners, Voltage Reg. DIL Sockets, Bridge Rectifiers, Potentiometers, Presets, Triacs, Diac, Plugs, Sockets, Cable, Vero. Carefully selected range, excellent despatch service. Same day turn round, S.A.E. List. Suppliers to A.E.R.E. U.K.A.E.A. Government Depts. Schools, Universities, Manufacturers. Accounts opened for trade and amateur. Join the professionals. Phone by 4 p.m. Goods out 1st class by 5 p.m. Try us and prove it!

ORCHARD ELECTRONICS

Flint House, High Street, Wallingford, Oxon
Telephone 0491-35529

VALVES—Radio, T.V., industrial, transmitting. We dispatch to any part of the world by return of post, Air or Sea Mail. 2,700 types in stock. 1930 to 1976 obsolete types a speciality. List 20p. Projector Lamps. Quotation S.A.E. Open to callers. Mon. to Sat. 9.30-5.00, closed Wed. 1.00. We purchase all types of new and boxed valves. And projector lamps. COX RADIO (Sussex) LTD., Dept. P.E., The Parade, East Wittering, Sussex PO20 8BN. West Wittering 2023. (STD code 024366).

CHIPS AND THINGS

I.C.s at give-away prices!—you test you save!
Untested devices (NOT manufacturers rejects, fallbacks etc.)

- PACK E1** (80% guaranteed good). 5 x MAM3 0.127" 7 segment LED displays **£1.00**
- PACK E2** (100% good). 1 x 8 digit (plus overflow) 0.33" 7 segment Liquid Crystal calculator style display **£3.95**
- PACK M1** (100% guaranteed good). 2 x Calculator keyboards **£1.00**
- PACK D1** (80% guaranteed good). 15 x Logic I.C.s mainly dual J-K DTL flip-flops, compatible with TTL. Could replace those costly TTL flip-flops in most projects. **£1.25**
- PACK D2**. 25 x 5N7400 type I.C.s. 100 two i/p nand gates. We guarantee 50 good. **£1.25**
- PACK L1** (marked and unmarked). 20 x Assorted Op-Amps. Could include LM301, 741, 709, 555 etc. **£1.25**
- PACK L2**. 20 x LM709 Op-Amps. (8 load TO5) **£1.50**
- PACK M2** (No guarantees). 50 Minidip I.C.s for **£1.00**. Mostly unmarked. We don't know what they are. (At 2p. each can you go wrong?)
Could be they are all O.K., but as they're untested — we don't know. For packs with no stated guaranteed minimum, we'll guarantee it works out much cheaper than average mail order prices buying this way. Satisfaction guaranteed or return complete pack for replacement or refund.

MAIL ORDER ONLY — NO CALLERS

P & P 20p
CODESPEED, P.O. Box 23, 34 Seafield Road, Copnor,
Portsmouth, Hants. PO3 5BJ.

L.B. ELECTRONICS, MJE3055 40p, BF195 9p, BC213 9p, BC108C 10p, OCP70 16p, BXY49 38p, 1N4148 4p, 3-3V, 24V, zeners 5p. 2102 (500NS) + data £1.50, 8080A £16, 1702A £7.50, CD4250 70p, 741 20p, 741 TO99 (DIL) 30p, 555 45p, 74H00 20p, 7 way DIL switches 60p, min push button switches (change over) 40p, 75450 38p, Fenwell Thermistors, pair potted + lead-plug 20p, PCB 1 watt amplifier LM 380 etc £1.20, ITT 5870ST nixi + data 50p, Sperry SP425-09 (9 digit 7 seg) + data £1, 747 6" (Red) £1.35, D.P.M. Display 4 digit (LED) with bezel £2.50. P & P 10p. L.B. ELECTRONICS, 43 Westcott, Hayes, Middx. UB4 8AH.

QUALITY COMPONENTS AT LOW PRICES

Transformers and IC's	BFY50	0.20	DA91	0.08	Electrolytic Caps	0.00	1.0 µF	18V	0.05
AC127	0.22	BFY52	0.20	MA4001	0.05	2.2 µF	83V	0.10	
AC128	0.21	2N3055	0.80	MA4002	0.05	4.7 µF	83V	0.10	
AD161	0.50	741	0.20	MA4003	0.05	10 µF	83V	0.10	
AD182	0.50	7400	0.16	MA4004	0.05	22 µF	25V	0.05	
BC107	0.10	555	0.48	MA4005	0.07	32 µF	18V	0.05	
BC108	0.10	7430	0.17	MA4008	0.07	47 µF	25V	0.05	
BC109	0.11	7490	0.42	MA4007	0.08	47 µF	83V	0.12	
BD147	0.08	72709	0.38	MA1448	0.04	100 µF	25V	0.05	
BD148	0.08	72741	0.35	IN5401	0.13	220 µF	25V	0.20	
BC149	0.09			IN5404	0.15	470 µF	35V	0.25	
BC207	0.10			IN5405	0.15	1000 µF	18V	0.28	
BD131	0.50	Diodes		IN5407	0.15	1000 µF	50V	0.32	
BD132	0.50	0A47	0.12	IN5408	0.18	1000 µF	70V	0.38	
BD140	0.40	0A80	0.08	8276 series	1.18	2200 µF	50V	0.85	

Resistors. Carbon film 5% 2W-0.05 1W-0.04 ½W-0.025 ¼W-0.02
Also stocked: Bridge Rectifiers, Fuses, Fuse Holders, Leads and Cables, Plugs and Sockets, Microphones, Multimeters, Antex Soldering Irons, Solder, Speakers, Speaker Cabinets and many other items all at low prices. Send for comprehensive stock list for full details. Quantity discounts available. All prices include VAT but please send 25p extra to cover post & packing.

D S M ELECTRONICS LIMITED

Unit 22, Low Mill Ind. Estate, Ravensthorpe,
Dewsbury, W. Yorks.
Tel: Mirfield (0924) 495871

GAMMA ENTERPRISES for transistors, resistors, capacitors, ICs, hardware etc. Large SAE for Catalogue. 18 Landale Road, Peterhead, Aberdeenshire AB4 6QP.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V—0.47, 1.0, 2.2, 4.7 and 10µF 5p; 22, 47 5µF (50V 9p); 100 7p (50V 9p); 220 8p (50V 10p); 470 11p (50V 10p); 1,000 (18V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p.
Subminiature Bead Tantalum Electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 at 3.5V, 4.7/25V 11p; 10/25V 13p; 22/16V, 47/6V 1 and 100/3V 16p.
Mullard Min. Ceramic E12 Series 63V 2%—10pF to 47pF—3p; 56pF to 330pF 4p.
Vertical Mounting Ceramic Plate 50V—E12 series 22—1,000pF and E6 series 1,500—47,000pF 2p.
Polystyrene E12 Series 63V Horizontal Mounting—10—1,000pF 3p; 1,200—10,000pF 4p.
Mullard Polyester 250V Vertical Mounting E6 Series—0.01—0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 5p; 0.68 11p; 1.0 13p; 1.5 20p; 2.2 22p.
Mylar (Polyester) Film 100V Vertical Mounting—0.001, 0.002, 0.005 3p; 0.01, 0.02 4p; 0.04, 0.05 4p.
Miniature Resistors Highstab E12 Series 5%, Carbon Film 0.25W 1Ω to 10M Ω. (10% over 1M) 1p. Metal Film 0.125W, 0.25W and 0.5W 10 Ω to 2M Ω 1½p. Metal Film 1W 27 Ω to 10M Ω 2p.
1N4148 3p; 1N4002 5p; 1N4006 7p; 1N4007 8p; BC107/8/9, BC147/8/9, BC157/8/9, BF194, 197 9p.
Fuses 20mm glass, 1½in glass, 1in ceramic 2½p.
Post 10p (free over 24). Prices inclusive of V.A.T.

THE C.R. SUPPLY CO.
127 Chesterfield Road, Sheffield S8 0RM

240/12-0-12V. 100mA. transformers with power supply P.C.B. 4 for £1.99. TO3 metal power transistors 35 for £1.99. U11. Push to make switches Red/Y/Blue 12 for £1.99. Please add 30p P&P VAT included. JONES SUPPLIES, 588 Ashton Road, Oldham, Lancs. 061 652 9879.



SPECIAL OFFERS.

Buy NOW while stocks last. PRICES INCLUDE V.A.T.
RESISTORS ½W 5% carbon film E24 range 10R-1M. 2p each 100 of one value £1.05, 1000 of mixed 100's **£9.95**
E12 series pack 10R-1M, 10 of each value (610 resistors) **£6.40**
E24 series pack 10R-1M, 10 of each value (1210 resistors) **£12.70**
E12-E24 expansion packs 10 of each value (600 resistors) **£6.30**
TRANSISTORS
BC107/8/9C 10p BC182/184L 12p
BCY71 15p BC212 12p
2N2924Y 10p 2N2926G 11p
2N3054 48p 2N3055 48p
INTEGRATED CIRCUITS
CA3089E IF System £1.99 CA3090AQ Ster. Decoder £3.99
741 8 pin DIL Op Amp 26p 748 1N4 Op Amp 38p
709 8 pin DIL Op Amp 27p 723 Voltage Regulator 54p
LM3900 Quad Amp 76p LM380 2W Amp 99p
LED's Red 3 or 5mm 13p Pack 10 LED's (seconds) 89p
RECTIFIERS 1N4001 5p 1A/50V Bridge 29p
POLYESTER CAPACITORS (250V)
0.1µF 3p, 0.22µF 4p, 0.47µF 7p, 1.0µF 12p.
Please add 15p for Postage. Send 2 stamps for Catalogue.
BARCLAYCARD phone service available. Tel. 0473 50975.

FRASER-MANNING LTD.

26 HERVEY STREET, IPSWICH, IP4 2ES.

P.C.B.s Paxolin 9½ in x 7in, 50p. 12in x 9in, 70p. 17½ in x 8½ in, £1.15. Fibre glass double sided 6½ in x 6in, 80p. 12in x 6in, £1.20. 10 74 Series I.C.s on panel(s) 75p. Three assorted meters £2.40. T.V. Convergence panels, full of good gear, £1.50. S/Mica caps 100 assorted 75p. 300 Small components, Trans, Diodes £1.30. 7 lb Assorted components £2.95. List 15p. Refundable. Post 20p under £1. Insurance add 15p

J. W. B. RADIO

2 Barnfield Crescent, Saie, Cheshire, M33 1NL.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 4188. Immediate settlement.

SOLAR CELLS

2.25" Dia. 250mW at 0.5V — **£8.00**
1.00" Dia. 35mW at 0.5V — **£4.50**
5.3 x 6.3mm 2.5mW at 0.5V — **£1.25**

Cells are supplied with leads attached and are coated with varnish. "Solar Cells" booklet 75p. Data sheets on above devices 20p. Mail Order only. Speedy service.

EDENCOMBE LIMITED

16 Princes Avenue, Kingsbury, London NW9 9JB

LOW, LOW PRICES FOR 7400 SERIES TTL

00	13p	32	24p	89	£2.20	145	69p
01/2/3	14p	37	27p	90/2/3	44p	153	63p
04/5	16p	40	14p	91	58p	157	64p
06	32p	41	61p	95	60p	174	94p
08	18p	42	54p	96	73p	175	75p
10/20	14p	45/7/8	73p	100	70p	181	£2.56
13	30p	73/4/6	27p	121	31p	190	£1.24
17	27p	75	43p	123	53p	192/3	£1.00
30	15p	86	27p	125/6	44p	196	84p

Full Spec. Devices. Prices include VAT
SAE for complete list! P & P (1st class) 20p. C.W.O.
J. C. JONES (PE29), Mail Order Only
46 Burstellars, St. Ives, Cambs. PE17 4XX.

BOOKS AT BARGAIN PRICES

BOOKS AT BARGAIN PRICES: Semiconductors, international dictionary in 7 languages, English-French-German-Italian-Portuguese-Russian-Spanish. 2 volumes (pub. price £15) £3. Freeman, Worked Examples in Alternating Current for Engineering Students £1. Frost-Smith, The Theory and Design of Magnetic Amplifiers (pub. price £2) £1. Post Free. From: F. WEATHERHEAD & SON LTD., 58 Kingsbury, Aylesbury, Bucks. Tel: 0296 23153.

SIMPLIFIED TV Repairs. Full repair instructions individual British sets **£4-50**, request free circuit diagram. Stamp brings details unique. TV PUBLICATIONS (Ausepe), 76 Church Street, Larkhall, Lanarkshire.

FOR SALE

P.E. 9 CH. RADIO CONTROL (Unfinished Project), Case, 5K sticks, P.C.B.s, etc. Offers. Tel: Christchurch 78339.

NEW ISSUES of "Practical Electronics" available from April 1974 edition up to date. Price 65p each. Post free. **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

FOR SALE, PE November 1964 (No.1) to July 1971 complete £15. Buyer Collects. 01-524 5350 (London E4).

UNENCODED ASCII Keyboard with case and Hexadecimal keyboard with case. Offers 01-828 8695.

MOTOROLA MEK 6800D2 with power supply cassette extra ram. £240. WILMOT, Horsham 69835.

E.T.I. 4600 SYNTHESIZER. Complete in case. OFFERS: Mr. Calderwood, 177 Duntocher Road, Clydebank, Scotland. *Phone Duntocher 74451.

ORION AMPLIFIER. One channel working. Ideal spares or repair. £20. Practical Electronics Feb. '74, August '76 £10. Everyday Electronics Nov. '73 to date £15. Tel: 07917 5450.

BACK ISSUES of P.E. from 1971 to 1974. Phone 0533 413646.

WANTED

"RADIO AND TELEVISION Servicing". Books wanted from 1964-1965 edition up to date. £3.00 plus postage paid per copy by return of post. **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorks. Telephone (0423) 55885.

WANTED-NEW VALVES, Transistors. Top Prices, popular types. **KENINGTON SUPPLIES**, (B) 367 Kensington Street, Bradford 8, Yorkshire.

EDUCATIONAL

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination, and obtain your G8 licence, with an RRC Home Study Course. For details of this, and other courses (GCE, Professional Examinations etc) write or phone **THE RAPID RESULTS COLLEGE**, Dept. J.S.I. Tuition House, London SW19 4DS. Tel. 01-947 7272 (Careers Advisory Service) or for a prospectus only ring 01-946 1102. (24hr recording service).

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272M Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272M Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272M Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

SITUATIONS VACANT

RADIO TECHNICIANS

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over.

Standards required call for a sound knowledge of the principles of electricity and radio, together with 2 years experience of using and maintaining radio and electronic test gear.

Duties cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer, and analytic machinery.

Qualifications: Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualifications.

Salary scale from £2,230 at 19 to £2,905 at 25 (highest pay on entry) rising to £3,385 with opportunity for advancement to higher grades up to £3,780 with a few posts carrying still higher salaries. Pay supplements total between £443 and £522 per annum.

Annual leave allowance is 4 weeks rising to 6 weeks after 27 years service.

Opportunities for service overseas.

Candidates must be UK residents.

Further particulars and application forms available from:
Recruitment Officer, Government Communications Headquarters
Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ
Tel.: Cheltenham (0242) 21491 (Ext. 2270)

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc. 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

MISCELLANEOUS

SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1.80, MOT CMOS Databk 3.50, 6800 Appl Man 12.95, 6800 Prog Man 5.35, SC/MP Intrakit Man 0.75 NS TTL Databk 2.10, RCA CMOS Databk 5.45, 8085 User's Man 5.15, Z80 Ass Lang Prog Man 7.50, Z80 CPU Man 5.60, Z80 CTC Spec 0.80, Z80 P10 Man 3.30. Also a full range of CMOS - send for free catalogue. MPUs: MEK6800D2 205.20, MC6820 8.66, Z80 30.72, Z80A 39.94, Z80CTC 13.82, Z80P10 13.82, Memories: 2102-A 2.55, 2112A-4 3.13. Displays: Type FND500 C.C. 1.40, Type TL321 C.A. 1.61, 51T01 5.29. Crystals: 32.768KHz 3.78, 5.12MHz 3.89. Clock ICs: AY51202 4.35, AY51224 3.78, MK50253 6.05. Soldercon Pins: 100 0.54, 1000 4.32, 3000 11.34. Free catalogue by return. All items CWO. Prices inclusive of VAT. Add 35p p.p. **SINTEL**, P.O. Box 75B, 209 Cowley Road, Oxford. Tel. (0865) 49791

SYNTHESIZER. Case, Chassis, Keyboard, Contacts, DEWTRON Modules; 2 VCO-2, SHE-1A, OFT-1A, VCF, Pots, Switches, etc., Full Plans, worth £250 + Gift at £100, or best offer. T.U.A.C. 2*100W. Amplifier, in verocase, perfect. £95 o.n.o. P.E. Mag. since March 73, offers? Ring Dick: WAKEFIELD (0924) 256949. After 7pm.

H. M. ELECTRONICS

275a Fulwood Road, Broomhill, Sheffield S10 3BD



BEC CABINETS

Give your project that professional looking finish. Build it in a BEC. Dry transfer lettering now available...

ORION cabinet still available punched or unpunched. Send 15p (refundable) for leaflets.

100 WATT GUITAR/PA/Music Amplifier superb treble bass overdrive slimline solidstate 12 months guarantee unbeatable offer at £39. Money returned if not absolutely delighted within 7 days. Send cheque or P.O. to: **WILLIAMSON AMPLIFICATION**, 62 Thorncroft Avenue, Dukinfield, Cheshire.

DIRECT READING FREQUENCY METER



- ★ Complete kit £29.50
- ★ Linear scale
- ★ 6 ranges up to 100 KHz
- ★ Accepts any waveform
- ★ Easy to calibrate - quartz standard supplied on loan.

Send S.A.E. for details to: James Cooper (Elec.) Ltd. 120 Castle Lane, Solihull, Warwickshire.

RECHARGEABLE BATTERIES

'AA' pcell (HP7) £1.32; sub 'C' £1.64; 'C' (HP11) £2.43; 'D' (HP2) £3.56; PP3 £4.98. Matching chargers £6-33 each except PP3 charger £4.99. Charging holders for 2, 3, 4, 5 or 6 pencils £5.0p. 'C' and 'D' size holders, 4 cell only, 80p. 250/12 volt inverters now available. Prices include VAT. Add 10% post, package and insurance orders under £20. 5% over £20. S.A.E. for full details plus 75p for 'Nickel Cadmium Power' booklet. Mail orders to:

SANDWELL PLANT LTD. DEPT. P.E.

201 Monmouth Drive, Sutton Coldfield, West Midlands. Tel. 021-354 9764
Callers to T.L.C., 32 Craven Street, Charing Cross, London, WC2.

ELECTRONIC COMPONENTS, Electrical fittings appliance spares, cables, hardware, tools, audio accessories, styli and cartridges, TV spares etc. At discount prices. 30p for catalogue. No Callers. **TROJAN ELECTRONICS**, 3 Station Road, Shortlands, Bromley, Kent.

NO MORE DING-DONG

Now get MUSIC from your DOORBELL - or your CAR. New programmable Chime announces you or your surprised guests. 119 easy-to-change tunes or PROGRAM YOUR OWN. Just needs speaker and existing bell transformer or 12V. All parts, instructions and programs, postage, money back assurance, send £17.90 now.


CAMBRIDGE KITS

45 (FB), Old School Lane, Milton, Cambridge.

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

INVENTORS. "Profit from Your Invention". Sources of Finance and other assistance. Details: Large S.A.E. **DELTA** (PE), 15 St. Mary Street, Southampton, Hants.

BUILD YOUR OWN TV CAMERA

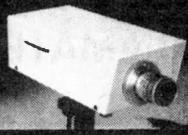

ONLY KNOWN HIGH PERFORMANCE SOLID STATE CAMERA IN KIT FORM. Also available factory assembled. Ideal for experimenters, industry security, education etc. *Will work with most other CCTV equipment. *Fully guaranteed. *Completely self-contained. With our modulator will connect to any domestic TV set. Model C1 complete with Vidicon £99. Less Vidicon £82.35. (Lens available as optional extra). SAE for info or phone your order through using your Barclay or Access Card.

CROFTON ELECTRONICS LIMITED
35 Grosvenor Road, Twickenham, Middlesex. 01-891 1923

CARBON FILM RESISTORS 5% E12 1/4W, 1/2W, 1W. Your mix, 90p/100. Metal Film 1/4W, £1.10/100. P. & P. 15p. Mail Order Only. CANDAR, 9 Galloway Close, Bletchley.

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Strap & Recess Handles, Feet, Castors, Jacks & Sockets, Cannons, Bulgin 8 ways, Reverb Trays, Locks & Hinges, Corners, Trim, Speaker Bolts etc.

Send 2 x 9p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)
Unit 6, Starline Works, Grainger Road
Southend-on-Sea, Essex.

BURGLAR ALARM equipment, safes, trade supplies. ASTRO-ALARMS, 25 Stockton Rd., Sunderland. Tyne and Wear. Tel.: 77825. Free list S.A.M.

BUILD THE TREASURE TRACER

MK III Metal Locator



- Variable tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete Kit **£15.95** Built and tested **£20.95**

Post £1.20 - £1.37 VAT Post £1.20 - £1.77 VAT

MINIKITS ELECTRONICS 69 CLEVELAND ROAD
LONDON E18 2AN (Mail Order Only)

ARMATURE AND COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied. All orders despatched within 24 hours.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices inclusive of P. & P. in U.K.

COPPER SUPPLIES

102 Parrwood Road, Withington,
Manchester 20 Telephone 061-445 8753

HIGH ENERGY LITHIUM BATTERIES outperform conventional dry cells for less volume and weight. Remarkable voltage stability, long shelf life. S.A.E. for details: **HIRST JACOBSON LTD.** 91 Marylebone High Street, London W.1.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a **MINI-STROBE** Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.M.U.s, sweep generators, test equipment, etc. Tel. Lower Beeding 236.

MAKE YOUR OWN PRINTED CIRCUITS

RUB-ON TRANSFERS - Starter pack (5 sheets, lines, pads, I.C. pads) £1.30, Single Sheets 27p.
FERRIC CHLORIDE - 1 lb bags 70p (P. & P. 40p).
SOLDERCON SOCKETS - 100 65p. (quantity rates). **PLASTIC SUPPORTS** - 7 or 8 hole 6p./pair.
S.A.E. lists sample. P. & P. 15p/order except*.
P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

LOW COST aluminium boxes with lids and screws. 3 x 2 x 1 42p, 4 x 3 x 1 49p, 4 x 3 x 2 56p, 6 x 4 x 2 62p, 6 x 4 x 3 72p, 8 x 6 x 2 97p, 8 x 6 x 3 £1.08. Prices include P & P. **HARRISON BROS.** P.O. Box 55, Milton Road, Westcliff-on-Sea, Essex SS0 7LQ.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

RAMAR CONSTRUCTOR SERVICES,
Masons Road, Stratford upon Avon, Warwick.
Tel. 4879.

STABILISED P.S.U.s. Large range of various voltages and currents, available cased or in chassis form. S.A.E. for full particulars and prices. **A. BARTON, PE,** Highbanks, Newport Road, Sandown, I.W.

THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA.

Featuring *24 key keyboard *Seven segment display *Cassette interface *Erom & Ram Expandable *Interface Capability *Full Documentation *5 Volt power supply Required *One years FREE membership of The Amateur Computer Club with every purchase*. £1.76 + £1.50 P & P + 8% VAT.

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2.60	1.40	.66	.55
20-29	2.80	1.60	.85	.65
30-34	3.00	1.70	.95	.70
35-40	3.35	1.90	1.10	.79
40-43	4.50	2.50	1.90	1.25
44-46	5.00	3.00	2.10	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb. Multicore 60/40 Solder 18SWG £3.24 per lb. Prices include P & P and VAT. SAE brings list of copper and resistance Wires.

THE SCIENTIFIC WIRE COMPANY

PO Box 30 London E.4.
Reg. Office, 22 Coningsby Gdns.

DO YOU UNDERSTAND I.C.'s and the workings of calculators? Then you can design and build a circuit for me. Will pay generously. Phone 01-328 7972. Or write to **DAVID PARFITT,** 40 Dunster Gardens, London NW6 for details.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager
PRACTICAL ELECTRONICS
GMG, Classified Advertisements Dept., Room 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846
Rate:
18p per word, minimum 12 words. Box No. 60p extra.

GLASS FIBRE P.C.B.'s

From your own tape, film or ink master. Send S.A.E. for quotation.
PRACTICAL ELECTRONICS P.C.B.'s in glass fibre, tinned and drilled. Complete set of Radio Control boards, June to Aug. 76 £5.80p. Cross Hatch Generator £2.85p.
 May 77 Burglar Alarm (1305-1) £1.68. June 77 Sports Centre (1306-1) and power supply p.c.b. £2.66. July 77 Digital Stopwatch (1307-1) £1. Oscilloscope trace doubler 95p. Earth Leakage C.B. (1307-2) £1.96p. Aug. 77 C/R Meter (1308-1) 97p. Sept. 77 Freq. Counter Timer (1309-2/3) £3.98 set of two boards. Scope Probe (1309-1) 56p. Oct. 77 Digital Multimeter (1401-1/2) £3.15 set of two boards. Guitar Sustain (1410-3) 55p. Dec. 77 Car Burglar Alarm (1412-1) 88p. 128 Note Sequence (1412-2/3) £2.71 set of two boards.

PROTO DESIGN

4 Highcliff Way, Wickford, Essex SS11 8LA

BURGLAR ALARM GOODIES! 12V siren £5.53, 240V siren £9.61, plastic coated and lettered bell box £5.25. Flush magnetic contact 60p, surface 65p. S.A.E. for price list. C.W.A.S. 11 Denbrook Walk, Bradford BD4 0QS. Tel: Bradford 682674. All prices fully inclusive.

YOUR OWN COMPUTER WHY NOT!

The Microprocessor Users Group can help you build it, with a regular magazine of circuits and software, plus free use of our software library, free technical and programming assistance and discounts on all components systems and services sold by us. For full details write with S.A.E. to Computabits Ltd, 41 Vincent Street, Yeovil, Somerset. Tel. (0935) 26522.

WIRE THREADING KIT: Consists, W.D. Pencil, W.D. Board, W.D. Strips (Glue and Press Fix), Spare Spool of Wire, I.C. Leg Deformer, Comprehensive Instructions £7.51 inc. P & P and VAT. Separates: W.D. Pencil £2.20 W.D. Board £2.60 (4 for £8.00), W.D. Strips 6" Glue Fix £1.30/pkt 10. W.D. Strips Press Fix £1.30/pkt 30, Spare Bobbins - Pink, Green, Blue, Copper (0.19mm) 40p ea. Misc: Orxy Temp. Cont. Iron and Stand £12.40, Cutters £2.84, Tweezers 90p, Conductive Paint (3g tube) £2.30.
 Terms: 35p P & P/£10 of goods then add 8% VAT. Overseas £1 extra. (Iron and Stand 54p P & P).
ZARTRONIX, 115 Lion Lane, Haslemere, Surrey.

LADDERS

LADDERS. Varnished 25 1/2ft extd. £35.70. Carr. £2.40. Leaflet. Immed. despatch. **THE LADDER CENTRE** (PEES), Halesfield (1), Telford, Salop. Tel. 586644.

ELECTRICAL

LIST NO. 28 now ready - Stylii illustrated equivalents also Cartridges, Leads, etc., free for long SAE. **FELSTEAD ELECTRONICS (PE)**, Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

SOLID STATE DESIGN FOR THE RADIO AMATEUR

by A. R. R. L.

Price £6-10

IC TIMER COOKBOOK by W. G. Jung
Price £7-50

HI FI YEAR BOOK 1978 by IPC
Price £3-65

RADIO & T.V. SERVICING 1976/77 MODELS
by R. N. Wainwright
Price £10-25

RADIO DATA REFERENCE BOOK by T. G. Giles
Price £4-10

MICROPROCESSORS & SMALL DIGITAL COMPUTER SYSTEMS FOR ENGINEERS & SCIENTISTS by G. A. Korn
Price £19-00

MASTER TRANSISTOR/IC SUBSTITUTION HANDBOOK by TAB BKS No. 970
Price £5-60

OP-AMP CIRCUIT DESIGN & APPLICATIONS by J. Carr
Price £3-85

INTRODUCTION TO MICROPROCESSORS
by D. Aspinall
Price £5-30

HOW TO BUILD & USE ELECTRONIC DEVICES WITHOUT FRUSTRATION, PANIC, MOUNTAINS OF MONEY, OR AN ENGINEERING DEGREE
by S. A. Hoenig
Price £7-70

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD etc

7400	14p	7426	25p	7473	30p	74121	25p	74179	140p
7401	14p	7427	25p	7474	30p	74122	40p	74180	100p
7402	14p	7428	40p	7475	30p	74123	60p	74181	200p
7403	14p	7430	15p	7476	30p	74125	50p	74182	75p
7404	14p	7432	25p	7483	85p	74126	50p	74184	150p
7405	14p	7437	25p	7485	100p	74130	130p	74157	70p
7406	40p	7438	25p	7486	30p	74131	100p	74180	90p
7407	40p	7440	15p	7489	250p	74132	85p	74181	90p
7408	20p	7441	85p	7490	35p	74135	100p	74182	90p
7409	20p	7442	85p	7491	75p	74136	80p	74163	90p
7410	15p	7445	80p	7492	45p	74137	100p	74164	125p
7411	20p	7446	85p	7493	40p	74138	125p	74165	125p
7412	20p	7447	75p	7495	80p	74139	100p	74166	125p
7413	30p	7448	70p	7496	70p	74141	80p	74167	325p
7414	80p	7450	15p	74100	95p	74142	270p	74170	200p
7416	30p	7451	15p	74104	40p	74143	270p	74173	150p
7417	30p	7453	15p	74105	40p	74144	270p	74174	100p
7420	15p	7454	15p	74107	30p	74145	75p	74175	75p
7422	20p	7460	15p	74109	50p	74147	230p	74176	100p
7423	25p	7470	30p	74118	90p	74148	180p	74177	100p
7425	25p	7472	25p	74120	90p	74150	120p	74178	140p

CMOS									
4000	20p	4030	80p	IN4148	BY	ITT/TEXAS	1200µF 63V, 2 for £1.00.		
4001	20p	4032	150p				2200µF 63V, 2 for £1.50.		
4002	20p	4043	220p	TEXAS	TIS88A	VHF FET	3300µF 63V, 2 for £1.60.		
4006	120p	4046	150p			10 for £2.30. 100 for £20.00.			
4007	20p	4047	115p						
4009	70p	4049	70p						
4011	20p	4050	50p						
4012	20p	4054	130p						
4013	55p	4055	140p						
4015	90p	4056	145p						
4016	55p	4060	130p						
4017	110p	4066	55p						
4018	250p	4069	30p						
4020	140p	4071	30p						
4022	180p	4072	30p						
4023	20p	4081	20p						
4024	100p	4082	30p						
4025	20p	4510	145p						
4026	200p	4511	200p						
4027	85p	4516	140p						
4028	155p	4518	110p						
4029	130p	4528	130p						

XEROZA RADIO

306 ST. PAUL'S ROAD,
HIGHBURY CORNER, LONDON N.1

Telephone: 01-226 1489

Easy access to Highbury via Victoria Line (London Transport) British Rail

CRESCENT RADIO LTD.

MAIL ORDER DEPT.

1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ
PHONE: 888-4474

MULTIMETER BARGAINS

A special bulk purchase of Eagle Multimeters enables us to offer two from their range at up to 15% off Eagle's own Recommended Retail Price.

EFFECTS PROJECTOR "150"

(150 watt)

Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6in. Liquid Wheel. Ready to use.

A bargain at £34 + 8% V.A.T.

KEW 7 POCKET MULTIMETER

Handy pocket-size (3 1/2" x 2 1/2" x 1") 1000 opv meter with 'off' damping. Includes all basic ranges: DC volts 0 to 10, 50, 250, 1000. AC volts: 0 to 10, 50, 250, 1000. DC amps: 0 to 100 MA. Resistance: 0 to 150K ohms. Decibels: -10 to +22dB. £5.97. + 8% VAT with leads and battery.



C1095 20,000 OPV MULTIMETER

with hinged 4-position scale for easy reading bench use. Antiparallax mirror, 3-colour scale, overload protection. Ranges: DC volts: 5, 25, 50, 250, 500, 2,500 (20,000 opv). AC volts: 10, 50, 100, 500, 1,000 (10,000 opv). DC amps: 50µA, 2.5mA, 250mA. Resistance: 50K ohms, 5 megohms. Decibels: -20 to +22dB. £14.31 + 8% VAT.



3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT (1000 Watt per channel)

Three channel. Bass, Middle, Treble. The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display. Full instructions supplied or S.A.E. for details.

Fantastic Value at £20-00 + 8% V.A.T.

LOUDSPEAKER SELECTION

+ 12 1/2% V.A.T.

2 1/2in. 8, 40, and 75 ohm at £1-10 (please state which impedance is required)
 5in. 8 ohm Ceramic at £1-70
 8in. Goodmans "Audiom 8PA" 8 ohm 15W £5-28
 10in. "ELAC" Dual Cone 8 ohm 10 watt at £4-75

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED
 ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E. WITH ALL ENQUIRIES PLEASE

Personal callers welcome at 164-166 High Road, Wood Green, N22. Phone: 888 3206 and 13 South Mall, Edmonton N9. Phone: 803 1685

TTLs by TEXAS		CMOS I.C.s.		OP. AMPS.		NES51V		MEMORY I.C.s.		MJE2955		2N2928G		DIODES		BRIDGE RECTIFIERS	
7400	14p	74112	28p	CA3130	100p	709	140p	P4040	625p	I401	500p	2N3053	11p	BY127	12p	1A	50V 25p
7401	14p	74116	28p	CA3140	100p	733	150p	D4280	800p	1702A	800p	MFF102/3	45p	OA47	9p	1A	50V 25p
7402	10p	74118	100p	CA3190	120p	747	75p	B4702A	£13	2102-2	210p	MFF104/5	45p	OA81	15p	1A	100V 37p
7403	10p	74118	100p	CA3200	120p	747	75p	P4002-1	400p	2107	800p	MPSA08	37p	OA85	15p	2A	50V 40p
7404	24p	74120	100p	CA3210	120p	778	40p	P4201A	600p	2112-2	430p	MPSA12	67p	OA90	9p	2A	50V 40p
7405	25p	74121	32p	CA324H	130p	778	77p	P4285	410p	6080A	£14	MPSA56	40p	OA91	9p	2A	200V 70p
7406	43p	74122	32p	MC1458P	127p	3000	70p	P3205	300p	AYS-1013	850p	MPSU05	72p	OA95	9p	3A	50V 90p
7407	43p	74123	77p					PS101-8	500p	RO3-2513	800p	MPSU08	70p	OA200	10p	4A	100V 90p
7408	22p	74125	70p									MPSU55	90p	IN1914	4p	8A	100V 180p
7409	22p	74126	60p									OC28	90p	IN1916	7p	8A	50V 90p
7410	10p	74128	82p									OC36	90p	IN4001/2	6p	25A	400V 430p
7411	20p	74132	81p									OC71	30p	IN4003/4	7p		
7412	20p	74136	81p									R2008B	225p	IN4005/7	8p		
7413	20p	74141	85p									R2010B	225p	IN4148	4p		
7414	60p	74142	300p									TIP29A	50p	IN5401/3	15p		
7416	60p	74145	90p									TIP29C	50p	IN5404/7	20p		
7417	60p	74147	200p									TIP30A	50p				
7421	40p	74150	120p									TIP30C	72p				
7422	20p	74151	81p									TIP31A	50p				
7423	30p	74154	100p									TIP31C	50p				
7425	33p	74155	97p									TIP32A	83p				
7426	43p	74158	87p									TIP32C	83p				
7427	60p	74157	97p									TIP33A	97p				
7428	60p	74159	250p									TIP33C	97p				
7430	10p	74180	90p									TIP34A	124p				
7432	37p	74181	130p									TIP34C	100p				
7433	43p	74186	87p									TIP35A	243p				
7437	37p	74183	130p									TIP35C	200p				
7438	37p	74184	130p									TIP38A	200p				
7440	10p	74185	150p									TIP38C	200p				
7441	80p	74186	100p									TIP39C	350p				
7442	80p	74187	200p									TIP41A	70p				
7443	130p	74170	200p									TIP41C	84p				
7444	120p	74172	70p									TIP42A	70p				
7445	100p	74173	100p									TIP42C	90p				
7446	100p	74174	130p									TIP2955	70p				
7447	70p	74175	97p									TIP3055	60p				
7448	80p	74176	130p									TIS43	40p				
7450	10p	74177	100p									2N697	25p				
7451	10p	74180	100p									2N698	43p				
7453	10p	74181	324p									2N708/8	22p				
7454	10p	74182	150p									2N708/9	22p				
7460	10p	74186	100p									2N708/1	43p				
7470	30p	74185	100p									2N710	30p				
7472	32p	74186	900p									2N713/2	25p				
7473	30p	74190	140p									2N713/3	25p				
7474	37p	74191	140p									2N713/4	25p				
7475	43p	74192	130p									2N716	22p				
7478	37p	74193	120p									2N717	22p				
7480	50p	74194	100p									2N718	22p				
7481	10p	74195	110p									2N719	22p				
7482	90p	74196	130p									2N720	22p				
7483	90p	74197	130p									2N721	22p				
7484	100p	74198	270p									2N722	22p				
7485	120p	74199	270p									2N723	22p				
7486	30p	74221	175p									2N724	22p				
7489	240p	74251	150p									2N725	22p				
7490	30p	74295	87p									2N726	22p				
7491	80p	74278	300p									2N727	22p				
7492	50p	74279	150p									2N728	22p				
7493	30p	74283	220p									2N729	22p				
7494	90p	74284	470p									2N730	22p				
7495	75p	74285	200p									2N731	22p				
7496	90p	74290	100p									2N732	22p				
7497	200p	74293	100p									2N733	22p				
74100	140p	74296	220p									2N734	22p				
74104	75p	74308	100p									2N735	22p				
74105	75p	74306	100p									2N736	22p				
74107	30p	74307	220p									2N737	22p				
74108	90p	74309	220p									2N738	22p				
74110	90p	74303	240p									2N739	22p				
74111	75p	74480	280p									2N740	22p				

INDEX TO ADVERTISERS

A.B.C. Electronics	391	Electrovalve Ltd.	427	Precision Petite	444
Ace Mailtronix Ltd.	456	Flairline Supplies	444	Progressive Radio	450
Adam Hall (P. E. Supplies)	460	Fotherby, Willis Electronics Ltd.	453	Proto Design	463
Aitken Bros.	440	Fraser-Manning Ltd.	460	Radio Component Specialists	cover iii
Alben Engineering	390	Gemini Electronics	450	Radio & T.V. Components	386
Alcon Instruments	455	Government Communications Headquarters	461	Ramar Constructor Service	462
Astra-Pak	427	Greenweld Electronics	397	R.S.T. Valve Mail Order	454
Aura Sounds	454	H.M. Electronics	461	Saga	393
Bamber B. Electronics	388	Harversons	440	Sandwell Plant Ltd.	461
Baron	458	Heathkit Ltd.	398	Saxon Entertainments	392, 393
Barrie Electronics	452	Home Radio	418	Scientific Wire Co.	462
Bi-Pak	394, 395	I.C.S. Intertex	455, 461	Sentinel Supply	390
Birkett J.	456	I.L.P. Electronics	449, 457	Sinclair	421
Boffin Projects	460	J. C. Jones	460	Sintel Limited	461
British National Radio & Electronics School	386, 439	J.W.B. Radio	460	Special Products	455
Cambridge Kits	461	James Cooper (Electronics) Ltd.	461	Sterling Sound	453, 459
Cambridge Learning	443	Lynx Electronics	418	Sugden A.R.	388
Chromatronics	387	Maplin Electronics Supplies	cover iv	Swanley Electronics	444
Clef Products	456	Marshall A. & Sons	451	Tamba Electronics	427
Component Centre, The	391	Minikits Electronics	462	Technomatic Ltd.	464
Computabits Ltd.	463	Modern Book Co.	463	Telecraft	458
Continental Specialties	417	Moulded Electronic Components Int. Ltd. (M.E.C.I.)	418	Tempus	454
Copespeed	460	Orchard Limited	452, 464	Tirro Electronics	398
Copper Supplies	462	Osmabet Ltd.	444	T.K. Electronics	453
Crecent Radio Ltd.	463	P.K.G. Electronics	462	Trampus Electronics Ltd.	440
Crimson Elektrik	391	Phoenix Electronics Ltd.	398	T.U.A.C.	389
Crofton Electronics	462	Phonosonics	396, 397	Watford Electronics	cover ii
C.R. Supply Co.	460			Williams, Michael Electronics	450
D.S.M. Electronics Ltd.	460			Wilmslow Audio	458
Davian Electronics	386			Xerox Radio	463
Doram Electronics	459			Zartronix	463
E.D.A.	390				
Edencombe Ltd.	460				

VAT INCLUSIVE PRICES—ADD 25p P. & P.—No other extras

MAIL ORDER ONLY

Govt., Colleges orders accepted

TECHNOMATIC LTD.

54 SANDHURST ROAD, LONDON NW9

Tel: 01-204 4333
Telex: 922800

PLEASE SEND SAE FOR OUR CATALOGUE

MCM6810
128 x 8 STATIC RAM
24 pin DIL £4.32

ZN425E
£4.20

ZENERS
2-7V-33V
400mW 11p
1W 22p

TRIACS
Plastic
3A 400V 85p
6A 400V 107p
8A 500V 120p
10A 500V 160p
15A 500V 225p
15A 500V 225p
40A30 130p
40A69 130p
BR100 36p

DIODES
BY127 12p
OA47 9p
OA81 15p
OA85 15p
OA90 9p
OA91 9p
OA95 9p
OA200 10p
IN1914 4p
IN1916 7p
IN4001/2 6p
IN4003/4 7p
IN4005/7 8p
IN4148 4p
IN5401/3 15p
IN5404/7 20p

BRIDGE RECTIFIERS
1A 50V 25p
1A 100V 37p
1A 400V 31p
2A 50V 40p
2A 100V 45p
2A 200V 55p
3A 200V 70p
3A 400V 80p
4A 100V 90p
4A 200V 90p
6A 50V 90p
8A 100V 180p
8A 400V 120p
8A 50V 90p
25A 400V 430p

U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductor components. The stereo kit uses 22 semiconductor components. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms, 7W into 15 ohms. Response 20c/s to 30kc/s. Input 100mV. High imp. Size 9 1/2 x 3 x 2 1/2 in. A/C mains operated.

Mono kit **£11.25** Stereo kit **£18** post 45p
Easy to build. Full instructions supplied.



ELAC 10 inch £4.50

Ribbed cone. Large ceramic magnet 50-16,000 c/s. Bass resonance 55 c/s. 10W. 15 ohm impedance.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp. per channel, with volume control and P.C. Board. Can be ganged to make multi-way mixers.

£2.95 Post 35p

MAINS TRANSFORMERS

	ALL POST 50p each
250-0-250V 70mA, 6 3 2A	£3.45
250-0-250 80mA, 6 3V 3 5A, 6 3V 1A or 5V 2A	£4.60
350-0-350 80mA, 6 3V 3 5A, 6 3V 1A or 5V 2A	£5.80
300-0-300 120mA 2 x 6 3V 2A C.T., 6 3V 2A	£8.50
220V 45mA, 6 3V 2A	£1.75
HEATER TRANS. 6 3V 3A, £1.45, 1/2 amp, £1.00	
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2A, 3A, 4A, 5A, 6A, 8A, 10A, 12A, 15A, 18A, 21A and 30V	£5.30
1A, 6 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£5.30
2A, 6 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.50
3A, 6 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.00
5A, 6 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14.50
5, 8, 10, 16V 1A £2, 12V 100mA £1, 12V 300mA £1, 12V 750mA £1.30, 40V 2A tapped 10V or 20V £2.95, 20V 3A £2, 40V 2A £2.95, 30V 5A, 34V 2A ct. £3.75, 2 - 18V 6A £9	
20-0-20V 1A £2.95, 30V 1A £2.75, 20V 1A £2.20, 60V, 40V, 20V or 20-0-20V, 1A £3.50, 30-0-30 2A £7	
AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W £5; 250W £8; 400W £7; 500W £8.	
CHARGER TRANSFORMERS Input 200/250V for 6 or 12V 1 1/2 £2.75; 4A £5.20	
FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs 1A 40p; 2A 55p; 4A 95p. HALF WAVE 12V 1 1/2A 25p.	


GOODMAN'S COMPACT 12in BASS WOOFER

Standard 12in diameter fixing with cut sides 10 1/2 in square 14,000 gauss magnet 30 watt r.m.s. 4 ohm impedance. Bass resonance 30 c.p.s. Frequency response 30-8,000 c.p.s. £10.95 each. Post £1.00. 20 Watt model £9.95.



ADAstra 3-3W STEREO AMPLIFIER.

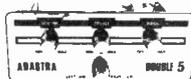10 Transistor Push-Pull Ready built with volume, treble and bass controls. 240V operated. Size 8 x 3 x 6in. **£10.95**



HEATING ELEMENTS WAFER THIN

Size 10 1/4 x 8 1/2 x 1/4 in Operating voltage 200-250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters etc. Must be clamped between two sheets of metal or asbestos.

ONLY **40p** EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity

E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter And crossover. State 4 or 8 ohm

10W Model **£7.95** Post 45p

15W model **£10.50** Post 65p

20W model **£11.50** Post 75p



TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A" 20 x 13 x 12in.

For 12in. dia. or 10in. speaker.

Illustrated **£14.50** Post £1.60

MODEL "B" BOOKSHELF

For 13 x 8in. EMI **£8.50** Post £1

Loudspeakers.

R.C.S. BOOKSHELF complete with speakers. Size 14 x 9 x 6in. approx.

Response 50 to 14,000 cps

6 watt rms 8 ohms **£16 pair** Post £1.30

ACOUSTIC WADDING 18in. wide, 20 ft.



MONO PRE-AMPLIFIER

A mains operated solid state pre-amplifier unit designed to complement amplifiers without low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket input and output are rear located. AC mains 240V. Size 6 x 3 x 2 1/2 in.

£4.50 ea. — 2 for £8. Post 50p.



BAKER MAJOR 12 INCH £15

30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms available.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle, 19 x 12 1/2 in. instructions. As illustrated. **£19** Post £1 60

'BIG SOUND' BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s. Bass Resonance 55 c/s

GROUP "25"	£12
12in 30W	Post £1
4, 8 or 16 ohms	
GROUP "35"	£14
12in 40W	Post £1
4, 8 or 16 ohms.	
GROUP 50/12in	£21
12in 60W	Post £1 60
4 or 8 or 16 ohms with aluminium presence dome	
GROUP 50/15in	£26
15in 75W	Post £1 60
8 or 16 ohms	

Disco, Group - PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.

BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music 4 way mixing Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£75** Carr £1 50



NEW "DISCO 100 WATT" £59 Carr. £1 20
ALL TRANSISTOR AMPLIFIER
2 inputs 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. Made by Jennings

PW SOUND TO LIGHT DISPLAY
Complete kit of parts with R.C.S. printed circuit. Three 1,000W channels AS featured in Practical Wireless **£14.00**
CABINET extra £3

GOODMANS CONE TWEETER
18,000 c/s 25W 8 ohm Price **£3.25**
E.M.I. 5in. mid range 25W £4.95.
E.M.I. 13 x 8in. 25W Bass Unit £10.50

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model. Four inputs. Treble, Bass, Master Volume Controls. Ideal disco, P.A. or groups. S.A.E. for **£94** details 5 speaker outputs 3 or 8 or 15 ohm 100V line to order. Suitable carrying case £16.50. plus £2.50 carr

LOW VOLTAGE ELECTROLYTICS
1 1/2 4 5 8 16 25 30 50 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p; 100mF 12V 17p; 25V 35p; 50V 47p; 100V 70p; 200mF 6V 25p; 25V 42p; 250mF 50V 62p; 300mF 25V 47p; 50V 65p; 390mF 10V £1.60, 4700mF 63V £1.20, 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.60; 1200/76V 80p.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS
All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required **£2.95** Post 45p

R.C.S. POWER PACK KIT
12V, 750mA Complete with printed circuit board and assembly instructions **£3.35** Post 30p
12V 300mA KIT. £3.15.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE £1.45
Ideal for Mike, Tape, P.U., Guitar. Battery 9-12V or H.T. line 200-300V d.c. operation Size 1 1/2 x 3 1/2 in 25 c/s to 25 kc/s 26 dB gain. For valve or transistor equipment. Instructions supplied.

ELECTRO MAGNETIC PENDULUM MECHANISM 95p Post 30p
1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc.


BSR HI-FI AUTOCHANGER
Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee, a.c. 200/250V. Size 13 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE. **£12.95** All Post 75p
Single Player version **£15.50**
BSR P128 with Magnetic Cartridge **£24.50**
GARRARD MINICHANGER plays all records **£9.95**
BSR P163 BELT DRIVE DECK, less cartridge **£27.50**



BSR DE LUXE AUTOCHANGER
Features balanced arm, Cueing device, stylus pressure gauge, 3 speed — plays all size records. Fitted with stereo ceramic cartridge. Size: 13 x 12 1/2 in. Post £1.10
Or with Sonotone V100 magnetic cartridge **£21.50**



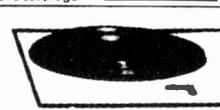R.C.S. DISCO DECK SINGLE RECORD PLAYER
Fitted with auto stop, stereo compatible cartridge, Baseplate. Size 11 x 8 1/2 in. Turntable Size 7in diameter. a.c. mains 220/250V. 3 speeds plays all size records **£7.95** Post 45p
Two for £15. Post 75p.



HEAVY METAL PLINTHS
With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 x 7 1/2 in. Model "B". Size 16 x 13 1/2 x 7 1/2 in. **£6.50** Post £1 30
Extra Large Plinth and Cover. For transcription decks Size 20 x 17 1/2 x 9in uncut board Callers only £18.50.

TINTED PLASTIC COVERS ONLY
Sizes: 14 1/2 x 12 1/2 x 4 1/2 in. £3.14 x 12 1/2 x 2 1/2 in. £3.50, 16 1/2 x 14 1/2 x 3 in. £3.75, 16 1/2 x 14 1/2 x 4 in. £4.19, 14 1/2 x 4 1/2 in. £4.15 x 13 1/2 x 3 in. £3.50, 17 1/2 x 9 1/2 x 3 in. £3.75
Ideal for record decks, tape decks, etc. Post 75p.

BAKER HI-FI SPEAKERS HIGH QUALITY—BRITISH MADE

SUPERB 12in 25 watt £22 Post £1 60

Quality loudspeaker, low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25 c/s Flux Density 16,500 gauss Useful response 20-17,000 c/s 8 or 16 ohms models



AUDITORIUM 12in 35 watt £21 Post £1 60

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques. Bass Resonance 35 c/s Flux Density 15,000 gauss Useful response 25-16,000 c/s 8 or 16 ohms models



AUDITORIUM 15in 45 watt £26 Post £1 60

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in. sides, 6 x 4 in. 95p; 8 x 6 in. £1.40; 10 x 7 in. £1.55; 14 x 9 in. £1.90; 16 x 6 in. £1.85; 12 x 3 in. £1.20; 16 x 10 in. £2.20; 12 x 8 in. £1.70.
ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in 20p; 8 x 6 in. 40p; 10 x 7 in. 50p; 12 x 5 in. 50p; 12 x 8 in. 50p; 16 x 6 in. 75p; 14 x 9 in. 80p; 12 x 12 in. 80p; 16 x 10 in. 95p.
ALUMINIUM ANGLE BRACKET, 6 x 1/2 x 3 in. 15p.
ALUMINIUM BOXES, MANY SIZES IN STOCK: 4 x 2 x 2 in. 55p; 3 x 2 x 1 in. 55p; 6 x 4 x 2 in. 65p; 8 x 6 x 3 in. £1; 9 x 4 x 4 in. £1.20; 12 x 4 x 4 in. £1.50

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER
Suitable for cassettes, and all sizes of tape reels. a.c. mains 200/240V Leaflet S.A.E. **£4.95** Post 50p



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

Published approximately on the 15th of each month by IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/Sia) Ltd., South Africa—Central News Agency Ltd.

Subscriptions not available at home or overseas. Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

MAPLIN

in a modern world of electronics


100W RMS STEREO DISCO

A genuine 100W RMS per channel (Both channels driven) stereo disco with auto fade on microphone, VU meters, full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41 price 25p. Cabinet comes complete with lid and carrying handles.




WIDE RANGE OF COILS & CHOKES

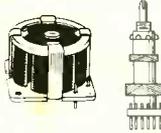Component section in our catalogue includes a wide range of coils, pot cores, ready-wound coils and chokes from microHenries to Henries, plus ranges of Denco coils and i.f. transformers etc.




T.V. GAME

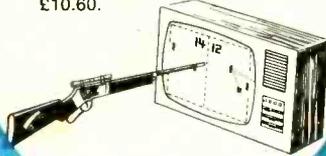A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 35p. Add-on rifle kit only £10.60.




THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists...an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £65 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES 49 price 25p.

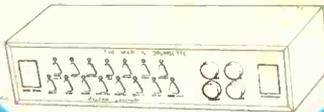

ELECTRONIC ORGAN

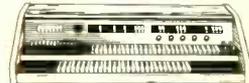The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks yet—(they're coming soon) but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



Who says the Maplin Catalogue's worth having?

"in our 'musts' for readers-to-collect list"
—P.E.

"contains just about everything the DIY electronic enthusiast requires"
—P.W.

"probably the most comprehensive catalogue we have ever come across"
—E.E.

"has been carefully prepared and is very well presented"
—R.E.C.

"makes the job of ordering components an easy, accurate and enjoyable pastime"
—P.W.

"Only one word describes the publication—superb!"
—E.T.I.

OVER 60,000 COPIES SOLD. DON'T MISS OUT!
SEND 60p NOW

MAPLIN ELECTRONIC SUPPLIES

P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 715155
Shop: 284 London Road, Westcliff-on-Sea,
Essex. (Closed on Monday) Tele-
phone: Southend (0702) 715157.

Our bi-Monthly newsletter keeps you up to date with latest guaranteed prices—our latest special offers—details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

Name _____

Address _____

