


PRACTICAL

Australia 85c New Zealand 85c South Africa 80c Malaysia \$2.75

# ELECTRONICS

FEBRUARY 1979

50p

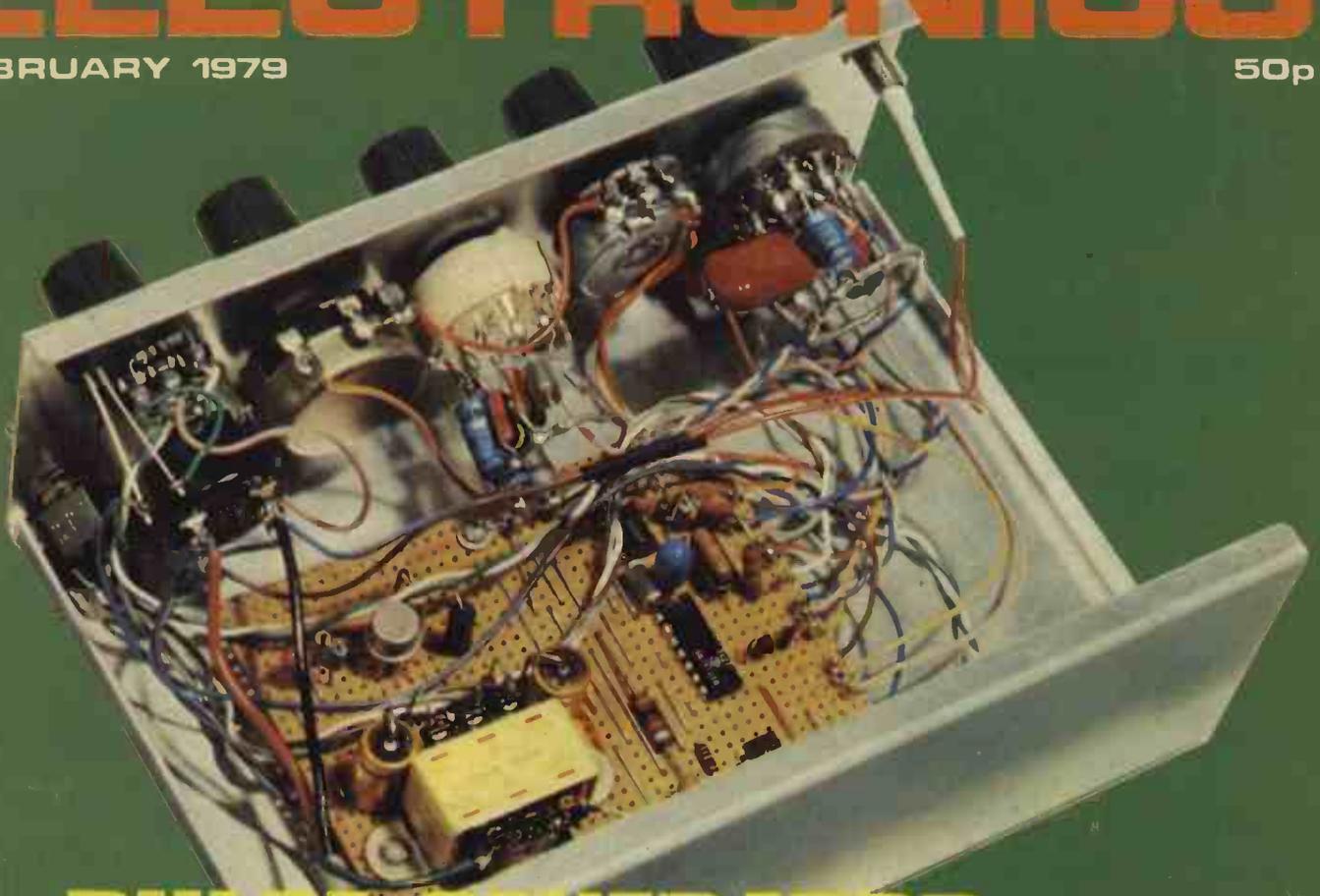

## PULSE GENERATOR



Also inside... ● **HOME COMPUTERS**  
● **ENVIRONMENTAL THERMOMETER**

# Introducing the personal computer you've waited for. THE EXIDY SORCERER.

## SORCERER COMPUTER SYSTEM

Complete with Monitor

The Sorcerer Computer is a completely assembled and tested computer system. Standard configuration includes 63-key typewriter-style keyboard and 16-key numeric pad, Z80 processor, dual cassette I/O with remote computer control at 300 and 1200 baud data rates, RS232 serial I/O for communications, parallel port for direct Centronics printer attachment, 4K ROM operating system, 8K ROM Microsoft BASIC in Rom Pac™ cartridge, composite video of 64 char/line 30 line/ screen, 128 upper/lower case ASCII set and 128 user-defined graphic symbols, operation manual, BASIC programming manual and cassette/video cables, connection for S-100 bus expansion.

only £950 Credit facilities available. + 8% VAT



### LOOK!

- \*32K RAM on board
- \*RS232 interface \*8K BASIC ROM
- \*CUTS interface \*4K MONITOR
- \*KANSAS CITY interface \*S100 BUS
- \*User defined graphic symbols \*Z80 cpu

## KEY BOARD

756 GEORGE RISK

Brand new professional ASCII keyboards (USA) Full technical details included. RRP £60.00

Only £49.90 + 8% VAT.

Ready built, tested and guaranteed.



## COMPUTER JOYSTICK

Plugs into your Nascom P.I.O. No extras. Software and full documentation supplied. Plus free game cassette. £14.90 each £28.90 per pair

## COMP PRO Mixer

Professional audio mixer that you can build yourself and save over £100.



6 into 2 with full equalization and echo, cue and pan controls. All you need for your own recording studio is a stereo tape or cassette recorder.

This superb mixer kit has slider faders, level meters and additional auxiliary inputs.

Only £99.90 plus 8% VAT for complete kit Plus FREE power supply valued at £25.00

Ideal for

DISCOS STAGE MIXING HOME STUDIOS AND MANY OTHER APPLICATIONS

## COMPUTER COMPONENTS

Send for our Spring 1979 catalogue. 0.60p Full of Computer Components, Peripherals and systems.

# Teleplay presents the PROGRAMAGAME of all time!

TELEPLAY have produced a new product of easy to assemble cartridge games, for you and all your family, that will not go out of date just ADD each new cartridge, as it becomes available, and your colour video centre will be up to date the Teleplay way. You will save pounds in the long run. Works OK on Black and White TV.



We offer all this to you for ONLY **£28.90** + £2.31 VAT Fully Assembled £35.90

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game.

- additional cartridges NOW available include:
- Stunt Cycle - 4 games Cartridges and Hand Controls £14.90 + £1.14 VAT Fully assembled add £3.00
  - Tank Battle - Cartridge and Hand Controls £18.90 + £1.51 VAT
  - Road Race - 2 games Cartridge Controls already with basic kit £12.90 + £0.93 VAT
  - NEW - WIPE OUT cartridge - 6 games £13.90 + £1.11 VAT
- Cartridges come complete with printed case and easy to follow assembly instructions.
- All parts fully guaranteed.

## INTERESTED IN HOME COMPUTING?

**FREE B BUG** valued at £23.00 plus 10 x C12 cassettes valued at £4.00 WITH EVERY NASCOM

Start now and don't get left behind THE NASCOM 1 is here Ex-stock with full technical services

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most out of your computer. You can OBTAIN and EXCHANGE programs and other software - many now available.

- The Powerful Z80 Microprocessor Professional Keyboard 1 Kbyte Monitor in EPROM 2 Kbyte RAM (expandable) Audio Cassette interface Plugs into your domestic TV Easy construction from straightforward instructions - no drilling or special tools - Just neat soldering required.



- Only £197.50 + 8% VAT (includes p & p + insurance)
- Manuals separately 2.95
  - Z80 programming Manual 6.90
  - Z80 Technical Manual 2.95
  - PIO Technical Manual 2.95
  - Monitor quality improved 2.50
  - TV Modulator 2.50
  - Power supply suitable for NASCOM 19.90

NASCOM AD ONS - Nascom improved monitor B Bug (2K) featuring - \*Four times tape speed \*Direct text entry without ASCII \*Extended keyboard facility \*Additional useful subroutines £23.00

Nascom Software library. Send SAE for lists and prices.

BLANK C12 Racial Quality CASSETTES £4.00 for 10

All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD or ACCESS number.



**COMP** COMPUTER COMPONENTS

14 STATION ROAD · NEW BARNET · HERTFORDSHIRE · TEL: 01-441 2922 (Sales) CLOSE TO NEW BARNET BR STATION - MOORGATE LINE 01-449 6596 OPEN - 10am to 7pm - Monday to Saturday

# PRACTICAL ELECTRONICS

VOLUME 15 No. 2 FEBRUARY 1979

---

## CONSTRUCTIONAL PROJECTS

- PULSE GENERATOR** *by M. Tooley B.A. and D. Whitfield B.A.*  
A versatile piece of test equipment for trouble-shooting digital circuits 18
- ENVIRONMENTAL THERMOMETER** *by M. Plant*  
A three range instrument capable of measuring temperatures from  $-15^{\circ}\text{C}$  to  $+50^{\circ}\text{C}$  22
- P.E. MICROPRINTER—2** *by Mark Simon*  
Driver circuits, power supplies, construction and software 34
- GUITAR SOUND MULTIPROCESSOR—3** *by M. A. Sawicki M.Sc(Eng) and A. Kowalewski*  
VU driver, p.s.u. and switch control module 48
- STEREO MIXER** *by J. P. Macaulay*  
Line and dynamic microphone inputs over three channels 62

## GENERAL FEATURES

- HOME COMPUTERS** *by R. W. Coles*  
The Microprocessor miracle 28
- INGENUITY UNLIMITED**  
Versatile Timer—Heads or Tails—Novelty Doorbell—  
6-12V Convertor—Envelope Shaper 44
- SEMICONDUCTOR UPDATE** *by R. W. Coles*  
A look at some recently released devices 47
- MICROBUS** *by D.J.D.*  
A bi-monthly focus on micro's for the home constructor 59

## NEWS AND COMMENT

- EDITORIAL** 17
- MARKET PLACE**  
New products 25
- SPACEWATCH** *by Frank W. Hyde*  
High Energy Astronomical Observatory—2, Another Goonhilly, Ice Sheets 43
- INDUSTRY NOTEBOOK** *by Nexus*  
What's happening inside industry 55
- PATENTS REVIEW**  
Thought provoking ideas on file at the British Patents Office 56
- NEWS BRIEFS**  
1978 Audio Writer is P.E. Contributor—New Olde Magazine 61
- BOOK REVIEWS** 68
- BREADBOARD COMPETITION RESULTS** 68
- POINTS ARISING**  
R.C. Motor Control 68
- READOUT**  
A selection of readers' letters 68

**OUR MARCH ISSUE WILL BE ON SALE FRIDAY, 9 FEBRUARY 1979**  
(for details of contents see page 67)

---

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

**U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE**

**BAKER LOUDSPEAKER, 12 INCH, 60 WATT.**  
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.  
FULL RANGE PROFESSIONAL QUALITY. **£22.68**  
RESPONSE 30-16,000 CPS  
MASSIVE CERAMIC MAGNET  
WITH ALUMINIUM PRESENCE CENTRE DOME. Post £1.60

**BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER**  
  
Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music 4 way mixing. Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. 100 volt line model E14 extra. **£85** Carr £1.50

**TINTED PLASTIC COVERS ONLY**  
Size: 14 1/2 x 12 1/2 x 4 1/2 in. £3. 17 1/2 x 14 x 4 1/2 in. £4.50.  
16 1/2 x 14 x 4 1/2 in. £4. 15 1/2 x 13 1/2 x 4 in. £3.75.  
15 1/2 x 14 1/2 x 3 in. £3.50. 17 1/2 x 9 1/2 x 3 1/2 in. £3.  
14 1/2 x 14 1/2 x 2 1/2 in. Rosewood sides £4.  
Ideal for record decks, tape decks, etc. Post £1.

**10 WATT PER CHANNEL STEREO AMPLIFIER**  
Ready made in chassis form. Mains operated.  
Volume balance, treble and bass slider controls.  
Pick up and tape inputs. Recording output.  
Front panel size: 16 1/2 x 1 1/2 in. **£18.50**  
Chassis size: 13 x 15 in. Bargain Post 50p

**BAKER 50 WATT AMPLIFIER**  
Two inputs with volume controls. Master treble, bass and volume controls. Takes all impedance loudspeakers. **£59** Post £1.

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS**  
All parts and instructions with Zener diode printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required. **£2.95** Post 45p

**HEATING ELEMENTS WAFER THIN**  
Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200-250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.  
**ONLY 40p EACH (FOUR FOR £1.50)**  
ALL POST PAID—Discounts for quantity

**R.C.S. SOUND TO LIGHT DISPLAY MK II**  
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. **KIT = £17.00**

**ELECTRO MAGNETIC PENDULUM MECHANISM** **95p** Post 30p  
1.5V d.c. operating over 300 hours continuous on SP2 battery fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome strobe, etc.

**MINI MODULE BAFFLE KIT**  
15 x 8 1/2 in. 3-way Loudspeaker System EMI 5in. Bass 5in. Middle 3in Tweeter with 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response=60 to 20 000 C.P.S. 12 watt RMS. 8 ohms. £10-95 per kit. Two kits £20. Postage 75p.

**R.C.S. 10 WATT AMPLIFIER KIT**  
  
This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms. 7W into 15 ohms. Response 20Hz to 30kHz. Input 100mV. high imp. Size 9 1/2 x 3 1/2 in. A/C mains operated.  
Mono kit **£12.50** Stereo kit **£20** Post 45p  
Easy to build. Full instructions supplied.

**MAINS TRANSFORMERS** ALL POST 75p each  
250-0-250V 70mA. 6.3 2A £3.45  
250-0-250 80mA. 6.3V 3 5A. 6.3V 1A or 5V 2A £4.60  
300-0-300 80mA. 6.3V 3 5A. 6.3V 1A or 5V 2A £5.80  
350-0-300 120mA 2 x 6.3V 2A C.T. 6.3V 2A £8.50  
220V 60mA. 6.3V 2A £1.75  
HEATER TRANS. 6.3V 3A £1.45; 5 amp. £1.00  
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at  
2A 3.4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V  
2 x 18V 6A £3. 12.5-12V 2 amp £2.95. 25-0-25V 2 amp £4.  
20-0-20V 1A £2.95. 30V 1A £2.75. 20V 1A £2.20  
9V 3 amp £2.75. 60V. 40V. 20V or 20-0-20V. 1A £3.50.  
30-0-30 2A £7. 9V 250mA £1.30. 30V 2 amp £3.  
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V  
150W £5; 250W £6; 400W £7; 500W £8.  
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V  
1A £2.75; 3A £4; 4A £5.20.  
FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs  
1 1/2 A 55p; 4A £1.25. HALF WAVE 12V 1A 25p.

**SINGLE RECORD PLAYER**  
  
Fitted with auto stop, stereo compatible cartridge, Baseplate. Size 11 x 8 1/2 in. Turntable Size 7 in diameter a.c. mains 220-250V. 3 speeds plays all size records.  
**£7.95** Post 45p  
Two for £15. Post 75p.

**LOW VOLTAGE ELECTROLYTICS**  
1 2 4 5 8 16 25 30 50 100 200mF 15V 10p. 500mF 12V 15p.  
25V 20p. 50V 30p. 1000mF 12V 17p. 25V 35p. 50V 47p. 100V 70p.  
2000mF 6V 25p. 25V 42p. 2500mF 50V 82p. 3000mF 50V 47p.  
50V 55p. 3900mF 100V £1.80. 4700mF 63V £1.20. 5000mF 5V 25p.  
12V 42p. 25V 75p. 35V 85p. 5600mF 76V £1.60. 1200/76V 80p.

**HIGH VOLTAGE ELECTROLYTICS**  
8/350V 22p 8+8/450V 50p 50+50/300V 50p  
18/350V 30p 8+16/450V 50p 32+32/450V 75p  
32/500V 75p 16+16/450V 50p 100+100/275V 65p  
50/350V 50p 32+32/350V 50p 150+200/275V 70p

**BLANK ALUMINIUM CHASSIS, 18 SWG 2 1/2 in. sides, 6 x 4 in 95p; 8 x 6 in. £1.40; 10 x 7 in. £1.55; 14 x 9 in. £1.90; 16 x 6 in. £1.85; 12 x 3 in. £1.20; 16 x 10 in. £2.20; 12 x 8 in. £1.70.**  
**ALUMINIUM PANELS, 18 SWG, 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 5 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1; 16 x 10 in. £1.16.**  
**ALUMINIUM ANGLE BRACKET, 6 x 1/2 x 1 1/2 in. 15p.**  
**ALUMINIUM BOXES, MANY SIZES IN STOCK.**  
4 x 2 x 2 in. 88p; 3 x 2 x 1 in. 65p; 6 x 4 x 2 in. 95p; 8 x 6 x 3 in. £1.50; 9 x 4 x 4 in. £1.70; 6 x 4 x 4 in. £1.30.  
**THE "INSTANT" BULK TAPE ERASER £4.95**  
Suitable for cassettes, and all sizes of tape reels. a.c. mains 200/240V Post Leaflet S.A.E. 50p  
Head demagnetiser £4.75

**RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665**  
Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Sat, 9-5 (Closed Wednesday all day).

**PE SUSTAIN UNIT** (P.E. OCTOBER 1977)  
  
BUILD A SUSTAIN UNIT EQUAL TO THE BEST COMMERCIAL MODELS.  
**COMPLETE KIT - £7.95\***  
ALL HIGH QUALITY COMPONENTS AS SPECIFIED.  
DESIGNER APPROVED.

**FERRANTI Semiconductors BUY FROM THE SPECIALISTS!**

We can supply any Ferranti semiconductor device at the lowest prices. Send S.A.E. for our data sheet & price list.

ZNA116E £3.75*	ZNA134J £21.00*	BC415P 16p	ZTX109 12p
ZN104DE £7.50*	ZN425E £3.50*	ZTX107 11p	ZTX213 11p
ZN1034E £1.65*	ZN424E £1.20	ZTX108 10p	ZTX384W 24p

TO CLEAR: P.C.B.'s for ZNA116 D.V.M. £1.00\* the pair, while stocks last.

**ORION** Complete set of semiconductors **£9.75**  
amplifier Glass fibre PCB, printed with component locations **£3.50**

**PHASE LOCKED STEREO DECODER KIT**  
Complete kit of parts to Motorola spec. only £2.95, including MC1310P all resistors & capacitors, glass fibre p.c.b., L.E.D. & instructions. Suitable for most tuners. Dist. 0.3%, Separation 40db. 8-14 volts.

**TONE BOOSTER** (Everyday Electronics Sept. 1978)  
The Tone Booster cuts out that dead, muddy sound and brings your guitar to life! Emphasises harmonics without reducing the low notes to give your guitar a clean penetrating tone. Complete kit of all parts as specified **£3.30\***

**PE TV SOUND SEPARATOR**  
Complete set of semiconductors £2.30. High quality glass fibre p.c.b. £1.50. Murata filters: SFE6.0MA 50p. CDA6.0MC 50p.  
P & P 15p per order. Orders over £5 post free.  
All devices are top grade, brand new and to full manufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list.  
Prices do not include VAT—add 8% to items marked\*, and 12 1/2% to all others.

**DAVIAN ELECTRONICS** (Mail order, callers by appointment only).  
13 Deepdale Avenue, Royton, Oldham OL2 6XD

**TOUCH CONTROLLED LIGHTING KITS (300W)**  
A Lightdimmer with NO knob. Dimming and on/off functions are controlled by touch. Features include:  
★ No mains rewiring.  
★ Easy to build - uses one MOS IC.  
★ Switches on to preset brightness.  
★ Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy.  
★ PRICE TD300K **£9.67** TDE/K **£1.62**

**TRIAC BARGAINS**

400V Plastic Case	64p
3A	86p
6.5A with trigger	80p
8A	90p
12A	113p
16A	178p
20A	205p
25A	54p
SCR (C106D) 5A/400V	23p
Diac	

**COMPONENTS**

0.2* L.E.D.s	
Red 13p	(£1.08/10)
Green 23p	Yellow 27p
DL727 5" display	£1.62
LCD 5" 4 digit	£8.75
LDR 5" dia	54p
NEM55 31p	(4 for £1.08)
741 27p	(5 for £1.08)
LM3911 temperature control/thermometer IC	£1.08
AY-5-1224	£3.81
AY-5-1230	£5.23
ZN1034E	£1.84
ICL7106 DVM IC	£11.05
IN4001	7p
IN4148	5p
BC182L	11p
2N3819	25p

**MINI MAINS TRANSFORMERS**

Standard 240V mains primary	
100mA secondary	
6-0-6V	92p
9-0-9V	97p
12-0-12V	102p

**DIGITAL VOLT/METER/THERMOMETER KIT**  
  
Based on the 7106 single IC 3 1/2 digit D.V.M., the kit contains a PCB, resistors, capacitors, pre-sets, I.C. and 0.5" liquid crystal display. Components are also included to enable the basic D.V.M. kit to be modified to a Digital Thermometer using a single transistor as the sensor. Requires a 2 mA 9V supply (PP3 battery).  
**ONLY £23.75**

**24HR CLOCK/APPLIANCE TIMER KIT**  
  
Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC. 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £16.09  
White box (56 x 131 x 71mm) - drilled **£2.70**  
- undrilled **£2.38**  
Ready built **£24.30**

ABOVE PRICES INCLUDE V.A.T.  
Quantity discounts on request. Add 25p postage and packing. Mail order only to:  
**T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.**

# ELECTROVALUE Buying Guide

## IMPORTANT ANNOUNCEMENT

With completion of our present series of itemised advertisements, we announce release of our new catalogue, CATALOGUE No. 9 - completely revised, enlarged and best yet. SEND FOR YOUR FREE COPY NOW TO DEPT. PE279.

# Section 1

## TRANSISTORS/ZENERS

IN914	5p	2N5192	85p
IN9142	7p	2N5195	99p
IN916	6p	2N5457*	39p
IN4007	8p	2N5458*	39p
IN4148	5p	2N5459*	39p
IN5402	16p	6F40	£1.46
IN5407	20p	16F40	£1.65
IS920	10p	40HF10	£1.64
IS940	5p	40HF40	£2.28
2N697	36p	40Z50	95p
2N706	22p	40361	38p
2N930	21p	40362	35p
2N1132	24p	40406	40p
2N1302	48p	40408	40p
2N1303	48p	40412	56p
2N1304	52p	40594	£1.18
2N1305	52p	40595	£1.50
2N1306	56p	40602	75p
2N1307	56p	40636	£1.80
2N1308	60p	40673	86p
2N1309	60p	A9903	44p
2N1599-SCR	88p	AA113	9p
2N1613	23p	AA116	9p
2N1711	22p	AA117	9p
2N1893	35p	AA118	10p
2N2218	24p	AA119	9p
2N2218A	24p	AC126	30p
2N2219	24p	AC127	48p
2N2219A	24p	AC128	28p
2N2270	75p	AC151R	56p
2N2369A	22p	AC153	40p
2N2484	26p	AC153K	40p
2N2646	69p	AC176	58p
2N2904	24p	AC176K	40p
2N2904A	24p	AC187K	70p
2N2905	24p	AC188K	70p
2N2905A	24p	ACY17	92p
2N2924*	25p	ACY1B	91p
2N2925*	25p	ACY19	99p
2N2926*	25p	ACY20	70p
2N3053	26p	ACY21	85p
2N3054	73p	ACY22	50p
2N3055	70p	ACY39	£1.70
2N3391A*	41p	ACY40	45p
2N3405*	64p	ACY41	54p
2N3663*	52p	ADY136	£2.09
2N3702*	11p	AD142	90p
2N3703*	10p	AD149	80p
2N3704*	11p	AD161	96p
2N3705*	10p	AD162	96p
2N3706*	9p	AF114	27p
2N3707*	12p	AF115	30p
2N3708*	8p	AF116	30p
2N3709*	12p	AF117	34p
2N3710*	12p	AF124	25p
2N3711*	12p	AF125	32p
2N3794*	21p	AF126	25p
2N3819*	22p	AF127	36p
2N3820*	56p	AF139	32p
2N3823E*	24p	AF200U	10p
2N3904*	24p	AF239	89p
2N3906*	28p	AF279	30p
2N4036	68p	AFY12	£2.04
2N4058*	12p	AFY16	£2.69
2N4059*	12p	AFY18D	£5.74
2N4060*	12p	AFY18E	£6.15
2N4061*	12p	AFY42	£3.07
2N4062*	12p	AL102	£1.60
2N4124*	22p	ASY26	£1.39
2N4126*	27p	ASY27	£1.39
2N4286*	18p	ASY28	£1.39
2N4289*	23p	ASY29	£1.39
2N4291*	24p	AU111	£2.25
2N4292*	21p	AUY21	£7.31
2N4303*	30p	AUY22	£10.95
2N4410*	39p	BO126-SCR	30p
2N4443	£1.14	BO140-SCR	35p
2N4444	£1.50	BO226-SCR	35p
2N4906	£1.00	BO240-SCR	40p
2N4915	£1.00	BO246-SCR	96p
2N4991	80p	BO680	10p
2N5062*-SCR	45p	B1906	38p
2N5163*	24p	B1912	38p

BA102	28p	BCY58	15p
BA127D	4p	BCY59	16p
BA133F	9p	BCY70	18p
BA138	20p	BCY71	18p
BA145	19p	BCY72	18p
BA156	14p	BCY78	25p
BA379	25p	BD130	45p
BAX13	4p	BD131	62p
BB103B	37p	BD132	77p
BB103G	37p	BD135*	36p
BB104G*	53p	BD136*	42p
BB105B	28p	BD139*	41p
BB109G*	39p	BD140*	46p
BC107A	14p	BDX18N	£1.10
BC107B	14p	BDY12	90p
BC108A	14p	BDY20	50p
BC108B	14p	BF115	38p
BC108C	14p	BF167	30p
BC109B	14p	BF173	34p
BC109C	14p	BF177	24p
BC121W	20p	BF178	24p
BC122Y	61p	BF194*	18p
BC125*	20p	BF195*	17p
BC126*	20p	BF244B	30p
BC140	43p	BF254*	14p
BC147A*	21p	BF255*	14p
BC147B*	21p	BF457*	36p
BC148A*	21p	BF458*	37p
BC148B*	21p	BF459*	40p
BC148C*	21p	BFR39*	24p
BC148C*	21p	BFR40*	24p
BC149C*	21p	BFR41*	24p
BC154*	16p	BFR79*	24p
BC157A*	21p	BFR80*	24p
BC157B*	21p	BFR81*	24p
BC158B*	21p	BFT66	£1.83
BC1598*	21p	BFX29	24p
BC160	49p	BFX84	24p
BC167A*	8p	BFX85	24p
BC167B*	12p	BFX87	24p
BC168A*	8p	BFX88	24p
BC168B*	12p	BFY50	24p
BC168C*	8p	BFY51	24p
BC169B*	8p	BFY52	24p
BC169C*	12p	BFY90	£1.05
BC177A	18p	BR81WA	80p
BC177B	20p	BR92QA	£1.36
BC178A	16p	BRY39	60p
BC178B	17p	BSX20	22p
BC179B	20p	BSX46	45p
BC182L*	12p	BSX63	£3.89
BC182*	12p	BT106	£1.47
BC183L*	12p	BT107	£1.60
BC183*	12p	BU105	£2.50
BC184L*	12p	BU208	£3.90
BC184*	12p	BUX28	£4.20
BC202Y	75p	BY164	8p
BC212L*	12p	BY238	8p
BC212*	12p	BYX38-300	65p
BC213L*	12p	BYX38-300R	65p
BC213*	12p	C106D1	45p
BC214L*	12p	C0326-SCR	£4.40N
BC214*	12p	C0340-SCR	£5.14N
BC238B*	8p	C407*	17p
BC238C*	8p	C1406	90p
BC239C*	12p	C1412	90p
BC257A*	8p	CS2925	20p
BC257B*	8p	E99A40-Triac	£7.87N
BC258A*	8p	E2506	£1.48
BC258B*	8p	E2512	£1.74
BC259B*	8p	MJ481	£1.48
BC267	16p	MJ491	£1.63
BC268C	17p	MJ2955	78p
BC269C	18p	MJE340	78p
BC300	26p	MJE2955	72p
BC301	24p	MJE3055	68p
BC303	30p	MKY7C38E	70p
BC327*	16p	MPF102*	44p
BC328*	12p	MPS6531*	24p
BC337*	14p	MPS6534*	25p
BC338*	12p	NAS206.S.5-SCR	81p
BC447	29p		
BCY31A	96p		

## Catalogue No. 9 now ready

NAS0164W3-Triac	58p	ZTX500*	15p
NAS0654X5-Triac	80p	ZTX502*	17p
NAS0654W4-Triac	£1.04	ZTX503*	19p
NAS1001X5-Triac	60p	ZTX504*	22p
NAS1004W5-Triac	£1.10	ZTX530*	12p
NAS1004X5-Triac	£1.04	ZTX530*	8p
NKT211	20p		
NKT212	20p		
NKT213	20p		
NKT274	20p		
NKT275	20p		
OA47	12p		
OA90	6p		
OA91	6p		
OA95	8p		
OA202	10p		
OC28	£1.02		
OC29	£1.07		
OC35	£1.07		
OC36	£1.02		
OC45	£1.15		
OC71	70p		
OC72	70p		
OC75	36p		
OC81	80p		
OC83	70p		
OC84	70p		
PM7A2	£2.68		
PN70*	5p		
PN72*	5p		
PN109*	5p		
PN1613*	5p		
PN2904*	5p		
SI10M1*	10p		
T2700D	£1.55		
T2800D-Triac	£1.04		
TAG3-400-SCR	£1.00		
TAG302-400-Triac	85p		
TAG302-600-Triac	£1.05		
TIP31A	45p		
TIP32A	45p		
TIP41A	60p		
TIP41C	60p		
TIP42A	60p		
TIP42C	60p		
TIS43*	35p		
W02	25p		
ZTX107*	12p		
ZTX108*	11p		
ZTX109*	12p		
ZTX300*	12p		
ZTX301*	16p		
ZTX302*	14p		
ZTX303*	18p		
ZTX304*	21p		
ZTX330*	8p		
ZTX331*	19p		
ZTX500*	12p		
HEAT SINKS			
Type Drilled			
2PI	-	53p	
2YT03 1 x T03	-	54p	
2YT0661 x T066	-	57p	
2.75R	-	£2.80	
5.5R	-	£3.95	
5F T05 clip	-	10p	
5F2 T05 clip	-	10p	
6W1	-	£2.05	
6W4 2 x T03	-	£2.25	
100NA	-	88p	
100NC 2 x T03	-	£1.14	
17C2 2 x AD161	-	20p	
18F T018 clip	-	10p	
18F2 T018 clip	-	10p	
224F T01 clip	-	10p	
244F 001 clip	-	10p	
268F 003 clip	-	10p	
A1032 T01 clip	-	6p	
A1053 2 x T01 clip	-	8p	
A1058 1 x T03	-	22p	
T0921 T092 clip	-	7p	
T0922 2 x T092 clip	-	9p	
TV2 T086	-	24p	
TV3 T03	-	25p	
TV4 80131	-	21p	
TV5 T0220	-	21p	
ZENER DIODES			
400mW 2.7-33V	9p		
1.3W 3.3-200V	15p		
1.5W 3.3-75V	55p		
(1.5W are metal case)			
20W 7.5V-75V			
		£1.25 each	
MOTOROLA			
Micro processor Evaluation Kit (for M.680 Microcomputer)			
		£175.87 + VAT (net)	
To remind you			
Section 2 - Capacitors			
Section 3 - Opto-Electronics			
Section 4 - Resistors, Pots			
Section 5 - Hardware etc.			
WE ARE NOW NATIONAL DISTRIBUTORS FOR			
NASCOM I MICROCOMPUTER KITS			
for delivery from stock, net from			
£197.50 + V.A.T.			
Quantity discounts			
Trade Enquiries Invited			
All communications, orders, etc., to Dept. PE279			

- GOODS SENT POST FREE U.K. WITH C.W.O. orders over £5 list value. If under, add 27p handling charge.
- ATTRACTIVE DISCOUNTS on C.W.O. mail orders—5% where list value is over £10, 10% where list value is over £25.
- TOP QUALITY MERCHANDISE - ALL GUARANTEED.
- V.A.T.— Add 8% to value of order. For items marked\*, add 12½%.

- For ACCESS or BARCLAYCARD orders, just phone or write your number. No discounts allowable.
- No discounts allowable on prices marked NET or N.
- OUR COMPUTER-AIDED SERVICE TAKES GOOD CARE OF YOUR ORDER NO MATTER HOW LARGE OR SMALL.
- Comprehensive price list free on request.

Every effort is made to ensure accuracy of information at time of going to press. Prices charged are those shown in our current price list.

# ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN,  
EGHAM, SURREY TW20 OHB  
Telephone Egham 3603 Telex 264475

Northern Branch - 680, BURNAGE LANE,  
BURNAGE, MANCHESTER M19 1NA(061)432 4945



# KITS! \* KITS! \* KITS!

You must try our fabulous new range of 'ELEKITS' for an easy build introduction to electronics. All kits, and there are many to choose from, come complete with case, easy to follow instructions and ALL COMPONENTS. Battery powered (not supplied) for safety and economy - ELEKITS will give hours of enjoyment - learning as you build. A small selection from the 'ELEKIT' range is shown below.

ACE MAILTRONIX LTD  
Dept. PE, Tootal Street  
Wakefield, W. Yorkshire WF1 5JR

Watch this space for future kits!

**NEW**  
**FABULOUS**  
**ELEKITS**  
FOR FREE BROCHURE  
SEND S.A.E.

only **£11.45**  
**ROULETTE**

**MINI ORGAN**  
**£7.95**  
only

**MORSE TRAINER**  
**£4.95**  
GREAT VALUE

ALL KIT PRICES INCLUDE V.A.T

### COMPONENTS

The ACE 2nd edition illustrated catalogue shows a considerably enlarged range of components, modules, 'Elekits'. Many PRICE REDUCTIONS from edition one. Component range includes - CAPACITORS, HARDWARE, CASES, LED's, VERO PRODUCTS, RESISTORS, RS COMPONENTS, TRANSISTORS, DIODES, SCR's, IC's (Linear, TTL, CMOS, Audio), SWITCHES, PLUG/SOCKETS, BOOKS, TRANSFORMERS, TOOLS, SPEAKERS AND TEST EQUIPMENT. Typical VAT inclusive prices:-

LED's RED . . . . .	15p	2N3702/3/4/5 . . . . .	11p
LED's GREEN . . . . .	25p	2N3819 . . . . .	24p
8-pin IC SKT . . . . .	15p	OA90/91 . . . . .	7p
AC126 . . . . .	20p	IN4148 . . . . .	4p
AC128 . . . . .	27p	IN4001 . . . . .	5p
BC107/8/9 . . . . .	13p	W04 . . . . .	25p
BC177/8/9 . . . . .	19p	Zener BZY88 . . . . .	12p
BC182/3/4L . . . . .	11p	741 8-pin. . . . .	22p
BC212/3/4L . . . . .	11p	555 . . . . .	35p
BC547/8/9 . . . . .	13p	4001 . . . . .	20p
BC557/8/9 . . . . .	15p	7400 . . . . .	15p
BCY70/71 . . . . .	20p	7490 . . . . .	62p
BFY50/1/2 . . . . .	23p	Push sw. . . . .	16p
OC71 . . . . .	16p	Slide toggle . . . . .	19p
TIS43 . . . . .	35p	W/C switches . . . . .	54p
ZTX107/8/9 . . . . .	14p	O.25 CF Res. . . . .	6p per 3
2N2926G. . . . .	13p		
2N3055 . . . . .	54p		

### MODULES

Ready built.  
Power supplies 1, 2 and 3 rail,  
Fixed and variable.  
DPM's 3 1/2 digit. LED and LCD  
Count/display 4 and 6 digit.



SEND 30p FOR THE ACE ILLUSTRATED CATALOGUE WHICH INCLUDES FULL LIST OF COMPONENTS, KITS AND READY-MADE MODULES. 30p REFUNDED WITH FIRST ORDER OF £5 OR MORE.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

STEREO PRE-AMPLIFIER BOARD, Tone Control Board, Filter Board from 60 + 60  
Watt Hi-Fi Amplifier with suggested assembly and circuits @ £3.50.  
PNP VERSION OF 2N 3055 BDX 94 @ 75p each.  
100 MINIATURE DIODES CV 9637 with preformed leads @ 50p.  
POLYSTYRENE CAPACITORS suffix type 12, 15, 20, 25, 30, 50, 56, 100, 120, 1000pf. All at 20p doz.  
WIRE ENDED CRYSTALS 28KHz, 28.5KHz, 31.5KHz. All at 50p each.  
TRANSISTORS BC 183, BC 548, BC 549. All 10p, 6 for 50p.  
McMURDO 8 PIN PLUG @ 20p, 8 PIN SOCKET @ 20p, COVER @ 15p.  
3 GANG VARIABLE CAPACITOR 25 + 25 + 25pf @ 75p.  
10 Amp S.C.R.'s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p,  
400mW ZENERS unmarked Good 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v,  
33v, 36 volt. All at 10 for 40p.  
GLASS WIRE ENDED MERCURY SWITCHES @ 25p.  
MC 3340 ATTENUATOR I.C. with data @ 50p.  
X BAND GUNN DIODES with data @ £1.65 each.  
MINIATURE ROTARY SWITCHES 3 Pole 3 way @ 40p, 2 Pole 4 way @ 20p, 1 Pole 10 way 2 Bank @ 40p.  
10 WATT ZENERS 18v, 33v, 57v, 100 volt. All 30p each.  
DIE CAST ALLOY BOXES 6" x 4" x 2" @ £1.15.  
TUBULAR TANTALUM CAPACITORS 2.2uf 20v.w., 68uf 15v.w., 100uf 20v.w., 150uf 20v.w. All at 5p each.  
10 MULTI-TURN TRIM-POTS Assorted for 60p.  
50 BC 107-8-9 TRANSISTORS assorted untested @ 57p.  
ELECTROLYTIC CAPACITORS 220uf 40v.w. @ 40p, 3,300uf 63v.w. @ 50p, 4500uf 25v.w., 6400uf 25v.w. @ 25p.  
UNIJUNCTION TRANSISTORS 2N 4871 @ 22p, 22N 6028 @ 25p, 2N 6029 @ 25p, MEU 21 @ 22p, MU 4894 @ 22p, 4JDSE29 @ 22p, TIS 43 Type @ 22p.  
30 ASSORTED 10XAJ CRYSTALS @ £1.10, 20 FT 243 CRYSTALS assorted @ £1.50, 20 FT 241A CRYSTALS assorted @ £1.10.  
MULLARD TAA 320 M.O.S.T. PRE-AMPLIFIERS I.C. with circuits @ 35p.  
PLASTIC BC 107, BC 108, BC 177 TRANSISTORS 8p, 10 for 60p.  
MULLARD STRIPLINE 800 MHz NPN BF 362 @ 25p.  
200 ASSORTED 1/2 watt RESISTORS for 75p.  
50 2 WATT ASSORTED ZENERS untested @ 57p.  
600 MHz 8 DIGIT FREQUENCY COUNTER @ £115.  
MAINS TRANSFORMERS 240 volt input. Type 1, 24 volt tapped at 14 volt 1 amp @ £1.30 (P&P 25p). Type 2, 22-0-22 volt 500mA @ £1.60 (P&P 25p). Type 3, 45 volt 6 amp @ £4.50 (P&P 95p). Type 4, 20 volt 1 amp twice 10 volt 1 amp twice @ £4.50 (P&P 95p). Type 5, 45 volt 2 amp 45 volt 500 mA @ £3.50 (P&P 85p). Type 6, 16 volt 2 amp @ £1.60 (P&P 25p). Type 7, 24 volt 1.75 amp @ £1.60 (P&P 25p). Type 8, 30 volt 1 amp @ £1.60 (P&P 25p). Type 9, 13-0-13 volt 1 amp @ £1.60 (P&P 25p). Type 10, 22 volt 500 mA @ 88p (P&P 20p). Type 11, 12 volt 100 mA @ 88p (P&P 20p). Type 12, 22 volt 1 amp, 7.5 volt 500 mA, 6v 1 amp @ £1.60 (P&P 25p). Type 13, 16.5 volt 1 amp @ £1.60 (P&P 25p). Type 14, 12 volt 1 amp @ £1.60 (P&P 25p). Type 15, 32-0-32 volt 500 mA @ £1.60 (P&P 25p).

Please add 20p for post and packing, on U.K. orders under £2, unless stated otherwise. Overseas post at cost.


**J. BIRKETT**  
**RADIO COMPONENT SUPPLIES**  
25 The Strait, Lincoln LN2 1JF Tel. 20767

## AT LAST! AVAILABLE IN KIT FORM
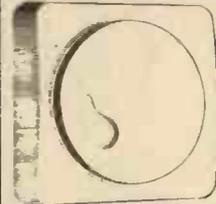
### SEEMET THE FAMOUS POCKETSIZE METAL DETECTOR



Seemet readily detects concealed ferrous and non-ferrous metals within range of its detector field. Ideal for finding concealed pipes, wires, nails etc. One-handed operation, uses standard PP3 Battery (not supplied).  
**ONLY £3.25 plus p. & p. 25p.** (inc. VAT), full instructions supplied.



### UNBEATABLE DIMMER OFFER

from Britain's largest Dimmer Makers.  
Complete Kit of Parts for our VCL 500M, 500W Dimmer Switch.  
**Only £2.00, plus p. & p. 25p.** (inc. VAT) full instructions supplied.  
Send coupon below with your remittance.

Please supply: — PE4 NAME \_\_\_\_\_  
 SEEMET KITS at £3.50 incl. of p. & p. ADDRESS \_\_\_\_\_  
 DIMMER KITS at £2.25 inc. of p. & p. \_\_\_\_\_  
I enclose cheque/P.O. POSTCODE \_\_\_\_\_  
for £..... BLOCK CAPS PLEASE

**Fotherby, Willis Electronics Ltd.**  
GLADSTONE TERRACE, STANNINGLEY, LEEDS, LS28 6NE.  
Telephone: Leeds (STD 0532) 563373 Telex 557111 **GLYNWED**



# KITS FOR SYNTHESISERS, SOUND EFFECTS



**COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

**CIRCUIT AND LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

**PHOTOCOPIES** of P.E. texts for most of the kits are available—prices in our lists.

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

## P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, mixer, power supply.

Set of basic component kits from £61.00  
Set of printed circuit boards £8.99

## P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage. Details in our lists.

## FORMANT SYNTHESISER (Elektor 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

## 128-NOTE TUNE-PROGRAMMABLE SEQUENCER

(P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

Main Circuit (Nov) excl. sw's (KIT 77-1) £18.03  
Power Supply (KIT 76-3) £4.72  
Trigger Inverter and Alt. Output (KIT 76-2) £1.15  
LED Counter (KIT 76-4) £2.10  
PCB (as published) for KITS 76-1 & 3 (PCB 76A) £2.61  
PCB for KITS 76-2 & 4 (PCB 76B) £2.54

## P.E. STRING ENSEMBLE (PE Mar-July 78)

The new keyboard string-instrument synthesiser.

Basic component sets:

Power Supply (KIT 77-1) £8.77  
Tone Generator (KIT 77-2) £14.66  
Diode Gates (KIT 77-3) £18.81  
Chorus Generator (KIT 77-4) £19.08  
Voicing System (KIT 77-5) £7.38

Printed Circuit Boards:

Double-sided PCB for Power Supply, Tone Generator & Diode Gates with most of the Matrix wiring as printed tracking (PCB 77L/R) £18.40  
PCB for Chorus Generator (PCB 77C) £2.65  
PCB for Voicing System (PCB 77D) £2.62

Fuller details of kits & PCBs are in our lists.

## P.E. JOANNA PLUS ORGAN VOICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Tonk, ordinary piano, and Harpschord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and vibrato.

Set of components (excl switches) for PSU, Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuitries. (Order as KIT 71-5) £99.25  
Set of PCBs (Order as PCB SET 71-6) £29.18

## GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.69  
Alternative component set with panel switches £5.05  
Printed circuit board £1.43

## ELEKTOR ELECTRONIC PIANO (Elektor Sept 78)

A touch-sensitive, multiple-voicing 5 octave piano using the latest integrated-circuit techniques for the keying and envelope shaping and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos. Details in our lists.

## DIGITAL REVERBERATION UNIT (Elektor May 78)

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring-lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main component set (KIT 78-1) £45.45  
Extension component set (KIT 78-2) £43.36  
PCB for Kit 78-1 (PCB 78A) £2.86  
PCB for Kit 78-2 (PCB 78B) £1.06

## ANALOGUE REVERBERATION UNIT (Elektor Oct 78)

Using i.c.s. instead of spring-lines, the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main component set (KIT 83-1) £26.18  
Additional Delay Set (KIT 83-2) £18.25  
PCB (as published) to hold both above kits (PCB 9973) £4.31

## RESONANCE FILTER (Elektor Oct 78)

This filter module has been designed to allow a synthesiser to produce a more realistic simulation of natural musical instruments.

Basic component set (KIT 82-1) £15.10  
PCB (as published) (PCB 9951) £3.29

## SYNTHESISER EXTERNAL INPUT INTERFACE

(P.E. Oct 78)

This unit allows external inputs, such as guitars, microphones etc. to be processed by the circuits within a synthesiser.

Basic component set (incl PCB) (KIT 81-1) £2.94

## GUITAR MULTIPROCESSOR (P.E. Dec/Feb 78)

An extremely versatile sound processing unit capable of producing, for example, Flanging, Vibrato, Reverb, Fuzz and Tremolo as well as other fascinating sounds. May be used with most electronic instruments. Details in our lists.

## RHYTHM GENERATOR KITS

Several available—details in our lists.

## GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published.

Component set and PCB £4.62

## GUITAR SUSTAIN (P.E. Oct 77)

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches £5.13  
Component set, PCB and panel switches £3.71

## WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds

Component set (incl. PCB) £4.26

## GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £7.58  
Component set using dual rotary pot £6.89  
Printed circuit board £1.62

## FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £2.05

## TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £2.94

## TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2.51

## WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektor". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw's) £8.40

## VOLTAGE CONTROLLED FILTER (P.E. Dec 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers

Component set (incl. PCB) (Order as Kit 65-1) £7.17

## RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers

Component set (incl. PCB) (Order as Kit 59-1) £5.50

## NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 60-1) £3.64

## ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier

Component set (incl. PCB) £4.77

## ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6.68

## TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo

Component set £4.87  
Printed circuit board £1.82

## SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektor", December 1976, and includes manual and automatic control over the rate of phasing and vibrato

Component set £17.38  
Printed circuit board £2.33

## PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £3.20

## PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing

Component set (incl. PCB) £4.74

## WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3.63

## AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.87  
Component set and PCB, with-panel switches £4.83

## VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows

Component set (incl. PCB) £3.97

## 10% DISCOUNT VOUCHER (PE 72)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT) Correctly coded. C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E.

## ADD: POST & HANDLING

U.K. orders—Keyboards add £2.00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1.00 for £100 cover, etc. pro-rata. N.B. Eire, C.I., B.F.P.O., and other countries are subject to higher export postage rates.

## ADD 12½% VAT

for current rate if changed. Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list—Europe send 20p, other countries send 50p.

PHONOSONICS · DEPT. PE72 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

# AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.



LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list: Europe—send 20p; other countries—send 50p.

## KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

- 3 Octave (37 notes) £25.50
- 4 Octave (49 notes) £32.25
- 5 Octave (61 notes) £39.75

Contact Assemblies (gold-clad wire) for use with the above KBDS (1 for each note):

- Type GJ: Single-pole change-over each 25½p
- Type GA: 1 pair of contacts, normally open each 24p
- Type GB: 2 pairs of contacts, each pair normally open each 28½p
- Type GC: 3 pairs of contacts, each pair normally open each 37½p
- Type GE: 4 pairs of contacts, each pair normally open each 46½p
- Type GH: 5 pairs of contacts, each pair normally open each 58½p
- Type 4PS: 3 pairs of contacts plus single-pole changeover each 57p

Printed Circuit Boards for use with most contacts (thus eliminating much interwiring) are available. Details in our lists.

### P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

- Main component set (incl. PCB) £14.93
- Power supply set (incl. PCB) £6.28

### SYNTHESISER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

- Component and PCB (but excl sw.) £7.45

### CONSTANT DISPLAY FREQUENCY METER (PE AUG 78)

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

- Component set £24.05\*
- Printed circuit board £3.03\*

\*This kit & PCB are at 8% VAT (all others are 12½%)

### TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs.

- Standard tolerance set of components £2.96
- Superior tolerance set of components £3.76
- Regulated power supply (will drive 2 sets) £4.69

### DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

- Component set (incl. PCB) £4.58

### DISCOSTROBE (P.E. Nov. 78)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

- Basic component set £18.19
- Printed circuit board £3.46

### BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

- Pre-Amp Module Components set (incl. PCB) £3.95
- Basic Output Circuits—combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lampdriver circuits. £6.69
- Audio Amplifier Module Type PC7 £7.75

### SOUND BENDER (P.E. May 74)

A multi-purpose sound controller. The functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

### SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

## NEW PCB SERVICE

PCBS FOR ALL NEW P.E. & E.E. PROJECTS FOR WHICH PCB LAYOUTS HAVE BEEN PUBLISHED AND FOR WHICH FULL COPY-RIGHT CLEARANCE IS AVAILABLE.

LIMITED QUANTITIES ONLY FOR AN EXPERIMENTAL PERIOD.

LET US KNOW YOUR NEEDS AND WE WILL ADVISE YOU OF AVAILABILITY AND PRICES.

### INTEGRATED CIRCUITS

- 301 8-pin DIL 48p
- 318 8-pin DIL 220p
- 320-15 --- 195p
- 324 14-pin DIL 87p
- 341-15 --- 87p
- 709 8-pin DIL 48p
- 723 T05 87p
- 723 14-pin DIL 51p
- 726 T05 1005p
- 741 8-pin DIL 24p
- 748 8-pin DIL 57p
- 4007 14-pin DIL 17½p
- 4011 14-pin DIL 17½p
- 4024 14-pin DIL 46½p
- 4069 14-pin DIL 18p
- 4136 14-pin DIL 126p
- AM2833 8-pin DIL 360p
- AY10212 16-pin DIL 617p
- AY16721/6 188p
- CA3046 14-pin DIL 71p
- CA3080 8-pin DIL 63p
- CA3084 14-pin DIL 209p
- FX209 16-pin DIL 729p
- LM323 --- 562p
- M252 16-pin DIL 680p
- MC3340 8-pin DIL 150p
- MCM3810 24-pin DIL 670p
- SG3402N 14-pin DIL 262p
- STK025 --- 595p
- TDA1022 16-pin DIL 582p
- XR2207 14-pin DIL 420p
- ZN425E 16-pin DIL 375p

### TRANSISTORS

- AC128 ..... 32p
- AC176 ..... 28p
- BC107 ..... 13p
- BC108 ..... 13p
- BC109 ..... 16p
- BC109C ..... 16p
- BC177 ..... 16p
- BC184 ..... 11p
- BC187 ..... 16p
- BC204 ..... 10p
- BC209C ..... 13p
- BC213 ..... 11p

## PHONOSONICS

PRICES ARE CORRECT AT TIME OF PRESS. E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

### Random FLASHER UNIT

Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random.

£21.95

### TWIN BANK 6 LIGHT UNIT

(less lamps) LENGTH 14½ inches

BC Fitting and ES Fitting

£12.50 ea.

### Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND PLUGS IN THE SOCKET

### TYPE A SPOT

(less lamp)

BC Fitting and ES Fitting

£2.55 ea.

### TYPE B 3 BANK UNIT

(Less Lamps)

BC Fitting and ES Fitting

£8.80 ea.

### TWIN BANK 12 LIGHT UNIT

Length 31½

(less lamps)

BC Fitting and ES Fitting

£20.35 ea.


100 WATT SPOT LAMPS RED, YELLOW, GREEN 3 lamps £4.95

BLUE CLEAR £1.65 each B.C. or E.S. Fitting

ALL PRICES INCLUDE P.A.T. and POST & PACKING (where applicable to the United Kingdom only)

**ALBEN ENGINEERING CO LTD.,**  
**DEPT. PE THE CRESCENT, WORSTHORNE,**  
**BURNLEY, LANCs. Tel: Burnley 20940**

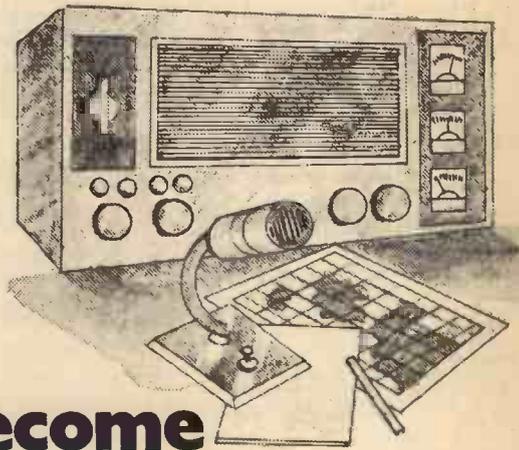Send 20p for illustrated leaflet & price list



# Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA

PEK 2/79

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O.Box 156, Jersey, Channel Islands.

**Free!** NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_ (Block caps please)

# It's W-W-WINTER S-S

## 74 SERIES TTL IC'S

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.07	7427	£0.21	7472	£0.19	74107	£0.22	74185	£0.65		
7401	£0.09	7428	£0.25	7473	£0.22	74110	£0.35	74186	£0.75		
7402	£0.09	7430	£0.08	7474	£0.22	74111	£0.55	74167	£2.00		
7403	£0.09	7432	£0.20	7475	£0.27	74118	£0.75	74174	£0.60		
7404	£0.09	7433	£0.28	7476	£0.22	74119	£1.10	74175	£0.60		
7405	£0.09	7437	£0.20	7480	£0.40	74121	£0.22	74176	£0.55		
7406	£0.22	7438	£0.20	7481	£0.80	74122	£0.35	74177	£0.55		
7407	£0.22	7440	£0.10	7482	£0.65	74123	£0.38	74180	£0.80		
7408	£0.12	7441	£0.45	7483	£0.55	74136	£0.50	74181	£1.25		
7409	£0.12	7442	£0.38	7484	£0.82	74141	£0.50	74182	£1.55		
7410	£0.09	7443	£0.68	7485	£0.65	74145	£0.54	74184	£1.00		
7411	£0.15	7444	£0.68	7486	£0.22	74150	£0.65	74190	£0.68		
7412	£0.14	7445	£0.64	7489	£1.60	74151	£0.45	74191	£0.68		
7413	£0.22	7446	£0.60	7490	£0.30	74153	£0.45	74192	£0.65		
7414	£0.45	7447	£0.45	7491	£0.60	74154	£0.80	74193	£0.60		
7416	£0.22	7448	£0.52	7492	£0.32	74155	£0.48	74194	£0.55		
7417	£0.22	7450	£0.09	7493	£0.28	74156	£0.48	74195	£0.55		
7420	£0.09	7451	£0.09	7494	£0.70	74157	£0.48	74196	£0.50		
7421	£0.19	7452	£0.09	7495	£0.45	74180	£0.55	74197	£0.58		
7422	£0.15	7453	£0.09	7496	£0.48	74161	£0.60	74198	£1.00		
7423	£0.20	7454	£0.09	7498	£0.80	74162	£0.60	74199	£1.00		
7425	£0.18	7460	£0.09	74104	£0.35	74163	£0.60	74279	£1.00		
7426	£0.21	7470	£0.24	74105	£0.35	74164	£0.65				

## CMOS I.C.'s

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.12	CD4017	£0.65	CD4031	£1.60	CD4055	£1.00
CD4001	£0.13	CD4018	£0.65	CD4035	£0.90	CD4056	£1.15
CD4002	£0.13	CD4019	£0.35	CD4037	£0.78	CD4069	£0.15
CD4006	£0.80	CD4020	£0.80	CD4040	£0.78	CD4070	£0.15
CD4007	£0.14	CD4021	£0.75	CD4041	£0.68	CD4071	£0.15
CD4008	£0.80	CD4022	£0.75	CD4042	£0.68	CD4072	£0.15
CD4009	£0.40	CD4023	£0.13	CD4043	£0.78	CD4081	£0.15
CD4010	£0.42	CD4024	£0.55	CD4044	£0.78	CD4082	£0.16
CD4011	£0.13	CD4025	£0.13	CD4045	£1.15	CD4510	£0.80
CD4012	£0.13	CD4026	£1.00	CD4046	£0.95	CD4511	£0.80
CD4013	£0.35	CD4027	£0.45	CD4047	£0.75	CD4516	£0.85
CD4014	£0.70	CD4028	£0.60	CD4049	£0.35	CD4518	£0.85
CD4015	£0.70	CD4029	£0.75	CD4050	£0.35	CD4520	£0.85
CD4016	£0.35	CD4030	£0.40	CD4054	£0.95		

## BOOKS BY BABANI

The following books are offered at 10% off their normal price.

		Normal Price	Sale Price
BP2	Handbook of Radio, TV & Industrial Transmitting Tube & Valve Equivalents	£0.60	£0.54
BP6	Engineers & Mechanists Reference Tables	£0.40	£0.36
BP7	Radio & Electronic Colour Codes & Data	£0.15	£0.14
BP10	Modern Crystal & Transistor Set Circuits for Beginners	£0.35	£0.32
BP14	Second Book of Transistor Equivalents & Substitutes	£1.10	£0.99
BP15	Constructors Manual of Electronic Circuits for the Home	£0.50	£0.45
BP22	79 Electronic Novelty Circuits	£0.75	£0.68
BP23	First Book of Practical Electronic Projects	£0.75	£0.68
BP24	52 Projects Using IC741 (or equivalents)	£0.75	£0.68
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	£0.85	£0.77
BP27	Giant Chart of Radio Electronic Semi-conductor and Logic Symbols	£0.60	£0.54
BP29	Major Solid State Audio Hi-Fi Construction Projects	£0.85	£0.77
BP32	How to Build Your Own Metal & Treasure Locators	£0.85	£0.77
BP34	Practical Repair & Renovation of Colour TVs	£0.95	£0.86
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	£0.95	£0.86
BP36	50 Circuits Using Germanium, Silicon & Zener Diodes	£0.75	£0.68
BP37	50 Projects Using Relays SCR's and Triacs	£1.10	£0.99
BP39	50 (FET) Field Effect Transistor Projects	£1.25	£1.13
BP43	How to make Walkie-Talkie	£1.25	£1.13
BP44	IC 555 Timer Projects	£1.45	£1.31
BP47	Mobile Discotique Handbook	£1.35	£1.22
BP49	Popular Electronic Projects	£1.45	£1.31
BP160	Coil Design and Construction Manual	£0.75	£0.68
BP196	AF-RF Reactance Frequency Chart for Constructors	£0.15	£0.14
BP202	Handbook of Integrated Circuits (ICs) Equivalents and Substitutes	£0.75	£0.68
BP205	First Book of Hi-Fi Loudspeaker Enclosures	£0.75	£0.68
BP213	Electronic Circuits for Model Railways	£0.85	£0.77
BP214	Audio Enthusiasts Handbook	£0.85	£0.77
BP215	Shortwave Circuits & Gear for Experimenters and Radio Hams	£0.85	£0.77
BP216	Electronic Gadgets and Games	£0.85	£0.77
BP217	Solid State Power Supply Handbook	£0.85	£0.77
BP219	Solid State Novelty Projects	£0.85	£0.77
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	£0.85	£0.77
BP222	Solid State Short Wave Receivers for Beginners	£0.95	£0.86
BP223	50 Projects Using IC Ca3130	£0.95	£0.86
BP224	50 CMOS IC Projects	£0.95	£0.86
BP225	A Practical Introduction to Digital IC's	£0.95	£0.86
BP226	How to Build Advanced Short Wave Receivers	£1.20	£1.08

## VPS30 Variable Regulated Stabilised Power Supply Module

Incorporating a short circuit protection and current limiting:  
 Voltage Regulation 2-30V  
 Regulated Current 0-2A  
 AC Input Maximum 25V  
 Eliminates the use of batteries and thus saves £'s-can be used time and time again ONLY £7.60 + V.A.T.

BRAND NEW	
ITT 923 Silicon Diodes 200mA 200V.	
100 off	£ 2.00
500 off	£ 9.00
1000 off	£ 15.00
10,000 off	£ 130.00

P.C. BOARD	
Single-Sided Fibre Glass Board 12" x 3 1/2" approx. 2 pcs	£0.60
S143	

## THYRISTORS

No. THY1A/50	1 Amp	50 volt	TO5	18p
No. THY1A/400	1 Amp	400 volt	TO5	32p
No. THY3A/50	3 Amp	50 volt	TO64	25p
No. THY3A/200	3 Amp	200 volt	TO64	32p
No. THY3A/400	3 Amp	400 volt	TO64	40p
No. THY5A/50	5 Amp	50 volt	TO66	25p
No. THY5A/400	5 Amp	400 volt	TO66	40p
No. THY5A/600	5 Amp	600 volt	TO66	50p
No. C106/4	6 Amp	400 volt	TO220	42p

## TRIAC

S84 8 Amp 400 volt TO220 80p

## DIACS

ITT. V413 equat 12p  
 8R100 D32 each 12p

## CAPACITORS

16201	18 Electrolytics	4.7µF - 10µF
16202	18 Electrolytics	10µF - 100µF
16203	18 Electrolytics	100µF - 680µF
All 3 at SPECIAL PRICE of £1.60*		
16160	24 Ceramic Caps	22pF - 82pF
16161	24 Ceramic Caps	100pF - 390pF
16162	24 Ceramic Caps	470pF - 3300
16163	21 Ceramic Caps	4700pF - 0.047µF
All 4 at SPECIAL PRICE of £1.60*		

## RESISTOR PAKS

Order No.			
16213	60jW.	100 ohm - 820 ohm	
16214	60jW.	1K - 8.2K	
16215	60jW.	10K - 82K	
16216	60jW.	100K - 820K	
All 4 at SPECIAL PRICE of £1.60*			
16217	40jW.	100 ohm - 820 ohm	
16218	40jW.	1W - 8.2K	
16219	40jW.	1K - 8.2K	
16220	40jW.	100K - 820K	
All 4 at SPECIAL PRICE of £1.60*			

## VOLTAGE REGULATORS

Positive			
No. MVR7805	µA7805	TO220	55p
No. MVR7812	µA7812	TO220	55p
No. MVR7815	µA7815	TO220	55p
No. MVR7818	µA7818	TO220	55p
No. MVR7824	µA7824	TO220	55p
Negative			
No. MVR7905	µA7905	TO220	75p
No. MVR7912	µA7912	TO220	75p
No. MVR7915	µA7915	TO220	75p
No. MVR7918	µA7918	TO220	75p
No. MVR7924	µA7924	TO220	75p
µA723C TO99	38p	72723 14 pin Dil LM309K TO3	£1.20 38p

## SWITCHES

No. 16178	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

## AUDIO LEADS

Order No.		
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug - Mirror Image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline lead	45p*

## AUDIO PLUG AND SOCKET PAKS

Order No.			
S1	5 x 3.5 mm Plastic Jack Plugs	40p*	
S2	5 x 2.5 mm Plastic Jack Plugs	40p*	
S3	4 x Std. Plastic Jack Plugs	50p*	
S4	2 x Stereo Jack Plugs	30p*	
S5	5 x 5 Pin 180° DIN Plugs	50p*	
S6	8 x 2 Pin Loudspeaker Plugs	50p*	
S7	6 x Phono Plugs	55p*	
S8	5 x 3.5 mm Chassis Sockets (Switched)	25p*	
S9	5 x 2.5 mm Chassis Sockets (Switched)	25p*	
S11	2 x Stereo Jack Sockets with instruction leaflet for H/Phone connection.	50p*	
S12	5 x 5 Pin 180° DIN Chassis Sockets	40p*	
S13	8 x 2 Pin DIN Chassis Sockets	60p*	
S14	6 x Single Phono Sockets	40p*	

P.C. BOARD		
S110	Mixed Bundle. P.C.B., Fibre-glass/paper, single and double-sided. Fantastic value	75p

## SPECIAL OFFER!

### UNTESTED SEMICONDUCTOR PAKS

Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/81	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like IN4148	40p
No. 16134	50 750mA Sil. top hat Rects.	40p
No. 16135	20 3 amp Sil. stud Rect.	40p
No. 16136	50 400mw Zeners D.O.7 case	40p
No. 16137	30 NPN Plastic trans. like 8C107/8	40p*
No. 16138	30 PNP Plastic trans. like 8C177/8	40p*
No. 16139	25 NPN trans. like 2N697/ 2N1711 TO39	40p
No. 16140	25 PNP trans. like 2N2905 TO39 40p	
No. 16141	30 NPN trans. like 2N706 TO18	40p
No. 16143	30 NPN Plastic trans. like 2N3906 40p*	
No. 16144	30 PNP Plastic trans. like 2N3905 40p*	
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN to 3 Power trans. like 2N3055	80p

## I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 24 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

## MAMMOTH I.C. PAK

Approx. 200 pieces Assorted fall-out integrated circuits, including Logic 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked - you to identify. £1.00

## MATCHED PAIRS OF PNP GERMANIUM MED. POWER TRANS

	2 amp	750mW	
VCE	VCB	HFE	
NKT301	40	60	30-100 35p per pair
NKT302	40	60	50-150 35p per pair
NKT303	20	30	30-100 25p per pair
NKT304	20	30	50-150 25p per pair

From U.S.A. by

DINDY SCREW CASED LOW NOISE CASSETTES



C90

Order No. 553 10 for £3.50\*

HEAD-CLEANING CASSETTE 45p each

## AUDIO AMPLIFIER

### RETURN OF THE AL20A

By popular demand - this useful 5 watt RMS Power Amplifier is offered at the re-introduitory price of £2.75\* - Hook-up data supplied.

## ETCH RESIST PENS

# SALE T-TIME again!

## SPECIAL OFFER!

### COMPONENT PAKS

Order No.	Quantity	Price
16168	5 pieces Assorted Ferrite rods	40p
16169	2 pieces Tuning gangs MW/LW	40p
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p
16172	3 Micro switches	40p
16174	15 Assorted Fuses 100mA-5 amp	40p
16176	20 Assorted electrolytics	40p
16177	Trans types	40p
16177	1 pack Assorted Hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p
16184	15 Assorted Fuses 100mA-5 amp	40p
16188	60 1/2W resistors mixed values	40p
16187	30 metres stranded wire assorted colours	40p
S100	120 1/2 watt resistors. Pre-formed. 1978 Prod. Our mix	60p*
S101	120 1/2 watt resistors. Pre-formed. 1978 Prod. Mixed values	60p*
S102	250 1/2 watt resistors. Range 100 ohms - 1.8 meg	£2.00*
S103	220 1/2 watt resistors. Range 100 ohms - 10 meg	£2.00*
S104	60 Low ohms 1/2 watt resistors. 10 - 100 ohms	60p*
S105	40 Low ohms 1/2 watt resistors. 12 - 100 ohms	60p*
S106	25 Mixed wirewound resistors	60p*
S107	20 Tantulum bead caps 0.22 - 100mF Our mix	£1.00*
S108	High quality electrolytics 10mF-500mF voltage range 15-50v. Our mix. 40 for	£1.00*
16204	C280 Pak. Contains 50 metal foil caps	£1.00*

### POTENTIOMETERS

Order No.	Quantity	Price
16191	6 x 470 Ohm LIN Single	40p*
S24	6 x 1 K LIN Single	40p*
S25	6 x 5 K LIN Single	40p*
16193	6 x 22 K LIN Single	40p*
16195	6 x 47 K LOG Single	40p*
16194	6 x 47 K LIN Single	40p*
S27	6 x 100 K LIN Single	40p*
S28	6 x 100 K LOG Single	40p*
S29	6 x 500 K LOG Single	40p*
S32	6 x 50 K LIN Single	40p*

### Slider 60mm TRAVEL

Order No.	Quantity	Price
S30	6 x 2.5 K LOG Single	40p*
S34	4 x 5 K LOG Dual	40p*
S36	4 x 100 K LOG Dual	40p*
S37	4 x 1.3 MEG LOG Dual	40p*
S94	6 x 220 K LIN Single	40p*
S95	6 x 100 K LOG Single	40p*
S96	6 x 500 K LIN Single	40p*
S38	Mixed slider pots - various values and sizes - our mix	only 40p*
S39	6 x Chrome slider knobs	40p*

### WIREWOUND

S90	Wirewound Pots. Linear 1 Watt rating. Mixed useful values. 5 for	£1.00*
-----	--	--------

### CARBON TYPES

S91	Car Radio type. Dual Switched Pot P.C. mounting 100 K Lin switched 2.5 K Lin	each 60p*
-----	--	-----------

### DUAL POTS P.C. MOUNTING

6mm Shaft	Quantity	Price
S92	4 x 100 K Lin	£1.00*
S93	4 x 100 K Log	£1.00*
16173	15 Rotary Pot Assorted	40p*
16186	25 Pre-sets Assorted Values	40p*

### ZENER PAKS

No. S55	20 mixed values 400mW Zener diodes 3-10V	£1.00
No. S56	20 mixed values 400mW Zener diodes 11-33V	£1.00
No. S57	10 mixed values 1W Zener diodes 3-10V	£1.00
No. S58	10 mixed values 1W Zener diodes 11-33V	£1.00

### SILICON POWER TRANS. N.P.N.

S97	8D371 2 Amp 1.2w. 60Vceo Hfe 40-400. Case T092 with heat tab. 5 for	60p*
S98	2N5293 R.C. 36w. 4 Amps 75Vceo Hfe 30-120. 5 for	£1.00*

Crystal Ear Pieces  
S126 Less plug **£0.20\***

Plugs for above  
No. 16106 2.5 plastic **£0.09\***  
No. 1697 3.5 plastic **£0.11\***

Mono Crystal Cartridge  
S127 GP91/1SC Special Offer **£1.00\***

Nickel Cadmium Rechargeable Batteries 1.25V  
S128 3500D Cell size=U2 **£2.50**  
S129 900C Cell size=1/2U11 **£0.90**

S130 Complete kit of parts to build nickel cadmium charger **£3.50**

Super Save Pak  
S124 6 x 741P **£1.00**  
S125 5 x 555 **£1.00**

S138 Surplus/End of Manufacturers Line/Pre-amp, with Base, Treble, Volume Control & circuit diagram supplied. **ONCE ONLY OFFER £1.25\***

S137 20 Assorted Slider Knobs - Chrome/Black **£1.00\***

S131 2 x 12v Relays plastic case **£0.70\***

S132 2 x 24v Relays plastic case **£0.60\***

S133 1 switch bank 5 way incl. silver knob **£0.75\***

S134 2 x Magnets suitable for reed switches **£0.10**

S135 .1 Veroboard pak 2 pcs 45 sq. ins. approx. **£0.80**

S136 .15 Veroboard pak 2 pcs 60 sq. ins. approx. **£1.10**

16199 .1 Veroboard pak pcs 30 sq. ins. approx. **£0.50**

16200 .15 Veroboard pak pcs 30 sq. ins. approx. **£0.50**

### TOOLS

No. 2011 5" wire cutters **£1.55**  
No. 2012 5" long wire pleyer **£1.45**

### SUPER DUPER COMPONENT BOX

Min. 3lbs in weight consisting of a fantastic assortment of Electronic Components - Pots, Resistors, Condensers, Switches, Relays, Board - Semiconductors, wire, hardware, Etc., etc.

\*This is a large box and is sent separate to your order\* **£2.50** including p & p. S140

### TRANSFORMERS SALE OFFER

S141 0235 240v primary, 0-55v at 2 amps secondary. **£4.50\*** + **£1.00** p&p.

S142 0349 240v primary, 0-20v at 2Amp secondary. **£3.50\*** + **£0.86** p&p.

### COMPLETE AUDIO AMPLIFIER KITS:

STA15 15 watts per channel amplifier kit  
Consists: 2 x AL60-1xPA100-1xSPM80  
1 x 2034 transformer- **£37.70inc VAT**  
2x coupling capacitors + **86p** p&p

STA25 25 watts per channel amplifier kit. Consists: 2xAL60-1xPA100-1xSPM120/45 **£41.45inc VAT**  
1xreservoir cap + **£1.16p** p & p

STA35 35 watts per channel amplifier kit. Consists: 2xAL60-1xPA100-1xSPM120, 1x2041 transformer, 1 reservoir capacitor **£48.45inc VAT**  
2x coupling capacitors + **£1.16p** p & p

STA50 50 watts per channel amplifier kit. Consists: 2xAL120-1xPA200-1xSPM120/65 1x2041 transformer  
1xreservoir capacitor **£58.20inc VAT**  
2x coupling capacitors + **£1.10p** p & p

STA125 125 watts per channel amplifier kit. Consists: 2xAL250-1xPA200-2xSPM120/65 2x2041 transformers-  
1xreservoir capacitor **£72.85inc VAT**  
2x coupling capacitors + **£1.25p** p & p

## TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p
AC128	16p	BC182	*9p	BF197	*12p	TIP41A	34p
AC128K	24p	BC182L	*9p	BF200	25p	TIP41B	35p
AC176	16p	BC183	*9p	BF229	22p	TIP41C	36p
AC176K	24p	BC183L	*9p	BFY50	18p	TIP42A	36p
AC187	16p	BC184	*9p	BFY50	12p	TIP42B	37p
AC187K	26p	BC184L	*9p	BFY51	12p	TIP42C	38p
AC188	16p	BC212	*10p	BFY52	12p	TIP2955	65p
AC188K	26p	BC212L	*10p			TIP3055	42p
AD161	80p	BC213	*10p	MPSA05	*22p	ZTX107	*6p
162MP	20p	BC213L	*10p	MPSA05	*22p	ZTX108	*6p
AF139	30p	BC214	*10p	MPSA55	*22p	ZTX109	*7p
AF239	30p	BC214L	*10p	MPSA58	*22p	ZTX300	*7p
BC107	6p	BC251	*10p	OC44	12p	ZTX301	*7p
BC108	6p	BCY70	12p	OC45	12p	ZTX302	*9p
BC109	6p	BCY71	12p	OC71	9p	ZTX500	*8p
BC118	*10p	BCY72	12p	OC72	10p	ZTX501	*10p
BC147	*8p	BD115	*40p	OC75	10p	ZTX502	*12p
BC148	*8p	BD131	*35p	OC81	14p	2N696	10p
BC149	*8p	BD132	*37p			2N697	10p
BC154	*16p	BF115	17p	TIP29A	35p	2N708	7p
BC157	*9p	BF167	15p	TIP29B	36p	2N706A	8p
BC158	*9p	BF173	20p	TIP29C	38p	2N708	8p
BC159	*9p	BF180	25p	TIP30A	36p	2N1302	12p
8C169C	*10p	BF181	25p	TIP30B	37p	2N1303	15p
8C170	*6p	BF182	25p	TIP30C	38p	2N1304	15p
8C171	*6p	BF183	25p	TIP31A	32p	2N1307	18p
8C172	*6p	BF184	25p	TIP31B	33p	2N1308	22p
8C173	*7p	BF185	25p	TIP31C	34p	2N1309	22p

### DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	8AX16/	5p	OA85	7p	1S44	3p
AA213	4p	OA202	5p	OA90	6p		
8A100	6p			OA91	7p	IN5400	10p
BA115	5p	BY100	15p	OA97	6p	IN5401	11p
BA144	5p	BY127	*10p	OA95	7p	IN5402	12p
8A148	10p	BY120	32p	IN34	5p	IN5404	13p
BA173	10p	BY211	32p	IN60	6p	IN5406	16p
BAX13/	*6p	BY212	32p	IN914	4p	IN5407	17p
OA200	5p	BY213	30p	IN4148	4p	IN5408	19p

### LINEAR I.C.'s

TBA800	£0.75*	UA711	£0.25*	UA748	£0.28*
TBA810	£0.85*	UA703	£0.25*	72558	£0.45*
TBA820	£0.85*	741P	£0.18*	MC1310P	£1.25*
LM380	£0.80*	72741	£0.20*	76115	£1.25*
LM381	£1.25*	UA741C	£0.20*	NE555	£0.22
72709	£0.20	72747	£0.55*	5L414A	£1.80*
UA709	£0.20	748P	£0.28*		

### ZN 414 RADIO CHIP 75\*

### OPTOELECTRONICS

Displays	Price	2nd Quality Led Paks	Price
No. 1510 707 LED Display	£0.70	No. 1507 10 Assorted Colours & Size	£0.75
No. 1511 747 LED Display	£1.50	No. S122 10 x .125 Red	£0.60
No. 1512 727 Dual LED Display	£1.55	No. S123 10 x .2 Red	£0.60
<b>LED's</b>		<b>LED Clips</b>	
No. S120 .125 Bright Red	£0.09	No. 1508/125 .125 5 for	£0.12
No. S121 .2 Bright Red	£0.09	No. 1508/2 .2 5 for	£0.15
No. 1502 .125 Green	£0.12		
No. 1505 .2 Green	£0.12		
No. 1503 .125 Yellow	£0.12		
No. 1505 .2 Yellow	£0.12		
No. S82 Clear .2 Illuminating Red	£0.10		

### P.O. RELAYS

S85 - 2 Off Post Office relays 40p\*

### BATTERY HOLDERS

to take 6 x HP7's  
Order No. 202 each 10p

### EX. G.P.O./MICROWATERS

Order No. S51 4 for 50p

### CABLE CLIPS

S85 - 50 2.5mm round single pin fixing 30p

### SPECIAL REDUCTIONS

No. 1514 NORP 12 each 45p  
No. S71 OCP71 5 for £1.00  
No. S83 5 NIXIE Tubes ITT 5870 ST £2.00 (including Data)

No. S77 Neon Indicator Lamps 230V A.C. State Colour (Red, Amber and Green.) 25p each

### POWER SUPPLY STABILIZER BOARD

Unused ex-equipment stabilizer board, Input 30V. D.C. Output 20V. Complete with circuit diagram.  
Order No. S81 **£1.25\***

### ORDERING

Minimum postage and packing for Sale Orders **£0.50** PLUS any further postage as stated as per this Sale Advertisement

Overseas Orders - ADD extra for Air-mail

### V.A.T.

Please ADD V.A.T. as follows:  
12 1/2% to items marked \* 8% to unmarked items NO V.A.T. on Books


SEND FOR YOUR BI-PAK CATALOGUE 65p post free.

I.C. INSERTION EXTRACTION TOOLS O/N 2015 30p each

**BI-PAK**  
DEPT. PE2, P.O. Box 6, Ware, Herts  
COMPONENTS SHOP: 18 BALDOCK STREET, WARE HERTS.

# YOUR COMPLETE RANGE OF ELECTRONIC HARDWARE....


## BIMENCLOSURES

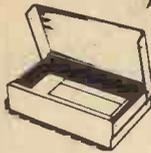


**ALL METAL BIMCASES**  
Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.  
BIM 3000 (250x167.5x68.5mm) £14.58



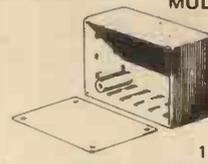**MINI DESK BIMCONSOLES**  
Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied. 1mm Grey Aluminium panel sits recessed with fixing screws into integral brass bushes.  
BIM 1005 (161 x 96 x 58mm) £2.18  
BIM 1006 (215 x 130 x 75mm) £3.05



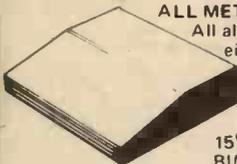
**MULTI PURPOSE BIMBOXES**  
Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes. 1.8mm pcb guides incorporated and 4 BIMFEET supplied.  
BIM 4003 (85x56x28.5mm) £1.18  
BIM 4004 (111x71x41.5mm) £1.62  
BIM 4005 (161x96x52.5mm) £2.19



**ALL METAL BIMCONSOLES**  
All aluminium, 2 piece desk consoles with either 15° or 30° sloping fronts, sit on 4 self-adhesive non-slip rubber feet. Ventilation slots in base and rear panel for excellent cooling.

Colour Code	Top Panel	Base
A	Off White	Blue
B	Sand	Green
C	Satin Black	Gold


15° Sloping Panel		30° Sloping Panel		
BIM7151 (102x140x51[28] mm)	BIM7301 (102x140x76[28] mm)	£10.67		
BIM7152 (165x140x51[28] mm)	BIM7302 (165x140x76[28] mm)	£11.44		
BIM7153 (165x216x51[28] mm)	BIM7303 (165x183x102[28] mm)	£12.61		
BIM7154 (165x211x76[33] mm)	BIM7304 (254x140x76[28] mm)	£13.82		
BIM7155 (254x211x76[33] mm)	BIM7305 (254x183x102[28] mm)	£15.36		
BIM7156 (254x287x76[33] mm)	BIM7306 (254x259x102[28] mm)	£16.67		
BIM7157 (356x211x76[33] mm)	BIM7307 (356x183x102[28] mm)	£17.58		
BIM7158 (356x287x76[33] mm)	BIM7308 (356x259x102[28] mm)	£18.55		

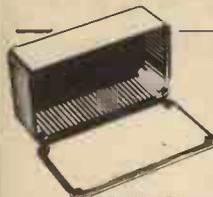

**ABS & DIECAST BIMBOXES**  
6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue, Black or Grey. Diecast Aluminium in Grey Hammettone or Natural. All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).

	ABS	Diecast	Hammettone	Natural
(50x60x31mm)	N/A	BIM5001/11	TBA	TBA
(100x50x25mm)	BIM2002/12	£0.96	BIM5002/12	£1.46
(112x62x31mm)	BIM2003/13	£1.13	BIM5003/13	£1.78
(120x65x40mm)	BIM2004/14	£1.35	BIM5004/14	£2.24
(150x80x50mm)	BIM2005/15	£1.52	BIM5005/15	£2.84
(190x110x60mm)	BIM2006/16	£2.37	BIM5006/16	£3.94

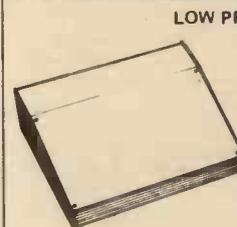Also available in Grey Polystyrene with no slots and self-tapping screws  
BIM 2007/17 (112x61x31mm) £1.00



## LOW PROFILE BIMCONSOLES

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes. 4 BIMFEET supplied.

BIM 6005 (143 x 105 x 55.5 [31.5] mm) £2.37  
BIM 6006 (143 x 170 x 55.5 [31.5] mm) £3.08  
BIM 6007 (214 x 170 x 82.0 [31.5] mm) £4.12



## EUROCARD BIMCONSOLES

Orange, Blue, Black or Grey ABS body accepts full or ½ size Eurocards, with bosses in the base for direct fixing. 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied. 1mm Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.

BIM 8005 (169x127x70[45] mm) £4.12  
BIM 8007 (to be announced shortly)

## BIMTOOLS



### MAINS BIMDRILLS

Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks. Drills brass, steel, aluminium and pcb's. Under 250g, off load speed 7500 rpm. Orange ABS, high impact, fully insulated body with spring return on/off switch £10.53

Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burrs and 2.4mm collet £2.48

Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burrs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £22.14



### 12 VOLT BIMDRILLS


2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia £ 8.10  
Major BIMDRILL with 4 collets up to 3mm dia £13.60

Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £15.12, Major Kit 1 - £19.44.

Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains 12V dc adaptor. Mini Kit 2 - £34.02, Major Kit 2 - £39.42.

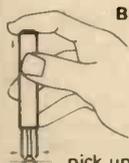Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £45.36, Major Kit 3 - £50.76.



### BIMDIPS


Rapidly inserts and withdraws any 4-18 pin, .3" pitch DIL package without bedding the legs. Adjustable metal jaws for MOS type devices grip the bottom of the leg for minimum strain. Will

pick up IC's from a bench, a carrier or a pcb. £13.77.

### BIMSNIPS

Precision made side cutters, spring action, ground steel fine pointed blades for intricate work.


5 1/4" long £3.34

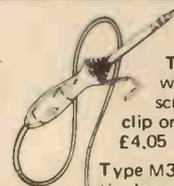
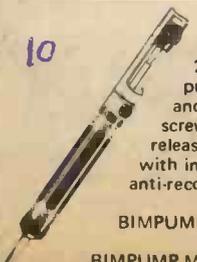
### BIMIRONS

Type 30 General Purpose 27 watt iron with long life, rapid change element, screw on tip, stainless steel shaft and clip on hook. Styled handle with neon. £4.05


Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip on hook £4.43


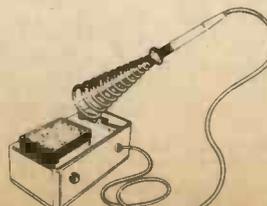
### BIMPUMPS

2 all metal desoldering tools provide high suction power and have easily replaceable screw in Teflon tips. Primed and released by thumb operation with in-built safety guard and anti-recoil system.

BIMPUMP Major (180mm long) £7.99  
BIMPUMP Minor (150mm long) £6.80



### BIMSTATION

Type PSU6 Soldering Iron Station complete with 6V, 6 Watt miniature iron having stainless steel shaft, quick change slide on tip and long life element.

Station contains 240V/6V transformer, neon, coiled iron support and sponge iron tip cleaning pad.

New product available shortly

## BIMDICATORS

### ECONOMY QUALITY LED'S



Mixed bags of .125" and .2" dia. lens in various colours  
50 for £5.67, 100 for £10.00

### FULL SPECIFICATION LED'S

.125" or .2" with mounting clips and data  
Red - £1.67/pack of 5, Green - £2.48/pack of 5, Yellow/Amber - £3.18/pack of 5



### 33 and 34 SERIES

Front viewing (30° angle) LED indicators

BIM 33 is nickel plated, uses 3.2mm dia LED and needs 6.5mm dia. fixing hole.



BIM 34 is chromium plated, uses 5mm dia. LED and needs 8mm dia. fixing hole.

Red - £2.80/pack of 5, Green/Yellow - £3.24/pack of 5



### A SERIES

240V Neon with integral resistor... held in 8mm hole by plastic bezel.

Red, Amber, Clear or Opal lens £2/pack of 5, Green lens £3/pack of 5

Low Voltage equivalent of above with Red, Amber, Clear, Opal or Green Lens.  
6V £0.54 each, 14V £0.58 each, 28V £0.65 each

State Voltage, lens style, colour and whether tags or flying leads.



### D SERIES

LES and Midget Flanged lampholder with 13mm dia. (A) and 18mm dia (B) lens. Solder tags. 1/8" dia. hole fixing (lamps not supplied) plus chrome bezel with A lens.

Red, Amber, Clear, Green, Opal £0.66 each




### G SERIES

T1 Midget Flanged lampholder. Lamps are available on request. 8mm fixing hole, solder tags. Front replaceable, 7.25mm dia. lens. Red, Amber, Clear, Green, Opal £0.43


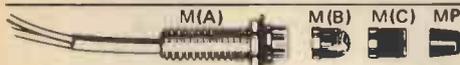
### 05 SERIES


240V Neon with integral resistor. Self retaining in 13mm hole. Solder/.25" push on blades. 13mm dia. lens with 19mm dia. chrome bezel. Red and Amber £0.61 each, Green £0.78 each.



### M & MP SERIES

(M) and Polycarbonate (MP) indicators, 150mm leads, 6.4mm fixing hole Red, Amber, Clear, Green, Opal

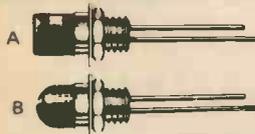
6.9mm dia. lens (M) 6V £0.65 each, 14V £0.68 each, 28V £0.79 each  
7.5mm dia. lens (MP) 6V £0.55 each, 14V £0.59 each, 28V £0.68 each


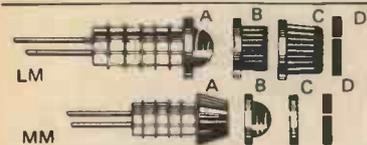
### BIM M LED SERIES

Nickel plated brass bodied LES indicator, 21mm wire wrappable leads, 6.5mm fixing hole, 2 styles, 6.8mm dia lens.


Red £0.67 each, Green £0.83 each, Amber £1.00 each


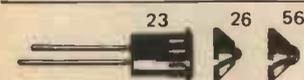
### BIM LM & MM LED SERIES

Subminiature nylon bodied LED indicators with 12mm wire wrappable leads

LM & MM push fit into 4.75mm & 4mm holes respectively. Each series has 4 lens styles in Red £0.67, Green £0.83, Yellow £1.00 each.



### BIM 23, 26 & 56 LED SERIES

Black nylon bodied LED indicators. BIM 23 has 7mm flat face, BIM 26 & 56 utilise 4 & 5mm dia LED's. Push

fit in 8mm hole. Red £0.46 each, Green £0.62 each, Yellow £0.77 each

## BIMACCESSORIES



### BIMDAPTOR

Allows pcb's to be flat mounted sandwich fashion in BIMBOXES, BIMCONSOLES, and all other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snapped off to length.

Packs of 25 £1.08 per pack

### BIMFEET



11mm dia, 3mm high, grey rubber self adhesive enclosure feet.

Packs of 24 £0.77 per pack

## BIMBOARDS



DIL COMPATIBLE BIMBOARDS



Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LED's. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple

units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1 £ 8.83

BIMBOARD 2 £21.01

BIMBOARD 3 £29.84

BIMBOARD 4 £38.79

### DESIGNER PROTOTYPING SYSTEM

1, 2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (±5 to ±15Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

DESIGNER 1 £55.62

DESIGNER 2 £61.02

DESIGNER 3 £66.42

...FROM

**BOSS**  
INDUSTRIAL MOULDINGS LIMITED

All quoted prices are 1 off and include Postage, Packing and VAT. Terms are strictly cash with order unless you have authorised BOSS account. For individual data sheets on all BOSS products send stamped, self addressed envelope.


2 Herne Hill Road, London SE24 0AU

Telephone: 01-737 2383

Telex: 919693 Answer Back 'LITZEN G'

Cables & Telegrams: 'LITZEN LONDON SE24'

### SUPERSOUND 13 HI-FI MONO AMPLIFIER

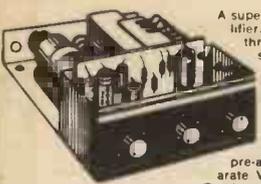

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume. Bass boost and

Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. AC 200/250V. PRICE £16.00 P. & P. £1.20.

### HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system. Disco, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200-240 volts. Size approx. 12in wide x 5in high x 7in deep. Special introductory price £28.00 + £2.50 carriage and packing.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11in x 14in x 1in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + P. & P. (one 90p, two £1.10). Now available in either 8in round version or 4 1/2 x 8in rectangular. 10 watts R.M.S. 60Hz-20KHz £5.25 + P. & P. (one 65p, two 75p.).

### MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200-240V Mains operated Solid State F.M. A.M. Stereo Tuner. Covering M.W. AM 540-1605KHz V.H.F. F.M. 88-108MHz.

Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator Built in Pre-amps with variable output voltage adjustable by pre-set control. Max. Output Voltage 600mV R.M.S. into 20K Simulated Teak finish cabinet. Will match almost any amplifier. Size 8in wide x 4in high x 9in deep approx.

Limited number only at £28.00 - £1.50 P. & P.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, ECC83, EF86 and E780 rectifier. Simple instruction booklet 25p + S.A.E. (free with parts). All parts sold separately. ONLY £15.50 P. & P. £1.40. Also available ready built and tested £20.00 P. & P. £1.40.

**STEREO MAGNETIC PRE-AMP SENS.** 3mV in for 100mV out. 15 to 35V neg. earth. Equ.  $\pm$ 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2in x 2 1/2in x 5 1/2in H. £2.60 + 20p. P & P.

Mullard LP1159 RF-IF module 470 kHz £2.25 + P. & P. 20p. Full specification and connection details supplied. Pye VHF FM Tuner Head covering 88-108 MHz 10.7 MHz I.F. output. 7-8V + earth. Supplied pre-aligned, with full circuit diagram with precision-gear F.M. gang and 323PF + 323PF A.M. Tuning gang only £3.15 + P. & P. 35p.

### SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coll speakers, telescopic aerial and internal ferrite aerial. Empiece socket for personal listening. Finished in attractive simulated leatherette.

Size 7 1/4 x 9 1/4" W x 4"D approx. Fully guaranteed.

Bargain price of only £10.00 + £1.30 p&p.

### MODEL FL4

Few only similar to above, but battery operation only. Twin speakers, four wave bands, MW, FM and two VHF bands for reception of aircraft and some public services. ONLY £9.50 + £1.30 p&p.

### MODEL MULTI 5

Specification as Model FL4 but with additional SW band. Twin speakers. ONLY £11.00 + £1.30 p&p.

### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification. Power output 14 watts R.M.S. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000Hz. Sensitivity better than 80mV into 1 M $\Omega$ . Full power bandwidth  $\pm$  3dB 12-15,000Hz. Bass boost approx to  $\pm$  12dB. Treble cut approx to  $\pm$  16dB. Negative feedback 16dB over main amp. Power requirements 35V at 1A.

Overall size 12in wide x 8in deep x 2 1/2in high.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S A E

AMPLIFIER KIT (Magnetic input components 33p extra) £14.50 P. & P. 80p

POWER PACK KIT £6.00 P. & P. 95p

CABINET £6.00 P. & P. 95p

SPECIAL OFFER—only £25.00 if all 3 items

ordered at one time plus £1.25 P. & P.

Full after sales service

Also available ready built and tested £31.25 P. & P. £1.50

### HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec. play socket are mounted on the printed circuit panel. Size approx. 9in x 2 1/2in x 1in max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10.00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £2.00 + 40p P. & P. If required. Full connection details supplied.

### STEREO DECODER

SIZE 2" x 3" x 1" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

## HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 MERTON HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station


(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## START THE NEW YEAR WELL

by treating yourself to this

famous  
Components  
Catalogue

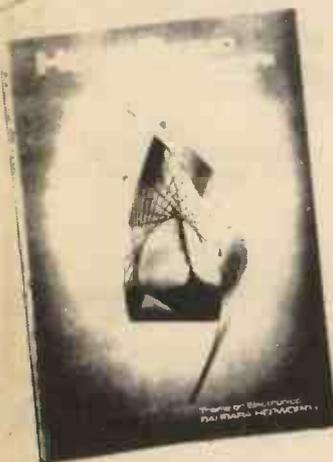

- The finest components catalogue yet published.
- 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Profusely illustrated.
- Bargain List sent free.
- At £1.25, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD 234-240 London Road Mitcham Surrey CR4 3HD

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD Dept PE 234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No. 912966 London

POST THIS COUPON with cheque or P.O. for £1.25

## NO DISCO SYSTEM IS COMPLETE WITHOUT...



### CITRONIC MM 313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch. mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £80.46 (P & P £1.50).

### PIEZO HORNS

FANTASTIC SPECIAL OFFER TO READERS OF THIS PUBLICATION  
Tweeters for your disco, PA system or Hi-Fi. Frequency range 5K-20K. No X over required. They can be used in any PA system up to 100W. Why pay more? OUR PRICE ONLY £4.99 each (P&P 35p each)



### BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 5A. Perfect for your Sound to Light System. P552 SOCKET £0.65 (P&P 35p) P551 PLUG £1.84 (P&P 35p) Carriage on 10 or more nominal £1.00 Also available 6-way multicore cable (6 Amps per core) ex stock. £0.85 per metre. Please phone for carriage quote.



### PROJECTORS SQUIRE MULTIFECT 150

— including rotator and effects wheel. A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use.

A BARGAIN AT £40.50 (P&P £1.00)



### STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250W quartz halogen bulb, fan cooled, accepts wide range of multifect attachments. Unique connection slot for orbit prism revolvers. Only £70.20 (P & P £2.00) attachments extra

### PLUS MANY DISCO ACCESSORIES

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example: Fane and H. H. Disco Speakers 12" and 16" BSR and Garrard decks at discount prices.

## Roger Squire's DISCO GEAR

Personal callers: ROGER SQUIRE'S DISCO CENTRES

LONDON: 175 Junction Road, Tufnell Park N19 5QQ 01-272 7474

BRISTOL: 125 Church Road, Redfield, Bristol BS5 9JR 0272-550550

MANCHESTER: 251 Deansgate M3 4EN 061-831 7676

GLASGOW: 1 Queen Margaret Road off Queen Margaret Drive, Kelvinside, Glasgow, G20 6DP

Open from 10.5 Tues-Sat

10.8 Weds.

Closed Mondays.

041-946 3303



# SAXON ENTERTAINMENTS

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT  
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

## CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,  
TWIN SPEAKERS & LEADS

### Standard 100W

£249 + carr. £15 + VAT  
or Deposit £57.12  
12 Months @ £21.94 or 24 Months @ £12.54

### Super 200W

£299 + corr. £15 + VAT  
or Deposit £68.12  
12 Months @ £26.19 or 24 Months @ £14.90

### GXL 200W (with twin 200 watt cabinets)

£389 + carr. £15 + VAT  
or Deposit £87.32  
12 Months @ £33.64 or 24 Months @ £19.19

BSR Decks – 17,000 Line Loudspeakers – Rugged Aluminium Trimmed Cabinets – Cue Light And Phones Output – Slove Output – Deck Lights/Motor Starts (GXL)  
ALSO CENTAUR 'CUSTOM' 400-600W £699 – ASK FOR DETAILS

COMPLETE STEREO  
ROADSHOWS – BUILT IN  
SOUND TO LIGHT/SEQUENCER  
& DISPLAY  
TWO YEAR GUARANTEE



illustration shows GXL Centaur System  
These systems feature full mixing for two decks  
tape & mic with monitoring facilities – override  
and ore supplied complete with sound to light +  
sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

## MINI DISCO 100 WATT MONO SYSTEM

£179.50 + carr. £15 + VAT  
Deposit £42.06  
12 Months @ £16.22 or 24 Months @ £9.24

Similar in appearance to the Centaur and  
complete with loudspeakers and leads.

Headphones to suit any system  
EM507 Electret Mic £15.00  
D1501 Electret Mic £18.50  
Boom Stand £15.50  
Carriage on all disco and PA systems £10.00  
(Included in H.P. Prices)

20% Deposit Terms  
12 to 24 Months  
– Low Interest

### AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers



**NEW** 240 WATT 4 OHM  
INDUSTRIAL  
MODULES EIGHT  
OUTPUT DEVICES  
£35 SUPPLY £24.75

SA308 8 ohms 30W 45V	£10.75*	Supply for 2 modules	£11.90*
SA604 4 ohms 50V	£14.50	Supply for one or 2 modules	£14.95
SA608 8 ohms 60W 65V	£15.50		
SA1204 4 ohms 120W 75V	£17.50	Supply for 1 module	£14.95
SA1208 8 ohms 120W 95V	£21.00	Supply for 2 modules	£24.75

### SAXON KLAXON



FOUR  
WAY  
SIREN

UK Police – Destroyer – US Police – Hawaii Five-O  
All the effects you need in one package  
£17.50  
Carr free

Individual sirens with any of the above effects  
£7.50

### SAXON 'SMASH' ALIEN VOICE SIMULATOR

Add a new dimension to your disco  
with this press button effect unit –  
just insert between mic and amplifier

£7.50 Carr free



### SAXON 'SCINTILLITE'

Rope light controller with auto reverse

£24.75 Carr free

SAXON Rope Lights multicolour  
25 feet long

Easy to change lamps £35.50 Carr £1 Spare bulbs 10p ea.



### CABINET FITTINGS

ICI Vynide 50" wide £3.50m Kick-res grille 50" wide £3.50m  
Netlon kick proof 24" wide £3.50m  
Corners/feet/recess plates 15p ea. Recess handle 45p  
Bar handles £2.50 Jack plugs/sockets 25p

### LOUDSPEAKER CABINETS – COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim – black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24)	£39.00	Carr £3 Deposit £9.36
Large 100W 1 x 12 (65 x 48 x 24)	£49.50	Carr £3 Deposit £12.70
P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24)	£66.50	Carr £3 Deposit £15.82
P.A. 2 x 12 200W (100 x 38 x 24)	£99.00	Carr £3 Deposit £20.92
Disco 2 x 12 200W (80 x 63 x 24)	£85.00	Carr £3 Deposit £19.80
PDF reflex bin (80 x 40 x 41)	£95.00	Carr £3 Deposit £20.60

### PDF100 Reflex Bin – Twin Horns – Integrated Slave Amplifier – Accepts mono or stereo signals

- Use with all types of mixer
  - Pan and volume controls
  - Send for details
- £130 Carr £3  
Deposit £28.40

### SOUND-TO-LIGHT UNITS

#### 3 CHANNEL – 3kW

- Operates from 1W upwards
- Bass/middle/treble/master controls



£29.50 + £1 carr  
complete

Module only £19.75 Panel £2.95

#### 4 CHANNEL – 4 kW SOUND/LIGHT SEQUENCER (illus)

- Dimmer on each channel
- Automatic sound light level
- Logic circuitry throughout

£39.50 Carr £1

Module only £26.75 Panel £2.95

### 100W SPOTS

Red – Blue – Amber – Green £1.50 ea. Carr 50p max  
Free on 10+

### HEAVY DUTY SPOT BANKS – MATCHES LOUDSPEAKERS


3 way 600W £35.50 4 way 800W £39.50 Carr  
£2

### FUZZ LIGHTS

Red, Blue  
Yellow, Green

£22.80

### DISCO MIXERS – COMPLETE OR MODULAR

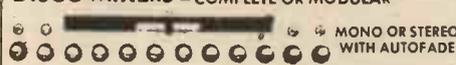

Available complete and ready to plug in or as  
an easy to connect module with all controls  
except monitor switch already fitted – full  
instructions supplied.

#### FEATURES INCLUDE:

Twin Deck – Mic & Tape Inputs – Wide range  
bass & treble controls – Full headphone  
monitoring – Crossfade – Professional stan-  
dard performance.

#### MONO OR STEREO WITH AUTOFADE

MODULES  
Mono module £27.50  
Stereo module £37.50  
Panel £3.95  
Kit of knobs/  
sockets etc £5.50

#### COMPLETE MIXERS

(with case)  
Mono mains £45.75  
Stereo mains £63.75

### PLUTO PROJECTORS & WHEELS

P140 150 Watt tungsten  
remarkable value

£38.50 Carr £1.00  
Deposit £8.66

P5000 250 Watt Q.I. + fan  
Interchange fitting

£89.50 Carr £1.00  
Deposit £20.28

Picture wheels from £4.95 – a wide range of wheels & effects  
available – send for leaflet



MOTOROLA PIEZO HORNS  
£4.50. YES!!



# MANCHESTER PACKAGE DEAL

## P.A. SYSTEMS

2 YEAR GUARANTEE

100 WATT £159.90 + Corr DEPOSIT £37.89  
 £15


12 mth @ £14.58 or 24 mth @ £8.30  
 ★ AP100 4 INPUT AMPLIFIER (see below)  
 ★ TWIN PIEZO HORN 100W COLUMNS & LEADS

200 WATT £249.00 + Corr DEPOSIT £57.12  
 £15

12 mth @ £21.94 or 24 mth @ £12.54  
 ★ USES NEW AP200 SIX INPUT AMPLIFIER (below)  
 ★ PAIR OF TWIN 200W PIEZO HORN COLUMNS

AP100 AMPLIFIER £45  
 ★ 4 mixing units + £1.50 Carr  
 ★ Bass, treble, master controls  
 ★ Twin outputs - vinylde case  
 Deposit £10.22

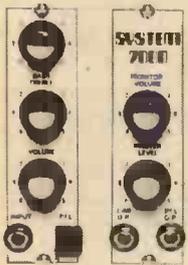AP200 NEW £89.50  
 ★ 6 mixing inputs + £2.50 Carr  
 ★ 3 set of bass/treble controls  
 ★ Master & Presence controls  
 Deposit £20.36



**D.I.Y. MODULES FOR P.A. SYSTEMS**  
 MONO/STEREO

Make your own mixer Mono/Stereo up to 20 channels accept all inputs available as PCB only or complete on front panels	Input Modules	Mono PCB only £6.50	Mono C/W Front panel £9.50
		Stereo PCB only £10.50	Stereo C/W Front panel £13.75
	Mixer/Monitor Modules	Mono PCB only £6.50	Mono C/W Front panel £9.50
		Stereo PCB only £10.50	Stereo C/W Front panel £13.75

Power supply to suit £9.50 - send for full details of uses

PA SYSTEM ACCESSORIES	D1501 Dual Imp High O/P condenser mic	£18.50*	TWIN PIEZO HORN BOXES to match other cabinets Carr £1.50 Deposit £7.32
	EM507 High output single impedance mic	£15.00*	
	ECM105 Low cost condenser mic	£5.00*	
Heavy chrome mic stand - collapsible £9.90 Boom version £16.95	MELOS CASSETTE ECHO/REVERB Twin input unit - infinitely variable speed, depth & delay - playback feature Suits all mics & instruments		ADD ANY ACCESSORIES TO YOUR TOTAL CREDIT ORDER
	Carr £59 Deposit £14.80		

All prices subject to 8% VAT except where asterisked (12½%)  
 Shop premises open Tues to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm  
 Mail order dept open Mon to Fri 10 am - 4 pm Ring 01-684 6385

### TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclay Card Number NOT THE CARD.  
 By Phone You may order COD, Access or Barclay Card.  
 Post & Packing 50p on all orders except where stated.

## SAXON ENTERTAINMENTS

327 Whitehorse Road, Croydon, Surrey.  
 All Enquiries Large SAE Please Brochures on request.

MANCHESTER DISCO CENTRE, 237 DEANSGATE, MANCHESTER  
 CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY

## MOTOROLA - 1 WATT AUDIO AMPLIFIER I.C.

9-16V, 8-16Ω, 10-400 MV. Sensitivity, S.C. Proof.

No Heat sink required.

Supplied with Data and Circuits, 90p each.

Don't Let Your Environment Dehydrate You! Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive, ½" shaft, 250V, 3.75A Contacts. Ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost! £1.50 ea. 3 for £4.	<b>SMOKE AND GAS DETECTOR</b> Uses TGS 105 plug in sensor, housed in neat 3½" die cast box. led indicator. 24V. (12V by altering 3 component values). Will operate lamp or relay, with data and circuit. £6.95 Relays for above £1 ea. state voltage
<b>CASSETTE MOTORS</b> Self Regulating, will operate 8-12V. Ideal for modelers. mechanical switching etc. 2000 R.P.M. approx. 90p ea.	<b>TRANSISTOR PACKS</b> 100. Full spec. new and marked. Includes BC148, BC184L, MED412, BF274, BC154 etc. etc. £4.95 200 as above and includes AC128, 2N3055, BFX50, BD131, BF200 etc. £9.95 Buy bulk and save money, these packs are worth at least double.
<b>ULTRASONIC TRANSDUCERS</b> Transmitter and receiver, 40 kHz 14 mm diam. £4.25 pair.	<b>P/B SWITCH BANKS</b> These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole etc. Can be modified. Can't be repeated. 3 Banks for £1
<b>6 x 6 POLE REED RELAYS ON BOARD</b> 12V ideal for burglar alarms, model railways etc. £2.45	<b>BULK BARGAINS, STOCK UP FOR WINTER</b> 300 mixed ½ & ¼ watt resistors £1.50 150 mixed 1 & 2 watt resistors £1.50 300 mixed capacitors, modern, most types £3.30 100 mixed ceramic and plate caps £1.20 25 pots and presets £1.50 25 presets, skeleton etc. £1.20 20 VDRs and thermistors £1.20 100 Hi-wattage resistors wirewound etc. £2.20 100 electrolytics, nice values £2.20 300 printed circuit resistors £1 300 printed circuit components £1.50
<b>100 MINIATURE REED SWITCHES</b> We are the cheapest! £3.30	<b>100K MINIATURE THUMBWHEEL SLIDER POTS</b> Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1 <b>100K STEREO SLIDER PDTS</b> Good quality. 25p ea. 5 for £1
<b>EARPIECES</b> Magnetic with plug and lead 25p ea. 5 for £1 Crystal with lead 40p ea. 3 for £1	<b>MINIATURE LEVEL/BATT. METERS 200µA</b> F.S.D. as fitted to many cassette recorders. 90p
<b>MAKE CHEAP BATTERY ELIMINATORS</b> Fully shrouded mini mains transformers. 240V in 8-0-8V at 100 MA out. Complete with mains lead and plug, ex new equip. 90p	
<b>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS</b> Includes 150 sq. ins. copper clad F/G board 1 lb ferric chloride. 1 dolo etch resist pan. Abrasive cleaner. Etch tray plus instructions. Special Price £4.95 1 lb FE. C1. To mil. spec. £1.25 5 lb FE. C1. To mil. spec. £5.00 150 sq. in. Single sided board £2.00 150 sq. in. Double sided board £3.00	

40p P & P on all above items. Cheque or P.O. with order to:

**SENTINEL SUPPLY, DEPT. P.E.**  
 149A BROOKMILL RD., DEPTFORD, LONDON, SE8

## THE BRIDGE BETWEEN MANUFACTURERS & USERS OF MICROELECTRONICS

MICROSYSTEMS '79

West Centre Hotel,  
 Lillie Road, Fulham,  
 London, SW6  
 January 31 to  
 February 2

09.30-18.00 hrs each day

Now in its second great year, Microsystems is a combined conference and exhibition aimed at alerting industrialists and businessmen to the meaning of the microelectronic revolution.

The Exhibition is free. The Conference costs £55 + VAT for each of the first two, professional days (£95 + VAT for a two-day ticket), and £7 + VAT for the final, personal computing, day.

Microsystems is sponsored by 'Computer Weekly'.

'Microprocessors', 'Data Processing', 'Electronics Weekly', 'Systems International', 'Electron', 'Electrical Times', 'Electrical Review' and 'Wireless World' and is organised for them by Iliffe Promotions Ltd, Dorset House, Stamford Street, London, SE1 9LU.

### USE THIS COUPON TO BOOK FOR MICROSYSTEMS

To: Microsystems, Room 821, Dorset House, Stamford Street, London, SE1 9LU.

Please send me:  Conference details and registration forms  
 A free exhibition ticket (Tick as required)

Name .....

Address .....

PE

# The professional scopes you've always needed.



**Super 6**  
£162.00 plus VAT



**Super 10**  
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

**CALSCOPE DISTRIBUTED BY**  
Marshall's Electronic Components,  
Kingsgate House,  
Kingsgate Place,  
London, N.W.6.

Audio Electronics,  
301 Edgware Road, London W.2.  
Tel: 01-724 3564  
Access and Barclay card facilities  
(Personal Shoppers)

Maplin Electronics Supplies Ltd.  
P.O. Box 3  
Rayleigh, Essex.  
Tel: 0702 715 155  
Mail Order

## CALSCOPE

## Connoisseur's New and Exceptional SAU4 Pick Up Arm

Especially designed for modern high compliance cartridges and featuring ...

1. Light weight metal headshell
2. Calibrated downforce pressure weight
3. Ball spirit level for visual indication of central balance.
4. De-coupled counter balance weight
5. Viscous damped unipivot
6. Lateral balance weights
7. Viscous damped raise/lower device
8. Light weight aluminium tube



**£45.00**  
plus V.A.T.

## Connoisseur

Write for further details to:  
A. R. Sugden & Co. (Engineers) Ltd.  
Manufacturers of Connoisseur Sound Equipment,  
Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES  
Telephone: Brighouse (0484) 712142, Telex: 517144 Sugden G  
Telegrams & Cables: Connoisseur Brighouse.

## AITKEN BROS.

35, High Bridge, Newcastle upon Tyne  
Tel: 0632 26729



**TMK 500 MULTIMETER** 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts: 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50µA, 5mA, 50mA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels: -20 to +56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included.  
**PRICE £24.95.**



**SINCLAIR PDM35 DIGITAL POCKET MULTIMETER**  
DC volts (4 ranges) 1MV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £32.95.** AC Adaptor/Charger £3.75 de luxe padded carrying case £3.50 MN1604 Battery. **99p.**



**SINCLAIR DM235 BENCH-PORABLE DIGITAL MULTIMETER.**  
DC volts (4 ranges) 1MV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1µA to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. **PRICE £54.75** Carrying case £9.50. AC adaptor/charger. £3.98 Rechargeable Battery Pack £9.14.



**PANEL METERS**  
DIMS 60MM x 45MM. 50µ amp, 100µ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, "S", "VU", 50-0-50µA, 100-0-100µA, 500-0-500µA. **PRICE £4.95.**



**DESOLDERING TOOL SUCTION PUMP. £5.95**



PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10. ALL PRICES INCLUDE POSTAGE AND VAT. CATALOGUE 50p. DEDUCTIBLE ON FIRST ORDER OF £5.00 OR MORE.

## MICRO MONEY

AS WE go to press the Government has announced a further £100 million investment in microelectronics. This makes the total investment something in the order of £400 million which exceeds the involvement of both the French and German governments. The extra money will be split with £60 million going to education and £40 million to encourage industry to employ microelectronics in products, in the automation of manufacturing equipment and in updating office equipment and practices.

The Prime Minister stated that the use of microelectronics would bring "some crucial job losses" but it was also pointed out that in the past the introduction of new technology had eventually given rise to an increase in jobs in particular industries. The Government Think Tank has also commented on "the contrast between the vehemence of those who claim that microelectronics will have a catastrophic effect on unemployment and the inadequacy of the analysis underlying the certainty of that prediction."

It is indeed heartening to hear such phrases as "dominant technology of the next decade" and to find ministers urging Britain to compete—fast and, what's

more, putting our money where their mouth is!

The point that saddens us is that £15 million has to be spent in making direct presentations to industry to encourage the use of microelectronics. Perhaps we are too conservative to have believed any of the predictions made a few years ago, but surely more of them should have been investigated without companies having to be pushed.

It is often said that the car mechanic is the man slowing down the introduction of electronics to our every day transport, but he will have to accept the computer controlled engine eventually so let's get on with it. Training is what is needed—or retraining as the case may be—and the reinjection of money has been welcomed by both the CBI and TUC.

## HOME COMPUTERS

One area where the microprocessor has found a ready market is in the home computer and now that a significant number of systems and peripherals are available we are taking another in-depth look at the subject. The interest being shown in the P.E. VDU System (published recently) and the P.E. Microprinter shows a demand for

peripherals at the right price and both these projects meet that need admirably. We hope to bring you more projects like these in future. We are now finding a number of hobbyists and engineers that did not follow the microprocessor teachings the first time around and it is our intention to publish a simple microprocessor system and describe the first steps in programming in the near future. So all those that want to learn the subject, and it appears to be of growing importance in many areas, watch out for further announcements.

## DON'T MISS OUT

Whilst looking at forthcoming subjects, we would urge you not to miss any issues and one way of ensuring your copy is to place a regular order with your newsagent. Often we find readers unable to get copies because of heavy demand and since our next issue will carry a 108-page Tandy catalogue (U.K. mainland sales only) and subsequent issues another catalogue and a free gift worth at least £1, demand is likely to be extra heavy—you have been warned.

Mike Kenward

## EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland TECH. SUB EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

### Editorial Offices:

Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

### Advertising Offices:

King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

## ADVERTISEMENT MANAGER

SECRETARY

REPRESENTATIVE

CLASSIFIED MANAGER

D. W. B. Tilleard

Christine Pocknell

Peter Mew 01-261 6819

Colin Brown 01-261 5762

01-261 6676

## Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

## Back Numbers

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

## Binders

Binders for PE are available from the same address as back numbers at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where ap-

propriate. Orders should state the year and volume required.

## Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Cheques and postal orders should be made payable to IPC Magazines Limited.

By MICHAEL TOOLEY B.A.  
and DAVID WHITFIELD B.A.

# PULSE GENERATOR

**E**LECTRONICS is a subject which is largely concerned with the generation and processing of a wide variety of electrical signals. While sine waves are still the most commonly generated waveforms, pulse waveforms are continuing to find ever-widening applications in communications and digital systems. The advent of cheap, readily available digital integrated circuits has brought with it the need for suitable test equipment which will allow the constructor to troubleshoot such digital systems under known conditions. This logic pulse generator is capable of providing waveforms of known characteristics over a wide range of frequencies and pulse widths and has the ability to slow down the operation of circuits to sub-Hertz frequencies to allow tests to be done at speeds low enough to enable functions to be verified with a conventional multimeter.

This instrument also features independent control over both pulse width and pulse frequency.

## CIRCUIT DESCRIPTION

The wave generation system used in the pulse generator features an astable multivibrator to control the pulse repetition frequency and a monostable to determine the output pulse width. The complete circuit diagram of the pulse generator is shown in Fig. 1.

The control circuit uses a 555 timer (IC1), to produce a wavetrain of the required pulse repetition frequency. The actual frequency is determined by the values of the fixed resistors, R1/R2, the setting of the potentiometer, VR1, and the value of capacitor selected, C3 to C8. The resistors set the ratio of the maximum-to-minimum frequency coverage in the ranges, while the capacitor selected determines the actual frequency coverage. The circuit allows modest values of timing components to be used in generating very low frequency signals, without requiring values for the higher ranges which are so low as to make stray capacitances unduly significant. The performance of the astable is independent of supply voltage fluctuations and the output is a stable wavetrain with a well-defined repetition rate and an arbitrary pulse width.

The monostable circuit (IC2) uses a 74121 to set the output pulse width. The astable output drives the monostable active-high input, the active-low inputs being disabled. This configuration causes an output pulse to be produced each time a low-to-high transition occurs at the input. The width of the pulse produced is determined by the timing components, VR2, R5 and C11 to C17. The circuit thus produces two complementary outputs whose repetition frequency is set by the astable and whose pulse width is set by the timing components of IC2. A single-shot facility is provided by using S3, to disable the output of the astable. The momentary switch action may then be used to generate a trigger pulse for the monostable whenever an output pulse is required.

The two monostable outputs are used directly to provide the normal and inverted TTL output signals. Each output will drive up to 10 normalised TTL loads. In addition, the inverted TTL output is used to produce the 0-10 volt variable output. The level translator, TR1, produces 180 degrees of phase shift and drives the emitter follower, TR2. The output signal is taken from a variable tapping on the emitter load resistance, VR3. The Zener diode, D1, serves to set the maximum output level and stabilise the collector potential of TR2.

Some typical operational waveforms are illustrated in the oscillograms in (Fig. 2, 3 and 4).



Front panel annotation

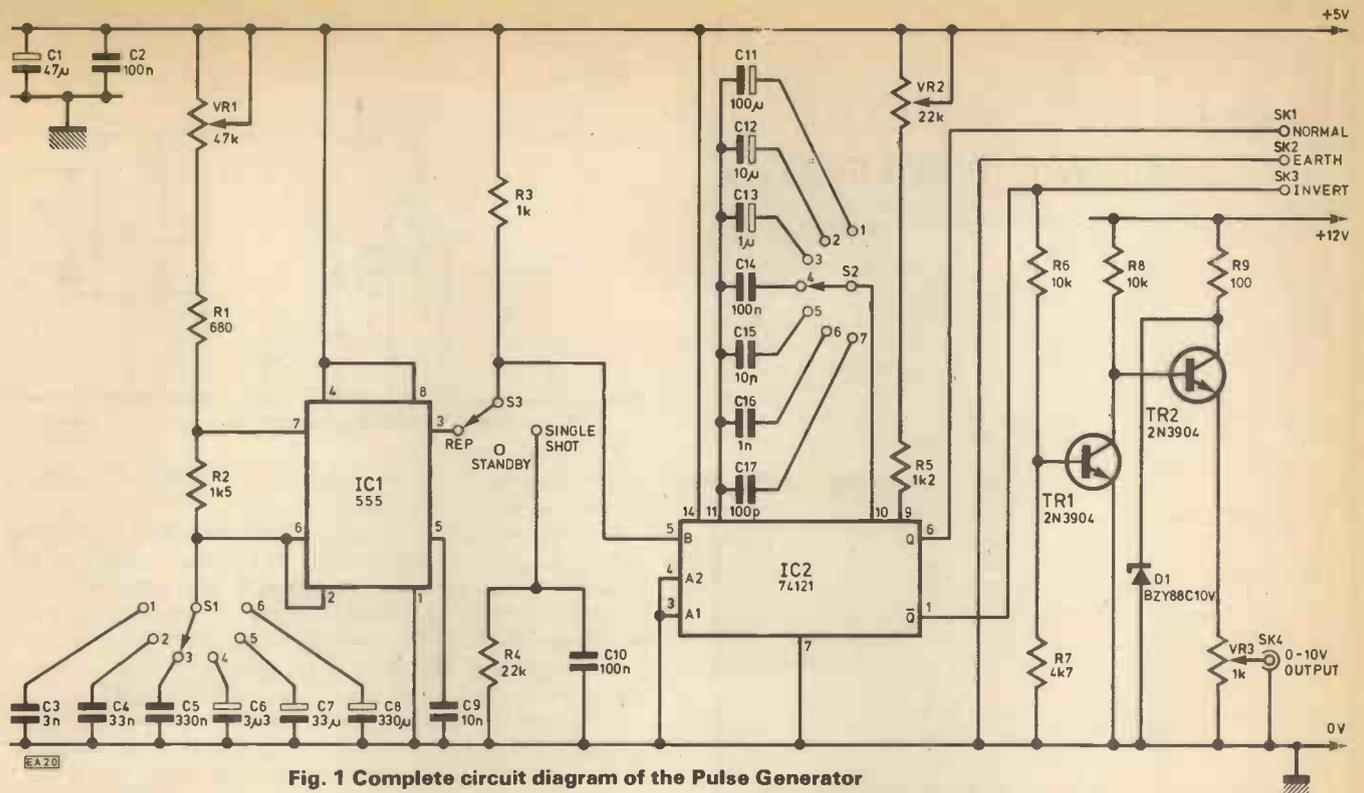


Fig. 1 Complete circuit diagram of the Pulse Generator

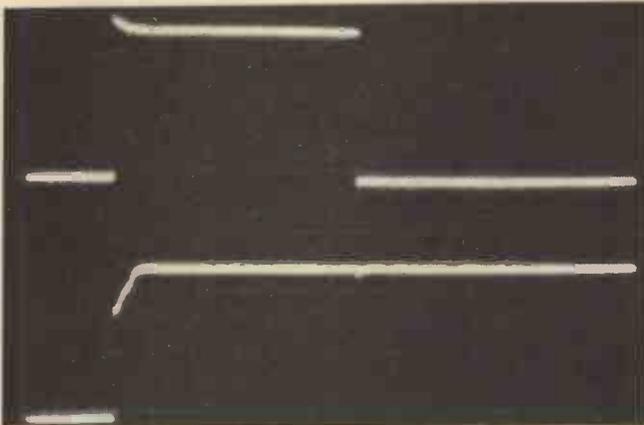


Fig. 2 Upper trace—Non inverted TTL output (IC2 pin 6)  
Lower trace—Output from the astable (IC1 pin 3)  
Oscilloscope setting  $1\mu\text{s}/\text{cm}$  and  $2\text{V}/\text{cm}$

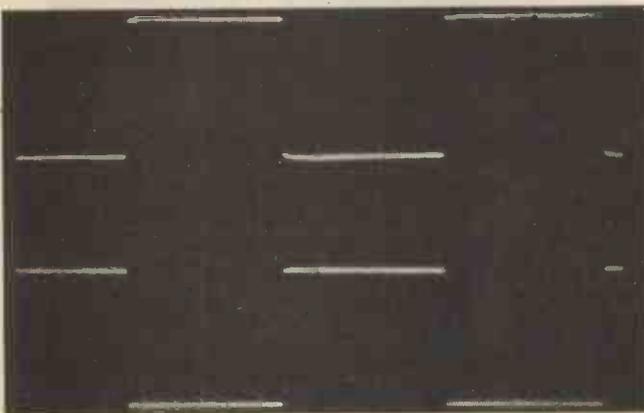


Fig. 3 Upper trace—Non inverted TTL output (IC2 pin 6)  
Lower trace—Inverted TTL output (IC2 pin 1)  
Oscilloscope setting  $10\mu\text{s}/\text{cm}$  and  $2\text{V}/\text{cm}$ . Pulse Generator set to 10kHz

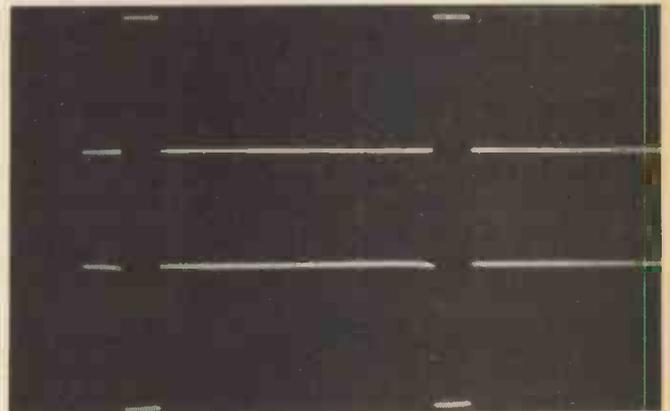


Fig. 4 Upper trace—Non inverted TTL output (IC2 pin 6)  
Lower trace—Inverted TTL output (IC2 pin 1)  
Oscilloscope setting  $10\mu\text{s}/\text{cm}$  and  $2\text{V}/\text{cm}$  (10:1 pulse at 10kHz)

### WAVEFORM MONITORING CIRCUIT

When using any form of pulse generator featuring independent control over both pulse width and repetition frequency, it is usually possible to select combinations which, between them, represent an unrealistic waveform. In practical terms this means that, whatever the front panel controls may say, it is impossible to repeat a 1ms pulse at a frequency greater than 1kHz. Indeed, in order to produce a square wave at 1kHz, a pulse width of  $500\mu\text{s}$  is required. In practical situations it was therefore felt that some form of advance warning of this condition would be a useful reminder to the user of the instrument, especially if it could be incorporated with little additional circuitry.

The circuit of Fig. 5 illuminates the l.e.d. when the duty cycle (the proportion of the cycle during which the normal output is "high") exceeds 50 per cent, a mark space ratio of 1:1. Thus, for a pulse repetition frequency of 1kHz, the l.e.d. will be illuminated when the pulse width exceeds  $500\mu\text{s}$ .

# SPECIFICATION

## OUTPUTS

Non-inverted TTL	Output impedance ("high" level) = 70 ohms
Inverted TTL	Output impedance ("low" level) = 12 ohms
	Each output will drive up to 10 normalised TTL loads, i.e. sink up to 16mA ("low") or source up to 400µA ("high").
	Rise and fall times better than 10ns unloaded.
High level output	Output impedance <math>\leq 1</math> kilohms
	Output continuously variable from 0 to 10V peak.

## RANGES

Pulse frequency	Pulse width
0.1Hz-1Hz	100ns-2µs
1Hz-10Hz	1µs-20µs
10Hz-100Hz	10µs-200µs
100Hz-1kHz	100µs-2ms
1kHz-10kHz	1ms-20ms
10kHz-100kHz	10ms-200ms
	100ms-2s

All ranges overlap by approximately 15 per cent of the maximum nominal range value at either end of the range in order to ensure both total coverage and simplicity of use.

The operational amplifier, IC3, acts as a low pass filter and comparator. The integrating components, R10 and C18, set the time constant of the filter and the mean level of the output from IC2 is compared with the potential at the junction

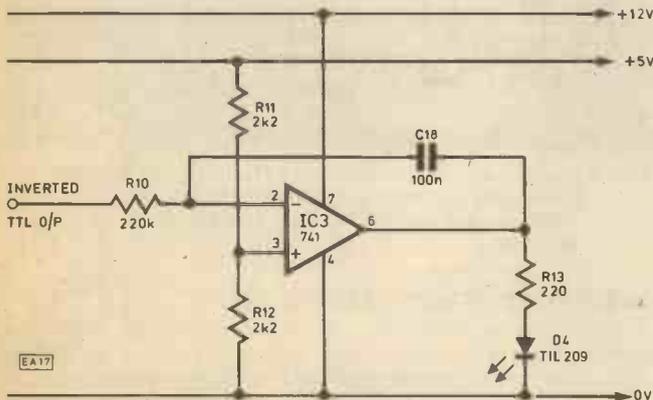


Fig. 5 Circuit diagram to illuminate the duty cycle i.e.d. when an unrealistic waveform has been selected

of R11 and R12. When the mean signal level exceeds this potential, the i.e.d. is illuminated. Making the values of R11 and R12 equal causes the i.e.d. to be illuminated at a duty cycle of 50 per cent. At very low frequencies the i.e.d. provides a direct visual indication of the waveform duty cycle.

## POWER SUPPLY

The circuit of Fig. 6 provides the necessary supply voltages for operating the pulse generator from the mains

supply. A centre-tapped transformer (T1), is used with a full-wave rectifier, D2 and D3, to build up a d.c. voltage across the reservoir capacitor, C19. This voltage is used directly to

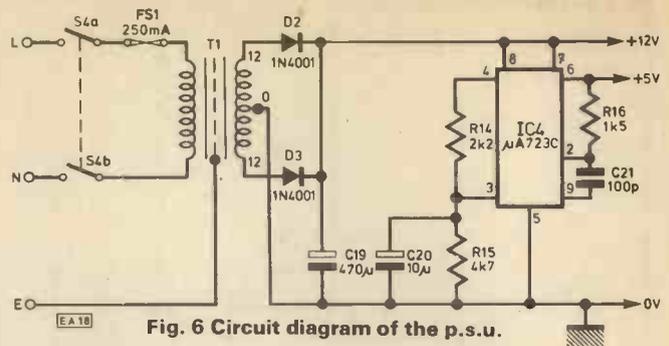


Fig. 6 Circuit diagram of the p.s.u.

provide the supply for the operational amplifier, IC3, and the variable-output buffer amplifier stages.

An integrated circuit regulator (IC4), is used to provide the 5V supply for the logic circuits. The output voltage of the regulator is set by the values of R14 and R15, with R16 selected to minimise temperature drift. The circuit has a line regulation of 0.5mV for a change of input voltage of 3V, and a load regulation of 1.5mV for a change in load current of 50mA. Frequency compensation is provided by C21.

For portable operation, the transformer and rectifier components may be omitted, and the d.c. supply (in the range 12 to 18 volts) connected across the reservoir capacitor, C19.

## CONSTRUCTION

The unit was constructed on a p.c.b. the layout of which is shown in Fig. 7 with the component overlay shown in Fig. 8. A careful check should be made that the semiconductors and integrated circuits are correctly orientated. The use of

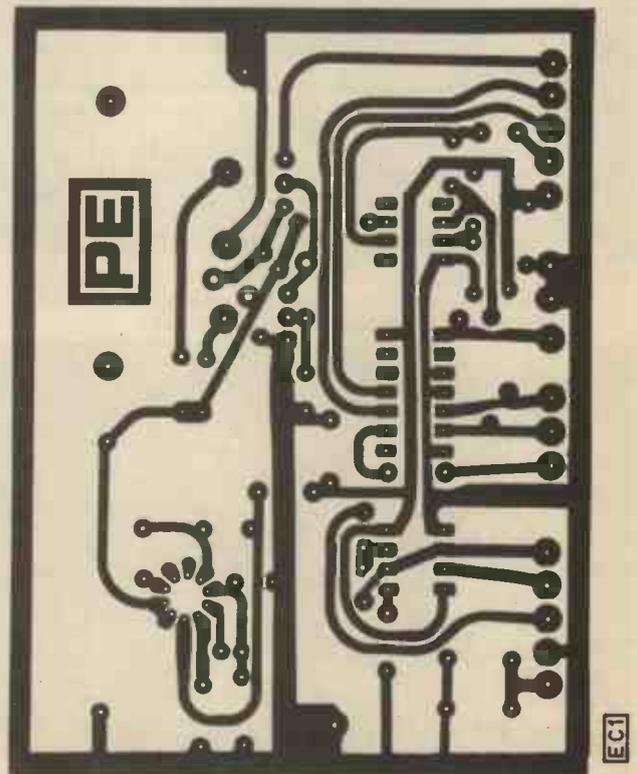


Fig. 7 P.c.b. layout for the Pulse Generator

# COMPONENTS . . .

## Resistors

R1	680
R2, R16	1k5 (2 off)
R3	1k
R4	22k
R5	1k2
R6, R8	10k (2 off)
R7, R15	4k7 (2 off)
R9	100
R10	220k
R11, R12, R14	2k2 (3 off)
R13	220
All resistors $\frac{1}{4}$ W 5% carbon	

## Capacitors

C1	47 $\mu$ elect
C2, C10, C14, C18	100n (4 off)
C3	3n polystyrene
C4	33n polystyrene
C5	330n
C6	3 $\mu$ 3 elect
C7	33 $\mu$ elect
C8	330 $\mu$ elect
C9, C15	10n (2 off)
C11	100 $\mu$ 10V elect
C12	10 $\mu$ elect
C13	1 $\mu$ elect
C16	1n polystyrene
C17, C21	100p polystyrene
C19	470 $\mu$ 25V elect
C20	10 $\mu$ 16V elect

## Potentiometers

VR1	47k log
VR2	22k lin.
VR3	1k lin. with d.p.s.t. switch

## Switches

S1	Rotary switch 2 pole 6 way
S2	Rotary switch 1 pole 12 way
S3	Sub min toggle switch, single pole c/o centre off, biased one way

## Semiconductors

D1	BZY88 C10V 400mW Zener
D2, D3	1N4001 (2 off)
D4	TIL209 l.e.d.
TR1, TR2	2N3904 (2 off)
IC1	NE555
IC2	SN74121P
IC3	741P
IC4	$\mu$ A723C

## Miscellaneous

T1	12-0-12V 50mA transformer
FS1	250mA
SK1	B.N.C. round socket
SK2, 3, 4	RS type 444-703
Control knobs	
Case	

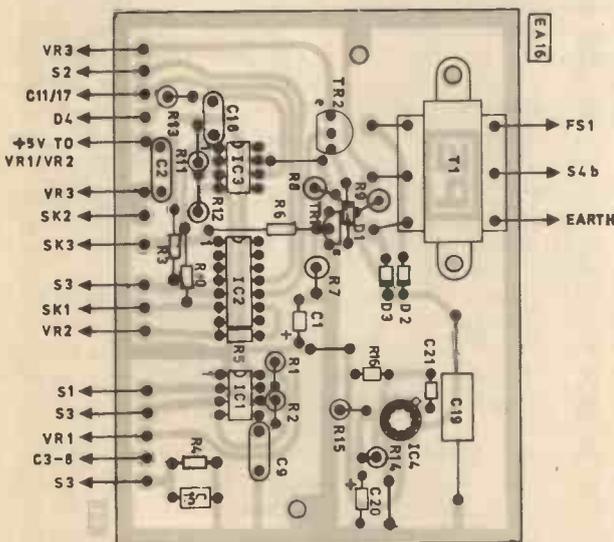


Fig. 8 Component overlay for p.c.b.

integrated circuit holders is also recommended.

The pulse generator is housed in a small aluminium case fitted with a detachable cover. The mains transformer is secured to the printed circuit board using two 4BA nuts and bolts and the board itself is supported by means of two pillars attached to the base of the case. Interconnecting

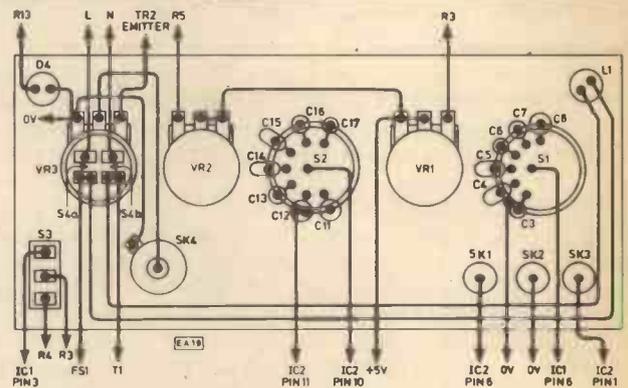



Fig. 9 Wiring diagram for front panel

wires, from the printed circuit board to the front panel, should be kept as short and as neat as possible. The use of colour coded wires is recommended as this further simplifies construction. The layout of the front panel is shown in the photograph with the corresponding internal wiring shown in Fig. 9. Capacitors C3 to C8 and C11 to C17 are mounted directly on S1 and S2 respectively. The common connection in each case consisting of a short length of 18 s.w.g. tinned copper wire formed into a circle of approximate diameter 22mm. The resulting capacitor assembly being self-supporting.

The front panel should be labelled using dry transfers and then given a light coating of clear protective lacquer. ★

# ENVIRONMENTAL THERMOMETER

M. PLANT

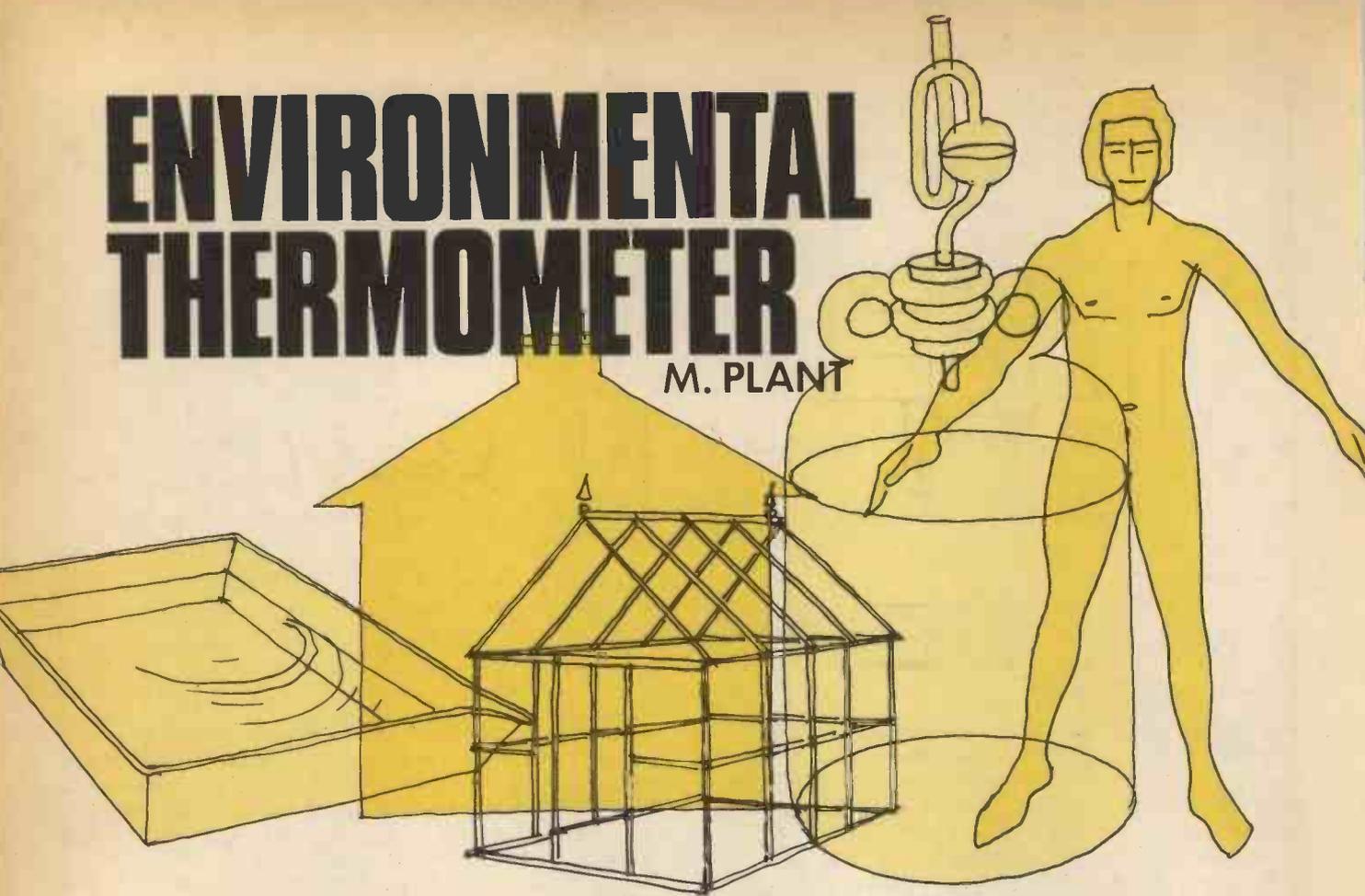

**T**HIS environmental thermometer which is capable of measuring temperatures from  $-15^{\circ}\text{C}$  to  $50^{\circ}\text{C}$  uses a moving coil meter that can be switched over three ranges ( $-15^{\circ}\text{C}$  to  $10^{\circ}\text{C}$ ,  $5^{\circ}\text{C}$  to  $30^{\circ}\text{C}$ ,  $25^{\circ}\text{C}$  to  $50^{\circ}\text{C}$ ) to display the temperature reading.

The thermometer is easy to calibrate since the zero setting and range controls are independent of each other. This means that once the range is set for one scale, only one calibration point is required for each of the other ranges.

## DESIGN CONSIDERATIONS

One of the problems to overcome when designing stable electronic circuits is the unwanted effect that changes in temperature have on the characteristics of the semiconductors being used. This effect is exploited in the thermistor although this is an unsuitable device for an electronic thermometer since the marked non-linearity of its resistance/temperature characteristics needs to be compensated for before a linear display on a meter can be obtained.

Since an ordinary silicon transistor is temperature sensitive, with the forward voltage drop of the pn junction varying linearly with the temperature (provided the current flowing through this semiconductor junction is maintained constant) it is ideal for use in a thermometer probe.

All three elements of the thermometer have linear characteristics, the pn junction temperature sensor produces a voltage which is directly proportional to temperature, the voltage amplifier has a linear transfer characteristic and the display element produces a visual reading which is proportional to the voltage fed to it from the amplifier.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the Environmental Thermometer is shown in Fig. 1. There are two main aspects of

this circuit. One is the constant current generator provided by IC2a and the other is the highly stabilised power supply provided by IC1. Once the latter is achieved, the former is automatically obtained. An integrated circuit regulator, IC1, is used for obtaining a split voltage stabilised supply for the operational amplifiers, IC2a and IC2b. The regulator i.c. is wired up to give a  $\pm 7\text{V}$  dual supply from a single ended input voltage in the range 18V to 27V. The current drawn by the circuit is only a few milliamps which the regulator can supply without the need for current buffer transistors. Thus two or three small PP3 batteries connected in series can operate the circuit for long periods. The advantage of relying on the internal reference diodes in the regulator i.c. is that they are internally temperature compensated.

The transducer pn junction (D3) may either be a silicon diode or the base-emitter junction of a silicon transistor. In the prototype probe a plastic packaged ZTX300 transistor was used to good effect since it is both small and resistant to the corrosive effects of any liquids into which it might be immersed.

In order to keep circuit interconnections as simple as possible, a dual op amp integrated circuit was used for IC2. Op amp IC2a is wired as a constant current generator with its non-inverting input placed at ground potential through R6. Due to the high gain of the op amp, the output voltage always moves sufficiently positive to maintain the inverting input at ground voltage as well. Thus the current through R5 is set at about  $7\text{V}/120\text{k}$  or  $60\mu\text{A}$  by the ground to  $-ve$  rail stabilised voltage. Since the current into pin 1 of the op amp is very small and can be neglected, all the constant current which flows through the pn junction is small enough not to cause self-heating of the junction.

The second op amp IC2b offsets the diode voltage to whatever range is selected and the second provides

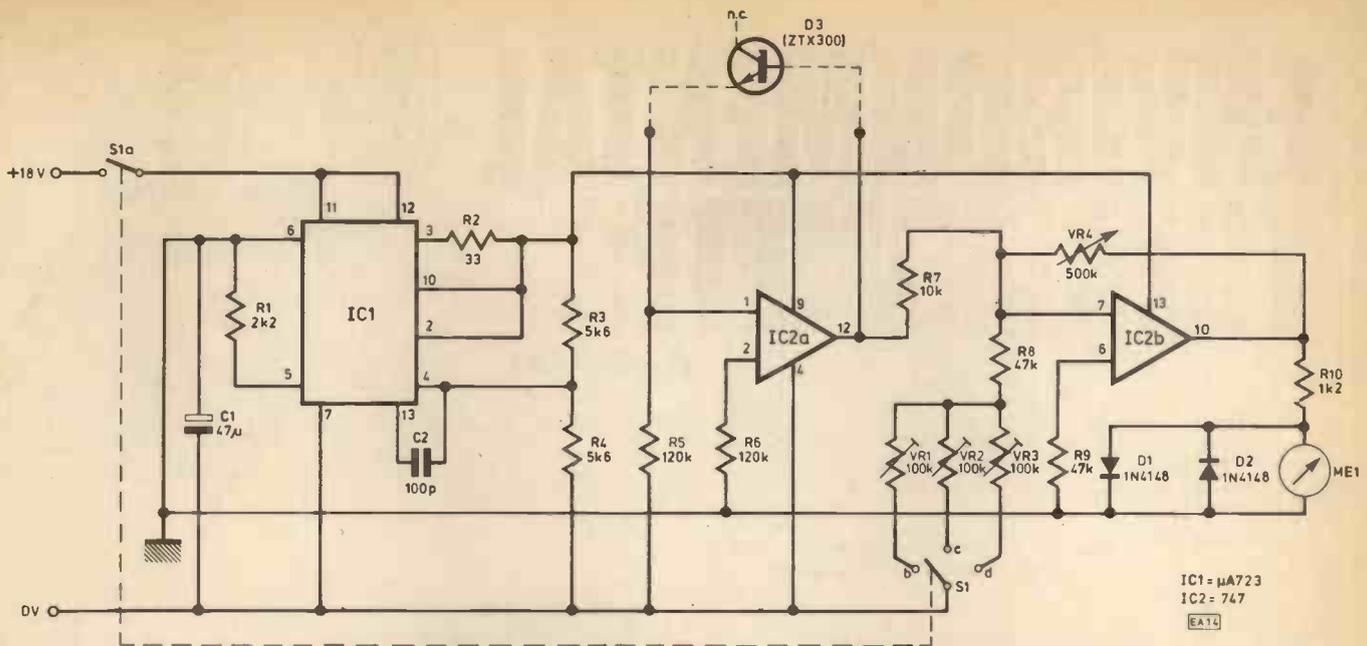


Fig. 1. Complete circuit diagram of the Environmental Thermometer

amplification of this voltage so that a deflection on the moving coil meter can be obtained. The offset is provided by the setting of the variable resistors VR1, VR2 and VR3 to give the three ranges as previously specified, and variable resistor VR4 sets the gain of the circuit to give the span of 25°C chosen for each range. The voltage gain is the ratio of VR4 to R7. Since the change of input voltage produced by the required range of 25°C is 25 x 2.2mV or 55mV, to produce an output voltage change of 2V requires a gain of 2V/55mV or about 37. This value of gain is within the ratio of 500k (max value of VR4) to R7, (i.e. 50.) Note that since the forward voltage across D3 falls with rising temperature, IC2b is connected as an inverting amplifier. The value of the series resistor R10 is chosen so that, with a maximum output at pin 10 of the op amp (i.e. 2V), only enough voltage is applied across the meter to produce full scale deflection. As the resistance and the full scale deflection current of the meter is known it is possible to work out the value of R10 using the equation

$$R10 = (2/I) - Rm \text{ (k}\Omega\text{)}$$

where I is the f.s.d. current for the meter in milliamps and Rm is its resistance in ohms. The value of Rm can usually be

neglected since it is small and the approximation  $R10 = (2/I)$  kΩ can be used. Note that the gain of the amplifier IC2b can be adjusted, so that the value of R10 is by no means critical. However, to avoid the possibility of saturating the amplifier, the maximum output voltage should be measured with a voltmeter so that it is in the range 2 to 4V.

Switch S1 is a three-pole four-way rotary switch wired so that one position is off and the other three positions select one of the three range resistors VR1, VR2 or VR3. Should more ranges be required this switch can be changed to a two-pole six-way version to accommodate two extra ranges (e.g. 45°C to 70°C and 65°C to 90°C).


Incidentally, if the current driving the meter is different from the setting of the range switch the movement of the meter could be damaged. Therefore, diodes D1 and D2 are connected back to back across the meter to provide protection (since the diodes only conduct when the full scale deflection voltage across the meter rises above 0.6V). Most meters will tolerate two or three times their f.s.d. current.

### CONSTRUCTION


As Fig. 2 shows, all the components can be mounted on a piece of 0.1 in. matrix Veroboard. Check that solder does not bridge between the tracks unintentionally and that the tracks are drilled cleanly at the points indicated. Use holders for the i.c.s since this will make replacement of faulty devices easier, and then check the layout carefully against the circuit diagram.

External connections are required to the switch S1, the meter, the sensor and the batteries. Note that in order to keep the wiring neat, the two common leads to the batteries are connected together via a spare track on the board. A miniature jack socket was used in the prototype for connecting the pn junction sensor to the circuit.

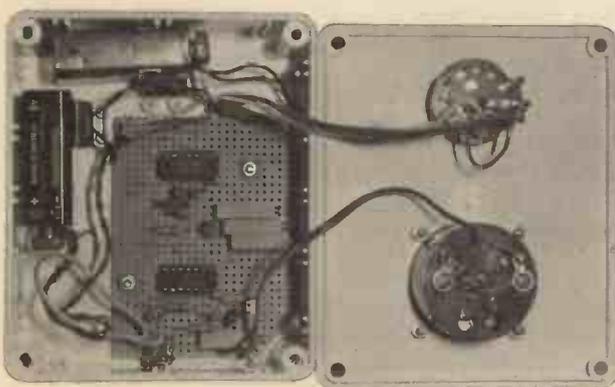An aluminium battery clamp is used to hold the PP3 batteries firmly in the case. Once the Veroboard has been fitted to the base of the case and the leads taken to the switch and the meter, four small holes should be drilled carefully through the side of the box so that a screwdriver can reach the variable resistors VR1, VR2, VR3 and VR4 to set the gain and the zero offset of the ranges.



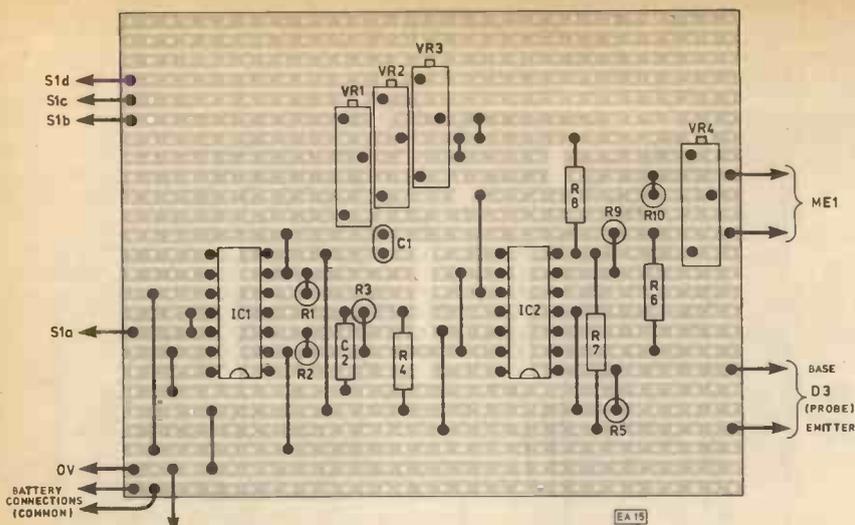Internal layout of the Environmental Thermometer



S1 (COMMON) Fig. 2. Veroboard layout for the Environmental Thermometer



## THE SENSOR

Carefully remove the collector lead from the ZTX300 transistor. Flexible insulated wire should be soldered to the base and emitter leads using sleeving to ensure that they cannot be shorted together. The wires should be passed down the body of a felt pen so that the transistor sits firmly in place at one end. The transistor should be sealed in place using Araldite to ensure that no water or other liquids can penetrate the probe.

## CALIBRATION

This is fairly straightforward since the range and offset adjustments are independent of each other. The top range (25°C to 50°C) is best set first using two cups of water at these two temperatures. A helper is needed here to ensure that these two quantities of water are well stirred and with occasional topping up, are maintained at these temperatures. An accurate ( $\pm 0.5^\circ\text{C}$ ) thermometer should be used. With the sensor at 25°C adjust VR1 to bring the meter to the (25°C) mark on the scale.

With the sensor at 50°C adjust VR4 to bring the reading to the upper end of the scale. Repeat these two adjustments until the needle swings between the upper and lower scale markings. The range is now set at 25°C and the lower point of one scale determined. Now switch the thermometer to the next lower scale (5°C to 30°C) and put the probe in the 25°C water. Adjust VR4 until the scale reading is 25°C which is four fifths of f.s.d. on the meter. This range is now set up, since the gain of the amplifier has already been determined in the first calibration, so that the lower end of this second scale corresponds to 5°C. Finally, for the lowest scale, stir some crushed ice in water and wait for the temperature to fall to 0°C. Adjust VR3 so that the needle reaches two fifths of f.s.d. The lower point of  $-15^\circ\text{C}$  could be reached during a very cold spell in this country but check your deep freeze on this scale for starters.

## SCALE READINGS

It should be obvious from the foregoing that the range chosen for the meter is entirely your own choice, subject to the gain of the op amp being sufficiently high. For example a range of 5°C not 25°C would require a gain of  $5 \times 37$  or about 200. Since the maximum gain with the components shown in the circuit is about 50, four times this gain requires VR4 to have a value of about 2 megohms. To a large extent the range chosen is determined by the graduations on the meter (25 divisions in steps of 5 for the meter was used in the prototype.)

## IMPROVED STABILITY

If greater stability against ambient temperature changes is required 748 op amps can be used in place of the 741's specified. However, these op amps require external frequency compensation by the connection of a 100pF capacitor between pins 1 and 8. Otherwise the component values remain the same as in the circuit described. ★

## COMPONENTS . . .

### Resistors

R1	2k2
R2	33
R3, R4	5k6 (2 off)
R5, R6	120k (2 off)
R7	10k
R8, R9	47k (2 off)
R10	1k2
All $\frac{1}{2}$ W 10% carbon	

### Potentiometers

VR1, VR2, VR3	100k 20 turn preset (3 off)
VR4	500k 20 turn preset

### Capacitors

C1	47 $\mu$
C2	100p

### Semiconductors

D1, D2	1N4148 (2 off)
D3	ZTX300
IC1	$\mu$ A 723
IC2	747

### Miscellaneous

S1	3 pole 4 way rotary switch
SK1	Min jack socket
PL1	Min jack plug
ME1	1mA meter
B1	PP3 battery (2 off)
Battery clips	(2 off)
Case	100 x 120 x 40mm
Veroboard	

# Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by  
**Alan  
Turpin**

and  
**David  
Shortland**

## LOGIC ANALYSIS TEST KITS

The 20 page professional products catalogue of Continental Specialties Corporation (CSC) has specifications on their following products: 550MHz Counter, 100MHz Counter, 50MHz Counter, 500MHz Prescaler; Function Generator, Pulse Generator; Digital Pulser, Logic Monitors, Logic Probes, Logical Analysis Test Kits; Breadboarding Equipment—Quick Test Sockets and Bus Strips, "Experimenter" Sockets and Bus Strips, Proto-Boards, Powered Proto-Boards, and i.c. Test Clips.




The Logical Analysis Test Kits comprise a Logic Probe, Digital Pulser, Logic Monitor, Probe Tips, Leads and Adapters, Manuals and Application Guides, all in rugged custom moulded cases. The kits are £127 and £143 plus VAT.

Catalogue, price list, order form from CSC UK Ltd, Shire Hill Ind. Est., Saffron Walden, Essex CB11 3AQ (0799 21682).
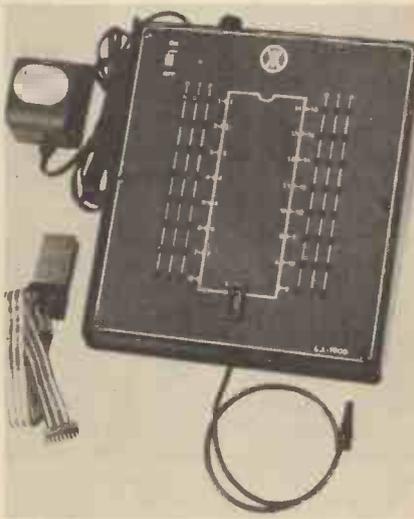
## LOGIC INTERPRETER

Introduced by the United States manufacturer Kurz-Kasch Inc. the L1-1000 Logic Interpreter automatically displays static and dynamic states of digital i.c.s in circuit. Logic high, low and transitions are accurate to plus or minus five per cent. All logic levels are current is drawn from the board under test as a fully isolated, regulated power supply accompanies the interpreter.



Singer Products are the exclusive export representatives of Kurz-Kasch and further information can be obtained from—Gil Williams, Electronic Division, Singer Products Company Inc., One World Trade Center, Suite 2365, New York, N.Y. 10048.

## DIGITAL PHOTO TACHOMETER

From Power Instruments of the USA is a touchless, digital photo tachometer, for measuring the r.p.m. of rotating objects from distances of between  $\frac{1}{4}$ in and 30in.

A piece of reflective tape is fixed on the surface of an object, and when the object is rotated a beam of light from the probe is focused on the tape path. A "target eye" lights up on the tachometer, showing when contact is made, and an r.p.m. readout is given on five  $\frac{1}{8}$ in l.e.d.s. A memory holds the reading indefinitely.




Being touchless, the tachometer can be used in places awkward to reach, and there is a 24in cord attached to the probe. The readout is quartz crystal controlled, with an accuracy of  $\pm 1$  digit up to 0.03 per cent. There is direct reading up to 30,000 r.p.m.

Powered by ordinary batteries, the model 1891 is provided with an aluminium carrying case, reflective tape and other accessories. It measures  $8\frac{1}{2}$ in  $\times$   $4\frac{1}{2}$ in  $\times$  2in and weighs  $1\frac{1}{2}$ lbs.

Optional extra accessories include measuring wheels, hand-held or permanent surface mounted to measure linear speed.

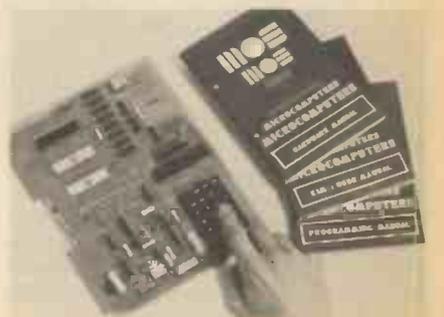Price is £155, plus VAT and carriage, and it is available from the sole UK importers, Electronic Brokers Ltd, 49/53 Pancras Road, London NW1 2QB (01-837 7781).



Price of the KIM 1 single board microcomputer was reduced to £99.95 +VAT in December. Full details from GR Electronics Ltd., Fairoak House, Church Road, Newport, Gwent.



### PRINTOUT CALCULATOR

A new hand-held calculator incorporating its own thermal printer has been introduced by Texas Instruments.

The TI-5025 operates from a rechargeable battery and has a large vacuum fluorescent display which can be used without the printer to conserve paper.

Functions provided are addition, subtraction, multiplication and division—plus percentage key and a 4-key memory.

It operates with the simple number-entry system used with other hand-held calculators in the Texas Instruments range.

The thermal printer is quiet in operation, has few moving parts and requires no ribbons; thermal-paper rolls are available in packs of three.

The TI-5025 measures 6.7 x 3.4 x 1.8in (170 x 86 x 46mm), and is supplied complete with a charger/adaptor, thermal paper and carrying case. VAT inclusive price is £64.95.

Details from **Texas Instruments Limited, European Consumer Division, Manton Lane, Bedford, MK41 7PA.**



### CAR CLOCK

This car clock from Speedograph is connected through the ignition system and when the ignition is off the l.e.d. display is also off, thus preventing undue battery drain. The time keeping circuit remains on. The readout which automatically dims at night reads hours and minutes with a flashing second indicator.

The unit can be mounted using either an adjustable bracket or a self adhesive pad both of which are supplied.

The clock is priced at £27.55 plus VAT and is available from many accessory shops.

### A-TO-D CONVERTORS

National Semiconductor has added two microprocessor-oriented analogue-to-digital convertor devices to its product range.

Available in both a 3½ digit version designated ADC 3511, and in a 3¾ digit version designated ADC 3711, the new devices are complementary CMOS circuits that provide addressed binary coded decimal output for digital systems.

Operating from a single isolated 5V supply, the devices are designed to convert input voltages from -2.00 to +2.00V. The sign of the input voltage is automatically determined and indicated on the sign output pin, and overflow is indicated by a Hex EEEE output reading as well as by an overflow output pin. Unipolar input voltages do not require the use of isolated supplies.

The ADC 3511 and 3711 have their conversion rates set by an internal oscillator whose frequency may be determined by an external RC network, or can be driven from an external frequency source. The timing of conversions may be controlled and monitored via the Start Conversion input and Conversion Complete output which have been included on both devices.

### STEREO MIXER

This portable four channel mic/line mixer by Soundex Limited was designed for stereo recording and features true PPM or VU metering, stereo gain control for a crossed pair of microphones and two "pan" controls for two spot microphones.



Frequency response is 20Hz to 20kHz, signal to noise ratio is 11db with 180µV from 150-600 ohms.

Optional variations are internal rechargeable cells, and XLR or jack connectors.

For further information contact **Tony Barnes, Bulgin Electronics Soundex Limited, Park Lane, Broxbourne, Hertfordshire EN10 7NQ (099 24 64455).**

### ALL THE PROJECTS IN EPI

The Libraries and Arts Department of North Tyneside Metropolitan Borough Council have published an Electronics Projects Index (EPI). This descriptive guide covers over 2,500 projects published by (in alphabetical order) Electronics Today International, Elektor, Everyday Electronics, Practical Electronics, Practical Wireless, Radio and Electronics Constructor, Television, and Wireless World.

Most of the coverage is from January 72 to December 77, and all amendments to October 78 are included. Price is £1.50 inc. p&p. Postal Orders and cheques should be made payable to North Tyneside M.B.C.

Copies of the index are available from: **M. L. Scaife, Central Library, Northumberland Square, North Shields, Tyne & Wear NE30 1QU. Enquiries (08945 82811).**

### FREQUENCY COUNTERS

Davis Electronics announce the introduction of their frequency counters. The basis of the design is an LSI chip which is a seven decade counter. This is extended to a full 8 digits by feeding the processed signal to a single decade counter, that is then decoded and fed to the least significant digit for display. The LSI then counts, decodes and feeds the digit drivers for the other seven digits. A further chip performs the functions of Xtal oscillator, gating dividers and driver, multiplexing signal generator, etc. Other discrete circuitry provides for signal conditioning, shaping, amplification and protection.



A pre-scaler and amplifier provide facilities for extending the 8 digit counter block to 600Mhz. This is switched in from the front panel. Also provided is switching for gate time and power. A "gate open" l.e.d. indicates when the count is active. A special Xtal in a proportionally controlled Xtal oven is also available.

Full specification and prices from distributors **Craef UK Ltd, 7 Hughendon Road, Hastings, Sussex TN34 3TG. (0424 428131).**

### ARE YOU BEING CHARGED?

Coinciding with the change of name from Ever Ready (Special Batteries) Limited, Berec (Special Batteries) Limited introduce a range of rechargeable batteries and chargers for the consumer market.



equivalents of HP2, HP11, HP7 and PP3, and three chargers, two for specific batteries and one to take the three cylindrical batteries so that it is possible to charge different sizes at the same time. The chargers will recharge a fully discharged battery in 14-16 hours.

*We are sorry to have to report a devastating fire at the Talk of The Town, Cambridge, 16 businesses were affected including that of Tempus. They are doing all they can to continue their normal service but apologise to anyone experiencing delay.*

**VERO ON VIEW**

In the interests of their products being in first class condition when they reach the home constructor, Vero are skin packaging Veroboards, Veropins and other accessories.

The full range of newly designed packs can be seen on floor standing displays which will also contain a range of boxes. Component



shops with little floor space are offered a simple wall stand with a limited range of Vero products.

All this, at no extra cost, say Vero.


**MEMORIES THAT LAST**

The latest scientific calculator from Casio has seven non-volatile memories which are powered by separate batteries that can hold stored figures when power is switched off—overnight, or for days or weeks at a time, even while exhausted main cells are being changed.

A powerful machine with 59 built-in functions, the FX-360 also offers a choice of power supplies: normal penlight batteries, rechargeable NiCad power pack, or a.c. mains via an adaptor.

Calculation capacity is 10 digits, plus two in the exponent. Trig functions and their inverses are handled in three types of measure, in degrees, radians or gradient. Statistical scope includes standard deviations, linear regression, or fitting logarithmic curves, exponential curves or power curves.

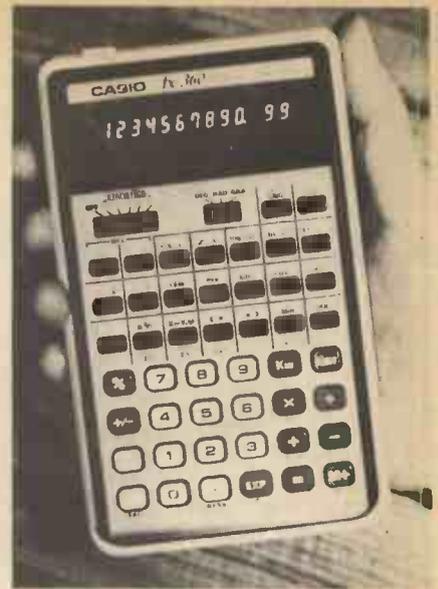All the usual log, trig and hyperbolic functions are provided, plus permutations/combinations, rectangular/polar conversion, and factorials. The unit also handles fractions and many types of problems involving percentages. It copes with parentheses up to eight levels, and features a random number generator.



There is one independent accumulating memory plus six constant memories. Their contents are fully protected by two silver oxide batteries when main power is switched off.

The recommended retail price of the FX-360 is £59.95 including VAT. For further information contact Casio Electronics Co Ltd, 28 Scrutton Street, London EC2A 4TY.



# Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

**PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM**

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for.....(amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53626. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

# Home Computers

## ...the Microprocessor Miracle!

PART ONE — R.W.COLES

FROM their barely noticed beginnings in the early seventies, microprocessors have mushroomed to become the number-one talking point among engineers and hobbyists alike. Industry is rapidly awakening to their power and capabilities, and many professional engineers are engaged in an undignified scramble to become conversant with this at first alien new technology. Meanwhile, most electronic hobbyists have been waiting on the sidelines for a convincing demonstration of how micros can help them; only a few have actually taken the plunge and built one of the simple "evaluation-card" systems which can be programmed in machine code.

Anyone who has purchased an evaluation card has probably learnt a great deal about microprocessors, but many will be disappointed by the problems involved in getting their system to do anything really useful. Persuading a micro to perform the functions of an ordinary calculator, for example, could take weeks of programming effort. A great chance to learn about computer arithmetic perhaps, but not really very practical. Using the microprocessor to replace random logic, to act as the controller of a domestic heating system for example, can, and is, being achieved with small evaluation cards. But how many hobbyists want to build logic systems of such complexity that the microprocessor becomes a viable alternative to say TTL or CMOS? Not very many.

### ENTER THE HOME-COMPUTER

Paradoxically, the microprocessor is about to take the hobby market by storm, but it's not really the electronic hobbyist who is the main target. Armed with a high level language interpreter, surrounded by semiconductor memory, a typewriter keyboard and a television display unit, the microprocessor now forms the heart of a general purpose computer system which can be sold not only to electronic



The PET home computer together with its printer and second "external" cassette recorder



The Micros Z80 based system

enthusiasts, but to anyone who is prepared to spend a few days learning the rudiments of BASIC language. The home-computer has arrived!

Already small-business men, doctors, dentists, and hotel owners, computer programmers and of course, electronics enthusiasts, are rushing to buy one of the few systems already on the market, even though a home-computer system worth the name will cost £500 or more!

Five hundred pounds may seem like a great deal of money, but thanks to the microprocessor, you will get a computer which would have cost £10,000 and filled a fair sized room, ten years ago.

Not surprisingly, the home-computer concept originated in the United States, and its proliferation there has been extremely rapid, catching even the manufacturers off guard to begin with. In the United Kingdom, economic constraints will probably result in a slower build up, but already that build up has begun!

### WHAT IS A HOME-COMPUTER?

A home-computer (also called micro-computer or personal-computer) has no universally accepted definition. Some manufacturers may wish you to believe that their small machine-code micro with a hexadecimal keyboard is a home computer, when in my view it certainly is not. I have also heard of avant garde computer hobbyists with old IBM systems installed in their garage, and this too falls outside my definition, which is as follows:

A home-computer is a small, low cost, general purpose digital computing system which uses an LSI microprocessor chip as its CPU (Central Processor Unit) and which is capable of storing and executing programs written in a high level language such as BASIC or PASCAL.

To get a clearer idea of what I mean, let's take as an example one of the more popular home-computers currently available, the Commodore PET (left). As you can see, the



**The Tandy TRS 80 which is supplied complete with a video monitor, mains transformer and cassette recorder**

PET is a fully integrated system which requires only a mains socket for instant use. Inputs are entered via a typewriter style keyboard, and outputs are displayed on a built-in 9in CRT screen which is arranged as 25 lines of 40 characters each. To the left of the keyboard is a built-in cassette recorder.

Using standard audio cassettes, programs or data entered via the keyboard may be recorded for later use, and commercial software such as business programs or games can be entered in cassette form without recourse to any tedious typing. Inside PET there lives a 6500 8 bit microprocessor surrounded by 8K bytes of RAM, 14K bytes of ROM, cassette, keyboard, and screen interface logic, and a bidirectional input/output port which can be used for a variety of external peripherals. The 8K of RAM forms a read/write memory area into which programs or data may be entered from the keyboard or cassette. Data is retained by this memory only while the power is "ON" of course, so it is normal for PET users to save any useful RAM data as a cassette tape data-file before the end of a programming session. The 14K of ROM appears to the microprocessor very much like the RAM, but in this case programs are stored in the mask programmed ROM chips during manufacture, programs which cannot be lost or modified and which form the all important firmware operating system and BASIC language interpreter. Putting all the system software in ROM is a technique pioneered by the PET and it confers several advantages over other machines which



**The Research Machines 380Z system**



**The Apple II system**

require these facilities to be loaded into RAM from a cassette or paper tape:

- (1) ROM is cheaper than RAM. This means the economics are better because RAM is traded for ROM.
- (2) No load-delay is incurred while cassettes or paper tape are read.
- (3) The software is more reliable because ROMs, unlike cassette tapes, do not wear out. The main disadvantage is, of course, that you are stuck with the BASIC language which PET is born with, and if your fancy should later turn to PASCAL or Assembly language, there is not much you can do!

#### **WHAT DO THEY DO?**

The PET then, is a typical home-computer, but there are many variations on the theme. Some home computers require a separate VDU and keyboard but display their outputs on an ordinary television via a UHF modulator; some provide a graphics, or picture-forming facility; still others have full-colour graphics, and so on. If there is one thing that they all have in common, it is their ability to run programs written in a high level language, usually BASIC.


#### **BASIC**

BASIC (Beginners All Purpose Symbolic Instruction Code) has been around for a long time and was originally conceived as an aid to teaching computer science and



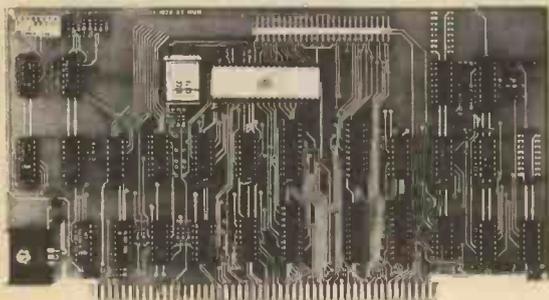**The Nascom I is supplied in kit form and requires a power supply and VDU for operation**


programming subjects. BASIC is an interpretive language, unlike for example FORTRAN which is compiled. Next month we will be examining home computer software in more detail and the distinction between interpreters and compilers will be discussed. For the moment all you need to remember is that interpretive languages are very easy to use, but quite slow in operation. In computer science terms this makes BASIC a less "powerful" language than say FORTRAN, but this is perhaps misleading because BASIC contains all the math, trig, and data handling functions you are likely to need, and most versions provide an arithmetic precision which is as good as, or better than, your trusty pocket calculator. For most home computer applications, the



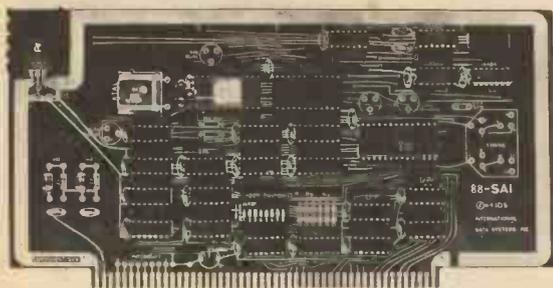**S100 Bus board**

slowness of BASIC programs is no real disadvantage, and anyway entering and debugging programs is actually much faster with BASIC because there is no wait while a compiler is used to process the newly entered program.

If you know anything at all about microprocessors and their instruction sets, just spend a few seconds considering the problem of producing a machine code program which will accept keyboard inputs, carry out decimal division, and print an answer. The keyboard input routine alone might take as many as 100 program lines, depending on the hardware, and a similar number might be needed to control a VDU or printer. The decimal arithmetic routine could be very tricky indeed and may need as many as 500 lines of code!



**S100 Bus board**

Now see how easy it is in BASIC. All you need to type in order to load the program is:

```
10 INPUT A, B
20 PRINT A/B
30 END
```

and to set it running you type:

```
RUN
```

followed by a pair of decimal numbers in response to the ? prompts printed by BASIC. Improving this simple program is easy. Adding another line:

```
5 PRINT "ENTER TWO DECIMAL NUMBERS A, B"
```

provides a better prompt, and changing line 20 to:

```
20 PRINT "A/B = "; A/B
```

gives an answer which is self explanatory. Changing line 30 to:


```
30 GOTO 5
```

removes the need to type RUN for each new pair of numbers, and of course, other enhancements can be added just as easily!
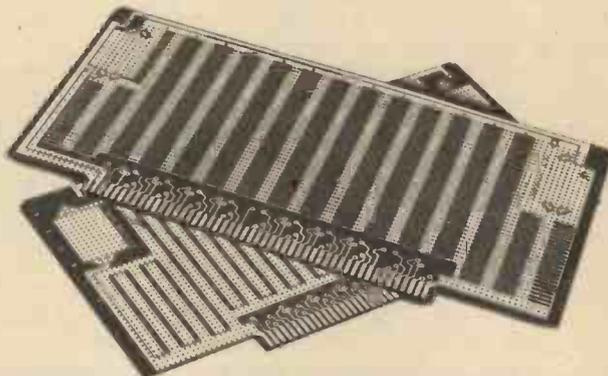
### TRANSPARENT

In home-computers then, the microprocessor chip together with its registers and instruction set is more or less transparent to the programmer. I say "more or less" because most home computers will allow you to dabble in machine language programming if you really must, and in fact this facility is very useful for anyone who wishes to hook their computer up to gadgets in the outside world, as many electronics hobbyists undoubtedly will.

Using a high level language, doing useful or entertaining things with a microprocessor is easy. Within a few hours of picking up a BASIC manual, you will be able to write small programs which sort lists of numbers into ascending or descending order, write amusing messages on the VDU, or calculate the surface area of a sphere given its diameter. After a few weeks of practice you will be writing programs which plot graphs or balance the household accounts or play games such as NIM with you. If your home computer has an interface port or ports, you will be able to attach all sorts of



**A Universal S100 prototyping board designed by Vero Electronics for breadboarding microprocessor systems**

external hardware to your system and control it via a program. In most cases you can still use BASIC to talk to your hardware. Home computer BASIC interpreters often have facilities to link you with peripherals, either by direct reference to memory locations using instructions such as PEEK and POKE, or by the ability to call complete machine code subroutines which you can write yourself.

### S100 BUS SYSTEM

Home-computers of the sort typified by PET are certainly the cheapest way into computing. You can learn and enjoy BASIC programming, make your system work for a living, and perhaps even connect it up to some of your own hardware. Unfortunately, there is a snag! After a few months or years, many users will want to squeeze more from their system than it can easily provide. At this point many people will wish that their system was a little more flexible and expandable, and this is where an extra investment at the start could pay dividends.

For a few hundred pounds more, it is possible to buy a home computer based on the S100 bus which will allow the later addition of all sorts of extra hardware and software so that one need never feel cramped. The S100 bus was actually introduced by the very first home-computer, the MITS Altair 8800 which appeared way back in 1975. Since then, many other home-computer designs have been

introduced which use the S100 bus, and many firms (well over 100, world-wide) manufacture circuit boards using the S100 format. The S100 bus was designed around the 8080 microprocessor chip, but since its introduction several other microprocessors, including the Z80, the 6800 and the 6500 have been built into S100 systems. In addition to microprocessor CPU cards, it is also possible to buy a bewildering variety of static and dynamic read/write memory cards, serial and parallel interface cards, floppy disc controller cards, cassette interface cards, logic analyser cards, PROM programmer cards, floating point arithmetic cards, and even speech recogniser and synthesiser cards!

I am sure from the foregoing, you will agree that the S100 bus makes for a versatile home-computer, but what is the bus and why is it so versatile?

## BUS ORGANISED

Many large computers are "bus organised" which means that all circuit cards connect to a comprehensive back-plane where all signal paths are common to each card. This means,

**Fig. 1.1. The S100 Bus connections**

pin 1	+8 Volts	pin 51	+8 Volts
pin 2	+16 Volts	pin 52	-16 Volts
pin 3	XRDY	pin 53	<u>SSW DSB</u>
pin 4	V10	pin 54	EXT CLR
pin 5	V11	pin 55	
pin 6	V12	pin 56	
pin 7	V13	pin 57	
pin 8	V14	pin 58	
pin 9	V15	pin 59	
pin 10	V16	pin 60	
pin 11	V17	pin 61	
pin 12		pin 62	
pin 13		pin 63	
pin 14		pin 64	
pin 15		pin 65	
pin 16		pin 66	
pin 17		pin 67	
pin 18	<u>STATUS DSBL</u>	pin 68	MWRITE
pin 19	C/C DSBL	pin 69	PS
pin 20	UNPROTECT	pin 70	PROTECT
pin 21	<u>SS</u>	pin 71	RUN
pin 22	<u>ADDR DSBL</u>	pin 72	PRDY
pin 23	<u>DO DSBL</u>	pin 73	<u>PINT</u>
pin 24	$\diamond_2$	pin 74	<u>PHOLD</u>
pin 25	$\emptyset_1$	pin 75	PRESET
pin 26	PHLDA	pin 76	PSYNC
pin 27	PWAIT	pin 77	PWR
pin 28	PINTE	pin 78	PDBIN
pin 29	A5	pin 79	A0
pin 30	A4	pin 80	A1
pin 31	A3	pin 81	A2
pin 32	A15	pin 82	A6
pin 33	A12	pin 83	A7
pin 34	A9	pin 84	A8
pin 35	DO1	pin 85	A13
pin 36	DO0	pin 86	A14
pin 37	A10	pin 87	A11
pin 38	DO4	pin 88	DO2
pin 39	DO5	pin 89	DO3
pin 40	DO6	pin 90	DO7
pin 41	D12	pin 91	D14
pin 42	D13	pin 92	D15
pin 43	D17	pin 93	D16
pin 44	SMI	pin 94	D11
pin 45	SOUT	pin 95	D10
pin 46	SINP	pin 96	<u>SINTA</u>
pin 47	SMEMR	pin 97	SWO
pin 48	<u>SHLTA</u>	pin 98	<u>SSTACK</u>
pin 49	<u>CLOCK</u>	pin 99	POC
pin 50	GND	pin 100	GND


for example, that pin 1 or pin N on one edge connector is connected to pin 1 or pin N on every other edge connector on the back-plane. The bus contains address, data, control and power lines and, in general, boards may be plugged into the bus in any slot, regardless of their function. In some ways this method of interconnection is very wasteful. Not all boards need all the facilities available on the bus; some need very few, and yet every board must connect to the bus via a multi-contact (and therefore expensive) edge connector. This inefficiency is more than made up for by the resulting versatility though, and bus organised systems are the norm for large computers.

The S100 bus (Fig. 1.1) is a very successful attempt to bring the large computer bus concept into the home-computer arena, and although there are one or two minor problems with it, its very popularity shows the vision and skill of the original MITS designers. Configured around a one hundred pin edge connector, the S100 bus has a 16 bit address bus, two unidirectional 8 bit data buses, 8 status lines, 5 control lines and a host of miscellaneous functions. Power is supplied to the bus in unregulated form so that individual board regulators can be used to reduce power line noise and distribute heat throughout the case.
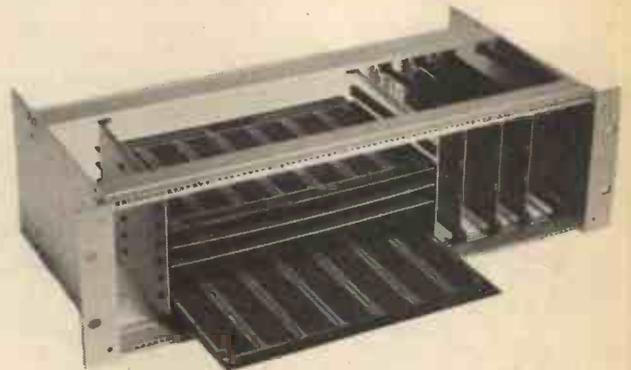
## BUILDING A HOME-COMPUTER

Using the S100 bus concept, you can literally design and build your own home-computer system.

To get started you need (at least) an S100 back-plane, a CPU board, a memory board, and a terminal interface board. The CPU board usually has a ROM or PROM included which contains simple monitor software to allow you to enter, modify, and run machine code programs in hexadecimal, so this minimum system is on a par with the (much cheaper)



**A suitable rack system for use with an S100 backplane. (Vero Electronics)**


evaluation cards. System expansion can begin with a cassette interface board. This provides the ability to save programs and also the ability to load commercial software such as BASIC. This four board system is at about the same level as a PET, but of course it is much more flexible. Unfortunately, when you add in the price of a power supply, a VDU, a cassette recorder and the necessary commercial software, it is also likely to be more expensive. It really depends on how much you make up yourself from kits. S100 memory board kits are particularly common, allowing electronics hobbyists to save some money and enjoy themselves at the same time! Power supplies can also be made up inexpensively by those who know how, unregulated supplies of plus 8, plus 16 and minus 16 volts are required, but beware—the current requirements of a large system can be a surprise!

## WINNER

The basic S100 system then, is only competitive with non-bus home computers under special circumstances, but from this point on, the S100 wins all the way. Want more RAM? Just plug in extra S100 boards up to the 64K maximum. Want to program PROMs? Plug in a Bytesaver board which provides sockets for, and programs, your 2708 PROMs. With a large RAM memory, you can use any software you like, BASIC, PASCAL, ASSEMBLER, all are possible. The cassette interface board probably handles more than one recorder anyway, so you can add the ability to copy tapes and sort files for only the cost of an extra cassette recorder. When it comes to serial or parallel interfaces for your "homemade" peripherals, there is a huge choice of S100 boards to help, and there are even S100 matrix boards so that you can wire up your own "special" interfaces and plug them into your system.

Finally, when you even outgrow all of these facilities, you can take the giant step and add a floppy disc controller and a drive or two to your system, and thus gain the ability to keep hundreds of kilobytes of data available for instant access. With floppy discs in your system you can swap from BASIC to ASSEMBLER in a few seconds, and keep all your programs and data in the form of easily edited, named files. We shall be returning to the subject of floppy discs later, but a final word on "buses" is now appropriate.

While the S100 bus is by far the most popular home computer bus, it is not the only one, and by being a "no compromise" design it is expensive. Another useful bus is championed by SWTPC (South West Technical Products Corporation) in their 6800 based system. The SWTPC bus has become known as the SS50, and it is inherently less expensive to use than the S100. Several firms in the U.S.A. now produce SS50 compatible boards. Other bus systems may be encountered occasionally. Intel have a very popular series of professional computer boards known as the SBC series for example, and these do turn up in the hobby market under the name of SBC-bus boards. No doubt there will be

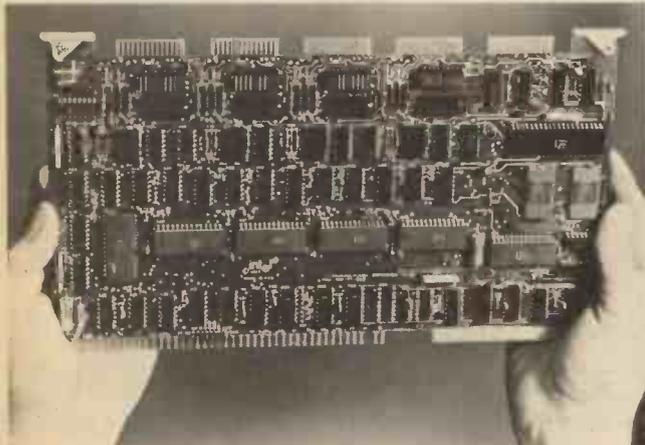

A typical SBC board designed by Intel

many other contenders, for the rewards of becoming a "standard" are high. A European bus standard will be particularly useful, when it finally becomes established.

## HOME-COMPUTER PERIPHERALS

A comprehensive list of possible home computer peripherals would be a very long one, but fortunately there is a short list of useful peripherals which have universal appeal, and a treatment of home-computers would not be complete without a look at these. In order of priority, these are as follows:

- (1) ASCII keyboard
- (2) VDU
- (3) Cassette system
- (4) Printer
- (5) Floppy disc system.

A practical home computer system will normally have at least the first two items on this list.


## KEYBOARDS

An ASCII keyboard is the minimum input device needed for a home computer because high level languages depend on the use of the full ASCII alphabet with punctuation and control characters (Fig. 1.2). ASCII keyboards, in the form of a full set of keys mounted on a printed circuit card, along with an encoder chip and debounce circuitry, are widely available at low cost. These keyboards usually produce a parallel 8 bit code (7 bit ASCII + 1 parity bit), and this data format can be interfaced directly with a parallel

MSD \ LSD	0	1	2	3	4	5	6	7	
	000	001	010	011	100	101	110	111	
0	0000	NUL	DLE	SP	0	@	P	\	p
1	0001	SOH	DC1	!	1	A	Q	a	q
2	0010	STX	DC2	"	2	B	R	b	r
3	0011	ETX	DC3	#	3	C	S	c	s
4	0100	EDT	DC4	\$	4	D	T	d	t
5	0101	ENG	NAK	%	5	E	U	e	u
6	0110	ACK	SYN	&	6	F	V	f	v
7	0111	BEL	ETB	'	7	G	W	g	w
8	1000	BS	CAN	(	8	H	X	h	x
9	1001	HT	EM	)	9	I	Y	i	y
A	1010	LF	SUB	*	:	J	Z	j	z
B	1011	VT	ESC	+	;	K	[	k	{
C	1100	FF	FS	=	<	L	\	l	
D	1101	CR	GS	-	=	M	]	m	}
E	1110	SO	RS	•	>	N	↑	n	~
F	1111	SI	VS	/	?	□	←	o	DEL

Fig. 1.2. Full ASCII alphabet with punctuation and control characters

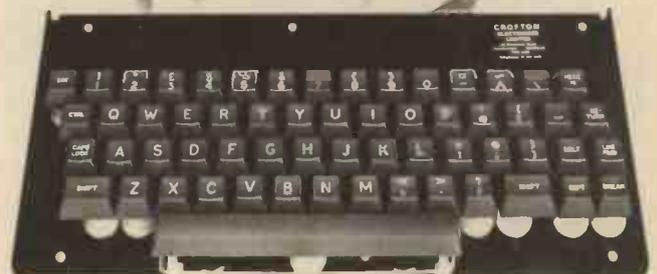microprocessor port if you write your own (simple) driver software. Most home computer operating systems already have driver software for a serial interface, and to make the cheap keyboards interface to this, it will be necessary to add a UART (Universal, Asynchronous, Receiver, Transmitter)



Keyboard layout

chip to the basic keyboard encoder. Home computer serial interface ports are typically of the RS232/V24 type, an international standard based on a 25 way D type connector which represents a logic one as -12 volts, and a logic zero as +12 volts. S100 serial interface cards can be programmed to operate at a range of speeds from about 10 characters per second, up to about 960 characters per second, to suit the peripheral to which they are to be connected. Fig. 1.3 shows the range of standard serial

interface speeds, along with their associated "baud rates".

For a keyboard alone, there is no point in using anything faster than 110 baud, because you can't type any faster, but

BAUD SPEED	CHARACTERS/ SECOND
110	10
300	30
600	60
1,200	120
2,400	240
4,800	480
9,600	960
19,200	1,920

**Fig. 1.3. Standard serial interface speeds and their associated "baud rates"**

keyboards are nearly always used with a printer or a VDU, and in the case of the VDU anyway, the higher baud rates can be useful.

### VDU SYSTEMS

VDU systems are the cheapest way to display home computer generated outputs, and it is possible to buy, for around £500 or less, a complete "glass-teletype" which has a keyboard and a display screen. "Glass teletypes" such as the Lyme 4000 series, are ideal for use with home computers of the S100 type. They can operate over a wide range of baud speeds, and are easily hooked up to any RS232/V24 serial port to provide full two-way communication facilities. An even cheaper alternative is to



**A Lyme 4000 VDU system**

use a simple ASCII keyboard for input, and use a standard TV set or monitor for output. In this case the home computer itself has to provide the screen refresh memory and character generator functions and, of course, there are S100 boards which can do just that. Using a TV as a VDU is also a popular ploy for the cheaper home-computer designs because it saves the cost of a special display monitor and does away with the need for UARTS and serial interface cards. Some designs have been published which describe the production of television based VDUs for less than £100, such as the PE VDU, but in general these have been parallel-load, non-keyboard designs which are only to be recommended to those who can produce their own driver software and interface arrangements.

### CASSETTE SYSTEMS

While you run your home computer programs you keep them in RAM, but when you hit the OFF switch, they're gone for good unless you can save them on some permanent storage medium. By changing your RAM data into serial form, and sending out one audio tone for a logic "zero" and another for a logic "one", you can store all those precious data and programs on an audio cassette recorder, and load them back into RAM whenever you choose. There is no need to modify the cassette recorder, and the interface circuitry is fairly simple, so simple in fact that many cassette recording standards have appeared which are unfortunately not compatible. The closest thing yet to a universal cassette recording protocol is the 300 baud "Kansas City" or C.U.T.S. standard which uses 2.4kHz for a logic "one" and 1.2kHz for a logic "zero". This has proved to be usable with a wide range of cassette recorders and has shown itself to be very reliable. By no means everyone uses this standard, however, and it is unwise to buy software in cassette form without making sure it is in a format compatible with one's own system!

The use of two cassette recorders is a great improvement to any system because it allows cassette copying and file sorting. It is, for example, possible to add a second (external) cassette unit to the PET, and most S100 cassette interface cards can control more than one as supplied. If you build up your own S100 home-computer, a cassette interface will allow you to buy and use BASIC interpreters, assemblers, and other software from the wide range now advertised in cassette form.

### PRINTERS

Although I would recommend the use of a VDU rather than a bulky, noisy and unreliable teletypewriter for use with a home computer, there are always occasions when the ability to print-out a program or graph is very desirable. You can of course use a teletypewriter to provide this function, but a neater solution is to use a small stand-alone printer of the type which is now becoming available at low cost, and to only turn it on when you really need a printed copy. These



**The Tandy TRS 80 printer uses 4in wide electrostatic paper** small new printers can be purchased with either a parallel interface (which is cheaper), or with a standard RS232/V24 serial interface (which will plug straight in to most systems). The printers use a variety of print-head designs, but to me the type which use electro-sensitive aluminiumised paper shows the most promise. Often containing a microprocessor of their own, these useful peripherals can operate much faster than a traditional teletype and some can also be used as a plotter for graphics output. The PET also has its own special add-on printer, known as the 2020, which plugs straight in to the parallel port provided.

**Next month: Software.**

# PE MICROPRINTER

## PART 2

MARK SIMON



**P**ART 1 covered the principle of electrosensitive printing, character formation, and gave the circuit diagram with a description of how the interface works.

In this part the driver circuits and power supply are described, along with the software necessary to run the printer with a microcomputer system.

### ELECTRODE DRIVER

To melt the aluminium coating and produce a dot on the paper will, as you can imagine, take a fair amount of current, albeit for a short space of time. The driver circuit shown in Fig. 2.1 amplifies the output from the character generator chip sufficiently to achieve this. It operates in the following way.

When an output from the character generator chip pulses active low the BC212 level changing transistor is turned on, supplying base drive current to the BD189.

When the BD189 turns on it throws 24V across the electrode which burns the dot on the paper. *Obviously not a circuit to leave with its input stuck low!*

### THE MOTOR DRIVER

The motor driver has a similar "front end" (Fig. 2.2). The motor flip-flop  $\bar{Q}$  going active low, turns on the BC212. This causes a positive voltage to be switched to the bases of the complementary power transistors. The 2N3053 turns on, supplying power to the motor, which will hopefully run.

When the motor flip-flop  $\bar{Q}$  output returns high and the BC212 is turned off, the power transistor bases will revert to a large negative voltage. The 2N3053 will turn off and the motor will develop a large back e.m.f. This will turn on the 2N4037 which dissipates the stored energy.

### POWER SUPPLIES

The voltages required for the system are, +5V, -12V and -24V. The +5 volts is required for the interface logic. As this is all MOS, the current requirement is low (typically 70mA) and so the host microcomputer system should have the capacity to supply this. The printer motor and electrodes work off a -24V rail and require quite high values of current for short durations of time. This seems to average out at around 130mA during printing. A good transformer preferably screened, of 5VA minimum and an output of 25V or greater will be required (see Fig. 2.3). The -12V supply is required solely to produce a bias voltage (V<sub>gg</sub>) to the character generator chip. The tolerance here is not particularly tight, so a Zener diode is used to pick the requisite voltage from the -24V rail. The actual circuit was built up on Veroboard and mounted on the transformer (Fig. 2.4).

To avoid component damage the supplies must be switched in the following sequence:

**on**—First +5V, and -12V, then -24V

**off**—First -24V, and then -12V and +5V

This action can be realised by a 4-pole 3-way lever switch (PO 1000 type), or rotary wafer switch, the wiring of which is shown in Fig. 2.5.

### CIRCUIT LAYOUT

With relatively large current pulses and motor starter currents so prevalent in this circuit, protecting noise prone logic circuitry is very important. Circuit layout is obviously crucial (see Figs. 2.5 and 2.6).

The first requirement is that the larger current carrying elements of the circuit, be grouped together and kept away from the more noise prone logic devices. Inputs and outputs must be kept separate. On the layout diagram the pickup coil, reed, and other inputs enter on one side of the circuit board. Whilst the motor driver output and electrode driver outputs leave at the other end of the board. The separation of these parts of the circuit even extends to supplies. The 5V line is brought in, via capacitors, to the logic at one end of the board. The 5V supply for the drivers, comes via another wire and enters the circuit at the driver end of the board. The 0V line is also separated; in fact a low value resistor, R (10 Ohms), is inserted between the logic and driver 0V lines to enhance noise immunity.

The final anti-noise measure is to place 100n capacitors across the 0V and 5V lines about the circuit. These are shown on Fig. 2.6, which gives pin-out information for all the integrated circuits and transistors used.

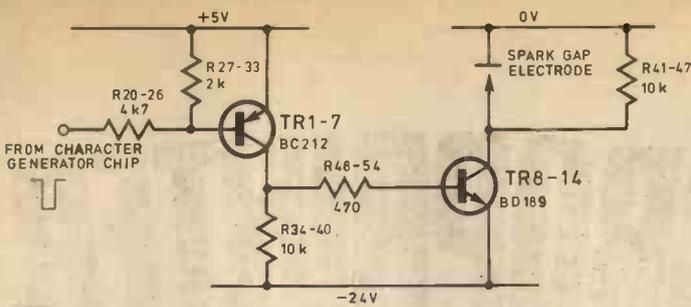


Fig. 2.1. Print electrode/head drivers

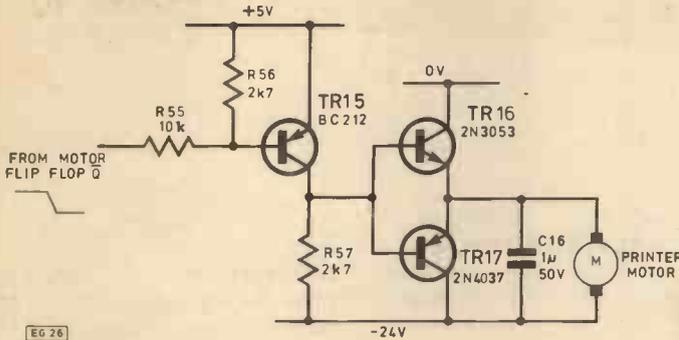


Fig. 2.2. Motor driver (-24 volt motor)

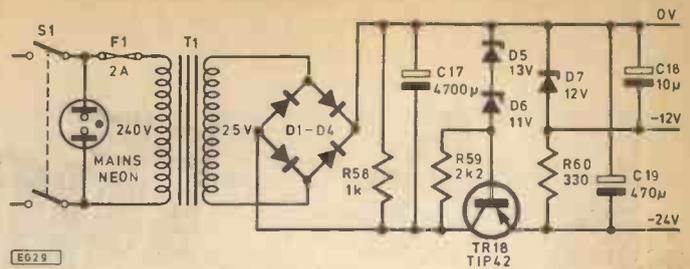


Fig. 2.3. Power supply circuit, -12V and -24V. Mains earth should connect to the transformer screen and the metal case

Fig. 2.4. Power supply construction. A strip-board can be mounted on top of the transformer using standoff pillars, and the capacitor strapped to the side

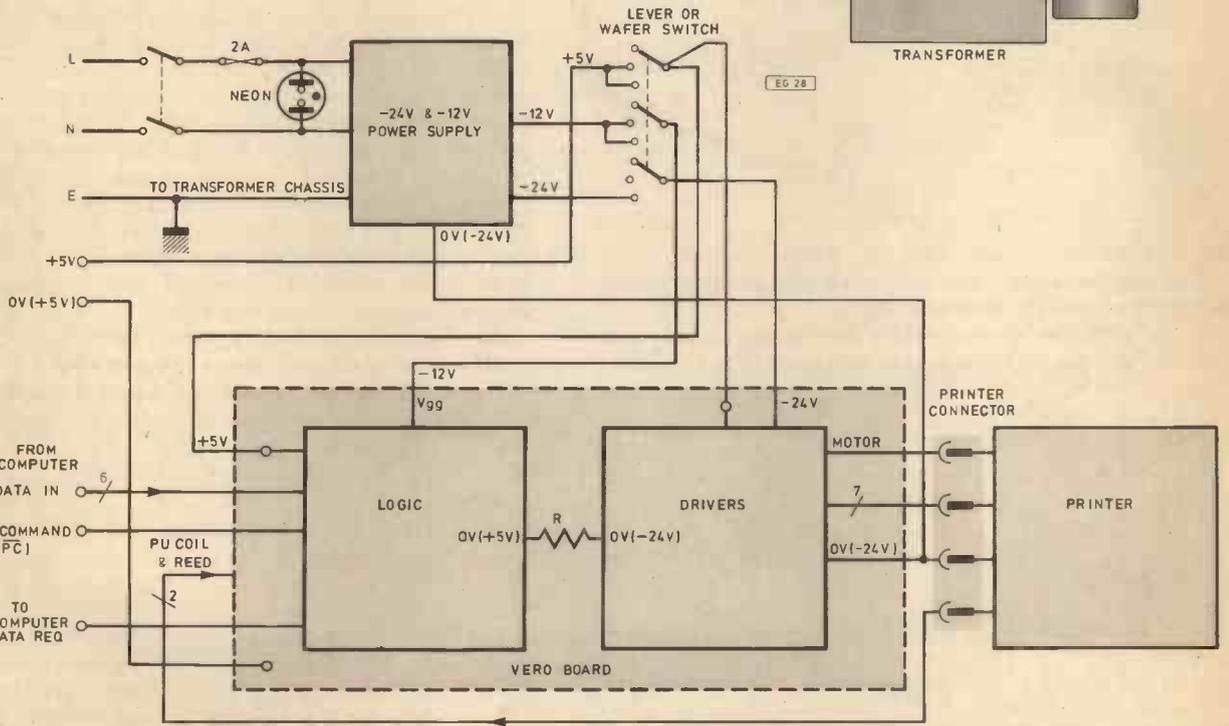
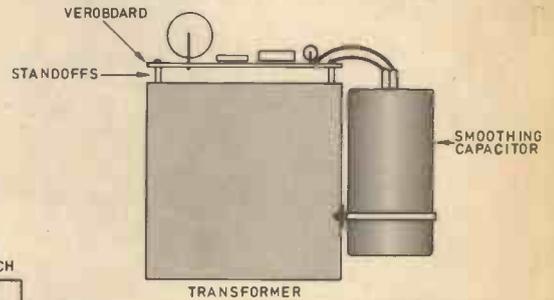


Fig. 2.5. System wiring. The supply line to which the 0V relates is shown in brackets. The two 0V systems are linked by a low value resistor

## BOXING

The main box used to house the prototype was chosen primarily because it happened to be lying about at the time of building! The circuit board was fixed to one side leaving the majority of the space free for the power supply and the cable runs. (Fig. 2.7 shows dimensions and internal layout.) The printer, its connector and its paper holder were mounted on top of the box (see Fig. 2.8).

During development lengthy printing runs were achieved

using no paper holder at all. Long lengths of printing paper were simply pulled off the roll and allowed to run through the printer. Although this worked well, it was thought that a more business-like approach was needed. Therefore the paper roll was placed on a mandrel with grooves notched at each end (Fig. 2.9). This assembly then sits in the roll holder which is screwed to the top of the box behind the printer. The paper roll holder was made from 16 gauge brass strip.



## CONSTRUCTORS NOTE

The Matsushita electrosensitive printer is available from **Datac Ltd., Tudor Road, Broadheath, Altrincham, Cheshire, WA14 5TN. (Telephone 061-941 2361).** Although type 245/L/40 is specified, type 245/L/20 may be supplied, preset for 40 columns.

An alternative supplier for this and most other components is **Technomatic Ltd.**

It was not mentioned in Part 1 that construction requires the use of a 15-way edge connector to link the Matsushita printer to the main control unit. This is Amphenol type 143-015-01, available from Celdis for £2.74 inclusive of handling charge. **Celdis Ltd, 37/39 Loverock Road, Reading, Berks, RG3 1ED.**

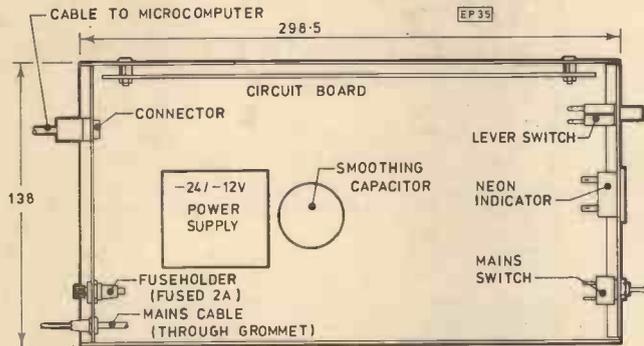


Fig. 2.7. Internal layout

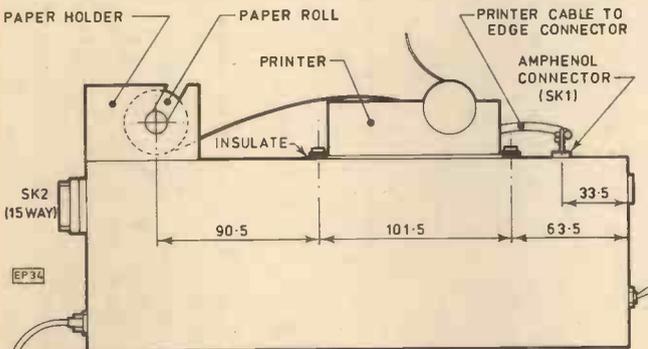


Fig. 2.8. Printer mounting. Fig. 1.1. last month showed the paper at  $-24V$  and the electrode energised at  $0V$ . The reverse is of course true, otherwise the printer casing would need to be insulated from the control box cabinet. However, some mechanical insulation from vibration is still advisable, and this can be done by sleeving the printer mounting lugs with rubber grommets

## SOFTWARE

The purpose of the software is to present data to the interface for conversion to printing pulses, whilst monitoring the status of the printer. The DUMP routine will also allow the printing of memory contents along with address information.

Although the system only uses six of the seven bits used in the Standard ASCII code, it will print all capital letters, numbers and symbols from the character set.

The only control characters required are Carriage Return, and End of Text, both of which are recognised by the software. For Carriage Return the ASCII code ODH is retained. For the End of Text character a non-standard code is used, FFH. In fact the software will terminate printing if it encounters any character byte with bit 7 set. Therefore it is important to remember that if printing text, the byte after the

## PRINTER TO MAIN UNIT CONNECTIONS

Pin No.	Signal
A	Reed
B	Pick-up coil
C	$0V$ for P/U coil & Reed
D	Motor +
E	Motor -
F	Head & Pinch Roller Common
H	N.C.
J	1st Dot
K	2nd Dot
L	3rd Dot
M	4th Dot
N	5th Dot
P	6th Dot
R	7th Dot
S	N.C.

## EXTERNAL CONNECTOR TO $\mu$ COMPUTER

Pin No.	Signal
A	DO
B	D1
C	D2
D	D3
E	D4
F	D5
H	Print command ( $\overline{PC}$ )
J	Data Request
W & X	+5V supply
M	$0V$

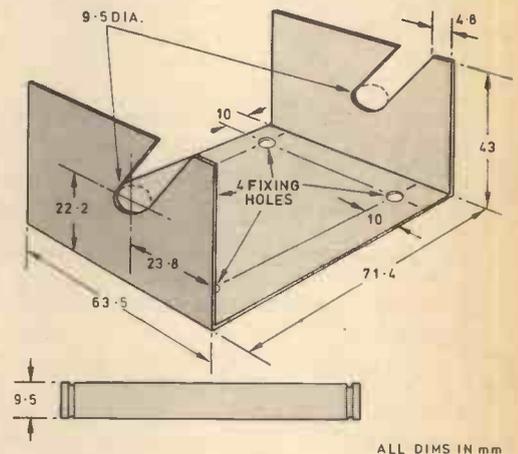


Fig. 2.9. Paper roll holder. The holder can be made of alloy sheeting. In the prototype the bobbin was made from brass rod, but a simpler solution would be to use wooden dowel, and insert screws in each end to key into the roller slots.

last character should contain FFH.

The software for the prototype is written in Z80 assembler code and the peripheral chip used is the Z80 PIO. Conversion to other microprocessor instruction sets and peripheral chips should not present too much difficulty, especially as fairly detailed flow charts are included in the article.

## INPUT OUTPUT REQUIREMENTS

The I/O requirements of the system are as follows:

**5 outputs**, latched, for DO-D5

**1 output**, latched, for PRINT COMMAND ( $\overline{PC}$ )

**1 input**, unlatched, for DATA REQUEST (DATA REQ)

In the prototype system the PIO was programmed to operate in Mode 3, the bit mode. Bit 0 to bit 6 were programmed as outputs and Bit 7 was programmed as an input (see Fig. 2.10). It may be cheaper in some cases to use two separate ports, one for input and one for output. A latched I/O device such as the Intel 8212 could be used for the outputs, and a separate simple tristate buffer part could be used for the DATA REQ input. This would require only slight alteration to the software.

### SYSTEM SOFTWARE

The majority of the software is involved with the DUMP routine. The actual PRINT routine itself is relatively small. We shall look at this routine first and then see how it fits into the DUMP programme.

### PRINT

The PRINT routine's function is to set the printer in motion and to sequentially present data to the interface at the required time. It also detects the carriage return and end of text codes and actually performs these control functions.

There are only 2 rules for its use:

- (a) The Start address of the text buffer must be in the HL register pair on entry.
- (b) That the end of text code (FFH) must be in the first memory location, after the text to be printed.

For example, say we want to print the word "HELLO", the ASCII code of which starts at memory location 2000H. Before entry to the print routine HL must be set to 2000H, and the text buffer should appear as in Fig. 2.12.

The flowchart for the PRINT routine is as Fig. 2.11 and its operation is as follows:

The peripheral chip (if used) is programmed. A down-counter (the character per line counter) is preset. This enables the processor to determine when it has filled the line.

The system activates the printer by generating a "low" to PC. It waits for DATA REQ to go active then moves the first character byte to the accumulator. Before outputting the character, bit 7 is tested. If set it is interpreted as an end of text character. If not set, it is then compared with 0DH to check if it is a carriage return. If not, then the routine decides if it is a valid character and outputs it for printing. The character per line counter is decremented and checked for 0 at this time to see if a line has been filled. After printing, the text buffer pointer (HL), is incremented to point to the next character and the process is repeated.

If a carriage return code is detected the routine calls the subroutine SPACES, which repeatedly outputs the SPACE code to the interface until the end of the current line. (When the character per line counter = 0.) A delay routine is then called to give the print-head time to return to the beginning of the next line, the routine then proceeds as before.

When the end of text character is detected the subroutine SPACES is again called, but after its completion a return code is loaded into the accumulator and PRINT is exited.

The subroutines used by PRINT are detailed in Figs. 2.13 and 2.14.

The printer system will run with the PRINT routine alone, for printing text and program listings. All the rest of the system software is used for the memory DUMP function, PRINT is called by the DUMP program as a subroutine. PRINT and its subroutines appear towards the end of the system software listing. It actually starts on line 143.

Fig. 2.10. PIO allocation

	7	6	5	4	3	2	1	0
I/P DATA REQ	O/P PC	O/P D5	O/P D4	O/P D3	O/P D2	O/P D1	O/P D0	


### DUMP

As previously mentioned the DUMP routine enables the user to print out the contents of areas of memory.

Firstly the hexadecimal memory address is printed, then the contents of that location and the following seven locations are printed, also in hexadecimal. The next line begins with the start address +8, followed by the contents of the next eight locations, and so on until the specified finish address is reached. Carriage return and end of text control characters are inserted automatically by the software.

The organisation of the software is as Fig. 2.15. DUMP is the controlling routine, which calls the conversion routine, the compare routine and the print line routine. This in turn calls PRINT and its associated routines, which have already been described.


Fig. 2.11. PRINT flowchart

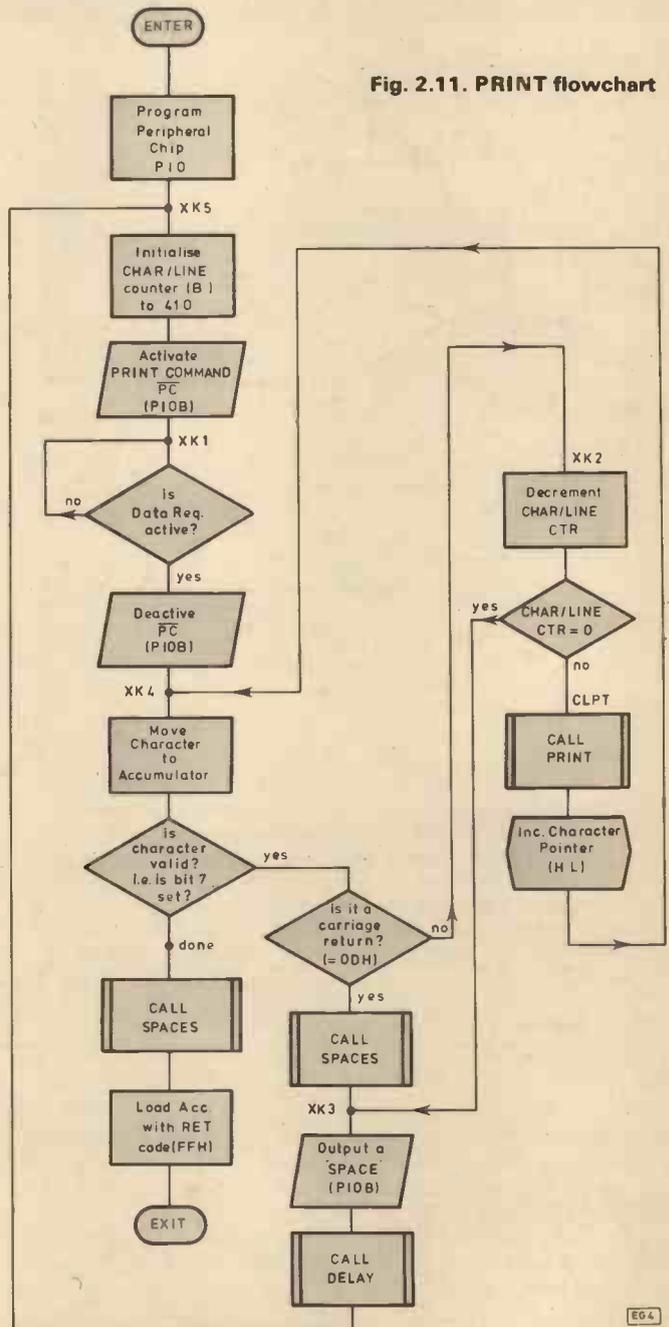



	location	2000	2001	2002	2003	2004	2005
HEX contents		08	05	0A	0A	0F	FF
		H	E	L	L	O	EOT

Fig. 2.12. Text buffer example

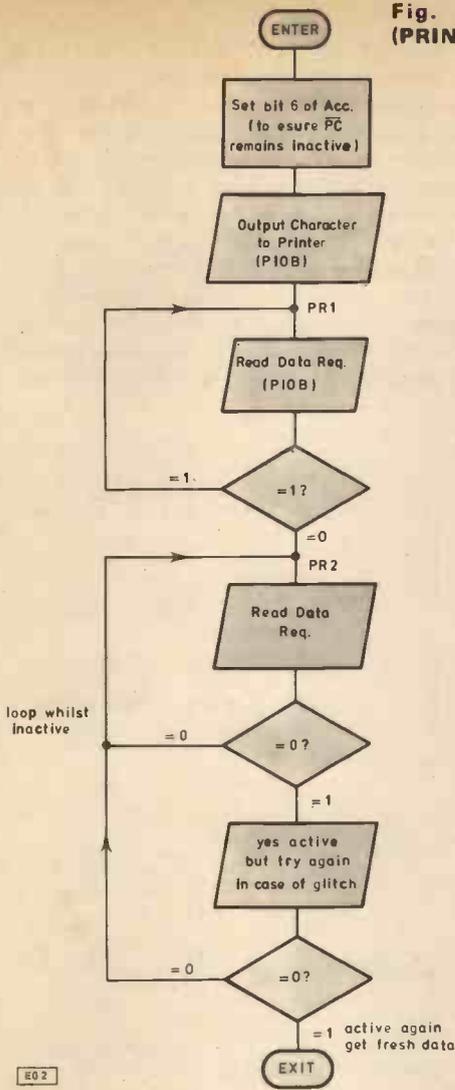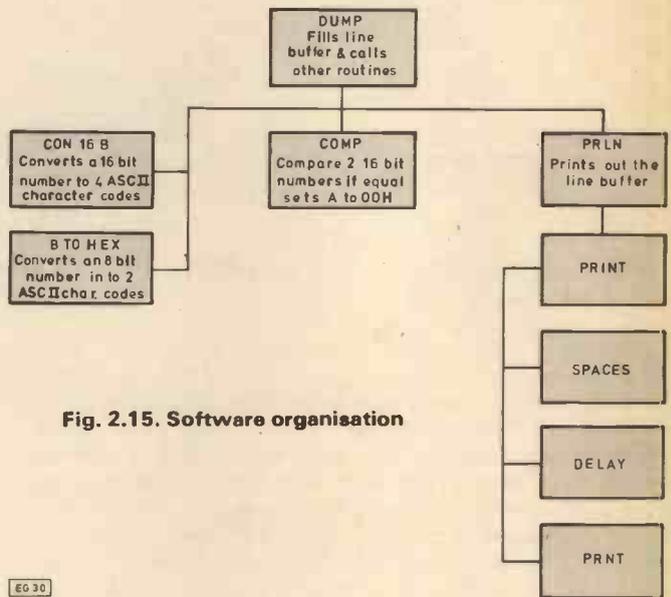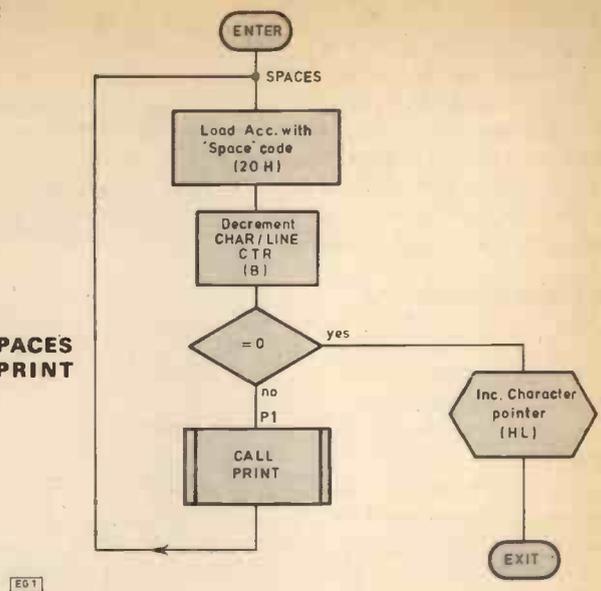**Fig. 2.13. PRNT flowchart (PRINT subroutine)**

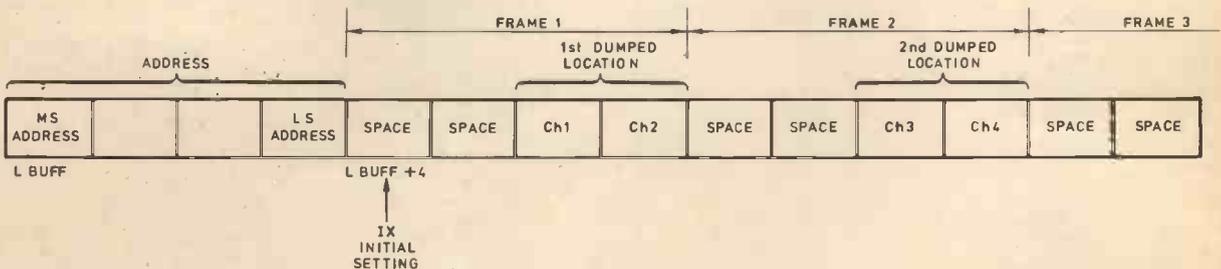


**Fig. 2.14. SPACES flowchart (PRINT subroutine)**



**Fig. 2.15. Software organisation**

**Fig. 2.16. Line buffer organisation**



**OPERATION**

DUMP operates by creating a line buffer in RAM, where it inserts the address, the spaces and the contents of the eight locations (see Fig. 2.16).

It then calls the PRINT routine to print that line. Each location and its spaces are referred to as a "frame" of four bytes. The line buffer consists of four address bytes and eight frames. It is filled in the following way:

The Start address is loaded into HL to serve as an indirect pointer (see Fig. 2.17). It is also loaded into DE where the subroutine CON16B converts it to hexadecimal and then to ASCII. The resulting four ASCII characters are placed at the beginning of the line buffer by CON16B. The line buffer pointer (IX) and the frame counter (B) are initialised. IX and C are used to place the first two spaces into the line buffer (see Fig. 2.16).

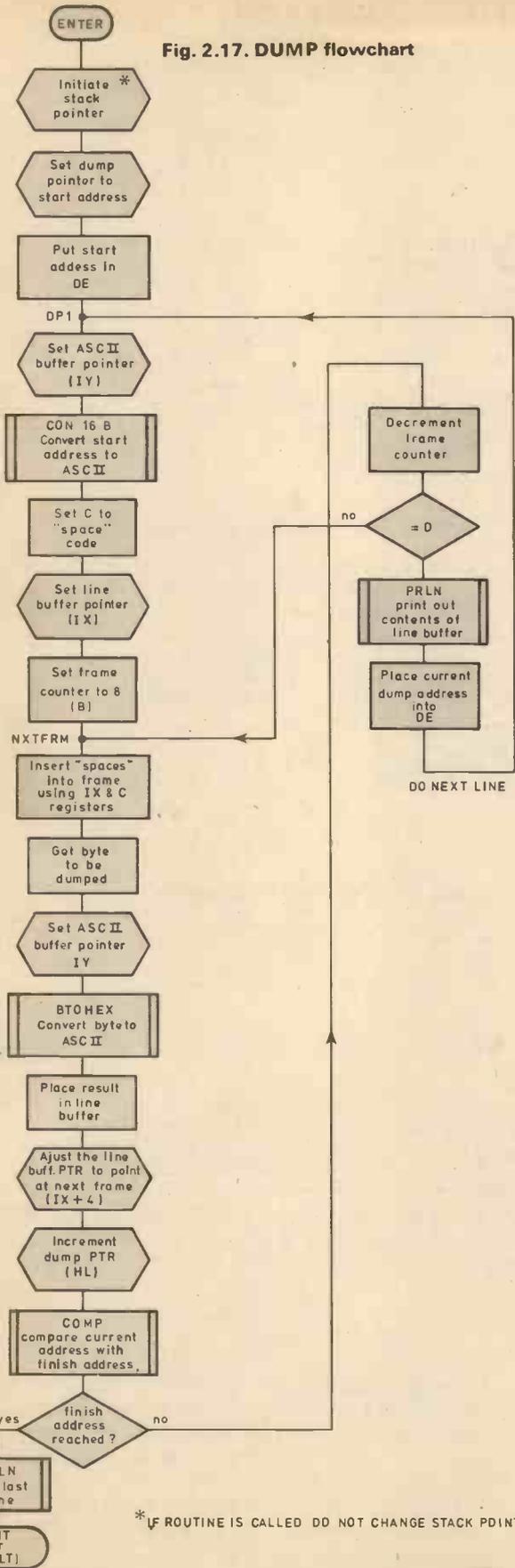


Fig. 2.17. DUMP flowchart

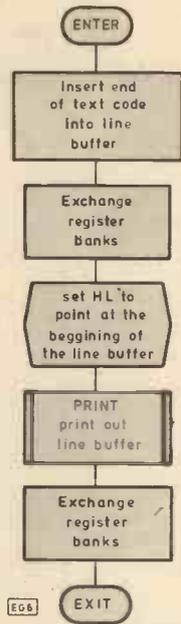


Fig. 2.18. PRLN flowchart

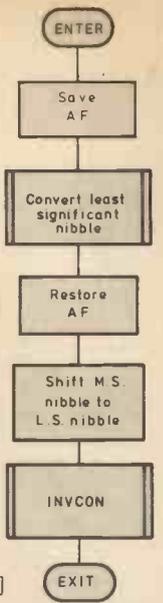


Fig. 2.19. BROHEX flowchart

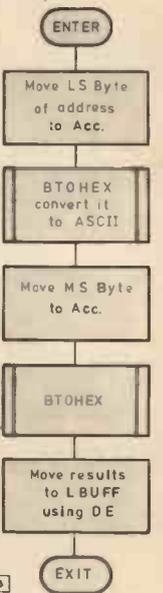


Fig. 2.20. CON16B flowchart

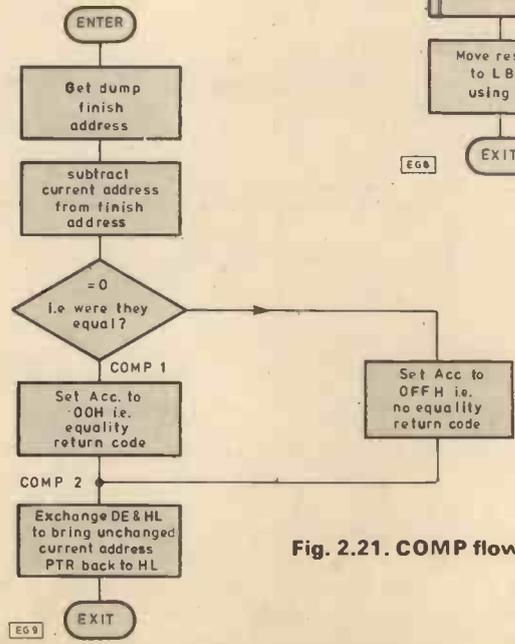


Fig. 2.21. COMP flowchart

# SOFTWARE LISTING FOR Z80 WORKING

LOC	OBJ CODE	STMT	SOURCE	DX2 LISTING STATEMENT	PAGE. 0001	LOC	OBJ CODE	STMT	SOURCE	DX2 LISTING STATEMENT
		0001		; DUMP IS THE CONTROL ROUTINE FOR A MEMORY				0110		;
		0002		; DUMP TO A MATSUSHITA PRINTER.				0111		;
		0003		;				0112		; COMP; THIS ROUTINE LOOKS FOR EQUALITY BETWEEN
1750		0004	DPG	1750H ;				0113		; THE DUMP POINTER DPTR; AND THE END OF DUMP
1750	310035	0005	LD	SP,3500H ;+++ DELETE IF CALLED				0114		; ADDRESS DPFIN.
1753	2A2821	0006	LD	HL,(DPST) ;SET DUMP PTR				0115		;
1756	ED582821	0007	LD	DE,(DPST) ;READY FOR CONVERSION				0116		;
175A	FD212F21	0008	DP1:	LD IY,ASCIB+3 ;SET ASCIB PTR				0117	COMP:	;
175E	CDC717	0009	CALL	CON16B ;DPST TO ASCII		17E0	ED582A21	0119	LD	DE,(DPFIN) ;GET FINISH ADDRESS
		0010		;		17E4	ER	0119	EX	DE,HL ;
		0011		;		17E5	AF	0120	XOR	A ;CLEAR CARRY
1761	0E20	0012	LD	C,20H ;ASCII 'SPACE' CODE		17E6	ED52	0121	SBC	HL,DE ;DPFIN-DPTR
1763	DD210421	0013	LD	IX,LBUFF+4 ;SET LBUFF PTR		17E8	2804	0122	JR	Z,COMP1-1 ;JUMP IF DPFIN=DPTR
1767	0608	0014	LD	B,8 ;SET FRAME CTR		17EA	3EFF	0123	LD	A,OFFH ;NO EQUALITY RET CODE
1769	DD7100	0015	NXTFRM:	LD (IX+0),C ;INSERT SPACES INTO		17EC	1801	0124	JR	COMP2-1 ;
176C	DD7101	0016	LD	(IX+1),C ; LINE BUFFER		17EE	AF	0125	COMP1:	XOR
		0017		;		17EF	EB	0126	COMP2:	EX
		0018		;		17F0	C9	0127	RET	DE,HL ;
		0019	LD	A,(HL) ;GET DUMP BYTE				0128		;
1770	FD212D21	0020	LD	IY,ASCIB+1 ;SET ASCIB PTR				0129		;
1774	CDAA17	0021	CALL	BTOMEX ;CONVERT TO ASCII				0130		;
1777	ED582C21	0022	LD	DE,(ASCIB) ;RESULT TO DE				0131	OE	;
177B	DD7302	0023	LD	(IX+2),E ;& THEN TO				0132		; PRINT IS THE ROUTINE THAT ACTUALLY CONTROLS
177E	DD7203	0024	LD	(IX+3),D ;LBUFF				0133		; THE MATSUSHITA PRINTER.
		0025		;				0134		; THE I/O HARDWARE USED IS THE Z80 PROGRAMMABLE
		0026		; THE ASCII CONVERSIONS OF THE DUMP BYTE ARE				0135		; INTERFACE CIRCUIT, THE P.I.D., THE FIRST SECTION
		0027		; NOW IN THE LINE BUFFER.				0136		; OF CODE DEALS WITH PROGRAMMING THIS DEVICE.
		0028		;				0137		;
1781	110400	0029	LD	DE,4 ;ADJUST LBUFF PTR TO				0138		;
1784	DD19	0030	ADD	IX,DE ;POINT AT NEXT FRAME.				0139		;
1786	23	0031	INC	HL ;INC DPTR.				0140		; PROG PID. MODE 3, B0-B5=DATA 0/PS,B6=PRINT COMM
1787	CDE017	0032	CALL	COMP ;COMPARE WITH DPFIN				0141		; B7=DATA REQUEST I/P.
178A	A7	0033	AND	A ;TEST RET CODE				0142		;
178E	2809	0034	JR	Z,FINISH-1 ;IF=0, JUMP OUT		17F1	3EFF	0143	PRINT:	LD
178D	10DA	0035	DJNZ	NXTFRM-1 ;DO NEXT FRAME		17F3	D303	0144	OUT	(PIOB),A ;
		0036		;		17F5	3E80	0145	LD	A,80H ;I/O CONTROL
		0037		;		17F7	D303	0146	OUT	(PIOB),A ;
		0038		; PRINT OUT THE CONTENTS OF THE LINE BUFFER.		17F9	3E03	0147	LD	A,03H ;DISABLE PID INTERRUPTS
		0039		;		17FB	D303	0148	OUT	(PIOB),A ;
		0040		;		17FD	3EE0	0149	LD	A,0E0H ;INIT SE 0/PS, PC=1
178F	CD9A17	0041	CALL	PRLN ;		17FF	D301	0151	OUT	(PIOB),A ;DO-D5 = 20H = SPACE.
		0042		;				0152		;
1792	E5	0043	PUSH	HL ;COPY HL TO DE		1801	0629	0153	KK5:	LD
1793	D1	0044	POP	DE ;		1803	3EA0	0154	LD	A,0A0H ;ACTIVATE P.C.
1794	18C4	0045	JR	DP1-1 ;DO NEXT LINE		1805	D301	0155	OUT	(PIOB),A ;
		0046		;		1807	D801	0156	IN	A,(PIOB) ;IS DATA REQ ACTIVE?
		0047		;		1809	C87F	0157	BIT	7,A ;
1796	CD9A17	0049	FINISH:	CALL PRLN ;		180B	28FA	0158	JR	Z,KK1-1 ;NO, JUMP BACK
		0050		;		180D	C87F	0159	SET	6,A ;YES, DEACTIVATE P.C.
1799	76	0051	HALT	+++PUT RET IF CALLED		180F	D301	0160	OUT	(PIOB),A ;
		0052		;				0161		;
		0053		;				0162		;
		0054		;		1811	7E	0163	KK4:	LD
179A	3EFF	0055	PRLN:	LD A,OFFH ;INSERT FINISH CODE		1812	C87F	0164	BIT	7,A ;VALID CHAR?
179C	DD7700	0056	LD	(IX+0),A ;		1814	201A	0165	JP	NZ,DONE-1 ;NO, MSB SET JP OUT
		0057		;		1816	FE0D	0166	CF	0DH ;IS CHAR CR?
179F	08	0058	EX	AF,AF' ;		1818	2005	0167	JR	NZ,KK2-1 ;JP IF NOT CR
17A0	D9	0059	EXX	;		181A	CD3618	0168	CALL	SPACES ;IF CR, FILL UP LINE
17A1	210021	0060	LD	HL,LBUFF ;SET PTR		181D	1802	0169	JR	KK3-1 ;
17A4	CDF117	0061	CALL	PRINT ;PRINT OUT LBUFF		181F	1009	0170	KK2:	DJNZ
17A7	D9	0062	EXX	;		1821	3EE0	0171	KK3:	LD
17A8	08	0063	EX	AF,AF' ;		1823	D301	0172	OUT	(PIOB),A ;
17A9	C9	0064	RET	;				0173		;
		0065		;		1825	CD5B18	0174	CALL	DELAY ;IF 0 DELAY
		0066		;		1828	18D7	0175	JR	KK5-1 ;DO NEXT LINE
		0067		; BTOMEX CONVERTS THE CONTENTS OF A INTO 2 ASCII				0176		;
		0068		; CHARACTERS.				0177		;
		0069		;		182A	CD4418	0178	CLPT:	CALL
17AA	F5	0070	BTOMEX:	PUSH AF ;SAVE AF		182D	23	0179	INC	HL ;
17AB	CDB717	0072	CALL	INVC0N ;CONVERT LS4 BITS		182E	18E1	0180	JR	KK4-1 ;GET NEXT CHAR
17AE	F1	0073	POP	AF ;RESTORE				0181		;
17AF	1F	0074	RRA	;				0182		;
17B0	1F	0075	RRA	;		1830	CD3618	0183	DONE:	CALL
17B1	1F	0076	RRA	;		1833	3EFF	0184	LD	A,OFFH ;FILL UP LINE
17B2	1F	0077	RRA	;		1835	C9	0185	RET	;
17B3	CDB717	0078	CALL	INVC0N ;MS4BITS TO LS4BITS				0186		;
17B6	C9	0079	RET	;				0187		;
		0080		;		1836	3E20	0188	SPACES:	LD
		0081		;		1838	1005	0189	DJNZ	P1-1 ;
17B7	E60F	0082	INVC0N:	AND 0FH ;MASK OUT MS 4BITS		183A	23	0190	INC	HL ;INC TEXT PTR
17B9	FE0A	0083	CP	10 ;0 - 9 ?		183E	C9	0192	RET	;
17BB	3802	0084	JR	C,INVI-1 ;IF YES JUMP		183F	CD4418	0193	P1:	CALL
17BD	C607	0085	ADD	A,7 ;ADJUST FOR A - F		1842	18F2	0194	JR	SPACES-1 ;
17BF	C630	0086	ADD	A,30H ;CON TO ASCII				0195		;
17C1	FD7700	0087	LD	(IX+0),A ;STORE IN ASCIBUFF				0196		;
17C4	FD2B	0088	DEC	IY ;ADJUST POINTER				0197	PRINT:	SET
17C6	C9	0089	RET	;		1844	C87F	0197	PRINT:	SET
		0090	OE	;		1846	D301	0198	OUT	(PIOB),A ;ENSURE P.C. STAYS=1
		0091		;		1848	D801	0199	PR1:	IN
		0092		;		184A	C87F	0200	BIT	7,A ;
		0093		; SUB ROUTINES		184C	20FA	0201	JR	NZ,PR1-1 ;IF DATA REQ=1 LOOP
		0094		;		184E	D801	0202	PR2:	IN
		0095		;		1850	C87F	0203	BIT	7,A ;
		0096		; CON16B CONVERTS THE NUMBER IN DE TO 4 ASCII		1852	28FA	0204	JR	Z,PR2-1 ;LOOP WHILST INACTIVE
		0097		; CHARACTERS.		1854	D801	0205	IN	A,(PIOB) ;ACTIVE BUT RECHECK
		0098		;		1856	C87F	0206	BIT	7,A ;IN CASE OF GLITCH
		0099		;		1858	28FA	0207	JR	Z,PR2-1 ;IF GLITCH JP BACK
		0099	CON16B:	LD A,E ;LSBYTE TO A		185A	C9	0208	RET	;
		0100	LD	A,E ;LSBYTE TO A				0209		;
17C7	7B	0101	LD	A,E ;LSBYTE TO A				0210		;
17C8	CDAA17	0102	CALL	BTOMEX ;CONVERT		185B	1640	0211	DELAY:	LD
17CB	7A	0103	LD	A,D ;MSBYTE TO A		185D	1E7D	0212	LP2:	LD
17CC	CDAA17	0104	CALL	BTOMEX ;CONVERT		185F	1D	0213	LP1:	DEC
		0105	LD	DE,(ASCIB) ;MOVE RESULTS TO LBUFF		1860	20FD	0214	JR	NZ,LP1-1 ;
17CD	ED582C21	0106	LD	(LBUFF),DE ;		1862	15	0215	DEC	D ;
17D7	ED582E21	0107	LD	DE,(ASCIB+2) ;		1863	20F8	0216	JR	NZ,LP2-1 ;
17DB	ED582E21	0108	LD	(LBUFF+2),DE ;		1865	C9	0217	RET	;
17DF	C9	0109	RET	;				0218		;
				;				0219		;

CONTINUED

```

                                DX2 LISTING
LOC  OBJ CODE  STMT SOURCE STATEMENT

                                0220 ; RESEVED RAM LOCATIONS
2100 0221 LBUFF: DEFS 210AH
2100 0222 DPST:  DEFS 40 ;LINE BUFFER
2120 0223 DPST:  DEFS 2 ;DUMP START ADDRESS
212A 0224 DPFIN: DEFS 2 ;DUMP FINISH ADDRESS
212C 0225 ASCIB: DEFS 4 ;CONVERSION BUFFER
0226 ;
0227 PIOB: EQU 01H ;PORT ADDRESS
0228 PIOBC: EQU PIOB+2 ;CONTROL ADDRESS
0229 ;
0230 ;
0231 END



```

```

CROSS REFERENCE                DX2 LISTING
SYMBOL  VAL  DEFN  REFS

ASCIB  212C 0225 0008 0020 0022 0105 0107
BTOHEX 17AA 0070 0021 0101 0103
CLPT   182A 0178 0170
COMP   17E0 0117 0032
COMP1  17EE 0125 0122
COMP2  17EF 0126 0124
CON16B 17C7 0099 0009
DELAY  105B 0211 0174 0191
DONE   1830 0183 0163
DPI    175A 0008 0045
DPFIN  212A 0224 0118
DPST   2120 0223 0006 0007
FINISH 1796 0049 0034
INVI   178F 0086 0084
INVC0N 1787 0082 0072 0073
LBUFF  2100 0222 0013 0060 0106 0108
LP1    185F 0213 0214
LP2    185D 0212 0216
NKTFRM 1769 0015 0035
P1     183F 0193 0189
PIOB   0001 0227 0150 0155 0156 0160 0172 0198 0199 0202 0205 0228
PIOBC  0003 0228 0144 0146 0148
PR1    1848 0199 0201
PR2    184E 0202 0204 0207
PRINT  17F1 0143 0061
PRLN   179A 0055 0041 0049
PRNT   1844 0197 0178 0193
SPACES 1836 0189 0168 0183 0194
XK1    1807 0156 0138
XK2    181F 0170 0167
XK3    1821 0171 0169
XK4    1811 0163 0189
XK5    1801 0153 0175
      17F1 0138

```

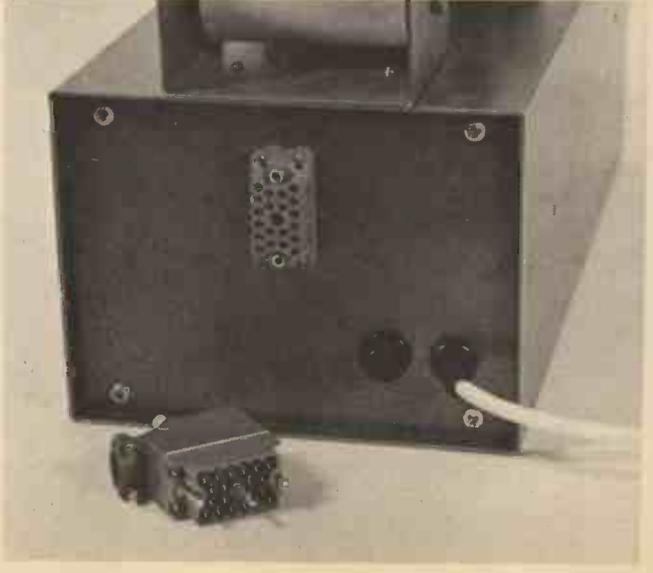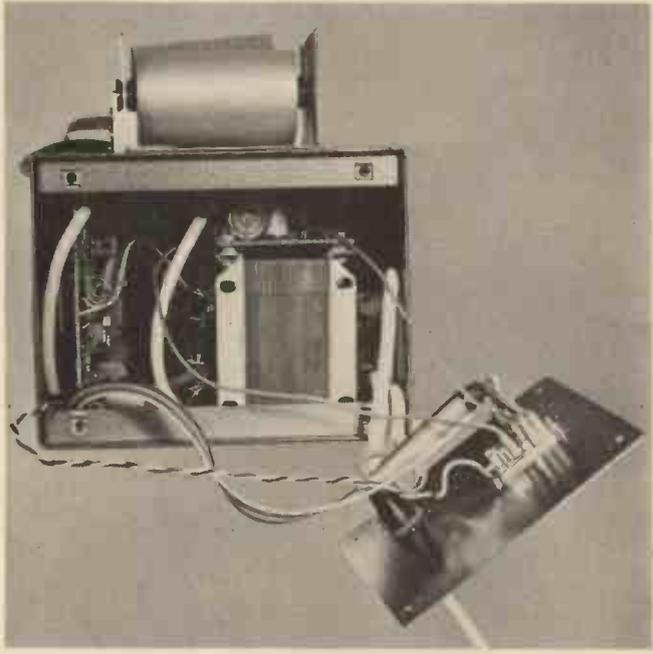

The first DUMP byte is then "fetched" from the start address by use of HL. It is then converted to ASCII characters using BTOHEX and placed in the line buffer using DE and IX. The first frame is now complete.

HL is now incremented to point at the next DUMP byte, but before being used it is compared with the DUMP finish address using the COMP routine. On returning from COMP the Accumulator is tested for the equality code OOH, if A = FFH there is no equality and the routine loops back to fill the next frame.


When all eight frames have been filled and the frame counter is at zero, the routine PRLN is called. PRLN inserts the end of text code at the end of the line buffer and causes the Processor to exchange register banks. It then calls the previously described PRINT routine to print the line buffer contents.

On returning from PRLN the next DUMP address is copied from HL to DE. The routine then loops back and starts converting the new address in DE and creating a new line of data.

DUMP is exited only when the current DUMP address held in HL and the DUMP finish address are found to be equal by the COMP routine. On return from COMP the accumulator contains OOH (equality code), when this is detected PRLN is called to print out the last line after which the program is exited (or halted).

The flowchart of subroutines PRLN, BTOHEX, CON16B and COMP are described in Figs. 2.18, 2.19, 2.20, 2.21, respectively. The full system software is listed.

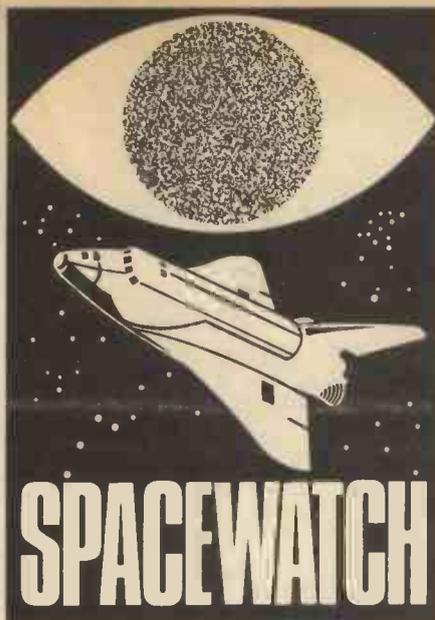This software section completes the description of the system. All that is now required are a few pointers along the stoney path of testing, and a few do's and don'ts about the printer itself. These will appear in Part 3 next month.



**FRANK W. HYDE**

### HEAO-2

The second High Energy Astronomical Observatory was successfully launched on November 13 1978. Its primary task is to investigate X-ray sources. This is a wide area for it includes stellar objects such as Pulsars, Quasars, Super Novae and Radio galaxies. The large glancing incidence X-ray telescope is the largest telescope that has so far orbited the Earth.

HEAO-1 which was launched in August 1977 was designed to be operational for six months. This period has been exceeded by many months and it is still active. During the time up to the launch of HEAO-2 it had added upwards of a thousand more X-ray sources to the 200 or so known at that date.

It must be remembered that the pioneer work on X-ray sources have been done by Ariel-1 and Ariel-5 and the teams working in the British Isles were responsible for this important branch of astronomy getting into the "big time".

The progress that follows such pioneer work does appear sometimes to overshadow what has gone before. The benefits however are the best tribute to the right thinking of the pioneers. HEAO-2 is to add to the extensive search; the sensitivity of the experiments means that it will be possible to look still deeper into space for data to help solve some of the problems facing astrophysicists.

One of the problems of HEAO-2 is that it is necessary to lock on to an object for a long period in order to obtain positive results, consequently the attitude control has had to be improved. The gas jet system has been supplemented with reaction wheels. This will give a pointing accuracy of about one arc-second.

The mirrors employed vary in diameter from 30mm to 560mm. There are three star dissectors used as star trackers which update the gyros during the pointing action. The total length of the telescope is 4.7 metres. A high resolution imager digitally records the central

field of the telescope which is about 25 arc-minutes at the central portion. This operates on the photo-multiplier principle. An incident X-ray photon triggers the emission of an electron and after successive impinging on other plates, its charge is detected. The detected result provides information as to position and features of the object. It is arranged that the imager can work in conjunction with two types of spectrometer.

### PROPORTIONAL COUNTER

Another experiment is a proportional counter. This is co-aligned with the telescope but independent of it. The counter covers a wider range of energies received from X-ray sources. In this case the range is 0.2 to 20keV and the instrument will scan much the same area as the main telescope.

There are three other focal plane experiments. One of these, the crystal spectrometer, will be used to provide spacial as well as spectral information about extended X-ray sources. In this category would come supernovae remnants. The mode of operation can be controlled to variable resolution. Four different apertures can be used and this instrument has its own proportional counters. It is possible with this instrument to obtain information on the chemical composition of the source.

### WIDE FIELD IMAGER

Another instrument is the wide field imager using a pair of counters. Each counter is divided into small regions which observe a portion of the source. The final image resolution is about one arc-minute. There is a further instrument which is a solid state spectrometer. This is capable of observing the whole spectrum over a range of 0.4 to 4KeV. The important part of this instrument is the silicon-germanium crystal. This is cooled by solid methane and ammonia.

The Telescope is orbiting at 537km with an inclination of 23.5 degrees. The vehicle is 6.7m long and 2.4m in diameter with a weight of 3,175kg. The designed life is for 12 months, though no doubt it will follow previous histories and be operational for much longer. To keep up the continuity of observations another vehicle HEAO-3 is planned.

### ANOTHER GOONHILLY

Goonhilly 4 is the first part of the United Kingdom's contribution to Eutelsat. In 1977 the U.K. became a participant in the 17 country Eutelsat. The system is based on the 11/14GHz communication satellite which is called ECS. At present there is a test satellite in orbit which is called OTS2. Since May 1978 it has been in a geo-stationary orbit at 10 degrees above Gabon. The degree is a line of longitude passing near Oslo through middle Europe by Hamburg, Lake Constance, Milan, Sardinia and Tunis.

The terminal is a joint venture of the Post Office, The Department of Industry and Marconi Communication Systems Ltd. The station was designed and built by Marconi's at a cost of some 3.5m and has already been in operation sending 14GHz signals to the satellite and receiving them back at 11GHz.

The aerial is a 19 metre dish with a Cassegrain feed a gain of 66dB at 14.14GHz and a gain of 65dB at a frequency of 10.95 to 11.8GHz. A special feature of the aerial system is that it allows identical frequencies to be transmitted at the same time one polarised horizontally and the other polarised vertically. There is therefore a saving of spectrum space. Part of the preliminary tests are to discover if meteorological conditions will adversely affect performance of those two modes.

The 14GHz transmitter is installed in a building below the dish and feeds the aerial through a waveguide system and horn. The r.f. amplifier consists of a five cavity klystron and gives a power of 1.6kW with a gain of 32dB at a bandwidth of 90MHz. This is fed from 14GHz signals. The convertor can operate on two modes 140MHz which can carry 120Mbits of digital information or 70MHz carrying 60Mbits of digital or f.m. video information.

In addition to dual polarisation further economies are to be obtained by means of digital speech interpolation. This equipment has been designed by Cambridge Consultants. It is a distributed microprocessor system which employs seven Texas Instruments TMS9900S devices. This was such an advanced design that a special simulator had to be built to test it. Simulation of activity in speech is equivalent to 240 terrestrial channels.

The EUTELSAT system is developing to handle European telephony and television programmes during the decade of 1980/90.


### GENERAL DESIGN

The general design of the satellite will be similar to the OTS2. The main differences are that ECS will have twelve 80MHz transponders instead of six different band widths. It will not have attitude control. It will therefore be seen from Earth moving daily in a figure of eight path between 3.5 degrees north and 3.5 degrees south. It will have three spot beam aerials instead of the five on OTS2 and is designed for a 7 year life. The satellite will carry sufficient batteries to power five transponders during an eclipse and is now expected to be launched by the ARIANE launcher instead of the U.S. Thor Delta.

The twelve transponders are accommodated within the frequency band of 500MHz. Six of these are vertically polarised and six are horizontally polarised. The output of the solar panels is capable of powering 9 of the transponders. Each of these transponders terminates in a travelling-wave-tube amplifier output of 20 watts. By the mid 80's it is expected that 15 earth stations will be operational.
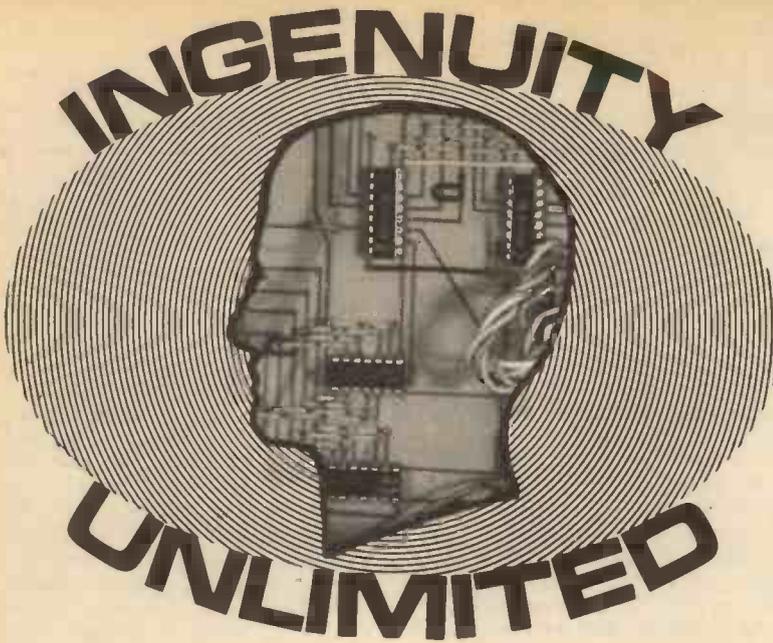
### ICE SHEETS SLOW UP MOON

Christopher Doake of the British Antarctic Survey suggests that the ice sheets floating in the Arctic are responsible for slowing down the Moon and thus cause it to recede. The bending of the ice sheets by about one metre must dissipate something like  $2 \times 10^{12}$  watts over the 26,000 km "hinge line" where the ice is 500 metres thick. Doake says that extensive glaciation occurs in the periods that precede turning points, that is, when the Earth increases its spin velocity.



A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

## VERSATILE TIMER

**T**HIS timer was designed for a full scale range of 60 minutes but by using an output of a lower order than  $2^{14}$ , of the divider, a shorter time can be more accurately achieved. Alternately C1 could be changed for a different range altogether.

IC1c and IC1d form a timing oscillator feeding a fourteen stage binary divider IC2. The output of the divider gates a 1kHz oscillator, IC1a and IC1b, which in turn powers a crystal mike insert as a bleeper. With the VR1 potentiometer of



the timing oscillator on maximum and output Q14 of the IC2 feeding the 1kHz oscillator, the bleeper comes on 60 minutes after closing the switch (R3 and C4 form an initialising circuit resetting the divider at the instant of turn on).

The current consumption is in the order of  $500\mu\text{A}$  when timing and  $1\text{mA}$  when bleeping.

VR1 should be calibrated to suit the timing range chosen. Comparing the inset with the full scale time, it can be seen that

if Q14 is chosen the maximum time is 60 minutes, if Q13 is chosen the maximum time is 30 minutes and if Q12 is chosen the maximum time is 15 minutes etc. By changing C2/C3 to suit the application, the timer has many uses. Examples are as a parking meter, egg timer etc.

D. P. Burton,  
Warrington,  
Cheshire.

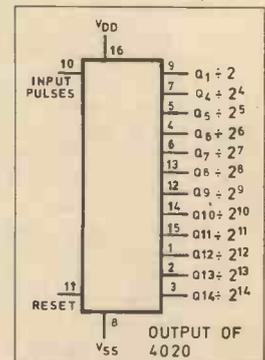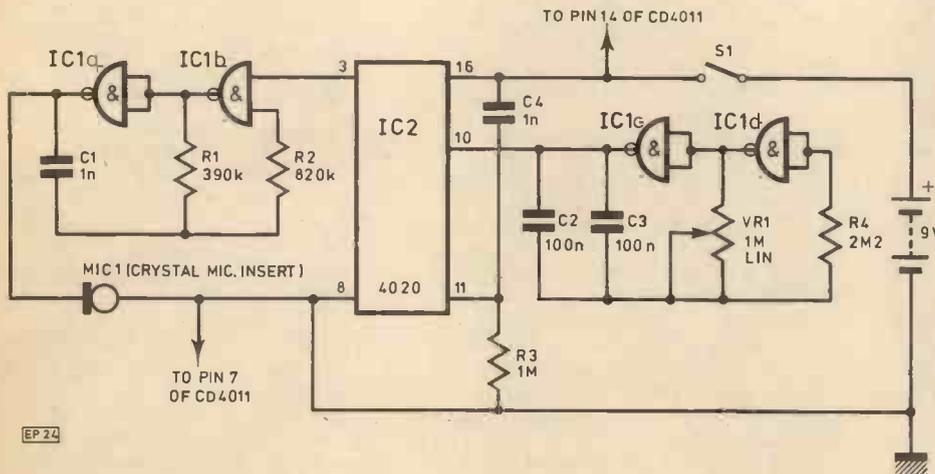

IC1 = 4011

## 6-12V CONVERTOR


**M**ANY imported cars used to have a 6 volt electrical system. Unfortunately, most British car accessories, notably, radio/cassette recorders, require a 12 volt power supply, which makes it impossible to use them in one of the older imported vehicles.

The unit described overcomes this problem by producing a 12 volt supply from a 6 volt battery, at an output current rating of about 0.5 amps, which should be adequate for most car accessories.

The complete circuit diagram. It consists of two main parts—an oscillator which drives a step-up transformer, then a rectifier and regulator circuit.

Transistor TR1 and its associated components form an audio frequency oscillator which operates at about 15kHz, although the exact frequency depends upon the load current. Resistor R1 provides d.c. bias to the transistor base and oscillation is achieved by positive feedback derived from winding L2 on the transformer. The output waveform is almost a square wave, which is stepped up to about 32 volts peak-to-peak in the transformer secondary before being rectified by diodes D1-D4. This produces a voltage of about 15 volts d.c. before the regulator circuit, with less than 0.1 volt peak-to-peak ripple. The transformer inductors should be pile wound on an FX2243 bobbin and enclosed in the pot core.

A simple series regulator circuit is all

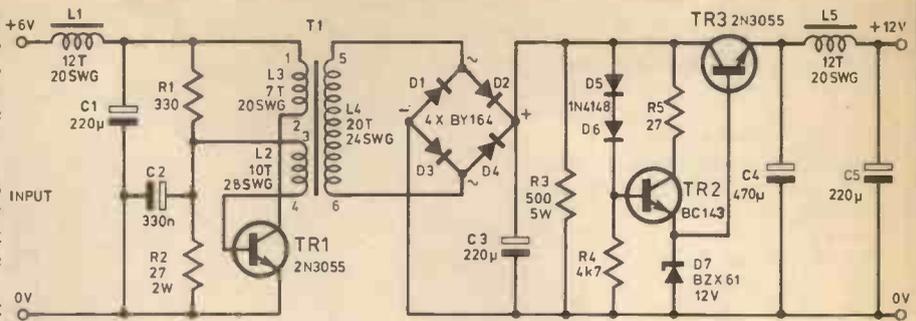

that is required to produce a constant 12 volt output. The base voltage of the series transistor TR3 is controlled by the 12 volt Zener diode D7. Transistor TR3 base current and the Zener current are supplied from transistor TR2, which together with D5, D6, R4 and R5 form a constant current source. This was used in place of the conventional resistor in this position since it prevents the Zener current from rising excessively in the "no load" condition. It also allows a smaller rating Zener diode to be used. The inclusion of R3 limits the rectifier output to about 35 volts when the regulator is not supplying any current.

Inductors L1 and L5 eliminate r.f. interference from the 6 and 12 volt supplies and should be wound on ferrite core.

The connections shown are for a car with a 6 volt, negative earth system. The diecast box can be bolted directly onto the chassis and the internal connection made between the box and the 6 volt negative supply. If a + 12 volt supply is required, the negative output lead may also be connected directly to chassis.

For a 6 volt positive earth system, the only change is that the internal chassis connection must be connected to the 6 volt positive supply.

Because the output is electrically isolated from the input, either one of the output leads may be connected to chassis so providing either a positive or negative 12 volt supply.

D. Turner,  
Plymouth,  
Devon.


## ENVELOPE SHAPER

**A** simple modification to the Autowah circuit (PE March '77) will add an envelope shaping facility and a more interesting Wah-Wah sound. This requires the replacement of the ramp generator (C7, VR2, VR3, R9 and R10) with a trapezoid waveform generator.

A pulse at the base of TR2, due to a signal at the input, causes TR3 to conduct and the voltage at pins 4 and 2 of the 555 to fall to the -ve rail. This resets and re-triggers the 555 monostable. The output of the 555—pin 3—goes high—toward 0V—and C102 charges through D102 and VR103 at a rate dependent on the setting of VR103.

After a period of time, dependent on VR101, pin 3 goes low—and C102 discharges through D101 and VR102 at a rate dependent on VR102.

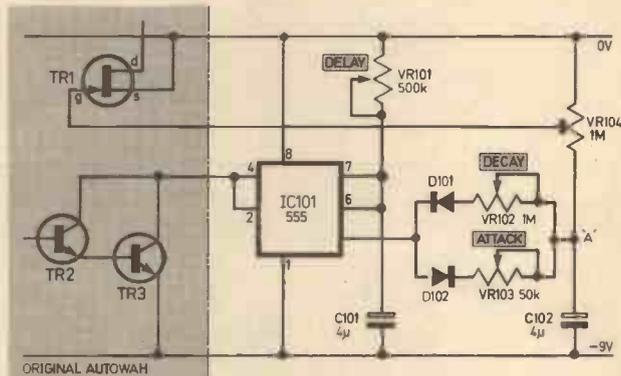Thus at the beginning of each note a trapezoid waveform will appear at point "A" with attack, delay and decay lines fully controllable. This voltage controls the VCA/VCF built around IC11 via VR104 and TR1.



VR104 should be adjusted for flat compromise between no signal at the output when the control voltage is low (-ve rail) and maximum signal when the control voltage is high—with the circuit in the VCA mode. D101 and D102 can be any g.p. silicon diodes.

The timing components (C101, VR101, VR102, VR103, C102) can be altered for those used in the prototype if desired. If

the control pulse breaks through onto the output this can be cured with 0.22µF capacitor across the output. Finally, a piece of advice about usage; the delay period must be long enough to allow the attack phase to occur, otherwise no control voltage will be generated.

A. N. Oliver,  
Brentwood,  
Essex.

## HEADS OR TAILS?


**T**HIS is a variation on "heads or tails".

By using l.e.d.s instead of small bulbs, the whole circuit can be constructed from a single integrated circuit, without the need for a separate transistor clock.

The circuit is shown where IC1a and IC1b form an astable or free-running multivibrator, which clocks the bistable or memory made up of IC1c and IC1d. When S1 is closed, the coin is in the "spinning" mode, in which the square wave output from the multivibrator switches the bistable, and hence the two l.e.d.s, alternately. When S1 is opened, the coin has "landed" and the bistable remains in the state it was last in, and the corresponding l.e.d. will light up indicating the visible side of the coin (heads or tails).

The whole can be constructed inside a tin, provided that a small enough battery is used (PP3 or similar), the "Spin" switch being a miniature push-to-make switch.

D. J. Taylor,  
Maidenhead,  
Berks.

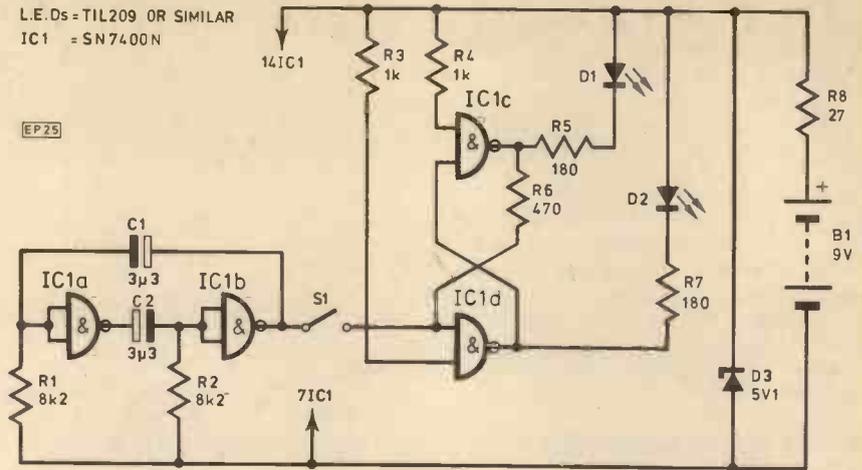

## NOVELTY DOOR-BELL

**T**HIS simple novelty doorbell produces an adjustable range of sounds which will surprise even the most travelled doorbell ringer.

The circuit shown below comprises a number of distinct sections: TR2 forms the on/off controller; TR3 and TR4 form a ramp generator; TR5 to TR8 form a voltage controlled oscillator (VCO) and TR9 and TR10 form an audio amplifier.

When the pushbutton S1 is pressed, C1 charges via R1. The voltage across C1 is


followed by the emitter of TR1. As this voltage rises, TR2 turns on which energises the remainder of the circuit. The ramp generator, running at about 20Hz modulates the VCO on one input, while the voltage on TR1 emitter controls the other input. The VCO output is amplified and passed to the loudspeaker.

When S1 is released, the circuit remains active for a few seconds while C1 discharges through R2. VR2 adjusts the ramp modulation, while VR1 adjusts the

rise and fall of frequency as the button is pressed and released. The range of frequencies produced is quite wide, hence the sound of the bell is difficult to mask (or ignore).

The standby current is infinitely small, and with normal use a PP9 battery will last several years.

P. R. Williams,  
Stevenage,  
Herts.

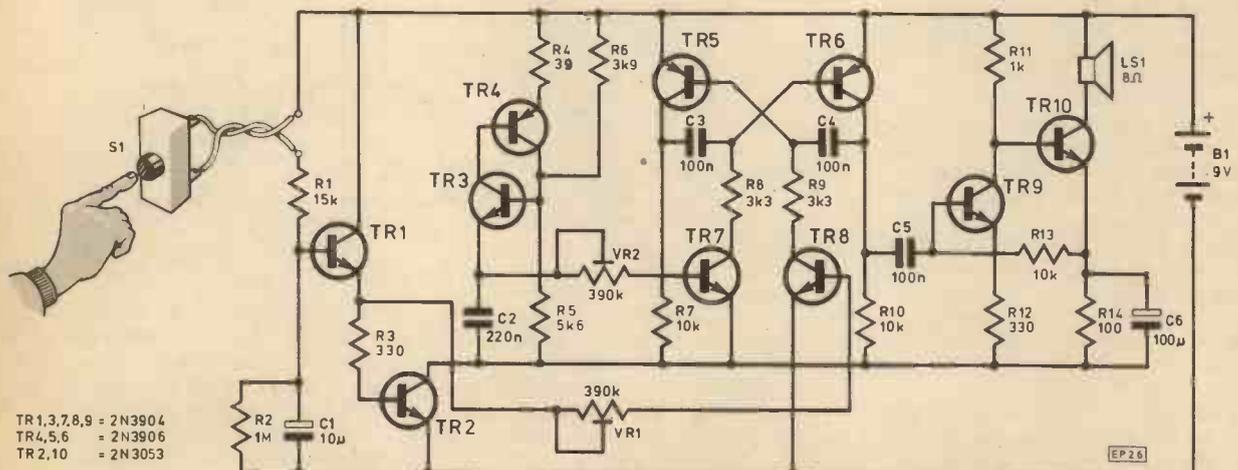

# Semiconductor UPDATE...

FEATURING MC68488, MC3448, ICL8211, ICL8212

R. W. Coles

## ON THE BUSES

Wouldn't it be nice to gather together an ad hoc collection of test equipment such as voltmeters, counters and signal generators, to connect them all together, daisy-chain fashion, and then be able to control the whole collection with the aid of, say, a microcomputer so that the result is a tightly controlled measuring system.

Imagine it, to test a radio receiver, the microcomputer sends out commands to set the frequency and output level of the signal generator, the voltage range of the voltmeter, and the timebase of the counter. While moving automatically through a measuring sequence, the microcomputer accepts output data from the measuring instruments and prints it out in the form of a fully formatted test report. Pipe dream? No, if you like you can do all of this right now, provided that your test instruments are fitted with IEEE488 bus interfaces.

The IEEE488 bus started life at Hewlett Packard as the HP-IB, and it turned out to be such a sound, well engineered design that it has now become accepted as an international standard, adopted by many instrument makers.

In essence the IEEE488 bus consists of an 8 bit wide bi-directional data bus and a further 8 bits of control and handshake data. Instruments connected to the bus are allocated individual addresses, and they may act as "talkers" or "listeners" as determined by the bus controller which could be a programmable calculator or a microcomputer.

Data transfer on the bus can be from any device activated as a talker to any (reasonable) number of devices activated as listeners, and data can be moved at up to two megabytes per second!

Individual instruments can act as talkers and listeners (to receive range commands and transmit measured data for example) and the bus controller can carry out "polling" operations to determine which devices need service.

Not that the bus is restricted only to sophisticated measuring systems, you can connect together a voltmeter talker and a printer listener to form a simple and controllerless system, and if further proof of the usefulness of the IEEE488 is necessary, the Commodore PET microcomputer comes equipped with an interface as a standard feature.

## BUS CHIP

Now, to get to the point of my story, Motorola have introduced an IEEE488 bus interface in a single 40 pin package, coded **MC68488**.

The new chip is a version of the GPIA (General Purpose Interface Adapter), and is a member of the MC6800 microprocessor family.

One side of the interface hooks up to the microprocessor data bus and control lines such as R/W and RESET, and the other side drives the IEEE488 bus via bi-directional Tri-state drivers such as the **MC3448** (which is designed for the job).

The MC68488 handles many of the complex bus protocol functions automatically, but some others do require extra effort from the microprocessor, under software control.

With a little imagination, you can use the MC68488 with other microprocessors, so come on, if you want to transfer data at a rapid rate, send it by bus!

## POSITIVE REGULATOR —

### THYRISTOR BOOST

## MICRO-POWER

No, not another microprocessor news item (sighs of relief!), but a pair of new low consumption voltage regulator building blocks which are optimised for use at very low voltages and/or currents where their fixed voltage (e.g. LM309) cousins fear to tread.

The new devices are made by Intersil and are coded **ICL8211** and **ICL8212**. Both are bipolar monolithic integrated circuits in 8 pin mini-d.i.p. packages, and both can be used in some interesting and diverse applications such as positive and negative voltage regulators, constant current sources, overvoltage crowbar circuits and power failure detectors.


The ICL8211 contains a low voltage (1.15 Volt) reference circuit, a differential error amplifier with a feedback reference input, a current limited common emitter output amplifier, and p.n.p. hysteresis transistor.

The ICL8212 is similar except that the common emitter stage is not current limited.

The new devices are really intended for the unusual, rather than the run-of-the mill, applications, particularly those where low consumption is essential.
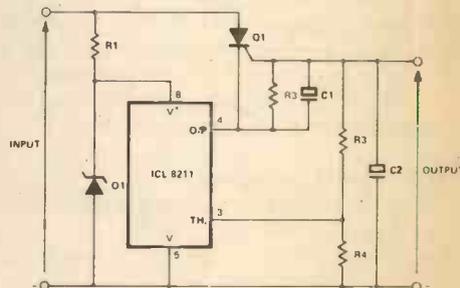
## APPLICATIONS

One application which caught my eye was the use of the ICL8212 as a programmable "Zener". This circuit uses two resistors and a capacitor in addition to the i.c., but by varying the ratio of the resistors, any "Zener" voltage from 2 to 30V can be selected, and a particular advantage is the extremely low "knee" current of less than 300 micro-amps.



Another application using an 8211, and shown here, is interesting for its use of an external thyristor as an n.p.n.-p.n.p. transistor structure, operating in a linear mode and providing increased output current in a positive voltage regulator circuit.

A unique feature of this circuit is that the cathode of the thyristor is acting as the control terminal, and the gate as the output terminal!

The only problem with this circuit is that manufacturers' data sheets for thyristors do not cover this strange mode of operation, and no gain figures will be given for the p.n.p. portion of the structure which is utilised here. This of course, need not hinder the experimenter!

# GUITAR SOUND MULTIPROCESSOR

## Part 3

Mark A. Sawicki M.Sc.(Eng.) Alex. Kowalewski

In part two we dealt with the clock system and the input and output filters. In this the VU driver, power supply board and the pushbutton switch control module will be described together with chassis design details and enclosure.

### PUSHBUTTON CONTROL MODULE

In the stacked pushbutton control module there are three boards, the top being the input filter, the second is the clock board, and the third is the output filter (see photos Part 2). The boards are separated from each other by means of eight 2.5cm p.v.c. spacers and from the bottom plate by four 1cm p.v.c. spacers. The whole module is fastened to the bottom plate by means of four 85mm steel wires threaded for 6BA self-locking nuts. The front panel is fastened to the bottom plate by the necks of the five jack sockets.

The centres of the pushbuttons are about 30mm apart in both horizontal and vertical directions.

### OPTIONAL VU DRIVER

Fig. 14 shows the complete VU driver circuit. The 748 is an op-amp packaged into a TO99 round metal can, with leads bent into an 8 pin d.i.l. configuration. C75 is provided to damp the movement of the meter.

The 748 is a similar device to the 741 op-amp except it has external frequency compensation for improved high frequency gain.

The power for this circuit is taken from the 0 and +15V d.c. rails only. Input is taken directly from the output of the first low pass filter.

Calibration is achieved by means of VR11.

Due to the simplicity of this optional unit it was constructed on a piece of 0.1in matrix Veroboard (45mm x 25mm) and fastened to the main board as can be seen in the photograph (page 1251—Part One).

### LED STATUS INDICATOR SYSTEM

Fig. 15 shows the complete circuit diagram of the l.e.d. status indicator system. The spare connections on the main front panel slider switches are used for this purpose. Note that the l.e.d. status indicators are independent of the remote control.


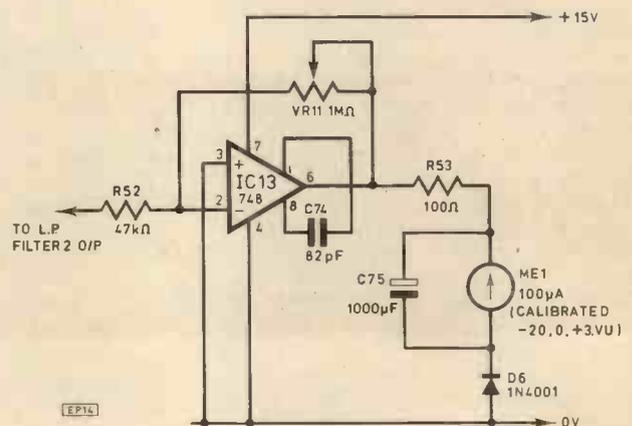


Fig. 14. VU driver circuit

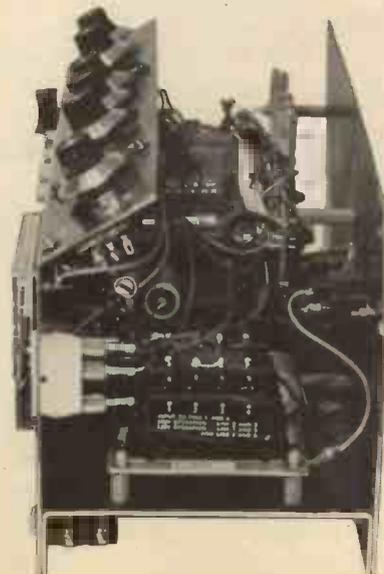

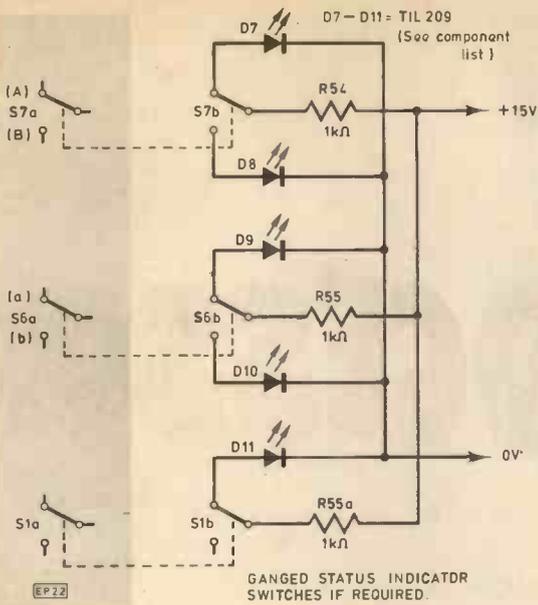


Fig. 15. L.e.d. status indicator


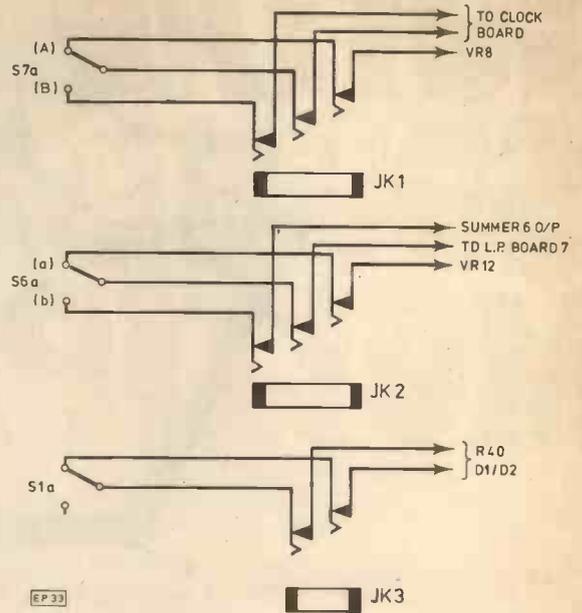


Fig. 16. Wiring for optional remote control jacks

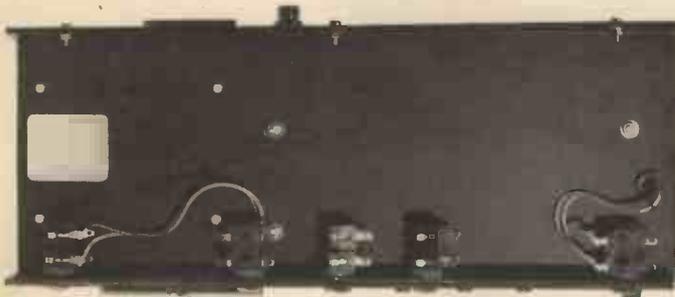

The l.e.d.s are very useful if the processor is used in a live performance situation where the ambient light is often very low. Here the upper switch positions are denoted by green and the bottom by red l.e.d.s. The fuzz effect however has a yellow l.e.d. for the on position.

### REMOTE CONTROL

Fig. 16 shows a complete circuit diagram of the remote control system. It employs three, two and three pole chassis mounting  $\frac{1}{4}$  in jack sockets. Consequently when a jack plug is inserted into the socket it automatically bypasses the slider switch on the front panel, thus preparing the unit for optional footswitch operation.



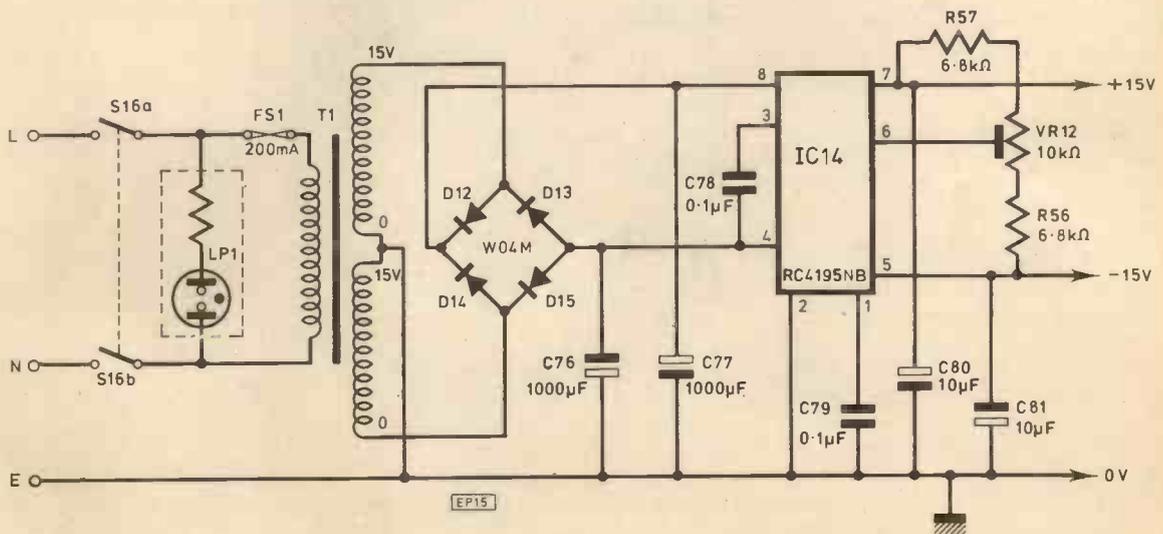


Fig. 17. Circuit of power supply unit

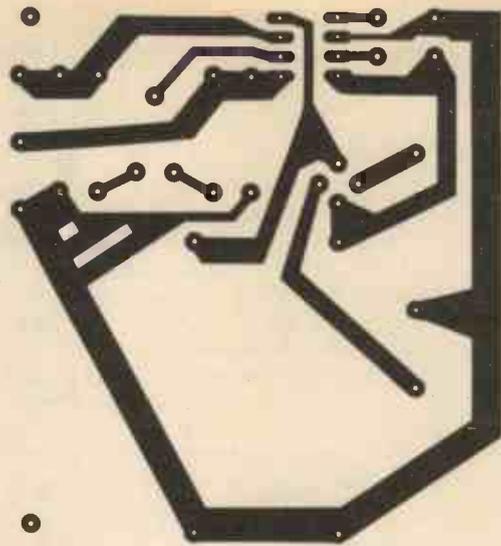

EP16

Fig. 18. P.s.u. printed circuit board

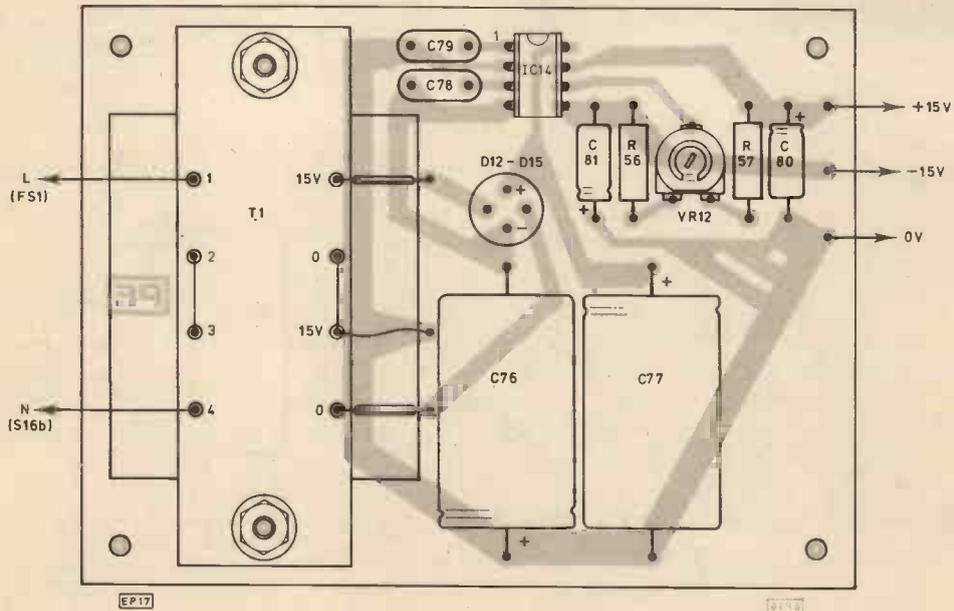

EP17

EP18

Fig. 19. P.s.u. board layout



Prototype board based entirely on RS components

This feature will prove to be essential for guitar work.

These footswitches are available from:

Re-An Products Ltd.,  
Burnham Road,  
Dartford,  
Kent, DA1 5BN.

### POWER SUPPLY

The complete circuit diagram of the power supply board is shown in Fig. 17. This employs a RS transformer, and monolithic voltage regulator. The prototype multiprocessor included an RS board; however an alternative p.c. layout is given in Fig. 18 with component and wiring details in Fig. 19.

The power supply is stabilised and regulated providing +15V, 0V, -15V d.c. The whole p.c.b. is mounted on four 1cm p.v.c. spacers on the right-hand side of the base plate as can be seen. The mains is switched on and off by means of an illuminated rocker switch.

Power is fed to the unit via a Euroconnector and then a 200mA fuse, both auxiliary devices are mounted on the rear panel.

### CHASSIS AND CASE CONSTRUCTION

Fig. 20 shows the dimensions of the individual metal plates required to construct the chassis unit for the guitar sound multiprocessor. All the aluminium used was 1.5mm thick. Basically all that is required is the main base plate (C), rear panel (B) and front panel (A) which has been bent to cater for the sloping front panel design. All the metal surfaces were sprayed with gloss paint and the artwork was carried out in Letraset which was later sprayed with lacquer in order to protect it.

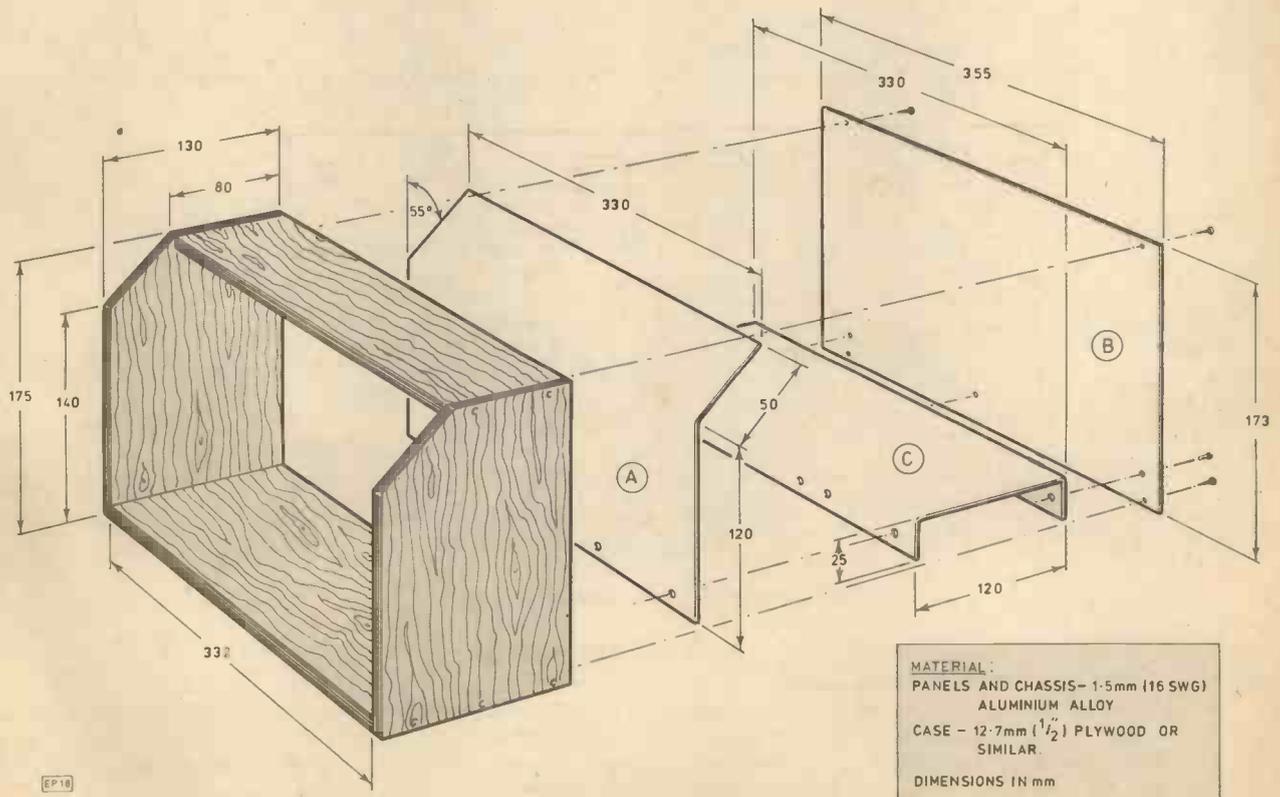


Fig. 20. Exploded diagram of chassis and case

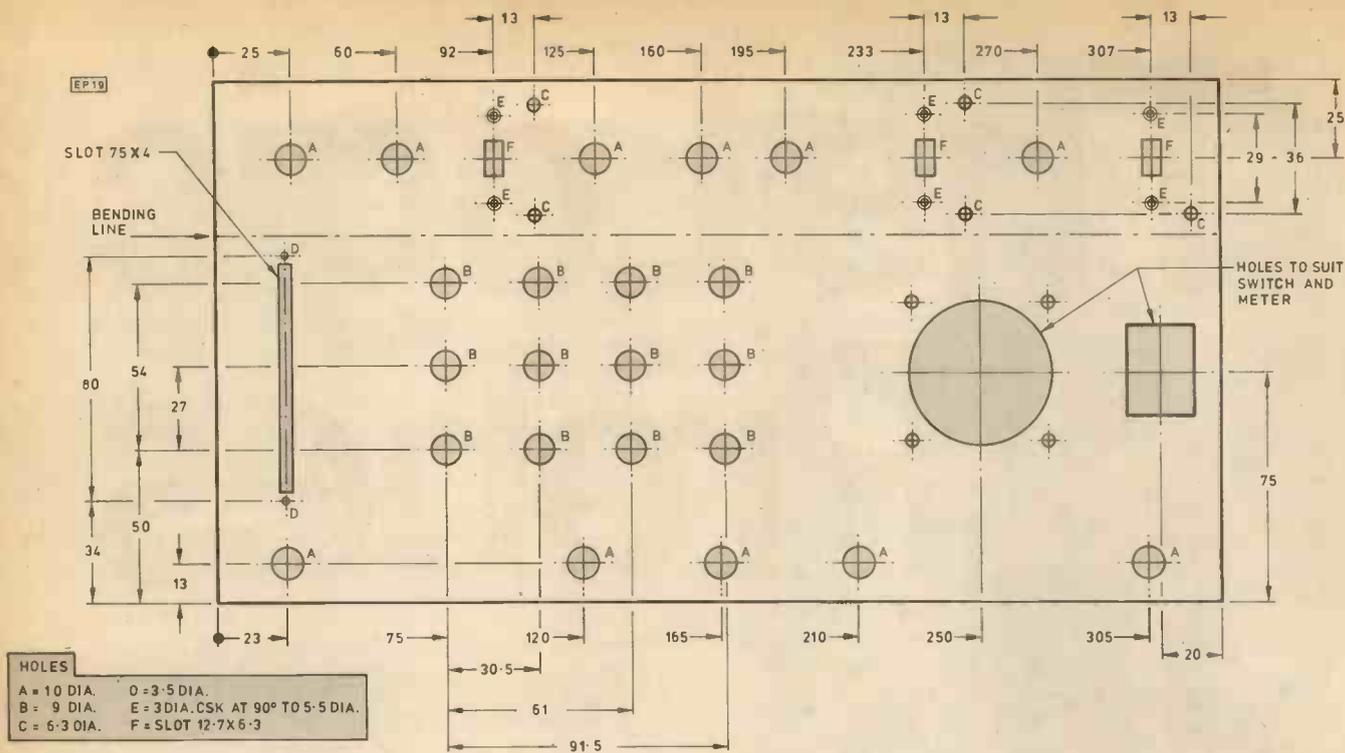


Fig. 21. Cutting details of front panel

**Switch positions and o'clock settings of potentiometers for sounds indicated**

Control	Rotary	Fuzz	Flanging	Phaser/Vibrato	Reverb	Computer Voice	Repeat Echo	Vibrato/Reverb
1	9	Min	9	Min	Min	9	10	9
2	5	Min	1	Min	6	Min	Min	Min
3	Down	Down	Up	Up	Down	Up	Up	Min
4	12	Min	Min	Min	11.30	12	Min	12
5	12 (delay 4mS)	Min (delay 4mS)	12 (delay 4mS)	12 (delay 4mS)	Min (delay 43mS)	12 (delay 9mS)	9 (delay 43mS)	4 (delay 4mS)
6	9	Min	10	6	Min	5.30	9	9
7	Down	Down	Down	Up	Down	Up	Up	Up
8	Min	5.30	Min	Min	Min	12	Min	Min
9	Up	Down	Up	Up	Up	Up	Up	Up

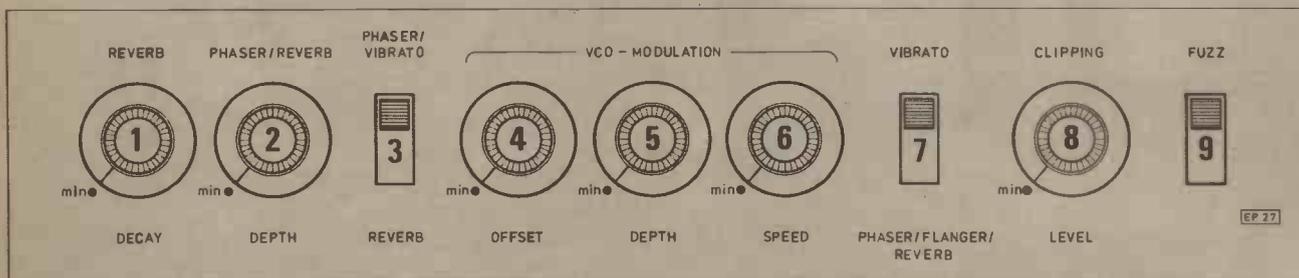


Table 2 and numbered related controls

Drilling details for the front panel are given in Fig. 21 but these should be modified as component sizes dictate.

Fig. 20 shows the dimensions of the case components which were comprised of 1/2 in plywood covered in plastic Vinyl Rexine. When gluing on the plastic use "Evostick" because it allows you to move the plastic into position before it sets.

It's a good idea to attach a carrying handle to the case for safety and ease in transportation.

**SETTING UP**

This instrument is experimental in nature so when using it let your imagination be your guide. However, Table 2 gives you a rough idea of what can be achieved with the processor.


Some component changes have been made and are correct as shown in the circuit diagrams.



# The Logic Probes

When you see what these new CSC logic probes can do, in such a small size, and at such small prices, there's only one word for it:—

## Amazing!

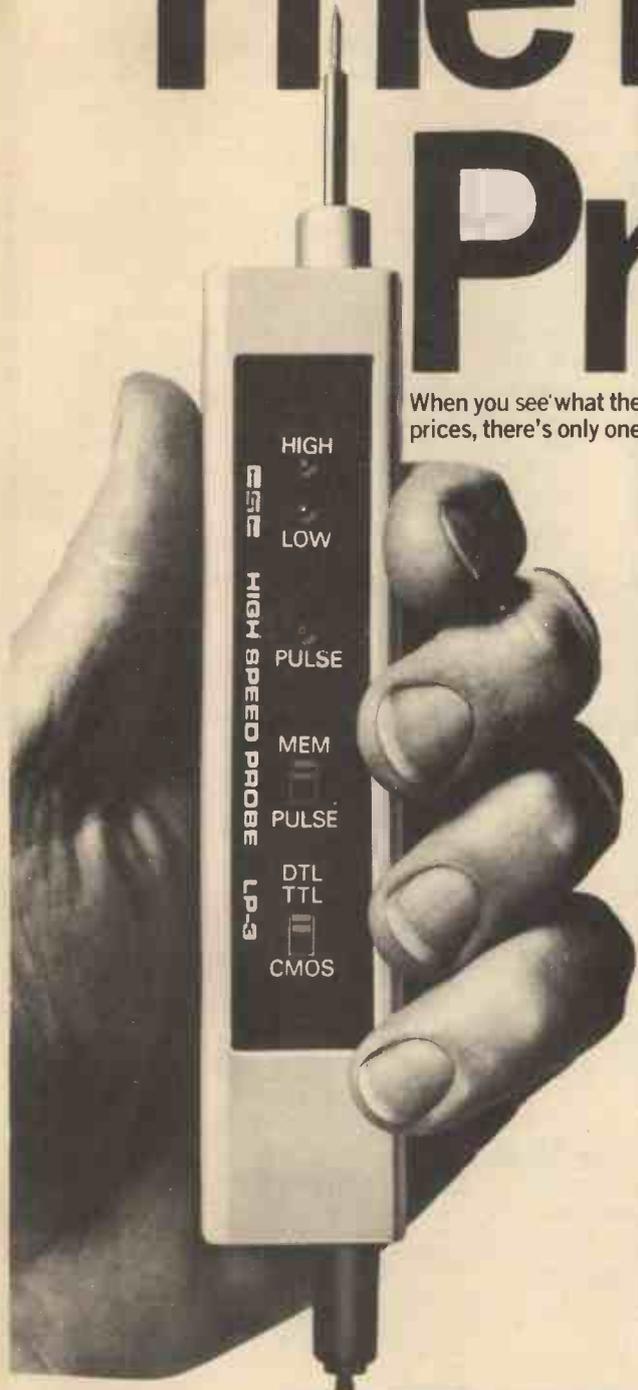

**LP-1** Unit Price £31.00·Post & Package £1.50·VAT £2.60·Total £35.10.  
Clip the leads to the power supply of the circuit under test, touch the probe tip to any pin, pad or component and you're in business. The 'HIGH' and 'LOW' LEDs show logic states 1 or 0; if neither come on you've got open circuit, tri-state, signal out of tolerance (or no power!). The 'PULSE' LED flashes once for any pulse 50nsec or longer, and flashes regularly at 3Hz for high frequency trains. Then, while 'PULSE' is flashing, 'HIGH' will come on alone to show duty-cycles over 85%, 'LOW' alone to show less than 15%, and with both on together duty-cycles can be estimated between 15% and 85% by relative brightness. In the MEMORY mode, the leading edge (positive- or negative-going) of any pulse will latch a flip-flop on and keep the PULSE LED lit as long as power is applied to the probe. You can catch events that are hard to see even with a high quality scope! LP-1 is switch-selectable for DTL/TTL and HTL/CMOS circuits.

**LP-2** Unit Price £18.00·Post & Package £1.25·VAT £1.54·Total £20.79.  
Economy version of LP-1, with the same HTL/CMOS and DTL/TTL capability. 'HIGH' or 'LOW' LEDs function as in LP-1; 'PULSE' catches pulses as short as 300nsec and shows pulse trains as 10Hz blink. When pulsing, 'HIGH' comes on to show duty-cycles above 70%, 'LOW' shows below 30%, both on together show between 30% and 70%. 300,000 Ohm input impedance protects your circuit under test, and the low price brings the advantages of our quick, easy LOGIC PROBE technique to anyone interested in logic circuitry.

**LP-3** Unit Price £49.00·Post & Package £1.50·VAT £4.04·Total £54.54.  
Super-high speed version, captures pulses as short as 10nsec, and monitors pulse trains as rapid as 50MHz. That's better performance than many oscilloscopes! And no bulky instruments, no set-up time. At frequencies up to 1.5MHz you can estimate duty-cycles by the High/Low relative intensity, as with LP-1. DTL/TTL and HTL/CMOS are switch-selectable, of course, plus 'MEM' memory mode to latch on to any pulse, pulse train or passing transient. LP-3 is the ideal trouble-shooter for your fastest logic circuits, and like all CSC probes is well-designed, handy and easy to use, robust, reliable and individually tested before it leaves the factory.

**And the new pulser DP-1** Unit Price £51.00·Post & Package £1.50·VAT £4.20·Total £56.70.  
The Digital Pulser, another new idea from CSC. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 100Hz. The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And a very reasonable price.

**How to order.** Telephone 0799-21682 and give us your Access, Barclaycard or American Express number, and your order will be in the post that night. Or, write your order, enclosing cheque or postal order, or stating credit card number and expiry date. (Don't post the card!). Alternatively, ask for our latest catalogue, showing all CSC products for the engineer and the home hobbyist.

(Prices are for UK only. For Europe add 10%, outside Europe add 12½% to total prices.)

Specification	LP-1	LP-2	LP-3	DP-1
Input Impedance	100,000Ω	300,000Ω	500,000Ω	Output Tri State
Minimum Detectable Pulse	50ns	300ns	10ns	Autopolarity Pulse Sensing
Max. Input Signal (Freq.)	10MHz	1.5MHz	50MHz	Sink and Source 100 ma
Pulse Detector (LED)	High Speed Train or Single Event	High Speed Train or Single Event	High Speed Train or Single Event	Pulse Train: 100pps
Pulse Memory	Pulse or Level Transition Detected and Stored	None	Pulse or Level Transition Detected and Stored	LED indicator flashes in Single Pulse. Stays lit on Pulse Train

CONTINENTAL SPECIALTIES CORPORATION (UK) LTD.,  
UNIT 1, SHIRE HILL INDUSTRIAL ESTATE, DEPT 5J,  
SAFFRON WALDEN, ESSEX CB11 3AQ TEL: 0799-21682.



REGISTERED IN LONDON, 1303780 VAT No. 224 8074 71  
DEALER ENQUIRIES WELCOME.

TRADE MARK APPLIED FOR © CSC (UK) LTD 1977.

# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, T.V. Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
Also MPT Radio Communications Certificate

## Diploma Courses

Colour T.V. Servicing  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name

Address

Age

**ICS**

To ICS, Dept. D273, Intertext House,  
London SW8 4UJ  
or telephone 01-622 9911 (all hours)



# Wilmslow Audio

THE firm for speakers!

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER  
BOWERS & WILKINS ● CASTLE ● CELESTION  
CHARTWELL ● COLES ● DALESFORD  
DECCA ● EMI ● EAGLE ● ELAC ● FANE  
GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON  
JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER  
McKENZIE ● MONITOR AUDIO ● PEERLESS  
RADFORD ● RAM ● RICHARD ALLAN ● SEAS  
SHACKMAN ● STAG ● TANGENT ● TANNYO  
VIDEOTONE ● WHARFEDAILE ● YAMAHA

## WILMSLOW AUDIO (Dept. P.E.)

SWAN WORKS, BANK SQUARE, WILMSLOW,  
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street  
Tel.: Wilmslow 529599 for Speakers Tel.: Wilmslow 526213 for Hi-Fi

# Clef Kits —

Designer approved quality kits for Electronic Musical Instrument Construction.



JOANNA 72 & 88 PIANOS  
Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. A new physical layout has been adopted to simplify construction.

P.E. STRING ENSEMBLE  
The only kit available to the proven A. J. Boothman Design for this versatile String Machine.

Send S.A.E. to —

Clef Products (Dept P.E.) 16, Mayfield Road,  
Bramhall, Cheshire SK7 1JU

SINCLAIR PRODUCTS microvision tv £90.  
PDM35 £27.25. Mains adaptor £3.24. Case £3.25. DM235 £48.30. Rechargeable battery units £8. Adaptor/charger £3.70. Case £8.50. Cambridge prog. calculator £13.13. Prog. library £3.45. Mains adaptor £3.20. Enterprise prog. calculator £21.95. DM350, DM450 p.o.a.

COMPONENTS send sae for full list. 1 lb FeCl £1.05. Dalo pen 73p. 60 sq ins pcb 55p. Laminate cutter 75p. Small drill 20p. zn414 £1.05. Pcb and extra parts for radio £3.85. Case £1. 1N4148 1.4p. 1N4002 2.9p. 723 29p. 741 15p. NE555 2.3p. bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p. Plastic equivs bc107, bc109 4.8p. 1W 5% E12 resistors 10R to 10M 1p. 0.8p for 50+ of one value. 16V electrolytics 5/1/2/5/10/22mf 5p. 100mf 6p. 1000mf 10p. Polyesters 250V .015, .068, .1mf 1½p. Ceramics 50V E6 22pf to 47n 2p. Polystyrenes 63V E12 10 pf to 10n 3p. Zeners 400mV E24 2V7 to 33V 7p.

TV GAMES send sae for data. AY-3-8500 + kit £8.95. AY-3-8600 + kit £12.50. Tank batteries chip + kit £13.95. Stunt cycle chip £6.90, kit £4.00. Rifle kit £4.95.

IC AUDIO AMPS with pcb JC12 6W £1.60. JC20 10W £2.95. JC40 20W £2.95.

BATTERY ELIMINATORS 3-way type 6/7½/9V 300mA £2.95. 100mA radio type with press-studs 9V £3.35, 9+9V £4.50. Stabilized type 3/6/7½/9V 400mA £6.40. 12V car converters 3/4½/6/7½/9V 800mA £2.50.


BATTERY ELIMINATOR KITS send sae for data. 100mA radio types with press-studs 41V £1.40, 6V £1.40, 9V £1.40, 4½+4½V £1.80, 6+6V £1.80, 9+9V £1.80. Stabilized 8-way types 3/4½/6/7½/9/12/15/18V 100mA £2.80, 1Amp £6.40. Stabilized power kits 2-18V 100mA £3.60, 2-30V 1A £6.95, 2-30V 2A £10.95. 12V car converter 6/7½/9V 1A £1.35.

T-DEC AND CSC BREADBOARDS s-dec £3.17, t-dec £4.02, u-deca £4.40, u-decb £6.73. 16 dill adaptor £2.14, exp 300 £6.21, exp 350 £3.40, exp 650 £3.89, exp 4b £2.48.

BI-PAK AUDIO MODULES S450 £23.51. AL60 £4.86, pa100 £16.71, spm80 £4.47. bmt80 £5.95. Stereo 30 £20.12.
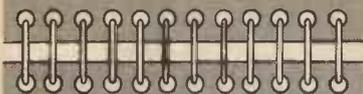
## SWANLEY ELECTRONICS

(Dept. PE), 32 Goldsel Rd.,  
Swanley, Kent BR8 8EZ  
Post 30p extra. Prices include VAT.



# INDUSTRY NOTEBOOK

By Nexus



## International

Electronics has always been an international industry. But never on such a vast scale as we are witnessing today or over such a variety of electronic products. Countries who had little or no capability in electronics are now becoming substantial producers.

At first, these "backward" countries were being used as low-cost labour areas for assembly work. They are now climbing the learning curve. Soon they, too, will be designing.

The process is being accelerated by technology transfer, especially in defence electronics. Few countries today, when procuring defence equipment, are content to let an overseas supplier provide everything. They want a share of the work themselves.

If they need, say, 1,000 military radios they will take the first 100 from the supplying country and set up a local assembly plant to build the balance of 900 radios, largely from kits but embodying as much as possible that can be built or acquired locally. This is very true of the Middle East.

But for commercial or other reasons it is also happening in the advanced electronics countries. Who could have imagined only a few years ago that one day the chairman of a substantial UK operation would be a Mr. Kenichero Hiyama, overseeing the production of radio and TV equipment carrying famous brand names such as Bush and Murphy. Mr. Hiyama is the Japanese chairman of Rank-Toshiba, the first joint Anglo-Japanese company of which 70 per cent is owned by the Rank Organisation, 30 per cent by Toshiba.

The company will plough in an extra £3 million investment to strengthen the existing Rank plants at Plymouth and Redruth with the target of a production rate of 350,000 colour sets and 100,000 monochromes a year.

We can expect further Japanese penetration in the years ahead. The advantage of a joint company is clear. At least, from the British viewpoint, production is maintained, even increased, in the UK and products will be exported under the Toshiba brand name to other European countries.

Thorn Consumer Electronics is expressing a willingness to learn from others. Half a dozen union men and four senior managers have been to Japan to see for themselves the conditions and work methods of their main competitors.

## Technology Transfer

Technology transfer has also been in the news. The biggest single new outlet for UK expertise looks like being China. At the time of writing no substantial new orders had been announced as definite but there were high hopes of substantial contracts for defence and other equipment. It is almost certain that China will want to build, for example, Harrier jump-jets and aero engines under a technology transfer agreement. Defence electronics will follow.

Nearer home, Racal has done a deal with Spain in which the Spaniards will build Racal-designed VHF military manpack radios in a factory near Madrid. A condition of tender was that bulk manufacture would take place in Spain. Refusal means no business. Acceptance of the condition still brings in Racal some £6 million, well worth having and, as there was plenty of competition for the contract, if Racal didn't win someone else would.

Discussing this type of deal with industry leaders I was told that high technology companies are confident they have the inventive muscle to stay ahead of the game. That by the time a technologically retarded country had mastered the present generation of equipment the advanced companies would already be in production of the next generation. As for example, in the giant Togliattigrad car assembly plant in the Soviet Union, designed by Italian Fiat but behind in technology compared with Fiat's present developments at Turin, or the production of ITT connectors in Poland which are technologically a generation behind those produced by ITT in Western Europe or the United States.

Nonetheless, the gap is bound to narrow and there are plenty of examples of intelligent pupils who have outclassed their masters, prime example being the Japanese who were non-starters in many fields a short 30 years ago but are now fearsome competitors, not least in electronics.

## Single Chip

The single-chip revolution is now well under way. I have quoted several examples in recent months and almost daily some complicated function or other is revealed as not only technically feasible on a single piece of silicon but with production samples available.

I remember the mixed feelings I had

when I looked into the guts of the first Racal 99 Series frequency counters, based on a Ferranti chip, when they appeared some three years ago. There was the box with practically nothing in it. Of course they worked beautifully but when you are laying out a few hundred pounds you expect to see something substantial inside for your hard-earned cash.

I was reminded of this early experience, almost shocked disbelief, when Hewlett-Packard announced their new 100MHz 5315A counter-timer which includes computing facilities from a microprocessor.

Only nine years ago the equivalent H-P product of that era had a dozen p.c.b.s packed with TTL circuits to perform the logic functions alone. The same work is now done by a couple of chips. In all, the new instrument contains just nine i.c.s. The 5315A, selling at about £500 and a low-cost sister instrument at about £230 have been introduced to meet fierce competition in the counter market.

Look to Philips, too, for intensification of competition in the instrument market. Philips was anything but a leader even five years ago.

Since catching the instrument bug Philips has made considerable inroads, especially with oscilloscopes. The 1978 sales of instrument products in the UK were 50 per cent higher than in 1977 and in the instrument business this is indeed fast growth.

## Prestel

The Post Office Prestel viewdata service is proving an exciting prospect for overseas administrations as well as at home. It could be a big export hit. West Germany, the Netherlands, Hong Kong and the USA (in agreement with a US company) have already signed, or are in process of doing so. The seventeenth country in which live demonstrations have been given is the Soviet Union with a presentation in Moscow.

Post Office researchers are now busy devising new ways of getting viewdata on the screen in different alphabets such as Arabic, Greek, Hebrew and the phonetic Japanese script known as Katakana.

There are great hopes that the British system will be adopted as the world standard, thus enhancing further export prospects.

## GEC/Fairchild

The GEC/Fairchild joint venture in the UK for the production of VLSI circuits appears to be on schedule with production still forecast for 1980. INMOS, a possible competitor backed by the National Enterprise Board, will pose no threat according to Fairchild chairman Wilf Corrigan who has gone so far as to forecast INMOS as "doomed" and "too late".

Well, time will tell, but as regular readers will remember I tend to agree that INMOS chances are slim if only because it has no established marketing outlets and no previous track record of its own.




# PATENTS REVIEW...

Copies of Patents can be obtained from :  
 the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each
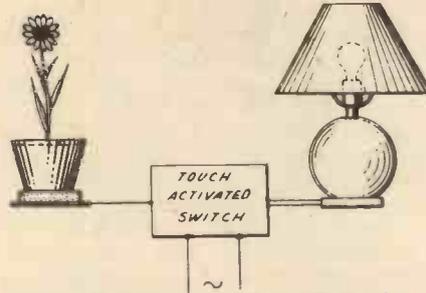
## ORGANIC TOUCH SWITCH

BP 1520625, from Harold Barkan of New York, describes a simple idea in lengthy prose which is characteristic of patents originating from the USA. The interest value of the simple idea does however justify the effort of cutting through the verbiage. The object is to modify a touch control switch so that it is actuated by touching a living plant!

Barkan has made the simple, but apparently novel, observation that if the touch sensitive element of an electrical touch switch (e.g. of the type used to control domestic lighting) is electrically connected



to the roots of a pot plant, then the plant itself will serve as the touch sensitive element.

Bearing in mind the high fluid content of a living plant, this is readily understandable. Barkan maintains that even cut flowers or fruit and vegetables in a bowl are sufficiently electrically conductive to function in the same manner.


The simplest approach recommended is merely to extend the touch sensitive element of an off-the-shelf touch sensitive switch. A length of wire connects with an electrode buried under the earth in which the plant grows. According to the inventor, a light or other load connected to the switch terminals can then be switched on and off merely by gently stroking the plant leaves or flowers.

## PIEZOELECTRIC TRANSDUCER

Audio designers are turning towards piezo-electric powered loudspeakers and several modern high fidelity speakers now incorporate piezo horns as their HF units or "tweeters". In BP 1 489 351, Philips patent a loudspeaker which is based on a diaphragm formed entirely from piezo-electric material and, in principle, appears adaptable to larger and wider bandwidth units than previously.

The Philips transducer has a circular diaphragm formed from a foil of polyvinylidene fluoride, a material which has piezo-electric properties. The diaphragm foil has metal electrodes vacuum deposited on each major surface and is circularly corrugated, so that its surface is covered with concentric rings of V-shaped cross-section. The opposite walls or flanks of each ring are oppositely polarised. Thus in Fig. 1 the flanks 2, 4 and 6 are

Fig.1

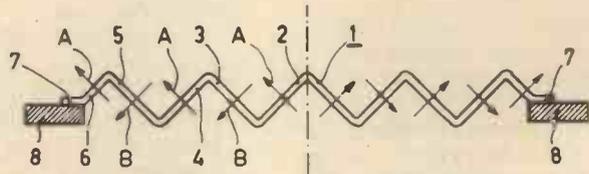

polarised in one direction (arrows A) and the flanks 3 and 5 are polarised in the opposite direction (arrows B). In Fig. 2 the flanks 20, 22 and 24 are polarised in the direction of the arrows P and flanks 21 and 23 in the direction of arrows Q. The diaphragm is polarised by electrodes 30 and 31 of the polarising device (Fig. 3).

When an alternating voltage audio signal is applied to the surface electrodes (not shown in the diagrams), all the flanks of the diaphragm behave in characteristic piezo-

electric manner and change in length. But as the flank pairs are oppositely polarised the action of all the flanks is concerted, and the diaphragm as a whole moves in an axial direction. It thus behaves in the manner of a conventional loudspeaker cone driven electromagnetically by a moving coil. So, the applied audio signal is converted directly into mechanical energy. This suggests that the unit will have high efficiency in terms of sound level transduced from audio signal input.

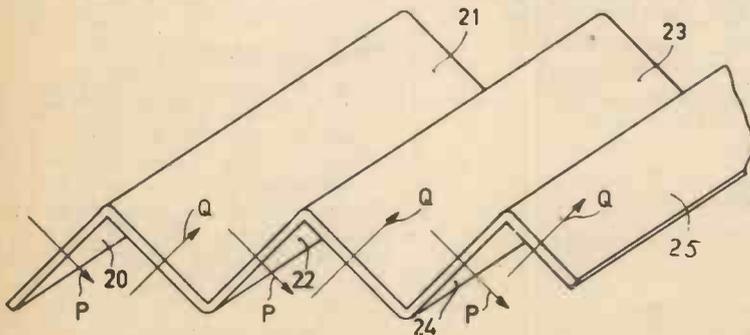


Fig.2


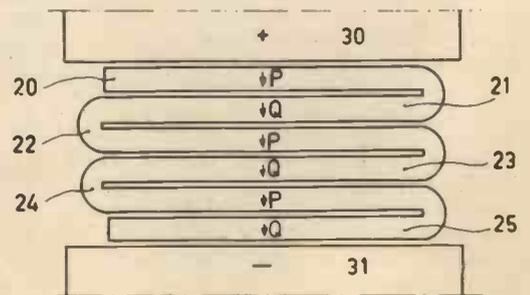


Fig.3

# The Sinclair PDM35.

## A personal digital multimeter for only £29.95

(+8% VAT)

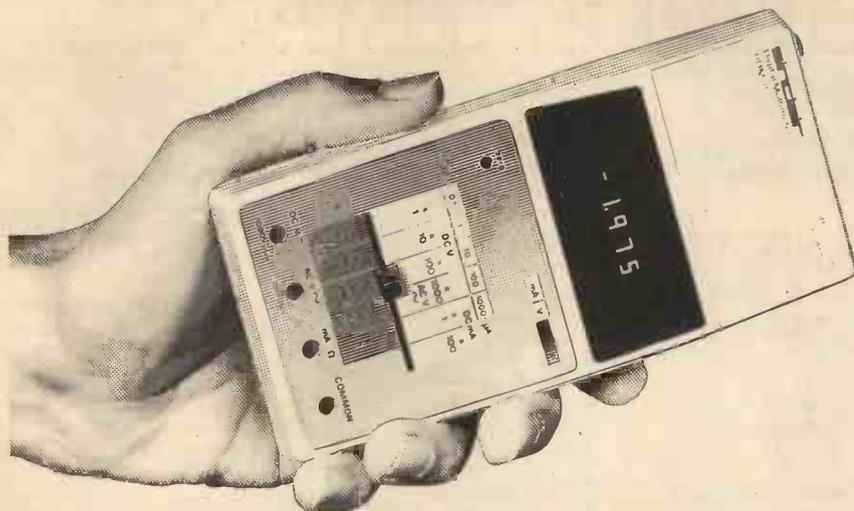

### Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter - quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

### What you get with a PDM35

- 3½ digit resolution.
- Sharp, bright, easily read LED display, reading to ± 1.999.
- Automatic polarity selection.
- Resolution of 1 mV and 0.1 nA (0.0001 µA).
- Direct reading of semiconductor forward voltages at 5 different currents.
- Resistance measured up to 20 MΩ.
- 1% of reading accuracy.

Operation from replaceable battery or AC adaptor.  
Industry standard 10 MΩ input impedance.

### Compare it with an analogue meter!

The PDM35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter - and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

### Technical specification

#### DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading 1.0% ± 1 count.

Note: 10 MΩ input impedance.

#### AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

#### DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

#### Resistance (5 ranges)

Range: 1 Ω to 20 MΩ.

Accuracy of reading: 1.5% ± 1 count.

Also provides 5 junction-test ranges.

**Dimensions:** 6 in x 3 in x 1½ in.

**Weight:** 6½ oz.

**Power supply:** 9 V battery or Sinclair AC adaptor.

**Sockets:** Standard 4 mm for resilient plugs.

**Options:** AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

### The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts - from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

### Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.


To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.		PE/ 2
Please send me _____ (qty) PDM 35(s)		
@ £32.35 (incl. VAT) each.....	£.....	Name.....
_____ (qty) De-Luxe carrying cases		
@ £3.24 (incl. VAT) each.....	£.....	Address.....
_____ (qty) AC adaptor(s) for 240V		
power @ £3.24 (incl. VAT) each.....	£.....	
Post and packing (please add).....	£0.65	
I enclose cheque/PO made payable to Sinclair Radionics Ltd for (indicate total amount).....		
I understand that if I am not completely satisfied with my PDM 35, I may return it within ten days for full cash refund.		
		<h1>sinclair</h1>
World leaders in fingertip electronics		

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

## STEREO PRE-AMPLIFIERS

MC 1

CPR 1

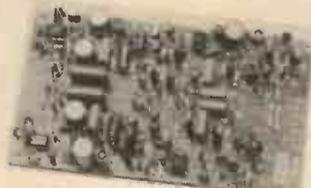

### CPR 1 – THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/μs; T.H.D. 20Hz – 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 x 80 x 20mm. Supply to be ±15 volts.

### MC 1 – PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

### REG 1 – POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

### POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms, T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

### POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).
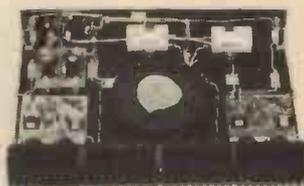
## POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



### POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-035v	£16.30
CE 1004 100W/4 ohms 35-0-35v	£19.22
CE 1008 100W/8 ohms 45-0-45v	£23.22
CE 1704 170W/4 ohms 45-0-45v	£29.12
CE 1708 170W/8 ohms 60-0-60v	£31.90

### TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004	£14.47
CPS2 for 2 x CE 1004 or 2/4 x CE 608	£16.82
CPS3 for 2 x CE 1008 or 1 x CE 1704	£17.66
CPS4 for 1 x CE 1008	£15.31
CPS5 for 1 x CE 1708	£22.68
CPS6 for 2 x CE 1704 or 2 x CE 1708	£23.98

### HEATSINKS

Light duty, 50mm, 2°C/W	£1.30
Medium power, 100mm, 1-4°C/W	£2.20
Disc/group, 150mm, 1-1°C/W	£2.85
Fan, 80mm, state 120 or 240v	£18.50
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules.	£29.16

### THERMAL CUT-OUT, 70°C

	£1.90
--	-------

### POWER AMP KIT

£32.40

### PRE-AMPS:

These are available in two versions – one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1 £29.49 CPR1S £39.98

MC1 £18.50 MC1S £29.49

### POWER SUPPLY:

REG1 £6.75 TR6 £1.75

### BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module.

BD1 £5.40

## CRIMSON ELEKTRIK

1A STAMFORD STREET,

LEICESTER LE1 6NL

Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra. £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information.

Distributor: Miric Teleproduktter, Box 12035, S-750 12 Uppsala 12, Sweden.

## LISTEN TO THE SECRET WORLD OF PLANTS

As featured on Horizon, Nationwide, Radio & Worldwide Press

First time in the U.K. in Kit Form, the revolutionary concept of a Biological Amplifier & Sound Synthesiser in one unit, the Amazing

## Bio Activity Translator™

- ★ Experience the unique Musical Form of Plants
- ★ Hear the beautiful patterns of sound – created by their natural response
- ★ Compare house plants' reactions to people – with the distinct tunes of those outside
- ★ Easy to operate, internal speaker & batteries

The naturally generated Bio Electric potential across a plant leaf is picked up by 2 carbon foam electrodes. When amplified and filtered, a VCO, VCA and

other exclusive synthesiser circuits are programmed by the control voltage from the plant to produce tracking sequences of notes. These follow in pitch, rhythm and volume the ever changing signal from the plant.

The kit includes 6 I.C.'s, 3 transistors, all high quality components, tinned and drilled fibre glass P.C.B., loudspeaker and comprehensive assembly instructions. Also included is a free case, ready punched, with wooden end cheeks and stick on silkscreened front panel for a really professional finish. Runs on 2 x 4½ volt batteries (not supplied).


**SPECIAL INTRODUCTORY OFFER INCLUDES FREE CASE**  
KIT £19.90 ASSEMBLED AND TESTED £27.50 PRICE INCLUDES P & P AND VAT

Allow 21 days for delivery. Offer extended to January 31st 1979.

**JEREMY LORD SYNTHESISERS, (Dept PE2)**  
52 Becmead Avenue, London SW16 1UQ



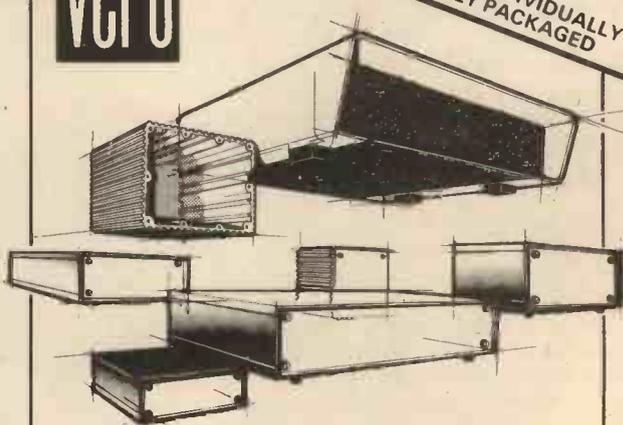OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED



Our new 1978 catalogue lists a whole range of metal cases to house all your projects. And we've got circuit boards, accessories, module systems, and plastic boxes – everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

**VERO ELECTRONICS LTD. RETAIL DEPT.**  
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR  
Telephone Chandlers Ford (04215) 2956

# MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus will present ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas will probably come from readers working on their own microcomputer systems, and payment will be made for any contribution featured here. This is also the place to air your views, in general, on this new technology, so let's be hearing from you!

## ADDING TO SC/MP INSTRUCTION SET

THE CIRCUIT to be described takes advantage of unassigned op-codes in the SC/MP instruction set and uses them to provide 16 one-byte subroutine calls so that effectively 16 one-byte user-defined instructions are added to the instruction set. This feature is especially useful for SC/MP systems since normally seven bytes are needed to set up a subroutine call and this overhead tends to discourage their liberal use.

The existing SC/MP instruction set is shown in Table 1; the first hex digit of each instruction appears down the left-hand edge of the table, and the second hex digit along the top. The circuit, shown in Fig. 1, takes advantage of the fact that the whole of row 2 is blank. When one of these codes is encountered as an instruction the circuit generates an interrupt; an interrupt service routine then determines which of the codes caused the interrupt and jumps to a different section of program for each one.

## CIRCUIT DESCRIPTION

Operation of the circuit is as follows: the SC/MP micro signals when an instruction will be on the data bus by preceding it with a high level on DB5 during the NADS signal. This status signal, called IFLAG, is latched into the D-type latch whose Q output consequently goes high. If during the following instruction-fetch an instruction X'20—X'2F appears on the data bus, the upper four data lines DB7—DB4 will be at '0010' and the output of the 8-input NAND gate will go low.

This output will thus go low when an instruction X'20—X'2F occurs, and not if one of these bytes occurs as an operand to another instruction. This low signal is clocked into a second D-type latch by the NRDS pulse, thus taking SC/MP's SENSE-A input high. Provided that interrupts are enabled in the micro this will generate an interrupt before the next instruction. The net effect of this circuit is that all the op-codes X'20—X'2F behave as if they were the XPPC 3 instruction (X'3F). With more complicated decoding circuitry other gaps in the instruction-set table could be utilized for user-defined instructions.

The circuit was used with a Science of Cambridge MK 14; the earlier MK 14 kits do

	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F				
0	HALT	XAE	CCL	SCL	DINT	IEN	CSA	CAS	NOP											
1										SIO			SR	SRL	RR	RRL				
2																				
3		XPAL					XPAH					XPPC								
		0	1	2	3		0	1	2	3				0	1	2	3			
4	LDE																			
5	ANE																			
6	XRE																			
7	ADE																			
8																			DLY	
9		JMP					JP					JZ					JNZ			
		0	1	2	3		0	1	2	3		0	1	2	3		0	1	2	3
A														ILD						
														0	1	2	3			
B														DLD						
														0	1	2	3			
C		LD					LD@					ST					ST@			
		0	1	2	3		LDI	1	2	3		0	1	2	3		1	2	3	
D		AND					AND @					OR					OR @			
		0	1	2	3		ANI	1	2	3		0	1	2	3		ORI	1	2	3
E		XOR					XOR @					DAD					DAD @			
		0	1	2	3		XRI	1	2	3		0	1	2	3		DAI	1	2	3
F		ADD					ADD @					CAD					CAD @			
		0	1	2	3		ADI	1	2	3		0	1	2	3		CAI	1	2	3

ONE BYTE

TWO BYTE


Table 1. Assignment of the 256 possible codes to instructions in the SC/MP instruction set

not disable the ROMs during NADS so there is a conflict between the contents of the ROMs and status signals such as IFLAG. Fortunately the remedy is simple, and can be implemented using two spare gates in the circuit. It involves breaking a track on the underside of the MK14 circuit board, as shown in Fig. 2(a), and inserting the circuit shown in Fig. 2(b) between the points labelled A and B. MK14 boards which are issue III or later incorporate this modification. In the prototype the circuit, which comprises four packages, was built on a small square of veroboard con-

nected to the underside of the MK14 circuit board by a length of ribbon cable.

## NEW INSTRUCTION PROGRAM

Obviously the assignment of operations to the new op-codes depends on the user's particular application. The program of Fig. 3 shows how the codes can be assigned to different functions: X'20 changes the state of the three flag outputs and X'21 writes a segment pattern to the display, where P1 is assumed to point to the display; the segment pattern to be

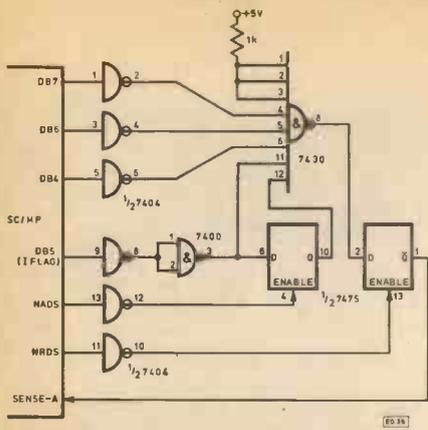

**Fig. 1. Circuit which generates an interrupt when one of the codes X'20-X'F occurs as an instruction**

displayed is taken from the subsequent byte. The remaining codes, X'22-X'2F, are undefined in this example and they behave as NOPs.

The program operates as follows: the address of the user's program minus one is stored at OF1E (high byte) and OF1F (low byte). Instead of starting execution at the beginning of the user's program, one enters at SETUP. This then points P3 to the user's program, enables interrupts, and jumps to the user's program with an XPPC 3. When one of the codes X'20-X'2F is encountered in the user's program an interrupt is generated and this causes a jump to the interrupt service routine, ISR, with the address of the code saved in P3. Thus the value of the code that caused the interrupt can be discovered by loading it using P3-relative addressing. In this example X'20 causes a jump to SRO which inverts the three flag outputs. The code X'21 picks up the second byte and stores it using P1-relative auto-indexed addressing. The user's program at OF80 demonstrates the use of the two new op-codes. It loops around loading P1 with the display address, displaying 'HO' in the rightmost two display positions with two X'21 instructions, and toggling the flags with an X'20 instruction.

```

0000          .=OF1D
OF1E OF1F P3: ASAVE:  .=-+1          ;FOR A-REGISTER
OF1E OF1F P3:         .DBYTE UPROG-1 ;FOR JUMP

OF20 COFD  SETUP: LD      P3          ;GET ADDRESS OF
OF21 37     XPAH  3          ;USER'S PROGRAM.
OF23 COFB  LD      P3+1
OF25 33     XPAL  3
OF26 COFE  RETURN: LD     ASAVE       ;RESTORE A-REG.
OF28 05     TEN   ASAVE            ;ENABLE INTERRUPTS
OF29 3F     XPPC  3          ;JUMP TO USER'S PROG.
OF2A C8F2  ISR:  ST      ASAVE       ;SAVE A-REG
OF2C C300  LD      (3)          ;GET 'OP-CODE'
OF2E B420  XRI    X'20         ;IS IT 20?
OF30 9806  JZ      SRO          ;
OF32 8401  XRI    X'01         ;IS IT 21?
OF34 9808  XRI    SRI          ;
OF36 90E2  JMP     RETURN      ;IGNORE OTHERS

; X'20 CHANGES FLAGS
OF38 06     SRO:  CSA          ;INVERT FLAG BITS
OF39 E407  XRI    7
OF3B 07     CAS
OF3C 90E8  JMP     RETURN


; X'21 DISPLAYS SEGMENT CODE IN NEXT BYTE
OF3E C701  SRI:  LD      @1(3)      ;BUMP P3
OF40 C300  LD      (3)          ;GET SEGMENT CODE
OF42 CD01  ST      @1(1)        ;DISPLAY IT
OF44 90D4  JMP     RETURN

; TEST PROGRAM TO ILLUSTRATE USE
0000 0000  DISP     .=OF80 0000 ;DISPLAY ADDRESS
OF46 0000  UPROG:  LDI    H(DISP)   ;POINT P1 TO
OF48 C400  XPAH  .1          ;DISPLAY ADDRESS.
OF49 31     LDI    L(DISP)
OF4B 31     XPAL  1
OF4D 213F  .BYTE  X'21,X'3F      ;DISPLAY '0'
OF4E 2176  .BYTE  X'21,X'76     ;DISPLAY 'H'
OF4F 20     .BYTE  X'20         ;TOGGLE FLAGS
OF50 90F3  JMP     UPROG        ;LOOP AROUND

0000 .END

```

**Fig. 3. Program for SC/MP which with the circuit of Fig. 1 extends the instruction set**

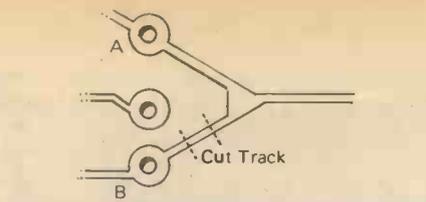

**(a) The track lying between IC8 and IC3 on the underside of the board should be cut as shown**

### SC/MP XPAL O INSTRUCTION

A program in the *Micro-Bus August 1978* demonstrated how a computed goto could be achieved with the M6800 by making use of the great variety of branch-on-condition instructions provided. The following letter, received from N. Feilden of Suffolk, shows how to take advantage of an undocumented SC/MP instruction to achieve a similar effect.

"Hands up all those SC/MP users who have used the instruction XPAL O (X'30). For those who have not, it exchanges the accumulator value with the lower half of the program counter. It thus effects a jump to the location AC+1 with the address from which it came in the accumulator. A subroutine call is thus available anywhere within a 256-byte page without having to set up one of the other pointers. XPAL O can also be used to achieve a computed goto, which makes up for not being able to use the extension register as a displacement in jump instructions. Of course all sorts of wonderful things can be done by writing programs which rewrite themselves, but not in ROM."

The program segment in Fig. 4 shows how a computed goto can be implemented; it jumps to one of four possible addresses for values in the accumulator of 0 to 3.

The corresponding higher-byte instruction XPAH O (X'34) also works but is less useful for obvious reasons. In a larger system it might be useful as a page selector.

```

; COMPUTED GO TO
; INDEX IN ACCUMULATOR
OF34 01     XAE
OF35 02     CCL
OF36 40     LDE
OF37 70     ACE
OF38 F43A  ADI    L(HERE)      ;DOUBLE INDEX
OF3A 30     HERE: JMP     LO     ;ADD TO PC
OF3B 90CC  XPAL  LO           ;PUT IN PC
OF3D 901A  JMP     L1
OF3F 9028  JMP     L2
OF41 L4:    JMP     L2          ;ROUTINES


```

**Fig. 4. Program segment for SC/MP jumps to one of four different labels depending on the value in the accumulator**

### ANALOGUE INFORMATION

If the properties of our environment such as temperature, pressure, light intensity, sound level, frequency, and position, are to be made accessible to a microprocessor system, they must first be converted into the digital form it understands. A new multi-input Analogue-to-Digital (or A/D) conversion chip known as the Data Acquisition System has recently become available, and its incorporation into a microprocessor system would make possible such applications as temperature sensing for household and industrial heating control, interfacing to joysticks for micro-based games and simulations, digitisation of speech waveforms for computer speech recognition and reproduction, and, in general, many machine control and interface applications.

1/2 7400

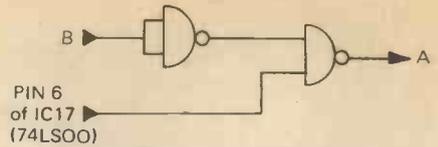

**(b) Two gates should be wired between the points shown**

**Fig. 2 (above). Modification needed to MK14 kits**

### ADC0817 DATA ACQUISITION SYSTEM

National Semiconductor's ADC0817 Data Acquisition System or DAS is a single 40-pin chip incorporating an 8-bit successive approximation A/D converter and a 16-channel analogue multiplexer. It is thus ideal for applications where information must be coordinated from a number of different analogue sources. It was originally designed for the automotive market and is currently being used in the instrument panel circuitry of General Motors' latest Cadillac. The ADC0817 has an accuracy of  $\pm 1$  bit; the ADC0816 is a prime version of the same part with an accuracy of  $\pm \frac{1}{2}$  bit. The multiplexer section is separate from the A/D conversion stage so that it is possible to insert circuitry, such as sample-and-hold, between the two. The ADC0817 is available from Marshall's for £15.63 (inc. VAT).

### INTERFACE CIRCUIT

The DAS can be interfaced directly to an M6800 microprocessor system bus as shown in Fig. 5; it is addressed as a single memory location (\$4000 in this case) and selected by the SELECT input. The required input channel is chosen by writing the channel number to the DAS; the lower four data lines are latched into the multiplexer on the rising edge of the WRITE pulse at the ALE (Address Latch Enable) input. The conversion is begun when the rising edge of the WRITE pulse occurs at the START input. When the conversion is complete EOC is taken high by the DAS and this generates an interrupt on the M6800's IRQ line. Note that EOC is also high for 1-8 clock periods after the rising edge of the START pulse, but this will be ignored. If there are other peripherals generating interrupts in the microprocessor system the EOC flag will have to be taken to the data bus via a tri-state buffer, enabled by a separate address from the DAS, so that it can be interrogated by the micro to determine the source of the interrupt.

The data outputs from the DAS are normally in a high-impedance state, but reading from the DAS takes TSC (Tri-State Control) high and puts the result of the A/D conversion on to the micro's data bus. The DAS is clocked by the M6800's  $\phi_2$  signal; the maximum clock rate permitted is 1.2MHz, giving a conversion time of about 60 microseconds. The circuit should work equally well with micros such as SC/MP and the 8080 which provide NRDS and NWDS signals; these should be inverted to give the READ and WRITE signals in the circuit of Fig. 5.

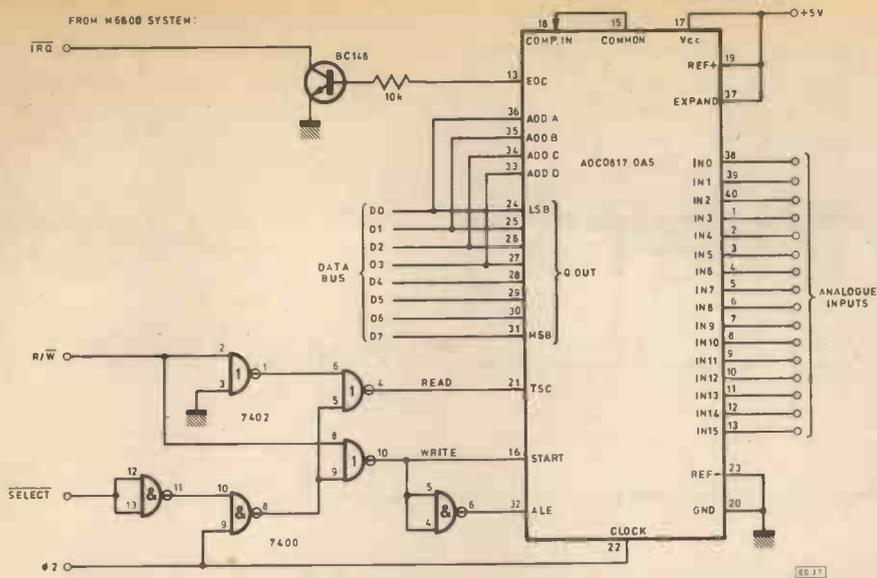


Fig. 5. Interface between a Data Acquisition System chip and an M6800 system

### DAS PROGRAMS

A complete program for the M6800 to drive the DAS circuit just described is given in Fig. 6. The program was developed on a Motorola D2 kit, and gives continuously-updated hexadecimal display of the conversion value, reading from 00 to FF for input voltages of from 0V to +5V. The program

makes use of two display routines in the D2 kit's JBUG monitor and these will have to be provided if the program is to be used with other systems. The first part of the program from \$0000 to \$000E puts the address of the interrupt service routine ISR at \$A000; on interrupts the monitor uses this as a jump address. The first conversion is started by

```

NAM DAS
* DATA ACQUISITION SYSTEM CHIP INTERFACE
4000 DAS EQU $8000
0000 INPUT EQU 0 INPUT CHANNEL (0 - F)
A000 * IN D2 KIT MONITOR:
E0FE IRQVEC EQU $A000 INTERRUPT VECTOR
E31C DISPLA EQU $E0FE DISPLAY ROUTINE
A00C REGST5 EQU $E31C CONVERT HEX TO 2 DIGITS
* INITIALISE DAS FOR FIRST CONVERSION
0000 ORG 0
0000 CE 0010 MAIN LDI $ISR
0003 FF A000 STZ IRQVEC
0005 86 00 LDA A $INPUT
0008 87 0000 STA A DAS SELECT INPUT
000B 0E CLI
000C 7E E0FE JMP DISPLA WAIT FOR INTERRUPT
* DISPLAY INPUT IN HEX (00 - FF)
0010 ORG $0010
0010 86 0000 TSR LDA A DAS
0013 8D E31C JSR REGST5
0016 86 00 LDA A $INPUT
0018 87 0000 STA A DAS START NEW CONVERSION
001B 3B RTI

```

Fig. 6. Program using interrupts to give a continuous display determined by the voltage at one input of the Data Acquisition System chip

writing the required channel number, 0 in this case, to the DAS; the program then jumps to the display loop in the monitor. This continuously displays the contents of the display buffer \$A00C—\$A011. On interrupts the ISR changes the contents of this buffer so that the latest A/D conversion result is displayed.

The interrupt service routine in Fig. 6 picks up the result of the conversion in accumulator A and the jumps to the subroutine REGST5 in the monitor which separates this into two 4-bit nibbles and puts them into the display buffer for display.

# News Briefs

## '78 AUDIO WRITER IS PE CONTRIBUTOR

THE 1978 Audio Writer Award, sponsored by BASF United Kingdom, has been made to Barry Fox who writes under the pen name of Adrian Hope. Barry's pen name may be known to regular readers but if we tell you that since March 1974 Barry has regularly contributed to P.E. with his column *Patents Review*, he will then be known to all. We have also published a number of special features by him and our next issue carries his article *Binaural Stereo Patents*.

The presentation of a silver tuning fork on mahogany base and a cheque for £300 was made by Charles Mackerras the international conductor. We are sure readers will join us in thanking Barry for his valuable contributions; he is shown below with the award, flanked by Henry Pattinson of BASF (left) and Charles Mackerras.



## NEW OLDE MAGAZINE

IF THE days when you could buy little "lozenge" tins containing cat's whiskers and crystals does more for your imagination than today's conductive foam packs containing I.s.i. chips, then this is the journal for you.

For the first time a magazine is to be launched exclusively for the vintage enthusiast. *Sounds Vintage* will be published bi-monthly, to cater for those interested in a wide field of subjects relating to the sounds of yesterday.

Among the areas covered will be vintage wireless equipment, gramophones and cylinder machines, records and cylinders, vintage amplifiers, pre-war literature. There will also be stories of the pioneers and of companies involved in the manufacture of the hardware and software since the early days.

Other reader attractions will include practical hints on the care, maintenance and restoration of vintage equipment, news from the major auction rooms, news of clubs and societies, reviews of books associated with vintage sound, readers letters and wants, reproduction of vintage advertisements, and anything which will be of value or interest to the collector, dealer or casual enthusiasts of the various aspects of sound reproduction in the days before it became too "electronic".

*Sounds Vintage* will start off as a 32-page A4 presentation, and will be available on subscription only. Top names are lined up for many leading articles and features.

No. 1 was scheduled for publication in mid-January 1979. The annual subscription will be £5.80 inland, £6.80 overseas, postage paid. A special offer is being made for No.1 only, a sample copy at 65p post paid. An illustrated subscription form is available from: Sounds Vintage, 28 Chestwood Close, Billericay, Essex.

# STEREO MIXER

J. P. MACAULAY

Will mix line and dynamic microphone inputs for a stereo image

**M**ANY readers must possess a hi-fi cassette or reel to reel tape recorder which is not used to it's full creative capacity for want of a good mixer. With a mixer one can produce one's own jingles or mix the output from several microphones to better capture the sound of a live performance. Alternatively announcements can be recorded onto a music tape without the tell tale clicks and pops that result from the microphone being plugged in and out.

## CIRCUIT

The circuit of a simple but effective mixer is shown in Fig. 1. Here the input signals are fed into a virtual earth amplifier which will accept both line and dynamic microphone inputs.

Line inputs enter the circuit via the resistors R1, R2 and R3. These form an attenuator with the input pots, VR1, VR2 and VR3.

Microphone inputs are fed directly to the "live" ends of the input pots and the sensitivity here for full output is some 3-5mV. The signals at the slider of the pots is fed to the virtual earth via the resistors R4, R5 and R6.

C1 both isolates the virtual earth amplifier from any d.c. present at the input and defines the -3dB point in the bass region at 10Hz. The virtual earth amplifier employs two transistors in what might be, to some readers, a novel circuit.

TR1 operates in the common emitter mode with a low collector current of about 100 $\mu$ A to minimise noise. The collector of load resistor R9 however is bootstrapped to the emitter of TR2, a *p.n.p.* device. Due to this bootstrapping the voltage gain open loop is around 1,000 times and independent of line variations.

Minimum noise is produced when the base of TR1 sees an input impedance of 600 ohms. This can be conveniently arranged by judicious selection of feedback resistor, R7, so that the virtual earth impedance between the base of TR1 and earth approaches that figure.

R7 and R8 provide overall feedback at both a.c. and d.c. and of course the bias current required by TR1. The gain of this stage has purposely been kept down to 20dB to provide the low noise conditions already described and a reasonable input impedance. In consequence further amplification is required to bring the signal up to a usable level, 350mV.

## SECOND STAGE

This is done by the next stage built around TR3. Again the virtual earth mode is used to define the gain of the stage.

Feedback is applied, and base bias, by the potential

divider R12, R13. The gain is defined by the ratio of R12 to R11. C4 blocks the d.c. from the emitter of TR2.

To maintain stability hefty decoupling is applied to both stages by R15, R16, C3 and C5.

The signal from the collector of TR3 is fed to the master volume control VR4 and from thence to the record input of the tape recorder, via R20. Headphone monitoring is provided on a large number of tape recorders although one can only listen to the actual recording as it is being made on three head machines.

Those that do provide a headphone monitoring facility are usually of inadequate volume to properly hear all the nuances of the recording. This is the reason for the inclusion of such a facility in this mixer. A separate board is used for this part of the circuit and those who would rather rely on the built-in monitoring provided by their recorders can omit this altogether without detriment to the performance of the mixer.

## POWER OUTPUT STAGE

A dual audio amplifier i.c. is used, National Semiconductor's LM377. In this application a heatsink is not required, a relief to anybody that has struggled to solder small pieces of tinplate to the pins of the i.c. whilst praying that the device is not overheating!

Reference to Fig. 1 will show that this stage is again operated in the virtual earth mode. The signal being applied to the inverting input via the d.c. blocking capacitor C8 and R17. Overall feedback is provided by R18.

The bias pin of the i.c. is connected to the non inverting inputs and tied to a.c. earth by C7. (The numbers in brackets refer to the corresponding pins on the other channel.)

## Specification

**S/N Ratio -76dB unweighted. 350mV output at master volume control.**

**Max. output before clipping, 3-6V r.m.s.**

**Harmonic distortion—none audible up to max. output!**

**Frequency response -3dB 10Hz-30kHz.**

**Line sensitivity 100mV.**

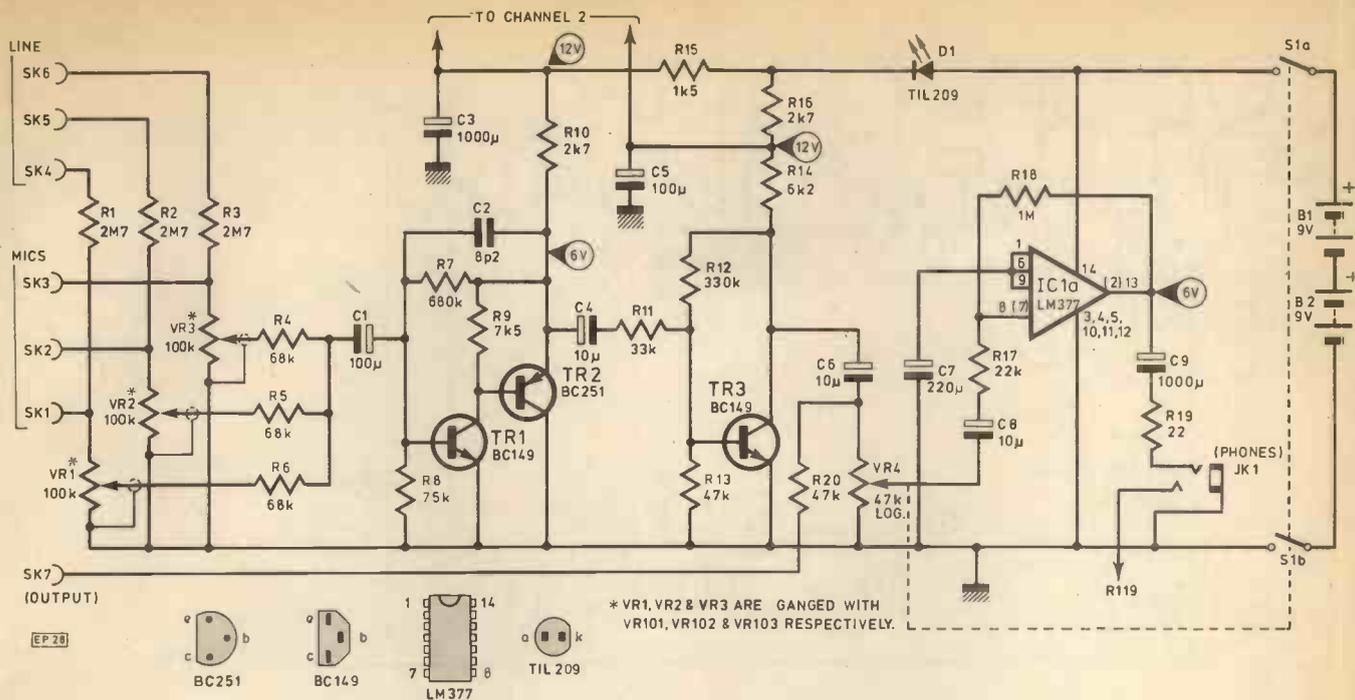


Fig. 1. Circuit of one channel of mixer

The output signal is fed to the headphones by both C9 and R19. One of the design considerations was portability. To enable the unit to be used in difficult locations, that is when only one mains socket is available, the unit is battery operated. This is no hardship however since the current consumption is quite low, the prototype takes only 12mA under quiescent conditions and around 30mA when the headphones are being driven hard. Two PP9s provide many hours of continuous use. Larger capacity batteries can be easily accommodated in the chassis space available.

### CONSTRUCTION

Construction begins with the wiring of the boards. The layout of both is shown (Figs. 2-3). Little comment is required on this although care must be exercised to ensure that the semiconductors and electrolytics are correctly orientated.

The boards are lifted clear of the case by means of 6BA screws and nuts and the constructor must ensure that the breaks in the Veroboard tracks near these are properly made or the circuit will not function.

## COMPONENTS

### Resistors (2 required except where asterisked)

R1, R101	2M7
R2, R102	2M7
R3, R103	2M7
R4, R104	68k
R5, R105	68k
R6, R106	68k
R7, R107	680k
R8, R108	75k
R9, R109	7k5
R10, R110	2k7
R11, R111	33k
R12, R112	330k
R13, R113	47k
R14, R114	6k2
*R15	1k5
*R16	2k7
R17, R117	22k
R18, R118	1M
R19, R119	22
R20, R120	47k
All ½W carbon 10%	

### Potentiometers

VR1, VR101	100k lin. dual gang
VR2, VR102	100k lin. dual gang
VR3, VR103	100k lin. dual gang
VR4, VR104	47k log. + d.p. switch

### Semiconductors

TR1, TR101	BC149
TR2, TR102	BC251
TR3, TR103	BC149
*IC1	LM377
*D1	TIL209

### Capacitors

C1, C101	100µ elect. 10V
C2, C102	8p2 silver mica
C3, C103	1,000µ elect. 25V
C4, C104	10µ elect. 25V
C5, C105	100µ elect. 16V
C6, C106	10µ elect. 16V
C7, C107	220µ elect. 16V
C8, C108	10µ elect. 16V
C9, C109	1,000µ 25V

### Miscellaneous

Stereo headphone jack socket, 14 phone sockets  
Aluminium case 11 x 7½ x 3½in  
4 knobs, 5 x 2½in Veroboard, 1¼ x 2in Veroboard


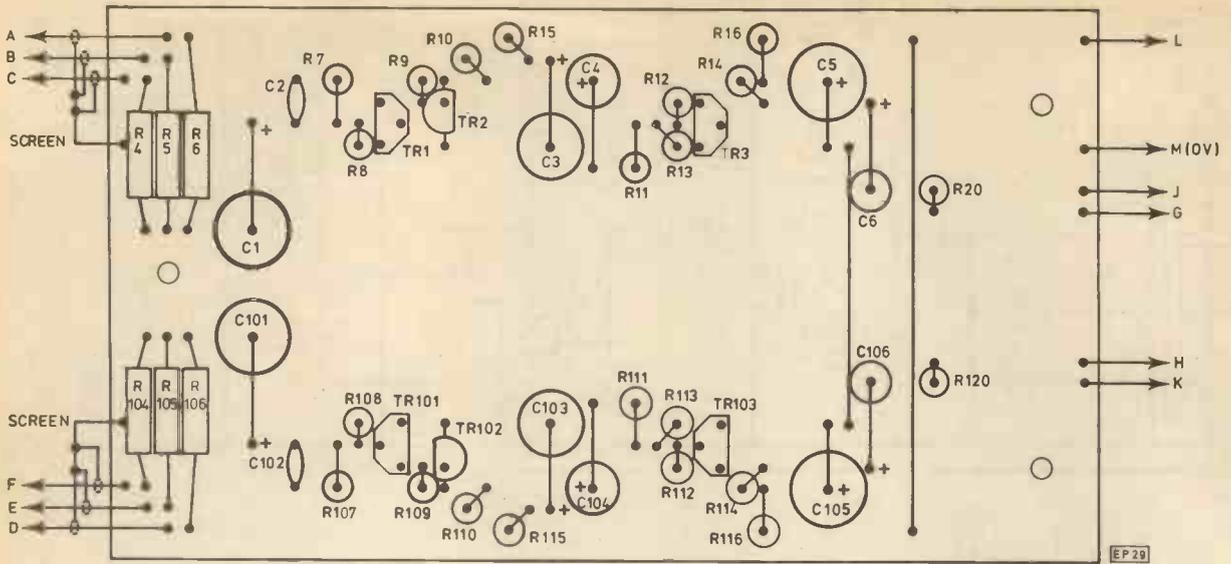


Fig. 2. Main board showing two channel transistor assembly

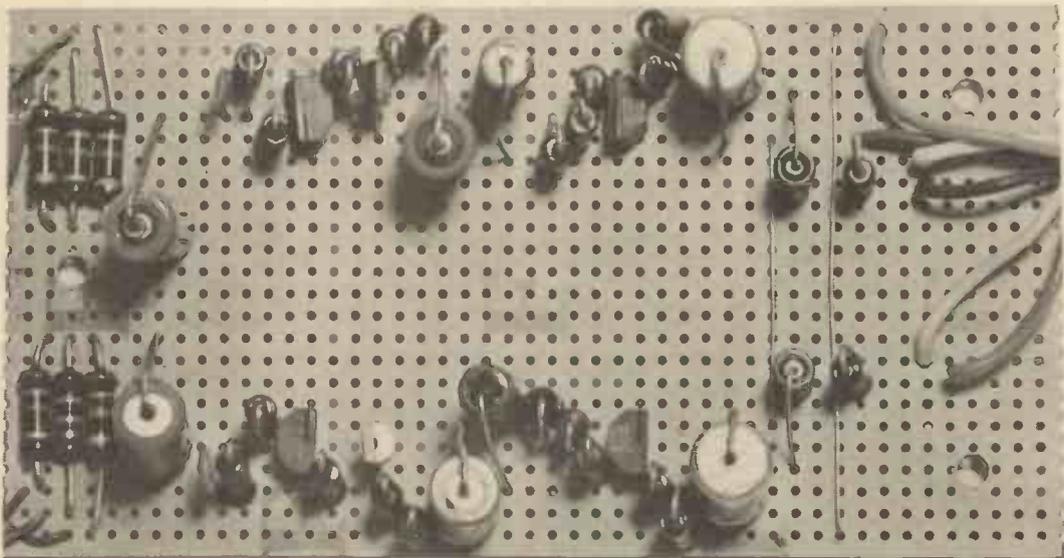




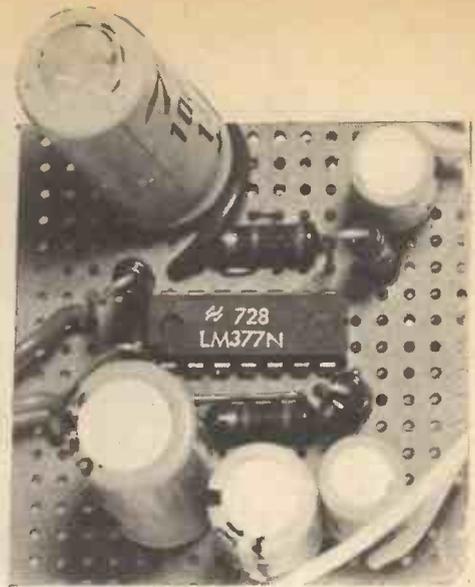
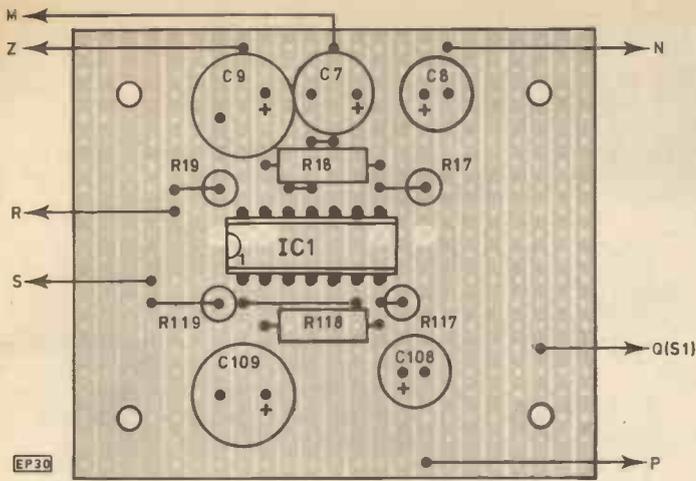


Fig. 3. I.c. power stage

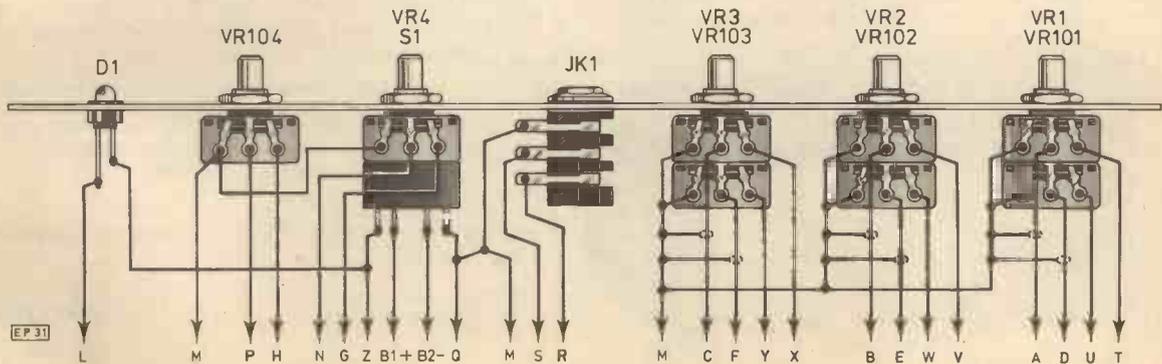

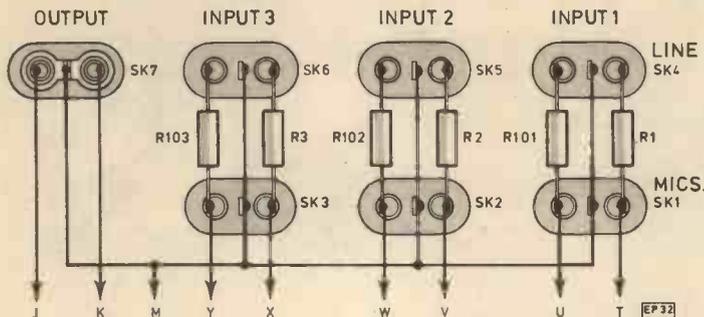(Left). Chassis interior showing board placement (Below). Wiring to control panel components. All lettered flying leads refer to the main board and the headphone amplifier board



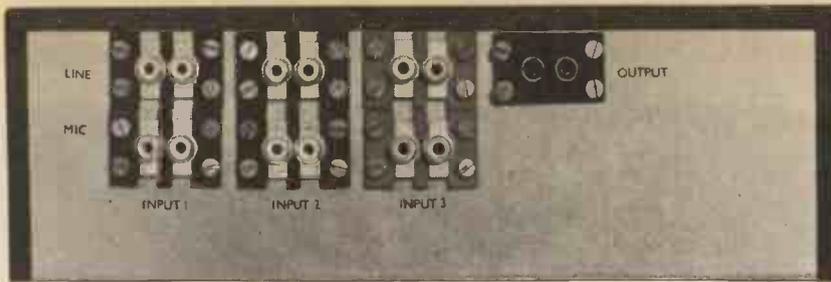

Showing phono socket assembly at rear panel for line and microphone inputs and mixer output. Note that the attenuator resistors are wired directly at the input sockets for all channels

### CASE

No case drilling details are shown as photographs make this quite straight forward. Readers will notice that rotary pots are used instead of the more usual slide types. The reason for this is that the latter tend to be more prone to the ingress of dirt and in consequence become sticky and noisy in use.

Needless to say, dual slide pots could be used but the layout of the case must be altered to suit. In practise, rotary controls are as simple and accurate as the linear slide type.

Linear pots are used at the input because they are better matched than logarithmic types, usually to within 1dB. Due to the inherently close tolerance between tracks of the input pots, overall balance is obtained by the manipulation of the master volume controls.

### LEGENDS

Legends are applied to the case with Letraset "magic lettering". These are clearly indicated for the front and rear panels in the photographs.

This should be fixed with either a proprietary varnish spray or alternatively clear nail varnish. The choice of control knob is, of course, a matter of personal choice although experience shows that a knob with a large diameter, say 1in, with a pointer is best. Push on types are less bothersome than the grub screw fitting types, and tend to be less expensive.

Once the case has been drilled the boards should have the necessary flying leads soldered in place and then mounted in

their respective positions. The pots, i.e.d. and sockets are then mounted. Finally the flying leads are connected to their destinations. At this point the wiring should be thoroughly checked. When satisfied that all is well connect the batteries, headphones and signal sources. Switch on and check the action of the controls. A final check that the voltages shown in Fig. 1 are present  $\pm 1V$  and the mixer is ready for use. ★



# PE

## A Volume of Practical Know-how

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At **£2.85** inc. VAT and postage (£3.45 overseas) they are obtainable from:

Post Sales Department, IPC Magazines Ltd.  
Lavington House, 25 Lavington Street  
London SE1 0PF

I enclose P.O./cheque value ..... for ..... binders at **£2.85** each (£3.45 overseas) for *Practical Electronics* Vol. No's .....

Name .....

Address .....

Date .....

# PE


# FREE!

## IN NEXT MONTH'S ISSUE



## TANDY CATALOGUE

(U.K. Mainland sales only)

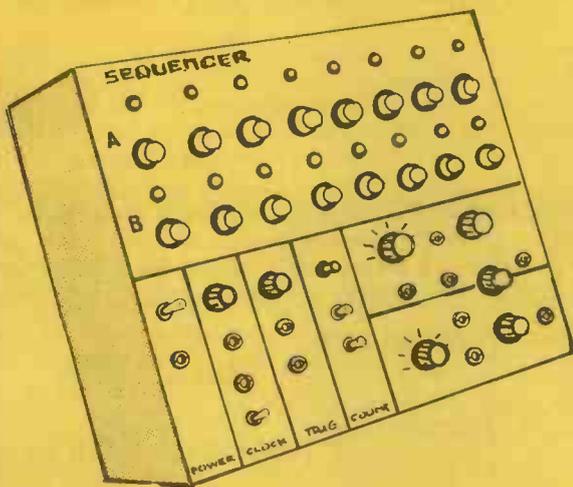


## 16 NOTE SEQUENCER

Enables the user of a synthesiser to program in voltage patterns to provide repeated melodies, rhythm accompaniments etc., which can be manipulated for speed and key change.
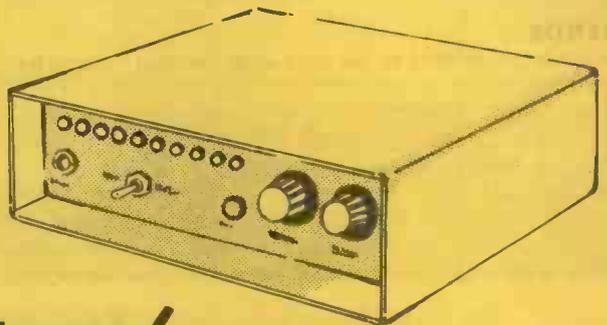
## LOGISCOPE

In addition to indicating whether a test point is at logic 1, logic 0, floating or pulsing this tester will provide information about the mark space ratio and the frequency of the input signal.



*Plus regular features!*

PRACTICAL

# ELECTRONICS

OUR MARCH ISSUE WILL BE ON SALE FRIDAY 9 FEBRUARY 1979



# BOOK REVIEWS

## MICROPROCESSOR PROGRAMMING FOR COMPUTER HOBBYISTS

By Neill Graham

Published by Tab Books

Available from W. Foulsham, 837 Yeovil Rd.,  
Slough, Bucks.

378 pages. Price £6.50

**T**HE problem with books about microprocessors is that the author either concentrates on one specific device and loses readers not interested in it, or else, as in many books on the subject currently available, devotes part of the book to a discussion of different devices being manufactured; this usually turns out to be a very expensive way of buying the manufacturers' data.

In this book Mr Graham overcomes this problem by giving programming examples in a high-level language, namely PL/M, and one section is devoted to describing its features. The routines given to illustrate the techniques presented in the remainder of the book can thus be converted from PL/M to any specific assembly language.

The subjects covered include: floating-point arithmetic, input, and output; pseudo-random number generators; manipulation and use of data structures including arrays, strings, stacks, queues, deques, chains, and trees; and finally, searching, hashing, indexing, and sorting methods. Within these sections the book covers the topics clearly, if a little briefly, and the use of data structures is illustrated with a number of clear diagrams.

Though prior familiarity with a high-level language like PL/1, on which PL/M is based, might be an advantage in understanding the examples, the book should be a valuable source for the microprocessor programmer. D.J.D.

## COMPETITION

**T**HE free entry competition we ran at Breadboard attracted a large entry and guesses at the number of projects published in P.E. from the December 1976 issue to December 1978 inclusive ranged from 2 to 2,000. The correct answer was 94. No one guessed this figure correctly but we had many with 93 and 95.

The winner eventually selected was Mr B Wallington of Chatham. He receives a P.E. VDU System (presented by Technomatic), and a year's supply of P.E.

The ten runners up were: A. C. Walkland (Liverpool), J. Green (London W.14), J. D. Parker (Buckhurst Hill), M. Davis (Nuneaton), P. D. Bond (South Godstone), J. Jones (Birmingham), Yan Lee (Tipton), M. Browne (Fleet), M. W. Keen (Bridgend), J. N. Jones (Basingstoke), each will receive a year's supply of P.E.

Two extra runners up prizes have been awarded to Mr. C Wysocki (London W9) and Dr. R. D. Bailey for their original "slogans". These were: "I think P.E. is to electronics magazines what St Michael is to underwear", and "I think P.E. is worth your trouble and my money". Well Dr. Bailey you can save your money for the next year, your copies will be sent by us. Our thanks to all those who participated, especially the staff of other magazines for their constructive comments!

## BREADBOARD EXHIBITION

**T**O all our readers who visited our stand at Breadboard, we are sorry that our technical staff were prevented from being there to demonstrate equipment and answer queries. This was due to an N.U.J. dispute within the I.P.C. Magazines Group. Thankfully the dispute has not affected P.E.s publication dates and is now over.

## POINTS ARISING

### R.C. MOTOR CONTROL (DECEMBER 1978)

The left hand side of Link-2 shown on the component overlay should connect to the junction of R13 and D5. This requires an extra p.c.b. pad at R13, and a longer link to clear the track running underneath.

# readout

## ... a selection from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope.

Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

### Of Bees And Keys

Sir—Congratulations to you and the authors on the CHAMP project. This ranks as perhaps the most exciting project to have been published in "Practical Electronics" for years. I have just had a very absorbing time in programming CHAMP to play the "Flight Of The Bumble Bee" (over 800 notes) using less than 512 program instructions, and look forward to other equally challenging problems.

The only criticism I have is that the authors use a keyboard which is apparently not readily obtainable. Readers may be interested to know that a good, robust, cheap hex keyboard can be obtained from Chiltmead Ltd, Arthur Rd, Reading. It is, however, somewhat too large to fit into the space allocated, but can nevertheless be accommodated by repositioning a few of the switches. The keyboard encoder and digit drivers can be mounted on a piece of Veroboard under the sloping panel at its top. The ground and 5V leads can then run to the terminals at the

front, and the ribbon cable to the main board need only be 16 wires, which is more convenient than 18. This cable can run through a rectangular hole in the chassis symmetrically placed with respect to the other cable hole. This arrangement seems to me to be neater than that described in the original article.

W. Gough  
Cardiff.

## EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p

★ As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions. Size approx 20" x 11" x 9 1/2" **£28.00** Per stereo pair + £5.00 p&p



**BSR** Manual single play record deck with auto-return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use. **OUR PRICE £10.95** p&p £2.55

### TURNTABLE BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck **£26.95**

GARRARD SP25 MKIV Deck with Shure head **£25.95**

Plinth and cover for BSR decks **£6.00**

### BARGAINS FOR PERSONAL SHOPPERS

PORTABLE STEREO RADIO CASSETTE RECORDER UNREPEATABLE



MW, LW, SW and Stereo VHF. 6 watts output Battery/Mains operation. 160 16 VOLT MAINS TRANSFORMER. 2 1/2 amp.

**£69.95**

**£2.50**

BSR Record auto deck on plinth with stereo cartridge ready wired. LED 5 function men's digital watch stainless steel finish. LCD 5 function men's digital watch stainless steel finish.

**£11.95**

**£5.95**

**£6.95**

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish.

**£13.95**

POCKET CALCULATOR. With LED display, memory and percentage key.

**£2.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

**£11.95**

125 Watt Power Amp Module

**£13.95**

Mains power supply for above unit.

**£3.50**

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/2" x 14 1/2" x 7 1/4" approx.

**£5.95**

MULLARD Built power supply

**£1.50**

DECCA DC 1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads.

**£2.95**

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers

**£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation

**£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock

**£41.95**

LW, MW, SW, VHF mains/Battery operation. 7" TAPE TRANSPORT Mechanism—a selection of models from

**£8.95**

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP 11 type batts. Size 3 3/4" x 1 1/4" x 2" approx.

**£7.50** p&p £1.50p



AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vo, On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary selection switch.

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz (150mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ± 1dB

Radio FM sensitivity for 3dB below limiting better than 10 uV

AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre Size approx length 16" x height 2 1/4" x depth 4 1/4"

240 Volts AC Complete with Circuit diagram. **£19.95** p&p £2.55

# Mullard

## AUDIO MODULES IN BARGAIN PACKS

### CURRENT CATALOGUE

PRICE & AT OVER **25** PER PACK

### SEE OUR PRICES

**1** PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £4.95** p+p £1.00

**2** PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE £7.45** p+p £1.00



## GARRARD BARGAIN

LIST PRICE ~~£95.00~~ **OUR PRICE £39.95**

86 SB MKII. Belt drive, 2 speed turntable module with plinth and cover.



ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.

### ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00 p+p**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. **£1.95** p+p 50p **95p**



### 20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers. **£29.90** + £2.50 p&p

**SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY**

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

**£23.00** + £2.50 (NOTE Cabinet not available separately.) **£29.00** + p&p £2.50 complete with cabinet.

**SPECIAL OFFER Complete with 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS**

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3 1/4" approx. tweeters and crossovers. **£49.00** + p&p £4.00

**BUILT AND READY TO PLAY 39.00** + p&p £2.50



323 EDGWARE ROAD, LONDON W2  
21D HIGH STREET, ACTON W3 6NG

ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at 1.12.78 and subject to change without notice.

### 50 WATT MONO DISCO AMP

**£29.95** P&P £2.50

Size approx. 13 1/2" x 5 1/4" x 6 3/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. **SPECIAL OFFER.** The above 50 watt amp plus 4 Goodmans Type 8P. 8" speakers. Package price **£45.00 + £4.00 P&P.**

### 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls. Five vertical slide controls master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **100 watt £57** p & p **£4.00** **100 watt £65**

## STEREO CASSETTE TAPE DECK ASSEMBLY

Consisting of ready built tape transport system/mechanism, mated to the electronics. Unit is ready built for installing into cabinet of own choice. Features include pause control, solenoid assisted auto-stop, 3 digit tape counter, belt driven balanced fly wheel by DC motor with electronic speed control, twin VU meters. Specification Power Output, more than 0.5v, mic -65dB 10K Hz, DIN -47dB 100K Hz. Track-2 channel stereo record play-back, Tape speed 4.8cm/sec. Freq. response 50.1200 Hz signal to noise ratio 42dB Recording system AC bias Erasing system AC erase Bias freq. 57KHz. Compatible for both normal and chrome dioxide tapes. Size of mechanism only 4 1/4" x 6 3/4" x 11 1/4" approx. included a moulded top-plate as illustrated. **£25.00** P&P £2.50

Opt. extras: Mains transformer to suite **£2.50 + £1 p & p.**

# Marshall's Electronics




A. Marshall (London) Ltd., Dept. PE, Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 8005  
 Retail Sales London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Road, W2. Tel: 01-723 4242.  
 Glasgow: 85 West Regent Street, G2 2OD. Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, B516 2LX. Tel: 0272 654201.

TRANSISTORS																									
2N696	0.30	2N2219	0.38	2N397	0.18	2N4062	0.20	2N5247	0.44	40410	0.82	BC2148	0.17	BC549B	0.14	BD244A	0.70	BF182	0.37	BF89B	1.37	MJE520	0.50		
2N697	0.31	2N2219A	0.39	2N398	0.18	2N4063	0.20	2N5248	0.44	40411	0.82	BC2149	0.17	BC549C	0.15	BD244B	0.67	BF183	0.44	BF950	0.27	MJE521	0.70		
2N698	0.49	2N2220	0.39	2N3440	0.75	2N4074	2.65	2N5294	0.44	40594	0.87	BC147	0.13	BC182B	0.13	BC2141	0.18	BC557	0.14	BD245A	0.89	BF184	0.41	BF951	0.27
2N699	0.58	2N2221	0.26	2N3441	0.87	2N4121	0.27	2N5295	0.44	40595	0.88	BC147B	0.13	BC182C	0.15	BC2142	0.18	BC558	0.13	BD245B	0.85	BF185	0.37	BF952	0.27
2N700	0.30	2N2221A	0.25	2N3442	1.05	2N4122	0.27	2N5296	0.44	40673	0.80	BC148	0.13	BC182A	0.15	BC2143	0.18	BC559	0.16	BD246A	0.72	BF194	0.16	BF950	0.35
2N700A	0.30	2N2222	0.25	2N3638	0.17	2N4123	0.19	2N5298	0.44	40689	1.30	BC148B	0.13	BC182B	0.15	BC2144	0.18	BC560	0.17	BD246B	0.93	BF195	0.16	BR101	0.55
2N700B	0.30	2N2222A	0.25	2N3638A	0.17	2N4124	0.19	2N5447	0.16	AC128	0.48	BC148C	0.13	BC183	0.12	BC2145	0.18	BC561	0.17	BD433	0.44	BF196	0.16	BR101	0.55
2N718	0.30	2N3689	0.27	2N3702	0.14	2N4125	0.19	2N5448	0.16	AC127	0.48	BC149	0.15	BC183A	0.12	BC2146	0.18	BC562	0.17	BD434	0.44	BF197	0.16	BR101	0.55
2N718A	0.30	2N3689A	0.27	2N3703	0.14	2N4126	0.19	2N5449	0.16	AC128	0.48	BC149C	0.15	BC183B	0.13	BC2147	0.18	BC563	0.17	BD435	0.44	BF198	0.16	BR101	0.55
2N720A	0.85	2N2846	0.80	2N3704	0.14	2N4204	2.38	2N5457	0.38	AC151	0.43	BC157A	0.15	BC183C	0.13	BC2148	0.18	BC564	0.17	BD436	0.44	BF199	0.16	BR101	0.55
2N722	0.65	2N2847	1.55	2N3705	0.14	2N4205	2.32	2N5458	0.35	AC152	0.54	BC158A	0.15	BC183D	0.15	BC2149	0.18	BC565	0.17	BD437	0.44	BF200	0.16	BR101	0.55
2N727	0.50	2N2903	1.00	2N3706	0.14	2N4207	2.22	2N5459	0.32	AC153	0.59	BC158B	0.15	BC183E	0.15	BC2150	0.18	BC566	0.17	BD438	0.44	BF201	0.16	BR101	0.55
2N914	0.38	2N2904	0.31	2N3707	0.14	2N4208	2.22	2N5460	0.35	AC153A	0.59	BC158C	0.15	BC183F	0.15	BC2151	0.18	BC567	0.17	BD439	0.44	BF202	0.16	BR101	0.55
2N916	0.33	2N2904A	0.31	2N3708	0.12	2N4209	2.22	2N5464	0.37	AC176K	0.70	BC159B	0.17	BC183G	0.15	BC2152	0.18	BC568	0.17	BD440	0.44	BF203	0.16	BR101	0.55
2N917	0.38	2N2905	0.31	2N3709	0.12	2N4210	2.20	2N5485	0.40	AC178	0.54	BC160	0.38	BC184	0.12	BC200	0.43	BC138	0.41	BD535	0.70	BF245A	0.44	BQ208	2.40
2N918	0.45	2N2905A	0.31	2N3711	2.16	2N4348	2.85	2N5486	0.40	AC187	0.59	BC181	0.38	BC184B	0.13	BC201	0.43	BC139	0.43	BD536	0.70	BF245B	0.44	BQ209	2.70
2N920	0.35	2N2906	0.25	2N3712	2.20	2N4349	2.88	2N5489	0.44	AC187K	0.65	BC182	0.13	BC184C	0.13	BC202	0.37	BD140	0.43	BD537	0.74	BF257	0.35	BQ210	2.70
2N923A	0.37	2N2906A	0.25	2N3713	1.15	2N4349	2.88	2N5492	0.44	AC188	0.54	BC187B	0.13	BC184D	0.15	BC203	0.54	BD181	1.00	BD538	0.77	BF258	0.35	ME401	0.22
2N930A	0.37	2N2907	0.26	2N3719	0.36	2N4320	0.83	2N5494	0.65	AC188K	0.65	BC188A	0.13	BC184B	0.15	BC207	0.18	BD182	2.20	BD539	0.60	BF259	0.35	ME402	0.22
2N930A	0.95	2N2907A	0.25	2N3820	0.39	2N4321	0.54	2N5496	0.67	AD181	1.00	BC188B	0.13	BC184C	0.15	BC207A	0.18	BD183	2.36	BD540	0.60	BF338	0.42	ME404	0.17
2N1171	0.30	2N2923	0.17	2N3821	0.96	2N4322	0.60	2N6027	0.64	AD182	1.00	BC188C	0.13	BC212	0.15	BC307B	0.16	BD187	0.95	BDX14	1.32	BF337	0.49	ME401	0.22
2N1889	0.30	2N2924	0.17	2N3900	0.28	2N4323	0.75	2N6107	0.45	AF106	0.60	BC189B	0.13	BC212A	0.15	BC308	0.16	BD235	0.46	BDX18	1.90	BF338	0.52	ME404	0.22
2N1890	0.30	2N2926	0.19	2N3901	0.20	2N4324	1.15	2N6108	0.55	AF109	0.52	BC189C	0.13	BC212B	0.15	BC308B	0.16	BD236	0.44	BDY20	1.10	BF339	0.52	ME401	0.16
2N1893	0.30	2N2927	0.17	2N3903	0.20	2N5085	0.60	2N6109	0.55	BC107	1.60	BC177	0.22	BC212L	0.18	BC309A	0.16	BD237	0.44	BDY55	0.90	BF340	0.52	ME402	0.16
2N1902	0.50	2N3053	0.25	2N3904	0.18	2N5087	0.30	2N6111	0.49	BC107A	0.16	BC177A	0.22	BC212LA	0.18	BC309B	0.16	BD238	0.44	BDY56	0.90	BF341	0.52	ME403	0.16
2N1912	0.58	2N3054	0.22	2N3905	0.18	2N5088	0.30	2N6121	0.41	BC107B	0.16	BC177B	0.25	BC212LB	0.18	BC309C	0.16	BD239A	0.44	BF115	0.39	BF879	0.30	ME410	0.11
2N1913	0.60	2N3055	0.25	2N3906	0.18	2N5089	0.30	2N6122	0.44	BC108	0.18	BC178	0.22	BC213	0.15	BC327	0.22	BD239C	0.59	BF180	0.33	BF880	0.30	ME410	0.11
2N1913A	0.52	2N3056	0.50	2N4031	0.55	2N5180	0.85	2N6123	0.48	BC108A	0.16	BC178A	0.25	BC213A	0.15	BC328	0.20	BD240A	0.49	BF181	0.65	BF881	0.30	ME410	0.11
2N1914	0.42	2N3057	0.40	2N4032	0.65	2N5191	0.75	2N6124	0.45	BC108B	0.16	BC178B	0.25	BC213B	0.15	BC337	0.20	BD240C	0.55	BF187	0.37	BF828	0.34	ME411	0.11
2N1914A	0.45	2N3058	0.45	2N4033	0.72	2N5192	0.80	2N6125	0.47	BC108C	0.17	BC178C	0.25	BC213C	0.15	BC338	0.23	BD241A	0.49	BF187	0.37	BF829	0.34	ME411	0.11
2N1915	0.40	2N3059	0.42	2N4034	0.60	2N5193	0.75	40381	0.55	BC109	0.15	BC179A	0.25	BC213L	0.17	BC547	0.17	BD241B	0.49	BF177	0.27	BF834	0.30	ME612	0.22
2N1950A	0.40	2N3093	0.17	2N4058	0.22	2N5194	0.80	40382	0.55	BC109B	0.17	BC179B	0.25	BC213LA	0.17	BC547A	0.17	BD242A	0.55	BF178	0.27	BF835	0.30	MJE295	1.35
2N2217	0.55	2N3394	0.17	2N4059	0.17	2N5195	0.97	40383	1.45	BC109C	0.18	BC179C	0.26	BC213LB	0.17	BC547B	0.13	BD242C	0.62	BF179	0.33	BF836	0.30	MJE340	0.62
2N2218	0.35	2N3395	0.19	2N4060	0.22	2N5245	0.37	40408	0.82	BC140	0.30	BC182	0.12	BC213C	0.17	BC548	0.13	BD243A	0.65	BF180	0.37	BF837	0.35	MJE370	0.62
2N2218A	0.38	2N3396	0.19	2N4061	0.22	2N5246	0.38	40409	0.82	BC141	0.32	BC182A	0.12	BC214	0.17	BC549	0.14	BD243C	0.67	BF181	0.37	BF838	0.35	MJE371	0.62

### LINEAR CIRCUITS

CA3018	0.75	LM379S	4.25	LM7815K	1.75	TA0100	2.00
CA3018A	1.10	LM3808S	0.96	LM7815L	1.75	TA0100	2.00
CA3020	2.20	LM3808L	1.08	LM7815CZ	1.75	TA0100	2.00
CA3020A	2.60						
CA3020B	1.25	LM3814N	1.69				
CA3030	1.50	LM3824	1.32	LM7815CZ	1.75	TA0100	2.00
CA3030A	2.20	LM3848	1.85				
CA3030B	2.90	LM3858	1.50	MMS5314	4.60	TA0100	2.00
CA3030A	4.10	LM3871N	1.10	MMS5316	4.60	TA0100	2.00
CA3045	1.55	LM3881N	1.00	NE555	0.33	TA0100	2.00
CA3046	0.77	LM3891N	1.00	NE556	0.85	TA0100	2.00
CA3048	2.45	LM702C	0.81	NE558N	1.98	TA0100	2.00
CA3052	1.78	LM709	0.70	NE560	4.50	TA0100	2.00
CA3060	0.85	LM709B	0.50	NE561	2.70	TA0100	2.00
CA3080A	2.10	LM7104	0.49	NE582	4.50	TA0100	2.00
CA3086	0.50	LM710	0.67	NE586	1.39	TA0100	2.00
CA3088B	1.87	LM7101A	0.64	NE586	1.78	TA0100	2.00
CA3089B	2.90	LM7112C	0.72	NE567	1.90	TA0100	2.00
CA3090	4.40	LM723C	0.75	NE571N	4.95	TA0100	2.00
CA3130	1.06	LM723C14	0.45	SAS580	2.70	TA0100	2.00
CA3140	1.04	LM741	0.70	SAS570	2.70	TA0100	1.30
LM3001	0.30	LM741C	0.30	SAJ110	2.10	TA0100	1.30
LM3007N	0.50	LM741C14	0.30	SO41P	1.35	TA0100	2.80
LM3008N	0.95	LM747CN	0.99	SO42P	1.25	TA0100	2.90
LM3093K	1.85	LM7488	0.50	SN76001N	TC4016	2.56	
LM317K	3.35	LM74814	0.90		1.30	TA0100	2.35
LM318N	2.45	LM7491	0.50	SN76003N	TC4070	4.50	
LM3202S	2.15	LM1304A	1.52		2.36	TA0100	4.50
LM32021S	2.15	LM1305M	1.20	SN76013N	TC4740	4.50	
LM32021S	2.15	LM1307N	1.22		1.50	TA0100	3.00
LM32024	2.15	LM1310M	2.10	SN76023N	TC4760	2.00	
LM3202S	1.15	LM1351N	1.30		1.50	TA0100	1.49
LM32021S	1.15	LM1458N	0.45	SN76033N	TC4440	1.65	
LM32021S	1.15	LM1498N	0.97		2.35	TA0102	7.50
LM32024	1.15	LM1808M	2.10	TA0263	1.35	TA0102A	1.75
LM323K	6.95	LM1812N	6.20	TA0264	3.70	TA0103A	4.24
LM3339A	0.60	LM1820N	1.16	TA0265A	1.16	TA0202AD	0.60
LM34015	0.88	LM1828N	1.30	TA0266	1.30		

# This Is The Famous

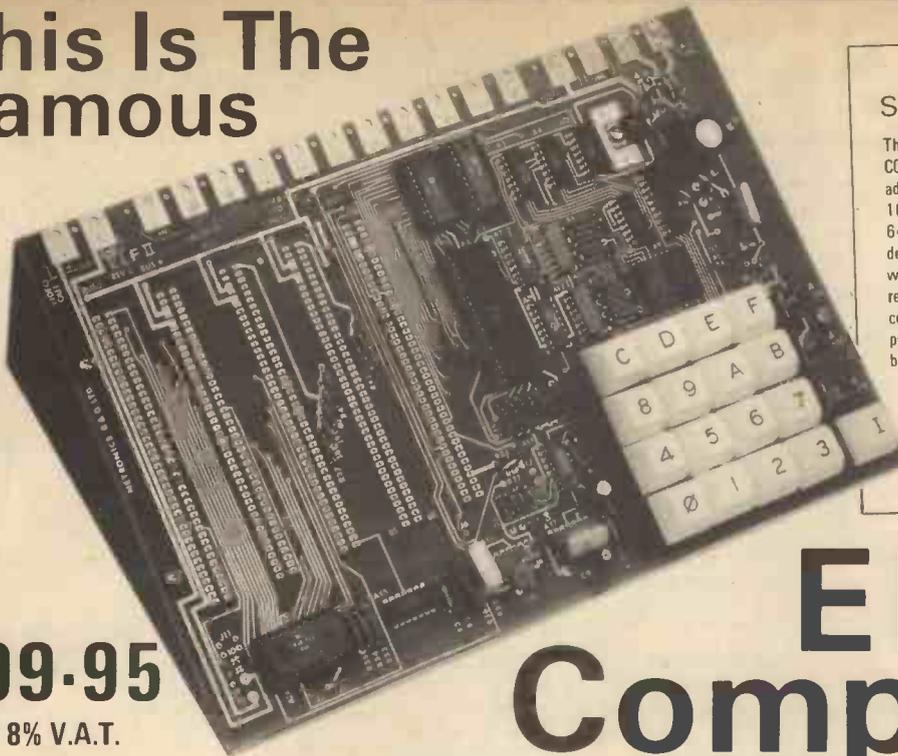

## SPECIFICATIONS

The £99.95 ELF II computer features an RCA COSMAC COS/MOS 1802 8-bit microprocessor addressable to 64K bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM expandable to 64K bytes, professional hex keyboard fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion bus (less connectors), stable crystal clock for timing purposes and a double-sided, plated-through pc board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with all the logic and support circuitry you need to learn every one of the RCA 1802's capabilities.

**£99.95**  
PLUS 8% V.A.T.

# ELF II Computer

Stop reading about computers and get your hands on one! With ELF II and our new *Short Course* by Tom Pittman, you can master computers in no time at all! ELF II demonstrates all 91 commands an RCA 1802 can execute and the *Short Course* quickly teaches you how to use each of the 1802's capabilities.

ELF II's video output lets you display an alphanumeric readout or graphics on any TV screen or video monitor and enjoy the latest video games.

But that's not all. Once you've mastered computer fundamentals, ELF II can give you POWER with add-ons that are among the most advanced found anywhere. American IEEE chapters plus hundreds of universities and major corporations have chosen the ELF II to introduce their students and personnel to microprocessor computing!

### Learn The Skill That May Soon Be Far More Important Than Your College Degree!

The ability to use a computer may soon be more important to your earning power than a college degree. Without a knowledge of computers, you are always at the mercy of others when it comes to solving highly complex business, engineering, industrial and scientific problems. People who understand computers can command MONEY and to get in on the action, you must learn computers. Otherwise you'll be left behind.

### ELF II Is The F-A-S-T Way to Learn Computer Fundamentals!

Regardless of how minimal your computer background is now, you can learn to programme a computer in almost no time at all. That's because Netronics has developed a special *Short Course on Microprocessor And Computer Programming* in non-technical language that leads you through every one of the RCA COSMAC 1802's capabilities so you'll understand everything ELF II can do... and how to get ELF II to do it!

All 91 commands that an 1802 can execute are explained to you, step-by-step. The text, written for Netronics by Tom Pittman, is a tremendous advance over every other programming book in print.

Keyed specifically to the ELF II, it's loaded with "hands on" illustrations. When you're finished, ELF II and the 1802 will no longer hold any mysteries for you.

In fact, not only will you be able to use a personal computer creatively, you'll also be able to understand computing articles in the technical press.

If you work with large computers, ELF II and our *Short Course* will help you to understand what makes them tick.

### A Dynamite Package For Just £99.95 Plus 8% V.A.T.!

With ELF II, you learn to use machine language - the fundamental language of all computers. Higher level languages such as FORTRAN and BASIC must be translated into machine language before a computer can understand them. With ELF II you build a solid foundation in computers so you'll really know what you're doing, no matter how complicated things get.

Video output also makes ELF II unique among computers selling such a low price. Attached to your TV set, ELF II becomes a fabulous home entertainment centre. It's capable of providing endless hours of fun for both adults and children of all ages! ELF II can create graphics, alphanumeric displays and fantastic video games.

Only a low cost RF modulator is required to connect ELF II to your TV's aerial socket! (To order see below.)

ELF II's 5-card expansion bus (connectors not included) allows you to expand ELF II as your needs for power grows. If you're an engineer or hobbyist, you can also use ELF II as a counter, alarm, lock, thermostat, timer, or for countless other applications.

### ELF II Explodes Into A Giant!

Thanks to ongoing work by RCA and Netronics, ELF II add-ons are among the most advanced anywhere. Plug in the GIANT BOARD and you can record and play back programmes, edit and debug programmes, communicate with remote devices and make things happen in the outside world. Add Kluge Board to get ELF II to solve special problems such as operating a more complex alarm system or controlling a printing press. Add 4k RAM board and you can write longer programmes, store more information and solve more sophisticated problems.

Expanded, ELF II is perfect for engineering, business, industrial, scientific and personal finance and tax applications. No other small computer anywhere near ELF II's low price is backed by such an extensive research and development programme.

The ELF-BUG Monitor is an extremely recent breakthrough that lets you debug programmes with lightning speed because the key to debugging is to know what's inside the registers of the microprocessor and, instead of single stepping through your programme, the ELF-BUG Monitor, utilising break points, lets you display the entire contents of the registers on your TV screen at any point in your programme. You find out immediately what's going on and can make any necessary changes. Programming is further simplified by displaying 24 bytes of RAM with full address, blinking cursor and auto scrolling. A must for serious programmers!

Netronics will soon be introducing the ELF II Colour Graphics & Music System - more breakthroughs that ELF II owners will be the first to enjoy!

### Now BASIC Makes Programming ELF II Even Easier!

Like all computers, ELF II understands only "machine language" - the language computers use to talk to each other. But, to make life easier for you, we've developed an ELF II Tiny BASIC. It talks to ELF II in machine language for you so that you can programme ELF II with simple words that can be typed out on a keyboard such as PRINT, RUN and LOAD.

### "Ask Not What Your Computer Can Do... But What Can It Do For YOU!"

Don't be trapped into buying a dinosaur simply because you can afford it and it's big. ELF II is more useful and more fun than "big name" computers that cost a lot more money.

With ELF II, you learn to write and run your own programmes. You're never reduced to being a mere keypunch operator, working blindly with someone else's predeveloped software.

No matter what your speciality is, owning a computer which you really know how to use is sure to make you a leader. ELF II is the fastest way there is to get into computers. Order from the coupon below!

**H.L. AUDIO LTD., Dept. P.E., 138, KINGSLAND ROAD, LONDON E2 8BY. TEL: 01-739 1582**

**- SEND TODAY!**

### NOW AVAILABLE FOR ELF II -

- Tom Pittman's *Short Course On Microprocessor & Computer Programming* teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language, it's a learning breakthrough for engineers and laymen alike. £5.00\* post paid!
- Deluxe metal cabinet with plexiglas dust cover for ELF II. £29.95\* plus £1.50 p&p.
- RF Modulator for use with TV set. £3.00\* post paid.
- GIANT BOARD kit with cassette I/O, RS 232-C/TTY I/O, 8-bit P I/O, decoders for 14 separate I/O instructions and a system monitor/editor. £39.95\* plus £1.00 p&p.
- Kluge (Prototype) Board accepts up to 36 IC's. £17.00 plus 50p. p&p.
- 4k Static RAM kit. Addressable to any 4k page to 64k. £89.95\* plus 50p. p&p.
- Gold plated 96-pin connectors (one required for each plug-in board). £5.70\* post paid.
- Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, onboard regulator, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer. £64.95\* post paid.
- Deluxe metal cabinet for ASCII Keyboard. £19.95\* plus £1.50 p&p.
- ELF II Tiny BASIC on cassette tape. Commands include SAVE, LOAD, +, x, -, ( ), 26 variables A-Z, LET, IF/THEN, INPUT,

- PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF II's hex keyboard as a joystick, 4k memory required. £14.95\* post paid.
- Tom Pittman's *Short Course on Tiny BASIC* for ELF II. £5.00\* post paid.
- Expansion Power Supply (required when adding 4k RAM). £19.95\* plus £2.00 p&p.
- ELF-BUG Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your TV at any point in your programme. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! £14.95\* post paid.
- Coming Soon: A-D, D-A Converter, Light Pen, Controller Board, Colour Graphics & Music System... and more!

Call or write for wired prices!

H. L. AUDIO LTD., Dept. P.E.,  
138, Kingsland Road, London E2 8BY.  
Tel: 01-739 1582.  
Sole European Distributors for Netronics R & D Ltd., U.S.A.

Yes! I want to run programmes at home and have enclosed:  
 £109.56 including postage and V.A.T. for RCA COSMAC ELF II kit.  £5.94 including postage and V.A.T. for power

- supply (required),  £5.95 for RCA 1802 User's Manual,  £5.95 including postage and V.A.T. for *Short Course on Microprocessor Computer Programming*.
- I want mine wired and tested with power supply, RCA 1802 User's Manual and *Short Course* included for just £164.10 including postage and V.A.T.
- I am also enclosing payment (including postage and V.A.T.) for the items checked at the left.

Total Enclosed £

USE YOUR  ACCESS  BARCLAYCARD

Account No. \_\_\_\_\_

Signature \_\_\_\_\_ Exp. Date \_\_\_\_\_

CREDIT CARD PHONE ORDERS ACCEPTED 01-808 6127.

Print Name \_\_\_\_\_

Address \_\_\_\_\_

DEALER INQUIRIES INVITED

# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders dispatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £8). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## OSCILLOSCOPES

We have available from stock the following SCOPEX models: 4D10A - DC-10MHz; 10mV sensitivity; Stab Power supplies; Dual beam; 3% accuracy; Excellent value at £214 inc VAT and Carr.  
4S6 - DC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for £150 inc VAT and Carr.

## RELAYS

WB47 Low profile PC mntg 10x33x20mm 6V coil, SPCO 3A contacts. 83p  
WB32 Sub. min type, 10x19x10mm 12V coil DPCCO 2A contacts £1.15  
WB17 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A, 95p  
WB19 12V 1250R DPCCO 1A contacts. Size 29x22x18mm, min plug-in type 72p  
WB39 50V ac (24V DC) coil. 11 pin plug in type. 3 pole c/o 10A contacts Only 85p  
WB46 Open construction mains relay. 3 sets 10A c/o contacts. £1.20  
Send SAE for our relay list - 84 types listed and illustrated.

## AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and Vol/on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add £2.20 for suitable transformer.) Blue vinyl covered aluminium case to suit (W372) £1.30

## RESISTOR PACK

Carbon Film 5% mostly 1/2W, few 1/4W resistors. Brand new, but have preferred leads, ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of £2.50 per 1000; £11 per 5000.

## DIN SOCKET OFFER

2 pin switched speaker socket. PC mounting; 5 pin 180° PC mntg or chassis mntg (clip fix). All the same price, any mix: 10 for 70p, 25 for £1.60 100 for £6.50.

## TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock  $\bar{V}$ ; Fully TTL compatible; Low power dissipation. Supplied with data £2.75

## MISCELLANEOUS IC's

Supplied with data if requested. MC3302 quad comp. 120p; 710 diff comp. (T099) 40p; 2N1034E precision timer £2.25; LM711 Dual diff comp 85p; LM1303 dual stereo pre-amp 75p; MC1468R voltage reg £1.50; URC1025H audio £3.50; 575C2 audio £2.88; TDA2640 audio £2.92; SN75110 dual line driver 70p; MC8500 CRCC gen POA

## EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!  
18 way 41p; 32 way 72p; 40 way 90p.

## HEAT SINK OFFER

Copper T05 sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1000 for £25

## 74 SERIES PACK

Selection of boards containing many different 74 series IC's. 20 for £1; 50 for £2.20; 100 for £4.

## THE NEW 1978-9 GREENWELD CATALOGUE

### FEATURES INCLUDE:

- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

## AIR FRESHENER KIT

As featured in Nov EE. Complete kit inc. case and instructions. Only £7.95 + 55p p & p.

## PUSH BUTTON BANKS

Illustrated list of types from 30p in our Bargain List No 6 - Send SAE.

## BC182B OFFER

Special Offer for quantity users 1k .035 V.A.T. 5k .032 V.A.T. Price negotiable on 10k. Approx 70K available.

## DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices - signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of £1.25/1000 - or a bag of 25,000 for £2.25. Bag of 10,000 £8. Box of 25,000 £17.50. Box of 100,000 £60.

## POLYTHENE SHEET

Size 36 x 18" 200g. Hundreds of uses around the home. 100 sheets for £1.50. Box of 1500 for £19.

## PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5% 10 of each value 22pF to 1000pF. Total 210, £3.35

K002 Extended range, 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75

K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, 10, 15, 20/125 15/16 22/16 33/10 47/6 100/3. Total 170 tanis for £14.20

K007 Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for £15.30

K042 As above but 5 of each value £8.70

## TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2.50, 6-0-6V 100mA 85p; 1 1/2A £2.40, 9-0-9V 75mA 85p; 1A £2.10. Multitapped type: 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.90, 20V 2 1/2A £3.90; 25V 1 1/2A £2.25; 12V BA £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50;

# CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,  
WOOD GREEN, LONDON,  
N22 4SJ (MAIL ORDER DEPT.)

888-3206

## FLIP

Push Button Heads or Tails.

Complete kit and full instructions supplied.

A pocket game. Easy to build and great to play. Kit price £5.25 + 8% VAT. Post free.



## 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max. A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier. S.A.E. for spec. sheet. Still only £20.00 + 8% VAT.

## SIRENS

CR 11 Siren. Rotating fan in metal unit. Adjustable mounting bracket. Gives high pitched wail. 12 volts DC. Dimensions: 75 x 80 x 75mm. £9.50 + 8%  
CR 12 Siren. 125mm diameter gold coloured horn with fixing plate. Emits high-pitched wailing note of varying frequency - 16 cpc. per minute. 12 volts DC. £9.00 + 8%  
CR 13. As above but rapid noise frequency change - 160 cpc. per minute.  
CR 14 Siren. 90mm (dia.) x 60mm. Red plastic case with fixing plate, emits high-pitched wailing note of varying frequency - 100 cpc. per minute. 12 volts DC. £5.50 + 8%.

## BARGAIN LOUDSPEAKER

Goodmans 5" 8 ohm long throw heavy duty LSPKR. Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 6 1/2" (diagonally) Only £5.00 + 12 1/2% VAT.

## 2 WAY 8 OHM HEAVY DUTY XOVER.

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100W. Input via screw terminals. Fitted with a 3 position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB. Buy now while stocks last! Only £3.00 + 8% VAT.

## POWER SUPPLY UNIT

PP1 switched 3, 4, 6, 7, 9 and 12 volts at 500mA, with on/off switch and pilot light. Size: 130 x 55 x 75mm approx. Our Price: £8.25 @ 8% VAT.

## SIX-PIECE MINIATURE SCREWDRIVER SET

Six precision screwdrivers in a hinged plastic box. Blade sizes: 0.8mm, 1.4mm, 2mm, 2.4mm, 2.9mm, 3.8mm. Our Price: £1.75 + 8% VAT



## PIEZO ELECTRIC HORN UNITS

High Quality, High Power Tweeter. No Xover reqd. Freq. Response: 3.8kHz-28kHz. Spec. sheet sent on receipt of S.A.E. Our Price: £6.50 + 8% VAT.

## BARGAIN TRANSFORMER

240V Primary 12-0-12V 500mA sec. Approx. size: 60 x 40 x 50mm. Fixing centres: 75mm. Price: £1.50 + 8% VAT.



'P&P' orders up to £5, Add 30p.  
Orders £5-£10, Add 50p.  
All orders over £10 post free!  
Please add V.A.T. as shown.  
S.A.E. with all enquiries please.



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.  
also 13 SOUTH MALL, EDMONTON GREEN, EDMONTON


## CHINAGLIA DINO—ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

THE
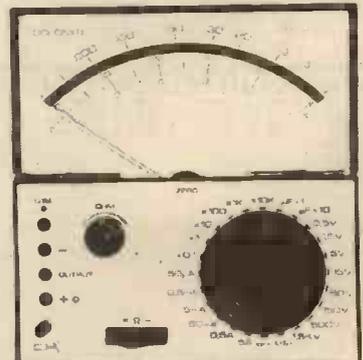
## DOLOMITI

20kΩ/V a.c. and d.c.

A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED



Accuracy: D.C. ranges, ± 2.0%. A.C. & Ω ranges ± 2.5%.  
39 ranges: d.c. V, 0-150mV, 500mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1.5kV; d.c.I, 0-50µA, 500µA, 5mA, 50mA, 0-5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1.5kV; a.c.I, 5mA, 50mA, 0-5A, 5A; dB - 10 to + 65 in 6 ranges; Ω 0-05kΩ, 5kΩ, 50kΩ, 500kΩ, 5MΩ, 50MΩ. pF 50kpf, 500kpf.

Automatic overload protection and high current range fusing.

Scale mirror and fine pointer for accuracy of reading. Single knob spring range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £50.00 incl. VAT (£1 P. & P.)  
30kV Probe £12.85 incl. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

## ALCON Instruments Ltd.

19 MULBERRY WALK. LONDON SW3 6DZ TEL: 01-352 1897

### TRANSISTORS

TYPE	PRICE	BC108A	0.07	BC177B	0.12	BC350A	0.15	BD508	0.50	BFX43	0.70	OC71	0.09	M2188	0.20
AC107	0.23	BC108	0.07	BC177B	0.12	BC350A	0.15	BD508	0.50	BFX43	0.70	OC71	0.09	M2188	0.20
AC125	0.17	BC109	0.06	BC179	0.12	BC441	0.20	BD537	1.02	BFX85	0.20	OC75	0.10	M2222	0.22
AC126	0.17	BC109B	0.07	BC182A	0.09	BC461	0.24	BD587	1.40	BFX88	0.20	OC82	0.48	M2222A	0.20
AC127	0.16	BC109C	0.07	BC182B	0.09	BC546	0.10	BDX32	1.90	BFY18	0.50	OC139	0.50	M2270	0.39
AC127K	0.23	BC113	0.12	BC183A	0.09	BC547	0.11	BDY16	0.50	BFY19	0.50	OC203	2.50	M2368	0.10
AC128	0.14	BC114	0.15	BC183LA	0.09	BC547A	0.11	BDY20	0.50	BFY33	0.50	OC207	2.70	M2484	0.18
AC128K	0.25	BC116	0.13	BC183BL	0.10	BC547C	0.11	BF121	0.20	BFY34	0.50	OC1072	2.50	M2484A	0.18
AC128/1760.42	0.87	BC117	0.15	BC184	0.08	BC548	0.11	BF123	0.20	BFY51	0.12	OC1074	2.50	M2906	0.18
AC142	0.18	BC118	0.12	BC184L	0.09	BC548A	0.11	BF125	0.20	BFY52	0.12	R2008B	2.10	M3053	0.15
AC153	0.65	BC119	0.25	BC184BL	0.10	BC548B	0.11	BF127	0.20	BFY81	4.00	TFP30	0.35	M3117	1.00
AC158	0.50	BC125	0.15	BC186	0.19	BC548C	0.11	BF137	0.21	BFY81	4.00	TFP31	0.45	M3340	0.70
AC176	0.16	BC125B	0.16	BC187	0.19	BC549A	0.11	BF157	0.21	BRY39	0.35	TFP32	0.45	M3638A	0.15
AC187	0.50	BC126	0.15	BC204	0.08	BC550	0.11	BF154	0.15	BSX52	0.23	TFP33	0.60	M3643	0.24
AC187K	0.55	BC136	0.15	BC204B	0.09	BC557	0.11	BF157	0.37	BSY20	0.31	TFP42	0.60	M3892	0.24
AC188K	0.55	BC137	0.15	BC206	0.10	BC557A	0.11	BF158	0.15	BSY26	0.30	TFP95	0.65	M3705	0.06
ACY20	1.02	BC138	0.30	BC206B	0.11	BC557B	0.11	BF167	0.25	BSY26	0.30	TIS90	0.18	M3706	0.06
ACY22	1.02	BC140	0.27	BC207	0.10	BC557C	0.11	BF173	0.20	BSY27	0.30	M3448	0.30	M3707	0.06
AD142	0.87	BC141	0.29	BC209B	0.09	BC558	0.11	BF174	0.20	BSY29	0.54	N2404	0.45	M3711	0.06
AD143	0.87	BC142	0.20	BC212A	0.10	BC558A	0.11	BF177	0.25	BSY39	0.15	N2524	0.48	M3819	0.20
AD149	0.65	BC147	0.06	BC213L	0.10	BC558B	0.11	BF178	0.25	BSY52	0.33	N2526	0.48	M3899	3.00
AD161	0.35	BC147B	0.07	BC214L	0.10	BC559B	0.11	BF179	0.25	BSY54	0.39	N2527	0.48	M3904	0.06
AD161/1620.70	1.02	BC148	0.06	BC237	0.15	BCY42	0.55	BF180	0.20	BSY56	0.36	N2685	3.50	M3905	0.06
AD162	0.35	BC148A	0.07	BC237A	0.15	BCY58	0.20	BF181	0.20	BSY60	0.36	N2705	0.10	M3906	0.06
AD262	0.36	BC148B	0.07	BC237C	0.21	BCY71	0.13	BF182	0.20	BSY84	0.30	N2706	0.10	M4037	0.25
AD263	0.36	BC149	0.06	BC238	0.15	BCY72	0.13	BF183	0.20	BU105	1.08	N2706A	0.11	M4058	0.10
ADY26	4.74	BC157	0.06	BC238B	0.15	BD115	0.30	BF184	0.20	BU105-04	1.08	N2708	0.12	M4222A	0.65
ADZ11	4.05	BC157A	0.07	BC238C	0.18	BD116	0.30	BF185	0.20	BU108	1.80	N21039	0.15	M4348	2.00
AF106	0.45	BC158	0.07	BC251A	0.15	BD123	0.60	BF194	0.06	BU126	1.00	N21059	0.15	M4448	1.50
AF109	0.36	BC158A	0.08	BC251B	0.17	BD128	1.02	BF194A	0.07	BU133	1.75	N21101	0.15	M4914	3.50
AF124	0.25	BC158B	0.09	BC252A	0.15	BD131	0.35	BF195	0.06	BU204	1.30	N21102	0.15	M6172	0.25
AF125	0.25	BC159	0.06	BC252B	0.17	BD133	0.40	BF195D	0.07	BU205	1.30	N21302	0.20	M2545	0.30
AF126	0.25	BC159A	0.07	BC252C	0.20	BD135	0.30	BF195G	0.07	BU208	1.50	N21304	0.50	M25296	0.40
AF127	0.25	BC159B	0.07	BC252D	0.20	BD136	0.30	BF196	0.06	BU208-02	1.75	N21305	0.50	M25458	0.25
AF139	0.32	BC161	0.25	BC261A	0.10	BD137	0.30	BF197	0.06	BU406	3.60	N21307	0.50	M25496	0.60
AF178	0.30	BC167	0.06	BC262	0.20	BD138	0.30	BF198	0.06	BU699A	6.75	N21309	0.50	M25670	0.65
AF179	0.30	BC168	0.06	BC267A	0.21	BD139	0.30	BF224	0.18	BU699B	2.00	N21613	0.18	M25926	0.55
AF200	0.36	BC169	0.06	BC267B	0.22	BD140	0.30	BF253	0.18	BU699C	7.00	N21671	1.10	M26123	0.65
AF201	0.39	BC170B	0.07	BC268	0.21	BD144	0.30	BF254	0.18	BU70A	5.00	N21671B	2.20	M2503	0.75
AS73	0.30	BC170C	0.07	BC304	0.25	BD168	0.50	BF255	0.18	BU71	4.50	N21711	0.20	M2303	0.90
ASZ15	0.60	BC171	0.06	BC307	0.15	BD178	0.72	BF257	0.16	MPS6517	0.48	N21893	0.25	M2304	0.90
ASZ16	0.60	BC171A	0.07	BC307A	0.15	BD181	1.32	BF258	0.28	MPS6523	0.27	N21905	0.25	M2305	0.90
ASZ17	0.60	BC171B	0.07	BC307B	0.15	BD183	1.50	BF259	0.28	MPSA06	0.90	N21990	0.25	M2323	1.00
AU103	0.90	B172	0.06	BC308	0.15	BD232	0.60	BF324	0.20	MV5053	0.72	N22060	1.00	M2572	1.00
AU107	1.00	BC172A	0.07	BC309A	0.15	BD233	0.60	BF335	0.25	NKT214	0.28				
AU110	0.90	BC172B	0.07	BC317B	0.18	BD234	0.60	BF338	0.45	NKT224	0.25				
AU120	0.90	BC172C	0.07	BC322	0.10	BD235	0.40	BF457	0.60	OC22	1.40				
BC107	0.06	BC173	0.06	BC327	0.16	BD236	0.40	BF523	0.22	OC26	1.40				
BC107A	0.07	BC173B	0.07	BC328	0.16	BD237	0.40	BF594	0.10	OC29	0.85				
BC107B	0.07	BC174B	0.07	BC337	0.16	BD238	0.40	BF691	5.00	OC36	1.00				
BC108	0.06	BC177A	0.12	BC338	0.16	BD507	0.50	BFX29	0.20	OC45	0.12				

### TTL

TYPE	PRICE	7400	.12	7476	.13	74161	.80	4000	1.15	4073	.20
7401	1.2	7476	.13	74161	.80	4000	1.15	4073	.20		
7402	1.2	7483	.75	74163	.80	4001	1.15	4075	.20		
7403	1.2	7484	.90	74164	.90	4002	1.15	4076	1.10		
7404	1.2	7485	.90	74165	.90	4006	1.15	4078	.20		
7405	1.2	7486	.26	74166	1.00	4007	1.15	4081	.20		
7406	1.2	7489	2.00	74167	2.00	4008	1.15	4082	.20		
7407	1.2	7490	3.50	74170	1.70	4009	1.15	4084	.20		
7408	1.2	7491	.65	74172	4.00	4010	1.15	4087	.20		
7409	1.2	7492	.45	74173	1.20	4011	1.15	4088	2.30		
7410	1.2	7493	.36	74174	.90	4012	1.15	4091	1.10		
7411	1.2	7494	.80	74175	7.00	4013	1.15	4093	.20		
7412	1.2	7495	.55	74176	.90	4014	1.15	4095	.20		
7413	1.2	7496	.62	74177	.90	4015	1.15	4096	.20		
7414	1.2	7497	2.40	74178	1.20	4016	1.15	4098	.65		
7415	1.2	7498	.95	74179	1.10	4017	1.15	4099	.20		
7416	1.2	7499	.40	74180	.70	4018	1.15	4101	.90		
7417	1.2	7500	.28	74181	1.95	4019	1.15	4102	.45		
7418	1.2	7501	.45	74182	.75	4020	1.15	4103	.60		
7419	1.2	7502	.46	74183	1.20	4021	1.15	4104	.85		
7420	1.2	7503	.46	74184	2.00	4022	1.15	4105	.85		
7421	1.2	7504	.62	74185	1.20	4023	1.15	4106	.85		
7422	1.2	7505	.62	74186	2.70	4024	1.15	4107	.85		
7423	1.2	7506	.62	74187	5.40	4025	1.15	4108	.85		
7424	1.2	7507	.62	74188	5.40	4026	1.15	4109	.85		
7425	1.2	7508	.62	74189	1.10	4027	1.15	4110	.85		
7426	1.2	7509	.62	74190	1.10	4028	1.15	4111	.85		
7427	1.2	7510	.62	74191	1.00	4029	1.15	4112	.85		
7428	1.2	7511	.62	74192	1.00	4030	1.15	4113	.85		
7429	1.2	7512	.62	74193	1.00	4031	1.15	4114	.85		
7430	1.2	7513	.62	74194	1.00	4032	1.15	4115	.85		
7431	1.2	7514	.62	74195	1.00	4033	1.15	4116	.85		
7432	1.2	7515	.62	74196	1.00	4034	1.15	4117	.85		

# GODDARD'S COMPONENTS

110 LONDON ROAD, ST. ALBANS, HERTS. AL1 1NX

MAIL  
ORDER  
DEPT.

Callers Welcome MON-SAT: 9.30-5.30

THURS: Closed all day

Lunch: MON-FRI: 1.30-2.30, SAT: 1.00-2.00

ALL PRICES INCLUDE VAT

## STEREO



### CASSETTE RECORDER DECK AND PRE AMPLIFIERS


with + solenoid auto-stop  
+ CrO2 switch  
+ piano key operation  
+ twin level meters  
+ mic. sockets

Tech. Spec.:  
Bias and erase freq. 88 kHz  
4 ICs 8 Transistors  
1 SCR 10 Diodes

Power supply extra  
Circuits, Diagrams and top  
panel template supplied  
Top Plate £3.50 + 50p P&P

**£25.75 + £1.25 p&p**

## HIT-BOX

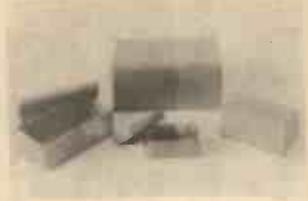

SHOCK-PROOF  
POLYSTYROL IN GREY  
4mm thick walls  
Larger sizes are pillar fixing  
Smaller sizes are slotted  
Inside Measurements:

Box No.	Breadth mm	Length mm	Height mm	Weight gm
1001	60	90	50	100
1002	75	130	61	175
1003	90	160	71	285
1004	93	193	95	340
1005	125	220	110	575

1001 - 90p 1004 - £2.00  
1002 - £1.60 1005 - £3.00  
1003 - £1.80 50p each p&p. £1.00 for 3 p&p

TRADE ENQUIRIES WELCOME!

## DIGITAL CLOCK

BATTERY DROP LEAF  
CLOCK MOVEMENT

Hrs. Mins. Date  
Easy-to-set regulator screw  
Size: 140mm x 85mm x 60mm  
Window size: 63mm x 28mm  
No. height: 19mm  
Date height: 10mm  
Weight: 270gm



**£4.95 + 50p p&p**

## LCD WATCHES

TOUCH GENTS  
CTG

**£9.95**



LADIES S/S AND  
GILT C652

**£10.95**

UNISEX C551

**£8.95**

Coloured Straps

Black Red  
Blue Brown  
Green Fawn



ALL WATCHES 5 FUNCTION ...  
1 YEAR GUARANTEE  
P & P 70p per watch, Inc. Insurance

# You know it's easy with Heathkit.

## Electronics Courses

New series of courses on car  
electrical systems.

New series of courses on electronic  
equipment.

DC electronics.

AC electronics.

Semi-conductors.

Electronic circuits.

Digital techniques.

Microprocessors.

Heathkit self-instruction electronics courses are complete, low-cost learning systems. All you need is the will to learn and the Heathkit courses will teach you at your own pace.

It's easy because the courses are based on step-by-step programmed instructions, with audio records (or optional cassettes), self evaluation quizzes to test your understanding, and interesting experiments that encourage you to learn the easy "hands-on" way with the optional Heathkit experimenter-trainers.

Thousands of people just like you have already learnt electronics the easy Heathkit way - at home, in educational establishments and in industry throughout the world.

You'll find it easy too. Full details are in the Heathkit catalogue, together with hundreds of kits you can build yourself; for the home, car and workshop.

Send for your copy now.

BARCLAYCARD

VISA

Access



## New Kits

Line printer.

Dual floppy disc.

Dual trace 5MHz and 35MHz  
oscilloscopes.

Memory expansion for digital trainer.

2M hand-held transceiver.

To Heath (Gloucester) Limited, Dept PE/2/79  
Bristol Road, Gloucester GL2 6EE. Please send the items I have ticked.  
 Heathkit catalogue (enclose 20p in stamps).  computer  
brochure (enclose 20p in stamps).

Name \_\_\_\_\_

Address \_\_\_\_\_

NB. If you are already on the Heathkit mailing list then you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon. Registered in England, number 606177.

HEATH  
Schlumberger

# LOOK!

## Here's how you master electronics.

### .... the practical way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

#### 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

#### 2. Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

#### 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.
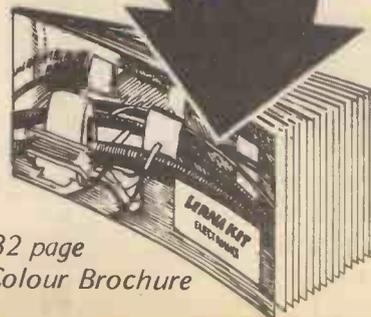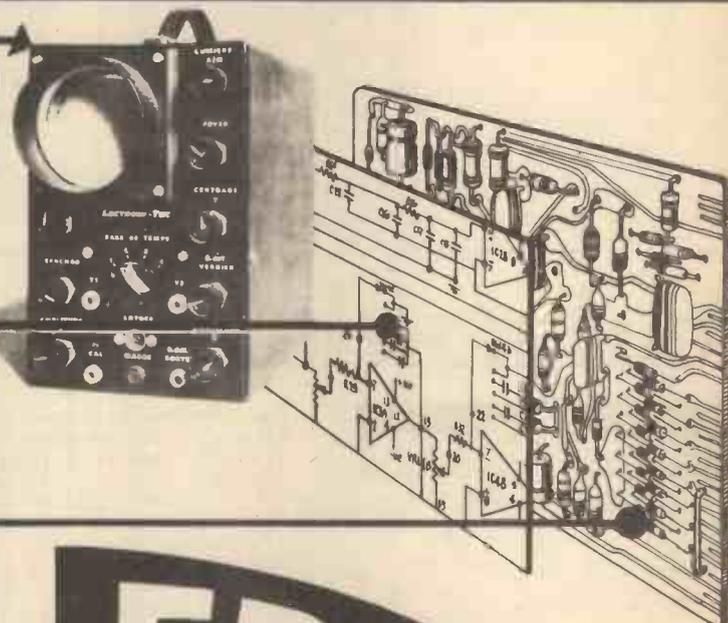
#### 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



32 page  
Colour Brochure

Post now, without obligation, to:-

### BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PEB 2/79

Block caps please




# VALVE MAIL ORDER CO.

Clim House  
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS  
MAIL ORDER SERVICE**

tp	tp	tp	tp	tp	tp
AA119	0-10	BCY70	0-15	*MPSA56	0-26
AA30	0-27	BCY71	0-17	*MPSU01	0-36
AA32	0-42	BCY72	0-13	*MPSU06	0-46
AA313	0-18	BCZ11	1-50	*MPSU56	0-49
AA315	0-34	BD115	0-45	NE555	0-45
AA317	0-27	BD121	1-20	NKT401	2-00
AC107	0-60	BD123	1-20	NK703	1-73
AC125	0-20	BD124	1-30	NKT404	1-73
AC126	0-20	BD131	0-35	OA5	0-95
AC127	0-20	BD132	0-38	OA7	0-55
AC128	0-20	BD136	0-34	OA10	0-60
AC141	0-25	BD137	0-35	OA7	0-14
AC141K	0-35	BD138	0-40	OA79	0-30
AC142K	0-30	BD139	0-43	OA81	0-30
AC176	0-20	BD140	0-44	OA85	0-30
AC187	0-20	BD144	2-00	OA90	0-08
AC188	0-20	BD181	1-10	OA91	0-08
AC189	0-80	BD182	1-18	OA95	0-08
AC191	0-75	BD237	0-40	OA200	0-09
AC192	0-75	BD238	0-55	OA202	0-09
AC193	0-75	BDX10	0-90	OA211	1-00
AC194	1-50	BDX32	2-00	OAZ200	1-00
AD149	0-70	BDY20	1-25	OAZ201	1-00
AD161	0-45	BDY60	1-50	OAZ206	1-00
AD162	0-45	BF115	0-25	OAZ207	1-00
AF106	0-45	BF152	0-20	OC16	2-00
AF114	0-35	BF153	0-28	OC20	2-50
AF115	0-35	BF154	0-27	OC22	2-50
AF116	0-35	BF159	0-23	OC23	2-75
AF117	0-35	BF160	0-16	OC24	3-00
AF139	0-40	BF167	0-20	OC25	0-90
AF186	1-20	BF177	0-24	OC28	2-00
AF239	0-45	BF178	0-24	OC29	2-00
AFZ11	2-75	BF179	0-25	OC35	1-50
AFZ12	2-75	BF180	0-25	OC36	1-50
ASV26	0-40	BF181	0-30	OC41	0-80
ASV27	0-40	BF182	0-30	OC42	0-75
ASZ15	1-25	BF183	0-25	OC43	2-25
ASZ16	1-25	BF184	0-25	OC44	0-60
ASZ20	1-50	BF185	0-25	OC45	0-55
ASZ21	2-00	*BF194	0-10	OC72	1-55
*AU110	1-70	*BF195	0-09	OC73	1-00
*AU113	1-70	*BF196	0-10	OC74	0-65
*AU110	1-70	*BF197	0-12	OC74	0-65
*BA145	0-13	*BF200	0-27	OC75	0-65
*BA148	0-13	*BF224	0-20	OC76	0-55
BA154	0-09	BF244	0-28	OC77	1-20
BA155	0-09	BF258	0-26	OC81	0-65
BA156	0-09	BF259	0-32	OC82	1-20
BAW62	0-05	BF336	0-30	OC83	0-65
BAX13	0-06	BF337	0-30	OC84	0-65
BAX16	0-09	BF338	0-31	OC122	1-50
BC107	0-12	BFS21	2-95	OC126	1-75
BC108	0-13	BFS28	2-23	OC139	2-25
BC109	0-13	*BFS61	0-20	OC140	2-25
*BC113	0-12	*BFS98	0-20	OC141	3-75
*BC114	0-13	BPW10	0-65	OC170	1-00
*BC115	0-14	BPW11	0-65	OC171	1-00
*BC116	0-15	BFX84	0-22	OC172	1-50
*BC117	0-15	BFX85	0-22	OC203	0-75
*BC118	0-15	BFX87	0-21	OC202	1-75
BC125	0-16	BFX88	0-21	OC203	1-75
*BC126	0-20	BFY50	0-26	OC204	2-50
*BC135	0-14	BFY51	0-26	OC205	2-50
*BC136	0-15	BFY52	0-26	OC206	2-50
*BC137	0-15	BFY64	1-25	*OC108B	1-75
*BC147	0-09	BFY90	1-25	TIC44	0-30
*BC149	0-09	BSX19	0-21	TIC226D	1-20
*BC157	0-09	BSX20	0-20	TL209	0-20
*BC158	0-09	BSX21	0-20	*R2008B	1-75
*BC168	0-08	BT106	1-25	*R2009	2-25
*BC169	0-12	*BTY79/4	1-25	*S2101B	0-75
*BC170	0-11	*BU205	1-75	TIC44	0-30
BC171	0-10	*BU206	2-25	TIC226D	1-20
BC172	0-10	*BU208	2-00	TL209	0-20
BC173	0-12	BY100	0-45	*TIP29A	0-41
BC177	0-12	BY125	0-14	*TIP30A	0-44
BC178	0-14	BY127	0-15	*TIP31A	0-44
BC179	0-16	BZX61	0-18	*TIP32A	0-48
BC182	0-11	Series		*TIP33A	0-69
BC183	0-10	BZY88	0-13	*TIP34A	0-73
BC184	0-11	Series		*TIP41A	0-63
BC185	0-11	CRS1/05	0-45	*TIP42A	0-70
BC186	0-12	CRS1/40	0-60	*TIP2955	0-67
BC213	0-12	CRS3/05	0-45	*TIP3055	0-56
BC214	0-15	CRS3/40	0-75	*T1S43	0-45
BC237	0-09	CRS3/60	0-90	*ZS140	0-25
BC238	0-12	GEX86	1-50	*ZS170	0-21
BC301	0-25	GEX541	1-75	*ZS178	0-54
BC303	0-24	GJM	0-75	*ZS271	0-23
*BC307	0-10	GJM5	0-75	*ZS278	0-57
*BC308	0-10	GL7M	0-75	*ZTX107	0-11
*BC327	0-20	GMO378A	1-75	*ZTX108	0-10
*BC328	0-18	*KS100A	0-45	*ZTX109	0-12
*BC337	0-18	MJE340	0-80	*ZTX300	0-12
*BC338	0-17	MJE370	1-75	*ZTX301	0-13
BC339	1-00	MJE371	0-61	*ZTX302	0-15
BCY31	1-00	MJE520	0-52	*ZTX303	0-17
BCY32	1-00	MJE521	0-55	*ZTX304	0-19
BCY33	0-90	MJE2955	1-25	*ZTX311	0-12
BCY34	0-90	MJE3055	0-75	*ZTX314	0-20
BCY39	3-00	*MPF102	0-30	*ZTX500	0-13
BCY42	0-25	*MPF104	0-30	*ZTX501	0-14
BCY43	0-25	*MPF105	0-30	*ZTX502	0-16
BCY58	0-16	*MPSA06	0-24	*ZTX503	0-17
				*ZTX504	0-20
				*ZTX505	0-24
				*ZTX506	0-24
				*ZTX507	0-24
				*ZTX651	0-24
				*ZTX652	

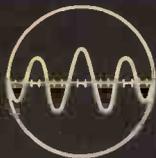

# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING  
CONTROL SYSTEMS


PRICES INCLUDE VAT. P & P FREE  
correct at 1.12.78  
TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE279) or quote  
Access/Barclaycard No. and post to TUAC LTD. (PE279) 119  
Charlton Road, London SW17 9AB. We accept phone orders from  
Access/Barclaycard Holders. Phone 01-672 9080.
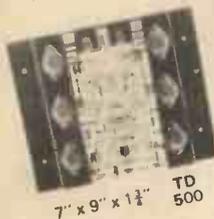
## NEW FROM TUAC ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS

Featuring  
Electronic Short Open & Thermal Overload Protection.


Brief Spec.  
Input Sensitivity 0.775v. R.M.S. (O.D.B.) at 25 K Ohms  
Frequency Response 20 Hz-20 KHz  
Hum & Noise - 100 dB Relative full output



7" x 9" x 1 1/2" TD 500  
T.H.D. at full power 0.1%  
T.D. 500 300W into 2 Ohms  
220W into 4 Ohms  
140W into 8 Ohms  
Power supply P.S. 300  
T.D. 150 150W into 4 Ohms  
100W into 8 Ohms  
Power supply P.S. 150  
T.D. 150. 60 Version 60W into 8 Ohms  
40W into 15 Ohms.  
Power supply P.S.60

£45.00  
£30.00  
£26.25  
£18.50  
£17.75  
£15.50

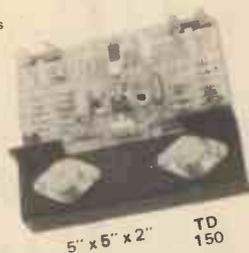
Note P.S. 300 will drive 2 T.D. 150 amplifiers



5" x 5" x 2" TD 150

All output ratings are R.M.S. continuous sine wave output.

## AMPLIFIER MODULES

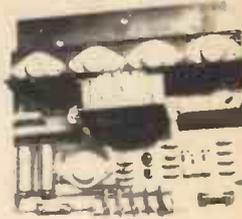

SPEC. INPUT  
SENSITIVITY 60 mV  
for full output  
Frequency response  
20 Hz-20 KHz  
HUM & NOISE - 70dB

TL30 5" x 5" x 2"  
\* 35 watt 10 amp output transistors **£13.25**  
TL60 5" x 5" x 3"  
\* 60 watt R.M.S. continuous sine wave output  
\* 2 R.C.A. 110 watt 15 amp output transistors **£18.50**  
TL100 5" x 5" x 3"  
\* 100 watt R.M.S. continuous sine wave output  
\* 2 R.C.A. 150 watt 15 amp output transistors **£21.50**  
TP125 7" x 6 1/2" x 3"  
\* 125 watt R.M.S. continuous sine wave output  
\* 4 R.C.A. 150 watt 15 amp output transistors **£27.50**


## 4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1

- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£21.50

Model 501 500W per channel as above without sound triggering

£14.00

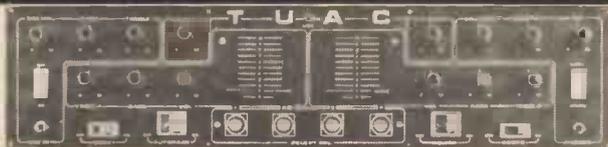

## STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A A. comp.). Flat 50mV at 1kHz. Bass controls ± 18dB at 60Hz. Treble controls ± 18dB at 15kHz.

OUTPUT: Up to 3 volts (+ 12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz ± dB.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions

Size: 25in long x 6in high x 3in deep

Mono Disco Mixer with autofade **£49.00**

**£149.00**

## 3 CHANNEL LIGHT MODULATOR SILMB


- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.75

Single Channel Version 1500 Watts

£9.75

## POWER SUPPLIES

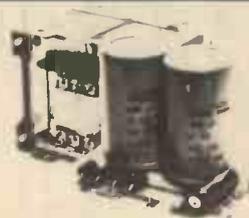

Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply:

PS250 for supplying 2 TP125s	£30.00
PS200 for supplying to TL100s	£30.00
PS60/60 for supplying 2 TL60s	£30.00
PS125 ± 45 volts for TP125	£18.50
PS100 ± 43 volts for TL100	£17.00
PS60 ± 38 volts for TL60	£15.50
PS30 ± 25 volts for TL30	£11.75
PSU 2 for supplying disc mixer	£7.50

## STOCKISTS - CALLERS ONLY

A1 Music, 88, Oxford Street, Manchester (Tel 061-236 0340)  
Geo Mathews, 85/87, Hurst Street, Birmingham (Tel 021-622 1941)  
Soccodi, 9, The Friars (Tel Canterbury 60948)  
Cookies Disco Centre, 126/128, West Street (Tel Crews 4739)  
Garland Bros. Ltd., Deptford Broadway, London 01-692 4412  
Luton Disco Centre, 88, Wellington Street, Luton (Tel Luton 411733)  
Session Music, 163, Mitcham Road, Tooting (Tel 01-672 3413)  
Mon-Sat 10am to 6pm. Closed Wed.  
Electra Centre, 58, Lancaster Road, Preston (Tel Preston 58488)

TRADE & EXPORT ENQUIRIES 01-672 3137

## ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDMI **£15.25**

## FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)  
as illustrated



For S1LMB **£7.25**  
Size 8" x 4 1/2"



4LSM1 **£6.00**  
Size 6 1/2" x 4 1/2"



FUZZ LIGHTS  
Red, Green, Blue,  
Amber. **£24.50**



S1LMB **£8.25**  
Combined with 3SDM1  
Size 9" x 4 1/2"

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED  
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE

# ASTRA-PAK

92 GODSTONE ROAD  
WHYTELEAF, SURREY CR3 0EB


# GRAND SALE

All prices INCLUDE VAT. Add .25p for P & P (extra for overseas). Send SAE for complete Special Offers list. Where more than one price appears, overall quantity prices apply to groups of devices OF THE SAME TYPE (74 and 74LS cannot be mixed).

7400 Series				74LS00 Series				7400 Series				74LS00 Series				CMDS				CMDS				STAR OFFER										
1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+					
7400	08	075	07	155	14	13	7485	62	58	55	67	60	56	74161	50	44	40	60	53	48	4000	13	11	10	4069	14	13	12	4538	180	80	82	*100 7418	16
7401	11	105	10	155	14	13	7486	22	20	19	28	25	23	74182	57	52	48	110	100	92	4001	13	12	11	4070	14	13	12	4539	72	60	54	*100 555-8	19
7402	11	105	10	155	14	13	7489	135	125	118	149	135	125	74183	57	52	48	60	53	48	4002	13	12	11	4071	14	13	12	4541	90	81	70	*100 MC1458P	24
7403	11	105	10	155	14	13	7490	30	28	26	42	38	36	74184	57	52	48	82	75	70	4006	70	62	58	4072	14	13	12	4543	110	97	88	*100 AD161/162 MP	50
7404	11	105	10	155	14	13	7491	60	55	52	74	68	64	74185	57	52	48				4007	13	12	11	4073	14	13	12	4549	300	250	225	*100 8C184	06
7405	12	115	11	16	15	135	7492	33	30	28				74186	70	64	59				4008	58	52	48	4075	14	13	12	4553	320	280	240	*100 BC214	062
7406	22	21	20				7493	28	25	23	43	40	38	74187	220	205	195				4009	32	29	27	4076	82	78	75	4554	30	28	25	*100 2N3055	35
7407	22	21	20				7494	50	45	43				74188				160	140	125	4010	36	32	30	4077	38	35	32	4555	75	62	56	1000 125" Red	05
7408	13	125	12	155	14	13	7495	50	45	42	64	58	55	74189				160	140	125	4011	13	12	11	4078	14	13	12	4556	75	62	56	1000 2" Red Led	06
7409	13	125	12	155	14	13	7496	48	42	38				74170	120	110	100	150	128	112	4012	13	12	11	4081	14	13	12	4557	320	280	240	1000 IN4001	025
7410	11	105	10	155	14	13	7497	180	170	165				74172	380	355	340				4013	30	25	22	4082	14	13	12	4558	90	80	72	1000 IN4002	028
7411	11	105	10	155	14	13	7498	80	72	68				74173	90	84	80	85	80	76	4014	68	62	56	4085	58	54	52	4560	300	250	220	1000 IN4003	038
7412	14	135	13	16	15	135	74104	40	36	34				74174	64	60	56	58	52	49	4015	60	55	52	4086	58	54	52	4560	145	120	105	1000 IN4004	038
7413	23	21	20				74105	37	34	32				74175	58	54	51	58	52	49	4018	32	28	26	4088	120	108	100	4561	188	167	140	1000 IN4007	042
7414	46	43	40				74107	22	20	18	32	28	28	74176	58	54	51				4017	50	46	44	4093	45	40	38	4562	420	360	325	1000 IN4017	031
7415							74109	28	26	24	32	28	25	74177	56	52	49				4018	55	50	47	4094	138	125	115	4566	98	86	80	*1000 LESS 10%	05
7416	22	20	18				74110	36	34	32				74178	90	80	75				4019	40	35	32	4095	85	80	77	4568	170	150	138	LINEARS	30
7417	22	20	18				74111	55	52	50				74179	108	100	95				4020	68	64	60	4096	85	80	77	4569	137	115	105	CA3045-14	40
7420	11	105	10	155	14	13	74112				32	28	25	74180	80	70	62				4021	66	62	58	4097	300	280	267	4580	420	365	340	CA3046-14	30
7421	22	21	20				74113	28	26	24				74181	115	95	80				4022	60	55	52	4098	80	84	78	4581	188	167	140	LM380W-14	68
7422	17	165	16	16	15	135	74114							74182	52	47	44				4023	13	12	11	4099	110	95	88	4582	82	74	68	LM381N-14	90
7423	20	19	18				74116	110	100	95				74184	125	108	100				4024	42	39	36	4160	88	83	80	4583	70	60	52	LM7100N-14	25
7425	20	19	18				74118	78	75	72				74185A	100	90	86				4025	13	12	11	4161	88	83	80	4584	30	27	25	LM7111N-14	26
7426	21	20	19	16	15	135	74119	110	100	95				74186	720	630	670				4026	90	84	78	4162	88	83	80	4585	88	78	70	MC1310P-14	130
7427	21	20	19	16	15	135	74120	80	76	74				74188	260	240	225				4027	30	27	25	4163	88	83	80	4589	198	170	150	NE555-4	23
7428	18	17	16				74121	24	22	20				74189				198	175	160	4028	46	42	40	4164	88	83	80	LOW PROFILE DIL	50				
7430	11	105	10	155	14	13	74122	32	29	27				74190	68	60	55	72	65	68	4029	52	47	44	4174	98	92	87	IC SOCKETS	125				
7432	21	20	19	23	20	16	74123	38	35	32	55	50	48	74191	68	60	55	70	63	56	4030	32	28	26	4175	98	92	87	8 pin	10	09	08	NE556-14	40
7433	20	19	18	24	21	185	74124	160	150	142	115	105	98	74192	62	55	48	68	62	58	4031	180	160	148	4194	98	92	87	14 pin	115	105		NC2501B-14	125
7437	20	19	18	24	21	185	74125	32	30	28	38	33	29	74193	60	50	46	68	62	58	4032	86	80	77	4501	14	13	12	16 pin	125	115		SN76003N	165
7438	20	19	18	24	21	185	74126	32	30	28	38	33	29	74194	58	50	46				4033	105	98	92	4502	72	66	63	18 pin	18	16	15	SN76023N	125
7440	12	115	11	18	16	15	74128	60	55	52				74195	58	50	46	100	92	85	4035	98	90	86	4506	42	36	34	20 pin	20	18	17	SN76033N	165
7441	48	45	43				74129	40	36	32				74196	56	50	45	78	71	65	4036	250	235	225	4507	42	36	34	22 pin	22	20	19	TA4550B	100
7442	40	36	34	50	44	40	74132	47	44	42	62	56	48	74197	50	44	40	92	83	78	4037	82	76	72	4508	190	168	150	24 pin	24	22	21	TA861B	100
7443	65	60	57				74134	32	30	28				74198	96	85	78				4038	84	78	74	4509	160	148	130	28 pin	28	25	23	TB4120S	56
7444	64	59	56				74135	62	58	55	38	33	29	74199	98	90	85				4039	230	218	210	4511	85	80	75	40 pin	40	37	35	TB4614A	168
7445	53	50	48				74136	52	48	46				74221	120	100	88	94	85	80	4039	230	218	210	4511	85	80	75	4512	82	76	70	TB4800	80
7446	55	52	50				74137	74	68	66				74247				90	82	75	4041	70	64	58	4513	142	130	120	12 pin	12	11	10	TB4810S	80
7447	50	48	40	67	60	56	74138				52	45	41	74248				90	82	75	4042	50	45	42	4514	235	220	208	12 pin	12	11	10	TB4820S	75
7448	55	50	48	82	73	65	74139				52	45	41	74249				90	82	75	4043	56	51	48	4515	235	220	208	12 pin	12	11	10	TC4220D	300
7449				67	60	56	74141	52	48	46				74257				68	50	56	4044	62	58	55	4516	66	60	56	2" 5mm				ZN414	90
7450	12	115	11				74142	185	175	168				74258				68	56	50	4045	105	95	88	4517	340	315	300					DP AMPS	80
7451	12	115	11	16	15	135	74143	230	210	200				74259				68	56	50	4046	90	85	80	4518	85	80	75	Red	08	07	06	CA3130-1099	80
7453	12	115	11				74144	230	210	200				74256				68	56	50	4047	84	79	75	4519	38	36	34	Yellow	13	125	12	LM301A-B	24
7454	12	115	11	155	14	13	74145	55	50	48				74273	190	170	155	200	185	150	4048	42	38	36	4520	82	76	70	Green	13	125	12	LM348-14	90
7455				16	15	135	74147	100	92	88				74279	110	90	82	46	40	34	404													

# Understanding Digital Electronics

## New teach-yourself courses

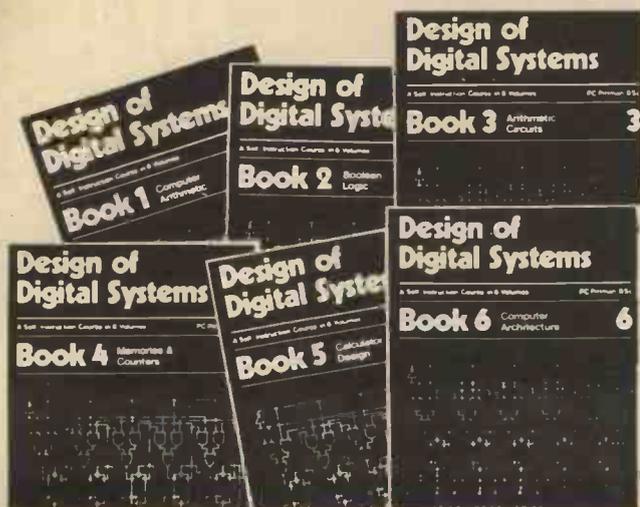

**Design of Digital Systems** is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of **Design of Digital Systems** include:

**Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

**Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

**Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

**Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

**Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

**Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



**Digital Computer Logic and Electronics** is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, Unit 25, Rivermill Site, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE22 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of **Design of Digital Systems** cost only: **£8.10** +90p post & packing

And the four volumes of **Digital Computer Logic and Electronics** cost only: **£4.60** +90p post & packing

But if you buy both courses, the total cost is only: **£12** +£1 post & packing

Price includes surface mail anywhere in the world: Airmail extra.

## Flow Charts & Algorithms

HELP YOU PRESENT:

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

**THE ALGORITHM WRITER'S GUIDE** explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

**£2.95** + 45p post and packing by surface mail anywhere in the world. Airmail extra.

**GUARANTEE**

If you are not entirely satisfied your money will be refunded.

Please allow 21 days for delivery.

Cambridge Learning Enterprises, Unit 25, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE22 4BR, England.

Please send me the following books:

.....sets Digital Computer Logic & Electronics @ £5.50, p & p included  
 .....sets Design of Digital Systems @ £9.00, p & p included  
 .....Combined sets @ £13.00, p & p included  
 .....The Algorithm Writer's guide @ £3.40, p & p included

Name .....

Address .....

I enclose a \*cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my \*Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number.....

Signature.....\*delete as appropriate.

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

PE25

<b>TLsby TEXAS</b> 7400 13p 74178 160p 7401 14p 74180 93p 7402 14p 74181 200p 7403 14p 74182 90p 7404 17p 74183 150p 7404 90p 74185 150p 7405 18p 74186 700p 7406 32p 74190 100p 7407 32p 74191 100p 7408 19p 74192 100p 7409 19p 74193 100p 7410 15p 74194 100p 7411 24p 74195 95p 7412 20p 74196 95p 7413 30p 74197 80p 7414 60p 74198 150p 7414 90p 74199 150p 7416 17p 74200 1000p 7417 17p 74201 1000p 7420 17p 74202 1000p 7421 40p 74251 140p 7422 22p 74259 250p 7423 34p 74265 90p 7423 30p 74278 50p 7426 40p 74279 140p 7427 34p 74283 190p 7428 36p 74284 400p 7430 17p 74285 400p 7432 30p 74290p 150p 7433 35p 74291 150p 7437 35p 74294 200p 7438 35p 74298 200p 7440 17p 74365 150p 7441 70p 74366 150p 7442A 60p 74367 120p 7443 112p 74368 150p 7444 112p 74390 200p 7445 100p 74393 200p 7446A 93p 74490 225p 7447A 60p 74LS SERIES 7448 80p 74LS00 14p 7450 17p 74LS02 14p 7451 17p 74LS04 16p 7453 17p 74LS08 21p 7454 17p 74LS10 20p 7460 17p 74LS11 40p 7470 36p 74LS13 45p 7472 30p 74LS14 72p 7473 34p 74LS20 20p 7474 30p 74LS21 20p 7475 36p 74LS22 28p 7476 35p 74LS27 38p 7480 50p 74LS30 20p 7481 100p 74LS32 27p 7482 80p 74LS42 70p 7483A 90p 74LS47 90p 7484 100p 74LS55 30p 7485 110p 74LS73 50p 7486 34p 74LS74 40p 7489 210p 74LS75 45p 7490A 33p 74LS83 110p 7491 80p 74LS85 100p 7492A 46p 74LS86 40p 7493A 33p 74LS90 60p 7494 84p 74LS93 60p 7495A 75p 74LS107 45p 7496 68p 74LS112 100p 7497 180p 74LS123 70p 74100 130p 74LS124 180p 74105 65p 74LS132 95p 74107 34p 74LS138 60p 74109 55p 74LS139 60p 74110 55p 74LS151 100p 74111 70p 74LS153 60p 74116 200p 74LS157 110p 74118 130p 74LS160 120p 74119 210p 74LS168 130p 74120 110p 74LS169 100p 74121 28p 74LS162 140p 74122 48p 74LS163 110p 74123 55p 74LS165 180p 74125 55p 74LS166 180p 74126 60p 74LS167 180p 74128 75p 74LS168 180p 74132 75p 74LS173 110p 74136 75p 74LS174 90p 74141 70p 74LS175 110p 74142 200p 74LS181 320p 74145 90p 74LS190 100p 74147 190p 74LS191 100p 74148 150p 74LS192 140p 74150 100p 74LS193 140p 74151A 70p 74LS195 100p 74153 70p 74LS196 120p 74154 100p 74LS221 140p 74155 90p 74LS240 175p 74156 90p 74LS241 175p 74157 70p 74LS242 170p 74159 190p 74LS243 170p 74160 100p 74LS244 170p 74161 100p 74LS245 170p 74162 100p 74LS251 140p 74163 100p 74LS253 140p 74164 120p 74LS257 120p 74165 130p 74LS259 160p 74166 140p 74LS266 100p 74167 200p 74LS273 130p 74170 240p 74LS279 90p 74172 720p 74LS298 249p 74173 120p 74LS324 200p 74174 93p 74LS373 180p 74175 85p 74LS374 200p 74176 90p 74LS378 200p	<b>4000 SERIES</b> 4000 15p 4001 17p 4002 17p 4006 95p 4007 18p 4008 60p 4009 40p 4010 50p 4011 17p 4012 18p 4013 50p 4014 84p 4015 84p 4016 45p 4017 80p 4018 85p 4019 48p 4020 100p 4021 110p 4022 100p 4023 22p 4024 50p 4025 25p 4026 130p 4027 50p 4028 84p 4029 100p 4030 55p 4031 200p 4033 180p 4034 200p 4035 110p 4040 100p 4041 80p 4042 80p 4043 90p 4044 90p 4046 110p 4047 100p 4048 55p 4049 35p 4050 48p 4051 80p 4052 80p 4053 80p 4054 150p 4055 125p 4056 125p 4059 60p 4060 115p 4063 120p 4066 55p 4067 45p 4068 22p 4069 20p 4070 30p 4071 22p 4072 22p 4073 22p 4074 22p 4075 107p 4081 22p 4082 22p 4093 80p 4094 250p 4098 107p 441 110p 4502 120p 4503 70p 4507 55p 4510 99p 4511 99p 4514 250p 4516 110p 4518 100p 4520 100p 4528 100p 4534 181p 4553 450p 4560 250p 4583 90p 4584 90p 4601 4 80p 4608 200p 4609 90p 1441 1100p 1442 1100p 1443 1100p	<b>93 SERIES</b> 9301 160p 9302 175p 9308 316p 9310 275p 9311 275p 9312 160p 9314 165p 9316 225p 9321 225p 9322 150p 9324 225p 9370 200p 9374 200p	<b>VEROBOARD</b> (Copper clad) 2 1/2 x 3 1/2 41p 33p 2 1/2 x 5 45p 45p 2 1/2 x 3 1/2 45p 45p 3 x 5 56p 60p 2 x 17 152p 121p 3 x 17 152p 163p 4 1/2 x 17 252p Pkt of 35 pins 85p Spot face letter 85p Pin insertion tool 99p	<b>VERO WIRING</b> Plus spool 325p Spare spool 80p Wire (wire) 80p Combs 7p each	<b>BUCKET BRIGADE</b> SAP1024 1800p	<b>LINEAR I.C.s</b> *AY1-0212 600p *AY1-1313 600p *AY1-1320 320p *AY1-5050 211p *AY5-1315 600p *AY5-1317 636p *CA3019 80p *CA3046 70p *CA3048 225p *CA3086 72p *CA3089E 225p *CA3090AQ 375p *CA3105 100p *CA3114QE 70p *CA3160E 100p FX209 750p ICL7106 850p ICL8038 340p LM301A 30p LM311 120p LM318 200p LM324 70p LM339 75p LM348 95p LM377 175p LM380 75p *LM381AN 160p *LM389AN 140p *LM389AN 140p *LM709 36p LM710 50p LM725 350p LM733 100p LM741 20p LM747 70p LM748 35p LM748 35p LM3900 70p LM3911 130p LM4136 20p *MC1310P 150p MC1458 55p MC1495L 350p *MC1496 100p *MC3340P 120p *MC3360P 120p	<b>TRANSISTORS</b> AC120 25p AC127/8 20p AC176 25p AC187/8 25p AF167 30p AD149 20p AD161/2 45p BLV83 110p BC109 11p *BC117 20p *BC147/8 9p *BC149 10p *BC157/8 10p *BC159 11p *BC169C 12p *BC172 12p *BC177/8 17p *BC179 18p *BC182/3 10p *BC184 11p *BC187 30p *BC12/3 11p *BC214 12p *BC241 36p *BC277/8 30p *BC516/7 50p *BC547B 16p *BC549C 18p *BC557B 18p *BC559C 18p *BCV70 40p *MPFA06 30p *MPSA12 50p *MPSA56 32p *MPSP06 63p *MPSP65 78p OC28 130p OC35 130p *RC008B 200p *R201A 200p *TP29A 40p *TP29C 55p *TP30A 48p *TP30C 62p *TP31A 58p *TP31C 62p *TP32A 80p *TP32C 80p *TP33A 90p *TP33C 114p *TP34A 110p *TP34C 110p	<b>MEMORIES</b> 2102 100p 2102-2 120p 2102L-4 140p 2107B 600p 2111-1 225p 2112-2 300p 2114 1000p 5101 510p 6810 350p	<b>ROM/PROMS</b> 74S188 225p 74S287 400p 74S387 400p 93427 400p 93436 400p 93436 650p 93448 1000p	<b>CPU's</b> 40A04 670p 6502 1200p 6800 900p 6801 TBA 8080A 550p	<b>EPROMS</b> 1702A 600p 2708 900p 2716 2500p 4702 900p	<b>TRANSFORMERS</b> (prim 220-240V) 6-0-6 100mA 88p 9-0-9 75mA 92p 12-0-12 100mA 95p 0-12-0 12 500mA 280p+ 0-25V (5VA) 250p 9-0-9 1A 270p+ 12V 2A 350p+ 0-12-15 1A 340p+ 20-24-30 1A 265p+ 15-0-15 1A 265p+ (Please add 50p p&p charge to all marked * above our normal p&p charge)	<b>DIODES</b> *BY127 12p *OA2 9p *OA8 15p *OA85 15p *OA90 9p *OA91 9p *OA95 9p *OA200 9p *OA202 10p *IN914 4p *IN916 7p *IN148 4p *IN4001/2 5p *IN4003/4 6p *IN4006 6p *IN4006/7 7p *IN5401/3 14p *IN5404/7 19p *IN5920 9p	<b>*ZENEERS</b> 2.7V 33V 9p 400mW 9p 1W 15p 3A 40V 60p 3A 50V 65p 6A 40V 75p 6A 50V 88p 6A 50V 85p 12A 50V 85p 16A 40V 105p 16A 50V 130p 16A 50V 130p 12A 50V 130p	<b>TRIACS</b> 3A 40V 60p 3A 50V 65p 6A 40V 75p 6A 50V 88p 6A 50V 85p 12A 50V 85p 16A 40V 105p 16A 50V 130p 16A 50V 130p	<b>HEAT SINKS</b> For TO220 Voltage Regs. and Transistors 22p For TO5 12p	<b>THYRISTORS</b> 1A 50V 40p 1A 40V 65p 1A 60V 70p 3A 40V 90p 8A 60V 140p 12A 40V 160p	<b>BRIDGE RECTIFIERS</b> *1A 50V 21p *1A 100V 22p *1A 400V 30p *1A 600V 35p *1A 600V 280p *2A 50V 30p *2A 100V 35p *2A 400V 45p *3A 200V 60p *3A 600V 72p *4A 100V 95p *4A 400V 100p 6A 50V 90p 6A 100V 100p 6A 400V 120p 10A 400V 200p 25A 400V 400p	<b>LOUD-SPEAKERS</b> Size 2 1/2" 64R 70p 2 1/2" BR 70p 2 1/2" BR 75p 1 1/2" BR 75p	<b>SUBMINIATURE SWITCHES</b> Toggle 51p SPST 53p SPDT 55p DPDT 85p DPDT (Centre-off) 85p Push to make (Red, Green, Yel., Blue) 15p Push to break (Black only) 25p	<b>CRYSTALS</b> 100KHz 300p 1MHz 370p 3.2768MHz 350p 10.7MHz 350p 18MHz 300p 27.135MHz 300p	<b>EDGEBOARD CONNECTORS</b> 0.156" Solder Tail 85p 2 x 10 way 100p 2 x 16 way 100p 2 x 18 way 135p 2 x 22 way 100p 2 x 25 way 160p	<b>LOW PROFILE DIL SOCKETS BY TEXAS</b> 8 pin 18 pin 25p 24 pin 33p 14 pin 12p 20 pin 28p 28 pin 41p 16 pin 13p 22 pin 30p 40 pin 52p	<b>WIRE WRAP SOCKETS</b> 8 pin 30p 24 pin 80p 14 pin 40p 28 pin 100p 16 pin 55p 40 pin 120p	<b>EDGE CONNECTOR</b> 31 Way Plug 105p 31 Way Skt. 110p (0.1" Pitch)
---	--	---	--	--	--	---	--	---	--	---	---	---	---	---	--	---	--	--	---	--	---	--	--	--	---

\* RESISTORS High Stat Carbon Film 5% Tol E12 Series  
1W 10R-1M 1p 90p/100 each valve  
1/2W 10R-10M 1.5p 120p/100 each valve

\* MINIATURE PRESETS, Horz/Vert  
100R-1M: 10p

\* CARBON TRACK POTENTIOMETERS  
1W LOG or LIN  
Single 5K-2M 26p  
Single with DP Switch 5K-2M 55p  
Dual 5K-2M 66p

\* CAPACITORS  
Low Voltage Electrolytic, Polyester, Tantalum Disc Ceramic available

VEROBOARDS ANTEX IC BREADBOARD (20 x 14 pin DIL ICs or 16 x 16 pin DIL ICs) 4.15" x 6.15" 270p

VQ BOARD Specially designed for DIL IC's - No track cutting 5.82" x 2.9" 105p

Model C 15W 360p  
CX 17W 360p  
X25 360p  
CCN 380p  
Spare Bits C/CX/CCN 46p  
X25 50p

**"PE" MICROPRINTER**  
SIND S.A.E. FOR DETAILS

Complete Kit £49  
Ready-built tested module £69  
(Above prices include VAT and P&P and a free Power Supply circuit design)

Trouble-shooting services available for kits or modules purchased from us.  
Demonstration now on at our shop.  
PCB £6.00 + VAT + P&P.  
SFF96364 £11.50 + VAT + P&P.

**TECHNOMATICS LTD.**  
17 Burnley Road, London NW10  
(2 minutes Dollis Hill tube station) (ample street parking)  
Tel: 01-452 1500 Telex: 922800

VAT RATE: All items at 8% except where marked\* where 12 1/2% applies.  
Please add 25p p&p & VAT at appropriate rates.  
Government, Colleges, etc. Orders accepted.  
Mon, Fri 9.30-5.30  
Saturday 10.30-4.30

PLEASE SEND SAE FOR LIST. CALLERS WELCOME

# 15-240 WATTS!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for Internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** complete pre-amplifier in single pack, multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

**APPLICATIONS:** hi-fi; mixers; disco; guitar and organ; public address.

**SPECIFICATION:** inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV, input impedance 47k $\Omega$  at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble  $\pm$ 12dB at 10kHz; bass  $\pm$ 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— $\pm$ 16-50V.

Price £6.27 + 78p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



## HY30 15W into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

**FEATURES:** complete kit; low distortion; short, open and thermal protection; easy to build.

**APPLICATIONS:** updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

**SPECIFICATION:** Output Power—15W R.M.S. into 8 $\Omega$ . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price £6.27 + 78p VAT. P. & P. free

## HY50 25W into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

**APPLICATIONS:** medium power hi-fi systems; low power disco; guitar amplifier.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 25V. Size—105 x 50 x 25mm.

Price £8.18 + £1.02 VAT. P. & P. free



## HY120 60W into 8 $\Omega$


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

**APPLICATIONS:** hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 35V. Size—114 x 50 x 85mm.

Price £19.01 + £1.52 VAT. P. & P. free

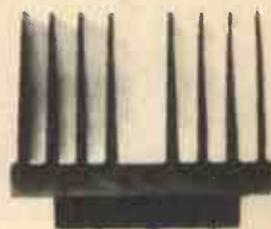

## HY200 120W into 8 $\Omega$


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

**FEATURES:** thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

**APPLICATIONS:** hi-fi; disco; monitor; power slave; industrial; public address.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 45V. Size—114 x 50 x 85mm.

Price £27.99 + £2.24 VAT. P. & P. free

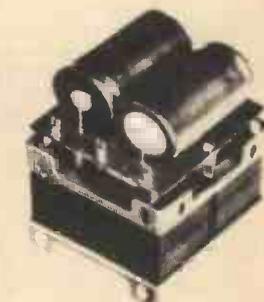

## HY400 240W into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** thermal shutdown; very low distortion; load line protection; no external components.

**APPLICATIONS:** public address; disco; power slave; industrial.

**SPECIFICATION:** Output Power—240W R.M.S. into 4 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price £38.61 + £3.09 VAT. P. & P. free

**POWER SUPPLIES:** PSU36—suitable for two HY30s £6.44 + 81p VAT. P. & P. free. PSU50—suitable for two HY50s £8.18 + £1.02 VAT. P. & P. free. PSU70—suitable for two HY120s £14.58 + £1.17 VAT. P. & P. free. PSU90—suitable for one HY200 £15.19 + £1.21 VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 £25.42 + £2.03. VAT. P. & P. free.

Free post + packing applicable to U.K. only.

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.  
Crossland House,  
Nackington, Canterbury  
Kent CT4 7AD  
Tel (0227) 64723

Please supply .....

Total Purchase price .....

I Enclose: Cheque  Postal Orders  Money Order

Please debit my Access account  Barclaycard account

Account number .....

Name and Address .....

Signature .....

Registered office No. 1032630

# ELECTRONI-KIT

**"EDUCATIONAL KITS OF EXCEPTIONAL QUALITY"**

(AUDIO magazine)



**THIS IS A POWERFUL RADIO RECEIVER!**

The same kit is also 150 other different actual working projects e.g.:

Computer & Logic Circuits, Electronic Organ, Timer, Light Control, Agility Tester, Lie Detector, Siren, Horn, Buzzer, Bird, Metronome, Cds cell light & sound control, Photogun, Light Oscillator, Light Switch, Light and Sound Morse Code, Field Strength Meter, Hygrometer, Sphygmometer, Etc.,

Radio Receiver, Transmitter, Amplifier, Audio Generator, Signal Tracer & Injector, Continuity Tester, Telegraph, Photoradio Receiver, Radio Receiver/Microphone Mixer, Illuminometer, Voltmeter, Ammeter, Sound Level Meter, Ohmmeter, Diode & Transistor Tester, Transparency Indicator, Etc., Etc.

The above is just a selection of the circuits available—you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for anyone to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

**ALL KITS ARE FULLY GUARANTEED.** Add-on sets (to increase the scope of each kit) are available, plus spares and accessories as required.

150 PROJECT KIT £39.75 60 PROJECT KIT £25.75  
120 PROJECT KIT £33.75 30 PROJECT KIT £18.95  
100 PROJECT KIT £29.25 15 PROJECT KIT £16.75

Prices include educational manuals, free book, VAT, p & p (in the U.K.), free introduction to the British Amateur Electronics Club. Also free list of low priced electronics books.

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque/P.O./Barclaycard/Access No. (or 14p for illustrated literature) to DEPT. PE.

**ELECTRONI-KIT LTD.**  
20 BRIDE LANE, LUDGATE CIRCUS,  
LONDON, EC4Y 8DX (01-353 6430)

# Codespeed

## ELECTRONIC MAIL ORDER

All Full Spec. Devices

**TO3 HEAT SINKS III** Two types of heat sink. Ex-equipment, but conditions as new. Most still contain a power transistor (condition unknown). Christmas tree type 92 x 86 x 35mm 20p each. Rectangular type 130 x 63 x 32mm 30p each. Please add 25p per heat sink post and packing.

**PACK M1** Contains two brand new multifunction calculator keyboards. Excellent key action. Only £1.00

**PACK T2** A high contrast 3½ digit Liquid Crystal wristwatch display with data. Don't miss out—only £1.00.

**PACK T3** Back in stock again! MM5316 digital alarm clock chip. Still only £2.75 including data.

**PACK T4** At a new low price, what a bargain. A 0.8" common cathode, 3½ digit, 12 hour clock display. Now offered at only £3.95.

**PACK S1** 25 miniature glass 1N3470 germanium diodes (600mA, 35v). All brand new (at just 2p each how can you go wrong?) 25 diodes for 50p.

**PACK S2** 4 x 1N6U2 programmable unijunction transistors (P.U.T.). Lots of uses, long delay timers, oscillators and many more. All brand new. With data and usage sheet. 4 for 50p.

**PACK S3** 10 x 1N4151 high speed switching diodes. Same as 1N4148, but has higher P.I.V. 10 for 35p.

**PACK P1** With this MM5330 digital voltmeter I.C. we include the data sheet and circuit diagram to build a high accuracy digital multimeter. Only £3.95.

**PACK E2** Calculator style L.C.D. B digit with right hand decimal points. Digit height 0.33". With data only £2.95.

**PACK E3** The same as Pack E2, but has 0.5" high digits. £4.25.

**EVER THOUGHT** of using 7 segment gas discharge displays as an alternative to LED's or LCD's? Gives a nice bright orange display and are comparatively very low in price. Requires 180v d.c. supply (easily achieved in mains operated projects). All have right hand decimal points and are supplied with data.

**PACK E4** 0.3" high 1½ digit display. Now only 50p.

**PACK E5** a 0.3" high dual digit display. Now only 50p.

**PACK E7** a 0.25" high 12 digit display with free socket. £1.50.

**PACK DM1** Want to buy 115 quality switching diodes for 50p? These 14 pin chips each contain 23 matrix diodes. 5 chips for 50p.

### All Untested Packs

**PACK M4 CALCULATORS III** This pack contains a production line reject calculator. Either repair them (not much wrong with some of them) or strip them for spares. Lots of accessible goodies inside, approximately 28 transistors, 2 chips, display, case and detachable keyboard. Such a bargain, you can't go wrong. Only £2.50.

**PACK MU1** (Untested—so no guarantee) 2 x Upper half of hand held calculator case with integral keyboard. Ex-equipment, but believed to be O.K. A gift at only 50p the pair.

**PACK DL1** (Untested—so no guarantee) A bumper pack of 30 mixed I.C.'s. You test them and save EEE's. Could include anything linear or digital. A snip at only £1.00.

**PACK E1** (80% guaranteed good) Contains 5 seven segment LED displays. Digit height 0.127" with right hand decimal. Common cathode. Still only £1.00.

Your satisfaction is guaranteed or return the complete pack for replacement or a refund.

For free catalogue send stamped addressed envelope.  
Postage and packing please add 25p. (Overseas orders add 60p)  
**CODESPEED, P.O. Box 23, 34 Seafield Road,  
Copnor, Portsmouth, Hants., PO3 5BJ**

## MORE SCOPE FOR YOUR MONEY

ELMAC 4810 4" Scope



**SPECIFICATIONS ELECTRICAL DATA**  
VERTICAL AXIS (Y). Deflection Sensitivity—100mV/division. Bandwidth (between 3 dB points)—DC—5MHz. Attenuator—(calibrated)—9 step 0:1, 0:2, 0:5, 1, 2, 5, 10, 20, 50/div. Input Impedance—1 Meg/40 pf in shunt. Input Voltage—Max—600V P.P.  
HORIZONTAL AXIS (X). Deflection Sensitivity—0.400mV/division. Bandwidth (between 3 dB points)—1Hz—350KHz. Gain Control—Continuous when time bases in EXT position. Input Impedance—1 Meg. Input Voltage—Max—600V P.P.  
TIME BASE. Sweep Range (calibrated)—100msec/div to 1µ sec/div in 5 steps. FINE

Control—Variable between steps—includes time-base calibration position. Blanking—Internal—on all ranges. SYNCHRONISATION. Selection—Internal, external Synchronisation Level—Continues from positive to negative.  
PHYSICAL DATA. Dimensions—15cm (h) x 20.5cm (w) x 28cm (d). Weight—4.3Kg (approx.). Stand—2 position flat and inclined. Case—Steel, epox, enamelled. Front panel—Aluminium enamelled epoxy printing. Test leads available £2.00 CASH WITH ORDER £59. (+ £7.92 V.A.T) Company Orders Accepted by Tele. & Telex 888941. Barclay & Access by arrangement. Dept PE.  
SAE for 6 and 10 meg. scopes.

### KRAMER & CO.

9 October Place, Holders Hill Road, London NW4 1EJ. Telex: 888941 attn. Kramer k7. Tel: 01-203 2473. Mail order only. Callers by appointment.

## HAVE YOU DONE IT LATELY!

Fit a new tape head and transform the performance of your tape recorder

**MONOLITH**  
THE MONOLITH ELECTRONICS CO. LTD.

QUALITY  
REEL TO REEL  
AND CASSETTE TAPE HEADS



Full Catalogue 25p

Please enclose 20p P&P with order

B24—RP stereo cassette glass/ferrite record/playback £9.84  
B12—01 mono cass. playbk. £1.60 B24—01 stereo cass. playbk. £2.80  
A28—05 stereo 8tk cartridge £1.80 E12—09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

# Put a Clamp on those small jobs with NODEX quick-grip vice



Adaptable on all drill supports. V-notch allows fixing of all profiles.

#### Dimensions

Overall length	150mm
Overall width	130mm
Overall height	50mm
Jaw opening	70mm
Jaw height	35mm
Jaw width	70mm
Weight	850 grammes

The patented locking system of the Nodex vice allows for instantaneous locking or loosening for use as a vice or as a press. Usable horizontally or vertically on the bench top or on the bench edge.

Descriptive leaflet and general catalogue available from:

**SPECIAL PRODUCTS DISTRIBUTORS LTD.**  
81 PICCADILLY, LONDON W1V 0HL

Tel: 01-629 9556

Cables: Speciproduct London W1

# LOOK!

## New 12" Monitor for your Micro



or CCTV application

Uncased £60

Cased £85

Available cased or uncased for OEM's

The above prices are for 1 off orders (plus VAT)

## 6800 Based

## Micro Computer now available - KIT £220

Power Supply £20 extra (+VAT)

INCLUDING Tiny Basic and on board Prom Programmer

(plus VAT)

# CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM MIDDLESEX • Telephone: 01-891 1923

# The latest kit innovation!

## from Sparkrite

*Sparkrite - was featured by Shaw Taylor in "DRIVE IN"*

the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

#### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV11) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing UK only.

Electronics Design Associates, Dept. PE 10, 82 Bath Street, Walsall, WS1 3DE. Phone: Walsall 614791

Electronics Design Associates, Dept. PE2  
82 Bath Street, Walsall, WS1 3DE. Phone: (0)614791

Name .....

Address .....

Phone your order with Access or Barclaycard

Send SAE if brochure only required

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X4 KIT £16.65

TACHOPULSE SLAVE UNIT £3.85

£  
Cheque No.

Please state polarity pos or neg earth.

Access or Barclaycard No. ....



### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### RECEIVERS AND COMPONENTS

#### BARGAIN PACKS

TTL 7400, 01, 02, 03, 04, 08, 10, 20, 30, 51 ANY MIX 10/£1.00, 100/£9.00, 7433, 48, 104, 105, 109, 122 ANY MIX 10/£1.90, 100/£18.00, 7445, 46, 92, 95, 151 ANY MIX 4/£1.00, 7443, 83, 96, 156, 160, 162, 163, 74165, 180, 193, 194 ANY MIX 3/£1.30, 10/£5.20, BC184, 2N1711 - 2/£1.00, OCP70 5/£1.00, Similar to 2N192 - 20/£1.00, MAN 10 0.27" - 4/£3.00, BAX13, IN4151 - 100/£1.50, T8A 120A 2/£1.00, IN5400 10/£0.80, 74S10, 20/£1.00, Panaplex 9 Digit 7 Seg. Display 2/£2.50, Thyristor 3A 25V - 3/£0.50, \*LSP 2 1/2" dia. 40 ohms - 2/£1.00\*

\*RESISTORS 10/£0.09, 100/£0.80 ANY MIX E12 - 10 ohms to 1 meg.

\*CAPACITORS Ceramic 27P to 8200P E12 Series 10/£0.30, Polyester 0.01 to 1 10/£0.50 ANY MIX 1 MF 10/£1.00, Electrolytic 63V 1 MF to 10 MF 10/£0.70, 16V 10 MF to 100 MF 10/£0.70.

#### TELEPHONE ORDERS

COV. (0203) 611597 Using Access Card No. V.A.T. Add 12 1/2% to items marked\* To all others add 8%

#### IBEK SYSTEMS Dept. PE.,

32 DUNSVILLE DRIVE, COVENTRY CV2 2HS.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs, 0945-4188. Immediate settlement.

#### BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V. 0.47, 1.0, 2.2, 4.7 & 10 mfd. — 8p. 22, 47—5 1/2p. (50V—6p), 100—7p. (50V—8p). 220—8p. (50V—10p), 470—11p. (50V—16p). 1000/15V—15p. 1000/25V—18p. 1000/40V—35p. Subminiature bead tantalum electrolytics. 0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 6.3V—8p. 2.2/35V & 4.7/25V—9p. 10/25V, 15/18V—12p. 22/16V, 33/10V, 47/6V, 68 & 100 @ 3V—14p. Mullard Miniature Ceramic E12 Series 63V 2%. 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p. Vertical Mounting Ceramic Plate Caps. 50V. E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p. Polystyrene E12 Series 63V. Hor. Mounting. 10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p. Mullard Polyester 250V Vert. Mtg. E6 Series. .01 to .1—4p. .15, .22—5p. .33, .47—8p. .68—11p. 1.0—14p. 1.5—20p. 2.2—24p. Mylar (Polyester) Film 100V. Vertical Mtg. .001, .002, .005—3p. .01, .02—4p. .04, .05—5p. Miniature Film Resistors Highstab. E12 5%. 0.125 watt 100 to 2MΩ ..... 1p. 0.250 watt 10 to 10MΩ (10% over 1M)..... 1p. 0.500 watt 100 to 2MΩ ..... 1p. 1.000 watt 100 to 10MΩ ..... 2p. 1N4148—3p. 1N4002—5p. 1N4006—7p. 1N4007—8p. BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—9p. 20mm. fuses .15, .25, .5, 1.0, 2.0, 3.0 & 5A—3p. Printed Circuit Holders for 20mm. fuses—5p. Post 10p (Free over £4). Prices VAT inclusive.

#### THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

## SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

P.C.Bs PAXOLIN 10 1/2" x 4 1/2" 4 - £1.25. 12" x 9" 70p. 17 1/2" x 9 1/2" £1.15. D.S. 10" x 8 1/2" 80p. Fibre Glass 9" x 8" £1.20. 18" x 8" £2.40. D.S. 13" x 6" £1.30. 11 1/2" x 7 1/2" £1.60. Panel with 42 assorted 74 series ICs £1.50, 20 wire ended neons £1, 300 small components, trans. diodes £1.50, 7 lbs assorted components £3.60, 3 1/2 lbs £1.95. List 15p. Refundable. Post 20p under £1. Insurance add 15p.

#### J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

TUNBRIDGE WELLS COMPONENTS, Ballard's, 108 Camden Road, Tunbridge Wells, Phone 31803. No Lists. Enquiries S.A.E.

#### SERVICE SHEETS

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

#### VALVES FOR SALE

### VALVES FOR SALE

CV 445 STC TYPE 5J/180E. Quantity 60 new at list price less 50%

CONTACT: STARAVIA LIMITED  
King's Ride, Ascot, Berks.  
Telephone: Ascot 23422

#### SITUATIONS VACANT

MONEY, KNOCKERS, GOTCHA! Wanna Earn a Few Bucks Moonlightin'? We need a Part-Time Design/Layout Personage. Phone Paul 579-2535 Day, 567-9705 Evns.

### ELECTRONIC ENGINEERS

We are:

A young energetic electronics company manufacturing patient monitoring equipment, utilising memory displays for E.C.G., blood pressure, temperature, etc.

We want:

Electronic Design Engineers - Graduate standard, with knowledge of C-Mos Digital and Logic Circuitry, Operational Amplifiers and CRT Drive Amplifiers. Engineers will use their own initiative and previous experience to design circuits around technical requirements.

Test/Service Engineers - with good experience of fault finding associated with Digital and Analogue Circuitry, and for checking and repairing equipment as described above.

You receive:

Good salaries - participation in bonus schemes - good working conditions and promotional prospects.

Apply:

In writing to the Personnel Manager,  
Albury Instruments Limited,  
165 Dukes Road, London W3 0SL.

### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

### EDUCATIONAL

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford, RM7 0XU (\*phone Romford 66841).

### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS  
Dept. D272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS  
Dept. D272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS  
Dept. D272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### TAPE EXCHANGES

RECORDER OWNERS (cassette/ree) can now speak to the world! All ages... every interest. Send stamp: WORLD-WIDE TAPETALK, 35 The Gardens, Harrow.

### BOOKS AND PUBLICATIONS

COMPREHENSIVE TV REPAIR INSTRUCTIONS for your set £5.00 with circuit (if requested). Free catalogue unique T.V./other publications AUSE (PE) 76, Church Street, Larkhall, Lanarkshire ML9 1HE.

### RECORD ACCESSORIES

STYL! for Hi-Fi, Music Centres. I11. List for s.a.e. Also cartridges, leads, accessories. Details-Felstead Electronics (PE) Longley Lane, Gatley, Cheshire, SK8 4EE.

### FOR SALE

SEEN MY CAT? 5000 Odds and ends. Mechanical Electrical. Cat free. Whiston, Dept. PRE, New Mills, Stockport.

NEW BACK ISSUES of "PRACTICAL ELECTRONICS" available 70p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

RAINBOW RIBBON Cable at silly prices SAE for details. Trading Post, 4 Castle Street, Hastings, Sussex.



### PRACTICAL ELECTRONICS P.C.B.'s

in glass fibre tinned and drilled

Dec. 77 Car Burglar Alarm 1412-1 69p.  
 May 78 Moving Light Display £2.76.  
 July 78 Dimwit £1.78. Aug 78 Touch Switch 65p.  
 Aug 78 Digital Thermometer, two boards £1.45.  
 Oct. 78 High Performance Power Supply £2.18.  
 Oct. 78 Analogue Computer:  
 Overlord £3.31. Relay £2.41. Main £6.85.  
 Nov. 78 Auto Light £1.00.  
 Dec. 78 RC Motor Control 67p. RC Fall Safe 39p.  
 Guitar Sound Multiprocessor £2.95.  
 For full list and current boards please send S.A.E.  
 P.C.B.'s also produced from customer's own master -  
 please send for quote.

Postage - On orders less than £10.00 please add 25p.  
 postage. C.W.O. please.

#### PRD TO DESIGN

14 Oownham Road, Ramsden Heath, Billericay,  
 Essex CM11 1PU

**CLEARING LABORATORY.** Scopes, recorders, testmeters,  
 bridges, audio, R.F. generators, turntables, tapeheads,  
 stabilised P.S.U.s, sweep generators, test equipment, etc.  
 Lower Beeding 236.

### BUILD THE TREASURE TRACER

#### MK III Metal Locator



- Variable tuning
- B-ring a best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Precut search coil assembly
- Fine transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC1 and BBC 2 TV

Send stamped, addressed envelope  
 for leaflet

Complete Kit £15.95 Built and tested £20.95  
 Post £1.20 - £1.37 VAT Post £1.20 - £1.77 VAT

MINIKITS ELECTRONICS 69 CLEVELAND ROAD  
 LONDON E18 2AN

**BAIRD STYLE TELEVISION.** Inexpensive, recordable, amateur  
 television, through NBTVA, membership £1.50. Write:—  
 I. Burnwood Drive, Wollaton, Nottingham.

#### NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1.13,  
 SUB C £1.47, HP 11 (C) £2.15, HP 2 (D) £3.27, PP3  
 £4.09, PP3 not suitable for fast charge, PP3 charger £5.81.  
 All above Nickel Cadmium batteries are guaranteed 'EVER  
 READY' full spec, and are supplied complete with solder  
 tags (except PP3). Just in stock—New rechargeable sealed  
 lead acid maintenance free batteries suitable for burglar  
 alarms etc., 1-2 amp hr 6v. £4.40 2-6 amp hr. 6v £5.65.

Quantity prices available on request. Oate and charging  
 circuits free on request with orders over £10 otherwise 30p  
 post and handling (specify battery type), all prices include  
 VAT. Please add 10% P & P on orders under £10. 5% over  
 £10.

Cheques, postal orders, mail order to **SOLID STATE  
 SECURITY DEPT PE 10, Bradshaw Lane, Parbold,  
 Wigan, Lancs. 02575-4726.**

## FOR YOUR GUIDANCE VALUE ADDED TAX

Unless otherwise shown,  
 all prices in advertisements  
 are inclusive of VAT. Where prices are  
 exclusive, readers should  
 ensure that they have  
 added the correct amount  
 of VAT before ordering.

Export orders are not  
 subject to the addition of  
 Value Added Tax.

Readily available Hardware and  
 Accessories for Home Constructors,  
 Dev. Engineers, Modelmakers.  
 Selected range of quality components,  
 Drawing materials for p.c. boards,  
 Reliable resist coated epoxy glass  
 laminate, no unusual chemicals.  
 Printed circuit boards, top quality to  
 personal designs, prompt service.  
 Photography for p.c.b.  
 Solid tungsten carbide drills.  
 All immediately available.  
 Catalogue 15p stamps please to:

### RAMAR CONSTRUCTOR SERVICES,

Masons Rd. Stratford on Avon  
 Warwks. CV37, 9NF 0789-4879

#### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Trans-  
 mitter-Receiver Kit. Only £9.75 plus 25p  
 P. & P.

'Brain-Freeze' 'em with a MINI-STROBE  
 Kit, pocket-sized 'lightning flashes', vari-speed,  
 for discos and parties. A mere £4.30 plus 20p  
 P. & P. Experiment with a psychedelic  
 DREAM LAB, or pick up faint speech/sounds  
 with the BIG EAR sound-catcher; ready-made  
 multi-function modules. £5 each plus 20p  
 P. & P.

LOTS MORE! Send 20p for lists. Prices include  
 VAT.

### BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh  
 Ewell, Surrey (P.E.)

#### I. C. EXPERIMENTAL/EDUCATIONAL KITS

This popular series of Kits on Digital Logic techniques has  
 now been further improved to include additional com-  
 ponents, resulting in greater constructional flexibility and  
 educational capacity. Each Kit contains selected I.C.'s,  
 Holders, Veroboard, L.E.D.'s and Instructions. Available at  
 £5.00 each (inc. p. & p.).

Kit One - Gates Kit Two - Flip-Flops  
 Kit Three - Shift Registers Kit Four - Counters  
 Kit Five - Displays

S.A.E. for further details to:

**AUTOMATED HOMES**  
 69 High Street, Ryton, Coventry CV8 3FJ  
 (mail order only)

**MICROJET WELDER**  
 A TINY FLAME UP TO  
 5000°F!  
 WELDS - BRAZES  
 SOLDERS

**£22.50  
 INC. FLAME  
 TIPS**

Precision tool using combination of  
 butane and compressed oxygen or  
 micronox. A pencil lead thin flame  
 size, adjustable to 5,000° F. Cuts metals, welds, brazes  
 and solders gold, silver. Ideal modelling, electricians,  
 opticians, dentists, silversmiths, jewellery, clockmakers,  
 electronic and computer servicing. Up to 30 minutes use  
 on fuel supplied. Replacement set of 2 micronox, 1  
 butane cylinder £2.10 + 25p p&p extra. Only £22.50 +  
 £1.35 p&p. Access accepted.  
**JOHN DUDLEY & CO. LTD. (Dept. PE17),**  
 Carolyn House, Water Road, Wembley, Middx.  
 (Mail Order).  
 Tel. 01-438 5456, before noon.

**AERIAL BOOSTERS.** Improve weak VHF Radio and Televi-  
 sion reception, price £5. S.A.E. for Leaflets. Electronic  
 Mailorder Ltd., Ramabottom, Bury, Lancashire. BL0 9AG.

#### TRANSISTORISED IGNITION KIT

\*£4.86 incl. carr & VAT\*

Complete pack of parts with p.c.b. to build our transistorised  
 ignition system based on Darlington Power Transistors specially  
 developed for auto ignition.

Send S.A.E. for FREE CIRCUIT diagram.

All components with p.c.b. (less case) £4.86.

**SOLEC PRODUCTS,**

68 Dole Street, Manchester, M1 2HS.

### INTERLOCKING PLASTIC STORAGE DRAWERS

NEAT!  
 ROBUST!  
 TIDY!

DISCOUNT  
 PRICES



5 SIZES  
 ALL INTERLOCK

Newest, neatest system ever  
 devised for storing small  
 parts and components: resistors,  
 capacitors, diodes, transistors, etc.  
 Rigid plastic units interlock together in  
 vertical and horizontal combinations.  
 Transparent plastic drawers have label slots. 1D and 2D  
 have space dividers. Build up any size cabinet for wall,  
 bench or table top.

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2 1/2in x 2 1/2in) £3.50 DOZEN.  
 DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in) £5.50 DOZEN.  
 TREBLE (3D) £5.50 for 8.  
 DOUBLE TREBLE 2 drawers, in one outer case (6D2),  
 £7.90 for 8.  
 EXTRA LARGE SIZE (6D1) £6.90 for 8.

#### PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%. Orders over £60, less 7 1/2%. PACK-  
 ING/POSTAGE/CARRIAGE: Add £1.00 to all orders under  
 £10. Orders £10 and over, please add 10% carriage.  
 QUOTATIONS FOR LARGER QUANTITIES.  
 Please add 8% V.A.T. to total remittance.  
 All prices correct at time of going to press.

**4-WAY  
 IN-LINE  
 13 AMP  
 POWER  
 PANEL**

NEON INDICATOR  
 LAMP

PATENT  
 CABLE  
 LOCK

EASILY  
 ACCESSIBLE  
 FUSE

**MOUNT IT  
 OR TRAIL IT!**

Modern, slim-line power panel, countless uses in home,  
 office, factory, showrooms. Perfectly safe, unbeatable. Can  
 be mounted on wall or trailed anywhere in room. Neat  
 rubber base. Smart PVC outer cover. White £3.30.  
 P&P 60p.

#### FLAIRLINE SUPPLIES (PE 2)

124 Cricklewood Broadway, London N.W.2  
 Telephone 01-450 4844

## NOTICE TO READERS

*Whilst prices of goods  
 shown in classified  
 advertisements are  
 correct at the time  
 of closing for press,  
 readers are advised  
 to check with the ad-  
 vertiser both prices  
 and availability of  
 goods before order-  
 ing from non-current  
 issues of the magazine*

# CHROMASONIC electronics

your soundest connection in the world of components

Dept PE1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

The items shown in this advert are just a small selection taken from our new 78/79 Catalogue which is now available. It contains everything from Resistors to the latest in Micro-processors. Don't delay order your copy today. The price is only 40p (inc. 45p vouchers).

TELEPHONE: 01-883 3705

## Low Power Schottky and TTL

## CMOS

I.C. sockets

## BITS and PIECES

## Regulators

## Linear I.C.'s

N	LS	N	LS	N	LS	4000	.15*	4053	81*	DIL (Texas)	Static RAM's	1+	17	63	64+	78M Series	CA3080	.75				
7400.13*	.19*	7449	.16*	74136	.39*	74191	1.21*	.75*	4001.16*	4054	1.29*	2102A	(350ns)	1.05*	.95*	.88*	4 (POS) 500mA	CA3130E	90			
7401.13*	.19*	7450	.16*	74138	.55*	74192	1.21*	1.85*	4002.16*	4056	1.46*	2102A-2	(650ns)	1.29*	1.15*	1.08*	5v. 8v. 12v. 15v.	LM3014AN	37			
7402.15*	.19*	7451	.16*	74139	.55*	74193	1.21*	1.85*	4006	92*	4059	5.18*	2111A	1	(500ns)	2.46*	2.19*	2.05*	LM324N	30		
7403.15*	.19*	7453	.16*	74141	.76*	74194	1.21*	1.85*	4007	18*	4060	1.24*	2112A-2	(250ns)	1.07*	.95*	.86*	79M Series	LM348N	99		
7404.16*	.21*	7454	.16*	74145	.75*	74195	1.81*	1.05*	4008	92*	4066	4.8*	2112A-2	(350ns)	1.07*	.95*	.86*	-NEG) 500mA	LM380N	97		
7405.16*	.21*	7455	.16*	74147	1.59*	74196	1.18*	1.05*	4009	54*	4068	2.1*	2114	(450ns)	8.10*	7.19*	6.75*	5v. 6v. 8v. 12v. 15v.	LM381N	1.33		
7406.26*	.19*	7460	.16*	74148	1.32*	74197	1.18*	1.05*	4010	54*	4069	2.1*	28 pin	26*	2114	(450ns)	8.10*	7.19*	6.75*	20v & 24v.	LM382N	1.33
7407.26*	.19*	7470	.27*	74150	1.02*	74198	1.81*	1.85*	4011	18*	4070	2.1*	40 pin	44*	8810	3.50*	2.97*	2.52*	All 85p* each	LM390N	65	
7408.17*	.19*	7472	.23*	74151	.67*	74199	1.81*	1.85*	4012	18*	4071	2.1*	8 pin	10*	8800	6.95*			78 Series	SN7601N	1.02	
7409.17*	.19*	7473	.28*	74153	.67*	74221		.99*	4013	48*	4072	2.1*	8 pin	23	8800	8.99*			4 (POS) 1A	SN7603N	2.32	
7410.15*	.19*	7474	.28*	74154	1.21*	74240		2.25*	4014	32*	4077	2.1*	14 pin	34*	9800	42.50*			5v. 8v. 12v. 15v.	SN76013N	1.55	
7411.25*	.19*	7475	.46*	74155	.67*	74241		2.25*	4015	32*	4081	2.1*	18 pin	37*	E-Prom's UV	8195P	1.49*		All 85p* each	SN76023N	1.55	
7412.18*	.19*	7476	.30*	74156	.67*	74242		2.25*	4016	43*	4082	2.1*	18 pin	43*	1702AD	5.57*			79 Series	TBAE10AS	.90	
7413.27*	.40*	7478	.29*	74157	.67*	74243		2.25*	4017	81*	4085	92*	18 pin	43*	2708D	7.87*			-NEG) 1A	ZN414	90	
7414.71*	.79*	7482	.73*	74158	.58*	74247		.95*	4018	92*	4086	92*	20 pin	55*	TriState Buffers	8198P	1.49*		5v. 8v. 12v. 15v.	ZN424E	1.35	
7415	.19*	7483	.75*	74160	1.21*	74248		.95*	4019	56*	4083	81*	24 pin	60*	81LS95	.75*			All £1.00* each	ZN425E	3.78*	
7416.25*	.19*	7485	1.18*	74161	1.21*	74249		.95*	4020	32*	4089	1.81*	28 pin	65*	81LS96	.75*			µA723 (OIL)	ZN1034E	2.04	
7417.34*	.19*	7486	.25*	74162	1.21*	74251		.95*	4021	32*	4092	92*	38 pin	95*	81LS97	.75*			LM304H	ZN1040E	8.43*	
7420.16*	.19*	7489	2.60*	74163	1.21*	74253		.99*	4022	92*	4098	2.46*	38 pin	95*	81LS97	.75*			LM323K	ZNA116E	6.75*	
7421	.19*	7490	.34*	74164	1.02*	74257		.99*	4023	18*	4510	1.07*	40 pin	105*	81LS98	.75*			CD4011	7 for £1.00*		
7422	.19*	7491	.73*	74165	.78*	74258		.99*	4024	.65*	4511	.95*			74365	.75*			LM380	3 for £2.50		
7423.25*	.19*	7492	.46*	74166	1.02*	74259		1.50*	4025	.18*	4514	2.70*			74366	.75*						
7425.25*	.19*	7493	.34*	74168	.65*	74266		.35*	4026	1.84*	4515	2.70*			74367	.75*						
7426.25*	.19*	7495	.54*	74169	.88*	74273		2.25*	4027	.51*	4516	1.07*			74368	.75*						
7427.39*	.19*	7496	.67*	74170	1.85*	74279		.48*	4028	.70*	4517	4.10*										
7428.38*	.19*	74107	.27*	74173	1.41*	74283		.99*	4029	1.18*	4518	.95*										
7430.16*	.19*	74109	.44*	74174	1.01*	74290		.83*	4030	.56*	4521	2.54*										
7432.25*	.25*	74112	.25*	74175	.81*	74293		.83*	4032	1.08*	4522	1.89*										
7433	.19*	74113	.35*	74176	1.01*	74295		1.85*	4034	1.89*	4526	1.89*										
7437.25*	.25*	74114	.35*	74177	1.01*	74298		1.25*	4035	1.06*	4528	.92*										
7438.25*	.25*	74121	.27*	74180	1.01*	74385		.51*	4040	.92*	4534	7.12*										
7440.17*	.19*	74122	.50*	74181	2.21*	74386		.51*	4042	.70*	4536	3.74*										
7441.70*	.19*	74123	.60*	74182	.81*	74387		.51*	4043	.81*	4543	1.62*										
7442.50*	.55*	74124	.25*	74184	1.81*	74388		.51*	4046	1.06*	4553	4.53*										
7445.60*	.19*	74125	.51*	74185	1.62*	74389		.39*	4049	.43*	4566	1.51*										
7446.60*	.19*	74126	.51*	74186	2.97*	74670		1.85*	4050	.43*	4583	1.02*										
7447.60*	.87*	74132	.72*	74189	3.17*				4051	.81*	4585	1.87*										
7448.60*	.87*	74133	.19*	74190	1.21*	.75*			40F2	.81*	4585	1.87*										

V.A.T. Inclusive prices \*8% others 12.5%. Export Customers deduct V.A.T. 2/27 from \*1/9 from others. Postage and Packing 25p. Trade and Export Inquiries most Welcome. Hours 9.00am-5.00pm.

Now available our ORDER-RING line, just phone your order through with your Access or Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00).



## IT'S EASY WHEN YOU KNOW!

To avoid missing your copy of **PRACTICAL ELECTRONICS** - simply complete this order form and hand it to your newsagent.

### ORDER FORM

To: ..... (name of newsagent)

Address .....

Please reserve/deliver every month one copy of **PRACTICAL ELECTRONICS** until further notice.

My Name .....

Address .....

## THE BASIC COOKBOOK

- by K. Tractor Price: £3.95
- 110 WAVEFORM GENERATOR PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price: £3.15
- YOUR OWN COMPUTER by M. Waite Price: £1.70
- UNDERSTANDING DIGITAL ELECTRONICS by G. McWhorter Price: £3.95
- BEGINNER'S GUIDE TO TAPE RECORDING by I. R. Sinclair Price: £3.15
- BEGINNING BASIC by P. E. Gosling Price: £3.15
- THE CATHODE-RAY OSCILLOSCOPE & ITS USE by G. N. Patchett Price: £4.00
- RAPID SERVICING OF TRANSISTOR EQUIPMENT by G. J. King Price: £2.75
- COLOUR T.V. WITH PART. REF. TO THE PAL SYSTEM by G. N. Patchett Price: £6.00
- ELECTRONICS & RADIO AN INTRO. by M. Nelkon Price: £3.20
- THE CHEAP VIDEO COOKBOOK by D. Lancaster Price: £6.95

\* ALL PRICES INCLUDE POSTAGE \*

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-23 PRAED STREET LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

## CANON COMPONENTS

Low imp Dynamic Mic's Brand new in packs £1.62

Triacs 10 amp. 400v brand new AEI full spec. all with fitted heavy duty heat sink £2.55

22 way edge connectors Ex equipment but clean 0.15 matrix gold plated complete with locating pin Only 58p

17 way edge connectors Brand new. 15 pitch complete with locating pin and fixing brackets. Tinned. Only 35p

Connecting wire 15p per 10 metres or mixed at £3.00 per kilo approx.

Tagstrips 30 way new 15p

Group Board 17 or 34 way brand new 12p and 24p

## DIAL-A-BOX

As featured in "P.E. MARKET PLACE" a comprehensive standard range of boxes for the constructor, or custom built to your specification. Send your requirements with S.A.E. or phone for quote.

Lamp panels with over thirty lampholders fitted ideal for light displays or moving light shows. Only 85p

Mains selector panels from 200v-250v. Brand new. 20p each

Cable Ties long re-usable 6" plus. 3p each.

Transformers 20-0-20v 400 mA £2.50 each.

4mm Screw Terminals assorted colours of our choice £1.00 for six.

## STOP PRESS!

P. E. Guitar Sound Multiprocessor Send SAE for quotation for a purpose built case for this project.

All prices include VAT - Please add 65p Post & Packing per item to total cost of order. Open daily 9.30am-6pm - Access or Barclaycard accepted - S.A.E. for lists.

322-334 WHITEHORSE ROAD, CROYDON, SURREY CR0 2LF

TEL: 01-684 9872

# TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

**12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS**

Ref	12V	24V	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2	1	3.81	0.78
18	4	2	4.03	0.96
85	5	2.5	5.00	0.79
70	6	3	5.35	0.96
108	8	4	7.42	1.14
72	10	5	8.12	1.14
116	12	6	8.99	1.32
17	16	8	10.72	1.32
115	20	10	13.98	2.08
187	30	15	17.06	2.08
226	60	30	36.14	OA

**50 VOLT RANGE**

Pri 220/240V Sec 0-20-25-33-40-50V. Voltages available 5, 7.8, 10, 13.15, 17, 20, 33, 40 or 20V-0-20V, 25V-0-25V.

Ref	Amps	£	P & P
102	0.5	3.41	0.78
103	1.0	4.57	0.96
104	2.0	7.16	1.14
105	3.0	8.56	1.32
106	4.0	11.41	1.50
107	6.0	15.06	1.64
118	8.0	20.26	2.08
119	10.0	24.98	OA

**MAINS ISOLATORS (SCREENED)**

Pri 120/240V SEC 120/240V (C. Tapped)

Ref	VA (Watts)	£	P & P
07*	20	4.40	0.78
149	50	6.70	0.96
150	100	7.61	1.14
151	200	11.16	1.50
152	250	13.28	1.84
153	350	16.43	1.84
154	500	20.47	2.15
155	750	29.06	OA
156	1000	37.20	OA
157	1500	51.38	OA
158	2000	61.81	OA
159	3000	86.66	OA

\*Pri 0-220-240 Sec 115 or 240V State volts required

**HIGH VOLTAGE ISOLATORS**

Prim 200/220V or 400/440V Sec 110/120V CT or 200/240 CT

VA	Ref	£	P & P
60	243	6.70	1.32
350	247	16.43	1.84
1000	250	37.10	OA
2000	252	61.81	OA

**30 VOLT RANGE**

Pri 220/240V Sec 0-12-15-20-24-30V. Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V, 15V-0-15V.

Ref	Amps	£	P & P
112	0.5	2.64	0.78
79	1.0	3.77	0.96
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.84

**60 VOLT RANGE**

Pri 220/240V Sec 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24V-0-24V, or 30V-0-30V.

Ref	Amps	£	P & P
124	0.5	3.88	0.96
126	1.0	5.91	0.96
127	2.0	7.60	1.14
125	3.0	11.00	1.32
123	4.0	12.52	1.84
40	5.0	18.84	1.64
120	6.0	18.06	1.84
121	8.0	25.56	OA
122	10.0	29.85	OA
189	12.0	34.06	OA

**AUTO TRANSFORMERS**

Ref	VA (Watts)	£	P & P
113	15 0-115-210-240	2.48	0.71
64	75 0-115-210-240	4.01	0.98
4	150 0-115-210-240	5.35	0.96
87	500 0-115-210-240	10.99	1.84
84	1000 0-115-210-240	18.76	2.08
93	1500 0-115-210-240	23.36	OA
95	2000 0-115-210-240	34.82	OA
73	3000 0-115-210-240	59.21	OA
80S	4000 0-10-115-200-220-240	78.86	OA
57S	5000 0-10-115-200-220-240	89.50	OA

**CASED AUTO TRANSFORMERS**

240V cable in & 115V USA 2 pin outlet

VA	£	P & P	Ref.
75	7.73	1.14	64W
150	10.01	1.14	4W
200	9.92	1.45	65W
250	10.49	1.45	69W
500	19.17	1.64	67W
150	23.41	1.76	83W
1000	27.88	OA	84W
1500	26.02	OA	93W
2000	49.97	OA	95W

**SCREENED MINIATURES**

Ref	mA	Volts	£	P & P
238	200	3-0-3	2.57	0.55
212	1A, 1A	0.6-0.6	2.85	0.78
13	100	0-0-9	2.14	0.38
235	330, 330	0-9-0-9	1.99	0.38
207	500, 500	0.8-9-, 0.8-9	2.77	0.71
208	1A, 1A	0.8-9-, 0.8-9	3.53	0.78
236	200, 200	0-15-0-15	1.99	0.38
214	300, 300	0-20-0-20	2.80	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-0-15-20	4.63	0.96
203	500, 500	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	6.04	0.96
239	50	12-0-12	2.87	0.38

**TEST METERS**

U4315 Budget Meter 20KΩ/V DC 2KΩ/V AC 1000Ω/V AC/DC 2.5A AC/DC 500K res. in robust steel case and leads £15.85.

AV08 £81.70  
AV071 £33.50  
AV073 £45.20  
EM272 £53.70  
MM5 £28.66  
DA116 digital £102.00

TT169 incircuit transistor tester £34.75  
Megger BM7 Battery. £45-15  
Wee Megger £66.90  
Ever Ready Avo B Leather Case £21.05

P & P £1.15 VAT 8%.

Full range of AVO's, Megger's and Cases.

**MINI-MULTIMETER**

DC-1000V AC-1000V DC-100mA Res 150kΩ 1000Ω/V Bargain £7.20 P & P 62p VAT 8%

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V. DC currents to 250mA. Resistance to 3 Megs. 5" x 3 1/2" x 1 1/2". £14.36 P & P £1.05 VAT 8%.

**ISOLATOR - Special Price**

0-200-220-240V, 0-240V Centre Tap, 250VA Ref. 62 £5.20 P & P 96p

**ELECTROSIL** Metal oxide low noise resistors.

**ELECTRONIC CONSTRUCTION KIT**

Home electronics teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. Full instructions. £8.29 + VAT + 96p p&p.

**43mmx43mm PANEL METERS 82mmx78mm**

0-50µA	6.20	0-50µA	6.70	Carriage
0-500µA	5.95	0-500µA	6.70	65p
0-1mA	5.95	0-1mA	6.70	VAT 8%
0-30V	5.95	0-30V	6.70	
VU Ind Panel 90mm	250µA		£3.36	
VU Indicator Edge 54mm x 14mm	250µA		£2.60	

**Cassette Tapes Low Noise**

C60 30p P. & P. 15p  
C90 42p P. & P. 15p VAT 8%.

**COMPONENT PACKS**

65 High Quality Metal Oxide 5% 1/4w, 1/2w Resistors  
150 Mixed Value Capacitors  
10 Read Switch.  
50 Wire Wound Resistors,  
10 Caps 3000mf 30v.  
25 assorted Presets.  
50 Wire Wound Resistors,  
Hardware, B.A. nuts, bolts  
10 Caps 3000mf 30v.  
1 1/2 1/2p P & P 40p.

**TMK 500**

30K/V Mirror Scale Meter  
AC 0-2.5-10-25-100-  
250-500-1000V  
DC 0-2.5-1.2-5-10-25-  
100-250-1000V  
Resistance 0-6K-60K-  
6M-60M auto./load  
protection £23.30  
P. & P. £1.05 VAT 8%.

**NEW RANGE TRANSFORMERS**

Pri 0-120 or 220-240V  
Sec. 0-36-48 twice. To give  
36-0-36, 48-0-48 72V or 92V.

3A	£14.70	P & P £1.48
4A	£18.77	P & P £1.84
5A	£28.64	P & P £2.15

Pri 0-220-240V 2 Amp. 45-36-0-  
36-45 £9.89

**Ref Amps Price P & P**

171	0-CT-15V	500MA	£2.09	0.45
172	1A	£2.96	0.78	
173	2A	£3.59	0.78	
174	3A	£3.75	0.86	
175	4A	£5.73	0.96	

**S-DECS**

Solderless bread boarding

S Dec 70 contacts	£3-10
T Dec 208 contacts	£4-35
U Dec "A" for I.C.s etc	£4-50
U Dec "B" for I.C.s etc	£6-99

VAT 8% P & P 40p

**ANTEX SOLDERING IRONS**

15W	£3.75	Stand £1.52
25W	£3.95	+ 12 1/2% VAT

P & P 46p VAT 8%

**BRIDGE RECTIFIERS**

100V*	100A	£2.10
200V	2A	£0.45
400V	4A	£0.88
400V with heat sink	6A	£1.40
*500V PM 7A5	12A	£2.85

VAT 12 1/2% P & P 15p VAT 8%

**AMPLIFIER MODULES**

10W (AL30)	£3.75
25W (AL60)	£4.57
35W (AL80)	£7.15
125W (AL250)	£17.25

Power Supply PS12 £1.30  
Power Supply SP8M0 £4.25  
Pre-amp PA12 PA100 £13.88  
VAT 12 1/2% P & P 35p

**ABS Plastic Boxes** inset brass nuts, slots to take PC cards, flush fitting lid.

PB1	80mmx62x40	65p
PB2	100mmx75x40	73p
PB3	120mmx100x45	87p
PB4	215mmx130x85*	£2.54

P & P 29p. VAT 8% (40p)

**Plug In Save Batteries**

P126 - fits into 13A SKT 6, 7, 5, 9V, 300MA multipin outlet £4.00. P & P 55p. VAT 12 1/2%.

**TRANSFORMERS**

Special Offer

P.W. Purbeck oscilloscope transformer in stock 250-0-250 6-3V, 12-9V £6.50 P & P 90p.

**BE3 100V line to 4.0 7/10W £2.05 P & P 66p**

**BE4 0-120V x 2 (120V or 240V) Screen sec 9-0-9V 1A £2.40 P & P 71p**

**BE5 15W matching trans. sec 150V suit EL89 £1.50 P & P 30p**

**BE6 PR1. 0-220V sec 4500V. 10 MA £4.50 P & P £1.00**

**BE7 0-110-120 220V Pri 240V Sec 20V 1A £1.50 30p P & P.**

**BE8 0-240 15-0-15V 2A £1.50 P & P 70p.**

**Ref 30 240-240 Isolator 200VA £4.20 P & P 96p.**

**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

## INDEX TO ADVERTISERS

Ace Mailtronix Ltd.....	4	Electrovalue.....	3	Norman Inskip.....	73
Adam Hall (P.E. Supplies).....	85	Fladar.....	76	P.K.G. Electronics.....	85
Altken Bros.....	16	Flairline Supplies.....	86	Phonosonics.....	6, 7
Alben Engineering.....	7	Fotherby, Willis Electronics Ltd.....	4	Progressive Radio.....	76
Albury Instruments Ltd.....	84	Garfields.....	85	Proto Design.....	86
Alcon Instruments Ltd.....	72	Goddards Components.....	74	Radio Component Specialists.....	2
Astra-Pak.....	78	Greenweld Electronics.....	72	Ramar Constructor Service.....	86
Automated Homes.....	86	H.L. Audio.....	71	R.S.T. Valve Mail Order.....	76
Barrie Electronics.....	88	Harversons.....	12	Radio & T.V. Components.....	69
Bi-Pak.....	8, 9	Heathkit Ltd.....	74	Saxon Entertainments.....	14, 15
Birkett, J.....	4	Home Radio.....	12	Scientific Wire Co.....	85
Boffin Projects.....	86	I.C.S. Intertext.....	54, 84	Sentinel Supply.....	15
Boss Industrial Mouldings Ltd.....	10, 11	I.L.P. Electronics.....	81	Service Trading.....	cover iii
British National Radio & Electronics School.....	17, 75	Ibek Systems.....	84	Sinclair Radionics Ltd.....	57
Cambridge Kits.....	85	J.W.B. Radio.....	84	Solec Products.....	86
Cambridge Learning.....	79	Kramer & Co.....	82	Solid State Security.....	86
Calscope (Scopex).....	16	Lektrokit Ltd.....	13	Special Products.....	83
Cannon Components.....	87	Lord, Jeremy.....	58	Squire, Roger.....	12
Chromasonic.....	87	Maplin Electronic Supplies.....	cover iv	Staravia Ltd.....	84
Clef Products.....	54	Marshall A. (London) Ltd.....	70	Sugden, A. R.....	16
Codespeed.....	82	Metac.....	78	Swanley Electronics.....	54
Continental Specialties.....	53	Micro Systems.....	15	Technomatic Ltd.....	80
Crescent Radio Ltd.....	72	Micron R/C.....	85	Teleplay (Logic Leisure).....	cover ii
Crimson Elektrik.....	58	Mill Hill Supplies.....	76	T.K. Electronics.....	2
Crofton Electronics.....	83	Minikits Electronics.....	86	T.L.C.....	85
C.R. Supply Co.....	84	Modern Book Co.....	87	T.U.A.C.....	77
Davian Electronics.....	2	Monolith.....	82	Vero Electronics.....	58
Dudley, John & Co. Ltd.....	86			Watford Electronics.....	5
E.D.A.....	83			Wilmslow Audio.....	54
Electroni-Kit Ltd.....	82				

## RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock, phone or write in your enquiries.

### FT3 NEON FLASH TUBE

High intensity multi turn, high voltage, neon glow, discharge flash tube. Design for ignition timing. etc. £1.50. P. & P. 25p (£1.89 inc VAT) 3 for £3. P. & P. 50p (£3.78 inc VAT & P.)



### RODENE UNISET TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding, mixing, etc. Price £6 P. & P. 60p.



### WHY PAY MORE?

MULTI RANGE METER Type MF15A a.c. d.c. volts 10 50 250 500 1000 Ma 0-5 0-10 0-100. Sensitivity 2000V. 24 range diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.10 inc VAT & P.)



### METERS (New) - 90 mm DIAMETER

A.C. Amp. Type 6272. 0-1A, 0-5A, 0-20A. A.C. Volt. 0-150V, 0-300V. D.C. Amp. Type 65C5. 0-2A, 0-10A, 0-20A. D.C. Volt. 0-15V, 0-30V. All types £3.50 ea. + P. & P. 50p (£4.12 incl VAT), except 0-1000A. D.C. price £5.00 + 50p P. & P. (£5.94 incl VAT).



### NEW HEAVY DUTY SOLENOID. mfg.

By Magnetic Devices. 240V a.c. operation approx. 10lbs pull (intermittent rating) at 1/2 in. Price £4.00 P. & P. 60p (£4.96 inc VAT & P.). N.M.S.



### A.C. SOLENOID pve ether type 176/2

240 AC. Approx 1lb at 1/2 inch, intermittent rating. Price £1 p&p 20p (£1.30 inc VAT + P).

WESTPOOL TYPE MM8 Model 2, 240V AC. Approx 1 1/2 lb pull at 1/2 inch. Rating 1. Price £1.50 p&p 20p. (£1.84 inc VAT + P) N.M.S.

### MINIATURE UNISELECTOR

12 volt. 11-way, 4 bank (3 non-bridging, 1 homing). £2.50. P. & P. 35p (£3.08 inc VAT & P.). N.M.S.



### 240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet/outlet. Precision made. British mfg. Price £3.50 Post 50p (£4.32 inc VAT & P.). N.M.S.



### MICRO SWITCHES

Sub min Honeywell roller m/s type 3115m 906t. 10 for £2.50 post paid. LEVER OPERATED 20 amp. C/O. Mfg. by Unimax USA. 10 for £4, P. & P. 50p (min. order 10) (£4.86 inc VAT). D.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total inc VAT £3.02 (min. 10). Sub min lever m/s switch type MML 46 10 for £2.50. Post Paid £2.70 inclusive. N.M.S.



### MERCURY SWITCH

Size 27mm x 5mm, 10 for £5.00 (inc VAT £5.72) min quantity 10.



### VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max air delivery of 1.5 cubic metres per min. Max static pressure 600mm WG. Suction or blow from 2 side-by-side 37mm ID circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions length 22cm x width 25cm x height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12 - £150 P. & P. (£14.58 inc VAT & P.) Suitable transformer for 230 240V a.c. £6 - £1 P. & P. (£7.56 inc VAT & P.)



### CENTRIFUGAL BLOWER

#### Smith type FFB

1606 022 220/240V a.c. Aperture 10 x 4 1/4 cm overall size 16 x 14 cm. Price £3.75 P. & P. 75p. (inc. VAT £4.86). Other types available. S.A.E. for details.



### 24 volt. D.C. BLOWER UNIT

A precision 24 volt. D.C. .8 amp blower that works well on 12V 4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P. & P. 75p (inc. VAT £5.61). N.M.S.

### INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work. constant speed clutch. Size L 8in W 4in H 6in weight 6lb. 500V, 500 megohms. £49. Post 80p (£53.78 inc VAT & P.). 1,000V .000MΩ. £55. Post 80p (£60.26 inc VAT & P.). S.A.E. for leaflet.



## VARIABLE VOLTAGE TRANSFORMERS

### INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

200 watt (1 amp inc. a.c. voltmeter) £14.50  
0.5 KVA (2 amp MAX) £17.00  
1 KVA (5 amp MAX) £22.50  
2 KVA (10 amp MAX) £37.00  
3 KVA (15 amp MAX) £45.50  
5 KVA (25 amp MAX) £74.00  
10 KVA (50 amp MAX) £168.00  
15 KVA (75 amp MAX) £260.00



### CARRIAGE AND PACKING EXTRA

### LT TRANSFORMERS

0-10-15V at 3 amp (ex new equip) £2.50 P. & P. 50p (£3.24 inc. VAT)  
13-0-13V at 1 amp £2.50 P. & P. 50p (£3.24 inc. VAT)  
25-0-25V at 2 amp £4.50 P. & P. 75p (£5.67 inc. VAT & P.)  
0-4V/6V/24V/32V at 12 amp £18.50 P. & P. £1.90 (£22.03 inc. VAT & P.)  
0-6V/12V at 20 amp £14.70 P. & P. £1.50 (£17.50 inc. VAT)  
0-12V at 20 amp £10.24V at 10 amp £12.00 P. & P. £1.50 (£14.58 inc. VAT & P.)  
0-6V/12V at 10 amp £8.25 P. & P. £1.25 (£10.26 inc. VAT)  
0-6V/12V/18V/20V at 20 amp £18.00 P. & P. £1.50 (£22.10 inc. VAT & P.)  
0-10V/17V/18V at 10 amp £10.50 P. & P. £1.50 (£12.96 inc. VAT)  
Other types in stock; phone for enquiries or send sae for leaflet.

### HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many so called 4 Joule strobes. Price £19.00. Post £1 (£21.60 incl. VAT & P.). Specially designed case and reflector for Hy-Light £8.80. Post £1 (£10.58 inc. VAT & P.).

### XENON FLASHGUN TUBES

Range available from stock S A E for details



### ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 20 watt £8.70 (callers only) 2ft. 20 watt £6.20. Post 75p. (£7.51 inc VAT + P.) (For use in stan bi-pin fittings) Mini 12 in. 8 watt £2.80. Post 35p. (£3.40 inc VAT + P.). 9 in. 6 watt £2.25. Post 35p. (£2.81 inc VAT + P.). 6 in. 4 watt £2.25. Post 35p. (£2.81 inc VAT + P.). Complete ballast unit, for either 6", 9" or 12" tube 230V AC op. £3.50. Post 45p. (£4.27 inc VAT + P.) Also available for 12V DC op. £3.50. Post 45p. (£4.27 inc VAT + P.). 400 watt UV lamp and ballast complete £31.50. Post £3. (£37.26 inc VAT + P.). 400 watt UV lamp only £11.25. Post £1.20 (£13.45 inc VAT + P.).

### SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Post 75p. S.A.E. (foolscap) for further details. Price only £60.00



### WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S A E (foolscap) for details

### Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding heavy duty brush assembly, continuously rated.  
25 WATT 10/25/50/100/150/250/500/1kΩ/1.5kΩ. £2.40. Post 20p (£2.81 inc. VAT & P.)  
50 WATT 100/250Ω £2.90. Post 25p (£3.40 inc. VAT & P.)  
100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £5.90 p & p 35p (£6.75 inc VAT).  
Black, Silver, Skirted knob calibrated in Nos. 1-9 1 1/2 in. dia. brass bush. Ideal for above Rheostats 24p each.



## RELAYS

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.84 inc. VAT & P.). T.E.C. open type 3 c/o. 10 amp £1.10 (£1.40 inc. VAT & P.). Omoron or Keywitch 1 c/o. 7 amp £1.00 (£1.30 inc. VAT & P.). D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.30 inc. VAT & P.). Sealed 12V 1 c/o 7 amp octal base £1.00 (£1.30 inc. VAT & P.). Sealed 12V 2 c/o 7 amp octal base £1.25 (£1.56 inc. VAT & P.). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P.). 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.67 inc. VAT & P.). (lamps = contact rating). P&P on any Relay 20p. Other types available — phone for details. N.M.S.

Diamond H heavy duty A.C. relay 230/240V a.c., two C/O contacts 25 amp res at 250 a.c. £2.50 p&p 50p. (£3.24 inc VAT + p&p) Special base 50p. N.M.S.

## VAT

AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED.

**SERVICE TRADING CO.**  
ACCOUNT CUSTOMERS MIN. ORDER £50.00

## PARVALUX MOTOR TYPE SD2

12 volt. D.C. shunt 1/2 H.P. Motor. Continuously rated 4,000 r.p.m. £10 P. & P. 75p (£11.61 inc. VAT). N.M.S.

## GEARED MOTORS

100 r.p.m. 115lb.in. 110V. 50Hz. 2 BA. single phase split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250mm. Dia 135mm. Spindle dia 15 mm. Length 145mm. Ex-equipment tested £12. Post £1 50 (£14.56 inc. VAT & P.). Suitable transformer 230/240V operation £8. Post 75p (£9.45 inc. VAT & P.).



## GEARED MOTORS

28 r.p.m. 20 lbs inch  
115v a.c. Reversible motor.  
71 r.p.m. 10 lbs inch  
115v a.c. Reversible motor.



Both types similar to above drawing. Price either type £4.75 p&p 75p (£5.94 inc VAT + p&p) Supplied complete with transformer for 240v a.c. operation £7.25 p&p £1.00 (£8.91 inc VAT + p&p)

CRUZEZ 230/240V AC 2RPM synchronous geared motor. £29.00 p&p 30p. (£3.45 incl VAT) (quantity discount available.)  
HAYDON 230/240V AC. 1RPM synchronous geared motor. £29.00 p&p 30p. (£3.45 incl VAT + P) N.M.S.

## FRACMO GEARED MOTOR

56 r.p.m., 50lb.in. 240V a.c. 50Hz. 0.7 amp. shap length 35mm. dia. 16mm. weight 6 kilos 600 grams. Price £15 00 P. & P. £1 50 (£17.82). N.M.S.



## PARVALUX GEARED MOTOR

230/240V A.C. 30 rpm 50lbs inch. Price £15.00 P. & P. £1.00 (£17.82 inc. VAT). N.M.S.

## PARVALUX GEARED MOTOR

230/250V a.c. 500 rpm. 3 1/2 inch. 2 right angled spindles £11.00 P. & P. £1.00 (£12.96 inc. VAT & P.). N.M.S.

## CITENCO 19 RPM

FHP motor type C 7333/15 220/240V a.c. 19 r.p.m. reversible motor. torque 14.5 kg. gear ratio 144-1. Brand new incl capacitors. our price £14.25. P. & P. £1 25 (£16.20 inc. VAT & P.). N.M.S.



## FRACMO MOTOR

1400 rpm H.P. continuously rated 115v a.c. fitted with anti-vibration cradle mounting. Supplied complete with transformer for 230/240V a.c. op. £10.00 P. & P. £1.00 (£11.88 inc. VAT & P.). N.M.S.

## ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon vana oil free vacuum pump and compressor. Approx 20 in. ch vacuum 10 P.S.I. at .79 CFM. Powered by 110V a.c. 1.8 amp. Parvalux motor fitted with additional shaft at rear, suitable light loads. inc. capacitor £14.00 p&p £1.50 (£16.74 inc VAT + p&p) Suitable transformer for 230/240V a.c. operation £5.00 p&p £1.00 (£6.48 inc VAT + p&p) N.M.S.



## BLOWER VACUUM PUMP

English Electric 3 phase AC motor 220/250V. Or 380/440V. 1,425 r.p.m. 1/2 h.p. continuously rated. Direct coupled to William Allday & Co. Aloosa carbon vein blower/vacuum pump 0.9 cfm 8.HG. Price £22 p&p £2 (£25.92 inc VAT + p) N.M.S.

## PROGRAMME TIMERS

12 cam model £7.50. Post 60p (£8.75 inc. VAT & P.). Also available for 50V operation. Price as above. N.M.S.



## Time Switch

Vanner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £7.75. P. & P. 75p (£9.18). R. & T.



## SANGAMO WESTON TIME SWITCH

Type S261 200/250V. a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia. 4 x 3 price £6.50 P. & P. 50p inc. VAT £7.56. Also available with Solar dia. R. & T.

## Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors. 10 for £1.50 p&p 50p. (£2.16 inc VAT + p&p) (Min 10) N.M.S.

## 230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2 in. Aluminium fan. Price £3.00. P. & P. 65p (£3.94). N.M.S.



KEY:  
N.M.S. New Manufacturers Surplus  
R. & T. Reconditioned and Tested

Personal callers only Open Saturdays

9 LITTLE NEWPORT STREET  
LONDON WC2H 7JJ  
Phone 01-437 0576

All Mail Orders—Callers—Ample Parking

Dept. PE, 57 BRIDGMAN ROAD  
CHISWICK, LONDON W4 5BB  
Phone 01-995 1560

Showroom open Mon.-Fri.



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disc to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

# MAPLIN

**ELECTRONIC SUPPLIES LTD**  
 All mail to:-  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road,  
 Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554155.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without! Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue—send the coupon now!

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.**  
 Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

PE2/7B

FLICKSON