

PRACTICAL

ELECTRONICS

MARCH 1979

50p

16 NOTE SEQUENCER



PROVIDES BASS
ACCOMPANIMENT,
BACKGROUND RHYTHMS
OR MELODY LINES

...also in this issue



... LOGISCOPE

Introducing the personal computer you've waited for. THE EXIDY SORCERER.

SORCERER COMPUTER SYSTEM

Complete with Monitor

The Sorcerer Computer is a completely assembled and tested computer system. Standard configuration includes 63-key typewriter-style keyboard and 16-key numeric pad, Z80 processor, dual cassette I/O with remote computer control at 300 and 1200 baud data rates, RS232 serial I/O for communications, parallel port for direct Centronics printer attachment, 4K ROM operating system, 8K ROM Microsoft BASIC in Rom Pac™ cartridge, composite video of 64 char/line 30 line/ screen, 128 upper/lower case ASCII set and 128 user-defined graphic symbols, operation manual, BASIC programming manual and cassette/video cables, connection for S-100 bus expansion.

only **£950** Credit facilities available. + 8% VAT



LOOK!

- *32K RAM on board
- *RS232 interface
- *8K BASIC ROM
- *CUTS interface
- *4K MONITOR
- *KANSAS CITY interface
- *\$100 BUS
- *User defined graphic symbols
- *Z80 cpu

KEY BOARD

756 GEORGE RISK

Brand new professional ASCII keyboards (USA)

Full technical details included. RRP £60.00

Only **£49.90**

+ 8% VAT.

Ready built, tested and guaranteed.



COMPUTER JOYSTICK


Plugs into your Nascom P.I.O. No extras. Software and full documentation supplied. Plus free game cassette.

£14.90 each £28.90 per pair

COMP PRO Mixer

Professional audio

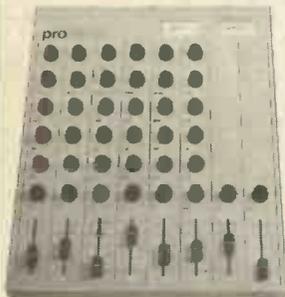mixer that you can build yourself and save over £100.



6 into 2 with full equalization and echo, cue and pan controls.

All you need for your own recording studio is a stereo tape or cassette recorder.

This superb mixer kit has slider faders, level meters and additional auxiliary inputs.

Only **£99.90** plus 8% VAT for complete kit Plus **FREE** power supply valued at £25.00

Ideal for

DISCOS STAGE MIXING HOME STUDIOS AND MANY OTHER APPLICATIONS

COMPUTER COMPONENTS

Send for our Spring 1979 catalogue. 0.60p Full of Computer Components, Peripherals and systems.

Teleplay presents the PROGRAMAGAME of all time!

TELEPLAY have produced a new product save pounds in the long run. Works OK on black and white TV. Just ADD each new cartridge, and your colour video centre will be up to date the Teleplay way. You will use the Teleplay way.

EX-STOCK IMMEDIATE DELIVERY

REALISTIC SOUND EFFECTS

We offer all this to you for ONLY **£28-90** + £2.31 VAT Fully Assembled **£35.90**

The Teleplay Kit consists of a Professional Finished Inject Moulded Box - Joystick Hand Controls - one cartridge which consists of 10 games - Football, Tennis, Solo Squash (1 & 2 players), Hockey, etc. Mains Adaptor. All holes are pre-drilled - No Special equipment required - It is to assemble this professional kit! Instruction Manual supplied separately at 0.45p. TELEPLAY GIVES YOU TWICE THE FUN BUILDING AND PLAYING THE MOST PROFESSIONAL TV GAME KIT EVER OFFERED.

Men Combs has 3 Facility Handicapping Switches

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game

Additional cartridges NOW available include:

- Stunt Cycle - 4 games - Cartridges and Hand Controls - £14.90 + £1.14 VAT
- Tank Battle - Cartridge and Hand Controls - £18.90 - £1.51 VAT
- Road Race - 2 games - Cartridge - £12.90 + £1.03 VAT

Wipe Out cartridge - 6 games £13.90 + £1.11 VAT

Cartridges come complete with printed case and easy to follow assembly instructions.

All parts fully guaranteed

Electrical knowledge is not a necessity to assemble this project - just simple soldering.

INTERESTED IN HOME COMPUTING?

FREE B BUG valued at £23.00 plus 10 x C12 cassettes valued at £4.00 WITH EVERY NASCOM

Start now and don't get left behind THE NASCOM 1 is here Ex-stock with full technical services

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most out of your computer. You can OBTAIN and EXCHANGE programs and other software - many now available.

The Powerful Z80 Microprocessor Professional Keyboard 1 Kbyte Monitor in EPROM 2 Kbyte RAM (expandable) Audio Cassette interface Plugs into your domestic TV Easy construction from straightforward instructions - no drilling or special tools - Just neat soldering required:



Only **£197.50** + 8% VAT (includes p & p + insurance)

Manuals separately	2.95	Monitor quality improved	
Z80 programming Manual	6.90	TV Modulator	2.50
Z80 Technical Manual	2.95		
P10 Technical Manual	2.95	Power supply suitable for NASCOM	19.90

(All prices add 8% VAT)

NASCOM AD ONS - Nascom improved monitor B Bug (2K) featuring - *Four times tape speed *Direct text entry without ASCII *Extended keyboard facility *Additional useful subroutines **£23.00**

Nascom Software library. Send SAE for lists and prices.

BLANK C12 Racal Quality CASSETTES £4.00 for 10

All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD or ACCESS number.



COMP COMPUTER COMPONENTS

14 STATION ROAD · NEW BARNET · HERTFORDSHIRE · TEL: 01-441 2922 (Sales)
CLOSE TO NEW BARNET BR STATION - MOORGATE LINE 01-449 6596
OPEN - 10am to 7pm - Monday to Saturday

PRACTICAL ELECTRONICS

VOLUME 15 No. 3 MARCH 1979

CONSTRUCTIONAL PROJECTS

- LOGISCOPE** by R. A. Penfold
Gives logic levels and mark space ratio/frequency data 18
- SEQUENCER—1** by Lindsay Robinson
Enables sixteen bits to be programmed into a synthesiser 22
- DIGITAL ENLARGING EXPOSURE METER** by A. A. Luha B.Sc.
For black and white prints without waste 34
- P.E. MICROPRINTER—3** by Mark Simon
Final part covers testing and routine maintenance 44
- HEADLIGHT WARNING DEVICE** by P. G. Wagstaff
Dual purpose, for lights on, lights off 62

GENERAL FEATURES

- BINAURAL STEREO PATENTS** by Adrian Hope
A new look at a not so new stereo system 28
- HOME COMPUTERS—2** by R. W. Coles
Peripherals and software 46
- CONSTANT CURRENT SOURCES** by D. F. Bowers B.Sc.
Transistor, op.amp. and transconductance amp. methods 54
- SEMICONDUCTOR UPDATE** by R. W. Coles
A look at some recently released devices 59
- INGENUITY UNLIMITED**
Variable Pulse Delay—Ultrasonic Proximity Detector—
Hazard Flasher Monitor—Simple Phaser—Livewire—Car Intruder Alarm 66

NEWS AND COMMENT

- EDITORIAL** 17
- POINTS ARISING**
Noughts and Crosses Game—ADSR Envelope Shaper 20
- SPACEWATCH** by Frank W. Hyde
Death of Skylab, Tiros-N, Vela Pulsar, Holography, Venus 21
- NEWS BRIEFS**
Away with Contactors—Model Aircraft Radar 31
More Bubbles!—Five-Step A to D 41
TV or Scope—FIR Filters—Countdown 43
Walky Talky Terminal—Floppy Saddle for your PET—Printer—John Miller-Kirkpatrick 53
Cherry-Picker Boom Boon 64
Micro' Courses—Take Over—Bubble Take Over—Power Supply Breaker—Video Library 70
- MARKET PLACE**
New products 32
- INDUSTRY NOTEBOOK** by Nexus
What's happening inside industry 42
- BOOK REVIEWS** 56
- READOUT**
A selection of readers' letters 60

OUR APRIL ISSUE WILL BE ON SALE FRIDAY, 9 MARCH 1979
(for details of contents see page 65)

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

kontite remote control switch


—Simple to install
even simpler to use



The Receiver:
contains input and
output cables which
are connected to the
appliance to be
controlled.

The Transmitter:

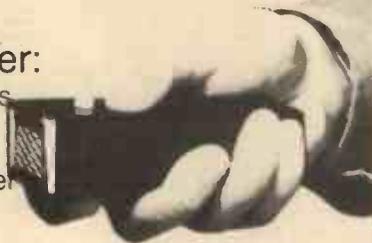is light and cordless
and housing the
battery. Simply,
point the transmitter
at the receiver to
turn on or off



Now available in the U.K. the 'Kontite' Remote Control unit switches electrical appliances and equipment on or off safely from distances of up to 35 feet.

Televisions, radios, hi-fi equipment, lighting, model trains etc. electric fans, electric fires (up to 2kw) and many other appliances are within its scope, providing that they have a power supply of 240/250 AC single phase. 50/60 Hz and a maximum 10 amp rating and also that the relevant safety regulations are applied.

The unit is ideal for use in the home, office, factory and hospital. Particularly useful as an aid to the disabled and invalid—wherever an electrical appliance is difficult to reach in the normal manner.

The Kontite Remote Control Switch
available now through
Electrical Component
Retailers.



If you have difficulty in locating a stockist please contact:

Kay & Co (Engineers) Ltd.

Acresfield House, 15 Exchange Street, Bolton. Lancashire.

Telephone: Bolton 21041 Telex: 63186

NO DISCO SYSTEM IS COMPLETE WITHOUT...



CITRONIC MM 313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch. mono. inc. LED indicators. connections via phono sockets at rear. Bargain price, including PS U £80.46 (P & P £1.50).

PIEZO HORNS

FANTASTIC SPECIAL OFFER!
TO READERS OF THIS PUB-
LICATION

Tweeters for your disco, PA system or Hi-Fi. Frequency range 5K-20K. No X over required. They can be used in any PA system up to 100W. Why pay more? OUR PRICE ONLY £4.99 each (IP&P 35p each)



BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System P552 SOCKET £0.65 (IP&P 35p) P551 PLUG £1.84 (IP&P 35p) Carriage on 10 or more nominal £1.00. Also available 6-way multicore cable (6 Amps per core) ex stock £0.85 per metre. Please phone for carriage quote.



PROJECTORS

SQUIRE MULTIFECT 150

—including rotator and effects wheel. A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use.

A BARGAIN AT £40.50 (P&P £1.00)



STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250 W quartz halogen bulb, fan cooled, accepts wide range of multifect attachments. Unique connection slot for orbit prism revolvers. Only

£70.20 (P & P £2.00) attachments extra

PLUS MANY DISCO ACCESSORIES

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example: Fane and H. H Disco Speakers 12" and 15" BSR and Garrard decks at discount prices



Plus sockets, Fuses, Plugs, etc. etc.

Roger Squire's DISCO GEAR

Personal callers: ROGER SQUIRE'S DISCO CENTRES

LONDON: 175 Junction Road, Tufnell Park N19 5QQ 01-272 7474

BRISTOL: 125 Church Road, Redfield, Bristol BS5 9JR 0272-550550

MANCHESTER: 251 Deansgate M3 4EN 061-831 7676

GLASGOW: 1 Queen Margaret Road off Queen Margaret Drive, Kelvinside, Glasgow, G20 6DP

Open from 10-5 Tues-Sat

10-8 Weds

Closed Mondays.

041-946 3303

TOUCH CONTROLLED LIGHTING KITS (300W)

A Lightdimmer with NO knob. Dimming and on/off functions are controlled by touch. Features include:

- ★ No mains rewiring.
- ★ Easy to build—uses one MOS IC.
- ★ Switches on to preset brightness.
- ★ Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy.

★★ PRICE TD300K £9.67
TDE/K £1.62



TSD300K TOUCH-SWITCH & DIMMER combined. One touchplate for on/off. Small knob controls brightness. £5.82
TS300K TOUCHSWITCH. Two touchplates. ON/OFF £4.64
TSA300K AUTOMATIC. One touchplate. Preset time delay off variable 2 secs to 3½ mins. £4.84
LD300K LIGHTDIMMER. £3.24

DIGITAL VOLTMETER/THERMOMETER KIT



Based on the 7106 single IC 3½ digit D.V.M. the Kit contains a PCB, resistors, capacitors, pre-sets, I.C. and 0.5" liquid crystal display. Components are also included to a Digital Thermometer using a single transistor as the sensor. Requires a 2mA 9V supply (PP3 battery).

ONLY £23.75

TRIAC BARGAINS

400V Plastic Case	64p
3A	86p
6.5A with trigger	80p
8A	90p
12A	113p
16A	178p
20A	205p
25A	23p
SCR (IC106D) 5A/400V	54p
Diac	23p

COMPONENTS

0.2" L.E.D.s	
Red 13p (£1.08/10)	
Green 23p Yellow 27p	
DL727 .5" display	£1.62
LCD .5" 4 digit	£8.75
LDR 5" dia.	54p
NE555 31p (4 for £1.08)	
741 27p (5 for £1.08)	
LM3911 temperature control/thermometer IC	£1.08
AY-5-1224	£3.51
AY-5-1230	£5.23
2N1034E	£1.94
ICL7106 DVM IC	£11.05
IN4001	7p
IN4148	5p
BC182L	11p
2N3819	25p

MINI MAINS TRANSFORMERS

Standard 240V mains primary	
100mA secondary	
6-0-6V	92p
9-0-9V	97p
12-0-12V	102p

24HR CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £16.09
White box (56 x 131 x 71mm) - drilled £2.70
- undrilled £2.38
Ready built £24.30

ABOVE PRICES INCLUDE V.A.T.

Quantity discounts on request. Add 25p postage and packing. Mail order only to:

T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.

TLabyTEXAS 7400 13p 7401 14p 7402 14p 7403 14p 7404 17p 74504 90p 7405 18p 7406 32p 7407 32p 7408 19p 7409 19p 7410 15p 7411 24p 7412 20p 7413 30p 7414 60p 7414 60p 7415 20p 7416 27p 7417 27p 7420 40p 7421 40p 7422 22p 7423 34p 7425 30p 7426 40p 7427 34p 7428 36p 7430 17p 7432 30p 7433 40p 7437 35p 7438 35p 7440 17p 7441 70p 7442A 60p 7443 112p 7444 112p 7445 100p 7446A 95p 7447A 60p 7448 80p 7450 17p 7451 17p 7453 17p 7454 17p 7460 17p 7470 36p 7472 30p 7473 34p 7474 30p 7475 36p 7476 35p 7480 50p 7481 100p 7482 84p 7483A 100p 7484 100p 7485 110p 7486 34p 7489 210p 7490A 33p 7491 80p 7492A 46p 7493A 33p 7494 84p 7495A 70p 7496 65p 7497 180p 74100 130p 74104 65p 74105 65p 74107 34p 74109 55p 74110 55p 74111 70p 74116 20p 74118 130p 74119 210p 74120 110p 74121 28p 74122 48p 74123 55p 74125 55p 74126 60p 74128 75p 74132 75p 74136 70p 74141 70p 74142 200p 74145 90p 74147 190p 74148 150p 74150 100p 74151A 70p 74153 70p 74154 100p 74155 90p 74157 70p 74159 90p 74160 100p 74162 100p 74163 100p 74164 100p 74165 130p 74166 140p 74167 200p 74170 240p 74172 70p 74173 120p 74174 93p 74175 85p 74176 90p	74177 90p 74180 93p 74181 200p 74182 90p 74184A 150p 74185 150p 74186 700p 74189 90p 74191 100p 74192 100p 74193 100p 74194 100p 74195 95p 74198 80p 74198 150p 74199 150p 74200 1000p 74221 160p 74221 160p 74221 160p 74221 160p 74259 250p 74266 90p 74278 290p 74279 140p 74283 190p 74289 140p 74285 400p 74290 150p 74293 150p 74294 200p 74298 200p 74365 150p 74366 150p 74367 120p 74368 150p 74390 200p 74393 200p 74490 225p 74LS SERIES 74LS02 14p 74LS04 16p 74LS08 25p 74LS10 20p 74LS11 40p 74LS13 75p 74LS14 75p 74LS20 20p 74LS21 40p 74LS22 28p 74LS27 38p 74LS30 20p 74LS32 27p 74LS47 90p 74LS55 30p 74LS73 50p 74LS74 40p 74LS75 55p 74LS83 110p 74LS85 100p 74LS86 40p 74LS90 60p 74LS93 60p 74LS107 45p 74LS123 70p 74LS124 180p 74LS132 95p 74LS133 60p 74LS138 60p 74LS139 60p 74LS151 100p 74LS153 60p 74LS157 60p 74LS158 120p 74LS160 130p 74LS161 100p 74LS162 140p 74LS163 110p 74LS164 120p 74LS165 180p 74LS166 180p 74LS173 90p 74LS175 110p 74LS181 320p 74LS190 100p 74LS191 100p 74LS192 140p 74LS193 140p 74LS195 140p 74LS196 120p 74LS221 140p 74LS240 100p 74LS241 175p 74LS242 170p 74LS243 170p 74LS244 170p 74LS245 170p 74LS251 140p 74LS253 140p 74LS257 120p 74LS259 160p 74LS266 100p 74LS273 130p 74LS279 90p 74LS298 240p 74LS324 200p 74LS373 180p 74LS374 195p 74LS378 200p	4000 SERIES 4000 15p 4001 17p 4002 17p 4006 95p 4007 18p 4008 80p 4009 40p 4010 50p 4011 17p 4012 18p 4013 50p 4014 84p 4016 84p 4018 84p 4017 80p 4018 89p 4019 45p 4020 100p 4021 110p 4022 100p 4023 22p 4024 50 4025 20p 4026 130p 4027 50p 4028 84p 4029 100p 4030 55p 4031 200p 4033 180p 4034 200p 4035 110p 4040 100p 4041 80p 4042 80p 4043 90p 4044 90p 4045 110p 4047 100p 4048 55p 4049 32p 4050 49p 4051 80p 4052 80p 4053 80p 4054 150p 4055 125p 4056 135p 4059 60p 4060 115p 4061 35p 4066 55p 4067 450p 4068 22p 4069 20p 4070 30p 4072 22p 4073 22p 4075 22p 4076 107p 4081 22p 4083 10p 4093 80p 4094 250p 4098 170p 4411 1100p 4502 120p 4503 70p 4507 55p 4510 99p 4511 150p 4514 250p 4516 110p 4518 110p 4520 100p 4528 100p 4543 180p 4553 450p 4560 250p 4563 90p 4584 90p 40014 90p 40085 200p 40097 90p 14411 1100p 14412 1100p 14433 1100p	93 SERIES 930 160p 9302 175p 9308 316p 9310 275p 9311 275p 9312 160p 9314 165p 9316 225p 9317 150p 9321 225p 9322 150p 9334 225p 9368 200p 9370 200p 9374 200p	VEROBOARD 0.1 0.15 (copper clad) 2 x 3 1/2 41p 33p 3 x 5 49p 45p 3 x 3 1/2 45p 45p 3 x 5 59p 60p 4 x 17 152p 121p 4 x 17 152p 163p 2 x 17 252p 9p Pkt of 35 pins 30p Spot face cutter85p Pin insertion 99p Tool 99p	TRANSISTORS AC126 25p AC127/8 20p AC176 25p AC187/8 25p AF116/7 9p AD149 70p AD161/2 45p BC107/8 11p BC109 11p BC111 20p BC147/8 9p BC149 10p BC157/8 10p BC159 11p BC169 12p BC172 12p BC177/8 17p BC182/3 15p BC184 11p BC187 30p BC123/13 11p BC21 12p BC461 35p BC47/8 30p BC516/7 50p BC547/8 16p BC549C 18p BC55 16p BC559C 18p BC70 18p BC71/2 22p BC131/2 50p BD135/6 54p BD139 56p BD140 50p BD189 60p BD242 70p BDY56 200p BF200 32p BF248 35p BF256/8 12p BF257/8 32p BF259 36p BF39 30p BF40 30p BF44 30p BF79 30p BF80 30p BF81 30p BF82 30p BF83 30p BF84/5 30p TIP34C 160p	VERO WIRING PEN Spare spool 325p Plus spool 80p (wire) 80p Combes 7p each	BUCKET BRIGADE* SAD1024 1800p	LINEAR I.C.s *AY1-0212 600p *AY1-1313 668p *AY1-1320 320p *AY1-5050 211p *AY8-1315 600p *AY5-1317 636p *CA3019 80p *CA3046 70p *CA3048 225p *CA3006 72p *CA3089E 225p *CA3090AQ 375p *CA3130S 100p *CA31140E 70p *CA3160E 100p *F209 750p *ICL7106 850p *ICL8038 340p *LM301A 30p *LM311 120p *LM318 200p *LM324 100p *LM339 80p *LM348 95p *LM377 175p *LM380 75p *LM381AN 160p *LM389N 140p *LM409 35p *LM710 50p *LM725 350p *LM733 100p *LM741 20p *LM747 70p *LM748 35p *LM3900 70p *LM3911 130p *LM4136 120p *MC1310P 150p *MC1458 55p *MC1495 35p *MC1496 100p *MC3340P 120p *MC3360P 120p *95H90 800p	MEMORIES 2102 100p 2102-2 120p 2102L-4 140p 2107B 600p 2111-1 225p 2112-2 300p 2114 1000p 5101 510p 6810 350p	ROM/PROMS 74S188 225p 74S287 450p 74S387 400p 93427 400p 93436 650p 93446 650p 93448 1000p	CPUs 4040A 670p 6502 1200p 6800 900p 8080A 900p	EPROMS 1702A 600p 2708 900p 2716 2500p 4702 900p	TRANSFORMERS (prim 220-240V) 6-0-6 100mA 88p 9-0-9 75mA 92p 12-0-12 100mA 95p 0-12-0-12 500mA 280p+ 0-25V (5VA) 250p 9-0-9 1A 270p* 12V 2A 350p* 0-12-15 1A 340p* 20-24-30 1A 265p* 15-0-15 1A 265p* (Please add 50p p&p charge to all marked * above our normal p&p charge)	DATA BOOKS TTLs, C.MOs, LInears, Memories, etc, by Mfrs stocked. Please send S.A.E. for details.	DIODES *2N3820 50p *2N3823 70p *2N3866 90p *2N3903/4 18p *2N3905/6 20p *2N4037 65p *2N4058/9 12p *2N4060 12p *2N4062/18p *2N4123/4 22p *2N4125/6 22p *2N4289 20p *2N4401/3 27p *2N442 90p *2N4871 60p *2N5087 27p *2N5089 27p *2N5172 27p *2N5179 95p *2N5191 85p *2N5194 90p *2N5245 40p *2N5296 55p *2N5401 50p *2N5457/8 40p *2N5459 40p *2N5460 27p *2N5485 44p *2N6027 48p *2N6247 190p *2N6254 130p *2N6280 65p *2N6292 65p *2N2484 0p *2N2456 25p *2N2904/5 25p *2N2906A 24p *2N2907A 30p *2N2926 9p *2N3053 20p *2N3054 65p *2N3055 48p *2N3442 140p *2N3553 240p *2N3565 30p *2N3643/4 48p *2N3658 20p *2N3702/3 68p *2N3704/5 12p *2N3706/7 14p *2N3708/9 12p *2N3773 300p *2N3819 25p	*ZENEERS *8Y127 12p *0A47 9p *0A81 15p *0A85 15p *0A90 9p *0A91 9p *0A95 9p *0A200 10p *1N914 4p *1N916 7p *1N4148 6p *1N4001/2 5p *1N4003/4 6p *1N4005 6p *1N4006/7 7p *1N5401/3 14p *1N5404/7 19p *15920 9p	TRIACS 3A 400V 60p 3A 500V 65p 6A 400V 70p 6A 500V 80p 8A 400V 75p 8A 500V 95p 12A 400V 85p 12A 500V 105p	HEAT SINKS For TO220 Voltage Regs. Transistors 22p For TO5 12p	THYRISTORS 1A 50V 40p 1A 400V 65p 1A 600V 70p 3A 400V 90p 8A 600V 140p 12A 400V 160p	BRIDGE RECTIFIERS *1A 50V 21p *1A 100V 22p *1A 400V 30p *1A 600V 35p *2A 50V 30p *2A 100V 35p *2A 400V 45p *3A 200V 60p *3A 600V 72p *4A 100V 95p *4A 400V 100p 6A 50V 90p 6A 100V 100p 6A 400V 120p	LOUD-SPEAKERS Size 2 1/2" 8R 70p 2 1/2" 8R 75p 2 1/2" 8R 75p	SUBMINIATURE SWITCHES AY-5-1015P 500p AY-5-1013 400p TMS6011NC 400p	CHARACTER GENERATOR 3257ADC 990p MC9657 750p RO-3-2513 U.C. 600p RO-3-2513 L.C. 550p SN74S262AN 1360p	OTHER 4205 400p 3245 390p 4289 970p 4801 500p 6820 600p 6850 700p 8205 320p 8212 225p 8216 225p 8224 400p 8228 525p 8251 700p 8253 1200p 8255 550p 8257 1100p 8259 1400p AY5-2376 1100p MC14411 100p	CRYSTALS 100KHz 300p 1MHz 370p 3.2768MHz 350p 10.7MHz 350p 18MHz 300p 17.135MHz 300p	EDGEBOARD CONNECTORS 0.156" Solder Tail 2 x 10 way 85p 2 x 15 way 100p 2 x 18 way 120p 2 x 22 way 135p 2 x 25 way 160p	LOW PROFILE DIL SOCKETS BY TEXAS 8 pin 11p 18 pin 25p 24 pin 33p 14 pin 12p 20 pin 28p 28 pin 42p 16 pin 13p 22 pin 30p 40 pin 51p	WIRE WRAP SOCKETS 8 pin 30p 24 pin 80p 14 pin 40p 28 pin 100p 16 pin 55p 40 pin 120p	EDGE CONNECTOR 31 Way Plug 105p 31 Way Skt. 110p (0.1" Pitch)
--	---	--	--	---	---	--	---	---	---	--	--	---	---	---	--	--	--	--	---	---	---	---	---	---	---	---	--	--	---

* RESISTORS High Stab Carbon Film 5% Tol E12 Series
1W 10R-1M 1p 90p/100 each valve
1/2W 10R-10M 1.5p 120p/100 each valve

* MINIATURE PRESETS, Horz/Vert
100R-1M 10p

* CARBON TRACK POTENTIOMETERS
1W LOG or LIN
Single 5K-2M 25p
Single with DP Switch 5K-2M 55p
Dual 5K-2M 66p

"PE" MICROPRINTER
SEND S.A.E. FOR DETAILS

VEROBOARDS ANTEX
IC BREADBOARD SOLDERING IRONS
(20 x 14 pin DIL ICs or 16 x 16 pin DIL ICs) Model C 15W 360p
4.15" x 6.15" 270p CX 17W 360p
X25 360p
CCN 380p

VQ BOARD
Specially designed for Spare Bits
DIL ICs - No track C/CX/CCN 46p
cutting 5.82" x 2.9" 105p X25 50p

VAT RATE: All items at 8% except where marked * where 12 1/2% applies. Please add 25p p&p & VAT at appropriate rates.

Government, Colleges, etc. Orders accepted.

TECHNOMATIC LTD.
17 Burnley Road, London NW10
(2 minutes Dollis Hill tube station) (ample street parking)
Tel: 01-452 1500 Telex: 922800

BD1-The Connoisseur's Budget Choice



BD1 Kit & Completed BD1 Assembly



BD1 with Plinth, Cover & SME Arm.

The Connoisseur BD1 transcription turntable is a precision engineered product designed to provide top grade performance at a moderate cost. Simplicity is the main feature of this unit giving excellent performance and reliability. A slow speed synchronous motor is used and because of its construction the hum field is very low, so that even the most sensitive of pickups can be used, including the Connoisseur SAU2 or the SME 3009 Series II.

Speed change is achieved by a press button unit at the rear of the platform which automatically moves the drive belt from one pulley groove to the other whilst the turntable is turning. The BD1 turntable kit can be assembled by the home constructor within the hour and when completed will give top quality performance. No soldering is required. Complete the unit with a modern BD1 plinth and cover. The plinth is finished in walnut veneer and fitted with spherical, anti-vibration feet. Add to this a strong Acrylic, bronze cover, hinged with 2-position lid stay and you have a first class turntable at a budget price!

Connoisseur

Write for further details to:

A. R. Sugden & Co. (Engineers) Ltd.
Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES
Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden Crighouse, Telegrams & Cables: Connoisseur Brighouse.

4 1/2 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £6.40. 19p P. & P.

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3.5 and 2.5mm Jack Plugs £1.66
DM229R 50K with 3.5 and 2.5mm Jack Plugs £2.20
DM18D 200 ohm with 5 and 3 pin Din Plugs £1.95
Postage on above microphones 11p.

CARDIOID DYNAMIC MICROPHONE

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £8.02. 26p P. & P.

2in x 2in meters 500µA, £3.65. 16p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £6.16. 11p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.

MULTI-METER

Model IT1-2
20,000 ohm/volt. £12.32.
33p P. & P.

TRANSFORMERS Primary 240V

6-0-6V	100mA	£0.75
9-0-9V	75mA	£0.75
12-0-12V	50mA	£0.85
12-0-12V	100mA	£1.05

Post on above transformers 30p.

9-0-9V	1A	£1.80
12-0-12V	1A	£2.15
15-0-15V	1A	£2.36
30-0-30V	1A	£3.10
6-3V	1 1/2 A	£1.80
6-0-6V	1 1/2 A	£2.20

Post on above transformers 45p.

All above prices include V.A.T. Send 40p for new fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,
WOOD GREEN, LONDON,
N22 4SJ (MAIL ORDER DEPT.)

888-3206

FLIP
Push Button Heads or Tails.

Complete kit and full instructions supplied.

A pocket game. Easy to build and great to play. Kit price £5.25 + 8% VAT. Post free.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT
1000W lighting per channel. max. A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier. S.A.E. for spec sheet. Still only £20.00 + 8% VAT.

SIRENS

CR 11 Siren. Rotating fan in metal unit. Adjustable mounting bracket. Gives high pitched wailing note of varying frequency - 16 cyc. per minute. 12 volts DC. £9.00 + 8%.

CR 12 Siren. 125mm diameter gold coloured horn with fixing plate. Emits high-pitched wailing note of varying frequency - 16 cyc. per minute. 12 volts DC. £9.00 + 8%.

CR 13. As above but rapid noise frequency change - 160 cyc. per minute.

CR 14 Siren. 90mm dia. l x 60mm. Red plastic case with fixing plate, emits high-pitched wailing note of varying frequency - 100 cyc. per minute. 12 volts D.C. £5.50 + 8%.

POWER SUPPLY UNIT

PP1 - switched 3, 4 1/2, 6, 7 1/2, 9 and 12 volts at 500mA, with on/off switch and pilot light. Size: 130 x 55 x 75mm approx. Our Price: £1.75 + 8% VAT.

BARGAIN LOUDSPEAKER
Goodmans 5" 8 ohm long throw heavy duty L/S/PR.
Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5 1/2" (diagonally).
Only £5.00 + 12 1/2% VAT.

SIX-PIECE MINIATURE SCREWDRIVER SET

Six precision screwdrivers in a hinged plastic box. Blade sizes: 0-8mm, 1-4mm, 2mm, 2.4mm, 2.9mm, 3-8mm. Our Price: £1.75 + 8% VAT.

2 WAY 8 OHM HEAVY DUTY XOVER.
A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100W. Input via screw terminals. Fitted with a 3 position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB.
Buy now while stocks last!
Only £3.00 + 8% VAT.

PIEZO ELECTRIC HORN UNITS
High Quality, High Power Tweeter. No Xover reqd. Freq. Response: 3.8kHz-28kHz. Spec. sheet sent on receipt of S.A.E.
Our Price: £6.50 + 8% VAT.

BARGAIN TRANSFORMER
240V Primary 12-0-12V 500mA sec. Approx. size: 60 x 40 x 50mm. Fixing centres: 75mm.
Price: £1.50 + 8% VAT.



'P&P' orders up to £5, Add 30p.
Orders £5-£10, Add 50p.
All orders over £10 post free!
Please add V.A.T. as shown.
S.A.E. with all enquiries please.



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.
also 13 SOUTH MALL, EDMONTON GREEN, EDMONTON

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, Herts., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SEA FREIGHT.

SEND 50p (plus 25p p&p) FOR OUR CATALOGUE

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am - 6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F)

400V: 0.001, 0.0015, 0.0022, 0.0033 3p; 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 10p; 0.047, 0.068 14p; 0.10 15p; 0.15, 0.22 22p; 0.33, 0.47 39p; 0.68 45p. 160V: 0.39, 0.15, 0.22 11p; 0.33 0.47 19p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p.

DUBILIER: 1000V: 0.01, 0.015 20p; 0.022 22p; 0.047 26p; 0.1 38p; 0.4 48p.

POLYESTER RADIAL LEAD (Values are in μ F) 250V:

0-0.1, 0-0.15, 0-0.22, 0-0.27 5p; 0-0.33, 0-0.47, 0-0.68, 0-1 17p; 0-1.5 11p; 0-2.2, 0-3.3 13p; 0-4.7 15p; 0-6.8 18p; 1-0 24p; 1-5 27p; 2-2 31p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F) 500V: 10 40p; 47 68p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22 8p; 47, 32, 50 11p; 63, 100 27p; 50V: 1.0 7p; 50, 100, 220 25p; 470 50p; 1000 68p; 40V: 22, 33 7p; 100 12p; 2200, 3300 62p; 4700 64p; 35V: 10, 33 9p; 330, 470 32p; 1000 48p; 25V: 10, 22, 47 6p; 80, 100, 180 8p; 220, 250 13p; 470, 640 25p; 1000 27p; 1800 30p; 2200 41p; 3300 52p; 4700 54p; 16V: 10, 40, 47, 68 7p; 100, 125 6p; 330 14p; 470 16p; 1000, 1500 20p; 2200 34p; 10V: 4, 10 6p; 640 10p; 1000 14p.

Tag-End 70V: 2000 89p; 4700 135p; 50V: 10,000 255p; 40V: 2500 65p; 3300, 4700 70p; 15,000 450p; 25V: 4700 68p; 2200 48p; 325V: 200 + 100 + 50 + 100 190p.

TANTALUM BEAD CAPACITORS 35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 μ F, 3.3, 4.7, 6.8, 25V: 1.5, 1.0, 20V: 1.5, 1.6V: 10 μ F 13p each; 47, 100 40p; 10V: 22 μ F, 33: 6V: 47, 68, 100: 3V: 68, 100 20p each.

POTENTIOMETERS (AB or EGEN) Carbon Track, 1W Load & 1W Linear values 5000, 1K & 2K (for only). Single 27p 5K Ω -2M Ω single gang 27p 5K Ω -2M Ω single gang DP switch 60p 5K Ω -2M Ω dual gang stereo 70p

MYLAR FILM CAPACITORS 100V: 0.001, 0.002, 0.005, 0.01 μ F 6p 0.015, 0.02, 0.04, 0.05, 0.056 μ F 7p 0.01 μ F, 0.2 9p 50V: 0.47 μ F 11p

CERAMIC CAPACITORS: 50V 0.5pF to 10nF 3p each 15nF, 22nF, 33nF, 47nF 4p each 0.1 μ F 6p, 0.2 μ F 7p

POLYESTER CAPACITORS 100pF to 1nF 8p; 1.5nF to 47nF 10p.

SILVER MICRA (Values in μ F) 3-3, 4-7, 6-8, 10 12 18 22 33 47 50 68 75, 82, 85, 100, 120, 150, 220, 250 9p each 250 300 330 360 390 600 820 16p each 1000, 1800, 2000, 2200 20p each

MINIATURE TYPE TRIMMERS 2.5 5pF 3 10, 10 40pF 30p 5 25pF 5 45pF 60pF 88pF 22p

COMPRESSION TRIMMERS 3-40pF, 10-80pF, 25-190pF 25p 100-500pF 45p, 1250pF 60p

SOLDERING PINS: 100 pins 50p; 1000 pins 395p

JACK PLUGS		SOCKETS	
2.5mm Screened chrome	13p	open metal	8p
3.5mm Plastic body	10p	moulded with break	11p
MONO	25p	4 contacts	12p
STEREO	32p	15p	24p

DIN	PLUGS	SOCKETS	In Line	SWITCHES * Miniature Non-Locking
2 PIN Loudspeaker	10p	6p	20p	Push to Make 15p
3, 4, 5 Pin Audio	10p	6p	20p	Push to Break 25p
Co-axial (plastic) (metal)	10p	12p	12p	SPST on/off 54p
PHONO assorted colours Metal Screened	10p	6p single 15p double	15p	DPDT 38p
BANANA 4mm	11p	10p	—	4 pole on/off 54p
2mm	10p	10p	—	SUB-MIN TOGGLE SP changeover 59p
1mm	6p	6p	—	TOGGLE 2A 250V 28p
WANDER 3mm	6p	6p	—	SPST on/off 54p

DIGITAL MULTIMETER Announcing DM900 - The Digital Multimeter with a difference - It measures Capacitance too. (as published in E.T.I. August 1978)

Throw away your analogue meters, here's digital accuracy at only half the price of an equivalent commercial Multimeter.

The DM900 is a 3 1/2 digit multimeter with an 0.5in L.C.D. display incorporating:

- 5 AC & DC Voltage ranges; 6 Resistance ranges.
- 5 AC & DC Current ranges; 4 Capacitance ranges.

The prototype accuracy is better than 1%.

This is a unique design using the latest MOS ICs and due to the minimal current drain, is powered by only one PP3 battery. There is also a battery check facility.

DM900 is an attractive hand-held lightweight device, built into a high impact case with carrying handle and has been ingeniously designed to simplify assembly.

Never before have all these features been offered to the electronics enthusiast in a single unit.

Price: £54.50* only (p&p insured add 80p)

Send SAE for leaflet.

Ready Built and tested units £78.50* including probes and carrying case (P&P insured 80p)

(Demonstration on at our shop)

PE VDU SYSTEMS

parts now available (send SAE for list)

Convert your TV into a VDU by using the new Thomson-CSF, TV-CRT controller chip SF.F 96364. 16 lines by 64 characters, text refreshment, cursor management on TV screen, line erasing, line end erasing. Compatible with any computing system.

SFF 96364E	£11.75*
AY-5-1013UART	£4.50*
71301 ROM SFC	£8.20*
SFS80102 RAM 1K	£2.05*
74LS163	£0.95*
MC1488	£0.85*
MC1489	£0.90*
SN75450	£1.20*
SN75451	£0.70*
SN75452	£0.70*
SN75454	£1.20*
2102 LF	£1.60*
2513	£5.95*
74LS132	£1.20*
81LS97	£1.09*
1 MHz crystal	£3.23*
14.31818 MHz	£2.70*
UHF Modulator	£2.50*

T400 13	7495 65	74195 98	4056 134	LINEAR'S	MC1303	88
7401 13	7496 57	74196 93	4057 2570	702*	MC1304P	260
7402 14	7497 189	74197 80	4058 480	709 14 pin	MC1310	149
7403 14	74100 119	74198 150	4060 1125	710*	MC1312P	195
7404 14	74105 62	74199 62	4061 999	723*	MC1495*	390
7405 14	74107 29	75491 75	4063 110	741C* 8 pin	MC1496*	92
7406 38	74110 54	75492 80	4064 1423	741C* 14 pin	MC1497*	210
7407 38	74111 68		4067 380	748C*	MC3401	52
7408 17	74112 125		4068 22	753*	MC3403*	135
7409 17	74116 198		4069B 20	810*	MC3404P*	120
7410 15	74118 83		4000 15	4070 32	MC3360P	120
7411 20	74120 169		4001 17	4071 21	MF4000P	85
7412 17	74120 115		4002 16	4072 21	MF6000P	77
7413 30	74121 25		4006 92	4073 21	MF60398*	635
7414 51	74122 46		4007 18	4075 23	MF60362*	650
7416 30	74123 48		4008 82	4076 85	MM2112*	105
7417 30	74126 38		4009 38	4077 40	MM2112-2*	210
7420 16	74128 37		4011 18	4078 21	MM5303*	635
7422 24	74132 73		4012 18	4082 21	MM57160*	620
7423 27	74136 73		4013 45	4085 74	MM57160*	620
7425 27	74141 56		4015 82	4086 73	NE555*	29
7426 36	74142 209		4016 45	4089 150	NE560DB*	60
7427 27	74143 314		4017 82	4093 85	NE560*	325
7428 15	74145 61		4018 87	4094 149	NE561*	395
7430 17	74145 65		4019 48	4095 130	NE562*	170
7432 25	74147 175		4020 99	4096 105	NE563*	120
7433 40	74148 109		4021 95	4097 372	NE566*	160
7437 30	74150 99		4022 85	4098 110	NE567*	175
7438 33	74151 64		4023 22	4099 145	NE571*	450
7441 74	74154 96		4024 56	4100 109	RC4136D*	120
7442 68	74155 53		4026 180	4103 09	SAD1024A*	250
7443 115	74156 80		4027 45	4104 09	SA1024B*	250
7444 112	74157 67		4028 81	4105 09	SN76033*	140
7445 94	74159 185		4029 59	4106 09	SN76033P*	140
7446 94	74162 82		4030 58	4107 09	SN76023N*	140
7447 82	74161 92		4031 205	4108 09	SN76033N*	175
7448 56	74162 92		4032 100	4109 72	SN76115N*	215
7450 17	74163 92		4033 145	4110 95	SN76115P*	225
7451 17	74164 105		4034 116	4122F1260	SN76227	115
7453 17	74165 105		4035 111	4122F1380	TA6A61BX1*	228
7456 17	74166 140		4036 58	4123F1380	TA960	300
7460 17	74167 200		4037 100	LD190*	TA1008*	310
7470 28	74170 185		4038 108	LD190*	TBA1205	75
7472 25	74172 625		4039 320	LD190*	TBA540A*	250
7473 32	74173 120		4040 105	LD190*	TDA1022	595
7474 32	74174 87		4041 80	LD190*	TD02020	320
7475 38	74175 87		4042 87	LD190*	TLO61CP*	48
7476 36	74176 75		4043 94	LD190*	TLO64CN*	199
7480 48	74177 78		4044 95	LD190*	TLO64CN*	199
7481 86	74178 102		4045 145	LD190*	TLO64CP*	76
7482 68	74180 85		4046 128	LD190*	TLO64CP*	76
7483 72	74181 185		4047 87	LD190*	TLO64CP*	76
7484 95	74182 185		4048 95	LD190*	TLO64CP*	76
7485 94	74183 82		4049 48	LD190*	TLO64CP*	76
7486 31	74185 135		4050 48	LD190*	TLO64CP*	76
7488 210	74188 275		4051 72	LD190*	TLO64CP*	76
7489 33	74190 95		4052 72	LD190*	TLO64CP*	76
7491 75	74191 95		4053 72	LD190*	TLO64CP*	76
7492 38	74192 98		4054 110	LD190*	TLO64CP*	76
7493 32	74193 98		4055 128	LD190*	TLO64CP*	76

TRANSISTORS

AC117*	35	BC170	18	BF184	38	OC41*	48	ZTX314	17	2N3563	20
AC125*	20	BC171	11	BF195	12	OC43*	32	ZTX314	17	2N3614*	169
AC126*	20	BC172	11	BF196	12	OC43*	55	ZTX326	36	2N3615*	135
AC127*	20	BC177*	18	BF197	14	OC45*	28	ZTX300	15	2N3702	11
AC128*	20	BC178*	16	BF200*	30	OC70*	28	ZTX501	19	2N3703	11
AC141*	24	BC179*	18	BF224A	18	OC71*	28	ZTX503	15	2N3705	11
AC141K*	38	BC182*	9	BF242A	29	OC72*	32	ZTX504	15	2N3706	11
AC142*	38	BC183*	9	BF255*	30	OC73*	36	ZTX504	25	2N3707	11
AC176*	20	BC183L	11	BF255*	30	OC79*	76	2N5250*	58	2N3709	11
AC187*	20	BC184	9	BF259*	30	OC81*	28	2N6936*	35	2N3710	16
AC188*	20	BC184L	11	BF394	27	OC82*	40	2N6937*	25	2N3711	12
AC197*	35	BC186	21	BF594	40	OC83*	48	2N6988*	44	2N3715*	250
AD1DPDT	14p	BC187*	11	BF595	38	OC84*	48	2N6989*	58	2N3716*	12
AD1DPDT	15p	BC190*	10	BF739	25	OC122*	48	2N7068*	19	2N3773*	288
AD1DPDT	13p	BC200*	11	BF740	28	OC123*	48	2N707*	39	2N3819	22
AD1DPDT	24p	BC213	11	BF779	28	OC139*	110	2N708*	19	2N3820	45
AD1DPDT	14p	BC213L	12	BF780	28	OC140*	110	2N709*	32	2N3823*	65
AD1DPDT	15p	BC214	9	BF782*	28	OC141*	85	2N716*	27	2N3824*	70
AD1DPDT	15p	BC214L	9	BF783*	28	OC142*					

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name

Address

Age

ICS

To ICS, Dept. E273, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

Do-it-Yourself Kits Or Factory Assembled

- WERSI Organs
- WERSI Pianos
- WERSI String Ensembles
- WERSI MATIC Rhythm
- WERSI MATIC Accompaniment
- WERSI VOICE Rotor Sound String Choir
- WERSI Professional Series
- WERSI Audio Mixer 2004
- WERSI TONE Rotating Baffles
- WERSI Speaker Cabinets

Send for our 104 page full-colour catalogue and 12-page price list, for £1.00 only.

AURA SOUNDS (P2),
Cophthorne Bank, Crawley, W. Sussex.

AITKEN BROS.

35, High Bridge, Newcastle upon Tyne
Tel: 0632 26729



TMK 500 MULTIMETER 30,000 o.p.v. AC volts 2-5, 10, 25, 100, 250, 500, 1000. DC volts. 0-25, 1, 2-5, 10, 25, 100, 250, 1000. DC current 50µa, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included. **PRICE £24.95.**



SINCLAIR PDM35 DIGITAL POCKET MULTIMETER DC volts (4 ranges) 1MV to 1000V AC volts iV to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £32.95.** AC Adaptor/Charger £3.75 de luxe padded carrying case £3.50 MN1604 Battery. 99p.



SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER. DC volts (4 ranges) 1MV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1µa to 1000MA Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £54.75** Carrying case £9.50. AC adaptor/charger. £3.98 Rechargeable Battery Pack. £9.14.



PANEL METERS DIMS 60MM x 45MM. 50µ amp, 100µ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50v AC, 300V ac, "S", "VU" 50-0-50µa, 100-0-100µa, 500-0-500µa. **PRICE £4.95.**



DESOLDERING TOOL SUCTION PUMP. **£5.95**



PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10. ALL PRICES INCLUDE POSTAGE AND VAT. CATALOGUE 50p.

DEDUCTIBLE ON FIRST ORDER OF £5.00 OR MORE.

EMI SPEAKER BARGAIN

Stereo pair 350 kl. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p.

As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions. Size approx 20" x 11" x 9 1/2" **£28.00** Per stereo pair + £5.00 p&p.



BSR Manual single play record deck with auto-return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use. **OUR PRICE £10.95** p&p £2.55

TURNTABLE BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck **£26.95** | GARRARD SP25 MKIV Deck with Shure head. **£25.95**

Plinth and cover for BSR decks **£6.00**

BARGAINS FOR PERSONAL SHOPPERS

PORTABLE STEREO RADIO CASSETTE RECORDER UNREPEATABLE



MW, LW, SW and Stereo VHF. 6 watts output Battery/Mains operation. **£69.95**
160 16 VOLT MAINS TRANSFORMER. 2 1/2 amp. **£2.50**

Garrard Record auto deck on plinth with stereo cartridge ready wired **£18.95**

LED 5 function men's digital watch stainless steel finish **£5.95**

LCD 5 function men's digital watch stainless steel finish **£6.95**

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish. **£13.95**

BATTERY/MAINS CASSETTE RECORDER with built in mic. **£12.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

£11.95

125 Watt Power Amp Module **£13.95**

Mains power supply for above unit. **£3.50**

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/2" x 14 1/2" x 7 1/2" approx. **£5.95**

MULLARD Built power supply **£1.50**

DECCA DC 1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads **£2.95**

DECCA 20W Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers **£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock. LW, MW, SW, VHF mains/battery operation. **£41.95**

7" TAPE TRANSPORT Mechanism—a selection of models from **£8.95**

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

£7.50 p&p £1.50p



AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE WITH DECODER

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vo, On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW. Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz (150mV/100K) deviation FM signal Frequency Range (Audio) 50KHz to 17KHz within ±1dB Radio FM sensitivity for 3dB below limiting better than 10 uV AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre Size approx length 18" x height 2 1/4" x depth 4 1/4" **£19.95** p&p £2.55

£19.95 p&p £2.55

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE

PRICE £ AT OVER **25** PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE p+p £1.00 £4.95**

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE p+p £1.00 £7.45**



GARRARD BARGAIN

LIST PRICE ~~£90.00~~
OUR PRICE **£39.95**

ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00 p+p £1.95**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. **p+p 50p 95p**

86 SB MKII. Belt drive. 2 speed turntable module with plinth and cover.



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers. **£29.90** + £2.50 p&p

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output, 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

£23.00 + £2.50 (NOTE Cabinet not available separately.) **£29.00** + £2.50 without cabinet. p&p complete with cabinet.

SPECIAL OFFER Complete with 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3 1/4" approx. tweeters and crossovers. **£49.00** + p&p £4.00

BUILT AND READY TO PLAY 39.00 + p&p £2.50

30x30 Viscount. Available fully built and tested.



323 EDGWARE ROAD, LONDON W2
21D HIGH STREET, ACTON W3 6NG

ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at 15.12.78 and subject to change without notice.

50 WATT MONO DISCO AMP

£29.95 P&P £2.50
Size approx. 13 1/2" x 5 1/4" x 6 3/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. **SPECIAL OFFER.** The above 50 watt amp plus 4 Goodman Type 8P. 8" speakers. Package price **£45.00 + £4.00 P&P.**

70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls. Five vertical slide controls master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control 70 watt peak (PFL) lets YOU hear next disc before fading 140 watt peak p & p £4.00
It in. VU meter monitors output level. 100 watt **£65**

STEREO CASSETTE TAPE DECK ASSEMBLY

Consisting of ready built tape transport system/mechanism, mated to the electronics. Unit is ready built for installing into cabinet of own choice. Features include pause control, solenoid assisted auto-stop, 3 digit tape counter, belt driven balanced fly wheel by DC motor with electronic speed control, twin VU meters. Specification Power Output, more than 0.5w. mic. -65dB 10K-FL DIN -47dB 100K FL. Track-2 channel stereo record play-back. Tape speed 4.8cm/sec. Freq. response 50-12000 Hz signal to noise ratio 42dB Recording system AC bias Erasing system AC erase Bias freq. 57KHz. Compatible for both normal and chrome dioxide tapes. Size of mechanism only 4 1/2" x 8 1/4" x 11 1/4" approx., included a moulded top-plate as illustrated. **£25.00** P&P £2.50

Opt. extras: Mains transformer to suite **£2.50** + £1 p & p.

ASTRA-PAK

92 GODSTONE ROAD
WHYTELEAFE, SURREY CR3 0EB

GRAND SALE

All prices INCLUDE VAT. Add 25p for P & P (extra for overseas). Send SAE for complete Special Offers list. Where more than one price appears, overall quantity prices apply to groups of devices OF THE SAME TYPE (74 and 74LS cannot be mixed).

7400 Series		74LS00 Series		7400 Series		74LS00 Series		7400 Series		74LS00 Series		CMOS		CMOS		CMOS		STAR OFFER		
1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	*100	741-8	
7400	08	075	07	155	14	13	7485	62	58	55	67	80	56	74161	50	44	40	60	53	48
7401	11	105	10	155	14	13	7486	22	20	18	28	25	23	74162	57	52	48	110	100	92
7402	11	105	10	155	14	13	7489	125	125	118				74163	57	52	48	60	53	48
7403	11	105	10	155	14	13	7490	30	28	26	42	38	36	74164	57	52	48	82	75	70
7404	11	105	10	16	15	135	7491	60	55	52				74165	57	52	48			
7405	12	115	11	16	15	135	7492	33	30	28				74166	70	64	59			
7406	22	21	20				7493	28	25	23	43	40	38	74167	220	205	195			
7407	22	21	20				7494	50	45	43				74168				160	140	125
7408	13	125	12	155	14	13	7495	50	45	42	64	58	55	74169				160	140	125
7409	13	125	12	16	15	135	7496	48	42	38				74170	120	110	100	150	128	112
7410	11	105	10	155	14	13	7497	180	170	165				74172	380	355	340			
7411	17	16	16	16	15	136	74100	80	72	68				74173	90	84	80	85	80	76
7412	14	135	13	16	15	136	74104	40	36	34				74174	64	60	56	58	52	49
7413	23	21	20	26	24		74105	37	34	32				74175	58	54	51	58	52	49
7414	46	43	40	65	57		74107	22	20	18	32	28	28	74176	58	54	51			
7415				16	15	135	74109	50	45	42	32	28	25	74177	56	52	49			
7416	22	20	18				74110	38	34	32				74178	90	80	75			
7417	22	20	18				74111	55	52	50				74179	108	100	95			
7420	11	105	10	155	14	13	74112				32	28	25	74180	80	70	62			
7421	22	21	20	16	15	135	74113	28	26	24	32	28	26	74181	115	95	80			
7422	17	165	16	15	135		74114				32	28	25	74182	52	47	44			
7423	20	19	18				74116	110	100	95				74184	125	108	100			
7425	20	19	18				74118	78	75	72				74185A	100	90	85			
7426	21	20	19	16	15	136	74119	110	100	95				74186	720	690	670			
7427	21	20	19	16	15	135	74120	80	76	74				74188	260	240	225			
7428				18	17	16	74121	24	22	20				74189				198	175	160
7430	11	105	10	155	14	13	74122	32	29	27				74190	68	60	55	72	66	58
7432	21	20	19	23	20	18	74123	38	35	32	55	50	48	74191	68	60	55	70	63	56
7433	30	27	26				74124	160	150	142	115	105	98	74192	62	55	48	88	82	58
7437	20	19	18	24	21	185	74125	32	30	28	38	33	29	74193	60	50	46	68	62	58
7438	20	19	18	24	21	185	74126	32	30	28	38	33	29	74194	58	50	46			
7440	12	116	11	18	16	15	74128	60	55	52				74195	58	50	46	100	92	85
7441	48	45	43				74130	40	36	32				74196	56	50	45	78	71	65
7442	40	36	34	50	44	40	74132	47	44	42	62	56	48	74197	50	44	40	82	83	78
7443	65	60	57				74134	32	30	28				74198	96	85	78			
7444	64	59	56				74135	62	58	55				74199	98	90	85			
7445	53	50	48				74136	52	48	46	38	33	29	74221	120	100	88	94	85	75
7446	55	52	50				74137	74	68	66				74247	90	82	75	40	35	30
7447	50	44	40	87	80	66	74138				52	45	41	74248				90	82	75
7448	55	50	48	87	80	65	74139				52	45	41	74249				90	82	75
7449				87	80	56	74141	52	48	46				74251	100	82	74	58	52	48
7450	12	115	11	16	15	135	74142	185	175	168				74257	68	50	56			
7451	12	115	11	16	15	135	74143	230	210	200				74258	68	56	50			
7453	12	115	11				74144	230	210	200				74266	33	28	25			
7454	12	115	11	165	14	13	74145	45	40	38				74273	190	170	155	200	185	150
7455	12	115	11	16	15	135	74147	100	92	88				74279	110	90	82	46	40	34
7460	12	115	11				74149	84	78	75				74283	150	130	120	58	53	50
7470	25	23	21				74150	60	55	50				74284	350	320	300			
7472	22	20	18				74151	46	41	38	50	44	40	74289				375	345	328
7473	23	21	20	26	23	21	74153	46	41	38	48	42	36	74290	52	48	45			
7474	23	21	20	26	23	21	74154	78	68	60	100	90	82	74293	120	100	80	90	72	65
7475	30	28	26	40	35	32	74155	50	46	44	75	67	60	74298	180	155	140	80	82	75
7476	26	24	23	26	23	21	74156	50	46	44	75	67	60	74352				84	75	70
7478				28	25	23	74157	45	40	38	44	40	38							
7479				28	25	23	74158	55	52	48	44	40	38							
7480	40	36	34				74159	195	180	170										
7483	52	48	46	59	55	52	74160	57	52	48	90	84	75							
7484	84	80	77																	

MIXED PRICES APPLY FOR QUANTITY DISCOUNT

MOTOROLA - 1 WATT AUDIO AMPLIFIER I.C.

9-16V, 8-16Ω, 10-400 MV. Sensitivity. S.C. Proof.

No Heat sink required.
Supplied with Data and Circuits, 90p each.

Don't Let Your Environment Dehydrate You!
Buy our Honeywell Humidity Controller.
Membrane actuated, very sensitive, 1/2 shaft, 250V, 3.75A
Contacts. Ideal for greenhouses, centrally heated homes,
offices etc. Build your own humidifiers or alarms. Fraction of
original cost. £1.50 ea. 3 for £4.

CASSETTE MOTORS
Self Regulating, will operate 8-12V. Ideal for modelers,
mechanical switching etc. 2000 R.P.M. approx. 90p ea.

ULTRASONIC TRANSDUCERS
Transmitter and receiver. 40 kHz 14 mm diam. £4.26 pair.

6 x 6 POLE REED RELAYS ON BOARD
12V ideal for burglar alarms, model railways etc. £2.45

100 MINIATURE REED SWITCHES
We are the cheapest! £3.30

EARPIECES
Magnetic with plug and lead 25p ea. 5 for £1
Crystal with lead 40p ea. 3 for £1

MAKE CHEAP BATTERY ELIMINATORS
Fully shrouded mini mains transformers. 240V in B-0-6V at
100 MA out. Complete with mains lead and plug. ex new
equip. 90p

**DE LUXE FIBRE GLASS
PRINTED CIRCUIT ETCHING KITS**
Includes 150 sq. ins. copper clad F/G. board, 1 lb ferric
chloride, 1 dolo etch resist pen, Abrasive cleaner, Etch tray
plus instructions. Special Price £4.95
1 lb FE. C1. To mil. spec. £1.25
5 lb FE. C1. To mil. spec. £6.00
150 sq. in. Single sided board £2.00
150 sq. in. Double sided board £3.00

SMOKE AND GAS DETECTOR
Uses TGS I05 plug in sensor, housed in neat 3 1/2" dia cast
box, led indicator, 24V, (12V by altering 3 component
values). Will operate lamp or relay, with data and data
circuit. £8.95
Relays for above £1 ea. state voltage

TRANSISTOR PACKS
100. Full spec. new and marked. Includes BC148, BC184L,
MD412, BF274, BC154 etc. £4.95
200 as above and includes AC128, 2N3055, 8P50,
BD131, BF200 etc. £9.95

P/B SWITCH BANKS
These cost a fortune! Were made for various music centres.
Includes independent and interdependent latching types multi
pole etc. Can be modified. Can't be repeated. 3 Banks for
£1

BULK BARGAINS. STOCK UP FOR WINTER
300 mixed 1/2 & 1/4 watt resistors £1.50
150 mixed 1 & 2 watt resistors £1.50
300 mixed capacitors, modern, most types £3.30
100 mixed ceramic and plate caps £1.20
25 pots and presets £1.20
25 resistors, skeleton etc. £1.20
20 VDRs and thermistors £1.20
100 Hi-wattage resistors wirewound etc. £2.20
100 electrolytics, nice values £2.20
300 printed circuit resistors £1
300 printed circuit components £1.50

100K MINIATURE THUMBWHEEL SLIDER POTS
Very neat, can be banded side by side. Ideal for v. cap
turning, graphic equalisers etc. 10 for £1


100K STEREO SLIDER POTS
Good quality. 25p ea. 5 for £1

MINIATURE LEVEL/BATT. METERS 200µA
F.S.D. as fitted to many cassette recorders. 90p

SINCLAIR PRODUCTS microvision tv UK
model £89.95. PDM35 £27.25. Mains adaptor
E96.50. Case £3.25. DM350 £67.80.
DM450 £96.50. DM235 £49.45. Recharge-
able batts. £7.50. Mains adaptor £3.70.
Enterprise prog. calculator £21.95. Cam-
bridge prog. calculator £13.13. Prog. library
£3.45. Mains adaptor £3.45.
COMPONENTS

Understanding Digital Electronics

New teach-yourself courses

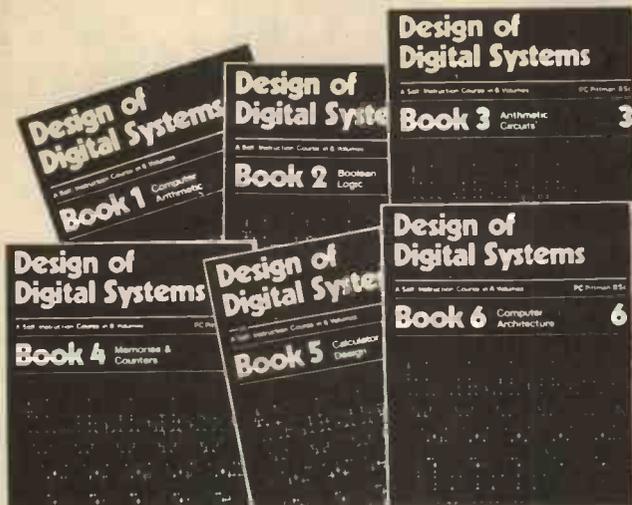

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.


Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

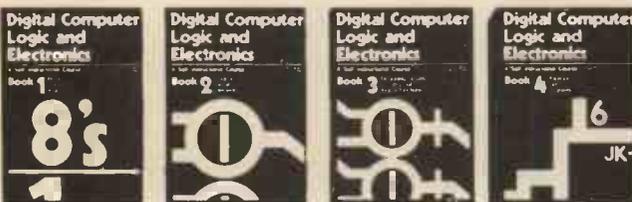Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, Unit 26, Rivermill Site, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only: **£8.10** +90p post & packing

And the four volumes of Digital Computer Logic and Electronics cost only: **£4.60** +90p post & packing

But if you buy both courses, the total cost is only: **£12** +£1 post & packing

Price includes surface mail anywhere in the world: Airmail extra.

Flow Charts & Algorithms

HELP YOU PRESENT:

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

£2.95 + 45p post and packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.

Please allow 21 days for delivery.

Cambridge Learning Enterprises, Unit 26, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.

Please send me the following books:

- sets Digital Computer Logic & Electronics @ £5.50, p & p included
- sets Design of Digital Systems @ £9.00, p & p included
- Combined sets @ £13.00, p & p included
- The Algorithm Writer's guide @ £3.40, p & p included

Name

Address

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number.....

Signature..... *delete as appropriate.

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

PE26

SAXON ENTERTAINMENTS

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,
TWIN SPEAKERS & LEADS

Standard 100W

£249 + carr. £15 + VAT
or Deposit £57.12
12 Months @ £22.23 or 24 Months @ £12.73

Super 200W

£299 + carr. £15 + VAT
or Deposit £68.12
12 Months @ £26.41 or 24 Months @ £15.11

GXL 200W (with twin 200 watt cabinets)

£389 + carr. £15 + VAT
or Deposit £87.32
12 Months @ £34.02 or 24 Months @ £19.47

BSR Decks - 17,000 Line Loudspeakers - Rugged Aluminium Trimmed Cabinets - Cue Light And Phones Output - Slave Output - Deck Lights/Motor Starts (GXL)
ALSO CENTAUR 'CUSTOM' 400-600W £699 - ASK FOR DETAILS

COMPLETE STEREO
ROADSHOWS - BUILT IN
SOUND TO LIGHT/SEQUENCER
& DISPLAY
TWO YEAR GUARANTEE



illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & mic with monitoring facilities - override and are supplied complete with sound to light + sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

MINI DISCO 100 WATT MONO SYSTEM

£179.50 + carr. £15 + VAT
Deposit £42.06
12 Months @ £16.43 or 24 Months @ £9.43

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system
EM507 Electret Mic £15.00
D1501 Electret Mic £18.50
Boom Stand £15.50
Carriage on all disco and PA systems £10.00
(Included in H.P. Prices)

20% Deposit Terms
12 to 24 Months
- Low Interest

AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers

NEW 240 WATT 4 OHM INDUSTRIAL MODULES EIGHT OUTPUT DEVICES
£35 SUPPLY £24.75

SA308 8 ohms 30W 45V	£10.75*	Supply for 2 modules	£11.90*
SA604 4 ohms 50V	£14.50	Supply for one or 2 modules	£14.95
SA608 8 ohms 60W 65V	£15.50	Supply for 1 module	£14.95
SA1204 4 ohms 120W 75V	£17.50	Supply for 2 modules	£24.75
SA1208 8 ohms 120W 95V	£21.00		

SOUND-TO-LIGHT UNITS


3 CHANNEL - 3kW

- Operates from 1W upwards
- Bass/middle/treble/master controls

£29.50 + £1 carr complete
Module only £19.75 Panel £2.95

4 CHANNEL - 4 kW SOUND/LIGHT SEQUENCER (illus)

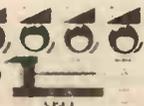- Dimmer on each channel
- Automatic sound light level
- Logic circuitry throughout



S.P. 1

£39.50 Carr £1
Module only £26.75 Panel £2.95

100W SPOTS

Red - Blue - Amber - Green £1.50 ea. Carr 50p max Free on 10+

HEAVY DUTY SPOT BANKS - MATCHES LOUDSPEAKERS

3 way 600W £35.50 4 way 800W £39.50 Carr £2

SAXON KLAXON



FOUR WAY SIREN



UK Police - Destroyer - US Police - Hawaii Five-O
All the effects you need in one package £17.50 Carr free
Individual sirens with any of the above effects £7.50

SAXON 'SMASH' ALIEN VOICE SIMULATOR

Add a new dimension to your disco with this press button effect unit - just insert between mic and amplifier £7.50 Carr free



SAXON 'SCINTILLITE'

Rope light controller with auto reverse £24.75 Carr free



SAXON Rope Lights multicolour 25 feet long
Easy to change lamps £35.50 Carr £1 Spare bulbs 10p ea.

FUZZ LIGHTS Red, Blue Yellow, Green £22.80

DISCO MIXERS - COMPLETE OR MODULAR



Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

MONO OR STEREO WITH AUTOFADE	
MODULES	
Mono module	£27.50
Stereo module	£37.50
Panel	£3.95
Kit of knobs/sockets etc	£5.50

FEATURES INCLUDE:
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.

COMPLETE MIXERS (with case)	
Mono mains	£45.75
Stereo mains	£63.75

CABINET FITTINGS

ICI Vynide 50" wide £3.50m Kick-res grille 50" wide £3.50m
Netlon kick proof 24" wide £3.50m
Corners/feet/recess plates 15p ea. Recess handle 45p
Bar handles £2.50 Jack plugs/sockets 25p

LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24)	£39.00	Carr £3 Deposit £9.36
Large 100W 1 x 12 (65 x 48 x 24)	£49.50	Carr £3 Deposit £12.70
P.A. 1 x 12 (+2 Piezos) (80 x 38 x 24)	£66.50	Carr £3 Deposit £15.82
P.A. 2 x 12 200W (100 x 38 x 24)	£99.00	Carr £3 Deposit £20.92
Disco 2 x 12 200W (80 x 63 x 24)	£85.00	Carr £3 Deposit £19.80
PDF reflex bin (80 x 40 x 41)	£95.00	Carr £3 Deposit £20.60

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals


- Use with all types of mixer
- Pan and volume controls
- Send for details

£130 Carr £3
Deposit £28.40

PLUTO PROJECTORS & WHEELS

P140 150 Watt tungsten remarkable value
£37.50 Carr £1.00
Deposit £8.66

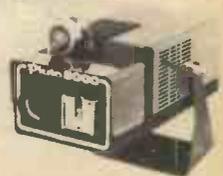P5000 250 Watt Q.I. + fan Intachange fitting
£87.50 Carr £1.00
Deposit £20.28



Picture wheels from £4.75 - a wide range of wheels & effects available - send for leaflet

MOTOROLA PIEZO HORNS £4.50. YES!!

NOW OPEN AT

MANCHESTER PACKAGE DEAL

P.A. SYSTEMS

2 YEAR GUARANTEE

100 WATT £159.90 + Carr **DEPOSIT £37.89**
 £15 + VAT £13.99

- 12 mth @ £14.77 or 24 mth @ £8.48
- ★ AP100 4 INPUT AMPLIFIER (see below)
- ★ TWIN PIEZO HORN 100W COLUMNS & LEADS

200 WATT £249.00 + Carr **DEPOSIT £57.12**
 £15 + VAT £21.12

- 12 mth @ £22.23 or 24 mth @ £12.73
- ★ USES NEW AP200 SIX INPUT AMPLIFIER (below)
- ★ PAIR OF TWIN 200W PIEZO HORN COLUMNS




AP100 AMPLIFIER £49.50 +VAT £4.08

- ★ 4 mixing units + £1.50 Carr
 - ★ Bass, treble, master controls
 - ★ Twin outputs – vynide case
- Deposit £10.22**



AP200 NEW £89.50 +VAT £7.28

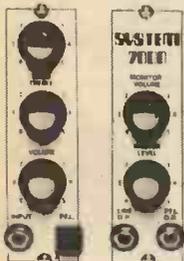- ★ 6 mixing inputs + £2.50 Carr
 - ★ 3 set of bass/treble controls
 - ★ Master & Presence controls
- Deposit £20.36**



Make your own mixer
SYSTEM 7000
 Mono/Stereo up to 20 channels accept all inputs available as PCB only or complete on front panels

D.I.Y. MODULES FOR P.A. SYSTEMS

MONO/STEREO

Input Modules	Mono PCB only	£6.50	Mono C/W Front panel	£9.50
	Stereo PCB only	£10.50	Stereo C/W Front panel	£13.75
Mixer/Monitor Modules	Mono PCB only	£6.50	Mono C/W Front panel	£9.50
	Stereo PCB only	£10.50	Stereo C/W Front panel	£13.75

Power supply to suit £9.50 – send for full details of uses

PA SYSTEM ACCESSORIES	D1501 Dual Imp High O/P Condenser mic	£18.50*	TWIN PIEZO HORN BOXES to match other cabinets Carr £1.50 Deposit £7.32
	EM507 High output single impedance mic	£15.00*	
	ECM105 Low cost condenser mic	£5.00*	
Heavy chrome mic stand – collapsible £9.90 Boom version £16.95	MELOS CASSETTE ECHO/REVERB Twin input unit – infinitely variable speed, depth & delay – playback feature Suits all mics & instruments	£65.00 Carr £1 Deposit £14.80	ADD ANY ACCESSORIES TO YOUR TOTAL CREDIT ORDER

All prices subject to 8% VAT except where asterisked (12½%)
 Shop premises open Tues to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm
 Mail order dept open Mon to Fri 10 am - 4 pm Ring 01-684 6385

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclay Card Number NOT THE CARD.

By Phone You may order COD, Access or Barclay Card.

Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS

327 Whitehorse Road, Croydon, Surrey.
 All Enquiries Large SAE Please Brochures on request.

MANCHESTER DISCO CENTRE, 237 DEANSGATE, MANCHESTER CALLERS ONLY – (061) 832 8772 – COMPLETE UNITS ONLY



Wilmslow Audio

THE firm for speakers!

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

- AUDAX ● AUDIOMASTER ● BAKER
 BOWERS & WILKINS ● CASTLE ● CELESTION
 CHARTWELL ● COLES ● DALESFORD
 DECCA ● EMI ● EAGLE ● ELAC ● FANE
 GAUSS ● GOODMAN ● I.M.F. ● ISOPHON
 JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER
 MCKENZIE ● MONITOR AUDIO ● PEERLESS
 RADFORD ● RAM ● RICHARD ALLAN ● SEAS
 SHACKMAN ● STAG ● TANGENT ● TANNOY
 VIDEOTONE ● WHARFEDAILE ● YAMAHA

WILMSLOW AUDIO (Dept. P.E.)
SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street
 Tel.: Wilmslow 529599 for Speakers Tel.: Wilmslow 526213 for Hi-Fi



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA

Free! Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, PEK 3/79
 P.O.Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)

It's W-W-WINTER S-S

74 SERIES TTL IC'S

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7440	£0.07	7427	£0.21	7472	£0.19	74107	£0.22	74165	£0.85
7401	£0.09	7428	£0.25	7473	£0.22	74110	£0.35	74166	£0.75
7402	£0.09	7430	£0.08	7474	£0.22	74111	£0.55	74167	£0.75
7403	£0.09	7432	£0.20	7475	£0.27	74118	£0.75	74174	£0.60
7404	£0.09	7433	£0.28	7476	£0.22	74119	£1.10	74175	£0.60
7405	£0.09	7437	£0.20	7480	£0.40	74121	£0.22	74176	£0.55
7406	£0.22	7438	£0.20	7481	£0.80	74122	£0.35	74177	£0.55
7407	£0.22	7440	£0.10	7482	£0.65	74123	£0.38	74180	£0.80
7408	£0.12	7441	£0.48	7483	£0.55	74136	£0.50	74181	£1.25
7409	£0.12	7442	£0.38	7484	£0.82	74141	£0.50	74182	£0.55
7410	£0.09	7443	£0.68	7485	£0.65	74145	£0.54	74184	£1.00
7411	£0.15	7444	£0.68	7486	£0.22	74150	£0.65	74190	£0.68
7412	£0.14	7445	£0.64	7489	£1.60	74151	£0.45	74191	£0.68
7413	£0.22	7446	£0.60	7490	£0.30	74153	£0.45	74192	£0.65
7414	£0.45	7447	£0.45	7491	£0.60	74154	£0.80	74193	£0.60
7416	£0.22	7448	£0.52	7492	£0.32	74155	£0.40	74194	£0.85
7417	£0.22	7450	£0.09	7493	£0.28	74156	£0.48	74195	£0.55
7420	£0.09	7451	£0.09	7494	£0.70	74157	£0.48	74196	£0.60
7421	£0.19	7452	£0.09	7495	£0.45	74160	£0.55	74197	£0.58
7422	£0.15	7453	£0.09	7496	£0.48	74161	£0.60	74198	£1.00
7423	£0.20	7454	£0.09	74100	£0.80	74162	£0.60	74199	£1.00
7425	£0.19	7460	£0.09	74104	£0.35	74163	£0.60	74279	£1.00
7426	£0.21	7470	£0.24	74105	£0.35	74164	£0.65		

CMOS I.C.'s

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.12	CD4017	£0.65	CD4031	£1.60	CD4055	£1.00
CD4001	£0.13	CD4018	£0.70	CD4035	£0.90	CD4056	£1.15
CD4002	£0.13	CD4019	£0.35	CD4037	£0.78	CD4069	£0.15
CD4006	£0.80	CD4020	£0.80	CD4040	£0.78	CD4070	£0.15
CD4007	£0.14	CD4021	£0.75	CD4041	£0.88	CD4071	£0.15
CD4008	£0.80	CD4022	£0.78	CD4042	£0.68	CD4072	£0.15
CD4009	£0.40	CD4023	£0.13	CD4043	£0.78	CD4081	£0.15
CD4010	£0.42	CD4024	£0.55	CD4044	£0.78	CD4082	£0.16
CD4011	£0.13	CD4025	£0.15	CD4045	£1.15	CD4510	£0.80
CD4012	£0.14	CD4026	£1.00	CD4046	£0.95	CD4511	£0.80
CD4013	£0.35	CD4027	£0.43	CD4047	£0.75	CD4516	£0.85
CD4014	£0.70	CD4028	£0.60	CD4049	£0.35	CD4518	£0.85
CD4015	£0.70	CD4029	£0.75	CD4050	£0.35	CD4520	£0.85
CD4016	£0.35	CD4030	£0.40	CD4054	£0.98		

BOOKS BY BABANI

The following books are offered at 10% off their normal price.

		Normal Price	Sale Price
BP6	Engineers & Machinists Reference Tables	£0.40	£0.36
BP14	Second Book of Transistor Equivalents & Substitutes	£1.10	£0.99
BP22	79 Electronic Novelty Circuits	£0.75	£0.68
BP24	52 Projects Using IC741 or equivalents	£0.75	£0.68
BP26	Radio Antenna Handbook for Long Distance Reception & Transmission	£0.85	£0.77
BP27	Giant Chart of Radio Electronic Semi-conductor and Logic Symbols	£0.60	£0.54
BP32	How to Build Your Own Metal & Treasure Locators	£0.85	£0.77
BP34	Practical Repair & Renovation of Colour TV's	£0.95	£0.86
BP35	Handbook of IC Audio Pre-amplifier & Power amplifier construction	£0.95	£0.86
BP36	50 Circuits Using Germanium, Silicon & Zener Diodes	£0.75	£0.68
BP37	50 Projects Using Relays SCR's and Triacs	£1.10	£0.99
BP39	50 (FET) Field Effect Transistor Projects	£1.25	£1.13
BP40	Digital IC Equivalents & Pin Connections	£2.50	£2.25
BP41	Linear IC Equivalents & Pin Connections	£2.75	£2.48
BP42	50 Simple LED Circuits	£0.75	£0.68
BP43	How to make Walkie-Talkie	£1.25	£1.13
BP44	IC 555 Timer Projects	£1.45	£1.31
BP45	Projects on Opto-Electronics	£1.25	£1.13
BP46	Radio Circuits using IC's	£1.35	£1.22
BP47	Mobile Discotage Handbook	£1.35	£1.22
BP48	Electronic Projects for Beginners	£1.35	£1.22
BP49	Popular Electronic Projects	£1.45	£1.31
BP50	IC LM3900 Projects	£1.35	£1.22
BP55	Radio Stations Guide	£1.45	£1.31
BP160	Coil Design & Construction Manual	£0.75	£0.68
BP202	Handbook of Integrated Circuits (ICs) Equivalents & Substitutes	£0.75	£0.68
BP205	First Book of Hi-Fi Loudspeaker Enclosures	£0.75	£0.68
BP213	Electronic Circuits for Model Railways	£0.85	£0.77
BP215	Shortwave Circuits & Gear for Experimenters and Radio Hams	£0.85	£0.77
BP216	Electronic Gadgets & Games	£0.85	£0.77
BP217	Solid State Power Supply Handbook	£0.85	£0.77
BP221	28 Tested Transistor Projects	£0.95	£0.86
BP222	Solid State Short Wave Receivers for Beginners	£0.95	£0.86
BP223	50 Projects Using IC CA3130	£0.95	£0.86
BP224	50 CMOS IC Projects	£0.95	£0.86
BP225	A Practical Introduction to Digital ICs	£0.95	£0.86
BP226	How to Build Advanced Short Wave Receivers	£1.20	£1.08
BP227	Beginners Guide to Building Electronic Projects	£1.25	£1.13
BP228	Essential Theory for the Electronics Hobbyist	£1.25	£1.13

VPS30 Variable Regulated Stabilised Power Supply Module

Incorporating a short circuit protection and current limiting:
 Voltage Regulation 2-30V
 Regulated Current 0-2A
 AC Input Maximum 25V
 Eliminates the use of batteries and thus saves £'s-can be used time and time again
 ONLY £7.60 + V.A.T.

BRAND NEW	
ITT 923 Silicon Diodes 200mA 200v.	
100 off	£ 9.00
500 off	£ 9.00
1000 off	£ 15.00
10,000 off	£130.00

P.C. BOARD	
Single-Sided Fibre Glass Board	
12" x 3 1/2" approx. 2 pcs	£0.60
S143	

THYRISTORS

No. THY1A/50	1 Amp	50 volt	T05	18p
No. THY1A/400	1 Amp	400 volt	T05	32p
No. THY3A/50	3 Amp	50 volt	T064	25p
No. THY3A/200	3 Amp	200 volt	T064	32p
No. THY3A/400	3 Amp	400 volt	T064	40p
No. THY5A/50	5 Amp	50 volt	T086	25p
No. THY5A/400	5 Amp	400 volt	T086	40p
No. THY5A/600	5 Amp	600 volt	T086	50p
No. C106/4	6 Amp	400 volt	T0220	42p

TRIAC

S84 8 Amp 400 volt T0220 80p

DIACS

ITT. V413 equit	12p
BR100	D32 each 12p

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF - 10µF
16202	18 Electrolytics	10µF - 100µF
16203	18 Electrolytics	100µF - 680µF
All 3 at SPECIAL PRICE of £1.20*		
16160	24 Ceramic Caps	22pF - 82pF
16161	24 Ceramic Caps	100pF - 390pF
16162	24 Ceramic Caps	470pF - 3300
16163	21 Ceramic Caps	4700pF - 0.047µF
All 4 at SPECIAL PRICE of £1.80*		

RESISTOR PAKS

Order No.			
16213	60 1/2W.	100 ohm - 820 ohm	
16214	60 1/2W.	1K - 8.2K	
16215	60 1/2W.	10K - 82K	
16216	60 1/2W.	100K - 820K	
All 4 at SPECIAL PRICE of £1.60*			
16217	40 1/2W.	100 ohm - 820 ohm	
16218	40 1/2W.	1W - 8.2K	
16219	40 1/2W.	1K - 8.2K	
16220	40 1/2W.	100K - 820K	
All 4 at SPECIAL PRICE of £1.60*			

VOLTAGE REGULATORS

Positive			
No. MVR7805	µA7805	T0220	55p
No. MVR7812	µA7812	T0220	55p
No. MVR7815	µA7815	T0220	55p
No. MVR7818	µA7818	T0220	55p
No. MVR7824	µA7824	T0220	55p
Negative			
No. MVR7905	µA7905	T0220	75p
No. MVR7912	µA7912	T0220	75p
No. MVR7915	µA7915	T0220	75p
No. MVR7918	µA7918	T0220	75p
No. MVR7924	µA7924	T0220	75p
µA723C T099 38p 72723 14 pin Dtl 38p			
LM309K T123 £1.20			

SWITCHES

No. 16178	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

AUDIO LEADS

Order No.		
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug - Mirror Image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p*

AUDIO PLUG AND SOCKET PAKS

Order No.		
S1	5 x 3.5 mm Plastic Jack Plugs	40p*
S2	5 x 2.5 mm Plastic Jack Plugs	40p*
S3	4 x Std. Plastic Jack Plugs	50p*
S4	2 x Stereo Jack Plugs	30p*
S5	5 x 5 Pin 180° DIN Plugs	50p*
S6	8 x 2 Pin Loudspeaker Plugs	50p*
S7	6 x Phono Plugs Plastic	50p*
S8	5 x 3.5 mm Chassis Sockets (Switched)	25p*
S9	5 x 2.5 mm Chassis Sockets (Switched)	25p*
S11	2 x Stereo Jack Sockets with instruction leaflet for Hi/Phone connection.	50p*
S12	5 x 5 Pin 180° DIN Chassis Sockets	40p*
S13	8 x 2 Pin DIN Chassis Sockets	50p*
S14	6 x Single Phono Sockets	40p*

P.C. BOARD	
S110	Mixed Bundle, P.C.B., Fibre-glass/paper, single and double-sided. Fantastic value 75p

SPECIAL OFFER!

UNTESTED

SEMICONDUCTOR PAKS
 Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/81	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like IN4148	40p
No. 16134	50 750mA Sil. top hat Rects.	40p
No. 16135	20 3 amp Sil. stud Rect.	40p
No. 16136	50 400mW Zeners D.O.7 case	40p
No. 16137	30 NPN Plastic Trans. like OC107/8	40p*
No. 16138	30 PNP Plastic trans. like BC177/8	40p*
No. 16139	25 NPN trans. like 2N697/2N1711 T039	40p
No. 16140	25 PNP trans. like 2N2906 T039	40p
No. 16141	30 NPN trans. like 2N706 T018	40p
No. 16143	30 NPN Plastic trans. like 2N3906	40p*
No. 16144	30 PNP Plastic trans. like 2N3905	40p*
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN to 3 Power trans. like 2N3055	80p

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 24 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

MAMMOTH I.C. PAK

Approx. 200 pieces Assorted fall-out integrated circuits, including Logic 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked-you to identify.
 Order No. 16223 £1.00

MATCHED PAIRS OF PNP GERMANIUM MED. POWER TRANS

VCE	VCB	HFE	
2 amp 750mW			
NKT301	40	60	30-100 35p per pair
NKT302	40	60	50-150 35p per pair
NKT303	20	30	30-100 25p per pair
NKT304	20	30	50-150 25p per pair

From U.S.A. by

DINDY SCREW CASED LOW NOISE CASSETTES



Order No. 553 10 for £3.50

HEAD-CLEANING CASSETTE 45p each

AUDIO AMPLIFIER

RETURN OF THE AL20A
 By popular demand - this useful 5 watt RMS Power Amplifier is offered at the re-introductory price of £2.75* - Hook-up data supplied.

ETCH RESIST PENS

Order No. 1609 50p each

UNIUNCTION TRANSISTORS

UT46	TIS43	20p
FET's		

SALE T-TIME again!

SPECIAL OFFER!

COMPONENT PAKS

Order No.	Quantity	Price
16168	5 pieces Assorted Ferrite rods	40p
16169	2 pieces Tuning gangs MW/LW	40p
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p
16172	3 Micro switches	40p
16176	20 Assorted electrolytics	40p
	Tran types	
16177	1 pack Assorted Hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p
16184	15 Assorted Fuses 100mA-5 amp	40p
16188	60½W resistors mixed values	40p
16187	30 metres stranded wire assorted colours	40p
S100	120 ½ watt resistors. Pre-formed. 1978 Prod. Our mix	60p*
S101	120 ½ watt resistors. Pre-formed. 1978 Prod. Mixed values	60p*
S102	250 ½ watt resistors. Range 100 ohms - 1.8 meg.	£2.00*
S103	220 ½ watt resistors. Range 100 ohms - 10 meg.	£2.00*
S104	60 Low ohms ½ watt resistors. 10 - 100 ohms	80p*
S105	40 Low ohms ½ watt resistors. 12 - 100 ohms	60p*
S106	25 Mixed wirewound resistors	80p*
S107	20 Tantalum bead caps 0.22 - 100mF Our mix	£1.00*
S108	High quality electrolytics 10mF-500mF voltage range 15-50v. Our mix. 40 for	£1.00*
16204	C280 Pak. Contains 50 metal foil caps	£1.00*

POTENTIOMETERS

Order No.	Quantity	Price
16191	6 x 470 Ohm LIN Single	40p*
S24	6 x 1K LIN Single	40p*
S25	6 x 5K LIN Single	40p*
16193	6 x 22K LIN Single	40p*
16195	6 x 47K LOG Single	40p*
16194	6 x 47K LIN Single	40p*
S27	6 x 100K LIN Single	40p*
S28	6 x 100K LOG Single	40p*
S29	6 x 500K LOG Single	40p*
S32	6 x 50K LIN Single	40p*

Order No.	Quantity	Price
S30	6 x 2.5K LOG Single	40p*
S34	4 x 5K LOG Dual	40p*
S36	4 x 100K LOG Dual	40p*
S37	4 x 1K LOG Dual	40p*
S94	8 x 220K LIN Single	40p*
S95	6 x 100K LOG Single	40p*
S96	6 x 500K LIN Single	40p*
S38	Mixed slider pots - various values and sizes - our mix	only £1.00*
S39	6 x Chrome slider knobs	40p*

WIREWOUND

S90	Wirewound Pots. Linear 1 Watt rating. Mixed useful values. 5 for	£1.00*
-----	--	--------

CARBON TYPES

S91	Car Radio type. Dual Switched Pot P.C. mounting 100K Lin switched 2.5K Lin	each 60p*
-----	--	-----------

DUAL POTS P.C. MOUNTING

6mm Shaft	Quantity	Price
S92	4 x 100K Lin	£1.00*
S93	4 x 100K Log	£1.00*
16173	15 Rotary Pot Assorted	40p*
16186	25 Pre-sets Assorted Values	40p*

ZENER PAKS

No. S55	20 mixed values 400mW Zener diodes 3-10V	£1.00
No. S56	20 mixed values 400mW Zener diodes 11-33V	£1.00
No. S57	10 mixed values 1W Zener diodes 3-10V	£1.00
No. S58	10 mixed values 1W Zener diodes 11-33V	£1.00

SILICON POWER TRANS. N.P.N.

S97	B0371 2 Amp 1.2w. 60Vceo Hfe 40-400. Case T092 with heat tab. 5 for	60p*
S98	2N5293 R.C.A. 36w 4 Amps 75Vceo Hfe 30-120. 5 for	£1.00*

Crystal Ear Pieces
S126 Less plug £0.20*

Plugs for above
No. 16106 2.5 plastic £0.09*
No. 1697 3.5 plastic £0.11*

Mono Crystal Cartridge
S127 GP91/1SC Special Offer £1.00*

Nickel Cadmium Rechargeable Batteries 1.25V
S128 3500D Cell size=U2 £2.50
S129 900C Cell size=½U11 £0.90

S130 Complete kit of parts to build nickel cadmium charger £3.50

Super Save Pak
S124 6 x 741P £1.00
S125 5 x 555 £1.00

S138 Surplus/End of Manufacturers Line/Pre-amp, with Base, Treble, Volume Control & circuit diagram supplied. DNCE ONLY OFFER £1.25*

S137 20 Assorted Slider Knobs - Chrome/Black £1.00*

S131 2 x 12v Relays plastic case £0.70*

S132 2 x 24v Relays plastic case £0.60*

S133 1 switch bank 5 way incl. silver knob £0.75*

S134 2 x Magnets suitable for reed switches £0.10

S135 .1 Veroboard pak 2 pcs 45 sq. ins. approx. £0.80

S136 .15 Veroboard pak 2 pcs 60 sq. ins. approx. £1.10

16199 .1 Veroboard pak pcs 30 sq. ins. approx. £0.50

16200 .15 Veroboard pak pcs 30 sq. ins. approx. £0.50

TOOLS

No. 2011 5" wire cutters £1.55

No. 2012 5" long wire plyer £1.45

SUPER DUPER COMPONENT BOX

Min. 3lbs in weight consisting of a fantastic assortment of Electronic Components - Pots, Resistors, Condensers, Switches, Relays, Board - Semiconductors, wire, hardware, Etc., etc.,

This is a large box and is sent separate to your order £2.50 including p & p. S140

TRANSFORMERS SALE OFFER

S141 O235 240v primary, 0-55v at 2 amp secondary. £4.50* + £1.00 p&p.

S142 O349 240v primary, 0-20v at 2Amp secondary. £3.50* + £0.86 p&p.

COMPLETE AUDIO AMPLIFIER KITS:

STA15 15 watts per channel amplifier kit
Consists: 2 x AL60-1xPA100-1xSPM80
1 x 2034 transformer-£37.70inc VAT
2x coupling capacitors + .86p p0p

STA25 25watts per channel amplifier kit. Consists: 2xAL60-1xPA100-1xSPM120/45
1x2040 Transformer -1xreservoir cap £41.45inc VAT
2xcoupling capacitors + £1.16p p & p

STA35 35 watts per channel amplifier kit. Consists: 2xAL80-1xPA100-1xSPM120. 1x2041 transformer-1 reservoir capacitor £48.45inc VAT
2xcoupling capacitors + £1.16p p & p

STA50 50 watts per channel amplifier kit. Consists: 2xAL120-1xPA200-1xSPM120/65
1x2041 transformer -1xreservoir capacitor £58.20inc VAT
2xcoupling capacitors + £1.10p p & p

STA125125 watts per channel amplifier kit. Consists: 2xAL250-1xPA200-2xSPM120/65
2x2041 transformers-1xreservoir capacitor £72.85inc VAT
2xcoupling capacitors + £1.25p p & p

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p	2N1893	28p
AC128	16p	BC182	*9p	BF197	*12p	TIP41A	34p	2N2218	15p
AC128K	24p	BC182L	*9p	BF200	25p	TIP41B	35p	2N2218A	18p
AC176	16p	BC183	*9p	BFX29	22p	TIP41C	36p	2N2219	15p
AC176K	24p	BC183L	*9p	BFX84	18p	TIP42A	36p	2N2219A	18p
AC187	24p	BC184	*9p	BFY50	12p	TIP42B	37p	2N2221	15p
AC187K	26p	BC184L	*9p	BFY51	12p	TIP42C	38p	2N2221A	16p
AC188	16p	8C212	*10p	BFY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	8C212L	*10p	MPSA05	*22p	TIP3055	42p	2N2222A	16p
AD161	8p	8C213	*10p	MPSA06	*22p	ZTX107	*6p	2N2369	10p
162MP	8p	8C213L	*10p	MPSA07	*22p	ZTX108	*6p	2N2904	14p
AF139*	30p	8C214	*10p	MPSA55	*22p	ZTX109	*7p	2N2904A	15p
AF239	30p	8C214L	*10p	MPSA56	*22p	ZTX300	*7p	2N2905	14p
BC107	6p	8C251	*10p	OC44	12p	ZTX301	*7p	2N2905A	15p
BC108	6p	8C252	*10p	OC45	12p	ZTX302	*9p	2N2906	12p
BC109	6p	8C253	*10p	OC71	12p	ZTX500	*8p	2N2906A	14p
BC118	*10p	8C254	*10p	OC72	12p	ZTX501	*10p	2N2907	12p
BC147	*8p	BD115	*40p	OC75	10p	ZTX502	*12p	2N2907A	13p
BC148	*8p	BD131	*35p	OC81	14p	2N696	10p	2N2926G	*8p
BC149	*8p	BD132	*37p	TIP29A	35p	2N697	10p	2N2926Y	*7p
BC150	*16p	BF115	17p	TIP29B	35p	2N706	7p	2N3053	12p
BC157	*9p	BF167	19p	TIP29C	38p	2N706A	8p	2N3055	35p
BC158	*9p	BF173	20p	TIP29C	38p	2N708	8p	2N3702	*7p
BC159	*9p	BF180	25p	TIP30A	36p	2N1302	12p	2N3703	*7p
BC169	*10p	BF181	25p	TIP30B	37p	2N1303	15p	2N3704	*6p
BC169C	*6p	BF182	25p	TIP30C	38p	2N1304	15p	2N3903	*11p
BC171	*6p	BF183	25p	TIP31A	32p	2N1307	18p	2N3904	*11p
BC172	*6p	BF184	25p	TIP31B	33p	2N1308	22p	2N3905	*11p
BC173	*7p	BF185	25p	TIP31C	34p	2N1309	22p	2N3906	*11p

RESISTORS

40 mixed values 1 watt & 2 watt Resistors no S143 £0.60*

PROGRAMMABLE UNIJUNCTIONS

2N6027 with Data £0.24

DIODES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	BAX18/	5p	BY218	5p	OA85	7p	IS44	3p
AA213	4p	OA202	5p	BY217	28p	OA80	7p		
BA100	6p			BY218	28p	OA91	7p	IN5400	10p
BA115	5p	BY100	15p	BY219	28p	OA95	7p	IN5401	11p
BA144	5p	BY127	*10p					IN5402	12p
BA148	10p	BY210	32p	OA47	5p	IN34	5p	IN5404	13p
BA173	10p	BY211	32p	OA70	5p	IN60	6p	IN5406	16p
BAX13/	5p	BY212	32p	OA79	7p	IN814	4p	IN5407	17p
OA200	5p	BY213	30p	OA81	7p	IN4148	4p	IN5408	19p

LINEAR I.C.'s

TBA800	£0.75*	UA711	£0.25*	UA748	£0.28*
TBA810	£0.88*	UA703	£0.20*	72558	£0.45*
TBA820	£0.65*	741P	£0.20*	MC1310P	£1.25*
LM380	£0.80*	72741	£0.20*	78115	£1.25*
LM381	£1.25*	UA741C	£0.20*	NE555	£0.22
72709	£0.20*	72747	£0.55*	SL414A	£1.80*
UA709	£0.20*	748P	£0.28*		

ZN 414 RADIO CHIP 75*

OPTOELECTRONICS

Displays	Price	2nd Quality Led Paks	Price
No. 1510 707 LED Display	£0.70	No. 1507 10 Assorted Colours & Size	£0.75
No. 1511 747 LED Display	£1.50	No. S122 10 x .125 Red	£0.60
No. 1512 727 Dual LED Display	£1.55	No. S123 10 x .2 Red	£0.60

LED's	Price
No. S120 .125 Bright Red	£0.09
No. S121 .2 Bright Red	£0.09
No. S102 .125 Green	£0.12
No. S105 .2 Green	£0.12
No. S103 .125 Yellow	£0.12
No. S106 .2 Yellow	£0.12
No. S82 Clear 2 Illuminating Red	£0.10

P.O. RELAYS

S85 - 2 Off Post Office relays 40p*

BATTERY HOLDERS

to take 6 x HP7's
Order No. 202 each 10p

EX. G.P.O. MICROSWITCHES

Order No. S51 4 for 50p

CABLE CLIPS

S65 - 50 2.5mm round single pin fixing 30p

LED Clips	Price
No. S108/.125 .125 5 for	£0.12
No. S108/.2 .2 5 for	£0.15

No. S139 Infra Red Emitter Fairchild FPE100 £0.50

SPECIAL REDUCTIONS

No. 1514 NORP 12 each 45p
No. S76 OCP71 5 for £1.00
No. S83 5 NIXIE Tubes ITT 5870 ST £2.00 (Including Data)

No. S77 Neon Indicator Lamps 230V A.C. State Colour (Red, Amber and Green.) 25p each

POWER SUPPLY STABILIZER BOARD

KITS FOR SYNTHESISERS, SOUND EFFECTS



COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHOTOCOPIES of P.E. texts for most of the kits are available—prices in our lists.

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, mixer, power supply.

Set of basic component kits **from £81.00**
Set of printed circuit boards **£8.99**

P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage. Details in our lists.

FORMANT SYNTHESISER (Elektor 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

128-NOTE TUNE-PROGRAMMABLE SEQUENCER

(P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

Main Circuit (Nov) excl. sw's (KIT 76-1) **£18.03**
Power Supply (KIT 76-3) **£4.72**
Trigger Inverter and Alt. Output (KIT 76-2) **£1.15**
LED Counter (KIT 76-4) **£2.10**
PCB (as published) for KITS 76-1 & 3 (PCB 76A) **£2.61**
PCB for KITS 76-2 & 4 (PCB 76B) **£2.64**

P.E. STRING ENSEMBLE (PE Mar-July 78)

The new keyboard string-instrument synthesiser.

Basic component sets:

Power Supply (KIT 77-1) **£8.77**
Tone Generator (KIT 77-2) **£14.66**
Diode Gates (KIT 77-3) **£18.81**
Chorus Generator (KIT 77-4) **£19.08**
Voicing System (KIT 77-5) **£7.38**

Printed Circuit Boards:

Double-sided PCB for Power Supply, Tone Generator & Diode Gates with most of the Matrix wiring as printed tracking (PCB 77U/R) **£18.40**
PCB for Chorus Generator (PCB 77C) **£2.65**
PCB for Voicing System (PCB 77D) **£2.62**

Fuller details of kits & PCBs are in our lists.

P.E. JOANNA PLUS ORGAN VOICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Tonk, ordinary piano, and Harpsichord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and vibrato.

Set of components (excl switches) for PSU, Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuits. (Order as KIT 71-5) **£99.25**
Set of PCBs (Order as PCB SET 71-6) **£29.18**

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches **£7.69**
Alternative component set with panel switches **£5.05**
Printed circuit board **£1.43**

ELEKTOR ELECTRONIC PIANO (Elektor Sept 78)

A touch-sensitive, multiple-voicing 5 octave piano using the latest integrated-circuit techniques for the keying and envelope shaping and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos. Details in our lists.

DIGITAL REVERBERATION UNIT (Elektor May 78)

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring-lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main component set (KIT 78-1) **£45.45**
Extension component set (KIT 78-2) **£43.36**
PCB for Kit 78-1 (PCB 78A) **£2.86**
PCB for Kit 78-2 (PCB 78B) **£1.06**

ANALOGUE REVERBERATION UNIT (Elektor Oct 78)

Using i.c.s instead of spring-lines, the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main component set (KIT 83-1) **£26.18**
Additional Delay Set (KIT 83-2) **£18.25**
PCB (as published) to hold both above kits (PCB 9973) **£4.31**

RESONANCE FILTER (Elektor Oct 78)

This filter module has been designed to allow a synthesiser to produce a more realistic simulation of natural musical instruments.

Basic component set (KIT 82-1) **£15.10**
PCB (as published) (PCB 9951) **£3.29**

SYNTHESISER EXTERNAL INPUT INTERFACE

(P.E. Oct 78)

This unit allows external inputs, such as guitars, microphones etc. to be processed by the circuits within a synthesiser.

Basic component set (incl PCB) (KIT 81-1) **£2.94**

GUITAR MULTIPROCESSOR (P.E. Dec/Feb 78)

An extremely versatile sound processing unit, capable of producing, for example, Flanging, Vibrato, Reverb, Fade and Tremolo as well as other fascinating sounds. May be used with most electronic instruments. Details in our lists.

RHYTHM GENERATOR KITS

Several available—details in our lists.

GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Component set and PCB **£4.52**

GUITAR SUSTAIN (P.E. Oct 77)

Maintains the natural attack whilst extending note duration. Component set, PCB and foot switches **£5.13**
Component set, PCB and panel switches **£3.71**

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds. Component set (incl. PCB) **£4.26**

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot **£7.58**
Component set using dual rotary pot **£6.89**
Printed circuit board **£1.62**

FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit. Component set (incl. PCB) **£2.05**

TREMOLO UNIT

Based upon P.E. "Sound Design" circuit. Component set (incl. PCB) **£2.94**

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable. Component set (incl. PCB) **£2.51**

WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektor". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw's) **£8.40**

VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers. Component set (incl. PCB) (Order as Kit 65-1) **£7.17**

RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers. Component set (incl. PCB) (Order as Kit 59-1) **£5.50**

NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers. Component set (incl. PCB) (Order as Kit 60-1) **£3.64**

ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier. Component set (incl. PCB) **£4.77**

ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions. Component set (incl. PCB) **£6.68**

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set **£4.87**
Printed circuit board **£1.82**

SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektor", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set **£17.38**
Printed circuit board **£2.33**

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music. Component set (incl. PCB) **£3.20**

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing. Component set (incl. PCB) **£4.74**

WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller. Component set (incl. PCB) **£3.63**

AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played. Component set, PCB, special foot switches **£7.67**
Component set and PCB, with panel switches **£4.83**

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows. Component set (incl. PCB) **£3.97**

10% DISCOUNT VOUCHER (PE 72)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly costed, C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E.

ADD: POST & HANDLING

U.K. orders - Keyboards add £2.00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1.00 for £100 cover, etc. pro-rata. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 12% VAT

(for current rate if changed). Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 20p, other countries send 50p.

PHONOSONICS · DEPT. PE72 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 20p; other countries—send 50p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes)	£25.50
4 Octave (49 notes)	£32.25
5 Octave (61 notes)	£39.75

Contact Assemblies (gold-clad wire) for use with the above KBOS (1 for each note):

Type GJ: Single-pole change-over	each 254p
Type GA: 1 pair of contacts, normally open	each 24p
Type GB: 2 pairs of contacts, each pair normally open	each 284p
Type GC: 3 pairs of contacts, each pair normally open	each 373p
Type GE: 4 pairs of contacts, each pair normally open	each 461p
Type GH: 5 pairs of contacts, each pair normally open	each 583p
Type 4PS: 3 pairs of contacts plus single-pole changeover	each 57p

Printed Circuit Boards for use with most contacts (thus eliminating much interwiring) are available. Details in our lists.

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

Main component set (incl. PCB)	£14.93
Power supply set (incl. PCB)	£6.28

SYNTHESIZER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesizers and other instruments, where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl sw.)	£7.45
----------------------------------	-------

CONSTANT DISPLAY FREQUENCY METER (PE AUG 78)

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

Component set	£24.05*
Printed circuit board	£3.03*

*This kit & PCB are at 8% VAT (all others are 12½%)

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

Standard tolerance set of components	£2.96
Superior tolerance set of components	£3.76
Regulated power supply (will drive 2 sets)	£4.69

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB)	£4.58
---------------------------	-------

DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic component set	£18.19
Printed circuit board	£3.45

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

Pre-Amp Module Components set (incl. PCB)	£3.95
Basic Output Circuits—combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feedback lampdriver circuits.	£6.59
Audio Amplifier Module Type PC7	£7.75

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

NEW PCB SERVICE

PCBS FOR ALL NEW P.E. & E.E. PROJECTS FOR WHICH PCB LAYOUTS HAVE BEEN PUBLISHED AND FOR WHICH FULL COPYRIGHT CLEARANCE IS AVAILABLE.

LIMITED QUANTITIES ONLY FOR AN EXPERIMENTAL PERIOD.

LET US KNOW YOUR NEEDS AND WE WILL ADVISE YOU OF AVAILABILITY AND PRICES.

INTEGRATED CIRCUITS

301 8-pin DIL	48p
318 8-pin DIL	220p
320-15 ---	195p
324 14-pin DIL	87p
341-15 ---	87p
709 8-pin DIL	49p
723 T05	87p
723 14-pin DIL	51p
726 T05	1005p
741 8-pin DIL	24p
748 8-pin DIL	57p
4007 14-pin DIL	171p
4011 14-pin DIL	171p
4024 14-pin DIL	461p
4069 14-pin DIL	18p
4136 14-pin DIL	126p
AM2833 8-pin DIL	360p
AY10212 16-pin DIL	17p
AY16721/6	188p
CA3046 14-pin DIL	71p
CA3080 8-pin DIL	63p
CA3084 14-pin DIL	209p
FX209	16-pin DIL
LM323	562p
M252	16-pin DIL
MC3340 8-pin DIL	150p
MCM6810 24-pin DIL	670p
SG3402N 14-pin DIL	262p
STK025 ---	695p
TDA1022 16-pin DIL	582p
XR2207 14-pin DIL	420p
ZN425E 16-pin DIL	375p

TRANSISTORS

AC128	32p
AC176	28p
BC107	13p
BC108	13p
BC109	15p
BC109C	16p
BC177	18p
BC184	11p
BC187	18p
BC204	10p
BC209C	13p
BC213	11p

PHONONICS

STEREO PRE-AMPLIFIER BOARD, Tone Control Board, Filter Board from 60 + 60

watt Hi-Fi Amplifier with suggested assembly and circuits @ £3.50.

PNP VERSION OF 2N 3055 BOX 94 @ 75p each.

100 MINIATURE DIODES CV 9637 with preformed leads @ 50p.

POLYSTYRENE CAPACITORS suffix type 12, 15, 20, 25, 30, 50, 56, 100, 120,

1000pf. All at 20p doz.

WIRE ENDED CRYSTALS 28KHz, 28.5KHz, 31.5KHz. All at 50p each.

TRANSISTORS BC 183, BC 548, BC 549, All 10p, 6 for 50p.

McMURDO 8 PIN PLUG @ 20p, 8 PIN SOCKET @ 20p. COVER @ 15p.

3 GANG VARIABLE CAPACITOR 25 + 25 + 25pf @ 75p.

10 Amp S.C.R.'s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.

400mW ZENERS unmarked Good 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v,

33v, 36 volt. All at 10 for 40p.

GLASS WIRE ENDED MERCURY SWITCHES @ 25p.

MC 3340 ATTENUATOR I.C. with data @ 50p.

X BAND GUNN DIODES with data @ £1.65 each.

MINIATURE ROTARY SWITCHES 3 Pole 3 way @ 40p, 2 Pole 4 way @ 20p, 1 Pole

10 way 2 Bank @ 40p.

10 WATT ZENERS 18v, 33v, 57v, 100 volt. All 30p each.

DIE CAST ALLOY BOXES 6" x 4" x 2" @ £1.15.

TUBULAR TANTALUM CAPACITORS 2.2uf 20v.w., 68uf 15v.w., 100uf 20v.w., 150uf

20v.w. All at 5p each.

10 MULTI-TURN TRIM-POTS Assorted for 60p.

50 BC 107-8-9 TRANSISTORS assorted untested @ 57p.

ELECTROLYTIC CAPACITORS 2240uf 40v.w. @ 40p, 3,300uf 63v.w. @ 50p.

4500uf 25v.w. @ 25p.

UNIJUNCTION TRANSISTORS 2N 4871 @ 22p, 22N 6028 @ 25p, 2N 6029

@ 25p, MEU 21 @ 22p, MU 4894 @ 22p, 4JDSE29 @ 22p, TIS 43 Type @ 22p.

30 ASSORTED 10XAJ CRYSTALS @ £1.10. 20 FT 243 CRYSTALS assorted

@ £1.50. 20 FT 241A CRYSTALS assorted @ £1.10.

MULLARD TAA 320 M.O.S.T. PRE-AMPLIFIERS I.C. with circuits @ 35p.

PLASTIC BC 107, BC 108, BC 177 TRANSISTORS 8p, 10 for 60p.

MULLARD STRIPLINE 800 MHz NPN BF 362 @ 25p.

200 ASSORTED ½ watt RESISTORS for 75p.

502 WATT ASSORTED ZENERS untested @ 57p.

6000 MHz 8 DIGIT FREQUENCY COUNTER @ £115.

MAINS TRANSFORMERS 240 volt Input. Type 1. 24 volt tapped at 14 volt 1 amp

@ £1.30 (P&P 25p). Type 2. 22-0-22 volt 500mA @ £1.60 (P&P 25p). Type 3.

45 volt 6 amp @ £4.50 (P&P 95p). Type 4. 20 volt 1 amp twice 10 volt 1 amp

twice @ £4.50 (P&P 95p). Type 5. 45 volt 2 amp 45 volt 500 mA @ £3.50

(P&P 85p). Type 6. 16 volt 2 amp @ £1.60 (P&P 25p). Type 7. 24 volt 1.75 amp

@ £1.60 (P&P 25p). Type 8. 30 volt 1 amp @ £1.60 (P&P 25p). Type 9. 13-0-13

volt 1 amp @ £1.60 (P&P 25p). Type 10. 22 volt 500 mA @ 88p (P&P 20p). Type 11.

12 volt 100 mA @ 88p (P&P 20p). Type 12. 22 volt 1 amp, 7.5 volt 500 mA, 6v

1 amp @ £1.60 (P&P 25p). Type 13. 16.5 volt 1 amp @ £1.60 (P&P 25p). Type 14. 12

volt 1 amp @ £1.60 (P&P 25p). Type 15. 32-0-32 volt 500 mA @ £1.60 (P&P 25p).

Please add 20p for post and packing, on U.K. orders under £2, unless stated otherwise. Overseas post at cost.

J. BIRKETT

RADIO COMPONENT SUPPLIES

25 The Strait, Lincoln LN2 1JF Tel. 20767



PHOENIX ELECTRONICS

(SOLENT) LTD

139/141 Havant Road,
Drayton, Portsmouth,
Hants. PO6 2AA

NOTE THE NEW ADDRESS

We have moved to larger premises to give you a wider range and a better service.

INTEGRATED CIRCUITS

DTL 930 series.

TTL 74 series.

Linear series.

Consumer circuits.

CMOS circuits.

CAPACITORS

Disc ceramic. Aluminium electrolytic. Tantalum bead.

PANEL HARDWARE

Connectors, lampholders, switches, fuses, knobs.

MISCELLANEOUS

Hand tools, instrument cases, Veroboard, relays, transformers.

RESISTORS

½W carbon film

½W metal film

SEMICONDUCTORS

SOLDERING EQUIPMENT

Buy More for Less Outlay with Our Bargain Packs

Please send your new catalogue—free!

Name


Address

.....

I.C.E. MULTIMETERS

TWICE the information
in **HALF** the size

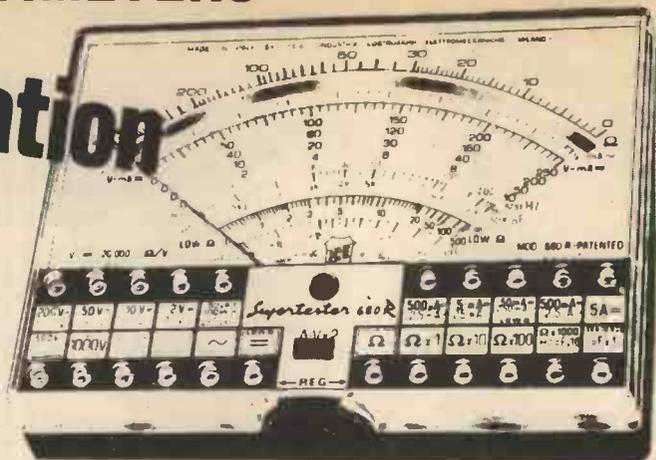The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



Supertester 680R (illustrated)

- * 20k Ω /V, $\pm 1\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 80 Ranges - 10 Functions
- * 140 x 105 x 55mm

£32.00 + VAT

(For Mail Order add 80p P&P)

Supertester 680G

- * 20k Ω /V, $\pm 2\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 48 Ranges - 10 Functions
- * 109 x 113 x 37mm

£24.50 + VAT

(For Mail Order add 80p P&P)

Microtest 80

- * 20k Ω /V, $\pm 2\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 40 Ranges - 8 Functions
- * Complete with case - only 93 x 95 x 23mm

£16.60 + VAT

(For Mail Order add 80p P&P)

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.



Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781



Model 8100 Frequency counter
Kit £ 69.95
assembled tested: £ 84.95
(plus p.p. £ 3.50 and VAT at 8%)

sabtronics

Model 2000 3 1/2 Digit DMM
Kit £ 49.95
assembled: £ 69.95
(plus p.p. £ 3.00 and VAT at 8%)

The Winners

These two products are our best sellers!

The two products shown above from Sabtronics are our best selling products. Both these products compare with similar equipment selling for at least £ 150.00. Is there more to these products than value? Let's take a closer look.

The Frequency Counter Model 8100

It employs LSI Technology, has the performance and characteristics you demand, guaranteed frequency range of 20 Hz to 100 MHz; selectable hi/lo impedance; superior sensitivity; selectable resolution and selectable attenuation. Plus an accurate time base with excellent stability. An 8 digit LED Display features floating decimal point, leading zero suppression and overflow indicator.

Brief specifications:

Frequency Range: 20 Hz to 100 MHz guaranteed, (10 Hz to 130 MHz typical) - Sensitivity: 10 mV RMS,

20 Hz to 50 MHz (5 mV typical); 15 mV RMS, 50 MHz to 100 MHz (10 mV typical) - Selectable Impedance: 1 M Ω /25 pF or 50 Ω - Attenuation: X1, X10 or X100 - Accuracy: ± 1 Hz plus time base accuracy - Aging Rate: ± 5 ppm/yr - Temperature Stability: ± 10 ppm, 0° to 50° C - Resolution: 0.1 Hz, 1 Hz, 10 Hz selectable - Display: 8-digit LED, floating DP, overflow indicator - Overload Protection - Power Requirement: 9-15 VDC. Optional prescaler will be available from around March 1979.

The DMM Model 2000

The model 2000 is all solid-state, incorporating a single LSI circuit and high quality components. It has five functions and a total of 28 ranges. Input overload protection, auto polarity and auto zero are provided on all ranges and a basic DCV accuracy of 0.1% ± 1 digit.

Brief specifications:

DC volts in 5 ranges: 100 μ V to 1 kV - AC volts in 5 ranges: 100 μ V to 1 kV - DC current in 6 ranges: 100 nA to 2A - AC current in 6 ranges: 100 nA to 2A - Resistance: 0.1 Ω to 20 M Ω in 6 ranges - AC frequency response: 40 Hz to 50 kHz - Display: 0.36" (9.1 mm) 7-segment LED - Input impedance: 10 M Ω - Size: 8" W x 6.5" D x 3" H (203 x 165 x 76 mm) - Power requirement: 4 "C" cells (not included).



Order yours now! Write to:

Timwood Ltd.
Prospect Road, Cowes,
Isle of Wight, England Telex 86892.
Send payment with your order.

PROSPECTS

AT THE time of writing we are at the start of a new year—a year which is an exciting prospect for the whole of the electronics industry. Every man in the street has now heard of the “chip” and we have all seen or at least read about the many products now available because of it. The next year should see hundreds more products and the microprocessor boom take off in a big way in the U.K.

Digital watches and calculators are now cheap, efficient and available in vast varieties to suit every requirement. Video recorders—promised for so long—are now a reality, as is the videodisc in the States, but may not be here until 1980. Perhaps we will see the introduction of electronics to our everyday transport during 1979. Solid state instruments are at present undergoing evaluation tests and it will not be too long before the microprocessor helps present every driver with better information and perhaps provide in-car entertainment for the kids.

TV

The P.O. Prestel system will become widely available and we should start to see cheaper Oracle, Ceefax and Prestel

equipped sets, though we doubt if many homes will be in touch with these systems by the end of '79. By then we may know for sure what and when our fourth TV channel will be—though having been subjected to North American TV we see no argument for continuing to add to the number of channels. TV games continue to become more sophisticated but with tape programmed computerised versions already around we doubt if '79 will see any further significant steps.

CB

We may also see some moves by the Government on citizens band radio, even if they are only attempts to stamp out the numerous illegal networks operating in our large cities at the present time. Maybe this illegal use will force the powers that be to assign a frequency for CB. We would not however expect this to provide a great advantage to the man in the street as it is highly probable that the allotted frequency will not be in the 27MHz band, but much higher and that the technical spec. for each set will be high and closely controlled, making equipment expensive.

This would however overcome the

interference problems of 27MHz and would probably provide a much more usable network for those that could justify the expense. If CB does come to Britain we hope the communications companies will be quick off the mark with British designed—if not made—equipment!

REVOLUTION

Of course all this new technology will require new test equipment and this, together with “the next industrial revolution”, of which many are talking, will probably be a far greater growth area than all those mentioned previously.

One “new product” which is now being used in the home and small business has not been mentioned above—the microcomputer. The Tandy catalogue, given free with our UK mainland issues this month, features their TRS 80 computer—probably the best selling micro in the world—and next month we hope to bring you a review of a Level II machine.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland TECH. SUB EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

Editorial Offices:

Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

ADVERTISEMENT MANAGER

SECRETARY

REPRESENTATIVE

CLASSIFIED MANAGER

D. W. B. Tilleard

Christine Pocknell

Peter Mew 01-261 6819

Colin Brown 01-261 5762

01-261 6676

Advertising Offices:

King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where ap-

propriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perry Mount Road, Haywards Heath, West Sussex RH16 3DH.

Cheques and postal orders should be made payable to IPC Magazines Limited.



LOGISCOPE

R.A.PENFOLD

WHILE a dual or multi-trace oscilloscope is in many ways ideal for checking logic circuits, the high cost of such an instrument is the main reason for the large number of logic tester designs that appear in electronic magazines.

Most logic testers are designed to show whether a test point is a logic 0, logic 1, floating, or pulsing. Such units can be extremely useful, but the fact that they merely indicate the presence of a pulsed input and do not usually provide any information about mark space ratio or frequency can be a drawback.

A few logic tester designs attempt to overcome this problem to some degree, and the unit described in this article can be used to give some idea of the mark space ratio and frequency of the input signal in most cases.

DISPLAY

This unit relies upon the fact that for the majority of logic testing the high definition of a cathode ray tube is considerably in excess of the minimum requirement, and a much simpler form of display can therefore be used. The reason for this is that in logic circuits the waveforms are produced by rapid switching between the two logic levels. This tends to produce oscilloscope traces of the type illustrated in Fig. 1a. There are really only two levels on the Y axis, which corres-

pond to logic 0 and logic 1. Obviously there are parts of the trace at intermediate levels, but as the switching action takes place extremely rapidly the intermediate parts of the trace are extremely faint, and may well not be visible at all.

A simple waveform of this type could be displayed on two rows of l.e.d.s as shown in Fig. 1b, and with further simplification a single row of l.e.d.s could be used in the manner illustrated in Fig. 1c. In the case of the latter, a l.e.d. is either switched on to indicate a logic 1 level, or switched off to indicate a logic 0 level.

Ideally a l.e.d. display of this type would have a large number of very small l.e.d.s in order to achieve the most accurate and meaningful results. However, in practice this would be difficult to achieve, and the unit described here uses a row of ten ordinary 3mm diameter l.e.d.s. This seems to provide acceptable results in most cases, and enables a circuit to be used which is no more complicated than many conventional logic testers.

BLOCK DIAGRAM

Although in operation this device is analogous to an ordinary oscilloscope, it employs digital rather than analogue techniques, and is of course very much simpler than an oscilloscope. Fig. 2 shows in block diagram form the general arrangement of the unit.

The timebase section of the circuit consists of a clock oscillator feeding a one of ten decoder, the ten outputs of this device being used to drive the display of ten l.e.d.s. As the name implies, one output of the one of ten decoder will be in the logic 1 state and the others will be at the logic 0

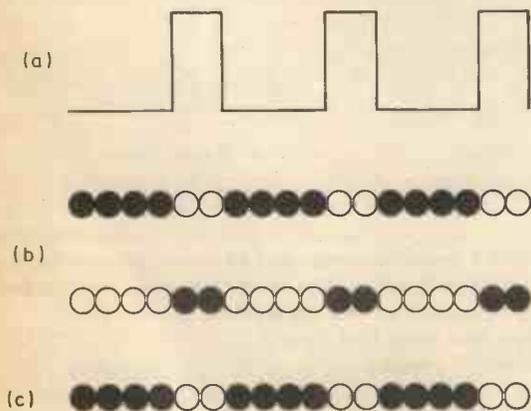


Fig. 1a. Typical logic circuit waveform.

Fig. 1b and 1c. The same waveform displayed first using two rows of l.e.d.s then one

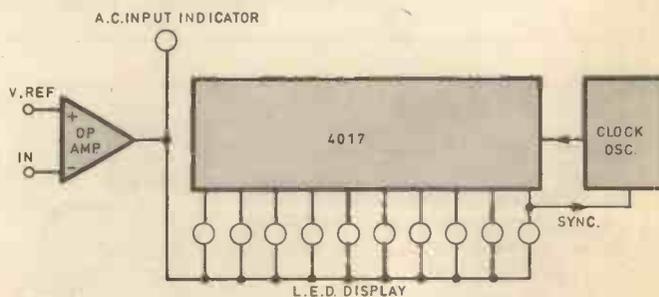


Fig. 2. Block diagram of the Logiscope

COMPONENTS . . .

Resistors

R1	1k
R2	47k
R3	2M7
R4	68k
R5	8k2
R6	10M
R7	1k8
R8	4k7
R9	15k

All resistors $\frac{1}{4}$ W 5% carbon.

Potentiometers

VR1	47k Lin. carbon
-----	-----------------

Capacitors

C1	100 μ 10V elect.
C2	100n type C280
C3	100n type C280
C4	220n 5% or better
C5	22n 5% or better
C6	2n2 5% or better
C7	220p 5% or better

Semiconductors

D1	TIL211 (green) or similar with panel holder
D2	1N4148
D3 to D12	TIL209 or similar with panel holders (10 off)
IC1	CA3130T
IC2	4017
IC3	NE555 or equivalent
TR1	BC109

Switches

S1	4 way 3 pole rotary type (only 1 pole used)
S2	S.p.s.t. toggle type

Miscellaneous

Verocase type 91-2672A or similar (about 134 x 123 x 44mm).
3.5mm jack socket (SK1), 3.5mm jack plug, test lead and prods
Two control knobs
PP3 battery and connector to suit
0.1in. matrix stripboard
Sockets for i.c.s, wire, solder, etc.

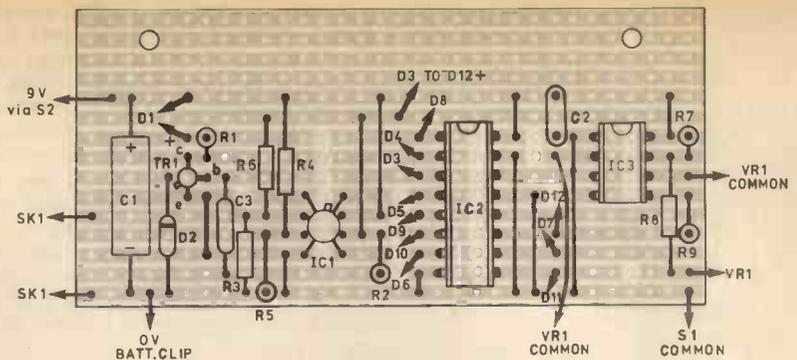


Fig. 4. Veroboard layout of the Logoscope

The input is coupled to the unit via an ordinary test lead and a 3.5mm jack mounted on the front panel, but the unit could easily be constructed in conventional logic probe form if preferred.

Except for the controls and l.e.d.s, most of the components are mounted on a 0.1in. matrix stripboard which has 32 holes by 15 copper strips. C4 to C7 are not mounted on this panel, but are soldered direct to the tags of S1. All the wiring of the unit is shown in Fig. 4.

USING THE UNIT

The maximum input frequency for which the unit can display the mark space ratio depends upon what the mark space ratio actually is. It is over 200kHz for a 1 to 1 mark space ratio, but decreases with higher ratios. As a pulse detector it will operate at higher frequencies and will detect pulses of less than 1 microsecond in duration.

When the mark space ratio is fairly long it may be found that the display will indicate a mark space ratio of, say, 10 to 1 and 5 to 1, and perhaps lower ratios as well. The correct result is always the highest ratio. The lower ratios are produced by higher timebase speeds and are the result of the pulse occurring on every second, third, or fourth sweep. This makes the pulse seem two, three or four times its actual length, but this is quite easy to detect since it results in the display being noticeably dimmer than normal.

The display is not exceptionally bright because even though the l.e.d.s are pulsed with a reasonably high current, they can only be on for a maximum of 10 per cent of the time. However, the display brightness has been found to be perfectly adequate under normal lighting conditions. ★

The timebase frequency can be altered slightly by applying a control voltage to pin 5 of IC3, and this enables a simple synchronisation circuit to be used. This merely consists of coupling one output of the display driver to pin 5 of IC3 via R9. The output voltages of IC2 are dependent to a large extent on the output state of IC1, and not just the logic state each particular output happens to be in, because none of the outputs have anything like zero output impedance. This seems to provide better sync. than is obtained by taking the signal from the output of IC1.

S2 is just an ordinary on/off control. Power is obtained from a 9V battery (PP3, etc.) and the current consumption varies between about 12 and 35mA, depending upon the timebase frequency and the state of the display.

CONSTRUCTION

The prototype is housed in a Verocase and the general arrangement of the unit can be seen from the photograph.

POINTS ARISING

NOUGHTS AND CROSSES GAME (January 1979)

In Fig.3 IC2, 3, 4 and 5 should have pins 2 and 4 linked. IC2, 3 and 4 should have pin 5 linked to the .4k7 resistor and in Fig. 8 the emitters of TR20 and TR21 should be linked.

ADSR ENVELOPE SHAPER (January 1979)

The Veroboard track layout was incorrectly reversed left-to-right in this article. Constructors can obtain a correct copy of the layout diagram from the editorial office at Poole.



FRANK W. HYDE

THE DEATH OF SKYLAB

The decision by the United States to jettison Skylab is on the face of things a great disappointment. However, there does seem to be a rather emotional reaction in some quarters as to the possible damage to life. Only one publicised case is on record of possible danger from an uncontrolled satellite, which in the event proved to be a safe fall on land.

The size and weight of skylab seems to be the main cause of concern. The precision that can be applied to the tracking of the dying vehicle seems to be overlooked. Perhaps it is because of the rarity of space disaster that the media tends to become a little on the "doom" and "destruction" side of reporting.

It is perhaps worth while to consider the matter a little more closely for it is a responsibility of those engaged in these matters to be honest and factual particularly when informing the public of the exact situation. There is so much tendency with the "doom" mongers to deal in conjecture and dire consequences without the least degree of reasonable accuracy.

The condition of Skylab and its relative position has been closely observed, and with the facilities available it is possible to state almost a minute to minute re-disposition. There are certain important points that should be remembered.

The first is that the vehicle does not have protective heat shielding. Some parts of it, the panels, the telescope mounting and various external attachments will almost certainly vaporise very early in the final fall. That it will be a spectacular sight there is no doubt and even this will yield data of some significance. It is a pity that some sources have already made exact statements as to the magnitude of casualties. Though it is possible during a continuing observation to determine very accurately the likely course of events, the last moments may pose difficulties. Nevertheless it

will be possible to form a workable programme of action during the event. Unless large pieces are scattered in the atmosphere as a result of explosion, possible damage may well be considerably less than may be feared.

If the fall is over an ocean area then the chances of material damage becomes more and more remote. Having said that there remains one important possibility and that is the deliberate destructive action by explosive controlled (killer) satellite. If it is found that a real danger could exist, what better justification for its agreed destruction by those with the means, is needed for the common cause of mankind.

TIROS-N SATELLITE

On the 13th of October 1978 the third generation polar-orbiting TIROS-N was launched. It has already justified its planning and is giving a better insight into the workings of the stratosphere, as well as improving the meteorological forecasts. The instrument which is supplied by the Meteorological Office was the stratospheric sounding unit (SSU). It is an infrared radiometer and provides world wide data relating to the temperatures existing between the heights of 25km and 50km above the Earth. Such temperature soundings enable weather forecasting models to be made and also provide facilities for the monitoring of pollution conditions in the atmosphere.

The SSU is an interesting and efficient instrument based on techniques already demonstrated by the Oxford University Department of Atmospheric Physics which flew aboard the Nimbus-6 satellite.

The original system was developed by the Oxford group and based also on work done by Professor Smith's group at Heriot-Watt University and Professor Houghton's team at Oxford. The three channel sounder measures outgoing radiation from the atmosphere 15µm band of carbon dioxide. The radiation enters the SSU through a set of absorption cells containing CO₂ the pressure of which is varied at about 40Hz using a piston vibrating in a cylinder. The strength and the width of the absorption lines vary with pressure, thereby modulating the radiation which is emitted by the carbon dioxide.

The modulated component is received by the detectors (pyroelectric triglycine sulphate) designed and built by the Allen Clerk Research Centre. The SSU has a 10° field of view. This can be varied in 10° steps at right angles to the satellites' line of flight. Each step is viewed for four seconds which means that an area of about 150km is then covered by the 10° field of view. The distance between the adjacent scan lines is about 210km. The instrument calibrates itself at regular intervals of 256 seconds. Two reference bodies are used in the calibration mode, an internal black body and the background of space.

Marconi Space and Defence Systems is building altogether eight of the SSU's and the remaining seven will be flown aboard a series of NOAA satellites to follow the TIROS-N. Two spacecraft will be in orbit at any one time. The remaining craft will be held in store until required. Data will thus be available at least to 1985. Initially the data will be used in research into the dynamics of the stratosphere

and the way in which it interacts with the troposphere. Man-made effects and natural effects will be studied in the variations of the ozone and carbon dioxide content.

Global maps will be available to other countries who ask for them. It will be possible to supply data on stratospheric behaviour within hours.

THE VELA PULSAR

A new technique to detect pulsars has been developed by a team of British and Australian astronomers at Sliding Spring Mountain in New South Wales. The pulsar which was first discovered as a radio pulsar flashing at 16 times a second in 1968 is now found also to be an optical pulsar. This neutron star is at a distance of 1,600 light years.

This new development was made possible by the installation of the 3.9m telescope. The pulsar is estimated to be about 10,000 years old. It is the second fastest pulsar known. It never completely turns off but settles to a steady state. It has a pattern of double flashes every 89ms. By using a time interval succession of pictures of 33ms interval the flashes can be caught in the on and off state.

The previous telescopes were not of sufficient light gathering power to detect the pulsar. The operation of this pulsar is similar to a lighthouse, there being one main pulse followed by the secondary pulse.

HOLOGRAPHY IN ASTRONOMY

New techniques of mathematical analysis have been developed by Dr Gerd Weigelt of the University of Erlangen-Nurnberg in Germany. They enable speckle interferograms of stellar objects to be made. The speckle interferogram is a very short exposure of a stellar object, which freezes the star image dancing because of the turbulence of the atmosphere. Already 240 speckle interferograms have been made. The telescope used is 1.8m in diameter.

VENUS

The unexpected result of the Venus multi-probe experiment was an indication of large quantities of Argon-36. By comparison with the Earth this is so high as to give cause for a very special look at the present theories of the origins of Venus. That the planets Venus and Earth evolved at about the same point in time seems to be in doubt with some planetologists.

Till now it has been thought that the primordial argon was blown away at a very early date in the lifetime of the two planets. The discrepancy that exists between Mars and the Earth was explained by saying that as Mars was a smaller planet less gas was released. Whether these sudden changes in the situation are thought to exist is to some extent in doubt because the results of the mass spectrometer differ by a factor of 10 from the results of the gas chromatograph on the probes. This alone should warn against hasty judgements. It may well be that still another mission will be required before any radical ideas can be allowed to prevail.

IN recent months the use of digital sequencers with music synthesisers has become very popular with contemporary music and completely new sound patterns have been created with these devices.

A sequencer enables the user of a synthesiser to program in voltage patterns that in turn produce a musical melody which can be further manipulated in terms of speed, rapid key changes, etc. all of which would be very difficult, if not impossible, for the human operator to do with such speed and precision. For example, a drum sequence can be programmed into the sequencer and replayed while the musician plays the synthesiser or other instrument.



16 NOTE SEQUENCER

PART ONE... LYNDSAY ROBINSON

SEQUENTIAL CONTROL

The sequencer to be described in this article enables up to sixteen different bits to be programmed and repeated at any speed required. The sixteen bits to be programmed and repeated at any speed required. The sixteen bits can refer to pitches, as is most common, or the timbre, loudness or length of the musical note. The notes are programmed into the sequencer by the use of potentiometers, one for each note. This is the method of sequential control most commonly adopted by all the main synthesiser/sequencer manufacturers, Moog, ARP and Roland for example.

While it may appear a rather simple and crude method of achieving a sixteen note memory compared with all the digital memories available, it is the cheapest and most reliable method as the tuning potentiometers used will remember indefinitely the selected voltage level.

Bearing in mind that the previously mentioned commercial sequencers cost several hundred pounds, the sequencer to be described has features as found on these designs and will cost around £35 in components and hardware.

The method used to generate the sequential function is simply an oscillator driving a digital counter with the output voltages going through a potential divider to obtain the processed voltage. This voltage then controls the frequency of a voltage controlled oscillator, or the cut-off frequency of a voltage controlled filter or the attenuation of a voltage controlled amplifier in the synthesiser.

A prototype sequencer has been used very successfully with a Mini-Moog synthesiser and the advanced features available on commercial versions are possible at a much reduced cost.

The basic layout of the sequencer is as shown in the block diagram (Fig. 1) and each block will now be considered in detail, referring to the appropriate circuit diagram.

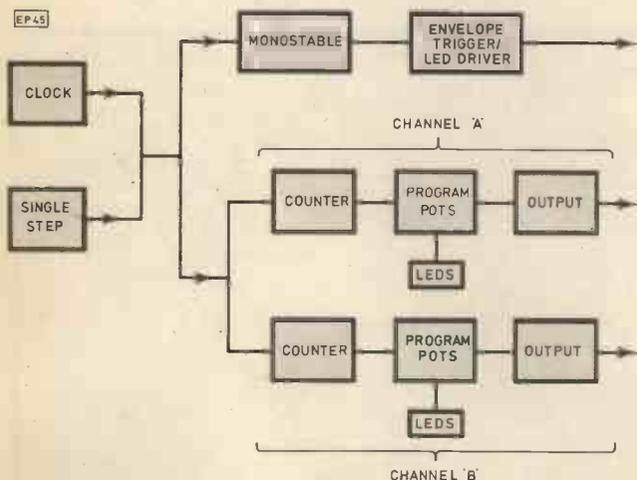


Fig. 1. Block diagram

CLOCK GENERATOR

IC1 is the control voltage adder for the voltage controlled clock (Fig. 2). R4, D1 and D2 protect the CMOS device from voltages more negative than 0V.

By applying a voltage to the gate of the *n*-channel MOSFET the resistance between the source and the drain will decrease with an increasing gate potential. This resistance is used as the timing resistor in the oscillator consisting of the two NOR gates in IC2.

The frequency of oscillation can be varied from about 0.2Hz to 100Hz by adjustment of VR2. The two preset resistors are adjusted so that VR2 will produce this variation.

The clock can be gated on or off by S1 or by a control

SPECIFICATION . . .

Sequence Channels

- (a)
 - (i) one channel of up to a maximum of sixteen programmable voltage levels
 - (ii) two channels of up to a maximum of eight programmable voltage levels
 - (iii) a 64 note sequence can be programmed (eight groups of eight notes)
- (b) two, eight-way switches select the number of notes in each sequence channel
- (c) the two counters (sequence channels) can be advanced by:
 - (i) integral clock oscillator
 - (ii) push button
 - (iii) external input pulses
- (d) reset push button
- (e) pulse output available from jack sockets at end of sequence
- (f) channel one, position one pulse output
- (g) single or repeating sequences possible

Clock

- (a) frequency range of approximately 0.2Hz–100Hz
- (b) voltage controllable frequency
- (c) clock can be switched off/on by manual switch or be gated off/on via jack socket
- (c) output from clock is directed to:
 - (i) counters
 - (ii) output trigger circuit

Envelope Shaper Trigger

- (a) variable pulse width to trigger either AD or ADSR envelope shapers, pulse time approximately 50mS–4S
- (b) positive trigger level 0–9V
- (c) L.e.d. shows on period of monostable

Sequential Analogue Outputs

- (a) voltage levels programmed by 16 potentiometers, typically 0–6V output (12V max)
- (b) master output controls for each channel
- (c) low output impedance
- (d) variable portamento (slew) on channel one output and 16 bit sequence

Lamp Indicators

- (a) L.e.d. for each note of each channel to show progress of sequence (total 16)
- (b) L.e.d. showing on period of envelope trigger

Power Supply

- ±12V for sequencer; can also be used to power additional synthesiser functions

voltage applied at JK1. The squarewave output is then inverted by part of a 4007 so that when the clock is gated off, the output is low. The remainder of the NOR gate is used to construct a latch for bounce-free operation of S2 which is a single step control and will advance the sequencer counters by one position each time.

MONOSTABLE TRIGGER

A monostable is seen after the inverter. A pulse of constant period is produced by C3 and R14 and this is used to switch an *n*-channel MOSFET which in turn is used to discharge the capacitor C2. Pins 5/6 of the AND gate will normally be at logic "1" and after a time period set by R10/VR4 and C2 the potential will fall to 0V.

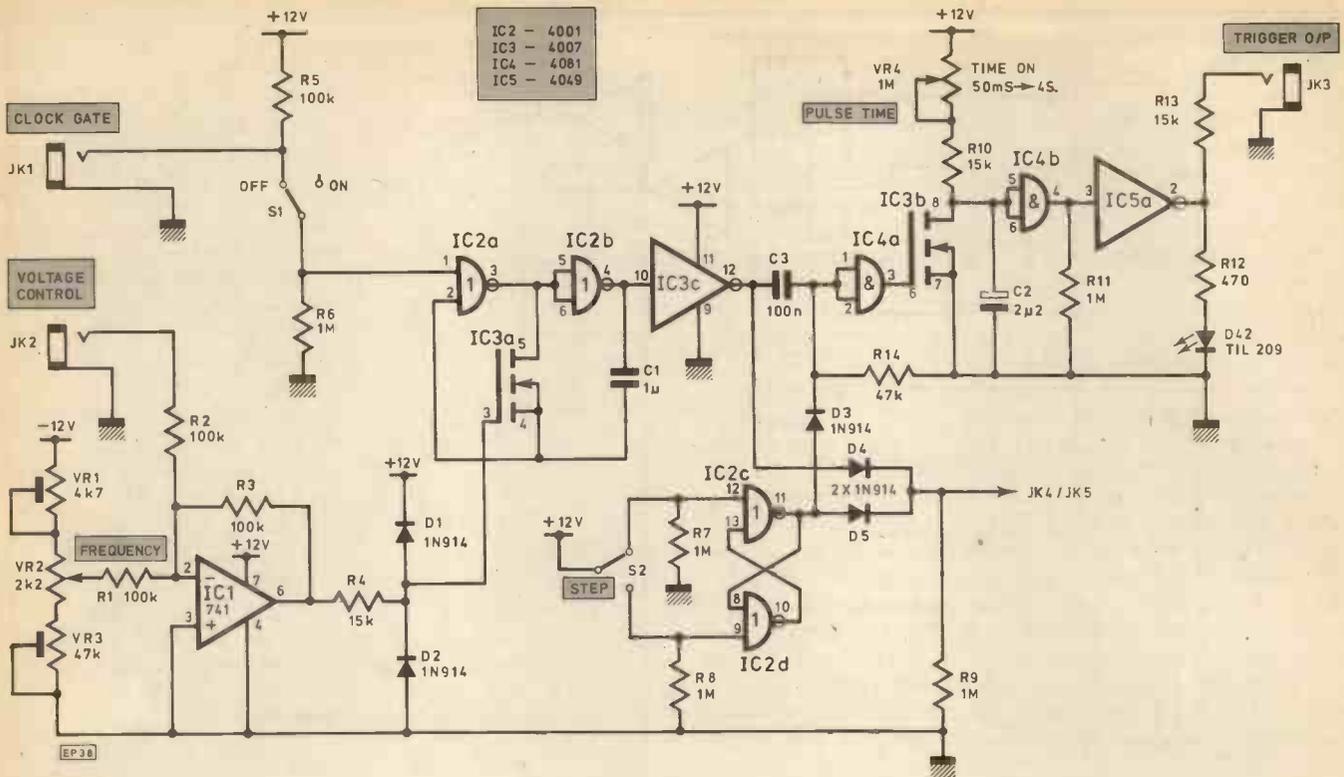


Fig. 2. Sequencer front end

COMPONENTS . . .

Resistors

R1-R3	100k
R4	15k
R5	100k
R6-R9	1M
R10	15k
R11	1M
R12	470
R13	15k
R14	47k
R15-R17	10k
R18-R33	680
R34-R40	100k
R41-R44	470k
R45	240k
R46	1k

All $\frac{1}{4}$ W carbon-film

Capacitors

C1	1 μ non polarised
C2	2 μ 2 16V elect.
C3	100n
C4-C7	1n
C8	2 μ 2 16V elect.
C9-C10	1,000 μ 25V elect.
C11-C12	1 μ 16V tantalum

Bridge Rectifiers

REC1-REC2	1A 50V (2 off) (W005)
-----------	--------------------------

Integrated Circuits

IC1	741
IC2	4001A
IC3	4007
IC4	4081B
IC5	4049B
IC6-IC7	4017A
IC8-IC9	4049B
IC10	4001
IC11	4016
IC12-IC14	741
IC15-IC16	LM341P-12

(12V 500mA positive regulators)

Potentiometers

VR1	4k7 preset
VR2	2k2 linear
VR3	47k preset
VR4	1M linear
VR5-VR20	100k linear
VR21	1M linear
VR22	1k linear
VR23	1k linear

Diodes

D1-D25	1N914
*D26-D42	Large red l.e.d.s plus clips

Switches

S1	s.p.s.t.
S2	s.p.d.t. spring biased
S3	Push to make
S4-S5	Single pole, eight-way rotary with end stop
S6	d.p.d.t.
S7	d.p. mains switch

Transformer

T1	0-12V 0-12V 6VA (Maplin)
----	-----------------------------

Miscellaneous

JK1-JK3	3-5mm jack sockets
JK4-JK7	3-5mm jack sockets with closed contacts
JK8-JK10	3-5mm jack socket
	14 pin i.c. sockets (5 off)
	Thin eight-way ribbon cable
	Graduated knobs (16 off)
	Plain knobs (7 off)
	Letraset, p.c.b., FS1 100mA 20mm fuse.
LP1	neon indicator

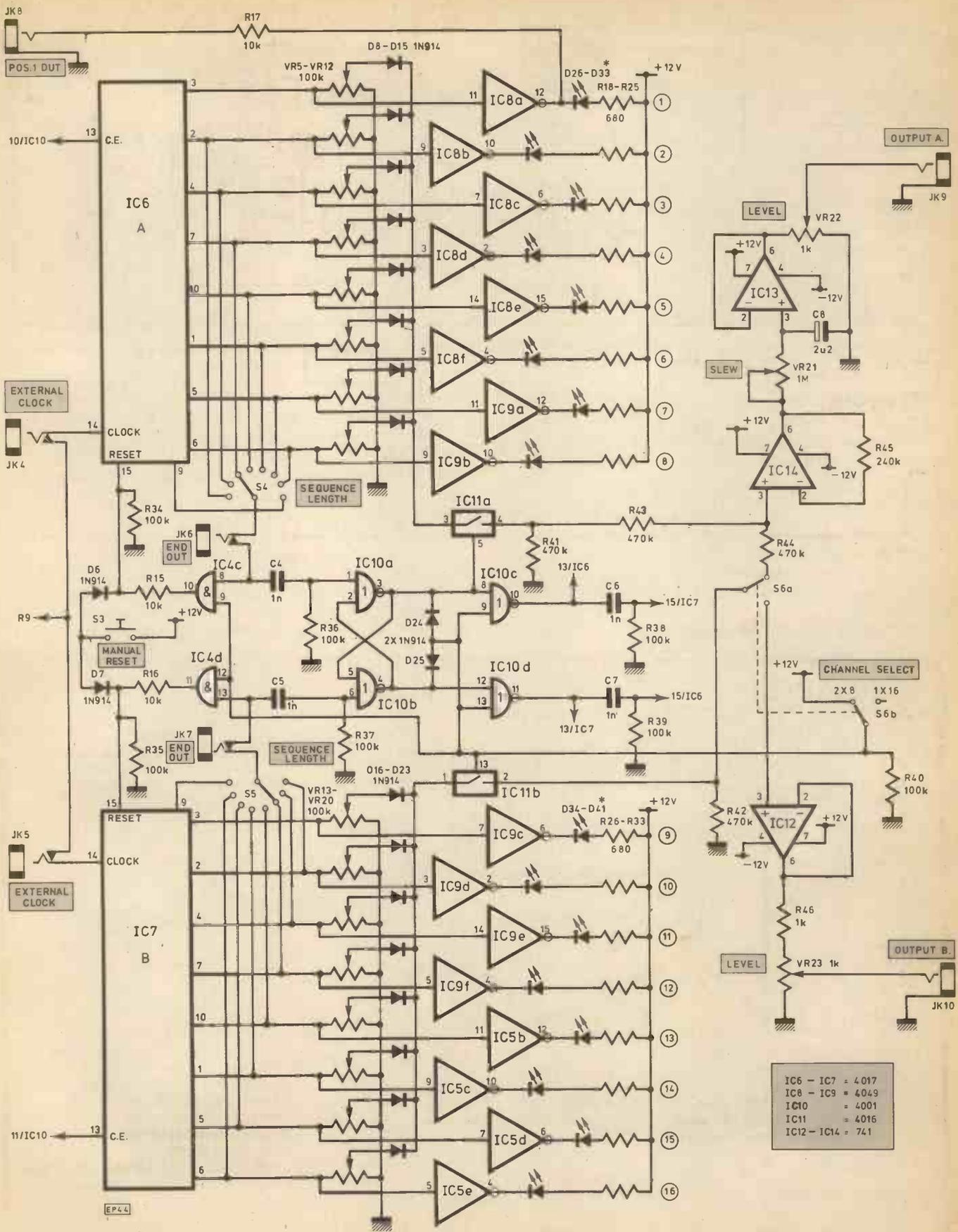


Fig. 3. Counters, channel switching and output stages

IC6 - IC7	= 4017
IC8 - IC9	= 4049
IC10	= 4001
IC11	= 4016
IC12 - IC14	= 741

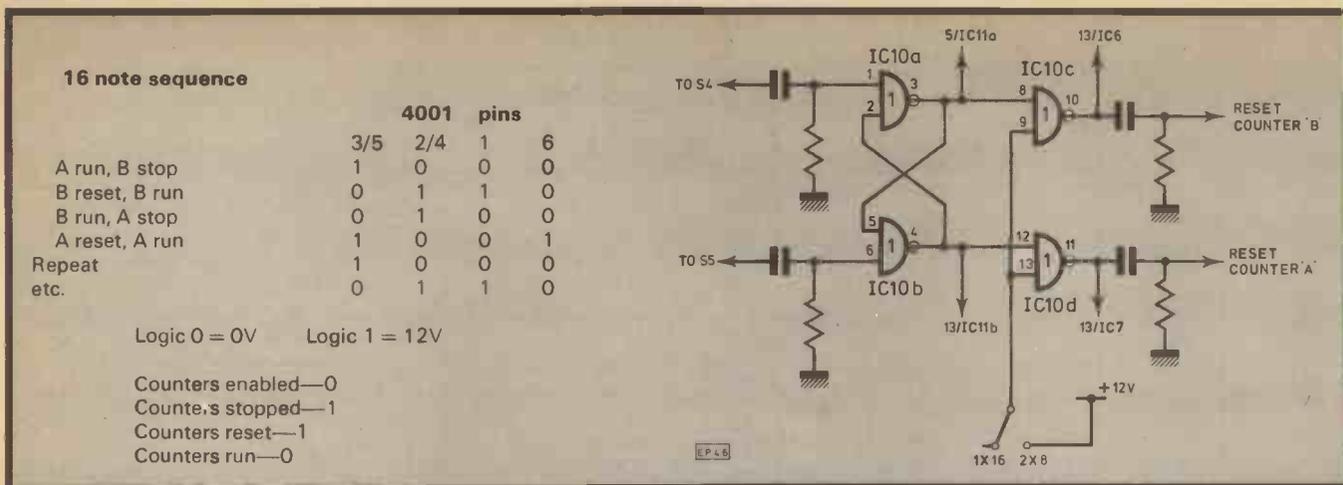


Fig. 4. Showing logic for 16 note sequence. For 2 x 8 sequence the latch is bypassed (IC10a/b). Each counter resets via IC4c/d

TAPPED VOLTAGES

Each sequential output (only eight are used per channel in this sequencer) is terminated by a 100 kilohm potentiometer which is used to tap off a precise voltage to control a VCO in the synthesiser. The outputs from the counter are also used to control the 4049 hex inverter buffers which are used to drive the l.e.d.s. For this purpose the new CMOS series of "B" devices is used. The RCA 4049B can sink up to 42mA at 12V per package and this is adequate for the sixteen l.e.d.s, one for each note, since there is a maximum of only three l.e.d.s being driven at once (including the envelope trigger l.e.d.).

This voltage is inverted by an inverter in IC5 and a positive pulse will be formed each time the MOSFET is turned on.

The pulse, of period from 50mS to 4S, is used to trigger the envelope shaper in the synthesiser, and for an AD type this trigger will correspond to the sustain time, and for an ADSR type of envelope shaper, this represents the time the keyboard note is depressed. An l.e.d. lights to show the "on" time.

CHANNEL COUNTERS

The output from either the clock, the "single step" or external pulses via JK4-5 is used to advance the CMOS counters (Fig. 3).

The 4017 is a decade counter which will decode a series of clock pulses into a sequential output. A "counter enable" terminal, pin 13, is used to inhibit the counter by application of logic "1". A "reset" terminal, pin 15 will cause the counter to be reset when "1" is applied.


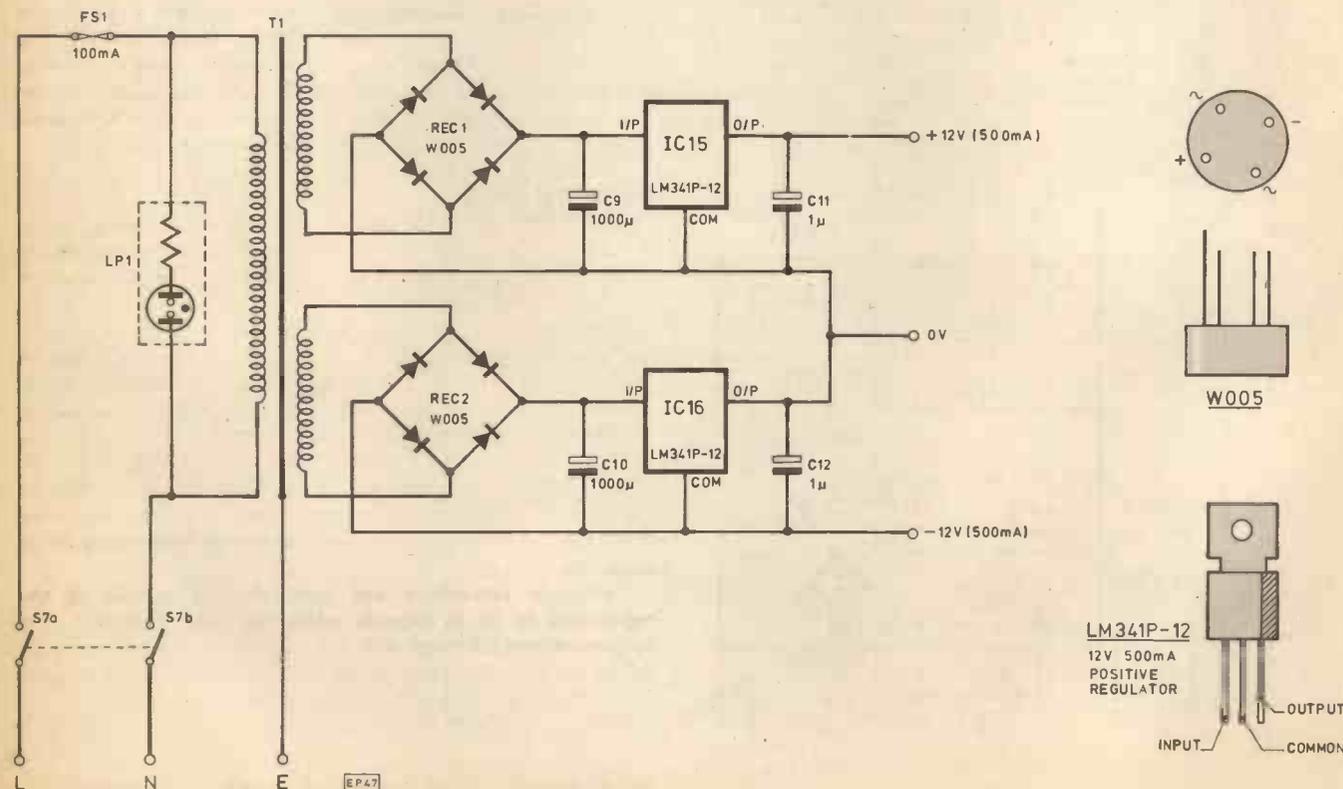


Fig. 5. Sequencer power unit

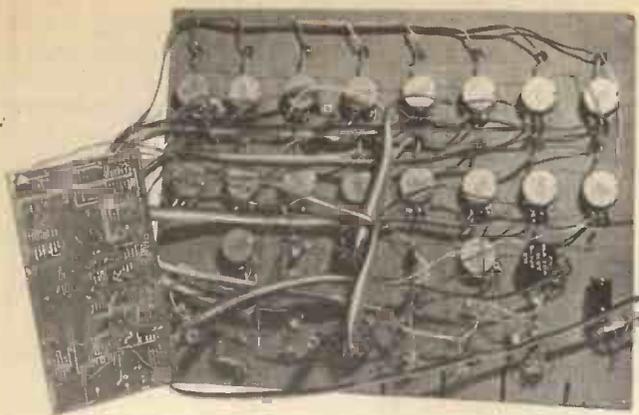

Sequencer interior


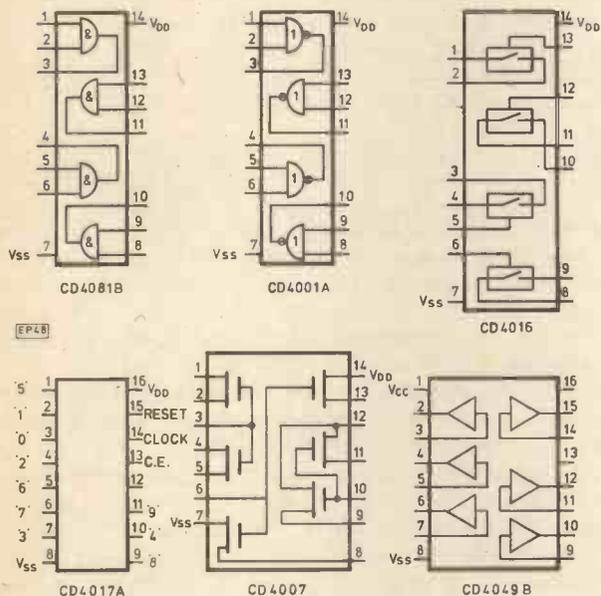


Fig. 6. I.c. pin-out details

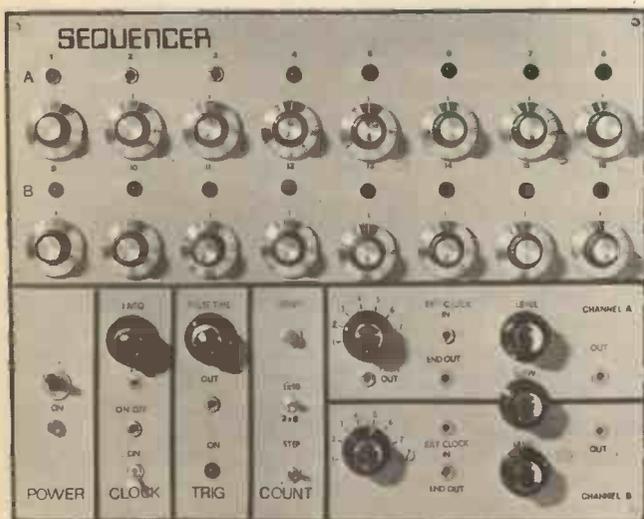

Control panel

The channel outputs from each of the programming potentiometers, passes through IC11, which is an analogue switch, and depending on the channel switching as controlled by IC10, the signal passes through to the 741 op-amp voltage adder.

Previously, each of the pot outputs is taken to the analogue switch via isolation diodes to prevent a programmed pot that is low, from lowering the potential of all the others.

Normally counter A only uses IC14 when the sequencer is in the parallel channel mode (2 x 8 channels operating simultaneously). But channel B is switched in for a 16 note sequence and the analogue switch and IC10 are used for this function.

IC13 is used to add a variable portamento to the sequence in the 16 note position and channel A only when the sequencer is used in the parallel channel position.

The voltage outputs from the channels are reduced to 6V maximum for convenience when used with a synthesiser, but by adjustment of R45 and R46 this can be altered.

CHANNEL SWITCHING LOGIC

The channel selection logic is shown in greater detail in Fig. 4. Such complexity is necessary for easy switching between series and parallel counter function, and also to ensure that the full number of counts is produced by each channel as originally selected by the "Sequence Length" rotary switch. It is also necessary that when a counter is at that instant not in use the l.e.d.s for that channel have stopped.

In the parallel mode, the sequential counters are reset via the AND gate and function completely independently, e.g. one channel can be used to produce a four note sequence, and the other an eight note sequence. None of the gates of IC10 are used and this is bypassed by the NOR gates in the remaining part of the i.c. and the counters are continually enabled.

In the series position, when one counter, say A, has come to its last count the latch is changed over and counter B is simultaneously reset and enabled. Counter B will then run to the last count as selected by S5 and the latch will be changed over again; counter B disabled, counter A enabled and reset. This continues for as long as necessary.

POWER SUPPLY

The power supply for the sequencer is shown in Fig. 5 and is based on positive voltage regulator i.c.s. The circuit will provide $\pm 12V$ at 500mA and can be used to power other synthesiser modules.

The circuit is designed around two positive regulators rather than a positive and negative regulator, since these are more readily available and cheaper, and this system requires the use of a transformer with separate secondary winding, available from Maplin or R.S. Components.

If the power supply is only to power the sequencer—no other synthesiser modules—then heatsinks will not be necessary, otherwise for the full power output adequate heatsinking must be used, and the transformer must be as specified.

Tantalum capacitors are used on the output of the regulators so as to provide adequate ripple rejection. The sequencer circuit itself will not malfunction, but the ripple could be superimposed on the sequential voltage outputs and hence the VCOs, etc. and be reproduced audibly.

Next Month: Constructional details and using the sequencer.



BINAURAL STEREO PATENTS

ADRIAN HOPE

THE BBC has recently transmitted several plays in binaural, or so called "dummy head", stereo and several commercial recordings have been issued to demonstrate the technique. Although binaural stereo is in fact an extremely old idea (just how old will subsequently emerge) there is still widespread confusion over what it is, how it works and what it offers.

The situation has not been helped by the rather inadequate press releases issued by the Broadcasting House Publicity Departments prior to the BBC binaural transmissions. These releases have been garbled by innocents in the national press with the result that many people who are in fact fully equipped to listen to binaural stereo radio transmissions may well not have realised the fact and thus missed opportunities.

CURRENT INTEREST

The current wave of interest in binaural stereo dates back to a demonstration given by the German firm Sennheiser at the Berlin radio exhibition in 1973. Soon afterwards, the test disc recording which was made for Berlin was used by the British magazine *Wireless World* for a small, almost casual, demonstration at the Olympia audio fair. First word of mouth, and then press enthusiasm, spread the news that binaural stereo reproduction can create far more effective surround-sound reproduction

than any quadrasonic or surround-sound loudspeaker system yet available.

The theory behind binaural stereo recording and reproduction is simple. Humans hear with two ears and are able to pinpoint the origin of a sound with remarkable accuracy, even with eyes closed. This is achieved thanks to the effect which the human head has on any sound arriving at both ears from a single sound source. Essentially the head serves as a baffle. When the arriving sound is of low frequency (a few hundred Hz) the head baffle has no discernible effect on the amplitude or volume of sound arriving at each ear. But it does have a discernible effect on the relative phasing of the long wavelength of the low frequency sound. When the pitch of the arriving sound rises, the head baffle has less discernible effect on the relative phase of the sounds. This is because the shorter the wavelength, the more anomalous the phasing becomes and the extra distance which the sound must travel between the two ears becomes less significant. But at these higher frequencies the head can attenuate the volume of the sound arriving at the furthest ear.

In other words the head acts as a potential obstruction to the sound arriving at each ear and this obstruction creates anomalies in either phasing or amplitude, depending on the soundwave frequencies and their direction of arrival. The human brain is remarkably adept at decoding these anomalies to pinpoint the sound source.

If a pair of omni-directional microphones are arranged one in each ear of the human head, or an imitation or dummy head which closely resembles the human head in shape, size and texture, then what the microphones capture is a reasonably accurate replica of the sound field at each ear. If the left and right ear replicas are recorded on the two tracks of a stereo tape recorder and replayed through an amplifier and stereo headphones, then the headphone listener will hear a reasonably accurate replica of what the ear microphones heard.

Although the system is not perfect (there may be difficulties in distinguishing front from back sounds) the headphone reproduction of a binaural (i.e. two eared) recording made using either a dummy or live head to hold the microphones, can produce a remarkable spread of sound all around and over the head of the listener. There is no real way of describing the effect, one can only recommend that anyone with a stereo hi fi system and a good pair of stereo headphones should listen either to a binaural stereo recording or a BBC binaural stereo transmission.

PATENTS

As so often happens, the history of binaural stereo and likely future developments are well documented by patent literature.

In 1881 Frenchman Clément Ader, who was fascinated by both aeronautics and telephony, arranged a demonstration at the Paris Electrical Exhibition to put the Bell telephone through its paces. He arranged eighty Bell telephone mouthpieces or "transmitters" across the front of the Grand Opera stage in Paris and connected them by hard wiring to eighty earpieces or "receivers" in the Exhibition Hall. The object was of course to demonstrate what was then regarded as high fidelity reproduction of sound by telephone wire communication. But listeners found that by using two earpieces instead of one they achieved a remarkably realistic image spread of the opera sound. They were, without realising it, discovering binaural stereo reproduction.

Until evidence to the contrary is produced it seems safe to take the next and most positive emergence of binaural stereo, as the patent application filed on April 13, 1927 by W. Bartlett Jones of Chicago. The patent was not granted until 1932 and carries the American number USP 1 855 149. It is still available for the public to read in the library of foreign patents attached to the British Patent Office in London.

Bartlett Jones was aiming to improve the reproduction of sound from recordings, for instance in a cinema. His experiments with a dummy head equipped with a microphone in each ear and connected to a pair of small speakers arranged as headphones one each side of a listener's head, convinced him that "a richer and more sonorous reproduction" than was obtainable from an ordinary phonograph was a practical possibility. Jones envisaged the idea of reproduction not only through headphones but also by a pair of loudspeakers "embodied into or secured to a seat so as to direct a right ear effect and a left ear effect to the seat occupant".

Last year at the Harrogate Hi Fi Festival one firm was demonstrating the modern equivalent of just such a seat, a lounging-all-enveloping chair with loudspeakers built into the side walls. Incidentally Jones in 1927 also proposed a technique of binaural stereo recording by cutting two grooves in a single disc or modulating a single groove both vertically and horizontally. He was certainly one of the forgotten audio pioneers.

It seems likely, from a reading of Bartlett Jones's patent, that the results he was obtaining from hard wire connections (it is doubtful whether he succeeded with recording) were comparable to those obtainable today from a lo fi system. Certainly a binaural system was installed in the Chicago Science Museum in the thirties and offered continual demonstrations to enthusiastic audiences.

One visitor recalls how the audience would be equipped with headphones through which they heard an announcer in a transparent soundproof booth talking into a dummy head microphone system. Half way through the demonstration each visitor heard an unfamiliar voice whispering in their left ear. "Could you please move a little to the right, you're blocking my view," said the voice. Like a field of corn every visitor, imagining that they were blocking the view of the listener behind, moved to the right.

LOUDSPEAKER STEREO

Why then did dummy head, or binaural, stereo not catch on permanently? Why was it forgotten again until the seventies? To answer the second question first, binaural stereo has never been entirely forgotten. Over the years, especially in the USA, there have been various test or demonstration recordings issued for minority interests. The answer to the first question lies again in the patent literature. In the early thirties Alan Dower Blumlein, working at EMI Hayes on improved sound reproduction, patented a system for reproducing stereo with a pair of loudspeakers in a room rather than a pair of headphones or a pair of loudspeakers in a chair.

The British patent number BP 394 325 (also still readily available) is perhaps the most famous audio patent of all time. It discloses in detail schemes for recording and reproducing sound in stereo using a coincident pair of microphones and spaced loudspeakers, with the sound recorded either in a double modulated disc groove (in the manner of every LP stereo disc now on the market) or on an optical film soundtrack (as now finding favour in Hollywood with films like *Star Wars*, *Close Encounters* and *Grease*). What Blumlein was aiming for, and achieved, was what we now call "stereo" reproduction without the anti-social limitations of headphone listening. In this respect he was too far ahead of his time.

The war years hampered progress and diverted public interest. But when the idea of stereo reproduction started to interest the trade and public again after the war, it was hardly surprising that the promise of reproduction with a pair of spaced loudspeakers in Blumlein fashion should capture the public imagination, rather than lonely reproduction by means of headphones or a loudspeaker chair. So loudspeaker stereo, not binaural headphone stereo, became the commercial norm—and still is.

SURROUND-SOUND

It was the upsurge of interest in surround-sound reproduction, and the various quadraphonic systems devised in an attempt to reproduce sound around the listener in a room, that set the scene for a major re-emergence of binaural stereo. Quite simply none of the quadraphonic systems foisted on the public in the early seventies could achieve what they set out to achieve, namely a true surround of sound around the listener. When Sennheiser demonstrated their first dummy head test disc (still obtainable from Hayden Labs, the British agents for Sennheiser at around 75p) the time was absolutely right for a rediscovery of binaural stereo. An ordinary stereo disc played on an ordinary stereo turntable through an ordinary stereo amplifier and through ordinary stereo headphones delivered far more than even the most sophisticated quadraphonic system. There are now several hi fi firms offering do-it-yourself binaural stereo recording kits, usually a dummy head with a pair of small capacitor microphones fitted to fit the ears. Sometimes the microphones are built into headphones, sometimes they can be worn in the ears of a human.

The over-riding disadvantage of binaural stereo is that a recording made in this fashion will produce the required result *only* when reproduced over headphones (or in a loudspeaker chair). The reason is obvious although repeatedly overlooked and misunderstood. In *loudspeaker* stereo reproduction the sound from the left speaker reaches *both* the left and right ears of the listener, and the sound from the right speaker reaches *both* the right and left ears of the listener. Also the sound is transferred to the listener via the room acoustics. Most normal recordings are made in a manner which presupposes that reproduction will be in this way and the entire chain of recording and room reproduction produces an illusion of a sound spread between the loudspeakers. When heard over headphones a recording made for loudspeaker reproduction will usually sound flat, as if coming from inside the listener's head. This is because there is direct interface between the headphones and ears.

A recording made with a dummy head and intended for *headphone* reproduction will produce a quite unsatisfactory stereo image when reproduced from loudspeakers. True binaural reproduction effect is only obtained when the sound picked up by the left ear microphone is channelled or interfaced only to the listener's left ear, and so on. When a binaural stereo recording is reproduced from loudspeakers, the sound picked up by the dummy head left ear will be reproduced by the left loudspeaker but will reach *both* the left and right ears of the listener, and so on. It will also be coloured by the room acoustics through which it travels. The result is a diffuse and confused stereo image. Loudspeaker and binaural stereo recordings are thus *not compatible*.

MODIFIED SYSTEMS

This incompatibility has prompted research all round the world to develop modified systems. In 1974 Herr Stahl of the German radio station RIAS, lectured broadcasters in London on how dummy head recordings can be doctored to make them compatible for loudspeaker reproduction. Essentially the undesirable acoustic crosstalk between left loudspeaker and right ear, and right loudspeaker and left ear, is cancelled. This is achieved by introducing phase shifts and delays into both sound channels.

A degree of frequency equalization is also used to compensate for, i.e. subtract, the effect of the acoustic transfer of the sound to the ears of the listener via the room rather than by direct interface between the headphones and the ears.

Stahl at the time stated that "the amount of electronic equipment required . . . is considerable . . . but with integrated circuits . . . manufacture would not be too expensive". Such manufacture is now under way in Japan. One of the firms

especially active in the field of binaural stereo reproduction is Matsushita. There are already on sale from JVC and National (so far in Japan only) add-on "black boxes" which doctor stereo signals so that they can be reproduced by loudspeakers with impressive binaural results. But listener position is *very* critical.

A Dutch inventor by the name of Johannes Van Den Berg recently patented in the UK (BP 1 503 400) an alternative approach to the problem which relies far less heavily on sophisticated electronics. Whether the Dutch idea works in practice is open to question but the theory is interesting.

Van Den Berg suggests that the original dummy head recording should be made with two dummy heads, rather than one. The two heads, each with a microphone in each ear, are set in front of the sound stage to be recorded a few metres apart, rather like two members of an audience on opposite sides of the stalls. The sound signals from the four microphones are channelled into stereo. The left ear signals from one head are mixed with the left ear signals from the other head to produce the left channel and the right ear signals from one head are mixed with the right ear signals from the other head to produce the right channel.

In this way the left channel output of the total system contains sound from both the extreme left of the sound stage and the centre of the sound stage, while the right channel output contains sound from the extreme right of the sound stage plus sound from the centre of the sound stage. According to the inventor the stereo output provides good results both with headphones and through a stereo pair of loudspeakers. Whether the inventor is right in claiming that "sound thus reproduced via loudspeakers gives the listener a considerably better spatial impression than sound reproduced by conventional techniques" must remain a moot point.

RECENT PATENTS

Patents recently granted to Matsushita in the UK show that the company is addressing itself not only to the enhanced reproduction of binaural recording with loudspeakers, but also to a closely related problem. This is how to improve headphone listening, especially with recordings intended for loudspeaker reproduction.

In BP 1520 612 three Matsushita inventors suggest that the characteristic "in the head" sound obtained from playing conventional stereo recordings over headphones is due to the lack of indirect or ambient sound heard by the listener. This point is also emphasised in a Matsushita paper in the Audio Engineering Society Journal for November 1976. The contention is that stereo recordings will sound dead and "inside the head" when replayed over headphones if they lack ambience or indirect sound. According to Matsushita, loudspeaker reproduction adds ambience from the listening room to such recordings, but normal headphone reproduction cannot of course add any such ambience. Thus, they say, the cure for "in the head" sound from headphones is to add artificial ambience or indirect sound to the signals to be reproduced.


It is certainly a fact that most modern recordings are made with close microphone techniques and added artificial reverberation and that these sound dead and "in the head" through headphones. It is also true that a good dummy head recording and a good recording made with a simple coincident microphone pair (suggested by Blumlein in the thirties and still thankfully finding favour with some recording engineers) do contain a considerable amount of natural ambient information and do sound "out-of-the-head" on headphones. Although Matsushita do not follow the train of thought, it may well be that our ears and brain are able to distinguish between natural ambience and un-natural added reverberation in a recording, rejecting the latter for the artifact that it is.

The Matsushita patent proposes that the sound of a conventional, dead stereo recording may be improved over headphones by introducing extra reverberation in mechanical manner. Essentially a mechanical spring is incorporated in the acoustic transmission path to the listener's ear. This introduces an artificial reverberant delay. The system sounds primitive and self-defeating in that the ambience added must surely be as unnatural as that already present in the recording. Certainly, and perhaps not surprisingly, there is no sign yet of such an acoustic ambience-adding system in the shops.


The approach suggested in the 1976 AES paper is much more encouraging, and indeed is now on demonstration in Japan. Instead of using a mechanical or acoustic circuit to add ambience or indirect sound artificially, an electronic circuit of bucket brigade devices is used to achieve the same object.

DIFFERENT SOLUTIONS

The same problems, but rather different solutions, are described in another recent Matsushita patent BP 1 517 938. Indeed this patent reads almost as if the issue of indirect sound and ambience has been forgotten by the Matsushita research department! "In the head" imaging is blamed partly on an abnormal sound pressure-versus-frequency characteristic which is created when recorded sound signals are delivered to the listener's ears with the intended acoustic link (loudspeaker-to-ear) "short circuited" by the use of headphones.

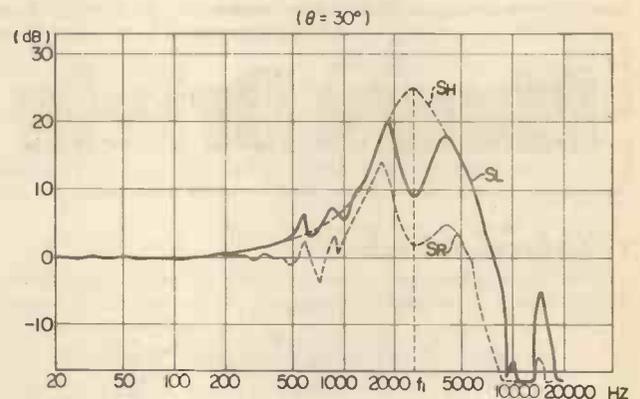

The patent includes graphs which show how sound pressure-versus-frequency characteristic measurements taken at the ears of a listener, first facing a pair of loudspeakers in a room, and then hard against a pair of hi fi headphones, do not match. The curves suggest that there is an un-natural peak introduced by headphone listening at around 3 kHz and the Matsushita patent proposes the incorporation of notch filters in the headphone circuitry to iron out this peak. The patent also lays blame for in-head imaging on the lack of acoustic crosstalk between left and

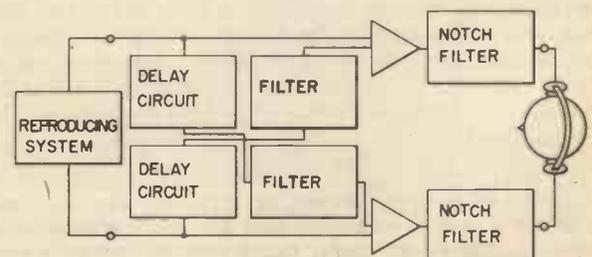


right channels when reproduction is through headphones rather than loudspeakers. To compensate for this Matsushita introduce electronic crosstalk (at low frequencies) between left and right channels. Additionally a slight delay is provided to simulate the slight delay which is introduced by the spacing of a pair of loudspeakers in front of a listener in a room.

SONY

Although there is of course some common ground between the theories proposed by Matsushita in the two patents and the AES paper, there is equally clearly no concerted agreement, even between workers in the same research lab, on how to tackle the single most important problem of headphone listening—how to ensure that the image is formed outside the listener's head, regardless of programme material. Moreover two patents recently granted to Sony, another Japanese electronics giant interested in the same field (BPs 1520 318 and 1 520 319) confirm that there is still plenty of room for dispute over the right approach to the problem.

Both Sony patents are concerned mainly with fairly trivial advances, for instance the incorporation of a miniature microphone in a headphone-like windshield for a dummy or human head to wear, and the incorporation of even more miniature microphones into windshield-like ear plugs for similar use. But both patents refer also to the loudspeaker reproduction of binaural stereo recordings. According to Sony when microphones at the ears of a human or dummy head receive sound from the front, the ear's physical structure produces peaks in the frequency response at 3kHz and 8kHz. These anomalies, according to Sony, help the listener to identify the source of sound and must be preserved in a binaural recording used for headphone listening. But when the binaural recording is

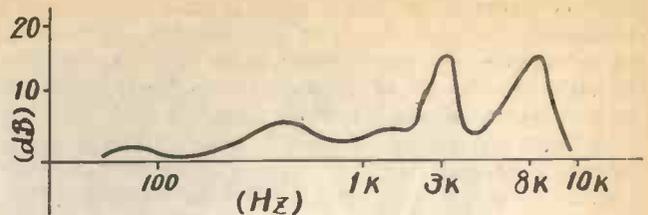

reproduced by loudspeakers in a room, the peaks will be artificially boosted because they are in effect created twice, *once* by the dummy head recording process and *once* by the real head listening process. Thus, say Sony, the frequency characteristic of a binaural recording intended for loudspeaker reproduction must be flattened with filters notching at 3kHz and 8kHz. But wait a minute? Doesn't Matsushita patent the apparently contradictory idea of flattening a 3kHz peak for *headphone* reproduction of a recording? You pay your money and you take your choice of interpretation!

One thing is certain. There is a considerable amount of research and development work yet to be done before the public is offered what has so far proved a chimera, namely a "black box" capable of making all kinds of loudspeaker stereo and binaural dummy head stereo recordings mutually compatible for either loudspeaker or headphone listening. ★

News Briefs

AWAY WITH CONTACTORS

IF YOU'VE ever tried to service an electromechanical timer unit, perhaps on a cooker or automatic washing machine, you've probably cursed. If you've had a vacuum cleaner switch jam up, or watched your freezer motor (*relay operated*) shake because it was switched *off* at the peak of the mains cycle, or dim the lights because it switched *on* at a peak, you've probably mumbled something about . . . "the sooner springs and contacts are banished from domestic appliances the better".

It's even more baffling to anyone with the slightest involvement in electronics, that solid state devices are not widely used, since there's nothing new, or expensive about triacs.

Fortunately solid state technology *is* advancing into this domain, and one arrival is the MOS-LSI microcircuit appliance timer by G.I.M., comprising central processor with on-chip memory.

The circuit (basically a 4-bit microprocessor) is essentially a versatile, low cost timer, providing designers with the type of facilities necessary for controlling cookers, driers, central heating, etc. The 28-lead version designated AY-3-1250, accepts instructions from "hours up", "hours down", "minutes up", or "minutes down" keys, where momentary depression of keys cause single increments or decrements, and continuous depression causes the displayed digits to cycle. In use, the circuit is linked to a 4-digit l.e.d. display indicating any function selected. It has three separate outputs for which on and off times may be programmed in.

The 40-lead version—designated AY-3-1251—is designed for more sophisticated systems where 10 × 4 keyboard or touchpad entry and 14-digit permanent display are required. It has four controlled outputs, each with a variable mark-space ratio for control of hotplate duty cycles, etc. The 14-digit display facility could be used for a minute minder (3 digits), oven temperatures (3 digits), time on/off (4 digits), and hotplate temperature (4 digits).

When used for fully automatic cooker control, the time programme would be entered and cooking temperature selected using a key pad. When the start time is reached the appropriate output would be activated and an "ON" indicator lamp energised. When the stop time is reached the output is deactivated and the minute minder audible alarm activated for 10 seconds. All three programmable outputs may be

separately controlled in this way, but the device can also be used in a semi-automatic or manual mode. A further facility allows a set programme to be repeated at 24 hour intervals by the simple depression of a "repeat" key.

Both 28-lead and 40-lead versions include a built-in standby frequency source, which allows the devices to function normally during mains failure. In this event the circuit detects the absence of 50/60Hz input, and a 200kHz oscillator takes over timing under external battery power and lights a "mains failure" warning lamp.

MODEL AIRCRAFT RADAR

EMISSION of sulphur dioxide is a subject of current interest in Europe, since industrial emissions in one country have been found to affect air quality and the acidity of rainfall in neighbouring countries. Pollution from the U.K. has been said to harm the ecology of Scandinavian countries.

The latest sale of the Plessey WF3 Windfinding Radar to the Central Electricity Generating Board has extended its application to that of tracking model aircraft.

Following successful trials at the Plessey Cowes plant on the Isle of Wight, a WF3 MK2 version was purchased by the Central Electricity Research Laboratories (CERL) for tracking and measuring plumes of gases and particles emitted from power station stacks, using radio controlled model aircraft carrying various sensors. The radar system will be used in a mobile mode so that equipment can be located in the optimum position for returning accurate aircraft flight tracking data.



Research staff of the CEGB are seen at the I.O.W. during trials with their radio controlled aeroplane. The Plessey radar system is in the background

Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.


by
**Alan
Turpin**

and
**David
Shortland**

INTERCHANGEABLE SCALE

A new range of IMO J Series analogue panel meters comprises ammeters, voltmeters (both moving coil and moving iron), varimeters and frequency meters. They feature interchangeable scale plates which are unplugged and reinserted without recourse to opening or tampering with the rest of the instrument.

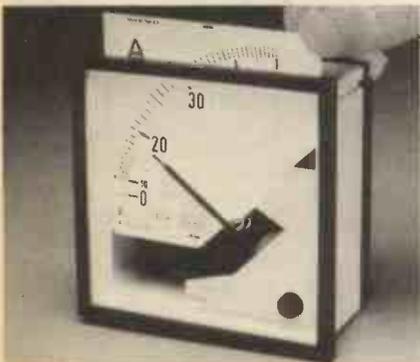They are available in three standard DIN sizes—72, 96 and 144mm square with quadratic scales for easy reading.



There is a wide range of scales from mA to MV. The meters have a full 90° sweep, compressed scales for overload, and employ silicon-damped, jewelled movements. The scales have "click" positive location for accurate reinsertion.


Transducers supplied with wattmeters or varimeters can be set for full or reduced power simply by switching an internal commutator, thus covering the majority of applications with a constant full scale output current of 5mA.

IMO Precision Controls, 439 Edgware Road, London W2 1BS. (01-723 2231/4)

EASY ACCESS BATTERY HOLDER

For projects needing a 9V battery this holder does away with having to take the project box apart when the battery gets flat.

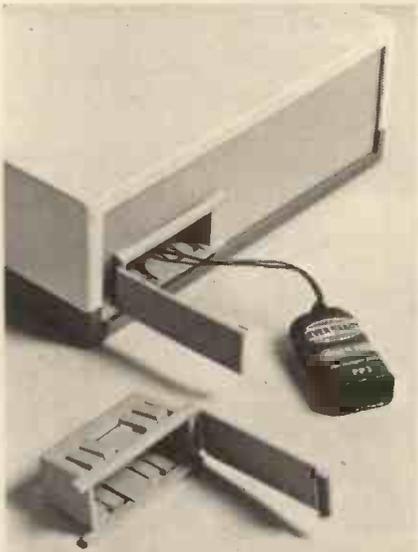A rectangular hole in a panel or enclosure with a thickness of 1.5 to 3mm is all that is required. The holder is simply pressed home.



Injection moulding has enabled the design to incorporate moulded retaining clips (holder to case and battery in holder) and also a flip-over hinged cover which snaps shut.

Complete with battery connector and lead for less than £1.

Battery Holder—Vero Electronics Ltd., Industrial Estate, Chandler's Ford, Eastleigh, Hants. SO5 3ZR. (042 15 69911).

ALTERNATIVE TO DAISIES

For frequent and fast setting these encoded numerical switches are worth consideration. They can be called up for decimal, hexadecimal, BCD, binary octal, and several other output codes, with options such as odd bit parity.

Each lever has a full travel of 90° and dial positions (8, 10 or 12) are selected by a positive click action. A bank of switches can be reset up or down with a single sweep of the hand. Number windows can be in the upper or lower part of the housing.




The housing is rear mounted into panels. A two bank switch is approximately 40mm wide and 30mm deep and takes about 40mm of space behind a panel.

Loading limits are 28V a.c. or d.c. at 50mA. Non-switching current is 1A. Life is over one million detent operations.

Full specification sheet, 1-0039, for series 28000 Minilever from sole suppliers (off the shelf), **Digitran UK, Melbourn, Royston, Herts SG8 6AQ (0763 61600).**

NEW TANDBERG CASSETTE DECK

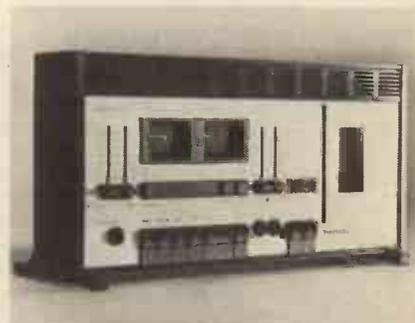The TCD 320 retains the three motor "Dual Capstan Closed Loop" tape transport system introduced by Tandberg. Seventy per cent of the cost of the machine is said to be devoted to the recording circuitry to ensure the most accurate recordings.



It can be operated in a variety of playing positions, mounted on a table-top, vertically or horizontally, or as a shelf model. It can be operated as either a front-loader or a top-loader.

Signal to noise ratio is 65dB minimum, according to DIN 45 500, while the frequency range is from 30 to 18,000Hz (DIN). The off-tape distortion is measured at 0.9 per cent.

A disengageable MPX filter cuts out the pilot signal when recording from FM stereo broadcasts, and the Dolby B noise reducing system cuts down tape-hiss by approximately 10dB at high frequencies.

MARSHALLS

The latest Marshalls catalogue which is now available features many new components and products including both the KIM and PET microcomputer systems which are available with a wide range of expansion units, peripherals and software.

The price of the catalogue is 50p post paid or 40p to callers. A Marshall (London) Ltd., 42 Cricklewood Broadway NW2 3ET.

ALPHANUMERIC PRINTER

The Printina CSC is a 24-column alphanumeric printer which can be adjusted by an internal trimmer to compress the characters until 32 columns can be printed on a single line.

Its fastest print rate is 1.2 lines/second with a 5-2V power supply (the unit will operate from 5V \pm 5 per cent). Write time is approximately 400ms and its working life is estimated at 10⁶ lines without service.



The printer uses standard rolls of metallised electro-sensitive paper with a 25 metres roll allowing 5,000 lines to be printed. The paper roll is stored internally and a new roll can be fitted easily in a matter of seconds.

The price of the Printina CSC is £240 plus VAT.

For further information contact Setek Instruments Limited, Hoddesdon Road, Stanstead Abbots, Herts SG12 8EJ.

ENCAPSULATED CONVERTER

A new range of miniature encapsulated d.c./d.c. converter power supplies for providing stabilised 5V or 12V outputs from unregulated 5V inputs is available from Gould Electronics. Both the MC (single-output) and MCD (dual-output) series have built-in metal casings for radio interference shielding, and are designed to be mounted on standard printed circuit boards.

Ten models are available in the range, with output current ratings of 1A or 2A for the 5V models, 400, 470, 800 or 940mA for the single-output 12V versions and \pm 190, \pm 230, \pm 412 or \pm 525mA for the dual-output 12V types.

Ripple is within 50mV peak-to-peak for single-output versions and 35mV peak-to-peak for dual-output versions and r.m.s. noise is within 1mV (20MHz bandwidth). The units measure 50 x 50 x 10mm for the 5W versions and 63.5 x 89 x 23mm for the 10W models.

For further information contact Gould Electronic Components Division, Raynham Road, Bishop's Stortford, Hertfordshire CM23 5PF.



ASCII KEYBOARD KIT

A 63 key ASCII standard keyboard capable of producing all upper and lower case alphanumeric symbols and control functions is now available from Newbear Computing Store. The keyboard requires only the addition of a 5V power supply, and the absence of MOS devices eliminates the need for either a negative power supply or any special handling precautions.


A simple optional switch allows the selection of upper case only or upper and lower case, and a red l.e.d. is provided as standard to indicate when the keyboard is in upper case mode.

All inputs and outputs are TTL compatible and follow normal 7400 series loading and level requirements. Positive logic is used, the eighth bit is an optional parity bit, and parallel output is standard. However, serial output can be provided by addition of a serial clock.

The price of the complete kit is £56 and full details are available from Jon Day, Newbear Computing Store, 7 Bone Lane, Newbury, Berks RG14 5SH. Newbury (0635 49223).

STRIPPERS . . .

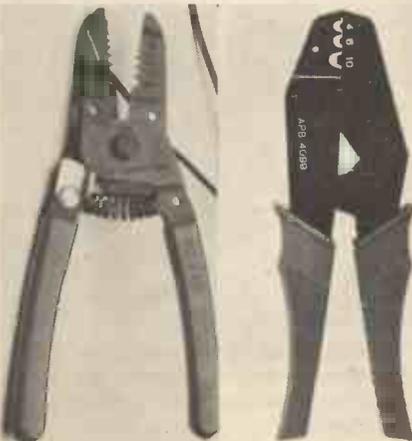The Milbar 15E which is covered by the Levermore "Belt and Braces" guarantee retails for a rec. price of £3.50 exc. VAT.



. . . AND CRIMPERS

AB Engineering have introduced a new range of light-weight crimping tools for 10-18 s.w.g. terminals.

BEEPI BEEP?

The new "Roadrunner" prototype wiring system is said to offer considerable economies on electronic and microprocessor development work and a fast, accurate means of producing pre-production circuit boards of any size, type or i.c. packing density.

Keys to the efficiency of the new system are the exclusive wiring instrument and the low-profile press-fix or glue-fix distribution strips employed. Together, they are said to allow fast, accurate working.



The wiring instrument, or "pencil", feeds the quick soldering enamelled wire from interchangeable bobbins. The instrument is balanced for easy handling and has a fine, long-life steel tip which aids accurate working, even in the most confined areas. Special features are the simple threading system which allows fast bobbin change and the facility provided for adjusting wire tension.

The castellated distribution strips have the capacity for retaining a large number of wires securely in position, without affecting the extremely low profile of finished boards. They have no posts to impede access when wiring.

"Roadrunner" systems are normally supplied in kits which include a circuit board, a wiring instrument, distribution strips and spare bobbins of wire in four different colours. However, individual components are available separately. A typical "Roadrunner" introductory kit retails at £8.50.

Agency enquiries are invited.

Further information from TJB Associates, Unit 116b, Blackdown Rural Industries, Haste Hill, Haslemere, Surrey, GU27 3AY.



DIGITAL ENLARGING EXPOSURE METER

A.A.LUHA B.Sc.

FOR THE PHOTOGRAPHER WHO DOES HIS OWN DEVELOPING

This device uses a photodiode to . . .

- (a) indicate the required black and white developing time
- (b) assess contrast on the negative, enabling suitable paper grade selection

FOR the amateur photographer who processes his own films and prints, the rapidly rising cost of photographic paper is a matter of serious concern, as is the pressure on one's time in our increasingly hectic life style. This article describes an exposure meter which enables the rapid and accurate assessment of printing times for black and white negatives and which will soon pay for itself in terms of saved time and bromide paper. The instrument was designed for the maximum possible convenience in use, together with a level of accuracy more than adequate for all black and white printing.

The meter consists of a light sensor, which is a small area high speed photodiode, an adjuster for paper speed, which may be a potentiometer or switch, a digital display, and an on/off switch. In use, the light sensor is used to find the area of maximum brightness on the enlarger baseboard, which of course corresponds to the darkest part of the print itself. This area gives a reading on the display, of the exposure time required for the print, directly in seconds. The meter itself is linear from one to more than five hundred seconds, which is way beyond the linearity of any photographic emulsion due to reciprocity failure. The inclusion of the third digit in the display, however, enables a second valuable measurement to be made very rapidly indeed, and that is the direct assessment of contrast range of the negative and hence the correct choice of paper grade for the enlargement.

Before describing the circuit and its method of operation, it will be useful to review what we require the instrument to do in a photo-physical sense. The exposure time required for a piece of bromide paper depends only on the intensity and wavelength of light falling on it. The distribution of wavelengths is dependent on the light source and, for the usual tungsten enlarger lamp, is both biased towards the red end of the spectrum and strongly dependent on filament temperature. The latter varies significantly with applied voltage and can be a considerable problem in colour printing. Fortunately, as far as black and white printing is concerned, mains voltage variation does not cause a real problem, even with completely unstabilised lamp supplies. Thus, as far as assessing exposure times is concerned, the only variable of interest is light intensity at the enlarger baseboard, and the

fundamental relationship is that exposure time is inversely proportional to light intensity. In mathematical terms we can write:

$$(a) \quad t = \frac{K}{L}$$

Where t is exposure time, L is light intensity, and K is a constant which takes account of the paper sensitivity and the spectral distribution of light from the enlarger lamp. We see then that an enlarger photometer is required to accept light intensity as an input variable, and output exposure time as the indicated parameter.

CIRCUIT DESCRIPTION

The basic operation of the instrument can most easily be understood by reference to the block diagram, Fig. 1(a). The light intensity at the enlarger baseboard is converted to a proportional photo-current by a reverse biased high speed silicon photodiode. This device offers a high degree of linearity of current with light intensity. The minute photo-current is converted to a proportional voltage by an op-amp connected as a current to voltage converter. The output of this stage is fed into an active low pass filter to remove the considerable 100Hz signal (due to alternate heating and cooling of the lamp filament twice during each mains cycle). The d.c. signal at the output of the low pass filter is passed to a voltage to frequency converter whose output frequency is proportional to the light intensity.

It is required to derive a signal which is inversely proportional to light intensity, and this is the *period* of the voltage to frequency output oscillation. This stage is therefore used to gate the output of a master clock generator (running at constant frequency) into the input of a digital counter/display module. Thus, as light intensity increases the time for which the gate is open is decreased, and the resulting number of clock pulses getting through to the counter is proportional to the exposure time required. Variable control of the master clock frequency establishes the constant of proportionality in equation (a), and this is brought out to the front panel of the instrument as the paper speed setting. Apart from the on/off switch, this is the only control requiring adjustment after initial setting up.

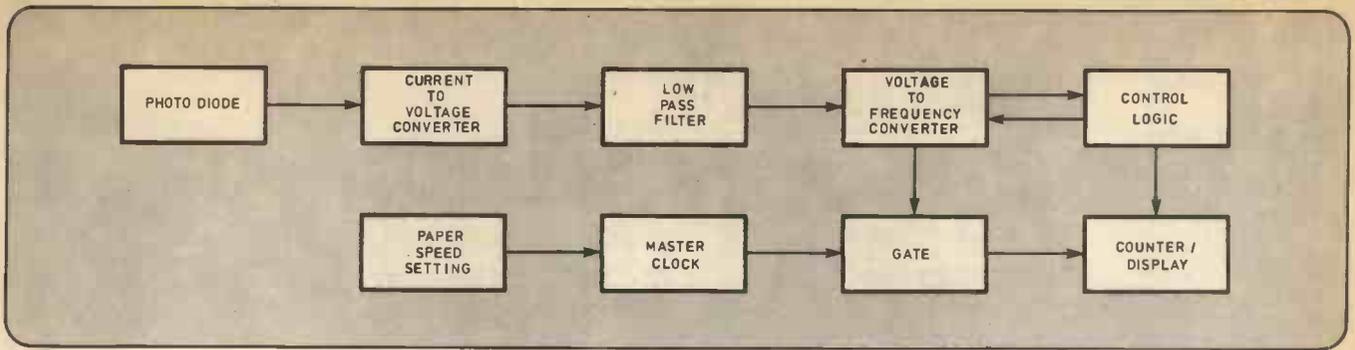


Fig. 1(a). Block diagram of Exposure Meter

Detailed operation of the circuit, shown by Fig 2, is best understood with reference to the timing diagrams of Fig. 3. IC1 is connected as an inverting amplifier and acts as a current to voltage converter in this application because the effective source resistance of the photodiode is many orders of magnitude greater than the input resistor R1. This resistor, which could be left out completely, serves to limit the input currents to IC1 in case of catastrophic failure of the photodiode. IC1 is one of the recently introduced BIMOS operational amplifiers and is used here because of the need for extremely low input bias current.

FILTER

The negative going signal at the output of IC1 consists of a d.c. level and a superimposed 100Hz sinewave. Although both the a.c. and d.c. components are proportional to light intensity, the d.c. signal is substantially larger than the a.c., and therefore using this reduces errors. The a.c. component is filtered out by the two-pole active filter formed by IC2, and R3, R4, R5, R6, C2 and C3. The CA3140 op-amp is used again in this stage because the very low input bias current permits the use of high value input resistors and hence relatively small capacitors, without the disadvantage of a large d.c. offset.

The negative d.c. level at the output of IC2 is applied to the inverting integrator IC3, R7, C4. Discharge of the integrator capacitor is accomplished by the transmission gate IC5(b), while IC5(a) shorts the input of IC3 to ground. The CA3140 is extremely valuable in this integrator because it permits a small integrator capacitor and large integrator resistor, which allows simple resetting of the integrator..

The output waveform of the integrator is shown in Fig. 3(a). It consists of a positive going linear ramp and an exponential discharge. The integrator output is applied to a fourth CA3140 operating open loop as a comparator. The reference voltage for the comparator is obtained from a simple Zener stabiliser, but the exact arrangement of earth return and positive supply is of crucial importance, and will be referred to in the constructional information. The use of the CA3140 in the comparator position is mainly due to its rapid slew rate, being approximately an order of magnitude faster than the standard 741.

The output of the comparator is a series of positive going pulses shown in Fig. 3(b). The pulses are applied to the input of the monostable multivibrator IC6(b) and IC6(c), via the NAND gate IC6(a). The NAND gate IC6(a) serves two purposes. Firstly it inverts and sharpens up the comparator pulses to the correct waveform for firing the monostable, and secondly it provides the vital power up reset pulse from R10, C5. The output of the monostable is inverted by IC6(d) thus giving two complementary pulses in response to the comparator pulse.

The positive going pulse at the output of IC6(d) is applied directly to the control inputs of IC5(a) and (b) where the high logic level opens the transmission gates and thus resets the integrator. The output of IC6(d) is further applied to the input of IC7(a) which is half of a CD4098 dual monostable multivibrator. The monostable is triggered by the rising edge of the reset pulse and complementary outputs are available at its Q and \bar{Q} output pins. The positive going pulse at pin 7 (\bar{Q}) is used to trigger the other monostable IC7(b) and also directly as the "transfer" pulse for the count display i.c. The output from IC7(b) is this time taken from the Q output since the counter display requires a negative going pulse to clear it.

The negative going pulse at the output of IC6(c) is used to inhibit the counter by closing the transmission gate IC5(c) during the reset period. The sequence of operation can be readily understood with the help of Fig. 3. Whilst the integrator is running up, clock pulses from the NE555V master clock generator are allowed through the transmission gate IC5(c) to the count input of the ZN1040E. When the comparator fires at the end of the integration period the count is disabled by the negative going pulse from IC6(c). One propagation delay later the main reset pulse at IC6(d) resets the integrator. During the reset period the transfer and clear pulses are generated sequentially. The transfer pulse causes the total count during the integration period to be latched by the display, and the clear pulse resets the counter to zero. It is important therefore that both transfer and reset are over before the next count is enabled. Fortunately the ZN1040E can respond to very short duration pulses which can easily be made to fit within the reset period without the need for precision components in the dual monostable circuit. The length of the reset period is not critical in any case, since the master clock is gated into the counter input.

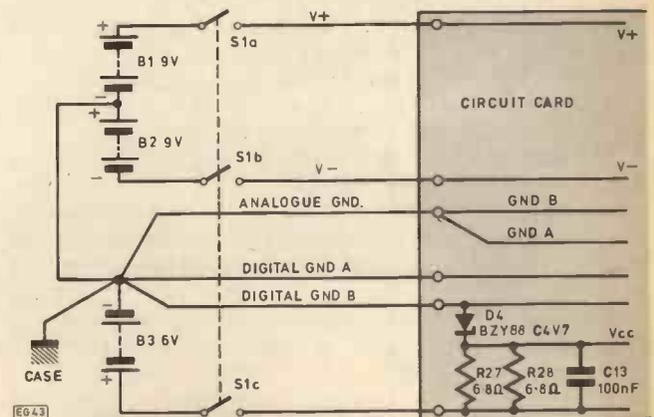


Fig. 1(b). Power supply arrangement


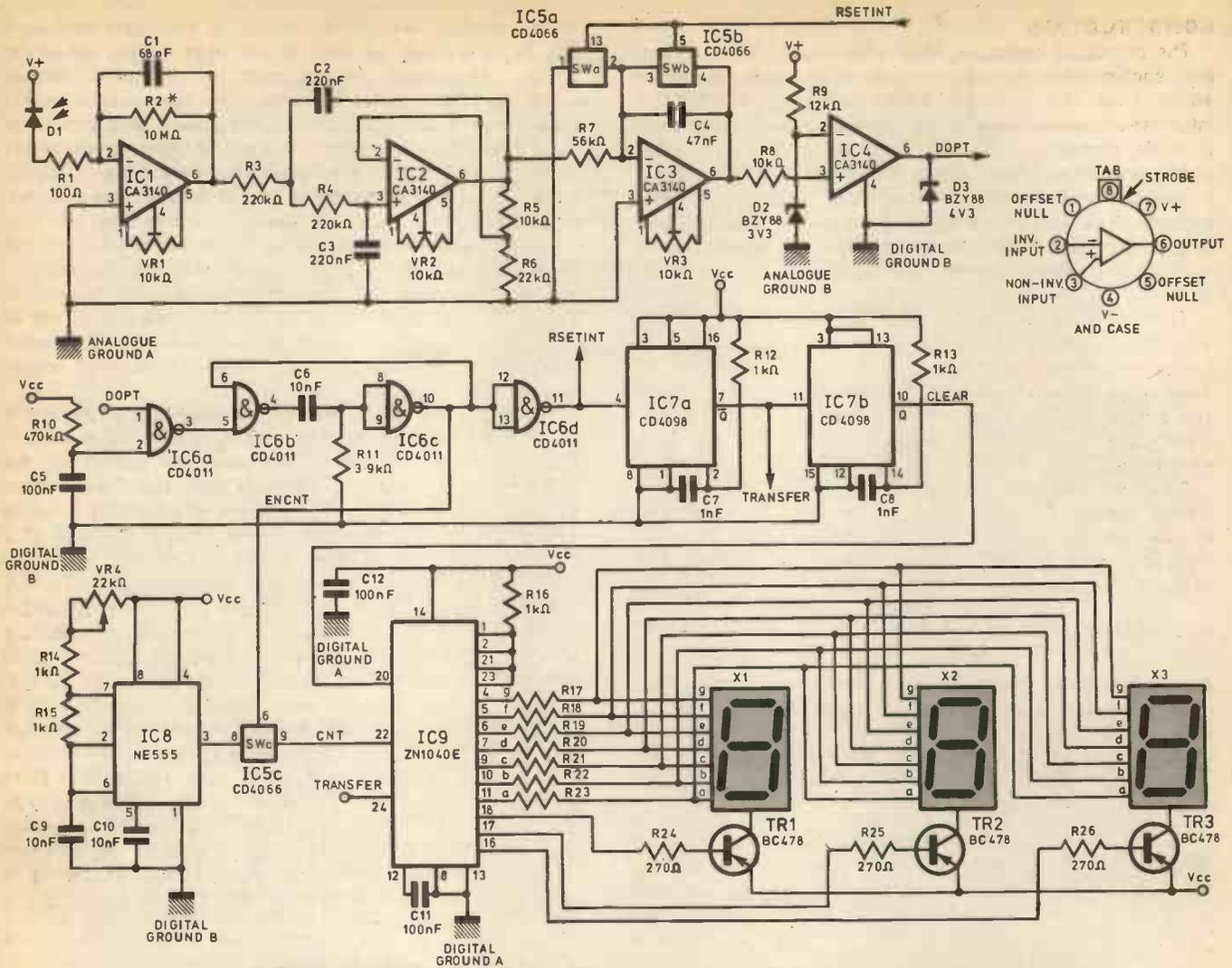


Fig. 2. Circuit diagram. IC1-3 powered by + and -9V, IC4 by +9V and DIGITAL GND B

Fig. 3. Correct waveforms for the various signals generated

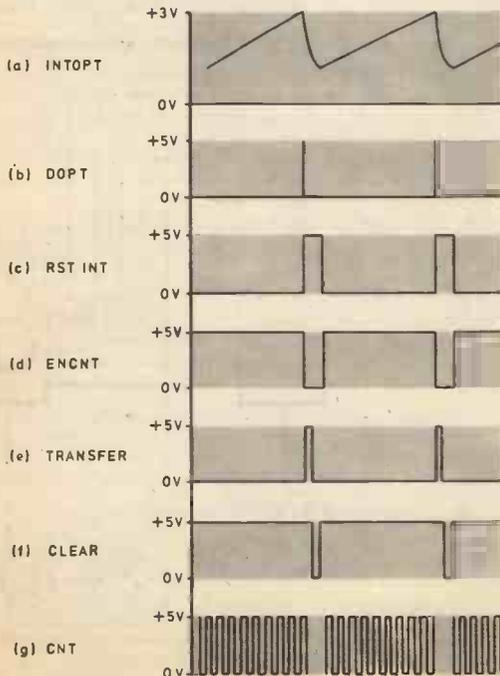

POWER-UP RESET

The only remaining parts of the circuit calling for some comment are the requirement for the power-up reset pulse and the use of the ZN1040E counter display i.e. The power-up reset pulse is essential because the integrator reset pulse is generated from a monostable. Thus, at start up, when power is first applied, if the comparator went to its high state before the reset monostable was enabled there would be no means of resetting the integrator. The simple RC network R10, C5 supplies a once only reset pulse approximately 50ms after switch-on, thus ensuring the integrator is reset.

The ZN1040E is a recent addition to the designer's armoury and a most valuable one. Its single package counts, latches, display-decodes and drives 7 segment displays together with full leading zero suppression and many other valuable features. The chip is capable of driving common anode or common cathode displays, and the circuit of Fig. 2 is shown wired for a common anode display. This configuration uses fewer resistors and transistors for interfacing, but the internal multiplex clock must be slowed down by external capacitor C11 in order to eliminate ghosting in the display segments (caused by the finite turn off time of the p.n.p. anode access transistors). Constructors wishing to use common cathode displays should refer to Fig. 4 which gives the necessary connection information. The use of the three most significant digits of the four digit counter is a simple but effective way of reducing jitter in the final display.

CONSTRUCTION

The prototype exposure meter was conceived as a hand held spot-measurement instrument which could be moved about over the enlarger baseboard, and display its information continuously at the baseboard itself, rather than a static metering unit with a probe at the end of a connecting cable. Thus there is the necessity that the meter should be both battery powered and small. The author experimented with the recently introduced "Verowire" wire wrapping system in an attempt to obtain the advantages of double-sided wiring, rather than designing a double-sided p.c.b.

The Verowire system proved a reasonable solution although a number of disadvantages became apparent. In particular, debugging the complete circuit proved to be much more difficult than with a conventional wiring method. The author would suggest that the use of standard 0.1in. Veroboard would be a wiser solution for the less experienced.

From the point of view of electronic construction and wiring, perhaps the most important single point is the need to use separate earth returns and positive supply lines for various parts of the circuit. This practice is an essential part of many professional instrument designs.

DECOUPLING

In a hybrid analogue and digital circuit, two major practical problems concerned with power supplies and their interactions are apparent. Digital integrated circuits change state so rapidly that the rising and falling edges of the transitions generate considerable switching spikes. In an undecoupled circuit the transients can cause sufficient amplitude supply line interference to cause unwanted or false switching of other circuits, but simple capacitive decoupling by the use of 10 to 100nF ceramic or polyester capacitors disposes of this problem. This measure may be insufficient, however, to eliminate problems in an analogue circuit using the same power supply, because by definition an analogue signal processing circuit should be capable of handling all signal levels with minimum distortion.

A second difficulty arises if the analogue circuit is used to process signals down to d.c., because now the possibility exists of the digital circuitry introducing d.c. offsets caused by the voltage drop of current flowing through the copper


interconnecting wire. This problem is especially serious if TTL logic is used because of the high current switching "gulps" associated with it, and for the same reason, whenever I.e.d. displays are used. These two reasons dictate that separate analogue and digital power rails should be used. There still remains the problem of referring one power supply to another. The simple guideline here is that no *digital current* should be permitted to flow in the analogue circuitry, and this is most simply achieved by connecting the two power supplies together at a single point and running separate analogue and digital ground wires to this point. In the present design two separate digital ground wires were used. One was used for the ZN104E and the second for all other logic circuitry. This is because by far the greatest current drain is taken by this i.c. and I.e.d. displays whose current flows through it.

In the present design the most critical part of the entire circuit is the comparator of the analogue to digital converter, because it is required to compare the output of the integrator with a stable reference potential. The method adopted here illustrates the problem of obtaining a stable potential from the analogue power supply. The use of a battery supply means that a simple potential divider is unsatisfactory because the internal resistance of the battery causes potential shifts on the supply rail as the current demand of the circuit alters. A simple Zener stabiliser removes both of these problems providing a stable ground reference potential is available. Here the only problem is in the voltage drop caused by the *analogue current* flowing in the copper conductor wire or strip of the analogue circuit return line. This too will be changing at each instant of time. The solution is to run a separate earth return wire from the ground end of the Zener diode (anode in this circuit) to the battery connection at the board. With these precautions the simple Zener stabiliser has adequate performance without the need for temperature compensation or a constant current source. Refer to Fig. 1(b) for details of the power line arrangement.

DEBUGGING AND SETTING UP

An oscilloscope is most useful but is not essential. Start by making the display circuitry operate in conjunction with the master clock. It will be helpful to slow down the clock

Fig. 4. Alternative wiring for common cathode displays

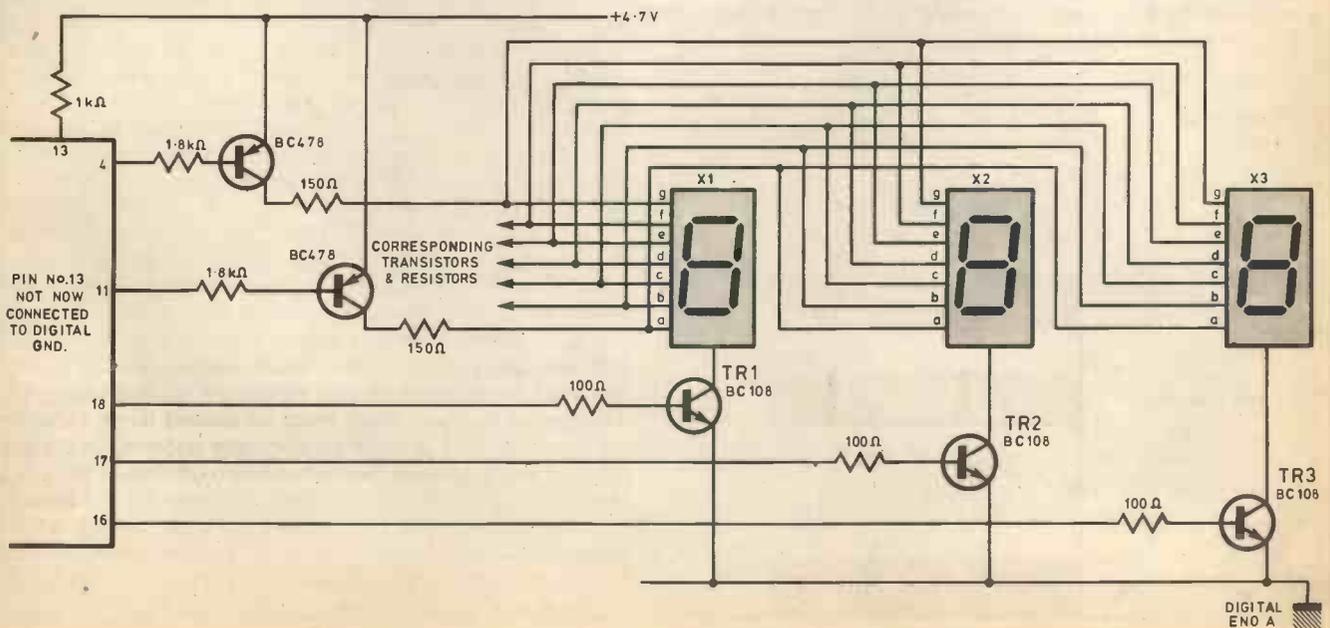

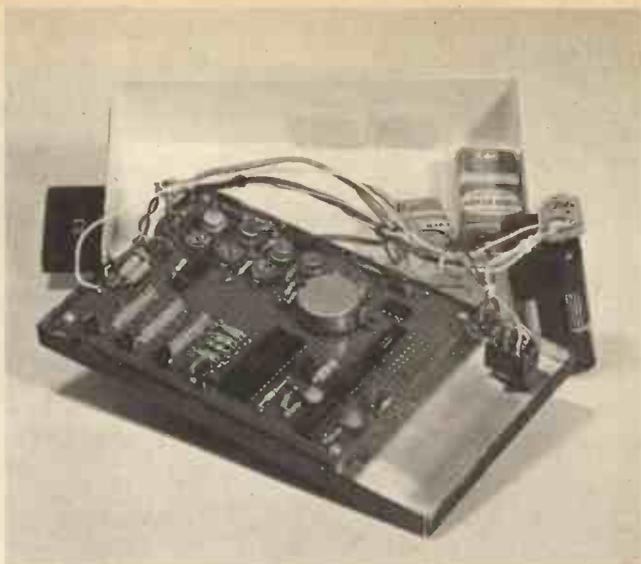
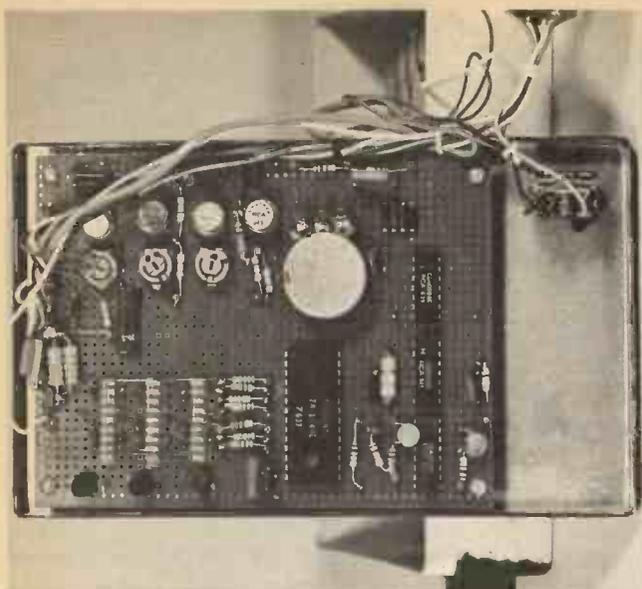


Table 1. CONTROL FUNCTIONS OF THE ZN 1040E

FUNCTION	PIN NO	LOGIC LEVEL TO OPERATE	EFFECT
Lamp Test	2	0	Displays 888
Digit Select Sense	13	0	For common anode displays.
		1	For common cathode displays.
Clear	20	0	Clears counter
Up/down Select	21	1	Count up
Count Input	22	0→1	Increments counter
Count Inhibit	23	0	Inhibits counter
Transfer	24	0	Latches display.
		1	Transfers current contents of counter

Potentiometers

- VR1-VR3 10k Ω Skeleton preset (3 off)
- VR4 22k Ω Carbon linear

Capacitors

- C1 68pF Silver mica or polystyrene
- C2, C3 220nF Ceramic (2 off)
- C4 47nF Ceramic
- C5, C12 100nF Ceramic (2 off)
- C6, C10 10nF Ceramic (2 off)
- C7, C8 1nF Ceramic (2 off)
- C9 10nF Polystyrene
- C11, C13 100nF Polystyrene (2 off)

Transistors and Diodes

- TR1-TR3 BC478 (3 off)

Displays

- X1-X3 Any common anode 7 segment led display

Integrated Circuits

- IC1-IC4 CA3140 (4 off)
- IC5 CD4066
- IC6 CD4011
- IC7 CD4098 or MC14528
- IC8 NE555
- IC9 ZN1040E

Semiconductors

- D1 BPW34
- D2 BZY88 3V3
- D3 BZY88 4V3
- D4 BZY88 4V7

Miscellaneous

- S1 3 pole toggle switch
- Battery connectors

COMPONENTS LIST . . .

Resistors

- R1 100 Ω
- R2 10M Ω *
- R3, R4 220k Ω (2 off)
- R5, R8 10k Ω (2 off)
- R6 22k Ω
- R7 56k Ω
- R9 12k Ω
- R10 470k Ω
- R11 3.9k Ω
- R12-R16 1K (5 off)
- R17-R23 470 Ω or 150 Ω * (7 off)
- R24-R26 270 Ω (3 off)
- R27, R28 6.8 Ω (2 off)

*R17-R23 select 150 Ω -470 Ω depending on display colour/brightness desired. *R2 see text.

generator to about 20 or 100Hz (by wiring a large capacitor across C9) and applying it directly to the count input of the ZN1040E. Refer to Table 1 to ensure that the count display operates correctly in response to the transfer and clear functions. Remember to establish a logic 1 condition by using a 1kΩ resistor between Vcc and the i.c. input. Remember also that the counter will divide the master clock frequency by 10 because only the three most significant digits are used. Next, ensure that the chain of inverters and monostables operates in the correct sequence. If an input pulse generator is available, together with an oscilloscope, things are easy, but the simple trick of slowing pulses down by wiring large value capacitors temporarily in parallel with the normal circuit values makes it possible to trace through the circuit with nothing more than a multimeter. Establish that a positive going pulse at pin 1 of IC6(a) fires the monostable IC6(b), (c) and that complementary outputs are available at pins 10 and 11 of this i.c. Check that the positive going pulse at pin 11 of IC6(d) is responsible for initiating the output of IC7(a) and that the negative going edge of IC7(a) output fires IC7(b). In normal operations it is essential that the transfer and clear pulses occur within the reset width. This is impossible to verify without an oscilloscope, but the circuit constants given allow a substantial margin for component tolerances.

Next establish that the analogue to digital converter is operating. Again it is possible to slow things down to multimeter speeds by temporarily increasing the value of the integrator capacitor C4. Short the input end of R7 to analogue ground and apply a signal to IC3 via a resistor of between 1MΩ and 10MΩ temporarily connected to pin 2 of IC3. Disconnect the output of IC4 from the input to IC6(a). Confirm that the integrator will ramp positively for a negative input signal and negatively for a positive input. With a negative input signal and positive ramp, check that the comparator output at IC4 pin 6 changes state at about 3.3 volts. If all seems well, reconnect IC4 to IC6(a) when the comparator transition should initiate resetting of the integrator. The output spike of the comparator will be too fast to observe with a multimeter but it is possible to ascertain that the integrator resets and ramps at pin 6 of IC3. When all is well remove the temporary input resistor and large value integrator capacitor. With the input end of R7 still grounded, adjust the d.c. offset potentiometer associated with IC3 for the minimum rate of positive going ramp. It should be possible to obtain a period of about 10 seconds between resetting of the integrator. Finally, remove the short from the output of IC2.

The next stage to set up is the active low pass filter IC2. It is not so easy to establish this stage is operating correctly without an oscilloscope. The stage acts as a non-inverting d.c. amplifier with a gain of about 1.5, for voltage inputs applied directly to pin 3. If this can be established it is probably safe to assume no wiring errors exist and that the circuit is also operating as a filter. The offset potentiometer is adjusted by grounding the input at pin 3 and adjusting for the minimum rate of positive going ramp at the output of IC3. If an oscilloscope is available the filter action is best established in conjunction with IC1.

IC1 operates as a straightforward current to voltage converter. The output of IC1 will contain a significant a.c. component of 100Hz if the photodiode has light from a normal household tungsten bulb incident on it. This should be absent at the output of IC2 if the latter stage is operating correctly. The d.c. offset adjustment of IC1 should be set up in an analogous manner to IC2 and IC3 (i.e. by adjusting for minimum rate of ramp at IC3 output). For this stage it is important to compensate for the dark current of the

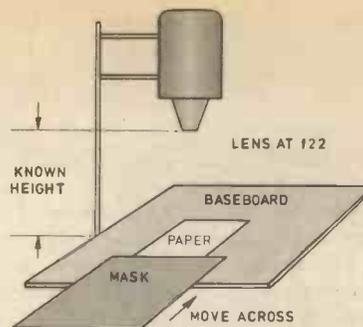


Fig. 5. Making a test strip

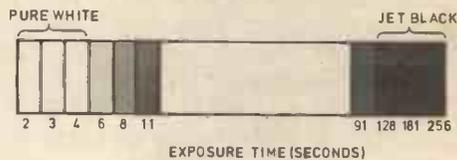


Fig. 6. Test strip


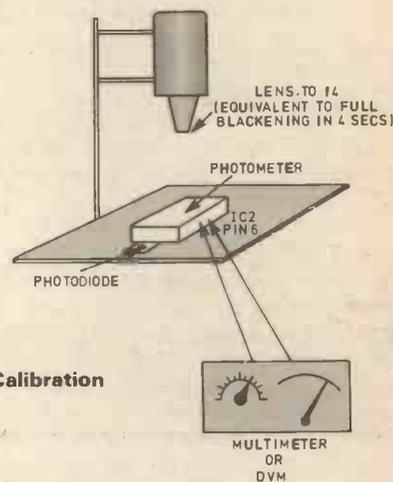


Fig. 7. Calibration

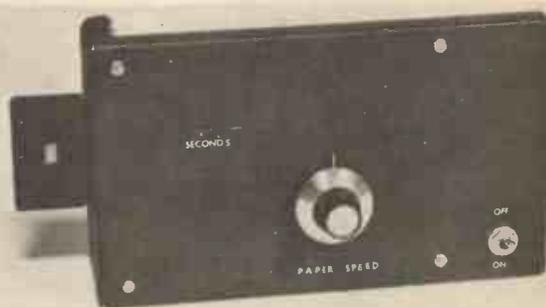

photodiode which must therefore be in circuit, but in total darkness. This offset adjustment constitutes the final electronic setting up with the possible exception of some adjustment to R2 depending on the light source used in the enlarger.

CALIBRATION AND PHOTOGRAPHIC USE

The method of calibration of the photometer is to adjust the display readout to give the exposure required to obtain a black level on the final print. Electronically this is accomplished by adjusting the clock frequency using the paper speed control, VR4, after ensuring that the photometer is operating in a linear region of its first stage amplifier for normal working light levels. It is necessary that the calibration is carried out in conjunction with a carefully prepared photographic test strip. The photometer is

sufficiently accurate and reproducible to make it feasible, and worthwhile for the advanced worker, to make separate test strips for each make, grade, and surface of paper normally used.

Start the calibration by making a test strip with the enlarger at an extension of about 800mm from the baseboard, with the lens fully stopped down, and with nothing in the negative carrier. Make a note of the settings so that they can be exactly reproduced at a later date. This will help if any modifications to the enlarger optical system or radical changes in photographic methodology are contemplated later on. Start using grade 2 (normal) paper.

Place a sheet or strip of paper on the baseboard and have ready a piece of cardboard sufficiently large to cover the entire piece of photographic paper. Switch on the enlarger and begin exposing the paper. Cover up strips of the paper at the following times (seconds): 2, 3, 4, 5, 6, 8, 10, 13, 16, 20, 25, 32, 40, 51, 64, 81, 102, 128, 161, 203, 256. This sequence gives increases in exposure approximately equivalent to one third of a stop. See Fig. 5.

Alternatively the sequence: 2, 3, 4, 6, 8, 11, 16, 23, 32, 45, 64, 91, 128, 181, 256, which gives increases equivalent to half a stop may be used. Switch off the enlarger and develop the test strips in the manner which will be used for developing actual prints. Pay particular attention to developing for a fixed time at a fixed, *certainly known*, temperature, and for these test strips, which will be reference items in the future, use freshly prepared developer.

FINISHED TEST STRIP

The resulting print should contain strips of grey each distinguishable from the other with one or more strips corresponding to pure white (i.e. indistinguishable from each other and from the paper base), and one or more strips corresponding to pure black and again indistinguishable from one another. If this result is not obtained, repeat the test strip until it is, by increasing or decreasing the light level at the base board. Thus, even if with a two second exposure some darkening of the paper is discernable, decrease the light level by increasing the extension of the enlarger or by inserting a neutral density filter in the light path. A piece of wiremesh such as a tea or coffee strainer would be ideal for this. Alternatively, if a difference between the two longest exposures is seen, increase the light level at the baseboard by opening the enlarger lens one or two stops. In any event aim for a test strip which encompasses full white and full black. Note that even for grade 1 glossy paper the range of densities which can be seen is unlikely to be more than 40:1. For non-glossy and harder papers this contrast range will be significantly less, reducing to about 5:1 for grade 5 paper. Mark on each distinguishable strip of density the actual exposure time as this will be valuable later on for more advanced work.

Consider the test strip made on grade 2 (normal) glossy paper (see Fig. 6). In the examples shown the first discernable strip occurs at 6 seconds whilst no further increase in blackening occurs after 128 seconds. This effect has taken place at a known enlarger extension (normally 800mm) and at a known aperture (say f22), which together define the intensity of light falling on the baseboard. We now require to adjust the photometer so that it indicates the correct exposure time in seconds to get a black level on the final print, and most importantly to ensure that it is working within its linear region of operation.

Switch on the photometer and place it on the enlarger baseboard. Monitor the output of the low pass filter at IC2 pin 6 with a multimeter or DVM if available. The aim is to

adjust the resistor R2 so that with the maximum light which will fall on the photodiode sensor in practice, the output of IC2 is well below saturation, i.e. about 4 volts. A suitable light level to aim for is that which would give complete blackening of the paper in about 1 second. This light level is unlikely to be exceeded under normal working conditions because of the difficulty of timing the exposure manually or of obtaining reproducible results from an electronic timer due to thermal lag of the filament at such short exposures.

BLACK TIME

In the example of Fig. 6 complete blackening has occurred at 128 seconds. In order to increase the light level so that complete blackening would occur at 1 second, an increase of light of seven stops is needed. Thus, if the test strip was made at f22 we need to open the enlarging lens to f2. On many enlarging lenses this is not possible because the maximum aperture may be only f4. If this is the case either change the enlarger-to-baseboard distance to 400mm which will give four times (2 stops) more light intensity at the baseboard, or more simply set up the photometer so that the output at pin 6 of IC2 will be about 1 volt (i.e. about $\frac{1}{4}$ of 4V). It should be found that the starting value of R2 given, 10M Ω , is not too far out. See Fig. 7.

It is absolutely essential that during the selection of R2 only light from the enlarging lamp reaches the photodiode.

A normal darkroom safelight is completely useless for this procedure because the photodiode specified has extended red sensitivity and light from even a tiny safelight yards away will be many times more than that coming from the enlarger. If a DVM with i.e.d. display is used there will be no difficulty, but if an analogue multimeter is used it means that the scale must be read either by the light of the enlarger itself or by a small torch which must be well screened from the photodiode. Select R2 so that when the light intensity would cause full blackening in 1 second, the output of IC2 pin 6 is about 4 volts. This adjustment is in no way critical, but is important to ensure that the amplifier is not saturating. A value for R2 giving 50 per cent less output than suggested will give perfectly good results.

When the value of R2 has been established the photometer has been calibrated photometrically. The value on the digital display should now be in the range of the paper speed control. Return the enlarger to 800mm extension and minimum aperture, and check that with all other lights extinguished the photometer can be adjusted to read 128 seconds. This reading is of course that value of exposure which will give a black level on the final print. Check the linearity of the photometer by opening up the enlarging lens. The indicated exposure should halve for each stop increase. Do not be too worried if there is not an exact twofold change in reading because the photometer is likely to be more accurate than the mechanical stop of the lens.

SIMPLE TO USE

Having calibrated the photometer, using it is simplicity itself. Put a negative in the carrier and using the photometer, select the area of maximum brightness. The indicated reading will be the exposure required to give a true black level for that area of the negative. This criterion is usually met in practice, but false readings will occur if no black level is present on the negative. An alternative means of using the photometer is to set the paper speed control so that the photometer indicates a correct flesh tone. To do this refer to the calibration test strip for the correct exposure needed to give the required flesh tone and set up the enlarger to the

standard conditions used for making the test strip. Adjust the paper speed control to give the required number and the photometer is now calibrated in terms of standard flesh tone.

PAPER GRADE

As stated at the beginning of the article the photometer can be used to assess the correct grade of paper needed for an enlargement. A brief indication only of this use will be given since the interested photographer will find the necessary information for himself. Suppose a negative has areas corresponding to pure black and pure white. When this is projected in the enlarger the photometer can be used (without alteration of the paper speed control) to compare

directly the intensities corresponding to pure black and pure white. For example, suppose the brightest part indicates an exposure time (for maximum blackness) of 10 seconds, and without altering the setting, the darkest part indicates an exposure time of 80 seconds, then the contrast range is 8:1. This contrast range of the negative must be fitted onto a printing paper with the same contrast range in order for a full black and a pure white to be apparent. In our example of Fig. 6 the paper had a contrast range of $128:6 = 21:1$. Thus it would be unsuitable for a negative whose range was only 8:1, because an exposure necessary to cause full blackening of the paper would cause the whites to come up very grey. It should now be apparent how the combination of test strips and photometer can be used to select both the correct exposure and the correct paper grade in conjunction. ★

News Briefs

MORE BUBBLES!

NATURE is full of bubbles! Just when magnetic bubbles are beginning to make their mark on memory technology, another type of bubble is discovered, *made of light*.

Last year, scientists at IBM's San Jose Research Laboratory discovered that microscopically small sources of light in a particular class of electroluminescent thin films can become mobile under certain conditions.



When a voltage oscillating at a high enough frequency is applied across one of these thin films, tiny light-emitting filaments, each about one micron ($1/25,000$ inch) in diameter, appear to pour out from isolated points in the material and to swarm randomly about in it.

Discovery of the mobile filaments occurred during experiments aimed at understanding the light-emitting properties of manganese-doped zinc sulphide films. Non-mobile light properties of these films are being investigated by a number of laboratories that are interested in information display technology.

Images can be formed in devices based on this material either by stimulating areas of the film with a light beam or an electron beam, or by applying an "addressing" voltage across the film to induce light emission from selected areas of the material. An important feature of these so-called ACTEL (alternating current thin-film electroluminescence) devices is a "storage" effect that enables them to retain an image for an extended length of time without the necessity of periodically refreshing the screen, as is needed in cathode-ray-tube storage displays.

In the IBM experiments, an AC voltage is applied to the film via sets

of crossed metallic lines about one millimeter wide, the horizontal lines being deposited on one surface of the material and the vertical lines on the opposite. When voltage is applied to a pair of intersecting electrodes, the intersected area of film will emit light. Each such area encompasses some tens of thousands of individual light-emitting filaments. It is these individual filaments that can become mobile.

As the frequency of the applied voltage reaches the neighbourhood of 10,000 hertz, the threshold of filament mobility is achieved. Looking at the light-emitting filaments through a microscope, one can see the tiny spots of light moving in small, discrete steps from one location in the material to another. On close examination, it appears that the illumination is being transferred from one site to another through a process in which the emission from a filament is extinguished at approximately the same time as emission from another begins.

Raising the frequency of the applied voltage still further (to about 50,000Hz) causes the mobility of the light bubbles to increase as they wander over relatively broad areas of the film. When one bubble approaches another, they repel each other. Isolated regions in which the mobile bubbles are generated can be clearly seen in microscopic views of the material, and at high frequencies, hundreds of the moving points of light appear to pour out of these sources like water from a bubbling spring.

The locations of the sources of mobile filaments are thought by the researchers to be associated with microscopic defects in the polycrystalline structure of the zinc sulphide films.

FIVE-STEP A TO D


A NEW five-step analogue level detector with a high impedance input has been announced by Texas Instruments. The TL489 consists of five comparators to digitise analogue input signals.

The five comparators and a reference voltage source detect the level of an input signal. Output 1 is switched to a low logic level at a typical input voltage of 200 millivolts. After each additional 200-millivolt step, the subsequent outputs are switched to low logic levels. All outputs are switched to low logic levels at a typical input voltage of 1000 millivolts (full scale). The open-collector outputs are capable of sinking currents up to 80 milliamperes and may be operated at voltages up to 18 volts. The analogue input has a high impedance of 100 kilohms.

Since all five trigger points have a switching hysteresis of typically 10 millivolts, the circuit may be operated with slow input signals without danger of oscillation at the outputs. To prevent pick-up of noise, a capacitor should be connected between the high-impedance input and ground, especially when the input is driven from a high-impedance source.

The TL489 is especially designed to detect and indicate analogue signal levels. The device may be used in various industrial, consumer, and automotive applications. Power outputs are suitable for driving a variety of display elements such as LEDs or filament lamps. The output may also drive digital integrated logic such as TTL, CMOS, or other high-level logic.

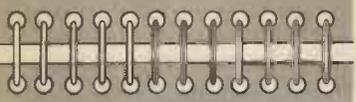The TL489 in an 8 pin plastic DIP is characterized for operation from 0°C to 70°C . Price in 100-piece quantities is £0.45. The new analogue level detector is available from TI authorised distributors and from TI Bedford.



INDUSTRY NOTEBOOK

By Nexus



The Real World

Let us now turn away from speculation and look at the real world and what real people are doing in it.

First, Racal Electronics Group who celebrated another successful half-year report (profits up 25 per cent on 11 per cent increase in turnover) with the announcement of a £20 million export order, the largest ever received in the Group's 28-year history. It is for a communications package for an unspecified country in the Middle East and takes in products from a number of Racal companies.

I have often referred to Racal as "unstoppable". They continue so with unparalleled vigour and determination to do even better. Racal exports average out at £16,000 in value per worker, a figure unmatched in the UK by any other manufacturing company. It does your heart good to talk to the directors, enthusiasts all, never harking back to the "good old days", instead looking forward to every new challenge ahead.

One such challenge is electronic warfare. Expect to hear later this year about Jaguar. Not an automobile but Racal's answer to battlefield jamming. In Racal's book Jaguar is the acronym for JAMming GUARded Radio on which one of Racal's top design teams has been engaged for the past two years. It is a frequency-hopping field radio which, because it is continuously changing its frequency, is difficult to intercept, or jam or get a bearing on.

Expect, too, to hear of more Racal acquisitions both at home and overseas. Parts of Decca and Plessey are still tipped as possibles, indeed probable, acquisitions for Racal in any industry rationalisation programme.

Meantime data communications is one of Racal's big growth areas in cash terms with a projected £75 million turnover this year. The business is world-wide and still expanding fast. Racal's main manufacturing bases and biggest single market are in the USA where the Racal pay-roll has now soared to 2,300 people.

Expansive Giant

The other front-runner is giant GEC, also busy expanding in the UK and overseas. The recent acquisition of the US company A. B. Dick has opened the door for GEC's entry into the profitable office equipment market, the negotiations with Avery provide an electronic weighing market if the deal goes through, and the joint venture with Fairchild will bring GEC into the major league in VLSI with both technology and marketing outlets.

The logic of all this activity is that apart from GEC's considerable existing in-house demands for microcircuits, both Avery and A. B. Dick are potential big users. So although office equipment and weighing machines look odd areas to get into, there is a direct connection with electronics and particularly the "chip". The forecast that GEC-Fairchild will be in production by 1980 was still firm at the time of writing and the initial phase of 100 people is planned to expand to 1,000 at a rate which will presumably be geared by market demand.

Both GEC and Racal are already in the microcircuit business, Racal at present only in thick-film hybrids and designing their own custom silicon i.c.s with processing by outside contractors. It is probable that Racal will set up diffusion facilities in the near future. GEC has the Hirst Research Centre for fabrication of exotic devices (such as c.c.d.s) and has a first-class thick-film hybrid plant at Marconi Space and Defence Systems at Portsmouth. I can say this with certainty, having recently visited it.

Wall-to-Wall

You don't expect to find wall-to-wall carpeting in a machine shop. Yet this is precisely what I found in the tool room of the Berg Electronics plant in Holland. Not only wall-to-wall carpeting but also a profusion of house-plants, many of them exotic varieties. A settee, armchairs and a TV set, though not present, would not have looked out of place.

Berg make connectors and the piece parts are of high precision demanding great skill in tooling for the high speed presses turning out millions of parts a day. The restful atmosphere no doubt pays off in quality of work. But wherever I went in the plant there was light and air and, above all, cleanliness. Even the plating shop was completely free of noxious fumes and the duckboards were dry. British firms please copy.

Avionics

Avionics companies get a new boost with plans for the Westland WG34 helicopter replacement for the current Sea King. Project definition contracts are already out for communications, radar, anti-submarine systems, data handling and flight control systems. Among the British companies involved are Marconi, Decca, Ferranti, Smiths and Louis Newmark. The WG34 is essentially a Royal Navy project but is expected to be also produced collaboratively in Europe, the Italians in particular having expressed an interest.

EMI's new Searchwater radar has had its first production delivery to the Royal Air Force for the Nimrod Mk 2 maritime reconnaissance aircraft.

Among avionics production units now using MPUs is the fuel flowmeter system designed by Marconi Avionics for use in the Hawk jet trainer and light attack aircraft, ordered for the RAF and for the Finnish and Indonesian air forces.

TRSB

Finally, remember the row over the proposed international microwave landing system, that finally chosen being the US Time-Reference Scanning Beam System (TRSB) in preference to the British Doppler System? Now, it looks as if TRSB is running into trouble on costs, apart from the fact that a full-scale working system has not yet been demonstrated. There could still be a chance of the British system re-emerging as a world standard.

VLSI Chat

The VLSI publicity bandwagon rolls on. Inevitably the word "chip" is the one that has caught on, sometimes qualified by "silicon". Few people in the UK can have missed hearing about it. Just as people now identify the "pill" with birth control, so the "chip" according to popular viewpoint means disaster (six million unemployed) or the dawn of an earthly paradise (unlimited wealth and leisure).

Lay people are now convinced that whatever the chip might be—few actually understand what it is or what it is supposed to be able to do—the one sure thing is that we must have it. Why else would the Government be backing it with first £50 million, then £100 million, now £200 million, tomorrow £500 million? Could it be for votes?

Inmos

Inmos, meanwhile, struggles manfully on, surrounded by unseemly squabbles on siting of technical centres and plants. Which development areas will get the plants, each with a thousand workers? Will prosperous Bristol have the technical centre? What's wrong with Newcastle? The debate rumbles on with the odd touch of hysteria, sudden swoops into farce, occasional excursions into fantasy.

Endless speeches and lobbying, even allocation of vast sums of money, are no substitute for policy. Yet to be decided are product lines and how they will be marketed. On these important topics both the National Enterprise Board and Inmos are strangely silent. There could be good reasons for remaining dumb. Commercial security, for example. Industry experts, however, remain sceptical that any organisation largely influenced by political considerations can be commercially successful.

News Briefs

by Mike Abbott

TV OR SCOPE

EXCELLENT for the engineer who likes to watch Magic Roundabout while appearing to work, is the oscilloscope designed for video monitoring applications, supplied by Gould Instruments Division to meet an order from the BBC.

The oscilloscope is a modified brighter version of the Gould Advance OS3300B with a BBC designed timebase module incorporating comprehensive video triggering facilities, which is being made by Gould under a manufacturing licence agreement from the BBC.

The new timebase generator allows the oscilloscope to be used for detailed line-by-line examination of 625-line television waveforms or to display a television picture. It accepts a standard level video signal, which may contain "Sound-in-Sync" signals and provides six different triggering modes: field 1, field 2, field 1 and 2 alternating, line repetitive, single line selectable by front panel switches (with the line number indicated on a 3 digit l.e.d. display) and line pairs in the range 16/329 to 22/335.

The triggering can be delayed continuously by up to 90 μ s via a multi-turn potentiometer, which allows the signal to be examined in detail.



The displayed video signal may be clamped or not, as required. When the unit is used to display a television picture, the triggering point selected may be observed as a "bright up line" on the picture, enabling the waveforms to be rapidly related to the picture. The changeover from waveform to picture is effected by a single front panel switch. The modified timebase retains its normal triggering facilities, so that the instrument may also be used as a general purpose single timebase oscilloscope.

FIR FILTERS

THE CTD (Charge Transfer Device) is now a commonplace device, which is at present, more frequently found performing the function of delay line—the most obvious application. However, it is probably in the field of application where the more interesting developments will take place with "bucket brigade devices". Suggestions include electronic "de-wow" and "de-flutter" circuits for tape replay systems, and speech compression machines for the recording of books for the blind.

The CTD has turned out to be very powerful in filter design, around which has evolved a completely new technique giving more filter power per square centimetre than any other.

An example of this is the Reticon R5602 CTD filter i.c. (claimed to have been the first commercially available i.c. of its kind). Previously

the only monolithic transversal filters for analogue signal processors were custom made large-scale integrated CCD's.

This transversal filter can do in one monolithic device the job of several boards full of components. The first four products in the R5602 family include low-pass and bandpass filters, each in a narrow and broadband version. The devices (also called Finite Impulse Response filters), are made using a 64 stage split electrode type bucket-brigade device architecture, utilising the fundamental metal-oxide-semiconductor structure as a capacitor. They use a new differential output sensing technique which offers such advantages as reduced insertion loss in the passband, simpler external circuitry and cancellation of common mode clock signals.



Reticon R5602: A family of 64 point Charge Transfer Device (CTD) Transversal Filters using the split electrode architecture. Pictured above is the narrow band low pass filter.

There are several unique features. First, they can be programmed (i.e. tuned), by simply varying the input clock frequency. Secondly, they have linear phase with no added device complexity which is essential when filtering waveforms where the information is contained in the shape of the signal (e.g. in geophysical, biomedical and transducer applications). Finally, the R5602 has a high transition, or roll-off, rate from passband to stopband that is typically greater than 200 dB/octave. These are extremely high values when compared with those of conventional multi-pole filters, and the sharp cut-off is particularly useful in rejecting close-in signals near a desired signal.

Typical applications are in generating single-sideband signals, where one sideband is rejected and the other passed, within very tight tolerances, or in data-acquisition systems, between the transducer and the analogue-to-digital converter, to band-limit the input signal without distortion.

The R5602 family comes in a 16 pin dual-in-line package with a usable sampling frequency range of 250Hz to 1MHz. Customised filters are easily and inexpensively achieved with a simple mask change.

Further information from Andy Longford, Herbert Sigma Limited, Spring Road, Letchworth, Herts.

COUNTDOWN

THE FOURTH *Intel Fair* is scheduled to take place on June 11, 1979, and will again be held at the Wembley Conference Centre.

There will be a series of seminars at elementary, intermediate and advanced levels, and an exhibition in which Intel, their distributors and customers will give demonstrations expected to reflect the state of the microcomputer art.

Rotterdam is the venue of the *Third International Symposium and Technical Exhibition of Electromagnetic Compatibility*, and the date is May 1-3, 1979. Organised by the Netherlands National Electrotechnical Committee of the IEC in co-operation with the Federal Institute of Technology, Zurich, the symposium will deal with the problems of interaction of electromagnetic energy with electronic and biological systems, and the immunity and compatibility of electronic systems regarding the electromagnetic environment. A total of 120 interesting papers will be presented, covering such subjects as ignition and gas discharge noise, and even the curious business of artificially triggered lightning.

Fee reductions for members of co-operating organisations, early registrants and students are envisaged. Contact: (Symposium) Dr T. Dvorak on (01) 326-211. Ext. 2790. (Exhibition) Mr R. E. Gerritsen on (070) 906-800.

Labex International '79 is an exhibition of laboratory diagnostic and medical instrumentation, and will be taking place at the National Exhibition Centre, Birmingham, during March 12-16. Details: 021-705 6707.

The same telephone number for details of *Electronics '79*; electronic components industry fair. This will take place November 20-23 at Olympia, London.

PE MICROPRINTER

PART 3

MARK SIMON



THE FINAL part in this series of articles describes a method of testing the system gradually. It also lists a few maintenance tips for using the printer.

TESTING THE INTERFACE BOARD

Before connecting the interface board to the switched supplies, check that the correct voltages are appearing on the correct wires, and that the switching sequence is as referred to in Part 2. Remember we have to pinch the 5V supply from the microcomputer system. Switch on power supplies and move the lever to the 5V only position. We can now check the CMOS logic.

With the REED I/P open circuit (logic 1), the result of switching on should be that the motor flip flop is reset. If the REED I/P is shorted to 0V, the result of switching on should be that the motor flip flop is set. Shorting the PRINT command (PC) I/P to 0V should also set the motor flip flop. If that part of the circuit works correctly we can move on to the pick up coil and amplifier. A sinewave oscillator set at around 800Hz with an amplitude of 0.6V p.p. should be connected to the pick-up coil input. This should be sufficient to produce a rectangular train of pulses at normal logic levels from the output of the 74C14 buffer. Remember that the circuit will not work if the MC14011 CP INAND gate is a B series or buffered part, MC14011BCP.

This pulse train should now be clocking the MC14013CP D Type flip flop. This can be checked by switching the REED input between 0V and open circuit. The Q output of the flip flop should follow this switching. The return of the Q out-

40 COLUMN, 5 × 7 DOT MATRIX, ELECTROSENSITIVE FOIL PRINTER.

put to zero should fire Monostable 2 which resets the motor flip flop. Monostable 1 should be triggered on the leading edge of each clock pulse. Set the variable resistor connected to Monostable 1 at mid-setting at this stage. The character generator circuit can now be tested. Switch the power supply switch to the fully on position. If REED is shorted to 0V, and pick-up pulses of some kind are being supplied, the character generator chip should be outputting the pulses required to print a question mark. This is because its data inputs should be held high by the pull up resistors on the I/P CMOS buffers. See Fig. 3.1. Check the output pulses carefully, for if transients are to cause any trouble, it is here that their effect will become apparent. If any disturbance is observed it may mean looking at wiring runs and, if not too painful, circuit layout. Different character outputs can be obtained at this stage by pulling different Data buffer inputs low.

The electrode drivers can be checked at this time, for although they are not yet connected, the output voltage will be developed across the 10k collector resistors on the BD189s.

To check the printer separately simply insert some metallized paper and supply 24V to the motor contacts. The print head should move back and forth and paper should advance.

THE PRINTER AND INTERFACE

With the printer and interface connected together proceed as follows:

With all data inputs at logic 1, briefly short \overline{PC} to 0V. The printer should start operation printing successive lines of question marks. The variable resistor connected to Monostable 1 can now be adjusted to give the required Print intensity.

If the printing is poor then investigate the current paths for the electrode currents—is there any resistance there? If the printing is erratic then there may be trouble caused by noise. If a scope is available look at the character generator outputs.

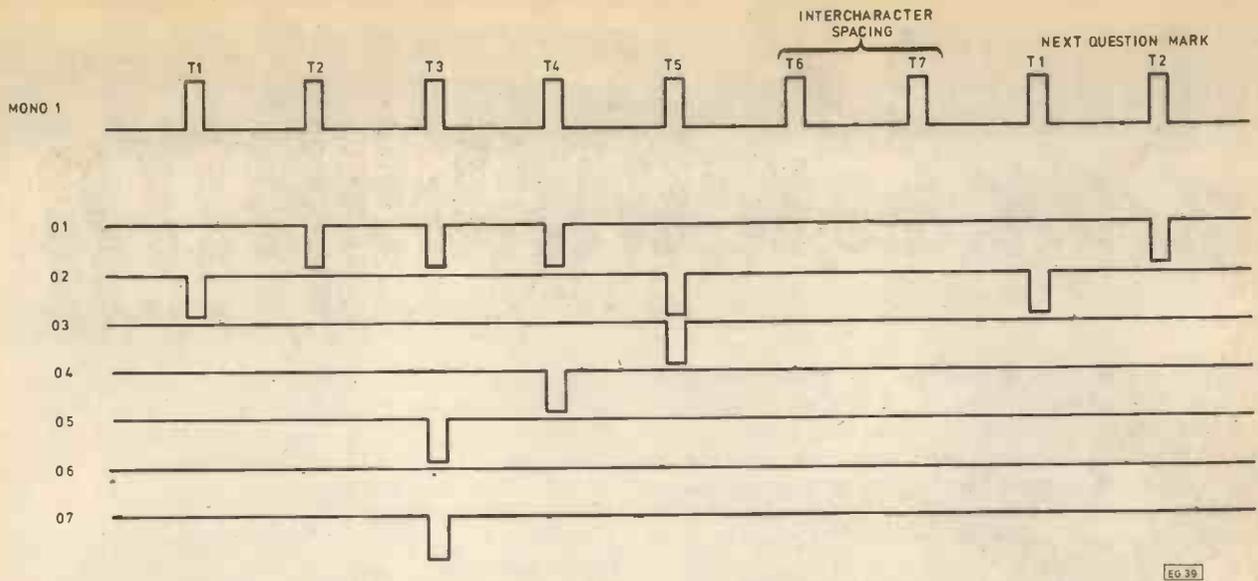


Fig. 3.1. Character generator chip O/P for all 1s I/Ps

THE COMPUTER TIE UP

Now we are ready to connect up to the Microcomputer system. Firstly it is worth loading PRINT into the microcomputer system and stepping through it to see if the output signals are being generated. It will be necessary to simulate DATA REQUEST with a switch at this stage.

If PRINT is being used alone its exit instruction (RET) should be changed to a HALT. Otherwise, on finishing, the PRINT routine the processor will RETURN to some unknown location and run amok.

Connect the printer system and switch on. As long as the PC is at logic 1 nothing should run.

Fill an area of RAM, say 10 locations with a character code, followed by an end of text character (FFH). Set HL to the address of the first character and "GO" from the beginning of PRINT.

The correct number of these characters should be printed, then the system should stop, ready for the next line. Now try inserting a carriage return (ODH) into the character string and repeating the procedure. This time when the printer hits carriage return it should stop printing until the next line, where the rest of the characters should be printed. If these tests work you should be able to write little test routines to fill areas of memory with ASCII characters then print them out.

Now the DUMP software can be loaded and run with PRINT (remember to change PRINT's exit instruction back to RET). It may be of interest to some constructors to step through parts of DUMP to see the number conversions taking place.

To save repeatedly loading the software it may be more convenient to have it "blown" into programmable read only memory. Although the software may have to be "re-originated", and the RAM addresses changed to suit your own microcomputer system.

MAINTENANCE

The prototype printer performed some fairly heavy test runs without any trouble. The manufacturer states that its useful life should be around 30 million lines. Below are listed a few maintenance pointers.

- (1) Don't operate the printer without paper or with paper that cannot be advanced.
- (2) After some time printing dust can accumulate in the bottom of the printer. This should be brushed out (gently).
- (3) If the printer scanning speed slows down, the scanning shaft should be lubricated with light machine oil.

That concludes this series of articles. I hope those of you who build this system will find its many diverse aspects of engineering as interesting as I did. Good luck. ★




Home Computers

...the Microprocessor Miracle!

PART TWO — R.W. COLES

WITHOUT any shadow of a doubt, the ultimate home computer peripheral is a floppy disc system. "Floppy discs" are thin flexible plastic discs coated with a magnetic material and permanently sealed inside a square protective envelope. The envelope has a central hole so that the disc can engage the drive, and further holes and slots for the read-write head and the sector marker holes. The disc in its envelope is inserted edgewise into the drive, and the gate closed. Now the fun begins! Loading a BASIC interpreter

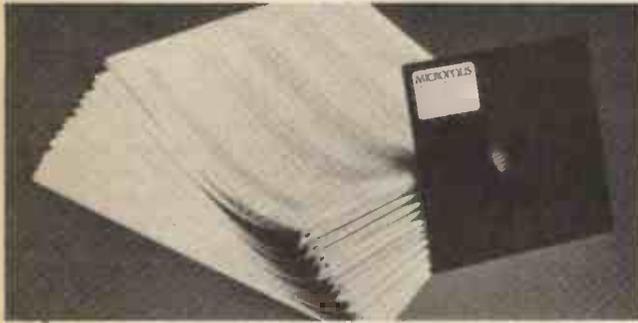

A typical floppy disc

from cassette takes many minutes, from disc it takes seconds. Finding a program or data file on tape is a tedious one-way search-and-rewind business; with a disc system you type the name and hey presto! it's in RAM already. Is your program too big for your RAM? With a disc system you can use overlays, so that only the currently active section of your program is in RAM at any time. When the next section is needed, it's loaded automatically in next to no time! Add to the above attributes, all the traditional advantages of magnetic storage media such as low cost, large capacity, reliability and transportable software, and you can see why the floppy disc reigns supreme in the home-computer-peripheral heirarchy. To add a disc drive or two to your



The Extel 950 floppy disc system

system, you will need a disc controller board, and these are widely available for S100 systems. The drives themselves are electro-mechanical devices, and they come in two basic sizes:

- (1) Standard-Floppies,
- and (2) Mini-Floppies.


A Standard Floppy disc drive takes 8in diameter discs which can each store over 200K bytes of data. A Mini-Floppy disc drive takes 5½in diameter discs which can each store about



The FD-8 floppy disc system. Available software includes a MINI-DOS routine

80K bytes of data. Variations on the theme allow double-density or double-sided recording, which increase the capacity still further so that it is unlikely that you will ever feel cramped for space.

Cost, of course, is the big problem. Even though floppy disc systems are known as low cost storage devices in comparison with their "hard-disc" cousins from the big-computer world, they still cost several hundred pounds per drive with the controller extra. With an S100 system you can upgrade gradually, starting with a single Mini-Floppy and controller. Even this basic facility opens the door to powerful software and a really effective home-computer system which can be used as a practical, problem solving tool.

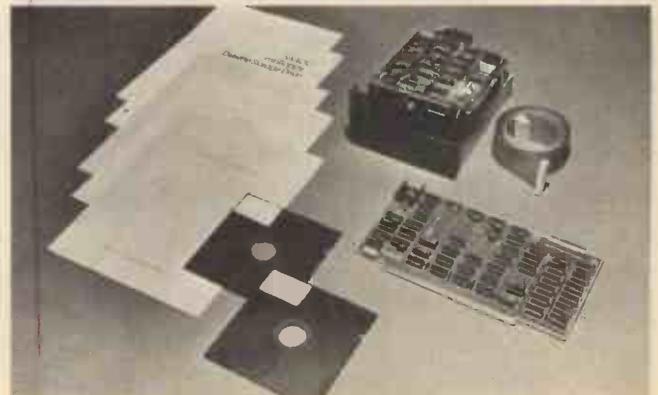

A complete floppy disc system for an S100 computer



The Micros 280 system

SOFTWARE

A microprocessor, even when connected up to external memory, a keyboard, a VDU and all the other necessary hardware bits and pieces, is really very dumb indeed until that extra "magic" ingredient, Software, is added. Without the software, you can hit any key you like and all you'll get is a sore finger. Press the reset button if you like, but alas, no friendly message will be flashed upon the VDU inviting you to communicate. Inside the microprocessor chip, the program counter will be running, looking in vain for a set of valid instructions which are not there.

Let's assume for a moment that we really do have a machine in this condition. What is the minimum software package that we need to help the system out of its misery? Well, first we need a keyboard input routine which checks for any keys pressed and loads the appropriate ASCII character into an area of RAM we can designate as an input buffer. Next we need a VDU driver routine which will take the contents of an area of RAM designated as an output buffer and send it in ASCII to the VDU hardware. So far so good. We can now type on the keyboard and see the result on the screen, but we still have a long way to go. To permit the microprocessor to do different things, in response to typed in commands, we need a command interpreter which will examine ASCII strings for a match with one of a set of commands it has been programmed to recognise. Useful commands might be:

- 1) ENTER ADDRESS
- 2) ENTER DATA (and increment address)
- 3) DISPLAY DATA (and increment address)
- 4) SET PROGRAM COUNTER
- 5) RUN PROGRAM
- 6) LOAD PROGRAM FROM TAPE
- 7) SAVE PROGRAM ON TAPE

This command interpreter could be designed to recognise a number, a single letter, or a complete string of characters for each command, depending on how sophisticated we wanted to make it. An important consideration is that we should be able to add extra commands at a later date should we so wish. Of course, commands like ENTER ADDRESS would be preceded or followed by a number, and these numbers will have to conform to a convention. A common format would be a four digit hexadecimal number for an address, but we

could use 16 bit binary, six digit octal or even five digit decimal numbers. It's up to us, but whatever number system we choose, we have to provide a routine to convert the ASCII characters from the keyboard (which occupy one byte per digit) into the packed binary which the microprocessor chip itself can deal with.

We could add all sorts of other bits and pieces, but let's stop there. The software package we have created is called a Monitor, and regardless of what other fancy software can be added, every system needs a monitor of some sort to get it started. Monitors are usually kept in ROM or PROM form, for obvious reasons, and it is this sort of software package that you have to rely on exclusively when you buy an "evaluation card" system. Using the Monitor on either an evaluation card or a home-computer, you can enter machine code programs in hexadecimal and then examine, alter, and run them. Unfortunately, writing machine code programs is a tedious business. The process of looking up the hexadecimal equivalents of MPU instructions such as ADD, LD A,B, OUT, and then keying these into the system with not a word of explanation for you to read when you come to examine the program next week or next year, is enough to put off even the keenest user!

We can escape from this tedium in one of three ways, made possible by yet more system software in the form of:

- (a) An Assembler package
- (b) A high level language Interpreter package
- (c) A high level language Compiler package

ASSEMBLERS

Machine code programming may be tedious, but it does have the advantage of a hardware intimacy which high level languages such as BASIC, lack. This intimacy makes



The MP-68 computer system is based upon the Motorola 6800 microprocessor

machine code programming particularly valuable where the objective is to write a program to interface with some quirky piece of hardware, a printer say, or where it is vital that a program be made as fast and as memory efficient as possible. To retain the advantages of machine code programming while removing much of the drudgery, you can add an Assembler to your system. An Assembler is a sizable software package which allows programs to be entered, not in hexadecimal, but as assembly language mnemonics, just as they are printed in the microprocessor manual. This means that the Z80 program sequence:

```
POP HL
LD A, H
RLCA
```

can be typed in just as you would write it down on your program sheet and not in the hexadecimal equivalent form:

```
E1
7C
07
```

which is more compact, but meaningless when you try to decipher it later. But this is only the start. Another problem of machine code programs is the specification of jump ad-



The AIM65 from Rockwell uses a 6500 microprocessor and includes both a 20 column printer and keyboard

dresses, for loops and subroutines for example, which has to be done in the form of an absolute value. This is not too bad until you need to insert one extra line into your program, whereupon all the addresses after the new instruction are changed, and redefining all the JSR and JMP destinations can become a task of nightmarish proportions! To cure this problem, assemblers allow the programmer to use named addresses (called symbolic addresses) which are assigned absolute values only when the input code is processed by the assembler software. When typing in your input code (called source code) in mnemonic form, you give each destination a name, and when you want to go to the destination you simply type the jump instruction followed by the name, like this:


```
FRED: LD A, C
      LD C, A
      JP FRED
```

When the assembler is entered (via the monitor) it makes a first pass through your source code to build up a symbol table which assigns each name an absolute address. On the second pass (Most assemblers make two passes through the

source code) it substitutes the absolute address value from its symbol table wherever a reference is made to it. To add extra instructions you can now type them into your source code using a software package called an Editor, and then the assembler can be run again to process the new instructions and sort out the address changes.

INTERPRETERS

Even assembly language programming can be a drag for some applications. Suppose you want to calculate your chequebook balance, or plot a graph on the VDU, the last thing you are going to want to worry about is the precise way in which the system carries out the arithmetic and controls the peripherals at its disposal. After all you don't have to worry about the way the machine operates when you use a scientific calculator—enter a number and press the \sqrt{X} key, and the answer is immediately displayed. Within the confines of the calculator chip a lengthy machine code program did the hard work, but we can be blissfully unaware of its presence. A similar technique can be used with home computers. With our Monitor program, discussed earlier, we were allowed to type in commands such as ENTER DATA which invoked lengthy machine code routines.

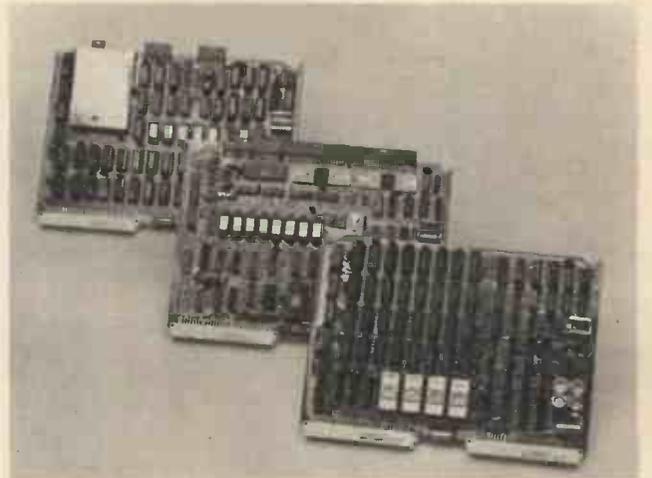

The SGS-ATES Euro card system is based upon the Z80 microprocessor

It is a fairly short step from this to the ability to enter whole programs using English language statements which have the effect of selecting machine code routines and stringing them together in a way transparent to the user, via a sort of super Command Interpreter. Home computer BASIC operates in this way and allows programs to be written in a high level form using selected English statements and a set of ASCII punctuation characters with defined significance. The BASIC language interpreter must reside in the system while programs are entered or run, and this means that a sizable memory is required to hold both the interpreter and the user program. The amount of memory required varies depending on the microprocessor used and the details of the particular version of BASIC to be loaded. At one end of the scale is a TINY BASIC for the 8080 which fits into only 2K bytes of memory. At the other end is Zilog disc extended BASIC which requires nearly 45K bytes! Between these extremes lie other variations and permutations, and this means that any intending home computer purchaser cannot simply say "Well, it runs BASIC so it must be a powerful system." BASICs differ in their available statements (Such as INPUT, GOTO, PRINT,) in their available functions (Such as SIN, EXP, SQR) and in their arithmetic precision. TINY BASIC is

restricted to the use of integer numbers in the range -32768 to +32767, while most BASICs of 8K bytes or more can give at least an eight digit decimal arithmetic precision and have a wide dynamic range due to the use of scientific number notation. The words to look for in the specification are:

"Integer only" (Like TINY BASIC)

"Floating Point" (Full arithmetic capability)

BASIC DETAILS

BASIC is a problem orientated language rather than a machine orientated language, and in theory BASIC programs written for one machine should run just as well on any other. In fact this is not strictly true because there are so many versions of BASIC around and these are not always compatible. Nevertheless, you only need to learn BASIC once, any differences between individual versions can be assimilated very quickly when the need arises.

A program in BASIC consists of a list of numbered lines or statements. For example:

```
5  REM *** CHEQUE BALANCE ***
10 PRINT "ENTER OLD BALANCE"
20 INPUT B
30 PRINT "ENTER CHEQUE AMOUNT"
40 INPUT A
50 LET B=B-A
60 PRINT "NEW BALANCE IS" B
70 PRINT "ANY MORE CHEQUES?"
80 INPUT C $
90 IF C $="YES" THEN 30
100 END
```

Once a program has been typed in, it can be run by typing RUN. Changes to the program can be made by retyping a line or by inserting new lines between old lines, a process made easier by the numbering of lines in increments of ten to start with! A line can be erased by typing in its line number followed by RETURN.

If a statement is typed in without a line number, it is executed as soon as RETURN is pressed. This makes a BASIC machine work like a calculator for simple arithmetic calculations, e.g. typing in

```
PRINT SQR 14.7 (RETURN)
```

results in the square root of 14.7 being displayed on the VDU immediately. Another use of the immediate mode is in programme debugging. If a line in your program is giving trouble, entering the line without a line number will allow immediate execution so that you can locate the problem easily. Before a line of code is interpreted it is checked for correct syntax. If you have made any mistakes, such as having unbalanced pairs of brackets in an expression, an error message will normally be displayed.

BASIC, then, is an ideal language for beginners (After all, BASIC does stand for Beginners All Purpose Symbolic Instruction Code!) but its capabilities should not be underestimated. Many professional programs have been written in BASIC, and you may progress a long way in the field of computer science before feeling the need for something better!

BASIC PROBLEMS

The problems of BASIC stem mainly from the fact that it is an interpreted language. One problem is that the Interpreter program and the user program both have to be in memory at the same time so that a lot of memory space is needed. This problem is perhaps not so valid in these days of

cheap and plentiful semiconductor memory, as it used to be in the days of expensive core stores. Perhaps the most serious problem with BASIC, and with any other interpretive language come to that, is its speed. The program is not represented by a long list of ready to run machine code instructions in memory, but as a series of ASCII strings as they were typed in. To carry out the operations intended by the programmer, the Interpreter (A machine code program) has to analyse each line and then call other machine code routines to do the necessary donkey work. As you can imagine therefore, the BASIC language is several times slower in operation than some alternative techniques, particularly assembly language for example, where the mnemonic strings typed by the programmer are converted into a machine language program before the program is run. Fortunately, the speed of BASIC is not a limiting factor for most home computer applications, and its ease of use more than makes up for its shortcomings in the speed department!

COMPILERS

A Compiler is a high level language software package which is used in a similar way to the Assembler package mentioned earlier. Unlike an Interpreter, the Compiler software does not have to be available in the system at run



The SOL terminal computer from Processor Technology is an S100 compatible system using the 8080 microprocessor time, rather it is used to process the high level language statements in the source program to produce a new machine code version of the program which can then be run by itself. A typical compiled high level language is FORTRAN (FORmula TRANslator) which is widely used for scientific applications. Programming in FORTRAN goes like this:

First, the high level program statements are typed into the system. These statements look somewhat similar to their BASIC counterparts.

Next, the Compiler software analyses the user program and produces an equivalent machine code program called the object program.

Finally, the object code can be loaded into memory and executed, whenever it is required.

This is the same sort of sequence as is used with an Assembler, except that in the assembly language case the source program starts out in mnemonic code and the machine code object program has a one for one relationship in terms of numbers of instructions. Compilers are a lot more sophisticated than Assemblers because they are able to convert compact high level language statements into much longer object code routines which do not of course have a one to one relationship with the source program.

DEBUG

Debugging compiled programs is more difficult than is the case with an interpretive language like BASIC. Every time a bug is found, the source program has to be modified and the Compiler re-run before the effect of the change can be tried out. For this reason it is better to cut your programming teeth on BASIC rather than FORTRAN!

The advantages of a compiled language are not hard to find:

- 1) Because the Compiler need not be resident in the system at run time, memory space is used more efficiently.
- 2) Because no analysis is done at run time, compiled languages usually operate several times faster than interpreted languages.
- 3) The object code is all that has to be supplied to a second user of the program. This makes valuable programs more secure.

OTHER LANGUAGES

Of course, FORTRAN is not the only language that is compiled, and although it is in widespread use elsewhere, it is probably not going to become very popular on home computer systems, where BASIC still reigns supreme. You can even get hold of a BASIC compiler, but this is aimed more at



The Horizon microcomputer has dual mini floppy drives and is available with a Disc Operating system

the industrial software market than the home-computer scene. A more recent and useful language for home-computer systems is PASCAL which actually uses interpreter and compiler techniques to produce the final object code. With PASCAL the Compiler turns source statements into a special low level code called P-code, the P-code is then run interpretively on the host machine. The Interpreter required in this case is quite small, but it does have to be resident at run time, unlike the PASCAL compiler. The advantage of this technique is that the Compiler itself does not have to be rewritten for every new microprocessor chip or main-frame, only the small interpreter need be different in each case. This means that programs written in PASCAL can be run on any other machine with a P-code interpreter without the need for re-compilation. Apart from its operational advantages, PASCAL is also hailed by some computer scientists as a great step forward because it encourages better, "Structured", programming in the users. Some home computer systems are already using PASCAL, and we may see more of it in the future.


DISC SOFTWARE

Once a floppy disc system has been added to a home computer system many enhanced software features are possible. Assemblers, Interpreters and Compilers can certainly be disc based, but perhaps the most powerful feature available to the lucky disc user is a software package known

as a Disc Operating System or DOS for short. A DOS is a sort of super disc based monitor with a menu of powerful commands such as COPY (disc) MOVE (file) DUMP (file to an output device) SET (baud rate etc.) and many others which can be invoked by name from the keyboard. Each of these powerful commands is stored on the disc as a ready-to-run program. Typing in the command name is sufficient to load the command program from disc and set it running. A ROM resident monitor or operating system which featured all these commands would be much too large and therefore impractical.

The best example of a home computer DOS is probably CP/M from Digital Research which runs on 8080 or Z80 systems and features an Assembler, Editor, and hexadecimal Debug package as standard, with lots of other bolt-on goodies also available from the same source.

The aim of this whistle-stop tour around home computer hardware and software has been to provide all P.E. readers with a basic grounding in home computer terminology and practice. Home computers are not a passing fad, they are here to stay, so why not go along to your local computer store and try one out? One word of warning though, if you get bitten by the programming bug, you may never be the same again.

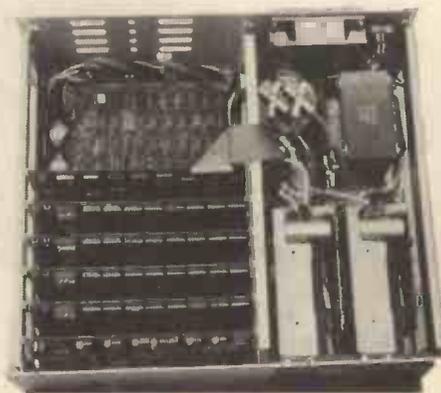

An internal view of the Horizon


CHECK-LIST

Before rushing out to buy a home-computer system, remember that it is a big investment. The following check-list may help in the evaluation of any particular system on offer.

- (1) Does it feature a high level language?
- (2) Is the language a "tiny" language (suitable for games but not maths) or is it a "standard" or "extended" language (suitable for most purposes; but examine available statements and arithmetic precision).
- (3) Does the system come complete with ACSII keyboard and VDU display or TV modulator?
- (4) How many characters can the VDU display at once, and can it handle graphics or colour?
- (5) How much RAM has it, and is this *easily* expandable?
- (6) Has it got software in ROM or must it be loaded into RAM? (In which case, more RAM is needed.)
- (7) Is it well supported by commercial software? (Interpreters, assemblers, maths packages, business programs, games, etc.).
- (8) Can you expand it by adding: A printer, extra cassette unit, floppy discs, homebrew hardware, etc?
- (9) Is it well made and built to last?
- (10) Is a service network available?

From Science of Cambridge: the new MK 14. Simplest, most advanced, most flexible microcomputer – in kit form.

**only
£39.95
(+8% VAT)**

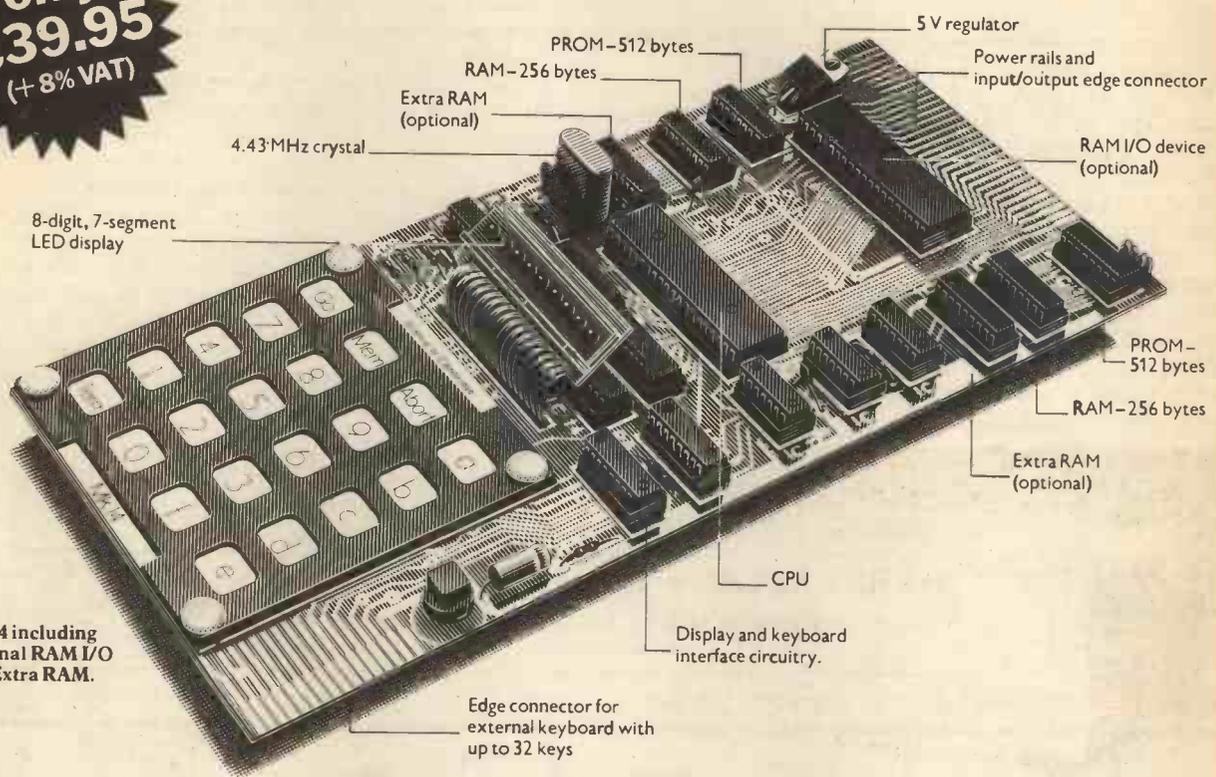

MK 14 including optional RAM I/O and Extra RAM.

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte pre-programmed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of user-written programs through the hexadecimal keyboard.

Yet in kit form, the MK 14 costs only £39.95 (+£3.20 VAT, and p&p).

More memory – and peripherals!

- Optional extras include:
1. Extra RAM – 256 bytes.
 2. 16-line RAM I/O device (allowed for on the PCB) giving further 128 bytes of RAM.
 3. Low-cost cassette interface module – which means you can use ordinary tape cassettes/recorder for storage of data and programs.
 4. Revised monitor, to get the most from the cassette interface module. It consists of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculations and single step, and single-operation data entry.
 5. PROM programmer and blank PROMs to set up your own pre-programmed dedicated applications.
- All are available now to owners of MK 14.

A valuable tool – and a training aid

As a computer, it handles operations of all types – from complex games to digital alarm clock functioning, from basic maths to a pulse delay chain. Programs are in the Manual, together with instructions for creating your own genuinely valuable programs. And, of course, it's a superb education and training aid – providing an ideal introduction to computer technology.

SPECIFICATIONS

- Hexadecimal keyboard • 8-digit, 7-segment LED display • 8 x 512 PROM, containing monitor program and interface instructions
- 256 bytes of RAM • 4 MHz crystal • 5 V regulator • Single 8 V power supply • Space available for extra 256-byte RAM and 16 port I/O • Edge connector access to all data lines and I/O ports

Free Manual

Every MK 14 kit includes a Manual which deals with procedures from soldering techniques to interfacing with complex external equipment. It includes 20 sample programs including math routines (square root, etc), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Please send me the following, plus details of other peripherals:

MK 14 Standard Microcomputer Kit " £43.55 (inc 40p p&p.)

Extra RAM " £3.88 (inc p&p.)

RAM I/O device " £8.42 (inc p&p.)

I enclose cheque/money order/PO for £_____ (indicate total amount.)


Name _____

Address (please print) _____

PE3 Allow 21 days for delivery.

Science of Cambridge

SUPERSOUND 13 HI-FI MONO AMPLIFIER

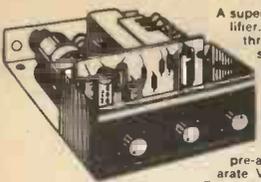

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7 1/2in deep. AC 200/250V.

PRICE £16-00 P. & P. £1-20.

HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Discos, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic, or guitar etc.). Input 3, 200mV into 1 meg, suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200-240 volts. Size approx 12 1/2in wide x 5in high x 7 1/2in deep.

Special introductory price £28-00 + £2-50 carriage and packing

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2in x 14 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £8-40 each + P. & P. (one 90p, two £1-10). Now available in either 8in round version or 4 1/2 x 8 1/2in rectangular. 10 watts R.M.S. 60Hz-20kHz £5-25 + P. & P. (one 85p, two 75p.).

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State F.M. A.M. Stereo Tuner. Covering M.W. A.M. 540-1605kHz V.H.F. F.M. 88-108MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max. o/p Voltage 600mV R.M.S. into 20K Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2in wide x 4in high x 9 1/2in deep approx.

Limited number only at £28-00 + £1-50 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + S.A.E. (free with parts). All parts sold separately. ONLY £15-50 P. & P. £1-40. Also available ready built and tested £20-00 P. & P. £1-40.

STEREO MAGNETIC PRE-AMP Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20kHz. Input impedance 47K. Size 1 1/2in x 2 1/2in x 5 1/2in. H. £2-60 + 20p. P. & P.

Mullard LP1159 RF-IF module 470 kHz £2-25 + P. & P. 20p. Full specification and connection details supplied. Pyle VHF FM Tuner Head covering 88-108 MHz 10-7 MHz I.F. output. 7-8V + earth. Supplied pre-aligned, with full circuit diagram with precision-ganged F.M. gang and 323PF + 323PF A.M. Tuning gang only £3-15 + P. & P. 35p.

SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated leatherette. Size 7 1/2" x 9 1/2" x 4" O approx. Fully guaranteed. Bargain price of only £10-00 + £1-30 p&p.

MODEL FL4

Few only similar to above, but battery operation only. Twin speakers, Four wave bands, MW, FM and two VHF bands for reception of aircraft and some public services. ONLY £9-50 + £1-30 p&p.

MODEL MULTI 5

Specification as Model FL4 but with additional SW band. Twin speakers. ONLY £11-00 + £1-30 p&p.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked. Smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification, Power output 14 watts R.M.S. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 1 M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 15dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A.

Overall size 12in wide x 8in deep x 2 1/2in high. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S A E

AMPLIFIER KIT £14-50 P. & P. 80p

POWER PACK KIT £6-00 P. & P. 95p

CABINET £6-00 P. & P. 95p

SPECIAL OFFER—only £25-00 if all 3 items ordered at one time plus £1-25 P. & P.

Full after sales service. Also available ready built and tested £31-25 P. & P. £1-50

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built-in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel. Size approx. 9in x 2 1/2in x 1in max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2-way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10-00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £2-00 + 40p P. & P. If required. Full connection details supplied.

STEREO DECODER

SIZE 2" x 3" x 1/2" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6-00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 MERTON HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985


A few minutes from South Wimbledon Tube Station

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HANIMEX Electronic LED Alarm Clock

Same as ET1 offer Thousands sold

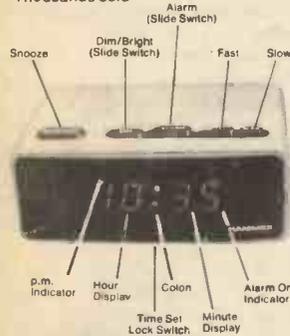

Feature and Specification

- ★ Hour/minute display
- ★ Large LED display with p.m. and alarm on indicator
- ★ 24 Hours alarm with on/off control
- ★ Display flashing for power loss indication
- ★ Repeatable 9-minute snooze
- ★ Display bright/dim modes control

Size 5.15 x 3.93 x 2.36 (131mm x 100mm x 60mm). Weight 1.43 lbs (0.65 kg).

Guaranteed same day despatch

£8.65

Telephone Special 24-hour phone service
Credit-card customers are welcome to buy by phone - simply phone 01-723 4753 with your credit-card number to place your order.

LADIES LCD

Only 25 x 20 mm and 6 mm thick. 5 function: hours, mins, secs, day, date, + back light and auto cal. Elegant metal bracelet in silver or gold. State preference.

£10.95

Guaranteed same day despatch

All products carry full 12 months guarantee. Please add 30p p&p with all orders. All prices include VAT.

Shops open 9.30 to 6.00 daily.

Trade enquiries welcome. Delivery: One week. Except where same day delivery is stated.

5 FUNCTION LCD

Hours, mins, secs, month, date, auto calendar, back-light, quality metal bracelet.

£7.65

Guaranteed same day despatch

Very slim, only 6mm thick.

ALARM CHRONOGRAPH WITH DUAL TIME ZONE FACILITY

- Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication.
- Perpetual calendar, day, date, month and year.
- 24 hour alarm with on/off indication.
- 1/10 second chronograph measuring net, lap and first and second place times.
- Dual time zone facility. Night light.

£29.95

THOUSANDS SOLD 11 FUNCTION SLIM CHRONO 6 digit 11 functions

- Hours, mins, secs.
 - Day, date, day of week.
 - 1/100, 1/10, secs 10 x secs, mins.
 - Split and lap modes.
 - Back light, auto calendar.
 - Only 8 mm thick.
- This same watch is being sold for £22.00 in newspaper and magazine special offer ads.

Metac Price £12.65

Guaranteed same day despatch

PLEASE NOTE

All our products carry full money back 10-day reassurance.

Watches are despatched by FIRST-CLASS POST. They are fitted with new batteries, and include guarantee and instructions.

Battery fitting service is available at our shops for no extra charge. We stock most watch batteries and this service is available to all. Metac have been selling electronic watches probably longer than anyone else in the UK. We take care of your watch not just this year but next year and the years after that.

METAC Electronics & Time Centre

67 HIGH STREET
DAVENTRY, NORTHANTS
Tel. (032 72) 76545

327 EDGWARE ROAD
LONDON W2
Tel. (01) 723 4753

Barclay & Access welcome

Phone or Send Card Number with order



News Briefs

by Mike Abbott

WALKY TALKY TERMINAL

INSTANTANEOUS access to computer information from a pocket-sized portable radio is provided by the new RDX 100 portable Data Terminal developed by Motorola. The RDX is a lightweight high-powered FM transmitter/receiver, fully self-contained, currently designed to be compatible with the IBM 360/370 Information Display System for data entry, retrieval and update applications. The radio has been developed for both indoor and outdoor use, requiring no telephone lines, interconnecting cables or external power source.

The RDX Data Terminal System comprises the RDX 100 Portable Terminal, a duplex FM radio base station and an RDX 1100 Control Unit, which can handle up to 32 portable terminals. Two-way, real time communications between the portable terminal and the computer is accomplished by an FM radio link between the terminal and the base station, and a synchronised landline link between the RDX 1100 Control Unit and the computer.

The radio operates in the UHF band, sending and receiving information from the base station at 80 characters a second, while the RDX 1100 Control Unit communicates with the IBM computer system at standard transfer rates from 1200 to 9600 bits per second. Because of its versatility, Motorola expects its RDX system to find a wide spread of applications, such as Freight Traffic Management, Stock Control, Materials Handling and Load Distribution Management.



One reason for its versatility is the optional detachable, solid state light pen powered from the portable terminal. Ideal for data entry applications, the RDX Light Pen permits very rapid and accurate bi-directional entry of bar-coded data. Utilising Code 39 (alphanumeric bar code), product information such as item, location, price, data and other descriptive information can be read by the RDX. Because this light pen is fully alphanumeric, existing product nomenclature can remain unchanged, eliminating the need to modify existing (or to develop new) product coding systems.

The system is expected to become available in the UK soon.

FLOPPY SADDLE FOR YOUR PET

ATWIN mini floppy disk system designed to preserve the integrated package approach adopted by Commodore for their Pet personal computer, has been released by Midland Micronics Ltd. of Solihull.

Pictured below, the M.M.3 floppy disk system is seen mounted saddle style over Pet's VDU to give data access nearly 1,000 times faster than by the internal cassette system.



Connection is via the Memory Expansion Socket, but still allows RAM expansion, and the additional instruction set for addressing the disk from software or keyboard is held in a PROM supplied with the system.

The disk controller itself uses a microprocessor, permitting self test operations, and the mini diskette media can be flipped for recording on both sides.

PRINTER

ANOTHER peripheral for Pet is a low cost business-quality printer which interfaces directly and is now available from GR Electronics Ltd. of Newport, Gwent. Based on the IBM 3982 "Golfball" unit, it gives full ASCII facilities with the ability to change typefaces and fonts to suit specific applications.

The Petprint 3982 printer will copy letters, invoices, program listings, etc. in caps and lower case either as set up on the computer's VDU screen or input through the cassette unit. Printing speed is 15 char/sec and line length 130 characters, with a 10 char/in pitch which may be modified to 12 pitch if required. The printer is driven from the Pet's user port (not the IEEE interface) and its operation is controlled by a machine code program supplied on cassette. This gives the user flexibility in code conversion and timing as well as carriage return, line feed, tab and backspace functions.

When loaded into the Pet, the printer program occupies less than $\frac{1}{4}$ K of store and will not normally be affected by loading of further information through the cassette unit. Routines included in BASIC are for listing of Peek/Poke characters, solenoid codes and characters actually printed. A further facility is a step/print function which allows "mapping" of other printing elements.

The printers themselves are "second-user" heavy-duty units, regularly maintained during their initial service life as satellite printers in a large distributed system. They have been reconditioned by an IBM specialist, from whom service and repair facilities will also be available. The price with fitted interface and software cassette is £475.

OBITUARY

IT IS with regret that we announce the death of John Miller-Kirkpatrick at the age of 31. A man with great ability, he successfully designed and marketed the Scruppi Microcomputer system until his recent illness. We offer our sympathy to his family and friends.

CONSTANT CURRENT SOURCES

D.F. BOWERS B.Sc.

IN THE field of analogue circuit design, it is often necessary to generate constant electrical currents. One example of this is capacitors being charged with constant currents to produce linear ramp waveforms. Constant current (dynamic) loading improves the voltage gain of common emitter transistor stages and the linearity of common collector ones. Constant currents can compensate for the internal resistance of Zener diodes, and in conjunction with resistor "ladders" can produce accurate programmed voltage drops.

Modern d.c. amplifiers make extensive use of constant-current biasing, particularly in the input stages where this form of biasing improves the common-mode and supply line rejection ratio. Constant current sources also find more mundane applications such as nickel-cadmium battery charging.

Before looking into methods of achieving constant currents, it is informative to examine the necessary design criteria.

WHAT IS A CONSTANT CURRENT SOURCE?

Fig. 1a shows the block diagram of a current source. The current I is fixed and is shown flowing in the conventional (positive to negative) direction. Fig. 1b shows two commonly used symbols for constant current sources, in both cases the arrow indicates the direction of conventional current flow.

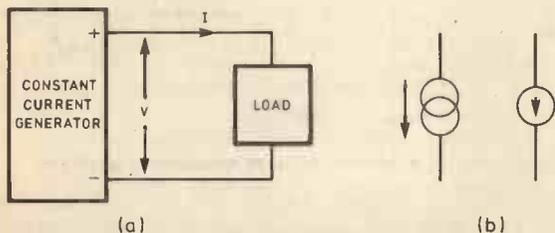


Fig. 1a. Block diagram of a current source
Fig. 1b. Constant current generator symbols

As with all black-box devices, we can specify the output of Fig. 1a with two parameters, voltage and current. The current, of course, is fixed and for this to be true the voltage must therefore be dependent on the load resistance,

$$i.e. V = IR_L \text{ where } V \text{ is output voltage}$$

$$I \text{ is the constant current}$$

$$R_L \text{ is the effective resistance}$$

$$\text{of the load at that current}$$

To ensure that is the case, the output impedance must in theory be infinite and with no load the output voltage should also be infinite. In practice, of course, neither of these parameters can be perfect, and figures for internal impedance and maximum output voltage are quite often used to specify the performance of a particular circuit. Another method is to specify a so-called output compliance, where the current is guaranteed to stay within a certain tolerance over a given range of output voltages. For example, a current generator of $10\text{mA} \pm 1$ per cent working over a 10V range would require an output impedance of greater than 50k.

DESIGNING CONSTANT CURRENT SOURCES

Unfortunately, constant currents are not quite as easy to generate as constant voltages, since devices such as constant current batteries do not exist. One way of getting round this is to use a large resistor in series with a voltage source (Fig. 2).

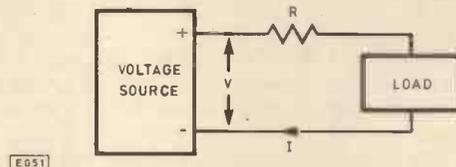


Fig. 2. Simple current generator

To satisfy our $10\text{mA} \pm 1$ per cent over a 10V range, R would need to be 50k, but V would have to be 500 volts. The circuit would also waste a minimum of 5 watts of power, only 100mW of which would ever be used in the load. Clearly this is a rather impractical solution.

TRANSISTOR SOURCES

The bipolar transistor when connected in a common emitter configuration acts as a type of current generator. In theory, for a given base current the collector current will be constant, the relationship between the two currents being β , the current gain. The value of β (like all transistor parameters) has the unfortunate habit of changing with temperature variations, so a little complication is necessary in a practical current source. Fig. 3 shows a current source of the type often used for biasing Zener

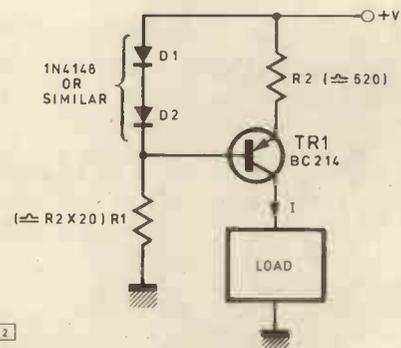


Fig. 3. Transistor current source

diodes (for example). Diodes D1 and D2 apply a voltage fixed at about -1.3 volts to the base of TR1. After the V_{be} of the transistor has been subtracted, around 0.65 volts will be developed across R_2 causing a current of $0.65/R$ amps to flow through the load, because of the transistor gain, and hence we have a constant current source, easily adjustable by changing R_2 . The lower voltage limit is the negative supply voltage, and the upper limit is set by the voltage drop across R_2 plus the saturation voltage of TR1. Note that this circuit can also provide negative current flow (current sinking) by using a $n.p.n.$ transistor and revers-

ing all polarities. The forward diode voltage drop has a temperature coefficient of $-2\text{mV}/\text{degree centigrade}$ which causes some drift of current with temperature change; applying a more accurate reference to the base of TR1 does not really help because a similar drift also applies to the emitter voltage of TR1. One method of alleviating this problem is to replace D1 and D2 by a forward biased gallium arsenide-phosphide i.e.d. The i.e.d. has an almost equal ($-2\text{mV}/\text{degree centigrade}$) temperature drift to the V_{be} of TR1, but around a volt extra forward voltage drop, producing a nearly constant 1 volt drop across R2.

For more accurate work, certain other factors must be taken into account. In particular, the collector impedance of a bipolar transistor is not all that high, usually around 100k for large signals, and also the emitter resistance of the transistor cannot be ignored. Additionally, a parameter known as the reverse transfer voltage ratio causes modulation of the effective base width (emitter resistance); all of these effects combine to reduce the output voltage compliance, and are extremely difficult to compensate for. To produce accurate current sources, it is necessary to make the circuitry independent of these parameters.

USING OPERATIONAL AMPLIFIERS

The precision current sink shown in Fig. 4 uses an operational amplifier to "design out" the awkward transistor parameters. As with all operational amplifier feedback circuits, stabilisation is achieved when the operational amplifier inputs are at equal potential. Thus the voltage V_{ref} must be impressed upon R. This

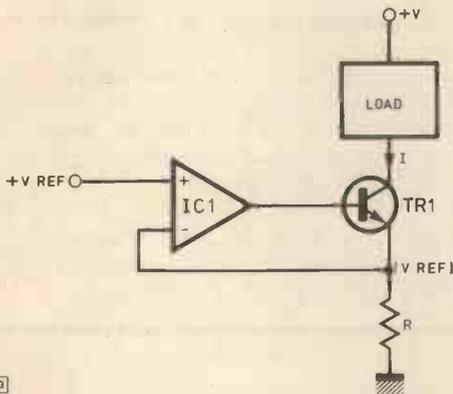


Fig. 4. Precision current sink using an op amp

causes an emitter current of V_{ref}/R to flow, and neglecting TR1 base current all this must flow through the load, producing a constant current (provided V_{ref} is constant). V_{ref} which should be kept quite low ($\approx 1\text{V}$) to keep the voltage compliance range as high as possible, could be derived from a Zener diode or other reference source. Circuits of this type are often called transconductance amplifiers, since they act as voltage/current amplifiers with a gain of $1/R$ amps/volt.

Two problems can arise with the circuit of Fig. 4. Firstly, a little of the current through R will actually flow into the op amp inverting input. If the current I is high, this will usually be of no consequence, but for low currents the operational amplifier should be an FET input or superbeta type. A certain portion of the emitter current also comes via TR1 base, and this constitutes an error (1 per cent with a transistor gain of 100) since the base current does not flow through the load. Replacing TR1 with a Darlington greatly reduces the error, and if the Darlington pair has an FET for its first transistor, the error will be almost zero.

Note that despite the extra transistor, operational amplifiers compensated for unity gain (such as the 741) will usually be stable in this configuration, since no extra loop gain is introduced.

BIPOLAR TRANSCONDUCTANCE AMPLIFIERS

Although the circuit of Fig. 4 can be adapted to source current as well as sink it (using a *p.n.p.* transistor for TR1 and a negative V_{ref}) it is sometimes necessary to accommodate both polarities of V_{ref} (and hence output current) with a single circuit. Rather complex versions of Fig. 4 can satisfy this requirement, but for low currents easier solutions are available. Of course, if the load is fully floating, the fact that the current through the feedback path of an operational amplifier can be kept essentially constant can be used (Fig. 5). This is often made use of in

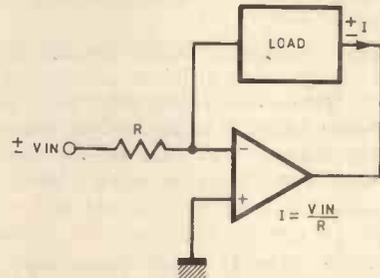


Fig. 5. Simple feedback current generator

integrator circuits (where the load is just a capacitor) but if the load is not fully floating, an alternative solution must be found.

The basic bipolar current generator (transconductance amplifier) shown in Fig. 6 is formed from a single operational amplifier. If the error current is very small (i.e. $R_3 + R_4$ very

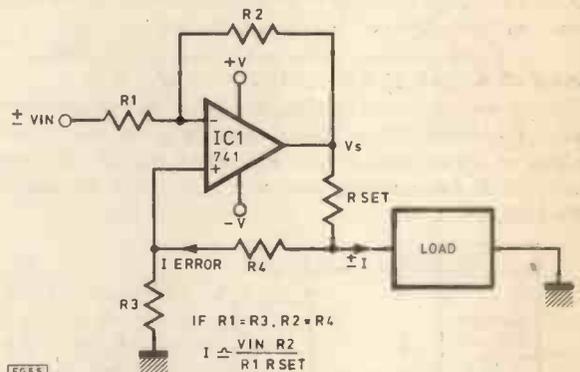


Fig. 6. A bipolar transconductance amplifier

large) then a constant current will flow through the load provided a constant voltage drop can be maintained across R_{set} . If $R_1 = R_3$ and $R_2 = R_4$, then any voltage at the output will be fed back to the non-inverting input in the correct proportion to ensure this condition, and the output current will be $V_{in}/R_{set} \times R_2/R_1$, which can be easily adjusted with R_{set} . This holds true for output voltages less than $\pm(V_{sat} - I_{out} R_{set})$ where V_{sat} is the maximum output swing of the operational amplifier. The highest value of I_{out} is naturally limited to the maximum


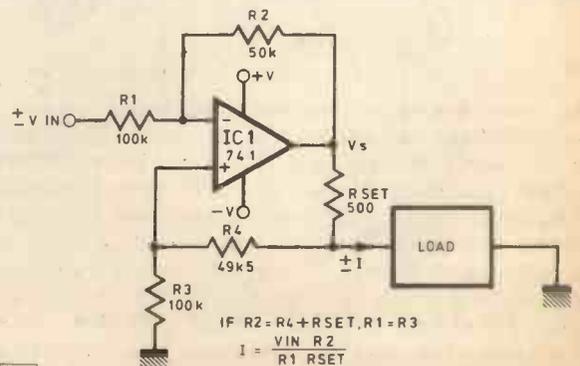


Fig. 7. An improved transconductance amplifier

operational amplifier output current. If the Error current is large enough to cause problems, the circuit of Fig. 7 can be used. In this circuit, the gain is adjusted to compensate for the Error current and for the highest accuracy very close tolerance resistors should be used. Adjustment of this circuit is not easy, since all resistor values are interrelated. The values shown are for a gain of 1mA/volt. Note that the load need not necessarily be earthed, but can be connected to any potential that maintains V_s within the operational amplifier voltage swing limit.

OPERATIONAL TRANSCONDUCTANCE AMPLIFIERS

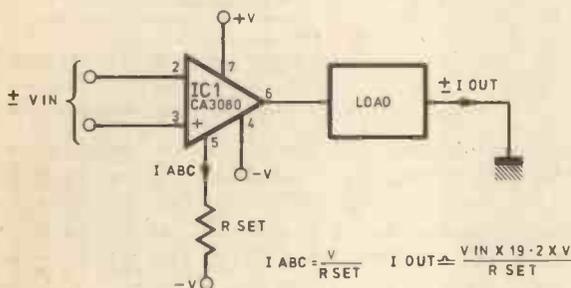Another way of obtaining a bipolar constant current source is to use an operational transconductance amplifier such as the CA3080 (Fig. 8). This device is designed to give a current output (up to 500µA) from a voltage input. The gain is given by $\Delta V_{in} \times g_m$ amps/volt where ΔV_{in} is the voltage between the input terminals and $g_m \approx 19.2 \times I_{abc}$ for the CA3080.




EG 57 Fig. 8. An operational transconductance amplifier

Other types of current amplifier such as voltage current transactors (VCTs) have been designed, but their application is not usually appropriate to the design of simple current generators, and in any case the latter are not yet commercially available.

FETs AS CURRENT SOURCES

If after all this you are puzzled as to why some enterprising manufacturer has not brought out some simple current generator devices (akin to Zener diodes) then you will be pleased to hear that Siliconix market a range of two terminal devices, often referred to as "constant current diodes".

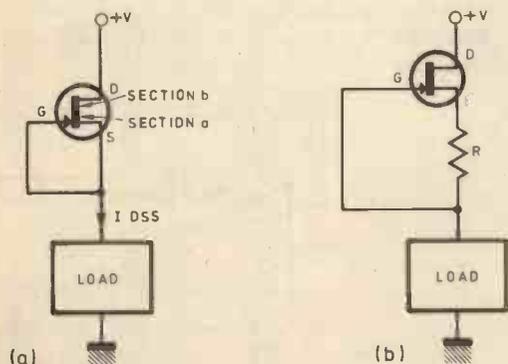Although ultra high precision cannot be achieved with these devices, they make very useful bias sources or dynamic loads. These devices use FET technology, and can in fact be made using ordinary junction FETs (such as the 2N3819). Fig. 9a shows the principle.




EG 58 Fig. 9. Constant current "diode" principle

When sufficient reverse bias exists on the gate of an FET, the current through the channel starts to reduce. If the gate and

source are connected together, then current will increase until the voltage dropped across the internal section of the source channel (section a) exceeds the required gate voltage. At this point, the current will be held almost constant. The actual value will depend on the channel resistance and pinch-off voltage of the particular FET, and is known as I_{DSS} . This value varies greatly from device to device with normal FETs, and for a 2N3819 can be anywhere from 2 to 20mA. The current can be reduced by inserting a resistor in the source of the FET (Fig. 9b).

VOLTAGE REGULATORS AS CURRENT SOURCES

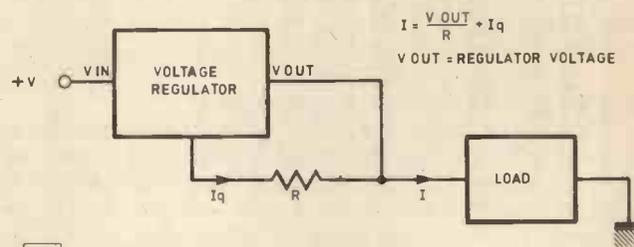Occasionally, current sources are required to deliver quite heavy currents (such as with battery chargers). Fig. 10 shows how a standard voltage regulator i.c. can be used to provide this function.



EG 59 Fig. 10. A voltage regulator as a current source

The regulator ensures a constant voltage across from V_{out} to ground, and this causes a current of V_{out}/R to flow through R (and hence through the load). Added to this we have the regulator quiescent current (I_q) which is typically several milliamps and usually constant enough to cause no problems. Low voltage regulators should be used to increase the output voltage range and to keep the power dissipation in R to a minimum. Currents of several amps, depending on the regulator, can be provided in this manner.



BOOK REVIEWS

UNDERSTANDING ELECTRONICS

By R. H. Warring
Published by Lutterworth Press
175 pages. Price £3.95

THIS book attempts to explain in everyday language basic electronic principles and behaviour of simple circuits. It is an interesting book, both to the layman for the simplicity and clarity of the explanations, and to the qualified reader for the ingenuity in avoiding recourse to mathematics. The reader is asked to accept on face value only the few circuit properties which defy this form of treatment.

The book contains much useful information regarding component types, their construction, marking, mounting, etc. One glaring omission is any mention of the principles of negative feedback, the basis of every modern amplifier circuit.

J.F.G.

Marshall's Electronics

A. Marshall (London) Ltd., Dept: PE. Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 8005
 Retail Sales, London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Road, W2. Tel: 01-723 4242.
 Glasgow: 85 West Regent Street, G2 2OD. Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, B516 2LX. Tel: 0272 654201.

2N1304	0.80	2N3905	0.18	AC151	0.43	BC147C	0.13
2N1305	0.80	2N3906	0.18	AC152	0.54	BC148	0.13
2N1306	1.00	2N4038	0.72	AC153	0.59	BC148A	0.13
2N1307	4.00	2N4037	0.80	AC153K	0.59	BC148B	0.13
2N1309	0.38	2N4400	0.16	AC176K	0.70	BC149C	0.13
2N1219A	0.38	2N4401	0.20	AC176	0.54	BC149	0.15
2N2369	0.27	2N4402	0.20	AC187	0.59	BC149B	0.15
2N2369A	0.27	2N4403	0.20	AC187K	0.85	BC149C	0.15
2N2646	1.70	2N5459	0.32	AC188	0.54	BC157	0.15
2N2647	1.55	2N6027	0.44	AC188K	0.65	BC157A	0.15
2N2904	0.31	2N6121	0.41	AD138	2.75	BC157B	0.15
2N2905	0.31	2N6122	0.44	AD142	1.45	BC159	0.15
2N2906	0.25	2N6123	0.48	AD143	1.45	BC158A	0.15
2N2907	0.25	2N6124	0.45	AD149	2.85	BC158B	0.15
2N2926	1.17	2N6125	0.47	AD150	3.10	BC159	0.17
2N2926	0.25	2N6126	0.48	AD161	1.00	BC159A	0.17
2N3054	0.72	2N61	3.50	AD152	1.00	BC159B	0.17
2N3055	0.75	3N140	1.10	AF124	0.70	BC121A	0.12
2N3402	0.21	3N141	0.95	AF125	0.70	BC121B	0.12
2N3404	0.21	3N142	0.75	AF200	1.30	BC169C	0.13
2N3405	0.21	3N200	2.85	AF239	0.70	BC169B	0.13
2N3663	0.29	3N201	1.35	BC107	0.16	BC177	0.22
2N3702	0.14	40361	0.55	BC107A	0.16	BC159B	0.17
2N3703	0.14	40362	0.61	BC177B	0.22	BC177	0.22
2N3704	0.14	40363	0.45	BC108	0.16	BC178	0.22
2N3705	0.14	40408	0.82	BC108A	0.16	BC178A	0.22
2N3706	0.14	40409	0.82	BC108B	0.16	BC178B	0.22
2N3707	0.14	40410	0.82	BC108C	0.16	BC179	0.22
2N3708	0.12	40411	3.10	BC109	0.16	BC179A	0.22
2N3709	0.12	40412	4.00	BC109B	0.16	BC179B	0.22
2N3710	0.12	40414	4.90	BC109C	0.16	BC182	0.22
2N3771	2.15	40594	0.87	BC140	0.30	BC182A	0.12
2N3772	2.20	40595	0.88	BC141	0.32	BC182B	0.12
2N3773	3.15	40636	1.37	BC142	0.32	BC182L	0.12
2N3779	0.36	40873	0.80	BC143	0.32	BC182LB	0.12
2N3820	0.38	41226	0.86	BC147	0.16	BC179B	0.22
2N3903	0.20	AC127	0.48	BC147A	0.13	BC183A	0.12
2N3904	0.18	AC128	0.48	BC147B	0.13	BC183B	0.12

TRANSISTORS

See catalogue for full range

BC183C	0.12	BC307	0.16	BC372	0.18	BF888	0.30	MJ4502	4.90	TP14C	0.97
BC183D	0.12	BC307A	0.16	BC377	0.18	BF899	1.37	MJE340	0.62	TP14Z	0.86
BC183E	0.12	BC307B	0.16	BD121	2.20	BF950	0.35	MJE350	0.62	TP14ZC	1.08
BC183L	0.12	BC308	0.16	BD124	2.20	BF951	0.35	MJE370	0.62	TP110	0.77
BC183M	0.12	BC308A	0.16	BD131	0.55	BF952	0.35	MJE371	0.66	TP112	0.93
BC183N	0.12	BC308B	0.16	BD132	0.75	BF950	1.35	MJE520	0.50	TP115	0.83
BC184	0.12	BC308A	0.16	BD135	0.40	BR101	0.85	MJE521	0.70	TP117	0.89
BC184B	0.12	BC308B	0.16	BD136	0.40	BR939	0.55	MJE2555	1.65	TP120	0.87
BC184C	0.12	BC308B	0.16	BD137	0.41	BS95A	0.37	MJE3055	1.05	TP122	1.04
BC184D	0.12	BC308B	0.16	BD138	0.41	BU104	1.80	MP8111	0.40	TP125	0.93
BC184E	0.12	BC308B	0.16	BD139	0.43	BU105	1.55	MP8112	0.45	TP127	1.11
BC184F	0.12	BC308A	0.16	BD140	0.43	BU128	2.00	MP8113	0.50	TP130	1.16
BC184G	0.12	BC308B	0.16	BD142	0.70	BU128	2.08	MP8121	0.40	TP132	1.33
BC184H	0.12	BC308B	0.16	BD147	0.70	BU204	2.20	MP8122	0.45	TP135	1.26
BC184I	0.12	BC308B	0.16	BD239C	0.59	BU205	2.40	MP8123	0.50	TP137	1.45
BC184J	0.12	BC308A	0.16	BD240A	0.59	BU206	2.70	MP8513	0.50	TP140	2.23
BC184K	0.12	BC308B	0.16	BD240C	0.59	BU209	2.70	MPF102	0.33	TP142	2.57
BC184L	0.12	BC308B	0.16	BD241	1.55	J310	0.84	MPF103	0.44	TP145	2.47
BC184M	0.12	BC308A	0.16	BD242	1.90	J300	0.84	MPF104	0.44	TP147	2.84
BC184N	0.12	BC308B	0.16	BD243	2.10	ME4001	0.22	MPF105	0.44	TP2955	0.70
BC184O	0.12	BC308B	0.16	BD244	2.10	ME4002	0.22	MPSA14	0.33	TP3055	0.59
BC184P	0.12	BC308B	0.16	BD245	2.10	ME4003	0.22	R2008B	2.15	TS34	1.05
BC184Q	0.12	BC308B	0.16	BD246	2.10	ME4004	0.22	R2010B	2.15	TS43	0.47
BC184R	0.12	BC308B	0.16	BD247	2.10	ME4005	0.22	TP29A	0.49	TS90	0.22
BC184S	0.12	BC308B	0.16	BD248	2.10	ME4006	0.22	TP29C	0.65	TS91	0.27
BC184T	0.12	BC308B	0.16	BD249	2.10	ME4007	0.22	TP30A	0.54	TS88A	0.44
BC184U	0.12	BC308B	0.16	BD250	2.10	ME4008	0.22	TP30C	0.70	ZX107	0.17
BC184V	0.12	BC308B	0.16	BD251	2.10	ME4009	0.22	TP31A	0.54	ZX108	0.17
BC184W	0.12	BC308B	0.16	BD252	2.10	ME4010	0.22	TP31C	0.72	ZX109	0.17
BC184X	0.12	BC308B	0.16	BD253	2.10	ME4011	0.22	TP32C	0.82	ZX300	0.17
BC184Y	0.12	BC308B	0.16	BD254	2.10	ME4012	0.22	TP33A	0.86	ZX302	0.27
BC184Z	0.12	BC308B	0.16	BD255	2.10	ME4013	0.22	TP33C	1.18	ZX303	0.27
BC185	0.12	BC308B	0.16	BD256	2.10	ME4014	0.22	TP34A	0.97	ZX304	0.27
BC185A	0.12	BC308B	0.16	BD257	2.10	ME4015	0.22	TP34C	1.31	ZX500	0.16
BC185B	0.12	BC308B	0.16	BD258	2.10	ME4016	0.22	TP35A	2.20	ZX501	0.17
BC185C	0.12	BC308B	0.16	BD259	2.10	ME4017	0.22	TP35B	3.00	ZX502	0.19
BC185D	0.12	BC308B	0.16	BD260	2.10	ME4018	0.22	TP41A	0.76	ZX503	0.16

NEW 1979 CATALOGUE

48 page catalogue - new enlarged micro section - largest range of quality components from franchised suppliers available in the UK. All VAT inclusive prices. Over 8,500 line items plus lots more. 50p post paid or 40p to callers at any of our four branches.

MAIL ORDER

Quick service on all orders - please add 40p for P&P. Telephone orders £10 minimum.

Buy it with Access

BARCLAYCARD

VISA

Credit cards welcome

LINEAR

See catalogue for full range

CA301B	0.75	LM377N	1.80	NE558N	1.98
CA301BA	1.10	LM378N	2.40	NE560N	4.50
CA3020	2.20	LM379S	4.25	NE561N	4.50
CA3020A	2.20	LM380N-8	0.96	NE562N	4.50
CA3020B	0.90	LM380N-14	1.08	NE563N	1.00
CA3028B	1.25	LM381AN	2.70	NE568N	1.75
CA3030	0.20	LM381N	1.69	NE567N	1.00
CA3030A	0.20	LM382N	1.32	NE571N	4.95
CA3038	2.90	LM384AN	1.55	SAJ110	2.10
CA3038A	4.10	LM388N	0.88	SA5560	2.70
CA3045	0.75	LM387N	1.10	SAS570	2.70
CA3046	1.55	LM389N	1.00	SN7601N	3.00
CA3048	2.45	LM389N	1.00	SN7603CN	3.08
CA3052	1.78	LM702C	0.81	SN7608KE	1.95
CA3080	0.85	LM709C	0.70	SN7613CN	2.04
CA3080A	2.10	LM708-8	0.50	SN7613ND	1.72
CA3080B	0.50	LM708-14	0.48	SN7618KE	1.90
CA3086	1.87	LM710C	1.67	SN7619N	2.05
CA3086E	2.90	LM710-14	0.48	SN76023ND	1.72
CA3090	4.40	LM711CN	0.48	SN76033N	3.08
CA3130	1.06	LM723C	0.82	SO41P	1.35
CA3140	1.04	LM723C-14	0.45	SO42P	1.35
LF355N	0.80	LM741C	0.50	TD190	2.00
LF356N	0.80	LM741C-6	0.30	TA4263	1.26
LF357N	0.80	LM741C-14	0.60	TA3000	3.70
LF1320N	3.00	LM747D	0.78	TAAS21	1.10
LF13331N	3.00	LM748-8	0.50	TAAS22	1.85
LF13741N	0.49	LM1303N	1.15	TAAS50	0.48
LF13741N	0.38	LM1304N	1.52	TA611B	2.30
LM3019	0.30	LM1305N	1.52	TA621	2.50
LM307N	0.50	LM1307N	1.22	TA651A	1.65
LM308N	0.55	LM1310N	2.10	TA661B	1.45
LM309KC	1.95	LM1351N	1.30	TA700	3.50
LM317K	3.35	LM1458N	0.45	TA930A	1.45
LM317MP	1.35	LM1458N	0.97	TA930B	1.45
LM317T	2.20	LM1800N	1.94	TB4120	8.00
LM3201B	2.45	LM1801N	2.25	TB451D	1.76
LM3201E	1.86	LM1808N	2.10	TB4520	2.60
LM320T-12	1.86	LM1812N	6.20	TB45200	2.70
LM320T-15	1.86	LM1820N	1.16	TB4530	2.35

EXPAND AND GROW WITH KIM

NOT A KIT-BUT A READY TO USE MICROCOMPUTER SYSTEM

AMERICA'S FASTEST SELLING MOST POPULAR 6502 BASED SYSTEM - EASILY EXPANDED INTO A PERSONAL HOME COMPUTER

The basic KIM 2 includes Hex keyboard and display, audio cassette interface, VDU interface, Superd documentation, 2K monitor software in ROM. Powerful instruction set. The beauty of this system is the ease of extension and versatility with all the possible future requirements catered for. Up and running in minutes. Any future benefits from Commodore PET computer will be software compatible with their KIM system and in fact your KIM system has the design flexibility to suit any requirements.

KIM IS EXPANDABLE - Expand as you learn up to 65K

- KIM 1 - Basic board with above features assembled £108.00
- KIM 3 - 8K static RAM card plugs into motherboard £141.00
- KIM 4 - Motherboard (takes 6 x KIM 3) + power supply £75.50

The Commodore PET and KIM are both based on the 6502 micro VDU INTERFACE - VDU card - takes control £151.00

Fully assembled TTY Card - ASC II keyboard in - converts TV set to cheap computer terminal via aerial socket. Also standard RS232C connector for micro computer or modem - 16 lines x 64 characters

SEND SAE NOW FOR FULL DETAILS.

PET 2001 COMPUTER

Suitable for educational, commercial, scientific and domestic applications

Memory - 8k ram (expandable to 32k externally)

Display - 1000 characters 40col x 25 rows

Keyboard - full ASCII character set + graphics separate numeric keyboard

Other features include - reliable cassette unit, comprehensive I/O facilities, 8k resident basic Interpreter

Send S.A.E. 9" x 6" for data and software list

HARDWARE PRICES

PET 2001-8 £695.00

PET SECOND CASSETTE £59.40

PET 2020 PRINTER £459.00

SIEMENS LEDS + OPTO

RED 7 SEG DISPLAYS

8mm C.A.N	large	red	1.9	19.19	19.19
HA1081	1.58	large extra			
8mm C.C.A	bright	44	44	44	44
HA1083	1.58	medium	30	30	30
18mm C.A.N	small	14	18	18	18
HA1181	1.95	small extra			
18mm C.C.A	bright	25	28	28	28
HA1183	1.95	TIL209	13	TIL211	22

LEDS

all prices are each

1-9	10-49	50-99	100+
A3F	1.80	1.81	1.44
A5F	3.90	3.32	2.95
A3M	1.63	1.33	1.23
A5M	2.97	2.66	2.35
AR3F	4.77	4.30	3.82
AR3M	4.41	3.96	3.52
D3F	2.46	2.17	1.98
D5F	3.92	3.65	3.13
D3M	2.45	2.17	1.98
D5M	2.69	2.43	2.16

F=female M=male R=right angle D=chassis A=cord 3=No of pins

MEMORIES


See catalogue for full range

AY2133	8.75	DP8304N	3.95	INSR900	14.86	SFF71301A	8.95	TMS4004	9.85
DM81S95	1.36	DP83500							

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIERS

MC 1

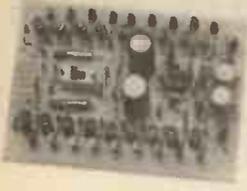

CPR 1



CPR 1 - THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/μs; T.H.D. 20Hz - 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 x 80 x 20mm. Supply to be ±15 volts.

MC 1 - PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 5V battery or from our REG 1 regulator board.

REG 1 - POWER SUPPLY

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

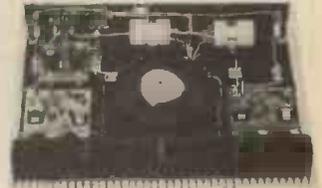The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-035v	£16.30
CE 1004 100W/4 ohms 35-0-35v	£19.22
CE 1008 100W/8 ohms 45-0-45v	£23.22
CE 1704 170W/4 ohms 45-0-45v	£29.12
CE 1708 170W/8 ohms 60-0-60v	£31.90

TOROIDAL POWER SUPPLIES

CPS 1 for 2 x CE 608 or 1 x CE 1004	£14.47
CPS 2 for 2 x CE 1004 or 2/4 x CE 608	£16.82
CPS 3 for 2 x CE 1008 or 1 x CE 1704	£17.66
CPS 4 for 1 x CE 1008	£15.31
CPS 5 for 1 x CE 1708	£22.68
CPS 6 for 2 x CE 1704 or 2 x CE 1708	£23.98

HEATSINKS

Light duty, 50mm, 2°C/W	£1.30
Medium power, 100mm, 1.4°C/W	£2.20
Disco/group, 150mm, 1.1°C/W	£2.85
Fan, 80mm, static 120 or 240v	£18.50
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules.	£29.16

Thermal cut-out, 70°C £1.90

POWER AMP KIT £32.40

PRE-AMPS:
These are available in two versions - one uses standard components, and the other (the S1) uses MO resistors where necessary and tantalum capacitors.

CPR1	£29.49	CPRIS	£39.98
MCI	£18.50	MCIS	£29.49
POWER SUPPLY:			
REG1	£5.75	TR6	£1.75

BRIDGE DRIVER, BDI
Obtain up to 340W using 2 x 170W amps and this module. £5.40

CRIMSON ELEKTRIK
1A STAMFORD STREET,
LEICESTER LE1 6NLL
Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information.

Distributor: Miric Teleprodukt, Box 12035, S-7512 Uppsala 12, Sweden.

PROGRESSIVE RADIO

31 CHEAPSIDE,
LIVERPOOL L2 2JD

FULL SPEC. SEMICONDUCTORS SPECIAL OFFER:-

TB800 10 for £5.00, ORP61 Mullard boxed 30p, 7418 Pin 6 for £1, L.E.D.'s, TL209 0-2" Red 10p each, Toshiba TLG113 0-2" Green 16p each, TLR120 0-2" Clear Infra Red 19p each, TLG107 Green 0-2" Flat Top 17p each, NE555 Timers 27p each.

TRANSFORMERS, 6-0-6v 100ma, 9-09 75ma, 12-012 50ma 75p each, 12-012 100ma 95p, 12v 500ma 95p, 1:1 triac/xenon pulse transformers 30p, CHOKES 6MH 3 amp 20p, U.H.F. TV Tuners, push button (not varicap) new and boxed £2.50p. Miniature toggle switches, SPST 8 x 5 x 7 45p, DPDT 8 x 7 x 7 50p, DPDT c/o 12 x 11 x 9 75p, Min. push to make or push to break 16 x 16mm 15p each type, Texas BY205 800v 6a Sil. Rects 18p each. Nat Sem. LM340T 6v 1a voltage regs 40p, AD161/162 matched pair 70p pair.

TOOLS Small side cutters 5" insulated handles £1.35p. Snub nosed pliers 5" insulated handles £1.35p. Board with 14 12 volt reed relays £1.95p. Large mains tester screwdrivers, fully insulated 8" 44p. Test lead jumper sets, 10 leads with insulated croc clips each end, different colours 80p. Telephone pick up coil, suction type with 3.5 mm jack plug 50p, 9 volt battery eliminators, 240v ac input 9v dc out at 120 mA, stabilised replaced PP3, PP6, PP7, PP9 £2.45p. Edge connectors, 0-1 64 way 65p, 34 way 40p, 0-2 18 way 15p, Murata MA401, 40KHz, Transducers Rec/Sender, £3.25p pair. Tape head demagnetisers, 240v ac with on/off switch, straight probe £2.00, curved probe (cassette) £2.35p.

TERMS: cash with order, (of official orders from colleges etc). Postage 30p unless otherwise shown, overseas post at cost, VAT inclusive prices S.A.E. for new illustrated lists.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY.

SOLVE your component buying problems with this famous Catalogue



- The finest components catalogue yet published.
- 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Profusely illustrated.
- Bargain List sent free.
- At £1.25, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD 234 240 London Road Mitcham Surrey CR4 3HD

Please write your Name and Address in block capitals

NAME _____

ADDRESS _____

HOME RADIO (Components) LTD Dept PE
234-240 London Road, Mitcham, Surrey CR4 3HD Regd. No. 912966 London

POST THIS COUPON with cheque or P.O. for £1.25

TOPS THE PACK!

ACE MAILTRONIX LTD
Dept. PE, Tootal Street
Wakefield, W. Yorkshire WF1 5JR

COMPONENTS — Now over 1,000 types in stock!

KITS — See the new range of low-cost 'ELEKITS'.

MODULES — New ready-built functions.

SERVICE — 1st Class same day despatch.

QUALITY — All guaranteed products.

PRICES — Many reductions!

MAGAZINE PROJECTS — Trouble-free!

I enclose 30p*, please send catalogue.

Name _____

Address _____

*Refundable with future orders over £5.00.

Semiconductor UPDATE...

FEATURING : TL496C 8202 IRF 100 IRF 305

R. W. Coles

PORTABLE POWER

Ever had the problem of providing power for a small portable unit that needs the regulation 9 volts? Easy you may say, bung in a PP3 or a PP6 battery and the problem is solved. These days though, batteries of that sort are expensive items and there may be a better way to solve the problem.

Rechargeable Nickel Cadmium cells, for example, are now freely available, and although they are initially more expensive than primary batteries, their long life can more than make up for that. Trouble is, while these rechargeable cells are great for one or two cell operation, stick to the requirement for the full 9 volts and at 1.2 volts per cell you've got an expensive battery.

To get the best out of rechargeable cells for calculators, radios, metal detectors and so on, what we need is a simple circuit which will step up the low voltage from a couple of A.A. size cells to a respectable 9 volts. Oh! and we need a built-in recharging circuit too, so that with the aid of only a small step down transformer, we can give our cells an overnight boost, or even let them trickle charge while we are using the unit indoors.

I don't suppose you will be too surprised when I tell you that somebody has put all of the necessary goodies into an itty-bitsy 8 pin mini-dip package, to make the job easy for us.

"Somebody" is no less than Texas Instruments, and the device in question is

the **TL496C**, termed a 9 volt Power-Supply Controller. All you need in addition to the TL496C is an IN4001 diode, a 330 μ capacitor, a 50 μ inductor and of course a couple of Ni Cad cells.

To recharge the cells you will also need a mains transformer with about a 6 volt r.m.s. secondary, but there is no need to build this into the portable equipment if you don't want to.

When running off the batteries, the TL496C acts as a switching regulator to generate the required 9 volts with the aid of a couple of the inductor.

When connected to the mains, an internal diode rectifies the positive half cycle and feeds it to a 9 volt series regulator to maintain the output. At the same time, the negative half cycle is rectified by an external IN4001 and used to recharge the batteries—clever, eh?

With two cells connected, you can get up to 80mA at 9 volts at 66 per cent efficiency. With a single cell, this drops to 40mA but the efficiency remains the same. At last a small, cheap i.c. which is down to earth and practical!

REFRESHES THE BITS OTHER PARTS CANNOT REACH!

Dynamic RAMs, such as the 4K 2104, the 16K 2117 and even the new Texas 64K device, have a problem. They keep forgetting. Not such a healthy characteristic in devices which are, after all, purchased for their *memory* capability!

To make matters worse they forget everything in just a few milliseconds, and have to be reminded every 2 milliseconds about just what it was they were supposed to remember!

This apparently devious behaviour is due to the fact that in dynamic (as opposed to static) RAMs data is stored as a charge on the gate capacitor of a MOSFET. This charge leaks away, but 2 milliseconds is a long time to a microprocessor, and the reduction in size and power dissipation possible with dynamic RAM techniques makes them cost effective for large memories.

To prevent the loss of data, the memories are "refreshed" every 2 milliseconds or so with the aid of external circuitry which can get very complicated, especially in systems using 16 pin RAM chips where the address lines have to be multiplexed too.

If you are contemplating the construction of a big memory for use with your home computer, hold everything! Using dynamic RAMs is now not only cheap but simple too, thanks to the **8202** from Intel. This new 40 pin chip puts the whole of the refresh circuit, and the address multiplexer into one easy to use package.

No need to wire up arrays of TTL gates and refresh counters, no need to worry about what happens to memory refresh while DMA (Direct Memory Access) transfers take place, the 8202 takes care of it all. It'll handle a full 64K of memory too, enough for a very capable "Star-Wars" program!

KILO-WHAT?


Some time ago I extolled the obvious virtues of the new Siliconix VMOS power FETs which eliminate many of the disadvantages of bipolar power transistor technology while providing CMOS compatibility and the wherewithal to switch 2 amps in just 10 nanoseconds.

International Rectifier have now joined the power MOSFET brigade with a couple of devices with a very impressive specification.

The **IRF 100** is rated for 16 amps at 80 volts and has an "on" resistance of just 0.2 ohms maximum.

The **IRF 305** is rated for "only" 5 amps but (hold on to your rubber mat!) at no less than 400 volts!

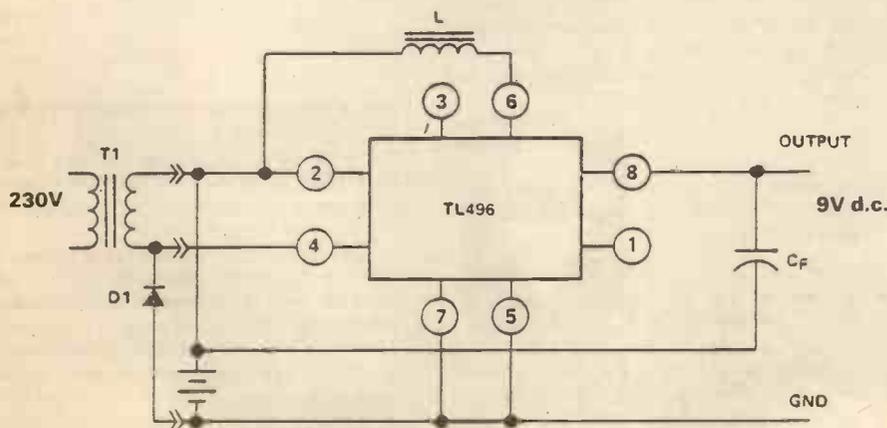Both devices can, in consequence, switch over a *kilowatt*. Just the job for that transistorised arc welder you always wanted to build!



TWO-CELL OPERATION

T1: $V_{sec} = 6.8V$ r.m.s. typ., $R_{sec} = 11\Omega$ typ.
D1: 1N4001

L: 40 to 50 μ , $O \approx 3$, $R < 0.15\Omega$
 C_f : 330 to 470 μ , 10 V electrolytic

readout

... a selection from our postbag


Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Extravagate

Sir—The article in the January issue's *Ingenuity Unlimited* section of P.E., describing a method of adding upper and lower bars on digits 6 and 9 of 7447 display drivers, is somewhat extravagant on gates. For the benefit of those readers who have not seen the method generally employed, these are the details:


Since the 7447 is an "open-collector" device, other similar devices may be connected across the outputs, using the "wired-or" mode.

Fig. 1

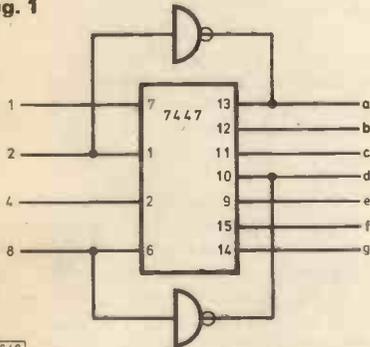

EG 49

Fig. 2

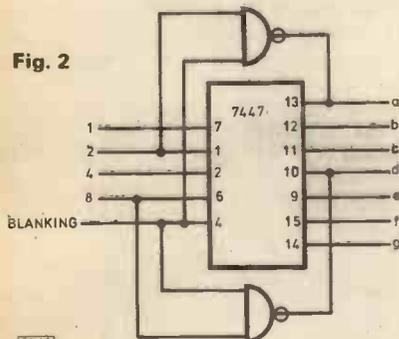

EG 48

Fig. 1 shows how just two inverters from a 7405 (5V) or 7406 (30V) hex. open-collector may be used. This arrangement does not allow the "blinking" facility to be used; if it is required, the circuit of Fig. 2 should be used. This method uses two gates from a 7403 (5V) or 7426 (15V) quad. two-input open-collector NAND gate. Both methods allow more displays to be driven from fewer packages.

Unfortunately, I cannot claim any originality for these circuits, as they are too well-known in the industry.

M. A. Priestley, B.Sc.,
Edinburgh.

Symbolism

Sir—A few comments on P.E. and circuit diagram symbols:

1. The new component value labelling system is a good step. However, be warned that for inductors, 100m could be ambiguous—Rank Service Spares use the suffix "m" in place of "μ" for capacitors. It's unlikely, of course, that an inductor and a capacitor would be confused—but it is worth while remembering that 100m could be interpreted as 100μ by some!
2. Keep your present symbols for components. The habit of naming transistors "Q" etc. instead of "T" or "TR" is terrible, after all, it's not a "Quansistor" now is it? Unusual symbols make reading very difficult, as do non-standard layouts of circuit diagrams. There is no quibble at all with your present circuit diagrams or symbols. Change for change's sake is all too prevalent today—and I don't need it.
3. The current craze for superfluous verbiage worries me, e.g.

This moment in time = this moment
Visible gallium arsenide red indicator device = i.e.d.
Advanced Technology = standard electronic circuitry
Total solution } an elegant
Total systems capability } solution?

Please let it stay on the other side of the Atlantic!

So to end, broadly speaking, keep P.E. as it is. Please try to avoid that which is insubstantial, trendy and "commercial" in character; and we speak British English here—and expect to read British English—not mid Atlantic slang.

B. J. Duncan,
Tattershall, Lincoln.

The above is an extract from a very lengthy letter on P.E. and other magazines from Mr. Duncan.

A Pointless Exercise?

Sir—Full marks! for using the "pointless" method of recording component values (6k8, 4μ7, etc.) and for using "nano" for capacitor values where appropriate.

I find no more difficulty visualising that 4n7 = 4700p = .0047μ than visualising that

6k8 = 6800Ω = .0068M.

Full marks! also for *not* using those silly boxes to represent resistors. Symbols, to me, should be functionally descriptive, and I am sure that the zig-zag is better for a resistor than any little boxes.

More power to your elbows, gentlemen.

Chris Finn, C.Eng.
Southwood Park
Beverley

Sir—A pointless exercise, you can say that again!!!! At the moment all the capacitors in my service kit are clearly marked. .01μf, .002μf etc., etc. I can, thank heavens, still order them like this. I have just received from the USA some circuit modifications to cinema equipment we service—the components (nice squiggles for resistors!) are clearly marked .1uf, .01uf, 1.5k etc.

I have just looked at a Japanese circuit diagram—again the components are clearly labelled as above. You really think that it is easier to write 470n than .47μf?? And 3K9 than 3.9K. I know which I prefer and which is easier to read. Who on earth wants to deal in nanofarads—I suspect that most service engineers like me will find the rigmarole of working these out an unnecessary chore.

You state that pointless values are less prone to printing or drawing errors—I would think you have no proof of this. Printing or drawing errors are only avoided by care in preparation and copy reading—making something easier to write does not necessarily make mistakes less easy to make.

How about an editorial rethink in the nice fresh air of Poole and a return to common sense?

P. Taylor,
St. Agnes,
Cornwall.

Maybe it is not easier to write 470n than .47μF but remember we have to put 0.47μF to help avoid confusion, and how about 0.002μF or 2,000pF rather than 2n; such long designations can also be a problem on a crowded circuit diagram.

Unfortunately, a point is easily lost in printing or a dot may appear in just the wrong place. No amount of checking or proof reading will overcome this.

We are sure you will find 3k9 just as easy to read once you are used to it and nF is a perfectly valid denomination of F—writing 470n as opposed to 0.47μF is the same as writing 1mV instead of 0.001V—it is only a question of familiarity.

Any more views?—Editor.

All Change!

Sir—In your January editorial you justify your “pointless” component values as “it is widely accepted”, while although you have no immediate plans to use boxes to represent resistors and capacitors, Toby Bailey expresses the view in his “letters” reply that such a move would be change for change sake, while you believe such a change would make circuits less easy to read.

In principle I agree but then must ask, why you have departed from using the widely accepted symbols for logic gates that almost everybody (Mullard, SGS, Harris, Texas etc.) use.


Please practice what you preach and use easy to read symbols that are in common use and let's not have change for change sake! I don't care if your new symbols are in accordance with the “BS”. BS will have to follow American practice in the end, it's happened before.

While I am writing may I ask your “Patents Reviewer” how Indesit of Turin got a patent (BP 1497418), January issue, on a technique that is common knowledge. I have read a number of articles on this topic over the years including one in the February 12th 1976 issue of “Electron” (pages 52-4) and I have known of the technique for at least 15 years.

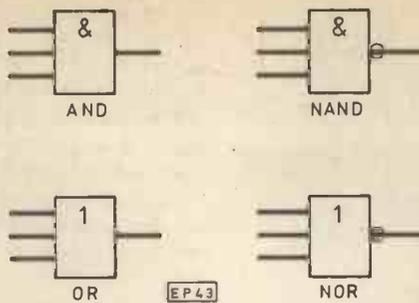B. H. Beeston
Enfield

We must point out that we have not “departed from using widely accepted symbols” or made “change for change sake”. In fact our logic symbols have been used in P.E. since January 1972. There may now be a case for change and we have noted your feelings. By

the way, we are not using BS gate symbols, some new BS symbols are:



Your point on the Indesit patent is taken up below.

Standard Patented

Sir— I am both dismayed and worried by the report, on page 68 of your January 1979 issue, that Indesit have been granted a British Patent on what has been the standard method of producing a log law potentiometer for several decades. I can remember being taught this method over twenty years ago as an apprentice and whenever I have needed a log law pot have used this method.

How then can a foreign washing machine maker claim to have invented such a technique? Does this mean that the British Patent Office is about to grant patents to foreign tea cup makers for the “new” method of obtaining a lower value resistor of non-preferred value, by putting another suitable resistor in parallel with the first one?

Perhaps some enterprising British company

should apply for foreign patents on all the standard methods used in our industry to produce components of different values or characteristics from those readily available.

D. Lands,
Dorset.

May we assure readers that a patent has been granted to Indesit as described in the January issue. Our contributor, Adrian Hope, bases the reviews on copies of patents obtained from the Patent Office. Sometimes he deliberately selects patents on apparently old ideas to draw attention to such anomalies. So how do these anomalies arise and what can be done about them? The Department of Trade Press Office inform us that a search of existing literature is made before new patents are granted. But no search can ever be conclusive and it is for this very reason that patents can be challenged. Under the laws previously existing in the UK this has been a rather tortuous procedure. However a new law came into force in June 1978 which streamlines procedures (see next month's Patents Review). But due to the inherent slowness of patenting, patents will continue to be granted under the old laws for a period of several years yet. Although these are still open to “revocation” under transitional legal provisions, readers will in most cases be well advised to let sleeping dogs lie and simply ignore obviously invalid patents granted under the old laws. In any case readers should bear in mind that it is only public knowledge prior to the original filing date of a patent that invalidates it. The published reference given by Mr. Beeston was after the original filing date of the Indesit patent—January 1975.

Editor



Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for.....(amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss

ADDRESS

POSTCODE

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53626. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

DUAL PURPOSE LIGHTS REMINDER FOR CARS REMINDS YOU TO TURN YOUR LIGHTS ON REMINDS YOU TO TURN YOUR LIGHTS OFF

FOR all those motorists who like me, have a wife with a predilection for leaving the car lights on whenever possible, this unit should prove useful, for it will also give a warning of failing daylight thus performing a dual function, that is, it will give a warning when it is time to switch on the car lights, and also when the lights have been left on after the ignition has been switched off. This is particularly useful when the lights have been used during the day in times of poor visibility.

CIRCUIT DESCRIPTION

Perhaps the easiest way to explain the circuit operation is to split the circuit in two, that part before D3 performs the monitoring whilst all the circuitry after D3 gives the warning. As this is the simplest part of the circuit we shall deal with this first. Nand gates IC2a and b together with C2, C3, R8 and R9 are designed to oscillate at about 1Hz and can be enabled by applying a "high" input to pin 1. The output of this low frequency oscillator switches on and off transistor TR3 and so flashes a l.e.d. mounted on the dashboard of the car. R13 serves to limit current through the l.e.d. in the usual manner. At the same time the output of IC2b also enables a second oscillator comprising IC2c and d, C4 and C5 which operates at audio frequency. This output is amplified by TR4 and the warning is given by LS1, which can be a surplus

COMPONENTS . . .

Resistors

R1	4k7
R2, R3	100k (2 off)
R4-R6, R12, R13	10k (5 off)
R7	270k
R8-R11	1M (4 off)
R14	270
R15	ORP 12(l.d.r.)

Potentiometers

VR1	4k7 preset
-----	------------

Capacitors

C1	100 μ
C2, C3	470n (2 off)
C4, C5	1000p ceramic (2 off)

Transistors and Diodes

TR1-TR3	BC109 (3 off)
TR4	BFY51
D1-D3	1N4148 (3 off)
D4	TIL209

Integrated Circuits

IC1	741
IC2	4011

Miscellaneous

S1	d.p.s.t. switch
LS1	Telephone earpiece (or loudspeaker)

Printed circuit board

Fig. 1. Full circuit diagram

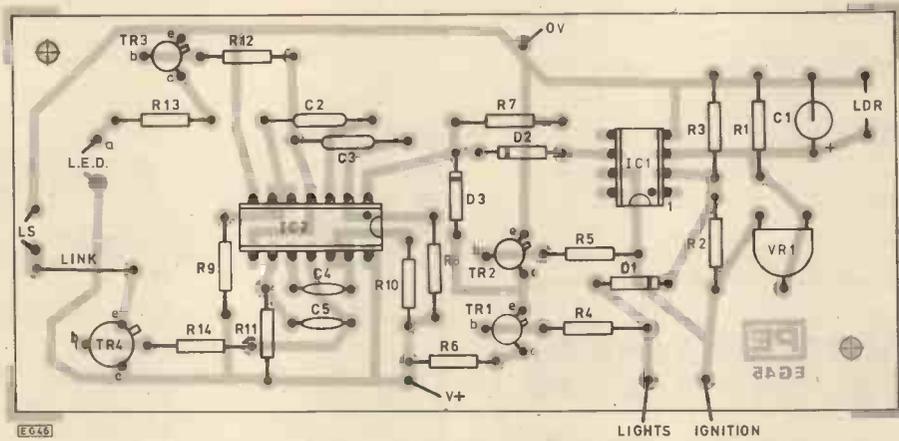
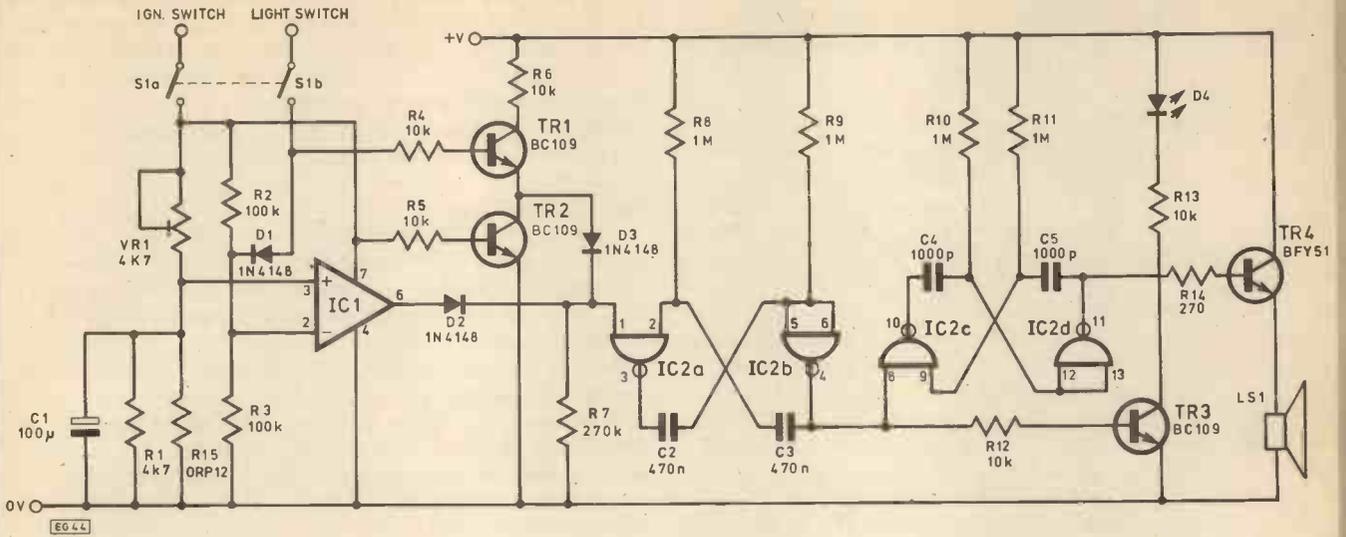


Fig. 2. Component overlay

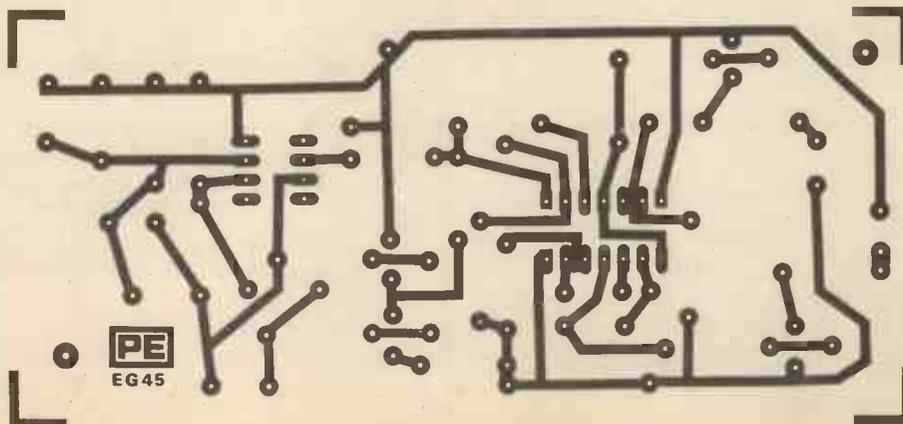


Fig. 3. Printed circuit

telephone earpiece. This part of the circuit is connected permanently to the car supply as it is necessary to give a warning when the ignition is switched off. This will not affect the car battery as the quiescent current consumption of the CMOS device is virtually zero. The only point of care here is that the outputs are taken from pins 4 and 11, as of course the outputs on pins 3 and 10 are high in the quiescent condition, and the alarm would operate.

MONITOR CIRCUIT


Now coming to the monitoring section of the circuit, the level of daylight is monitored by the light dependent resistor R15. As the level of daylight falls, so the resistance of the l.d.r. increases until it exceeds the level set by VR1. This potential is applied to the non-inverting input of IC1 pin 3. The potential at the inverting input of IC1 is held at half supply voltage by the potential divider R2-R3, when the non-inverting input exceeds this level by a few millivolts, the output at pin 6 will swing high due to the large open loop gain of IC1. This output is applied via D2 to pin 1 of IC2a to trigger the warning device. If the lights are now switched on, this would apply full battery voltage via D1 to the inverting input of IC1 and thus bring the output at pin 6 low again, turning off the warning. It will be noticed that this part of the circuit is fed via the ignition switch, and so will only give a warning of low light level when the ignition is switched on. However, if the ignition is switched off when the lights are switched on, this would turn transistor TR1 hard on, and because the ignition is switched off transistor TR2 would be turned hard off, thus the potential at the emitter of TR1 would be applied via D3 to the gate IC2a and so trigger the alarm circuit again. When the lights are now turned off TR1 would then be turned off and so pin 1 of IC2a would be returned to a low condition by R7 and the alarm would be disabled. The resistor R1 is included in parallel with the l.d.r. to prevent its resistance rising significantly above the maximum setting of VR1, C1 prevents spurious light changes affecting the circuit by providing a time constant of one or two seconds.

News Briefs

CHERRY-PICKER BOOM BOON

ACOUSTIC emission techniques have afforded the Georgia Power Company an early warning of failure in the booms of their overhead maintenance trucks (nicknamed cherry-pickers).

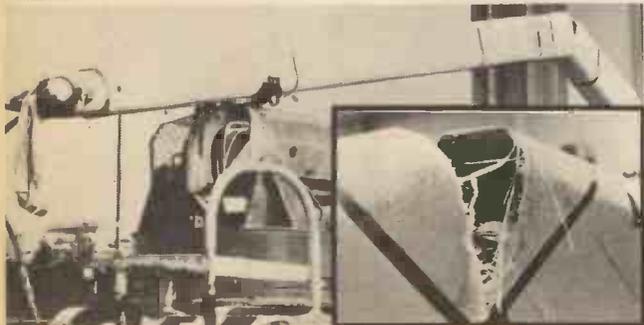The sophisticated acoustic emission system supplied by Dunegan Endeveco Ltd. listens to the high frequency "cries for help" of the material under stress, and by using this technique to determine the useful life of the booms, Georgia Power estimates that it has saved thousands of dollars in unnecessary "play it safe" scheduled replacements.



CONSTRUCTION

All the components are easily obtained and are fairly cheap; the usual precautions should of course be taken when handling the CMOS device, and for those readers who, like myself, actually enjoy etching their own circuit boards, a p.c.b. layout is provided. Incidentally if it is desired to use a small loudspeaker instead of a telephone earpiece, then the link shown on the p.c.b. layout may be removed and a suitable resistor inserted in place of this. The value would depend on the impedance of the loudspeaker, but 470 ohms should be about right for an 8 ohm speaker.

INSTALLATION

The switch S1a-b may be omitted, but would prove useful for disabling the alarm system in certain circumstances, such as when the lights are required to be left on for night parking. As mentioned previously the l.e.d. may be mounted in a prominent position on the dashboard, and LS1 concealed behind it. However, the l.d.r. is best mounted as near to the windscreen as possible.

The prototype unit was not mounted in any form of box, but was fastened to the rear of a convenient insulated panel with double sided servo tape, which can be obtained from most model shops. The best size is about 13mm wide ($\frac{1}{2}$ in.) and 3mm ($\frac{1}{8}$ in.) thick, and is ideal for mounting small p.c.b.s. However, if this method is used, precaution should be taken to ensure that none of the tracks on the p.c.b. can make contact with any metal surface.

The trigger level may best be set by waiting until daylight has fallen to a level where it is necessary to switch on the lights, VR1 can then be adjusted until the unit just begins to operate. ★

PE

A Volume of Practical Know-how

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At **£2.85** inc. VAT and postage (£3.45 overseas) they are obtainable from:

**Post Sales Department, IPC Magazines Ltd.
Lavington House, 25 Lavington Street
London SE1 0PF**

I enclose P.O./cheque value for binders at **£2.85** each (£3.45 overseas) for **Practical Electronics Vol. No's**

Name


Address

Date

PE

NEXT MONTH

Autoranging MULTIMETER

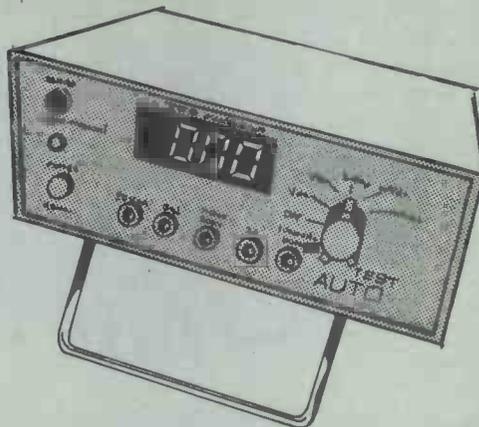

Full five function capability autoranging instrument that measures accurately a.c. and d.c. voltages, current and resistance.

BUBBLE MEMORIES

With non-volatile bubble memories no longer a lab' curiosity, it's time to learn just how they work. Next month's article by Dr. P. V. Cooper of Plessey Microsystems is your chance!

Also... PHASER

With six phase shift networks this offers improvements in this most popular of guitarist's sound effects.

FREE INSIDE!
MAPLIN
40 PAGE
ILLUSTRATED
GUIDE
& PRICE LIST

PRACTICAL

ELECTRONICS

OUR APRIL ISSUE WILL BE ON SALE FRIDAY, 9 MARCH 1979

INGENUITY



A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.



VARIABLE PULSE DELAY

THIS circuit delays a TTL pulse by a variable time, without altering the length of the pulse. It was originally developed to delay trigger pulses between keyboard and ADSR in a synthesiser, to produce "repeat" and "double-tracking" effects, etc.; although other uses are possible.

Monostable IC1 is triggered by the positive-going edge of the input waveform, and IC2 is triggered by the negative edge. The pulse lengths are identical, and controlled by the ganged potentiometer VR1a/b. The outputs are differentiated and the short pulses applied to an RS flip-flop IC3a/d. This is alternately set and reset, so the output appears as a delayed version of the input. Note that further input pulses will be ignored until the first pulse is output; also that an inverted output is available. Network R1/C1 ensures that IC2 is triggered when the power is applied, so that the flip-flop is reset on switch-on.

The circuit can provide delays from 5 μ S to 30S, depending on the value of C2 and C3; the accuracy of the output pulse depends mainly on the matching of C2/C3. In the prototype, C2 and C3 were 1 μ , 10 μ and 100 μ (tantalum), switch selected, allowing delays from 1mS to 2S.

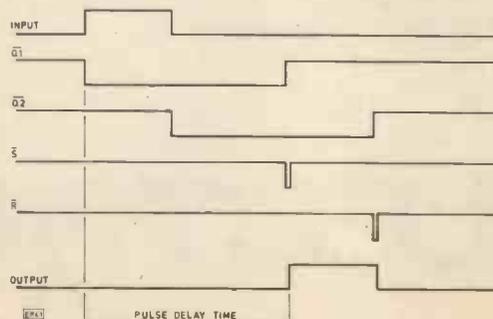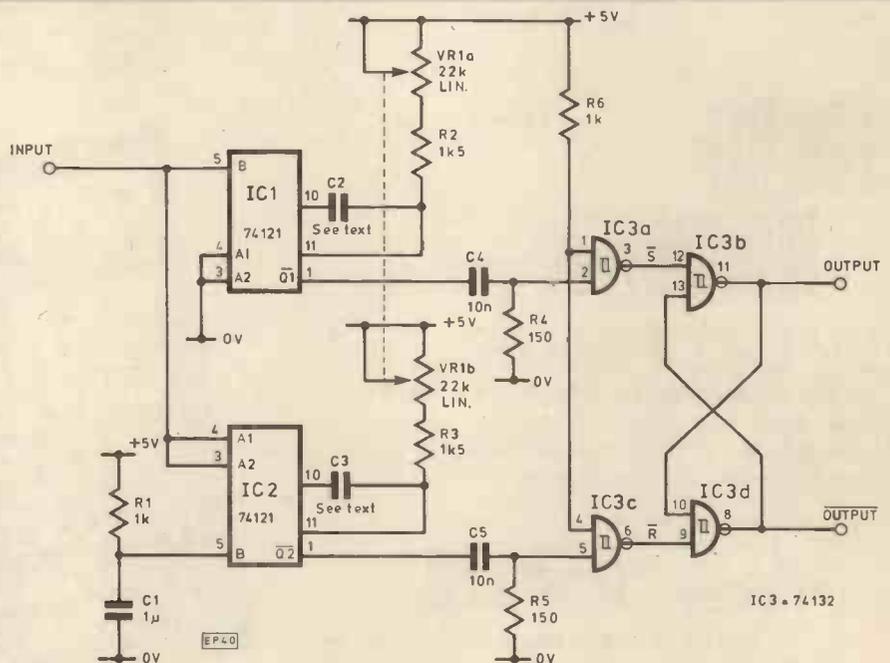T. P. Hopkins,
Haywards Heath,
West Sussex.



ULTRASONIC PROXIMITY DETECTOR


THIS circuit consists of an ultrasonic transmitter and receiver in the same unit and relies on the reflection of the signal to detect the presence of a nearby object. As such, it may be used for burglar alarms, industrial batch counters or to prevent collisions in an electronic robot.

The transmitter consists of a 40kHz oscillator modulated by a second oscillator to provide a series of ultrasonic bleeps from the transducer. The oscillator does not self-stabilise to 40kHz, so VR3 is provided to adjust this frequency.

The received signal is amplified by IC4, and fed to IC2, an NE567 tone decoder. This responds only to signals of 40kHz—adjusted by VR2—having a small bandwidth. The output of this and the output of IC1 are combined, and fed to TR1.

Thus, if an echo is heard by the receiver during a signal bleep from the transmitter, TR1 is turned off momentarily. This transistor has been left open collector in the circuit diagram, and users should connect this to suit their own requirements.

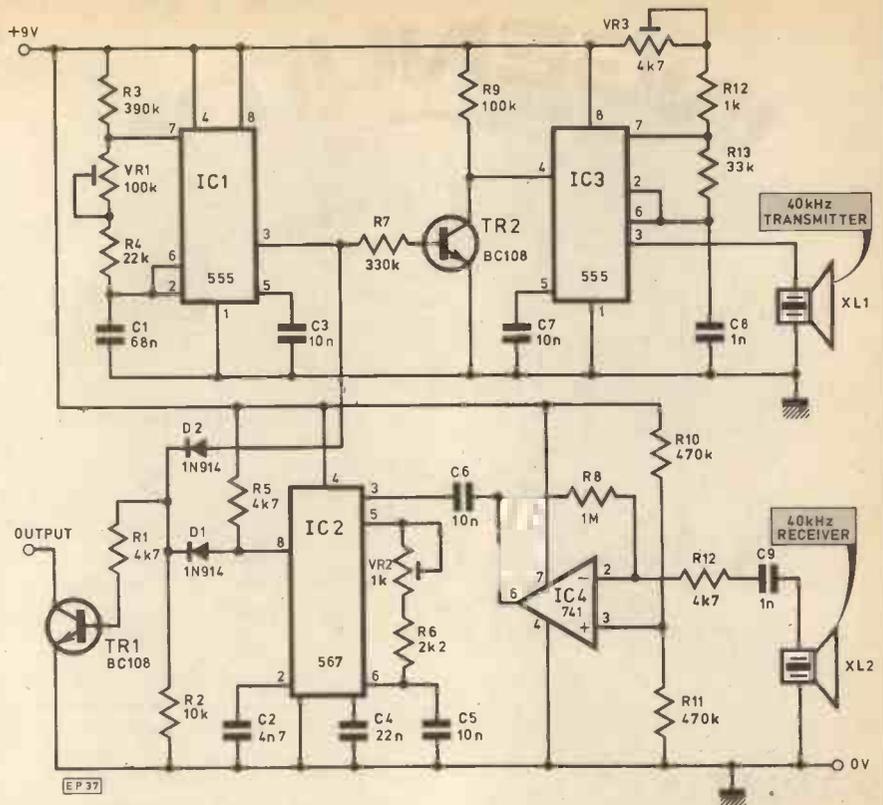VR1 controls the duty cycle of IC1, and should be adjusted to set the maximum distance at which the circuit will respond. The supply voltage range is 5V to 9V, and current consumption is around 40mA. Although not shown on the diagram, supply decoupling capacitors should be included, particularly around the NE567



which is rather sensitive to supply noise. For this reason, attention should be paid to avoiding earth loops.

40kHz transducers are used since the higher ultrasonic frequencies are more directional. However, it is important to

ensure that there is no direct sound path between the transmitter and receiver—cotton wool or fibre glass wadding are useful here.

D. F. Akerman,
Coventry.

TRAILER HAZARD FLASHER MONITOR


MY car was fitted as standard with a 42/84W flasher unit in order to operate the hazard warning system but had no provision for the extra warning light required by law when towing a trailer and, in my case, owing to a preformed cable loom, fitting another type would have been tricky.


The circuit shown can be made in a couple of hours from common components and simply mounted in the boot of the car. The 1.2W lamp monitor indicates the operation of the trailer indicators and should be mounted at the dashboard.

The 0.6 ohm resistors (R1, R2) are small lengths of electric fire spiral filament. R3 prevents excessive current through TR3 at switch on due to low lamp filament resistance.


Note that this design is for negative earth vehicles only.

J. B. Farmer,
Melton Mowbray,
Leics.

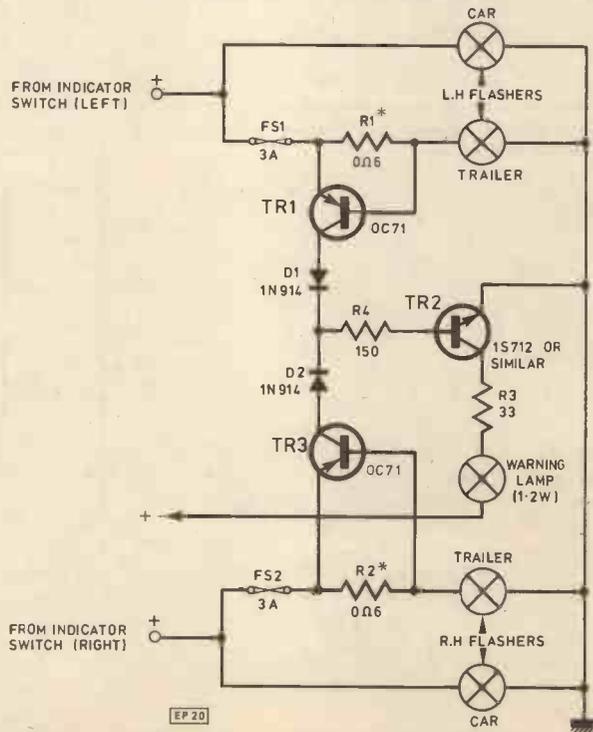

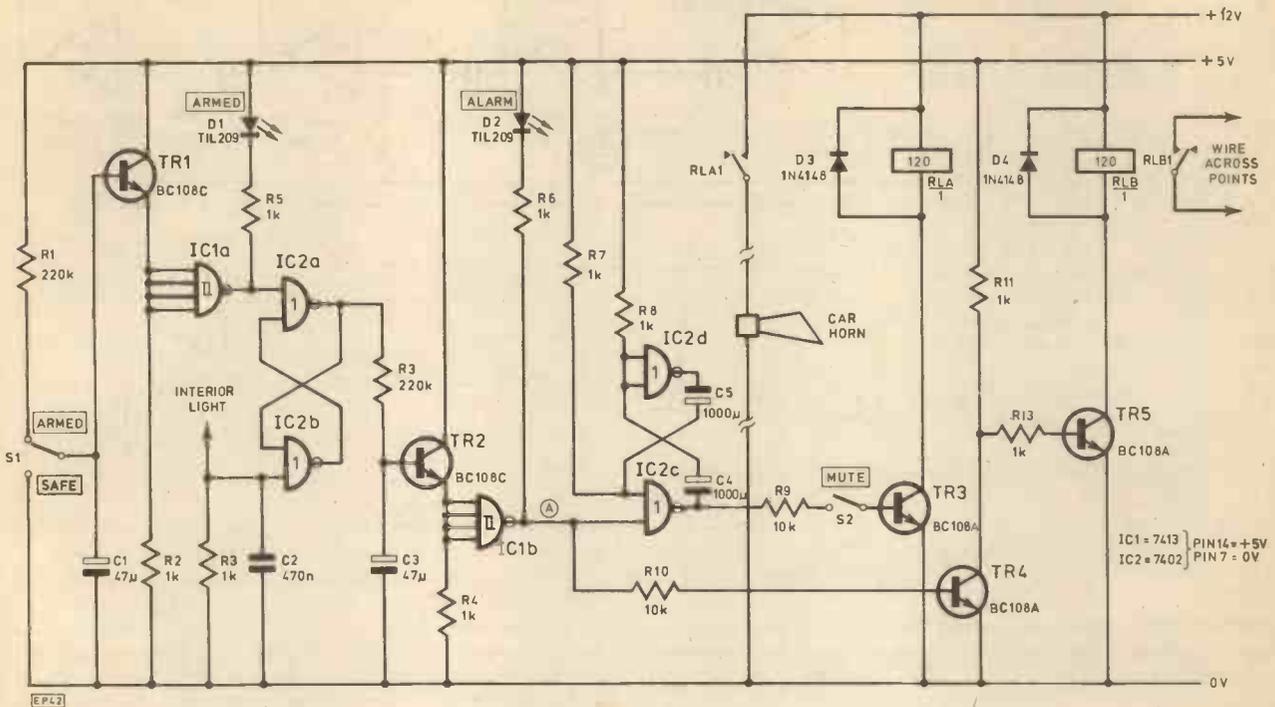

CAR INTRUDER ALARM

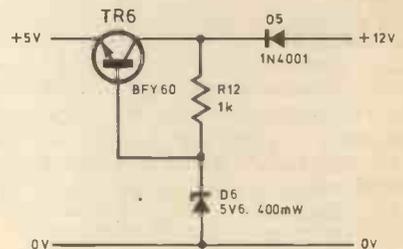

THIS circuit was devised as a simple car alarm which did not require an external de-sense switch. The circuit consists of two parts, the sensor and timer and the relay drivers.

The circuit operates as follows. When S1 is put into the armed position, C1 begins to charge via R1. This produces a slowly rising potential at the emitter of TR1 until after about 5 seconds the Schmitt's output goes low, and hence the reset input of the latch formed by part of IC2 also goes low, so that the output of the latch will go high as soon as the set input is made positive.

When the would-be intruder opens the door, he has set the latch by making the non earthy end of the interior light go positive. The latch will not reset until the hidden arm switch is restored to the safe

position. When the output of the latch has gone positive, C3 is charged via R3 until the output of the second Schmitt avalanches from high to low. If, however, the hidden switch is put into the safe position, which will reset the latch, C3 will discharge. D1 is lit when the output of the first Schmitt is low, and the latch is not being continuously reset. C2 prevents spontaneous triggering by noise on the line, and R3 holds the set input of the latch to low if the bulb is blown or if the interior light is switched off (D1 is green, D2 red).

When the second Schmitt goes low, the alarm l.e.d. (D2) lights and the oscillator using the remaining part of the 7402 starts oscillating at about 1.4Hz. The frequency could be much lower than this due to the tolerance of the electrolytic capacitors (C4 and C5). Should the mute be closed,

the coil of RLA1 will energise and de-energise at this frequency, sounding the horn. When point A goes low, apart from enabling the oscillator, it turns off TR4 pushing the base of TR5 positive through R11 and R13. This switches on TR5 and energises the coil of RLA2, the contacts of which short out the points so immobilising the car. D3 and D4 are to protect the transistors from the transients caused by the relay coils.

Included is a simple series regulator circuit which could be used to obtain 5 volts for the TTL i.c.s. Note the inclusion of D5; this is to prevent reverse polarity voltage causing damage to the circuit.

N. J. Bailey,
Yatton,
Bristol.

News Briefs

by Mike Abbott

MICRO' COURSES

TWO TRAINING courses, approved by the Department of Industry under the Microprocessor Application project scheme, are being run by Bleasdale Computer Systems Ltd. Course attendees will receive a contribution of £50.00 from the Department of Industry towards the cost of the course fee.

The Bleasdale courses *Introduction to Microprocessors* and *Designing Systems with Microprocessors* are intended to give the course attendees a good understanding of the aspects of designing and building microprocessor based systems. To achieve this, Bleasdale has designed and developed a range of microprocessor Input/Output units for use on the course.

The schedule for the 1 week *Introduction to the 6800* and the advanced 2 week course *Designing Systems with the 6800* for 1979 is:

Introduction to the 6800

5th Mar 79— 9th Mar 79
7th May 79—11th May 79
3rd Sept 79— 7th Sept 79
12th Nov 79—16th Nov 79

Designing Systems with the 6800

12th Mar 79—23rd Mar 79
14th May 79—25th May 79
10th Sept 79—21st Sept 79
19th Nov 79—30th Nov 79

For further details contact: June Dove, Course Registrar, Bleasdale Computer Systems Ltd., 7 Church Path, Merton Park, London SW19. Tel: 01-540 8611.

TAKE OVER

A TAKE OVER of Hacker, manufacturers of portable radios and music centres, has brought about the move of Hacker production from Maidenhead to Motoradio's modern plant at Bournemouth, where a fully equipped after sales and service department is also being established.

BUBBLE TAKE OVER

NOW available on an off-the-shelf basis from Texas Instruments, is the Model 765 portable bubble-memory terminal which offers a unique method of data entry, editing and storage for commercial applications such as remote sales-order entry, computer time-sharing systems and newspaper reporting. Because the terminal's bubble memory retains data even when the power is switched off, information from a variety of sources can be stored in the terminal for as long as required, and then transmitted in a single batch over a normal telephone line using the built-in acoustic coupler.

Unlike other methods of data storage the Model 765's bubble memory has no moving parts, and requires no external storage media. In addition, it has specifically been designed for ease of use in the normal business environment, with a standard typewriter-like keyboard and simple English-language commands.

Using TI's Silent 700 thermal-printer technique, the Model 765 is a full-capability 30-characters-per-second terminal with a full ASCII keyboard, a powerful command mode, and a file management system.

Prompting and operator lead-through routines can easily be developed to allow fast and efficient data entry, and the built-in editing facility allows on-the-spot correction of data. The terminal transmits data at 300 baud using the acoustic coupler, or at up to 9600 baud using an RS-232 serial EIA interface.

Further information from Texas Instruments Ltd., Digital Systems Division, Manton Lane, Bedford, MK41 7PA.

POWER SUPPLY BREAKER

WITH essential data being held and processed these days, by electronic equipment working around the clock, it is vital to know the degree of immunity a machine has to mains power interruption.

Any engineer who has had the task of ensuring that a system meets the specification laid down in this respect, will know the problems when it comes to generating a programme of known interruptions in the mains power, without purpose-built equipment to do this.

What is described as invaluable in the study and solving of interference problems, is the NS251 unit from Seltek Instruments Ltd. of Stanstead Abbots, Herts. Measuring 430 x 88 x 360mm, the NS251 will simulate breakdowns on a.c. and d.c. power lines. Pre-selection of the breakdown period is completely independent of the phase of the power line voltage. Breakdown time is fully adjustable from 1ms to 1,000ms. Both positive and negative trigger can be selected. Triggering is effected by a manual front panel knob, or may be activated automatically by an external signal. Two monitor outputs are available for measurement purposes when using an oscilloscope.

The effective voltage range of the NS251 is 0 to 250V a.c./d.c. with current to 4A (peak current 40A at 10ms knob.). The unit is switched in series with the power line and the test object or system. Phase range covers the full 180° and extreme values (90°, 180°) can be adjusted. Breakdowns for both the positive and negative half cycles are separate and selectable.

VIDEO LIBRARY

GOING to the pictures today seems synonymous with the long drive to find a cinema that hasn't been converted to a bingo hall, battling through the traffic to a rip-off car park, the long open air queue outside a multi-studio cinema that's been showing the same films for months on end, and the "full up" sign. It is with relief that most of us will witness the first signs of an alternative to this expensive agony. The chance to watch a feature film with one's feet up in the comfort of one's own home (perhaps with a few friends), starting when you like, with an interval when you like, and whatever *inexpensive* refreshments you may fancy.

For the first time in the UK, the growing number of video cassette recorder owners (now estimated to number 25,000), are being offered a comprehensive software library. Intervision Video now offer over 200 full length feature films, including such titles as *Blow out*, *Sunday In The Country*, and *The Happy Hooker* as well as films of *Chess Masterclass*, *Angling*, *Music* and other light entertainment.

The service Intervision has launched offers the home video consumer the opportunity to obtain tapes from either the Intervision Video Club (basically a mail-order or personal collection service operating from the company's new headquarters), or through selected dealers throughout the country who hold copies of Intervision programme cassettes.

Copies are available on all of the popular home video cassette formats, and Intervision have their own in-house videocassette duplicating facilities, which are claimed the most sophisticated in the country.


Despite the very high investment cost embracing both the equipment and the acquisition of the legal copyrights, the joint Managing Directors, Richard Cooper and Michael Tenner, are very confident that the service is going to be successful. Response so far has been described as "phenomenal."

Hiring a programme on a one-cassette format such as VCR-LP, BETAMAX, or VHS costs only £5.95 including VAT for a two day hire period. Intervision have not lost sight of the hotel, disco and club market, where a hire charge of £15.95 enables a programme to be shown to a large nonpaying audience. The company's range of music programmes featuring such top names as *Roberta Flack*, *Neil Sedaka*, and *Donna Summer* are much in demand from 'discoland'.

Video cassette recorders are not cheap, although significant price avalanches are forecast, but already it would be feasible to club together with a group of friends for film evenings. Perhaps the day will come when new films are like new books and go straight into shops and libraries, making drunk-dodging on the way home from the cinema a thing of the past!

More details from Intervision Video Ltd, 102 Holland Park Ave, London, W11 4UA.

This Is The Famous

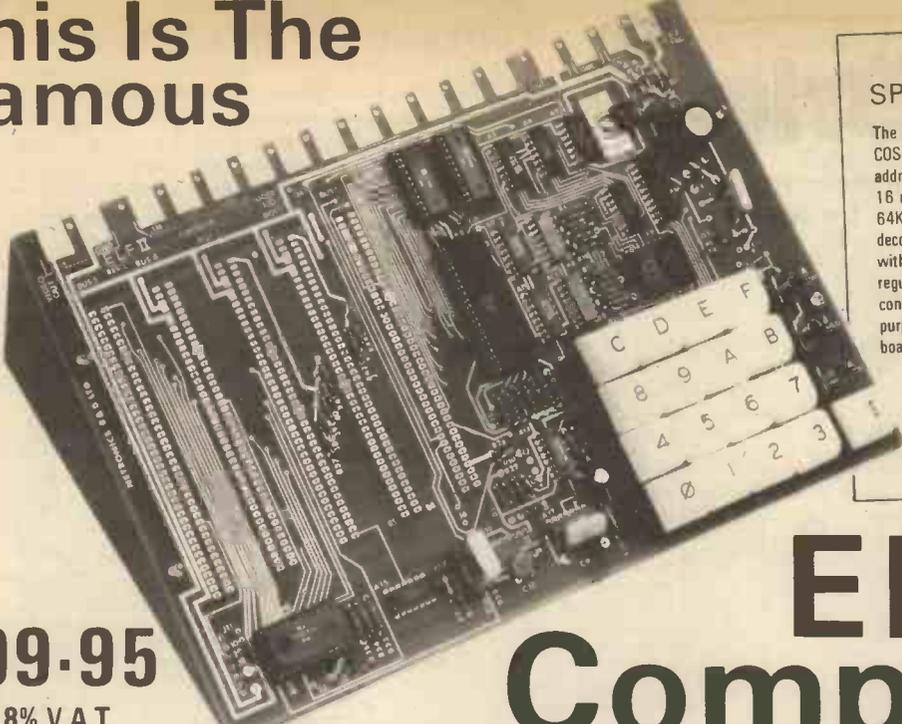

SPECIFICATIONS

The £99.95 ELF II computer features an RCA COSMAC COS/MOS 1802 8-bit microprocessor addressable to 64K bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM expandable to 64K bytes, professional hex keyboard fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion bus (less connectors), stable crystal clock for timing purposes and a double-sided, plated-through pc board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with all the logic and support circuitry you need to learn every one of the RCA 1802's capabilities.

£99.95
PLUS 8% V.A.T.

ELF II Computer

Stop reading about computers and get your hands on one! With ELF II and our new *Short Course* by Tom Pittman, you can master computers in no time at all! ELF II demonstrates all 91 commands an RCA 1802 can execute and the *Short Course* quickly teaches you how to use each of the 1802's capabilities.

ELF II's video output lets you display an alphanumeric readout or graphics on any TV screen or video monitor and enjoy the latest video games.

But that's not all. Once you've mastered computer fundamentals, ELF II can give you POWER with add-ons that are among the most advanced found anywhere. American IEEE chapters plus hundreds of universities and major corporations have chosen the ELF II to introduce their students and personnel to microprocessor computing!

Learn The Skill That May Soon Be Far More Important Than Your College Degree!

The ability to use a computer may soon be more important to your earning power than a college degree. Without a knowledge of computers, you are always at the mercy of others when it comes to solving highly complex business, engineering, industrial and scientific problems. People who understand computers can command MONEY and to get in on the action, you must learn computers. Otherwise you'll be left behind.

ELF II Is The F-A-S-T Way to Learn Computer Fundamentals!

Regardless of how minimal your computer background is now, you can learn to programme a computer in almost no time at all. That's because Netronics has developed a special *Short Course on Microprocessor And Computer Programming* in non-technical language that leads you through every one of the RCA COSMAC 1802's capabilities so you'll understand everything ELF II can do... and how to get ELF II to do it!

All 91 commands that an 1802 can execute are explained to you, step-by-step. The text, written for Netronics by Tom Pittman, is a tremendous advance over every other programming book in print.

Keyed specifically to the ELF II, it's loaded with "hands on" illustrations. When you're finished, ELF II and the 1802 will no longer hold any mysteries for you.

In fact, not only will you be able to use a personal computer creatively, you'll also be able to understand computing articles in the technical press.

If you work with large computers, ELF II and our *Short Course* will help you to understand what makes them tick.

A Dynamite Package For Just £99.95 Plus 8% V.A.T.!

With ELF II, you learn to use machine language — the fundamental language of all computers. Higher level languages such as FORTRAN and BASIC must be translated into machine language before a computer can understand them. With ELF II you build a solid foundation in computers so you'll really know what you're doing, no matter how complicated things get.

Video output also makes ELF II unique among computers selling such a low price. Attached to your TV set, ELF II becomes a fabulous home entertainment centre. It's capable of providing endless hours of fun for both adults and children of all ages! ELF II can create graphics, alphanumeric displays and fantastic video games.

Only a low cost RF modulator is required to connect ELF II to your TV's aerial socket! (To order see below.)

ELF II's 5-card expansion bus (connectors not included) allows you to expand ELF II as your needs for power grows. If you're an engineer or hobbyist, you can also use ELF II as a counter, alarm, clock, thermostat, timer, or for countless other applications.

ELF II Explodes Into A Giant!

Thanks to ongoing work by RCA and Netronics, ELF II add-ons are among the most advanced anywhere. Plug in the GIANT BOARD and you can record and play back programmes, edit and debug programmes, communicate with remote devices and make things happen in the outside world. Add Kluge Board to get ELF II to solve special problems such as operating a more complex alarm system or controlling a printing press. Add 4k RAM board and you can write longer programmes, store more information and solve more sophisticated problems.

Expanded, ELF II is perfect for engineering, business, industrial, scientific and personal finance and tax applications. No other small computer anywhere near ELF II's low price is backed by such an extensive research and development programme.

The ELF-BUG Monitor is an extremely recent breakthrough that lets you debug programmes with lightning speed because the key to debugging is to know what's inside the registers of the microprocessor and, instead of single stepping through your programme, the ELF-BUG Monitor, utilising break points, lets you display the entire contents of the registers on your TV screen at any point in your programme. You find out immediately what's going on and can make any necessary changes. Programming is further simplified by displaying 24 bytes of RAM with full address, blinking cursor and auto scrolling. A must for serious programmers!

Netronics will soon be introducing the ELF II Colour Graphics & Music System — more breakthroughs that ELF II owners will be the first to enjoy!

Now BASIC Makes Programming ELF II Even Easier!

Like all computers, ELF II understands only "machine language" — the language computers use to talk to each other. But, to make life easier for you, we've developed an ELF II Tiny BASIC. It talks to ELF II in machine language for you so that you can programme ELF II with simple words that can be typed out on a keyboard such as PRINT, RUN and LOAD.

"Ask Not What Your Computer Can Do... But What Can It Do For YOU!"

Don't be trapped into buying a dinosaur simply because you can afford it and it's big. ELF II is more useful and more fun than "big name" computers that cost a lot more money.

With ELF II, you learn to write and run your own programmes. You're never reduced to being a mere keypunch operator, working blindly with someone else's predeveloped software.

No matter what your speciality is, owning a computer which you really know how to use is sure to make you a leader. ELF II is the fastest way there is to get into computers. Order from the coupon below!

H.L. AUDIO LTD., Dept. P.E., 138, KINGSLAND ROAD, LONDON E2 8BY. TEL: 01-739 1582

— SEND TODAY! —

NOW AVAILABLE FOR ELF II —

- Tom Pittman's *Short Course On Microprocessor & Computer Programming* teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language, it's a learning breakthrough for engineers and laymen alike. £5.00* post paid.
- Deluxe metal cabinet with plexiglas dust cover for ELF II. £29.95* plus £1.50 p&p.
- RF Modulator for use with TV set. £3.00* post paid.
- GIANT BOARD kit with cassette I/O, RS 232-C/TTY I/O, 8-bit P I/O, decoders for 14 separate I/O instructions and a system monitor/editor. £39.95* plus £1.00 p&p.
- Kluge (Prototype) Board accepts up to 36 IC's. £17.00 plus 50p. p&p.
- 4k Static RAM kit. Addressable to any 4k page to 64k. £89.95* plus 50p. p&p.
- Gold plated 86-pin connectors (one required for each plug-in board). £5.70* post paid.
- Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, onboard regulator, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer. £64.95* post paid.
- Deluxe metal cabinet for ASCII Keyboard. £19.95* plus £1.50 p&p.
- ELF II Tiny BASIC on cassette tape. Commands include SAVE, LOAD, ±, x, +, (). 26 variables A-Z, LET, IF/THEN, INPUT,

- PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF II's hex keyboard as a joystick. 4k memory required. £14.95* post paid.
- Tom Pittman's *Short Course on Tiny BASIC* for ELF II. £5.00* post paid.
- Expansion Power Supply (required when adding 4k RAM). £19.95* plus £2.00 p&p.
- ELF-BUG Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your TV at any point in your programme. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! £14.95* post paid.
- Coming Soon: A-D, D-A Converter, Light Pen, Controller Board, Colour Graphics & Music System... and more!

Call or write for wired prices!

H. L. AUDIO LTD., Dept. P.E.,
138, Kingsland Road, London E2 8BY.
Tel: 01-739 1582.

Sole European Distributors for Netronics R & D Ltd., U.S.A.

Yes! I want to run programmes at home and have enclosed:
 £109.56 including postage and V.A.T. for RCA COSMAC ELF II kit. £5.94 including postage and V.A.T. for power

- supply (required). £5.95 for RCA 1802 User's Manual.
- £5.95 including postage and V.A.T. for *Short Course on Microprocessor Computer Programming*.
- I want mine wired and tested with power supply, RCA 1802 User's Manual and *Short Course* included for just £164.10 including postage and V.A.T.
- I am also enclosing payment (including postage and V.A.T.) for the items checked at the left.

Total Enclosed £

USE YOUR ACCESS BARCLAYCARD

Account No.

Signature

Exp. Date

CREDIT CARD PHONE ORDERS ACCEPTED 01-739 1582

Print Name

Address

DEALER INQUIRIES INVITED



Handy size reels and dispensers

of the world's finest cored solder to do a professional job at home



SAVBIT

handy solder dispenser
Contains 2.3 metres approx. of 1.22mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 58p inc. VAT

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71mm solder for fine wires, small components and printed circuits.
69p inc. VAT

Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.
Size 19A 63p inc. VAT



Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

handy size reels of **SAVBIT, 40/60, 60/40 and ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. (mm)	Length metres approx.	Use	Price inc. VAT
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£2.16
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.46
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£2.38
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£2.29

Sole U.K. Sales Concessionaires
Bib Hi-Fi Accessories Limited,
Kelsey House, Wood Lane End
Hemel Hempstead, Herts. HP2 4RQ

Prices shown are recommended retail inc VAT. From electrical and hardware shops. In difficulty send direct, plus 20p P & P. Prices and specifications subject to change without notice.



SOLDERING FLUX PASTES

'ERSIN' A non-corrosive, rosin based flux for general and electrical soldering in conjunction with 'Ersin' Multicore solders.

Ref AF14 48p inc. VAT

'ARAX' For general metal joining in conjunction with 'Arax' Multicore solders.
Ref RF10 48p inc. VAT

BIB WIRE STRIPPER and CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.

Model 8B 97p inc. VAT
Pat. No. 144913



EMERGENCY SOLDER

Self-fluxing, tin/lead solder tape that melts with a match. For electrical and non-electrical applications.

Size ES36 39p inc. VAT



MULTICORE DESOLDERING WICK

Absorbs solder instantly from tags, printed circuits, etc. Only needs 40-50 watt soldering iron. Quick and easy to use.

Non-corrosive. Size AB10 97p inc. VAT


ECONOPAK

A reel of 1.2mm 'Ersin' Multicore solder for general electrical use.
Size 13A £2.59 inc. VAT

A reel of 3mm 'Arax' Multicore solder for general non electrical use.
Size 16A £2.59 inc. VAT



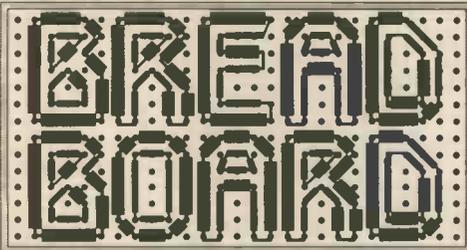Following the success of Breadboard '78, Trident Exhibitions announce



1979

The second hobby electronics show

Information on exhibiting from:
Trident International Exhibitions Limited,
Abbey Mead House, 23a Plymouth Road,
Tavistock, Devon. PL19 8AU.
Telephone (0822) 4671 Telex 45412 TRITAV

December 4th-8th Royal Horticultural Hall, Westminster, London SW1

LISTEN TO THE SECRET WORLD OF PLANTS

Now in Modular Kit Form, a Biological Amplifier & Sound Synthesiser In one instrument, the *Amazing*

Bio Activity Translator™.



- ★ Experience the unique Musical Form of Plants
- ★ Hear beautiful patterns of sound created by their natural response
- ★ Compare house plants' reactions to people - with the distinct tunes of those outside
- ★ Easy to operate, internal speaker & batteries
- ★ P.C.B. available as a separate kit, or assembled and tested

Natural Bio Electric signals, generated within the plant, are monitored by an electrode attached to the leaf. When amplified and filtered, a VCO, VCA and

other exclusive synthesiser circuits are programmed by the control voltage from the plant to produce tracking sequences of notes. These follow in pitch, rhythm and volume the ever changing signal from the plant. A plant reacts as a total living system to many stimuli, with a response above that of the natural biological level. This activity is an indication of their extraordinary sensitivity, which varies from day to day and plant to plant, producing a fascinating insight into the plant kingdom.

Complete Printed Circuit Kit £13.95

Assembled & Tested Printed Circuit £17.35

Case, Speaker & Hardware Kit £12.30

Complete Assembled & Tested Unit £33.10

Requires 350 speaker, £1.50 extra when ordered with kit. D.P. switch and two: 4½ volt batteries.

Includes all screws, wire, punched case & wood end cheeks.

Requires two 4½ volt batteries. Case size 7½ x 5½ x 3½"

All prices include P & P and VAT. Please allow 21 days for delivery.
JEREMY LORD SYNTHESISERS, (Dept PE4)
52 Becmead Avenue, London SW16 1UQ

15-240 WATTS!

HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload, two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; input impedance 47k Ω at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16-50V.

Price £6.27 + 78p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit; low distortion; short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price £6.27 + 78p VAT. P. & P. free

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price £8.18 + £1.02 VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

Price £19.01 + £1.52 VAT. P. & P. free

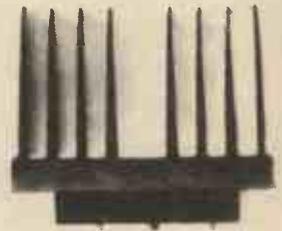

HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

APPLICATIONS: hi-fi; disco; monitor; power slave; industrial; public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Size—114 x 50 x 85mm.

Price £27.99 + £2.24 VAT. P. & P. free

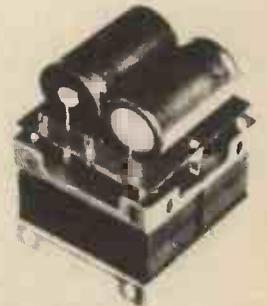

HY400 240W into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price £38.61 + £3.09 VAT. P. & P. free

POWER SUPPLIES: PSU36—suitable for two HY30s £6.44 + 81p VAT. P. & P. free. PSU50—suitable for two HY50s £8.18 + £1.02 VAT. P. & P. free. PSU70—suitable for two HY120s £14.58 + £1.17 VAT. P. & P. free. PSU90—suitable for one HY200 £15.19 + £1.21 VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 £25.42 + £2.03. VAT. P. & P. free.

Free post + packing applicable to U.K. only.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 64723

Please supply
Total Purchase price
I Enclose: Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name and Address
Signature

Registered office No. 1032630

ELECTROVALUE

FOR A GOOD DEAL BETTER THAN MOST

WE PAY POSTAGE on U.K. C.W.O. orders over £5.00 list value. Under £5.00 add 25p handling charge.

WE GIVE DISCOUNTS on C.W.O. in U.K. orders - 5% on list value over £10.00; 10% on list value over £25.00

WE GUARANTEE all goods are brand new, clean and to specification - no seconds, no surplus.

WE GIVE SERVICE to all orders large or small - we use microfilm order storage, computer processing and double-check personal supervision.

This month's ELECTROVALUABLES

'Electrovaluables' are our own overstock items offered from time to time at greatly reduced prices. Orders should quote 'Electrovaluables' and state description and price as advertised. **PRICES ARE NET & V.A.T. MUST BE ADDED** @ 8% or 12% where prices show * subject to prior sale.

Resistors
 1/2 watt: 5R6, 56, 5K6, 22K, 27K, 220K, 820K, 1M, 2M, 7.5 watt:
 4R7, 5R6, 330, 330, 1K, 1K1, 1K5, 2K4, 2K7, 3K9, 5K1, 5K6, 6K8, 10K, 120K, 150K, 240K, 56K, 82K, 120K, 150K, 240K, 270K, 330K, 560K, 3M9, all at 60p per pk of 100.

Integrated Circuits 16p
 7450 9p 7470 55p
 7480 25p 74190 55p
 709 (metal) 30p TAA991D* 65p
 TAA2761A 45p

Transistors ACY40 30p
 2N4906 £1,
 AD161 10 for £5,
 BC1488, BC157A, BC183,
 BC2380 any 10 for 60p*
 BC328, BC338 any 10 for 80p*
 BD1301=2N3055 10 for £4
 BF194, BF195 any 10 for £1
 OC83, OC84 any 10 for £1

Potentiometers Carbon track
 P20: 2K 2 log standard spindle 8 for £1*
 P20: + switch 470K 1M log 3 for £1*
 JP20: 47K 1in. short spindle 3 for £1*
 2M2 1in. long spindle 3 for £1*
 100K log, 2M2 log 3 for £1*

1M log, rev log short-spindle 3 for £1*
 PG58: slider, 1M 1in, 10K log, 47K log, 100K log, 220K log, 1M log, any 6 for £1*

Wire wound
 Colvern 905C, 100, 150, 1K5, 5K, 10K, 15K, 25K, 50K, any 2 for £1*

PR15 presets
 Horiz: 220, 1K, 2K2, 47K, 470K, 4M7 any 10 for 40p*

PR140 Presets
 10M horiz, 100K vert any 10 for 60p*

Plessey MPWT moulded track
 47Ω, 220, 47K, 220K, 1M any 3 for £1

Diodes AA113, AA116, AA117, AA118, BA1133F, any 10 for 60p

Rectifier diodes BO680, S10M1 any 10 for 80p

Bridge rectifiers B1906, B1912 any 5 for £1.20

Thyristors BO126, BO140, BO226, any 5 for £1.25

WE ARE NATIONAL DISTRIBUTORS FOR

NASCOM MICROCOMPUTER KITS
 for delivery from stock. Brochure and prices on application. Also full supporting programme of Nascom items. Enquiries invited. Quantity discounts to bona fide traders.

MOTOROLA
 D.2 MICROPROCESSOR EVALUATION KIT
 (for the M.6800 Microcomputer - £175.87 net + V.A.T.)

CATALOGUE 9

Yours for the asking - and it's FREE

Completely revised and up-dated. 120 pages. Semi-conductors, I.C.s, Opto-electronics, Rs, Cs, materials, etc. etc. And you'll be delighted with our comprehensive three-month stabilised price list.



Two depots to serve you - one SOUTH, one NORTH

Written communications and orders by post to head office Englefield Green address Dept P.E.3.

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
 Telephone Egham 3603 Telex 264475
 Northern Branch - 680, BURNAGE LANE, BURNAGE, MANCHESTER M19 1NA(061) 432 4945


Specialist
 Mail order
 supplies
 since
 1964



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
 PHONE 01-672 3137/672 9080
 MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

NEW FROM TUAC

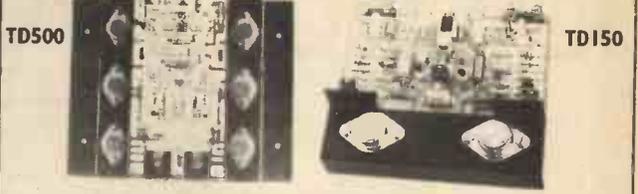

7" x 9" x 1 3/4" ULTRA QUALITY HIGH POWER 5" x 5" x 2" New D.C. Coupled Design AMPLIFIERS

Featuring—Electronic Short Open and Thermal Overload Protection.
Brief Spec.—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms. Frequency Response 20 Hz - 20 KHz. T.H.D. at full power 0.1%. Hum and Noise—100 dB Relative full output.

T.D. 500 300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms. £45.00
 Power supply P.S.300 £30.00

T.D. 150 150W into 4 Ohms. 100W into 8 Ohms. £26.25
 Power supply P.S. 150 £18.50

T.D. 150 60 Version 60W into 8 Ohms. 40W into 15 Ohms. £17.75
 Power supply P.S.60 £15.50

Note—P.S. 300 will drive 2 T.D. 150 amplifiers
 All output ratings are R.M.S. continuous sine wave output.

TO ORDER BY POST
 Make cheques/P.O.s payable to TUAC LTD., or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080.)

Send stamp for our free 28 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.
TUAC LTD., 119 CHARLTON ROAD, LONDON SW17 9AB.

Codespeed

ELECTRONIC MAIL ORDER

All Full Spec. Devices

- TO3 HEAT SINKS** III Two types of heat sink. Ex-equipment, but conditions as new. Most still contain a power transistor (condition unknown). 'Christmas tree' type, 92 x 68 x 35mm 20p each. Rectangular type 130 x 83 x 32mm 30p each. Please add 25p per heat sink post and packing.
- PACK M1** Contains two brand new multifunction calculator keyboards. Excellent key action. Only £1.00
- PACK T2** A high contrast 3 1/2 digit Liquid Crystal wristwatch display with data. Don't miss out - only £1.00.
- PACK T3** Back in stock again! MM5316 digital alarm clock chip. Still only £2.75 including data.
- PACK T4** At a new low price, what a bargain. A 0.8" common cathode, 3 1/2 digit, 12 hour clock display. Now offered at only £3.95.
- PACK S1** 25 miniature glass 1N3470 germanium diodes (600mA, 35v). All brand new (at just 2p each how can you go wrong?) 25 diodes for 50p.
- PACK S2** 4 x MEU21 programmable unijunction transistors (P.U.T.). Lots of uses, long delay timers, oscillators and many more. All brand new. With data and usage sheet. 4 for 50p.
- PACK S3** 10 x 1N4151 high speed switching diodes. Same as 1N4148, but has higher P.I.V. 10 for 35p.
- PACK P1** With this MM5330 digital voltmeter I.C. we include the data sheet and circuit diagram to build a high accuracy digital multimeter. Only £3.95.
- PACK E2** Calculator style I.C.D. 8 digit with right hand decimal points. Digit height 0.33". With data only £2.95.
- PACK E3** The same as Pack E2, but has 0.5" high digits. £4.25.
- EVER THOUGHT** of using 7 segment gas discharge displays as an alternative to LED's or LCD's? Gives a nice bright orange display and are comparatively very low in price. Requires 180v d.c. supply (easily achieved in mains operated projects). All have hand decimal points and are supplied with data.
- PACK E4** 0.3" high 1 1/2 digit display. Now only 50p.
- PACK E5** a 0.3" high dual digit display. Now only 50p.
- PACK E7** a 0.25" high 12 digit display with free socket. £1.50.
- PACK DM1** Want to buy 115 quality switching diodes for 50p? These 14 pin chips each contain 23 matched diodes. 5 chips for 50p.

All Untested Packs

- PACK M4 CALCULATORS** III This pack contains a production line reject calculator. Either repair them (not much wrong with some of them) or strip them for spares. Lots of accessible goodies inside, approximately 25 transistors, 2 chips, display, case and detachable keyboard. Such a bargain, you can't go wrong! Only £2.50
- PACK MU1** (Untested - so no guarantee) 2 x Upper half of hand held calculator case with integral keyboard. Ex-equipment, but believed to be O.K. A gift at only 50p the pair.
- PACK DL1** (Untested - so no guarantees) A bumper pack of 30 mixed I.C.'s. You test them and save ££'s. Could include anything linear or digital. A snip at only £1.00.
- PACK E1** (80% guaranteed good) Contains 5 seven segment LED displays. Digit height 0.127" with right hand decimal. Common cathode. Still only £1.00.

Your satisfaction is guaranteed or return the complete pack for replacement or a refund.
 For free catalogue send stamped addressed envelope.
 Postage and packing please add 25p. (Overseas orders add 60p)
CODESPEED, P.O. Box 23, 34 Seafield Road, Copnor, Portsmouth, Hants., PO3 5BJ

A breadboard as big as your ideas.

EXPERIMENTOR 325 £2.54

The ideal Breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin IC's. Has 130 contact points including two 10-point bus-bars.

EXPERIMENTOR 650 £4.70


Perfect for checking out Microprocessors. EXP 650 has 270 contacts including two 20-point bus-bars with 0.6" centres.

EXPERIMENTOR 600 £7.88

The Breadboard for quick construction of Microprocessors and other circuits. EXP 600 has 550 contacts including two 40-point bus-bars with 0.6" centres.

EXPERIMENTOR QUAD BUS STRIP £3.29

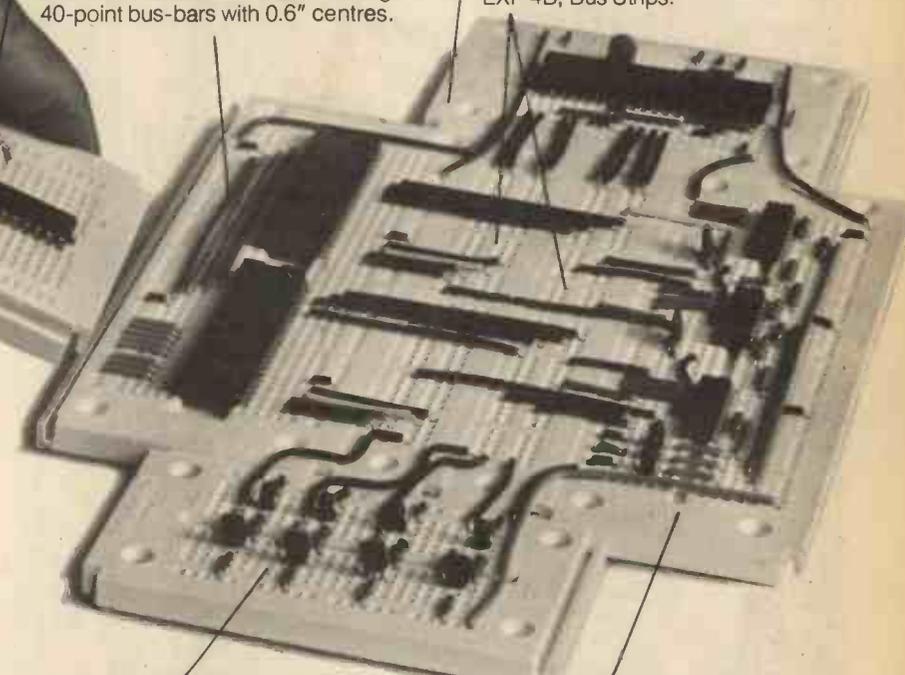Need more bus-bars, clip on an EXP 4B and you have four 40-point bus-strips with 8-, 12- and 16-line address, create data-buses by combining EXP 4B, Bus Strips.



No soldering simply plug all standard components in and out, nickel-silver contacts allow Breadboard and components to be used over and over again without damage.

Adaptable accepts any component without adaptors or jumper leads, use 22-30 gauge solid wire for jumper leads.

Mix and Match large and small chips in the same circuit. Use 300 series for smaller and 0.3" pitch DIP's. 600 series for Microprocessors with 0.6" centre channel for full fan-out with larger chips.

Smallest to Biggest, remember CSC's Breadboards "snap-lock" together so you can start with a small idea and expand your ideas to as Big a Breadboarding area as you like.

Easy Permanent Mounting, using four screws from front or six self-tappers from rear. Vinyl-insulated backing lets you fasten to any surface.

Pick any project that you want to build, or any part of a project that you want to test or modify. Count up the number of IC's you need for the project. Then simply look up in the box opposite the Breadboard you require. If you need more than two bus-bars simply add the correct number of Quad-Bus Strips. **GET STARTED NOW FOR AS LITTLE AS £2.54.**

EXPERIMENTOR 350 £4.21

EXP 350, specifically designed for the hobbyist working with up to 3 x 14 DIP IC's. With 270 contact points including two 20-point bus-bars the EXP 350 accepts any size DIP with 0.3" spacing.

EXPERIMENTOR 300 £7.29

The hobbyists ideal Breadboard, accepts 6 x 14 DIP or 5 x 16 DIP, has 550 contact points including two 40-point bus-bars, accepts any size DIP with 0.3" spacing.

Marked Contact Points transfer component by component from letter/number position on Breadboard to finished P.C. Board or Wiring Table.

Ruggedly built of abrasion-resistant materials that withstand 100°C.

Tailor-Made Breadboards e.g. a project requires up to 5 x 14 DIP chips and needs up to six bus-bars. Which to buy? Easy from the table below select an EXP 300 plus an EXP 4B, total cost £10.58.

MODEL NO.	NUMBER OF CONTACT HOLES	IC CAPACITY (14-pin DIP's)	UNIT PRICE (includes Post & VAT)
EXP 300	550	6	£7.29
EXP 600	550	use with 0.6" PITCH DIP's	£7.88
EXP 350	270	3	£4.21
EXP 650	270	use with 0.6" PITCH DIP's	£4.70
EXP 325	130	1	£2.54
EXP 4B	FOUR 40-point Bus-Bars	—	£3.29

How to order. Telephone 0799 21682 and give your Access, American Express or Barclaycard number, and your order will be in the post that night. Or send your order, enclosing cheque, postal order, or stating credit card number and expiry date. For full catalogue showing all CSC products for the engineer and hobbyist send large S.A.E.

CONTINENTAL SPECIALTIES CORPORATION



Europe, Africa, Mid-East: **CSC UK LTD.** Dept. 5K Shire Hill Industrial Estate, Units 1 and 2 Saffron Walden, Essex CB11 3AQ Telephone Number: SAFFRON WALDEN 21682 TLX 817477


TO ALL TRADERS, MAIL ORDER HOUSES CONTACT MRS TINA KNIGHT FOR "PROFIT-PACKAGE" DETAILS

The latest kit innovation!

from **Sparkrite**

*Sparkrite -
was featured by Shaw Taylor
in "DRIVE IN"*

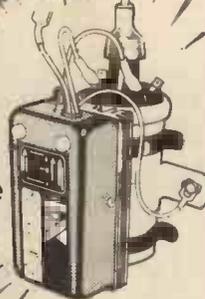the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption.

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE — Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing UK only.

Electronics Design Associates, Dept. PE 10, 82 Bath Street, Walsall, WS1 3DE. Phone: Walsall 614791

Electronics Design Associates, Dept. PE3
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Send SAE if brochure only required

Inc. V.A.T. and P.P. QUANTITY REQ'D.

Send cheque/PO's for

£

Cheque No.

X4 KIT	£16.65
TACHOPULSE SLAVE UNIT	£3.85

Please state polarity pos or neg earth.
Access or Barclaycard No.

VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS
MAIL ORDER SERVICE**

	tp	tp	tp	tp	tp	tp	tp		
AA119	0.10	BCY70	0.35	*MPSA56	0.26	*ZTX550	0.56	7405	0.56
AAV30	0.27	BCY71	0.17	*MPSU01	0.36	1N914	0.05	7406	0.40
AAV32	0.42	BCY72	0.13	*MPSU06	0.46	1N916	0.07	7407	0.40
AAZ13	0.18	BCZ11	1.50	*MPSU56	0.49	1N4001	0.06	7408	0.20
AAZ15	0.34	BD115	0.45	NE555	0.45	1N4002	0.06	7409	0.20
AAZ17	0.27	BD121	1.20	NKT401	2.00	1N4003	0.07	7410	0.16
AC107	0.60	BD123	1.20	NKT403	1.73	1N4004	0.05	7412	0.25
AC125	0.20	BD130	1.74	NKT404	0.30	1N4005	0.08	7413	0.32
AC126	0.20	BD131	0.35	OA5	0.95	1N4006	0.08	7416	0.32
AC127	0.20	BD132	0.38	OA7	0.55	1N4007	0.09	7417	0.32
AC128	0.20	BD135	0.34	OA10	0.60	1N4009	0.06	7420	0.17
AC141	0.25	BD136	0.34	OA47	0.14	1N4148	0.06	7422	0.20
AC141K	0.35	BD137	0.35	OA70	0.30	1N5400	0.13	7423	0.32
AC142	0.20	BD138	0.40	OA79	0.30	1N5401	0.13	7425	0.30
AC142K	0.20	BD139	0.43	OA81	0.30	1S44	0.04	7427	0.30
AC176	0.20	BD140	0.44	OA85	0.30	1S920	0.07	7428	0.43
AC187	0.20	BD144	2.00	OA90	0.08	1S921	0.07	7430	0.17
AC188	0.20	BD181	1.10	OA91	0.08	2G301	1.00	7432	0.30
ACV17	0.85	BD182	1.18	OA95	0.08	2G302	1.00	7433	0.36
ACV18	0.80	BD237	0.40	OA130	0.05	2G305	1.10	7437	0.32
ACV19	0.75	BD238	0.55	OA202	0.09	2N404	1.00	7438	0.32
ACV20	0.70	BDX10	0.91	OA211	1.00	2N696	0.25	7440	0.18
ACV21	0.75	BDX32	2.00	OA2200	1.00	2N697	0.25	7441A	0.85
ACV39	1.50	BDY20	1.25	OA2201	1.00	2N698	0.30	7442	0.72
AD149	0.70	BDY60	1.50	OA2206	1.00	2N705	1.20	7447A	0.90
AD181	0.45	BF115	0.09	OA2207	1.00	2N706	1.00	7450	0.18
AD182	0.45	BF152	0.18	OC16	2.00	2N708	0.20	7451	0.18
AF106	0.45	BF153	0.20	OC20	2.50	2N930	0.20	7453	0.18
AF114	0.35	BF154	0.17	OC22	2.50	2N1131	0.26	7454	0.18
AF115	0.35	BF159	0.23	OC23	2.75	2N1132	0.26	7460	0.18
AF116	0.35	BF160	0.16	OC24	3.00	2N1302	0.35	7470	0.35
AF117	0.35	BF167	0.25	OC25	0.95	2N1303	0.45	7472	0.33
AF139	0.40	BF173	0.20	OC26	0.90	2N1304	0.45	7473	0.36
AF188	1.20	BF177	0.24	OC28	2.00	2N1305	0.45	7474	0.40
AF239	0.45	BF178	0.24	OC29	2.00	2N1306	0.50	7475	0.54
AF211	2.75	BF179	0.25	OC35	1.50	2N1307	0.50	7476	0.40
AF212	2.75	BF180	0.30	OC36	1.50	2N1308	0.55	7480	0.55
ASV26	0.40	BF181	0.25	OC41	0.80	2N1309	0.55	7482	0.50
ASV27	0.40	BF182	0.30	OC42	0.75	2N1613	0.26	7483	0.90
ASZ15	1.25	BF183	0.25	OC43	2.25	2N1671	1.50	7484	1.00
ASZ16	1.25	BF184	0.25	OC44	0.60	2N1893	0.25	7486	0.35
ASZ17	1.25	BF185	0.25	OC45	0.55	2N2147	1.75	7490	0.52
ASZ20	1.50	BF194	0.09	OC71	0.55	2N2148	1.65	7491A	0.80
ASZ21	2.00	BF195	0.09	OC72	0.55	2N2218	0.77	7492	0.80
*AU110	1.70	*BF196	0.10	OC73	1.00	2N2219	0.24	7493	0.80
*AU113	1.70	*BF197	0.12	OC74	0.65	2N2220	0.18	7494	0.80
*ALY10	1.70	BF200	0.27	OC75	0.65	2N2221	0.18	7495	0.72
*BA145	0.13	*BF224	0.20	OC76	0.55	2N2222	1.18	7496	0.80
*BA148	0.13	BF244	0.28	OC77	1.20	2N2223	2.75	7497	3.00
BA154	0.09	BF257	0.24	OC81	0.65	2N2368	0.17	74100	1.50
BA155	0.09	BF258	0.24	OC82	0.65	2N2369A	0.21	74107	0.45
BA156	0.09	BF259	0.32	OC82	0.65	2N2484	0.20	74109	0.70
BAW62	0.05	BF336	0.30	OC83	0.65	2N2646	0.55	74110	0.50
BAX13	0.06	BF337	0.30	OC84	0.65	2N2904	0.25	74111	0.70
BAX16	0.09	BF338	0.31	OC122	1.50	2N2905	0.25	74116	1.75
BC107	0.12	BE521	3.96	OC123	1.75	2N2906	0.21	74118	1.00
BC108	0.12	BF528	0.20	OC139	0.65	2N2907	0.19	74120	0.85
BC109	0.12	*BFS61	0.20	OC140	0.65	*2N2924	0.21	74120	0.83
*BC113	0.13	*BFS98	0.20	OC141	3.25	*2N2925	0.22	74121	0.40
*BC114	0.13	BFW10	0.65	OC170	1.00	*2N2926	0.14	74122	0.60
*BC115	0.14	BFW11	0.65	OC171	1.00	2N3053	0.25	74123	1.00
*BC116	0.15	BFX84	0.22	OC200	1.50	2N3054	0.50	74125	0.55
*BC117	0.17	BFX85	0.23	OC201	1.75	2N3055	0.60	74126	0.55
*BC118	0.17	BFX86	0.23	OC202	1.75	2N3440	0.60	74128	0.60
*BC125	0.16	BFX88	0.21	OC203	1.75	2N3441	0.80	74132	0.70
*BC126	0.20	BFY50	0.26	OC204	2.50	2N3442	1.10	74138	0.55
*BC136	0.14	BFY51	0.26	OC205	2.50	2N3525	0.80	74141	0.80
*BC136	0.15	BFY52	0.26	OC206	2.50	2N3614	1.50	74142	2.30
*BC137	0.15	BFY64	0.26	OC207	1.75	2N3702	0.13	74151	0.60
*BC147	0.18	BFY90	0.21	OCP71	1.25	*2N3703	0.13	74145	2.50
*BC148	0.08	BSX19	0.21	ORP12	0.75	*2N3704	0.13	74145	0.90
*BC149	0.09	BSX20	0.20	*R2008B	1.75	*2N3705	0.13	74147	2.00
*BC157	0.09	BSX21	0.20	*R2009	2.25	*2N3706	0.13	74148	1.75
*BC158	0.08	BT106	1.25	*R2108	1.75	*2N3707	0.13	74150	1.60
*BC159	0.10	BTY79/4	3.19	T1C44	0.30	2N3708	0.13	74151	0.85
*BC167	0.12	BU206	2.25	T1C226D	1.20	2N3709	0.13	74152	0.85
BC170	0.11	*BU206	2.25	T1L209	0.20	2N3710	0.10	74155	0.85
BC171	0.10	*BU208	2.00	*T1P29A	0.41	2N3711	0.10	74156	0.85
BC172	0.10	BY100	0.45	*T1P30A	0.44	2N3711	1.75	74157	0.75
BC173	0.12	BY126	0.14	T1P31A	0.45	2N3712	0.90	74159	2.10
BC177	0.15	BY127	0.15	T1P32A	0.79	2N3713	1.90	74170	2.30
BC178	0.14	BZP12	0.18	T1P33A	0.69	2N3819	0.36	74172	4.40
BC179	0.16	Series		T1P34A	0.73	2N3820	0.45	74173	1.40
BC182	0.11	BZYBB	0.13	T1P41A	0.63	2N3823	0.55	74174	1.50
BC183	0.10	Series		T1P42A	0.70	*2N3866	0.72	74175	0.90
BC184	0.11	CRS1/05	0.45	T1P2955	0.87	*2N3904	0.13	74178	1.10
BC212	0.13	CRS1/40	0.60	T1P3055	0.56	*2N3905	0.13	74178	1.25
BC213	0.12	CRS3/05	0.45	*T1S43	0.45	*2N3906	0.13	74179	1.25
BC214	0.15	CRS3/40	0.75	*ZS140	0.25	*2N4058	0.14	74180	1.15
BC237	0.09	CRS3/60	0.90	*ZS170	0.21	*2N4059	0.10	74190	1.50
BC238	0.12	GEX86	1.50	*ZS178	0.54	*2N4060	0.12	74191	1.50
BC301	0.25	GEX541	1.75	*ZS271	0.23	*2N4061	0.12	74192	1.35
BC303	0.24	GJ5M	0.25	*ZS278	0.57	*2N4062	0.13	74193	1.35
BC307	0.10	GJ5M	0.75	*ZTX107	0.11	*2N4124	0.15	74194	1.25
*BC308	0.10	GL7M	0.75	*ZTX108	0.10	*2N4126	0.15	74195	1.00
*BC327	0.20	GMO378A	1.75	*ZTX109	0.12	*2N4286	0.20	74196	1.20
*BC328	0.18	*KS100A	0.45	*ZTX300	0.12	*2N4288	0.22	74197	1.10
*BC337	0.18	MJE340	0.80	*ZTX301	0.13	*2N4289	0.24	74198	2.25
*BC338	0.17	MJE370	1.17	*ZTX302	0.15	*2N4547	0.35	74199	2.25
BCY30	1.00	MJE371	0.61	*ZTX303	0.17	*2N4548	0.35	*76013N	1.75
BCY31	1.00	MJE520	0.52	*ZTX304	0.19	*2N4549	0.35		
BCY32	1.00	MJE521	0.55	*ZTX311	0.12				
BCY33	0.90	MJE2985	1.25	*ZTX314	0.20				
BCY34	0.90	MJE3055	0.78	*ZTX501	0.13				
BCY39	3.00	*MPF102	0.30	*ZTX501	0.14	7400	0.16	Plugs in socket	
BCY40	1.00	*MPF103	0.30	*ZTX502	0.16	7401	0.16	—low profile	
BCY42	0.25	*MPF104	0.30	*ZTX503	0.17	7402	0.16	8 pin DIL	0.15
BCY43	0.25	*MPF105	0.30	*ZTX504	0.20	7403	0.16	14 pin DIL	0.15
BCY58	0.16	*MPSA06	0.24	*ZTX531	0.20	7404	0.17	16 pin DIL	0.17

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7
Quotations for any types not listed S.A.E.
Post and Packing 25p per order + 8% V.A.T.
Items marked * 12½%

Prices correct
when going
to press

GLOUCESTER INDUSTRIAL SALES AND AUCTIONS LIMITED

Eastington Trading Estate, Nr. Stonehouse, Glos.

Tel: Stonehouse 4118

(M.5 Motorway - Exit No. 13)

We hold regular monthly auction sales of mostly new electronic and electrical goods consisting of transistors, triacs, integrated circuits, diodes, capacitors and resistors, together with fractional motors, transformers, power packs, etc., etc.

Next auction 27th March 1979.

Phone or write to be put on our auction mailing list.

Why not get in touch with our Mr. Jack Bailey and enquire about our terms for the disposal of your surplus stocks, etc., through our auctions.

FLADAR DUAL VOLTAGE TRANSFORMERS

PRIMARY 220-240 50HZ.
ALTERNATIVE SECONDARY VOLTAGE AND CURRENT
AVAILABLE BY SERIES OR PARALLEL CONNECTION

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
08FE08	8+6	0.8A EACH	1.50	50p	20FE24	24+24	0.4A EACH	2.60	70p
08FE08	6+6	0.6A EACH	1.80	50p	50FE24	24+24	0.8A EACH	3.10	70p
12FE08	6+6	1A EACH	2.00	60p	60FE24	24+24	1.2A EACH	3.60	85p
20FE08	6+6	1.6A EACH	2.60	70p	80FE24	24+24	1.5A EACH	4.50	100p
50FE08	6+6	3A EACH	3.10	70p	50FE28	28+28	0.75A EACH	3.10	70p
80FE08	6+6	4A EACH	3.60	85p	60FE28	28+28	1.1A EACH	3.60	85p
08FE09	9+9	0.3A EACH	1.50	50p	80FE28	28+28	1.4A EACH	4.50	100p
08FE09	9+9	0.5A EACH	1.80	50p	20FE30	30+30	0.35A EACH	2.60	70p
12FE09	9+9	0.75A EACH	2.00	60p	50FE30	30+30	0.75A EACH	3.10	70p
20FE09	9+9	1A EACH	2.60	70p	60FE30	30+30	1A EACH	3.60	85p
50FE09	9+9	2.5A EACH	3.10	70p	80FE30	30+30	1.2A EACH	4.50	100p
80FE09	9+9	3A EACH	3.60	85p					
06FE12	12+12	0.25A EACH	1.50	50p	MULTI-TAP RANGE, VOLTAGE				
08FE12	12+12	0.3A EACH	1.80	50p	AVAILABLE 3, 4, 5, 6, 8, 9, 10, 12, 15, 18,				
12FE12	12+12	0.5A EACH	2.00	60p	12-0-12 OR 15-0-15				
20FE12	12+12	0.8A EACH	2.60	70p	30FE30	0-12-15	1A	3.40	70p
50FE12	12+12	2A EACH	3.10	70p		24-30			
80FE12	12+12	2.5A EACH	3.60	85p	80FE36	0-12-15	2A	3.70	85p
80FE12	12+12	3A EACH	4.50	100p		24-30			
08FE15	15+15	0.2A EACH	1.50	50p	80FE36	0-12-15	3A	4.50	100p
08FE15	15+15	0.25A EACH	1.80	50p		24-30			
12FE15	15+15	0.4A EACH	2.00	60p	100FE40	0-12-15	4A	5.60	115p
20FE15	15+15	0.6A EACH	2.60	70p		24-30			
50FE15	15+15	1.6A EACH	3.10	70p	CENTRE TAP SECONDARY				
80FE15	15+15	2A EACH	3.60	85p	FE06	6-0-6	1A EACH	2.00	60p
80FE15	15+15	3A EACH	4.50	100p	FE09	9-0-9	1A EACH	2.60	70p
08FE20	20+20	0.15A EACH	1.50	50p	FE12	12-0-12	1A EACH	2.60	70p
08FE20	20+20	0.2A EACH	1.80	50p	FE18	15-0-15	1A EACH	3.10	70p
12FE20	20+20	0.25A EACH	2.00	60p	FE20	20-0-20	1A EACH	3.10	70p
20FE20	20+20	0.5A EACH	2.60	70p	60FE52	26-0-26	1A EACH	3.60	100p
50FE20	20+20	1.2A EACH	3.10	70p	60FE28	28-0-28	1A EACH	3.60	100p
80FE20	20+20	1.5A EACH	3.60	85p	60FE60	30-0-30	1A EACH	3.80	100p
80FE20	20+20	2A EACH	4.50	100p	100FE26	26-0-26	2A EACH	5.15	115p
					100FE30	30-0-30	2A EACH	5.15	115p
					100FE36	36-0-36	2A EACH	5.15	115p
CHARGER TRANSFORMER					AIR CORED AUDIO CROSS OVER COILS				
48FE12	0-8-12	4A	3.10	70p	FE01	0.1mH	0.26	20p	
66FE12	0-8-12	5A	3.80	85p	FE03	0.3mH	0.26	20p	
70FE12	0-8-12	6A	4.66	100p	FE05	0.5mH	0.30	20p	
08FE24	24+24	0.15A EACH	1.80	50p	FE10	1.0mH	0.60	25p	
12FE24	24+24	0.2A EACH	2.00	60p	FE26	2.0mH	0.75	30p	

FLADAR ELECTRIC
P.O. BOX 19
WESTCLIFF-ON-SEA
ESSEX. 0702-613314

TRADE ENQUIRIES
WELCOME
PLEASE ENQUIRE
FOR OTHER TYPES
NOT SHOWN

PAYMENT TERMS:
C.W.O. Cheques,
Postal Orders
Please Add 8% VAT
After post & packing.

GREENWELD

443 Millbrook Road Southampton

SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted

from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

OSCILLOSCOPES

We have available from stock the following SCOPEX models: 4D10A - DC-10MHz; 10mV sensitivity; Stab Power supplies; Dual beam; 3% accuracy; Excellent value at £214 inc VAT and Carr.
456 - OC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for £150 inc VAT and Carr.

NIXIE TUBES

ITT Type GNP7AH. Supplied with data 60p each
7-seg display, wire ended tube NEC type LD8012 1/2" high, with data 65p
7-seg display, (as above) Futaba type DG-10Q1 0.3" char. 70p with data

PUSH BUTTON BANKS

Illustrated list of types from 30p in our Bargain List No 6 - Send SAE.

BC182B OFFER

Special Offer for quantity users 1k .035VAT; 5k .032VAT. Price negotiable on 10k. Approx 70k available.

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices - signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of £1.25/1000 - or a bag of 2500 for £2.25. Bag of 10,000 £8. Box of 25,000 £17.50. Box of 100,000 £60.

Disc Ceramic caps - big variety of values and voltages from a few pF to 2.2uF; 3V to 3kV. 200 for £1; 1000 £4.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- ★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- ★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!
- ★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%. 10 of each value 22pF to 1000pF. Total 210. £3.35

K002 Extended range, 22pF to 0.1uF. 330 values £4.90
K003 Polyester capacitors, 10 each of these values: 0-01, 0-015, 0-022, 0-033, 0-047, 0-068, 0-1, 0-15, 0-22, 0-33, 0-47uF. 110 altogether for £4.75

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

K006 Tantulum bead capacitors. 10 each of the following: 0-1, 0-15, 0-22, 0-33, 0-47, 0-68, 1, 2, 2.2, 3, 4.7, 6.8, 10, all 35V; 10/25/15/16 22/16 33/10 47/6 100/3. Total 170 tans for £14.20

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100uF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000uF. Total 100 for £6.30

K021 Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for £15.30.

K042 As above but 5 of each value £8.70

TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2.40. 9-0-9V 75mA 85p; 1A £2.10. Multitapped type: 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.90. 20V 2A £3.90; 25V 1A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50;

RELAYS

W847 Low profile PC mntg 10x33x20mm 6V coil, SPCO 3A contacts. 93p
W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A. 95p

W839 50V ac (24V DC) coil. 11 pin plug in type. 3 pole c/o 10A contacts Only 85p

W846 Open construction mains relay. 3 sets 10A c/o contacts, £1.20

W877 675R 12-27V DPCO 23x20x10mm sealed can 85p

W880 230V ac DPCO 10A contacts, enclosed case £1.30

W830 200R 6-12V DPCO 23 x 20 x 10mm sealed can 88p

Send SAE for our relay list - 84 types listed and illustrated.

AMPLIFIER KIT £1-75

Mono gen. purpose amp with tone and Vol/on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add £2.20 for suitable transformer.) Blue vinyl covered aluminium case to suit (W372) £1-30

RESISTOR PACK

Carbon Film 5% mostly 1/4W, few 1/2W resistors. Brand new, but have preformed leads. Ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of £2.50 per 1000; £11 per 5000.

DIN SOCKET OFFER

2 pin switched speaker socket, PC mounting; 5 pin 180° PC mntg or chassis mntg (clip fix). All the same price, any mix: 10 for 70p 25 for £1-60 100 for £5-50.

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock \bar{v} ; Fully TTL compatible; Low power dissipation. Supplied with data £2-75

MISCELLANEOUS IC's

Supplied with data if requested. MC3302 quad comp. 120p; 710 diff comp. (T099) 40p; 2N1034E precision timer £2-25; LM711 Dual diff comp 66p; LM1303 dual stereo pre-amp 75p; MC1469R voltage reg £1-50; UPC1025H audio £3-50; 575C2 audio £2-88; TDA2640 audio £2-92; SN75110 dual line driver 70p; MC8500 CRCC gen POA

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!

32 way 72p; 40 way 90p

HEAT SINK OFFER

Copper T05 sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1000 for £25

74 SERIES PACK

Selection of boards containing many different 74 series IC's. 20 for £1; 50 for £2.20; 100 for £4.

THE NEW 1978-9 GREENWELD CATALOGUE


FEATURES INCLUDE:

- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

ANNOUNCING

THE NEW EUROBREADBOARD

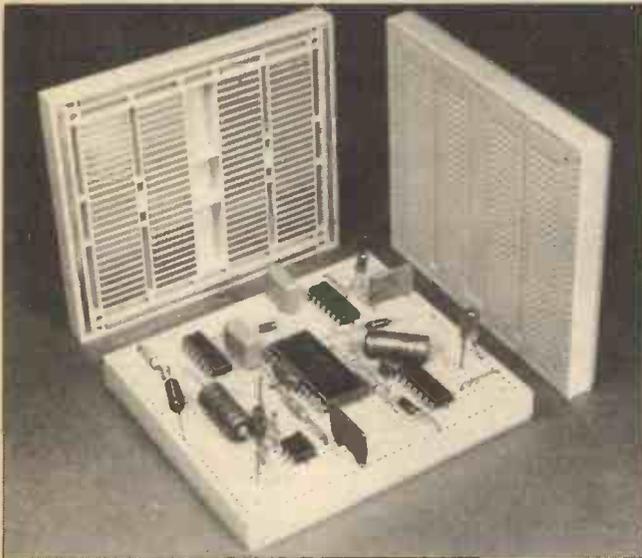

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points.

4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

Double-sided, nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m.ohms)

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

What other breadboarding system has as many individual contacts, offers all these features and only costs £5.80 inclusive of VAT and P.P. - NONE.

At £5.80 each The EuroBreadBoard is unique value for money. At £11 for 2 The EuroBreadBoard is an indispensable design aid.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent, DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

Please send me 1 EuroBreadBoard @ £5.80 Please
or 2 EuroBreadBoards @ £11.00 Tick

(All prices include VAT and P.P., but add 15% for overseas orders).

Name

Company

Address

Tel. No. PE/3/79

Please make cheque/P.O.'s payable to David George Sales


CHINAGLIA DINO—ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

THE

DOLOMITI

20kΩ/V a.c. and d.c.

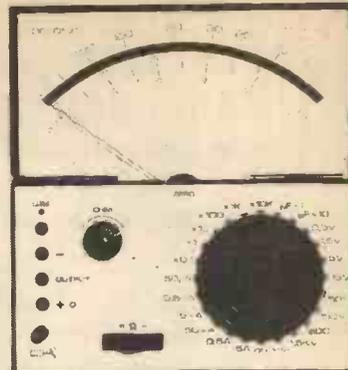A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED



Accuracy: D.C. ranges, ± 2.0%, A.C. & Ω ranges ± 2.5%

39 ranges: d.c. V, 0-150mV, 500mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1.5kV; d.c.I, 0-50μA, 500μA, 5mA, 50mA, 0.5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1.5kV; a.c.I, 5mA, 50mA, 0.5A, 5A; dB - 10 to + 65 in 6 ranges; Ω 0-0.05kΩ, 5kΩ, 50kΩ, 500kΩ, 5MΩ, 50MΩ, pF 50kPF, 500kPF.

Automatic overload protection and high current range fusing.

Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £50.00 incl. VAT (£1 P. & P.)

30kV Probe £12.85 Incl. VAT


For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

ALCON Instruments Ltd.

19 MULBERRY WALK, LONDON SW3 6DZ TEL: 01-352 1897

LOOK!

New 12" Monitor for your Micro

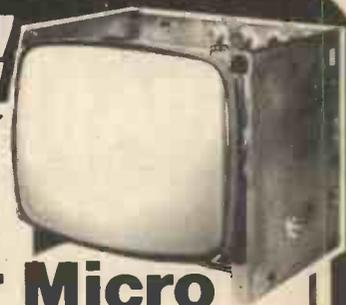

or CCTV application
Uncased £60
Cased £85

Available cased or uncased for OEM's

The above prices are for 1 off orders (plus VAT)

6800 Based Micro Computer now available - KIT £220 (plus VAT)
INCLUDING Tiny Basic and on board Prom Programmer
Power Supply £20 extra (+VAT)

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM MIDDLESEX - Telephone: 01-891 1923

TRANSISTORS

TYPE	PRICE	BC108A	0.07	BC177B	0.12
AC107	0.23	BC108	0.07	BC178B	0.12
AC125	0.17	BC109	0.06	BC179	0.12
AC126	0.17	BC109B	0.07	BC182A	0.09
AC127	0.16	BC109C	0.07	BC182B	0.09
AC127K	0.23	BC113	0.12	BC183A	0.09
AC128	0.14	BC114	0.15	BC183LA	0.09
AC128K	0.26	BC116	0.13	BC183LB	0.10
AC128/1760.42		BC117	0.15	BC184	0.08
AC142	0.18	BC118	0.12	BC184L	0.09
AC153	0.55	BC119	0.25	BC184LB	0.10
AC158	0.50	BC125	0.15	BC186	0.19
AC176	0.16	BC125B	0.16	BC187	0.19
AC187	0.50	BC126	0.15	BC20A	0.08
AC187K	0.55	BC136	0.15	BC204B	0.08
AC188K	0.55	BC137	0.15	BC206	0.10
ACY20	1.02	BC138	0.30	BC206B	0.10
ACY22	1.02	BC140	0.27	BC207	0.10
AD142	0.87	BC141	0.29	BC209B	0.09
AD143	0.87	BC142	0.29	BC212A	0.10
AD149	0.65	BC147	0.06	BC213L	0.10
AD161	0.35	BC147B	0.07	BC214L	0.10
AD161/1620.70		BC148	0.06	BC237A	0.16
AD162	0.35	BC148A	0.07	BC237C	0.21
AD262	0.36	BC148B	0.07	BC238	0.15
AD263	0.36	BC149	0.06	BC238B	0.16
ADY26	4.74	BC157	0.06	BC239C	0.18
ADZ11	4.05	BC157A	0.07	BC239C	0.18
AF106	0.45	BC158	0.07	BC251A	0.15
AF109R	0.36	BC158A	0.08	BC251B	0.17
AF124	0.25	BC158V1	0.09	BC252A	0.15
AF125	0.25	BC159	0.06	BC252B	0.17
AF126	0.25	BC159A	0.07	BC252C	0.20
AF127	0.25	BC159B	0.07	BC258	0.20
AF139	0.32	BC161	0.25	BC261A	0.10
AF178	0.30	BC167	0.06	BC262	0.20
AF179	0.30	BC168	0.06	BC267A	0.21
AF200	0.36	BC169	0.06	BC267B	0.22
AF201	0.39	BC170B	0.07	BC268	0.21
AS73	0.30	BC170C	0.07	BC304	0.25
AS215	0.60	BC171	0.06	BC307	0.15
AS216	0.60	BC171A	0.07	BC307A	0.15
AS217	0.60	BC171B	0.07	BC307B	0.15
AU103	0.90	B172	0.06	BC308	0.15
AU107	1.00	BC172A	0.07	BC309A	0.15
AU110	0.90	BC172B	0.07	BC317B	0.15
AU210	0.90	BC172C	0.07	BC322	0.10
BC107	0.06	BC173	0.06	BC327	0.16
BC107A	0.07	BC173B	0.07	BC328	0.16
BC107B	0.07	BC174B	0.07	BC337	0.16
BC108	0.06	BC177A	0.12	BC338	0.16

TTL

TYPE	PRICE	OC71	0.09	2N2188	0.20
OC74	0.10 <td>2N2218A</td> <td>0.22 <td>7400</td> <td>.12</td> </td>	2N2218A	0.22 <td>7400</td> <td>.12</td>	7400	.12
OC75	0.10 <td>2N2222</td> <td>0.18 <td>7401</td> <td>.12</td> </td>	2N2222	0.18 <td>7401</td> <td>.12</td>	7401	.12
OC82	0.48 <td>2N2222A</td> <td>0.20 <td>7402</td> <td>.12</td> </td>	2N2222A	0.20 <td>7402</td> <td>.12</td>	7402	.12
OC139	0.80 <td>2N2270</td> <td>0.39 <td>7403</td> <td>.12</td> </td>	2N2270	0.39 <td>7403</td> <td>.12</td>	7403	.12
OC203	2.50 <td>2N2368</td> <td>0.10 <td>7404</td> <td>.13</td> </td>	2N2368	0.10 <td>7404</td> <td>.13</td>	7404	.13
OC207	2.70 <td>2N2484</td> <td>0.18 <td>7405</td> <td>.13</td> </td>	2N2484	0.18 <td>7405</td> <td>.13</td>	7405	.13
OC1072	2.50 <td>2N2804</td> <td>0.18 <td>7406</td> <td>.29</td> </td>	2N2804	0.18 <td>7406</td> <td>.29</td>	7406	.29
OC1074	2.50 <td>2N2806</td> <td>0.18 <td>7407</td> <td>.29</td> </td>	2N2806	0.18 <td>7407</td> <td>.29</td>	7407	.29
R2008B	2.10 <td>2N3053</td> <td>0.15 <td>7408</td> <td>.14</td> </td>	2N3053	0.15 <td>7408</td> <td>.14</td>	7408	.14
TIP30	0.36 <td>2N3117</td> <td>1.00 <td>7409</td> <td>.14</td> </td>	2N3117	1.00 <td>7409</td> <td>.14</td>	7409	.14
TIP31	0.45 <td>2N3440</td> <td>0.70 <td>7410</td> <td>.13</td> </td>	2N3440	0.70 <td>7410</td> <td>.13</td>	7410	.13
TIP31A	0.45 <td>2N3638</td> <td>0.15 <td>7411</td> <td>.18</td> </td>	2N3638	0.15 <td>7411</td> <td>.18</td>	7411	.18
TIP32	0.45 <td>2N3638A</td> <td>0.16 <td>7412</td> <td>.21</td> </td>	2N3638A	0.16 <td>7412</td> <td>.21</td>	7412	.21
TIP33	0.60 <td>2N3643</td> <td>0.24 <td>7413</td> <td>.25</td> </td>	2N3643	0.24 <td>7413</td> <td>.25</td>	7413	.25
TIP42	0.60 <td>2N3692</td> <td>0.24 <td>7414</td> <td>.54</td> </td>	2N3692	0.24 <td>7414</td> <td>.54</td>	7414	.54
TIP2955	0.65 <td>2N3705</td> <td>0.06 <td>7415</td> <td>.27</td> </td>	2N3705	0.06 <td>7415</td> <td>.27</td>	7415	.27
TIS90	0.18 <td>2N3706</td> <td>0.06 <td>7416</td> <td>.27</td> </td>	2N3706	0.06 <td>7416</td> <td>.27</td>	7416	.27
2N3448	0.30 <td>2N3707</td> <td>0.06 <td>7417</td> <td>.27</td> </td>	2N3707	0.06 <td>7417</td> <td>.27</td>	7417	.27
2N404	0.45 <td>2N3711</td> <td>0.06 <td>7418</td> <td>.25</td> </td>	2N3711	0.06 <td>7418</td> <td>.25</td>	7418	.25
2N524	0.48 <td>2N3819</td> <td>0.20 <td>7419</td> <td>.22</td> </td>	2N3819	0.20 <td>7419</td> <td>.22</td>	7419	.22
2N526	0.48 <td>2N3899</td> <td>3.00 <td>7420</td> <td>.25</td> </td>	2N3899	3.00 <td>7420</td> <td>.25</td>	7420	.25
2N527	0.48 <td>2N3904</td> <td>0.06 <td>7421</td> <td>.28</td> </td>	2N3904	0.06 <td>7421</td> <td>.28</td>	7421	.28
2N685	3.50 <td>2N3905</td> <td>0.06 <td>7422</td> <td>.34</td> </td>	2N3905	0.06 <td>7422</td> <td>.34</td>	7422	.34
2N705	1.00 <td>2N3906</td> <td>0.06 <td>7423</td> <td>.34</td> </td>	2N3906	0.06 <td>7423</td> <td>.34</td>	7423	.34
2N706	1.00 <td>2N4037</td> <td>0.25 <td>7424</td> <td>.32</td> </td>	2N4037	0.25 <td>7424</td> <td>.32</td>	7424	.32
2N706A	1.10 <td>2N4058</td> <td>0.10 <td>7425</td> <td>.32</td> </td>	2N4058	0.10 <td>7425</td> <td>.32</td>	7425	.32
2N708	0.12 <td>2N4222A</td> <td>0.65 <td>7426</td> <td>.25</td> </td>	2N4222A	0.65 <td>7426</td> <td>.25</td>	7426	.25
2N1039	1.10 <td>2N4348</td> <td>2.00 <td>7427</td> <td>.25</td> </td>	2N4348	2.00 <td>7427</td> <td>.25</td>	7427	.25
2N1059	1.15 <td>2N4448</td> <td>1.50 <td>7428</td> <td>.34</td> </td>	2N4448	1.50 <td>7428</td> <td>.34</td>	7428	.34
2N1101	0.15 <td>2N4914</td> <td>3.50 <td>7429</td> <td>.34</td> </td>	2N4914	3.50 <td>7429</td> <td>.34</td>	7429	.34
2N1102	0.15 <td>2N5172</td> <td>0.25 <td>7430</td> <td>.34</td> </td>	2N5172	0.25 <td>7430</td> <td>.34</td>	7430	.34
2N1132	0.20 <td>2N5245</td> <td>0.30 <td>7431</td> <td>.28</td> </td>	2N5245	0.30 <td>7431</td> <td>.28</td>	7431	.28
2N1304	0.50 <td>2N5296</td> <td>0.40 <td>7432</td> <td>.28</td> </td>	2N5296	0.40 <td>7432</td> <td>.28</td>	7432	.28
2N1305	0.50 <td>2N5458</td> <td>0.25 <td>7433</td> <td>.28</td> </td>	2N5458	0.25 <td>7433</td> <td>.28</td>	7433	.28
2N1307	0.50 <td>2N5496</td> <td>0.60 <td>7434</td> <td>.32</td> </td>	2N5496	0.60 <td>7434</td> <td>.32</td>	7434	.32
2N1309	0.50 <td>2N5670</td> <td>0.65 <td>7435</td> <td>.32</td> </td>	2N5670	0.65 <td>7435</td> <td>.32</td>	7435	.32
2N1613	1.10 <td>2N5926</td> <td>0.55 <td>7436</td> <td>.32</td> </td>	2N5926	0.55 <td>7436</td> <td>.32</td>	7436	.32
2N1671	1.10 <td>2N6123</td> <td>0.65 <td>7437</td> <td>.32</td> </td>	2N6123	0.65 <td>7437</td> <td>.32</td>	7437	.32
2N1671B	2.20 <td>2S003</td> <td>0.75 <td>7438</td> <td>.32</td> </td>	2S003	0.75 <td>7438</td> <td>.32</td>	7438	.32
2N1711	0.20 <td>2S307</td> <td>0.90 <td>7439</td> <td>.32</td> </td>	2S307	0.90 <td>7439</td> <td>.32</td>	7439	.32
2N1893	0.25 <td>2S304</td> <td>0.90 <td>7440</td> <td>.28</td> </td>	2S304	0.90 <td>7440</td> <td>.28</td>	7440	.28
2N1905	0.25 <td>2S305</td> <td>0.90 <td>7441</td> <td>.28</td> </td>	2S305	0.90 <td>7441</td> <td>.28</td>	7441	.28
2N1990	0.25 <td>2S323</td> <td>1.00 <td>7442</td> <td>.28</td> </td>	2S323	1.00 <td>7442</td> <td>.28</td>	7442	.28
2N2060	1.00 <td>2S732</td> <td>1.00 <td>7443</td> <td>.28</td> </td>	2S732	1.00 <td>7443</td> <td>.28</td>	7443	.28

CMOS

TYPE	PRICE	74161	.80	4000	.15
7400	.12	74163	.80	4001	.15
7401	.12	74164	.90	4002	.20
7402	.12	74165	.90	4006	.95
7403	.12	74166	1.00	4007	.20
7404	.13	74167	2.00	4008	.90
7405	.13	74168	2.00	4009	.46
7406	.29	74169	3.50	4010	.50
7407	.29	74170	4.00	4011	.15
7408	.14	74171	1.90	4012	.15
7409	.14	74172	1.90	4013	.35
7410	.13	74173	1.90	4014	.85
7411	.18	74174	5.50	4015	.80
7412	.21	74175	9.00	4016	.65
7413	.25	74176	2.00	4017	.55
7414	.54	74177	1.10	4018	.60
7415	.27	74178	1.10	4019	.45
7416	.27	74179	1.10	4020	.85
7417	.27	74180	1.10	4021	.85
7418	.25	74181	1.10	4022	.85
7419	.22	74182	1.10	4023	.20
7420	.25	74183	1.10	4024	.68
7421	.28	74184	1.10	4025	.20
7422	.34	74185	1.10	4026	1.35
7423	.34	74186	1.10	4027	.85
7424	.34	74187	1.10	4028	.70
7425	.32	74188	1.10	4029	.90
7426	.32	74189	1.10	4030	.50
7427	.32	74190	1.10	4031	.40
7428	.32	74191	1.10	4032	.88
7429	.32	74192	1.10	4033	.88
7430	.32	74193	1.10	4034	.88
7431	.32	74194	1.10	4035	.88
7432	.32	74195	1.10	4036	.88
7433	.32	74196	1.10	4037	.88
7434	.32	74197	1.10	4038	.88
7435	.32	74198	1.10	4039	.88
7436	.32	74199	1.10	4040	.88
7437	.32	74200	1.10	4041	.88
7438	.32	74201	1.10	4042	.88
7439	.32	74202	1.10	4043	.88
7440	.32	74203	1.10	4044	.88
7441	.32	74204	1.10	4045	.88
7442	.32	74205	1.10	4046	.88
7443	.32	74206	1.10	4047	.88
7444	.32	74207	1.10	4048	.88
7445	.32	74208	1.10	4049	.88
7446	.32	74209	1.10	4050	.88
7447	.32	74210	1.10	4051	.88
7448	.32	74211	1.10	4052	.88
7449	.32	74212	1.10	4053	.88
7450	.32	74213	1.10	4054	.88
7451	.32	74214	1.10	4055	.88
7452	.32	74215	1.10	4056	.88
7453	.32	74216	1.10	4057	.88
7454	.32	74217	1.10	4058	.88
7455	.32	74218	1.10	4059	.88
7456	.32	74219	1.10	4060	.88
7457	.32	74220	1.10	4061	.88
7458	.32	74221	1.10	4062	.88
7459	.32	74222	1.10	4063	.88
7460	.32	74223	1.10	4064	.88
7461	.32	74224	1.10	4065	.88
7462	.32	74225	1.10	4066	.88
7463	.32	74226	1.10	4067	.88
7464	.32	74227	1.10	4068	.88
7465	.32	74228	1.10	4069	.88
7466	.32	74229	1.10	4070	.88
7467	.32	74230	1.10	4071	.88
7468	.32	74231	1.10	4072	.88
7469	.32	74232	1.10	4073	.88
7470	.32	74233	1.10	4074	.88
7471	.32	74234	1.10	4075	.88
7472	.32	74235	1.10	4076	.88
7473	.32	74236	1.10	4077	.88
7474	.32	74237	1.10	4078	.88
7475	.32	74238	1.10	4079	.88
7476	.32	74239	1.10	4080	.88
7477	.32	74240	1.10	4081	.88
7478	.32	74241	1.10	4082	.88
7479	.32	74242	1.10	4083	.88
7480	.32	74243	1.10	4084	.88
7481	.32	74244	1.10	4085	.88
7482	.32	74245	1.10	4086	.88
7483	.32	74246	1.10	4087	.88
7484	.32	74247	1.10	4088	.88
7485	.32	74248	1.10	4089	.88
7486	.32	742			

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON

Tick or state subject of interest.
Post to address below.

- | | | |
|--|--|---|
| ELECTRICAL & ELECTRONICS | Radio, Servicing & Repairs <input type="checkbox"/> | Painting & Decorating <input type="checkbox"/> |
| Practical Radio & Electronics (with KIT) <input type="checkbox"/> | Radio Amateur's Exam. <input type="checkbox"/> | MECHANICAL |
| Electronic Engineering Certificate <input type="checkbox"/> | AUTO & AERO | A.M.S.E. (Mech.) <input type="checkbox"/> |
| General Elect. Eng. Certificate <input type="checkbox"/> | Motor Mechanics <input type="checkbox"/> | General Mech. Eng. <input type="checkbox"/> |
| C. & G. Elect. Installations <input type="checkbox"/> | C. & G. Motor V. Mechanics <input type="checkbox"/> | Inst. Engineers & Technicians <input type="checkbox"/> |
| Elect. Install. & Work <input type="checkbox"/> | General Auto Engineering <input type="checkbox"/> | Maintenance Engineering <input type="checkbox"/> |
| C. & G. Elect. Technicians <input type="checkbox"/> | A.M.I.M.I. <input type="checkbox"/> | Welding <input type="checkbox"/> |
| | Air Registration Board Certs. <input type="checkbox"/> | |
| | M.A.A./I.M.I. Dip. <input type="checkbox"/> | MANAGEMENT & PRODUCTION |
| RADIO & TELECOMMUNICATIONS | CONSTRUCTIONAL | Computer Programming <input type="checkbox"/> |
| Colour TV Servicing <input type="checkbox"/> | Heating, Ventilating & Air Conditioning <input type="checkbox"/> | Inst. of Cost & Managements Accts. <input type="checkbox"/> |
| C. & G. Telecoms. Technician's Cert. <input type="checkbox"/> | Architectural Draughtsmanship & Design <input type="checkbox"/> | DRAUGHTSMANSHIP & DESIGN |
| C. & G. Radio, TV & Electronics Mech. Cert. <input type="checkbox"/> | L.I.O.B. <input type="checkbox"/> | General Draughtsmanship <input type="checkbox"/> |
| Radio & TV Engineering Course <input type="checkbox"/> | Carpentry & Joinery <input type="checkbox"/> | A.M.I.E.D. <input type="checkbox"/> |
| | Plumbing Technology <input type="checkbox"/> | Electrical Draughtsmanship <input type="checkbox"/> |
| | General Building <input type="checkbox"/> | |



G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPE 24, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, London EC2Y 9DT. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

TRANSISTORS.

P	P	P	P	P	P	P	P	P	P	Bridge Rectifiers	
AC126	17	BCY34	66	TIP36A	165	7421	20	74183	55	4073	16
AC127	16	BCY59	24	TP41A	54	7422	15	74184	60	4081	14
AC128	14	BCY70	14	TP42A	60	7427	22	74185	60	4082	14
128/178*	35	BCY71	14	TP2955	65	7428	25	74186	75	4086	59
AC141	24	BD115	30	TP3055	55	7430	12	74173	80	4510	60
AC142	18	BD121	70	ZTX108	12	7432	20	74174	60	4511	70
AC151	22	BD123	80	ZTX109	12	7433	24	74175	60	4516	64
AC152	22	BD124	77	ZTX300	14	7437	20	74176	50	4518	65
AC153	26	BD131	35	ZTX500	16	7438	20	74177	50	4520	65
AC176	16	BD132	35	2N706	10	7440	12	74180	80	4528	55
AC187	23	BD135	30	2N1131	20	7441	46	74181	130		
AC188	20	BD136	30	2N1132	20	7442	40	74182	50	LINEARS	
AD149	66	BD137	30	2N1302	20	7443	60	74190	70		
AD181	35	BD138	30	2N1304	20	7444	60	74191	70	710CN	40
AD162	35	BD139	30	2N1305	20	7445	64	74192	60	741-8	22
AF114	23	BD140	30	2N1306	27	7446	50	74193	60	747C-14	50
AF118	30	BF115	25	2N1308	33	7447	50	74194	55	748C-8	30
AF125	25	BF167	25	2N1613	18	7448	50	74195	50	CA3011	80
AF126	25	BF173	20	2N1711	20	7450	12	74196	50	CA3018	80
AF127	25	BF178	25	2N1893	25	7451	42	74197	50	CA3028A	85
AF139	32	BF179	25	2N2217	24	7453	12	74198	100	CA3035	140
AF186	54	BF180	20	2N2219	21	7454	12	74199	100	CA3036	120
AF239	40	BF181	20	2N2369	15	7460	14			CA3046	75
ASV53	33	BF182	20	2N2483	25	7470	24	CMOS		CA3054	110
ASV54	33	BF183	20	2N2484	18	7472	24	4000	12	CA3080	70
ASV55	33	BF184	20	2N2505	19	7474	25	4001	12	CA3140E	51
BC107	7	BF185	20	2N2506	19	7474	25	4002	12	LM301AN	28
BC108	7	BF194	7	2N2907	20	7475	25	4006	68	LM308N	64
BC109	7	BF196	7	2N2926	10	7476	25	4007	14	LM380N	61
BC113	12	BF197	7	2N3053	15	7480	40	4008	64	LM381N	20
BC117	15	BF198	7	2N3054	44	7485	60	4009	30	NE555	25
BC119	25	BF200	33	2N3055	44	7488	24	4010	35	NE555	60
BC140	27	BF224	16	2N3702	8	7490	25	4011	12	78A641	143
BC142	20	BF257	16	2N3703	8	7491	40	4012	12	78A800	70
BC143	24	BF258	28	2N3704	8	7492	35	4013	30	78A810	100
BC147	7	BF259	28	2N3706	8	7493	30	4014	60		
BC149	7	BF339	18	2N3707	8	7494	51	4015	50	0100ES	6
BC157	7	BF340	18	2N3710	8	7495	45	4016	30		
BC158	7	BF379	18	2N3711	8	7496	45	4017	50	BY127	16
BC159	7	BF380	27	2N3772	172	7497	120	4018	55	DA47	10
BC168	7	BFX29	20	2N3773	275	74100	80	4019	40	OA91	15
BC170	7	BFX30	32	2N3888	54	74105	40	4020	50	OA200	6
BC171	7	BFX85	20	2N3904	8	74107	25	4021	60	GA202	9
BC172	7	BFX86	27	2N4081	12	74109	30	4022	50	IN4148	4
BC173	7	BFX87	20	2N4082	12	74110	46	4023	12	IN5915	5
BC182	9	BFY50	15			74118	75	4024	45	IN4001	4
BC183	9	BFY51	12	TTL		74121	25	4025	12	IN4002	4
BC184	9	BFY53	17	7400	10	74122	33	4027	30	IN4003	5
BC186	19	BSX19	20	7401	10	74123	40	4028	45	IN4004	5
BC187	19	BSX20	18	7402	10	74125	35	4029	50	IN4005	7
BC207	10	BUZ05	130	7403	10	74126	35	4030	30	IN4006	8
BC212	10	BUZ08	160	7404	12	74132	45	4035	60	IN4007	9
BC213	10	OC25	75	7405	12	74141	50	4041	57	IN5400	13
BC214	10	OC28	87	7406	24	74142	180	4042	54	IN5401	14
BC237	12	OC35	76	7407	24	74145	55	4043	54	IN5402	15
BC238	14	OC71	16	7408	12	74150	65	4044	50	IN5404	20
BC301	30	OC72	26	7409	12	74151	45	4047	80		
BC303	30	OC84	42	7410	12	74153	45	4048	50		
BC328	13	TP29	37	7411	15	74154	70	4049	25		
BC338	13	TP30	35	7412	15	74155	45	4050	25		
BC547	11	TP31	45	7413	25	74156	46	4056	35		
BC548	11	TP32	45	7414	45	74157	45	4069	12		
BC549	11	TP33	58	7416	24	74180	55	4070	12		
BC557	11	TP34	54	7417	24	74181	55	4071	12		
BCY30	60	TP35A	168	7420	12	74182	55	4072	12		

SAE for complete list.
Add 25p for p. & p.
DELTA TECH
62 NAYLOR ROAD
LONDON N20 0HN

Clef Kits -



Designer approved quality kits for Electronic Musical Instrument Construction.

JOANNA 72 & 88 PIANOS
Six and 7 1/2 Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. A new physical layout has been adopted to simplify construction.

P.E. STRING ENSEMBLE
The only kit available to the proven A. J. Boothman Design for this versatile String Machine.

Send S.A.E. to -
Clef Products (Dept P.E.) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU

L&B

A RANGE OF HIGH QUALITY AUDIO POWER AMPLIFIERS MODULES AT VERY COMPETITIVE PRICES. FAST DESPATCH SERVICE, BULK PURCHASE DISCOUNTS.

- LB25** 25W. RMS. into 4Ω. 25 Hz-50 KHZ. 0.1% THD (TYP), 94dB S/N £ 6.80 *
- LB100** 100W. RMS. into 4Ω. 10 Hz-30 KHZ. 0.4% THD (TYP), 80 dB S/N £14.19
- LB250** 250W. RMS. into 4Ω. 10 Hz-25 KHZ. 0.3% THD (TYP), 110 dB S/N £26.44

Please include VAT (8%), except * (12 1/2%) & 50p post and packing. Also available, Power Supplies, Preamps and Light Effect Modules. For further information, SAE TO:

L&B ELECTRONICS 45 WORTLEY ROAD, W. CROYDON SURREY. CRO 3EB. TELEPHONE: 01-689 4138

BAKER LOUDSPEAKER, 12 INCH, 60 WATT.
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.
 FULL RANGE PROFESSIONAL QUALITY.
 RESPONSE 30-16,000 CPS
 MASSIVE CERAMIC MAGNET
 WITH ALUMINIUM PRESENCE CENTRE DOME.
£21
 Post £1.50

BAKER "BIG-SOUND" SPEAKERS
 Post £1 each

'Group 25'	'Group 35'	'Group 50/15'
12in 30W 4 or 8 or 16ohm	12in 40W 4 or 8 or 16ohm	15in 75W 8 or 16ohm
£12	£14	£33

10 WATT PER CHANNEL STEREO AMPLIFIER
 Ready made in chassis form. Mains operated.
 Volume balance, treble and bass slider controls.
 Pick up and tape inputs. Recording output.
 Front panel size: 16½ x 1½in.
 Chassis size: 13 x 1½in. Bargain **£18.50**

HEATING ELEMENTS WAFER THIN
 Size 10½ x 8½ x ½in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or similar. ALL POST PAID - Discounts for quantity.
ONLY 40p EACH (FOUR FOR £1.50)

MINI MODULE BAFFLE KIT Post 75p
 15 x 8½in. 3-way Loudspeaker System EMI 5in. Bass 5in, Middle 3in Tweeter with 3-way Crosser & Ready Cut Baffle. Full assembly instructions supplied. Response-60 to 20 000 C.P.S. 12 watt RMS. 8 ohms. £10.95 per kit. Two kits **£20.**

SINGLE RECORD PLAYER
 Fitted with auto stop, stereo compatible cartridge. Baseplate. Size 11 x 8½in Turntable Size 7½in diameter a.c. mains 220 250V 3 speeds plays all size records **£7.95** Post 45p Two for £15. Post 75p.

NEW BSR SINGLE PLAYER **£22.50**
 Model P182 3-speeds flared aluminium turntable. Post £1. "S" shaped arm, cueing device, stereo ceramic cartridge.
£14.95

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER



Ideal for Groups Disco P.A. and Musical Instruments 4 inputs speech and music 4 way mixing. Output 4/8/16 ohm a.c. Mains 240V. Separate treble and bass controls. 100 volt line model £14 extra.
£79 Carr £1 50

BAKER 50 WATT AMPLIFIER IDEAL FOR DISCOS, GROUPS AND P.A.
 Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£59** Post £1.

R.C.S. SOUND TO LIGHT DISPLAY MK II
 Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. **KIT = £17.00**

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms. 7W into 15 ohms. Response 20c to 30Kcs. input 100M.V. high imp. Size 9½ x 3 x 2½in. A/C mains operated.
 Mono kit **£12.50** Stereo kit **£20** Post 45p
 Easy to build Full instructions supplied

LDW VOLTAGE ELECTROLYTICS
 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 6V 25p; 25V 42p. 2500mF 50V 82p. 3000 mF 25V 47p; 50V 85p. 3900mF 100V £1.60. 4700mF 63V £1.20. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p. 5600mF 76V £1.60. 1200mF 76V 80p.

HIGH VOLTAGE ELECTROLYTICS

8/350V 22p	8+8/450V 50p	50+50/300V 50p
16/350V 30p	8+16/450V 50p	32+32/450V 75p
32/500V 75p	16+16/450V 50p	100+100/275V 65p
50/350V 50p	32+32/350V 50p	150+200/275V 70p

TINTED PLASTIC COVERS ONLY
 Sizes: 14½ x 12½ x 4½in. £3.17; 14 x 4 x 4in. £4.50. 16½ x 14 x 4in. £4.15; 13½ x 13½ x 4in. £3.75. 15 x 13½ x 3in. £3.50. 17½ x 9½ x 3½in. £3. 14½ x 14½ x 2½in Rosewood sides £4. Ideal for record decks, tape decks etc. Post £1.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS
 All parts and instructions with Zener diode printed circuit rectifiers and double wound mains transformer. Input 200 240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2½ x 1½in. Please state voltage required.
£2.95 Post 50p

ELECTRO MAGNETIC PENDULUM MECHANISM **95p** Post 30p
 1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed ideal displays. teaching electro magnetism or for metronome, strobe etc

MAINS TRANSFORMERS ALL POST 75p each

250-0-250V 70mA. 6 3 2A	£3.45
250-0-250 80mA. 6 3V 3 5A. 6 3V 1A or 3V 2A	£4.60
350-0-350 80mA. 6 3V 3 5A. 6 3V 1A or 3V 2A	£3.40
300-0-300 120mA. 2 x 6 3V 2A C.T. 6 3V 2A	£8.50
220V 45mA 6 3V 2A	£1.75
HEATER TRANS. 6 3V 3A. £1.45. amp. £1.30	£1.30
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2A 3. 4. 5. 6. 8. 9. 10. 12. 15. 18. 24 and 30V	£5.30
1A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£5.30
2A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£8.50
3A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£11.00
5A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£14.50
5. 8. 10. 16V ½A £2. 12V 100mA £1. 12V 300mA £1.	

12V 750mA £1.30. 40V 2A tapped 10V or 30V £2.95. 10-0-10V. 2A £2.50. 40V 2A £2.95. 30V 5A 3A 2A C.T. £3.75. 2 x 18V 6A £9. 12-0-12V 2 amp £2.95. 25-0-25V 2 amp £4. 70-0-20V 1A £2.95. 30V 1½A £2.75. 20V 1A £2.20. 5V 3 amp £2.75. 60V. 40V. 20V or 20-0-20V. 1A £3.50. 30-0-30 2A £7. 9V 250mA £1.30. 30V 2 amp £3. AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150V £5. 250V £6. 400V £7. 500V £8. CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V 1½A £2.75; 3A £4; 4A £5.20. FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs 1½A 55p; 4A £1.25. HALF WAVE 12V 1½A 25p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½in. sides. 6 x 4in. 85p; 8 x 6in. £1.40; 10 x 7in. £1.58; 14 x 8in. £1.90; 16 x 6in. £1.85; 12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70. ALUMINIUM PANELS. 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 8in. 50p; 12 x 8in. 70p; 16 x 6in. 30p; 14 x 9in. 94p; 12 x 12in. £1.15; 16 x 10in. £1.16. ALUMINIUM ANGLE BRACKET. 6 x 1 x ½in. 15p. ALUMINIUM BOXES. MANY SIZES IN STOCK 4 x 2 x 2in. 86p; 3 x 2 x 1in. 65p; 6 x 4 x 2in. 96p; 8 x 6 x 3in. £1.50; 9 x 4 x 4in. £1.70; 6 x 4 x 4in. £1.30.

THE "INSTANT" BULK TAP ERASER **£5.50**
 Suitable for cassettes, and all sizes of tape reels a.c. mains 200 240V Post Leaflet S A E 50p
Head demagnetiser £4.75



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Sat. 9-5 (Closed Wednesday all day).

You know it's easy with Heathkit.

Electronics Courses

- New series of courses on car electrical systems.
- New series of courses on electronic equipment.
- DC electronics.
- AC electronics.
- Semi-conductors.
- Electronic circuits.
- Digital techniques.
- Microprocessors.

Heathkit self-instruction electronics courses are complete, low-cost learning systems. All you need is the will to learn and the Heathkit courses will teach you at your own pace.

It's easy because the courses are based on step-by-step programmed instructions, with audio records (or optional cassettes), self evaluation quizzes to test your understanding, and interesting experiments that encourage you to learn the easy "hands-on" way with the optional Heathkit experimenter-trainers.

Thousands of people just like you have already learnt electronics the easy Heathkit way - at home, in educational establishments and in industry throughout the world.

You'll find it easy too. Full details are in the Heathkit catalogue, together with hundreds of kits you can build yourself; for the home, car and workshop.

Send for your copy now.



New Kits

- Line printer.
- Dual floppy disc.
- Dual trace 5MHz and 35MHz oscilloscopes.
- Memory expansion for digital trainer.
- 2M hand-held transceiver.

To Heath (Gloucester) Limited, Dept PE/3/79
 Bristol Road, Gloucester GL2 6EE. Please send the items I have ticked.
 Heathkit catalogue (enclose 20p in stamps). computer brochure (enclose 20p in stamps).

Name _____
 Address _____

NB. If you are already on the Heathkit mailing list then you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon. Registered in England, number 606177.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester. (Gloucester 29451).

CHROMASONIC electronics

your soundest connection in the world of components

The items shown in this advert are just a small selection taken from our new 78/79 Catalogue which is now available. It contains everything from Resistors to the latest in Micro-processors. Don't delay order your copy today. The price is only 40p (inc. 45p vouchers).

Dept PE1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TELEPHONE: 01-883 3705

Low Power Schottky and TTL

CMOS

I.C. sockets

BITS and PIECES

Regulators

Linear IC's

7400.13*	.19*	7449	—	.87*	74136	—	.39*	74191	1.21*	.75*	4000	.15*	4053	81*	DIL (Texas)	Static RAM's	1+	17-63	64+	78M Series	CA3080	.75	
7401.13*	.19*	7450	.16*	—	74138	—	.55*	74192	1.21*	1.85*	4001	.16*	4054	1.29*	8 pin .10"	2102A	(350ns)	1.05*	.95*	.88*	+ (POS) 500mA	CA3130E	.90
7402.15*	.19*	7451	.16*	.19*	74139	—	.55*	74193	1.21*	1.85*	4002	.16*	4058	1.46*	14 pin .12"	2102A-2	(650ns)	1.29*	1.15*	1.08*	5v. 8v. 12v. 15v.	CA3140E	.37
7403.15*	.19*	7453	.16*	—	74141	.76*	—	74194	1.21*	—	4006	.92*	4059	5.18*	18 pin .13"	2111A-1	(500ns)	2.46*	2.19*	2.05*	20v & 24v.	LM301AN	.30
7404.16*	.21*	7454	—	—	74145	.75*	1.05*	74195	1.01*	1.05*	4007	.18*	4060	1.24*	20 pin .18"	21102	(250ns)	1.07*	.96*	.86*	All 60p* each	LM324N	.73*
7405.16*	.21*	7455	—	.19*	74147	1.59*	—	74198	1.16*	1.05*	4008	.92*	4061	.21*	22 pin .24"	MM5257 (TMS4044)	(450ns)	8.10*	7.19*	6.75*	79M Series	LM380N	.99
7406.26*	—	7460	.16*	—	74148	1.32*	—	74197	1.18*	1.05*	4009	.54*	4068	.21*	26 pin .26"	2114	(450ns)	8.10*	7.19*	6.75*	— (NEG) 500mA	LM382N	1.73
7407.26*	—	7470	.27*	—	74150	1.02*	—	74198	1.81*	—	4011	.18*	4070	.21*	28 pin .30"	6810		3.50*	2.97*	2.52*	5v. 8v. 12v. 15v.	LM387N	1.33
7408.17*	.19*	7472	.23*	—	74151	.82*	.88*	74199	1.81*	—	4012	.18*	4071	.21*	40 pin .44"	CPU's					20v & 24v.	LM390N	.56
7409.17*	.19*	7473	.28*	.29*	74153	.67*	.46*	74221	—	.99*	4013	.48*	4072	.21*	Wire Wrap	8060	5.95*	—	—	—	All 85p* each	LM3909N	.70*
7410.15*	.19*	7474	.28*	.29*	74154	.75*	1.25*	74240	—	.225*	4014	.92*	4077	.21*	8 pin .23"	8800	8.93*	—	—	—	78 Series	SN78001N	1.02
7411.25*	.19*	7475	.46*	.43*	74155	.87*	.78*	74241	—	.225*	4015	.92*	4081	.21*	14 pin .34"	9900	42.50*	—	—	—	+ (POS) 1A	SN78003N	2.32
7412.18*	.19*	7478	.30*	.29*	74156	.67	.78*	74242	—	.225*	4016	.43*	4082	.21*	14 pin .37"	E-Prom's UV					5v. 8v. 12v. 15v.	SN78013N	1.55
7413.27*	.40*	7478	—	.29*	74157	.67*	.55*	74243	—	.225*	4017	.81*	4085	.92*	16 pin .37"	1702A0	5.57*	—	—	—	All 85p* each	SN78023N	1.55
7414.71*	.79*	7482	.73*	—	74158	—	.58*	74247	—	.95	4018	.92*	4086	.92*	20 pin .43"	27080	7.87*	—	—	—	All 85p* each	TA810AS	.90
7415. —	.19*	7483	—	.75*	74160	1.21*	.89*	74248	—	.95*	4019	.56*	4093	.81*	20 pin .55"	TriState Buffers					TC9A40	ZN414	.90
7416.25*	—	7486	1.18*	.86*	74161	1.21*	.65*	74249	—	.95*	4020	.92*	4099	1.81*	24 pin .60"	81LS95	.75*	—	—	—	ZN424E	ZN425E	1.35
7417.34*	—	7486	.25*	.29*	74162	1.21*	1.25*	74251	—	.35*	4021	.92*	4502	.92*	28 pin .65"	81LS96	.75*	—	—	—	ZN459CT	ZN1034E	3.54
7420.16*	.19*	7489	2.60*	—	74163	1.21*	.65*	74253	—	.99*	4022	.92*	4508	2.46*	36 pin .95"	81LS97	.75*	—	—	—	ZN1040E	ZN116E	8.43*
7421. —	.19*	7490	.34*	.62*	74164	1.02*	1.16*	74257	—	.99*	4023	.18*	4510	1.87*	40 pin 1.05"	81LS98	.75*	—	—	—	CD4011	7 for £1.00*	
7422. —	.19*	7491	.73*	1.05*	74165	—	.78*	74258	—	.39	4024	.65*	4511	.95*	20 pin .55"	74365	.75*	—	—	—	LM380	3 for £2.50	
7423.26*	—	7492	.46*	.75*	74166	1.02*	—	74259	—	1.50*	4025	.18*	4514	2.70*	20 pin .60"	74366	.75*	—	—	—			
7425.25*	—	7493	.34*	.65*	74168	—	1.85*	74266	—	.35*	4026	1.84*	4515	2.70*	28 pin .65"	74367	.75*	—	—	—			
7426.25*	.19*	7495	.54*	.80*	74169	—	1.85*	74273	—	2.25*	4027	.51*	4516	1.07*	28 pin .65"	74368	.75*	—	—	—			
7427.39*	.19*	7498	.67*	1.25*	74170	1.85*	1.65*	74279	—	.48*	4028	.70*	4517	4.10*	40 pin 1.05"	74368	.75*	—	—	—			
7428.38*	.19*	74107	.27*	.35*	74173	1.41*	.88*	74283	—	.99*	4029	1.18*	4518	.95*	40 pin 1.05"	74368	.75*	—	—	—			
7430.16*	.19*	74109	.44*	.35*	74174	1.01*	1.05*	74290	—	.83*	4030	.56*	4521	2.54*	40 pin 1.05"	74368	.75*	—	—	—			
7432.25*	.26*	74112	—	.35*	74175	.81*	1.05*	74293	—	.83*	4032	1.08*	4522	1.89*	40 pin 1.05"	74368	.75*	—	—	—			
7433. —	.19*	74113	—	.35*	74176	1.01*	—	74295	—	1.05*	4034	1.89*	4528	1.89*	40 pin 1.05"	74368	.75*	—	—	—			
7437.25*	.25*	74114	—	.35*	74177	1.01*	—	74298	—	1.25*	4035	1.08*	4528	1.89*	40 pin 1.05"	74368	.75*	—	—	—			
7438.25*	.25*	74121	.27*	—	74180	1.01*	—	74365	—	.51*	4040	.92*	4534	7.12*	40 pin 1.05"	74368	.75*	—	—	—			
7440.17*	.19*	74122	.50*	.75*	74181	2.21*	2.99*	74366	—	.51*	4042	.70*	4536	3.74*	40 pin 1.05"	74368	.75*	—	—	—			
7441.70*	—	74123	.80*	.75*	74182	.81*	—	74367	—	.51*	4043	.81*	4543	1.62*	40 pin 1.05"	74368	.75*	—	—	—			
7442.50*	.56*	74124	—	1.25*	74184	1.81*	—	74368	—	.51*	4046	1.06*	4553	4.53*	40 pin 1.05"	74368	.75*	—	—	—			
7445.60*	—	74125	.51*	.39*	74185	1.82*	—	74368	—	.39*	4049	.43*	4583	1.82*	40 pin 1.05"	74368	.75*	—	—	—			
7446.60*	—	74126	.51*	.39*	74188	2.97*	—	74670	—	1.85*	4050	.43*	4583	1.82*	40 pin 1.05"	74368	.75*	—	—	—			
7447.60*	.87*	74132	.72*	.65*	74189	3.17*	2.25*	—	—	—	4051	.81*	4585	1.07*	40 pin 1.05"	74368	.75*	—	—	—			
7448.60*	.87*	74133	—	.19*	74190	1.21*	.75*	—	—	—	4052	.81*	—	—	40 pin 1.05"	74368	.75*	—	—	—			




VAT. Inclusive prices *8% others 12.5%. Export Customers deduct V.A.T. 2/27 from *1/9 from others. Postage and Packing 25p. Trade and Export Inquiries most Welcome. Hours 9.00am-5.00pm.

Now available our ORDER-RING line, just phone your order through with your Access or Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00).



The professional scopes you've always needed.

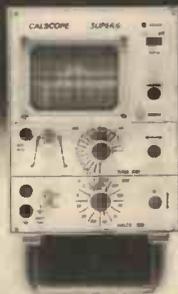

Super 6
£162.00 plus VAT



Super 10
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

CALSCOPE DISTRIBUTED BY
Marshall's Electronic Components,
Kingsgate House,
Kingsgate Place,
London, N.W.6.

Audio Electronics,
301 Edgware Road, London W.2.
Tel: 01-724 3564
Access and Barclay card facilities
(Personal Shoppers)

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

LOOK! Here's how you master electronics.

.... the **practical** way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

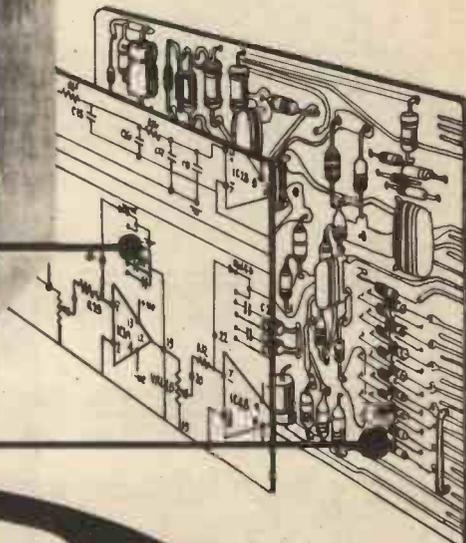1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



Post now, without obligation, to:-

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL


P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

PEB3/79

Block caps please

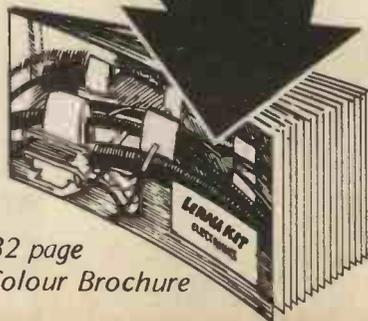

32 page
Colour Brochure



RECEIVERS AND COMPONENTS

POWER PARTS. VMOSFET VN84GA 12.5Amps £21.34, VN66AF 2Amps £1.25. TRIACS: T6411D 400V 25Amps £10.53, T6420M 600V 40Amps £12.96. Inverter SCR 2N3658 400V 35Amps £22.97. Bulgin 8way disco lighting Plug £1.64 socket £0.56. CWO to ANENT POWER, 2 Kelvin Sq., Livingston, West Lothian.

TUNBRIDGE WELLS COMPONENTS, Ballard's, 108 Camden Road, Tunbridge Wells, Phone 31803. No Lists. Enquiries S.A.E.

P.C.Bs PAXOLIN 10½" x 4½" 4—£1.25. 12" x 9" 70p. 17½" x 9½" £1.15. D.S. 10" x 8½" 80p. Fibre Glass 9" x 8" £1.20. 18" x 8" £2.40. D.S. 13" x 6" £1.30. 11½" x 7½" £1.60. Panel with 42 assorted 74 series ICs £1.50. 20 wire ended neons £1.300 small components, trans, diodes £1.50. 7 lbs assorted components £3.60. 3½ lbs £1.95. List 15p. Refundable. Post 20p under £1. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

TRIACS 500V 3A Tested 50p each. M. Manning, 114 Dumbreck Road, Eltham, SE9.

GLASS FIBRE PRINTED CIRCUIT BOARDS from your film or tape masters 14p per square inch + P&P 30p. C.W.O. please. P. A. YATES, 22 Ambleside Drive, Darwen, Lancs.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 mfd. — 5p.
22, 47—8½p (50V—6p), 100—7p. (50V—8p).
220—8p. (50V—10p), 470—11p. (50V—16p).
1000/15V—15p. 1000/25V—18p. 1000/40V—35p.
Subminiature bead tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 @ 35V & 4.7 @ 6.3V—8p.
2.2/35V & 4.7/25V—9p, 10/25V & 15/16V—12p.
22/16V, 33/10V, 47/6V, 68/3V, 100/3V—14p.
Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.
10% 390 pf. to 4700 pf.—4p.
Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf.—1000 pf.—E6 1500 pf. to 47000 pf.—2p.
Polystyrene E12 Series 63V. Horizontal Mtg.
10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p.
Miniature Polyester 250V Vert. Mtg. E6 Series.
.01 to 0.1—4p. .15 & .22—6p. .33 & .47—8p.
0.68—11p. 1.0—14p. 1.5—20p. 2.2—22p.
Mylar (Polyester) Film 100V. Vertical Mtg.
.001, .002, .005—3½p. .01, .02—4½p. .04, .05—5½p.
Miniature resistors Highestab. 5% E12 Series.
0.125W mixed metal/carbon film 100—2M2Q—1p.
0.25W carbon film 10—10MΩ (10% over 1MΩ)—1p.
(E24 series in 1W c.film 2.00—2M00 only).
0.25W, 0.5W & 1W metal film 2.20—2M2Q—2p.
1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—9p.
8 pin i.c.s. 741 Op.amp.—18p. 555 timers—24p.
20mm. fuses .15, .25, .5, 1.0, 2.0, 3.0 & 5A—3p.
Printed circuit fuseholders for 20mm. fuses—5p.
400 mW. zener diodes E24 series 2V7—33V—8p.
Prices VAT inclusive Post 10p. (Free over £4).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN

GRADE 1 SEMICONDUCTORS, PASSIVES, HARDWARE, + SECURITY. Immediate service:- Texas 1N4148 £1.50 per 100. RCA CD4001/11 18p. RCA 741 8 pin dil. £1.00 per 5. 555 £1.00 per 4. CEH. PC. housings 60p. Capacitors, resistors, keyswitches, Texas IC. sockets, control panels. S.A.E. brings complete catalogue:- CEH Audio-Visual (A), 48 Whistler Rd. Tonbridge, Kent.

1P EACH plus S.A.E. Diodes 20V 10uA. Rush, 23 Campus Road, London E17.

GUARANTEED ICs 7400/10p 7447/55p 7473/24p 74121/24p 4000/15p 4011/15p 4017/55p 4027/32p 709/22p 741/22p 7805/60p NE555/25p. Many more! SAE full list CP ICs 22 Oakfield Road, Croydon, Surrey.

SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wibeck, Cambs, 0945-4188. Immediate settlement.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

LADDERS

LADDERS. Varnished 25ft. extd. £35.70. Carr. £2.80 Leaflet Callers welcome. Open Sat. Ladder Centre (PEE5), Halesfield (1) Telford S86644.

RECORD ACCESSORIES

STYLII for Hi-Fi, Music Centres. 111. List for s.a.e. Also cartridges, leads, accessories. Details-Felstead Electronics (PE) Longley Lane, Gatley, Cheshire, Ches. SK8 4EE.

EDUCATIONAL

TELEVISION TRAINING

18 MONTHS full-time course for beginners to include all the undermentioned subjects. Short courses, combining one or more subjects, for applicants with suitable education and electronics background such as C & G, HND, BSc etc.

- 13 WEEKS TECHNICAL MATHEMATICS & ENGLISH
- 13 WEEKS ELECTRONICS & RADIO
- 13 WEEKS MONOCHROME TELEVISION
- 13 WEEKS COLOUR TELEVISION
- 13 WEEKS VIDEO SYSTEMS (CCTV, VCR, TELETEXT etc)

The training incorporates a high percentage of practical work.

Next session starts on April 23rd

(Also available 2½ year course in Marine Electronics & Radar for employment as Ship's Radio Officer)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. PE3, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. E272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. E272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. E272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford, RM7 0XU (phone Romford 66841).

FOR SALE

NEW BACK ISSUES of "PRACTICAL ELECTRONICS" available 70p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

SEEN MY CAT? 5000 Odds and ends. Mechanical Electrical. Cat free. Whiston, Dept. PRE, New Mills, Stockport.

MINISONIC 2. Many additions, working, needs some attention, £250. Details, Ottershaw 2522.

WANTED

WANTED. Personal computer pet similar. Exchange Hi Fi. Cash. 50 Queen Anne Street, S-O-T, ST4 2EQ.

BOOKS AND PUBLICATIONS

INTRODUCTION TO MICROPROCESSORS AND COMPUTING. 50 pages of explanation and diagrams to get you started. Contents include: binary arithmetic, codes, micro-processor operation, machine language programming, summary of higher level languages and systems, glossary of terms. Price £2.30 plus 45p P&P. (Crossed cheques and P.O.'s.) Educational Data and Technical Services, 59 Station Road, Cogenhoe, Northampton NN7 1LU.

COMPREHENSIVE TV REPAIR INSTRUCTIONS for your set £5.00 with circuit (if requested). Free catalogue unique T.V./other publications AUSE (PE) 76, Church Street, Larkhall, Lanarkshire ML9 1HE.

WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS. A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated Manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED,** as the Manual covers in 13 Chapters, where to obtain all the work you need, materials required, all instructions rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4.00 plus 30p P & P. **UK. C.W.O. to INDUSTRIAL SUPPLIES, 102 Parrwood Rd., Withington, Manchester 20, Dept. PE.**

SITUATIONS VACANT

SOUTH OF SCOTLAND ELECTRICITY BOARD INVERKIP POWER STATION INSTRUMENT MECHANICS

- Salary:** Up to £91.17 per week, plus Travel Allowance of up to £2 per week.
- Hours:** 5 cycle shift pattern or 7 day stagger.
- Conditions:** Superannuation Scheme; Sick Pay Scheme; Generous Holiday entitlement.
- Housing:** Rented Housing may be available in appropriate circumstances; re-location expenses paid.
- Requirements:** Applicants should have served a recognised apprenticeship and should have relevant experience.
- Training:** Specialist/refresher training will be given in appropriate circumstances.
- Security:** These posts are permanent and offer long term security.
- Applications (quoting reference 52/G6/79) should be submitted on the standard form obtainable from and returnable to the Station Manager, Inverkip Power Station, Inverkip, Nr. Greenock, Renfrewshire PA16 0ED (Telephone Largs 675421)



POWER SUPPLIES

POWER SUPPLY CARDS. + 12 volts and + 5 volts. Fully regulated with S/C protection. £19.99 + £1 P&P. C.W.O. To ANENT POWER, 2 Kelvin Square, Livingstone, West Lothian.

MISCELLANEOUS

CABINET FITTINGS

FOR
Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Strap & Recess Handles, Feet, Castors, Jacks & Sockets, Cannons, Bulgin B ways, Reverb Troys, Locks & Hinges, Corners, Trim, Speaker Bolts etc.

Send 2 x 9p Stamps for samples and illustrated catalogue.

ADAM HALL (P.E. SUPPLIES)
Unit 3, Carlton Court, Grainger Road
Southend-on-Sea, Essex.

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI, Dept: No. 23, St. Wilfred's, Foundry Lane, Halton, Lancaster. LA2 6LT.**

PRACTICAL ELECTRONICS P.C.B.'s

In glass fibre tinned and drilled
Dec. 77 Car Burglar Alarm 1412-1 68p.
May 78 Moving Light Display £2.76.
July 78 Dimwit £1.78. Aug 78 Touch Switch 85p.
Aug 78 Digital Thermometer, two boards £1.45.
Oct. 78 High Performance Power Supply £2.18.
Oct. 78 Analogue Computer:
Overlord £3.31. Relay £2.41. Main £6.85.
Nov. 78 Auto Light £1.00.
Dec. 78 RC Motor Control 67p. RC Fail Safe 39p.
Guitar Sound, Main board £2.95.
Jan. 79 Guitar Sound, clock £1.87.
Low pass filter £1.95.

Noughts and Crosses, set on boards £8.38.
For full list and current boards please send S.A.E. P.C.B.'s also produced from customer's own master - please send for quote.

Postage - On orders less than £10.00 please add 25p. postage. C.W.O. please.

PROTO DESIGN

14 Downham Road, Ramaden Heath, Billericay,
Essex CM11 1PU

BLOWN UP ANY GOOD CIRCUITS LATELY?

ELIMINATE THE GUESSWORK WITH AN A.C. MILLIVOLTMETER

This valuable piece of test equipment enables the amateur or professional to measure A.C. voltages accurately and easily. The unit is mains operated and comes complete with test lead.

Specifications: Range 1mV f.s.d. to 100V f.s.d. in 6 ranges. Frequency response: 10Hz to 100kHz ± 1 dB. Accuracy: within 1% typ. Input impedance: 1 megohm.

Price £48.50 inclusive. Send your cheque or postal order for £48.50 to Magna Electronics, 18 De La Warr Road, East Grinstead, West Sussex, RH19 3BP

ALARM EQUIPMENT AND ELECTRONIC COMPONENTS. Car alarm control units: Type 'A', immediate operation, automatic reset, kit - £5.50, assembled - £6.80. Type 'B', timed exit/entry, automatic reset, kit - £8.25, assembled £10.90 (10% discount 10+). Lockswitches £3.50. 12v sirens £5.90. Bell boxes £5.75. 12v Bells £8.25. BC 108 10p (10+). 555's 32p (10+). 741's 24p (10+). P&P 10% extra. **WEBB ELECTRONICS, 41 Winwick Street, Warrington. (Tel. 54174).**

Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c.boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills

All immediately available.
Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,
Masons Rd. Stratford on Avon
Warwks. CV37, 9NF 0789-4879

PRINTED CIRCUIT BOARDS in glass fibre, drilled tinned or varnished, from your own or published designs. S.A.E., for quotations. R. F. DARLISON, 12 Whiteoaks Road, Oadby, Leicester.

GUITAR/PA/MUSIC AMPLIFIERS

100 watt with superb treble bass overdrive. 12 months guarantee. Unbeatable at £40; 60 watt £35; 200 watt £56; 1 twin channel sep treble/bass per channel £52; 60 watt £46; 200 watt £69; 100 watt four channel sep treble/bass per channel £65; 200 watt £78; Slaves 100 watt £32; 200 watt £48; Fuzz boxes great sound £7.90; Bass fuzz £8.50; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £85; Twin channel £95; Bass Combo £95; Speakers 12in. 100 watt £22.50; 60 watt £14.50; Shure mic unidyne B £26.

Send Cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Ave, Dukinfield, Cheshire
Tel. 061-344 5007

TOUCH SENSITIVE Lightdimmer P.C.B. + circuit 75p. Electronic Siren 12v 4 watts, kit £2.99. P.C.B. + circuit 90p. Electronic siren attractively cased with internal loudspeaker. Kit £5.99. Details on request from H.T.E. 50 Milnefield Avenue, Elgin, Morayshire.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a **MINI-STROBE Kit**, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT.

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

micron

RADIO CONTROL SPECIALISTS

Kits for multi channel systems. Special parts and accessories.

S.A.E. FOR LEAFLETS
Tel: 0602 395418

**MICRON R/C, Hayworth Road,
Sandiacre, Nottingham.**

TRANSISTORISED IGNITION KIT

£4.86 incl. carr & VAT

Complete pack of parts with p.c.b. to build our transistorised ignition system based on Darlington Power Transistors specially developed for auto ignition.

Send S.A.E. for FREE CIRCUIT diagram.
All components with p.c.b. (less case) £4.86.

SOLEC PRODUCTS,

68 Dale Street, Manchester, M1 2HS.

**DEAD or ALIVE
OR JUST
MIXED UP?**
The remarkable
**SOCKET
TESTER**

Shows you
instantly
the exact
fault or if
all correct



Safety fast! Shows at once; 1, If all wires correct. 2, Live wire fault. 3, If neutral fault. 4, Live and neutral reversed. 5, Earth fault. 6, Live and earth reversed.

British made. 13-amp plug type or remote readout type to use with any plug. Both same price £4.20 post free from the manufacturers. (2 for £7.95, 3 or more £3.90 each).

GALATREK ENGINEERING

Dept. PE3, Scotland Street,
LLANRWST, Gwynedd, N. Wales.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1.13, SUB C £1.47, HP 11 (C) £2.15, HP 2 (D) £3.27, PP3 £4.09, PP3 not suitable for fast charge, PP3 charger £5.81. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec, and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc., 1-2 amp hr 6v. £4.40 2-6 amp hr. 6v £5.65.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to: **SOLID STATE SECURITY DEPT PE, 10, Bradshaw Lane, Parbold, Wigan, Lancs. 02575-4726.**

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2	1	4.51	0.78
18	4	2	4.03	0.96
85	5	2.5	5.00	0.79
70	6	3	5.35	0.96
108	8	4	7.42	1.14
172	10	5	8.12	1.14
116	12	6	8.99	1.32
17	16	8	10.72	1.32
115	20	10	13.98	2.08
187	30	15	17.05	2.08
226	60	30	36.14	DA

30 VOLT RANGE
Pri 220/240V Sec 0-12-15-20-24-30V. Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 16, 20, 24, 30V or 12V-0-12V, 15V-0-15V.

Ref	24V	£	P & P
112	0.5	2.64	0.78
79	1.0	3.57	0.96
3	2.0	8.77	0.96
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.84

60 VOLT RANGE
Pri 220/240V Sec 0-24-30-40-48-60V. Voltages available 5, 7, 8, 10, 12, 15, 17, 20, 30, 40 or 20V-0-20V, 25V-0-25V, or 30V-0-30V.

Ref	Amperes	£	P & P
124	0.5	3.88	0.96
126	1.0	5.91	0.96
127	2.0	7.60	1.14
125	3.0	11.00	1.32
123	4.0	12.52	1.84
40	5.0	15.84	1.64
120	6.0	18.06	1.84
121	8.0	25.56	DA
122	10.0	29.55	DA
189	12.0	34.06	DA

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40-50V. Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V, 25V-0-25V.

Ref	Amperes	£	P & P
102	0.5	3.41	0.78
103	1.0	4.57	0.96
104	2.0	7.16	1.14
105	3.0	8.56	1.32
106	4.0	11.41	1.50
107	6.0	15.06	1.64
118	8.0	20.28	2.08
119	10.0	24.98	DA

MAINS ISOLATORS (SCREENED)
Pri 120/240V Sec 120/240V (C. Tapped)

Ref	VA (Watts)	£	P & P
07*	20	4.40	0.79
149	60	6.70	0.96
150	100	7.61	1.14
151	200	11.16	1.50
152	250	13.28	1.84
153	350	16.43	1.84
154	500	20.47	2.15
155	750	29.06	DA
156	1000	37.20	DA
157	1500	51.38	DA
158	2000	61.81	DA
159	3000	86.66	DA

*Pri 0-220-240 Sec 115 or 240V State volts required

AUTO TRANSFORMERS

Ref	VA (Watts)	£	P & P
113	15 0-115-210-240	2.48	0.71
64	75 0-115-210-240	4.01	0.86
4	150 0-115-200-220-240	5.35	0.98
87	500 0-115-200-220-240	10.99	1.84
83	1500 0-115-200-220-240	18.76	2.08
93	1500 0-115-200-220-240	23.26	DA
95	2000 0-115-200-220-240	34.82	DA
73	3000 0-115-200-220-240	59.21	DA
805	4000 0-115-200-220-240	78.86	DA
575	5000 0-115-200-220-240	89.50	DA

CASED AUTO TRANSFORMERS
240V cable in & 115V USA 2 pin outlet

VA	£	P & P	Ref
75	7.73	1.14	64W
150	10.01	1.14	4W
200	9.92	1.45	65W
250	10.49	1.45	69W
500	19.17	1.64	67W
750	23.41	1.76	83W
1000	27.88	DA	84W
1500	28.02	DA	93W
2000	49.97	DA	95W

HIGH VOLTAGE ISOLATORS
Prim 200/220V or 400/440V Sec 110/120V CT or 200/240 CT

VA	Ref	£	P & P
60	243	6.70	1.32
350	247	16.43	1.84
1000	250	37.10	DA
2000	252	61.81	DA

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	0-0-3	2.67	0.55
212	1A, 1A	0-0-6	2.85	0.78
13	100	9-0-9	2.34	0.38
235	330, 330	0-9, 0-9	1.99	0.38
207	500, 500	0-8-9, 0-8-9	2.77	0.71
208	1A, 1A	0-8-9, 0-8-9	3.53	0.78
236	200, 200	0-15, 0-15	1.99	0.38
214	300, 300	0-20, 0-20	2.80	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-0-15-20	4.63	0.96
203	500, 500	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	6.04	0.96
239	50	12-0-12	2.67	0.38

TEST METERS
U4315 Budget Meter 20,000 ohm/V Ranges 1000V AC/DC 2.5A AC/DC 500K resistance in steel robust case £16.85

Model	Price
AV08	£81.70
AV071	£33.50
EM273	£45.20
AV072	£53.70
MM15	£28.66

BE9 Miniature Transformer
Pri 0-240V Scr 28 x 26 x 20mm Sec. 12-0-12V 50MA 90p P & P. 38p + 12 1/2 p P & P.

MINI-MULTIMETER
DC-1000V AC-1000V DC-100mA Res 150kΩ 1000Ω/V Bargain £7.20 P & P 62p VAT 8%

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V, DC current to 250mA. Resistance to 3 Megs. 5" x 3 1/2" x 1 1/2" £14.36 P & P £1.05 VAT 8%.

ISOLATOR - Special Price
0-200-220-240V, 0-240V Centre Tap, 250VA Ref. 62 £5.20 P & P 96p

ELECTROSIL Metal oxide low noise resistors.

ELECTRONIC CONSTRUCTION KIT
Home electronics teacher. Start simple and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. Full instructions. £8.29 + VAT + 96p p&p.

43mm x 43mm PANEL METERS 82mm x 78mm

Model	Price
0-50µA	6.20
0-500µA	5.95
0-1mA	5.95
0-30V	5.95
VU Ind Panel 90mm 250µA	£3.36
VU Indicator Edge 54mm x 14mm 250µA FSD	£2.60

Cassette Tapes Low Noise
C60 30p P & P. 15p
C90 42p P & P. 15p VAT 8%.

COMPONENT PACKS

65 1/2w Metal Oxide Resistors	£3.76
65 1/2w Metal Oxide Resistors	£4.57
150 Mixed Value Capacitors	£1.30
10 Read Switch	£1.30
60 Wire Wound Resistors.	£1.30
10 Caps 3000mf 30V.	£1.30
25 assorted Presets.	£1.30
50 Wire Wound Resistors.	£1.30
Hardware B.A. nuts, bolts, washers etc. 70p each pack	£1.30

BE9 Miniature Transformer
Pri 0-240V Scr 28 x 26 x 20mm Sec. 12-0-12V 50MA 90p P & P. 38p + 12 1/2 p P & P.

NEW RANGE TRANSFORMERS
Pri 0-220-240V 2 Amp. 45-36-0-36-45 £9.89
Sec. 0-36-48 twice. Tap give 36-0-36, 48-0-48 72V or 92V.

Model	Price
3A	£14.70
4A	£18.77
5A	£26.64

S-DECS
Solderless bread boarding

Model	Price
S Dec 70 contacts	£3.10
T Dec 208 contacts	£4.35
U Dec "A" for I.C.s etc	£4.50
U Dec "B" for I.C.s etc	£6.99

ANTEX SOLDERING IRONS

Model	Price
15W	£3.75
25W	£3.95

BRIDGE RECTIFIERS

Model	Price
100V*	2A £2.10
200V	25A £0.45
400V	4A £0.85
400V with heat sink	6A £1.40
*500V PM 7A6	12A £2.85

AMPLIFIER MODULES

10W (AL30)	£3.76
25W (AL60)	£4.57
35W (AL80)	£7.15
125W (AL250)	£17.26
Power Supply PS12	£1.30
Power Supply SPMB0	£4.25
Pre-amp PA12	£6.70
PA100	£13.88

TRANSFORMERS
Special Offer

P.W. Purbeck oscilloscope transformer in stock 250-0-250 6-3V, 12-9V £6.50 P & P 90p.

BE3 100V line to 4Ω 7/10W £2.05 P & P 66p

BE4 0-120V x 2 (120V or 240) Screen sec 9-0-9 1A £2.40 P & P 71p

BE5 15W matching trans. sec 150 suit £LB9 £1.50 P & P 30p

BE6 PR1. 0-220V sec. 4500V, 10 MA £4.50 P & P £1.00

BE7 0-110-120 220V Pri 240V Sec 20V 1A £1.60 30p P & P

BE8 0-240 15-0-15V 2A £1.50 P & P. 70p.

Ref 30 240-240 Isolator 200VA £4.20 P & P 96p.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

SEND 15p STAMPS FOR CATALOGUE

Prices correct 17.8.78. Please add VAT after P & P.

INDEX TO ADVERTISERS

Ace Mailtronix Ltd.....	58
Adam Hall (P.E. Supplies).....	85
Aitken Bros.....	6
Alcon Instruments Ltd.....	78
Astra-Pak.....	8
Aura Sounds.....	6
Automated Homes.....	86
B.I.E.T. (Collier Macmillan).....	80
Barrie Electronics.....	88
Bib Hi-Fi Accessories.....	72
Bi-Pak.....	12, 13
Birkett, J.....	15
Boffin Projects.....	85
British National Radio & Electronics School.....	11, 83
Cambridge Learning.....	9
Calscope (Scopex).....	82
Cannon Components.....	88
Chromasonic.....	82
Clef Products.....	80
Codespeed.....	74
Continental Specialties.....	75
Crescent Radio Ltd.....	4
Crimson Elektrik.....	58
Crofton Electronics.....	78
C.R. Supply Co.....	84
Delta Tech.....	80
Dzuibas, M.....	4
E.D.A.....	76
Electronic Brokers.....	16
Electrovalue.....	74
Fladar Electric.....	77
G.I.S.A.L. (Gloucester Industrial Sales & Auctions Ltd).....	77
Galatex Engineering.....	85
George, David Sales.....	78
Greenwood Electronics.....	77
H L Audio.....	71
Haversons.....	52
Heathkit Ltd.....	81
Home Radio.....	58
I.C.S. Intertext.....	6, 84
I.L.P. Electronics.....	73
Inskip, Norman.....	79
J.W.B. Radio.....	84
K & A Distributors.....	87
Kay & Co Ltd.....	2
L & S Electronics.....	80
London Electronic College.....	84
Lord, Jeremy.....	72
Magna Electronics.....	85
Maplin Electronic Supplies.....	cover iv
Marshall A. (London) Ltd.....	57
Metac.....	52
Micron R/C.....	85
Mill Hill Supplies.....	8
Minikits Electronics.....	86
Modern Book Co.....	87
P.K.G. Electronics.....	86
Pentagon Electronics.....	86
Phoenix Electronics.....	15
Phononics.....	14, 15
Progressive Radio.....	58
Proto Design.....	85
Radio Component Specialists.....	81
Ramar Constructor Service.....	85
R.S.T. Valve Mail Order.....	76
Radio & T.V. Components.....	7
Sabtronic.....	16
Saxon Entertainments.....	10, 11
Science of Cambridge.....	51
Scientific Wire Co.....	86
Sentinel Supply.....	8
Service Trading.....	cover iii
Solec Products.....	85
Solid State Security.....	85
South Scotland Electricity Board.....	85
Squire, Roger.....	2
Sugden, A.R.....	4
Swanley Electronics.....	8
Technomatic Ltd.....	3
Teleyap (Logic Leisure).....	cover ii
Timetron.....	87
T.K. Electronics.....	72
Trident Exhibitions.....	2
T.U.A.C.....	74
W.K.F. Electronics.....	86
Watford Electronics.....	5
West London Direct Supplies.....	87
Williamson Amplification.....	85
William Stuart Systems Ltd.....	86
Willmslow Audio.....	11

CANON COMPONENTS

Low Imp Dynamic Mic's Brand new in packs £1.62
Triacs 10 amp. 400v brand new AEI full spec. all with fitted heavy duty heat sink £2.55
22 way edge connectors Ex equipment but clean 0.15 matrix gold plated complete with locating pin Only 58p
17 way edge connectors Brand new. 15 pitch complete with locating pin and fixing brackets. Tinned. Only 35p
Connecting wire 15p per 10 metres or mixed at £3.00 per kilo approx.
Tegstrips 30 way new. 15p
Group Board 17 or 34 way brand new 12p and 24p

DIAL-A-BOX

As featured in "P.E. MARKET PLACE" a comprehensive standard range of boxes for the constructor, or custom built to your specification. Send your requirements with S.A.E. or phone for quote.

Lamp panels with over thirty lampholders fitted ideal for light displays or moving light shows. Only 85p
Mains selector panels from 200v-250v. Brand new. 20p each
Cable Ties long re-usable 6" plus. 3p each.
Transformers 20-0-20v 400 mA £2.50 each.
4mm Screw Terminals assorted colours of our choice £1.00 for six.

STOP PRESS!

P. E. Guitar Sound Multiprocessor
Send SAE for quotation for a purpose built case for this project.

All prices include VAT - Please add 65p Post & Packing per item to total cost of order.
Open daily 9.30am-6pm - Access or Barclaycard accepted - S.A.E. for lists.

322-334 WHITEHORSE ROAD, CROYDON, SURREY CR0 2LF
TEL: 01-684 9872

RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock phone or write in your enquiries

FT3 NEON FLASH TUBE

High intensity multi turn, high voltage, neon glow, discharge flash tube. Design for ignition timing. etc. £1.50. P & P 25p (£1.89 inc VAT) 3 for £3. P & P 50p (£3.78 inc VAT & P).



RODENE UNISET TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding, mixing, etc. Price £6 P & P. 60p.



WHY PAY MORE?

MULTI RANGE METER TYPE MF15A a.c. d.c. volts 10 - 50, 250, 500, 1000. Ma 0-5, 0-10, 0-100. Sensitivity 2000V: 24 range, diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P & P. (£8.10 inc. VAT & P.)




METERS (New) - 90 mm DIAMETER

A.C. Amp., Type 62T2. 0-1A, 0-5A, 0-20A. A.C. Volt. 0-50V, 0-300V. D.C. Amp., Type 65C5. 0-2A, 0-10A, 0-20A. D.C. Volt. 0-15V, 0-30V. All types £3.50 ea. + P & P. 50p (£4.32 inc VAT), except 0-100A D.C. price £5.00 + 50p. P & P (£5.94 inc. VAT).



NEW HEAVY DUTY SOLENOID. mfg. by Magnetic Devices.

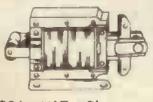240V a.c. operation. 10lbs pull (intermittent rating) at 1/2 in. Price £4.00 P & P. 60p (£4.96 inc. VAT & P.). N.M.S.



A.C. SOLENOID pyc ether type 176/240 AC.

Approx 1lb at 1/2 in. intermittent rating. Price £1 p&p 20p (£1.30 inc VAT & P).

WESTPOOL TYPE MMB Model 2, 240V AC. Approx 1 1/2 lb pull at 1/2 in. Rating 1. Price £1.50 p&p 20p. (£1.84 inc VAT & P) N.M.S.



MINIATURE UNISELECTOR

12 volt. 11-way, 4 bank (3 non-bridging, 1 homing), £2.50. P & P. 35p (£3.08 inc. VAT & P.). N.M.S.



240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring. In b.s.p. inlet outlet. Precision made. British mfg. PRICE £3.50 Post 50p (£4.32 inc. VAT & P.). N.M.S.



MICRO SWITCHES

Sub min Honeywell roller m/s type 3115m 906t. 10 for £2.50 post paid. LEVER OPERATED 20 amp. C/O. Mfg. by Unimax USA. 10 for £4. P & P. 50p (min. order 10) (£4.86 inc. VAT). O.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P & P. 30p. Total inc. VAT £3.02 (min. 10). Sub min lever m/s switch type MML 46 10 for £2.50. Post Paid £2.70 inclusive. N.M.S.



MERCURY SWITCH

Size 27mm x 5mm. 10 for £5.00 (inc VAT £5.72) min quantity 10.



VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max air delivery of 1.5 cubic metres per min. Max static pressure 600mm WG. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions: length 72cm, width 25cm, height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12 - £150 P & P (£14.58 inc VAT & P). Suitable transformer for 230 240V a.c. £6 - £1 P & P (£7.56 inc VAT & P).



CENTRIFUGAL BLOWER Smith type FFB

1606-022 220/240V A.C. Aperture 10 x 4 1/4cm overall size 16 x 14cm. Price £3.75 P & P 75p (inc. VAT £4.86). Other types available. S.A.E. for details. N.M.S.



24 volt. D.C. BLOWER UNIT

Production 24 volt. D.C. 8 amp Blower that works well on 12V 4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P & P. 75p (inc. VAT £5.61). N.M.S.

INSULATION TESTERS NEW!

Test to I.E.E. Spec Rugged metal construction suitable for bench or field work constant speed clutch. Size L8in W4in H6in weight 6lb. 500V 500 megohms. £49. Post 80p (£53.78 inc. VAT & P.). 1,000V 1,000MΩ. £55. Post 80p (£60.26 inc VAT & P.). SAE for leaflet.



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp inc. a.c. voltmeter)	£14.50
0.5 KVA (2 amp MAX)	£17.00
1 KVA (5 amp MAX)	£22.50
2 KVA (10 amp MAX)	£37.00
3 KVA (15 amp MAX)	£45.50
5 KVA (25 amp MAX)	£74.00
10 KVA (50 amp MAX)	£168.00
15 KVA (75 amp MAX)	£260.00



CARRIAGE AND PACKING EXTRA

LT TRANSFORMERS

0-10-15V at 3 amp (ex new equip) £2.50 P. & P. 50p (£3.24 inc. VAT)
13-0-13V at 1 amp £2.50 P. & P. 50p (£3.24 inc. VAT)
25-0-25V at 2 1/2 amp £4.50 P. & P. 75p (£5.67 inc. VAT & P.)
0-4V/6V/24V/32V at 12 amp £18.50 P. & P. £1.90 (£22.03 inc. VAT & P.)
0-6V/12V at 20 amp £14.70 P. & P. £1.50 (£17.50 inc. VAT)
0-12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£14.58 inc. VAT & P.)
0-6V/12V at 10 amp £8.25 P. & P. £1.25 (£10.26 inc. VAT)
0-6V/12V/17V/18V/20V at 20 amp £18.00 P. & P. £1.50 (£22.10 inc. VAT & P.)
0-10V/17V/18V at 10 amp £10.50 P. & P. £1.50 (£12.96 inc. VAT)


Other types in stock; phone for enquiries or send sae for leaflet.

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £19.00. Post £1 (£21.60 inc. VAT & P.). Specially designed case and reflector for Hy-Light £8.80. Post £1 (£10.58 inc. VAT & P.).

XENON FLASHGUN TUBES

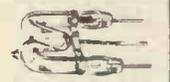Range available from stock SAE for details



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 watt £8.70 (callers only) 2ft. 20 watt £6.20. Post 75p. (£7.51 inc. VAT & P.) (For use in stan bi-pin fittings) Mini 12 in. 8 watt £2.80. Post 35p. (£3.40 inc. VAT & P.). 9 in. 6 watt £2.25. Post 35p. (£2.81 inc. VAT & P.). 6 in. 4 watt £2.25. Post 35p. (£2.81 inc. VAT & P.). Complete ballast unit, for either 6", 9" or 12" tube 230V AC op £3.50. Post 45p. (£4.27 inc. VAT & P.). Also available for 12V DC op £3.50. Post 45p. (£4.27 inc. VAT & P.). 400 watt UV lamp and ballast complete £31.50. Post £3. (£37.26 inc. VAT & P.). 400 watt UV lamp only £11.25. Post £1.20 (£13.45 inc. VAT & P.).

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Post 75p. S.A.E. (foolscap) for further details. Price only £60.00



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding heavy duty brush assembly, continuously rated. 25 WATT 10/25/50/100/150/250/500/1kΩ/1.5kΩ. £2.40. Post 20p (£2.81 inc. VAT & P.). 50 WATT 100/250/500. £2.90. Post 25p (£3.40 inc. VAT & P.). 100 WATT 15/10/25/50/100/250/500/1kΩ/1.5kΩ/2-5kΩ. £3.90 P & P 35p (£6.76 inc. VAT). Black, Silver, Skirted knob calibrated in Nos. 1-9 1/2 in. dia. brass bush. Ideal for above Rheostats 24p each.



RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.84 inc. VAT & P.). T.E.C. open type 3 c/o. 10 amp £1.10 (£1.40 inc. VAT & P.). Omoron or Keyswitch 1 c/o. 7 amp £1.00 (£1.30 inc. VAT & P.). D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.30 inc. VAT & P.). Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.30 inc. VAT & P.). Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.56 inc. VAT & P.). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P.). 24V. Sealed 3 c/o 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P.). (amps = contact ratings). P&P on any Relay 20p. Other types available — phone for details. N.M.S. Diamond H heavy duty A.C. relay 230/240V a.c., two C/O contacts 25 amps res at 250 a.c. £2.50 p&p 50p. (£3.24 inc. VAT & p&p) Special base 50p. N.M.S.

VAT

AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED.

SERVICE TRADING CO.

ACCOUNT CUSTOMERS MIN. ORDER £10.00

PARVALUX MOTOR TYPE SD2

12 volt. D.C. shunt 1/2 H.P. Motor. Continuously rated 4,000 r.p.m. £10 P. & P. 75p (£11.61 inc. VAT). N.M.S.

GEARED MOTORS

100 r.p.m. 115lb.in. 110V. 50Hz 2.8A. single phase split capacitor motor Immense power Continuously rated Totally enclosed. Fan cooled in-line gearbox. Length 250mm. Dia. 135mm. Spindle dia 15 5mm Length 145mm. Ex-equipment tested £12. Post £1 50 (£14.58 inc. VAT & P.). Suitable transformer 230/240V operation £8. Post 75p (£9.45 inc. VAT & P.).



GEARED MOTORS

28 r.p.m. 20 lbs inch 115v a.c. Reversible motor. 71 r.p.m. 10 lbs inch 115v a.c. Reversible motor.



Both types similar to above drawing. Price either type £4.75 p&p 75p. (£5.94 inc. VAT & p&p) Supplier complete with transformer for 240v a.c. operation £7.25 p&p £1.00 (£8.91 inc. VAT & p&p)

CROUZET 230/240V AC 2RPM synchronous geared motor. £2.90 p&p 30p. (£3.45 inc. VAT) (quantity discount available.) HAYDON 230/240V AC. 1RPM synchronous geared motor. £2.90 p&p 30p. (£3.45 inc. VAT & P.) N.M.S.

FRACMO GEARED MOTOR

56 r.p.m., 50lb.in. 240V a.c. 50Hz. 0.7 amp. shaft length 35mm. dia 16mm. weight 6 kilos 600 grammes. Price £15.00 P & P. £1.50 (£17.82). N.M.S.



PARVALUX GEARED MOTOR

230/240V A.C. 30 rpm 50lbs inch. Price £15.00 P. & P. £1.00 (£17.82 inc. VAT). N.M.S.

PARVALUX GEARED MOTOR

230/250V a.c. 500 rpm, 3 1/2 lbs inch. 2 right angled spindles £11.00 P & P £1.00 (£12.96 inc. VAT & P.). N.M.S.

CITENCO 19 RPM

FHP motor type C 7333/15 220/240V a.c. 19 r.p.m. reversible motor. torque 14.5 kg. gear ratio 14:1. Brand name capacitors. our price £14.25. P & P. £1.25 (£16.20 inc. VAT & P.). N.M.S.



FRACMO MOTOR

1400 rpm H.P. 1/2 continuously rated 115V a.c., fitted with anti-vibration cradle mounting. Supplied complete with transformer for 230/240V a.c. op. £10.00 P. & P. £1.00 (£11.88 inc. VAT & P.) N.M.S.

ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon vana oil free vacuum pump and compressor. Approx 20 inch vacuum 10 PSI at .79 CFM Powered by 110V a.c. 1.8 amp Parvalux motor fitted with additional shaft at rear, suitable light loads. Inc. capacitor £14.00 p&p. £1.50 (£16.74 inc. VAT & P.) Brand name transformer for 230/240V a.c. operation £5.00 p&p £1.00 (£6.48 inc. VAT & p&p) N.M.S.



BLOWER VACUUM PUMP

English Electric 3 phase AC motor 270/250V. Or 380/440V. 1.425 r.p.m. 1/2 h.p. continuously rated. Direct coupled to William Alday & Co. Alcosa carbon vein blower vacuum pump 0.9 cfm 8.H.G. Price £22 p&p £2 (£25.92 inc. VAT & p) N.M.S.

PROGRAMME TIMERS

12 cam model £7.50. Post 60p (£8.75 inc. VAT & P.). Also available for 50V operation. Price as above. N.M.S.



Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £7.75. P. & P. 75p (£9.18). R. & T.



SANGAMO WESTON TIME SWITCH

Type S251 200/250V. a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia. 4 x 3 price £6.50 P & P. 50p (inc. VAT £7.56. Also available with Solar dial. R. & T.

Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors. 10 for £1.50 p&p 50p. (£2.16 inc. VAT & p&p) (Min 10) N.M.S.

230V a.c. FAN ASSEMBLY

Powerful continuously rated a.c. motor complete with 5 blade 6 1/4 in. Aluminium fan. Price £3.00. P. & P. 65p (£3.94). N.M.S.



KEY: N.M.S. New Manufacturers Surplus R. & T. Reconditioned and Tested

Personal callers only Open Saturdays

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576



A quality range of British made electrical accessories plus a How to... book. Do your own home electrical work with complete confidence. See cat. pages 129 to 134.



This superb organ - build the first working section for just over £100. Full specification in our catalogue.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.



A pulse width controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.

MAPLIN

ELECTRONIC SUPPLIES LTD


All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



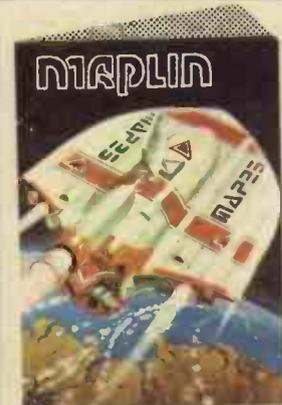An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £13.88 (incl. VAT & p) MA1023 module only £8.99 (incl. VAT).



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.

Post this coupon now for your copy of our 1979-80 catalogue price 75p. Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____