

Australia 95c

New-Zealand 95c

South Africa 90c

Malaysia \$2.75

PRACTICAL

# ELECTRONICS

AUGUST 1979

50p



COMPUTER UK 101  
SINGLE  
BOARD  
COMPUTER

- \* IN HIGH SPEED BASIC
- \* FULLY EXPANDABLE


Also: HOME FREEZER ALARM

# COMPUKIT UK101


## LOW COST SUPERBOARD

### IN KIT FORM

**SAMPLE TAPE included FREE**

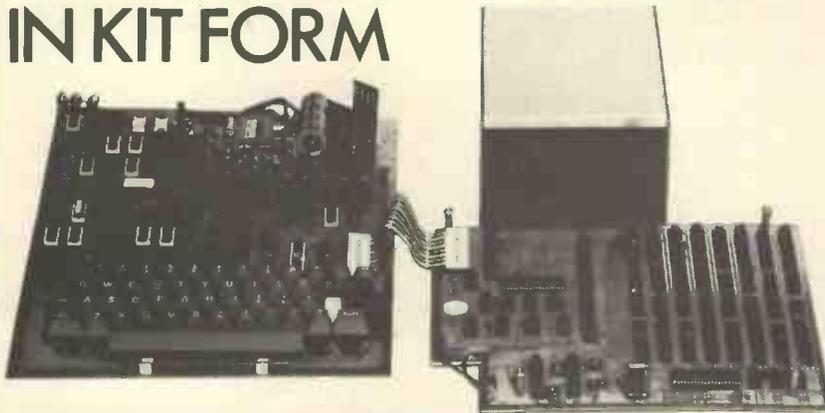

The CompuKit UK101 Character Set

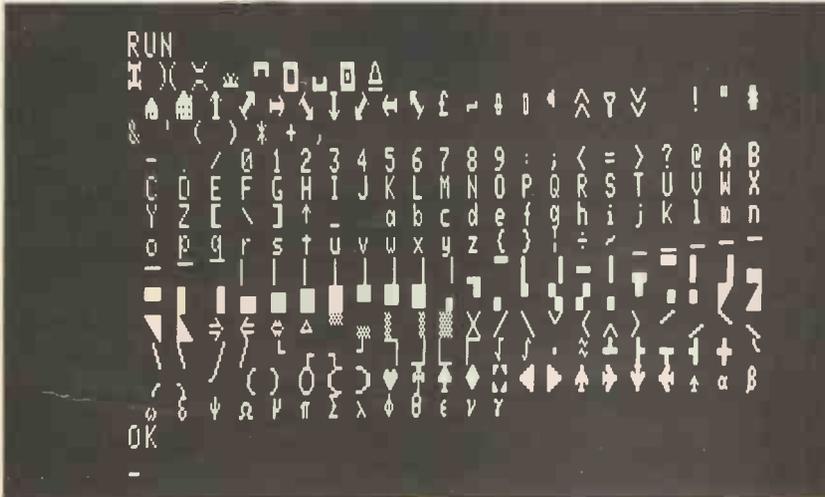

- The CompuKit UK101 has everything a one board 'superboard' should have.
- ★ Uses ultra-powerful 6502 microprocessor.
  - ★ 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
  - ★ 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs.
  - ★ Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen
  - ★ 8K full Microsoft Basic in ROM compatible with PET. APPLE SORCERER hence taking the headache out of programming by using simple English statements. Much faster than currently available personal computers.
  - ★ Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software.
  - ★ Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF.
  - ★ Fully stabilised 5V power supply including transformer on board.
  - ★ Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder.
  - ★ 4K user RAM expandable to 8K on board £49 extra.
  - ★ 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible).
  - ★ 6502 machine code accessible through powerful 2K machine code monitor on board.
  - ★ High quality thru plated P.C.B. with all I.C.'s mounted on sockets.

**FULL CONSTRUCTION DETAILS IN P.E. AUG 1979 EDITION**

**Delivery date June 1979**  
at the 1979 MicroComputer Show  
Customer orders in strict rotation only.

A tape of 10 programs on cassette — educational games, etc. will be supplied free of charge with each kit.

Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc,PhD

**NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.**

Build, understand, and program your own computer for only a small outlay.

**ONLY £219 + VAT**  
Including RF Modulator & Power supply.  
Absolutely no extras.

Due to the new prices of TTL this price will be increased shortly. So order now to beat the price increases and the rush.

- SPECIAL CHARACTERS**
- @ Erases line being typed, then provides carriage return, line feed.
  - ⏏ Erases last character typed.
  - CR Carriage Return — must be at the end of each line.
  - ↵ Separates statements on a line.
  - CONTROL/C Execution or printing of a list is interrupted at the end of a line.
  - "BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.
  - CONTROL/O No outputs occur until return made to command mode. If an Input statement is encountered, either another CONTROL/O is typed, or an error occurs.
  - ? Equivalent to PRINT
- COMMANDS**
- |              |          |         |            |
|--------------|----------|---------|------------|
| CONT LIST    | NEW      | NULL    | RUN        |
| STATEMENTS   |          |         |            |
| CLEAR DATA   | DEF      | DIM     | END FOR    |
| GOTO GOSUB   | IF GOTO  | IF THEN | INPUT LET  |
| NEXT ON_GOTO | ON_GOSUB | POKE    | PRINT READ |
| REM          | RESTORE  | RETURN  | STOP       |

<b>FUNCTIONS</b>	ABS(X) LOG(X) SPC(I)	ATN(X) PEEK(I) SQR(X)	COS(X) POS(I) TAB(I)	EXP(X) RND(X) TAN(X)	FRE(X) SGN(X) USR(I)	INT(X) SIN(X)
<b>STRING FUNCTIONS</b>	ASC(X\$) RIGHT\$(X\$,I)	CHR\$(I)	FRE\$(X\$) STR\$(X)	LEFT\$(X\$,I)	LEN\$(X\$) VAL(X\$)	MID\$(X\$,I,J)

**EXPRESSIONS**  
OPERATORS  
+ , \* / % ^ NOT, AND, OR, >, <, <=, >=, RANGE 10<sup>32</sup> to 10 + 32

**VARIABLES**  
A, B, C, ..., Z and two letter variables  
The above can all be subscripted when used in an array. String variables use above names plus \$ e.g. AS

**COMP COMPUTER COMPONENTS**

Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number.  
14 STATION ROAD, NEW BARNET, HERTS. TEL: 01-441 2922 (Sales) 01-449 6596  
OPEN — 10 am to 7 pm — Monday to Saturday



(Part of the Compshop Ltd. Group)

# PRACTICAL ELECTRONICS

VOLUME 15 No. 8 AUGUST 1979

## CONSTRUCTIONAL PROJECTS

- HOME FREEZER ALARM** by *P. E. Chaplin*  
Early warning of an expensive thaw 18
- AF/RF SIGNAL GENERATOR** by *J. Gerrard*  
Simple test gear for field servicing 21
- COMPUKIT UK 101—PART 1** by *A. A. Berk, B.Sc.Ph.D.*  
Single board computer with resident BASIC 24
- CLASS A HEADPHONE AMPLIFIER** by *Stephen Price*  
Quality headphone listening 62
- CHIMESONIC** by *P. E. Copeland*  
Door chime with retunable melody modules 66

## GENERAL FEATURES

- MICROBUS** by *D.J.D.*  
A bi-monthly focus on micro's for the home constructor 42
- SEMICONDUCTOR UPDATE** by *R. W. Coles*  
A look at some recently released devices—INS 8295, MK 4816,  $\mu$ A78MGU1C 45
- INGENUITY UNLIMITED**  
Lightning Chess Timer—TTL Oscillator—D.C. Ringing for Intercoms—Shorted Turns Detector—Sound Operated Flash—Meter for Electrolytics 46
- SOLDERS AND SOLDERING** by *P. Dinsdale*  
Industrial theory and practice plus advice for the amateur 50

## NEWS AND COMMENT

- EDITORIAL** 17
- SPACEWATCH** by *Frank W. Hyde*  
Astronomy Satellite, UV Explorer, Shuttle, Second Fleetsatcom, Venus, Fall of Skylab 33
- MARKET PLACE**  
New products 34  
Spring Trade Shows 36
- NEWBEAR 77-78** by *P. Birnie*  
Review of a ready to use microkit 38
- NEWS BRIEFS**  
Flicker to Fluorescent—No Cause for Alarm—Countdown—Return of Steam—B.A.E.C. Hon. Sec. Move 53  
Japanese Production in USA—Yorkshire Computer Club—A Fluke Occurrence—Fast Delivery—Fight-It-Yourself 65
- PATENTS REVIEW**  
Torsional Metering—Doughnut Damping 54
- INDUSTRY NOTEBOOK** by *Nexus*  
What's happening inside industry 57
- READOUT**  
A selection of readers' letters 58
- BOOK REVIEWS** 70
- POINTS ARISING**  
Metermate—Autoranging Multimeter—Guitar Sound Multiprocessor—Constant Display Frequency Meter—Ultrasonic Remote Control—Sound Operated Switch 70

**OUR SEPTEMBER ISSUE WILL BE ON SALE FRIDAY, 10 AUGUST 1979**  
(for details of contents see page 61)


© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

# PROOPS

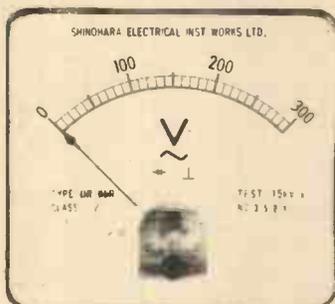**BROTHERS LIMITED**

Special purchase of Shinohara's SEW Panel meters at fantastic low prices

**MR RANGE —  
DC MOVING COIL TYPE**  
(Accuracy  $\pm 2\%$ )



### DIMENSIONS

110 x 120 x 47 mm	Ref 85P	<b>£3.00</b>
78 x 86 x 41 mm	Ref 65P	<b>£2.50</b>
60 x 60 x 40 mm	Ref 52P	<b>£2.50</b>
50 x 50 x 34 mm	Ref 45P	<b>£1.50</b>
42 x 42 x 32 mm	Ref 38P	<b>£1.50</b>

Prices inclusive of VAT. Add 25p per item carriage and packing.

### References:

$\pm 50\mu A$	50mA - DC	5V - DC
$\pm 100\mu A$	100mA - DC	10V - DC
$\pm 500\mu A$	200mA - AC	15V - AC
$\pm 1mA$	500mA - AC	15V - DC
50 $\mu A$	500mA - DC	50V - AC
200 $\mu A$	1A - AC	50V - DC
1mA 'S'	1A - DC	150V - AC
5mA	10A - DC	150V - DC
10mA	30A - DC	300V - AC
50mA - AC	50A - AC	300V - DC
	50A - DC	500V - AC

Most values available in most sizes.

Please state second preference when ordering.

## ED 107 EDUCATIONAL RANGE



Dimensions: 78 (H) x 90 (D) x 100 (W) mm

**£3.50** each including VAT. Add 50p per item carriage and packing.

50 $\mu A$	$\pm 1mA$	5/50V DC	50V DC
100 $\mu A$	10V	20V DC	300V DC

Barclaycard & Access Accepted - Order by phone or post.

**Mail Orders to Proops Bros. Limited, Dept PE8**  
The Hyde Industrial Estate, Edgware Road,  
London, NW9 6JS. Tel. 01-205 8006

**Personal Shoppers: 52 Tottenham Court Road,**  
London, W1P 0BA. 9-6 Mon-Sat.

## Now, complete your system!



### Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system 4/6 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £84.24.

### The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor: 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.77, or our fabulous Pazo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.18 each.



### Projectors

Come and see our specially selected projectors from £42.12 (Isaure Multifect 150) to £94.50 (Tutor 11E) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



### Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive. ONLY £28.12.



### Bulgin Octal plugs and sockets

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.65. P551 PLUG £1.94.



### Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES.

Multiway Cables  
4 core (6A) 50p/metre  
8 core (6A) 73p/metre  
6 core (6A) 86p/metre

**PERSONAL CALLERS ONLY**

# Roger Squire's

## Disco Centres

ALL SHOPS OPEN TUE SAT  
LATE NIGHT WED.  
(UP TO 6 PM)

LONDON 176 Junction Road, N19, 50yds Tufnell Park Tube Station. Tel: 01 272 7474  
BRISTOL 125 Church Road, Redfield (Near St. George) 1 mile from end of M32  
MANCHESTER Tel: 0272 550550  
GLASGOW 251 Deansgate 3, 15 mins from City Centre  
Margaret Drive/Kelvinside 20, just behind the BBC. Tel: 041 946 3303

## J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF. Tel: 20767

- 50, OC 71 TRANSISTORS untested for 75p.
- 4 watt 100K LINEAR WIRE WOUND POTENTIOMETERS @ 30p each.
- VARIABLE CAPACITORS 25-25-25pf @ 75p.
- MINIATURE ELECTROLYTICS 8uf 300v.w. or 10uf 250v.w. Both 10 for 60p.
- LED'S TIL 209 - 6 for 50p, 2" Red - 6 for 70p, 2 Green @ 15p.
- 10 ASSORTED SLIDER POTENTIOMETERS for £1.
- 25 5 AMP STUD MOUNTING THYRISTORS untested @ 75p.
- 10 20 AMP STUD MOUNTING DIODES untested @ 57p.
- 50 1 AMP THYRISTORS T05 case untested @ £1.
- 50 VARI-CAP DIODES like 8A 102 untested for 57p.
- 100 C280 CAPACITORS assorted for 57p.
- ERIE REDCAP .01uf 100v.w. CAPACITORS miniature @ 5p each.
- 10 ASSORTED PUSH BUTTON BANKS less knobs for £1.30.
- TANTALUM BEAD CAPACITORS 4.7uf 16v.w., @ 9p, 10uf 10v.w., @ 9p, 33uf 10v.w., @ 9p, 100uf 10v.w., @ 25p.
- UA 742 ZERO CROSSING A.C. TRIGGER TRIGAC with data @ 25p.
- MULLARD TAA 320 M.O.S.T. PRE-AMPLIFIER I.C. with data @ 35p.
- UNI-UNION TRANSISTORS 2N 4871 @ 22p, 2N 6028 @ 25p, 2N 6029 @ 25p, MEU 21 - 22p, MU 4894 - 22p, 4JD5E29 - 22p, TIS 43T @ 20p, D13T1 @ 25p.
- 200 RESISTORS  $\frac{1}{2}$ ,  $\frac{1}{4}$  watt assorted for 75p.
- 20 PHOTO TRANSISTORS AND DARLINGTONS assorted untested @ £1.
- 50, 2 watt ZENERS assorted untested for 57p.
- CRYSTALS: - Glass 87G Base, 3600 C/S, 3660 C/S at £1.30 each, Wire Ended 28KHz, 28.5KHz, 29.75KHz, 29.78KHz, 31.5KHz, 83.997KHz, all at 50p each.
- MINIATURE LOUDSPEAKERS  $1\frac{1}{2}$ " Dia. 8 ohm @ 75p.
- MULLARD BC 548 or BC 549 at 10p each, 8 for 50p.
- ELECTRET MICROPHONE INSERTS with FET Pre-Amp @ £1.85.
- 400mW ZENERS unmarked Good. 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36volt. All at 10 for 40p.
- MULLARD C281 CAPACITORS 1uf 250v.w., @ 20p doz.
- 50 PIV 2 $\frac{1}{2}$  AMP WIRE ENDED DIODES @ 7p, 6 for 25p.
- RCA FM I.C. CA 3089E @ £1.20 each.
- SUB-MINIATURE 470pf TUBULAR CERAMICS at 20p doz.
- PLASTIC BC 108 TRANSISTORS with house numbers at 10 for 60p.
- 10 AMP S.C.R.'s 100 PIV., @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
- 100 MULLARD C280 CAPACITORS assorted @ 57p.
- 50, AC 128 TRANSISTORS. Branded but untested @ 57p.
- PL 504 CERAMIC VALVE HOLDERS at 5 for 60p.
- 600 MHz FREQUENCY METER @ £115. S.A.E. for leaflet.
- 50 PLASTIC PNP-NPN MIXED TRANSISTORS untested @ 57p.
- 50 PLASTIC NPN TRANSISTORS untested for 57p.
- MOTOROLA CMOS CD 4011 10 for £1.
- 10 ASSORTED SLIDER POTENTIOMETERS for £1.
- ELECTROLYTICS 100, 200uf 275v.w., @ 15p, +10p P.P. 10 for £1.45, 150 - 150, 75uf 350v.w., @ 25p, 10 for £2.
- 2 watt WIRE WOUND POTENTIOMETERS 10K or 2K @ 30p, 4 watt 100K @ 30p.
- MINIATURE NON POLARISED CAPACITORS 1uf 63v.w., @ 5p, 4.7uf 63v.w., @ 10p, 10uf 63v.w., @ 15p.
- 5 WATT NPN T05 DARLINGTON TRANSISTORS at 3 for 50p.
- MULLARD POLYESTER capacitors 1uf 160v.w., at 20p doz.
- SUB/MINIATURE TANTALUM CAPACITORS 4.7uf 10v.w., 15uf 10v.w. Both 5p ea.

Please add 20p for post and packing, unless otherwise stated on U.K. orders under £2. Overseas postage at cost.




— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

## STEREO PRE-AMPLIFIER

CPR 1



## POWER AMPLIFIER

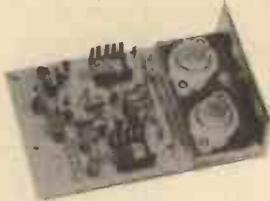

### CPR 1 - THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slew rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/μs; T.H.D. 20Hz - 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 x 80 x 20mm. Supply to be ±15 volts.

### MC 1 - PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

### XO2: XO3 - ACTIVE CROSSOVERS

XO2 - two way, XO3 - three way, Slope 24dB/Octave. Crossover points set to order within 10%.

### REG 1 - POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

### POWER AMPLIFIERS

It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

### POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

## POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



### PRE-AMPLIFIER KIT

This includes all metalwork, pots, knobs, etc. to make a complete pre-amp with the CPR 1(S) module and the MC 1(S) if required.

### ACTIVE CROSSOVERS

XO2 £14.83  
XO3 £23.06

### POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-035v £18.33  
CE 1004 100W/4 ohms 35-0-35v £21.62  
CE 1008 100W/8 ohms 45-0-45v £24.38  
CE 1704 170W/4 ohms 45-0-45v £29.12  
CE 1708 170W/8 ohms 60-0-60v £23.90

### TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £15.55  
CPS2 for 2 x CE 1004 or 2/4 x CE 608 £17.86  
CPS3 for 2 x CE 1008 or 1 x CE 1704 £18.54  
CPS4 for 1 x CE 1008 £16.08  
CPS5 for 1 x CE 1708 £22.68  
CPS6 for 2 x CE 1704 or 2 x CE 1708 £23.98

### HEATSINKS

Light duty, 50mm, 2°C/W £1.35  
Medium power, 100mm, 1.4°C/W £2.20  
Disc/group, 150mm, 1.1°C/W £2.85  
Fan, 80mm, state 120 or 240v £18.50  
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules. £29.16

### THERMAL CUT-OUT, 70°C

£1.45

### POWER AMP KIT £32.90

**PRE-AMPS:**  
These are available in two versions - one uses standard components, and the other (the S1) uses MO resistors where necessary and tantalum capacitors.

CPR1 £30.96 CPR1S £39.98

MC1 £20.81 MC1S £32.44

**POWER SUPPLY:** £37.24

REG1 £6.75 TR6 £1.92

**PRE-AMP KIT** £37.24

**BRIDGE DRIVER, BDI** £37.24

Obtain up to 340W using 2 x 170W amps and this module.

**BD1** £6.40

**CRIMSON ELEKTRIK**  
1A STAMFORD STREET,  
LEICESTER LE1 6NL

Tel. (0533) 553508

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information. UK - please allow up to 21 days for delivery.

**Distributors:** Badger Sound Services Ltd, Minic Teleprodukt, Box 12035 S-750 12 Uppsala 12, Sweden. 46 Wood St. Lytham St. Annes, Lancashire, FY10 1QC.

## DIGITALLY SYNTHESIZED DOOR CHIME

• 24 tunes including "Rule Britannia", "Col. Bogie" etc.

Adjustable speed and tone.

In sturdy moulded case, taking internal PP3 batteries.

1 year guarantee. Special reduced price for PE readers only £14.95.

### Don't Let Your Environment Dehydrate You!

Buy our Honeywell Humidity Controller.  
Membrane actuated, very sensitive 1/2 shaft, 250V, 3.75A  
Contacts: Ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 50p ea. 5 for £2.

### CASSETTE MOTORS

Self Regulating will operate 8-12V Ideal for modelers, mechanical switching etc. 2000 R.P.M. approx. 90p ea.

### ULTRASONIC TRANSDUCERS

Transmitter and receiver. 40 kHz 14 mm diam. £4.25 pair.

### 6 x 6 POLE REED RELAYS ON BOARD

12V ideal for burglar alarms, model railways etc. £2.45

### 100 MINIATURE REED SWITCHES

We are the cheapest! £3.30

### EARPIECES

Magnetic with plug and lead 25p ea. 5 for £1  
Crystal with lead 40p ea. 3 for £1

### MAKE CHEAP BATTERY ELIMINATORS

Fully shrouded mini mains transformers: 240V in 8.0-8V at 100 mA out. Complete with mains lead and plug, ex new equip. 90p

### DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq ins copper clad F.G. board, 1 lb ferric chloride, 1 dialo etch resist pen, Abrasive cleaner, Etch tray plus instructions. Special Price £6.95  
1 lb FE. C1. To mil. spec. £1.25  
6 lb FE. C1. To mil. spec. £5.00  
150 sq in. Single sided board £2.00  
150 sq in. Double sided board £3.00

### SMOKE AND GAS DETECTOR

Uses TGS 105 plug in sensor, housed in neat 3 1/2" dia cast box. led indicator. 24V, (12V by altering 3 component values). Will operate lamp or relay, with data and circuit £8.95  
Relays for above £1 ea. state voltage

### TRANSISTOR PACKS

100. Full spec, new and marked. Includes BC148, BC184L, MEG412, BF274, BC154 etc. etc. £4.95  
200 as above and includes AC128, 2N3055, BFY50, BD131, BF200 etc. £9.95

Buy bulk and save money, these packs are worth at least double.

### P/B SWITCH BANKS

These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole etc. Can be modified. Can't be repeated. 3 Banks for £1

### BULK BARGAINS, STOCK UP FOR WINTER

300 mixed 1/2 & 1/2 watt resistors £1.50  
150 mixed 1 & 2 watt resistors £1.50  
300 mixed capacitors, modern, most types £3.30  
100 mixed ceramic and plate caps £1.20  
25 pots and presets £1.50  
25 presets, skeleton etc. £1.20  
20 VDRs and thermistors £1.20  
100 Hi-wattage resistors wirewound etc. £2.20  
100 electrolytics, nice values £2.20  
300 printed circuit resistors £1  
300 printed circuit components £1.50

100K MINIATURE THUMBWHEEL SLIDER POTS  
Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1

### 100K STEREO SLIDER POTS

Good quality. 25p ea. 5 for £1

### MINIATURE LEVEL/BATT. METERS 200μA

F.S.D. as fitted to many cassette recorders. 90p

40p P & P on all above items. Cheque or P.O. with order to:

**SENTINEL SUPPLY, DEPT. P.E.**  
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

# ARE YOU A MICRO-COMPUTER MANIAC?

Then cut along the dotted line...

Send this ad. today and receive by return of post, a FREE brochure - the complete enthusiasts guide to the microcomputer market.

Name: \_\_\_\_\_

Address: \_\_\_\_\_

Postcode: \_\_\_\_\_

## MICRODIGITAL

25 Brunswick Street,  
Liverpool.

051-227 2535

# PRIME TTL & CMOS AT LOWEST PRICES

ALL NEW

# REAL-STATE OF-THE-ART

NEW LOW PRICES

54xxTTL	74126 35u	74152/71 60u	74515 65u
5400 60u	74122 50u	74152/83 100u	74520 70u
5401 60u	74161 55u	74152/90 100u	74522 80u
5402 90u	74145 50u	74152/95 120u	74530 60u
5403 60u	74148 90u	74152/98 100u	74532 70u
5404 90u	74150 90u	74153/05 60u	74551 40u
5405 90u	74151 50u	74153/07 60u	74564 70u
5406 15u	74152 80u	74153/08 80u	74566 70u
5408 90u	74153 90u	74153/09 80u	74575 90u
5409 90u	74154 90u	74153/10 150u	745112 150u
5410 90u	74155 50u	74153/13 180u	745113 120u
5413 15u	74156 50u	74153/14 100u	745115 100u
5416 120u	74157 50u	74156/0 100u	745132 150u
5417 90u	74158 80u	74160 80u	745133 70u
5420 90u	74159 80u	74160 80u	745134 60u
5423 90u	74160 80u	74160 80u	745135 100u
5425 90u	74161 80u	74202 24u	745138 15u
5426 90u	74162 80u	74204 75u	745139 15u
5427 90u	74163 80u	74208 25u	745140 70u
5430 90u	74164 80u	74210 24u	745151 195u
5432 90u	74165 80u	74214 120u	745152 210u
5433 90u	74166 120u	74220 25u	745157 275u
5440 90u	74167 175u	74230 24u	745158 195u
5442 150u	74170 125u	74232 25u	745174 280u
5445 150u	74173 110u	74242 94u	745175 175u
5446 275u	74174 75u	74248 96u	745189 175u
5447 400u	74175 75u	74273 62u	745194 175u
5450 90u	74176 75u	74274 75u	745200 32u
5451 90u	74177 75u	74275 65u	745273 180u
5453 90u	74178 130u	74283 125u	745274 115u
5454 90u	74179 80u	74285 60u	745275 115u
5460 90u	74180 70u	74286 80u	745280 220u
5470 120u	74181 140u	74289 395u	745287 280u
5472 120u	74182 80u	74290 92u	745290 400u
5473 150u	74184 125u	74293 92u	745305 195u
5474 150u	74185 125u	74295 104u	745310 295u
5475 150u	74188 200u	74297 107u	745312 105u
5476 150u	74190 85u	74251 178u	745313 115u
5480 150u	74191 85u	74254 200u	745316 200u
5483 400u	74192 80u	74257 178u	745317 178u
5485 300u	74193 80u	74260 108u	745347 120u
5490 300u	74194 80u	74261 108u	745343 495u
5491 200u	74195 30u	74262 108u	745346 108u
5493 200u	74196 80u	74263 108u	745367 215u
5495 400u	74197 70u	74264 108u	745371 300u
5496 150u	74198 120u	74265 108u	
54100 400u	74199 120u	74273 116u	
54107 200u	74201 130u	74274 108u	
54109 150u	74202 100u	74275 150u	4000 13u
54121 200u	74203 125u	74276 130u	4001 13u
54125 200u	74204 125u	74277 130u	4002 13u
54126 200u	74203 125u	74278 130u	4006 90u
54132 400u	74205 110u	74279 130u	4007 100u
54145 300u	74206 110u	74221 48u	4008 80u
54150 400u	74207 110u	74201 48u	4009 35u
54151 300u	74208 110u	74202 48u	4010 150u
54153 300u	74209 110u	74203 48u	4011 16u
54154 400u	74210 110u	74204 48u	4012 16u
54155 300u	74211 110u	74205 48u	4013 16u
54157 300u	74212 110u	74206 48u	4014 90u
54164 300u	74213 110u	74207 48u	4015 80u
54165 300u	74214 110u	74208 48u	4016 80u
54166 300u	74215 110u	74209 48u	4017 40u
54174 500u	74216 110u	74210 48u	4018 85u
54177 400u	74217 110u	74211 48u	4019 40u
54180 300u	74218 110u	74212 48u	4020 85u
54181 400u	74219 110u	74213 48u	4021 85u
54182 300u	74220 110u	74214 48u	4022 85u
54185 400u	74221 110u	74215 48u	4023 85u
54190 400u	74222 110u	74216 48u	4024 16u
54191 400u	74223 110u	74217 48u	4025 16u
54193 400u	74224 110u	74218 48u	4026 16u
54194 400u	74225 110u	74219 48u	4027 16u
54195 400u	74226 110u	74220 48u	4028 75u
54197 300u	74227 110u	74221 48u	4029 98u
54221 600u	74228 110u	74222 48u	4030 50u
54251 600u	74229 110u	74223 48u	4031 200u
74xxTTL	74100 10u	74101 10u	4034 190u
7401 10u	74102 10u	74102 10u	4035 100u
7402 10u	74103 10u	74103 10u	4036 100u
7403 10u	74104 10u	74104 10u	4040 100u
7404 12u	74105 10u	74105 10u	4041 75u
7405 15u	74106 10u	74106 10u	4042 75u
7406 25u	74107 10u	74107 10u	4043 75u
7407 25u	74108 10u	74108 10u	4044 75u
7408 15u	74109 10u	74109 10u	4045 75u
7409 15u	74110 10u	74110 10u	4046 75u
7410 12u	74111 10u	74111 10u	4047 75u
7411 18u	74112 10u	74112 10u	4048 85u
7412 15u	74113 10u	74113 10u	4049 100u
7413 21u	74114 10u	74114 10u	4050 100u
7414 40u	74115 10u	74115 10u	4051 65u
7416 24u	74116 10u	74116 10u	4052 65u
7417 24u	74117 10u	74117 10u	4053 65u
7420 20u	74118 10u	74118 10u	4054 100u
7421 20u	74119 10u	74119 10u	4055 22u
7423 20u	74120 10u	74120 10u	4056 20u
7425 20u	74121 10u	74121 10u	4057 30u
7426 20u	74122 10u	74122 10u	4058 21u
7427 20u	74123 10u	74123 10u	4059 21u
7430 12u	74124 10u	74124 10u	4060 100u
7432 20u	74125 10u	74125 10u	4061 75u
7437 22u	74126 10u	74126 10u	4062 22u
7438 22u	74127 10u	74127 10u	4063 22u
7439 30u	74128 10u	74128 10u	4064 22u
7440 16u	74129 10u	74129 10u	4065 22u
7441 58u	74130 10u	74130 10u	4066 20u
7442 38u	74131 10u	74131 10u	4067 20u
7443 100u	74132 10u	74132 10u	4068 20u
7444 100u	74133 10u	74133 10u	4069 20u
7445 70u	74134 10u	74134 10u	4070 20u
7446 52u	74135 10u	74135 10u	4071 21u
7447 57u	74136 10u	74136 10u	4072 21u
7448 60u	74137 10u	74137 10u	4073 21u
7450 15u	74138 10u	74138 10u	4074 21u
7451 15u	74139 10u	74139 10u	4075 21u
7453 15u	74140 10u	74140 10u	4076 21u
7454 12u	74141 10u	74141 10u	4077 40u
7459 20u	74142 10u	74142 10u	4078 29u
7460 16u	74143 10u	74143 10u	4079 70u
7460 27u	74144 10u	74144 10u	4080 70u
7472 24u	74145 10u	74145 10u	4081 150u
7473 20u	74146 10u	74146 10u	4082 150u
7474 22u	74147 10u	74147 10u	4083 85u
7475 30u	74148 10u	74148 10u	4084 145u
7476 30u	74149 10u	74149 10u	4085 65u
7480 45u	74150 10u	74150 10u	4086 70u
7482 55u	74151 10u	74151 10u	4087 90u
7483 48u	74152 10u	74152 10u	4088 90u
7485 55u	74153 10u	74153 10u	4089 90u
7486 27u	74154 10u	74154 10u	4090 90u
7489 135u	74155 10u	74155 10u	4091 90u
7490 25u	74156 10u	74156 10u	4092 90u
7491 55u	74157 10u	74157 10u	4093 90u
7492 30u	74158 10u	74158 10u	4094 90u
7493 25u	74159 10u	74159 10u	4095 90u
7494 50u	74160 10u	74160 10u	4096 90u
7495 45u	74161 10u	74161 10u	4097 90u
7496 45u	74162 10u	74162 10u	4098 90u
7497 187u	74163 10u	74163 10u	4099 90u
74103 24u	74164 10u	74164 10u	4100 90u
74109 45u	74165 10u	74165 10u	4101 90u
74121 24u	74166 10u	74166 10u	4102 90u
74122 35u	74167 10u	74167 10u	4103 90u
74123 35u	74168 10u	74168 10u	4104 90u
74125 35u	74169 10u	74169 10u	4105 90u

Two new 10Hz to 600MHz frequency counters from Optoelectronics USA each c/w built-in Nicads + charging circuits.

MODEL OPTO 8000.1A ONLY £275 (was £320)



- Precision TCXO time base 0.1 PPM stability
- Super sensitivity with preamps in both HI-Z & 50 ohm inputs <math>< 10\text{mV to } 50\text{mV } 25\text{MHz } @ 150\text{MHz } < 50\text{mV to } 600\text{MHz}</math>
- Auto decimal point
- Aluminum case
- Socketed IC's
- Three position attenuator X1, X10, X100 (avoids false counting)

MODEL OPTO 7000 ONLY £125 (was £155)



- TCXO time base 0.08 PPM/PC
  - Aluminum case
  - HI-Z & 50 ohm inputs
  - 1 sec & 1/10 sec gate times
  - Auto decimal point
  - Built-in preamps & prefilter standard
- Frequency Counter Accessories
- P-100 50 ohm I-X £12
  - P-101 Lo Pass £12
  - P102 HI-Z 2X £13
  - Rubber duck RF pick up aerials 146.5 or 450MHz @£17 each



### TELEPHONE ANSWERING BREAKTHROUGH

Let a new remote control answering computer free you from your next telephone call - thanks to microprocessor technology. Code-a-phone 1400 Wirecom command ONLY £225

- Forget about tapes - there are no tapes to buy
- Forget about microphones - just a button, record your message and let go - message does not have to be recycled
- Forget about going home or to the office - hold the small pocket sized remote control paper to any telephone in the world and you can playback all your messages
- Forget about service - Code-a-phone is 100% solid state and will stand up to years of heavy use
- Monitoring facility you can listen to the caller leave his message and pick up the phone to intercept

4xxxCMOS

BRAND NEW FROM EICO MODEL 390 Function/Sweep Generator £137.50



- Offers linear, logarithmic sweeps
- Six position calibrated attenuator
- BNC Front panel output jack
- Generates discrete sine, square and triangle waves from 0.2Hz to 200kHz
- Ideal for checking frequency response of audio amplifiers, driving digital circuits and servo systems
- Features 1000:1 ratio, variable control, 10 volts peak to peak into 50 ohms

ELENCO PRECISION Digital multimeter 1200B The most versatile DMM we have ever offered at lowest ever price!



- 3 1/2 digit jumbo LED display 0.05% basic accuracy
- Measures AC/DC voltages from 100 microvolts to 1000 volts AC/DC current from 1 microamp to 2 Amp, resistance from 0.01 ohm to 20 Megohms
- Fully overload protected to 1000 Volt
- High input impedance 10 Meg-ohm
- Mainly (with adaptor) or battery operation (both disposable and Nicads)
- Uses 1% precision resistors & not unstable trim pots
- High-low power ohms hi for diodes, 10 for resistors in circuit (on how many DMM's costing less than £100 do you find this feature!)

ELENCO POWER SUPPLIES Model XP 600 dual metered regulated variable 0-40V, 0-3 Amp £75 Model XP 90 regulated 13.8V @ 8 Amp - converts your CB/Ham & mobile units to base station £55

MICROPROCESSORS

CPU's	£	RAM'S	£
6502	10.00	SYP2114	6.50
6800	8.00	TMS4044	18.00
8080A	5.00	2120LFPCC	1.50
Z80	11.00	4060	4.50
EPROM			
INTEL			
1702A	4.00	4027	3.50

BRAND NEW! JUST RELEASED 1979 IC MASTER 2500 pages Complete integrated circuit data selector Master guide to the latest IC's including microprocessors and consumer circuits £39.95 inc.

FAIRCHILD RED LED LAMPS #FLV57 Medium Size Clear Case RED EMITTING These are not restated off-spec units as sold by some of our competitors. These are factory prime, first quality, new units

9p each 100 off 6p each 100 off

# AITKEN BROS!

35, High Bridge, Newcastle upon Tyne  
Tel: 0632 26729



**EXP300**  
560 contacts with two 50-point blis-bars. Size 152x53mm. £8-95.  
**PROTO-BOARD 6 KIT**  
630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10-98.

**CSC LOGIC PROBES**  
**LP-2 ECONOMY PROBE**  
Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CHOS circuits. £20-95.

LP-1 Memory Probe £35-65  
LP-3 High Speed Memory Probe £56-75  
CSC catalogue available. Please send S.A.E.

**CALSCOPE SUPER 6 £186-30**  
A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1μs to 100 ms/cm. Full specification to request. Please send S.A.E.

**CALSCOPE SUPER 10 £251-85**  
A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

**TE20D TECH R.F. SIGNAL GENERATOR**  
Accurately covers 120 KCS to 500 MCS in 6 bands. Directly calibrated. Variable RF attenuator 240 VAC. Size 140x215x170mm.  
Price £52-50 (£50-58 to callers).

**TE22D TECH AUDIO GENERATOR**  
Sine & square wave audio generator. Sine wave range -20 cps to 20K cps in four bands.  
Square wave range 20 cps to 15K cps in four bands 240V A.C. Size 140x215x170mm.  
Price £63-31 (£61-31 to callers).

**TMK 500 MULTIMETER** 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts. 0-25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50μa, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included.  
**PRICE £25-95.**

## CSC EXPERIMENTER BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.



**SINCLAIR DM350 £79-95**  
**SINCLAIR DM450 £114-95**

Size 255x148x40mm.  
DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (100μV on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 above. Full spec on request. Please send S.A.E.

**Sinclair PMM200 frequency meter**  
Size 157x76x32mm.  
Range 20Hz to 200MHz. Accessories and illustration as for PDM35 above. £57-95.

**SINCLAIR PDM35 DIGITAL POCKET MULTIMETER**  
DC volts (4 ranges) 1MV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £34-95. AC Adaptor £3-95 de luxe padded carrying case £3-50 MN 1604 Battery £1-14. Size 157x76x32mm.

**SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER.**  
DC volts (4 ranges) 1MV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1μa to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. PRICE £57-95. Carrying case £9-95. AC adaptor/charger. £4-50. Rechargeable Battery Pack. £9-70  
Size 255x148x40mm.

**PANEL METERS**  
DIMS 60MM x 45MM: 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50v AC, 300V ac, "S", "VU" 50-0-50μa, 100-0-100μa, 500-0-500μa. PRICE £5-95.

**DESOLDERING TOOL £6-45**  
SUCTION PUMP.

Education Establishment Orders Accepted.  
PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10.  
ALL PRICES INCLUDE POSTAGE AND VAT.

## Prototyping Micro's for Industry

**VDU-Monitors**  
**Micro Evaluation Kit** (Motorola D2)  
**Keyboards**  
**CCTV Camera** Also available in Kit Form with Comprehensive Manual, available separately at £5-00  
**Standard & Computer Components**  
**Floppy's**  
**P.E. P.C.B.'s**

WRITE OR PHONE TODAY!!!

# CROFTON Electronics Limited

35 Grosvenor Road, Twickenham Middlesex • Tel: 01-891 1923

## Clef Kits -

Designer approved quality kits for Electronic Musical Instrument Construction.

**JOANNA 72 & 88 PIANOS**  
Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. A new physical layout has been adopted to simplify construction.

**P.E. STRING ENSEMBLE**  
The only kit available to the proven A. J. Boothman Design for this versatile String Machine. Specialists in all sizes of Square Front Keyboards. Send S.A.E. to -

**Clef Products (Dept P.E.) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU**

## TOPS THE PACK!

**ACE MAILTRONIX LTD**  
Dept PE Torral Street  
Wakerfield, W. Yorkshire WF1 5JR

**COMPONENTS** - Now over 1,000 types in stock!  
**KITS** - See the new range of low-cost 'ELEKITS'.  
**SERVICE QUALITY PRICES** - 1st Class same day despatch. - All guaranteed products. - Many reductions!  
**MAGAZINE PROJECTS** - Trouble-free!  
S.A.E. for list of PE projects

I enclose 30p\*, please send catalogue.

Name \_\_\_\_\_  
Address \_\_\_\_\_

\*Refundable with future orders over £5.00.



### 20 x 20 WATT STEREO AMPLIFIER

Vacount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red m.m.s indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

£29.90  
£2.50 p&p

### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4.15 ohms speakers.

+ p&p  
£29.00 £2.50

### SPECIAL OFFER

**30 x 30 WATT AMPLIFIER KIT** with BSR P200 belt drive deck and Shure M75 cartridge.

£55.00  
+ p&p £5.00

### EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95  
Per stereo pair  
+ £3.40 p&p.

### BSR P200

Belt drive chassis turntable unit semi automatic, cueing device.

£24.95  
p&p £2.55

A.D.C. DLM 30 Mk III Magnetic Cartridge to suit.

£7.75




**BSR** Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use.

OUR PRICE £10.95 £2.55

### GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£7.95 p&p £2.00 Size 12" x 8 1/2"

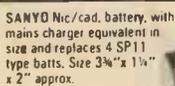

**SANYO** Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

£7.50  
p&p £1.50p



**BARGAIN FOR PERSONAL SHOPPERS ONLY**  
**Altone UA4 Stereo System**

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones complete with speakers.

£34.95

### Micro Cassette Recorder

Pocket size—home or office use or when travelling.

£13.95

### Battery operated fluorescent camping lamp.

Runs off 8 U2 batteries.

£4.50

# Mullard

## AUDIO MODULES IN BARGAIN PACKS

### CURRENT CATALOGUE

PRICE & AT OVER **25** PER PACK

### SEE OUR PRICES

**1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.

OUR PRICE £4.95  
+p&p £1.00

**2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.


illus. OUR PRICE £7.45  
+p&p £1.00

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT.
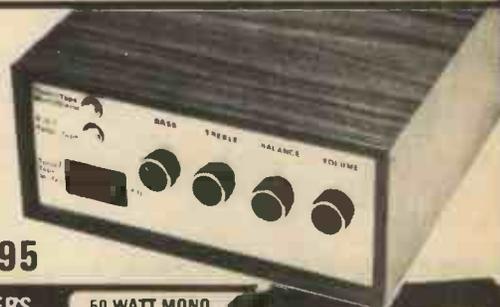
### 10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

Size approximately 9 1/2" x 8 1/2" x 4" p&p £2.05 **£11.95**



### ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance.

£2.90  
plus £1.50 p&p

### Two Way Speaker Kit

Comprising of two 8" x 5" approx 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors.

£3.95  
per stereo pair plus £1.50 p&p

### BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish

£5.95

LCD 5 function men's digital watch stainless steel finish

£6.95

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish

£12.95

POCKET CALCULATOR. With LED display, memory and percentage key

£2.95

AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer

£11.95



125 Watt Power Amp Module

£13.95

MULLARD Built power supply

£3.50

DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc crossovers

£1.50

VIDEOMASTER Super Score TV Game with pistol mains operation

£20.00

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation

£14.95

VIDEOMASTER COLOUR SHOT TV GAME

£41.95

Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED.

OPPORTUNITY AT £9.95 ONLY

### 50 WATT MONO DISCO AMP

£29.95

P&P £2.50

Size approx. 13 1/4" x 5 1/4" x 6 1/4"

50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

### 70 & 100 WATT MONO DISCO AMP

Size approx 14" x 4" x 10 1/4"

Brushed aluminium fascia and rotary controls

Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No 2, or vice versa. Pre fade level control (PFL) lets YDU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

70 watt £57

140 watt peak p&p £4.00

100 watt £65

### DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 speaker units—6" approx. woofer and 2 1/2" approx tweeter 45 to 1800 Hz Impedance 8 ohms. Power 15 watts RMS 20 watts max. Per stereo pair.

For personal callers only. £17.00



### FOR PERSONAL SHOPPERS ONLY

### STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice.

Price £10.95

Size approximately 47" x 15 1/2" x 15"



323 EDGWARE ROAD, LONDON W2  
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 7/5/79 and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

£5.95 - 12 1/2% + 15%



Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits — the very first night — even if you've never used a computer before!

**ELF II featuring RCA COSMAC £79.95**  
microprocessor/  
mini-COMPUTER + VAT

THE FASTEST WAY TO LEARN COMPUTER FUNDAMENTALS! Owning an ELF II is probably the fastest, easiest, most foolproof way to gain a working knowledge of computers the world has ever known. First of all, you get your hands on *your own* computer, so you can spend all the time you want with it and use it for anything that turns you on.

Secondly, our *Short Course in Microprocessor and Computer Programming* makes it impossible for you to fail. We take you inside the RCA 1802 and teach you every instruction it can be given. Everything is explained in plain English. When you're finished, you'll know everything there is to know about using an ELF II. You'll be able to make ELF II do whatever you want it to do. You won't be limited to predeveloped software.

Third, once you understand ELF II inside and out, you'll be ready to use its highly sophisticated add-ons intelligently. And, as you expand your ELF II, you'll begin to appreciate just how advanced its technology really is.

Now Available! Text Editor, Assembler, Disassembler and a new Video Display Board!

The **TEXT EDITOR** gives you word processing ability and the ability to edit assembly language programs while they are displayed on your video monitor. Lines and characters may be quickly inserted, deleted or changed. Add a printer and ELF II can type letters for you — error free — plus insert names and addresses from your mailing list!

ELF II'S **ASSEMBLER** translates assembly language programs into hexadecimal machine code for ELF II use. The Assembler features mnemonic abbreviations rather than numerics so that the instructions on your programs are easier to read — this is a big help in catching errors.

ELF II'S **DISASSEMBLER** takes machine code programs and produces assembly language source listings. This helps you understand the programs you are working with and improve them when required.

The new **ELF II VIDEO DISPLAY BOARD** lets you generate a sharp, professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor — dramatically improving your expanded £79.95 ELF II.

**SPECIFICATION**

- ★ RCA 1802 8 bit microprocessor with 256 byte RAM expandable to 64K bytes
- ★ RCA 1861 video IC to display program on TV screen via the RF Modulator
- Single Board with professional hex keyboard fully decoded to eliminate the waste of memory for keyboard decoding circuits
- Load, run and memory project switches
- 16 registers
- Interrupt, DMA and ALU
- Stable crystal clock
- Built in power regulator
- 5 slot plug in expansion bus (less connectors)

**NEW FROM U.S.A.**  
**the 3rd Hand**

**MAKES CIRCUIT ASSEMBLY A BREEZE!**

Lets you work with both hands!  
Sturdy aluminium construction!  
Accepts boards of any size!



**STEP 1.** Clamp '3rd' hand on edge of bench, table or workboard. Insert circuit board, position components. Note: convenient working angle.



**STEP 2.** Flip circuit board to flat position for soldering and clipping. Reverse procedure for double-sided boards.

Dealer enquiries invited

**INTRODUCTORY OFFER**

**£7.85 inc.**

Sole importers  
**PARA SALES, 1 Hook Road, Kingsclere, Newbury, Berks.**

**SYSTEM DESIGN WITH MICROPROCESSORS**

by D. Zissos Price: £7.00

**BASIC FOR HOME COMPUTERS A SELF TEACHING GUIDE**

by B. Albrecht Price: £4.55

**BEGINNER'S GUIDE TO HOME COMPUTERS**

by M. Grosswirth Price: £3.20

**MASTER OP-AMP APPLICATIONS HANDBOOK**

by H. W. Fox Price: £7.75

**UNDERSTANDING DIGITAL ELECTRONICS**

by Texas Inst. Price: £3.90

**PRACTICAL ELECTRONICS**

by B. Woollard Price: £3.65

**DIGITAL ELECTRONIC CIRCUITS & SYSTEMS**

by N. M. Morris Price: £4.30

**ELECTRONIC FAULT DIAGNOSIS**

by G. C. Loveday Price: £3.20

**SOLID STATE BASICS FOR THE RADIO AMATEUR**

Price: £4.00

**MICROELECTRONICS**

Price: £3.60

\*ALL PRICES INCLUDE POSTAGE\*

**THE MODERN BOOK CO.**

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books

**19-21 PRAED STREET  
LONDON W2 1NP**

Phone 01-723 4185

Closed Saturday 1 p.m.

In addition to I/O, monitor, memory, ASCII keyboard and BASIC, ELF II offers you exotic add-on features such as the ELF II Light Pen and the ELF II Colour Graphics and Music System.

It's no wonder ELF II's are being used by schools and universities, factory training programmes, trade schools and R&D Labs.

ELF II and all ELF II add-ons are also available — wired and tested. And, as if all that weren't enough, the help that's always available from our Service Department further guarantees your success!

To: NEWTRONICS, HL AUDIO LTD  
138 Kingsland Road, London E2 8BY  
Please send me the items below:

**PHONE ORDERS ACCEPTED**  
Call 01-739 1582

- Power Supply (required) £6 + VAT
- RCA 1802 User's Manual £4
- Tom Pittman's Short Course on Microprocessor & Computer Programming teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language it's a learning breakthrough for engineers and laymen alike. £4
- Deluxe Metal Cabinet with Plexiglas dust cover for ELF II £23.01 + VAT

- I am also enclosing payment (including postage and handling) for the items checked above.
- I want my ELF II wired and tested £99.95 + VAT
- Add £2 p&h for orders over £15
- Total enclosed £
- Charge it to:
- Access  Barclaycard
- Account No. ....

LET, IF/THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tic-tac-toe plus a drawing game that uses ELF II's hex keyboard as a joystick. 4K memory required £13.50 + VAT

Tom Pittman's Short Course on Tiny Basic for ELF II £4

ELF-BUGTM Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your TV at any point in your program. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! £13.50 + VAT

Text Editor on cassette tape gives you the ability to insert, delete or edit lines and words from your programs while they are displayed on your video monitor. (Add printer and you can use ELF II to type error-free letters plus insert names and addresses from your mailing list) £16.95 + VAT

Assembler on cassette tape translates assembly language programs into hexadecimal machine code for ELF II use. Mnemonic abbreviations for instructions (rather than numerics) make programs easier

to read and help prevent errors £16.95 + VAT

Disassembler on cassette tape takes machine code programs and produces assembly language source listings to help you understand and improve your programs on cassette tape £16.95 + VAT

SAVE 10% Text Editor, Assembler and Disassembler purchased together only £46.76 + VAT (requires Video Display Board plus 4K memory)

ELF II Light Pen, assembled and tested £6.50 + VAT

ELF II Colour Graphics & Music System Board kit £65.95 + VAT

ELF II connects directly to the video input of your TV set without additional hardware. To connect ELF II to your antenna terminals instead, order RF Modulator £2.77 + VAT

Coming soon: A-D, D-A Converter, Controller Board and more!

Print Name.....

Address.....

DEALER ENQUIRIES INVITED



RCA COSMAC ELF II kit @ £79.95 + VAT and handling (requires 8-3 to 8 volts AC power supply)

**ALSO AVAILABLE FOR ELF II**

GIANT BOARDKIT kit with cassette I/O, RS 232-C/TTY I/O, 8 bit P I/O, decoders for 14 separate I/O Instructions and a system monitor/editor £39.00 + VAT

Kluge (Prototype) Board accepts up to 36 ICs £12.33 + VAT

4K Static RAM kit. Addressable to any 4K page to 64K £69.44 + VAT

Gold plated 86-pin connectors (one required for each plug in board) £4 + VAT each

Expansion Power Supply (required when adding 4K RAM) £19 + VAT

Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, on-board regulator, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer £50.58 + VAT

Deluxe metal cabinet or ASCII Keyboard £15.02 + VAT

Video Display Board kit lets you generate a sharp professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor — dramatically improving your unexpanded £79.95 ELF II. Fits inside ASCII Keyboard cabinet £69.95 + VAT

ELF II Tiny BASIC on cassette tape Commands include SAVE, LOAD, ± x + () 26 variables A-Z.

# LOOK!

## Here's how you master electronics.

### .... the practical way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

#### 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

#### 2. Read, draw and understand circuit diagrams.


In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

#### 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.
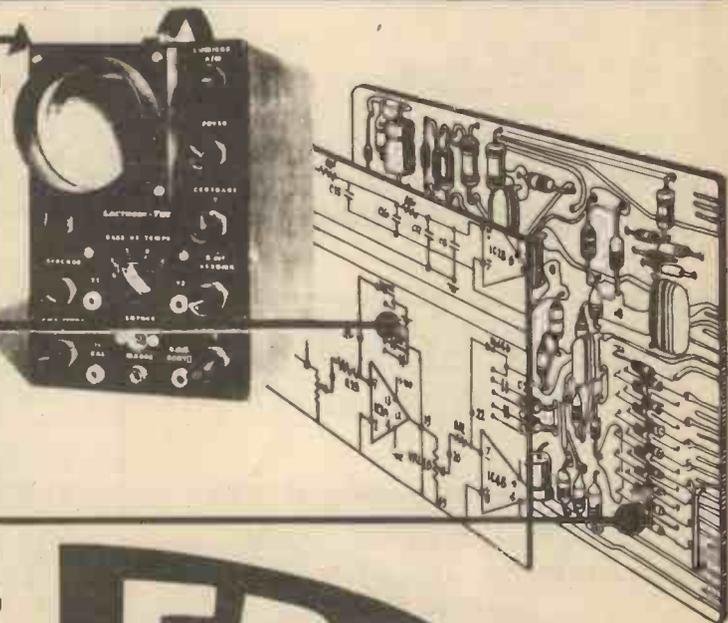
#### 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



# FREE

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**


P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PEB 8/79

Block caps please

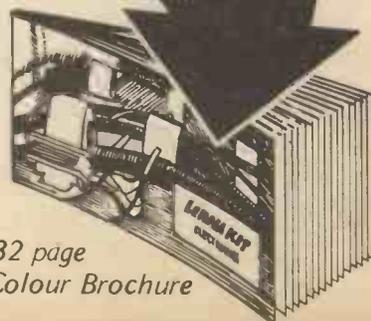

32 page  
Colour Brochure



# NewBear



## 77-68 KITS

BEAR BAG No. 1	77-68 CPU Kit	£45.00
BEAR BAG No. 2	77-68 LEDS & SWITCHES	£14.95
BEAR BAG No. 3	77-68 POWER SUPPLY	£19.95
BEAR BAG No. 4	RACK & BACKPLANE	£27.70
BEAR BAG No. 5	77-68 4K RAM Kit	£65.00
BEAR BAG No. 6	77-68 MON 1 Kit	£50.70
BEAR BAG No. 12	77-68 VDU Kit	£69.50
BEAR BAG No. 13	77-68 MON 2 Kit	£64.10
BEAR BAG No. 16	77-68 ROMA Kit	£29.50
BEAR BAG No. 17	77-68 PIO Kit	£45.00
BEAR BAG No. 23	77-68 32K DYNARAM Kit	t.b.a.
	77-68 MANUAL	£7.50
	P & P 50p.	

## ACORN

The Acorn consists of two single Eurocards:

1. MPU card: 6502 microprocessor: 512 x 8 ACORN monitor; 1K x 8 RAM: 16 way I/O with 128 bytes of RAM: 1MHz Crystal, 5V regulator, sockets for 2K Eprom and second RAM I/O chip.
2. Keyboard card: 25 click-keys (16 hex, 9 control): 8 digit, 7 segment display CUTS standard crystal controlled tape interface circuitry.

Kit **£65.00**  
Ready built **£75.00**

**HEAD OFFICE:** 40 Bartholomew St., Newbury, Berks. 0635 30505

**NORTHERN BRANCH:** 2A Gatley Road, Cheadle, Cheshire.

061 491 2290

## 77-68 P.C.B.'s

77-68	CPU P.C.B.	£10.00
77-68	4K RAM P.C.B.	£10.00
77-68	MON 1 P.C.B.	£10.00
77-68	MON 2 P.C.B.	£10.00
77-68	VDU P.C.B.	£10.00
77-68	PIO P.C.B.	£10.00
77-68	ROM-A P.C.B.	£10.00
77-68	32K RAM P.C.B.	£10.00
77-68	Proto Board (low density)	£9.95
77-68	Proto Board (high density)	£12.00
77-68	Backplane	£4.80
	(P & P 75p)	

## Memories

4116	£8.50
2708	£6.99
2716 (T.I. Type)	£29.50
2102-1	£0.85
2102L-1	£0.99
2112	£2.25
2114	£6.99
SWATBUG	£16.00
MIKBUG	£13.65
<b>Character Generators</b>	
2513(U)	£6.50
2513(L)	£6.50

## CRYSTALS

100.0KHz	£3.25
200.0KHz	£4.20
204.8KHz	£3.35
1.0MHz	£3.50
1.008MHz	£2.80
1.8432MHz	£2.80
2.0MHz	£2.60
4.0MHz	£2.60
5.0MHz	£2.60
10.0MHz	£2.60
13.478MHz	£3.25
37.0MHz	£3.25

**SEND FOR OUR CATALOGUE**

P & P 30p unless otherwise stated. Please add 15% VAT to all prices. Min. official order £10. Barclaycard & Access welcome.

# AURA SOUNDS

THE WERSI SPECIALISTS

Announce the opening of their  
**NEW SHOWROOM**

at Purley Oaks Centre

01-668 9733

for Do-It-Yourself Kits and Ready-Assembled  
Organs, Accessories and Pianos

SEE the **WERSI** KITS

TALK to the **WERSI** SPECIALISTS

HEAR the **WERSI** SOUNDS

SEND £1 FOR OUR 104 PAGE FULL COLOUR CATALOGUE  
AND PRICE LIST TO: -

## AURA SOUNDS

14/15 Royal Oak Centre,

Brighton Rd.,

Purley, Surrey.


Also at 17 Upper Charter Arcade, Barnsley

# ASTRA-PAK

92 GODSTONE ROAD  
WHYTELEAF SURREY CR3 0EB

All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%. Send SAE for complete list of components.

74N 74LSN	74N 74LSN	74N 74LSN	LINEARS	24 pin	0 30
7400 0.12 0.21	7486 0.26	74167 2.70	CA3045 -14 0.45	25 pin	0.44
7401 0.12 0.21	7486 1.50	74169 2.10	CA3046 -14 0.70	40 pin	0.55
7402 0.12 0.21	7489 2.00	74170 1.68 1.94	LM380N -14 0.82		
7403 0.12 0.21	7490 0.35	74172 4.00	LM381N -14 1.20		
7404 0.13 0.21	7491 0.85	74173 1.18 1.12	LM710N -14 0.32	4000 0.14	4067 3.50
7405 0.13 0.21	7492 0.46 0.82	74174 0.89 1.12	LM711N -14 0.32	4001 0.16	4068 0.24
7406 0.28	7493 0.40 0.95	74175 0.68 1.12	MC1310P -14 1.50	4002 0.16	4069 0.17
7407 0.28	7494 0.80	74S175325	NE555N -8 0.30	4005 0.92	4070 0.17
7408 0.14 0.21	7495 0.54 1.05	74176 0.80	NE558N -14 0.65	4007 0.16	4071 0.17
7408 0.40	7498 0.50 1.30	74177 0.82	NE2501B -14 2.00	4008 0.92	4072 0.17
7409 0.14 0.21	7497 2.00	74178 1.20	SN72702N 0.50	4009 0.45	4073 0.17
7410 0.13 0.22	74100 0.94	74179 1.10	SN75110N 0.50	4010 0.48	4075 0.17
7411 0.18 0.21	74104 0.40	74180 0.90	SN78003N 1.95	4011 0.15	4076 1.05
7412 0.21 0.21	74105 0.40	74181 1.75 3.38	SN78013N 1.35	4012 0.18	4077 0.46
7413 0.26 0.46	74109 0.28 0.40	74182 0.75	SN78023N 1.35	4013 0.42	4078 0.22
7414 0.54 1.05	74109 0.45 0.40	74S1822.30	SN75033N 1.95	4014 0.80	4081 0.17
7415 0.21	74110 0.48	74H1830.99	TA6550B 0.35	4015 0.77	4082 0.20
7416 0.27	74111 0.70	74184 1.20	TAA681 1.40	4016 0.42	4085 0.72
7417 0.27	74112 0.40	74185A 1.20	TBA120S 0.64	4017 0.77	4086 0.76
7420 0.13 0.21	74115 0.30 0.40	74186 1.20	TBA641A 1.88	4018 0.87	4089 1.55
7421 0.28 0.21	74114 0.40	74188 2.70	TBA800 0.75	4019 0.42	4093 0.65
7422 0.17 0.21	74116 1.60	74189 3.60	TBA810S 1.04	4020 0.92	4094 1.80
7423 0.25	74118 0.82	74190 1.05 0.96	TA2705D 2.00	4021 0.82	4095 1.10
7425 0.20	74119 1.25	74191 0.99 0.96	TD2020 3.20	4022 0.82	4096 1.10
7428 0.25 0.28	74120 0.82	74192 0.89 1.50	ZN414 1.00	4023 0.15	4097 3.50
7427 0.25 0.30	74121 0.25	74193 1.05 1.50		4024 0.66	4098 1.12
7428 0.34 0.34	74122 0.40	74194 0.90 2.00		4025 0.15	4099 1.90
7430 0.13 0.21	74123 0.50	74195 0.84 1.40	DP AMPS	4026 1.28	4404 1.00
7432 0.24 0.31	74124 1.25	74196 0.90 1.15	CA3130 -1099 1.00	4027 0.50	4412 0.30
7437 0.24 0.26	74125 0.40 0.46	74197 0.90 1.15	LM301A -14 0.32	4028 0.67	4428 0.80
7438 0.24 0.26	74126 0.65 0.46	74198 1.48	LM301A -1099 0.46	4029 0.86	4445 1.50
7440 0.13 0.22	74128 0.82	74199 1.48	LM348N -14 1.00	4030 0.48	4449 0.30
7441 0.52	74132 0.88 0.82	74200 0.80	LM709 -8 0.40	4031 2.34	4501 0.17
7442 0.55 0.70	74134 0.36 0.40	74201 1.50 1.05	LM709 -14 0.42	4033 1.25	4502 0.85
7443 0.90	74135 0.88	74202 1.50 1.05	LM709 -1099 0.50	4034 2.00	4503 2.80
7444 0.90	74138 0.55 0.40	74203 1.50 1.05	LM741 -8 0.22	4035 1.00	4508 2.25
7445 0.70	74137 0.94	74204 1.50 1.05	LM741 -14 0.20	4036 2.40	4510 1.05
7446 0.70	74138 0.62	74205 1.00 0.95	LM741 -1099 0.45	4037 0.99	4511 0.98
7447A 0.60 0.94	74139 0.62	74206 1.10	LM747 -14 0.70	4038 1.00	4512 0.92
7448 0.80 0.94	74141 0.58	74207 1.15	MC1455P -8 0.42	4039 2.00	4514 2.05
7449 0.94	74142 2.00	74208 0.28	VOLTLATE REG	4040 0.88	4515 2.80
7450 0.13	74143 2.00	74209 3.25	LM3000 -1099 1.00	4041 0.77	4518 0.92
7451 0.13 0.21	74144 2.00	74210 2.15 1.80	LM309K -1099 1.00	4042 0.72	4518 0.92
7453 0.13	74147 1.30	74211 0.55	uA723 -14 0.40	4043 0.82	4519 0.50
7454 0.13 0.21	74148 1.15	74212 0.15	7805 TO220 0.85	4044 0.82	4520 1.05
7455 0.26	74150 0.99	74213 0.85	7812 TO220 0.85	4045 1.40	4521 2.00
7460 0.13	74151 0.80 0.90	74214 0.85	7815 TO220 0.85	4046 1.32	4522 1.35
7470 0.28	74153 0.60 0.58	74215 0.85	7824 TO220 0.85	4047 0.96	4527 1.80
7472 0.22	74154 1.00 1.32	74216 0.85	7905 TO220 1.10	4048 0.80	4528 0.82
7473 0.28 0.36	74155 0.83 0.88	74217 0.85	7912 TO220 1.10	4049 0.42	4529 1.10
7474 0.28 0.36	74156 0.82 0.88	74218 1.00	7915 TO220 1.10	4050 0.42	4536 3.50
73574 0.60	74157 0.83 0.80	74219 0.85	DIL SOCKETS	4051 0.84	4553 4.20
7475 0.28 0.42	74158 0.58 0.62	74220 0.85	8 pin	0.11	4052 0.84
7476 0.28 0.36	74159 1.70	74221 0.85	14 pin	0.12	4053 0.84
7478 0.39	74160 0.60 1.30	74222 0.85	18 pin	0.13	4054 1.10
7480 0.46	74161 0.80 0.80	74223 0.85	20 pin	0.23	4055 1.00
7481 0.80	74162 0.80 1.30	74224 0.85	22 pin	0.27	4056 0.98
7482 0.28	74163 0.80 0.82	74225 0.85		0.29	4058 0.48
7483 0.72 0.87	74164 0.80 1.20	74226 0.85			4558 1.25
7484 0.80	74165 0.89	74227 0.85			4559 1.00
7485 0.89 0.87	74166 0.89	74228 0.85			4560 0.86
		74229 0.85			4561 0.86
		74230 0.85			4562 0.86
		74231 0.85			4563 0.75
		74232 0.85			4564 0.86
		74233 0.85			4565 1.03

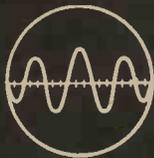

# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING  
CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE

correct at 8.6.79


TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD. 121 Charlmont Road, London SW17 9AB. We accept phone numbers from Access/Barclaycard Holders. Phone 01-672 9080.
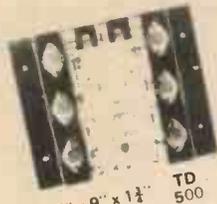
## NEW FROM TUAC ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS

Featuring  
Electronic Short Open & Thermal Overload Protection.


Brief Spec.  
Input Sensitivity 0.775.v. R.M.S. (O.D.B.) at 25 K Ohms  
Frequency Response 20 Hz-20 KHz  
Hum & Noise - 100 dB Relative full output



T.H.D. at full power 0.1%  
T.D. 500 300W into 2 Ohms  
220W into 4 Ohms  
140W into 8 Ohms  
Power supply P.S. 300  
T.D. 150 150W into 4 Ohms  
100W into 8 Ohms  
Power supply P.S. 150  
T.D. 150. 60 Version 60W into 8 Ohms  
40W into 15 Ohms.  
Power supply P.S. 60


£45.00  
£30.00  
£26.25  
£19.75  
£19.75  
£15.50

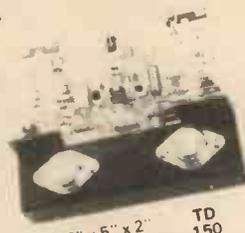Note P.S. 300 will drive 2 T.D. 150 amplifiers



All output ratings are R.M.S. continuous sine wave output.

## AMPLIFIER MODULES

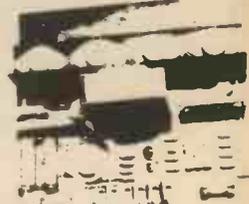

SPEC. INPUT  
SENSITIVITY 60 mV  
for full output  
Frequency response  
20 Hz-20 KHz  
HUM & NOISE 70dB

TL30 5" x 5" x 2"  
\* 35 watt 10 amp output transistors £13.25  
TL60 5" x 5" x 3"  
\* 60 watt R.M.S. continuous sine wave output £18.50  
\* 2 R.C.A. 110 watt 15 amp output transistors  
TL100 5" x 5" x 3"  
\* 100 watt R.M.S. continuous sine wave output £21.50  
\* 2 R.C.A. 150 watt 15 amp output transistors  
TP125 7" x 6 1/2" x 3"  
\* 125 watt R.M.S. continuous sine wave output £27.50  
\* 4 R.C.A. 150 watt 15 amp output transistors


## 4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1

- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2 W to 125W
- Speed control for fixed rate sequence from B per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£21.50

Model 501 500W per channel as above without sound triggering

£14.00

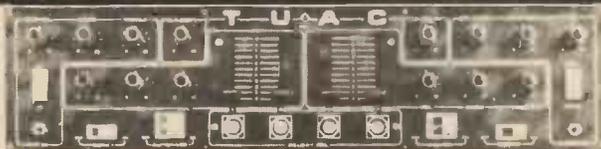

## STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A. comp.) Flat 50mV at 1kHz. Bass controls - 18dB at 60Hz. Treble controls - 18dB at 15kHz.  
OUTPUT: Up to 3 volts (12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz - dB.  
P.F.L. Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.  
Miscellaneous Facilities: Two illuminated deck on off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.  
Size 25in long - 6in high - 3in deep

Mono Disco Mixer with autofade £52.00

£189.00


## 3 CHANNEL LIGHT MODULATOR SILMB

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.75

Single Channel Version 1500 Watts

£9.75

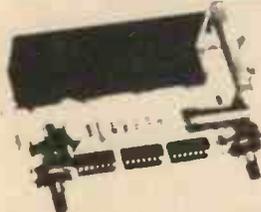

## FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)  
as illustrated



For S1LMB £7.25  
Size 8" x 4 1/2"



4LSM1 £6.00  
Size 6 1/2" x 4 1/2"




FUZZ LIGHTS  
Red, Green, Blue,  
Amber. £24.50



S1LMB £8.25  
Combined with 3SDM1  
Size 9" x 4 1/2"

## POWER SUPPLIES

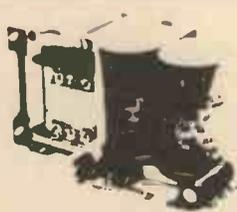

Vacuum varnish impregnated. Transformers  
with supply board incorporating pre-amp supply:

PS250 for supplying 2 TP125s £30.00  
PS200 for supplying to TL100s £30.00  
PS60/60 for supplying 2 TL60s £30.00  
PS125 ± 45 volts for TP125 £18.50  
PS100 ± 43 volts for TL100 £17.00  
PS60 ± 38 volts for TL60 £15.50  
PS30 ± 25 volts for TL30 £11.75  
PSU 2 for supplying disco mixer £7.50

## STOCKISTS—CALLERS ONLY

A1 Music, 88, Oxford Street, Manchester (Tel 061-236 0340)  
Geo. Mathews, 85/87, Hurst St., Birmingham (Tel 021-622 1941)  
Soccodi, 9, The Friars (Tel. Canterbury 60948)  
Cookles Disco Centre, 126/128, West Street (Tel Crewe 4739)  
Garland Bros. Ltd., Deptford Broadway, London 01-692 4412  
Luton Disco Centre, 88, Wellington Street, Luton (Tel Luton 411733)  
Session Music, 163, Mitcham Road, Tooting (Tel 01-672 3413).  
Mon-Sat 10am to 6pm. Closed Wed.  
Electrosure Ltd., Four St., Exeter. Tel. 56687.  
Salcoglen Ltd., 43 Borough Rd., Cleveland, Middlesbrough.  
(Tel. 242851).  
Menhouse Ltd., 82, St. Mary St., Southampton. (Tel 28028)  
Electra Centre, 58 Lancaster Road, Preston (Tel. Preston 58488)  
TRADE & EXPORT ENQUIRIES 01-672 3137

## ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1 £15.25

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED  
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE

# KITS FOR SYNTHESISERS, SOUND EFFECTS



**COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

**CIRCUIT AND LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

**PHOTOCOPIES** of P.E. texts for most of the kits are available—prices in our lists.

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

## P.E. MINISONIC Mk. 2 SYNTHESIZER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, mixer, power supply.

Set of basic component kits (excl. KBD R's and tuning pots - see list for options available). from **£61.00**  
Set of printed circuit boards **£8.99**

## P.E. SYNTHESIZER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage. Details in our lists.

## FORMANT SYNTHESIZER (Elektor 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

## 128-NOTE TUNE-PROGRAMMABLE SEQUENCER

(P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

Main Circuit (Nov) excl. sw's (KIT 76-1) **£19.03**  
Power Supply (KIT 76-3) **£4.72**  
Trigger Inverter and Alt. Output (KIT 76-2) **£1.15**  
LED Counter (KIT 76-4) **£2.10**  
PCB (as published) for KITS 76-1 & 3 (PCB 76A) **£2.61**  
PCB for KITS 76-2 & 4 (PCB 76B) **£2.54**

## P.E. STRING ENSEMBLE (PE Mar-July 78)

The new keyboard string-instrument synthesiser.

Basic component sets:

Power Supply (KIT 77-1) **£8.77**  
Tone Generator (KIT 77-2) **£14.66**  
Diode Gates (KIT 77-3) **£18.81**  
Chorus Generator (KIT 77-4) **£19.08**  
Voicing System (KIT 77-5) **£7.38**

Printed Circuit Boards:

Double-sided PCB for Power Supply, Tone Generator & Diode Gates with most of the Matrix wiring as printed tracking (PCB 77L/R) **£18.40**  
PCB for Chorus Generator (PCB 77C) **£2.65**  
PCB for Voicing System (PCB 77D) **£2.62**

Fuller details of kits & PCBs are in our lists.

## P.E. JOANNA PLUS ORGAN VOICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Tonk, ordinary piano, and Harpsichord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and vibrato.

Set of components (excl switches) for PSU, Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuitries. (Order as KIT 71-5) **£99.25**  
Set of PCBs (Order as PCB SET 71-6) **£29.18**

## GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches **£7.69**  
Alternative component set with panel switches **£5.05**  
Printed circuit board **£1.43**

## ELEKTOR ELECTRONIC PIANO (Elektor Sept 78)

A touch-sensitive, multiple-voicing 5 octave piano using the latest integrated-circuit techniques for the keying and envelope shaping and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos. Details in our lists.

## DIGITAL REVERBERATION UNIT (Elektor May 78)

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring-lines. The basic delay range of 24 to 90ms can be extended up to 450ms using the extension unit. Further delays can be obtained using more extensions.

Main component set (KIT 78-1) **£45.45**  
Extension component set (KIT 78-2) **£43.38**  
PCB for Kit 78-1 (PCB 78A) **£2.86**  
PCB for Kit 78-2 (PCB 78B) **£1.06**

## ANALOGUE REVERBERATION UNIT (Elektor Oct 78)

Using i.c.s instead of spring-lines, the main unit has a maximum delay of up to 100ms, and the additional set extends this up to 200ms. May be used in either mono or stereo mode.

Main component set (KIT 83-1) **£26.18**  
Additional Delay Set (KIT 83-2) **£18.25**  
PCB (as published) to hold both above kits (PCB 9973) **£4.31**

## RESONANCE FILTER (Elektor Oct 78)

This filter module has been designed to allow a synthesiser to produce a more realistic simulation of natural musical instruments.

Basic component set (KIT B2-1) **£15.10**  
PCB (as published) (PCB 9951) **£3.29**

## SYNTHESIZER EXTERNAL INPUT INTERFACE

(P.E. Oct 78)

This unit allows external inputs, such as guitars, microphones etc. to be processed by the circuits within a synthesiser.

Basic component set (incl PCB) (KIT B1-1) **£2.94**

## GUITAR MULTIPROCESSOR (P.E. Dec/Feb 78)

An extremely versatile sound processing unit capable of producing, for example, Flanging, Vibrato, Reverb, Fuzz and Tremolo as well as other fascinating sounds. May be used with most electronic instruments. Details in our lists.

## RHYTHM GENERATOR KITS

Several available - details in our lists.

## GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Component set and PCB **£4.52**

## GUITAR SUSTAIN (P.E. Oct 77)

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches **£5.13**  
Component set, PCB and panel switches **£3.71**

## WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) **£4.26**

## GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot **£7.58**  
Component set using dual rotary pot **£8.89**  
Printed circuit board **£1.62**

## FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) **£2.05**

## TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) **£2.94**

## TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) **£2.51**

## WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektor". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw/s) **£8.40**

## VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 65-1) **£7.17**

## RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 59-1) **£6.50**

## NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 60-1) **£3.84**

## ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) **£4.77**

## ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) **£6.68**

## TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set **£4.87**  
Printed circuit board **£1.82**

## SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektor", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set **£17.38**  
Printed circuit board **£2.33**

## PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) **£3.20**

## PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) **£4.74**

## WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) **£3.83**

## AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches **£7.67**  
Component set and PCB, with panel switches **£4.83**

## VOICE OPERATED FAOER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) **£3.97**

## 10% DISCOUNT VOUCHER (PE 74)

**TERMS:** Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly coded, C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E.

## ADD: POST & HANDLING

U.K. orders - Keyboards add £2.00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1.00 for £100 cover, etc. pro-rata. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

## ADD 12½% VAT

(for current rate if changed). Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports.

**EXPORT ORDERS ARE WELCOME** but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 20p, other countries send 50p.

# AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list: Europe—send 20p; other countries—send 50p.



## KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

- 3 Octave (37 notes) £25-50
- 4 Octave (49 notes) £32-25
- 5 Octave (61 notes) £39-76

Contact Assemblies (gold-clad wire) for use with the above KBDS (1 for each note):

- Type GJ: Single-pole change-over each 25½p
- Type GA: 1 pair of contacts, normally open each 24p
- Type GB: 2 pairs of contacts, each pair normally open each 28½p
- Type GC: 3 pairs of contacts, each pair normally open each 37½p
- Type GE: 4 pairs of contacts, each pair normally open each 48½p
- Type GH: 5 pairs of contacts, each pair normally open each 58½p
- Type 4PS: 3 pairs of contacts plus single-pole changeover each 57p

Printed Circuit Boards for use with most contacts (thus eliminating much interwiring) are available. Details in our lists.

### P.E. TUNING FORK (P.E. Nov. 75)

Produces B4 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

- Main component set (incl. PCB) £14-93
- Power supply set (incl. PCB) £6-28

### SYNTHESISER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

- Component and PCB (but excl sw.) £7-45

### CONSTANT DISPLAY FREQUENCY METER (PE AUG 78)

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

- Component set £24-05\*
- Printed circuit board £3-03\*

\*This kit & PCB are at 8% VAT (all others are 12½%)

### TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

- Standard tolerance set of components £2-96
- Superior tolerance set of components £3-76
- Regulated power supply (will drive 2 sets) £4-89

### DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

- Component set (incl. PCB) £4-58

### DISCDSTRDBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

- Basic component set £18-19
- Printed circuit board £3-45

### BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

- Pre-Amp Module Components set (incl. PCB) £3-95
- Basic Output Circuits—combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lampdriver circuits. £6-59
- Audio Amplifier Module Type PC7 £7-75

### SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Details in lists.

### SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

PRICES ARE CORRECT AT TIME OF PRESS.  
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

## NEW PCB SERVICE

PCBS FOR ALL NEW P.E. & E.E. PROJECTS FOR WHICH PCB LAYOUTS HAVE BEEN PUBLISHED AND FOR WHICH FULL COPYRIGHT CLEARANCE IS AVAILABLE.

LIMITED QUANTITIES ONLY FOR AN EXPERIMENTAL PERIOD.

LET US KNOW YOUR NEEDS AND WE WILL ADVISE YOU OF AVAILABILITY AND PRICES.

### INTEGRATED CIRCUITS

- 301 8-pin DIL 48p
- 318 8-pin DIL 220p
- 320-15 --- 195p
- 324 14-pin DIL 87p
- 341-15 --- 87p
- 709 8-pin DIL 48p
- 723 T05 --- 81p
- 723 14-pin DIL 81p
- 726 T05 1005p
- 741 8-pin DIL 24p
- 748 8-pin DIL 67p
- 4007 14-pin DIL 17½p
- 4011 14-pin DIL 17½p
- 4024 14-pin DIL 46½p
- 4069 14-pin DIL 18p
- 4136 14-pin DIL 126p
- AM2833 8-pin DIL 360p
- AY10212 16-pin DIL 817p
- AY16721/6 188p
- CA3046 14-pin DIL 71p
- CA3080 8-pin DIL 63p
- CA3084 14-pin DIL 209p
- FX209 16-pin DIL 729p
- LM323 --- 662p
- M252 16-pin DIL 680p
- MC3340 8-pin DIL 150p
- MCM6810 24-pin DIL 670p
- SG3402N 14-pin DIL 262p
- STK025 --- 595p
- TOA1022 16-pin DIL 582p
- XR2207 14-pin DIL 420p
- ZN425E 16-pin DIL 375p

### TRANSISTORS

- AC128 ..... 32p
- AC176 ..... 28p
- BC107 ..... 13p
- BC108 ..... 13p
- BC109 ..... 16p
- BC109C ..... 16p
- BC177 ..... 18p
- BC184 ..... 11p
- BC187 ..... 18p
- BC204 ..... 10p
- BC209C ..... 3p
- BC213 ..... 11p

## PHONOSONICS



# Make your hobby more Constructive and Profitable!

## NOW WHAT — 'A' levels, OND, C&G of London Institute . . . ?

Are you thinking about a career in Electronics? If you have Maths, Physics and English Language 'O' levels then why not consider our Technician Engineer Certificate Course. This 2 year full time course gives you a qualification recognised by industry — the Full Technological Certificate — and also provides an entrance qualification for a degree course. Specialisations include Computer Engineering (including Microprocessors), Sound Studio Engineering and Radar and Microwaves. Write to the Secretary, Department of Electronic and Communications Engineering, Polytechnic of North London, Holloway Road, London N7 8DB for details.

The Polytechnic of North London

# FLADAR DUAL VOLTAGE TRANSFORMERS

PRIMARY 220-240 50HZ.  
ALTERNATIVE SECONDARY VOLTAGE AND CURRENT AVAILABLE BY SERIES OR PARALLEL CONNECTION

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
06FE06	6+6	0.5A EACH	1.71	54p	12FE24	24+24	0.2A EACH	2.27	65p
08FE06	6+6	0.6A EACH	2.05	54p	60FE24	24+24	1.2A EACH	4.30	92p
12FE06	6+6	1A EACH	2.27	65p	80FE24	24+24	1.5A EACH	5.10	1.08p
20FE06	6+6	1.6A EACH	2.96	76p					
50FE06	6+6	3A EACH	3.51	76p	50FE28	28+28	0.75A EACH	3.51	76p
60FE06	6+6	4A EACH	4.30	92p	60FE28	28+28	1.1A EACH	4.30	92p
					80FE28	28+28	1.4A EACH	5.10	1.08p
06FE09	9+9	0.3A EACH	1.71	54p					
08FE09	9+9	0.5A EACH	2.05	54p	20FE30	30+30	0.35A EACH	2.96	76p
12FE09	9+9	0.75A EACH	2.27	65p	50FE30	30+30	0.75A EACH	3.51	76p
20FE09	9+9	1A EACH	2.96	76p	60FE30	30+30	1A EACH	4.30	92p
50FE09	9+9	2.5A EACH	3.51	76p	80FE30	30+30	1.2A EACH	5.10	1.08p
60FE09	9+9	3A EACH	4.30	92p					

MULTI TAP RANGE  
VOLTAGES AVAILABLE 12-0-12 or 15-0-15  
3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30

30FE30	1A	3.83	76p
60FE36	2A	5.16	92p
80FE36	3A*	6.48	1.08p

### CENTRE TAP SECONDARY

08FE30	6-0-6	1A	1.66	54p
08FE40	9-0-9	1A	2.00	54p
12FE50	12-0-12	1A	2.21	65p
20FE80	15-0-15	1A	2.89	76p
50FE80	20-0-20	2A	3.43	76p
60FE100	28-0-28	2.2A	4.05	92p
08FE70	24-0-24	3A	4.97	1.08p
80FE60	20-0-20	4A	5.24	1.24p
100FE26	26-0-26	3.5A	5.40	1.24p
100FE28	28-0-28	3.5A	5.40	1.24p
100FE30	30-0-30	3A	5.40	1.24p
100FE36	36-0-36	3A	5.40	1.24p

### CHARGER TRANSFORMER

48FE12	0-6-12	4A	3.51	76p
66FE12	0-6-12	5A	4.32	92p
70FE12	0-6-12	6A	5.50	1.08p

FLADAR ELECTRIC  
P.O. BOX 19  
WESTCLIFF-ON-SEA  
ESSEX. 0702-613314

TRADE ENQUIRIES WELCOME  
PLEASE ENQUIRE FOR OTHER TYPES NOT SHOWN

PAYMENT TERMS:  
C.W.O. Cheques.  
Postal Orders  
All Prices include V.A.T.

# Quality audio modules and accessories for

## S450

STEREO FM TUNER fitted with phase lock-loop

£26.14 + 40p p&p



FREQUENCY RANGE	88-108 MHz
SENSITIVITY	3.0 µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

The S450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage, Varl-Cap diode tuning, Switched AFC LED Stereo Indicator.

## Stereo 30

COMPLETE AUDIO CHASSIS

£21.57 + 66p p&p



7 + 7w R.M.S.

OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dBs
tone CONTROL RANGE	± 12 dBs at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V.A.C. rated at 1A
DIMENSIONS (Less controls and panel)	200mm x 130mm x 33mm

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.

## AL60

AUDIO AMPLIFIER MODULE 25 Watts RMS

£5.27 + 35p p&p



25w R.M.S.

OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

## AL80

AUDIO AMPLIFIER MODULE

£7.92 + 35p p&p



35w R.M.S.

OUTPUT POWER	35 Watts RMS
SUPPLY	40-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

## AL250

POWER AMPLIFIER

£19.24 + 66p p&p



125w R.M.S.

OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50-80 V
LOADS	4-16 ohms
FREQUENCY RESPONSE	25 Hz 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS O/P AT 1 kHz	450 mV
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	0-1% 50 WATTS into 4 ohms 50 WATTS into 8 ohms

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

## AL30A

AUDIO AMPLIFIER MODULES

£4.26 + 35p p&p



10w R.M.S.

MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .25%
LOAD IMPEDANCE	8-16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	50 Hz-25 kHz ± 3 dBs
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm x 63mm x 28mm

These low cost 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

## SPM80

STABILISED POWER SUPPLY

£4.95 + 35p p&p



INPUT A.C. VOLTAGE	33-40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	10 mA-1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm x 63mm x 30mm

Designed to power two AL60s at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

## PA100

STEREO PRE-AMPLIFIER

£18.05 + 40p p&p



FREQUENCY RESPONSE	20 Hz to 20 kHz x 1 dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY	1. TAPE 100 mV/100 K ohms } For an 2. RADIO TUNER 100 mV/100 K ohms } output 3. MAGNETIC P.U. 3.5 mV/50 K ohms } 250 mV
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10-20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All inputs)
INPUT OVERLOAD	Better than 26 dBs (All inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300 x 90 x 33mm (less controls)

A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution to the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

## MPA30

MAGNETIC CARTRIDGE PRE-AMPLIFIER

£3.35 + 35p p&p



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

SENSITIVITY	3.5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V—re earth
DIMENSIONS	110 x 50 x 25mm (inc DIN socket)

## PA12

STEREO PRE-AMPLIFIER

£8.75 + 35p p&p



The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL20/30 Audio Amplifier Modules, the PS12 Power supply and the T538 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.


FREQUENCY RESPONSE	20 Hz-20 kHz (-3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	-60 dB
SIGNAL/NOISE RATIO	-65 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 84mm x 29mm

## PS12 POWER SUPPLY MODULE

Power supply for AL20A-30A, PA12, S450 etc. Transformer T538.

Input A.C. Voltage 15-20V. Output D.C. Voltage 22-30V approx. (Dependent upon input.)

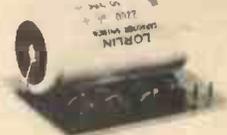Output Current 800mA maximum. Dimensions 60 x 43 x 26mm.



£2.13 + 35p p&p.

## BP124 SIREN ALARM MODULE

American Police siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes.

ONLY £3.78 + 35p p&p.

5 WATTS—



## MA60 HI-FI AMPLIFIER KIT

Build your own top quality amplifier, save yourself pounds. The MA60 kit comprises the following BI-kits modules, 2 x AL60 amps, 1 x PA100 pre-amp, 1 x SPM80 stab. power supply, 1 x BMT80 transf. giving 15 watts RMS per channel STEREO. All modules covered by the BI-PAK satisfaction or money back guarantee. Details of the above modules are in this ad. Price £38.00 + 62p p&p.

## TC60 KIT

A beautifully designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. Front & Back Panels, Knobs, Chassis, Fuses, Sockets, Nolen, etc. Ideal for the MA60. Size: 425mm x 290mm x 95mm. Price £22.44 + 86p p&p.

## TRANSFORMERS

T538 For use with S.450 AL30A MPA30 Order No. 2036 Price: £3.60 + 55p p&p.  
T2050 For use with Stereo 30 Order No. 2050 Price: £3.66 + 55p p&p.  
BMT80 For use with AL60 SPM80 Order No. 2034 Price: £6.08 + 86p p&p.  
BMT250 For use with AL250 Order No. 2035 Price: £7.14 + £1.10 p&p.  
2040, For use with AL60 Order No. 2040 Price: £5.85 + 80p p&p.  
2041, For use with AL80, AL120 and AL250 Order No. 2041. Price: £7.65 + 86p p&p.

## CASES

TEAK 30, 32 x 23 x 8cm, designed mainly for use with our stereo 30 Audio System but has proved very helpful to home constructors. Fitted with solid uncut front and back, o/n 139. £6.69. p&p 70p.

TEAK 60, 42 x 29 x 9cm, for use with AL60/MK60 Audio Kit. Useful for the home constructor requiring an amplifier sleeve — has no front or back panel. o/n 140. £7.87. p&p 85p.

# Professionals and Enthusiasts from BI-PAK

## AL120 AUDIO AMPLIFIER

(With integral heat sink and short-circuit protection)

**£12.91**

+ P. & P. 35p



**50W  
R.M.S.**

Introduced to fulfill the demand for a fully protected power amp., capable of driving high quality speaker systems at up to 50w., with distortion levels below 05%. Ideal for domestic use, Discos, P.A. systems, electronic organs etc. The generously rated components ensure continuous operation at high output levels.

## SPM120 STABILISED POWER SUPPLIES

SPM120/45  
SPM120/55  
SPM120/65

**£6.52**

+ P. & P. 35p



SPM120 is a fixed voltage stabiliser available with an output of either 45v, 55v, or 65v. Designed primarily for use in audio applications, the stabiliser which provides output currents up to 2.5A., operates direct from a mains transformer requiring only the addition of 2 electrolytic capacitors to complete the s/c protection.

## GE100 Mk2.

10 CHANNEL MONOGRAPHIC  
EQUALISER

**£22.50**

+ P. & P. 35p



Only 155mm x 65mm x 50mm including the 10 x 10K 1in slider potentiometers and knobs which are mounted on a board positioned above the circuitry. In the frequency range of 31Hz to 20KHz you can cut and boost  $\pm 12$ dB with the 10 sliders, each of which has its frequency marked on the circuit board. The GE100 has numerous uses including mixers, P.A. systems and discos. It will also greatly improve the sound reproduction of your existing audio equipment. Power Supply for GE100, o/d SG30 £3.80.

## VPS30

REGULATED VARIABLE  
STABILISED POWER SUPPLY

**£8.20**

+ P. & P. 35p



This NEW versatile Regulated Variable Stabilised Power Supply with short circuit protection and current limiting, is a must for all electronics enthusiasts. It incorporates adjustable voltage from 2v-30v, with a current limiting range of 0-2A. With this module there is no need to build a separate power supply for each of your projects, with the simple addition of a transformer (o/d 2033), 0-1ma (o/d 1310 or 1305), plus a suitable shunt, a voltmeter (o/d 1311 or 1306), a 470ohm pot (o/d 1896), a 4K7 pot (o/d 1899), it can be used again and again as a self-contained bench, power supply, eliminating the use of batteries and thus saving ££'s!

## PA200

STEREO  
PRE-AMPLIFIER

**£18.61**

P. & P. 40p



The PA200 is basically our popular PA100. Modifications have been made to make it compatible with the higher output AL120 and AL250 amplifiers.

## HEADPHONES

A top quality headphone with cushioned earpads and headband. Separate balance/volume controls. Stereo or Mono switch. Impedance: 8 ohms. Frequency: 30-18,000Hz. o/n 884. **£9.78. p&p 70p.**

A brilliant compromise between price and performance. Superb stereo reproduction for the newcomer to Hi-Fi. Impedance 8 ohms. Frequency: 30-15,000Hz. o/n 885. **£4.95. p&p 50p.**

## BIB HI-FI ACCESSORIES

Parallel Tracking GROOV KLEEN

The very latest in automatic record cleaning. Designed to suit all modern single play decks. Simple to fit, it is extremely efficient. Complete with two types of base and three height extensions. o/n 8101. **£3.97. p&p 35p.**

**Cassette Tape Editing Kit**  
Enables cassette tapes to be edited and joined easily, quickly and accurately. Kit comprises: Tape Splicer (3.2mm), 2 Precision Tape Cutters, Tape Piercer, 9 Self-adhesive Labels, Reel of Splicing Tape, 3 Winders and removers and instructions, all in a handy wallet. o/n 8111. **£2.69. p&p 35p.**

**GROOV-STAT**  
The BIB Groov-Stat static reducer neutralises the static charge on records and other plastic surfaces. o/n 8103. **£5.89. p&p 35p.**

**Cassette Head Cleaner**  
Essential for cleaning of tape heads, capstans and rollers. Pack contains Tape Head Applicator and tape head polisher tools. Plus bottle of special formula cleaning fluid and full instructions. o/n 832. **£0.72. p&p 35p.**

OUTPUT POWER	50 Watts R.M.S.
SUPPLY	70 Watts
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	05% Max. (Typically 02%)
FREQUENCY RESPONSE	25Hz-20KHz $\pm 1$ dB
SENSITIVITY	500mV
MAX HEAT SINK TEMP.	45 deg. C
DIMENSIONS	192 x 89 x 49 mm

## ADAPTORS

AC-DC enables a large range of battery powered radios, recorders, calculators to be run off the mains (220-240v AC). Switchable for 3-6-9-12 volts. Current rating 300mA. Polarity reversing switch. Universal plug incorporated. o/n 137. **£4.05. p&p 35p.**

DC-DC for use in all cars, boats etc., with pos. or neg. earth for a regulated output of 6, 7.5 or 9 volts DC at 300mA. For radios, recorders etc. o/n 138. **£3.15. p&p 35p.**

## CROSSOVER NETWORKS

2-WAY channels for high and low frequencies to correct speakers - high to tweeters, low to woofers. Complete with instructions. Frequency: 3,000Hz. o/n 1904. **£1.24. p&p 35p.**

2-WAY for 8 ohm speakers up to 30 watts. Frequency: .3KHz. o/n 1905. **£1.81. p&p 35p.**

3-WAY for 8 ohm speakers up to 30 watts. Frequency: 800Hz and 4.5KHz. o/n 1906. **£3.32. p&p 35p.**

## MICROPHONES

### DYNAMIC CASSETTE

For equipment requiring a high quality microphone. Sturdy, solid moulded body in black with neat chrome surround. Pick-up pattern is omnidirectional. On/Off switch, 1 metre of tough lead with floating 2.5 and 3.5mm plugs. Matching moulded strut. Impedance: 200 ohms. Sensitivity: 90dB. Frequency: 90-10,000Hz. Size: 20mm dia x 120mm. o/n 1326. **£1.80. p&p 35p.**

### DYNAMIC MICROPHONE

Superior quality portable cassette recorder mike with built-in remote control switch and lead fitted with 5-pin 240° DIN plug (remote switch) and 3-pin DIN plug (microphone). Provides a direct replacement for those supplied with recorders. With detachable stand. Omnidirectional. Impedance: 200 ohms. Freq. response: 100 to 10,000Hz. Sensitivity: 79dB at 1,000Hz. o/n 1327. **£2.98. p&p 35p.**

### RE-317: DYNAMIC MICROPHONE

Highly sensitive, high-grade desk or hand mike suitable for use with many popular cassette decks. Incorporates On/Off switch and 1 metre lead with moulded standard jack plug. Complete with desk stand. Omnidirectional. Impedance: 5,000 ohms. Freq. response: 100, at 12,000Hz. Sensitivity: (-7dB at 1,000Hz). o/n 1338. **£4.48. p&p 35p.**

### OMNIDIRECTIONAL CARDIOID

Powered by a 1.5v battery located within the aluminium body. Satin silver finish with front disk protection to the diaphragm housing. On/Off switch. Also with 'Busby' type windshield, 'U' bracket and stem and extremely supple cable. Consumption: 0.2mA from 1.5v battery providing approx. 8-10,000 hours continuous life. Impedance: 600 ohms. Sensitivity: 70dB. Frequency: 30-16,000Hz. Size: 23mm dia x 267mm. o/n 1329. **£14.40. p&p 35p.**

### UNIDIRECTIONAL CARDIOID

Dual imp. 600 and 50,000 ohms. Response 50 to 14,000Hz. Sensitivity 54dB at 50K/ohms. Size: 1 1/2" dia x 6 1/2" long. Weight approx. 190gm. o/n 1328. **£12.32. p&p 35p.**

## STANDS

### GOOSENECK CHROME FLEXIBLE HOLDERS

Length 320mm. o/n 1333. **£2.70. p&p 35p.**

Length 515mm. o/n 1334. **£3.83. p&p 35p.**

**FLOOR STAND** Heavy chrome. Stow-away feet with rubber ends for maximum stability. Draws to a height of 5' maximum. o/n 1335. **£10.69. p&p 85p.**

**BOOM ARM** for use with the above stand. Heavy chromed metal. It gives 30" reach from the stand. o/n 1337. **£10.35. p&p 70p.**

## WINDSHIELD COVERS

o/n 1331 Medium per pair **£1.35. p&p 35p.** o/n 1332 Large per pair **£2.03. p&p 35p.**

## AUDIO LEADS

107	FM Indoor Ribbon Aerial	<b>£0.68</b>
113	3.5mm Jack plug to 3.5mm jack plug. Length 1.5m	<b>£0.84</b>
114	5 pin DIN plug to 3.5mm. Jack connected to pins 3&5. Length 1.5m	<b>£0.95</b>
115	5 pin DIN plug to 3.5mm. Jack connected to pins 1&4. Length 1.5m	<b>£0.96</b>
116	Car aerial extension. Screened insulated lead. Fitted plug & ski.	<b>£1.24</b>
117	AC mains connecting lead for cassette recorders & radios. 2 metres	<b>£0.76</b>
118	5 pin DIN phono plug to stereo headphone jack socket	<b>£1.18</b>
119	2 + 2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m	<b>£1.01</b>
120	Car stereo connector. Variable geometry plug to fit most car cassette, 8 track cartridge & combination units. Supplied with inline fused power lead and instructions.	<b>£0.68</b>
123	6.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	<b>£1.62</b>
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	<b>£0.84</b>
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	<b>£0.84</b>
126	5 pin DIN plug to Tinned open end. Length 1.5m	<b>£0.84</b>
127	5 pin DIN plug to 4 Phono Plugs.	
	All colour coded. Length 1.5m	<b>£1.46</b>
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	<b>£0.90</b>
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	<b>£1.18</b>
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	<b>£0.76</b>
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3&5. Length 1.5m	<b>£0.93</b>
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	<b>£1.10</b>
133	5 pin DIN plug to 2 phono plugs. Connected pins 3&5. Length 1.5m	<b>£0.84</b>
134	5 pin DIN plug to 2 phono sockets. Connected pins 3&5. Length 23cm	<b>£0.76</b>
135	5 pin DIN socket to 2 phono plugs. Connected pins 3&5. Length 23cm	<b>£0.76</b>
136	Coiled stereo headphone extension lead. Black. Length 6m	<b>£1.97</b>
178	AC mains lead for calculators etc.	<b>£0.54</b>

AC INPUTS	
SPM120/45	40-48v
SPM120/55	50-55v
SPM120/65	60-65v
OUTPUT CURRENT	2.5A
RIPPLE	1A 100mV 2A 150mV

Control Range	$\pm 12$ dB
Dynamic Range	110dB
Maximum Output	$\pm 15$ dB
Frequency Response	30Hz-20KHz ( $\pm 1$ dB)
Power Supply	15-0-15v.
Voltage Handling Input	3v R.M.S.
T.H.D.	0.05%

AC Input Maximum	25v
Voltage Regulation	2-30v
Regulated Current	0-2A
Incorporating short circuit protection	

FREQUENCY RESPONSE	20Hz to 20kHz x 1dB
TOTAL HARMONIC DISTORTION	Less than 1% (Typically .70%)
SENSITIVITY	1. TAPE 100mV/100 K ohms For an input 2. RADIO TUNER 100mV/100 K ohms output 3. MAGNETIC P.U. 3.5mV/50 K ohms 500mV
EQUALISATION	Within $\pm 1$ dB from 20Hz to 20kHz
BASS CONTROL RANGE	$\pm 15$ dBs at 75Hz
TREBLE CONTROL RANGE	$\pm 10-20$ dBs at 15kHz
SIGNAL/NOISE RATIO	Better than 65dBs (All inputs)
INPUT OVERLOAD	Better than 2dBs (All inputs)
SUPPLY	35 to 706v
DIMENSIONS	300 x 90 x 33mm (less controls)

## METERS

**Miniature Balance & Tuning Meter**  
Miniature moving-coil meter for stereo balance indicator, tuning indicator for FM or similar application. Pointer at centre indicates zero or null position. Robust construction. Sensitivity: 100 0-100mA. Dimensions: 23 x 22 x 26mm. o/n 1318. **£2.11. p&p 35p.**



**Balance and Tuning Meter**  
Clear view edge-wise meter. Centre zero application. Sensitivity: 100 0 100UA. Dimensions: 45 x 22 x 34mm. o/n 1319. **£2.16. p&p 35p.**



**Miniature Level Meter**  
Moving coil, for accurate level indication for tape recorders, amplifiers etc. Neat design, rugged construction will withstand five times rated value. Sensitivity: FSD 200UA. QdB, 130UA. Dimensions: 23 x 22 x 26mm. o/n 1320. **£3.02. p&p 35p.**




**Vu Meter**  
Calibrated 20 to +3 and 0-100%, making it suitable for use as a recording level meter or as a power output indicator. Sensitivity: 130uA. Dimensions: 40 x 29mm. o/n 1321. **£2.16. p&p 35p.**



**BI-PAK**  
DEPT. PE8, P.O. Box 6,  
18 Baldock Street, Ware, Herts.

# From Science of Cambridge: the new MK 14. Simplest, most advanced, most flexible microcomputer – in kit form.

**only  
£39.95  
(+ 8% VAT)**

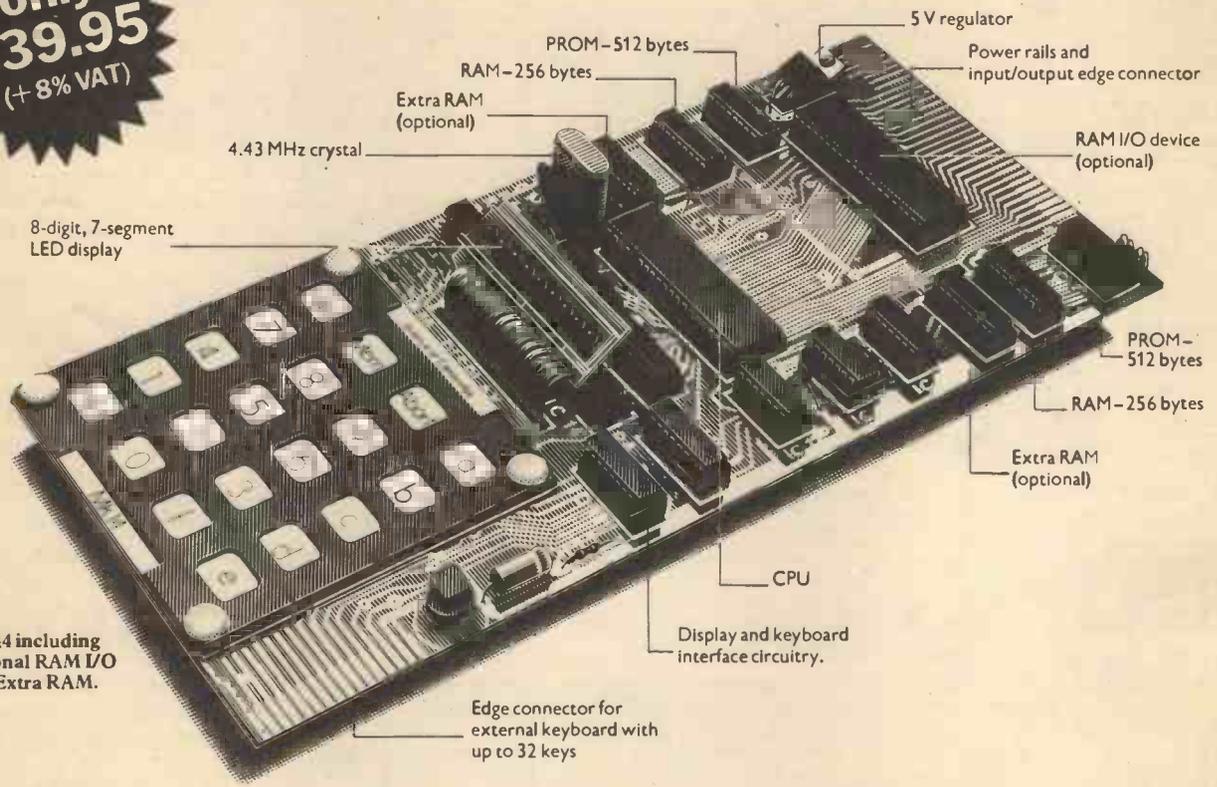

**MK 14 including optional RAM I/O and Extra RAM.**

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte pre-programmed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of user-written programs through the hexadecimal keyboard.

Yet in kit form, the MK 14 costs only £39.95 (+ £3.20 VAT, and p&p).

### More memory – and peripherals!

Optional extras include:

1. Extra RAM – 256 bytes.
  2. 16-line RAM I/O device (allowed for on the PCB) giving further 128 bytes of RAM.
  3. Low-cost cassette interface module – which means you can use ordinary tape cassettes/recorder for storage of data and programs.
  4. Revised monitor, to get the most from the cassette interface module. It consists of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculations and single step, and single-operation data entry.
  5. PROM programmer and blank PROMs to set up your own pre-programmed dedicated applications.
- All are available now to owners of MK 14.

### A valuable tool – and a training aid

As a computer, it handles operations of all types – from complex games to digital alarm clock functioning, from basic maths to a pulse delay chain. Programs are in the Manual, together with instructions for creating your own genuinely valuable programs. And, of course, it's a superb education and training aid – providing an ideal introduction to computer technology.

### SPECIFICATIONS

● Hexadecimal keyboard ● 8-digit, 7-segment LED display ● 8 x 512 PROM, containing monitor program and interface instructions ● 256 bytes of RAM ● 4 MHz crystal ● 5 V regulator ● Single 8 V power supply ● Space available for extra 256-byte RAM and 16 port I/O ● Edge connector access to all data lines and I/O ports

### Free Manual

Every MK 14 kit includes a Manual which deals with procedures from soldering techniques to interfacing with complex external equipment. It includes 20 sample programs including math routines (square root, etc), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

### Designed for fast, easy assembly

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

### How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,  
6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me the following, plus details of other peripherals:

- MK 14 Standard Microcomputer Kit " £43.55 (inc 40p p&p.)
- Extra RAM " £3.88 (inc p&p.)
- RAM I/O device " £8.42 (inc p&p.)

I enclose cheque/money order/PO for £\_\_\_\_\_ (indicate total amount.)

Name \_\_\_\_\_

Address (please print) \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

# Science of Cambridge

PEB

Allow 21 days for delivery.

## WARMING UP

**T**HE QUESTION of C.B. in Britain has been a debating point for many years, recently however the debates have been warming up—not at government level but down here among the people and technical press. Not only has the argument warmed but so have the air waves, with an estimated 18,000 illegal users in the U.K. We hope to be looking in more depth at this use and at what the equipment is, where it's coming from etc. in the near future.

It would appear that whether the government likes it or not C.B. is here and it is highly unlikely that it will ever go away or that the Home Office will ever be able to totally stamp out its use. It is also a fact that because people are prepared to break the law and use such equipment, they are not particularly bothered about power output and possible interference etc. Obviously it is better from a detection viewpoint not to use an easily spotted C.B. aerial on a vehicle and therefore many sets are being used with ordinary car aerials which cause increased interference problems.

"In for a penny, in for a pound", as the saying goes and since it is just as

easy to buy high power linear amplifiers as C.B. gear, these are now being used to boost outputs up to 50' or even 100 watts which, of course, compounds all the problems caused to other, legal systems. Clearly we are fast approaching a situation which is far worse than we might have if C.B. were legalised and legislation drawn up and enforced to control the problems now being caused.

From recent raids on C.B.'ers and the confiscation of the equipment, the Home Office are obviously trying to track down and deal with offenders but can they realistically expect to achieve a C.B. free community? The Home Office recently commented to us that they are endeavouring to control illegal use especially where interference is being caused. They also made the point that the whole area of C.B. use is under review. Presumably our "new" Government will be looking at all the facts.

Of course, C.B. is legal in many continental countries and with the ever increasing flow of commercial and holiday traffic across the channel, not only is it impossible to keep out equipment but it also poses problems for Customs and Excise when a vehicle which has been fitted—quite legally—with C.B.

equipment in say, Germany or Spain comes across the channel. To comply with the law the equipment should be torn out and confiscated before the vehicle is allowed in.

One other interesting fact is that if you look in the "for sale" pages of one well known weekly "classified magazine", you will regularly discover secondhand and sometimes new C.B. equipment being openly advertised for sale. Of course, there is nothing illegal in this. You can own it, even sell it, but you must not use it and, of course, you must not import it.

What does this really mean? Since you must not import C.B. equipment, any that is in the country has been smuggled in and can therefore be confiscated. If it can be proven that any individual has smuggled it in, a fine or worse could be the result and, of course, even if you purchased the gear secondhand it can still be confiscated even if you never use it. If you built it yourself you can keep it, but you must not use it.

What a ridiculous situation! Any further comments anyone—Home Office, Minister of Posts and Telecommunications, readers?

*Mike Kenward*

## EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland PROJECTS EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

*Editorial Offices:*

Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191

**We regret that lengthy technical enquiries cannot be answered over the telephone (see below).**

## ADVERTISEMENT MANAGER

SECRETARY

CLASSIFIED MANAGER

D. W. B. Tilleard

Christine Pocknell

Colin Brown

01-261 6676

01-261 5762

*Advertising Offices:*

King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Telex: 915748 MAGDIV-G

**Make Up/Copy Dept.: 01-261 6601**

### Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

### Back Numbers

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

### Binders

Binders for PE are available from the same address as back numbers at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where ap-

propriate. Orders should state the year and volume required.

### Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Cheques and postal orders should be made payable to IPC Magazines Limited.



# HOME FREEZER ALARM

P. E. CHAPLIN

**M**ANY people now own a deep freezer or fridge-freezer unit and anyone who has suffered a "thaw-out" will never want a repeat of that experience.

If the contents are insured, it is true that the insurance company will pay compensation for the loss, but if the freezer is full of home and local farm produce this cannot be replaced out of season, and considerable inconvenience is felt.

This is where the freezer alarm can help. Although it cannot prevent the possibility of such a catastrophe, it can give some warning of impending disaster!

Thaw-out of the freezer can be caused either by failure of the power supply, or by mechanical failure of the freezer itself. This unit is designed to cope with each of these events.

## ELECTRICAL/MECHANICAL FAILURE

An essential feature of any freezer alarm should be the ability to detect mains failure and still continue to function.

Mains failure could be due to a power cut (in which case it is usually known) or a blown fuse at either the distribution board or in the freezer's own plug. The power can even be accidentally switched off before going on holiday by an over-enthusiastic desire to have everything turned off!

Similarly, it must have the ability to detect a rise in temperature because of a fault in the freezer's own mechanism.

When all is well, the alarm is silent and each l.e.d. remains illuminated, red for mains and green for temperature.

Failure of the mains supply causes the audible alarm to sound intermittently and the red l.e.d. to flash at a set rate. In the same way, increase in temperature will trigger the alarm and cause the green l.e.d. to flash at a different rate from the red (just to make things extra clear in an emergency!)

In addition, a test circuit was added for checking that the temperature sensor and connecting wires have not become open circuit. This was felt necessary owing to the negative temperature characteristics of the temperature sensor.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the alarm is shown in Fig. 1. When the unit is operated from the mains, the voltage at pin 4 of IC1 will be zero; the NE555 will sink current in this condition and l.e.d. D8 will be illuminated.

If the mains fails, the voltage at pin 4 will rise above the threshold value of 0.4V to about 2V via R2, as pin 4 is

isolated from the 0V rail by D6 and the rectifier diodes. When this happens IC1 will be triggered and run in the astable mode, the mark to space ratio being governed by the values of R3, R4 and C2. The duration of high output  $t_1$  is given by:

$$t_1 = 0.693(R3 + R4)C2 \text{ seconds.}$$

and the low output  $t_2$  by:

$$t_2 = 0.693(R4)C2 \text{ seconds.}$$

The frequency of operation is given by:

$$f = \frac{1}{(t_1 + t_2)} \text{ Hz.}$$

In the prototype, the frequency of oscillation was chosen to be about 1Hz.


## TEMPERATURE DETECTION

The temperature detection circuit is a Wheatstone Bridge, one arm formed by R6, VR1 and R7, and the other by R8 and the thermistor TH1 (via JK1).

The operational amplifier (IC3) acts as a comparator across the bridge circuit. A polarity change of a few millivolts across the input of the 741 is sufficient to swing the output from a low to high state or vice versa.

As TH1 cools down, its resistance increases, thus swinging the voltage at pin 2 slightly positive relative to pin 3 for a particular setting of VR1. Further cooling down of TH1 maintains pin 2 positive with respect to pin 3. The output of IC3 will be low in this condition, allowing the NE555 timer (IC4) to sink current, thus l.e.d. D10 will be illuminated.

If the temperature rises above the pre-set level, the voltage at pin 2 will be negative with respect to pin 3 and

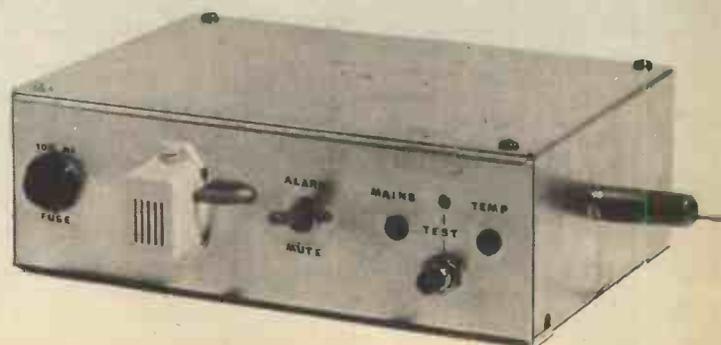

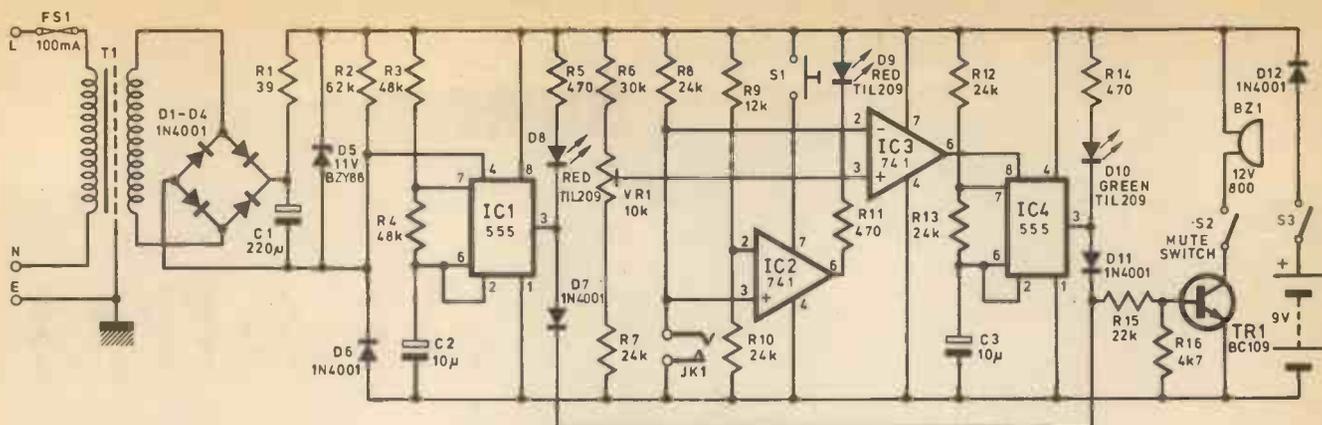


Fig 1. Circuit diagram of the Freezer Alarm.

the output of IC3 will be high, thus energising IC4, causing l.e.d. D10 to flash. In the prototype, the values of R12, R13 and C3 were chosen so that the frequency of operation was twice that of the mains failure circuit.

### TEST CIRCUIT

The test circuit consists of another bridge circuit, one arm common with the temperature sensing circuit comprising R8 and TH1 and the other by R9 and R10. The values of R9 and R10 were chosen to allow for a thermistor at  $-22^{\circ}\text{C}$  at its extreme tolerance limit of +20 per cent of its nominal value. When the test button (S1) is pressed, IC2 is energised and under normal conditions pin 2 will be positive with respect to pin 3. The output of the operational amplifier will be low and sink current, thereby illuminating l.e.d. D9. If, on the other hand, open circuit conditions have occurred, then pin 3 will be positive with respect to pin 2 and the output will be high and the l.e.d. will not be illuminated.

### REMAINDER OF CIRCUIT

Diodes D7 and D11 isolate the outputs of IC1 and IC4 from each other. The voltage at the common ends of the

diodes was found to be about 2V under normal conditions and this was sufficient to make the audible alarm hum. So TR1 was introduced to act as a switch, and R15 and R16 prevent the transistor from switching on until the outputs of IC1 and/or IC4 goes high. D12 in effect isolates the battery from the rail, and prevents current drain into the battery.

The output voltage of the power supply unit is not too critical provided it is greater than the no load potential of the battery plus the voltage drop across D6. Therefore the unit was designed for 11V output. The value of C1 should be kept to about 220µF—otherwise a time delay in excess of 10 seconds will occur between mains failure and the flashing of the l.e.d. D8. This is important if the power supply is inadvertently turned off, and the unit is near the switch board.

## COMPONENTS . . .

### Resistors

R1	39
R2	62k
R3, R4	48k (2 off)
R5, R11, R14	470 (3 off)
R6	30k
R7, R8, R10,	24k (5 off)
R12, R13	
R9	12k
R15	22k
R16	4k7

All resistors  $\frac{1}{2}\text{W}$  0.5% except where stated

### Capacitors


C1	220µ 16V
C2, C3	10µ 16V (2 off)

### Semiconductors

TH1	VA1066S rod thermistor
D1-D4, D6, D7,	1N4001 (8 off)
D11, D12	
D5	BZY88 11V Zener
D8, D9, D10	TIL 209 l.e.d. (3 off)
TR1	BC109
IC1, IC4	NE555 (2 off)
IC2, IC3	741 op amp (2 off)

### Miscellaneous

BZ1	Buzzer 12V 800Ω (Maplin)
T1	12V mains transformer
S1	push button
S2	S.p.s.t.
S3	Min slide switch
FS1	100mA fuse and holder
JK1	3.5 mm jack socket

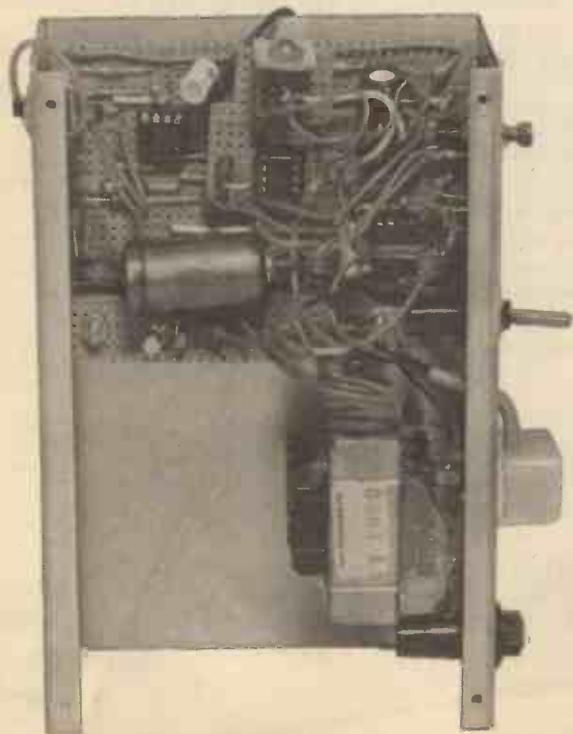

Internal view of the Freezer Alarm

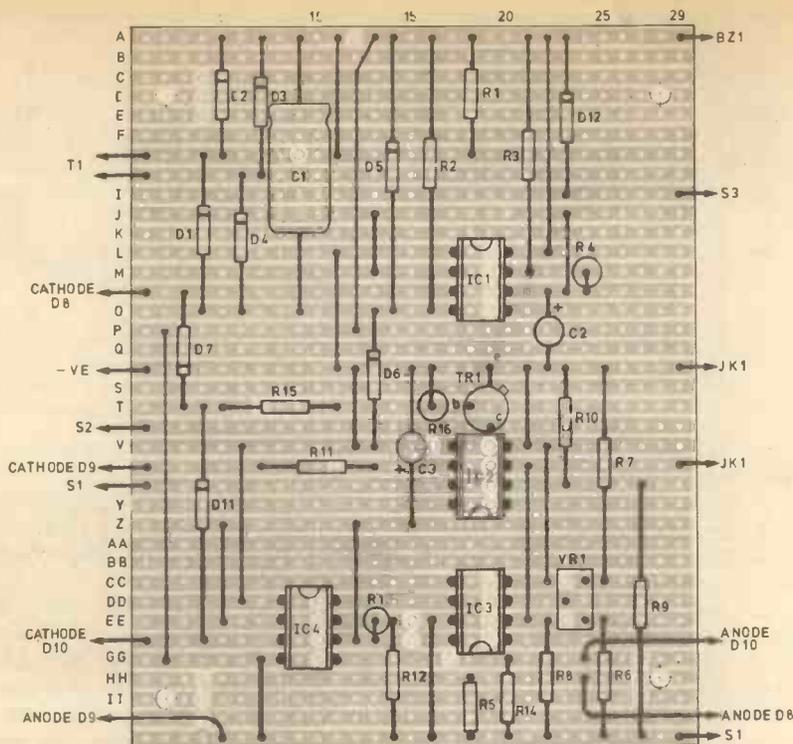


Fig 2. Veroboard layout

A battery switch was added so that the unit could be turned off during de-frosting.

### CONSTRUCTION

The circuit was assembled on a piece of 0.1in matrix Veroboard and a suggested layout is shown in Fig. 2. The board and mains transformer were mounted in a pressed aluminium box measuring 150 x 100 x 50mm deep. The circuit board was spaced off the floor of the box on plastic collars. They were made by cutting the barrel of a ball point pen into 6mm lengths.

The internal layout of the aluminium box and front panel were arranged to be suitable for sitting on top of an upright freezer. Constructors with chest freezers may wish to devise their own internal layouts, for example to make the unit suitable for wall-mounting. The layout was detailed so that no wires were attached to the lid of the box, thus making battery replacement simple.

Two wire links are required which are not shown on the Veroboard layout: BZ1 to S2 and S3 to +9V.

### THERMISTOR PROBE ASSEMBLY

The thermistor was mounted on a small piece of Veroboard and thin wires were anchored and soldered to the board. The board and thermistor were then covered with Araldite.

Providing the wires are thin enough, they can pass between the freezer cabinet and door or lid without causing any problems. Connection to the unit was by a 3.5mm jack plug and socket.

When finished, it is advisable to measure the resistance of the probe to ensure that there are no short circuits, and to see that the resistance changes with temperature.

### SETTING UP

The freezer should be maintained at a temperature of -18°C or less. The unit was designed to trigger at about -10°C, thus giving some margin before setting off the alarm. The higher the trigger temperature, the less warning time is available.

The ice box of the refrigerator was used for setting up the unit. The probe and a freezer thermometer were positioned in the ice box, and the thermostat of the refrigerator was gradually lowered until the thermometer read the desired temperature. VR1 is adjusted so that the unit is just triggered.

Finally, it is advisable to plug the alarm unit into the same socket as the freezer! ★

## A Compendium of Electronic Erudition

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At £2.85 inc. VAT and postage (£3.45 overseas) they are obtainable from:

Post Sales Department, IPC Magazines Ltd.  
Lavington House, 25 Lavington Street  
London SE1 0PF

I enclose P.O./cheque value ..... for ..... binders at £2.85 each (£3.45 overseas) for Practical Electronics Vol. No's .....

Name .....

Address .....

Date .....

**PE**




frequency is reached governed by the value of C3 and associated circuitry. Turning the wiper of VR1 to C4 decreases the feedback applied by C3, and increases the feedback via TR1 and C4. Because the output of the i.c. is out of phase with the input at low frequencies, taking the signal from the collector of TR1 and applying that to the input provides positive feedback at low frequencies. C4 determines the low frequency limit. Referring back to Fig. 1, R5 is in series with C4 to keep the mark/space ratio of the oscillations fairly even at low frequencies. C5 and R6 apply more feedback from TR1 through VR2, thus reducing the frequency of oscillations still further.

The components are mounted on a piece of Veroboard 75mm x 30mm (Fig. 3). The potentiometers should be put on last of all. The type used on the prototype were Radiohm, and it was found necessary to enlarge the holes for the pots with a 1.2mm drill. Care should be taken when soldering to prevent accidental shorts, and excessive flux between tracks should be cleaned off. The author finds an old toothbrush and white spirit very effective.

Keep the component leads as short as possible to avoid stray r.f.

Fig. 2. Showing simplified feedback paths

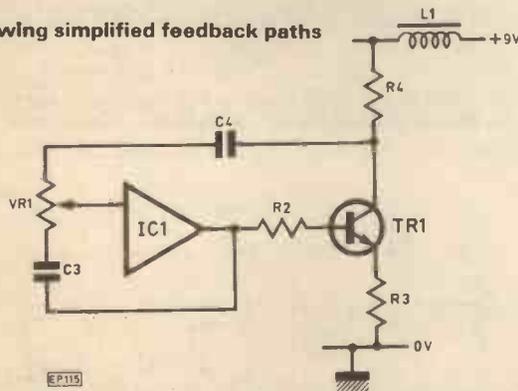

If the Veroboard layout is changed, and the pots mounted off the board, there may be trouble with stray capacitance. The board, BNC output socket and switch should be mounted in an all metal box for screening. For the prototype a 40 x 100 x 70mm aluminium box was used, with the pots mounted on the lid. These were considered sufficient support for the board.

There is plenty of room for the 9V battery. In fact, if the unit were to be used for long periods, two batteries could be utilised, with a double pole on/off switch.

The board should be checked over for errors. Then, if all is in order, the signal generator should be connected up to an oscilloscope and frequency meter if available. Check that there is about 4V across pin 2 and 0V; the total current consumption should be about 3mA. The frequency controls are adjusted so that they work in series. For example, for a frequency of 25kHz or less, VR1 is turned to 25kHz, and VR2 to the required frequency. For over 25kHz, VR2 is turned to 25kHz and VR1 to the required frequency. The output voltage should be 2.5V peak-to-peak, measured at 1kHz. The unit should produce a good square wave up to 25kHz.

Calibration should ideally be done with a frequency meter, but if one is not available compare the signal generator frequency to that of a known one. Alternatively, for r.f. calibration a wire from the output thrown over a radio can be used.


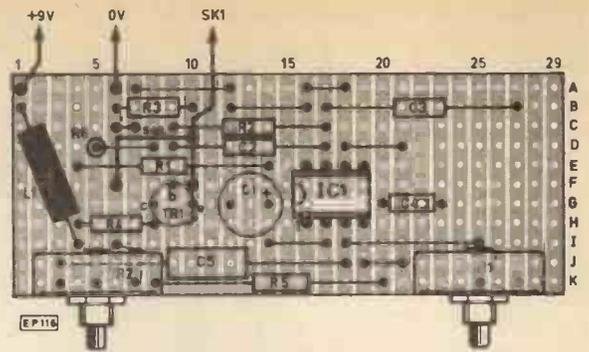


Fig. 3. Board layout

The radio is tuned into the signal generator's frequency, and the reading taken off the radio tuner.

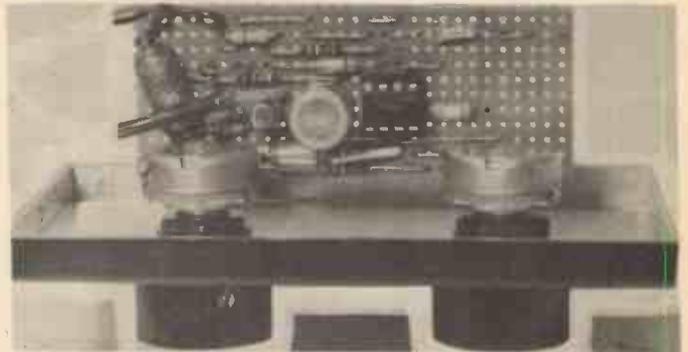When using the unit, loading should be kept to a minimum of 10kΩ, as the frequency does vary with load. It also varies with supply voltage, and this could be largely overcome by using a Zener regulated supply, at the cost of greater current consumption.



#### Resistors

R1	2k2
R2, R5, R6	100k (3 off)
R3	1k
R4	3k3
All 1/4W 5% carbon	

#### Capacitors

C1	100μ 16V elect
C2, C4	100p
C3	47p
C5	2n2

#### Semiconductors

IC1	ZN459
TR1	BC108

#### Potentiometers

VR1, VR2	1M (2 off)
----------	------------


#### Inductors

L1	150μH
----	-------
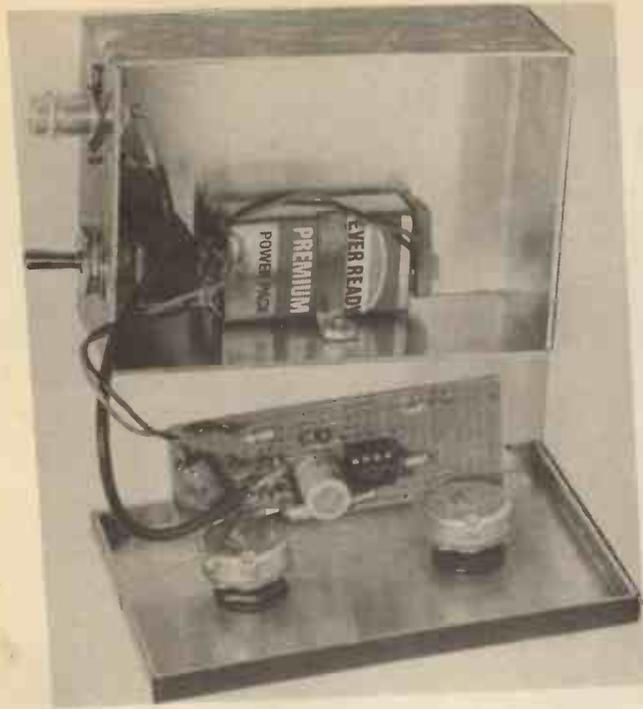
#### Miscellaneous

BNC output socket, on/off switch, metal case, 9V battery, battery connector, holder for 8 pin i.c. (if required), Veroboard 0.1 in matrix, knobs (2)

Should an output voltage control be required, R3 could be replaced by a 1k $\Omega$  pot with the wiper going to the output socket.



Although the prototype oscillated up to 7.5MHz, it was only calibrated up to 3MHz, because of the cramping of frequency above this. With a little thought, a fine tuning control could be connected around VR1 to make these frequencies available.

The harmonics generated by the unit go well past 100MHz, making it suitable for f.m. radio and TV work.

When using the unit at r.f. frequencies, it should be earthed, and for direct coupling into a radio, for example, a small capacitor should be connected in the output.

Although this unit is by no means a precision generator, for its size and cost to build, it should prove to be a useful tool in the field or at the workbench. ★



## New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

## New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself — computers, oscilloscopes, transceivers etc. . . . Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451).

Registered in England, No. 606177.

Soldering Iron offer FREE



## New Heathkit CI 1265 Digital Tach/Speedometer.

Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.



To: Heath (Gloucester) Limited, Dept PE 8/79 Bristol Road, Gloucester, GL2 6EE.  
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.   
Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

When you receive your catalogue you will get details of this free offer.



# HEATHKIT

HEATH  
Schlumberger

# COMPUKIT UK 101 SINGLE BOARD COMPUTER

A.A. BERK B.Sc. Ph.D.

- \* 8K Microsoft, full feature, BASIC
- \* Fully expandable via on board sockets
- \* Up to 8K RAM on board
- \* Cassette interface (CUTS)
- \* VDU—with its own dedicated RAM (1K)
- \* Full ASCII keyboard
- \* UHF modulator on board
- \* PSU on board—transformer included in kit
- \* Full machine code monitor and I/O utilities in ROM
- \* Upper/lower case—graphics and gaming characters

**T**HE COMPUKIT UK-101 has been prepared to provide all sectors, from the amateur constructor/hobbyist to the engineer, programmer, teacher, business man and scientist, with the cheapest computer on the market which is programmable using an 8K BASIC package. In addition, it is fully expandable, capable of being programmed in machine code, and absolutely complete from mains input to TV Aerial feed output. It includes full typewriter-style keyboard, printer, and cassette-storage interface. The BASIC package employed is the industry standard Microsoft interpreter, and will run much of the available software for many other more expensive machines on the market with little modification. Floating-point calculations in this BASIC are extremely fast and versatile, making scientific calculation projects of the most complex kind perfectly feasible in one's own home. The areas of suitable use for the COMPUKIT stretch fully across the board.

The business man will find that the string handling facilities and excellent video display of the COMPUKIT make the machine perfectly fitted for everything from general accounts and planning calculations, to formatting of invoices and stationery to be printed out on hard copy when complete.

The Statistician will find that the high speed of calculation with facilities such as random number generation and user-defined functions, enable analyses of data and simulation of models to be performed particularly easily. The results may then be displayed with the graphics available in almost any form from bar-charts to tree-diagrams!

The Engineer wishing to control equipment with a computer, will benefit from being able to write the necessary routines in BASIC (making the software easy to design) while being able to jump to fast and efficient machine-code routines for servicing external hardware.

Perhaps most importantly; for the first time, anyone, technical or otherwise, can have an affordable easily programmable home-computer for domestic use—a much neglected area at the moment, but one which is about to take off.

Imagine being able to run a program to help your child (or yourself) revise for exams. Animated diagrams are possible, such as an internal combustion engine shown reciprocating, with mathematical equations to match. Picture an *automobile* program designed to accept daily input from you on petrol and oil use, along with mileage, etc. The machine could accumulate information, and at any time give you the average m.p.g., plot performance versus time or some other parameter, and remind you when to check the tyres and drive to the Garage for a service.

- ★ Based on the popular 6502 micro
- ★ Supports all Ohio Scientific expansions including floppy disc
- ★ Fast resident BASIC
- ★ Total of 19K addressable memory on p.c.b.
- ★ Memory mapped VDU. Line width selectable from 16 to 49 characters by 16 lines

## IMPROVEMENT

This computer is based on the Ohio Scientific Superboard (reviewed PE June 79), which only displayed 23 characters per line on a normal TV, and produced the USA standard 60Hz frame frequency unsuited to UK TVs. These and other disadvantages have been rectified in the COMPUKIT UK-101. For example, the keyboard has been altered to show certain missing characters on the Superboard, and the BREAK key is less prone to accidental operation.

This month, the COMPUKIT hardware is briefly described in block diagrammatic form, along with some technical details of the 6502 Microprocessor. A section on the specifications of the BASIC package is included, for which the reader will require some previous knowledge of BASIC—a library book would be useful at this point for those just beginning in the world of programming.

A BASIC primer article is to be published in this magazine very soon and will help with an understanding of this very popular microcomputer language.

## HARDWARE

Based around the 6502 MPU and a set of binary counters as clocks, the COMPUKIT has been designed and set out to be as flexible and easily modified as possible while making no compromises for those who will only use the machine as it stands.

The 6502 is a reasonably typical 8-bit microprocessor with a 16-bit address bus and 8-bit data bus (see Fig. 1) and the control lines are similar to the 6800. There are two interrupt lines: IRQ and NMI. When forced low, the latter will interrupt execution at the end of the current instruction cycle and branch to a routine whose address (vector) is stored in two bytes at the top of memory. IRQ is similar but may be rendered inoperative by setting (to "1") the MASK flag of the P-register. RES is a reset line whose vector is also stored at the top of memory.

There are five more control lines which have the following effects. R/W informs the system as to whether a READ or WRITE operation is being performed. SYNC is used to identify an Op-Code fetch cycle. RDY is used to halt the processor for DMA or slow memory, etc. S.O. is a line which may be used to set the Overflow bit in the P-Register.  $\emptyset 1$  out and  $\emptyset 2$  out are system clock lines.

Other pins on the MPU's 40-pin package are used for Data, Address and Power Supply (+5V).

The register set of the 6502 is smaller than that of the 6800 and Z80 as only one primary accumulator is included and there are no 16-bit data or index registers available to the user. This is partly made up for by an enhanced set of addressing modes which use pairs of memory locations to hold addresses. However, there are no 16-bit Load, Store or Compare instructions to manipulate these pairs directly and all such operations must be constructed from 8-bit arithmetic operations.

**WARNING: Computing is highly addictive.**



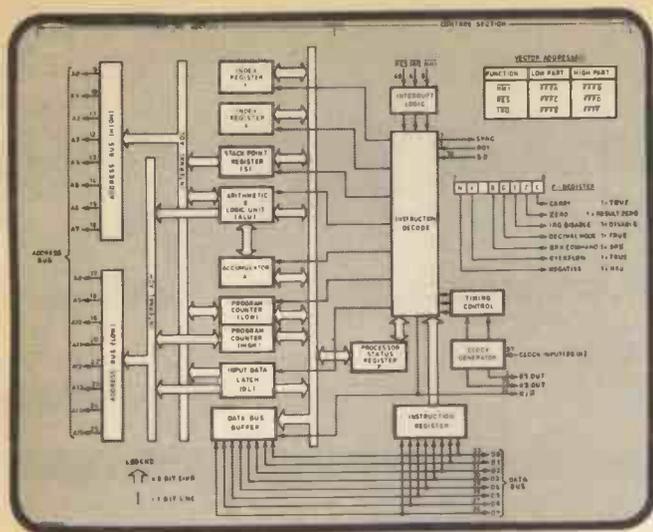


Fig. 1. 6502 internal architecture

The Stack is implemented in Page One (the second 256 bytes of memory), as the Stack pointer is only of 8-bit length—a ninth bit exists but is permanently set to "1".

Page Zero (the first 256 bytes of memory) is very heavily used by the 6502 instruction set as its two Index registers are both 8-bits in length. However, as referred to above, indirect addressing exists whereby an instruction may take its effective address for execution from a pair of bytes, stored anywhere in memory. Various Offset modes exist using the index registers. In this way, pairs of memory locations act as 16-bit registers; but, again, they are not able to be manipulated with 16-bit instructions. Try writing a program to clear a block of memory greater than 256 bytes in length and you'll see what I mean!

If you have worked on the Z80 or 6800 you will find certain aspects of the 6502 code most frustrating while others you will discover to be something of a breakthrough. Readers who are used to the SC/MP or 1802 instruction set will probably be most surprised at the difference when working on such an advanced machine.

The speed of processing is similar to the Z80 and 6800 and all three exist in various speed options. One interesting point is the 6502's "rise to power" as probably the most widely used Micro on the market. APPLE, PET and KIM all use the 6502 and there are several other 6502-based systems in the pipeline, all of which implies that the software backup for the 6502 is very wide and increasing in size.

## SYSTEM DESCRIPTION

The Block Diagram, Fig. 2, shows the main parts of the COMPUKIT in a condensed form. The heart of the system is a set of binary clocks fed from an 8MHz crystal controlled clock generator. The clocks are not only used for the MPU but form the main control for the VDU, which is continually polling the VDU RAM for information to be displayed at exactly the right time on the screen. Those familiar with the PE VDU (*P.E. Oct.-Dec., 1978*) will note that the clocks perform most of the functions associated with the Thompson CSF Cathode Ray Tube Controller chip.

The most dominant block on the diagram, is in fact the VDU—a fairly typical memory mapped system run from the binary counters. The screen of information to be presented is stored in the VDU RAM in a binary-coded form (ASCII) for the 128 ASCII characters, and extended to include codes for the various graphic characters (128 in all) available on the COMPUKIT.

Address bits are sent to the VDU RAM from the binary counters in sequence starting at the location to be displayed at top left of the screen. As the counters ripple through all the addresses, the full screen of (theoretically) 1024 characters is accessed and the data at each location passed on to the character generator which interprets it as video dots to be displayed on the TV. Each character occupies 16 TV lines (in pairs to form eight vertically arranged dots) and the binary counters supply the necessary counting information along the character generator row-address lines.

When the MPU wishes to interrupt this process and access the VDU RAM, it switches the Address Switches and tri-state buffers over to the MPU Buses.


In order to display the information from the character generator on a TV, it must be serialised by the Parallel In Serial Out (PISO) device, mixed with Frame and Line synchronisation pulses, converted from TTL levels and fed to the UHF modulator. The output may then be plugged directly into a TV aerial socket and the TV tuned to around Channel 36.

The Sync. pulses for the TV are generated by a set of monostables from the main binary counter chain and the design includes a display-blanking stage to prevent MPU access to the VDU from causing excessive "noise" on the screen. This allows fast real-time updating of the video information without upsetting the display.

The VDU Dot clock on the COMPUKIT oscillates at 8MHz, which is fast enough to display about 48 characters per line on a normal TV. 768 characters are thus displayed on the 16 lines. The rest of the 1024 remain "hidden" off the screen but are perfectly valid Read/Write memory locations. This number of characters keeps the bandwidth down to a value acceptable by the I.F. stages of all domestic sets, and straight video need never be used due to the resulting excellence of definition in the characters displayed by the COMPUKIT.


The "hidden" characters of the VDU are never used by the BASIC interpreter, of course, as the software is carefully modified to use just the 49 characters per line which appear. The number of characters thus used per line is also selectable by the user for those TVs which will only comfortably display 48 or less characters across their screens.

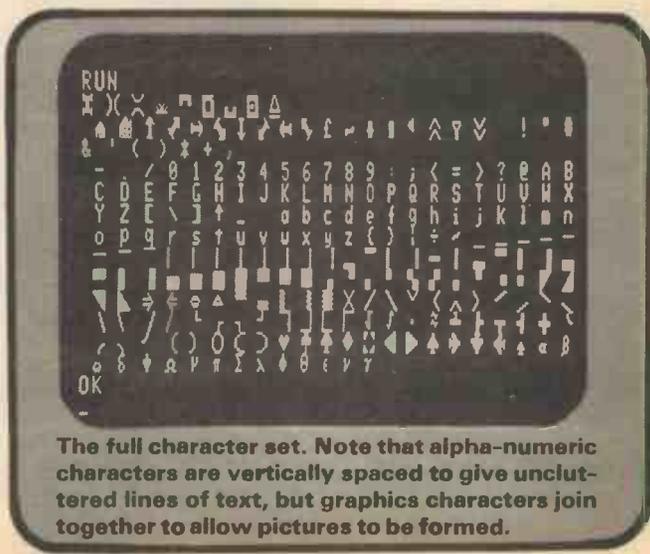The other sections of the COMPUKIT are shown connected to the Address and Data buses as well as to Address Decoding logic which selects each block as its address comes up on the Address Bus. The various control lines are omitted for simplicity.



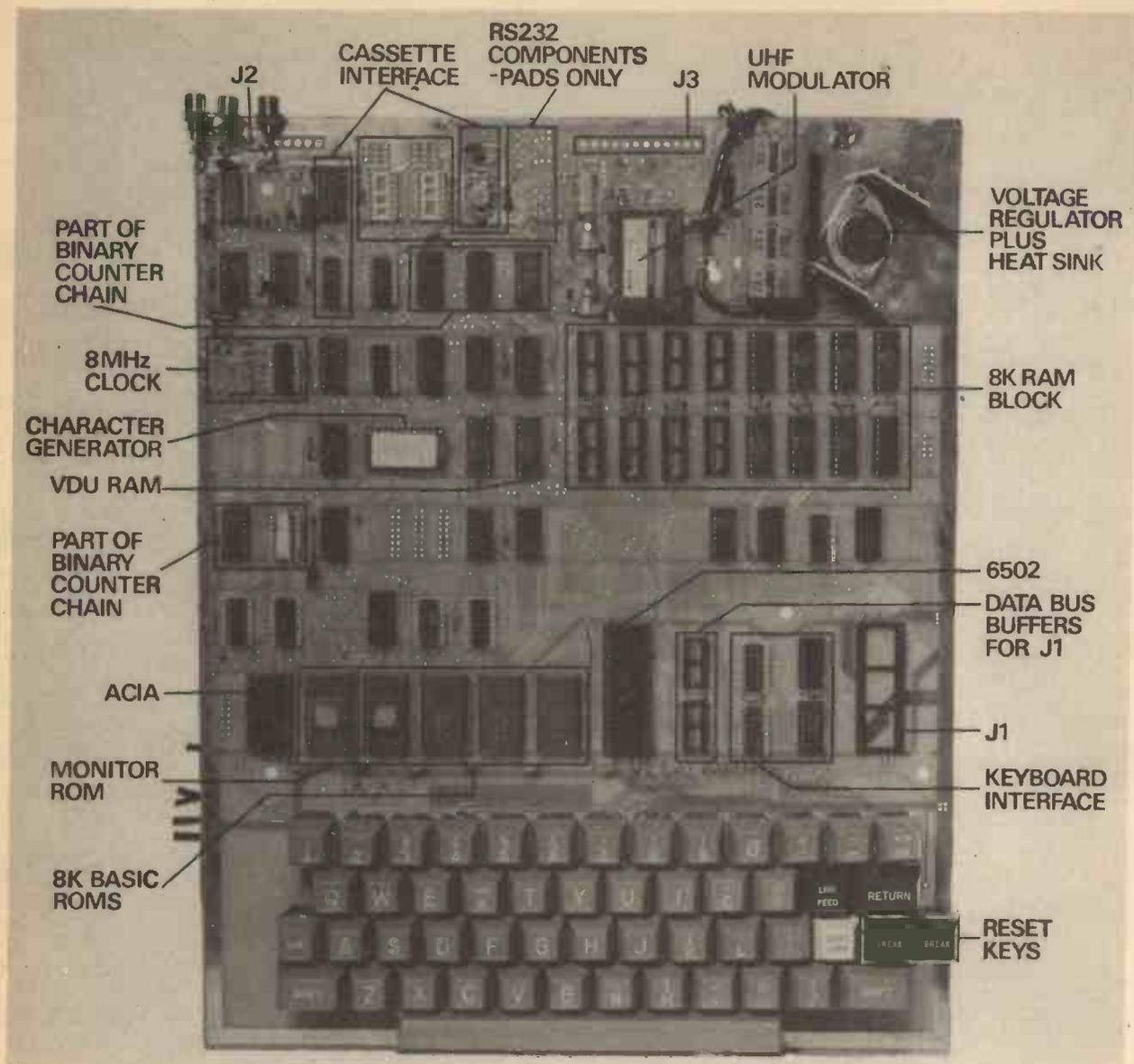The full character set. Note that alpha-numeric characters are vertically spaced to give uncluttered lines of text, but graphics characters join together to allow pictures to be formed.





**The COMPUKIT UK-101 board. A transformer is supplied but does not mount on the p.c.b.**

**(Note that this is the prototype board)**

The Bus lines are controlled and operated by the 6502 MPU which derives its instructions from the ROM and RAM blocks which take up between them 18K of memory. 2K of this is a Monitor (operating system) with BASIC support, keyboard handling, machine-code monitor, floppy-disc bootstrap, etc. 8K is the BASIC interpreter and 8K is for the RAM block, of which around  $\frac{3}{4}$ K bytes are used as a scratchpad by the various ROM-based programs.

Another important block is the Asynchronous Serial Communications section—including the cassette interface. This is driven by an ACIA (Asynchronous Communications Interface Adapter—the 6850 chip). The clocking comes, of course, from the binary counter chain and may be fed from higher up the chain to effect faster transfer speeds than the 300 BAUD for which the system is set up. In addition, there is provision, on board, for a RS232 interface run by the

same software as the Cassette. This allows connection of the system to any standard serial device from teletypes to modems and extra VDUs.

The keyboard section is also shown connected to the Data Bus and Address decoding, and this is run by software scanning for speed and efficiency. The software scans the keyboard for a key-closure and identifies the character being accessed from ROM.

Finally, and of great importance, is an expansion socket (40-pin d.i.l.) for the Address, Data and Control lines to allow expansion to a separate Motherboard. This could easily be extended to the S100 Bus, but is plug-compatible with the Ohio Scientific OSI-48 Bus and Floppy-Disc interface. Anyone wishing to use the COMPUKIT for control purposes will find the expandability via this socket of great assistance.

The 5V Power Supply Unit (PSU) gives 3 amps.

# COMPONENTS . . .

## Resistors

R1-R12, R68, R80, R81	4k7 (15 off)
R33	6k8
R34, R50	15k (2 off)
R37, R55, R63, R64	10k (4 off)
R35	560
R36, R60, R61, R65	470 (4 off)
R51, R74	270 (2 off)
R52, R54, R59, R72, R82	1k (5 off)
R53	22k
R56	100k
R58	560
R62	100
R67	27k

All  $\frac{1}{4}$ W 5% carbon film

## Capacitors

C6	150p ceramic
C7, C12, C55	1n mylar (3 off)
C8	100n mylar
C9	68p ceramic
C10, C13	10n mylar (2 off)
C11	1 $\mu$ mylar
C48	220n ceramic
C57	27p ceramic
C58	47 $\mu$ electrolytic
C59	3,300 $\mu$ electrolytic
C60	100p ceramic
remainder	100n disc ceramic (31 off) (These are all supply decoupling capacitors)

## Diodes

D1-D10	1N914 (10 off)
D15	1N4001
D17, D18	Any 3A rectifier diode (2 off) (1N5401 will do)

## Integrated Circuits

IC1	Any 5V, 3A TO3 type regulator
IC2, IC3	74LS75 (2 off)
IC4, IC5	74LS125 (2 off)
IC6, IC7	8T28 (used only for expansion)


IC8	6502 microprocessor
IC9-IC12	ROMs for BASIC (4 off)
IC13	ROM for monitor
IC14	6850
IC15	7402
IC16, IC18, IC21, IC62	7404 (4 off)
IC17	74LS139
IC19	74LS20
IC20, IC22, IC23	74LS138 (3 off)
IC24, IC25	8T28 (2 off)
IC28, IC65, IC69	74LS123 (3 off)
IC29	7493
IC30, IC59-IC61	74163 or 74161 (4 off)
IC31-IC40, IC45-IC52	2114 (18 off)
IC41	00000 Character Generator
IC42	74165
IC53-IC55	74LS157 (3 off)
IC56	7420
IC57	74163
IC58	7400
IC63	7474
IC64	7476
IC66	CA3130
IC70	7403

## Miscellaneous

### d.i.l. sockets

40-pin	2 off
24-pin	7 off
18-pin	18 off
16-pin	21 off
14-pin	13 off
8-pin	1 off
FS1	3 Amp fuse plus holder
X1	8MHz crystal
UHF modulator	Astec 8MHz bandwidth
Double-sided plated-through p.c.b.	
Set of keyboard switches and key tops	
Regulator heatsink plus fixing screws	
Transformer—240V/50HZ : 9-0-9V 3A	

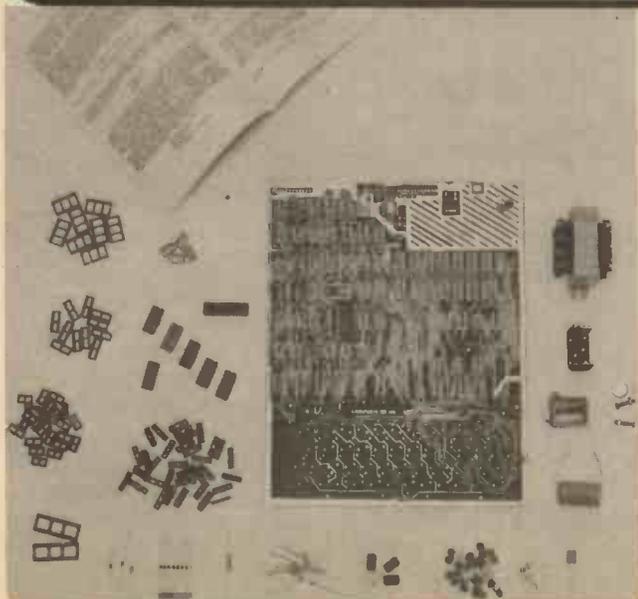Please note that component numbers do not run contiguously



## CONSTRUCTORS' NOTE

The *Compukit UK-101* is being produced by **Comp Components** (see advertisers' index), for £219 + VAT. This will include a full power supply on-board (including power transformer), and a UHF modulator. The graphic character set also includes such symbols as £ and  $\pi$ .

The p.c.b. is of a professional standard with plated-through holes and silk-screened component legends, and a full set of i.c. sockets is included in the kit price as is—with 4K of user RAM (a further 4K may be purchased to upgrade the board to its full capacity).

The *Compukit* comes with full manual (written by the author), but the beginner would be advised to obtain a book on BASIC, and perhaps even on 6502 machine code programming, as the *Compukit* manual is not intended to be a primer on either subject.

The computer is available for demonstration at **Comp Components**.

## SOFTWARE

The machine accepts its instructions in the programming language called BASIC as well as 6502 machine-code. It is the use of BASIC which will be paramount and its specifications are given below.

There are many versions of BASIC (Beginner's All Purpose Instruction Code) for many different machines. There are Tiny BASICS, Integer BASICS, Double Precision BASICS, etc., etc. Minis and Main Frames usually offer a version of BASIC in Compiler form which includes all the Scientific and other functions plus the ability to manipulate matrices and Disc files. Few if any of these versions, however, allow direct manipulation of memory locations within the computer when programming or debugging. Access to machine-code routines is also a rather complex operation and use of the machine to control even such simple things as a bank of lights is usually impossible. It was not until the advent of the MPU-based computer with its feet firmly embedded in memory address decoding, machine-code programming and control applications that such interplay became common. BASIC has become the high-level language of the micro-computer, and interpreters rather than compilers are the normal implementation method. The interpreter's ease of use made it the order of the day and Microsoft's BASIC interpreter was born. This is a very powerful package and exists in many versions of which the COMPUKIT's is one of the very fastest.

It is quite different from the 1K and 2K BASICS with their incredibly restricted instruction sets. The COMPUKIT's version, as its name implies, occupies 8K (8192) bytes of the machine's memory and is stored in Read Only Memory (ROM). This type of memory has two advantages:

- (1) The BASIC interpreter is not lost when the machine is switched off—indeed it is almost impossible to lose it short of crushing the chips in a vice.
- (2) The language is available instantly upon switch-on and does not need to be loaded from some external medium into the machine's memory.

Other methods of offering BASIC include storage on disc. The COMPUKIT can be expanded (by a direct plug-in option) to run the Ohio Scientific's Disc System which comes complete with a powerful disc BASIC, as well as 24K of extra memory to run it in.

Despite the fact that the resident BASIC (in ROM) is at the top end of the scale for speed and sophistication, this does not mean that it is difficult to program. On the contrary, BASIC's use has blossomed for one paramount reason—it is sophisticated enough to satisfy the most technical user in industry, business and research while being remarkably easy even for total beginners to learn and use. The reader will recognise that most of the language is written in a kind of formalised logical English.

## SUMMARY OF BASIC SPECIFICATIONS

There are three modes of use of BASIC on the COMPUKIT:

- (a) Command mode
- (b) Immediate-mode execution
- (c) File-mode execution

The computer is said to be in the Command Mode whenever the message:

**OK**

appears. This is usually after a system Reset following initial power-up, or at the end of a program. The "—" is a cursor which moves around the VDU screen and keeps the user updated as to his/her position. In this mode, the following commands are allowed:

Software has unexplored dimensions awaiting the adventurous, and sophisticated games are possible which can be as much fun to devise as to play.



CONT (short for CONTINUE), LIST, NEW, NULL, RUN, SAVE, LOAD. These include editing, running programs, continuing after a Breakpoint and Cassette handling. Most of these commands may also form statements within a program.

Immediate mode of execution is similar to Command mode but involves normal BASIC statements which may be ganged together to form complete programs executed when the RETURN key is pressed. In this mode, for instance, the machine is available as a super calculator with Scientific calculations of great complexity able to be executed *immediately*.

To file program statements *for later execution*, and to build up complete programs, statements are given line numbers to distinguish them uniquely and place them in instruction sequence in the computer's memory. The finished program may be started by using the command RUN and this is termed File-mode execution.

## STATEMENTS AVAILABLE

CLEAR	LET
DATA	ON ... GOTO
DEFFN	ON ... GOSUB
DIM	GOSUB ... RETURN
END	PRINT
FOR ... NEXT	READ
GOTO	REM
IF ... THEN	RESTORE
IF ... GOTO	STOP
INPUT	WAIT

## RELATIONS, OPERATION AND FUNCTIONS

-	SUBTRACT (OR NEGATION)	NOT	} Boolean operations from which complex logical functions may be constructed, e.g. IF ... THEN
+	ADD	AND	
•	MULTIPLY	OR	
/	DIVIDE		
↑	RAISE TO THE POWER OF		
>	GREATER THAN	>=	EQUAL TO OR GREATER THAN
<	LESS THAN	<=	EQUAL TO OR LESS THAN
<> (OR ><)	NOT EQUAL TO	=	EQUAL TO

ABS (X)	SGN (X)
EXP (X)	SIN (X)
FRE (X)	COS (X)
INT (X)	TAN (X)
LOG (X)	ATN (X)
PEEK (I)	SPC (I)
POKE (I, J)	SQR (X)
POS (I)	TAB (I)
RND (X)	USR (X)

The variables I and J denote integers and X denotes any number. This is a collection of scientific and other functions which includes calculation of the number of bytes left free for program storage, manipulations of address locations directly, and calls to machine code subroutines.

## STRING FUNCTIONS

ASC (X\$)	MID\$ (X\$, I, J)
CHR\$ (I)	RIGHT\$ (X\$, I)
FRE (X\$)	STR\$ (X)
LEFT\$ (X\$, I)	VAL (X\$)
LEN (X\$)	

These functions allow a string of alphanumeric and graphic characters to be stored, manipulated, sorted, etc. to a very sophisticated degree. A numeric string may, for example, be converted to its numeric equivalent and back again. The use of all these BASIC statements will be clearly explained in subsequent issues of PE, for the benefit of the beginner.

## VARIABLES, TYPES, ACCURACY

Numeric variable names may be any alphanumeric string starting with a letter and containing no special BASIC words. Only the first two characters define the variable. The number of variable names thus available is of the order of 900. String variables are similar but their names must end with a \$. For example A1 is numeric and A1\$ is a string. Numeric and string arrays are also allowed, and increase the already large number of variables available by a considerable factor.

An accuracy of  $6\frac{1}{2}$  digits is used for Scientific calculations, and numbers from  $10^{-38}$  to  $10^{+38}$  are allowed. The computer automatically shifts into exponent form (Scientific representation) as necessary. String variables are from 0 to 255 characters in length. Both string and numeric arrays of several dimensions are allowed.

## ABBREVIATIONS AND SPECIAL CHARACTERS

The character ? may be used instead of the word PRINT, and LET and END are optional, as is the variable in a NEXT statement under certain conditions. Spaces are irrelevant to the BASIC and colons may be used to separate statements on the same program line.

The above features allow fast programming with improved use of memory space, in addition, errors in typing may be deleted by use of the DEL key.

This completes the general overview of the system, and next month the details are given in full. Some details of programming in BASIC will be given and will be selected to "tie in" with the introduction to BASIC to be published in P.E. in the near future. 6502 machine-code is of a more specialised nature and the reader is well advised to buy a good primer on this subject along with a technical description of the 6502 if it is intended to use the machine at this level. Those with any expertise in machine-code programming on another machine will find that learning the 6502 code is quite simple however, and a 6502 data sheet will probably suffice.

## HARDWARE AND SOFTWARE INGENUITY

In this series of articles, applications for the UK 101 will be suggested, and it is hoped that software houses will be interested in providing cassette packages for as many uses as can be dreamed up.

The hardware will also be described in such detail as to allow maximum freedom to modify or add to the basic design, and readers are welcomed to let us know of any software/hardware accomplishments or suggestions they may have.

## KEYBOARD HARDWARE

The photograph shows the positioning of the keys on the keyboard; while Fig. 3 shows the arrangement of the keyboard switches and interface logic.

The keyboard looks like a matrix of 8 rows and 8 columns to the computer; the Rows being one *Write-Only* memory location, and Columns being *Read-Only*. These two occupy the same memory location (DFOO in HEX) and the computer distinguishes between Rows and Columns by writing to or reading from DFOO.

The MPUs R/W line is used to control WKB and RKB accordingly by some logic to be described next month.

Essentially, the software is designed to send a "walking bit" to RO-R7. Thus, the RO line is set to a "1", then back to "0", followed by the same on the R1 line, and so on, up to R7 and back to RO again. The "1" scans along the Rows waiting for a key closure to transmit it to a Column (one of the C0 to C7 lines). If character A on the keyboard is pressed, the contact time must be long enough for the "1" to reach R1 (a very short time at worst). The A key then transmits it to C6, and the Computer receives and processes an A character. The fact that the walking 1 was being sent to R1 and immediately received along C6 makes the A key unique. RO is used to decode the control keys at the same time; thus, if RO and C1 followed immediately by R1 and C6 is decoded, the computer receives a SHIFT A character. The encoding for the keyboard is thus stored in the Monitor ROM.

When the computer has written to a Row, the Data Bus switches to *Reading* from the Columns. Normally, therefore, the Row information would thus be lost and the 1 would never reach any of the Columns. Hence the reason for the latches IC2 and IC3 which store the walking bit long enough to be read from the Columns as necessary. The diodes on IC2 and IC3's O/Ps protect against multiple key closures shorting two or more O/Ps together. IC4 and IC5 are tri-state buffers which ensure that the keyboard information is presented to the Data Bus only when the computer is reading the Columns, otherwise the keyboard would present its information at a time when the Bus was being used elsewhere, thus causing an electrical conflict. Pull-up resistors are included on the inputs of IC4 and IC5, as C0-C7 are open circuit most of the time.

The keyboard decoding is thus dependent upon a particular program in the Operating System, and whenever that routine is inoperative, for instance while certain parts of a user's program are under way, the keyboard is unusable. However, the INPUT statement in BASIC allows the operator to input data via the keyboard during a program. In addition, the address of the keyboard routine itself is available for use via the USR function within a BASIC program.

The only two keys not mentioned in the diagram are the two BREAK (or RESET) keys. These connect directly to the RESET line of the MPU and must *both* be pressed to reset. This prevents accidental breaking in most circumstances.


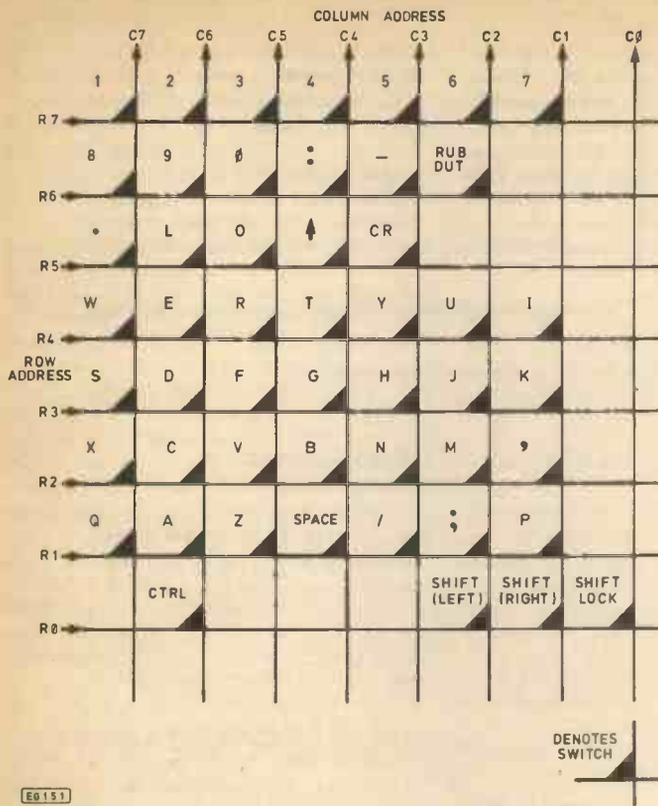


Fig. 3. Above: Keyboard switching matrix  
Below: Keyboard interface circuit

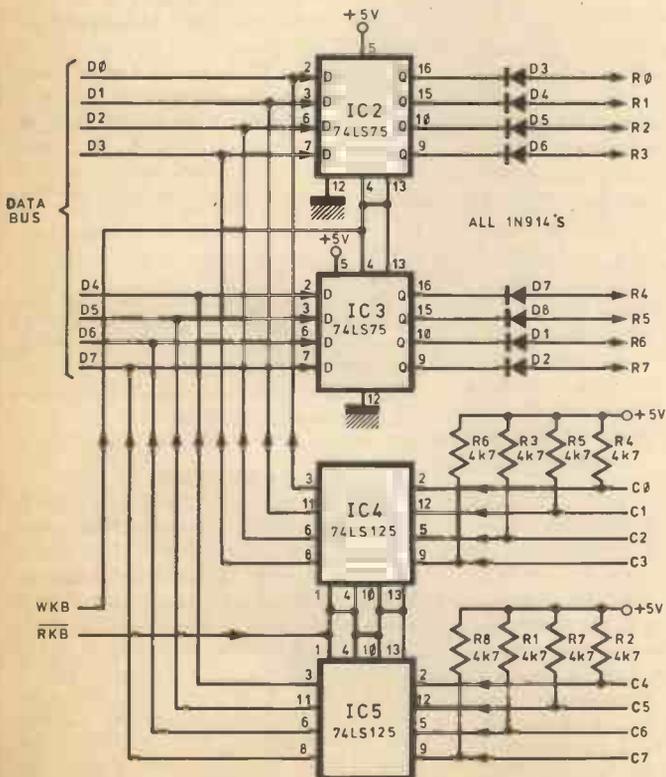


EG150

### POWER SUPPLY UNIT

The power supply is very straightforward since the Cornpukit is a single supply device with distributed capacitive decoupling on the board. All but the transformer are mounted on the p.c.b. and a heat sink is provided for the 5V regulator. The photograph shows the extent to which supply noise decoupling is allowed for on the p.c.b. 100n capacitors appear at the most important places to prevent spikes and crosstalk being transmitted along the power lines.


The PSU also has a 3A fuse and a polarity compliance diode to give some protection against accidentally reversing the +5V and 0V lines by those using an external PSU for any reason.

The UHF Modulator used on the board is the 8 MHz Astec device which gives an excellent output when supplied with five volts. This device was chosen to ensure that the p.c.b. remained a single-supply system.

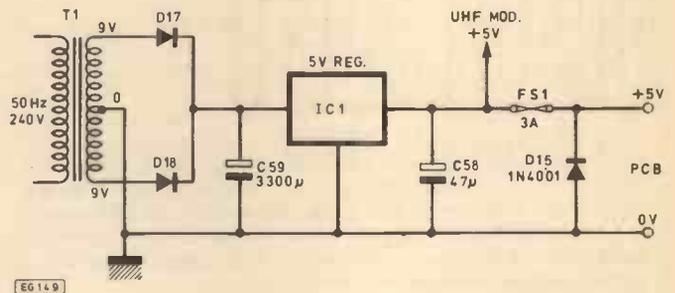

EG149

Fig. 4. Power supply circuit diagram

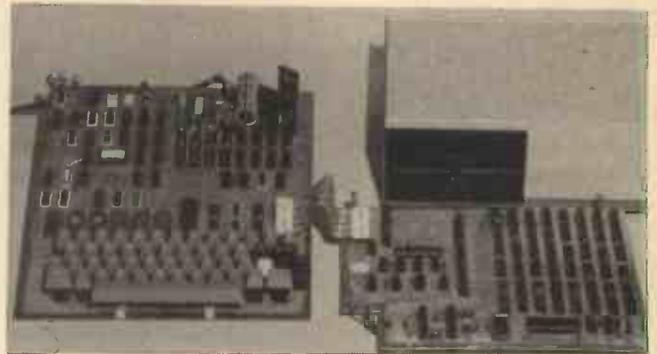

The UK-101 working happily with a floppy disk.

**NEXT MONTH:** Constructional details of this powerful computer are given, so learn computing the comprehensive way, using a high level language and working down to hex code programming. The UK-101 is capable of both!



#### END OF TASK

The third small astronomy satellite launched by NASA ended its task and life by burning up over the Pacific Ocean in April. During its lifetime it made important discoveries which are being studied at the Massachusetts Institute of Technology and the Smithsonian Astrophysical Observatory.

The satellite was launched in 1975 and placed in a 500km circular orbit. It was designed for a life of one year but in fact lasted three times that period. Data was continuously returned up to the time when atmospheric drag (accentuated by the rise in sun-spot activity) ended in the decay of the orbit to burn-up destruction of the satellite.

Several X-ray sources were discovered and also two quasars. The most interesting objects discovered were the X-ray 'bursters'. These objects have the characteristic of giving short intense bursts of X-rays. Such is the intensity that in some cases bursts appear, at intervals of a few hours, at a level of 100,000 times the intensity of the Sun in a fraction of a second, and then fade away over a period very much greater. A theory offered in explanation of these events, and this is supported by other satellite observations, is that the bursts of energy derive from thermo-nuclear reactions. About 35 such 'bursters' are now known; more than half of them were discovered by the satellite.

The astronomy satellite also discovered an X-ray burster which emitted bursts several times a minute. The nearest of this type of object is about 15 light years distant.

#### INTERNATIONAL ULTRA-VIOLET EXPLORER

This spacecraft is an astronomical telescope in a geostationary orbit which has been used recently by the European Space Agency to look at a new supernova. The supernova was observed by an American amateur astronomer

Gus E. Johnson of Swanton, Maryland. He has the distinction of being only the third person in history to have made a direct observational discovery of a nova in another galaxy. Gus Johnson was observing NGC 4321, number M100 in the Messier catalogue. Using his eight inch telescope he saw a 12th magnitude star southeast of the nucleus of the galaxy. It is not possible to see the nova with the naked eye. Its distance is about 100 million light years; what is being seen now happened 100 million years ago.

The European Space Agency, ESA, have observed rapid changes in the ejected material of the nova and modified spectral features similar to those found in earlier examples. Also there was shown the absorption of ultra-violet emission lines. These lines are similar also to that found in the interstellar gas in our own galaxy.

The satellite is controlled through the tracking station at Villafranca near Madrid. The US contribute the major share of the cost, other funding coming from the ESA and British Science Research Council. Access to the International Ultra-Violet Explorer is divided between NASA at the Goddard Spaceflight Centre in Maryland and the ESA's station at Villafranca. This spacecraft was launched last year.

#### THE SHUTTLE—TOWARDS THE LAUNCH

The Orbiter named Enterprise was moved from the assembly pad to launch pad 39A at Cape Canaveral at the beginning of May. It consisted of the Enterprise assembled on the external tank and a pair of Solid Rocket Boosters, SRBs. It is proposed to use the Enterprise to prepare the way for Orbiter Columbia which will make the first flight. The gross lift-off weight of the shuttle is a little over 2,000 tonnes. The shuttle is fixed to the launch platform at four hard points at the base of each SRB.

The purpose of the launch pad trials with the Enterprise are to check procedures and mechanical clearances. One important part of the tests will be that of opening and closing the payload bay doors while the shuttle is in the vertical launch position. This appears to be a vital stage because in the procedure of the first launch the payload will be loaded at a late stage. It is expected that a number of launches will take place in this position. Though some launches may be requested in this manner it is thought that it may be a procedure to save time between successive launches. It is probable that after the tests have been carried out Enterprise will be refurbished for a mission later.

The last date for the first launch was scheduled for September 1979 and the success of the tests will determine the exact date for the first mission, which is now thought to be for November. The completion for the work on Columbia will naturally be the determining factor. Columbia left the Rockwell plant in March but there remained a number of things to be done and some of the temporary work has led to certain difficulties. A very considerable number of man hours are required to bring matters to the right timetable, something of the order of 70,000.

The attitude control system used in orbit is erected below the cockpit windows and had to be removed in order that the propellant could be loaded. Columbia is fuelled by hypergolic propellants. These are mono-methyl, hydrazine and nitrogen tetroxide. These are subject to ignition on contact.

Other work involved in preparation was the powering of the electrical system and connecting up the automatic test systems. There were no problems. The data processing and warning systems were also tested. The test instrumentation has a very extensive task, for this is to give vital information as to stresses, acoustic levels of vibration and temperatures. Installation of the fuel cells for electrical power has yet to be accomplished. An auxiliary power unit is an important item for installation since this is to be used for the operation of the control surfaces during ascent and descent. All this could mean that the final date for the first launch will be delayed until 1980.

Meanwhile the two astronauts John Young and Robert Crippen, the first pilots of the Space Shuttle Age, continue to prepare. Many programmes have already occupied their time in the simulator and the remaining programmes are now being studied and practised.

#### THE SECOND FLEET SATCOM

The United States Navy's new fleet Satcom was launched from Cape Canaveral on May 4th 1979. This was one day later than set because of certain last minute confirmation checks. Two days after launch the apogee 'kick' motor boosted the satellite from its transfer position to the geostationary orbit.

The satellite will provide radio links between ground stations, ships, submarines and aircraft. It will be controlled by the USAF at its own centre at Sunnyvale, California. The USAF will use the facility for ground to air communications but the Navy has independent access.

The coverage is the eastern United States, the Atlantic Ocean, Europe and a part of Africa. The position of the satellite is at the geostationary longitude 23° West. Three more such satellites will be added at the rate of one a year. The average life of each one is of the order of five years.

#### VENUS

The first full disc view of Venus has been provided by the Pioneer Venus Orbiter. The direction of the clouds clearly indicate to east-west rotation of the planet, that is retrograde. It was taken from a distance of 65,000km from the planet.

#### THE FALL OF SKYLAB

By the time this is in print Skylab might be down. British and American satellite experts forecast Skylab's re-entry at 1st, 2nd, 10th or 20th July. Of the 20 tonnes of fragments falling at 320km/h the largest pieces likely to pass through our atmosphere are: a lead film vault weighing 1,800kg, an aluminium airlock shroud of 2,250kg and six oxygen tanks at 1,215kg each. A total of about 500 pieces are expected to fall over an area 6,400km long by 160km wide, between latitudes 50° north and 50° south. Most of the pieces will vaporise.

# Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by  
Alan  
Turpin

and  
David  
Shortland

## IC TEST CLIPS

This new Lektrokit i.c. test clip offers a simple and inexpensive means of assessing any i.c. pin or lead. Test probe attachment is made simple and the chance of damaging i.c. pins is avoided. The test clip simply clips over the i.c. bringing its individual lead connections out to a set of easily accessible contacts at the top of the clip.



8, 14 and 16 pin sizes are available. The 14 pin version costs £2.95p, (pre-budget).

A contact "comb" separating individual contacts gives positive positioning and prevents accidental shorting of adjacent leads.

Lektrokit Limited, Sutton Industrial Park, London Road, Earley, Reading, Berks RG6 1AZ (0734 669116/7).

## D.I.L. SWITCH BROCHURE

A new, six page, four colour brochure is available free from Erg Components. It contains full technical specifications and switching configuration diagrams for all types of Erg d.i.l. switches. Prices are given and there is no minimum order charge for items held in a maintained stock.

Erg Industrial Corporation Ltd., Luton Road, Dunstable, Bedfordshire, LU5 4LJ. (0582 62241).

## LOW PROFILE KEYBOARD CONSOLES

A new range of keyboard enclosures has recently been introduced by BOSS Industrial Mouldings. They are available in three sizes, are all aluminium and have a textured black base which contrasts with either the semi-gloss sand or charcoal grey top panels. The top panels slope at approximately 20°.



Prices from £16.05 to £21.83, plus VAT and carriage.

BOSS Industrial Mouldings, Higgs Industrial Estate, 2 Herne Hill Road, London, SE24 0AU (01-737 2383).

## CHEAP CHIPS

A special price is being offered by Chromasonic Electronics this month on ZN414 i.c.s. Two chips will cost £1.25 including VAT, p.&p. If you check the normal price and include VAT, etc. we think you will find this is a saving of almost 50 per cent!

## BECKMAN DMM

A new 3½ digit l.c.d. multimeter has been introduced by Beckman Instruments. Measurements can be made on five d.c. voltage ranges from 200mV to 1,500V; five a.c. voltage ranges from 200mV to 1,000V and five a.c. and d.c. current ranges of 200µA to 2A which can be extended to 10A through a separate input. The six resistance ranges have f.s.d. values from 200Ω to 2MΩ.

The low power resistance ranges permit in-circuit resistance measurements to be made without turning on semiconductors, which would affect the measurements. For applications that require diodes and semiconductors to be tested, a separate semiconductor test function provides a 5mA test current, enough to check the operation of most semiconductor junctions, even circuits with as low as 200 ohms of equivalent parallel resistance.

An Insta-Ohms continuity test indicator allows continuity to be checked. When an in-range resistance is measured an ohms symbol is displayed in less than a millisecond.



The meter has an input impedance of 22MΩ. Accuracy is to within 0.1 per cent + 1 digit on all d.c. voltage ranges. Both a.c. voltage and current are average r.m.s. measurements.

The inputs are protected against overload conditions that may arise from measuring unknown signals or from operator error. Voltage ranges are protected from inputs in excess of 1,500V r.m.s. a.c. Resistance ranges are protected to 300V d.c. or r.m.s. a.c. The current inputs are protected with a 2A fuse, a replacement fuse being included inside the instrument's case. The 10A range is rated for 20A for 30 sec.

A 9V battery provides up to 2,000 hours of continuous instrument operation, giving up to two years typical use. During the final 200 hours of battery life a decimal point blinks on the display to warn the user to change the battery. Calibration, guaranteed for one year, requires only the simple adjustment of an internal trimming potentiometer.


Accessories include two carrying cases, a radio-frequency probe for voltage measurements up to frequencies of 200MHz, a current clamp for measurements up to 200A, and a de-luxe test-lead kit with test leads and ten screw-in probe tips.

The price of the 3020 is £115, plus VAT and p.&p. For further details contact Beckman Instruments Ltd., Queensway, Glenrothes, Fife KY7 5PU (0592 753811).
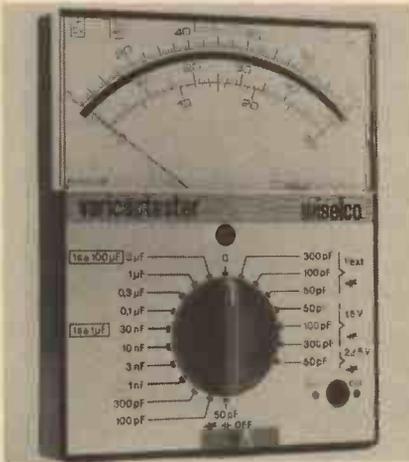
## MULTIRANGE CAPACITANCE METER

This simple-to-use instrument is now available on the UK market from Alcon Instruments. Known as the Varicaptester, it is a pocket-sized multirange capacitance meter with abilities extending from pF to thousands of  $\mu$ F.

It is constructed in tough ABS plastic with simple range selection, full-view cover, and can cope with all types of capacitor. Component values up to  $3\mu$  are read in conjunction with a green illuminated indicator (overflow) which clearly shows when the value of the component under test is too high and it requires a higher range.



For values above  $3\mu$  a system of timing the interval between flashes of an l.e.d. provides direct indication of capacitance value. On two selected ranges, capacitance can be indicated as  $1\mu$  per second or  $100\mu$  per second, thus extending the range to several thousand  $\mu$ F.

Maximum sensitivity is  $1\text{pF} \times$  division, accuracy is 2.5 per cent. Power for all normal uses is supplied using internal batteries. The user may apply an external voltage.

The Varicaptester comes complete with instructions, leads, case and batteries. Price is £82.50 (pre-budget) and delivery is at this time 'off the shelf'.

Alcon Instruments, 19 Mulberry Walk, London, SW3 6DZ. (01-352 1897).

## 100W MOSFET

The PA100 from Ambit is a power amplifier module which uses Hitachi power MOSFETs and is suitable for audio applications at power levels up to 100W r.m.s.

The drive circuitry is greatly simplified with MOSFETs while bandwidth is up to 300kHz and the harmonic distortion less than 0.01 per cent in the audio range.

The use of MOSFETs increases the reliability of the amplifier because of their inherent freedom from thermal runaway and secondary breakdown as well as loads that are potentially hazardous for bipolar amplifiers (i.e. reactive loads).

The price of the PA100 is to be announced in the near future.


Ambit International, 2 Gresham Road, Brentwood, Essex (0277 216029).

## NANO TRAINER

The Nanocomputer training system has been specifically designed by SGS-ATES for the educational environment. The system which is based on the Z80 microprocessor includes a solderless experiment section, specially written user software, many optional peripherals and a three volume series of training books.

The modular construction of the system allows the student to enter the course at a level to suit his ability.

The three main levels in the course cater for: students with no knowledge of computers or digital electronics—book one with the basic micro-computer; students with a knowledge of digital electronics—book two and the experiment station; students with a more advanced knowledge—book three plus the micro-computer, the experiment station, and additional software. At the very highest level of education it is possible to upgrade the Nanocomputer to a full industrial microcomputer, thus allowing individual research programs to be carried out.

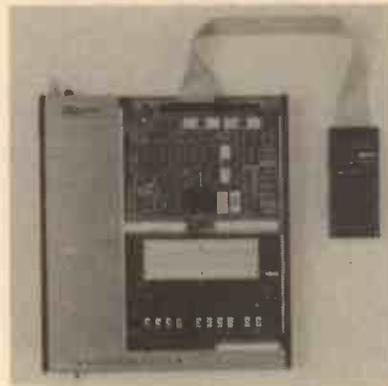


The price of the Nano trainer is between £250 and £450 depending on the model.

SGS-ATES (UK) Ltd, Planer House, Walton Street, Aylesbury, Bucks. (0296 5977)
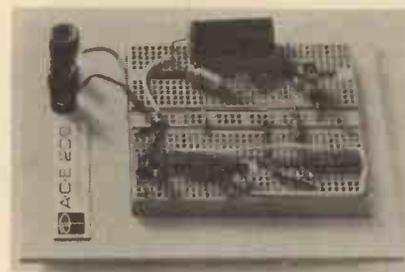
## ACE 200

Lektrokit have introduced an evaluation breadboard kit called the ACE 200. The unit has a universal matrix of 728 plug in tie points which include 136 separate tie points in lines of 5, and has two distribution buses each consisting of 24 tie points.



Measuring  $11.5 \times 14\text{mm}$  the unit is mounted on a baseboard which enables two power terminal connections to be fitted.

The cost of the ACE 200 is £11.48 plus VAT and p&p.

Lektrokit Ltd., Sutton Industrial Park, London Road, Earley, Reading RG6 1AZ. (0734 669116).

## MICRO TRAINER

The Signetics Instructor 50 has been designed as a microprocessor training aid suitable for teaching CPU operation, programming and applications. The self contained unit can be interfaced with a conventional audio cassette recorder for program storage.

The Instructor 50 incorporates a single-line l.e.d. prompting display together with a 16-key hexadecimal keyboard for entering data values and a 12-key command keyboard for issuing instructions and selecting operating modes. The system uses a monitor known as USE (User System Executive) which eliminates the need for complicated start-up routines and allows a variety of operations to be carried out on programs and stored data.



The unit, which is based on the Signetics 2650 microprocessor, is equipped with an S-100 expansion interface which allows it to be used as a small computer limited only by the peripheral boards used. In addition, the program/data-entry and debug facilities of the basic Instructor 50 can be extended to any device connected to the interface.

The Instructor 50, which is supplied complete with a user's guide, introductory manual and leads for audio-cassette interfacing, is priced at £300 plus VAT.

SASCO, PO Box 2000, Crawley, Sussex RH10 2RO.

## ONE MEGABIT BUBBLE FROM ROCKWELL

The latest addition to the AIM65 microcomputer system from Rockwell is a fully addressable add-on one megabit bubble memory system.

This external memory is interfaced to the AIM65 via a buffered expansion motherboard which has five connector slots that can accommodate any of the other types of Rockwell or Motorola Exorcisor modules as well as those from other manufacturers.

The motherboard extends the 6502 bus. The bus lines (address, data and control) are buffered to provide drive capability. Address decode logic for mapping internal and external addresses in 4K byte increments is also provided. Sixteen switches enable the user to define whether each 4K byte portion of the 6502 address space of 65K bytes is internal or external to the AIM65. Thus under software control the megabit bubble memory module can provide 128K bytes of memory expansion.

The price of the motherboard is £136.50 plus VAT and p&p. Pricing of the various options allowed by the motherboard can also be obtained from Pelco (Electronics) Ltd., Enterprize House, 83-85 Western Road, Hove, Sussex, BN3 1JB. (0273 722155).



## SPRING TRADE SHOWS


Every year the TV, Radio and Hi-fi manufacturers gather in London for the Spring Trade Shows. However instead of gathering under one roof, they spread themselves out over 26 hotels with anything from one to nine exhibitors at each. For those with the stamina it was a chance to see the very latest products before they reach the high street retailers, or blister in the attempt.

On the TV scene, Ferguson and Ultra were showing their new television ranges, featuring the latest TX9 single board chassis from Thorn featured in a News Brief last month. Philips were also launching a range of TVs with their new chassis the KT3 which is also used in the latest Pye range of colour sets. The KT3 chassis was especially developed for use with the smaller (14in to 20in) picture tubes.

Many of the larger manufacturers had sets suitable for both teletext and Prestel on view, and Hitachi had their "Instaview" TV on display which provides sound and picture one second after switch on by eliminating the need for preheating the tube.


One area of the market which seems to have really expanded is the small screen TVs

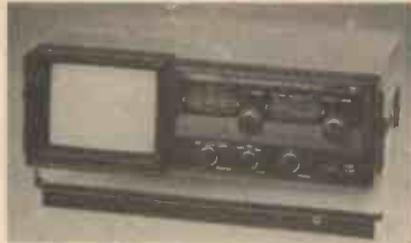must be its realistic limit with their 2in sets. These miniature TVs vary considerably with many having radios and/or cassette recorders, some of which are stereo.



Crown's 5TV priced at £125 and supplied complete with rechargeable battery pack.

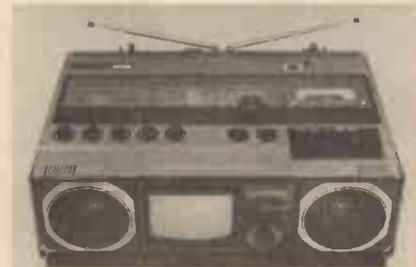Crown launched their 5TV, a 5in set with a 3 band radio and a totally flat screen which is said to give a larger viewing area than conventional tube. Crown hope the 5TV will increase their share of the small screen market (currently claimed to be 48 per cent) but the competition will be intense.




The K50 and K62 TVs from Hitachi retail for £220 and £249 respectively.

Hitachi had two 5in monochrome sets on display, the K50 and K62, both of which have cassettes and radios with the radio in the K62 being stereo. The small screen offerings from Sony were two very different models. The TV



The TV511UK from Sony is priced at £127.

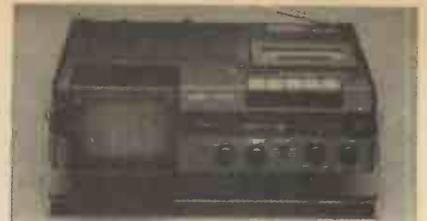511UK is a robust looking set with a screen angle adjustment ring to enable the picture to be moved through 90° for horizontal or vertical viewing, whilst the FX412UK is a



The FX412UK also from Sony, priced at £209.

smart lightweight unit with a 4in screen, 3 band radio and a cassette recorder.

The latest innovation in the hi-fi field is a continuation of the micro TV trend with micro hi-fi separates being exhibited by Aiwa and



The complete Amstrad system includes the pre amp, power amp and tuner, priced at £185.

Amstrad. The Amstrad system includes a P101 preamplifier, A101 power amplifier and T101 tuner which has a digital frequency display, i.e.d. signal strength indicator and centre zero tuning.



The Aiwa system is priced at around £500 excluding speakers (SCEII) and record deck.

The Aiwa micro system on show consisted of a pre amp (SAC22), power amp (SAP22), tuner (STR22) and cassette deck (STL22).

Toshiba's latest music centre, the SM4750 has microprocessor memory tuning which can store preset information of eight stations on each of the four wavebands. Long, medium, shortwave and VHF are available with auto tuning on VHF and medium. The 4750 has a direct drive turntable with a strobe, Dolby stereo cassette deck and built in clock timer.



The SM4750 has a retail price of £664.50 excluding speakers. British made SS45GB speakers are recommended for the 4750, priced at £109.50 a pair.

TV, Radio and Hi-fi were the main categories of the shows but other small and interesting products were on view. Here are



The Plustronics CTV55D from Plustronics, a 5½in. colour model priced at £299.

with Plustronics, JVC, Hitachi and Toshiba all showing 4½ to 6in colour sets. Many more were showing 4 to 5in monochrome sets with JVC and Sinclair taking screen size to what



The P100 TV from JVC with a 2in. screen which retails for around £165.

a few examples of the way developments in technology and changing consumer interest are being responded to by manufacturers and marketers.

### DESTROY—DESTROY

You control the destroyer to protect your convoy against enemy torpedo attack. Direct your destroyer to intercept and destroy the enemy torpedoes. Play against the clock.

Approx. size— $6\frac{1}{2} \times 3\frac{1}{2} \times 1$  in.  
Priced at around £16.



Other hand held games from Adam Imports: **SOCCER.** The computer defends the goal with its six defenders. You attack using the keys provided. Shoot for goal and score as many goals as you can in the time allotted.

Full timing for first and second halves, scoring for Team A and Team B. Change side indicators. You change sides when you have scored and when you have played for a set period of time without scoring.

The game can be played in amateur or professional status and operates off a heavy duty PP3 battery or equivalent (supplied), or an alternative Grandstand mains adaptor (extra). Game priced at around £20.

**4-IN-1. Speedway:** Red l.e.d.s travel along the display being controlled by the gas and brake pedals. Steering is done by the two steering keys. Play against the clock.

**Blackjack/Pontoon:** Play this card game to Las Vegas rules. The bank will automatically take your losses or add your winnings.

**Brain Drain:** The computer generates four hidden numbers. Guess the numbers in the least number of tries.

**Calculator:** A full 4-key memory calculator is incorporated with all major functions: dividing, multiplying, adding and subtracting.

Power source—5 x HP7 batteries or equivalent (not included). Grandstand mains adaptor (extra). Game priced at around £20.

The complete range of products in the Adam Collection comprises: Video Sports Centres, Video Entertainment Centres, Video Entertainment Computer, Hand-Held Electronic Games, Electronic Calculators, Quartz

Watches, Clock and Portable Radios, Digital Clock, Clock Radio Cassette Recorder, Stereo Clock Radio, Mains Adaptors, Audio Whistle Switch.

See the range at an Adam stockist or write for leaflets to Adam Imports Ltd., Unit 2a, Ripon Way, Ripon Rd. Ind. Est., Harrogate, Yorks. (0423 501151).

### HYPERSPACEWARPIEOUT

Star Chess is a TV game for two players which combines sophisticated technology with skill and luck.

Both players are Admirals of a fleet of spaceships. Using all your resources, your mission is to annihilate your opponent's flagship, the Commander, and at all times protect your own Commander from destruction.



To help you in your task, you have Starfighters, Supercruisers, Superfighters, Starcruisers and an extremely powerful Destroyer. Each of these spaceships has an armoury of missiles to blast your enemy's forces off the screen.

When one of your spacecraft is in danger and has no apparent means of escape—all is not lost, it can be warped into hyperspace and out of immediate danger. But beware, for that ship will re-materialise in almost any square on screen, wiping out any spaceship occupying that square—even your own Commander. When one of the Commanders has been destroyed—cosmic pandemonium breaks out on your TV screen. R.R.P. is £64.95.

Literature on other games from Waddingtons Videomaster Ltd., 36-44 Tabernacle Street, London EC2A 4DT.

### BE YOUR OWN VIDEO CAMERAMAN/DIRECTOR

Do your own video thing with a portable video cassette recorder and zoom camera.



Video cameras from Ferguson can be powered from their Videostar portable cassette recorder as well as mains. The monochrome camera has a 2 to 1 zoom lens, automatic iris,

and a built-in directional microphone in case you don't have a sound assistant. The colour camera has a 6 to 1 zoom. Likely prices, monochrome camera—£214; colour camera—£856; portable recorder—£856; mains adaptor—£20; tuner/timer—£214.

### MULTI-INTERFACE SCENARIO

What to do with a Cassette/Clock/Radio.

- Listen to the radio.
- Listen to cassettes.
- Note the time.
- Record speech onto cassette.
- Record from radio onto cassette.



- Auto-record at a preset time.
- Be lulled to sleep with auto-stop.
- Sleep-learn from cassette.
- Have the radio wake you up.
- Have cassette music wake you up.

All this seems to be possible with the Nova 309 which has a R.R.P. of £57.50.

If a microwave oven and a home computer were incorporated what couldn't you do?

Novalline Ltd., 14-20 Headfort Place, London SW1X 7HN (01-235 5444).


### UHF VROOM

If a second TV set is a portable it is likely that its integral aerial will not provide as good reception as an outdoor array. There may be sufficient signal strength from the outdoor aerial to feed both sets but parallel fed sets are almost certain to cause each other interference. So a properly designed splitter must be used. Then there is still the possibility that there is insufficient signal strength to feed both sets.



A solution to both problems is offered by a Second Set Amplifier by Labgear. It is expressly designed to operate two UHF TV sets from one aerial. The device is mains powered and provides a modest boost to the signal on each outlet. R.R.P. £7.30.

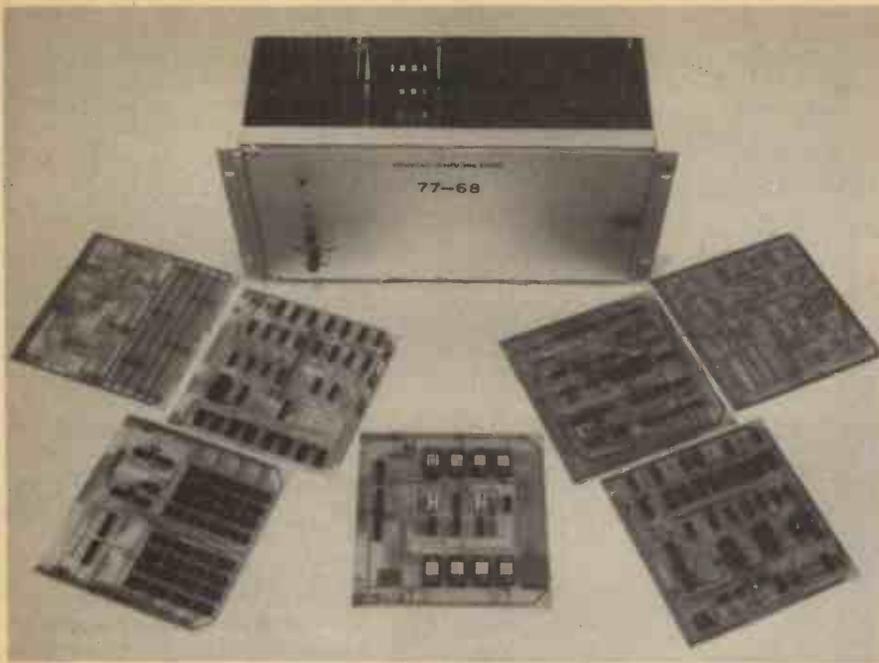A leaflet on Labgear's—Signal Amps., Splitter/Combiner, and Log-periodic room aerial, is available from Labgear Ltd., Abbey Walk, Cambridge CB1 2RQ, England (0223 66521).



# 77-68

## review

P. BIRNIE

Would-be microprocessor system constructors are today faced with a bewildering variety of systems to choose from. These range from cheap systems which are relatively easy to build, but may be difficult or impossible to extend beyond the 'keys and lamps' stage, to the expensive systems aimed more at the professional market which require the purchase of many hundreds of pounds worth of equipment before any results can be seen. When Tim Moore of Newbear Computing Store designed his 77-68, he was clearly aiming at a minimum cost system capable of expansion to a 'full house' system without the necessity for spending a large amount of money before results were seen. His claim in 1977 that 77-68 only cost £50 to get going was proven by many members of the Amateur Computer Club and even today the kit of parts for the basic system costs less than £50.

This review looks at the 77-68 CPU board, which utilises the Motorola 6800 processor, and goes on to examine in detail the VDU and monitor boards presently available. Brief mention will also be made of the boards currently under development—these include a dynamic RAM

board and floppy disc controller. It is worth noting at this point that in common with all systems employing complex logic devices of the TTL and MOS families, 77-68 should be regarded as a project for the constructor with at least limited experience of assembling projects utilising

these devices. The complete beginner would be well advised to make several of the simpler projects offered in *Practical Electronics* before tackling an ambitious project such as this—when later on the construction is referred to as 'simple', this should be taken strictly as a relative term.


### THE SYSTEM


76-68 uses the Motorola 6800 8 bit microprocessor. This device is a firm favourite with both the amateur constructor and the professional user and although the device has in its basic form some software 'nasties', these can be overcome by a bit of thoughtful programming (new software compatible versions of the 6800 such as the 6809 overcome these problems, but will not be considered here).

The basic CPU board is designed to operate as a 'stand-alone' unit interfacing with keys and lamps to allow simple programs to be written and executed without the necessity for a VDU or teletype. This same board, when plugged into the 77-68 bus, will operate as the CPU card for a system with RAM, ROM, I/O etc., in other words the constructor can start at the simplest and cheapest end of home computing and grow his system as time and money allows into a powerful computer capable, for instance, of running BASIC or performing complex computing tasks.


A block diagram of the CPU card is shown in Fig. 1 and those with knowledge of microprocessors will recognise the familiar blocks of circuitry needed around the 6800 to turn it into the heart of a computer system. For those who may be new to the subject—the blocks shown are essential to allow the microprocessor to communicate with the address and data busses and the keys and lamps are used to allow the user to input programs and read data bus contents.

Fig. 1. Block diagram of CPU board

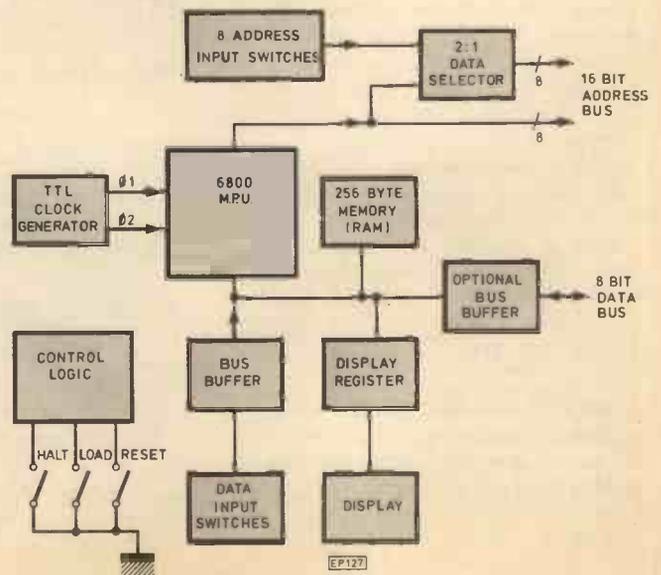

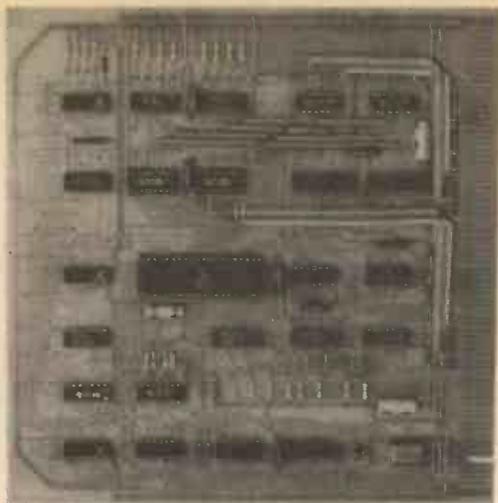

**CPU board**

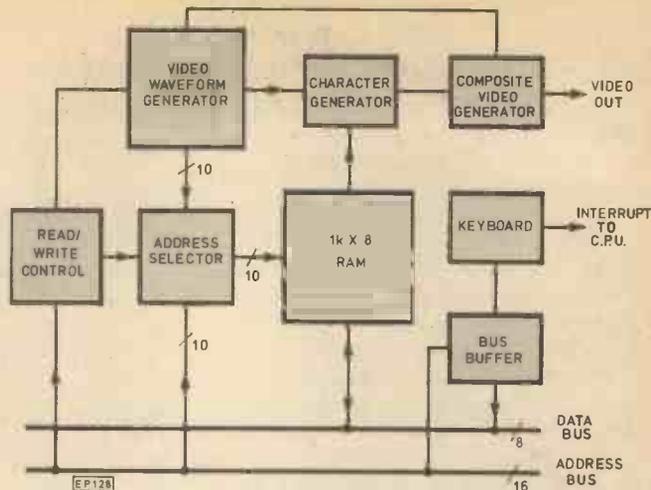

**Fig. 2. VDU block diagram**

The data input switches are buffered from the data bus by a tri-state buffer allowing the processor bus to be freed from the keys except when data is actually being entered from them.

The data display register latches the data bus information at the appropriate instant and displays this information on an array of l.e.d.s. As the 6800 is a dynamic device, this latch is necessary since data bus information only 'appears' for part of the microprocessor clock cycle and must be 'caught' by appropriately gated signals in an 8-bit latch. The 77-68 CPU board allows bus buffers to be fitted to the data bus and this should be considered essential if a system with other 77-68 cards is being constructed. The address bus from the microprocessor has its lower order eight bits passed through a 2:1 data selector to allow either a microprocessor generated or switch generated address to be output from the card.

These address switches, data switches and lamps are the users input/output path, allowing memory to be written with programs or data (256 bytes of RAM are provided as shown in Fig. 1), and when programs are being run or debugged, data from memory or the processor to be output onto the l.e.d. display.

The 77-68 CPU card also contains a TTL clock generator which is crystal controlled, allowing accurate software timing should this be required by the user—and finally control logic which interlocks the keys and lamps described above with three switches, halt, load and reset, which will be described later.

### CARD CONSTRUCTION

Construction of the CPU is facilitated by the use of an 8in square printed circuit card with a 78 way, 0.1in gold plated edge connector etched along one edge. The instruction manual *'The construction*

*of a simple microcomputer'*, which can be obtained separately from Newbear, contains full and detailed descriptions of the 77-68 system and the construction of the CPU.

The card assembled as part of this review was completed in a couple of evenings and worked first time when connected to a 'keys and lamps' interface.

The card being single sided for reasons of economy, requires a large number of insulated links and two pieces of ribbon cable to complete the interwiring pattern of the integrated circuits. This part of the assembly takes more than half of the total assembly time and requires care since any errors in linking holes, or faulty insulation, solder bridges, etc., can prove difficult to track down later. The considerable economy affected by using a single sided board is probably worth while since a double sided plated through hole board of this size would almost certainly add £15-£20 to the overall cost of the system; to an amateur constructor with 'free' time at his disposal this additional cost will in most cases be undesirable. The remainder of the construction simply involves 'plugging in' the i.c.s and the discrete components and carefully soldering them in place with the usual earthed soldering iron.

### RUNNING A PROGRAM

Having completed the CPU card and made up a simple keys and lamps interface as described in the manual, a 5 volt 1 amp power supply must be used to power it, this being supplied by the constructor.

Having followed the Newbear instructions for testing what can be achieved with this basic CPU system? The manual briefly describes the 6800 instruction set in terms of its addressing modes and then gives a number of small programs which allow the user to immediately see and hear the processor at work. Several lamp

flasher programs can be run which cause varying lamp patterns to flash on the data l.e.d.s. In addition, if a simple add-on amplifier interface is built then a tone generator program and even a program to play tunes can be run.

These programs, whilst showing in no uncertain terms that the CPU is operational also allow the user an opportunity to study the mode of operation of the 6800 software since clear notes are included in the manual of the changes which can be made to the software, for instance the lamp flasher programs, and the user can see for himself just what effect such changes have on program operation.

A couple of evenings spent loading programs from keys in pure binary form and reading back program and data in binary will convince most constructors of the transitory nature of any 'keys and lamps' system—in simple terms the possibility of error is so great in entering and retrieving data in binary form, that such a simple system can only be considered as suitable for educational purposes. This is not to say that relatively sophisticated programs cannot and have not been run using only keys and lamps, but that operation of such a system in conjunction with lengthy software is a painfully slow process.

### VDU AND MONITOR BOARDS

Confronted with the above dilemma, one can either purchase a teletype or consider the construction of a VDU, and it is the latter approach which is greatly favoured by the reviewer. The inconvenience of a VDU in terms of the lack of hard copy, is countered by its silent operation and the convenience of a 'screen' when it comes to playing most computer games and displaying data as program output in many cases. In addition


a VDU, if constructed round a domestic TV set, will almost without exception cost less to construct than a teletype would cost to buy.

Newbear have a 77-68 VDU board which offers a bus compatible interface between a keyboard and a video monitor or with the addition of one of the cheap readily available video modulators—a domestic TV set. The resulting VDU has a 24 line display with 40 characters per line, upper and lower characters being displayed in a 7 × 10 dot matrix. As is becoming virtually standard in 6800 base systems, the video memory (constructed from eight 2102 devices) is memory mapped as far as the CPU is concerned, giving a vector driven display. This means in simple terms that if a single character on the screen is to be modified then by generating the address of the character to be modified, and sending that to the VDU, that character can be modified on its own, rather than in a serial VDU system where to modify a single character, then the whole screen must be re-written.

The VDU board is the Newbear standard 8in square unit with a 78 way 0.1in pitch edge connector etched along one side. Rather than use one of the many CRT Controller (CRTC) chips now available, Newbear implement their VDU using LS-TTL and this allows the use of a good character generator with upper and lower case alpha characters and a variety of semi-graphics characters.

The use of this device, the Texas Instruments 74S262, turns any home-built VDU from the familiar upper case only device into a truly professional unit which is easy to read and offers scope for limited graphics. In addition to the devices necessary to generate the line and frame waveforms, and form characters, this board also contains 1K × 8 of static RAM—seven bits in each type being used to store a ASCII code for that character,

Fig. 3. Block diagram of MON 1

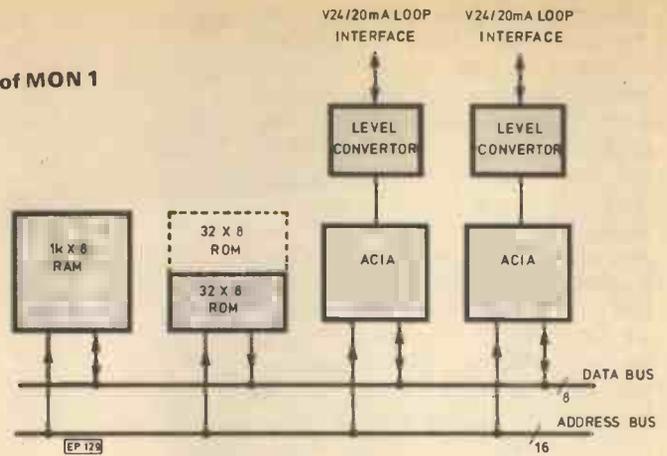

the eighth bit being used to over video invert/normal on a character by character basis.

This facility allows highlighting of text and considerably extends the scope for graphics production. As with the 77-68 CPU board, and others in the 77-68 family, the VDU board is a high quality single sided fibre glass printed circuit board and as with the CPU board, more than half the construction time is taken up in linking points on the circuit using single cored insulating wire. The remainder of the time is taken up in soldering in place the thirty-four integrated circuits used in the system, and an experienced constructor should have no problems in completing the assembly in two or three evenings.


The VDU card has a video output which will direct drive any standard video monitor, or by means of one of the cheap modulators now available feed into the aerial socket of any TV receiver. The card provides an 8-bit port for a keyboard which of course must be provided by the constructor.

Any ASCII keyboard will be suitable provided that it has a positive going strobe in addition to the eight data lines—this strobe being used to cause a 'Non Maskable Interrupt' to the processor when a key is depressed. Newbear have thoughtfully provided a breadboard area on the VDU board which could be used to interface a non-standard keyboard to the VDU card if required.


It was during testing on this board that the only design fault was found in 77-68; one of the fixed resistors used to determine the range over which the line and frame pulse generator may be adjusted, was too large a value and only by changing this resistor could a stable locked display be obtained. This minor fault, whilst being easy to trace with an oscilloscope, could prove tricky for the constructor with only a multimeter to hand.
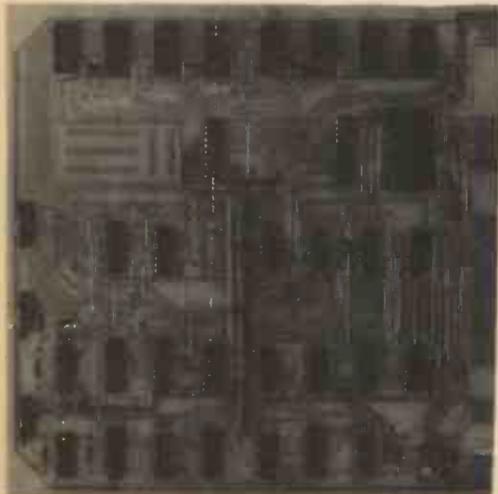
#### EXCELLENT DISPLAY

The complete VDU offers a really excellent professional quality display and the keyboard quality is obviously determined by whatever is connected to the



(Left) VDU board

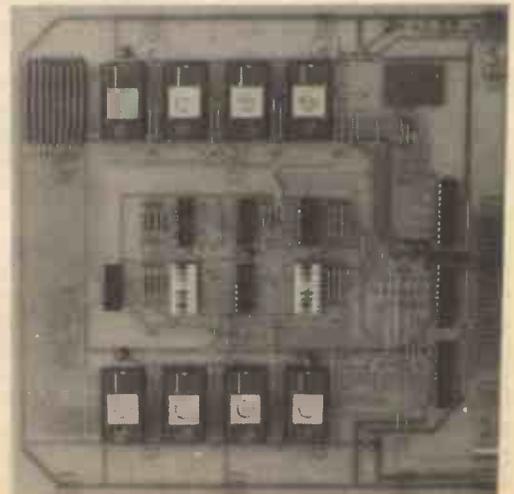

(Right) ROM A—the 16K byte EPROM card


interface provided by Newbear. As has been said before, there are significant advantages in using a good (if expensive) character generator and these advantages clearly show up when even simple video graphics are displayed, let alone when text is being viewed. The video is absolutely rock steady (which is more than can be said of some commercial units) even although the 'timebase' of the VDU is centred round a 556 dual timer chip. This is undoubtedly due to the digital circuitry used to generate all timing waveforms, rather than the inaccurate monostable approach adopted by some designers.

## BUG 2 MONITOR

Completion of the CPU and VDU boards results in a processor capable of operating (via the keyboard and VDU) only when a monitor program is loaded into the system and set running. The best known 6800 monitor is of course the Motorola MIKBUG software familiar to most 6800 users. This software allows the user to communicate at machine-code level with the processor via a teletype or serial port VDU. Since 77-68 uses a parallel port VDU and keyboard, MIKBUG would not be a suitable piece of software and thus Newbear supply their BUG 2 monitor listing along with the VDU hardware. This monitor must be toggled in using the keys and lamps of the basic control panel and when set running, allows VDU access to the system—fine while power is applied to the system, but the software is of course lost on power-down, resulting in a lengthy 'toggling in' procedure before each session. This could be overcome by Newbear providing BUG 2 in a ROM and the reviewer feels that this expense would be justified (perhaps as a plug-in option). The Newbear view is that due to the simplicity of BUG 2, most users will go on to develop their own monitor software and though this may well be true, for many this omission will be a great nuisance.
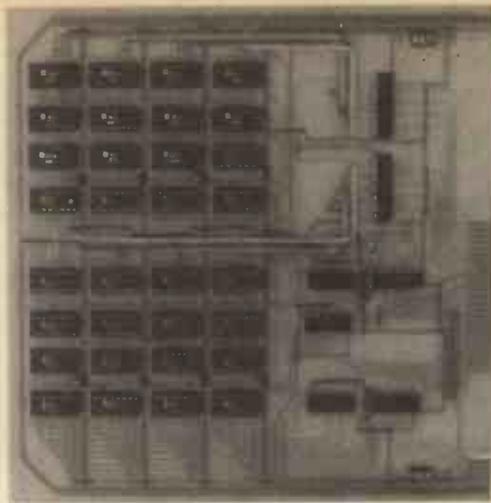
## THE SYSTEM IN USE

With BUG 2 installed in the system, what can be achieved? The VDU will produce a 16 line by 32 character display and on depression of the reset button will display an "\*" on the screen. Five 'commands' allow memory locations to be examined and altered, MPU registers to be displayed, user programs to be run and also allow the running of a program to be continued following software interrupt. The software should prove adequate for most experimenters in their early work and will of course allow the user to develop a more advanced monitor should this be felt necessary.



4K RAM board

Newbear users will almost certainly want to extend their system by adding RAM and an interface port of some sort and this is conveniently provided by the 77-68, MON1 board. Constructed as before on an 8in square single sided printed circuit board, this unit gives access to bulk storage media such as paper tape and cassette units and also provides 1K x 8 of RAM. The board also allows a 'bootstrap' ROM to be used to load a monitor from, for example, cassette tape, into the system. In practice this allows the user to develop his own monitor or monitors which he can save on tape for subsequent easy reloading into the system. Serial communication is by means of the Motorola ACIA, the 6850, and provision is made for two such devices on this one board, in addition to a variable baud-rate generator (crystal controlled). Both V24 and current loop interfaces are provided, offering interfaces to most serial driven peripherals such as cassette recorder interfaces, teletypes etc.

In practice the 77-68 MON1 board might be used in the following fashion. With the Newbear 'BOOT' ROM installed in its socket on the board, a previously-punched monitor is boot-strapped into RAM from a paper tape reader. The monitor could contain 'CUTS' input-output software allowing access to recorded software via an ACIA port and a 'CUTS' interface, and with this software loaded into the system, it may be modified, run etc., using the VDU as a man/machine interface. Newbear provides a listing of 'DUMP', allowing the user to off-load software to, say, a paper tape punch for subsequent re-use. Clearly this board turns the 77-68 system into a very versatile and powerful processor capable of supporting a variety of hardware peripherals and of running relatively large programs.

Most constructors will aim for a basic system comprising the CPU, VDU and MON boards and when they have gained

experience of machine code programming, look for a way of operating in BASIC or some other high level language. This will require the use of more memory than is offered by the basic system and Newbear offer a 4K byte static RAM card (which many would consider as part of the basic system in any case), a 32K byte dynamic RAM card and a 16K byte EPROM card using 2708s. This range of memory cards is bus-compatible with the other 77-68 of course and will shortly be joined by a floppy disc interface board, offering a good range of memory types to suit all tastes.

## IMPRESSIONS

The 77-68 system has been thought out to allow low price 'start-up' costs while at the same time offering a wide range of bus-compatible boards which build into a comprehensive processor system. The quality of the hardware supplied is excellent. The only constructional problems encountered were very minor in nature—under-size p.c.b. drillings for instance were encountered on a number of occasions. The documentation supplied is clearly written although it would be helpful if a description of the overall system existed which could be studied before boards were bought to allow each user to determine exactly which way his system was going to grow.

Purchasers of 77-68 VDU systems automatically become members of the '77-68 User Group' which circulates a quarterly Newsletter which allows users to share software and hardware information. In addition lists of members are circulated and the formation of local groups is encouraged—activities designed to assist newcomers, in particular to microprocessors, to get their first system 'up and running'.

To summarise the above points, Newbear have put together a thoroughly practical system suitable for amateur or professional for a first system.

# MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas often come from readers working on their own systems, and payment will be made for any contribution featured.

## EIGHT EIGHTS PROBLEM

THIS MONTH'S Micro-Bus begins with a challenge for all owners of the Science of Cambridge MK14 microprocessor system, and a chance to win a kit. A program for the MK14 is given in Fig. 1 and with this program running it is possible, by pressing the keys on the keyboard in a certain order, to get eight '8's lit up on the display. Only the correct sequence of key presses will give this result. Alternatively you may like to try to solve the problem from the program listing (Fig. 1). Either way, the problem is extremely tantalising until you discover the rule governing the operation of the keys.

The *Eight Eights* program occupies locations OF18 to OF47 in the MK14's memory. Enter it as usual, either from the listing or from the hexadecimal dump in Fig. 2, and then execute it at OF18. The display should then go blank except for one '8' in the rightmost digit position; you can then use any of the number keys 0-F to try to solve the problem. Do not press ABORT or you will have to re-enter the last eight bytes before running the program again.

```

; EIGHT EIGHTS PROBLEM
;
OF18 C484 BEGIN: LDI X'84
OF1A 33 XPAL 3
OF1B C40F LDI X'OF
OF1D 36 XPAH 2
OF1E C401 BACK: LDI 1
OF20 37 XPAH 3
OF21 01 XAE
OF22 C440 RIGHT: LDI X'40
OF24 32 XPAL 2
OF25 C47F LDI X'7F
OF27 E280 XOR -128(2)
OF29 CA80 ST -128(2)
OF2B 3F SHOW: XPPC 3
OF2C 90FD JMP SHOW
OF2E 03 SCL
OF2F C402 LDI 2
OF31 78 CAE
OF32 94EE JP RIGHT
OF34 C601 LD @1(2)
OF36 98FC JZ LOOP
OF38 32 XPAL 2
OF39 60 XRE
OF3A D40F ANI X'OF
OF3C 98E4 JZ RIGHT
OF3E 90DE JMP BACK
OF40 0000 .BYTE 0,0,0,0,0,0,0,0
0000 .END
    
```

Fig. 1. Program for the SC/MP micro which sets up the Eight Eights problem described in the text

## HEX DUMP

```

OF18 C4 84 33 C4 OF 36 C4 01
OF20 37 01 C4 40 32 C4 7F E2
OF28 80 CA 80 3F 90 FD 03 C4
OF30 02 78 94 EE C6 01 98 FC
OF38 32 60 D4 OF 98 E4 90 DE
OF40 00 00 00 00 00 00 00 00
    
```

Fig. 2. Listing of the bytes to be entered to run the Eight Eights program

## WIN A KIT

Readers sending in the shortest sequence of key presses that will light up eight '8's on the display can win one of the MK14 VDU interfaces that have been kindly donated as prizes by Science of Cambridge. The first three correct entries opened on the 31st August will each receive a kit, and entries should be posted to: *Micro-Bus Problem*, Practical Electronics, Westover House, West Quay Road, Poole, Dorset BH15 1JG. The next Micro-Bus will reveal the solution to this problem, and give a full explanation of how the program works.

## MICRO DRIVES A TRAIN

The speed and direction of an electric motor can be controlled by a microprocessor, and by way of illustration a simple program is presented here which can vary the speed and direction of movement of an electric model train. As it stands, the train can be set to one of eight forward or reverse speeds, but the program could form the heart of a more complex system which incorporated the switching of signals and points, and the use of sensors to detect the train's position on the track.

The program was developed and run on an Acorn microprocessor system which makes an ideal controller for such applications. Control of the train is from the Acorn's keyboard; the keys 0-7 give forward motion, and 8-F give reverse. The number pressed determines the speed; 7 and F give maximum speed in forward and reverse respectively, and 0 or 8 stops the train.

## OPERATION

The polarity of the power applied to the motor is controlled by a bridge circuit of power transistors; see Fig. 3. The transistors are not critical, and the ones shown, chosen for economy, will drive several amps. Two

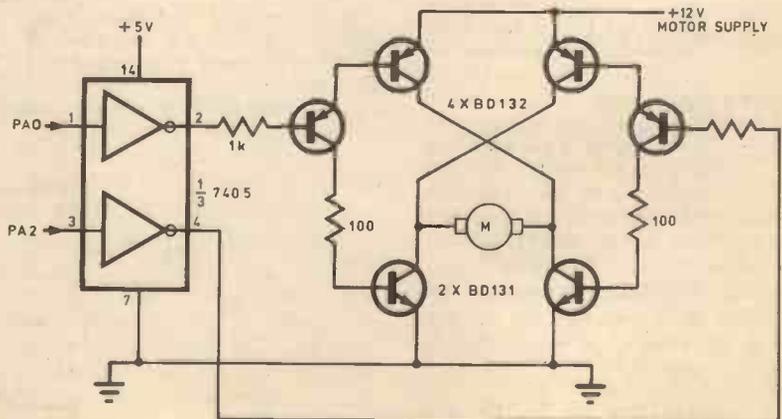


Fig. 3. Circuit which provides control of an electric motor from two logic-level lines

gates in a 7405 package (a hex inverter with open-collector outputs) act as buffers between the bridge circuit and two lines from the Acorn's RAM I/O device, PA0 and PA2. With both lines high, or both lines low, the voltage across the motor is zero. If one line is taken high the motor is connected between the power rails, and the polarity depends on which line is high.

Control of the motor's speed is achieved by pulsing the power to the motor rapidly on and off, and varying the ratio of on-time to off-time. This control is performed by software timing.

### MOTOR CONTROL PROGRAM

The motor controller program, shown in Fig. 4, requires some understanding of how the Acorn's keyboard is connected. The keyboard uses six bits of port A in the RAM I/O chip addressed at \$0E00. The lower three bits, PA0-PA2, are decoded to enable one of the eight keyboard columns. The next three bits, PA3-PA5, are inputs from the keyboard rows. Each key, when pressed, makes a connection between a row and a column; keys 0-7 correspond to PA5 low, and keys 8-F correspond to PA3 low. When no key is pressed all three rows are high.

```

MODEL TRAIN CONTROLLER
WAIT      =%FPCD      DELAY ROUTINE
USERIO    =%D920      SPARE RAM I/O CHIP
KYBDIO    =%E020      KEYBOARD/DISPLAY I/O
DIRN      =%D00D      FOR DIRECTION CODE
SPEED     =%D020      FOR SPEED CODE 0 - 7

0000
0210 A9 07 SETUP STA *%S0210 PA0-PA2 AS OUTPUTS
0212 8D 22 0E LDA KYBDIO+2 DATA DIRECTION
0215 8D 22 09 STA USERIO+2 REGISTERS.
0218 A4 20 RESET LDY SPEED
021A A9 00 LDA #0 TURN MOTOR OFF
021C 8D 00 09 STA USERIO D COUNTER
021F A2 07 LDX #7
0221 8E 20 0E SCAN STX KYBDIO SELECT KEYBOARD COLUMN
0224 AD 20 0E LDA KYBDIO READ FOR ROWS
0227 29 3F AND #%F3 MASK TOP BITS
0229 C9 38 CMP #%38 KEY PRESSED?
022B 90 07 BCS NOKEY
022D 4A LSR MOVE ROW
022E 4A LSR BITS
022F 4A LSR DOWN.
0230 85 00 STA DIRN SAVE AS DIRECTION
0232 86 20 STX SPEED AND UPDATE SPEED
0234 CA NOKEY DEX SCAN 8 TIMES
0235 30 #1 BHI RESET
0237 C8 BVC
0238 C0 08 CPY #8 ENABLE MOTOR?
023A D0 05 BNE MISS NOT YET.
023C A5 00 LDA DIRN
023E 80 20 09 STA USERIO SWITCH MOTOR ON
0241 20 CD FE NESS JSR WAIT DELAY
0244 4C 21 02 JMP SCAN LOOP.

.END


```

Fig. 4. Program for the 6502 micro which, with the circuit of Fig. 3, varies the speed and direction of rotation of an electric motor

Bits PA0 and PA2 of the spare RAM I/O chip, which is addressed at \$0900, are used to control the motor. When run, the program first configures bits PA0-PA2 of both RAM I/O chips as outputs. It then performs the SCAN routine eight times, for values in the X register of from 7 down to 0. The SCAN routine selects a keyboard column and checks for keypress in that column. If a key has been pressed it shifts down the row bits PA5 and PA3, one of which will be low, to coincide with the lines PA2 and PA0, and saves them at DIRN. It also updates SPEED with the current value of X.

The value of SPEED determines for how many of the seven time slots the motor is turned on, see Fig. 5. A delay, provided by the WAIT routine in the Acorn monitor, is inserted at the end of the SCAN loop. The program works without this, but the train motor acts as a loudspeaker coil and, due to the high frequency of the pulses applied to it, emits an audible whistle which is rather disturbing!

Fig. 5. Timing diagrams showing how the speed of the motor is varied by altering the point in each cycle at which power is applied

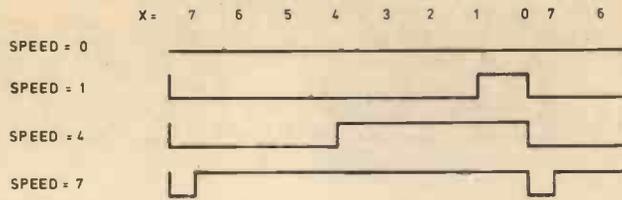

EG153

### AN INSIGHT INTO MICROPROCESSORS

Many people seek to gain an introduction to microprocessors by building one of the excellent kits currently available; but running programs on a kit still leaves one fairly mystified about the internal operation of the micro. The problem is that the microprocessor executes many thousands of instructions every second, and a whole program can be executed in an instant.

The circuit to be described provides one solution. Designed for use with SC/MP microprocessors (the INS8060), it makes it possible to execute programs one cycle at a time, suspending execution between cycles so that the status of the micro can be examined. In addition to giving an insight into the operation of a micro that is not gained by simply running programs on it, the single-cycler also make it a simple matter to fault-find microprocessor kits.

### SINGLE-CYCLER DESIGN

The single-cycler was designed by Nick Toop, whose cassette interface appeared in the October 1978 Micro-Bus, and though intended for use with a Science of Cambridge MK14, it should work with any SC/MP-based system. The circuit, shown in Fig. 6, uses two TTL integrated circuits and its operation is controlled by two push buttons, of which one should have changeover contacts and can be a biased toggle-switch. The single-cycler is connected to the MK14 by five wires, and there is no need to make any changes to the MK14 itself. The connection points are as follows:

Wire	SC/MP pin no.
+5V	40
NWDS	1
NRDS	2
NHOLD	6
0V	20

There are more convenient points on the upper side of the MK14 where connection can be made, and the photograph of the prototype shows these.


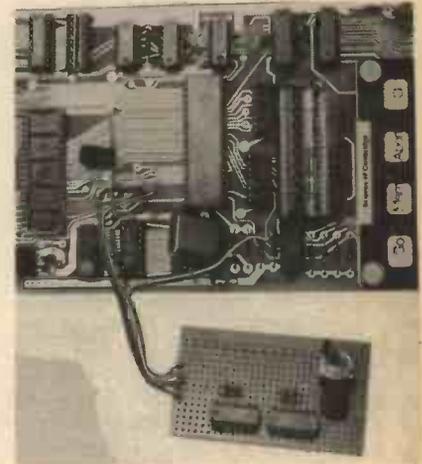


Fig. 7. The Single-Cycler circuit described in the text attached to an MK14 microprocessor kit

Fig. 6. Circuit of the Single-Cycler which clarifies the operation of a SC/MP-based microprocessor system

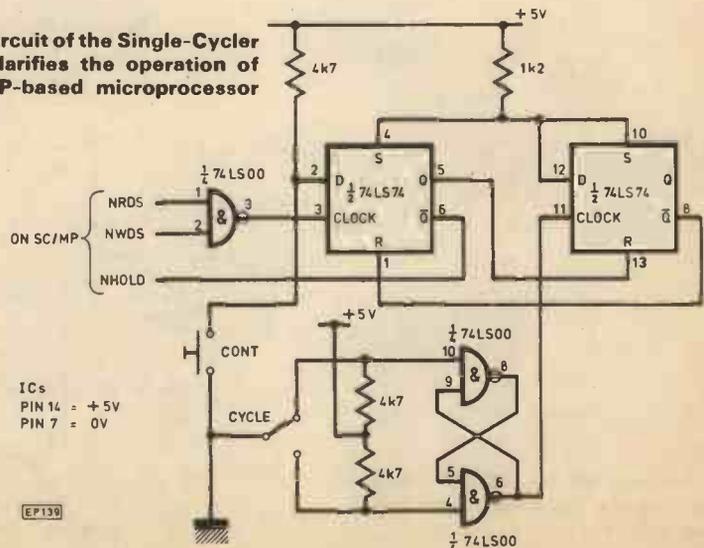

EP139

## OPERATION

Instructions executed by a microprocessor consist of a number of read and write cycles, during each of which the micro accesses the memory (or I/O devices). Every instruction must have at least one cycle—the *instruction fetch*—during which the micro reads the instruction op-code from memory. During this cycle the address of the instruction appears on the address bus, and the instruction itself appears on the data bus. Some SC/MP instructions have as many as four read/write cycles; for example, *increment-and-load (ILD)* has three read cycles (instruction fetch, operand fetch, and read data) and one write cycle (write incremented data). The number of read and write cycles for any particular instruction is fairly obvious from what it does, and a full list can be found on pages 30-31 of the MK14 manual (page 42 in the new manual).

The SC/MP micro signals a read cycle by taking NRDS low, and a write cycle by taking NWDS low. The single-cycler circuit of Fig. 6 works by taking NHOLD low whenever either of these lines goes low; this halts the micro in the middle of the cycle, leaving the address and data for that cycle on the buses so their state can be interrogated. Pressing the CYCLE switch releases NHOLD, and the micro runs until the next read/write cycle is reached. For continuous operation the CONT switch is held down, and the CYCLE switch pressed once to start execution; releasing the CONT switch at any time will halt the micro in the next read/write cycle.

Note that the operation of this single-cycler circuit is quite different from the operation of the single-step facility described in the MK14 manual. Whereas the single-step circuit just generates an interrupt so that control is transferred to the monitor program after each instruction is executed, the single-cycler actually stops the micro between cycles.

Old Monitor (SCHPEB)					
Address lines	Data lines	NRDS	NWDS	Comments	
001	CF	low	high	Instruction fetch	ST @ (3)
002	7F	low	high	Disp. for instruction	
77F	00	high	low	Store data to RAM	
003	90	low	high	Instruction fetch	JMP
004	1E	low	high	Disp. for jump	
023	C8	low	high	Address jumped to.	

Revised Monitor (SCIOS)					
Address lines	Data lines	NRDS	NWDS	Comments	
001	90	low	high	Instruction fetch	JMP
002	1D	low	high	Disp. for jump	
020	C8	low	high	Instruction fetch	ST
021	DC	low	high	Disp. for instruction	
7FD	00	high	low	Store data to RAM	
022	40	low	high	Instruction fetch	LD.

**Table 1. The results expected when single-cycling through the first few instructions of the old and revised MK14 monitors**

## FAULT-FINDING WITH THE SINGLE-CYCLER

The Single-Cycler should be used in conjunction with some means of reading the state of the address, data, and NRDS/NWDS lines, such as logic probe, oscilloscope, or voltmeter. The following steps illustrate how to fault-find a non-functional MK14:

(a) Attach the Single-Cycler circuit as described above, and press the RESET button on the MK14. This should cause pin 7 of the SC/MP, NRST, to go low.

(b) Release RESET and check that the clock, pin 38, is working. Verify that all the address lines are tri-stated (neither high or low). Data lines D4-D7 should also be tri-stated, but D0-D3 will be pulled high by the resistors R12-R15. NWDS and NRDS should also be tri-stated. Any departure from this indicates a fault, probably a short between two adjacent tracks on the printed-circuit board.

(c) Now press the CYCLE switch once. The SC/MP should then be outputting the address X'001; in other words A11 to A1 should be low and A0 high. The cycle is a read cycle so NRDS should be low, and the data lines should be reading the first instruction in the monitor, which is X'90 for the old monitor X'CF for the revised monitor.

(d) By repeatedly pressing CYCLE one can single-cycle through the monitor program, at each stage comparing the observed states of the address, data, and NWDS/NRDS lines with the results expected from the monitor listing. Table 1 shows the first five cycles for the old and revised MK14 monitors. Departures from this table will point to shorts, faulty components, or incorrect PROMs.

(e) To get into the keyboard and display routine, KYBD, continuous run for a while by holding down CONT, pressing CYCLE, and releasing CONT. One can then single-cycle through the KYBD routine to check the display circuitry. One display digit should be enabled at a time, and every 26 operations of the CYCLE switch should move to the next display digit.

## IMPROVEMENTS

It is possible to incorporate this circuit into a more sophisticated device that will give a continuous display of the state of the address, data, and NWDS/NRDS lines, thus making it unnecessary to test each line in turn. It is also possible to make the circuit single-cycle within limited address ranges, such as only in the user RAM so that it is possible to cycle through one's own programs. But even the simpler circuit just described, whether it is used to examine the operation of a working microprocessor system or to repair a faulty one, should prove a valuable addition to a micro.



# Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS. Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

## PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for.....(amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss

ADDRESS

POSTCODE

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53626. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

# Semiconductor UPDATE...

FEATURING INS 8295 MK 4816  $\mu$ A78MGU1C

R. W. Coles

## NIBL ROM

Devotees of the SC/MP microprocessor (used in the MK 14 and Scrumpl micro kits) may already have heard of NIBL.

NIBL stands for National Industrial BASIC Language, and it started life as an adaptation of the original Tiny BASIC as described in the first issue of the now famous "Dr. Dobb's Journal of Computer Calisthenics & Orthodontia." This version of BASIC, like most other Tiny BASICs, has *integer only* arithmetic with an effective 16-bit precision, but it also sports a few features not found on the others, including a DO-UNTIL statement in addition to the usual FOR-NEXT.

The "Industrial" part of NIBL refers to the SC/MP manufacturer's conviction that many control programs used in industrial situations could be written in a high level language such as BASIC, rather than in the more usual machine code or assembly language form.

The advantages of this sort of approach are obvious. Programs to control a central heating system or a machine tool become lists of easy to write English-like statements which can be readily understood by almost anyone, and programs also become more portable, since one BASIC is very much like any other.

The disadvantages stem mainly from the fact that NIBL is an Interpretive language which requires a large "Interpreter" program to be resident in the system as well as the user program itself.

Each of the concise NIBL statements has the effect of calling a large machine language subroutine in the Interpreter at run time, leading to inefficiencies and a drastic reduction in speed compared with an assembly language equivalent.

The resulting choice is simple. Either you stick to assembly language and get compact code which runs fast but takes a great deal of time to write and debug, or you use a language like NIBL which means your programs run slower but are much easier and quicker to write.

So much for using NIBL for control applications, but what about hobby use? Well, you can use NIBL anywhere you would use a standard Tiny BASIC, for games and other purposes, and it would certainly add a great deal to any existing machine code system.

The best news of all is that National have now put the NIBL interpreter into a single, cheap, 4K by 8 masked ROM which will go into a 24-pin socket. The new ROM is coded **INS 8295** and is intended for use in an 8060 SC/MP system with at least 2K of RAM available.

Being a high level language, NIBL requires an alphanumeric communication channel, and the interpreter in the 8295 contains a software driver for a 110 baud ASCII terminal connected to the SC/MP SENSE B and FLAG 0 lines.

I should think that an SC/MP system equipped with NIBL is one of the cheapest ways possible into the world of the Home Computer, so why don't you try it, all you SC/MP fans?

## BYTE RAM

One nifty way to get the 2K bytes of RAM you need for an SC/MP based system using NIBL could be to buy a *single MK 4816*.

The MK 4816 from Mostek is a wonderful new RAM chip which eats and spits out data, not in mere *bits* but in whole *bytes*.

Now for the bad news: The MK 4816 is dynamic (groans). Now the good news: The

MK 4816 has on-chip refresh! (Cheers). Yes folks, someone has finally done away with all that horrible address multiplexing circuitry and those nasty RAS and CAS strobes and refresh clocks by organising a 16K bit dynamic RAM into a sensible byte-wide format, and putting all the necessary support circuits right there on the chip.

To the outside world, the MK 4816 can appear just like a static RAM, but inside it's dynamic, so you get all the advantages of dynamic chips with none of the disadvantages.

One of the most striking advantages is the low power consumption of only 150mW when active, but that's not all, because there is also a low power standby mode when the chip is de-selected which reduces consumption to just 25mW (that's only 5mA from a 5V supply so you could power your RAM from batteries during a power loss if you needed to preserve valuable data.)

The MK 4816 comes in a 28 pin package where the lower 24 pins (3-26) conform to the standard 24 pin ROM/PROM format so that sockets can be used for either RAM or ROM as required by a particular system.

The MK 4816 is just becoming available, but in the future we can expect to see more chips following the lead it has set, including a 4K by 8 monster from Zilog!


## QUADRUPLED

Voltage regulator circuits are old hat these days, and not the stuff of which headlines are made. Development continues however, and there is now such a range of regulator chips to choose from that it is important to keep up to date so that you can make the right choice for any new application that needs a stable d.c. supply voltage.

Most of the glamour seems to lie with the fixed voltage types, and their ever increasing current capability, but coming along strongly are the three terminal adjustable types which are good for the hobbyist's spares box because they can be used for any power supply application which takes one's fancy.

They can be a bit pricey though, and Fairchild have tackled this problem with a whole new family of *four-terminal* adjustable regulators which come in low cost plastic TO202 packages.

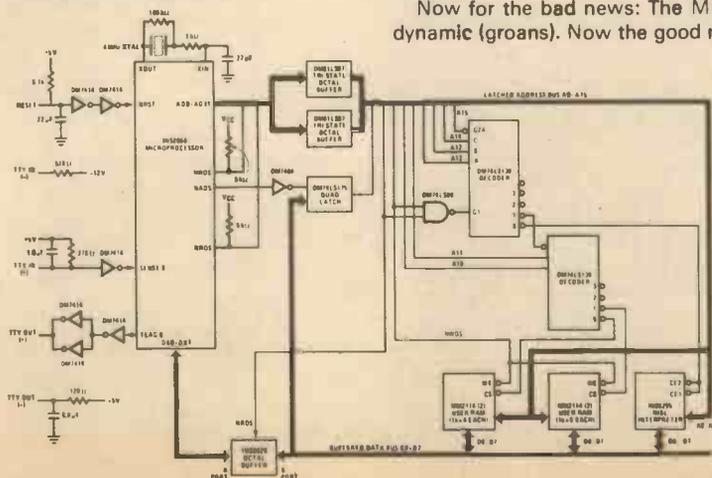There are 0.5A and 1.0A, positive and negative versions, and typical advice codes are  $\mu$ A78MGU1C for a 0.5A positive regulator and  $\mu$ A79GU1C for a 1.0A negative regulator.



# INGENUITY UNLIMITED

A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.


Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

## LIGHTNING CHESS TIMER

An interesting and lively variation of the ancient game of chess is lightning chess. The rules for this game are very similar to those of ordinary chess, the main difference being the short time allowed each player to make his move (usually five seconds).

A lightning chess timer should give a distinct buzz (or bleep if a speaker is used in place of a buzzer) at regular intervals. The duration of each bleep should be about a quarter of a second while the interval between bleeps must be variable, and range up to fifteen seconds.

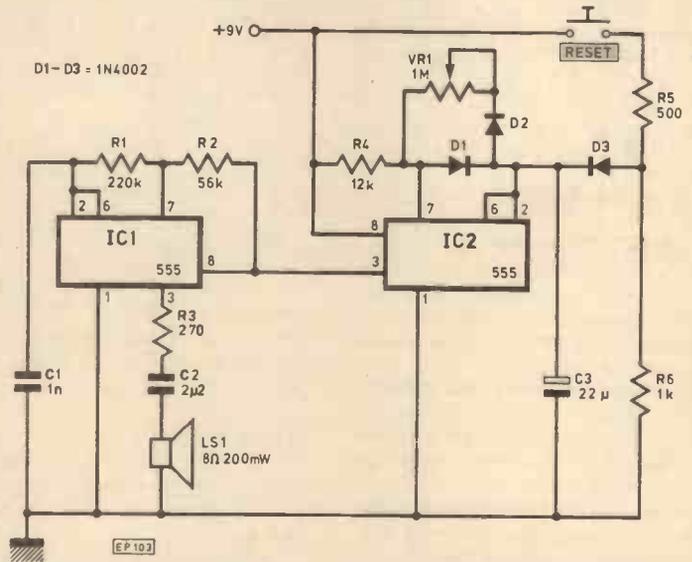The circuit employs two 555 timers, both operating in a free-running mode. IC1 acts as an audio oscillator, delivering a frequency of about three kilohertz to the speaker. IC2 switches IC1 on and off at predetermined intervals.




A reset facility is included whereby the timer may at any time be reset at the push of a button. This allows a slightly different version of lightning chess to be played. Every player presses the reset button after he has played his move, so that when the

timer does bleep it means that the player whose turn it was to move has overstepped his time limit and he loses the game.

Y. H. Diamant,  
Zaria,  
Nigeria.


The 7400 quad NAND gate is often used as an astable multivibrator but has poor starting characteristics, usually requiring a "spike" on the supply line at switch on to initiate oscillation. This simple circuit uses the two spare gates in the package plus one extra resistor to ensure the circuit has positive self start characteristics.

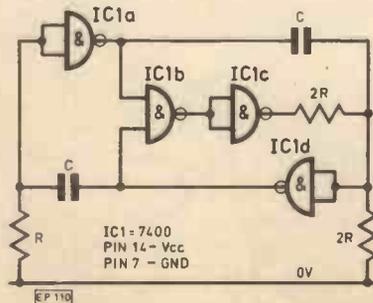R. D. Homerstone,  
Daventry,  
Northants.



## TTL OSCILLATOR

## D.C. RINGING FOR INTERCOMS

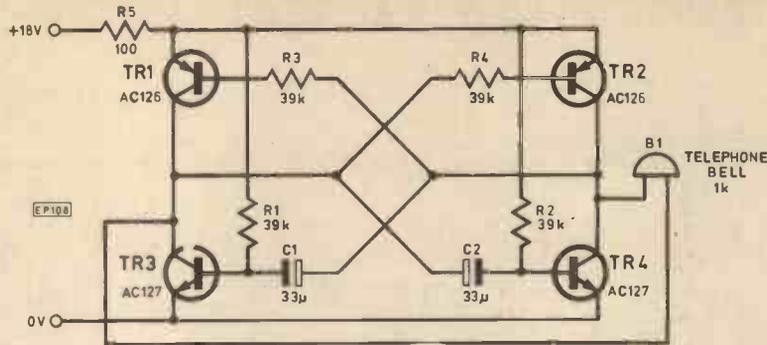

THE circuit shown is suitable for operating a polarised telephone bell from an 18V d.c. power supply (*on no account should P.O. systems be interfered with*).

A low impedance output of approximately 35V peak to peak is obtained without the use of transformers. The circuit is basically an astable multivibrator formed by R1, R2, C1, C2, TR3 and TR4. However, the normal collector load resistors have been replaced by an active load, namely TR1 and TR2. TR1 base is fed via

R3 to the collector of TR4. Consequently TR1 is always on when TR3 is off and vice versa. At each side of the circuit there now arises a push-pull output. By utilising both of these outputs and feeding them to the telephone bell, the output voltage is approximately double that of the supply voltage. R5 simply limits any excessive current surges from the power supply during transition of switching states when all transistors are partially on.

This circuit may be built on to a small


piece of tag strip, placed inside a telephone, and inserted into the two existing bell wires. The telephone may now be treated as having a d.c. operated bell and the basis for a home intercom using d.c. ringing. The relatively low voltage required for operating the telephone bell may be derived from the power supply feeding the speech circuits.

R. A. Sudron,  
Leeds.
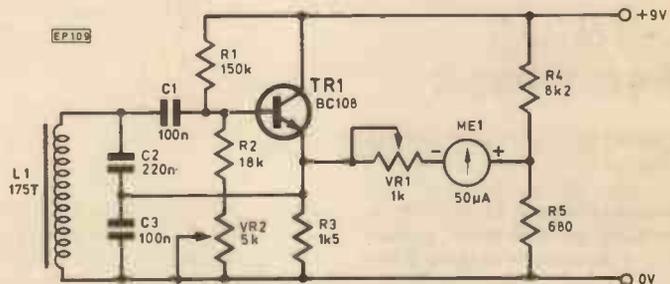
## SHORTED TURNS DETECTOR

THE accompanying circuit shows a shorted turns detector of high sensitivity which may be built at low cost. The detector is based on a standard Colpitts oscillator.

Initially TR1 is biased into conduction by R1, R2 and VR2. As the oscillations build up rectification occurs at the base/emitter junction resulting in increased emitter current and therefore increased voltage across R4 if oscillations are damped by a shorted turn placed around



L1, it follows that the voltage across R3 will now fall towards its quiescent value. This change of voltage is indicated by a 50µA meter, zero adjustment being performed by VR2.

VR1 is adjusted for full scale deflection with a shorted turn placed around L1. L1


is not critical, consisting of 175 turns of 30 s.w.g. enamelled copper wire close wound on a piece of 1/4 in. diameter ferrite rod.

R. D. Homerstone,  
Daventry,  
Northants.
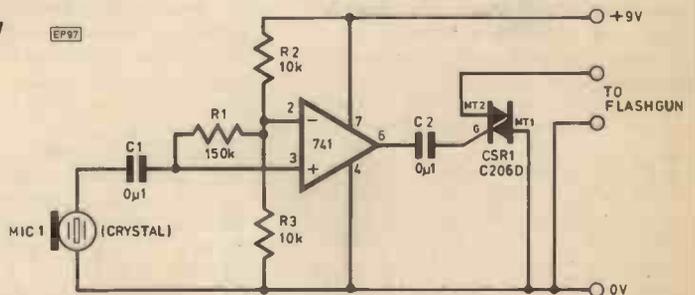
## SOUND OPERATED FLASH

THIS very simple circuit will fire a photographic flashgun of any polarity, because of the use of a triac rather than a thyristor.

The output from the crystal microphone is coupled by C1 to the comparator, IC1. Positive input bias is supplied by R1 which, due to the input bias voltage drop, determines the input sensitivity. With the values shown this is about 30mV peak, although it can vary considerably depending on the characteristics of the op-amp.




When a sound is made near the microphone, the output of IC1 swings between the supply rails at the frequency of the input. On the first negative going excursion, the triac switches on firing the flashgun.

The triac will remain on until the flash is complete, at which time the circuit is ready to supply another flash trigger.

P.R Williams,  
Stevenage, Herts.

# METER FOR ELECTROLYTICS

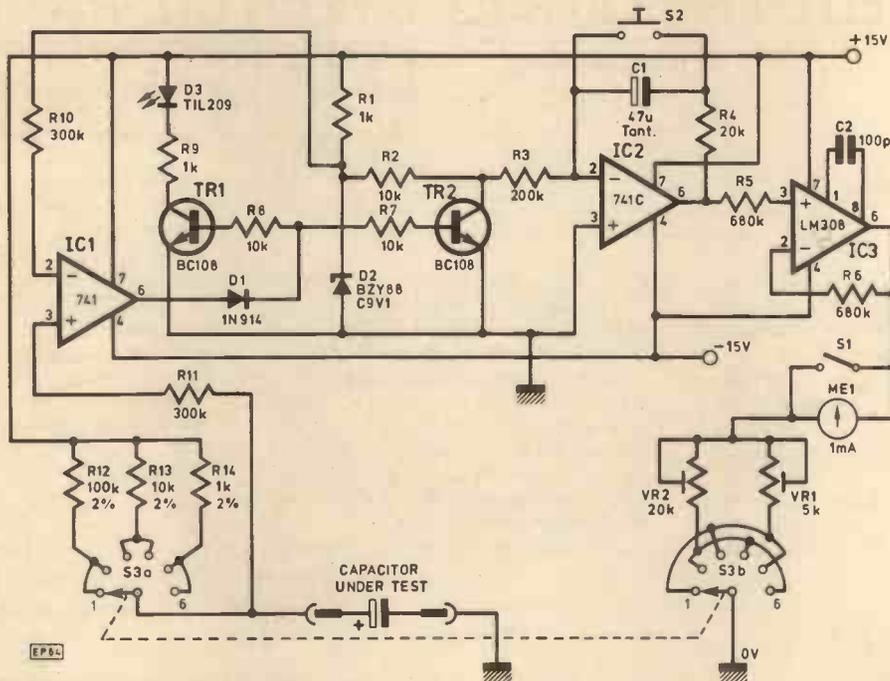

**C**APACITORS of values up to 10,000µF can be measured with this instrument, and 6 ranges are available as follows:

- |       |   |            |
|-------|---|------------|
| Range | 1 | 0-30µF     |
|       | 2 | 0-100µF    |
|       | 3 | 0-300µF    |
|       | 4 | 0-1,000µF  |
|       | 5 | 0-3,000µF  |
|       | 6 | 0-10,000µF |

The smallest value that can be measured accurately depends on the resolution of the meter used. No new meter scale need be made since the scale is linear and forward-reading, this simplifies construction.

There is one slight disadvantage with this instrument, this being that the capacitor under test may have over 10V across its terminals, and so low voltage capacitors may be damaged.

Before the capacitor under test is connected into circuit, the non-inverting input of IC1 is connected to the positive rail via a resistor. IC1 acts as a comparator, its inverting input being connected to a 9.1V Zener reference. The output of IC1 is high in value, about +13V. TR1 and TR2 are thus turned fully on, TR1 lighting the l.e.d. D1 protects the base-emitter junctions of the transistors from reverse breakdown. IC2, which is connected as an integrator,

is fed with the output of TR2. When TR2 is turned off, IC2 produces a negative-going ramp output, this is buffered by IC3 and fed to ME1. When a capacitor is connected, the voltage of the non-inverting input of IC1 is lowered to zero, IC1 thus switches and TR1 and TR2 turn off. The l.e.d. extinguishes, and 9V is fed to the integrator. The negative-going ramp produced moves the needle of ME1, linearly with time, hence time is recorded on the meter.

Meanwhile the capacitor under test is charging up. When it reaches 9V, the comparator is switched and the integrator is stopped. The time for all this to happen is measured on ME1, and is approximately equal to the time constant of Cx and its series resistor, R12, R13 or R14.

Tolerances in the circuit, especially C1, are large, so the meter is calibrated using a capacitor of known value by varying VR1 and VR2. When the timing process has finished, D3 lights, showing that the capacitance can be read.

C1 is a low-leakage tantalum capacitor. In practice, however, its leakage is apparent since the meter needle does not remain at a steady value after the timing period. To counter this, current is fed into the capacitor when TR2 is turned off. This

current is about 1µA. Since R3 is 200kΩ, then to counter the leakage the saturation voltage of TR2 needs to be 0.2V.

If needed, R7 can be adjusted to cancel the leakage exactly. The prototype needed a value of 10kilohm for R7.

R4 limits the current from IC2 when S2, a reset button, is depressed. The internal resistance of C1 is such that S2 needs to be closed for a few seconds to discharge it completely.

The power supply should be at least ±12V, and no more than ±15V. The prototype employed a power supply with two regulator i.c.s. S1, which shorts the meter to prevent damage when not in use, is ganged to switch the power supply.

D. P. Akerman,  
Coventry.

# Simply ahead!

**HIGH PERFORMANCE MODULAR UNITS  
BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE**

**30 WATTS R.M.S.  
INTO 8 OHMS**

**I.L.P. POWER AMP  
MODEL HY50**

**PROFESSIONAL  
FINISH**

**ENCAPSULATED FOR  
OPTIMUM THERMAL  
STABILITY**

**EXTRA RUGGED  
CONSTRUCTION**

**SHORT/OPEN  
PROTECTION**

**ONLY 5 SIMPLE  
CONNECTIONS**

**NO EXTRA HEAT  
SINK NECESSARY**



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build or up-grade a hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practise or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make HY50 the ideal all-purpose quality power amp – and it is unconditionally guaranteed for five years. Tens of thousands are in use throughout the world.

**... and a spec that means just what it says!**

Encapsulated power amp with integral full-rated heatsink.  
Input – 500mV  
Output 30 watts RMS/8Ω  
Load Impedance – 4 to 16Ω  
Distortion – 0.04% from 100mW to 25 watts at 1KHz/8Ω  
Supply Voltage – ±25V. Size 105 x 50 x 25mm  
Inc. V.A.T. and postage in U.K.

**£8.15**

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership for I.L.P. Now we have up-graded output ratings and down-graded prices to bring I.L.P. within easier reach of all who want the best.

**New production techniques enable us to reduce prices by an average of 20%, making I.L.P. a better buy than ever. Prices subject to amendments if VAT rate is changed.**

**Guaranteed 7 days despatch on all products**

**USE OUR FREE POST SERVICE** for sending your orders, requests for information sheets etc. Simply address envelope.


**NO STAMPS REQUIRED.**



**FREEPOST 2**  
Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP  
Phone (0227) 54778 Telex 965780
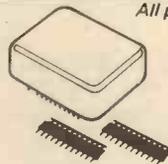
## OTHER UNITS IN THE RANGE


*All prices inc. V.A.T. & Postage in the U.K.*



### HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps. and P.S.U.'s. In a single pack, needs external pots and switches. Multi-function equalization. 5 inputs. High overload margin. Active tone controls, 500 mV out. Distortion at 1 KHz – 0.01%.


Two connect easily for stereo. **£5.22**

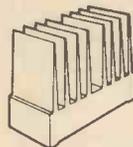
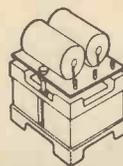
### THE POWER AMPS

*With heatsinks, full load line and thermal protection. Distortion typically 0.05% at 1 KHz.*

HY120 60 Watts RMS/8Ω 114 x 50 x 85mm **£16.42**  
HY200 120 Watts RMS/8Ω 114 x 50 x 85mm **£19.92**  
HY400 240 Watts RMS/4Ω 114 x 100 x 85mm **£29.89**



### THE POWER SUPPLY UNITS

*(Split line outputs to suit I.L.P. power amps and HY5)*

PSU60 for 1 or 2 x HY50 **£9.11**  
PSU70 for 1 or 2 x HY120 **£14.70**  
PSU90 for one HY200 **£14.70**  
PSU180 for one HY400 or 2 x HY200 **£24.80**

*Information sheets on application – Use our FREEPOST Service.*

## ★ NOW-PRICES DOWN BY 20%

Please supply .....  
Total Purchase Price .....  
I Enclose Cheque  Postal Orders   
Please debit my Access/Barclaycard Account number .....  
Name .....  
Address .....  
Signature .....

Reg. Bus. No. 1032630 Eng.

FP 2/7



**P. Dinsdale**

# Solders & Soldering

**S**OLDERING is probably one of the aspects of this hobby to which the amateur radio or home electronics enthusiast gives least consideration. Applying a hot iron to a soft silvery coloured metal, which then melts and flows to form a joint is such a straightforward process that beyond taking a few simple precautions, for example, avoiding dry joints, not too much concern needs to be expended. It is this reliability in the formation of mechanically and electrically sound joints that has assured that soldering is still an accepted joining technique used by the enthusiast and by the electronics industry. The efforts of soldering equipment manufacturers have made sure that for the user, soldering remains a straightforward technique, despite more obvious advances in other areas of electronics and the increasingly stringent demands being placed on the production of electronic assemblies.

## DEFINITION

Before discussing solders and soldering methods in detail it might be helpful to outline some of the basics. Soldering (sometimes known as soft-soldering) has been defined as the joining together of two metals using a low melting temperature tin-containing alloy as the filler metal. The melting temperature of this filler metal (the solder alloy) is usually considerably lower than that of its constituent elements, or than the melting points of the metals being joined. In fact the term "soldering" generally refers to processes taking place below 450°C.

Solders act in the following three ways:

- (a) Wetting the basis metal surfaces forming the joint.
- (b) Flowing between these surfaces by capillary action so as to fill the space between them completely.
- (c) Metallurgically bonding to the surfaces when solidified.

The surfaces to be joined should be perfectly clean in order to ensure that wetting, and subsequent metallurgical bonding can take place. Part of the job of the flux is to dissolve any oxide coating adhering to the basis metal. Wetting of the basis metal surfaces is of prime importance. The nature of the wetting action itself is quite complex and results from the mutual solubility of tin (the active constituent) in the liquid solder and in the substrate.

The primary requirement of soldered joints in electronics is to provide an electrically conductive path, but considerations of mechanical strength may also be relevant on occasions. Although the electrical conductivity of solder is only about 8 to 13% that of copper, the short conducting path through the solder in a joint does not normally have to be considered as adding significant electrical resistance to the circuit.

## SOLDER ALLOYS AND FLUXES

One of the most obvious characteristics of solders is that they are low melting point alloys; most of the commercially important solder alloys being fully molten below 250°C. It is also accepted that in general the higher the tin content of the alloy the better are its wetting properties.

A great many of the solder alloys in common usage are binary mixtures of tin and lead. The tin-lead mixture is known as a simple eutectic system. The eutectic is the composition of the binary mixture at which the two component metals solidify as a whole when the liquid is cooled, forming a solid solution. This point occurs at the lowest attainable temperature. In the tin-lead system the eutectic point occurs at the composition 62% tin – 38% lead, at a temperature of 183°C. At other compositions, particularly in alloys containing around 80% lead, the mixture has a wide temperature range over which it is neither completely molten nor completely solid; this is known as the "pasty" range. All tin-lead alloys will be partially molten at 183°C but only the 62% tin – 38% lead alloy, the eutectic alloy is fully molten at this temperature. For example, the commercially available 30% tin – 70% lead alloy is only fully molten above 255°C. The most commonly used tin-lead solders employed in electronic applications are 60% tin – 40% lead and 63% tin – 37% lead, of which both alloys are close to the eutectic composition and melt over temperature spans of 5 and 2°C respectively.

Sometimes up to 5% of antimony or silver may be added to tin or tin-lead mixtures to produce solders with slightly different properties. Such alloys may be useful in certain applications but may also introduce a number of undesirable factors, such as higher cost or deterioration in mechanical or wetting properties. Because of this they are only used when absolutely necessary. Tin-zinc solders are used for soldering aluminium, and alloys containing cadmium or indium may be employed when low melting point solder is required.

As already stated, for normal service in electrical and electronic applications, binary tin-lead alloys containing between 60 and 65% tin are chiefly used since they solidify at low temperatures over a short temperature range and, since they contain a high proportion of tin, have excellent wetting power, permitting short soldering times. This last factor is particularly important in industry where high production rates are necessary for economic operations. Sometimes such solder alloys are saturated with copper additions (around 1.5% copper) to reduce the corrosive attack by the solder on unclad copper soldering-iron bits. Tin-lead solders containing 50% or more lead are used for such applications as sheet metal assembly, copper plumbing,

automobile radiator manufacture, and repairing and shaping car bodywork.

It may be necessary in some instances for joints to retain their strength at temperatures above 100°C, and here alloys of tin with 5% antimony or 3.5% silver can be used. In contrast, at very low temperatures a 90% lead - 10% tin alloy should be used where strength and toughness is important.

In the increasingly important commercial thick film hybrid circuits employing palladium-silver conductive tracks, a 62% tin - 38% lead - 2% silver alloy is frequently used to prevent the silver-containing layer on the circuit from dissolving in the solder alloy. A tin-lead-indium-zinc solder has been formulated to reduce the risk of embrittlement when soldering onto thick gold coatings, and a 70% cadmium - 30% tin alloy has been employed for systems where stray e.m.f.s due to thermo-electric effects must be kept to a minimum.

### PHYSICAL TYPES OF SOLDER

Solder is manufactured in many different forms to meet the needs of particular applications. Perhaps the most familiar form for soldering with an electrically heated iron is that of solder wire, normally supplied in reels, in a range of diameters from about 0.7mm to over 5mm. These wires are manufactured by extrusion of the alloy followed by conventional cold drawing. Often there are one or more strands of rosin-based flux contained within the wire, introduced during the extrusion process. Normally the proportion of flux in the wire is around 3% by weight, and a number of flux cores are usually employed so that in event of a void in one of the cores there is sufficient flux available in other cores. The advantages of flux-cored solder wire include rapid flow of flux onto the joint when the wire is melted and quick melting of the wire on contact with the heated surface.

Solder paints, pastes and creams are made of finely divided solder particles suspended in a viscous flux together with a neutral carrying agent. Solder paints can be applied by brush or roller for tinning purposes. Pastes and creams, containing around 85% by weight of metallic solder, are applied by brush, syringe or spatula (in industry screen printers and automatic dispensers are also used) to the joint area to ensure exactly the right quantity of solder is employed. The viscous, tacky pastes readily stay in position and can act as temporary adhesives to hold components in place until the solder is melted.

In recent years the use of solder preforms has grown in the electrical and electronics industry and they are now available in a wide range of shapes and sizes, with or without flux cores. The types of preforms manufactured include washers, rings, discs, pellets and spheres as well as more elaborate shapes for more complex soldering jobs. Solder preforms are ideally suited to ap-

plications where a precisely controlled amount of solder needs to be applied to every joint, either by hand or automatic soldering.

Other forms of solder available include ingots, bars, sticks, sheet and foil strips, all of which are intended for different types of soldering jobs.

### FLUXES

Soldering fluxes are liquid or solid materials which when heated are capable of promoting or accelerating the wetting of metals by solder. Any flux used in a given application should provide a liquid cover to exclude air from the joint up to the soldering temperature and dissolve away any oxide on the metal surface or on the solder. It should also be readily displaced from the basis metal by molten solder, and any residues should be easily removable following the soldering operation.

In electrical and electronics applications so-called "non-corrosive" fluxes are mainly used. It is possible to use pure, natural rosin dissolved in proportions of 20 to 50%w/v in a suitable organic solvent such as isopropanol. The active constituents in such a flux are abietic acid and its isomers, which become mildly active at soldering temperatures. However, it is usually necessary to improve the fluxing power by adding small quantities of organic halide activators. These activated rosin fluxes are formulated so as not to give rise to corrosive products after soldering.

In the case of more difficult to solder non-ferrous alloys, organic acid and organic halide fluxes are used, and for soldering steels and other alloys in general engineering, highly reactive and corrosive zinc chloride fluxes are necessary.

### SOLDERING METHODS

Before undertaking soldering operations it is essential to assure that the surfaces to be soldered are perfectly clean. Some metals are more readily solderable than others; for example gold-, silver- and tin-coated parts normally display excellent solderability, copper and its alloys have quite good solderability, whilst aluminium can at best be regarded as difficult to solder. Whatever the substrate, it is necessary that the surfaces should be in a suitable condition for soldering. If soldering difficulties are encountered it may be that some sort of cleaning operation should be carried out before satisfactory joints can be obtained.


The surfaces should be free from all oil and grease. This consideration is of more importance for soldering in industry where quite elaborate degreasing procedures may be employed. Oxide films which form over a long period of time can be removed by using abrasive papers, although these should not be used for soft metals such as tin, as particles of abrasive may become embedded in the metal. Immersion in dilute acid may remove certain oxide and tarnish films.

### MANUAL SOLDERING

Before applying solder to a joint it should be considered whether it is necessary to prevent heat flowing into areas that have already been soldered, or to heat-sensitive components. Heat shunts can take the form of specially designed tweezers, although the judicious use of a pair of pliers during hand soldering can also form an effective heat shunt.

In all irons the key component is the bit; it is essential that the bit surface is wetted or "tinned" by the solder in order to encourage the flow of solder onto the joint. The bit stores heat

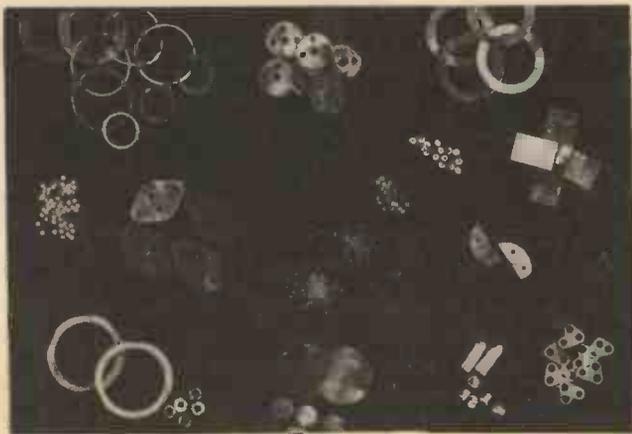**Solder preforms for various applications, which can be positioned prior to heating.**



and conveys it to the work, stores and delivers a minimal amount of molten solder to encourage heat transfer (the bulk of solder should be applied simultaneously with the soldering iron), and the bit should also be capable of removing surplus solder from the joint. The size of the bit and the power rating of the iron are related to the amount of heat to be supplied during each soldering operation and to the intended rate of working. Copper is the material used most frequently for bit construction as it combines good melting properties with optimum heat capacity and thermal conductivity. To prevent erosion of copper bits by solder, copper saturated solders, or iron or nickel plated bits may be employed.

During the soldering operation the pre-heated iron is held against the proposed joint, and the solder, usually in the form of flux-cored wire, is applied to the work close to the bit, where it should melt immediately. If sufficient solder has been applied it should completely penetrate and fill the joint gap. The time required to keep the bit on the work will depend on the nature of the joint and the characteristics of the iron. Gentle movements of the bit during soldering can assist rapid penetration of solder into the joint spaces. It is important to keep the bit properly tinned.

There are other, more specialised forms of manual soldering, used in industry in certain applications. These include such methods as radio frequency induction soldering, ultrasonic soldering and hot gas soldering.

### HIGH QUANTITY SOLDERING

In the industrial production of printed circuit boards it would be far too costly and time-consuming to make each individual joint manually using a soldering iron. It is necessary therefore to




Here, thick film hybrid circuits are being soldered, using a technique more recognisable by the home constructor—the soldering iron!

employ mass soldering methods in which large numbers of joints are made simultaneously by using the molten solder itself as the source of heat. The most common forms of mass soldering involve immersion in, or contact with, a molten solder bath. Another important advantage of mass soldering techniques is that they allow better control over all individual stages.

The simplest method of mass soldering is known as dip soldering. In this process the prefluxed assembly on which all the components have been mounted is lowered vertically into the solder bath sufficiently for the solder to spread and form all the joints, but not enough for the solder to flow over the top of the board. The temperature of the bath is maintained in the range 220 to 260°C for a 60% tin - 40% lead alloy. The solder surface is kept free of dross by a scraping mechanism which skims aside oxides and flux residues immediately before soldering takes place.

Perhaps the most widely used technique of mass soldering is that of wave soldering which solves the problem of maintaining a clean, bright solder surface by having the solder in continuous motion. In this process the circuit board, mounted on a conveyor, moves horizontally across the crest of a continuously circulating, standing wave of molten solder. The wave is formed by pumping solder up through a narrow slot, where it overflows back into a sump. Various wave configurations are available. The path of travel towards the solder wave may be inclined upwards at an angle of about 15° to facilitate drainage of solder from the board after it has passed over the wave.

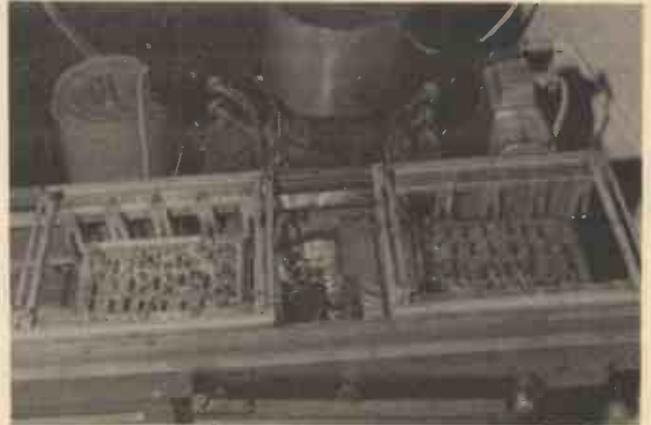

A wave soldering machine in use for large quantity production.

### QUALITY CONTROL

The application of quality control techniques to the production of soldered joints in industry is extremely important since the failure of a joint may not only result in the job having to be reworked, but also a fault occurring during service may be potentially dangerous. Therefore, high reliability is demanded, particularly in applications such as aerospace, military equipment, telecommunications and computers.


For the amateur, if the few relatively simple precautions outlined in this article are taken, soldering defects should not occur. One of the most common defects, known as dewetting, happens when the surfaces to be soldered have not been properly prepared. In dewetting there is a pronounced retraction of the solder into globules, after initial wetting has taken place, leaving an extremely thin, matt film of solder on the surface which the globules rest. A common cause of dewetting is the presence of a thin, discontinuous layer of surface oxide, or embedded particles of abrasive. If this phenomenon occurs it is necessary to further clean the surface before good wetting can be achieved.

It is also important during soldering to use the right amount of flux (this is controlled if flux-cored wire is used), not to apply too much solder, or to overheat the joint.

### CONCLUSION

To sum up, the advantages of soldering (where soldering is applicable) may be stated as follows:

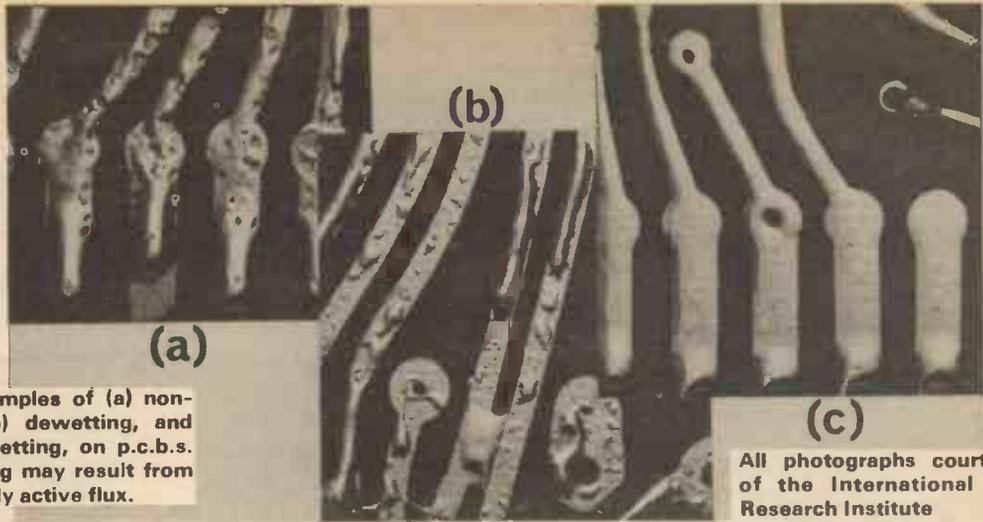- (a) Relative ease and speed with which it can be carried out.
- (b) Versatility and range of heating techniques.
- (c) Low cost when compared to other joining methods.
- (d) Low temperatures involved do not normally affect the properties of the basis metals.
- (e) Soldered joints may usually be taken apart by reheating, thus facilitating easy repair of circuits.



Typical examples of (a) non-wetting, (b) dewetting, and (c) good wetting, on p.c.b.s. Non-wetting may result from insufficiently active flux.

All photographs courtesy of the International Tin Research Institute

# News Briefs

by Mike Abbott

## FLICKER TO FLUORESCENT

LONDON'S South Kensington Science Museum now has a new lighting gallery showing artificial lighting from primitive oil lamps to the latest electric discharge lamps.

Scenes show visitors how people managed after dark throughout most history, and a variety of modern electric lights can be seen through filters for comparison of light source.

We are told that oil lamps have been mass produced for two thousand years, but until the 1780s they gave no more light than a candle. Argand's circular burner, patented in 1784, gave a much brighter light but suitable fuel was expensive until paraffin became readily available in the 1860s. The light of a gas flame was first used generally in the early 19th century, but the much brighter gas mantle dates only from the 1880s.

The exhibition includes a room lit by gas, and a pair of shop windows illustrate problems with the colour rendering properties of fluorescent lighting. (Too true! Have you ever discovered that those *chocolate brown* socks you bought are actually *maroon* when you get them outside the shop).

The museum is open from 10.00-18.00, Mon.-Sat., and 14.30-18.00, Sundays. Visit Gallery 41 on the second floor.

## NO CAUSE FOR ALARM

IN PURSUIT of its ubiquity the microprocessor is creeping into the twilight world of crime prevention. The Silent Security System now available from Asmap Environmental Products of Newport, Isle of Wight, is Z80 based, and can be hooked up to an intruder alarm to watch out for that thief about! If it detects one, it doesn't reduce the burglar to jelly with a breathtaking siren, or ring a bell for the neighbours to ignore, it panics and phones the police. Well, it doesn't panic, but it *does* phone the police.

Up to nine digits can be preset (in PROM) for direct dialling to send an alarm message or tone to either a security officer, or via the normal police/public alarm system by means of a 999 call and a pre-recorded message.

Up to sixty hours of stand-alone operation is possible in the event of a power failure, and should the telephone lines be engaged a second number may be dialled, or if faulty, alternative actuations may take place such as that siren, or perhaps cameras or loudspeakers.

Of course, the system can operate from fire or smoke detectors, and make the appropriate alert.

## COUNTDOWN

**B.A.E.C. Amateur Electronics Exhibition**—July 21-28. Held at the shelter at the centre of the Esplanade, Penarth, South Glamorgan. The exhibition is to display a large number of projects and electronic games made by members, and will be open every evening from 7 p.m. (except Sunday, July 22), and also on the afternoons of July 21, 22 and 28. Proceeds go to the Cancer Research Campaign.

**Harrogate International Festival of Sound**—August 18-19 (public), August 20-21 (trade) 1979. The Exhibition Centre + hotels. Details: Exhibition and Conference Services Ltd. Tel: 0423 62677.

**Telecom '79**—September 20-26. Palais des Expositions, Geneve. Details: Secretariat Telecom '79, Orgexpo, 18 Quai Ernest Ansermet, Case Postale 65, CH-1211, Geneve 4 (Suisse).

**Eltro Hobby '79**—October 3-7, Killesberg Exhibition Grounds, Stuttgart. Details: 01-236 0911.

**Personal Computer World Show**—November 1-3. West Centre Hotel, London. The *computer versus computer* Chess Championship will again take place, and this year the prize money has been increased to £1,500 (a considerable sum to give a computer we are told). Further details to be announced.

**Compec**—November 6-8, 1979. Grand Hall, Olympia, London. Details: Iliffe Promotions Ltd. Tel: 01-261 8437/8.

**Professional Viewdata Exhibition '79**—November 7-8. West Centre Hotel, London. Business orientated exhibition sponsored by Viewdata & TV User Magazine. An exposé of who's doing what on the Teletext and Prestel scene.

**Electronics '79**—November 20-23. Olympia, London. Details: 021-705 6707.

**Breadboard '79**—December 4-8. Royal Horticultural Halls, Westminster. Details: Trident International Exhibitions. Tel: 0822 4671.

**IEA/Electrex**—February 25-29, 1980. National Exhibition Centre, Birmingham. Details: Industrial and Trade Fairs Ltd. Tel: 021-705 6707.

**Communications '80**—April 14-18. National Exhibition Centre, Birmingham. Details: ITF Exhibitions. Tel: 021-705 6707.

**All-Electronics Show (1980)**—April 29-May 1, Grosvenor House, London. Details: 0799-22612.

## RETURN OF STEAM

THE M-O Valve Company, in response to a demand for high quality audio valves, has reintroduced its *Gold Lion* range of output tetrodes. The valves are packed in a distinctive Gold Lion carton, each containing a test report, and the back-up literature includes full amplifier and pre-amp circuit information covering 30 to 200 watts.

## B.A.E.C. HON. SEC. MOVE

THE B.A.E.C. Hon. Sec. has moved from Bristol to Cheltenham, the full address being: J. G. Margetts, Hon. Sec., B.A.E.C., 3 Bishopstone Close, Golden Valley, Cheltenham, Glos.


# PATENTS REVIEW...

Copies of Patents can be obtained from :  
the Patent Office Sales, St. Mary Cray,  
Orpington, Kent Price 95p each
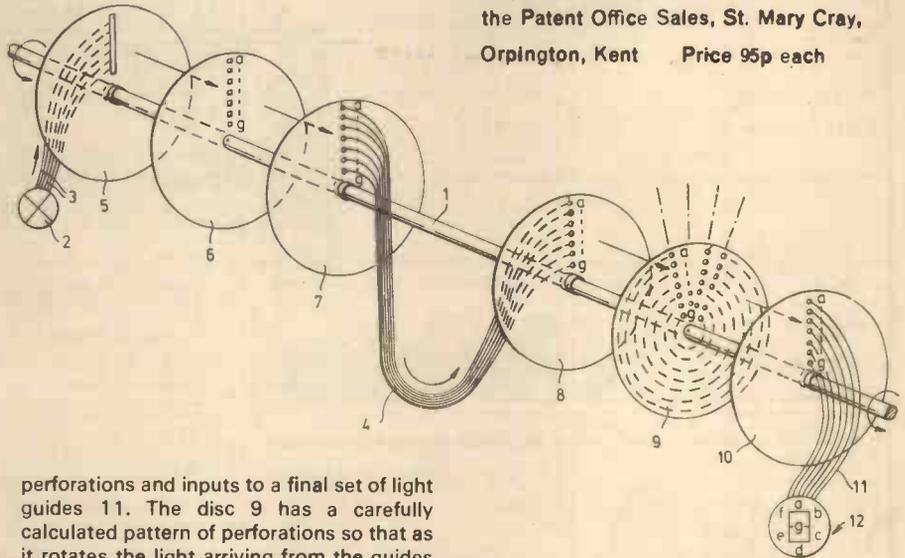
## TORSIONAL METERING

An interesting opto-mechanical approach to metering is being patented by Ferranti Ltd. of Lancashire in GB 2 001 431 A. The application is under the new laws and dates back to June 1977. The object is to provide an instant digital readout of the torsion in a shaft, but the idea could well be applicable to other mechanical situations where digital readout is required.

As shown shaft 1 carries a series of discs, variously perforated with slits, holes and bars. At one end of the shaft a source 2 inputs light to the ends of a batch of optical fibre light guides 3. The light from the output ends of these guides can reach the input ends of further guides 4 only when the perforations of a first series of discs 5, 6, 7 are correctly aligned. This alignment gives the system a datum position. The light guides 4 output through perforations in disc 8 and the output light passes through perforations in disc 9 to disc 10 with



perforations and inputs to a final set of light guides 11. The disc 9 has a carefully calculated pattern of perforations so that as it rotates the light arriving from the guides passes through different perforation patterns. Thus as the disc rotates a varying pattern of light reaches the inputs of the guides 11. The guides 11 output to a readout disc 12 with an arrangement of seven windows in a figure of eight configuration. In this way slight movement of the disc 9 can cause the transitional display of digits in the windows of the disc 12 to

provide a readout which is representative of torsion in the shaft 1 between the discs 9 and 6. The patent describes these and other refinements of the system in great detail, including one arrangement for rotating the datum position to provide a continuous display.

## DOUGHNUT DAMPING


A good example of how the new patents law can benefit the public and inventors alike is to be had from comparison of BP 538 847, in the name of the Rank Organisation, and GB 2 002 200A, in the name of the Nissan Motor Company of Yokohama City, Japan.

The Rank patent was applied for in 1975 and is thus granted under the old law; the Nissan patent is still in the pending stage and has been published under the new law. There is interesting common ground between the two patents and this common ground could be damaging to Nissan's chances of securing a granted patent.


Both patents concern methods of damping the rearward, antiphase radiation of sound from a loudspeaker. As the Rank patent explains, it is customary to mount a loudspeaker in a cabinet containing wool or plastic to damp the rear radiation. But the damping material results in high stiffness of the air cushion inside the cabinet and the cabinet walls tend to vibrate. Moreover there is a risk of overheating in the cabinet space due to heat dissipation by the loudspeaker voice coils.

Nissan make much the same point with particular reference to the problems encountered when mounting a loudspeaker in a motor car. Both teams of inventors propose a similar solution; an annulus of sound damping material clamped to the rear of the loudspeaker.

Nissan (see Fig. 1) show an acoustic absorber 1 of bitumen-containing urethane foam which takes the form of a ring like a large doughnut. This ring sits on the loudspeaker magnet 2 and overlies virtually the whole rear area of the conical diaphragm 3. Thus all sound radiating to the rear of the diaphragm 3 meets acoustic resistance. Nissan claim that in this way undesirable resonant peaks in the range 50 to 500Hz are suppressed to an acceptable level.

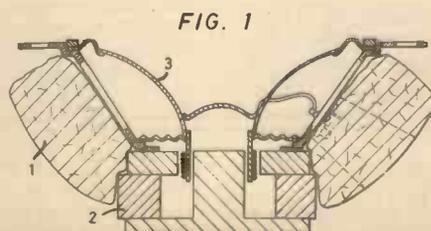

The earlier idea from Rank goes a stage further. As shown (in Fig. 2) there is again a doughnut shaped ring 1 which sits on the loudspeaker magnet 2 and backs onto the rear of the loudspeaker diaphragm. But additionally Rank provide a second damping element 3 which takes the form of an open cylinder of foam surrounding the loudspeaker unit. Together the damping elements 1 and 3 absorb and deflect the rearward directed sound from the diaphragm.

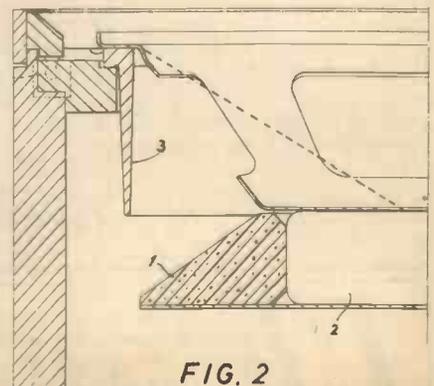

### QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch. Very slim, only 6mm thick.



M1

### SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins., secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

**£8.65**

Guaranteed same day despatch.



M2

### QUARTZ LCD 11 Function

SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£10.65** Thousands sold! Guaranteed same day despatch.



M3

### QUARTZ LCD ALARM 7 Function

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

**£12.65**

Guaranteed same day despatch.



M4

### MULTI ALARM 6 Digits 10 Functions

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual zone.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

**£18.65**



M5

### FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet.

**£22.65**

Guaranteed same day despatch



M6

### SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

**£27.95**

Guaranteed same day despatch



M7

### ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs.
- In 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

**£29.65**

Guaranteed same day despatch



M8

### SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£12.65**

Guaranteed same day despatch.



M9

### SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00  
METAC PRICE  
**£105.00**



M10

### SEIKO MEMORY BANK

Calendar watch M354. Hours, mins., secs. Month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display month, year and all dates for any selected month over 80 year period. Memory bank function. Any desired dates up to 11 can be stored in advanced. 2 year battery life. Water resistant.

List Price £130

Metac Price **£105**



M11

### SEIKO-STYLE Dual time-alarm Chronograph

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

**£35.00**

Guaranteed same day despatch



M12

### HANIMEX Electronic LED Alarm Clock



Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 111mm x 60mm). Weight: 1.43 lbs (0.65 kgl). AC power 220V.

**£9.65** Thousands sold!

Mains operated.

Guaranteed same day despatch.

M13

### HANIMEX portable LCD clock radio



- Time set & alarm controls.
- Snooze & sleep controls.
- Wake to music or alarm.
- AM/PM indicator.
- Battery operated. No plug required.
- Receives all standard AM radio broadcasts.
- Drawstring carrying case included.
- Back-light.
- Batteries supplied free.
- Quartz crystal controlled.

**£17.95**

M14

### HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

### QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

### Price breakthrough only £18.95



- OUTSTANDING FEATURES**
- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
  - **CALENDAR FUNCTIONS** include the date and day in each time zone.
  - **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
  - On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
  - **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch. **M16**

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

# MICRO CHIMES

FROM THE INVENTORS  
OF MICROPROCESSOR  
MUSICAL CHIMES

New price for the  
original

## CHROMA- CHIME KIT

24 tune model!

Due to the fantastic  
success of this product right  
across the World we are able to offer it at

only **£9.95 + 75p p&p**

Comes complete with:

- \* TMS1000 Micro
- \* Superb cabinet
- \* All R's & C's
- \* Switches & pots
- \* Fully prepared PCB
- \* All semiconductors
- \* Loudspeaker
- \* Socket & Hardware
- \* Fully detailed kit manual

**TMS 1000N** - MP0027A Micro-  
computer chip available separately if  
required. Full 24 tune spec device  
supplied with data sheet and fully  
guaranteed.

New low price only **£4.95** inc. p&p  
(Only present 24 tune repertoire currently available.)

## A COMPLETE KIT FOR THE NEW MICRO CHIME

This easy to  
build kit includes:

- \* TMS1000 Custom MPU Chip
- \* Special purpose designed case
- \* Fully drilled and legended PCB
- \* All transistors, Resistors and Capacitors
- \* Full set of mechanical parts
- \* Smart fascia labels
- \* IC Socket and Loudspeaker
- \* Really Low Price!

only **£8.95 + 55p p&p**

CHROMATRONICS RIVER WAY HARLOW ESSEX U.K. ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me: PE1  
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX, U.K.



NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/PO value £ \_\_\_\_\_  
or debit my ACCESS/BARCLAYCARD account no. \_\_\_\_\_

Signature \_\_\_\_\_

# CHROMATRONICS

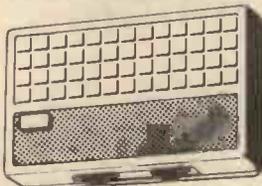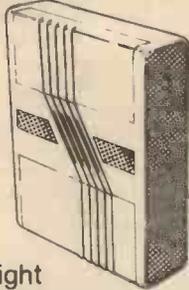

# Wilmslow Audio

**THE firm for speakers!**

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF  
SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND  
DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER  
BOWERS & WILKINS ● CASTLE ● CELESTION  
CHARTWELL ● COLES ● DALESFORD  
DECCA ● EMI ● EAGLE ● ELAC ● FANE  
GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON  
JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER  
MCKENZIE ● MONITOR AUDIO ● PEERLESS  
RADFORD ● RAM ● RICHARD ALLAN ● SEAS  
SHACKMAN ● STAG ● TANGENT ● TANNOY  
VIDEOTONE ● WHARFEDALE ● YAMAHA

**WILMSLOW AUDIO (Dept. P.E.)**  
SWAN WORKS, BANK SQUARE, WILMSLOW,  
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street  
Tel.: Wilmslow 529599 for Speakers Tel.: Wilmslow 526213 for Hi-Fi

# ELECTROVALUE

All the many types of components we supply are BRAND NEW and guaranteed and only from manufacturers direct or approved suppliers. No surplus, no seconds

ICS - TTL 7400 series			
7400 13p	7413 22p	7451 14p	7483 58p
7401 13p	7414 60p	7453 14p	7485 74p
7402 13p	7420 14p	7454 14p	7486 27p
7403 13p	7430 14p	7460 14p	7490 40p
7404 18p	7440 14p	7470 24p	7491 71p
7405 14p	7442 54p	7472 24p	7492 46p
7407 22p	7443 60p	7473 23p	7493 40p
7408 18p	7444 60p	7474 23p	7494 66p
7409 18p	7447 70p	7475 45p	7495 57p
7410 14p	7450 14p	7476 32p	7496 63p
		7480 41p	74100 73p
		7482 61p	74104 40p

### OUR COMPUTER TAKES GOOD CARE OF YOUR ORDERS

#### SIEMENS CAPACITORS\*

World famous for quality and dependability -  
PCB TYPES - 7.5mm PCM 0.001 to 0.015  
6p each; 0.015 to 0.047 7p each.  
5mm PCM 0.068 8p, 0.1 9p, 0.22 12p.  
CERAMIC 2.5mm PCM 0.01 5p, 0.022,  
0.033, 0.047 5p, 0.068 6p, 0.1 6p.  
ELECTROLYTICS - 1/100, 10/25, 10/63,  
100/25, etc. For full range see our current lists.

#### RESISTORS

1/2, 1/4 watts\* - 2p each\*; metal film, metal  
oxide and 1 watt carbon 5p ea\*; good quantity  
discounts. Magnetic field dependent  
from £1.50. Half Effect from £1.23.

#### SIEMENS TRANSISTORS

Silicon npn and pnp from 8p ea; LEDs, red  
19p; yellow or green from 23p (3 or 5mm);  
Photo transistors from 46p.

### KEEN PRICES ★ GOOD SERVICE ★ WIDE RANGES

#### DISCOUNTS

5% if list value of order  
over £10  
10% if list value of order  
over £25. Discounts available  
where cash (P.O. or cheque)  
is sent with order. Not applicable to net prices.

V.A.T. - Add 8% to value of order or  
12 1/2% with items marked\*  
(No V.A.T. on overseas orders)  
Goods sent post free on C.W.O. orders in  
U.K. over £5 list value. If under, add 27p  
per order.

Latest 120 page  
catalogue on request.

Cash with order (P.O. or cheque payable to Electrovalue Ltd) or your Access or Barclaycard number.

TRADE AND INDUSTRIAL ENQUIRIES INVITED

For all round satisfaction - be safe - buy it from ELECTROVALUE

## ELECTROVALUE LTD

Dept. PE8 28 St Judes Rd, Englefield Green, Egham, Surrey TW20 0HB.  
Phone Egham 3603; Telex 264475.  
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage,  
Manchester M19 1NA. Phone (061) 432 4945.



# INDUSTRY NOTEBOOK

By Nexus



## Right Turn

It is far too early to assess with any assurance the effect of the change of government on the industrial climate. The private sector almost universally welcomed the return of the Conservatives with a working majority which guarantees four or five years in which policies thought favourable to private industry can be implemented. Less central direction, less bureaucracy, less taxation, are all welcome. But, of course, nothing can change overnight in any material way.

The instant change was in morale. A fresh start became possible. Or so it seemed. In fact top performers like GEC and Racal historically have prospered as much under socialist governments as any other. The general feeling, however, was that the shackles are now off, or soon will be, and there is a real chance of winning. At least a company that does well financially will, one hopes, escape the old charge of "profiteering", while those who do less well are told they are "failing the nation". All will now get encouragement to do better.

To find out what will happen in the public sector we shall need to wait and see. Similarly, the future of the National Enterprise Board with its mixed bag of investments, not least the controversial Inmos venture.

Specifically helpful to the electronics industry is the new government's attitude to defence spending. Defence electronics has always been the spearhead of technological innovation and countries with a powerful defence industry traditionally maintain their lead.

Of perhaps less significance but worth recording is that Mrs Thatcher, as well as being Britain's first woman Prime Minister, is also the first with scientific training and laboratory experience.

For the past four years the most used political slogan has been "the regeneration

of British industry". The electronics sector has done better than most during a difficult period. In some areas it has been outstanding and in the next decade it will be central to advance in all industries. No change of government in itself can regenerate anything, but a whiff of optimism and a return of confidence is not a bad start.

## Manpower

However well intentioned a new Government, it inevitably inherits a number of constraints, both internal and external. It finds, on taking office, that it cannot move, except cautiously, if severe disruption is to be avoided. This is why the prospect of stable administration is welcome. There is a long haul ahead but over a period of five years much can be achieved, not least in attitudes.

A particular constraint in the electronics industry is the shortage of skilled manpower, particularly design engineers. The shortage was highlighted by Mr D. W. Morrell, President of the Electronic Engineering Association, in his recent address to members, as "one of our greatest problems of the moment". You can see how right he is just by reading the job ads in the papers.

Why the shortage? Relatively low pay for high qualifications (often mentioned in this column) is one, though not the primary, reason. Prospects are dazzling compared with most industries. The work is challenging, often exciting. It is a clean industry in which to work and has one of the best industrial relations records. It seems a "natural" for any youngster with talent. And yet not nearly enough come forward to take advantage of the opportunities offered.

An important factor is that engineering as a profession has been tarnished in recent years by adverse publicity eagerly taken up and propagated by socially conscious teachers in schools. Engineering is often represented as being somehow morally reprehensible—even obscene when topics like atomic power are mentioned. And quite unjustifiably so because engineers as a body are also socially conscious and responsible and ordered to be so by their professional institutions.

Much damage has been done. One thing the new government might do is to attempt to change the attitude in the schools and colleges to one of encouragement to budding engineers. A little more stress on the benefits of science and technology and a little less knocking might do a lot of good.

## Cable & Wireless

Cable & Wireless, perhaps the most consistently successful of all our nationalised industries this year celebrated its 50th anniversary. It came into public ownership following the merger of the competing submarine cable and beam wireless businesses. From 1929 to the present day these two primary methods of long distance communications, one very old, the other then quite new, have been regarded as complementary.

Today the company has diversified into many new communications fields, all electronic based, and implemented throughout the world. In fact it is far better known overseas than in the UK and some 80 per cent of the employees work outside the British Isles.

## British Aerospace

The newest of our nationalised industries, British Aerospace, has just completed its first full year and with good results. Trading profit was £79 million on a turnover of £894 million and the company went into its second full year with a record order book of close on £3,000 million, with nearly 70 per cent ticketed for export.

British Aerospace is the channel through which many of our most important electronics exports flow, especially in avionics and missile guidance and control systems. The possible termination of substantial contracts from Iran are not expected to seriously affect the overall buoyant outlook.

## Convergence

The recent announcement by Racal Microelectronics Systems Ltd that their private in-house service to the Racal Group is now open to all comers is another interesting example of an equipment company expanding into the supply of sophisticated components. It is the opposite of the semiconductor manufacturers moving into the equipment field, of which there have been a number of recent examples. Perhaps in a decade or so the demarcation line between component and equipment people will have entirely disappeared.

Although only one year old, Racal Microelectronics Systems already claims to have developed over 20 complex LSI circuits for inclusion in Racal advanced products. The new service offered to industry includes designing with Uncommitted Logic Arrays (ULA) as well as LSI and thick-film hybrids. Using a standard Racal ULA wafer, working samples of new circuits can be designed and manufactured in less than three months, in some cases as little as seven weeks.

Keith Thrower, managing director, is an old Racal hand. He joined the company as an engineer in 1960 and was responsible for much of the design of early Racal digital instruments and frequency synthesisers before becoming head of Racal's Advanced Development Division some five years ago.

## Musical Bargain

Semiconductor prices are keener than ever. Typical is the MPU chip used in the Chromatronics 24-tune electronic door chime which is based on the TI TMS1000. Now I note that you can buy this 28-pin package with all its built-in complexity for £4.95 (VAT included); even cheaper in quantity. Chromatronics believe that it will have many other applications, apart from door chimes, in the electronics toy and hobbyist markets.

# readout

## ... a selection from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope.  
Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

### Gertcha!

Sirs—On seeing the cover of the May edition of "Practical Electronics", and on reading subsequent disclosures inside, we noted several anomalies on the instrument panel of the car illustrated.

The car was apparently travelling at sixty miles an hour (engine speed 4,000 r.p.m.) with the handbrake on. This we feel was a rather pointless gesture, as the engine was in imminent danger of seizure, due to the fact that there was no oil pressure. The battery also seemed to be under a heavy discharge for such a high engine speed. This was presumably due to the current being drawn by the instrumentation, or the heated rear window and headlamps.

Anyway, function of the car apart, we consider that the driver was running a great risk as he was wearing no seat belt. The risk was compounded by the fact that he was driving with no hands on the wheel while initiating a right turn with the hazard warning lights on AND THE BONNET UP!

Assuming the car survived the almighty crash which followed, we would like to suggest a few repairs which should be undertaken:

1. New fan belt or alternator.
2. Top up with brake fluid (or release the hand brake!)
3. Top up with oil.
4. Replace clutch.

Alternatively, the car should be taken to the nearest scrap yard (after only 36.9 miles). Not one of Leyland's better attempts (We hope!)

A. Lorimer & A. Birse,  
Clydebank.  
Scotland.

### Bouquet and Brickbat

Sir—Please accept this as a constructively critical letter—which is what it is intended to be.

First of all the bouquet. I have had subscriptions to several electronic magazines over the years, and still buy others on an occasional basis when they happen to have an item which interests me, but for some years now I have had a regular order for *PE*. My interests must be the very common ones—general "educational" items about new developments and, mainly, general constructional features. As it happens my particular interests are radio control and audio.

Overall a fairly typical reader and quite satisfied enough with *PE* to go on buying.

Now the brickbat. An increasing percentage of your magazine seems to be devoted to computer and microprocessor projects and programming. This was fair enough when it was a new field for the amateur, and I

appreciate that it is still a growth area for the "home builder". However, there are now several magazines devoted entirely to home computers and, while I would not suggest that you exclude the field entirely, I would be grateful to see some of the space that you now devote to it returned to a wider range of constructional projects.

J. A. Purvis,  
Sholing,  
Southampton.

*Thank you for your interesting letter—the points made have been noted and will obviously add to any others in a similar vein.*

*In reply we would like to make two points. Firstly, due to the increase, last year, in the relative number of editorial pages in PE we do not believe that we have reduced the number of projects in which you might be interested! We have published only four m.p.u. projects since the end of the Champ series—the fifth is Compukit.*

*Secondly, a recent survey showed more regular readers are interested in m.p.u.s and related areas than in any other subject covered in our pages.*

*These points do not necessarily mean we have the mix right and we would like to thank you for passing on your views. The following letter may give you and others food for thought. Any more bouquets or brickbats?—Ed.*

### Logical software?

Sir—I would like to comment on the "symbols" used in diagrams—basically I'm in agreement with you regarding the decimal point. However, the use of 0V2 in the text describing an amplifier input of 200mV destroys the flow. Personally I've used boxes for resistors for 10 years when drawing (also transformer windings) as they are neater and quicker to draw.

Please let's have more *Microbus*. There seem to be many mags devoted to those who have £XXX to spend upon a self-contained toy computer, monthly offerings of games and the like. However, your recent venture into the low-cost peripherals is most welcome, even though I'm not likely to extend my micro just yet.

Could I suggest another subject for a long series?—"Logical Software".

I have two projects which are nearing completion in that their requirements are known and the TTL/CMOS logic needed is reasonably understood. This normally leads to the next stage: buying the logic and making it work. The last stage is frequently omitted: pulling it apart and doing the job properly using the knowledge gained from the prototype.

Project 1—House alarm, giving various levels of entry/warning so the unit can be "on guard" most of the time.

Project 2—Heating control, giving various switching-on times and heat levels to optimise the fuel.

Both of these can be realised using "hard" logic—what I bought a micro for was to (eventually) design a universal micro-board which would cater for such projects by altering the software. Both require many inputs (door switches/temperature) and a few outputs (enter key code/hot water solenoid).

Your boffins could develop such a unit which would be of great use to engineers that want to use micros (rather than play with systems). There are countless projects which could be software-implemented so the interest could be renewed from time-to-time. However, may I give you a warning? Be careful not to have the whole thing written by a boffin. Your title is "Practical . . ." and you will realise there is a large gulf between building a "KOJAK" horn using multivibrators or 555 type timers and realising the same end (together with "Col. Bogey") by writing software.

There is yet another project for a "PE Micro project p.c.b." receiving hex data from micro and contact closures and displaying it on 7-segment readouts.

H. S. Lynes,  
Carshalton Beeches,  
Surrey.

### Springs and Buckets

Sir—I was very interested to read your article on binaural stereo patents in March's *PE*. Of particular interest was mention of the Matsushita mechanical spring and the capacitance bucket brigade methods of introducing artificial reverberation, in headphone listening.

There is, as far as I am aware, no spring device on sale in the UK for hi-fi use, although systems for use with P.A. (disco's, etc.) are quite cheap (about £50). This compares with some bucket brigade equipment (for use with hi-fi) selling for £500 to £1,000.

Considering what is required of a reverberation system, I do not see why spring devices fall outside the scope of hi-fi as their ranges (100–10,000Hz) and distortion (1 per cent) compare with electronic systems.

I think Matsushita's spring transducer could be very successful and it may pay a British manufacturer to think of the mechanical system for other uses, say loudspeaker stereo, or surround sound experiments (dare I mention those words?).

J. W. Jones,  
Widnes,  
Cheshire.

# SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE EQUIPMENT AT INCOMPARABLE PRICES

## STANDARD CENTAUR 100W

£249 + Carr £15 & VAT £21.12 Deposit **£57.12**  
12 months @ **£22.23** or 24 months @ **£12.73**

## SUPER CENTAUR 200W

£299 + Carr £15 & VAT £25.12 Deposit **£68.12**  
12 months @ **£26.41** or 24 months @ **£15.11**

## GXL 200W

With Twin 200 Watt Cabinets

£389 + Carr £15 & VAT £32.32 Deposit **£87.32**  
12 months @ **£34.02** or 24 months @ **£19.47**

## GXL WITH PDF BINS

£417 + Carr £15 & VAT £34.56 Deposit **£93.56**  
12 months @ **£36.36** or 24 months @ **£20.81**

## CUSTOM CENTAUR 400/600W WITH FOUR PDF 100A BINS

£699 + Carr. £20. & VAT £57.52 Deposit **£155.52**  
12 months @ **£60.54** or 24 months @ **£34.66**

## CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY TWIN LOUSPEAKERS & LEADS 100W-600W

20% DEPOSIT CREDIT TERMS



6XL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Boss/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

**JUST PLUG IN AND GO!!**  
SEND TODAY FOR YOUR FREE BROCHURE

## MINI DISCO 100 WATT

MONO SYSTEM WITH LOUSPEAKERS

£179.50 + Carr £15 & VAT £15.56 Deposit **£42.06**  
12 months @ **£16.22** or 24 months @ **£9.24**

## P.A. SYSTEMS

2 YEAR GUARANTEE

100 WATT **£159.90**  
+ Carr £15 & VAT £13.99 Deposit **£37.89**  
12 months @ **£14.77** or  
24 months @ **£8.48**

★ Four Mixing Inputs  
★ Bass & Treble Controls  
★ Twin Piezo Horn Columns

200 WATT **£249.00**  
+ Carr £15 & VAT £21.12 Deposit **£57.12**  
12 months @ **£22.23** or  
24 months @ **£12.73**

## AMPLIFIER UNITS ONLY

API00 AMPLIFIER

£49.50 + Carr £1.50 & VAT £3.96  
★ 4 Mixed Inputs  
★ Bass/Treble Controls  
★ Vynide Case  
★ 100 Watts Output

AP200 AMPLIFIER

£89.50 + Carr £1.50 & VAT £7.16  
★ Six Mixed Inputs  
★ Three Sets Boss/Treble  
★ 200 Watts Output  
★ Slave Socket



## NEW SAXON KLAXON

UK Police Hawaii 50  
US Police Destroyer

Four Sirens in one package **£18.75** + VAT £1.50

Individual Sirens **£8.50** + VAT 68p



## NEW SAXON SMASH

ALIEN VOICE SIMULATOR

Add a new dimension to your disco with this press button effect unit  
Insert between mic & amp **£8.50** + VAT 68p



## PLUTO PROJECTORS

P140 **£38.50**  
150 WATT INC WHEEL



P250 **£69.90** + VAT £5.59  
250 watt Q.I. inc Cassette/Wheel (Full range of wheels - ask for list)

## D.I.Y. MODULES FOR P.A. SYSTEMS MONO/STEREO

Input Modules  
Mono PCB only **£6.50** + 52p  
Stereo PCB only **£10.50** + 84p  
Mono C/W Front panel **£9.50** + 76p  
Stereo C/W Front panel **£13.75** + £1.10  
Mixer/Monitor Modules  
Mono PCB only **£6.50** + 52p  
Stereo PCB only **£10.50** + 84p  
Mono C/W Front panel **£9.50** + 76p  
Stereo C/W Front panel **£13.75** + £1.10



Make your own mixer Mono/Stereo up to 20 channels accept all inputs available as PCB only or complete on front panels

Power supply to suit **£9.50** send for full details. +VAT 76p

ELECTRECT MIC DI501 **£18.50\***  
TOP QUALITY UNIT + VAT £2.31

ECM105 LOW COST ELECTRECT CONDENSER MIC + VAT 62p **£5.00\***

MELOS CASSETTE ECHO-REVERB UNIT - Twin input VARIABLE SPEED & DEPTH + VAT £5.52 **£69.00**

## AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers



SA308 8 ohms 30W 45V **£10.75\*** + £1.34  
Supply for 2 modules **£11.90\*** + £1.49  
SA604 4 ohms 50V **£14.50** + £1.16  
Supply for 1 or 2 modules **£14.95** + £1.20  
SA608 8 ohms 60W 65V **£15.50** + £1.24  
Supply for 1 or 2 modules **£14.95** + £1.20  
SA1204 4 ohms 120W 75V **£17.50** + £1.40  
Supply for 1 module **£14.95** + £1.20  
SA1208 8 ohms 120W 95V **£21.00** + £1.68  
Supply for 2 modules **£24.75** + £1.98

## DISCO MIXERS - COMPLETE OR MODULAR



MONO OR STEREO WITH AUTOFADE  
Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE:  
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.

COMPLETE MIXERS (with case)  
Mono mains **£45.75** + £3.66  
Stereo mains **£63.75** + £5.10

MODULES  
Mono module **£27.50** + £2.20  
Stereo module **£37.50** + £3.00  
Panel **£3.95** + 32p  
Kit of knobs/sockets etc **£5.50** + 44p

## SOUND-TO-LIGHT UNITS



3 CHANNEL - 3kW **£29.50**  
 Operates from 1W upwards +VAT £2.36  
 Boss/middle/treble/master controls + £1 corr. complete

Module only **£19.75** + VAT £1.58  
Panel **£2.95** + VAT 24p

## 4 CHANNEL - 4 kW SOUNDLIGHT SEQUENCER (illus)

**£39.50** Carr £1 + VAT £3.16  
 Dimmer on each channel  
 Automatic sound light level  
 Logic circuitry throughout  
Module only **£26.75** + VAT £2.14  
Panel **£2.95** + VAT 24p

MOTOROLA PIEZO HORNS **£4.99 YES!!**  
+ VAT 40p

FUZZ LIGHTS Red, Blue, Yellow, Green **£23.90**  
+ VAT £1.91

HEAVY DUTY SPOT BANKS - MATCHES LOUSPEAKERS  
3 way 600W **£35.50** 4 way 800W **£39.50** Carr £2  
+ VAT £2.84 + VAT £3.16

100W SPOTS  
Red - Blue - Amber - Green **£1.50 ea.** + VAT 12p

CABINET FITTINGS  
ICI Vynide 50" wide **£3.50m** + VAT 28p  
Kick-res grille 50" wide **£3.50m** + VAT 28p  
Netlon kick proof 24" wide **£3.50m** + VAT 28p  
Corners/feet/recess plates 15p ea. + VAT 1p  
Recess handle 45p + VAT 3p  
Bar handles **£2.50** + VAT 20p  
Jack plugs/sockets 25p + VAT 2p

## LOUSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) **£39.00**  
Carr £3 + VAT £3.12  
Large 100W 1 x 12 (65 x 48 x 24) **£49.50**  
Carr £3 + VAT £3.96  
P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24) **£66.50**  
Carr £3 + VAT £5.32  
P.A. 2 x 12 200W (100 x 38 x 24) **£99.00**  
Carr £3 + VAT £7.92  
Disco 2 x 12 200W (80 x 63 x 24) **£85.00**  
Carr £3 + VAT £6.80  
PDF reflex bin (80 x 40 x 41) **£95.00**  
Carr £3 + VAT £7.60

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals  
 Use with all types of mixer  
 Pan and volume controls  
 Send for details **£130** Carr £3 Deposit £28.40 + VAT £10.64

100 W Chassis loudspeaker **£25.75** + VAT £2.86

VAT 8% shown in brackets - where asterisked (12 1/2%) Shop premises open Tues to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm Mail order dept open Mon to Fri 10 am - 4 pm Ring 01-684 6385

## TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclaycard Number NOT THE CARD.

By Phone You may order COD, Access or Barclaycard. Post & Packing 50p on all orders except where stated.

## SAXON ENTERTAINMENTS

327 Whitehorse Road, Croydon, Surrey.

All Enquiries Large SAE Please Brochures on request

MANCHESTER DISCO CENTRE, 237 DEANS GATE, MANCHESTER CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY

# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

## Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical engineering, Installations & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE BOOK**

Post this coupon or 'phone today for free ICS careers guide.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_

**ICS**

To ICS, Dept. K273, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

# CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,  
WOOD GREEN, LONDON,  
N22 4SJ (MAIL ORDER DEPT.)


888-3206

## FLIP

Push Button  
Heads or Tails.

Complete kit and full instructions supplied.

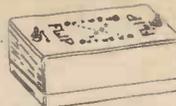A pocket game. Easy to build and great to play. Kit price £5.25 + 42p VAT. Post free.



## PANEL METERS.

Dims - 60 x 47 x 33mm.  
Require 38mm dia. cut out

- T22 0-100µA
- T23 0-500µA
- T24 0-1 M/A
- T25 0-5 M/A
- T26 0-10 M/A
- T27 0-50 M/A
- T28 0-100 M/A
- T30 0-1 AMP
- T31 0-2 AMP
- T36 VU Meter
- T43 0-30 V.DC
- T35 "S" Meter



## BARGAIN LOUDSPEAKER

Goodmans 5" 8 ohm long throw heavy duty L/SPKR.

Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 51" (diagonally).  
Only £5.00 + 60p VAT.

## 2 WAY 8 OHM HEAVY DUTY XOVER.

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100W. Input via screw terminals. Fitted with a 3 position 'HF LEVEL' switch which selects either 'Flat', -3dB or -6dB.

Buy now while stocks last!  
Only £3.00 + 24p VAT.

## 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max. A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier. S.A.E. for spec. sheet.  
Still only £20.00 + 1.60 VAT.



## STEREO CONDENSER MICROPHONE

SPECIAL STEREO 600 ohms Sensitivity deviation within 3dB between right and left microphone. In carrying case. Fitted TWO 3.5mm JACK PLUGS.  
£13.00 + 1.62 VAT.

## CR. 100 MONO AMPLIFIER MODULE

Output power:- 15 watt  
Circuit:- I.C. with protection  
Frequency response:- 50-25K HZ  
Output Impedance:- 4 ohms  
Power source:- 10-18 volts DC  
Dimensions:- 80 x 50 x 22mm  
£8.50 + 68p VAT.

## PIEZO ELECTRIC HORN UNITS

High Quality, High Power Tweeter. No Xover reqd. Freq. Response: 3-8kHz-28kHz. Spec. sheet sent on receipt of S.A.E.  
Our Price: £5.50 + 44p VAT.

## BARGAIN TRANSFORMER

240V Primary 12-0-12V 500mA sec. Approx. size: 60 x 40 x 50mm. Fixing centres: 75mm.  
Price: £1.50 + 12p VAT.



'P&P' orders up to £5. Add 30p.  
Orders £5-£10, Add 50p.  
All orders over £10 post free!  
Please add V.A.T. as shown.  
S.A.E. with all enquiries please.




Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.  
also 13 SOUTH MALL, EDMONTON GREEN, EDMONTON

**M.E.C.A.**  
14 HOPETON STREET  
BATHGATE  
WEST LOTHIAN  
Tel: Bathgate 632337

TERMS: C.W.O. No Min. 12p P & P  
ACCESS AND BARCLAYCARD ACCEPTED  
Min. £5 Post & Packing 25p.  
GOVERNMENT, SCHOOLS, COLLEGES  
ORDERS ACCEPTED  
Send or Phone for Catalogue.

CMOS	4522	70p	N LSN	REGULATORS	MICROS.
4000 10p	4528 70p	7472 24p	7473 16p	78L 31p	CPU's £9
4001 10p	4529 70p	7474 19p	7475 25p	78M 40p	Z80 £11
4002 12p	MC14409 999p	7475 26p	7476 30p	7805 55p	2800 £7
4004 250p	MC14419 295p	7476 25p	7480 35p	7812 55p	8080 £4
4006 70p	74C151 80p	7480 35p	7481 60p	7815 55p	SC/MP11 £7
4007 45p	All prices include VAT.	7481 60p	7482 45p	7824 55p	
4008 28p		7482 45p	7483 45p	LM309 90p	
4009 28p		7483 45p	7484 58p	LM323 37p	
4010 26p	BUFFERED	7484 58p	7485 60p	LM340K 75p	MEMORIES:
4011 12p	types on request	7485 60p	7486 20p	79 80p	2102 £1
4012 12p	according to our	7486 20p	7489 99p		2102L £1
4013 26p	stock position.	7489 99p	7490 28p		2114 £5
4014 55p		7490 28p	7491 40p		4044 £6
4015 50p	TTL:-	7491 40p	7492 29p		4116 £8
4016 21p	N LSN	7492 29p	7493 28p		2107B4 £4
4017 45p	7400 7p	7493 28p	7494 69p		
4018 45p	7401 9p	7494 69p	7495 45p	62p	PROMS
4019 25p	7402 9p	7495 45p	7496 48p		1702A £4
4020 50p	7403 9p	7496 48p	7497 79p		2708 £6
4021 50p	7404 7p	7497 79p	74107 19p	32p	2716 £18
4022 45p	7405 13p	74107 19p	74121 22p		2758 5V £15
4023 12p	7406 15p	74121 22p	74122 35p		
4024 45p	7407 24p	74122 35p	74123 35p	55p	CHARACTER GENERATORS
4025 12p	7408 9p	74123 35p	74125 30p	40p	2513 £5
4026 95p	7409 9p	74125 30p	74126 29p	40p	
4027 28p	7410 9p	74126 29p	74127 44p	60p	CA3046 55p
4028 45p	7411 15p	74127 44p	74131 49p		CA3130 90p
4029 60p	7412 15p	74131 49p	74150 39p	49p	LM301 25p
4030 20p	7413 15p	74150 39p	74151 39p	49p	LM308 70p
4033 80p	7414 45p	74151 39p	74153 45p	49p	LM3900 40p
4034 150p	7416 16p	74153 45p	74154 65p	120p	LM1458 35p
4035 50p	7417 24p	74154 65p	74156 39p	78p	NE555 20p
4037 90p	7420 10p	74156 39p	74157 39p	45p	NE556 50p
4040 50p	7426 15p	74157 39p	74161 49p	75p	NE557 75p
4041 45p	7427 15p	74161 49p	74163 49p	75p	NE566 75p
4042 40p	7430 10p	74163 49p	74164 55p	75p	NE567 100p
4043 30p	7432 12p	74164 55p	74165 59p		LM382 110p
4044 50p	7437 12p	74165 59p	74166 69p		CA3080 68p
4046 75p	7438 13p	74166 69p	74175 55p	58p	CA3140 68p
4048 50p	7440 12p	74175 55p	74176 49p		
4049 26p	7441 52p	74176 49p	74180 60p		
4050 28p	7442 26p	74180 60p	74181 125p		
4052 45p	7443 42p	74181 125p	74182 45p		
4053 45p	7444 42p	74182 45p	74190 69p	78p	1N4148 1.3p
4056 30p	7445 42p	74190 69p	74191 69p	90p	100 £1
4059 29p	7446 42p	74191 69p	74192 55p	89p	1N4002 3p
4071 15p	7447 42p	74192 55p	74193 55p	65p	1N4003 3.5p
4081 16p	7448 42p	74193 55p	74194 55p		1N4005 4p
4082 17p	7450 13p	74194 55p	74195 49p	60p	1N4007 5p
4507 48p	7451 13p	74195 49p	74196 49p	78p	
4511 55p	7453 13p	74196 49p	74197 49p	78p	AUDIO
4512 65p	7454 13p	74197 49p	74198 35p		SN76003 190p
4515 195p	7460 13p	74198 35p	74221 99p	90p	SN76013 130p
4519 42p	7470 26p	74221 99p	74367 99p	45p	SN76023 130p
		74367 99p			SN76033 190p
					TA800 70p
					TA810S 90p
					TA820 86p
					TDA1022 600p
					RESISTORS
					1-w 5%
					0-7p each
					100+ 0-6p

# NEXT MONTH! 6 CHANNEL MIXER

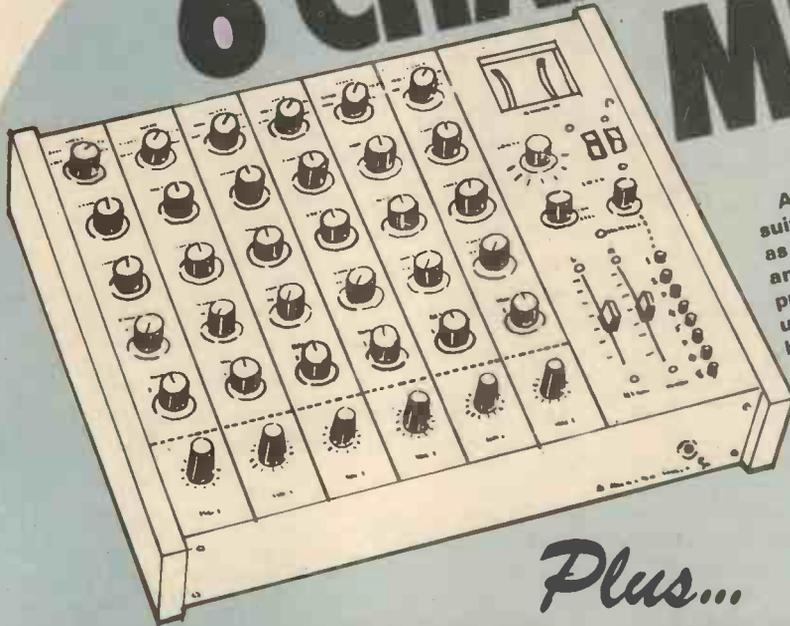

A high specification stereo mixer to suit sound processing equipment such as organ, synthesiser, microphones and electric guitars out to semi-professional tape recorder. Combines unbalanced signal sources for a well balanced output.

*Plus...*



## WAVEFORM GENERATOR

Provides sine, square and triangular wave outputs of up to 10V pk/pk over a 1Hz to 100kHz frequency range.

**FREE ENTRY COMPETITION**  
**OVER £300 WORTH OF BREADBOARDING**  
**from LEKTROKIT**  
**TO BE WON**

PRACTICAL  
**ELECTRONICS**

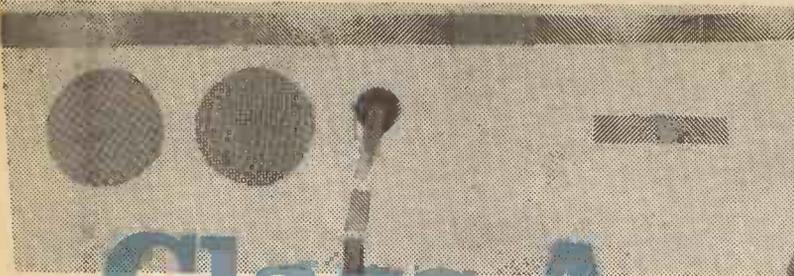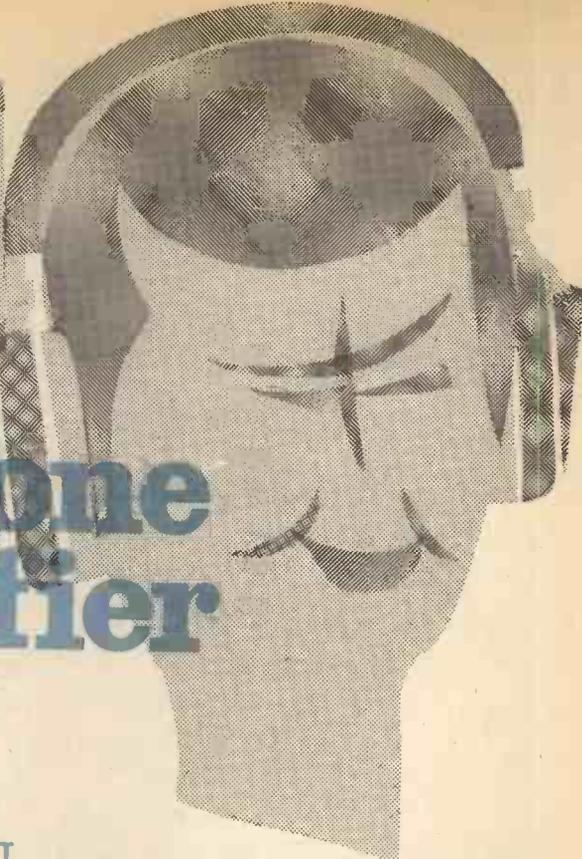OUR SEPTEMBER ISSUE WILL BE ON SALE FRIDAY 10 AUGUST 1979



# Class A Headphone Amplifier

Stephen Price

THE stereo headphone amplifier described makes use of a straightforward design specifically intended to drive dynamic headphones with impedances as low as 50 ohms per channel. It includes its own mains power supply and will accept a low level stereo input direct from a radio tuner or tape deck. However, as the basic amplifier does not provide facilities such as source switching, disc equalisation, tone control and filtering it is best suited for use in conjunction with a separate preamplifier.

Numerous designs for solid state preamps have been published in recent years, but as an alternative, any ready built preamplifier unit or circuit module of commercial origin may be employed.

A trend in recent years has been the increasing popularity of stereo headphones as an alternative to loudspeakers. This is hardly surprising as headphones offer a number of important advantages: Firstly, they are very economical—a pair of headphones costing £30 might reasonably be expected to give the same quality of reproduction as a loudspeaker system which retails at over £100. Secondly, the nuisance factor of headphones is practically nil.

It is common practice for hi-fi manufacturers to provide a headphone output socket on the front panel of their amplifiers and stereo receivers. This headphone feed is derived from the final transistors of the two class B output stages and will normally be routed via a simple resistive attenuator.

There are numerous advantages to be gained, however, in the formulation of an amplifier design specifically intended for headphone operation. Dynamic stereo headphones have impedances far higher than moving coil loudspeaker systems. A typical high quality loudspeaker will present an impedance of between 6 and 8 ohms to the amplifier. In contrast, dynamic headphones have impedances in the range 50 to 2,000 ohms depending on their exact design. It will be apparent, therefore, that far less power is required to drive these transducers satisfactorily. High output power not being a requirement, a return to true class A operation with solid state transformer-less circuitry becomes practicable.


## CIRCUIT

Fig. 1 shows the amplifier circuit diagram. For the sake of simplicity, only one channel is given. Two such amplifiers are, of course, required for stereo operation.

The input signal is taken via R1 and C1 to VR1, which functions as a volume control. Separate potentiometers are employed allowing gain adjustment of the left and right channels independently. This configuration eliminates the need for a balance control (if satisfactory volume control is already provided on the preamplifier to be used in conjunction with this design, then VR1 can be made an internal, preset component).

The signal from VR1's wiper is coupled to the base of TR1 through C2. TR1 forms a common emitter voltage amplifier which is shunt biased by R2. A small amount of negative feedback and stabilisation is provided by the emitter resistor, R5. C4 has no effect at audio frequencies but serves to suppress radio frequency interference. The first stage is decoupled from the supply lines by R6 and C3. The series combination of R3 and R4 provides a collector load for TR1.

The main function of the output stage is to obtain impedance transformation. TR2 and TR3 are therefore employed in the familiar Darlington pair configuration with R7 forming an emitter load for the final transistor. The output signal developed across R7 is taken via C5 to the headphone jack socket.

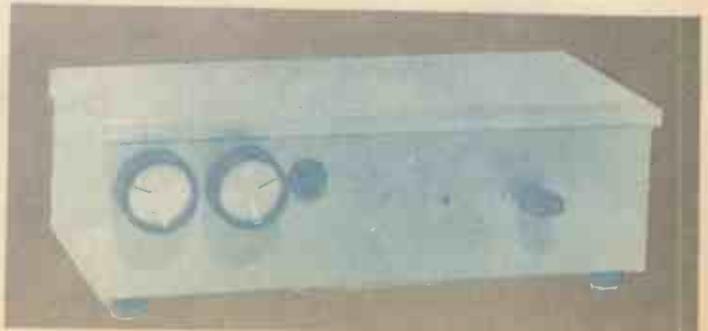

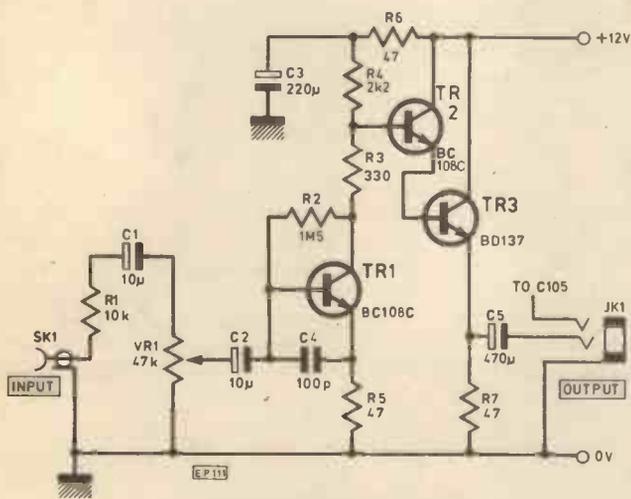
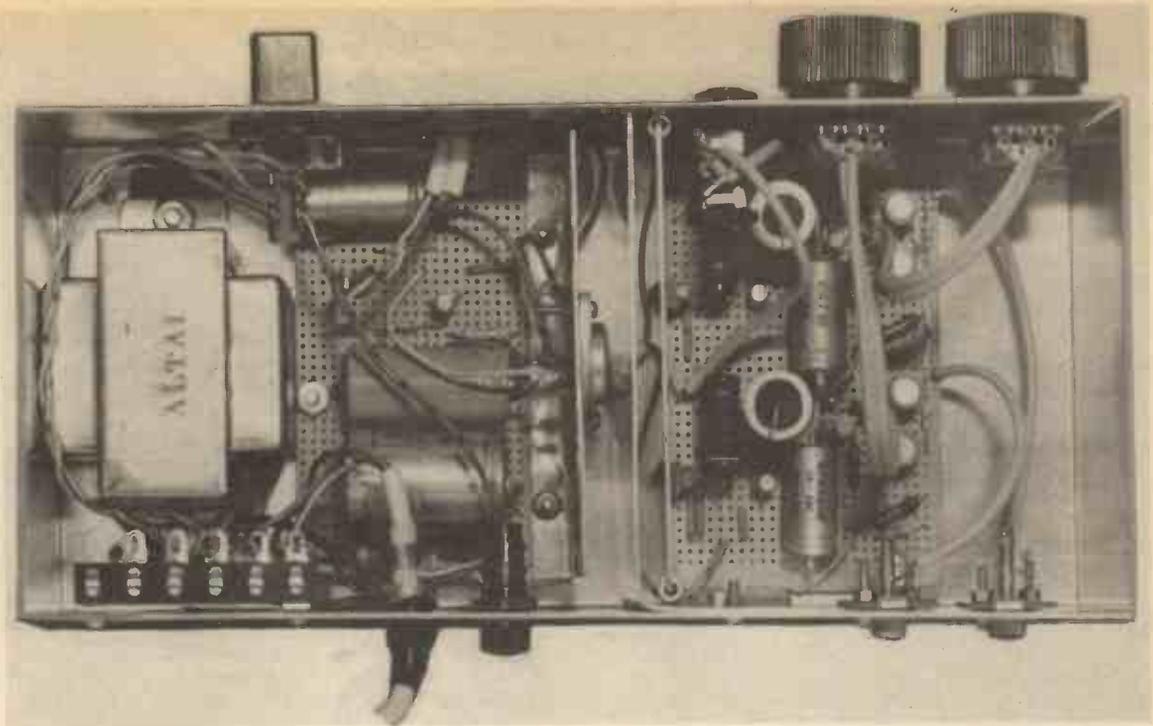


Fig. 1 Single channel of amplifier

TR1 must be biased so that its collector voltage equals half the supply value within 0.5 volts (i.e. between 5.5 and 6.5 volts for a nominal 12 volt rail). If when the circuit is first powered-up this is found not to be so, then the value of R2 should be altered accordingly (reducing R2 will drop the collector voltage and vice-versa).

R3 has the purpose of raising the potential at TR2 base so as to overcome the combined base/emitter voltage drops of this transistor and TR3 (approximately 1.2 volts). In consequence, the potential at TR3 emitter will equal roughly half the supply value also.

#### POWER SUPPLY

Fig. 2 shows the power supply circuit for both channels. The mains input is taken via a double pole on/off switch and fuse to the primary windings of transformer T1. The secondary voltage is full wave rectified by D1 and D2. C6 serves to suppress switching transients, thus eliminating interference and the possibility of damage to other components.

C7 is the main reservoir, or smoothing, capacitor which removes most of the 100 hertz ripple. Transistors TR4 and TR5 form another Darlington pair. The base of TR4 is held at a constant voltage by the potential divider consisting of

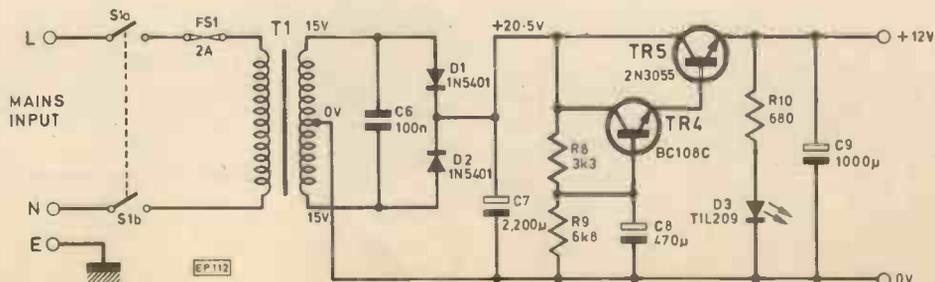


Fig. 2 Power supply circuit for both channels

R8 and R9. It is this resistive divider that determines the final output voltage of the supply. As all ripple is removed from this reference voltage by C8, the 12 volt output appearing at TR5's collector is absolutely hum-free.

A light emitting diode, D3, gives visual indication that the equipment is switched on. C9 decouples the power supply output.

The total current consumption of the stereo amplifier when operating from a 12 volt supply is approximately 260 milliamps (130 milliamps per channel) and the output transistors will dissipate 770 milliwatts each which necessitates the use of a small heat sink. The emitter resistor of TR3 also dissipates roughly 770 milliwatts and a 2 watt power rating has been specified for R7. The series regulator transistor TR5 operates with a potential difference of approximately 8.5 volts between its collector and emitter junctions. Therefore, assuming a supply current of 260 milliamps, this component will dissipate around 2 watts so it will also require a small heat sink.

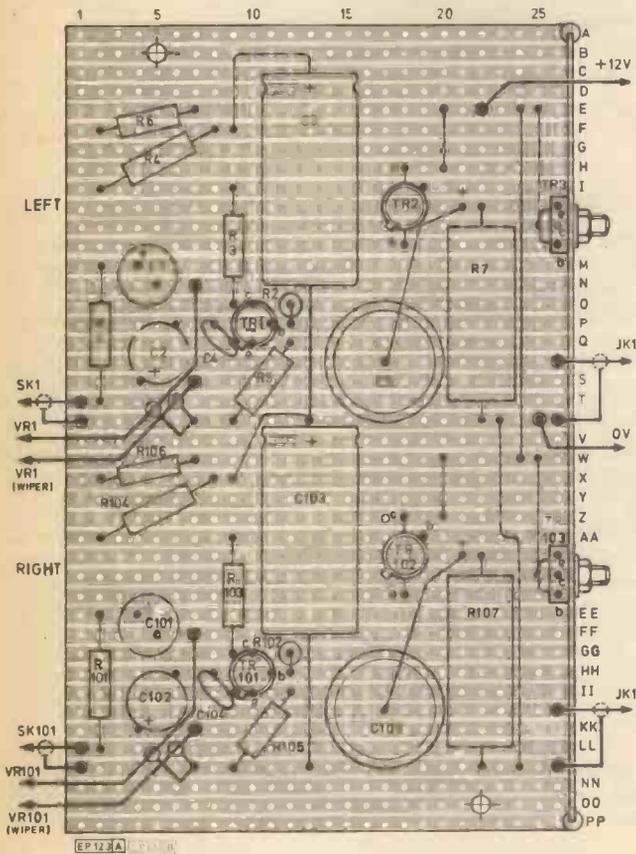


Fig. 3 Layout of stereo amplifier board

## CONSTRUCTION

Most small components which comprise the amplifier and power supply are mounted on two separate pieces of 0.1 inch matrix Veroboard.

The amplifier circuitry can be assembled on a section of approximately  $2\frac{1}{2}$  by  $4\frac{1}{4}$  inches, as shown in Fig. 3. The BD137 power transistors are small plastic encapsulated devices which are easily mounted to a suitable heat sink. A piece of 18 s.w.g. aluminium measuring  $4\frac{1}{4}$  by 2 inches is drilled with two 6BA clearance holes and bolted directly to the output transistors.

The BD137s act as physical supports to this heat sink and it should be noted that the metal face of each transistor, which will come in direct contact with the aluminium, is live at collector potential. As the collectors of both devices are connected to the positive supply rail, this mutual shorting will not affect the amplifiers' operation.

Short lengths of screened cable are soldered to the amplifier board where shown. These provide "flying lead" connections for input, output and volume controls. All resistors, except R2, are mounted horizontally. The leads of R7 should be cut to approximately 1 inch and then bent at right angles to the component body. Using long leads enables this resistor (which runs rather hot) to be mounted well above the Veroboard surface, thus ensuring adequate ventilation. The output coupling capacitors are mounted vertically.

## COMPONENTS . . .

### Resistors

R1, R101	10k
R2, R102	1M5
R3, R103	330
R4, R104	2k2
R5, R105	47
R6, R106	47
R7, R107	47 2W
R8, R108	3k3
R9, R109	6k8
R10, R110	680
All $\frac{1}{2}$ W carbon, 5%	

### Potentiometers

VR1, VR101	47k log
------------	---------

### Capacitors

C1, C101	10 $\mu$
C2, C102	10 $\mu$
C3, C103	220 $\mu$
C4, C104	100p ceramic
C5, C105	470 $\mu$ elect. 12V
C6	100n
C7	2,200 $\mu$ elect. 25V
C8	470 $\mu$ elect. 25V
C9	1,000 $\mu$ elect. 25V

### Semiconductors

TR1, TR101	BC108C (2 off)
TR2, TR102	BC108C (2 off)
TR3, TR103	BD137 (2 off)
TR4	BC108C
TR5	2N3055
D1	1N5401
D2	1N5401
D3	TIL209

### Transformer

T1	Pri. 240V; Sec. 15-0-15V 1A
----	-----------------------------

### Miscellaneous

FS1 (2A) fuse plus chassis mounting holder, tag strip, Veroboard, miniature audio coax cable, phono sockets (chassis mounting), stereo jack socket (chassis mounting), clip-on heat sink, four rubber feet, knobs, aluminium box  $10 \times 4\frac{1}{2} \times 3$ in.

The power supply circuit board (Fig. 4) measures approximately  $3\frac{3}{4}$  by  $2\frac{5}{8}$  inches and carries all components shown in Fig. 2 except D3, S1, T1 and FS1. TR5, the series regulator transistor, is mounted on its own aluminium heat sink. This heat sink, which measures  $3\frac{3}{4}$  by  $2\frac{5}{8}$  inches,

# News Briefs

## JAPANESE PRODUCTION IN USA

A \$4m investment by Hitachi to establish a facility for the production of colour television sets and home appliances at Compton, California, has resulted in the birth of "Hitachi Consumer Products of America Inc." Initially with 120 employees, operations are expected to commence in January 1980, with partial operation starting this August.

## YORKSHIRE COMPUTER CLUB

THE South Yorkshire Personal Computing Group (SYPCG) has been formed for the d.i.y. microprocessor and computing enthusiast. Initially the group will meet on the second Wednesday of each month at Sheffield University, and membership for 1979 has been set at £3 (nominal charge only for those still at school).

Details: Tony Rycroft, SYPCG Secretary, 88 Spinneyfield, Moorgate, Rotherham, S. Yorks.

## A FLUKE OCCURRENCE

A NEW service centre has been opened by Fluke, based near Manchester. The full address is: Fluke International Corp, Middle Floor, Mersey House, 220 Stockport Road, Stockport, Cheshire

## FAST DELIVERY

A NEW service called "Datapost" now replaces the Securicor service previously in operation at RS Components. Orders received at London, Birmingham or Manchester before 3.30 p.m. will normally be delivered the next day (Mon-Fri), with Saturday delivery if requested. Datapost should be specified when ordering, whereupon a nominal charge of £1 plus standard rate VAT will be made irrespective of the number of parcels to be despatched.

## FIGHT-IT-YOURSELF

THE mechanical and electrical appliances which fill our homes, we all know can do anything. Freeze, fry, wash, dry, suck, blow, entertain, sew. What we don't know is that these contrivances talk to each other after we go to bed. The subject of discussion at their meetings each month is, naturally, the most inconvenient time to break down. A decision to fail might depend upon the holiday plans of your regular plumber, or the approach of a Bank Holiday. Two or three contraptions might simply agree to break down simultaneously. And the mower having chugged past your window while you sleep, to attend the kitchen summit, might suggest burning out at the height of the growing season.

After the blows have been dealt you contact a service engineer, for whom you may await the non arrival of repeatedly. When he turns up, one of two things will happen. He shakes his head and tells you it would cost more to repair than buy a new one, or the machine offers up a fault for him to find, to which he responds, "Ah, I can see what's wrong." He fixes it. Unfortunately this fault had nothing to do with the original trouble, and the machine ceases to operate again once the serviceman has left.

A new idea which may be the answer to the expense and uncertainty of picking telephone numbers from the Yellow Pages is MAC (Mutual Aid Centre), where £1 will buy you three hours in a kind of public workshop in which you can do-it-yourself! You might shudder, but skilled supervision and the right tools are part of the deal. The only additional expense is the prerequisite of being a member, costing £2 per annum (£1 for pensioners). The first MAC is in Longden Coleham, Shrewsbury, but it is hoped that they will eventually become as commonplace as public libraries. Open six days a week and nine hours a day, the first centre is expected to run training courses on the premises, in conjunction with Shrewsbury Technical College. The workshop has been launched by the Mutual Aid Centre, the London-based charity founded by Michael Young, originator of "Consumers' Association" and "Which?" magazine.

cannot be made self supporting and so the bottom  $\frac{3}{8}$  inch is bent at right angles to form a bracket. Two fixing holes then enable it to be bolted to the edge of the Veroboard. Mounting holes are also drilled for TR5. The case of this transistor forms its collector connection and a solder tag affixed to one of the mounting bolts provides a collector terminal. This heat sink, therefore, is also live.

The amplifier was enclosed in a standard aluminium box measuring 10 by  $4\frac{1}{2}$  by 3 inches. The two circuit boards can be affixed to the bottom of the case using 4BA nuts and bolts. Spacers are employed here to ensure separation of the Veroboard underside from the metal base. An aluminium screen is provided where shown in order to isolate the amplifier and power supply sections.

Chassis mounting phono sockets provide input connections and automatically give an earthing contact to the amplifier case. A stereo jack socket forms the standard headphone outlet.

A 3 core mains lead enters the power supply section through a sleeved rubber grommet and is terminated at a


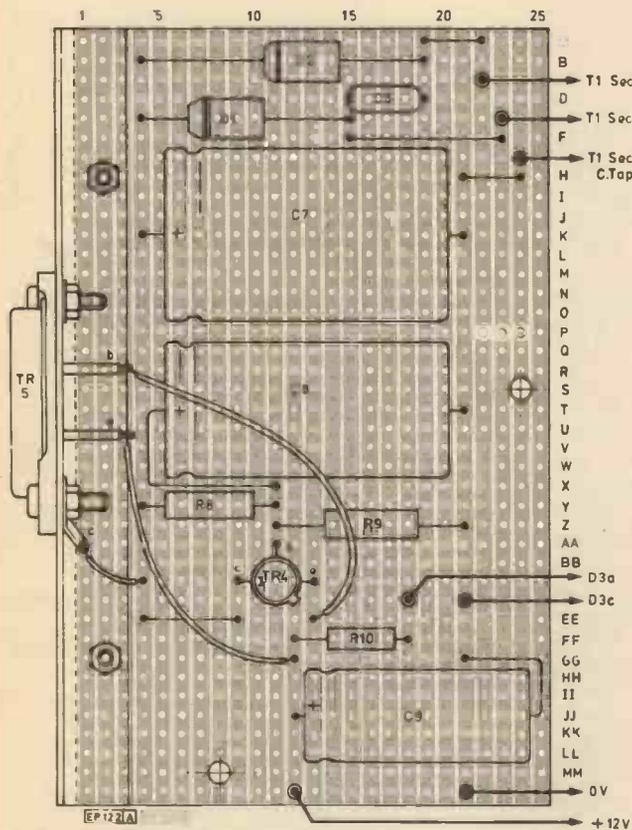


Fig. 4 Layout of p.s.u. board

tag strip. An earthing point is available on one of the end tags which will be bolted directly to the metal casing.

A small light emitting diode, is pushed through a  $\frac{1}{8}$  inch hole drilled into the casing. It can be held in place with a blob of Araldite.

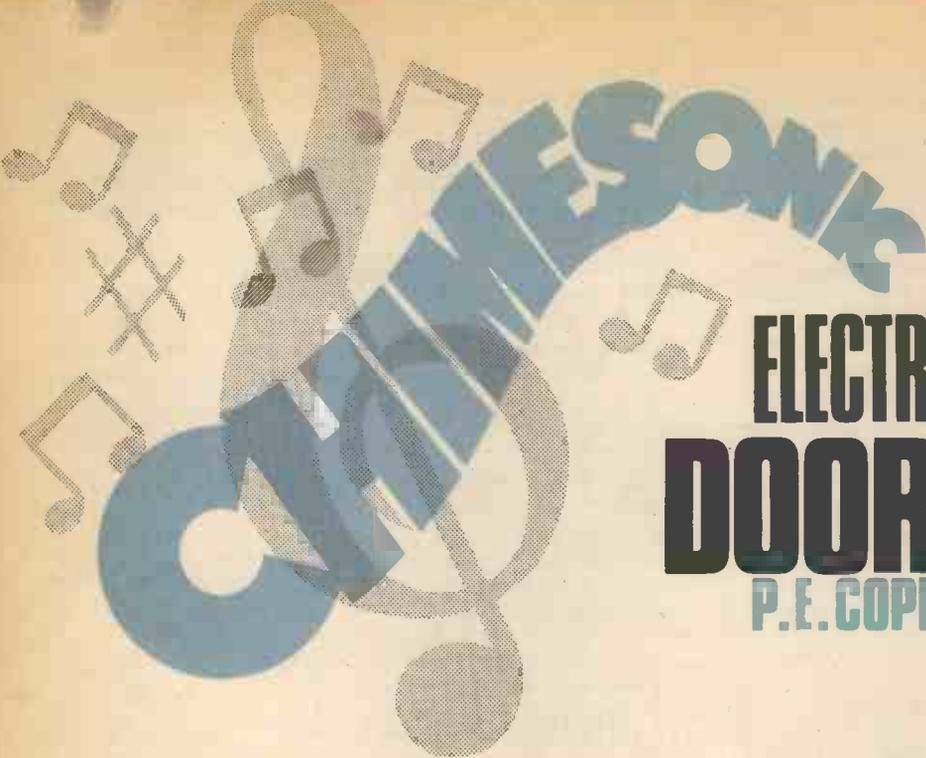Finally, four rubber feet are affixed to the base of the aluminium box with large self tapping screws. Ventilation holes were not drilled into the casing of the prototype as they reduce screening. But the underside of the casing lid has been painted matt black to assist transfer of heat from within the amplifier. ★



# ELECTRONIC DOOR CHIME

P.E. COPELAND

**T**HE Chimesonic is a nine note electronic door chime which can be powered by either battery or transformer and its design enables it to be easily installed or substituted for most existing door chimes or bells without rewiring. The Chimesonic unit enables a variety of melody modules to be plugged in so that the tunes can be varied to suit taste, occasion or season. These modules consist of a number of diodes and pre-sets which are simply adjusted to the particular note required. The same module can thus be "retuned" when a different melody is required or a selection of modules can be built-up and pre-tuned ready for use.

Installing the chime is quite straightforward since it will work from either a battery or transformer and can be operated from the simple type of push switch or the illuminated kind. The connections to the unit are marked on the p.c.b. and made using a standard 2A 6-way strip connector.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the Chimesonic is shown in Fig. 1 and circuit diagram of the melody module in Fig. 2.

If the unit is being used with a simple push switch, the power supply can either be a 9V battery (PP6) or alternatively a transformer supplying between 6 and 8V at  $\frac{1}{2}$ A. If an illuminated bell push is being used a transformer supplying 8V at 1A is required. It is important to remove the fuse (FS1) for battery operation in order to conserve battery life.

The tempo generator produces a clock pulse, which determines the "beat" of the melody. If required this can be varied by altering the value of C3 and/or C4. The clock pulse drives IC3 which is a CMOS decade counter decoder. Each of the counter outputs go high in turn and drive their respective presets (VR1 to VR9) on the melody module to produce a series of notes.

The note generator is the familiar 555 timer with VR1 to VR9 each forming the variable element of the CR network when each counter output becomes active. The overall pitch of the melody is determined by C6 and although this could be varied, it will be found that a 100nF capacitor enables a good range of notes to be obtained simply by adjusting each of the presets on the melody module.


An output of sufficient drive for a number of speakers is provided by TR5 and TR6. With an 8 ohm load the output is approximately 2W square-wave and this is more than adequate for most applications. Should additional speakers be required these should be connected in series. The output loading is not critical (4 ohms min.) and a speaker or combination of speakers up to 80 ohms total impedance may be connected to still produce an adequate volume level. Remember to connect a link wire between terminals D and Ext Spk on TB1 if an extension speaker is not being used.

A staccato effect is made possible by joining the connections 3 and 17 on the melody module. This separates each note from the next and may be useful during tuning even if it is not used in the final melody.

If a 470nF capacitor is connected between pin 3 and 17 on the melody module an "echo" effect can be obtained.

The supply voltage is applied to the regulating circuit formed around TR3 and TR4. Diode D10 prevents possible damage due to the battery being incorrectly connected.

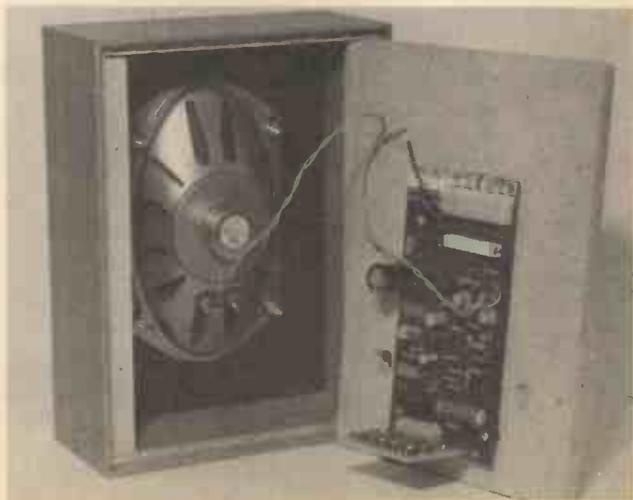When TR4 is conducting the Zener diode D15 will maintain the voltage at the emitter of TR3 at 5V.



For TR4 to conduct, the voltage at its base must be low (ie 0V). This is achieved initially by the action of the push switch which when pressed connects the base of TR4 via R13 to the 0V rail. This action enables TR3 to supply a regulated voltage of 5V to the circuit which is maintained by the operation of IC1, IC2 and TR2.

IC2 is a monostable which is arranged to trigger whenever the regulated voltage is applied. This is achieved by the capacitor C5 charging via R3. A rising voltage thus appears at the Schmitt input of monostable IC2 (pin 5). At a certain threshold voltage the input triggers the monostable and a pulse (Q pin 6,  $\bar{Q}$  pin 1) of duration determined by C7 and R8 is produced.

The negative going pulse ( $\bar{Q}$  pin 1) is applied to the "set" input of IC1 (pin 9) and the bistable is latched to give a "high" output (+5V) on pin 8.

This "high" output drives the base of TR2 which is turned on maintaining the regulated supply to the circuit.

formed from the remaining gates of IC1. This output goes "high" due to the action of IC2 when the push switch is pressed.

One output of the astable multivibrator is taken to the "clock" input (pin 14 of IC3) which is a CMOS decade counter/decoder. This same output is also taken to the melody module socket (SK1).

The "clock enable" input (IC3 pin 13) is held "low" (0V) and the decade counter IC3 counts on the positive going edges of the pulses from the astable multivibrator.

Initially the Q output (high) generated by IC2 on switch-on is applied to the "reset" input of IC3. This ensures "count" output '0' in "high" and "count" outputs '1' to '9' are "low" immediately after the push-button is pressed.

Each of the ten "count" outputs of the counter/decoder IC3 go "high" (5V) in turn. "Count" outputs '0' to '8' are

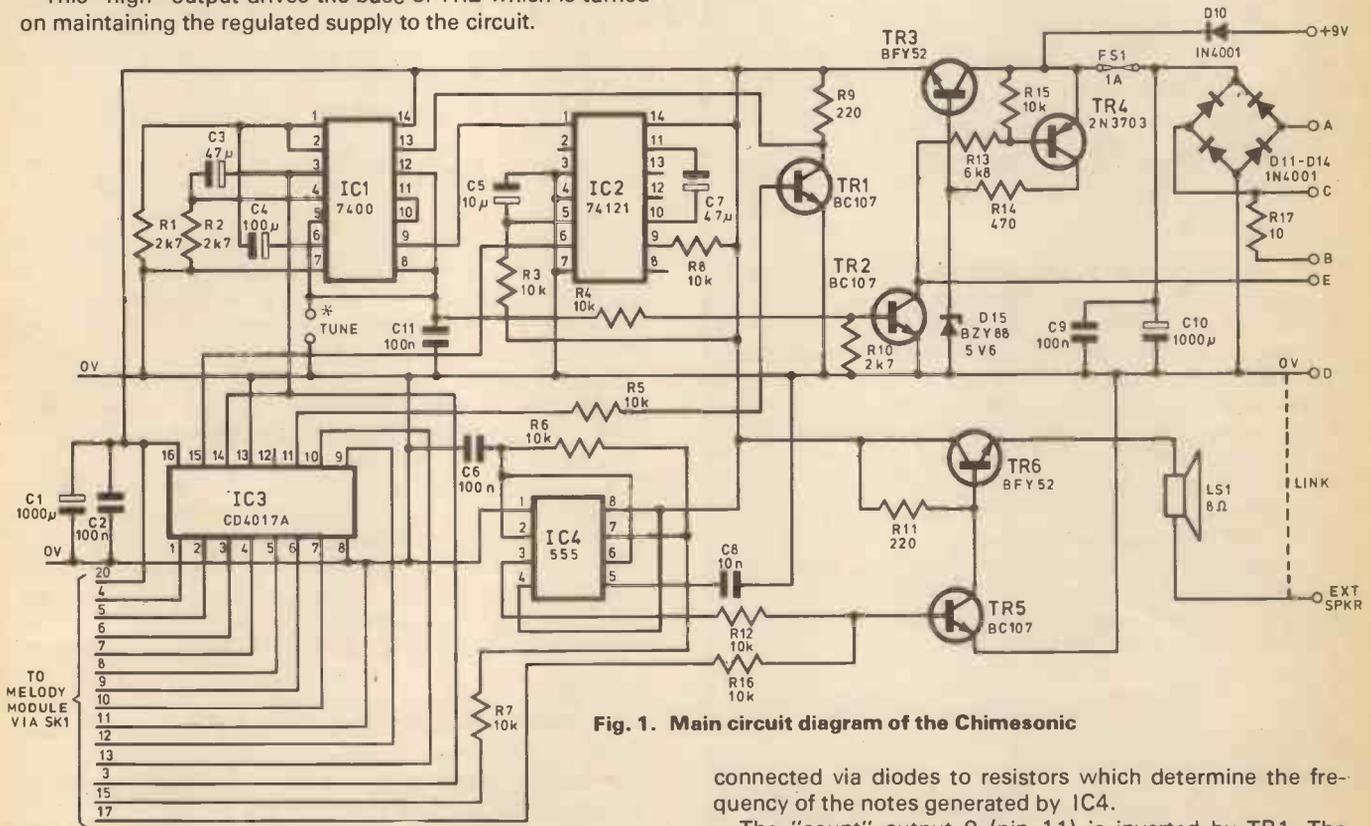


Fig. 1. Main circuit diagram of the Chimesonic

connected via diodes to resistors which determine the frequency of the notes generated by IC4.

The "count" output 9 (pin 11) is inverted by TR1. The arrival of "count" 9 thus causes the voltage at the collector of TR1 to go "low". Since this voltage is applied to the "reset" input (pin 13 IC1) of the bistable ( $\frac{1}{2}$  IC1) the bistable changes state causing the Q (high) output to go "low". This action inhibits the astable multivibrator ( $\frac{1}{2}$  IC1) and switches TR2 off. The voltage at the emitter of TR3 falls to zero unless the illuminated push switch is used. In which case the circuit remains on but the output remains silent since the tempo generator is inhibited and the count remains at 9.

#### NOTE GENERATOR

The notes played by the Chimesonic are generated by IC4 and their frequency is determined by the value of the particular resistor being driven by the IC3 counter/decoder.

The overall pitch of the notes is determined by the values of VR1 to VR9 which are adjusted according to the melody required.

For melodies containing "rests" the particular preset and diode is not present at the "count" output (IC3) at which the "rest" occurs.

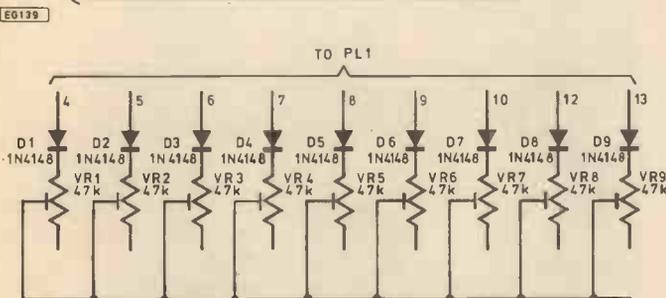


Fig. 2. Circuit diagram of the melody module.

#### TEMPO GENERATOR

Two gates of IC1 are used to form an astable multivibrator together with R1, R2, C3 and C4. Capacitors C3 and C4 may vary in value to those given in the components list to meet the tempo of the melody played. The astable is enabled when the input to pin 5 (IC1) goes "high" (+5V). This is achieved by using the Q output (pin 8 IC1) of the bistable

For melodies of less than nine notes certain resistors and their associated diodes are not included in the melody module circuit.

If it is necessary at some stage to retune notes then increasing the value of the presets concerned (VR1 to VR9) will lower the respective notes, and decreasing the resistor value will make the note higher.

For tuning purposes two small pins (Tune) are provided next to IC2 on the p.c.b. When these are linked together this

## COMPONENTS . . .

### Resistors

R1, R2, R10	2k7 (3 off)
R3, R4, R5, R6, R7	10k (9 off)
R8, R12, R15, R16	
R9, R11	220 (2 off)
R13	6k8.
R14	470
R17	10 7W

All resistors  $\frac{1}{4}$ W except where otherwise stated.

### Potentiometers

VR1-VR9	47k min. hor. preset (9 off)
---------	------------------------------

### Capacitors

C1	1000 $\mu$ 10V elect
C2, C6, C9, C11	100n 250V polyester (4 off)
C3, C7	47 $\mu$ 10V elect (2 off)
C4	100 $\mu$ 10V elect
C5	10 $\mu$ 10V elect
C8	10n 250V polyester
C10	1000 $\mu$ 16V elect

### Semiconductor

D1-D9	1N4148 (9 off)
D10-D14	1N4001 (5 off)
D15	BZY 88 5V6 Zener
TR1, TR2, TR5	BC107 (3 off)
TR3, TR6	BFY 52 (2 off)
TR4	2N3703
IC1	7400
IC2	74121
IC3	CD4017A
IC4	555

### Miscellaneous

20mm fuse  
Fuse holder  
LS1 8 $\Omega$  loudspeaker and case  
Battery connector  
Battery PP6  
Veropins  
Terminal block (6 way) 2A  
Plug and socket 0.1in 20 way (RS 488-365)  
i.c. holders (if req)  
Transformer\*

\* See text

inhibits the astable multivibrator and enables each note to be held whilst being tuned. To facilitate tuning solder a short wire to the pin marked with an asterisk on the p.c.b. layout.

### OUTPUT STAGE

The output from the note generator IC4 (pin 3) is taken via R12 to the base of TR5. This transistor is used to provide enough voltage and current drive for the output transistor TR6. Both TR5 and TR6 are operated in the switching mode and thus the final output is square-wave.

Loudspeakers for Chimesonic should present an emitter load of approximately 8 ohms to TR6. Additional loudspeakers may be connected in series by replacing the wire link joining the terminals 'D' and 'ext spkr' with the leads from the extension loudspeaker(s). The impedance of the extension speaker is not critical and acceptable volume levels can be obtained with up to 80 ohm loading.

Alternatively the extension speaker output can be used to drive additional amplifiers for PA applications etc. For this application connect the unit into the high level input of the amplifier and take the screen of the connecting cable to the terminal labelled D, and the signal core to the 'ext spkr' terminal. A load resistor of 22 ohms may be substituted for the internal speaker if this sound source is not required.

### CONSTRUCTION

The main p.c.b. of the Chimesonic is shown in Fig. 3 with the component overlay shown in Fig. 4. It is recommended that i.c. holders are used especially for IC3 since this is a CMOS device which should be placed in the circuit after the rest of the construction work is completed.

The melody module p.c.b. and overlay are shown in Fig. 5 and Fig. 6.

The use of Veropins or similar is recommended for the battery leads termination points, speaker connections and Tune contacts.

The p.c.b. has been designed to enable the constructor to have a choice in the melody module connection method. In the prototype a 20 way plug and socket was used. The socket should be mounted on the p.c.b. and the plug soldered onto the module board.

Alternatively the p.c.b. itself may be the 0.1 edge plug mating with an edge connector mounted on the module board. The first method is preferred since mating connection is positive via gold contacts.

If an illuminated bell push is to be used the 8V 1A transformer should be connected to terminals A and B with the bell push connected to terminals A and C. Terminals D and E should be linked together and the fuse (FS1) inserted in the p.c.b. fuse holder.

The lamp in the bell push together with R17 form a circuit driven by the a.c. voltage applied to terminals A and B.

### TUNING

An appropriate tuning procedure for the Chimesonic is shown in Table 1

1. Temporarily link together the two Tune pins next to IC2 on the p.c.b.
2. Press the push-button and keep it pressed.
3. The first note will be heard constantly and it can be varied in frequency by altering the value of the resistor connected to the 'O' "count" output.
4. Remove the wire and the next note should be heard. If it is not bring the wire briefly in contact with the end of the resistor R8.
5. As soon as the note is heard link the two Tune pins again. The note for "count" output '1' (IC3) will now be held and the value of the resistor connected to "count" output '1' can be altered as necessary.
6. This procedure is continued and the link is removed and replaced for each count.
7. If any note is missed then the link must be removed and the sequence begun again.

TABLE 1

The "tempo" of the melody is determined by C4. A higher value capacitor will slow the tempo—a lower value will quicken it. ★

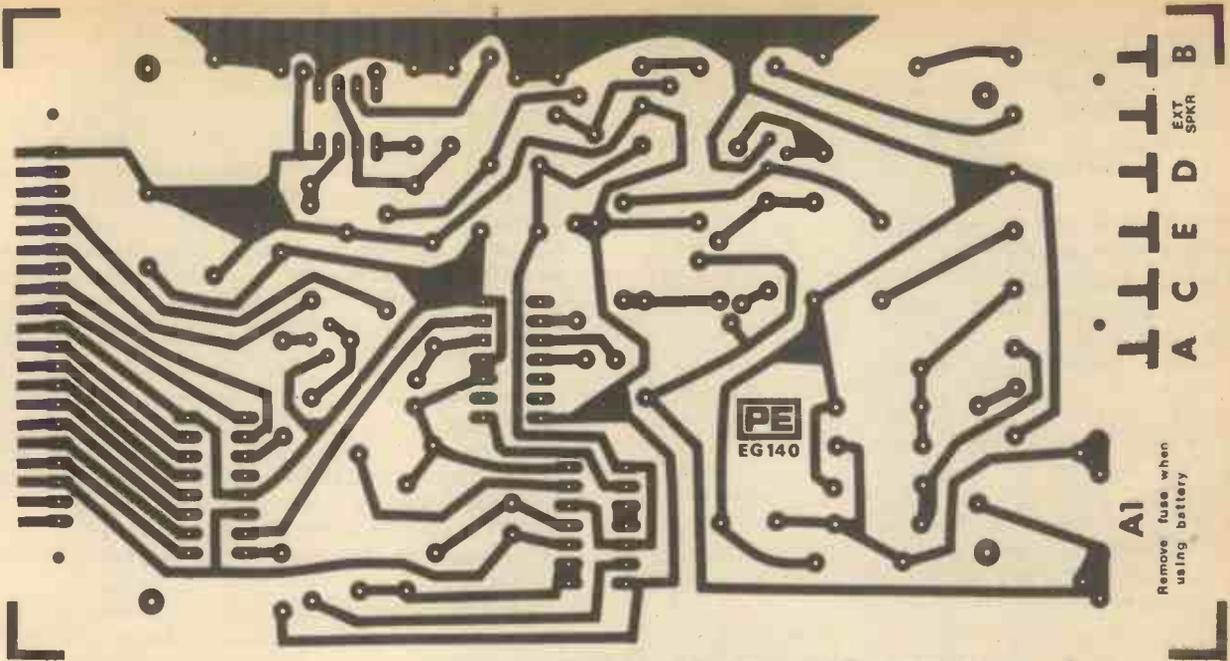


Fig. 3. P.c.b. layout for the Chimesonic

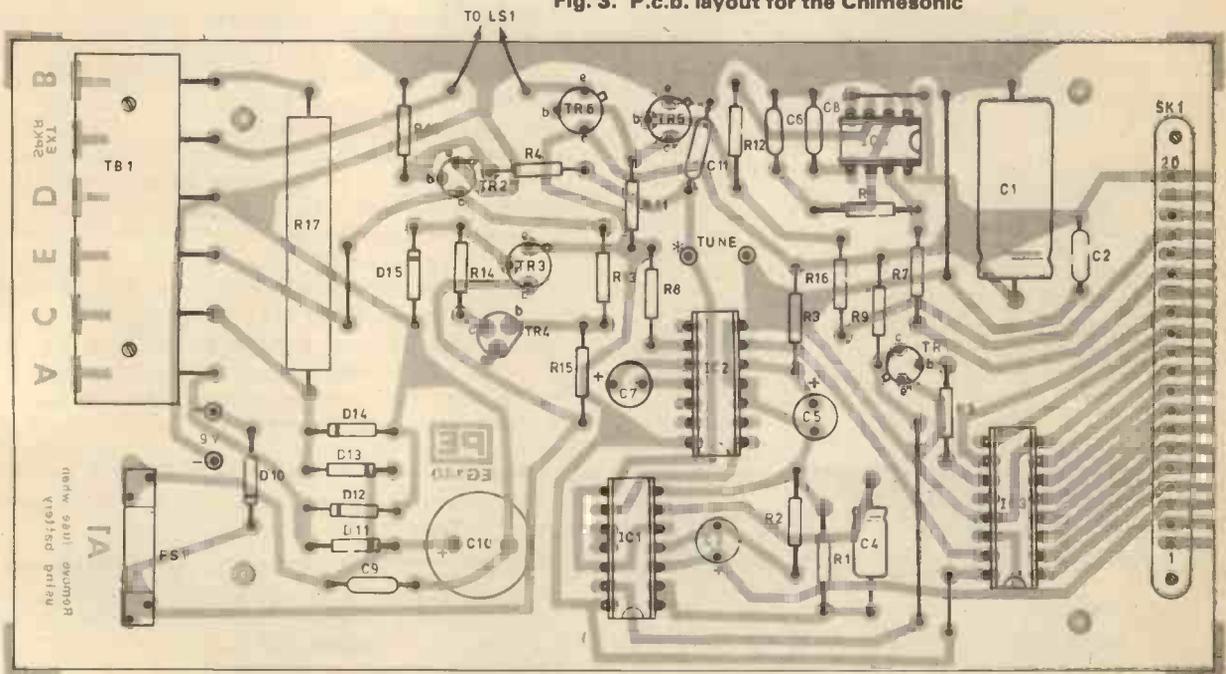


Fig. 4. Component overlay

EG141

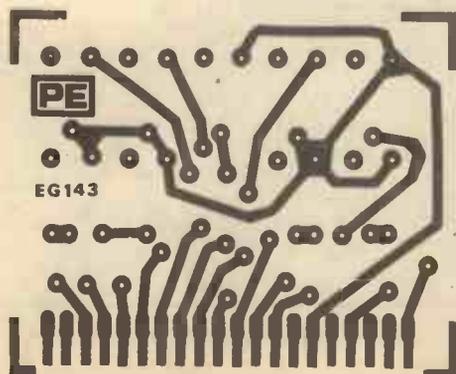


Fig. 5. P.c.b. layout of melody module

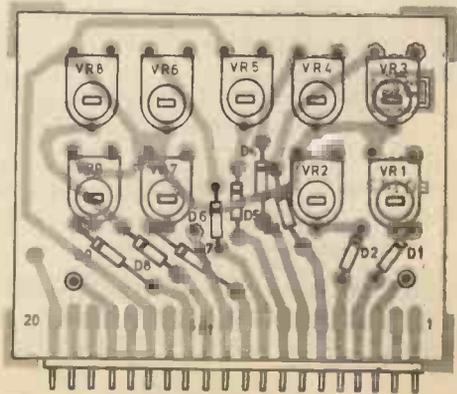


Fig. 6. Component overlay



# BOOK REVIEWS

## RADIO AMATEURS' EXAMINATION MANUAL

By G. L. Benbow, G3HB

R.S.G.B., 35 Doughty St., London WC1N 2AE

120 pages; paperback; 248 by 184mm; 8th edn; 1979

£1.85 (£2.16 from RSGB inc. p&p)

THE standard work for all would-be licensed radio amateurs studying for the UK Radio Amateurs' Examination, which has also proved popular in other countries which have similar licensing examinations.

This edition has been completely revised in order to take account of the current changes in RAE format and syllabus. A valuable feature is the provision of two sample examination papers, each containing 95 multiple-choice questions, answers being given separately.

Chapter titles are: Becoming a radio amateur: Electrical theory and calculations; Semiconductors; Radio receivers; Transmitters; Power supplies; Propagation and antennas; Transmitter interference; Measurements; Licence conditions; Operating practices and procedures; Tackling the Radio Amateurs' Examination; plus four appendices.

## THE BASIC COOKBOOK

By Ken Tracton

Published by Tab Books

138 pages. Price £3.60

ORIGINALLY developed in the 1960s at Dartmouth College, by John Kemeny and Thomas Kurtz, the programming language BASIC has grown to become the primary home computer language today, and although rivals are appearing, anyone contemplating involvement in small business and home computing can ill afford to ignore it.

The book does not take you through the list of commands beginning with the simplest, but curiously goes through them alphabetically. This does however, allow quick reference to a particular command should you forget what it does, and examples with flow charts accompany each one. Basic is an easy language to learn, requiring no specialised knowledge, and the complexity of programs possible, built on simple instructions, is limited only by the logic and clarity of thought of the programmer. If you digest the contents of this book there should be nothing but "hands on" time between you and fairly complex programs.

There is one instruction not covered in the Basic Cookbook which you will find on a personal computer such as the Commodore PET, and that is GET, which enables the user to input single characters without hitting the Carriage Return key. This facility speeds up graphical games considerably, but unlike the INPUT instruction, requires a loop in the listing to operate successfully. The TRS-80 equivalent is INKEY\$.

This is a good clearly laid out book, which of course, is what the beginner needs!

M.A.

## ILLUSTRATED DICTIONARY OF MICROCOMPUTER TERMINOLOGY

By Michael Hordeski

Published by Tab Books (available W. Foulsham, Slough)

322 pages. Price £5.75

JUST when you think you've caught up on all the buzzwords and abbreviations used in microcomputer terminology, you read something like this:

*Fully edified 8K system with Line Queue Multiplexing for the low end ZIF users, complete with turbulation shift and dummy-zero interpreter.*

In fact, the above might be nonsense, but a newcomer to the technology could be forgiven for reading it and going away convinced if a little confused. The only answer to this state of affairs is to get yourself a comprehensive microcomputer dictionary, and with 4,000 terms listed, this one is as good as I've seen yet, although I was surprised to find CUTS missing!

Armed with this illustrated reference you can blast your way through OEMs (original equipment manufacturer), KSR teletypewriters (keyboard send/receive), PLAs (programmed logic arrays), and PIAs (peripheral interface adapters). In an instant, you would discover that not only magazines have editors, how machines shake hands with each other, and that the above, in *italics*—is a leg pull. Recommended.

M.A.

# POINTS ARISING

## METERMATE (July 1979)

The printer has reversed (left-to-right) the stripboard part of Fig. 8, so that the track cuts as shown are meaningless.

Any constructor requiring a correct copy of this can obtain one from the editorial offices at Poole.

## AUTORANGING MULTIMETER (April 1979)

The Precision Monolithics Inc. REF-02 is *not available from Bournes Ltd.* (PMI agent) of Hounslow, to the amateur in one-off quantities, but may be obtained from **Ace Mailtronix Ltd., Tootal Street, Wakefield, West Yorkshire, WF1 5JR.**

## GUITAR SOUND MULTIPROCESSOR (Dec. 78)

In Fig. 3 R1 should be 10k $\Omega$ . In Fig. 14 R53 is 100 $\Omega$  not 100k $\Omega$  as in the components list.

## CONSTANT DISPLAY FREQUENCY METER

(August 1978)

In Fig. 4, a wire should be shown connecting the mains earth tag at IC17 to the negative terminal of C4.

## ULTRASONIC REMOTE CONTROL (June 1979)


Transistor TR1 which is adjacent to TR2 in Fig. 4 is incorrectly annotated, it should be TR3. In the same diagram C1 should be C7. C1 which can be mounted off the board should have its positive terminal connected to the cathode of diode D1 and its negative terminal to the anode of diode D4.

## SOUND OPERATED SWITCH (May 1979)

Operation of the Sound Operated Switch is improved by wiring an OA47 diode with its anode to IC2 pins 6 and 7, and its cathode to the junction of IC1 pin 7 and IC2 pin 2. This is easily carried out on the top side (component side) of the board using the lead to R12 (10k $\Omega$ ) and the wire link between IC1 and IC2. Alternatively, the diode may be wired to the under side (copper track) of the p.c.b. This modification ensures that C6 does not start to charge until the audio input falls below the threshold level. The diode holds down the voltage across C6 until the output voltage from the comparator, IC1(b), goes high.


The sensitivity of the device can be increased when using low impedance inputs by reducing the value of R1 to 1k $\Omega$ , or less.

# Three Trumps from Acorn

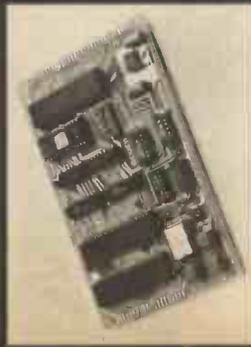
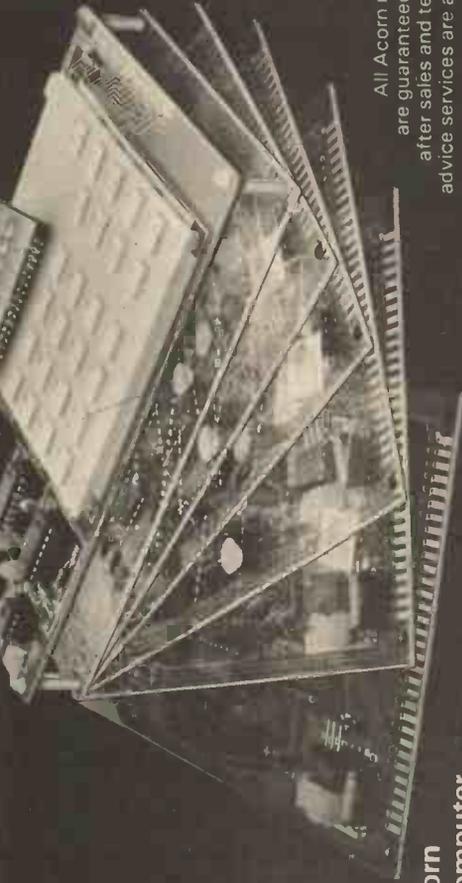
## Acorn Controller

Designed as an industrial controller module, it is based on the 6502 CPU with 2K Eprom, 1-25K ram and 32 I/O lines. In eurocard format it is provided with an onboard monitor (2 x 74S571) giving comprehensive development and debugging facilities. Also available in minimum configuration for low cost OEM applications.



## The Acorn Microcomputer

The Acorn controller module mounted beneath a matching eurocard with hex keyboard, 8 digit seven segment display and CUTS tape interface requires only a single unswitched power supply to form the powerful Acorn microcomputer.


All Acorn modules are guaranteed and full after sales and technical advice services are available.

Although designed for expandability, the Acorn Microcomputer is a complete development system for the Acorn controller and together with the Acorn Users Manual, provides the perfect introduction to hex programming; the carefully optimised monitor has the following functions:

- System Program
- Set of sub-routines for use in programming
- Powerful de-bugging facility displays all internal registers
- Tape load and store




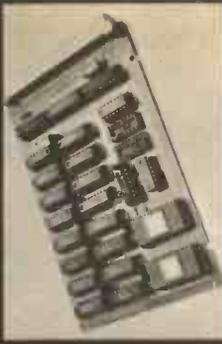Software available soon includes 4K Editor Assembler-Disassembler, 4K Proprietary Fast Basic, Disc operating system with full file handling. Although a standard strip of


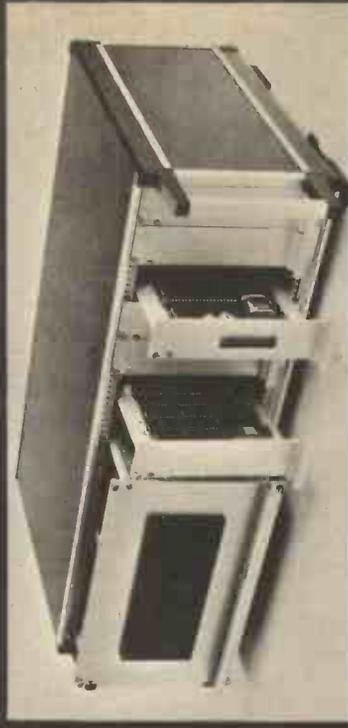
## Acorn Memory

The first in our series of expansion cards is the Acorn 8K + 8K "state of the art" memory module. On a matching eurocard it provides 8K of ram (2114) and 8K of Eprom (2732) or 4K of Eprom (2716). It requires a single 5V rail, is designed for direct connection via a 32 way edge connector to the Acorn bus and is fully buffered for wiring into any system. Two onboard sockets provide independent positioning of Eprom and ram.



veroboard is all that is required for a full backplane, a racking system can be made available by Acorn Computers. The rack shown includes the VDU interface, two memory cards and dual floppy disc interface.

## ACORN COMPUTERS LTD.

4A Market Hill, Cambridge, Cambs.

### Order form

Send to: Acorn Computers Ltd. 4A Market Hill, Cambridge, Cambs.

- (qty) Acorn Microcomputer(s) in kit form at £65.00 plus £5.20 VAT
- (qty) Acorn Microcomputer(s) assembled and tested at £75.00 plus £6.00 VAT
- (qty) Acorn controller(s) (minimum configuration) at £35.00 plus £2.80 VAT
- (qty) Acorn Memory(s) assembled and tested at £95.00 plus £7.60 VAT

N.B. Price shown is for full 8K of ram, prices for smaller memory options and Eprom additions available on request.

Enclose a cheque for £..... made out to Acorn Computers Ltd.

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

PE8

Regd No  
1403810



# Digital accuracy. Analogue price!

The new Fluke 8022A DMM now offers the best  
of both worlds at only

**£89**

#### CRISP LCD DISPLAY

Automatic polarity indication plus auto-zeroing  
"BT" Low battery indications when 20 hours remain.

#### 6 RESISTANCE RANGES

200  $\Omega$  to 20M  $\Omega$  In-circuit test of semi-conductor junctions available on 3 ranges.

#### 8 CURRENT RANGES

From 2mA to 2A AC or DC.  
10A Current SHUNT available.

#### 10 VOLTAGE RANGES

200mV-1000V DC  
or 750V AC.

#### POCKET SIZE

Lightweight unit only  
370gms

#### FULL OVERLOAD PROTECTION

Will withstand 6kV spikes.

#### RUGGED CASE

Meets tough mil-Specs - virtually  
indestructible.

It's true! The 8022A brings you digital precision and ruggedness—at analogue prices, from the world leader in digital multimeters.

Featuring the Fluke in-line pushbutton concept for easy single handed operation this pocket sized lightweight meter has a 0.25% DC accuracy, incorporates a custom designed CMOS chip for low power consumption and offers a full two year warranty.

For only £89.00 you can now hold the world of measurement in the palm of your hand.

**FLUKE** No.1 in DMM's

Fluke International Corporation, Colonial Way, Watford, Herts. WD2 4TT. Telephone: (0923) 40511. Telex: 934583

Also available from ITT Instruments Services, Harlow, Essex.

Northern Ireland and Eire contact Euro Electronic Instruments, 32 Brews Hill, Mavan, County Meith, Eire.

# 8022A Checklist

Whether you are buying your first multimeter or moving up to digital from analogue, check these features against your existing meter.

- |  |  |
|--|--|
|  | ? 8022A  |
| FULL 2 YEAR WARRANTY.  | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| 1 YEAR GUARANTEED ACCURACY FROM 18°C to 28°C.  | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| DROP PROOF! Meets tough Mil-Spec tests for shock & vibration.                            | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| 10 times better Accuracy than most analogue meters.                                      | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| Single handed operation.   | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| USER PROTECTION!<br>Recessed input jacks and new Fluke designed safe test leads.         | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| PROTECTED THREE WAYS against accidental over-voltage, over-current and transient to 6kV. | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| Easily accessible battery and current fuse.  | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| 200 Hours continuous operation plus "BT" low battery volt indication.                    | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| Handy size. Fits easily into pocket, brief-case or toolbox.                              | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| Large, readily available range of accessories.   | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| Worldwide parts and servicing facilities.  | <input type="checkbox"/> <input checked="" type="checkbox"/> |
| Price £89.00 complete with test probes.  | <input type="checkbox"/> <input checked="" type="checkbox"/> |

**A no compromise Digital Multimeter at an analogue price.**



Hello everybody – we're back again!

## SEIKO 20% off!

### LATEST MODELS – LOWER PRICES

Japanese versions – similar to UK models listed.  
 GG003 Chronograph (RRP £69.50) £55.50  
 GD007 Chronograph (£92.50) £74.00  
 FW007 Alarm/Chronograph (£115) £92.00  
 GC003 Programmable Alarm/Chrono (£135) £108.00  
 FX003 Memory Bank (£130) £104.00

### LCD PROGRAMMABLES

with non-volatile Stores and Memories and almost infinite programmability (Using FA-1)

#### FX-501P

128 steps  
 11 memories  
 5 levels ( )  
 RRP £59.95  
**£49.95**



#### FX-502P

256 steps  
 22 memories  
 10 levels ( )  
 RRP £79.95  
**£69.95**

FA-1 Adaptor  
 RRP £24.95  
**£19.95**

### LATEST LCD SCIENTIFICS

#### Casio's new FX-68 Mini Card



37 Scientific functions including trigs, logs, exponentiations. Statistical – standard deviations. Polar to Rectangular, R-P and sexagesimal conversions. Pi cube, root, 6 levels of parenthesis, full memory. 500 hours continuous use battery life. A very convenient 3/16" x 21/8" x 35/8". Complete with wallet. RRP £24.95 **£19.95**

FX-80 Specification as above plus Engineering key, 4000 hour battery life from 2 x AA size batteries. 3/4" x 3" x 5 1/4".  
 RRP £21.95 **£16.95**

FX-48 (£18.95) £14.95. FX-58 (£29.95) £24.95.  
 FX-2500 (£24.95) £19.95. FX-3100 (£28.95) £23.95.  
 FX-8000 (£35.95) £29.95.

#### CASIO calculating Alarm Clocks

CQ-81 (£18.95) £14.95. CQ-82 (£24.95) £19.95  
 AQ-2000 (£29.95) £24.95. MELODY 80 (£29.95) £25.95  
 MQ-1£1 (£34.95) (£29.95. MQ-10 (£39.95) £35.95

## NEW CASIO CHRONOGRAPH

Puts most solar watches in the shade!

CASIO  
 95QS-31B  
 Lithium battery  
 1P100 sec  
 chrono  
 Dual  
 time  
 RRP  
 £29.95  
 Our  
 price  
**£24.95**



4 year Lithium battery outlasts most solar watches. Chronograph measures net, lap and 1st & 2nd place times from 1/100 second to 6 hours. Constant LC Display of hours, minutes, seconds, am/pm and day. (12 or 24 hour system). Automatic day, date, month & year calendar. Dual time facility (12 or 24 hour system). Stainless steel encased. Mineral glass face. Water resistant to a depth of 66 feet (2 at). Quality s/s bracelet with easily removable links.

### EXCEPTIONAL VALUE

In our opinion this watch represents the finest value for money available today. At Christmas the 46CS-27B had a RRP of £89.95 and you would reasonably expect to pay at least this amount for a watch of this quality and specification.

CASIO  
 46CS-27B  
 46CS-29B  
 (Slight case variation)  
 Alarm  
 Chimer  
 1/100 sec  
 chrono  
 RRP  
 £49.95  
**£39.95**



Constant LC Display of hours, minutes, seconds, am/pm and day (12 or 24 hour system). Automatic day, date, month and year calendar. 24 hour alarm. Optional hourly chime facility. Chronograph measures net, lap and 1st and 2nd place times from 1/100 second to 6 hours. Genuine stainless steel case (not "stainless" or "finish") only 7.8mm thick. Mineral glass face. Water resistant to 100 feet (3 at). Backlight. ±10 seconds/month accuracy. Easily removable links in high quality stainless steel bracelet.

UNBEATABLE QUALITY AND VALUE FOR MONEY FROM JAPAN – WHY SETTLE FOR LESS?

Most CASIO products in stock.

Send 25p for our illustrated mail order catalogue.

Prices include VAT, P. & P. Send cheque or phone your Access or Barclaycard Number to:

**TEMPUS**

Dept. PE. Beaumont Suite, 164-167 East Road, Cambridge CB1 1DB. Telephone 0223 67503


**THE NEW**

# EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

**THE UNIQUE**

# EUROBREADBOARD

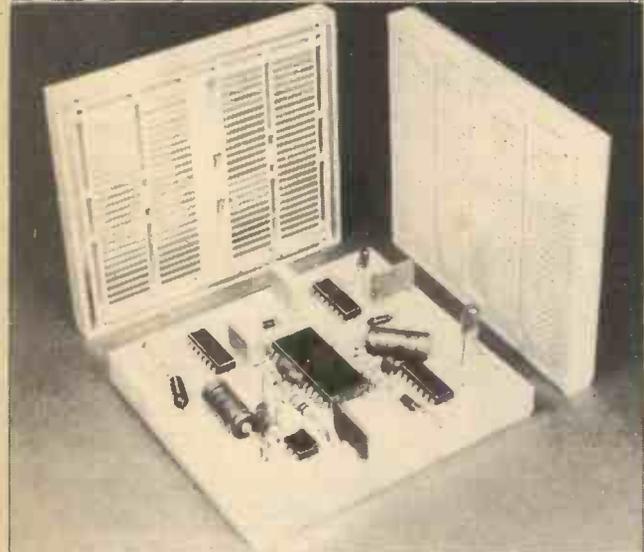

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF

PE879

David George Sales  
r/o 74 Crayford High Street,  
Crayford, Kent, DA1 4EF.

Please send me  1 EuroSolderSucker @ £6.80  Please  
 or 1 EuroBreadBoard @ £5.80  Tick  
 or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name .....

Company .....

Address .....

Tel. No. ....

Please make cheque/P.O.'s payable to David George Sales

## TOUCH CONTROLLED LIGHTING KITS (300W)

A Lightdimmer with NO knob. Dimming and on/off functions are controlled by touch. Features include:

- ★ No mains rewiring.
- ★ Easy to build - uses one MOS 1C.
- ★ Switches on to preset brightness.
- ★ Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy.
- ★★ PRICE TD300K £6.50 TDE/K £1.50

TSD300K TOUCH-SWITCH & DIMMER combined. One touchplate for on/off. Small knob controls brightness. £5.50  
TS300K TOUCHSWITCH. Two touchplates. ON/OFF £4.30  
TSA300K AUTOMATIC. One touchplate. Preset time delay of variable 2 secs to 3½ mins. £4.30  
LD300K LIGHTDIMMER. £2.90  
SPECIAL OFFER  
10% Discount on any 4 lighting control kits.


## DIGITAL VOLTMETER/THERMOMETER KIT



Based on the 7106 single IC 3½ digit D.V.M. the Kit contains a PCB, resistors, capacitors, pre-sets, I.C. and 0.5" liquid crystal display. Components are also included to enable the basic D.V.M. kit to be modified to a Digital Thermometer using a single transistor as the sensor. Requires a 2mA 9V supply (PP3 battery).

ONLY £20.75

## 24HR CLOCK/APPLIANCE TIMER KIT

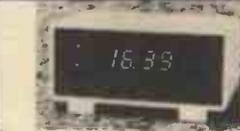

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £14.90  
White box (56 x 131 x 71mm) - drilled £2.50  
- undrilled £2.20  
Ready built £22.50

Please add VAT to the above prices.

Quantity discounts on request. Add 25p postage and packing. Callers by appointment only to:

**T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.**  
01-579 9794

## TRIACS

400V Plastic Case	16A	90p
3A	49p	
8A	82p	20A 105p
12A	70p	25A 100p
6A with trigger		80p
SCR (C106D) 5A/400V		38p
Diac		18p
8A isolated		82p

## LEDs/DISPLAYS

0.2" Red 1p	10p	10p
Green or Yellow		17p
DL27 Dual 0.5" CA		£1.50
	(two for £2.75)	
LCD 3½ digit 0.5" diil		£8.10

## SUPER SAEVS

5 x 741 90p	5 x 555	£0.80
LM3911 Thermometer IC		£1.00
ZN1034E Timer IC		£1.80
10 x BC108 Transistors		£0.60

## RESISTORS

¼W (CR25 size) E12 series  
Values 22 ohm to 10 Mohm  
Pack 10 (one value) 10p  
10 packs (mixed values) 80p

## TRANSFORMERS

Standard 240V mains primary  
100mA secondary (miniature)  
6-0-6V 80p 9-0-9V 85p  
12-0-12V 90p

## TEMPERATURE CONTROL KIT

Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. PCB (4 cm. sq.) potentiometer, plus all other components included with instructions. 500W - £3.20 1KW - £3.50

## PROGRESSIVE RADIO

31 CHEAPSIDE,  
LIVERPOOL L2 2JD

**SPECIAL OFFER SEMICONDUCTORS**—  
TB800 50p. LM3400 40p. 741 8 Pin 6 for £1. NE555 22p. ZN414 75p. LM380 80p. 741S 35p. IN4005 recs, 10 for 35p. 723 Regs 35p. 16 Pin D.I.L. Switch 45p. AD161/2 matched pair 70p.

**L.E.D.s.** 0.2" Red 10p. 0.2" Green 12p. 0.2" Clear 15p.  
**MINIATURE MAINS TRANSFORMERS.** 240v AC Primary. 6-0-6v 100ma, 9-0-9v 75ma, 12-0-12v 50ma all 73p each. 12-0-12v 100ma 92p. 0-6, 0-6v 280ma, £1.20. 12v 500ma 96p. **PULSE TRANSFORMERS.** Miniature P.C. board mounting 1:1 Plus 1 55p. Larger type 1:1 30p.

**NEW LOW PRICED POCKET MULTIMETERS.** KRT100 1,000 ohms per volt, 1,000 volts AC/DC, 100K resistance, 150ma DC current, mirror scale range selector switch £4.65. **KRT101** As above but range selection is via Prod Tip insertion £3.75.

**MINIATURE TOGGLE SWITCHES.** SPST 8 x 5 x 7mm 49p. DPDT 8 x 7 x 7mm 53p. DPDT centre off 12 x 11 x 9mm 78p. **PUSH SWITCHES.** Push to make 16 x 6mm 14p, push to break version 15p.

**TOOLS.** Good quality side cutters 5" insulated handles £1.35. Matching snub nosed pliers also £1.35. Neon mains tester screwdriver 8" long 44p. **PRECISION TOOL KIT.** Supplied in plastic hinged case consists of 5 spanners 4 to 6mm, 5 Hex. nut drivers 3 to 5mm, 3 small screwdrivers, 2 Philips screwdrivers, 1 swl, 3 Alan Keys £3.35. **TEST LEAD JUMPER SET.** 10 leads with various coloured croc clips each end 80p.

**CASSETTE HEAD REPLACEMENTS.** Mono cassette £1.60. Stereo cassette £3.40. **TAPE HEAD DEMAGNETISERS.** 240v AC £2.00.

TERMS CASH WITH ORDER (OR OFFICIAL ORDERS FROM SCHOOLS ETC) POSTAGE 30p. (OVERSEAS POST AT COST) VAT INCLUSIVE. SAE FOR ILLUSTRATED LIST.

PROGRESSIVE RADIO, 31 CHEAPSIDE, LIVERPOOL L2 2DY.



## MONOLITH

**REEL & CASSETTE TAPE HEADS**

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01 MONO PLAYBACK . . . . . £1.84	E12-09 MONO/STEREO ERASE . . . . . £1.80
B12-02 MONO RECORD/PLAYBACK . . . . . £3.92	B22-02 TWIN HALF TRACK RECORD/PLBK £5.82
B24-01 STEREO PLAYBACK . . . . . £3.22	C44RPS02 QUAD QUARTER TRACK REC/PLBK £9.14
B24-02 STEREO RECORD/PLAYBACK . . . . . £5.50	C22ES02 TWIN HALF TRACK ERASE . . . . . £4.60
B24-RP STEREO GLASS FERRITE REC/PLBK £11.32	MAGNETIC TAPE HEADS CATALOGUE 25 PENCE

AUDIO AND HI-FI CATALOGUE (80 PAGE FULL COLOUR) 50 PENCE

# MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.  
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&H WITH ORDER  
ALL PRICES INCLUDE VAT

# STEVENSON

## Electronic Components

### REGULATORS

78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p

### HARDWARE


#### MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.

Available with secondaries of:

6 - 0 - 6, 9 - 0 - 9 and	92p. each.
12 - 0 - 12.	

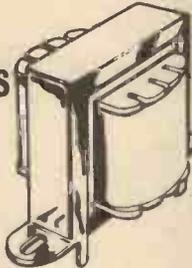

#### LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



#### TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red . . . . . 22p

#### SWITCHES

Subminiature toggle. Rated at 3A 250V.  
SPDT 70p SPDT centre off 75p  
DPDT 80p DPDT centre off 95p



Standard toggle

SPST 34p DPDT 48p

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

Slide switches (DPDT)

Miniature 14p Standard 15p



#### CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



### TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	2N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N2907 22p
BC108 8p	BD140 35p	2N3053 18p
BC109 8p	BF244B 36p	2N3055 50p
BC147 7p	BFY50 15p	2N3442 135p
BC148 7p	BFY51 15p	2N3702 8p
BC149 8p	BFY52 15p	2N3704 8p
BC148 9p	MJ2955 98p	2N3705 9p
BC177 14p	MPSA06 20p	2N3706 9p
BC178 14p	MPSA56 20p	2N3707 9p
BC179 14p	TIP29C 60p	2N3708 8p
BC182 10p	TIP30C 70p	2N3819 22p
BC182L 10p	TIP31C 65p	2N3904 8p
BC184 10p	TIP32C 80p	2N3905 8p
BC184L 10p	ZTX107 14p	2N3906 8p
BC212 10p	ZTX108 14p	2N4058 12p
BC214 10p		2N5457 32p
BC214L 10p		2N5458 30p
BC477 19p		2N5459 32p
BC478 19p		2N5777 50p
BC479 19p		
BC548 10p		
BCY70 14p		

### DIODES

1N914 3p	1N5401 13p
1N4001 4p	BZY88ser. 8p
Full spec. product.	
1N4148	£1.40/100. £11/1000

### LINEAR

THIS IS ONLY A SELECTION!

CA3140 38p	NE555 21p
LM301AN 26p	NE566 50p
LM318N 85p	NE565 85p
LM324 45p	NE567 170p
LM339 45p	SN76003 200p
709 28p	LM380 75p
741 16p	LM382 120p
747 40p	LM1830 150p
748 30p	LM3900 50p
CA3046 55p	LM3909 65p
CA3080 70p	MC1496 60p
CA3130 90p	MC1458 32p
	ZN414 75p

### CAPACITORS

**TANTALUM BEAD** each

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

**MYLAR FILM**

0.001, 0.01, 0.022, 0.033, 0.047	3p
0.068, 0.1	4p

**POLYESTER**

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

**CERAMIC**

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p

**RADIAL LEAD ELECTROLYTIC**

63V 0.47 1.0 2.2 4.7 10	5p
	22 33 47
	13p
	20p
25V 10 22 33 47	5p
	100
	8p
	10p
	15p
	1000
	23p

### CONNECTORS

**JACK PLUGS AND SOCKETS**

	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

**DIN PLUGS AND SOCKETS**

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

**1mm PLUGS AND SOCKETS**

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

**4mm PLUGS AND SOCKETS**

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

**PHONO PLUGS AND SOCKETS**

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

### 74LS

LS00 13p	LS73 25p	LS156 60p
LS01 13p	LS74 25p	LS157 48p
LS02 13p	LS75 30p	LS164 65p
LS03 13p	LS76 25p	LS174 48p
LS04 13p	LS77 35p	LS175 48p
LS08 15p	LS78 35p	LS190 62p
LS10 13p	LS83 35p	LS192 60p
LS13 28p	LS85 70p	LS193 60p
LS14 45p	LS86 30p	LS196 60p
LS20 13p	LS90 36p	LS251 50p
LS30 13p	LS93 38p	LS257 50p
LS32 16p	LS95 45p	LS258 50p
LS37 24p	LS123 70p	LS266 30p
LS40 17p	LS125 38p	LS283 60p
LS42 40p	LS126 38p	LS290 60p
LS47 90p	LS132 60p	LS365 40p
LS48 70p	LS136 28p	LS366 40p
LS54 15p	LS138 50p	LS367 40p
	LS139 50p	LS368 40p
	LS151 50p	LS376 35p
	LS153 50p	LS380 140p
	LS155 55p	

### TTL

7400 10p	7454 12p	74132 45p
7401 10p	7473 20p	74141 55p
7402 10p	7474 22p	74148 90p
7404 12p	7475 25p	74150 55p
7408 12p	7476 20p	74151 40p
7410 10p	7485 55p	74156 40p
7413 22p	7489 135p	74157 40p
7414 32p	7490 25p	74164 55p
7420 10p	7492 30p	74165 55p
7427 20p	7493 25p	74170 100p
7430 10p	7494 45p	74174 50p
7442 38p	7495 35p	74177 50p
7447 45p	7496 45p	74190 50p
7448 50p	74121 25p	74191 50p
	74122 38p	74192 50p
	74123 38p	74193 50p
	74125 35p	74196 50p
	74126 35p	74197 50p


### CMOS

4001 12p	4018 55p	4050 25p
4002 12p	4023 12p	4066 35p
4007 12p	4024 40p	4068 18p
4011 12p	4026 90p	4069 12p
4013 28p	4027 30p	4071 12p
4015 50p	4028 48p	4081 13p
4016 30p	4029 50p	4093 45p
4017 48p	4040 60p	4510 65p
	4042 50p	4511 65p
	4046 90p	4515 65p
	4049 25p	4520 60p

FULL DETAILS IN CATALOGUE!

### SKTS

Low profile by Texas

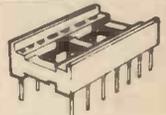

8 pin	8p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p

Soldercon pins: 100:50p, 1000:370p

### OPTO

**LED's**

0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p 8p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	

**DISPLAYS**

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

### RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:

	each	100+	1000+
0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

**METAL FILM RESISTORS**

Very high stability, low noise rated at 1/4W 1%. Available from 51 ohms to 330k in E24 series. Any mix:

	each	100+	1000+
0.25W	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 80 PAGE CATALOGUE OF COMPONENTS.

CONTAINS OVER 2500 STOCK ITEMS.



ORDERS DESPATCHED BY RETURN POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



Mail orders to: STEVENSON (Dept PE)

# 76 College Road, Bromley, Kent, England

# U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE

**BAKER "BIG-SOUND" SPEAKERS** Post £1 each

'Group 25'	'Group 35'	'Group 50/15'
12 inch 30 watt 4 or 8 or 16 ohm	12 inch 40 watt 4 or 8 or 16 ohm	15 inch 75 watt 8 or 16 ohm
<b>£12</b>	<b>£14</b>	<b>£33</b>

**BAKER LOUDSPEAKER, 12 INCH, 60 WATT.**  
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.  
FULL RANGE PROFESSIONAL QUALITY.  
RESPONSE 30-16,000 CPS  
MASSIVE CERAMIC MAGNET  
WITH ALUMINIUM PRESENCE CENTRE DOME.

**£21**

**4 CHANNEL TRANSISTOR MONOMIXER**  
Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated.

**£6.75**

Two channel stereo version **£8.50** each.

**HEATING ELEMENTS WAFER THIN**  
Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or similar. ALL POST PAID - Discounts for quantity.

**ONLY 40p EACH (FOUR FOR £1.50)**

**MINI MODULE BAFFLE KIT** Post 75p  
EMI 15 x 8 1/2 in. 3-way Loudspeaker System 5in. Bass 5in. Middle 3in Tweeter with 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response=60 to 20,000 C.P.S. 12 watt RMS. 8 ohms. £10.95 per kit. Two kits £20. Suitable Bookshelf Cabinet **£8.50** each.



**SINGLE RECORD PLAYER**

Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable Size 7in. diameter a.c. mains 220 250V 3 speeds plays all size records.

**£7.95** Post 45p

**NEW BSR SINGLE PLAYER** £22.50  
Model P182 3-speeds flared aluminium turntable. Post £1. "S" shaped arm, cueing device, stereo ceramic cartridge.

**£18.00**

B.S.R. De-Luxe Autochanger with stereo cartridge, plays all size records. P. & P. £1.

**BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER**



Ideal for Groups, Discos, P.A. and Musical Instruments. 4 inputs speech and music 4 way mixing

Output 4/8/16 ohms a.c. Mains 240V. Separate treble and bass controls.

100 volt line model **£14** extra.

**£79** Carr. £1.50

**BAKER COMPACT 50 WATT AMPLIFIER**



**IDEAL FOR DISCOS, GROUPS, PUBLIC ADDRESS**  
Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£59** Post £1.

**R.C.S. SOUND TO LIGHT DISPLAY MK II**  
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4.

**KIT = £17.00**

**R.C.S. 10 WATT AMPLIFIER KIT**

This kit is suitable for record players, tape play back, guitars electronic instruments or small PA systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume bass and treble controls. Spec. 10W output into 8 ohms 7W into 16ohms. Response 20c to 20Kc.a. Input 100mV. High Imp. Size 9 1/2 x 3 x 2 1/2 in. A/C mains operated

Mono kit **£12.50** Stereo kit **£20** Post 45p

Easy to build. Full instructions supplied

**LOW VOLTAGE ELECTROLYTICS**  
1, 2, 4, 5, 10, 16, 25, 30, 50, 100, 200mF 15V 10p, 500mF 12V 15p; 25V 20p; 50V 30p, 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p, 2000mF 6V 25p; 25V 42p, 2500mF 50V 62p, 3000 mF 25V 47p; 50V 65p, 3900mF 100V £1.60, 4700mF 63V £1.20, 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p, 5600mF 76V £1.60, 1200mF 76V 80p.

**HIGH VOLTAGE ELECTROLYTICS**

8/350V 22p	8+8/450V 50p	50+50/300V 50p
16/350V 30p	8+16/450V 50p	32+32/450V 75p
32/500V 75p	8+16/450V 50p	100+100/275V 65p
50/350V 50p	32+32/350V 50p	150+200/275V 70p

MANY OTHERS IN STOCK

**TINTED PLASTIC COVERS ONLY**  
Sizes: 14 1/2 x 12 1/2 x 4 1/2 in. £3. 16 x 14 x 3 1/2 in. £5. 15 1/2 x 13 1/2 x 6 in. £4. 17 1/2 x 9 1/2 x 3 1/2 in. £3. 14 1/2 x 14 1/2 x 2 1/2 in. Rosewood sides £4. 18 x 13 1/2 x 3 in. £6. 18 x 12 1/2 x 3 in. £8. Ideal for record decks, tape decks, etc. Post £1.

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS** £2.95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200 240V a.c. Output voltages available 6 or 7, 5 or 9 or 12V d.c. up to 100mA or less Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required.

Post 45p

**ELECTRO MAGNETIC PENDULUM MECHANISM** 95p Post 30p

1.5V d.c. operation over 300 hours continuous on SP2 battery fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome, strobe etc

**MAINS TRANSFORMERS** ALL POST 75p each

250-0-250V 70mA, 6.3 2A	£3.45
250-0-250 80mA, 6.3V 3 SA 6.3V 1A	£4.40
350-0-350 80mA, 6.3V 3 SA 6.3V 1A	£5.80
300-0-300 120mA 2 x 6.3V 2A C.T. 6.3V 2A	£8.50
220V 45mA, 6.3V 2A	£1.75
HEATER TRANS. 6.3V 3A, £1.45, 1/2 amp	£1.00

**GENERAL PURPOSE LOW VOLTAGE Tapped outputs at**

2A 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£5.30
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£5.30
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.50
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.00
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14.50
5, 8, 10, 15V 1A £2, 12V 100mA £1, 12V 300mA £1.	

12V 750mA £1.30, 40V 2A tapped 10V or 30V £2.95, 10-0-10V 2A £2.50, 40V 2A £2.95, 30V 5A 34V 2A ct. £3.75, 2 x 18V 6A £9, 12-0-12V 2 amp £2.95, 25-0-25V 2 amp £4, 20-0-20V 1A £2.95, 30V 1A £2.75, 20V 1A £2.20, 9V 3 amp £2.75, 60V, 40V, 20V or 20-0-20V, 1A £3.50, 30-0-30 2A £7, 9V 250mA £1.30, 30V 2 amp £3.

**AUTO TRANSFORMERS.** 115V to 230V or 230V to 115V 150W £7; 250W £8; 400W £9; 500W £10.

**CHARGER TRANSFORMERS.** Input 200/250V for 6 or 12V 1 1/2A £2.75; 3A £4; 4A £5.20.

**FULL WAVE BRIDGE CHARGER RECTIFIERS.** 6 or 12V outputs 1 1/2A 55p; 4A £1.25, HALF WAVE 12V 1 1/2A 25p.

**BLANK ALUMINIUM CHASSIS.** 18 s.w.g. 2 1/2 in. sides, 6 x 4 in. 95p; 8 x 6 in. £1.40; 10 x 7 in. £1.85; 14 x 9 in. £3.90; 16 x 6 in. £1.85; 12 x 3 in. £1.20; 16 x 10 in. £2.20, 12 x 8 in. £1.70.

**ALUMINIUM PANELS.** 18 s.w.g. 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 6 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 8 in. 84p; 12 x 12 in. £1; 16 x 10 in. £1.16.

**ALUMINIUM ANGLE BRACKET.** 6 x 1 x 1 in. 20p.

**ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK**  
4 x 2 x 2 in. 86p; 3 x 2 x 1 in. 65p; 6 x 4 x 2 in. 95p; 8 x 6 x 3 in. £1.80; 9 x 4 x 4 in. £1.70; 10 x 7 x 3 in. £2.20; 12 x 6 x 3 £2.50.

**THE "INSTANT" BULK TAPE ERASER**  
Suitable for cassettes, and all sizes of tape reels a.c. mains 200 240V **£5.50**

Leaflet SAE. Post 50p.

**Head demagnetiser £4.75**



## RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K.

Minimum post 30p. Access and Barclaycard Same day despatch Radio Books and Components Lists 20p Open 9-6 Sat. 9-5 (Closed Wednesday all day). Tel. 01-684 1665

## OUR 1979 CATALOGUE including the first edition of

### STOP PRESS

- ★ Latest low prices
- ★ Fascinating new items
- ★ Special offers — a bargain on their own
- ★ Lowest prices ever for TTL
- ★ Free 45p worth of vouchers

**RAM 2102A-2**  
1024 x 1 250ns  
£1.19  
16 for £16.96

**C.P.U. 8080**  
£5.49

**E. PROM 1702**  
£5.57

**CATALOGUE 40p**

**JUST SEND S.A.E. FOR STOP PRESS**

**CHROMASONIC electronics**  
DEPT. 16, 56 FORTRIS GREEN ROAD  
MUSWELL HILL, LONDON N10 3HN  
TELEPHONE: 01-883 3705/2289



**USE OUR "ORDER RING" LINES**



VAT INCLUSIVE PRICES P&P 25p

## integrated circuits

How to Make them Work

### integrated circuits

HOW TO MAKE THEM WORK

R. H. Warring



**R. H. WARRING**

Eighty Four working circuits described and illustrated representing the wide variety of types readily available. A basic and practical book which is an essential introduction to the subject for anyone interested in, or in any way concerned with, modern electronics practice.

**PRACTICAL HANDBOOK SERIES**

From leading bookshops

**£3.95 net**

**LUTTERWORTH PRESS**  
Luke House, Farnham Road, Guildford, Surrey

Largest range of quality components in the U.K. - over 8,000 types stocked

# Marshall's

Head Office and Mail Order to Dept. P.E.,  
A. Marshall (London) Ltd.,  
Kingsgate House, Kingsgate Place,  
London NW6 4TA. Tel: 01-624 8005.  
Telex: 21492.

Retail Sales: London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 ALSO 325 Edgware Road, W2. Tel: 01-723 4242.  
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133 AND Bristol: 108A Stoke's Croft, Bristol. Tel: 0272 854201

## BRIDGE RECTIFIERS

Type	Rating	Price	Type	Rating	Price	Type	Rating	Price
W005								
T1005	1A	50V	028	PW01	6A	100V	0.95	S005
W01	1A	100V	0.30	PA02	6A	200V	0.97	501
W02	1A	200V	0.32	PW04	6A	400V	1.08	S04
W04	1A	400V	0.40	PW06	6A	600V	1.18	S06
W06	1A	600V	0.50	PW08	6A	800V	1.28	S08
W08	1A	800V	0.60	PW10	6A	1000V	1.60	S10
W18	1A	100V	0.44	K005	25A	50V	1.20	P40C1500
W28	1A	200V	0.48	K01	25A	100V	1.20	P40C3200
W48	1A	400V	0.50	K02	25A	200V	2.75	880C1500
W64	1A	600V	0.50	K04	25A	400V	3.00	880C3200
W179	1A	800V	0.70	K06	25A	600V	3.99	PW005

## CMOS (see catalogue for full range)

74C00N	0.24	74C78N	0.54	74C160N	1.11	74C221N	1.36	74C911N	7.70
74C02N	0.24	74C83N	1.30	74C181N	1.11	74C373N	1.87	74C112N	7.70
74C04N	0.24	74C85N	1.30	74C182N	1.11	74C374N	1.87	74C141N	1.41
74C08N	0.24	74C86N	0.64	74C183N	1.11	74C010N	0.54	74C915N	1.11
74C10N	0.24	74C89N	4.39	74C184N	1.04	74C020N	0.54	74C918N	1.15
74C14N	0.95	74C90N	0.85	74C165N	1.04	74C030N	0.54	74C922N	3.90
74C20N	0.24	74C93N	0.85	74C173N	0.90	74C040N	0.54	74C923N	3.74
74C30N	0.24	74C95N	1.04	74C174N	0.90	74C050N	0.78	74C925N	5.22
74C32N	0.24	74C107N	1.22	74C175N	0.90	74C060N	0.54	74C928N	5.22
74C42N	0.92	74C150N	4.14	74C192N	1.11	74C070N	0.54	74C927N	5.22
74C48N	1.38	74C151N	2.47	74C193N	1.11	74C080N	0.96	74C928N	5.22
74C73N	0.54	74C154N	3.68	74C195N	1.04	74C090N	1.63	74C932N	1.56
74C74N	0.56	74C157N	2.21	74C200N	6.70	74C910N	6.79		

## MULTI-WAY EDGE CONNECTORS

2.54mm (1 inch)	Price
16 Way Single	£3.00
24 Way Single	£3.90
32 Way Single	£5.25

3.96mm	Double	£2.03
6 Way	Double	£2.06
10 Way	Double	£3.08
15 Way	Double	£3.66
22 Way	Double	£4.60

## BRINDLEY TOOLS AND CUTTERS

GENERAL PURPOSE	Price
100mm (4 inch)	£3.40
Diagonal Cutters	£3.25
Round Nose Pliers	£3.20
Flat Nose Pliers	£3.20
Snipe Nose Pliers	£3.20
End/Top Cutters	£3.60

Also in stock -  
BAHCO Quality Tool range.  
See catalogue for full details.

## SINGLE IN LINE PLUGS AND SOCKETS

Providing a simple and economical alternative to edge connectors for bringing cable into a pcb.  
12 Way £0.90, 24 Way £1.20

## New - SIEMENS TURN-SLIDE SWITCHES

This new version of the rotary switch is especially suitable for setting programs. The rotary switch is of a 1 element non stop type.  
Voltage rating  $\leq 60V \text{ AC}$   
Current rating  $\leq 0.5A$   
fixed contacts gold-plated. £2.65

## RESISTORS

**CARBON FILM**  
25 watt  $\pm 5\%$  Tol. Available in E12 range 100 to 1 meg ..... 2p each  
0.5 watt  $\pm 5\%$  Tol. Available in E12 range 100 to 10 meg ..... 3p each  
1.0 watt  $\pm 10\%$  Tol. Available in E12 range 100 to 10 meg ..... 5p each  
2.0 watt  $\pm 10\%$  Tol. Available in E12 range 100 to 10 meg ..... 9p each

**WIRE WOUND**  
2.5 watt  $\pm 5\%$  Tol. 22 to 330 ohms ..... 10p each\*  
5 watt  $\pm 5\%$  Tol. 5 to 12K ..... 12p each\*  
10 watt  $\pm 5\%$  Tol. 1 to 25K ..... 14p each\*

**METAL OXIDE**  
0.5 watt  $\pm 2\%$  Tol. E24 range 100 to 1 meg ..... 4p each\*

\*See catalogue for full list of available values.

## NEW 1979 CATALOGUE

40 page catalogue - new enlarged micro section - largest range of quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more. 45p post paid or 36p to callers at any of our four branches.

### ★ MAIL ORDER ★

Quick service on all orders - please add 40p credit cards to all orders. Telephone orders on p/p cards £10.00 minimum.



## Get a great deal from Marshall's

### 3 1/2 DIGIT LCD AND LED PANEL METER KITS

Low-cost, easy-to-assemble kits using the new Intersil 7106-7 A/D converters

Intersil's 7106 is the first single-chip CMOS A/D for driving LCD displays - including backplane - directly. The 7107 is the first single-chip CMOS A/D for driving instrument-size LED displays directly without buffering. Each provides parallel seven-segment outputs, ideal for DVMS, DPMs and anywhere modern digital displays are needed. Both have internal reference and clock, and both are CMOS so you get low noise (12 to 15µV) comparable with the finest bipolar devices, and low power (10 mW max.  $\pm 10V$ ).

Kits provide all materials... including PC board, for a functioning panel meter. Assembly time is only 1/2 hour.

ICL 7106V(LED) £28.99 SPECIAL OFFER £19.90  
ICL 7107V(LED) £21.99 SPECIAL OFFER £15.90  
Chip alone ICL 7106CP SPECIAL OFFER £7.90

**L200 - 5 Terminal Adjustable Voltage and Current Regulator**  
The L200 is a silicon monolithic integrated circuit for voltage and current programmable regulation.  
● ADJUSTABLE OUTPUT CURRENT UP TO 2A  
● ADJUSTABLE OUTPUT VOLTAGE DOWN TO 2.85V  
REDUCED PRICE NOW ONLY £1.95 each.

## TTL (see catalogue for full range)

SN74A05N	0.60	74LS194N	0.58	74LS194N	0.70	74LS490N	0.90
SN74A10N	0.55	74LS195N	0.42	74LS195N	0.70	74LS567N	1.90
SN74A11N	0.55	74LS196N	0.42	74LS196N	0.80	SN74595N	0.77
SN74A20N	0.55	74LS200N	0.80	74LS197N	0.80	SN74596N	0.77
SN74A21N	0.55	74LS201N	0.85	74LS221N	0.80	SN74598N	0.94
SN74A30N	0.55	74LS206N	0.44	74LS242N	1.50	SN74510N	0.77
SN74A40N	0.55	74LS209N	0.64	74LS241N	1.50	SN74520N	0.77
SN74A51N	0.55	74LS210N	1.20	74LS242N	1.25	SN74540N	0.77
SN74A53N	0.55	74LS212N	0.90	74LS243N	1.25	SN74549N	0.77
SN74A54N	0.55	74LS214N	0.80	74LS244N	1.50	SN74555N	0.77
SN74A55N	0.55	74LS216N	0.90	74LS245N	1.65	SN745112N	1.70
SN74A60N	0.55	74LS218N	1.35	74LS247N	1.09	SN745114N	1.70
SN74A62N	0.55	74LS217N	0.42	74LS248N	1.09	SN745140N	0.77
SN74A00N	0.55	74LS109N	0.42	74LS249N	1.09	SN745157N	2.95
SN74A02N	0.55	74LS112N	0.42	74LS251N	1.00	SN745188N	2.70
SN74A04N	0.60	74LS113N	0.42	74LS252N	1.00	SN745200N	3.50
SN74A74N	3.10	74LS114N	0.42	74LS257N	1.00	SN745201N	3.71
SN74A74N	0.90	74LS122N	0.62	74LS259N	1.55	SN745282N	12.50
SN74A85N	2.62	74LS123N	0.83	74LS261N	3.25	SN745287N	2.95
SN74A93N	2.30	74LS124N	1.70	74LS261N	3.25	SN745287N	2.95
SN74A00N	0.26	74LS125N	0.50	74LS266N	0.44	SN745288N	2.70
SN74A01N	0.26	74LS126N	0.50	74LS272N	1.30	SN745295N	1.81
SN74A02N	0.26	74LS127N	0.85	74LS275N	3.25	SN745300N	5.06
SN74A04N	0.29	74LS136N	0.42	74LS279N	0.58	SN745301N	3.71
SN74A04N	0.29	74LS138N	0.65	74LS282N	1.65	SN745387N	3.09
SN74A05N	0.29	74LS139N	0.65	74LS283N	1.20	SN745470N	5.06
SN74A08N	0.26	74LS145N	1.30	74LS289N	3.74	SN745471N	5.06
SN74A09N	0.26	74LS147N	1.65	74LS290N	1.00	SN745472N	13.48
SN74A10N	0.26	74LS148N	1.35	74LS291N	1.00	SN745473N	13.48
SN74A11N	0.26	74LS149N	1.35	74LS295N	1.35	SN745474N	13.48
SN74A12N	0.26	74LS153N	0.58	74LS298N	1.35	SN745475N	13.48
SN74A13N	0.58	74LS154N	1.45	74LS299N	2.95	SN745490N	0.36
SN74A14N	0.75	74LS155N	0.80	74LS323N	3.50	SN74911N	0.60
SN74A15N	0.26	74LS156N	0.80	74LS324N	1.65	SN7492N	0.36
SN74A20N	0.26	74LS157N	0.60	74LS325N	2.40	SN7493N	0.36
SN74A21N	0.26	74LS158N	0.65	74LS326N	0.70	SN7494N	0.90
SN74A22N	0.26	74LS160N	0.80	74LS327N	2.55	SN7495N	0.76
SN74A26N	0.32	74LS161N	0.85	74LS348N	1.10	SN7496N	0.54
SN74A27N	0.26	74LS162N	0.80	74LS352N	1.07	SN7497N	1.95
SN74A28N	0.29	74LS163N	0.85	74LS353N	1.07	SN74100N	1.40
SN74A30N	0.26	74LS164N	1.10	74LS354N	0.55	SN74101N	0.26
SN74A32N	0.27	74LS165N	1.15	74LS366N	0.55	SN74118N	0.95
SN74A33N	0.29	74LS166N	1.45	74LS367N	0.55	SN74119N	1.40
SN74A37N	0.32	74LS168N	1.65	74LS368N	0.55	SN74121N	0.28
SN74A38N	0.32	74LS169N	1.45	74LS373N	0.85	SN74122N	0.55
SN74A40N	0.26	74LS170N	1.90	74LS374N	0.85	SN74123N	0.55
SN74A42N	0.80	74LS171N	2.65	74LS375N	0.85	SN74124N	0.55
SN74A47N	1.09	74LS174N	0.75	74LS377N	1.30	SN74125N	0.45
SN74A48N	1.00	74LS175N	0.75	74LS378N	1.00	SN74141N	0.58
SN74A49N	1.09	74LS181N	2.75	74LS379N	1.25	SN74145N	0.86
SN74A51N	0.26	74LS183N	2.70	74LS386N	0.44	SN74148N	1.35
SN74A54N	0.26	74LS189N	3.74	74LS390N	0.90	SN74150N	0.76
SN74A55N	0.26	74LS190N	3.74	74LS393N	0.90	SN74151N	0.76
SN74A62N	1.26	74LS191N	1.00	74LS395N	1.90	SN74153N	0.65
SN74A73N	0.42	74LS192N	0.95	74LS398N	1.90	SN74154N	1.20
SN74A74N	0.42	74LS193N	0.95	74LS399N	1.45	SN74155N	0.70

## TRANSISTORS (see catalogue for full range)


2N333	3.00	2N708	0.30	2N1420	0.55	2N2219	0.38	40081	1.20	AC188	0.54	BC118	0.22	BCY33A	1.10	BD140	0.43	BF157	0.48
2N338	0.80	2N718	0.30	2N1483	1.85	2N2219A	0.39	40232	0.60	AC188K	0.54	BC119	0.33	BCY34A	1.10	BD142	0.70	BF159	0.37
2N384A	0.77	2N1718A	0.54	2N1485	2.20	2N2220	0.39	40233	0.70	AD136	2.75	BC122	0.61	BCY38	2.20	BDX14	1.32	BF160	0.33
2N434	0.80	2N1720A	0.45	2N1507	0.35	2N2221	0.25	40235	0.65	AD142	1.45	BC123	0.65	BCY40	1.05	BDY24	1.90	BF161	0.65
2N436	2.20	2N1721	1.05	2N1524	0.60	2N2221A	0.25	40237											

# The latest kit innovation!
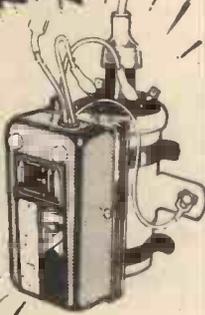
## from Sparkrite

*Sparkrite was featured by Shaw Taylor in "DRIVE IN"*

the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE — Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing UK only.

Electronics Design Associates, Dept. PE 10, 82 Bath Street, Walsall, WS1 3DE. Phone: Walsall 614791

Electronics Design Associates, Dept. PE 8  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name .....

Address .....

Phone your order with Access or Barclaycard

Send SAE if brochure only required.

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X4 KIT £16.65

TACHOPULSE SLAVE UNIT £3.85

£

Cheque No.

Please state polarity pos or neg earth.

Access or Barclaycard No.

ZENER DIODES (400mW)	DPTO/DISPLAY	TTL	74122	30p	4025	12p	8C173	4p	8FX2	9	25p
2-7V to 33V 8p	2N5777 50p	7400 10p	74123	40p	4027	30p	8C182	10p	8FX5	25p	25p
	OC71 70p	7401 10p	74125	35p	4028	45p	8C183	10p	8FX7	20p	
	ORP12 70p	7402 10p	74126	35p	4029	50p	8C184	10p	8FX10	15p	
	DL704 100p	7403 10p	74132	45p	4030	30p	8C186	19p	8FX19	15p	
	DL707 100p	7404 12p	74141	45p	4035	99p	8C187	28p	8FX19	18p	
	LEDS:-	7405 12p	74142	180p	4041	73p	8C207	10p	8SX20	20p	
	2.5"x5" 51p	7406 20p	74145	50p	4042	54p	8C212	10p	8U05	130p	
	3.75"x5" 60p	7407 24p	74151	45p	4043	60p	8C213	10p	8U208	150p	
		7408 12p	74153	45p	4044	70p	8C214	10p	OC25	75p	
		7409 12p	74154	45p	4047	80p	8C237	12p	OC28	86p	
		7410 12p	74155	45p	4048	50p	8C301	22p	OC35	86p	
		7411 15p	74156	40p	4049	25p	8C303	24p	OC71	9p	
		7412 15p	74157	40p	4050	25p	8C328	17p	OC72	32p	
		7413 25p	74160	55p	4066	35p	8C338	17p	OC84	47p	
		7414 45p	74161	50p	4069	12p	8C547	11p	TIP29	35p	
		7416 24p	74162	55p	4070	12p	8C548	11p	TIP298	40p	
		7417 24p	74163	50p	4071	12p	8C549	11p	TIP30	35p	
		7420 12p	74164	60p	4072	12p	8C557	11p	TIP308	40p	
		7421 20p	74165	55p	4073	16p	8C559	25p	TIP31	40p	
		7422 15p	74166	75p	4081	14p	8C710	14p	TIP32	40p	
		7427 15p	74173	80p	4082	14p	8C711	16p	TIP33	60p	
		7428 25p	74174	60p	4086	60p	8D115	44p	TIP33C	90p	
		7432 15p	74175	55p	4510	60p	8D121	60p	TIP34A	65p	
		7433 28p	74176	50p	4511	70p	8D123	90p	TIP35A	230p	
		7437 16p	74177	50p	4516	85p	8D124	100p	TIP36A	290p	
		7438 17p	74180	80p	4518	65p	8D135	35p	TIP41A	70p	
		7440 10p	74181	110p	4520	65p	8D132	35p	TIP42A	70p	
		7441 46p	74182	45p	4528	80p	8D135	35p	TIP295	65p	
		7442 40p	74190	65p			8D136	35p	TIP305	55p	
		7443 40p	74191	70p			8D137	40p	ZTX108	12p	
		7445 64p	74192	55p			AC126	17p	8D138	38p	
		7448 50p	74193	60p			AC127	19p	8D139	38p	
		7449 50p	74194	55p			AC128	19p	8D140	38p	
		7450 10p	74195	50p			12B/176 MP		8F157	28p	
		7451 12p	74197	50p					8F173	42p	
		7453 12p	74198	100p					8F178	25p	
		7454 10p	74199	90p					8F179	24p	
		7460 14p	CMOS						8F180	23p	
		7470 20p	4000	12p					8F181	18p	
		7472 20p	4001	12p					8F184	20p	
		7473 20p	4002	12p					8F185	23p	
		7474 22p	4006	78p					8F194	10p	
		7475 25p	4007	14p					8F198	10p	
		7476 25p	4008	64p					8F199	30p	
		7477 35p	4009	30p					8F200	28p	
		7480 14p	4010	40p					8F224	18p	
		7486 8 40p	4011	40p					8F240	24p	
		7490 25p	4012	12p					8F80	24p	
		7491 30p	4012	12p					8F84	24p	
		7492 30p	4013	30p					8F86	24p	
		7493 25p	4014	75p					8F90	24p	
		7494 50p	4015	50p					8F92	24p	
		7495 40p	4016	30p					8F94	24p	
		7496 40p	4017	50p					8F98	10p	
		74100 70p	4018	55p					8F99	10p	
		74105 40p	4019	40p					8F100	10p	
		74107 22p	4020	50p					8F108	10p	
		74109 30p	4021	73p					8F111	11p	
		74110 45p	4022	50p					8F112	11p	
		74118 75p	4023	12p					8F117	16p	
		74121 25p	4024	45p					8F172	11p	

SINCLAIR PRODUCTS	IC AUDIO AMPS
case £3.24, adaptor, £3.24, connector kit £10.58. Microvision TV UK model £89.95, mains adaptor £6.73. PDM38 £28.95, mains adaptor £3.19, case £3.19, case £3.19, DM350 £87.45, DM450 £95.50, DM235 £49.45, rechargeable battery £7.50, mains adaptor £3.70, case £8.45, enterprise prog calculator £12.13, prog library £4.45, mains adaptor £3.20.	with pcb. JC12 6W £1.60, JC20 10W £2.95.
CSC MAX100 freq meter £83.75.	<b>BATTERY ELIMINATORS</b> 3-way type 6/7/9v 300ma £2.95, 100ma radio type with press-studs 9V £3.35, 9V+9V £4.50, car converter 1.2v input, output 4/6/7/9v 800ma £2.60.
<b>COMPUTER GAMES</b> Star chess £59, chess challenger £7.95, checker challenger £8.4, Atari Video computer £13.88, cartridges £13.45.	<b>BATTERY ELIMINATOR KITS</b> 100ma radio types with press-studs 4.5v £1.40, 8v £1.40, 9v £1.40, 4.5v+4.5v £1.80, 6+6v £1.80, 9+9v £1.80, stabilized 8-way types 3/4/6/7/9v/12/15/18v 100ma £2.80, 1amp £6.40, stabilized power kits 1.2v 100ma £2.80, 2.30v 1A £6.95, 2.30v 2A £10.95, 12v car converter 6/7/9v 1A £1.35.
<b>COMPONENTS</b> IN4148 1.4p, IN4002 2.9p, 741 15p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p, resistors 1/4W 5% E12 10R to 10M 1p, 0-8p for 50+ of one value, 16V electrolytics, 5/1/2/5/10/22uf 5p, 100uf 6p, 1000uf 10p, 1lb FcCl £1.13, dolo pen 79p, 40 sq ins pcb 60p.	<b>T-DEC AND CSC BREADBOARDS</b> s-dac £3.80, 1-dac £4.02, u-dac £4.40, u-dac £6.73, 16 id adaptors £2.17, exp4B £2.48, exp300 £6.21, exp350 £3.40, exp325 £1.73.
<b>TV GAMES</b> AY-3-8500 + kit £8.95, rifle kit £4.95, AY-3-8610 + kit £15.70, stunt cycle chip + kit £15.70, AY-3-8603 chip £8.90.	<b>BI-PAK AUDIO MODULES</b> s450 £23.51, AL80 £4.86, PA100 £16.95, spm80 £4.47, dm180 £5.95, stereo 30 £20.12, AL30 £3.95, PA12 £7.60, PS12 £1.39, MA60 £35.44.
<b>TRANSFORMERS</b> 6-0-6V 100ma 74p, 1.1a £2.35, 6.3V 1.1a £1.89, 9-0-9V 75ma 74p, 1a £2, 2a £2.60, 12-0-12V 100ma 90p, 1a £2.49.	<b>SWANLEY ELECTRONICS</b> Dept PE, 32 Golds Rd., Swanley, Kent Post 30p extra, prices include VAT. Official and overseas orders welcome. Lists 20p post free.

## HOME RADIO COMPONENTS

### EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25, with a free bargain list. Send your cheque or postal order now.

**Home Radio Components Ltd.**  
Dept. PE, 234 London Road, Mitcham, Surrey CR4 3HD

# Cambridge Learning Enterprises

## SELF-INSTRUCTION COURSES

### UNDERSTANDING DIGITAL ELECTRONICS

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.



**Digital Computer Logic and Electronics** is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought, it consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems, AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

**FLOW CHARTS & ALGORITHMS** help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

### The Algorithm Writer's Guide


explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a **MUST** for those with things to say.

**NEW** from Cambridge Learning Enterprises
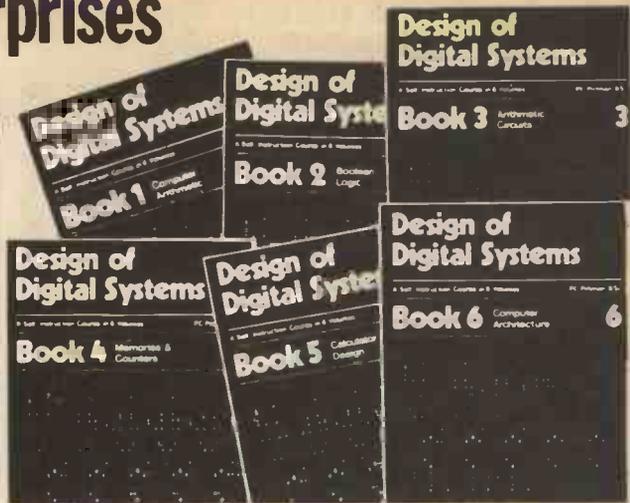
### O - LEVEL ENGLISH LANGUAGE

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on **COMPREHENSION**, Book 2 covers **SUMMARY, PUNCTUATION & SPELLING**, and Book 3 coaches you in the principles of **COMPOSITION**. Size: 3 A4 volumes totalling 250 pages.

**CAMBRIDGE LEARNING ENTERPRISES, UNIT 21, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND**  
TELEPHONE: ST. IVES (0480) 67446.  
PROPRIETORS: DAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES  
REGD. IN ENGLAND No. 1328762



**Design of Digital Systems** is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

**Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

**Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

**Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

**Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

**Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

**Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; Input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Four volumes Digital Computer Logic & Electronics at £6.50 inc p & p  
Six volumes Design of Digital Systems at £10.50 inc p & p  
Three volumes O-Level English Language at £6.50 inc p & p  
The Algorithm Writer's Guide at £3.40 inc p & p

If your order exceeds £14 deduct £2 from your payment  
Price includes surface mail anywhere in the world, airmail extra  
**GUARANTEE** If you are not entirely satisfied your money will be refunded  
Please allow 21 days for delivery

Cambridge Learning Enterprises, Unit 21, Rivermill Site,  
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR,  
England.

Please send me the following books:

..... sets Digital Computer Logic & Electronics at £6.50, p & p  
..... sets Design of Digital Systems at £10.50, p & p included  
..... O-Level English Language at £6.50 p & p included  
..... The Algorithm Writer's guide at £3.40, p & p included

Name .....

Address .....

.....

I enclose a \*cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my \*Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number .....

Signature .....

\*delete as appropriate.  
Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

PE21

# RFT

## VALVE MAIL ORDER CO.

Climax House  
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS  
MAIL ORDER SERVICE**

Ep	Ep	Ep	Ep	Ep	Ep
AA119	0-11	BCY70	0-18	MPSU01	0-41
AA190	0-29	BCY71	0-18	MPSU06	0-52
AA193	0-45	BCY72	0-14	MPSU56	0-55
AA213	0-19	BC211	1-62	NE555	0-49
AA215	0-37	BO115	0-49	NKT401	2-16
AA217	0-29	BO121	1-30	NKT403	1-87
AC107	0-65	BD123	1-30	NKT404	1-87
AC125	0-22	BD124	1-40	OA5	1-03
AC126	0-22	BD131	0-38	OA7	0-59
AC127	0-22	BD132	0-41	OA10	0-65
AC128	0-22	BD135	0-37	OA47	0-15
AC141	0-27	BD136	0-37	OA70	0-32
AC141K	0-38	BD137	0-38	OA79	0-32
AC142	0-22	BD138	0-43	OA81	0-32
AC142K	0-32	BD139	0-46	OA85	0-32
AC176	0-22	BD140	0-48	OA90	0-09
AC187	0-22	BD144	2-16	OA91	0-09
AC188	0-22	BD181	1-19	OA95	0-09
ACV17	0-92	BD182	1-27	OAZ200	1-08
ACV18	0-86	BD237	0-43	OAZ202	1-08
ACV19	0-81	BD238	0-69	OAZ211	1-08
ACV20	0-76	BDX10	0-98	OAZ220	1-08
ACV21	0-81	BDX32	2-16	OAZ201	1-08
ACV39	1-62	BDY20	1-35	OAZ208	1-08
AD149	0-76	BDY60	1-62	OAZ207	1-08
AD161	0-49	BF115	0-27	OC16	2-16
AD162	0-49	BF152	0-19	OC20	2-70
AF106	0-49	BF153	0-22	OC22	2-70
AF114	0-81	BF154	0-18	OC23	2-97
AF115	0-81	BF159	0-25	OC24	2-97
AF116	0-81	BF160	0-17	OC25	0-97
AF117	0-81	BF167	0-22	OC26	0-97
AF139	0-43	BF173	0-22	OC28	2-16
AF186	1-30	BF177	0-26	OC29	2-16
AF239	0-49	BF178	0-26	OC35	1-62
AFZ11	2-97	BF159	0-25	OC36	1-62
AFZ12	2-97	BF180	0-32	OC41	0-86
ASV26	0-43	BF181	0-32	OC42	0-81
ASV27	0-43	BF182	0-32	OC43	2-43
ASZ15	1-35	BF183	0-27	OC44	0-85
ASZ16	1-35	BF184	0-27	OC45	0-59
ASZ17	1-35	BF185	0-27	OC71	0-59
ASZ20	1-62	BF194	0-10	OC72	0-59
ASZ21	2-16	BF195	0-10	OC73	1-08
AU110	1-84	BF196	0-11	OC74	0-70
AU113	1-84	BF197	0-14	OC75	0-70
AU110	1-84	BF200	0-29	OC76	0-59
BA145	0-15	BF224	0-23	OC77	1-30
BA148	0-15	BF244	0-10	OC78	0-70
BA154	0-10	BF257	0-26	OC81Z	1-30
BA155	0-11	BF258	0-28	OC82	0-70
BA156	0-10	BF259	0-35	OC83	0-70
BAW62	0-06	BF336	0-32	OC84	0-70
BAX13	0-07	BF337	0-32	OC122	1-62
BAX16	0-10	BF338	0-33	OC123	1-89
BC107	0-13	BF341	0-28	OC124	1-89
BC108	0-13	BFS28	2-41	OC140	2-97
BC109	0-14	BFS61	0-23	OC141	3-51
BC113	0-14	BFS98	0-23	OC170	1-08
BC114	0-16	BFW10	0-70	OC171	1-08
BC115	0-16	BFW11	0-70	OC200	1-62
BC116	0-17	BFX44	0-30	OC201	1-62
BC117	0-19	BFX85	0-25	OC202	1-89
BC118	0-11	BFX87	0-23	OC203	1-89
BC125	0-18	BFX88	0-23	OC204	2-70
BC126	0-23	BFY50	0-28	OC205	2-70
BC135	0-16	BFY51	0-28	OC206	2-70
BC136	0-17	BFY52	0-28	OC207	2-89
BC137	0-27	BFY64	0-28	OCP71	1-35
BC147	0-10	BFY90	1-35	ORP12	1-08
BC148	0-09	BSX19	0-23	R2008B	1-97
BC149	0-10	BSX20	0-22	R2009	2-43
BC157	0-10	BSX21	0-22	R2010B	1-97
BC158	0-09	BT106	1-35	T1C44	0-32
BC159	0-27	GJ37/4	0-28	T1C26D	1-30
BC167	0-14	BW205	1-97	T1L209	0-22
BC170	0-12	BW206	2-53	T1P29A	0-46
BC171	0-11	BW208	2-25	T1P30A	0-50
BC172	0-11	BY100	0-49	T1P31A	0-49
BC173	0-13	BY126	0-16	T1P32A	0-52
BC177	0-16	BY127	0-16	T1P33A	0-75
BC178	0-16	BZK61	0-19	T1P34A	0-79
BC179	0-17	Series		T1P41A	0-68
BC182	0-12	BZY88	0-14	T1P42A	0-76
BC183	0-11	Series		T1P295B	0-72
BC184	0-12			T1P305B	0-60
BC212	0-14	CRS1/40	0-65	T1S43	0-51
BC213	0-14	CRS3/40	0-81	ZS140	0-28
BC214	0-17	CRS3/60	0-97	ZS170	0-24
BC237	0-10	GEX66	1-62	ZS178	0-61
BC238	0-14	GEX541	1-89	ZS278	0-62
BC301	0-27	GJ37	0-28	ZS78	0-64
BC303	0-26	GJ5M	0-81	ZTX107	0-12
BC307	0-11	GL7M	0-81	ZTX108	0-11
BC308	0-11	GM0378A	1-89	ZTX109	0-14
BC327	0-23	KS100A	0-51	ZTX300	0-14
BC328	0-21	MJE340	0-86	ZTX301	0-15
BC337	0-21	MJE370	0-66	ZTX302	0-17
BC338	0-19	MJE371	0-66	ZTX303	0-19
BCY30	1-08	MJE520	0-56	ZTX304	0-21
BCY31	1-08	MJE521	0-59	ZTX311	0-14
BCY32	1-08	MJE2955	1-35	ZTX314	0-23
BCY33	0-97	MJE3055	0-81	ZTX500	0-15
BCY34	0-97	MPF102	0-34	ZTX501	0-16
BCY39	3-24	MPF103	0-34	ZTX502	0-18
BCY40	1-08	MPF104	0-34	ZTX503	0-19
BCY42	0-27	MPF105	0-34	ZTX504	0-23
BCY43	0-27	MPSA06	0-26	ZTX531	0-23
BCY58	0-17	MPSA56	0-29	ZTX550	0-18

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.  
Valves, Tubes and Transistors · Closed Saturday  
Terms C.W.O. only · Tel. 01-677 2424-7  
Quotations for any types not listed S.A.E.  
Post and Packing 30p per order  
All prices include V.A.T.

Prices correct  
when going  
to press

## Codespeed

## Electronics

PO Box 23, 34 Seaford Road,  
Copnor, Portsmouth, PO3 5JL

### MM5314 Clock Chip Bonanza

Offered at the unbelievable price of only £1.99 each. All brand new and fully guaranteed. Supplied with data sheet. Can be interfaced with either led or gas discharge displays. Order catalogue number 207

### ELECTRONICS MAIL ORDER SPECIALISTS



### DIGITAL CLOCKS

A ready built and tested 12 hour alarm clock module with built-in LED display (0.8" digits). Only requires a mini mains transformer and time setting switches to make a fully functional clock. Supplied with full data £6.50 each. Order catalogue number 205

**Polarising Filter Material**  
A lightly tinted 0.006" thick plastic polarising film made by Polaroid. Any size cut from 1 sq. inch to a maximum size of 19" by 250 feet. Only 2p per square inch. (State dimensions required) Order catalogue number 701

**8 Digit L.C.D.**  
These liquid crystal displays are dynamic scattering type LCD's and give white digits on a clear background. Digit height is 0.33" with right hand decimal points. Only £2.95 with data. Order catalogue number 302

**Factory Reject Calculators**  
Production line reject LED calculators with lots of accessible goodies inside (calc chip, display, keyboard etc). Ideal for breaking for spares (some could be repairable and we include a reprint of an article on repairing calculators). £2.50 each Cat. No. 104

**MM5725 Calculator Chip**  
Originally made for desk calculators, these 28 pin i.C.s. can be used to build a useful 8 digit calculator. Not compatible with our calc. keyboards (cat. 101). With data - only £1.00 Order catalogue number 103

**9 Digit Gas Discharge Display**  
A super bright 9 digit display with 0.25" high digits. Requires 180v dc anode volts but this is easily achieved in mains operated projects. Supplied with data sheet and edge connector socket. 75p each Order catalogue number 310

**4 Digit L.E.D. Display**  
A 4 digit non-multiplexed led display with centre colon. Ideal for digital clock (and other) projects. Digits are 0.8" high and the display is common cathode. With data £3.95 each. Order catalogue number 204

**2 CALCULATOR for £1.00 KEYBOARDS**

Lots of uses for these neat multi-function keyboards. Each keyboard has 20 keys and size is approx. 3 1/2" X 3". Order catalogue no. 101

**Super 4 Digit L.C.D.**  
A 4 digit, non-multiplexed Liquid Crystal display with 0.6" high digits (black digits on grey background). Supplied with data £6.95 Order catalogue number 206

**Digital Multimeter Chip**  
Build a highly accurate digital voltmeter or panel meter with this MM5330 integrated circuit. Requires additional circuitry but can be built for half the cost of a ready built D.V.M. £3.95 each (with data)

Order catalogue no. 404

A full refund guarantee on all items.  
Post and Packing please add 25p (Overseas orders add 60p)  
Lots more goodies in our catalogue. Send a medium sized SAE for your free copy.

## SUPERBOARD II (8K BASIC)

4K RAM - £229 8K RAM - £269  
(modulator included)  
FIBRE GLASS CASE £24.95

## TRS 70 KEYBOARD

4K LEVEL II - £390\* 16K - £490\*  
(modulator included)  
POWER SUPPLY £9.90\*

## PHILIPS VIDEO COMPUTER G7000 - £139\* VIDEOPACS MOSTLY - £10.25\*

COMPLETE RANGE OF GAMES INCLUDING A  
BEGINNERS COMPUTING COURSE

## SOFTY EPROM DEVELOPMENT- BURNER SYSTEM

(kit) - £79.50\*

\*PRICES EXCLUDE VAT - FULL DETAILS ON REQUEST



## VIDEOTIME PRODUCTS

56 Queens Road, Basingstoke,  
Hants. RG21 1REC  
Tel. (0256) 56417. Tlx. 858747



Buy it with Access

# TRANSFORMERS

**30 VOLT RANGE**  
Pri 220/240 sec 0-12-15-20-24-30V  
Voltages available 3, 4, 5, 6, 8, 9, 10,  
12, 15, 18, 20, 24, 30V or 12V-0-12V  
and 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.84	0.78
79	1.0	3.57	0.96
3	2.0	5.77	0.96
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.64
90	12.0	19.17	1.95
91	15.0	21.96	2.08
92	20.0	29.45	O.A.

**EX-STOCK—  
SAME DAY DESPATCH  
+ VAT 8%**

## TRANSFORMERS END OF LINE OFFERS

Ref	Price	P & P
30-Isolator 240V:240V 200VA	£4.54	P+P £1.04
62-Isolator 240V:240V 250VA	£5.62	P+P £1.04
63-Isolator 240V:240V 500VA	£11.50	P+P £2.15
6-250-0-250 @ 100ma 1) Sec 6-3V @ 3-5A 2) Sec 0-5V, 6-3V @ 2/1 amp	£3.20	P+P 78p
7-350-0-350V @ 100ma 1) Sec 6-3V @ 3-5A 2) Sec 0-5V, 6-3V @ 2/1 amp	£4.10	P+P 96p
218-250-0-250V @ 0-15V CT1) Sec 6-3V @ 4A 2) 0-5V, 6-3V @ 2/1 amp	£3.60	P+P 78p
27-250-0-250 @ 60ma 1) Sec 6-3V @ 2.5A 2) Sec 6-3V @ 1 amp	£3.00	P+P 72p
220-410-0-410V @ 180ma 1) Sec 6-3V @ 4 amp CT 2) Sec 6-3V @ 2A 5V @ 2 amp	£5.30	P+P 96p
82-4 amp lead acid Battery Charger (transformer only)	£4.81	P+P £1.04
86-6 amp lead acid Battery Charger (transformer only)	£5.80	P+P £1.04

M184 - To match EL84 15W	£1.62	P+P 32p
M616 - 0-240V: Screen 1) 13-0-13 1A, 2) 12V 150ma	£2.10	P+P 60p
M489 - 0-240V: 1400V @ 150ma, 6-3V @ 4A	£5.50	P+P £1.04
M708 - 6K to 3KΩ matching transformer 5V	90p	P+P 40p
M679 - 120V x 2; 36V 1.6A	£3.00	P-P 78p
M865 - 100V Line to 4Ω 10 watts	£1.90	P-P 60p
M973 - 100V Line to 8Ω 40 watts	£2.90	P+P 60p
M1015 - Choke 8A @ 5 watt 150A Serge	£1.50	P+P 45p
M1020 - 0-240V 12-0-12V @ 50n	97p	P+P 41p
M1126 - 0-120 x 2; 9-0-9 1A	£2.40	P+P 71p
M1130 - 0-240 4500V @ 10ma	£4.86	P+P £1.08
M1165 - 0-115-240V; 14V 50ma	75p	P+P 30p
M624 - 0-380V; 110V @ 13-6A	£12.70	P+P £1.40
B68 - 0-240 15-0-15V 2A	£1.62	P+P 76p
P.W. Purbeck oscilloscope transformer 250-0-250 6-3V 12-9V	£7.51	P+P 90p

**50 VOLT RANGE**  
Pri 220/240V Sec 0-20-25-33-40-50V  
Voltages available 5, 7, 8, 10, 13,  
15, 17, 20, 33, 40 or 20V-0-20V and  
25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.11	0.78
103	1.0	4.57	0.96
104	2.0	7.16	1.14
105	3.0	8.58	1.32
106	4.0	11.41	1.50
107	6.0	15.08	1.64
118	8.0	20.26	2.08
119	10.0	24.98	O.A.
109	12.0	28.90	O.A.

**MAINS ISOLATORS (SCREENED)**  
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.40	0.79
149	60	6.70	0.96
150	100	7.62	1.14
151	200	11.16	1.14
152	250	13.28	1.50
153	350	15.43	1.84
154	500	20.47	2.15
155	750	29.06	O.A.
156	1000	37.20	O.A.
157	1500	51.38	O.A.
158	2000	61.81	O.A.
159	3000	86.68	O.A.

\*Pri 0-220-240V Sec 115 or 240V.  
State sec. volts required.

**CASED AUTO TRANSFORMERS**  
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	5.95	0.90	56W
75	7.73	1.14	64W
150	10.01	1.14	4W
200	10.92	1.45	65W
250	11.59	1.45	63W
500	19.17	1.64	67W
1K	27.88	2.30	84W
1.5K	26.02	O.A.	93W
2K	49.97	O.A.	95W

**12 OR 24V OR 12-0-12V**  
Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0-5	0-25	2.20	0-45
213	1-0	0-5	2.84	0-78
71	2	1	3.81	0-78
18	4	2	4.03	0-96
85	0-5	2-5	5.00	0-96
70	6	3	6.36	0-96
108	8	4	7.42	1-14
72	10	5	8-12	1-14
116	12	6	8-99	1-32
17	16	8	10-72	1-32
115	20	10	13-98	2-08
187	30	15	17-93	2-08
226	60	30	36-74	O.A.

**COMPONENT PACKS**

- 65 1/2W Metal Oxide Resistors.
- 65 1/2W Metal Oxide Resistors.
- 180 Mixed Value Capacitors
- 10 Reed Switches.
- 50 Wire Wound Resistors.
- 10 3000mf 30V Capacitors.
- 26 Assorted presets.
- 50 3 tag terminal strips.
- Hardware, 8A nuts, bolts.
- 200 Mixed Resistors.
- 10 mixed value electrolytic caps.
- 32 mf to 2000 mf.
- each pack
- 70p x 12 1/2 VAT
- P&P 40p + 8% VAT

**AMPLIFIER MODULES**

10W (AL30)	£3.75	
25W (AL60)	£4.95	
35W (AL80)	£7.79	
125W (AL250)	£18.74	
Power Supply PS12	£2.05	
Power Supply SPM80	£4.25	
VAT 12 1/2%	PA12	£6.70
P & P 35p	PA100	£13.88

**ABS PLASTIC BOXES** inset brass nuts, internal slots to take P.C. cards, flush fitting lid.

- P81 180mm x 62 x 40 65p
- P82 100mm x 75 x 40 73p
- P83 120mm x 100 x 45 87p
- \*P84 215mm x 130 x 85 £2.66

P & P 29p. VAT 8% (\*P & P 40p)

**TEST METERS**

AVO 8 MK5	£88-10
AVO 71	£36-00
AVO 73	£48-70
AVO MM5 minor	£32-95
Wee Megger	£74-25
TT169 in circuit transistor tester	£39-53
EM272	£57-80
DA116	£108-90
BM7 Megger	£51-76

Clamp meter 3101 0-30DA without piercing insulation £37.70

All accessories available. P & P £1-15 8% VAT

**NEW RANGE TRANSFORMERS**  
Pri 0-220, 240V Sec. 0-36-48 twice. To give 36-0-36, 48-0-48 72V or 96V.

Pri 0 120 or 220-240V.

Ref.	Price	P & P
3 amp	14.70	1.48
4 amp	18.77	1.84
5 amp	26.64	2.15
171	2.09	0.45
172	2.96	0.78
173	3.59	0.78
174	3.75	0.86
175	5.73	0.96

VAT 8%

**MINI-MULTIMETER**  
DC-1000V AC-1000V DC-500V Res-150kΩ  
1000Ω/V Bargain £7.20 P&P 62p VAT 8%

**TMK500 30KΩ/V Meter Mirror Scale, overload protected, resistance to 60 MegΩ AC/DC to 1000V, DC to 12A 26 ranges £27.55 P&P £1-05 VAT 8%**

**ELECTROSIL** metal oxide low noise resistor.

**ELECTRONIC CONSTRUCTION KIT**  
Home electronics teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. Full instructions and clear diagrams.  
Price £8.29 P&P 96p. VAT 8%

**PANEL METERS**

43mm x 43mm	82mm x 78mm
0-50μA 6-20	0-50μA 6-70
0-500μA 5-95	0-500μA 6-70
0-1mA 5-95	0-1mA 6-70
0-30V 5-95	0-30V 6-70
VU Ind. Panel 48mm x 45mm	2-60
VU Ind. Edge 90mm 500μA	2-36
VU Ind. Edge 54 x 14mm	
250μA F.S.D.	2-60
Carriage 65p.	VAT 8%

**S-DECS**  
Solderless bread boarding

S Dec 70 contacts	£3.55
T Dec 208 contacts	£4.35
U Dec "A" for I.C.s etc	£4.60
U Dec "B" for I.C.s etc	£6.99

P & P 40p. VAT 8%

**ANTEX SOLDERING IRONS**

15W	3-95
25W	3-95
Stand £1-52 VAT 12 1/2%	
P & P 46p. VAT 8%	

**BRIDGE RECTIFIERS**

100V	25A*	£2.10
200V	2A	£0.45
400V	4A	£0.85
400V	6A	£1.25
500V PM7A6 12A*		£2.85

VAT 12 1/2% P & P 15p. VAT 8%\*

**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL 5

**STORAGE CABINETS**

Metal Cabinets 12" wide x 5 1/4" deep, finished blue with transparent plastic drawers.

Type	H (ins)	No. of Drawers	Price
1118	11	15	2 1 £9-85
1633	16	30	2 1 £12-75
1838	18	35	2 1 £14-95
2236	22	30	4 2 £16-85
2260	22	60	- £16-95

Prices include VAT and Post. Cheque/P.O. to:

**Millhill Supplies (Tools),**  
35 Preston Crowmarsh, Benson,  
Oxon OX9 6SL.

Type 1838

**LOW VOLTAGE POWER SUPPLIES**

Low cost, compact, attractively styled, protected and fully guaranteed, the

**EDU-ELEQUIP P.25 and P.30 SERIES**

are the first choice for stabilized power supply units for industrial, educational and general purpose applications.

Quality and reliability with a fast service at prices which solve your low budget problems.

Details and prices from:

**EDU-ELEQUIP**  
28 BUCKINGHAM AVENUE,  
DUNSTABLE, BEDFORDSHIRE.

JAYkit + Standard Parts =

**DM-2**

**DIGITAL MULTIMETER**

- ★ DC Volts ..... 1mV to 1000V
- ★ AC Volts ..... 1V to 500V
- ★ DC Current ..... 0.1mA to 0.2A
- ★ Resistance ..... 1Ω to 20MΩ
- ★ 3 1/2 digit LCD
- ★ Battery Test Point
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (Incl. case)

**FG-1a**

**FUNCTION GENERATOR**

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult pieces of hardware such as screws, washers etc. are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments  
21 Gladeside, Bar Hill  
Cambridge CB3 8DY  
Tel: (0954) 80285

Name \_\_\_\_\_  
Address \_\_\_\_\_

Please send:

- DM-2 @ £4.85
- FG-1a @ £4.50

(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

**JAYkits**



## SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

## NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## RECEIVERS AND COMPONENTS

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO ELECTRONICS, Grenfell Place, Maidenhead, Berks.

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 18V, 25V, 50V.**  
 0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.  
 22 & 47—54p (50V—6p), 100—7p. (50V—8p).  
 220—8p. (50V—10p), 470—11p. (40V—16p).  
 1000/15V—15p. 1000/25V—18p. 1000/40V—35p.  
**Subminiature bead tantalum electrolytics.**  
 0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V—9p.  
 2.2/35V & 4.7/25V—10p. 10/25V & 15/16V—14p.  
 22/16V, 33/10V, 47/8V, 68/3V & 100/3V—16p.  
 15/25V, 22/25V, 47/10V—24p. 47/16V—30p.  
**Subminiature Ceramic Caps. E12 Series 100V.**  
 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.  
 10% 390 pf. to 4700 pf.—4p.  
**Vertical Mounting Ceramic Plate Caps. 50V.**  
 E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.  
**Polystyrene E12 Series 63V. Horizontal Mntg.**  
 10 pf. to 1000 pf.—3p. 1200 pf. to 10,000 pf.—4p.  
**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
 .01 to 0.1—4p. .15 & .22—5p. .33, .47—8p.  
 0.88—11p. 1.0—14p. 1.5—20p. 2.2—22p.  
**Mylar (Polyester) Film 100V Vertical Mounting.**  
 .001, .002, .005—3½p. .01, .02—4½p. .04, .05—5½p.  
**Miniature Film Resistors Highstab. E12 Ser. 5%.**  
 0.125W mixed carbon/metal 10Ω to 1MΩ—1p.  
 0.25W Carbon 10 to 10MΩ (10% over 1MΩ)—1p.  
 (E24 Series av. in 1W C. Film 1Ω to 25MΩ).  
 0.25W, 0.5W & 1.0W Metal Film 10Ω to 2MΩ—2p.  
 1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.  
 8C107/8/9, 8C147/8/9, 8C157/8/9, 8F194 & 7—9p.  
 8 Pin Lcs 741 Op. amp.—18p. 555 Timer—24p.  
 Dil Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.  
 LED's. 3 & 5mm. Red—10p. Green & Yellow—14p.  
 Grommets for 3mm.—1½p. 2 pce. holders 5mm.—2½p.  
 20mm. O.B. Fuses .15, .25, .5, 1, 2, 3 & 5A—3p.  
 20mm. Anti-Surge 100mA, to 5.0A—8p.  
 20mm. Fuseholders P.C. or Chassis Mtg.—5p.  
 Solid Al. knobs 15mm.—25p. 25mm.—35p. 30mm.—50p.  
 400mW Zener diodes E24 series 2V7 to 33V—8p.  
 Prices VAT inclusive Post 10p. (Free over £4).

### THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs, 0945-4188. Immediate settlement.

P.C.B.s Paxolin 10½" x 4½" 4-£1.25. 12" x 9½" 80p. 16" x 11½" £1.35. D.S. 10" x 8½" 80p. Fibre Glass 12" x 7½" £1.50. D.S. 10½" x 7" £1.30. 8" x 7" £1.10. Unit with 8 silicon diodes 800V 20 amp, 8 SCR's 400V 16 amp, 8 Vinkors, W.W. resistors etc. £8.75. 300 small components, trans. diodes £1.50. 7 lbs. assorted components £3.80. List 15p refundable. Post 20p under £1. Insurance add 15p.

### J.W.B. RADIO

28arnfield Crescent, Sale, Cheshire M33 1NL

SURPLUS stocks of Electronic Components at less than wholesale prices. SAE brings free lists. Bardwell Ltd., 212 Stubley Lane, Dronfield-Woodhouse, Sheffield, S18 5YP.

MINIATURE PANEL METERS approx. 1" cube. Left pointer rest position. Scale calibrated 1-10. 600 ohm resistance. Sensitivity 400µA £1.25 each inc. P&P. Wilkinsons Ltd., Industrial Estate, Pocklington, York.

741 T05 can DIL 16p. Plastic 19p. MC1458 (Dual 741) 36p. LM3900 42p. 2N3055 40p. Insulators 3p. 8C107/8/9, 8C147, 148, 158, 182 8p. OC71 25p. 555 22p. 3A70v bridge 40p. 400mW zeners 8p. 1N4148 2½p. 1N4001 3½p. 1N4007 5p. Red led 0.12" 9p. 0.2" Gr. yell. led 12p. 0.2" clips 3p.  
**Resistors, 0.5w 5% E12 10Ω-10MΩ 1p ea. 10+ one value 3p.**  
 Ceramic caps 68pf-6800pf E6 range 1½p.  
 Polyester 0.01-0.22 2½p. 0.33-0.47 8p. 0.68-1.0 9p.  
 Electrolytic 25v 2-160µF 4½p. 220, 500 9p. 1000 16p.  
 Post 20p.

### PROTON ELECTRONICS

Dept. A, 1A, 2 & 4 STOPES ROAD  
 RADCLIFFE, MANCHESTER M26 0TN

TUNBRIDGE WELLS COMPONENTS, Ballards, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquires S.A.E.

100 MIXED COMPONENTS £2.75, 10 LEDS 90p Lists 15p. Sole, 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

## AERIALS

### AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.

B45-UHF TV, B11-VHF Radio.

For next to the set fitting.

Price £5. S.A.E. for leaflets.

### ELECTRONIC MAILORDER LTD.

Ramsbottom, Bury, Lancs, BL0 9AG.

## SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

## BOOKS AND PUBLICATIONS

COMPLETE REPAIR information any requested T.V. £5 (With diagrams £5.50). Any requested service sheet for £1. plus SAE. SAE brings newsletter + special offers - service sheets from 50p, bargain vouchers, unique publications.

AUS (PE) 76 Church Street, Larkhall, Lanarkshire

## RECORD ACCESSORIES

STYLII Cartridges for MUSIC CENTRES, &c. FREE List No.29 for S.A.E. includes Leads, Mikes, Phones &c. FELSTEAD ELECTRONICS, (PE), Longley Lane, Gatley, Cheshire, Cheshire. SK8 4EE.

## LADDERS

LADDERS. Varnished 25½" ext. £40.34. Carr. £3. Leaflet. Callers welcome. Ladder Centre (PEE5) Halesfield (1), Telford S86644.

## FOR SALE

MK14 COMPUTER, extra ram, ramio, revised monitor, fully assembled, working. £70. 01-749 2799.

ELECTRONIC ORGAN. Two manuals, RCO pedals, solid oak console. 150 free phase oscillators. Church voicing. £325. Read, 180 Hillmorton Road, Rugby. Tel: 3107.

PRACTICAL ELECTRONICS SINCE 1967. 01 737 2511

NEW BACK ISSUES OF "PRACTICAL ELECTRONICS" available 70p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

PRACTICAL ELECTRONICS. September 1968 to June 1973. 1969, 1970, 1971, 1972 complete in binders. Offers Greenock (0475) 32548.

UNFINISHED PROJECT. Minisonic 2, all parts including Keyboard, P.C.B.'s, case, switches. Offers. Ring Park Street 72809.

MK14: Fully Working, with extra: Ram, Ram I/O, Keyboard, interface, decoding, PSU. £60. 01-653 1810.

## EDUCATIONAL

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford EM7 0XU. (Tel: Romford 66841).

## TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

### ICS SCHOOL OF ELECTRONICS

Dept. K272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

## CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

### ICS SCHOOL OF ELECTRONICS

Dept. K272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

## COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

### ICS SCHOOL OF ELECTRONICS

Dept. K272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

# What's an electronics enthusiast like you doing in an advertisement like this?

We reckon that if you're a regular reader of this magazine, you might very well be the sort of man or woman who'd be interested in joining Marconi Avionics as an **Electrical Inspector**.

We say this with some confidence because if you're used to building up your own equipment, you're probably well used to finding your way round electronic circuits and wiring and that's just the sort of background we're looking for.

As an Electrical Inspector with us you'll be involved in the inspection of printed circuit boards and assemblies against drawings on a wide range of equipment. Mind you, this equipment will be considerably more complex than any you're likely to have worked on previously, for at Borehamwood we're engaged on a variety of

exciting and challenging projects relating to advanced electronic systems and hardware for such technically sophisticated aircraft as Nimrod and Tornado. But, provided you have a good basic background knowledge of electronic circuitry, we can soon train you to take your place in one of our inspection teams.

We offer a good salary, an attractive range of benefits and the opportunity to make your hobby pay off both financially and in terms of job satisfaction.

Write with details of your experience to Chris Hill at Marconi Avionics Limited, FREEPOST, Elstree Way, Borehamwood, Herts WD6 1BR. Telephone 01-953 2030 ext 3449 during office hours or 01-207 3455 anytime.

**MARCONI  
AVIONICS**

A GEC-Marconi Electronics Company

MINISTRY OF DEFENCE  
**TELECOMMUNICATIONS MECHANIC**

at  
**26 COMMAND WORKSHOP REME  
 FORTHSIDE, STIRLING**

Wage £56.25 plus £20.35 Incentive Scheme per week  
 (Non-Contributory Pension and Good Sick Pay Scheme)

**PROMOTION PROSPECTS**

Experienced craftsmen are invited to apply for this post.

Applications to:

**Personnel Officer**  
 26 Command Workshop REME  
 Fortside, STIRLING  
 Tel: Stirling 2881 Ext. 6

# RESEARCH ASSISTANT

Microprocessors

FISONS have a vacancy in the Statistics Section at Levington Research Station near Ipswich for a Research Assistant to work on the application of mini computer (microprocessor) technology to scientific and industrial research projects. This work bridges the gap between electronics and computerised mathematical methods used in the control of chemical processes, automated laboratories and various agricultural systems.

Ideally, applicants should have at least 'A' level Maths plus a keen practical interest in electronics and computing. Training in programming and other more advanced methods will be given. The section has PDP11, PET, ROCKWELL, INTEL and ZILOG equipment. This is a rapidly developing field in which there are opportunities for advancement.

If this job appeals to you please write for an application form to:

Mike Sharp, Divisional Personnel Officer,  
 Fisons Limited, Fertilizer Division  
 Levington Research Station,  
 Ipswich.

# FISONS FERTILIZER DIVISION



**MISCELLANEOUS**

**NICKEL CADMIUM BATTERIES**

Rechargeable and suitable for 'fast charge' HP7 (AA) £1-13, SUB C £1-47, HP 11 (C) £2-15, HP 2 (D) £3-27, PP3 £4-09, PP3 not suitable for fast charge, PP3 charger £5-81. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec, and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc., 1-2 amp hr 6v. £4-40 2-6 amp hr. 6v. £5-65.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to **SOLID STATE SECURITY DEPT PE 10**, Bradshaw Lane, Parbold, Wigan, Lancs. 02575-4726.

**SUPERB INSTRUMENT CASES BY BAZELLI**, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. **BAZELLI** (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA 6LT.

**CABINET FITTINGS**

FOR  
**Stage Loudspeakers and Amplifier Cabs**  
 Fretcloths, Coverings, Strap & Recess Handles, Feet, Castors, Jacks & Sockets, Cannons, Bulgin 8 ways, Reverb Trays, Locks & Hinges, Corners, Trim, Speaker Bolts etc.  
 Send 2 x 9p Stamps for samples and illustrated catalogue

**ADAM HALL (P.E. SUPPLIES)**  
 Unit 3, Carlton Court, Grainger Road  
 Southend-on-Sea, Essex.

**P.C. BOARDS  
 FOR INDUSTRY 'and' THE AMATEUR**

- One off or production runs
- Assembly of P.C.Bs or kits
- Expert hand soldering
- Design service if required
- Artwork & Photography

**SEAHORSE ELECTRONICS LTD.**  
 Unit 2 Picow Farm Road  
 Service Industry Estate,  
 Runcorn, Cheshire.  
 (09285) 75950

**YOUR PE PROJECT** that never worked, free estimate for diagnosis or repair. By Electronic Engineer, S.A.E. Miller, 53 Falstaff Ave., Reading, Berks.

**MAKE YOUR OWN PRINTED CIRCUITS**

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £1.45. Large range of single sheets in stock at 30p per sheet.  
 Ferric Chloride - 1 lb bags 80p (P&P 50p)\*  
 Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.25.  
 S.A.E. lists and information. P&P 25p/order except\*

**P.K.G. ELECTRONICS**  
 OAK LODGE, TANSLEY, DERBYSHIRE

**NO LICENCE EXAMS NEEDED**

To operate this miniature, solid-state **Transmitter-Receiver Kit**. Only £10.25 plus 25p P. & P. 'Brain-Freeze' 'em with a **MINI-STROBE** Electronics Kit. pocket-sized 'lightning flashes', variable, for discs and parties. A mere £4.50 plus 25p P. & P. Experiment with a psychedellic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher: ready-made multi-function modules. £5 each plus 25p P. & P.  
**LOTS MORE!** Send 25p for lists. Prices include VAT.

**BOFFIN PROJECTS**

4 Cunliffe Road, Stoneleigh  
 Ewell, Surrey (P.E.)

**BURGLAR ALARM CONTROL PANELS** Direct from the manufacturer (Trade enquiries welcome) Type 'A' Mains/battery with adjustable timed exit/entry (sounded), push-button test £33.00 Type 'B' Mains/battery, manual exit, push-button test £20. SAE for list. **WEBB ELECTRONICS**, 41 Winwick Street, Warrington. Tel: 54174.

**TIME WRONG?**

**MSF 60KHz Time Receiver**, data output, £13.70. Sequential year, month, date, day, hours, minutes, seconds Display £10.70 (no case or pcb).  
**RADIO 47 200KHz to Med. Wave Converter** £11.40.  
**OFF FREQUENCY?** Crystal Calibrator £15.80.  
**V.L.F. EXPLORE**, 10-150KHz Receiver £10.70.  
**SIG. GEN.**, 10Hz-200KHz. sine/square, £23.50.  
**PROGRAM YOUR Doorbell**, £19.50, needs speaker.

Each easy-assembly kit includes all parts, printed circuit, case, postage etc, money back assurance so **SEND off NOW.**

**CAMBRIDGE KITS**

45 (FV) Old School Lane, Milton, Cambridge.

**CLEARING LABORATORY.** Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

**RECHARGEABLE BATTERIES**

**TRADE ENQUIRIES WELCOME**

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.26 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021-354 9784, or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

**STOCK** of downgraded capacity cells, type AA, Sub C, C, D and F. Cells are of the rechargeable Sealed Nickel Cadmium type. Please write to Box No. 80.

**GUITAR/PA/MUSIC AMPLIFIER**

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable at £42; 60 watt £37; 200 watt £58; 100 watt twin channel sep. treble/bass per channel £55; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt £32; 200 watt £49; fuzz boxes, great sound, £8.50; bass fuzz £9.50; overdriver: fuzz with treble and bass boosters £14; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable, £89; twin channel £98; bass combo £99; speakers 15 in. 100 watt £35; 12 in. 100 watt £22.50; 60 watt £14.50; 10 watt 10 in. £3.50; 8 in. £3.00.

Send cheque or P.O. to:

**WILLIAMSON AMPLIFICATION**  
 62 Thorncliffe Avenue, Dukinfield, Cheshire  
 Tel: 061-344 5007 or 061-308 2064

**PRACTICAL ELECTRONICS P.C.B.'s**

in glass fibre, Fry's solder tinned and drilled


Dec. 7B RC Motor control 67p. RC Fall safe 39p.  
 Apr. 79 Phaser (EG80) 98p.  
 May 79 Sound operated switch (ES9) 88p.  
 Auto ranging multimeter. Set of 5 pcb's £5.70  
 For full list and current pcb's please send SAE. Pcb's also produced from customers own masters, please send for quote.  
 Postage - On orders less than £10 please add 25p postage. CWO please.

**PROTO DESIGN**

14 Downham Road, Ramsdon Heath,  
 Billericay, Essex CM11 1PU

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P & P. Dataplus Developments, 81 Cholmesley Road, Reading, Berks.

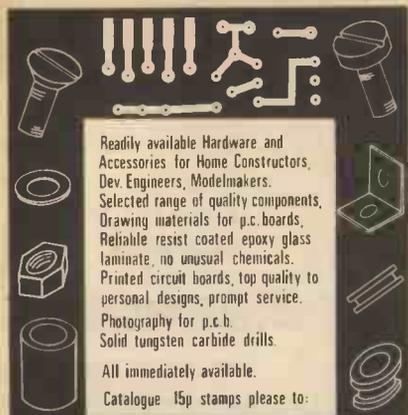MICRO SWITCHES. 21p Stamps for fully illustrated technical literature. IMCO Ltd. 22 Cheapside, Wakefield, Yorkshire.



Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c. boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills. All immediately available. Catalogue 15p stamps please to:

**RAMAR CONSTRUCTOR SERVICES,**  
Masons Rd. Stratford on Avon  
Warwks. CV37, 9NF 0789-4879

CONSTRUCT A VHF TRANSMITTER (not licensable in UK) hand held, range 500yds. Complete kit only £5.25. WEBB ELECTRONICS, 41 Winwick Street, Warrington.

**P.C.B.'s from P.E. DESIGNS**  
in high quality glass fibre, flux varnished and drilled.

DEC. 79: Guitar Sound Multiprocessor Main Board £2.49.  
JAN. 79: Guitar Sound Clock £1.67; L.P. Filter £1.99;  
Noughts and Crosses, full set 5 boards £6.22.  
FEB. 79: Guitar Sound PSU £1.19; Pulse Generator £1.36.  
MAR. 79: Headlight Warning p.c.b. £1.36.  
APR. 79: Phaser £1.38; Sequencer PSU £1.12; Bleepers 75p.  
MAY 79: Multimeter Set £5.85; Sound Switch £0.90.  
For June, July & August prices Tel: (0254) 73755.  
Quotations for P.C.B.'s to customers artworks, send S.A.E.  
All orders P.A.W.K. & I. YATES 25p P. & P. Under £10.00  
C.W.O. to 22, Ambleside Dr., DARWEN LANCs. BB338G.

**THE SCIENTIFIC WIRE COMPANY**  
PO Box 30, London E.4  
Reg. Office 22 Coningsby Gdns

**ENAMELLED COPPER WIRE**

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

**SILVER PLATED COPPER WIRE**

	4.50	2.25	1.44	.90
14, 16, 18	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT  
SAE brings list of copper & resistance Wires  
Dealer Enquiries Invited.

SOLAR CELLS, Batteries, Panels, Thermoelectric Generators, heat pipes, books etc., Details: Edencombe Ltd., 34 Nathans Road, N. Wembley, Middx. HA0 3RX.

**LOGIC PROBE**

A logic probe for detecting logic levels, LED indication for high and low levels TTL over voltage protected. A must for all builders of Microprocessor and Logic Circuitry, simply connect to 5V supply and touch circuit board with probe point for indication. Continuous pulses indicated by proportional brightness glow. Send Cheque or P.O. to C.B.S., Cleveland House, Routh Nr. Beverley, North Humberside.

**£6.75** Plus 50p P/P.

**PLEASE MENTION PRACTICAL ELECTRONICS**  
When replying to advertisements

## NOTICE TO READERS

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.*

## FOR YOUR GUIDANCE VALUE ADDED TAX

In view of changes affecting V.A.T. at the time of going to press, readers should ensure that they have added the correct amount of V.A.T. before ordering.

Export orders are not subject to the addition of Value Added Tax.

## BUILD A SYNTHESISER!

**NO SPECIAL SKILLS REQUIRED**  
**SPECIAL EQUIPMENT REQUIRED**



Using **Dewtron** (Reg'd) PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

**D.E.W. LTD.**  
254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

**CMOS** **AMPLUS ELECTRONICS** **TTL**  
12 Home Close, Bletchley MK3 6JE

Mail Order  
Callers by appointment

C.W.O. only.	P/Packing 35p	Tel. 0908 75898 evenings					
BC107/8/9	12p	BFX88	£1.10	2N514	30p	2N3108	35p
BC119	32p	BFX81	48p	2N516	30p	2N3205	33p
BC140	30p	BFX84	28p	2N518	44p	2N3440	70p
BC142	33p	BFX85	32p	2N530	20p	2N3724	80p
BC143	33p	BFX86	32p	2N1322	24p	2N3725	80p
BC150	46p	BFX87	33p	2N1513	26p	2N3866	£1.20
BC177	70p	BFX88	30p	2N1893	31p	2N4037	67p
BC441	30p	BFY18	75p	2N2218	37p	2N4238	£1.67
BC461	30p	BFY50	28p	2N2219	22p	2N4898	£1.66
BC477	27p	BFY51	28p	2N2221	26p	2N4910	£1.20
BD142	84p	BFY52	28p	2N2222	22p	2N5190	90p
BD538	77p	BFY72	80p	2N2297	48p	2N5191	70p
BD875	60p	BFY75	77p	2N2368	23p	2N5192	80p
BD876	65p	BF167	35p	2N2389	17p	2N5193	70p
BD877	70p	BF173	34p	2N2483	31p	2N5194	80p
BD878	82p	BF257	34p	2N2484	27p	2N5195	87p
BPW43	£1.65	BF258	34p	2N2848	£1.82	2N6038	£1.30
BF113	33p	BF259	34p	2N2894	33p	2N6039	£1.17
BF119	48p	2N696	40p	2N2905	24p	2N6099	82p
BF129	34p	2N697	27p	2N2906	24p	2N6121	41p
BF130	34p	2N698	48p	2N2907	24p	2N6122	44p
BF134	80p	2N706	21p	2N3053	22p	2N6123	48p
BF137	48p	2N708	21p	2N3055	80p	2N6124	49p

All components Brand New and Top Grade. No Seconds. All prices include VAT

# kontite remote control switch


—Simple to install  
even simpler to use



**The Receiver:**  
contains input and  
output cables which  
are connected to the  
appliance to be  
controlled.
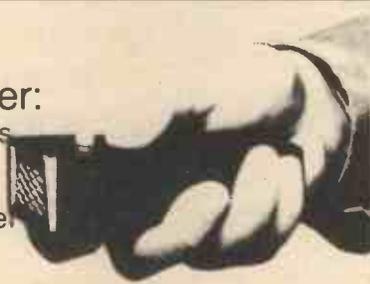
## The Transmitter:

is light and cordless  
and housing the  
battery. Simply,  
point the transmitter  
at the receiver to  
turn on or off



Now available in the U.K. the 'Kontite' Remote Control unit switches electrical appliances and equipment on or off safely from distances of up to 35 feet.

Televisions, radios, hi-fi equipment, lighting, model trains etc. electric fans, electric fires (up to 2kw) and many other appliances are within its scope, providing that they have a power supply of 240/250 AC single phase. 50/60 Hz and a maximum 10 amp rating and also that the relevant safety regulations are applied.

The unit is ideal for use in the home, office, factory and hospital. Particularly useful as an aid to the disabled and invalid—wherever an electrical appliance is difficult to reach in the normal manner.

The Kontite Remote Control Switch  
available now through  
Electrical Component  
Retailers.



If you have difficulty in locating a stockist please contact

## Kay & Co (Engineers) Ltd.

Acresfield House, 15 Exchange Street, Bolton, Lancashire.  
Telephone: Bolton 21041 Telex: 63186

## L.C.D. DIGITAL WATCHES



### ALARM MODEL (illustrated)

- \* Constant 6 digit display shows Hours, Minutes, Seconds or Date.
  - \* 24-hour alarm with on/off indication.
  - \* Night Light.
  - \* Matching adjustable stainless steel strap.
- £12.50 inclusive**

### SLIM 11 FUNCTION CHRONOGRAPH

Time, Date,  $\frac{1}{100}$  second stop-watch.

**£12.50 inclusive**

### ALARM CHRONO WITH DUAL TIME

All functions of alarm model with  $\frac{1}{10}$  second stopwatch and dual time.

**£24.95 inclusive**

### SOLAR ALARM CHRONO

As above but solar assisted.

**£27.50 inclusive**

### LADIES 5 FUNCTION

Hours, Minutes, Seconds, Month and Date.

**£7.95 inclusive**

All products carry full 7 day money back reassurance plus 12 month guarantee.

Please add further 50p for spare battery if required (£1 for No. 4.)

SAE for more details of large range of digital watches, clock/radios, clocks, car stereos, headphones etc.

**SPARKS DEVELOPMENTS,  
53 North Street, Melbourne,  
Derbyshire DE7 1FZ.**

## PE PHASER UNIT

A superb six stage phaser that really gives your guitar lift off. Equals the best commercial models. Uses latest FET op-amps. Glassfibre p.c.b.

COMPLETE KIT OF ALL PARTS AS SPECIFIED.....**£15.95\***

- Pack 1. All semiconductor devices.....**£6.00\***
- Pack 2. Resistors, capacitors & preset pot.....**£3.75\***
- Pack 3. Footswitch, jacks, pot, knob, printed circuit & hardware.....**£4.25\***
- Pack 4. Diecast box and feet.....**£2.00\***

Separate parts: TL062 80p, BF245B 50p, PCB £1.50\*, 8 pin sockets (not included in kit) 21p\* each.

### DESIGNER APPROVED KITS

## PE SUSTAIN UNIT

P.E. OCT.  
1977

Superb quality, low noise, low distortion sustain unit equal to the very best commercial models. Suits all guitars. Glassfibre p.c.b.

COMPLETE KIT OF ALL PARTS AS SPECIFIED.....**£7.95\***

- Pack 1. Resistors, capacitors & p.c.b.....**£1.75\***
- Pack 2. All semiconductor devices.....**£1.75\***
- Pack 3. Footswitch, jacks, pot, knob, and battery clip.....**£2.75\***
- Pack 4. Diecast box and feet.....**£2.00\***

Separate parts: XC5053R 50p\*, RPY5BA 75p\*, Printed circuit board 95p\*, Footswitch £1.50\* each.

### ORION AMPLIFIER

Complete set of semiconductors .....**£9.75**  
Quality glass fibre p.c.b., printed with component locations .....**£3.50**

### PE TV SOUND SEPARATOR

Complete set of semiconductors .....**£2.30**  
High quality glass fibre p.c.b. ....**£1.50**  
Murata filters: SFE6.0MA 50p, CDA6.0MC 50p.

### FERRANTI SEMICONDUCTORS

ZNA116E	£3.75*	ZN425E	£3.50*	ZTX107	11p
ZNA216E	£4.12*	ZN459CP	£2.10*	ZTX108	10p
ZNA134J	£21.00*	ZN1034E	£1.85*	ZTX109	12p
ZN423	£1.00*	ZN1040E	£7.50*	ZTX213	11p
ZN424E	£1.20	BFS61	18p	ZTX384W	24p
ZN424P	£0.66	BFS98	19p	BC415P	16p

Send SAE for quote.

**TO CLEAR! P.C.B.'s for ZNA116 D.V.M. £1.00\* the pair while stocks last.**

POSTAGE & PACKING 15p per order. Orders over £5.00 post free.

All devices are top grade, brand new and to full manufacturers spec.

Send S.A.E. for our data sheet and price list of Ferranti semiconductors.

**PRICES DO NOT INCLUDE VAT.** Add 8% to items marked \* and 12½% to all others.

MAIL ORDER ONLY  
CALLERS BY APPOINTMENT


**DAVIAN ELECTRONICS**  
13 DEEPDALE AVENUE, ROYTON, OLDHAM OL2 6XD.

# GUARANTEED LOW PRICES AND EXPRESS DELIVERY

TTL 74		N LSN		CMOS		DIODES		TRANSISTORS	
7400	9 15	7473	25 42	74155	45 80	741 (8 or 14 pin)	12	2N3440	60
7401	9 15	7474	20 30	74156	45 80	748 (14 pin)	30	2N3442	110
7402	9 15	7475	20 58	74157	45 50	723 (14 pin)	35	2N3702	12
7403	9 15	7476	20 42	74158	50 65	733 (14 pin)	80	2N3703	12
7404	9 15	7478	40 42	74160	50 80	MC1458 (8 pin)	50	2N3704	12
7405	9 15	7480	40 40	74161	50 85	TIL111	75	2N3705	12
7406	22	7481	85	74162	50 80	NE555	20	2N3706	12
7407	22	7482	75	74163	50 60	NE555	80	2N3707	250
7408	12 16	7483	75 60	74164	55 110	LM304	180	2N3819	20
7409	12 18	7484	70	74165	55 115	LM305AH	100	2N3866	95
7410	10 16	7485	60 95	74166	70	LM311 (8 or 14 pin)	100	2N3904	8
7411	15 16	7486	25 30	74168	145	LM324	60	2N3905	8
7412	15 16	7487	25 64	74169	145	LM339	50	2N3906	8
7413	22 30	7488	40	74170	100 190	LM710 (14 pin)	50	AC126	20
7414	45 70	7489	30 70	74171	75 110			AC127	20
7415	16	7490	30 64	74172	55 60			AC128	20
7416	22	7491	30 64	74173	55 60			AC176	20
7417	22	7492	30 70	74174	50			AD149	80
7418	22	7493	70	74175	80			AD161	30
7419	10 16	7494	45 90	74177	125 275			AD162	30
7420	20 26	7495	45 135	74180	70			IN914	4
7421	15 26	7496	75	74181	70 100			IN916	6
7422	20	7497	40	74190	60 70			IN4001-7	4
7423	18	74100	40	74191	60 70			IN4148	4
7424	20 32	74101	22 42	74192	50 70				
7425	20 26	74102	22 42	74193	50 70				
7426	25 29	74103	45	74194	50 80				
7427	12 26	74104	42	74195	50 70				
7428	12 26	74105	42	74196	50 80				
7429	20 20	74106	42	74197	95				
7430	28 30	74107	42	74198	95				
7431	20 32	74108	72	74199	120 70				
7432	20 32	74109	75	74200	58				
7433	12 26	74110	22	74201	60				
7434	45	74111	32 62	74202	90				
7435	40 50	74112	35 55	74203					
7436	60	74113	170	74204					
7437	60	74114	32 50	74205					
7438	65	74115	42 85	74206					
7439	50	74116	42 85	74207					
7440	45 109	74117	42 85	74208					
7441	50 100	74118	52 42	74209					
7442	109	74119	65	74210					
7443	12	74120	50	74211					
7444	12 26	74121	50 130	74212					
7445	12	74122	100	74213					
7446	12 26	74123	80	74214					
7447	12	74124	60	74215					
7448	12 26	74125	60	74216					
7449	25	74126	40 58	74217					
7450	25	74127	40 50	74218					
7451	20	74128	65 145	74219					
7452		74129		74220					
7453		74130		74221					
7454		74131		74222					
7455		74132		74223					
7456		74133		74224					
7457		74134		74225					
7458		74135		74226					
7459		74136		74227					
7460		74137		74228					
7461		74138		74229					
7462		74139		74230					
7463		74140		74231					
7464		74141		74232					
7465		74142		74233					
7466		74143		74234					
7467		74144		74235					
7468		74145		74236					
7469		74146		74237					
7470		74147		74238					
7471		74148		74239					
7472		74149		74240					

PRICES INCL. OF VAT  
PLEASE ADD 25p P&P  
MAIL ORDER ONLY  
**A & M ELECTRONICS**  
DEPT PE1  
2 BRIARDALE,  
EDGWARE WAY, EDGWARE, MIDDXX.

## INTERLOCKING PLASTIC STORAGE DRAWERS

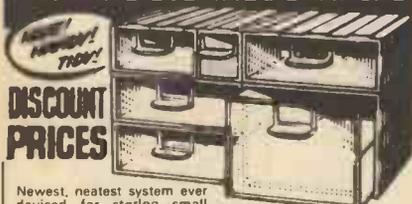

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

As supplied to Post Office, Industry and Government Depts.  
SINGLE UNITS (1D) (5in x 2 1/2in x 2 1/2in) £3.50 DOZEN.  
DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in) £5.50 DOZEN.  
TREBLE (3D) £5.50 for 8.  
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £7.90 for 8.  
EXTRA LARGE SIZE (6D1) £6.90 for 8.

**PLUS QUANTITY DISCOUNTS**  
Orders over £20, less 5%. Orders over £60, less 7 1/2%. PACKING/POSTAGE/CARRIAGE. Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage.  
QUOTATIONS FOR LARGER QUANTITIES.  
Please add 8% V.A.T. to total remittance.  
All prices correct at time of going to press.



Modern, slim-line power panel, countless uses in home, office, factory, showrooms. Perfectly safe, unbeatable. Can be mounted on wall or trailed anywhere in room. Neat rubber base. Smart PVC outer cover. White £3.30. P&P 60p.

**FLAIRLINE SUPPLIES (PE 8)**  
124 Cricklewood Broadway, London N.W.2  
Telephone 01-450 4844

## INDEX TO ADVERTISERS

A & M Electronics	87	Kay & Co.	76
Ace Malltronix	6	Lutterworth Press	76
Acorn Computers	71	Maclin-Zand	5
Adam Hall (P.E. Supplies)	84	Maplin Electronics	Cover IV
Aitken Bros.	6	Marconi Avionics	83
Amplus Electronics	85	Marshall A. (London) Ltd.	77
Astra-Pak	10	M.E.C.A.	60
Aura Sounds	10	Metac	55
A.U.S.	82	Microdigital	4
Barrie Electronics	81	Mill Hill Supplies	81
Bi-Pak	14, 15	Ministry of Defence	84
Birkett J.	15	Modern Book Co.	8
Boffin Projects	84	Monolith	74
British National Radio & Electronics School	9	New Bear	10
Cambridge Kits	84	North London Polytechnic	13
Cambridge Learning	79	Para Sales	8
C.B.S.	85	P.A.W.K. & I. Yates	85
Chromasonic	76	P.K.G. Electronics	84
Chromatronics	56	Phonosonic	12, 13
Clef Products	6	Progressive Radio	74
Codespeed	80	Proops Bros.	2
Colour Print Express	Cover III	Proto Design	84
Computer Components (Teleplay)	Cover II	Proton Electronics	82
Crescent Radio	60	Radio Component Specialists	76
Crimson Elektrik	4	Ramar Constructor Service	85
Crofton Electronics	6	R.S.T. Valve Mail Order	80
C.R. Supply Co.	82	Radio & T.V. Components	7
Davian Electronics	86	Sandwell Plant Ltd	84
Delta Tech	78	Saxon Entertainments	59
D.E.W.	85	Science of Cambridge	18
E.D.A.	78	Scientific Wire Co	85
Edu-Elequip	81	Seahorse Electronics	84
Electronic Mail Order	82	Sentinel Supply	4
Electrovalue	56	Solid State Security	84
Fisons Limited	84	Sparks Developments	86
Fladar	13	Squires, Roger	2
Flairline Supplies	87	Stevensons Electronic Components	75
Fluke International	72, 73	Swanley Electronics	78
George Sales, David	74	T.K. Electronics	74
H.L. Audio	8	Technomatic	88
Heathkit Limited	23	Timetron	73
Home Radio	78	T.U.A.C.	11
I.C.S. Intertext	60, 82	Videotime	80
I.L.P. Electronics	49	Watford Electronics	3
Jayan Developments	81	Willamson Amplification	84
JWB Radio	82	Wilmslow Audio	56

<b>TTL by TEXAS</b> 7400 13p 7401 14p 7402 14p 7403 14p 7404 17p 7405 90p 7406 32p 7407 32p 7408 19p 7409 19p 7410 15p 7411 24p 7412 20p 7413 30p 7414 30p 7415 90p 7416 27p 7417 27p 7420 17p 7421 40p 7422 22p 7423 34p 7424 30p 7425 30p 7426 40p 7427 34p 7428 36p 7430 17p 7431 30p 7432 30p 7433 40p 7434 35p 7435 35p 7440 17p 7441 70p 7442 60p 7443 112p 7444 112p 7445 100p 7446A 90p 7447A 60p 7448 60p 7449 17p 7450 28p 7451 17p 7452 17p 7453 17p 7454 17p 7455 17p 7456 17p 7457 30p 7458 17p 7459 17p 7460 17p 7461 30p 7462 30p 7463 30p 7464 30p 7465 30p 7466 30p 7467 30p 7468 30p 7469 30p 7470 30p 7471 30p 7472 30p 7473 30p 7474 24p 7475 36p 7476 150p 7477 35p 7480 50p 7481 100p 7482 84p 7483A 90p 7484 100p 7485 110p 7486 110p 7487 110p 7488 110p 7489 110p 7490A 33p 7491 80p 7492A 46p 7493A 33p 7494 84p 7495A 70p 7496 65p 7497 180p 74100 130p 74101 65p 74105 65p 74107 34p 74109 55p 74110 55p 74111 70p 74112 200p 74118 130p 74119 210p 74120 110p 74121 28p 74122 48p 74123 58p 74125 55p 74126 60p 74127 60p 74128 75p 74129 75p 74130 75p 74131 70p 74132 200p 74133 200p 74134 200p 74135 200p 74136 200p 74137 200p 74138 200p 74139 200p 74140 200p 74141 200p 74142 200p 74143 200p 74144 200p 74145 200p 74146 200p 74147 200p 74148 200p 74149 200p 74150 200p 74151 200p 74152 200p 74153 200p 74154 200p 74155 200p 74156 90p 74157 90p 74158 90p 74159 90p 74160 90p 74161 90p 74162 100p 74163 100p 74164 100p 74165 100p 74166 100p 74167 100p 74170 240p 74172 720p 74174 120p 74174 90p 74175 85p 74176 90p 74177 90p	74178 160p 74180 93p 74181 200p 74182 90p 74184A 150p 74185 150p 74186 150p 74187 150p 74188 700p 74189 100p 74190 100p 74191 100p 74192 100p 74193 100p 74194 100p 74195 95p 74196 95p 74197 95p 74198 100p 74199 100p 74200 1000p 7421 150p 7422 150p 7423 150p 7562 150p 7563 150p	<b>4000 SERIES</b> 4000 15p 4001 17p 4002 17p 4003 17p 4004 18p 4005 18p 4006 32p 4007 32p 4008 32p 4009 32p 4010 32p 4011 32p 4012 32p 4013 32p 4014 32p 4015 32p 4016 32p 4017 80p 4018 85p 4019 85p 4020 100p 4021 110p 4022 100p 4023 22p 4024 50p 4025 50p 4026 130p 4027 50p 4028 84p 4029 100p 4030 55p 4031 200p 4032 180p 4033 180p 4034 200p 4035 110p 4036 110p 4037 110p 4038 80p 4039 80p 4040 80p 4041 80p 4042 80p 4043 90p 4044 90p 4045 110p 4046 110p 4047 100p 4048 55p 4049 32p 4050 45p 4051 80p 4052 80p 4053 80p 4054 150p 4055 150p 4056 135p 4057 60p 4058 60p 4059 115p 4060 115p 4061 120p 4062 55p 4063 22p 4064 22p 4065 22p 4066 22p 4067 22p 4068 22p 4069 20p 4070 30p 4071 22p 4072 22p 4073 22p 4074 22p 4075 107p 4076 107p 4077 22p 4078 22p 4079 22p 4080 22p 4081 22p 4082 22p 4083 22p 4084 22p 4085 22p 4086 22p 4087 22p 4088 22p 4089 22p 4090 22p 4091 22p 4092 22p 4093 22p 4094 22p 4095 22p 4096 22p 4097 22p 4098 22p 4099 130p 4100 130p 4101 130p 4176 130p 4177 130p	<b>93 SERIES</b> 9301 0.1 9302 0.15 9303 0.15 9304 0.15 9373 0.15 9374 0.15	<b>VERO BOARD</b> 0.1 0.15 (copper clad) 2 1/2 x 3 1/2 33p 2 1/2 x 4 1/2 45p 3 1/2 x 4 1/2 49p 3 1/2 x 5 1/2 56p 4 1/2 x 17 180p 4 1/2 x 22 190p 4 1/2 x 27 340p Pkt of 35 pins 30p Pkt of 50 pins 85p Pin insertion tool 99p <b>VERO WIRING PEN</b> Plus spool 325p Spare spool 320p Wire 7p each Combes 7p each <b>NE5618</b> 425p <b>NE5628</b> 425p <b>NE565</b> 130p <b>NE566</b> 155p <b>NE567</b> 125p <b>NE571</b> 475p <b>RC4151</b> 400p <b>SAD1024A</b> £14 <b>SFF96364</b> 1150p <b>SN76003N</b> 175p <b>SN76013N</b> 140p <b>SN76013ND</b> 120p <b>SN76023N</b> 140p <b>SN76023ND</b> 120p <b>SN76477</b> 250p <b>SP8515</b> 750p <b>TAA621</b> 275p <b>TAA641811</b> 225p <b>TAA651</b> 200p <b>TBA800</b> 90p <b>TBA810</b> 90p <b>TBA820</b> 90p <b>TBA830</b> 90p <b>TBA840</b> 90p <b>TBA850</b> 90p <b>TCA940</b> 175p <b>TCA4500</b> 250p <b>TDA1004</b> 300p <b>TDA1008</b> 320p <b>TDA1022</b> 350p <b>TDA1034B</b> 250p <b>TDA2020</b> 320p <b>TL071</b> 60p <b>TL072</b> 95p <b>TL073</b> 150p <b>TL074</b> 150p <b>TL082</b> 90p <b>TL084</b> 130p <b>TL111-2</b> 250p <b>TL170</b> 50p <b>XR2206</b> 350p <b>XR2207</b> 400p <b>XR2211</b> 600p <b>XR2216</b> 600p <b>XR2240</b> 400p <b>ZN414</b> 70p <b>ZN424E</b> 135p <b>ZN425E</b> 400p <b>ZN1034E</b> 200p <b>95H90</b> 800p <b>NE555</b> 70p	<b>TRANSISTORS</b> AC126 25p AC127 20p AC176 25p AC187/8 25p AF16/7 30p AD149 30p AD161/2 45p AU107 250p BSX19 20p BC109 11p BC117 20p BC147/8 9p BC149 10p BC157/8 10p BC159 11p BC169C 12p BC172 12p BC177/8 17p BC179 18p BC182/3 10p BC184 11p BC187 30p BC212/3 11p BC214 12p BC461 30p BC477/8 30p BC480 30p BC547/8 16p BC549C 18p BC557/8 18p BC559C 18p BC561 18p BC71/2 22p BC131/2 50p BD135/6 54p BD139 56p BD140 60p BD189 80p BD242 70p BDY56 200p BF200 32p BF244 35p BF256 70p BF278 32p BF285 36p BF330 30p BF339 30p BF340 30p BF341 30p BF688 30p 
--	--	--	---	---	--

# Why buy colour films?

When you get a Kodak colour film

# FREE

for every one you send in for processing by the Practical Electronics Colour Print Service!



## Reliability at less cost

Photography can cost you a lot less these days. If you know how to go about it. Like the hundreds of thousands of magazine readers who are delighted with this reliable Colour Print Service — and the replacement films that come FREE to every customer! So why don't you give it a try? Here's what you do. Send us any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with your film in a strong envelope to: The Practical Electronics Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. No stamp is required.

### Send no money

But don't send any money until you see the colour of your prints. We're so confident in the reliability of the service and the quality of our prints, every one of which is checked by professionals at our laboratories.

### Luxury colour prints

You'll be amazed at the crisp, sharp, high-definition sheen finish of the prints we supply . . . borderless to give you maximum picture area. And coming with the prints will be your FREE Kodak colour film, worth around £1, the same size as the one you sent us for processing.

### Unbeatable value

What about prices? Ours are certainly much less than those you would pay in most shops — quite apart from the free film you get every time we develop and print for you.

Our Colour Print Service charges you only 15p for each print, plus 85p towards developing, postage and packing. The minimum charge is 85p inc. VAT (that is, if no prints can be made). The offer is limited to the UK, Eire, CI and BFPO.

### More benefits to you

You benefit in two additional ways. Firstly, you enjoy a personal service with every care taken over each individual order. And secondly, you pay only for what you get — with no credit vouchers as with many other companies. An invoice comes with your prints so it's a straight business transaction.

Use this label if you haven't got an envelope, or pass it to a friend who might like to take advantage of our offer. It is used to send your prints and free film.

*(Offer Exc. Minolta & Sub-miniature. Roll Film 10p surcharge 400 ASA 20p surcharge).*

**From: Practical Electronics Colour Print Service, Freepost, Teddington, Middlesex TW11 8BR**

Mr/Ms \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_

Postcode \_\_\_\_\_



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

# MAPLIN

**ELECTRONIC SUPPLIES LTD**

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554000

Shop: 284 London Road,

Westcliff-on-Sea, Essex.

(Closed on Monday).


Telephone: Southend (0702) 554000



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



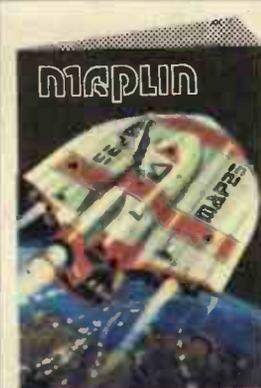A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.**

Please send me a copy of your 280 page catalogue.

I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_