

PRACTICAL

ELECTRONICS


OCTOBER 1978

50p



FREE!
**I.C.
REMOVAL
TOOL**

SOLID STATE INSTRUMENTS

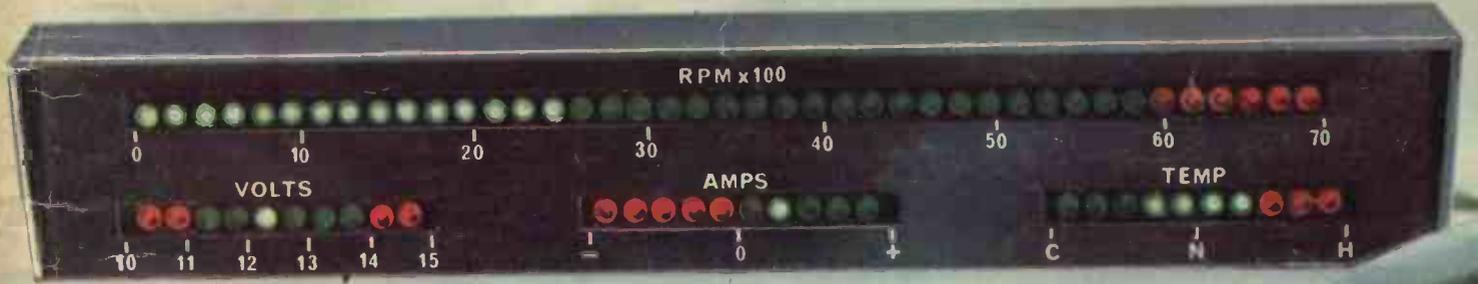

No.1 Battery Voltage Indicator



Also...

DIGITAL TEMPERATURE CONTROLLER

SEND LARGE S.A.E. FOR OUR FREE '79 CATALOGUE

AS SEEN IN
P.E. AUGUST, SEPTEMBER
OCTOBER 1979

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER —
JUST CHECK THE SPEC'S.

COMPUKIT UK101

SAMPLE TAPE
WITH EXTENDED
MACHINE CODE MONITOR
AND DISSASSEMBLER
INCLUDED FREE

LOW COST SUPERBOARD IN KIT FORM

The CompuKit UK101 has everything a one board 'superboard' should have.

- * Uses ultra-powerful 6502 microprocessor.
- * 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- * 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs.
- * Extensive 256 character set which includes full upper and lower case alphanumerics. Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen.
- * Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF
- * Fully stabilised 5V power supply including transformer on board.
- * Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder
- * 4K user RAM expandable to 8K on board £49 extra.
- * 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible).
- * 6502 machine code accessible through powerful 2K machine code monitor on board.
- * High quality thru plated P.C.B. with all I.C.'s mounted on sockets.
- * Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software.



*8K Microsoft Basic means conversion to and from Pet, Apple and Sorcerer easy. Many compatible programs already in print.
SPECIAL CHARACTERS
@ Erases line being typed, then provides carriage return, line feed.
Erases last character typed.
CR Carriage Return — must be at the end of each line.
: Separates statements on a line.
CONTROL/C Execution or printing of a list is interrupted at the end of a line.
"BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.
CONTROL/O No outputs occur until return made to command mode. If an Input statement is encountered, either another CONTROL/O is typed, or an error occurs.
? Equivalent to PRINT

Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

KIT ONLY **£219** + VAT including RF Modulator & Power supply. Absolutely no extras.

Available ready assembled and tested, ready to go for **£269** + VAT

COMMANDS
CONT LIST NEW NULL RUN
STATEMENTS
CLEAR DATA DEF DIM END FOR
GOTO GOSUB IF GOTO IF THEN INPUT LET
NEXT ON GOTO ON GOSUB POKE PRINT REAC
REM RESTORE RETURN STOP
EXPRESSIONS
OPERATORS
+ . / . ↑ NOT . AND . OR . > < . <> . >= <= RANGE 10³² to 10⁺³²
VARIABLES
A.B.C. . Z and two letter variables
The above can all be subscripted when used in an array. String variables use above names plus S.e.g A\$

FUNCTIONS
ABS(X) ATN(X) COS(X) EXP(X)
LOG(X) PEEK(I) POS(I) RND(X)
SPC(I) SQR(X) TAB(I) TAN(X)
FRE(X) INT(X)
SGN(X) SIN(X)
USR(I)
STRING FUNCTIONS
ASC(X\$) CHR\$(I) FRE(X\$) LEFT\$(X\$,I)
RIGHT\$(X\$,I) STR\$(X)
LEN(X\$) MID\$(X\$,I,J)
VAL(X\$)

EXTRAS AVAILABLE SOON

COLOUR ADD-ON enables you to choose your foreground and background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form.

AD-A-RAM EXTENDER CARD provides up to 32K Dynamic RAM Expansion, 8 Eprom sockets for 2708's or 2716's. Parallel Port (centronics compatible) and an RS232C serial port.

WIN YOURSELF AN ANADEX DP8000 LINE PRINTER

There's never enough good software around. That's why COMPUKIT LTD. are sponsoring a software contest. There are 2 categories:

- 1) Business and Education
- 2) Fun and Games

One lineprinter will be awarded to the winner of each category.

Send or bring along to the address shown below the following:

- 1) The program on cassette in the format used by the COMPUKIT UK101
- 2) Any documentation that you have for the program (source listing not necessary)
- 3) This coupon signed by you accepting the rules and conditions of the competition.

RULES:

- 1) Entries, including documentation, must be printed by computer or typed double spaced, with your name on every page.
 - 2) Send or bring your entries to the address shown below.
 - 3) Entries must be received by midnight on 29/2/80, any received after this time are void.
- Winners will be notified by post before 31/3/80.
- 4) You warrant by your signature that all programs and documentation material included is entirely your own creation, and that no rights to it have been given or sold to any other party, and you agree to allow COMPUKIT LTD. to use, publish, distribute, modify, and edit it as it sees fit.

- 5) All entries become the property of COMPUKIT LTD. No entries will be returned nor any questions answered regarding individual entries.
- 6) Judging will be by a selected panel chosen by, and including representatives of COMPUKIT LTD. Judges may assign programs to any of the categories as they see fit. Decision of the judges is final.
- 7) Employees of COMPUKIT LTD, its dealers, distributors, advertising agencies and media are not eligible to enter.

Name _____

Address _____

I agree to abide by the above mentioned rules.

Signature _____

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number. OPEN — 10am to 7pm — Monday to Saturday CREDIT FACILITIES ARRANGED



COMP COMPUTER COMPONENTS

14 STATION ROAD, NEW BARNET, HERTFORDSHIRE TEL: 01-441 2922 (Sales)
CLOSE TO NEW BARNET BR STATION — MOORGATE LINE 01-449 6596
OPEN — 10am to 7pm — Monday to Saturday TELEX: 298755



All Products Ex-Stock Please check availability

(Part of the Compshop Ltd. Group)

PRACTICAL ELECTRONICS

VOLUME 15 No. 10 OCTOBER 1979

CONSTRUCTIONAL PROJECTS

SOLID STATE INSTRUMENTS <i>by Michael Tooley B.A. and David Whitfield B.A., M.Sc.</i>	
Battery Voltage Indicator—1. <i>First of a series</i>	24
DIGITAL TEMPERATURE CONTROLLER <i>by D. Coutts and P. McAllister</i>	32
V.L.F. RECEIVER <i>by C. R. Francis B.Sc.</i>	
Listen to Sferics, Tweeps and Whistlers	42
6 CHANNEL MIXER—2 <i>by S. R. W. Grainger and C. R. Harding</i>	
Wiring and final setting up	50
COMPUKIT UK101—Part 3 <i>by A. A. Berk B.Sc., Ph. D.</i>	
Error codes, program recording and playback, running BASIC	56

GENERAL FEATURES

SEMICONDUCTOR UPDATE <i>by R. W. Coles</i>	
A look at some recently released devices—MM74C911/7, ICL 7611	23
INGENUITY UNLIMITED	
Freezer Temperature Alarm—Digital Servo Amplifier—Fridge/Freezer Thermostat—Sequential Light Chaser—Motion Detector	37
MICROBUS <i>by D.J.D.</i>	
A bi-monthly focus on micro's for the home constructor	67
SCHMITT TRIGGER CIRCUITS <i>by D. F. Bowers B.Sc.</i>	72

NEWS AND COMMENT

EDITORIAL	17
MARKET PLACE	
New products	18
Chicago Consumer Electronics Show	20
INDUSTRY NOTEBOOK <i>by Nexus</i>	
What's happening inside industry	22
Using the I.C. Removal Tool	30
NEWS BRIEFS	
Electronic Club at Margate—On Course—Automatic Fare Collection	30
SPACEWATCH <i>by Frank W. Hyde</i>	
More about Jupiter, Interesting Io, Galilean Satellites	48
PATENTS REVIEW	
Class A Transistor Amplifier	54
COUNTDOWN	62
CB IN THE UK <i>by Dr. Mark Sawicki</i>	66
READOUT	
A selection of readers' letters	70

OUR NOVEMBER ISSUE WILL BE ON SALE FRIDAY, 12 OCTOBER, 1979
(for details of contents see page 65)

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	BRIDGE RECTIFIERS	SPEAKERS	ZENERS
AA119 15	1A/50V 20	8Ω 0.3W 74	Rng. 2V7 39V
AA129 25	1A/100V 22	2.5x3" 74	400mW 9p
AA130 25	1A/200V 22	4.0x2.5" 78	400mW 9p
AA15 15	1A/200V 25	6.0x2.5" 74	Rng. 3V3-33V
BA100 10	1A/400V 29	8Ω 0.5W 74	1 3W 15p
BY100 24	1A/600V 34	7x4" 250	
BY126 12	2A/50V 35	8Ω 3W 160	
BY127 12	2A/100V 44	6"x4" 160	
CRO33 167	2A/200V 46		
OA9 75	2A/400V 53	ALUM. BOXES	
OA47 12	2A/600V 62	3x2x1" 54	
OA70 12	4A/200V 75	2 1/2 x 5 x 1 1/2 72	
OA79 12	4A/400V 79	4x2x1 1/2 72	
OA81 15	4A/800V 120	4x2 1/2 x 1 1/2 85	
OA85 12	6A/100V 73	4x2 1/2 x 2 72	
OA90 6	6A/200V 78	5x4x2 98	
OA91 6	6A/400V 85	6x4x2 108	
OA95 8	6A/800V 85	6x5x2 145	
OA200 9	VM18 DIL 40	8x6x3 185	
OA202 8		10x7x3 210	
IN914 4		12x5x3 215	
IN916 5		12x8x3 265	
IN400/2 5			
IN4003 6			
IN4004/5 6			
IN4006/7 7			
IS44 4			
3A/100V 18			
3A/400V 20			
3A/600V 27			
3A/1000V 30			
SCR's			
Thyristors			
0.6A/200V 30			
0.8A/30V 28			
0.8A/100V 30			
0.8A/200V 35			
1A/600V 70			
5A/300V 35			
5A/600V 43			
8A/300V 48			
8A/600V 85			
12A/300V 59			
12A/600V 92			
15A/700V 150			
15A/100V 95			
15A/200V 105			
15A/400V 160			
15A/800V 295			
TIC44 22			
TIC45 28			
TN4444 140			
	DIAC		
	ST2 20		

OPTO ELECTRONICS

LEDS Plus. Clip	OPTO Isolators
TIL209 Red 125" 13	TL111/2 48
TIL211 Grn 125" 18	TL117 110
TIL212 Yellow 22	
TIL32 Infra Red 58	
0.2" Red TIL220 15	
0.2" Yellow, 19	
Grn, Amber 18	
Square LEDES 48	
OP71 120	
ORP12 63	
ZNS5777 45	
	7 Segment Displays
	LS400 265
	TL1307 675
	TIL312 & 313-3" 106
	TIL321 5" C.Anod 115
	TIL322 5" C.th 115
	DL704 3" C.Cth 99
	DL707 3" C.Anod 99
	DL74 7.5" An 180
	FND357 120
	MAN3640 165
	XAN351 3" Green 180
	Liquid Crystal Display
	3 1/2 digit 875p; 4 digit 975p
	VEROBOARD
	Pitch 0-1 0-15 0-15
	(copper clad) 31p 24p
	(plain) 31p 24p
	2 1/2 x 3 1/2 46p 39p
	2 1/2 x 5 1/2 56p 50p
	3 1/2 x 3 1/2 55p 50p
	3 1/2 x 5 1/2 62p 67p
	3 1/2 x 7 1/2 218p 180p
	4 1/2 x 7 1/2 280p 20p
	Pt of 36 pins 20p
	Spot face cutter 85p
	Pin insertion tool 120p
	VERO WIRING PEN Spool
	Spare Wire (Spool 80p); Combs 7p ea.
	FERRIC CHLORIDE
	1 lb bag Anhydrous 70p + 35p P&P
	DALO ETCH RESIST
	Pen + Spare tip 75p
	COPPER CLAD BOARDS
	Fibre Single-sided Double-sided SRBP
	6" x 6" 75p 90p 80p
	6" x 12" 130p 175p
	SOLDERCON PINS
	100 pins 50p; 500 pins 200p

VOLTAGE REGULATORS

1A TO3 +ve -ve	5V 7805 145p 7905 220p	12V 7812 145p 7912 220p	15V 7815 145p	18V 7818 145p	1A TO20 Plastic Casing	5V 7805 65p 7905 75p	12V 7812 65p 7912 75p	15V 7815 65p 7915 75p	18V 7818 65p 7918 75p	24V 7824 65p 7924 75p	100mA TO92 Plastic Casing	5V 78L05 30p 79L05 65p	6V 78L62 30p	8V 78L82 30p	12V 78L12 30p 79L12 65p	15V 78L15 30p 79L15 65p
CA3085 95	LM323K 625	LM300H 170	LM325N 240	LM305H 140	LM326N 240	LM309K 135	LM327N 270	LM317K 350	LM723 39							
SWITCHES	TOGGLE 2A 250V	SPST 28	DPST 34	1A DPDT 14	1A DPDT C/OFF 15	4 pole 2-way 13	4 pole 2-way 24	PUSH BUTTON	SP changeover	SPST on off 54	SPST biased 85	DPDT 6 tags 70	DPDT C/OFF 79	DPDT Biased 115	3 pole C/OFF 150	
SLIDE 250V	SPST 28	DPST 34	1A DPDT 14	1A DPDT C/OFF 15	4 pole 2-way 13	4 pole 2-way 24	SP changeover	SPST on off 54	SPST biased 85	DPDT 6 tags 70	DPDT C/OFF 79	DPDT Biased 115	3 pole C/OFF 150			
ROCKER: (white) 5A 250V SP change-over centre off	30	ROCKER: Lights red when on. Chrome Bezel, 3A 250V, SPST	52	ROTARY: "Make-A-Switch" Make your own multiway Switch. Adjustable Stop Shafting Assembly. Accommodates up to 6 Wafers	75	Mains Switch DPST to fit	34	Break Before Make Wafers, 1 pole/12 way, 2p/6 way, 3p/4 way, 4p/3 way, 6p/2 way	47	Spacer and Screen	5	ROTARY: (Adjustable Stop)	1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	41	ROTARY: Mains 250V AC, 4 Amp	45

OHIO SUPERBOARD II Only £188.00 ex stock

Yes, we are now selling this single board microcomputer at only £188.00. Due to the recent devaluation of US Dollar against £ Sterling, we have been able to purchase a limited number of Superboards at lower price. Naturally, we wish to pass this price advantage on to our customers. Buy now to avoid disappointment should Mrs. Thatcher & Co. decide to devalue the pound. Superboard II is supplied fully assembled and tested. Requires +5V at 3A and a Video Monitor or TV with RF Converter to be up and running. (Data sheet supplied. We can also supply the RF Converter and Power Supply in kit form or ready-built). 8k Microsoft BASIC IN ROM. 4k Static RAM on BOARD expandable to 8k. Full 53 Key Keyboard with Upper/Lower Case & user programmability and a lot more. See it for yourself. Continuous demonstration on at our retail shop. Specially designed case for Superboard available at £25.00.

CRYSTALS	6 5536MHz 200p	100kHz 385p	7.680MHz 323p	455kHz 385p	9.375MHz 323p	1MHz 323p	10MHz 323p	1.008MHz 323p	10.7MHz 323p	1.80MHz 385p	12MHz 392p	1.832MHz 362p	14.318118M 300p	1.6MHz 395p	18MHz 323p	3.2768MHz 323p	18.432M 33p	4MHz 290p	20MHz 362p	4.032MHz 323p	27.648MHz 350p	4.433619M 135p	48MHz 323p	5 0MHz 355p	100MHz 300p								
VDU BOARD	Thompson SFKEX 68364-1-1, ready built 7 tested £69.00.	UHF Modulator 250p.	Wide Bandwidth Special for Computer 470p.	Full Ascii KEYBOARD Model 756	Low cost, ready-built, tested & Guaranteed. Full technical details supplied. Only £49.75.	KEYPADS	4x4 matrix, push button read switches assembly. Extremely reliable. Only 450p.	DIL SOCKETS (TEXAS)	Low profile	8 pin 10p	14 pin 12p	16 pin 13p	18 pin 16p	20 pin 22p	22 pin 25p	24 pin 36p	28 pin 39p	36 pin 50p	40 pin 50p	DIL PLUGS (Headers)	14 PIN 35p	16 PIN 39p	EDGE CONNECTORS	double type	2 x 10 way 85p	2 x 15 way 99p	2 x 18 way 115p	2 x 22 way 130p	2 x 25 way 149p	2 x 30 way 170p	2 x 35 way 194p	2 x 40 way 210p	2 x 43 way 232p
TRANSFORMERS (mains Prim. 220-240V)	6.0-6V 100mA; 9.0-9V 75mA; 12.0-12V 75mA 95p	8VA type: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A 195p	12VA: 4.5-1.3A 4.5V-1.3A; 6V-1.2A 6V-1.2A 12V-1.5A 12V-1.5A 220p (20p p&p)	24VA: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A 15-8A; 20V-6A 20V-6A 290p (45p p&p)	50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-8A 30V-8A 350p (50p p&p)	100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A 650p (60p p&p)	(N.B. P&P charge to be added above our normal postal charge.)																										

S. & R. BREWSTER LIMITED

WHY PAY MORE?

for Miniature Soldering Irons & Accessories

18 watt Soldering Iron available in 12, 110 & 240Volts, fitted with No. 20 bit	PRICE EACH	P & P Extra EACH
SPARE BITS		
No. 19 size 1.5mm or No. 20 size 3mm or No. 21 size 4.5mm or No. 22 size 6mm	£4.43	+ 24p
No. 78, I.C. Desoldering Bit	52p	—
No. 1920L Long Life Bit	£1.04	+10p
	£1.12	10p
SAFETY STAND	£4.23	+ 70p
SOLDER		
Savbit 20"	61p	+ 9p
Savbit 10"	32p	+ 5p
Lowmelt 10"	76p	+10p



We also Offer & Recommend for Mail Order & Personal Callers Only

Oxy 50 Temperature Controlled Soldering Iron	PRICES EACH including V.A.T. and P & P
Spare tips for above	£11.75
Isotip quick charge rechargeable Soldering Iron	£1.39
Spare tips for above	£24.60
Cable 7/0.2 11 Colours 100 meter reel	£3.42
0.1 Veroboard 3 1/2" x 11 1/2"	£2.40
0.1 Veroboard 4 1/2" x 18"	£4.50
Copper Clad board single sided	75p
Watchmakers Side Cutters	£5.95
Watchmakers Pliers	£4.75
Transformer 100VA 2 X 12V 4.1A	£11.20

OTHER ITEMS ALSO AVAILABLE ASK FOR LIST S.A.E.

MAIL ORDER DEPT.
86-88 Union Street, Plymouth
PL1 3HG Tel: (0752) 65011

Please Quote your Number when ordering



THE MIGHTY MIDGETS

Now, complete your system!

Citronic MM313 Mixer
Ideal for the DIY enthusiast building up a complete disco system 4/8 ch mono, inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU E89.70

The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor, 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.80, or our fabulous Piezo Horns which handle a 5K-20K frequency range. In any PA system up to 100W (No x over required) and cost only £6.32 each.

Projectors Come and see our specially selected projectors from ESO 60 (Stura Multi-flect 150) to E83 37 (Tutor HE DDU) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.

Turntables Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive ONLY £28.75

Repolights Great effect at discos 7 metres long, Multiway connectors, 4 channel £46.00 (inc pack of spare bulbs)

Bulgín Octal plugs and sockets There's always hundreds of Bulgín Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.69 P551 PLUG £1.72.

Many disco accessories All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

Roger Squire's DISCO CENTRES

ALL SHOPS OPEN TUE SAT LATE NIGHT WED (TUP TO 8 PM)

PERSONAL CALLERS ONLY

LONDON 176 Junction Road, N19, 50yds Tolpudden Post, Tube Station. Tel: 01 272 7474

BRISTOL 125 Church Road, Bristol (Near St. George) 1 mile from rail M.2 Tel: 0272 550550

MANCHESTER 251 Deansgate, 4, 5 mins from City Centre Tel: 061 831 7676

GLASGOW 1 Queen Margaret Road (off Queen Margaret Drive) Kelvinhall 20, just behind the BBC. Tel: 041 946 3303

Send your orders to:-

DEPT. PE10, PO BOX 6, WARE, HERTS. Tel: 0920-3182

Visit our NEW shop: 3 BALDOCK ST., WARE, HERTS. Telex: 81786


EXPERIMENTOR BREADBOARDS

FROM 


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


EXP.325. The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin IC's.

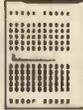


EXP.350. £3.73
270 contact points with two 20-point bus-bars.

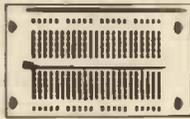

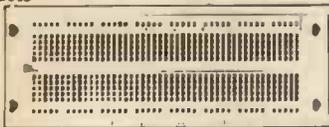EXP.300.
550 contacts with two 40-point bus-bars. £6.13



EXP.650 for Micro-processors. £3.83

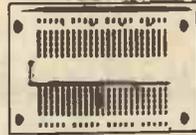

EXP.4B.
More bus-bars. £2.45
ALL EXP.300 Breadboards mix and match with 600 series.



ANTEX IRONS

- 1943 15 watt quality soldering iron with 3/32" bit £4.88
- 1947 Replacement element for 1943 £2.18
- 1944 Iron coated bit 3/32" for 1943 £0.53
- 1945 Iron coated bit 1/8" for 1943 £0.53
- 1946 Iron coated bit 3/16" for 1943 £0.53
- 1948 18 watt iron with iron coated bit £4.59
- 1952 Replacement element for 1948 £2.18
- 1949 Iron coated bit 3/32" for 1948 £0.53
- 1950 Iron coated bit 1/8" for 1948 £0.53
- 1951 Iron coated bit 3/16" for 1948 £0.53
- 1931 X25 25 watt iron, ceramic shaft and another shaft of stainless steel to ensure strength. £4.88
- 1935 Replacement element for 1931 £1.84
- 1932 Iron coated bit 1/8" for 1931 £0.57
- 1933 Iron coated bit 2/16" for 1931 £0.57
- 1934 Iron coated bit 3/32" for 1931 £0.57
- 1953 SK1 soldering Kit - contains 15 watt soldering iron with 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to Solder' £6.38
- 1939 ST3 iron stand made from high grade bakelite chrom plated steel spring, suit all models - includes accommodation for six bits and two sponges to keep the iron bits clean £1.86
- 1724 Model MLX as X25 iron but 12 volts £5.29

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA110	£0.09	BY100	£0.25	BY211	£0.52	OA90	£0.11
AA120	£0.09	BY101	£0.25	BY212	£0.46	OA91	£0.11
AA129	£0.09	BY105	£0.25	BY213	£	OA95	£0.11
AA300	£0.10	BY114	£0.25	BY216	£0.47	OA182	£0.15
AAZ13	£0.17	BY124	£0.25	BY217	£0.41	OA200	£0.09
BA100	£0.11	BY126	£0.17	BY218	£0.41	OA202	£0.09
BA102	£0.37	BY127	£0.18	BY219	£0.41	SD10	£0.07
BA148	£0.17	BY128	£0.18	OA5	£0.07	SD19	£0.07
BA154	£0.14	BY130	£0.19	OA10	£0.69	IN34	£0.08
BA195	£0.16	BY133	£0.24	OA47	£0.09	IN34A	£0.08
BA173	£0.17	BY164	£0.58	OA70	£0.09	IN914	£0.07
BB104	£0.17	BY176	£0.86	OA79	£0.11	IN916	£0.07
BAX13	£0.08	BY206	£0.34	OA81	£0.11	IN4148	£0.07
BAX16	£0.09	BY210	£0.51	OA85	£0.11	IS44	£0.06
						IS920	£0.07

CASES AND BOXES

INSTRUMENT CASES in two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.72
156	11in	6in	3in	£2.92
157	8in	4 1/2in	1 1/2in	£1.79
158	9in	5 1/2in	2 1/2in	£2.43

ALUMINIUM BOXES made from bright aluminium, folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.85
160	4in	4in	1 1/2in	£0.85
161	4in	2 1/2in	1 1/2in	£0.85
162	5 1/2in	4in	1 1/2in	£0.97
163	4in	2 1/2in	2in	£0.87
164	3in	2in	1in	£0.60
165	7in	5in	2 1/2in	£1.43
166	8in	6in	3in	£1.62
167	6in	4in	2in	£1.18

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front - strong construction easily accessible.

No.	Length	Width	Height	Price			
169	2 1/2in	5 1/2in	2 1/2in	12in	3 1/2in	8in	£5.45
168	2 1/2in	7 1/2in	4in	16in	4 1/2in	11in	£8.21

VERO plastic case box. These boxes consist of top and bottom sections which include fixings points for horizontal mounting PC boards/chassis plate the two sections are held together by four screws which enter through the base end and are concealed by plastic feet.

No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4.14
171	140mm	75mm	205mm	£4.62
172	140mm	110mm	205mm	£6.00

SPECIAL OFFERS

MINIDRILL 12v hand held battery-operated mini drill. 7.500 r.p.m. Collet chuck. Ideal for drilling printed circuits or model making. No.1402. £7.79

TRANSFORMER 240v Primary 0-20v @ 2A Secondary. By removing 5 turns for each volt from the secondary winding, any voltage up to 20v @ 2A is obtainable. Ideal for the experimenter. No.2042. £1.50 + 86p. P & P

ANTEX MLX Soldering Iron. Sturdy 25 watt Iron complete with: 4j metres of 2-core cable. Works off a 12 volt battery. Ideal for Car, Boat, Caravan, No.1724. £5.29

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors assorted into the following groups.

16213	60 mixed 1/8w 100ohms-920ohms	£0.69
16214	60 mixed 1/8w 1kohms-82kohms	£0.69
16215	60 mixed 1/8w 10kohms-82kohms	£0.69
16216	60 mixed 1/8w 100kohms-820kohms	£0.69
16217	40 mixed 1/2w 100ohms-820ohms	£0.69
16218	40 mixed 1/2w 1kohms-82kohms	£0.69
16219	40 mixed 1/2w 10kohms-82kohms	£0.69
16220	40 mixed 1/2w 100kohms-820kohms	£0.69

CERAMIC PAKS

16160	24-3 or each value 22pf 27pf 33pf 39pf 47pf 68pf	£0.69
16161	24-3 of each value 100pf 120pf 150pf 180pf 220pf 270pf 330pf	£0.69
16162	24-3 of each value 470pf 560pf 680pf 1000pf 1500pf 2200pf 3300pf	£0.69
16163	24-3 of each value 470pf 680pf 01uf 015uf 022uf 033uf 047uf	£0.69

ELECTROLYTIC PAKS

16201	values from 47mfd - 10mfd	£0.69
16202	values from 10mfd - 100mfd	£0.69
16203	values from 100mfd - 680mfd	£0.69

COMPONENT PAKS

16164	200 resistors mixed value approx (count by weight)	£0.69
16165	150 capacitors mixed value approx (count by weight)	£0.69
16167	80 1/2w resistors mixed values	£0.69
16168	5 pieces assorted ferrite rods	£0.69
16169	2 tuning gangs MW LW VHF	£0.69
16170	1 pack wire 50 metres assorted colours single strand	£0.69
16171	10 reed switches	£0.69
16172	3 micro switches	£0.69
16173	15 assorted pots	£0.69
16175	30 paper condensers - mixed values	£0.69
16176	20 electrolytic trans. types	£0.69
16177	1 pack assorted hardware - nuts, bolts gromets etc	£0.69

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	40p
BP14	2nd book Transistor Equivs & Subs	£1.10
BP22	79 Electronic Novelty Circuits	75p
BP23	52 Projects Using IC741 for Equiv	75p
BP26	Radio Antenna Book Long Distance Reception & Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	80p
BP32	Built Metal & Treasure Locator	85p
BP34	Practical Repair/Renovation CTV	95p
BP35	Handbook of IC Audio Preamp & Power Amplifier Construction	95p
BP36	50 Ccts using Germ/Sil/Zener Diodes	75p
BP37	50 Projects Using Relays/SCR/Triacs	£1.10
BP39	50 Field Effect Trans Projects	£1.25
BP40	Digital IC Equivs & Pin Connection	£2.50
BP41	Linear IC Equivs & Pin Connection	£2.75
BP42	50 Simple LED Circuits	75p
BP43	How to make Walki-Talkies	£1.25
BP44	IC 555 Timer Projects	£1.45
BP45	Projects on Opto-electronics	£1.25
BP46	Radio Circuits Using IC's	£1.35
BP47	Mobile Discotheque Handbook	£1.35
BP48	Electronics Projects for Beginners	£1.35
BP49	Popular Electronic Projects	£1.45
BP50	IC LM3900 Projects	£1.35
BP55	Radio Stations Guide	£1.45
BP180	Coil Design & Construction Manual	85p
BP202	Handbook of Integrated Circuits Equivalents & Substitutes	75p
BP205	1st Book Hi-Fi Speaker Enclosures	75p
BP213	Circuits for Model Railways	85p
BP215	Shortwave Circuits & Gear for Experiments & Radio Hams	85p
BP216	Electronic Gadgets & Games	85p
BP217	Solid State Power Supply Handbook	85p
BP221	28 Tested Transistor Projects	95p
BP222	Short-wave Receivers for Beginners	95p
BP223	50 Projects using IC CA3130	95p
BP224	50 CMOS IC Projects	95p
BP225	A Practical Intro to Digital IC's	£1.20
BP226	Built Advanced Short-wave Receivers	£1.20
BP227	Beginners Guide to Building Electronic Projects	£1.25

REGULATORS

Positive	Price
uA7805 TO220	£0.85
uA7812 TO220	£0.85
uA7815 TO220	£0.85
uA7824 TO220	£0.85
uA7818 TO220	£0.85

Negative	Price
uA7905 TO220	£0.92
uA7912 TO220	£0.92
uA7915 TO220	£0.92
uA7924 TO220	£0.92
uA7818 TO220	£0.92
72723 14 pin DN	£0.62
uA723C TO99	£0.52
LM309K TO3	£1.72

CASSETTES

a/no.3193	30 min lettertape	£0.38
a/no. 301	Dindy C60 tape	£0.41
a/no. 302	Dindy C90 tape	£0.52
a/no. 303	Dindy C120 tape	£0.75

SILICON 1 amp	Type	No.	Price
	50v RMS	BR1/50	£0.23
	100v RMS	BR1/100	£0.25
	200v RMS	BR1/200	£0.29
	400v RMS	BR1/400	£0.41

SILICON 2 amp	Type	No.	Price
	50v RMS	BR2/50	£0.52
	100v RMS	BR2/100	£0.55
	200v RMS	BR2/200	£0.60
	400v RMS	BR2/400	£0.67
	1000v RMS	BR2/1000	£0.78

SILICON 10 amp	Type	No.	Price
	50v RMS	BR10/50	£1.50
	200v RMS	BR10/200	£1.70

SILICON 25 amp	Type	No.	Price
	50v RMS	BR25/50	£1.90
	200v RMS	BR25/200	£2.20

TRIACS

2 amp	TO5 case	Price
100	TR1A/100	£0.38
200	TR1A/200	£0.59
400	TR1A/400	£0.82

6 amp	TO5 case	Price
100	TR16A/100	£0.59
200	TR16A/200	£0.78
400	TR16A/400	£0.80

10 amp	TO5 case	Price
100	TR10A/100	£0.88
200	TR10A/200	£1.06
400	TR10A/400	£1.29

10 amp	TO5 case	Price
400	TR10A/400P	£1.29

ZENER DIODES

400 mw (Bzy88) D007. Glass encapsulated range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v. No. Z4 10p

1w-1.5w Plastic and metal encapsulated. Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v. No. Z13 18p

10w Metal stud type 5010 case. Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v. No. Z10 44p

METAL FOIL CAPACITOR PAKS

16204 - Containing 50 metal foil capacitor like Mullard C280 series - Mixed values ranging from 01uf - 2.2uf. Complete with identification sheet £1.38

JUST QUOTE YOUR ACCESS OR BARCLAYCARD NO.



kontite remote control switch

—Simple to install
even simpler to use



The Receiver:
contains input and
output cables which
are connected to the
appliance to be
controlled.

The Transmitter:

is light and cordless
and housing the
battery. Simply,
point the transmitter
at the receiver to
turn on or off



Now available in the U.K. the 'Kontite' Remote Control unit switches electrical appliances and equipment on or off safely from distances of up to 35 feet.

Televisions, radios, hi-fi equipment, lighting, model trains etc. electric fans, electric fires (up to 2kw) and many other appliances are within its scope, providing that they have a power supply of 240/250 AC single phase. 50/60 Hz and a maximum 10 amp rating and also that the relevant safety regulations are applied.

The unit is ideal for use in the home, office, factory and hospital. Particularly useful as an aid to the disabled and invalid—wherever an electrical appliance is difficult to reach in the normal manner.

The Kontite Remote Control Switch
available now through
Electrical Component
Retailers.



If you have difficulty in locating a stockist please contact:

Kay & Co (Engineers) Ltd.

Acresfield House, 15 Exchange Street, Bolton. Lancashire.
Telephone: Bolton 21041 Telex: 63186

SWEET MUSIC

INTERESTED IN ACCURATE, STABLE, EASILY-BUILT AND CALIBRATED SYNTHESIZER MODULES; POLYPHONIC SYNTHESISERS; COMPUTER MUSIC; OR SOUND PROCESSING? IF SO, FOLLOW THE EXAMPLE OF MANY PROFESSIONAL EQUIPMENT MANUFACTURERS AND USE THE CUSTOM I.C.'s FROM SOLID STATE MICRO TECHNOLOGY, U.S.A. STANDARD D.I.L. PACKAGES.

SSM 2020 DUAL VOLTAGE CONTROLLED AMPLIFIER

Dual two quadrant multipliers with independent control selection. Simultaneous exponential and linear gain with 100dB control range. Differential control inputs. Fully temperature compensated. 84dB S/N ratio at 0.1% distortion with 6V P-P input. Synthesiser V.C.A.'s and a wide variety of audio applications, such as mixers, equalisers, companders, filters and AGC can be realised with the 2020.

SSM 2030 VOLTAGE CONTROLLED OSCILLATOR

Simultaneous exponential and linear inputs for a sweep range of 1,000,000 to 1 up to 200kHz. Accuracy better than 0.25% over 1,000 to 1 range. Simultaneous sawtooth, triangle and pulse outputs. Pulse width modulation on chip with control range of 0 to 100%. Hard and soft synchronisation inputs for a wide variety of modulation and harmonic locking effects.

SSM 2040 VOLTAGE CONTROLLED FILTER CIRCUIT

Four section filter whose cut off frequency can be exponentially controlled over a 10,000 to 1 range. Virtually any active filter can be created and roll off characteristics selected as desired. Low noise and distortion allow use in phase shifters, parametric equalisers, etc.

SSM 2050 VOLTAGE CONTROLLED TRANSIENT GENERATOR

The 2050, 4 pots., 5 resistors, and 2 small capacitors makes an envelope shaper with greater versatility than designs published in the U.K. Min. range of 2 msec. to 20 secs.; exponential response; ADSR and AD outputs; independent gate and trigger. Voltage control of the A, D, S and R functions offers unlimited scope for creation of realistic or unusual envelope shapes.


ALSO: TEL LABS Q81 1k TEMPCO RESISTOR

This 1% tolerance resistor has a temperature coefficient of 3500 ppm per degree Centigrade and is widely specified for temperature compensation of logarithmic amplifiers.

DEVICES MAY BE PURCHASED SEPARATELY BUT P.C.B.'s OR COMPLETE KITS ARE ALSO AVAILABLE FOR SEVERAL SYNTHESIZER MODULES. SEND 35p FOR COMPREHENSIVE APPLICATION NOTES AND SPECS.



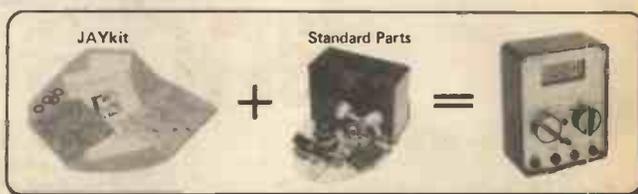DIGISOUND LIMITED,
13 THE BROOKLANDS, WREA GREEN,
PRESTON, LANCS. PR4 2NQ
Tel.: 0772 683138 (MAIL ORDER ONLY)



DM-2



DIGITAL MULTIMETER

- ★ DC Volts 1mV to 1000V
- ★ AC Volts 1V to 500V
- ★ DC Current 0.1mA to 0.2A
- ★ Resistance 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult pieces of hardware such as screws, washers etc. are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments
21 Gladeside, Bar Hill
Cambridge CB3 8DY
Tel: (0954) 80265

Name _____
Address _____

Please send:

- DM-2 @ £5.45
- FG-1a @ £4.95
- (Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

JAYkits

P.E.10



How to make a hobby.

The opportunities in electronics, today, and for the future are limitless — throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics — especially for the servicing of radio, TV and all associated equipment — can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.

We give modern training courses in all fields of electronics — practical D.I.Y. courses — courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.

All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

and a career.

- COURSES AVAILABLE
- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page Colour Booklet.



WE ARE AN INTERNATIONAL SCHOOL SPECIALISING IN ELECTRONICS TRAINING ONLY AND HAVE OVER 40 YEARS EXPERIENCE IN THIS SUBJECT.

PEA 10

NAME

ADDRESS

.....

Block Caps Please

Post now, without obligation, to:-

BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

The professional scopes you've always needed.



Super 6
£162.00 plus VAT



Super 10
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to press

CALSCOPE DISTRIBUTED BY

Watford Electronics,
33-35 Cardiff Road,
Watford, Herts.
Tel: 0923 40588

Audio Electronics,
301 Edgware Road, London W.2.
Tel: 01-724 3564
Access and Barclay card facilities
(Personal Shoppers)

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

Another Crofton First Brand New Full Specification

10" Metal Cased Industrial Video Monitor

£115.00
Total to Personal
Callers-Subject to
availability.

Video Bandwidth 8MZ (3db down).

Ideal for Computer Terminal or General
Video Monitor.

Complete With Own Power Supply.

Input Sensitivity IV Composite.

2102 RAM	£1-05	6402 UART	£3-65
2114 RAM	5-50	2111 RAM	1-50
6800 CPU	5-20	1-008Mhz XTAL	2-50
68A10 RAM	2-25	8T26 Bus Driver	1-05
2513 Char Gen	4-50	81LS95	1-30
96364 Crt Gen	12-10	2516 +5vROM	30-00
96364 ROM	4-50	74LS374	1-40


and CMOS at Competitive Prices • Qty Discounts
can be agreed • Plus VAT 15%+P&P

CROFTON
Electronics Limited
35 Grosvenor Road, Twickenham
Middlesex • Tel: 01-891 1923

SUPER VALUE STORAGE CASES



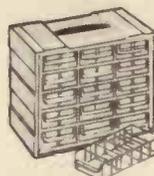Excellent quality high impact
styrene 18 compartment case.
See thru lid. Suitable for all
small, high value parts. 10 $\frac{3}{4}$ " x
6 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ "
£1-99 + P & P 30p.



Rugged construction 15
drawer plastic cabinet. Carrying
handle, easily wall mounted.
Two or more cabinets can be
interlocked. Free dividers in
each pack. 10" x 8" x 6 $\frac{1}{2}$ "
£5-95 + P & P 50p.

ALL PRICES INCLUDE VAT

Send cheque/PO to: **SUMICO LTD.**
Clare, Sudbury, Suffolk CO10 8QN

100 WATT POWER AMPLIFIER MODULES only... £8.99 + 55p



■ 4-16 ohms ■ 100watts rms. **POWER £8.95**
■ 65volts2A ■ full protection **SUPPLY ; P&P 55P**

pre-amp module complete
■ 500mv output **£8.25** **kit only £39.95**
■ bass,treb,vbl.contrls. **POST 55P**
■ high sensitivity

H.S.B.C. 27, HOPE STREET, HANLEY,
STOKE ON TRENT. tel 0782-273815
Amp, pre-amp, power-
supply, chassis, facia,
knobs, all controls, etc, etc.,
postage £1.50.

SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE EQUIPMENT AT INCOMPARABLE PRICES

STANDARD CENTAUR 100W

£309 incl. of carr. & VAT Deposit **£62.00**
12 months @ £24.47 or 24 months @ £14.19

SUPER CENTAUR 200W

£366 incl. of carr. & VAT Deposit **£74.00**
12 months @ £28.94 or 24 months @ £16.78

GXL 200W

With Twin 200 Watt Cabinets

£470 incl. of carr. & VAT Deposit **£94.00**
12 months @ £37.27 or 24 months @ £21.60

GXL WITH PDF BINS (illus)

£502 incl. of carr. & VAT Deposit **£102.00**
12 months @ £39.66 or 24 months @ £23.00

CUSTOM CENTAUR 400/600W WITH FOUR PDF 100A BINS

£833 incl. of carr. & VAT Deposit **£167.00**
12 months @ £66.03 or 24 months @ £38.28

CENTAUR STEREO DISCS C/W LIGHT SHOW & DISPLAY TWIN LOUDSPEAKERS & LEADS 100W-600W

20% DEPOSIT CREDIT TERMS



GXL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Bass/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

JUST PLUG IN AND GO!!
SEND TODAY FOR YOUR FREE BROCHURE

MINI DISCO 100 WATT

MONO SYSTEM WITH LOUDSPEAKERS incl. of carr. & VAT Deposit **£229.00** & VAT **£46.00**
12 months @ £18.13 or 24 months @ £10.52

P.A. SYSTEMS

2 YEAR GUARANTEE
100 WATT incl. of carr. & VAT Deposit **£207.00**
12 months @ £16.35 or 24 months @ £9.49 **£42.00**

- ★ Four Mixing Inputs
- ★ Bass & Treble Controls
- ★ Twin Piezo Horn Columns

200 WATT incl. of carr. & VAT Deposit **£309.00**
12 months @ £24.47 or 24 months @ £14.19 **£62.00**

AMPLIFIER UNITS ONLY

AP100 AMPLIFIER **£56.92** + Carr. £1.50 incl. of VAT
★ 4 Mixed Inputs
★ Boss/Treble Controls
★ Vynide Case
★ 100 Watts Output

AP200 AMPLIFIER **£102.92** + Carr. £1.50 incl. of VAT
★ Six Mixed Inputs
★ Three Sets Bass/Treble
★ 200 Watts Output
★ Slave Socket



NEW SAXON KLAXON

UK Police Hawaii 50 Destroyer
US Police Destroyer

Four Sirens in one package **£20.12** incl. of VAT
Individual Sirens **£8.62**

NEW SAXON SMASH

ALIEN VOICE SIMULATOR

Add a new dimension to your disco with this press button effect unit
Insert between mic & amp **£8.62**

PLUTO PROJECTORS

P140 **£44.27**
150 WATT
INC WHEEL

P5000 **£102.92**
250 watt Q.I. inc Cassette/Wheel
(Full range of wheels - ask for list)

ELECTRECT MIC D1501 **£21.27**
TOP QUALITY UNIT + VAT £2.31

ECM105 LOW COST ELECTRECT CONDENSER MIC + VAT 62p **£5.75**

MELOS CASSETTE ECHO-REVERB UNIT - Twin input VARIABLE SPEED & DEPTH **£74.75**

AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers

SA308 8 ohms 30W 45V **£12.36**
Supply for 2 modules **£13.68**

SA604 4 ohms 50V **£16.67**
Supply for 1 or 2 modules **£17.19**

SA608 8 ohms 60W 65V **£17.82**
Supply for 1 or 2 modules **£17.19**

SA1204 4 ohms 120W 75V **£20.12**
Supply for 1 module **£17.19**

SA1208 8 ohms 120W 95V **£24.15**
Supply for 2 modules **£28.46**

DISCO MIXERS - COMPLETE OR MODULAR

MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE:
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.

COMPLETE MIXERS (with case)
Mono mains **£45.75** + £3.66
Stereo main **£73.31**

MODULES
Mono module **£31.82**
Stereo module **£43.12**
Panel **£4.54**
Kit of knobs/sockets etc **£0.32**

D.I.Y. MODULES FOR P.A. SYSTEMS

MONO/STEREO

Input Modules
Mono PCB only **£7.47**
Stereo PCB only **£12.07**

Mono C/W
Front panel **£10.92**
Stereo C/W
Front panel **£15.81**

Mixer/Monitor Modules
Mono PCB only **£7.47**
Stereo PCB only **£12.07**

Mono C/W
Front panel **£10.92**
Stereo C/W
Front panel **£15.81**

Power supply to suit **£10.92**

send for full details.

SOUND-TO-LIGHT UNITS

3 CHANNEL - 3kW **£33.92**
 Operates from 1W upwards
 Boss/middle/treble/master controls + £1 corr complete
Module only **£22.71**
Panel **£3.39**

4 CHANNEL - 4 kW SOUNDLIGHT SEQUENCER (illus) **£46.57**
 Dimmer on each channel
 Automatic sound light level
 Logic circuitry throughout
Module only **£30.76** Panel **£3.39**

MOTOROLA PIEZO HORNS £5.46 YES!!

FUZZ LIGHTS Red, Blue, Yellow, Green **£26.22**

HEAVY DUTY SPOT BANKS - MATCHES LOUDSPEAKERS
3 way 600W **£40.82** 4 way 800W **£47.72**

100W SPOTS
Red - Blue - Amber - Green **£1.72**

CABINET FITTINGS
ICI Vynide 50" wide **£4.02m**
Kick-res grille 50" wide **£4.02m**
Netlon kick proof 24" wide **£4.02m**
Corners/feet-recess plates 17p
Recess handle 52p
Bar handles **£2.87**
Jack plugs/sockets 29p

LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) **£50.60**

Large 100W 1 x 12 (65 x 48 x 24) **£62.67**

P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24) **£82.22**

P.A. 2 x 12 200W (100 x 38 x 24) **£119.60**

Disco 2 x 12 200W (80 x 63 x 24) **£103.50**

PDF reflex bin (80 x 40 x 41) **£115.00**

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals

- Use with all types of mixer
- Pan and volume controls
- Send for details **£155.25** Deposit **£31.25**

ABOVE PRICES INCL. OF CARR. & VAT

All prices are inclusive of 15% VAT. Shop premises open Tues to Sat 9 am - 5 pm. Lunch 12.30 - 1.30 pm. Mail order dept open Mon to Fri 10 am - 4 pm. Ring 01-684 6385.

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclaycard Number NOT THE CARD.

By Phone You may order COD, Access or Barclaycard. Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS
327 Whitehorse Road, Croydon, Surrey
All Enquiries Large SAE Please Brochures on request

MANCHESTER DISCO CENTRE, 237 DEANS GATE, MANCHESTER CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY

KITS FOR SYNTHESISERS, SOUND EFFECTS



COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. 128-NOTE PROGRAMMABLE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic component kits	KIT 76-5	£28.92
Set of PCBs & layout charts	KIT 76-6	£5.66
Set of text photocopies		£1.36

P.E. 16-NOTE PROGRAMMABLE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic component kits	KIT 86-3	£22.90
Set of PCBs	KIT 86-4	£5.09
Set text photocopies		£1.84

P.E. STRING ENSEMBLE

A multivoiced string instrument synthesiser.

Set of basic component kits	KIT 77-6	£68.70
Set of PCBs & layout charts	KIT 77-7	£24.19

P.E. JOANNA PLUS ORGAN VOICING

A modified version of the P.E. 5-octave piano that retains all the original facilities and also includes switchable organ voicing circuitry.

Set of basic component kits	KIT 71-5	£89.87
Set of PCBs & layout charts	KIT 71-6	£29.51
"Sound Design" booklet		£1.00

ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic components	KIT 80-6	£100.84
5-octave set of PCBs (as published)	KIT 80-7	£26.02
Additional 3-octave extension basic parts	KIT 80-5	£40.98
Additional 3-octave set of PCBs (as published)	KIT 80-8	£9.45
Set of text photocopies		£1.81

P.E. MINISONIC MK2 SYNTHESISER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available)	KIT 38-23	£67.05
Set of PCBs (incl. layout charts)	KIT 38-24	£9.87
"Sound Design" booklet		£1.00

P.E. SYNTHESISER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Main Unit basic component kits	KIT 23-27	£86.99
Main Unit set of PCBs & layout charts	KIT 23-28	£14.52
Keyboard Unit basic component kits	KIT 23-29	£82.07
Keyboard Unit set of PCBs & layout charts	KIT 23-30	£8.42
Main Unit set of text photocopies		£5.91
Keyboard Unit set of text photocopies		£2.30

ELEKTOR FORMANT SYNTHESISER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic component kits	KIT 66-12	£193.68
Set of PCBs (as published)	KIT 66-13	£53.92
Set of text photocopies		£7.83

P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic parts with foot switches	KIT 42-1	£8.45
Basic parts with panel switches	KIT 42-2	£5.55
PCB & layout chart	PCB 43A	£1.57
Text photocopy		28p

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic component kit	KIT 78-1	£49.99
Main unit PCB (as published)	PCB 9913	£3.69
Extension unit basic component kit	KIT 78-2	£47.69
Extension unit PCB (as published)	PCB 788	£1.16
Text photocopy		

ELEKTOR ANALOGUE REVERB UNIT

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set	KIT 83-1	£29.49
Additional Delay basic components	KIT 83-2	£20.07
PCB (as publ.) to hold both kits	PCB 9973	£4.31
Text photocopy		

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic component kits	KIT 85-3	£43.75
Set of PCBs & layout charts	KIT 85-4	£10.62
Set of text photocopies		£2.52

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Set of basic components, incl. PCB & chart	KIT 88-1	£10.14
Text photocopy		68p

ELEKTOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic components	KIT 70-1	£19.11
PCB & layout chart	PCB 70A	£2.56
Text photocopy		67p

P.E. PHASING UNIT

A simple but effective manually controlled phasing unit.

Set of basic components incl. PCB & chart	KIT 25-1	£3.52
Text photocopy		28p

PHASING CONTROL UNIT

For use with Phasing Kit 25 to automatically control rate of phasing.

Set of basic components incl. PCB & chart	KIT 36-1	£5.21
Text photocopy		10p

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Set of basic components, PCB & chart	KIT 89-1	£3.82
Text photocopy		78p

P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control of depth.

Set of basic components, PCB & chart	KIT 53-1	£2.76
--------------------------------------	----------	-------

ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic components	KIT 82-1	£16.61
PCB (as published)	PCB 9951	£3.29
Text photocopy		

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments.

Set of basic components	KIT 56-1	£7.57
PCB & layout chart	PCB 56A	£1.78
Text photocopy		68p

P.E. FUZZ UNIT

A simple fuzz unit. Slightly modified from the original.

Set of basic components, PCB & chart	KIT 65-1	£2.25
--------------------------------------	----------	-------

TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Set of basic components, PCB & chart	KIT 54-1	£3.23
--------------------------------------	----------	-------

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.

Set of basic components, PCB & chart	KIT 74-1	£4.97
Text photocopy		39p

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, foot switches, PCB & chart	KIT 75-1	£5.64
Basic components, panel switches, PCB & chart	KIT 75-2	£4.08
Text photocopy		38p

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control.

Set of basic components, PCB & chart	KIT 51-1	£3.99
--------------------------------------	----------	-------

P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played.

Basic components, foot switches, PCB & chart	KIT 58-1	£8.43
Basic components, panel switches, PCB & chart	KIT 58-2	£5.31
Text photocopy		58p

ELEKTOR WAVEFORM CONVERTOR

Converts a saw-tooth waveform into sinewave, mark-space saw-tooth, regular triangle, or square-wave with variable mark-space ratio.

Basic components, PCB & chart, but excl. sw's.	KIT 67-1	£9.24
--	----------	-------

P.E. VOLTAGE CONTROLLED FILTER

Extracted from P.E. Minisonic project.

Set of basic components, PCB & chart	KIT 65-1	£7.88
--------------------------------------	----------	-------

P.E. RING MODULATOR

Extracted from P.E. Minisonic project.

Set of basic components, PCB & chart	KIT 59-1	£6.05
--------------------------------------	----------	-------

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic components	KIT 87-1	£4.66
PCB (as published)	PCB 79040	£1.74
Text photocopy		38p

10% DISCOUNT VOUCHER (PE 70)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly coded, C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E.

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.30 each. Other goods: Under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 20p, other countries send 50p.

PHONOSONICS · DEPT PE70 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH TERMS: C.W.O. MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list: giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list: Europe—send 20p; other countries—send 50p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50
4 Octave (49 notes) £32.25
5 Octave (61 notes) £39.75

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each KBD note:

Type GJ — SPCO 26½p ea. Type GA — 1 pr of contacts, normally open 24p ea. Type GB — 2 pr N/O 28½p ea. Type GC — 3 pr N/O 37½p ea. Type GE — 4 pr N/O 46½p ea. Type GH — 5 pr N/O 58½p ea. Type 4PS — 3 pr N/O plus SPCO 57p ea.

P.E. NOISE GENERATOR

Extracted from the P.E. Minisonic.

Set of basic components,
PCB & chart

KIT 60-1 £4.00

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Set of basic components,
PCB & chart

KIT 28-1 £4.68

Text photocopy 28p

P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.

Set of basic components,
PCB & chart

KIT 44-1 £5.24

Text photocopy 49p

P.E. ENVELOPE SHAPER WITH VCA

Has an integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R functions.

Set of basic components,
PCB & chart

KIT 50-1 £7.34

Text photocopy 58p

P.E. GENERATOR

An ADSR envelope shaper without VCA, and additional providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Set of basic components

KIT 63-1 £5.13

PCB & layout chart

PCB 63A £2.00

Text photocopy 58p

P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphones etc., to be processed by synthesiser circuits.

Set of basic components,
PCB & chart

KIT 81-1 £3.23

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic components,
PCB & chart

KIT 46-1 £16.42

Power Supply components,
PCB & chart

KIT 46-2 £6.90

Text photocopy 97p

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.

Set of basic components,
PCB & chart, but excl. sw.

KIT 69-1 £8.19

Text photocopy 58p

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Set of basic components,
PCB & chart

KIT 62-1 £5.03

P.E. CONSTANT-DISPLAY FREQUENCY COUNTER

A 5-digit counter for 1Hz to 55KHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Set of basic components

KIT 79-1 £26.45

PCB (as published)

PCB 79A £3.33

Text photocopy 78p

INTEGRATED CIRCUITS

301	48p
318	220p
320-15	195p
323	562p
324	87p
341-15	87p
356	101p
709	48p
723	81p
726	1005p
741	24p
748	57p
4001	15½p
4007	17½p
4011	17½p
4013	34p
4016	33p
4017	54p
4024	46½p
4046	96p
4049	37½p
4066	40½p
4069	18p
4081	16½p
4136	126p
AM2833	396p
AY-1-0212	617p
AY-1-1320	636p
AY-1-6721/6	188p
CA3046	71p
CA3080	63p
CA3084	209p
FX209	729p
M252	680p
MC3340	150p
MCM6810	670p
RC4195	117p
SA01024	1762p
SG3402	262p
TD1A1022	582p
TL074	120p
KR2207	420p
2N425	375p
7400	20p
7402	20p
7404	18p
7413	31p
7420	15p
7447	72p
7472	22½p
7473	37½p
7474	31½p
7478	241p
7490	42p
7493	49½p
74121	53p
74123	55½p
7805	145p
7808	145p
7812	145p
7815	145p
7818	145p



PHONOSONICS

Random Electronic


EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete
or
Kit



PCB
Layout

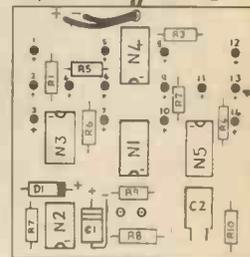

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice £3.95
- b *Ready built Dice £4.75 (INCL. P+P)

Order now from: **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk 0473-210151

Amount enclosed £

Name

Address

please state amount required in appropriate box a b

LIGHTING & AMPLIFIER MODULES FROM L&B

JUST LOOK AT THESE PRICES!

Superior high quality lighting control modules.
No additional power supply, just ready to go!

— LB31000SL —

Sound-light, 3 channel x 1000W. Zero mains voltage switching, high sensitivity, high input impedance, excellent separation.

£18.90

— LB41000LS —

Light sequencer, 4 chan. x 1000W. Suedo-random, zero switching.

£14.90

Two-speed controls, excellent for stage lighting.

— LB31000LD —

Light dimmer, 3 chan. x 1000W. Stage lighting from full off to full on.

£12.90

Massive audio power at your fingertips! For use in many applications.

— LB25 —

25W, RMS 4Ω
10Hz-50kHz
T.H.D. 0.1% 90dB S/N

£8.20

PREAMPLIFIERS

LBPA1 Stereo disc/tape £14.50

LBPA2. 4 channel gen. purpose mixer £13.50

LBPA3. Stereo disco with mic. £22.00

— LB250 —

250W R.M.S. 4Ω
10Hz-20kHz
T.H.D. 0.3% 110dB S/N

£29.50

— LB100 —

100W R.M.S. 4Ω
10Hz-25kHz
T.H.D. 0.4% 80dB S/N

£15.70

POWER SUPPLIES

LB25PS£10.00

LB100PS£12.20

LB250PS£21.20

All above prices include VAT. Please add 50p p/packing. Quantity/trade discounts, up to 33% available. Export enquiries welcome. SAE for further info.

L&B ELECTRONICS 45 WORTLEY ROAD, W. CROYDON SURREY CRO 3EB. TEL: 01-689 4138



BUY an ELF 11 microcomputer for less than some TV games

only **£79.95** + VAT

ADD-ONS

- POWER SUPPLY (6.3V AC) for ELF 11
 - ELF 11 DE LUXE STEEL CABINET (IBM Blue)
 - GIANT BOARD KIT System/Monitor, Interface to cassette - RS232, TTY etc
 - 4K STATIC RAM board kits (requires expansion power supply)
 - Expansion power supply (required when adding 4K Rams)
 - ASC11 Keyboard Kits 96 printable characters etc
 - ASC11 d/lux steel cab. (IBM Blue)
 - KLUGE prototype board (build your own circuits)
 - 86 pin Gold plated connectors (each)
 - ELF Light pen writes/draws on TV screens
 - Video graphics board 32/64 characters by 16 lines on TV/monitor screens
 - ELF 11 Tiny basic on cassette
 - ELF 11 Bug/monitor powerful systems monitor/editor
 - T. PITMANS short course in programming manual (Nil VAT)
 - T. PITMAN short course on tiny basic manual (Nil VAT)
 - RCA 1802 users manual (NIL VAT)
 - † Text Editor: Assembler, Disassembler (each)
- SAVE 10% AND BUY ALL THREE TOGETHER
All units can be supplied wired and tested
New Games on tape. Send for list.

EX-VAT

- 5.00
 - 23.01
 - 36.00
 - 69.44
 - 19.00
 - 50.58
 - 15.02
 - 12.83
 - 4.00
 - 6.50
 - 69.95
 - 13.50
 - 13.50
 - 4.00
 - 4.00
 - 4.00
 - 16.95
- P & P £2.00

ELF 11 BOARD WITH VIDEO OUTPUT

STOP reading about computers and get your "hands on" an ELF 11 and Tom Pitman's short course. ELF 11 demonstrates all the 91 commands which an RCA 1802 can execute, and the short course speedily instructs you how to use them. ELF 11's VIDEO OUTPUT makes it unique among computers selling at such a modest price: The expanded ELF 11 is perfect for engineers, business, industry, scientific and educational purposes.

Send S.A.E. for comprehensive brochure

SPECIFICATION

- RCA 1802 8 bit microprocessor with 256 byte RAM expandable to 64K bytes
- RCA 1861 video IC to display program on TV screen via the RF Modulator
- Single Board with professional hex keyboard fully decoded to eliminate the waste of memory for keyboard decoding circuits
- Load, run and memory project switches
- 18 registers
- Interrupt, DMA and ALU
- Built in power regulator
- 5 slot plug in expansion bus (less connectors)

Name

Address


Barclaycard/Access

To Newtronics 138 Kingsland Road
London E2 8BY
Tel: 01-739 1582
DEPT. P.E.

SOLE U.K. AGENTS

BI-PRE-PAK

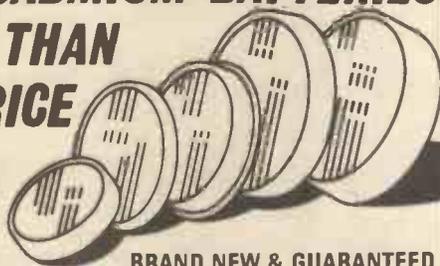NICKEL-CADMIUM BATTERIES AT LESS THAN HALF-PRICE



BY A WORLD-FAMOUS MANUFACTURER IN 5 VALUABLE SIZES

BRAND NEW & GUARANTEED

Type	Capacity in mAh	Voltage	Charge Rate mA/12 hrs	Size in mm dia. x Thickness	Our price inc. 18% VAT
NC20	200	1.24	20	24.8 x 7.4	45p
NC28	280	1.24	28	34.4 x 5.3	60p
NC50	500	1.24	50	34.3 x 9.5	80p
NC90	900	1.24	90	50.5 x 8.3	£1.20
NC175	1750	1.24	175	50.7 x 14.9	£1.75

- High capacity for very small size
- Wide temperature operating range
- Low internal resistance
- Very simple charging circuit required
- INDEFINITE SHELF LIFE
- Ideal for portable & emergency equipment, instruments, radio control, etc.

TO ORDER
Please send cash with order. Minimum order £3.00 plus 30p p/p in U.K. Orders over £10 carr. paid U.K. All prices inc. VAT. To pay by ACCESS or BARCLAYCARD simply Phone or send your account number when ordering.

TRADE ENQUIRIES INVITED
(PE1) 222-224 West Road
Westcliff-on-Sea, Essex
SS0 9DF
Telephone 03708 5543

BI-PRE-PAK LTD.

SUPER SPOT DISCO SYSTEM 2

- ★ Fully enclosed drive unit ★ 8A triacs ★ Fused ★ Suppressed
- ★ Expandable using slave units connected via 9 way socket
- ★ Stand takes 16 Spots ★ Regd. Design
- ★ 450 watt/channel ★ Sequence, auto or audio drive
- ★ Fully adjustable ★ Fully Isolated audio input and output sockets ★




	Built & tested	Kit	Slave	Slave kit
3 Ch. 3 Spots	£64.95	£48.95	£39.95	£37.95
3 Ch. 6 Spots	£78.95	£63.95	£59.95	£56.95
4 Ch. 4 Spots	£76.95	£69.95	£54.95	£41.95
4 Ch. 8 Spots	£89.95	£76.95	£67.95	£62.95
4 Ch. 16 Spots	£117.95	£102.95	£96.95	£90.95

Price Includes: Spot stand, Swivel spot holders, Coloured spot lamps, Sequence drive or slave unit, Fitting kit for ceiling hung & surface or wall mounting V.A.T. Post & Packing and Guarantee.

NOBLE ELECTRONICS (PE)
26 Lloyd Street, Altrincham, Cheshire WA14 2DE.
Tel: 061-941 4510

Trade enquiries welcome

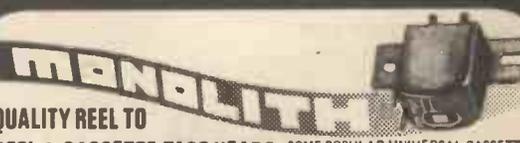

QUALITY REEL TO REEL & CASSETTE TAPE HEADS

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

812-01 MONO PLAYBACK	£1.89	E12-09 MONO/STEREO ERASE	£1.85
812-02 MONO RECORD/PLAYBACK	£4.02	822-02 TWIN HALF TRACK RECORD/PLBK	£5.97
824-01 STEREO PLAYBACK	£3.30	C44RPS02 QUAD QUARTER TRACK REC/PLBK	£9.37
824-02 STEREO RECORD/PLAYBACK	£6.88	C22S02 TWIN HALF TRACK ERASE	£4.72
824-RP STEREO GLASS FERRITE REC/PLBK	£11.80		


MAGNETIC TAPE HEADS CATALOGUE 25 PENCE
AUDIO AND HI-FI CATALOGUE 180 PAGE FULL COLOUR! 50 PENCE

MONOLITH
THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER
ALL PRICES INCLUDE VAT

TRITON SINGLE PERSONAL COMPUTER

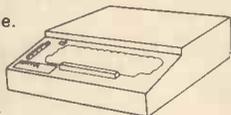Three new exciting expandable systems designed for ease of construction and flexibility. Kits come complete with case, power supply, full keyboard, PCB. All components available separately. See catalogue. Full hardware & programming manual available. The system is easy to expand and is well supported. Features:- 2, 2.5 or 7k basic in Eprom (See catalogue)



- Single board
- Holds up to 8k memory
- UHF or video output
- Cassette interface
- Three firmware options
- Basic in eprom
- 64 graphic characters
- Plug in expansion boards

From **£286** +VAT

BI DIRECTIONAL MATRIX PRINTER £595 +VAT

The BD80 is a low cost, 80 column line printer with microprocessor control to provide excellent reliability and performance.

- 5x7 Dot matrix
- 10 char per inch
- 6 lines/inch
- 400 char buffer
- Full asch char set
- 10 lines/sec
- paper advance
- 112 char/sec
- 84 lines per minute
- Self test
- Fully cased




A UNIQUE PRINTER FAST AND RELIABLE

Switch selectable baudrate from 110 to 9600 on a standard V24 and RS232 interface. Send SAE for further details. Ideal printer for Triton or any system requiring high speed reliable hard copy. We can supply consumables.

EXPANSION MOTHERBOARD

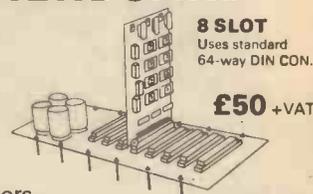TRITON. Expand your Triton simply and easily with our new 8-slot motherboard complete with its own P.S.U. takes 8 plug-in Euro cards. Plug-in 8k RAM card and Eprom cards now available. Kit complete with PSU & 1 set connectors.



8 SLOT
Uses standard
64-way DIN CON.

£50 +VAT

8K RAM CARD

Triton 8k static Ram card. Kit uses 2114 Low power 4k. Static Rams. On board regulation. jump select. PCB only £15 Rams £5.50 MEM Kit less Rams £31 incl. Kit & components.



Compl. kit
£97 +VAT

8K EPROM CARD

Triton 8k Eprom card kit. Designed to take up to 8x2708 Eprom (1kx8) as Ram card. PCB only £15 Kit less Eproms £31 Eproms (blank) £9 Plus VAT



Complete kit £97 +VAT


VIDEO MONITOR NEW

A brand new fully cased (metal) high resolution 10" video monitor with PSV for only £69 +VAT

Ideal for Triton or any home computer system. Carriage by Securicor can be arranged.

Send SAE for details or see our new catalogue.


ONLY £69! +VAT

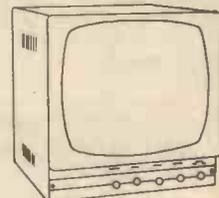

PCB CONNECTORS


Edge connectors, gold contact double sided

PCB connectors	Price	156"	Price
22/44	£3.20	6/12	£1.62
25/50	£3.60	10/20	£1.40
28/56	£3.90	15/30	£3.00
30/60	£4.15	18/36	£3.00
35/70	£4.60	22/44	£3.00
36/72	£4.75	28/56	£3.40
40/80	£5.00	36/72	£3.90
43/86	£5.50	43/82	£4.60
50/100	£5.80 (£100 BUS)		Plus VAT

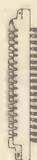

Video Display Interface Module £69 +VAT

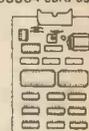Completely built and tested the SFKE68364 card uses the industry standard SFF96314 CRT control chip & allows ASCII parallel input of data to be output to video monitor. 64 character by 16 line display. Full cursor control. Single 5v supply. Full details available on request (Send SAE). UHF modulator available £2.50 extra and VAT.



COMPONENTS 74LSXX

SN74LS00N .10	SN74LS40N .25	SN74LS113N .44	SN74LS185N 1.70	SN74LS248N 1.95
SN74LS01N .10	SN74LS42N .78	SN74LS114N .44	SN74LS186N 1.75	SN74LS249N 1.20
SN74LS02N .20	SN74LS47N .85	SN74LS122N .78	SN74LS188N 1.95	SN74LS251N 1.45
SN74LS03N .10	SN74LS48N .85	SN74LS123N .99	SN74LS169N 1.85	SN74LS253N 1.25
SN74LS04N .20	SN74LS49N 1.09	SN74LS124N 1.50	SN74LS170N 2.50	SN74LS257N 1.40
SN74LS05N .26	SN74LS54N .21	SN74LS125N .85	SN74LS173N 2.20	SN74LS258N .86
SN74LS08N .20	SN74LS55N .21	SN74LS126N .86	SN74LS174N 1.15	SN74LS259N 1.48
SN74LS09N .22	SN74LS56N 1.50	SN74LS127N .75	SN74LS175N 1.05	SN74LS260N .38
SN74LS10N .18	SN74LS573N .35	SN74LS133N .38	SN74LS181N 2.75	SN74LS261N 1.50
SN74LS11N .20	SN74LS574N .40	SN74LS136N .75	SN74LS190N 1.75	SN74LS266N .38
SN74LS12N .26	SN74LS575N .48	SN74LS138N .40	SN74LS191N 1.75	SN74LS273N 1.85
SN74LS13N .56	SN74LS576N .36	SN74LS145N 1.29	SN74LS192N 1.46	SN74LS279N .79
SN74LS14N .88	SN74LS578N .36	SN74LS146N 1.75	SN74LS193N 1.75	SN74LS280N 1.75
SN74LS15N .25	SN74LS583N 1.15	SN74LS151N .85	SN74LS194AN 1.89	SN74LS283N 1.80
SN74LS20N .20	SN74LS585N 1.10	SN74LS152N .60	SN74LS195AN .85	SN74LS290N 1.80
SN74LS21N .28	SN74LS586N .40	SN74LS154N 1.80	SN74LS196N 1.20	SN74LS293AN 1.80
SN74LS22N .28	SN74LS590N .85	SN74LS155N 1.25	SN74LS197N 1.20	SN74LS295AN 2.20
SN74LS29N .29	SN74LS591N .89	SN74LS156N 1.25	SN74LS221N 1.25	SN74LS298N 2.20
SN74LS27N .35	SN74LS592N .80	SN74LS167N .80	SN74LS240N 2.20	SN74LS324N 1.80
SN74LS28N .35	SN74LS593N .86	SN74LS168N .89	SN74LS241N 1.90	SN74LS325N 2.55
SN74LS30N .25	SN74LS595AN 1.20	SN74LS169N 1.15	SN74LS242N 1.90	SN74LS326N 2.55
SN74LS32N .27	SN74LS596N 1.75	SN74LS161N 1.15	SN74LS243N 1.95	SN74LS327N 2.55
SN74LS33N .39	SN74LS607N .39	SN74LS162N 1.15	SN74LS244AN 2.10	SN74LS352N 1.35
SN74LS37N .28	SN74LS610N .38	SN74LS163N .90	SN74LS245N 2.80	SN74LS353N 1.60
SN74LS38N .29	SN74LS6112N .38	SN74LS164N 1.50	SN74LS247N 1.25	SN74LS365N .85

MEMORY AND SUPPORT CHIPS (Prices exclude VAT)

SUPPORT	1MS8011	5.00	4118	20.00	LINEARS	LM748CN-8	45	7915K	1.50	1M56011	5.00	
8212	2.20	81LS95	1.80	280P10	10.00	LM301AH	30	LM748CN	45	7912K	1.50	
8218	2.28	81LS96	1.85	280 CTC	10.00	LM301AN-8	30	LM1458H	77	7905	1.10	
8224	2.80	81LS97	1.80	280A P10	14.00	(Memo Digi)	30	LM1459M-8	48	7912	1.10	
8225	2.20	81LS98	1.80	280A CTC	14.00	LM308N	38	LM1480	05	7915	1.10	
8228	4.20	RAMS				LM309K	38	LM1490	05	7924	1.10	
8238	4.20	2101	2.32	1702		(T03)	1.45	LM1499AD	1.25	7905K	1.00	
8245	11.00	2102L-4	1.20	1702	6.00	LM311N	1.29	LM1495N-14	05	7912K	1.00	
8248	11.00	2111	2.32	520K	8.00	LM318N	2.25	LM3302N	05	7915K	1.50	
8251	6.00	8154	2.48	2516	8.00	LM323K	8.00	LM3401N	05	7924K	1.80	
8253	11.00	2112	2.48	2516	28.00	LM324AN	7.00	LM3402N	1.20	8085	12.95	
8255	6.00	5910	4.00	2718	22.00	LM335N	5.4	LM3900N	5.4	OIL SOCKETS		
8257	11.00	2114	6.50			LM555N	1.40	8014	14	8502	8.00	
8259	12.50	2102L-3	1.60			LM555N	7.6	TL081C*	05	16 DL	17	
8292	18.00	74C92D	11.00	745267	4.00	LM709CN	37	TL082CP	1.20	18 DL	24	
6820P	4.80	74C92D	11.00	745472	12.00	LM709CN	38	TL083CN	1.65	18 DL	24	
6821P	4.80	74C92D	11.00	745472	5.00	LM723CN	5.8	TL084CN	1.80	20 DL	27	
6850P	4.80	74C92D	11.00	745473	12.48	LM723CN	48	VOLT REGS	20 DL	28 DL	35	
6852P	5.60	4044	8.00	745474	12.48	LM733CN	1.30	7805	80	48 DL	50	
AY-5-2378	11.50	4045	8.15			LM733CN	1.30	7812	80	48 DL	50	
MC14411	12.00	4050	8.00	I/O		LM741CH-14	33	7815	80	100K	18 DL	
MS7108	12.43	4060	7.80	2513	7.50	LM741CH-5	25	7824	80	100K	3.00	
MS7160	10.00	4060	7.80	2513	10.95	LM747CN-14	78	7805K	1.50	250K	3.70	
MS7181	10.00	2107	7.80	95384	12.00	LM747CN	1.10	7812K	1.50	1MHZ	3.00	
		4118	8.00	14412							40 DL	86

TRITON DOCUMENTATION

Available separately as follows Prices include P&P
Triton manual. Detailed circuit description and constructional details and user documentation on level 4-1 monitor and basic £5.70
L4-1 Listing listing of 1k monitor 2k tly basic £4.20
L5-1 User documentation on level 5-1 firmware £1.20
L5-1 Listing listing of 1.5k monitor and 2-5k basic £5.50
L6-1 User documentation on 7k basic Interpreter £1.50
Motherboard, 8k Ram and 8k Eprom constructional details £5AE
User group newsletter subscription £4 per annum. Triton software send SAE for list of programs available for Triton.

HOME COMPUTING CATALOGUE

If you're in town, visit our showroom in Chapel Street, next to Edgware Road tube station. We have Tritons on display plus a comprehensive range of components and accessories, specifically for personal computer users. Books, mags, tapes, data, cables plus much more. Showroom open 6 days a week. (Half day Thurs., from 1.30).



NEW
A4 size catalogue filled with our latest products
40p +SAE
All prices exclude VAT

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates, ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. M273, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

AUTUMN SALE

24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit £12.00
CT1000KB with white box (56x131x71mm) £14.00
Ready Built £19.00

OPTO

LEDs	DL727 0.5" 2 digit Display	Square LED
0.1" Red	9p	Red, Size: 5x2.5
0.2" Red	9p	CA £1.00
0.2" Green	12p	Liquid Crystal Display 0.5" 3 1/2 digit
0.2" Yellow	12p	D134M 0.1" magnified 4 digit c.c. 7 segment display 14 dil
0.2" Red LEDs 25 at	Special offer 0.2" Red LEDs 25 for	£8.10 £1.25
		£4.50

BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black or white.

PB2 95x71x35mm 65p

PB3 115x95x37mm 70p



RESISTORS

1/4W 22ohm-10M Pack of 10 (one value) 10p
400mW 3.3V-30V 8p
1.3W 7.5-30V 15p
10 packs (mixed values) 80p

TRIACS



400V Plastic Case (Texas)

3A	49p	16A	90p
BA	82p	20A	185p
12A	70p	26A	190p
6A with trigger			80p
BA isolated tab			82p
Diac			18p

LIGHTING CONTROL KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark £8.00

TDE/K Extension kit for TD300K for 2-way switching etc. £1.50

TS300K - TOUCHSWITCH & DIMMER. Single touchplate, small knob controls brightness. £8.50

TS300K - ON/OFF TOUCHSWITCH. Two touchplates. £3.50

TSA300K - AUTOMATIC. Single touchplate. Time delay variable 2 secs to 3 1/2 mins. £3.50

LD300K - LIGHTDIMMER KIT £2.50

DIGITAL VOLT/METER/THERMOMETER KIT

Based on the ICL 7106. This Kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply. (PP3 battery) £17.50

INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	18p
AY-5-1224 Clock	£2.80
AY-5-1230 Clock/Timer	£3.80
AY-5-1232 Clock/Timer	£3.80
ICL7106 D.V.M. (L.C.D. Drive)	£7.00
ICM7217 Counter (L.C.D. Drive)	£7.90
TDA1024 Zero Voltage Switch	£1.20
LM3911 Thermometer	£1.00
LM3914 Dot/bar Driver	£2.60
MM57160 (stac) Timer	£5.95
S566B Touchdimmer	£2.80
S9263 Touchswitch	£4.85
ZN1034E Timer	£1.80

All ICs supplied with data and circuits Data Sheets only 5p

All components are brand new and to manufacturers specification. Add VAT at current rate to above prices plus 30p P&P. Mail Order - Callers welcome by appointment.

T.K. ELECTRONICS (PE) 106 Studley Grange Road, London W7 2LX Tel: 01 579 9794



FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation second to none for our catalogue - and for the service that backs it up. Experience both for yourself. Just send £1.25 with the coupon and a catalogue will come by return of post.

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.,
Dept. PE., 234-240 London Road, Mitcham, Surrey CR4 3HD

POST THIS COUPON with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME _____

ADDRESS _____



HOME RADIO (Components) LTD., Dept. PE 234-240 London Road, Mitcham, Surrey. CR4 3HD (Regn. No London 912966)

Top value test equipment from TANDY

LCD DIGITAL MULTIMETER.

Low-cost hand held digital multimeter with a full 3½ digit LCD display, 0.5% basic accuracy, auto polarity operation. 10 Mohm DC input impedance.

Reading to ± 1999.

Scales:
DC volts:
 1mV to 1000V
 (1% ± 1 digit accurate).
AC volts:
 1mV to 500V
 (1% ± 2 digits accurate).
DC current:
 1µA to 200mA
 (1% ± 1 digit accurate).
Resistance:
 10Ω to 20 MOhms
 (1.5% ± 1 digit accurate).
Power source:
 9V battery or AC
 with optional adaptor.
Size:
 155 x 75 x 30 mm.
 22-198




PRICE
53.19

AC/DC 8 MHz OSCILLOSCOPE

A new approved 8MHz version of last years' winner! The advance design features of this oscilloscope make it an absolute essential for industrial uses on production lines, in laboratories and schools. Ideal for radio and TV servicing, audio testing, etc.

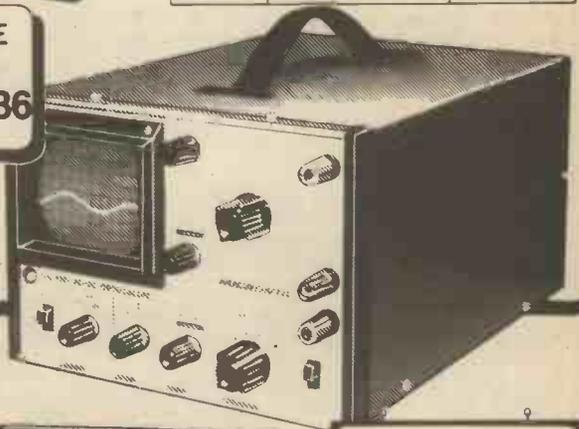Specifications:
 Horizontal axis: Deflection sensitivity better than 250mV/DIV. Vertical axis: Deflection sensitivity better than 10mV/DIV (1DIV - 6mm). Bandwidth: 0.8MHz. Input impedance: 1MOhm parallel capacitance 35pF. Time base: Sweep range: 10Hz - 100kHz (4 ranges). Synchronization: Internal (-) Size: 200 x 155 x 300 mm. Supply: 220/240/50Hz. 22-9501.




PRICE
137.36

LOW-COST LCD MULTIMETER

A portable, compact sized multimeter with a full 3½ digit LCD display. Auto polarity operation, low battery indicator. 10 MOhm Input impedance.

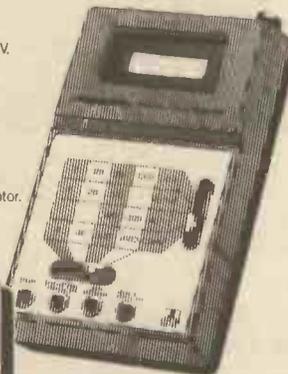Scales:
DC volts:
 2 - 20 - 200 - 1000V.
AC volts:
 200 - 500V.
DC current:
 2 - 20 - 200mA.
Resistance:
 2 - 20 - 200 - 2000 KOHM.
Power source:
 9V battery or AC adaptor.
Size:
 37 x 85 x 130 mm.
 22-197



PRICE
39.93

COMPONENTS AND PARTS

CAT. No.	DESCRIPTION	PRICE
276-032	LED	4 for 69p
276-033	LED	2 for 48p
276-034	LED	2 for 59p
276-142	Infra-Red Emitter Detector Pair	£1.37
277-1003	12V DC Automotive Digital Clock Module	£17.52
276-9110	6 pin edge connector for 277-1003	40p
276-1373	Power Transistor Mounting Hardware	50p
276-1363	TO-220 Heat Sink	60p
276-1364	TO-3 Heat Sink	81p

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80.

TANDY



TANDY
 DEALER

Most items also available at Tandy Dealers. Look for this sign in your area



Access, Barclaycard and Trustcard welcome.

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.

MORE-MORE-MORE

EXACTLY a year ago we published an editorial similar to this one. The ways of the world are dictating the position and it is sad to realise that these editorials are probably going to be recurring at even shorter intervals in the future.

What is it all about? We are asking you to spend another 5p on P.E. next month—doesn't sound much does it and perhaps it won't worry you, but our view is that in these inflationary days every extra 5p must be fully considered. We have not put the price up just for the hell of it, we need you and we want you to keep buying P.E.—that's why we take a lot of care to try to bring you the best mag. on the market—and that we believe, is why we have a total sales figure that is higher than any other British hobby electronics magazine and that is an unqualified fact.

We have been under pressure on the price front for some time as the cost of paper in particular has risen dramatically yet again. Our costs have now risen by just under 20 per cent and we must reluctantly pass some of this on.

At this stage we have increased the price by 10 per cent but just how long we can hold it remains to be seen. If we use the standard argument 10 per cent in a year is less than the rate of inflation, but of course it is another 5p and adds to all the others, as we know.

Since our paper is shipped from Scandinavia and our issues are distributed by road, the cost of oil plays an important part and, with a forecast of £2 a gallon for petrol next year, we do not see P.E. staying at 55p. All we can say is that we will do our best.

VALUE

We hope we can give you good value for money—this issue is fatter than usual and carries a free gift. By designing and making these tools ourselves in very large quantities (108,000 in fact) we can get the price right down and give you a useful tool that is worth about 60p—that's what an equivalent would cost you.

Next month we will also be presenting a Marshall's catalogue free with each issue sold in Britain and that again is worth 50p. The catalogue is larger than previous ones from Marshall's,

carries a full colour cover, shows reductions in price on almost all their top 500 lines and contains some prepaid order forms—at least the price of some things continues to go down!

Marshall's are also the first British component suppliers to be offering a budget account available through their four retail shops and making use of a Marshall's credit card. This card can also be used in any other store that is a member of RETRA. Quite an innovation in our market and it will certainly help spread the cost of one of our larger projects or of test gear etc.

What else are we planning? Well we have some excellent projects in the pipeline but you will have to wait and see just what they are, we are also working on special offers which should save you some of that cash we have been discussing. One exclusive offer on an incredible new Seiko watch should produce a saving of about £45 and, with luck, we will bring you the offer in time for Christmas! That sort of saving should buy P.E. for a good few years on its own.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland PROJECTS EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

Editorial Offices:

Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

ADVERTISEMENT MANAGER

SECRETARY
CLASSIFIED MANAGER

D. W. B. Tilleard } 01-261 6676
Christine Pocknell }
Colin Brown 01-261 5762

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £3.75 each to UK or overseas addresses, including postage and packing, and VAT where appropriate.

Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Cheques and postal orders should be made payable to IPC Magazines Limited.

Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by
Alan Turpin

RING THEIR B.E.L.

Well worth an S.A.E. is the catalogue of Barrie Electronics Ltd. (B.E.L.), particularly for reference to their range of transformers, the nine pages of which cover the following categories:—Auto, Battery Charger, Cased Auto, Equipment, Filament, Ignition and Inverter, Miniature, New Range, Output, Safety Isolating, Valve, 12V, 24V, 30V, 50V, 60V, Specials.

Barrie Electronics Ltd., 3 The Minories, London EC3N 1BJ (01-488 3316).

STOCK O' SCHOTTKY

A new company holding substantial stocks of those increasingly hard to find LS devices has just launched itself on the hobbyist market. Romane Electronics are based in Sale, Cheshire and are advertising a good range of LS devices at very competitive prices.

They say that customer orders will be dealt with in strict rotation so get in quick or the bigger buyers may be topping up supplies from this source.

Romane Electronics, 64 Newlyn Drive, Sale, Cheshire M33 3LE (061-962 2606).

CODESPEED CATALOGUE

Most of their components are full specification devices but Codespeed also offer untested packs in varying degrees of guarantee of satisfaction. So if you are a bit of a gambler you could chance your shirt in the following way; "4/5 digit displays in manufacturer's support frames, header and tie bars to be cut, four for a £1"; "n.p.n. transistors, designated F107, spec. unknown, 10 for 70p"; "Op. amps., 20 assorted, £1"; "Factory reject calculators, £2.50 each"; "Two min. relays, 25p"; "15 logic i.c.s £1"; "30 mixed i.c.s £1".

S.A.E. to Codespeed Electronics, Box 23 34 Seaford Road, Copnor, Portsmouth PO3 5BJ.

and
David Shortland

WHEN QUADS ARE WELCOME

Siliconix has given birth to a quad VMOS power FET device in a standard 14 lead d.i.l. package.

The VQ1000 contains four independently accessible high speed VMOS FETs each with a maximum switching capability of 60V and 0.5A continuous or 1A pulsed. For higher power applications the FETs can be externally paralleled to load share.



Switching times are typically as low as 5ns and uses suggested are TTL/CMOS logic to high power interfacing, i.e.d. digit strobe drivers, high speed line drivers, stepping motors, peripheral controls, solenoids, etc. Switching capabilities comparable with bipolar transistors can be achieved without the many disadvantages such as secondary breakdown, thermal runaway, low gain, low speed due to minority carriers, and current hogging when used in parallel.

Each FET is Zener protected and overall power dissipation for the plastic or ceramic package is limited to 1.75W at 25°C.

Siliconix Ltd., Morriston, Swansea SA6 6NE (0792 74681).

BIO CLOCK

Much has been said and published on the usefulness and results of biorhythms; we are told that Japanese insurance companies even advise clients not to drive on certain days because they are critical "switching" days in the biorhythm curves. Whether you take notice of biorhythms or not, it is quite interesting to check results against the predictions for each day—a bit like reading your horoscope! We will refrain from passing any opinions on how much reliance anyone should place on biorhythms, what interests us is a biorhythm clock that is now available.




The clock provides three readouts which are colour coded to correspond to a graph showing the rhythm curves for physical, emotional and intellectual capacities. It is thus easy to check where on each curve an individual lies each day—the clock can only be set to one birth date so is normally only usable by one person. Initial setting of the clock involves a calculation of the days one has lived for and divisions of this total to set each readout. This is however a once only operation, provided the unit is not unplugged—or until the next power cut!

In use we found the displays were a little dim but since it is only normal to read the clock once a day this is hardly a problem.

The clock is available in kit form from Maclin-Zand, Unit 10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP (01-837 1165).

30 METRE AUTO-SWITCH

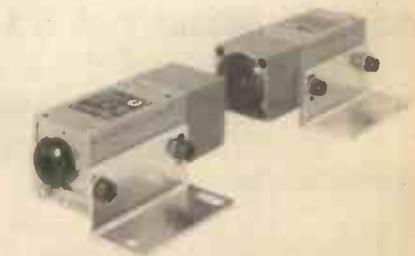This photoelectric switch has an operating range of 30 metres. The infra red i.e.d. light source ensures long operating life and high immunity to ambient light. Transmitter and receiver are compact units measuring only 90.5 x 40 x 40mm.



Available in operating voltages from 12V d.c. with a voltage output, or 24V d.c. with a power output capable of switching up to 200mA. 110/240V a.c. operation is also available.

IMO Precision Controls Ltd., 349 Edgware Road, London W2 1BS (01-723 2231).

4½ DIGIT L.E.D. METERS

Lascar Electronics have introduced two new 4½ digit panel meters priced from under £40. They are fitted with high efficiency 0-43in red l.e.d. displays and are available with f.s.d.s of 2V or 200mV.



Accuracy is guaranteed to ± 1 count over the entire range, giving a resolution of up to $10\mu\text{V}$. Auto-polarity, auto-zero, b.c.d. outputs, digital hold and programmable decimal points are standard features.

Six auxiliary inputs/outputs are available for interfacing to UARTS, microprocessors or other complex circuitry.


Also available is a panel mounting bezel with a red circularly polarised filter. A mains power supply option is also offered.

Lascar Electronics Ltd., Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH (0268 727383).

SOLAR CELL

Ferranti have developed a silicon solar cell specifically for educational use, but maybe hobbyists will find a use for it too.

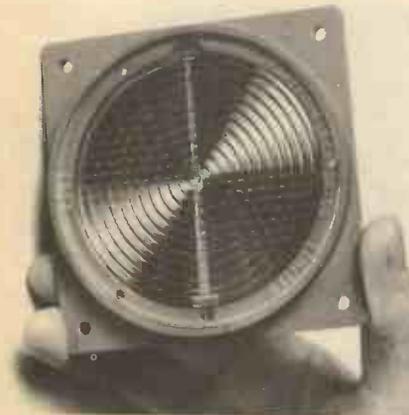The cell, designated the ESC3 series, is 3in in diameter and is capable of producing 0.9A at 0.5V under good sunlight conditions. Physical protection is provided by a tough moulded case and by a Fresnel lens which also acts as a light collector.



Power take off is from metal pins on the rear of the case. Accidental short circuiting of the output will not damage the cell, and any number of cells can be arranged in series/parallel combinations to provide increased output values.


How many of these would you need to bolt on your bonnet to power all the car instruments in our new series?

Ferranti Electronics Limited, Fields New Road, Chadderton, Oldham, Lancs OL9 8NP (061-624 0515).

RCA SINGLES

Not to be left out of the single board race RCA Solid State has introduced a family of single board microcomputer systems based on the CDP1802 COSMAC microprocessor. The family consists of two single board microcomputers with differing memory capacities, a range of add-on memory boards and expansion modules, 5-card and 25-card chassis/backplane units, a milliwatt power supply, and two prototyping systems. All Microboard modules are compatible with existing RCA COSMAC Development Systems. Each module measures 4.5 x 7.5in. (114 x 191mm), and any module works in any location on the backplane. Software development can commence as soon as the modules are plugged in.

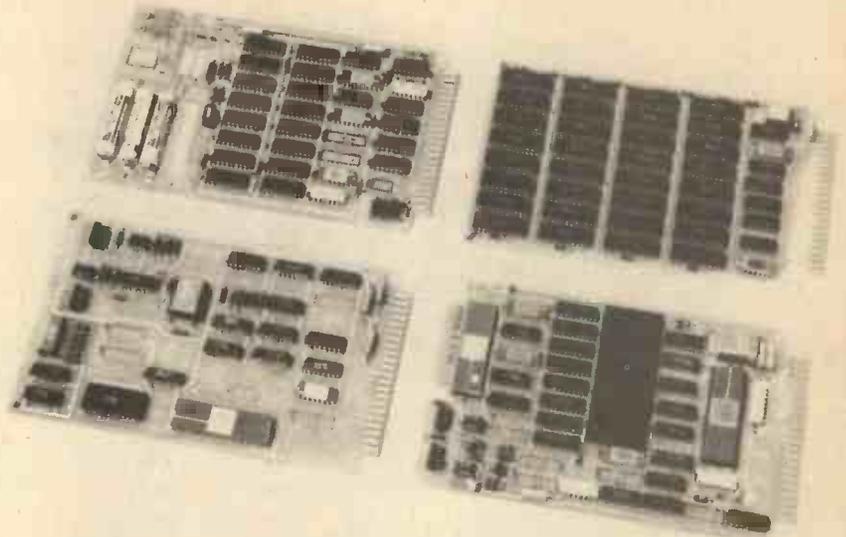The use of CMOS means that power consumption is measured in milliwatts, and a complete system can be powered from nickel-cadmium batteries. Alternatively, the ability of the CMOS circuitry to operate over a wide voltage range allows low-cost power supplies with extended regulation limits to be used. Also there is excellent immunity to electrical noise.



Each of the computers contains a CDP1802 microprocessor, crystal-controlled clock, read/write memory, parallel input/output ports, serial communications interface, 'power-on' reset, expansion interface, and sockets for user-selected ROMs. The two computers are designated CDP18S601 (4Kbyte RAM; sockets for 4/8Kbyte ROM/PROM) and CDP18S603 (1Kbyte RAM; sockets for 4/8Kbyte ROM/PROM).

Memory modules include 4Kbyte, 8Kbyte and 16Kbyte RAM boards, 4Kbyte and 8Kbyte RAM boards with battery backup, and an 8/16Kbyte ROM/PROM board. Other expansion modules available on Microboards are a UART interface, a combination memory-input/output module, digital/analogue and analogue/digital convertors, and a control and display module.

The two Microboard prototyping systems available from RCA each contain a Microboard computer together with a control/display module, a 5-card chassis in a protective case, a power convertor, a breadboard for prototyping, cables and connectors, utility software, and technical literature.

RCA Solid State-Europe, Sunbury-on-Thames, Middlesex TW16 7HW (093-27 85511).



MAINS STABILISERS

Of particular interest to our overseas readers are these mains voltage stabilisers. Regulation of two per cent is achieved on the ferro resonant range; VA ratings, 175, 250, 500, 1000 or 2000. The other models which make up the full range of 21 are thyristor controlled buck and boost transformers. Also available are three models of cutout, one of which is an OEM version. Trade enquiries are welcomed world wide.

Galatrek, Scotland Street, Llanrwst, Gwynedd LL26 0A1, North Wales, Great Britain. Telephone (0492 640311). Telex 617114.

FUNCTION GENERATOR

This function generator can produce square, triangular or sine waves over a frequency range of 1Hz–100kHz, and incorporates an electronic sweep facility which gives a sweep range of up to 100 : 1 from an a.c. signal.

The instrument has five overlapping frequency ranges with pushbutton selection and a vernier frequency dial to give an accuracy within ± 5 per cent dial setting.

In addition to the normal high and low-level outputs for sine, triangular and square waveforms, a separate TTL square-wave output is provided which will drive ten TTL loads with rise and fall times of less than 25ns.

Sine, square and triangular waveform outputs are variable over a range of more than 40dB. The high-level output is rated at 0.1–10V (peak-to-peak) into an open circuit, and 0.005–5V (peak-to-peak) into a 600 Ω load. A separate low-level output, 40dB down from the high-level output, is rated at 1–100mV into an open circuit and 0.5–50mV into a 600 Ω load.



The variable d.c. offset amplitude control, once set, holds the output signal to within ± 0.5 dB over the entire frequency range.

Distortion on the sinusoidal waveform is less than two per cent, and linearity error of the triangular waveform is within one per cent. The standard square wave has rise and fall times of less than 100ns and a time symmetry error within ± 2 per cent.

The voltage-controlled sweep oscillator can be zero-referenced from any frequency setting, and the sweep input can be within the range ± 10 V.

Price of the Model 2001 is £75 plus VAT.

Continental Specialties Corporation, Shire Hill Ind. Est., Saffron Walden, Essex CB11 3AQ (0799 23101).

HAND HELD DMM

A new $3\frac{1}{2}$ digit multimeter has been introduced by Lascar Electronics. It is claimed to combine the accuracy of a digital instrument with the low cost of an analogue type.

The LMM-200 has a basic accuracy of 0.5 per cent, a 200 hour battery life and 0.5in. l.c.d. read-out. The display also indicates when the battery has only 20 hours life left.



The instrument has 15 different ranges and can resolve voltage to 0.1mV, current to 0.1 μ A and resistance to 0.1 Ω . Auto-polarity and auto-zero are standard. Inputs are via 4mm terminals and are protected against overloads and transients.

Housed in a black ABS case, the instrument is £34.95 and is supplied with a battery, instructions for use and a 2-year warranty. Suitable test leads are also available.

Lascar Electronics Ltd., Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH (0268 727383).



CHICAGO CONSUMER ELECTRONICS SHOW

VERA LIVES

Do you remember VERA, the BBC's Video Electronic Recording Apparatus? VERA's passion was the rapid consumption of yards of magnetic tape to record her signals. Tape pass speeds for video and audio dropped dramatically after VERA's debut and she went into early retirement.

It appears now that VERA's style of working may be the new vogue, for Toshiba were showing a cartridge recorder with a tape speed



This Harmonizer, for recording studios, can change the pitch of a signal by three octaves (one up, two down); has two outputs, each with 400ms of delay; a frequency response of 15kHz and a signal to noise ratio of 96dB. It is also capable of flanging, repeat, random delay, and reverse effect. Price is \$2,400 Eventide Clockworks Inc., 265 West 54th Street, New York, N.Y. 10019. Telephone (212-581 9290).

of six metres per second. The tape is in a loop of 100 metres, and 220 longitudinal tracks store the recording. It takes only 17 seconds to make one circuit of the loop but 17 x 220 gives just over one hour of recording time. Seventeen seconds is also the access time to any part of the loop.

The half-inch wide tape, on a non-revolving fixed reel cartridge, is pulled from the centre of the reel, and driven by a direct drive capstan

motor near the centre of the reel. The head, near the capstan, moves vertically across the 220 tracking positions, powered by a stepping motor.

Apart from domestic TV recording Toshiba are expecting this system to be valuable where rapid random access to digital information is required (20ms to access track in use, 4.4s to range all tracks). Just the device to bolt on to a home computer. The simplified mechanism




eliminates about two thirds of the mechanical parts used in other video recording systems. The prototype LVR (Longitudinal Video Recorder) shown at Chicago was NTSC compatible, to EIA standard. Weight of the unit is a readily portable 17-6lbs.

Consumer Electronics Division, Toshiba America Inc., 280 Park Avenue, New York, N.Y. 10017.

HAND HELD PRINTER

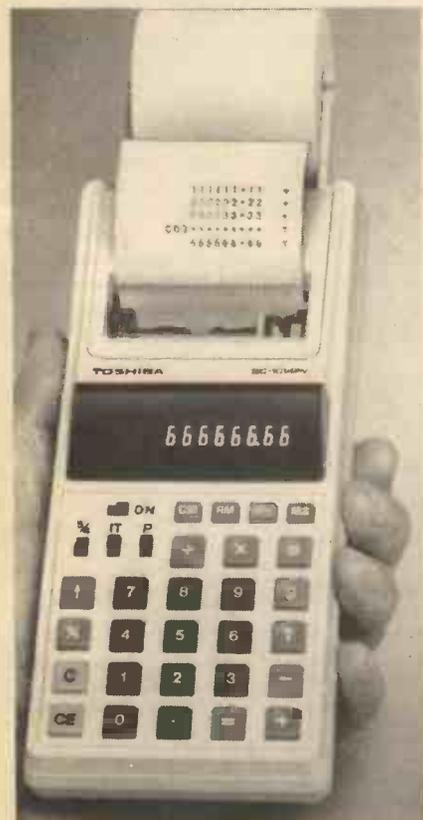Toshiba have brought out a 10 digit cordless printing calculator with: memory, per cent, constant, and item counter. The model shown has a Digitron display and there is also an l.c.d. version with floating decimal.



The machines print at two lines per second. The model shown has a suggested price of \$90 which includes a Ni Cad battery and an a.c. adapter. The l.c.d. version (\$100) has a Ni Cad pack as an optional extra.

Business Equipment Division, Toshiba America Inc., 280 Park Avenue, New York, N.Y. 10017.

WHISTLE STOP

The Whistle Switch is a sonic receiver which plugs into a mains outlet and can switch on or off any mains device up to 300W. It is activated at up to 50ft by a hand held remote control which emits a barely audible whistle.

If you can't get in to Bloomingdale's or Macy's with your \$25 there was a project in the June issue of PE which had a similar capability although not the same range.




Universal Controls Corporation, Suite 868, Kirkeby Center, 10889 Wilshire Boulevard, Los Angeles, California 90024. Telephone (213 477 4509).

MORE HEADROOM

Dolby have developed and are making available their HX (Headroom Extension) system for incorporation in their present B-type systems.

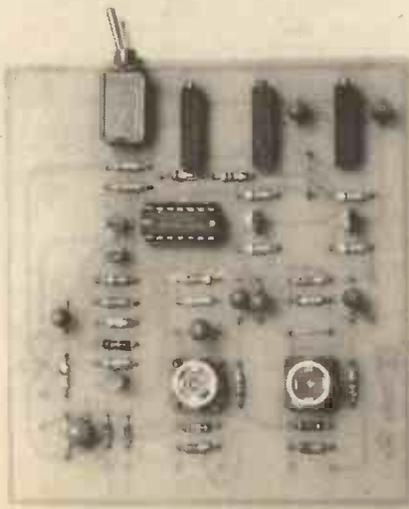The HX module (prototype shown) "automatically and continuously varies the record bias level and record equalisation to optimise both, in response to changes in the recorded level and high-frequency content". It permits recording at 10kHz and above at a level 10 or more dB higher than is currently possible, while at low and middle frequencies perfor-



mance is optimised for minimal distortion, modulation noise and drop-out effects. The HX system works with any tape formulation (for which a recorder is nominally set up).

The technology is available to all Dolby licencees for inclusion in cassette recorders with Dolby B-type noise reduction, without further royalty or licensing charges. The parts required for the new system add about a third to the manufacturing cost of the Dolby circuits within a recorder.

Dolby Laboratories, 731 Sansome Street, San Francisco, CA 94111. Telephone (415-392 0300); Telex 34409.

Dolby Laboratories, 346 Clapham Road, London SW9 9AP. Telephone (01-720) 1111. Telex 919109.

MAGIC MIKE

No not our editor, although he does seem to have been on the button as far as CB goes (see August editorial and recent reports of Home Office announcements in the daily press). Magic Mike is, according to the manufacturers, the first cordless CB mike. The mike can be installed without any modification to the existing CB rig, and is powered by a nine volt battery. Effective range is three metres, allowing back-seat CB-ing.

The system operates on VHF and receiver and transmitter are certified in compliance with FCC rules and regulations.

Autoalert Inc., 4488 Spring Valley Road, Suite #102, Dallas, Texas, 75240. Telephone (214-233 0187).

PET ANALYSER


If you have a PET computer and a spare \$600 you can have yourself a Real Time Third Octave Spectrum Analyser. The analyser divides the audio spectrum from 20Hz to 20kHz into 31 third-octave bands and displays them on the PET screen.



The manufacturers suggest that the plug in board can be used for measuring sound and noise levels, for optimising the equalisation of a hi-fi or public address system, for checking the frequency response of audio components, and for speech and sound pattern recognition.

Of course the PET can be used to store, recall and compare data. Programs to access the analyser are written in BASIC and three are provided with the unit.

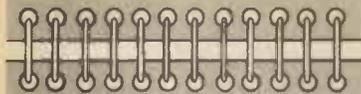Eventide Clockworks Inc., 265 West 54th Street, New York, N.Y. 10019. Telephone (212-581 9290).



INDUSTRY NOTEBOOK

By Nexus



Energy

Recently the popular rave topic has been chips. Every aspect has been talked out—technical, industrial, economic and social consequences. It went on for months and seemed like years. But at least the prices of chips were expected to fall and fall.

Now the rave topic is something which keeps going up in price—energy. And as with doom-laden prophecies on the chip, so they say, we are doomed by the energy crisis.

You might imagine there was a world shortage. Not so. Our earth came from the sun. And so does all its energy, whether ripening the corn today or stored up as a fossil fuel from way back. And the sun is still out there shining away and our earth is still collecting energy in the same old way and, very slowly, a few new ones too.

The crisis, if there is one, is not a shortage of total energy available but, with oil particularly, its price structure and geographical distribution. It's amazing that the Middle East, with its distinguished history in the mathematical sciences, took so long to work out the simple economic equation of supply and demand. Equally amazing that an area closely associated with hashish (an Arabic word) and its consequences, should so tardily recognise that the industrial West was so completely hooked on oil-guzzling that withdrawal from the drug would be unthinkable. So, with the customers hooked and the aid of a revolution in Iran, not to mention a price-fixing ring (OPEC), the going rate is what the market will stand.

Good and Bad News

Although bad news for us all in general, the crisis is good news for the electronics industry. British companies have prospered well over the North Sea exploration and production phases of development and in other oil-producing areas as well. Marconi, for example, has just picked up yet another troposcatter contract, this time worth

£750,000, for communications with Shell's Fulmar platform, a link 280km from the Post Office base station at Fraserburgh. But as well as big business in communications, companies have been supplying electronic survey and navigational equipment, instrumentation and industrial control gear.

Now even more business is in prospect because many of the less promising oil fields not worth touching at \$10 a barrel are beginning to look attractive at a going rate of over \$20 a barrel. More platforms, more drilling, more pipelines, more and more electronics.

But the industry will also score from conservation and alternative energy. In conservation, microprocessor control will 'fine-tune' temperature and other systems far better than old fashioned thermostats. Gains in efficiency measured in single percentage points, even one per cent, are significant for big energy-intensive enterprises. Self-adaptive energy saving systems, mini or microcomputer based will be big business in the 80s.

For alternative energy sources there is a choice of solar, wind, falling water, wave and tidal power, biomass (organic matter of biological origin) and the way-out prospect of tapping the enormous heat concentrations in tropical oceans. The trouble with most of these is that they are intermittent and the collecting mechanism is seldom conveniently situated near the point of use, at least for large generation.

Nonetheless, all the techniques are being vigorously pursued, with thermal technologies, particularly direct and indirect solar energy, as favourites. In the direct form, in which solar heat collectors are attached to rooftops, electronics will be there for system management.

Solar Cells

In the indirect form, using photovoltaics typified by the silicon solar cell, electricity is generated by sunlight falling on a panel of cells. The mass market here is for the cells themselves and there is much development work going on to get production costs down to a level where systems are competitive in price with conventional power from a national grid.

In looking at systems, costs have to be measured which include the cost of delivering power to the point of use. Thus, although initially expensive, a solar cell array on the top of a mountain and used to power a navigational beacon can already score over a conventional supply involving miles of cable and supports to get the power there. In fact there are hundreds, if not thousands, of such installations already in use. Intermittency of output is not a problem when the solar energy is used to charge a battery. A panel four feet square will, with present technology, deliver 8.5A at 28V.

The attack on costs of solar cells is on two fronts. One is to reduce manufacturing costs of high efficiency devices using expensive materials, the other to make present low efficiency devices using cheap materials more efficient.

In the first case, according to a recent report from RCA, attempts are being made

to cut costs on crystal growth, slicing and encapsulation for high performance devices. In the second, completely new materials are being studied, notably amorphous silicon, which has electrical and optical properties quite different from crystalline silicon. It has better sunlight collecting properties and can be deposited readily with only a little material as thin film on cheap substrates. The only snag is that conversion efficiency is, at present only 6 per cent compared with a minimum target of 10 per cent, preferably 15 per cent, to make amorphous silicon competitive. The twin attack could result in the two technologies drawing together in cost per watt output which is the decisive factor.

The immediate attraction of the solar cell is that photovoltaics is a technology already established, in contrast, for example, to harnessing wave or tide power which is still experimental. And semiconductor manufacturers are already conversant with the manufacturing processes. For low power local use, the solar cell will become big business in the next decade.

Wind Power

The other local energy technology about which we know quite a lot is wind power, and since cheap rural electricity finished off the windmill we have learnt a lot more about aerodynamic design. Before cheap electrical power was piped nation-wide, the United States had some six million windmills, nearly all used for pumping water. The new name is wind energy converters and it is a fair guess that we shall see a lot more installed in the year ahead. Conversion efficiency is high, 35 per cent has been achieved, and examples delivering 200kW of power are already operating. Although still an intermittent source, depending on wind force, the wind energy converter has the advantage that it will keep turning during the hours of darkness. A belt-and-braces solution would be a hybrid wind and solar cell structure when one or other, sometimes both, would be working.

Large wind energy converters capable of delivering two megawatts are being built in the United States. These will be used for feeding into the big supply networks. At local level, small on-site units which could be mass produced will deliver a kilowatt or so.

It only needs another couple of hikes in world oil prices to make these cranky ideas look completely realistic and the obvious thing to do. The big electricity suppliers don't like the prospect of having their customers switching to home-brew power, but the anti-pollution brigade will love it because sun power and wind power produce no effluent. Nonetheless it seems quite certain that although the pattern might change we shall still need and have huge generating stations, oil fired, coal fired and nuclear, for many years to come.

Moreover, we shall still use petrol in cars. Petrol is stored energy in portable form and there is no comparable storage medium—83 gm of petrol contains a kilowatt hour of energy compared with 55kg weight of lead-acid batteries to store the same amount.

Semiconductor UPDATE...

FEATURING MM 74C911/2/7 ICL 7611

R.W. Coles

DISPLAY COMBO

The cheapest way to display numeric data is to use seven segment l.e.d.s in a multiplexed drive scheme. Static l.e.d. drive circuits require a decoder for each digit, and that gets expensive when more than three or four digits are required. In a multiplexed scheme only one display digit is turned on at any given instant, but the scanning, or multiplexing, rate is made sufficiently high that to the human eye, all display digits appear to be "on" simultaneously.

In a multiplexed display scheme only one decoder is required for the whole system, because it too is multiplexed with its input, and therefore output, data changing in synchronism with the digit strobes which are used to enable each l.e.d. in turn.

Most familiar systems such as watches, clocks, calculators and digital multimeters, employ display multiplexing because it is more economic and because it uses fewer pins on an LSI chip (seven segment lines and N digit strobes as compared with 7N lines for a static scheme), but for homebrew systems a multiplexed display may seem a bit of a problem at first.

You'll need a decoder of course, something like the 7447 would do nicely, and you can use TTL for most of the other bits and pieces too. These include a multiplex clock oscillator, a digit counter and decoder or a shift register, and a method for multiplexing the data into the seven segment decoder, such as a recirculating shift register or some tri-state gates if that data is already latched in parallel.

To drive the digit lines you may need some discrete transistors, because in a multiplexed system the display currents are N times greater for the same effective brightness as can be obtained with an N digit static system.

THINK TWICE

Hmmm! enough to make you think twice about the "economies" of multiplexing, isn't it? Well, not to worry, because National have spotted the problem and built up some very nifty multiplexed display subsystems and put the whole mess on to a single CMOS chip.

The new devices are called display controllers, and there's one to suit every system. Typical of the family is the **MM 74C912**, which is intended for use in eight segment (that's seven plus a decimal point), six digit decimal displays. You give it your data in parallel four bit b.c.d. form, by addressing one of the six latch registers in turn via the three address lines and the chip enable. It does all the rest.

The on chip oscillator drives the digit multiplexer which generates one of six digit strobes while gating the correct latch contents to the decoder (actually at 16 x 7 ROM). The ROM outputs are buffered to drive the segment lines directly, at least for the smaller l.e.d.s.

Another family member, the **74C917**, does all that the 74C912 does, but its decoder ROM is programmed to do the full hexadecimal character set of 0-9 and A-F, instead of just 0-9. The **74C911** does away with the decoder altogether but allows you to store data a byte at a time. This could

be data that's already been decoded, by a microprocessor say, or it could be followed by an external decoder for a full alphanumeric dot matrix or "Union-Jack" type display.

The 74C911 drives four digits, but devices can be used together for more digits or a wider word. These devices are especially useful when used to relieve a microprocessor of the display driving chore, but no doubt they will find many applications in non-micro systems, where their single five volt supply and compact 28 pin packages will make them excellent replacements for steam TTL!

MICRO-AMPS

Last month I dealt with the amazing CAZ-AMPS from Intersil, but those CMOS wizards have tricks up their sleeves, like the incredible **ICL 7611** family for example.

If you have ever balked at the prospect of having to provide plus and minus 15 volt supplies for a solitary 741 op-amp, then the ICL 7611 devices could be for you, because they will run from plus and minus half a volt! You don't have to go that far though. This super-low-power operational amplifier family will run at up to plus and minus eight volts, or you can use a single supply like a 1½ volt pen cell or a five volt logic supply.


Don't worry about running the pen-cell flat either. Many of the family have a current programming pin which allows you to set quiescent bias current to between 10 microamps and one milliamp. Even at one milliamp that pen cell will last a long time, and at that current you get almost 1.5MHz of bandwidth! Regardless of bias current, you can expect 100dBs of open loop gain, 90dBs of CMRR, an input offset voltage of three millivolts and a one pico amp input bias current.

You can have these devices in all sorts of shapes and sizes—singles, duals, quads—internally or externally compensated, and some with unique features like plus and minus 200 volt input protection. And all at very low prices (less than £1.00 for a single device).

You can now gain the benefits of operational amplifier circuitry in just about any kind of battery powered gadget you care to think of; no more messing with discrete transistors or converted CMOS logic gates!

National Semiconductor, 19 Goldington Road, Bedford MK40 3LF. (0234 211262)

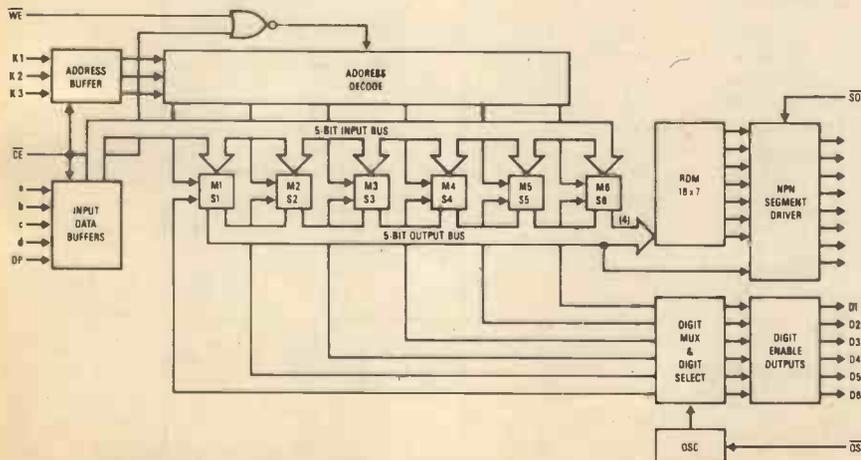Intersil Inc., 8 Tessa Road, Richfield Trad. Est., Reading RG1 8NS. (0734 595011)



Internal circuitry of National MM 74C917

SOLID STATE

No.1 • Battery Voltage Indicator

THE shape of vehicle instrument displays will undergo radical change in the next decade, or so we are constantly assured. A recent *PE* article gave an insight into some of the changes we can expect to see on the dashboard. At present, however, most of these predictions belong to the realms of publicity for such dreams as the Aston Martin Lagonda; the province of the lucky few! The real question for the amateur constructor is how to take advantage of the technological revolution in vehicle instrumentation without indulging in the seemingly obligatory multi-million pound development programme.

This is the first in a series of articles which will describe a range of solid state instruments for motor vehicle applications which involve no moving parts, make use of readily available inexpensive components, and which are easily added to any vehicle with a 12 volt electrical system. The instruments may alternatively be constructed as self-contained test units.

VEHICLE INSTRUMENTATION DESIGN

The purpose of vehicle instrumentation is to provide the driver with an indication of the current state of the vehicle in a form which is easily and quickly understood. In practice, this usually means some form of visual indication.

To make use of the solid state display requires that the information to be displayed is available as an electrical signal. In many cases, therefore, the quantity to be displayed must first be converted to an electrical signal, and often further processed, before it is suitable for display. Fig. 1 shows the overall block schematic of such an instrument. In some cases, blocks 1 and/or 2 may not be required owing to the nature of the variable being measured. The requirements of a solid state vehicle instrument are given below.

- (1) Transducer to convert from the physical variable (e.g. temperature) to an electrical signal (e.g. voltage).
- (2) Signal processing unit to convert the output of the transducer (which could be a low-level pulsating voltage) into a suitable level.
- (3) Driver and reference level to translate the processed level into appropriate commands to the display.
- (4) Display unit to provide a physical display of the measured physical variable.

The design should give good rejection to supply fluctuations, which are of a considerable level in motor vehicles.


INSTRUMENT DISPLAYS

Over the last decade, the seven-segment display device in its various forms has become almost synonymous with the advances in measurement technology. Such numeric displays are well suited to the many applications where a precise indication of the measured parameter is required.

But there are many situations where such precision is unnecessary, even confusing. This is especially true in the situation where a number attached to a particular measurement has no immediate significance to the user. For example, the number "35" in the FUEL window of the dashboard requires an appreciation that the units are litres, and the user must perform some mental arithmetic in order to learn that the tank is, in fact, about one-quarter full. Rather better assimilation would result from a display which presents information to the user on a related proportional scale. Such a trend is currently apparent in the move towards electronic watches with analogue (dial and pointers) display, and away from the original digital display, despite the unquestioned 'precision' of the 6 digits.

One approach to the problem of a low-cost analogue type solid state display is to make use of a linear array of light emitting diodes. The diodes may be arranged in a straight line or in a circular arc, to suit the particular application. A single l.e.d. may be lit at one time to give the effect of a moving pointer, or the l.e.d.s may be accumulatively illuminated to give a bar graph display. In the "Dot" mode, the individual l.e.d.s may be coloured appropriately to represent safe and unsafe regions of operation according to the variable being measured.

Fig. 1. Flow diagram of a vehicle instrument display

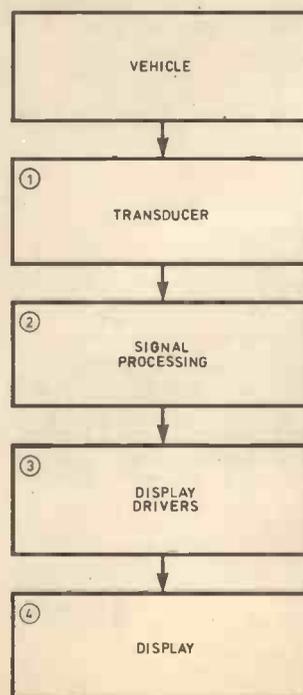


EA37

INSTRUMENTS

Michael Tooley B.A.

David Whitfield B.A. M.Sc.

Fig. 2. LM3914 block diagram

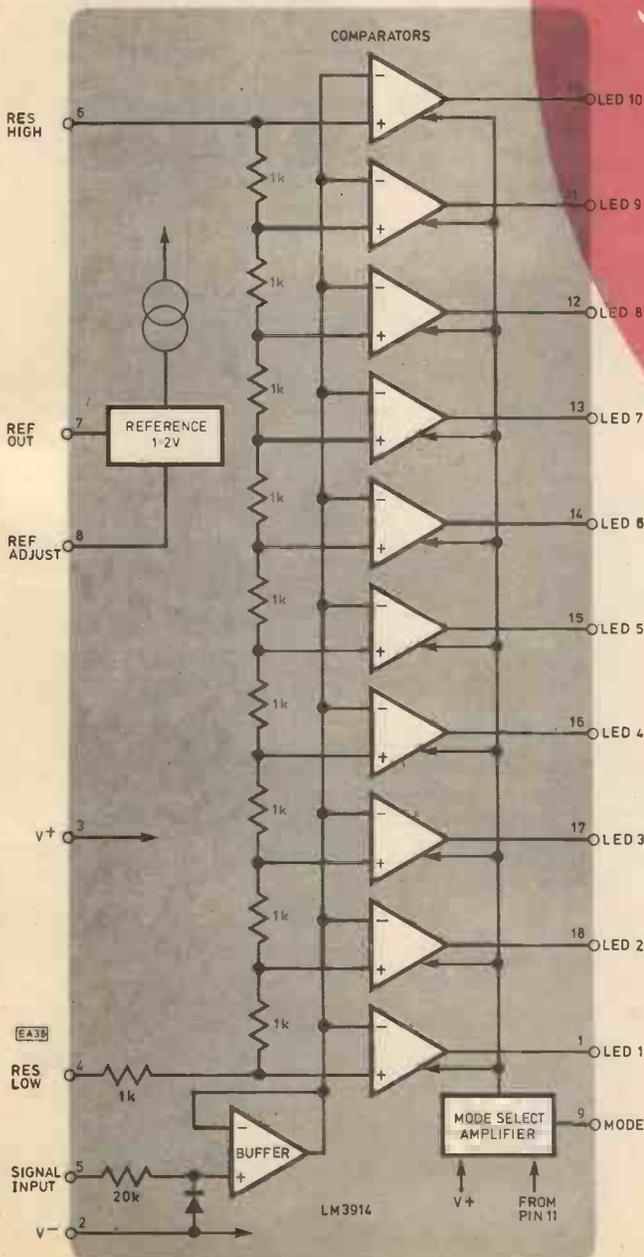

A series of articles
on vehicle projects
using the LM3914

DISPLAY MODULE

There is now a wide range of integrated circuits designed specifically for use in automotive applications. One device in particular is the *National Semiconductor* LM3914 Dot/Bar Display Driver. The LM3914 is a monolithic i.c. that senses analogue voltage levels and drives 10 l.e.d.s, providing a linear analogue display. A single pin changes the display from moving dot to a bar graph. Current drive to the l.e.d.s is regulated and programmable, eliminating the need for current-determining resistors. The circuit, shown in outline in Fig. 2, contains its own adjustable reference, and accurate 10-step voltage divider. The low-bias-current input buffer accepts signals down to ground, or V^- , yet requires no protection against inputs of 35V above or below ground. The buffer drives 10 individual comparators referenced to the precision divider, allowing the indication non-linearity to be held typically between one and two per cent. The flexible design of the LM3914 allows many devices to be "chained" to form displays of 20 to over 100 segments. Both ends of the divider chain are externally accessible so that two drivers may be used in a centre-zero meter. When in Dot mode, there is a small amount of "fade" (about 1mV) between adjacent segments to ensure that at no time will *all* l.e.d.s be off.

The use of the LM3914 allows a basic circuit building block to be designed which represents units 3 and 4 in Fig. 1, and which may be used in the whole range of instruments to be described in this series of articles. The block diagram in Fig. 3 shows the features of the basic 10-bar display module. Full-scale indication is achieved with an input of +5 volts, and the display may be set to either Dot or Bar graph mode. In the design of this basic module, consideration must be given to the range of possible supply voltages, and the attendant problem of power dissipation. In Bar graph mode, with +15 volt supply and an input of +5 volts, the power dissipation involved in the i.c. and l.e.d. supply regulator will be 120mW for each milliampere of individual l.e.d. current. Also to be considered are the decoupling requirements to prevent oscillations in applications where long leads are used. The circuit diagram of the 0-5 volt Dot or Bar graph display module suitable for use with supplies of 7-15 volts is shown in Fig. 4.

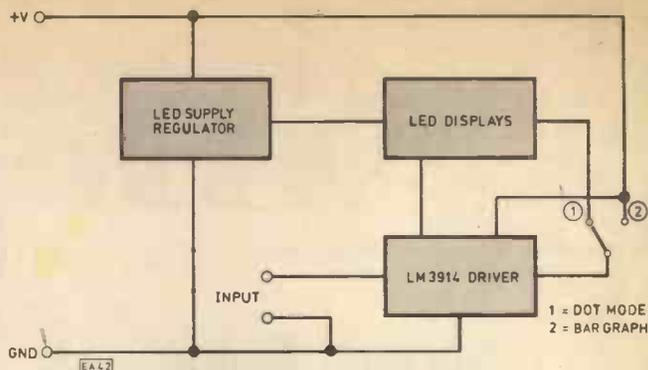


Fig. 3. Block diagram of basic 10-l.e.d. display

BATTERY CONDITION INDICATOR




A measure of the general condition of a motor vehicle battery may be obtained by measuring the terminal voltage under operational conditions. The nominal open-circuit terminal voltage of the conventional 6-cell lead/acid accumulator is 13.2 volts. This value falls under load, especially as the internal resistances of the cells rise due to physical deterioration; and the voltage rises when the cells are on charge. At no time, however, will the terminal voltage fall much below 10 volts, and the voltage regulator should ensure that the terminal voltage does not rise much above 15 volts when charging. For these reasons, a battery condition indicator need only have a display range of approximately 10 to 15 volts.

The transducer requirement is therefore to convert a voltage in the range 10-15 volts into a signal of range 0-5 volts, to be compatible with the display module described earlier. A Zener diode has characteristics ideally suited to this problem. The reverse characteristics of these diodes of Zener voltage above 6 volts are illustrated in Fig. 5 (three graphs). The nominal Zener voltage is usually given at a reverse current of 10mA. The Zener voltage may be increased by the use of a forward-biased conventional diode placed in series with the reverse-biased Zener. This also has the effect of reducing the overall temperature coefficient of the diode combination. The method of generating a zero-referred signal for driving the display unit (i.e. the signal processing unit number 2) in this application is shown in Fig. 6.

The overall circuit of the battery condition indicator is shown in Fig. 7 and it closely follows the block diagram of Fig. 1. The battery voltage is actually measured from the supply to the instrument, which is fully protected against reverse polarity. Using the circuit values given, the first l.e.d. will light at a supply voltage of 9.8 volts, and the tenth l.e.d. will light at a supply voltage of 15.2 volts.

CONSTRUCTION

The detailed construction of the battery condition indicator is a matter which is very much influenced by the preferences of the individual constructor. Two particular constructional examples will be described in some detail, but these are intended only as illustrations of the wide range of practical implementations which are possible. Individual constructors may wish to make different use of the range of displays currently available. There is, for example, a linear array of 12 matched l.e.d.s available in a 24-pin d.i.l. package for those wishing to produce a miniaturised display; such units may be cascaded using additional drivers.

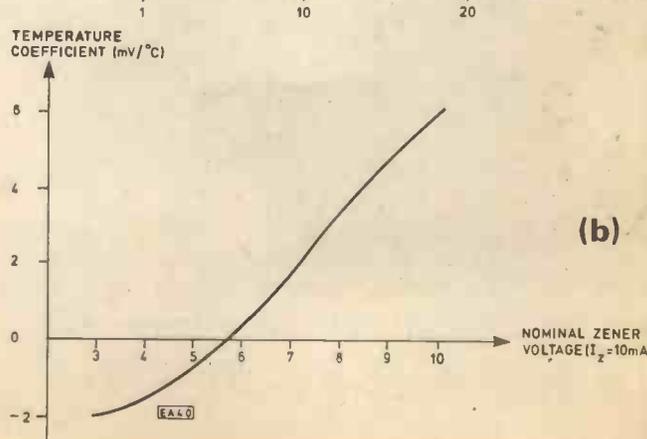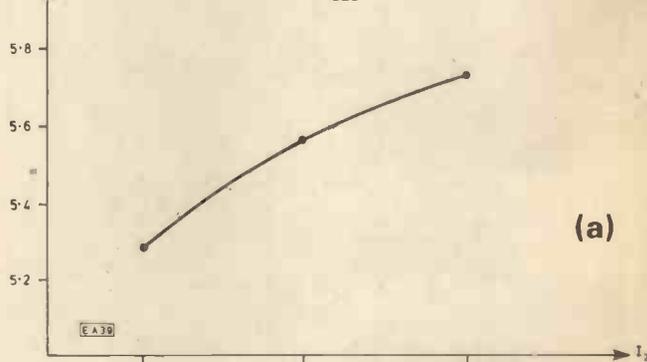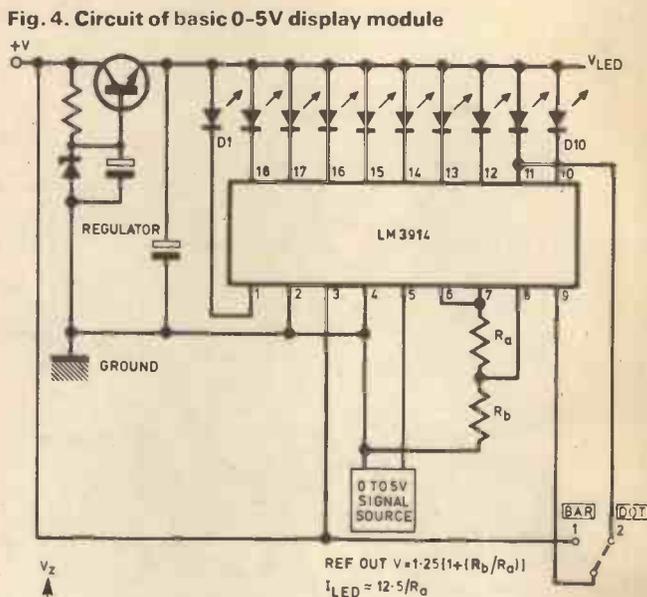

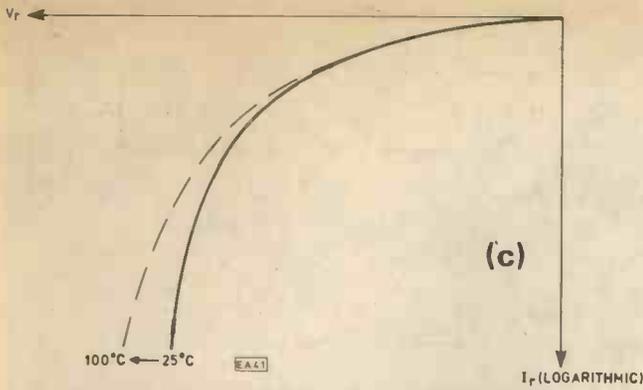


Fig. 5 (above and opposite). Graphs showing reverse characteristics of Zener diodes. (a) Voltage vs. bias current for BZY88 C5V6. (b) Temperature coefficient vs. voltage at I const. (c) Voltage vs. bias current and temp.

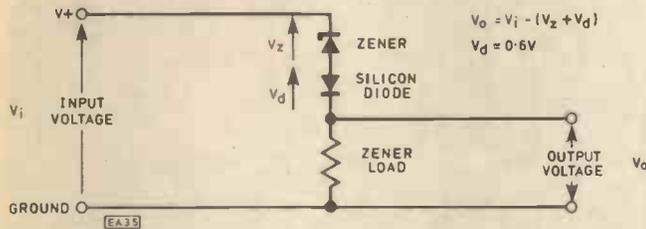


Fig. 6. Zero-referred signal circuit


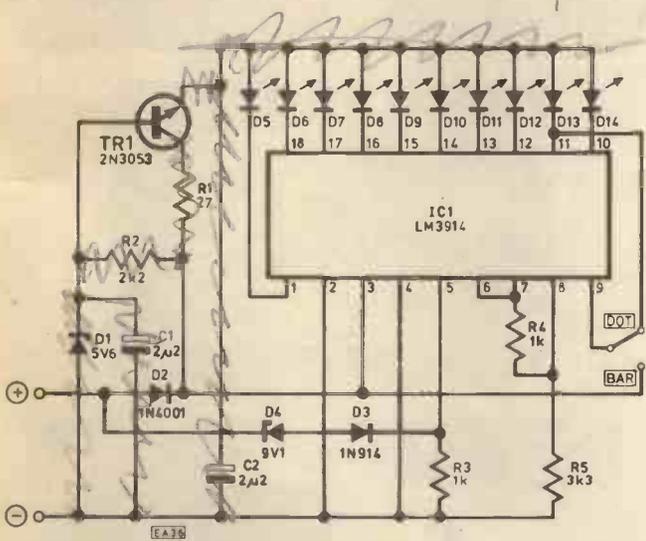


Fig. 7. Full circuit diagram of the Voltage Indicator

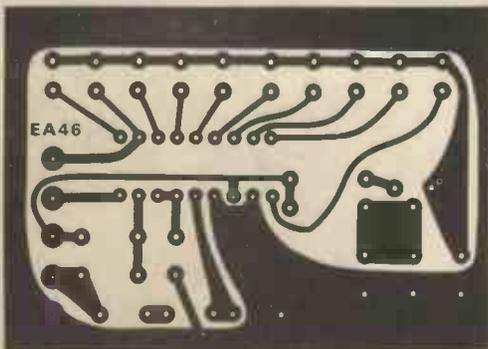

One area of decision at the construction stage is in the mode of display. For a Bar graph display, it seems reasonable to make use of 10 l.e.d.s of the same colour. In Dot mode, however, it is possible to colour-code the individual l.e.d.s to give an indication of satisfactory and unsatisfactory conditions e.g. red for the first three and last two l.e.d.s, and green for the remainder.

Fig. 8 shows the printed circuit track pattern for use in a dashboard instrument mounted in a rectangular moulded "instrument pod". The component layout, shown in Fig. 9, is designed to accommodate 10 standard 5mm diameter l.e.d.s in a straight line. The wire link is shown set up for Dot mode display, and the l.e.d.s are colour-coded as described above. The power supply connections are brought out to two small sockets on the back of the unit; the measurement of battery condition also uses this supply. The p.c.b. should be mounted on spacers to bring the l.e.d.s up level with the back of the front panel window. This front panel cut-out is approximately 56mm long x 5mm high.

The power supply for the instrument should be taken from a low impedance line via the vehicle ignition switch. In use, the instrument has been found to display in the green zone (except when starting!) for batteries and charging systems in good condition.

An alternative arrangement is to build the battery condition indicator as an item of test equipment. For this application a Bar graph display seems more appropriate, though it remains a matter of individual choice. The circuit is the same as before, but in this case the prototype used a piece of 0.1 inch veroboard 60 x 40mm mounted in an all-plastic case measuring 100 x 50 x 25mm. This case is a comfortable size for hand-held operation. The l.e.d.s this time are TIL209 red subminiature types, and are mounted across the short side of the case on a 0.1 inch pitch. A convenient component layout is given in Fig. 10. The l.e.d.s are mounted using the full length of the leads, and the circuit board is secured to the base of the case—an arrangement which brings the active elements up level with the lid of the case. The cutout should be approximately 26 x 3mm. The power supply connections are brought out to flying leads and terminated in crocodile clips; these may then be attached directly across the battery terminals or any other point of interest. The individual illumination voltages for the l.e.d.s may be measured and marked on the case. Typical calibration is given in Table 1. The calibration is determined by the characteristics of D3 and D4, and the accuracy of R4 and R5.

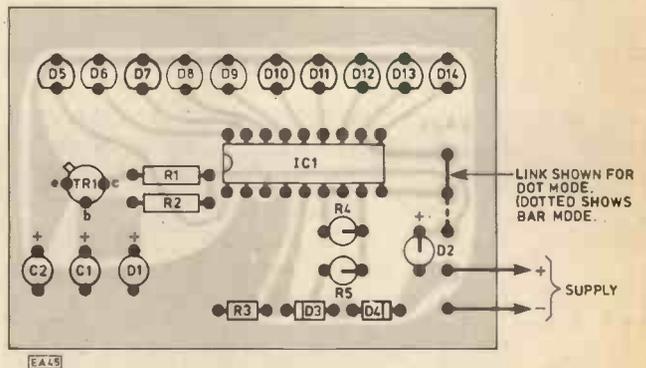


Fig. 9 (above). Component layout of p.c.b. version of Battery Voltage Indicator

Fig. 8 (left). Printed circuit layout (actual size)


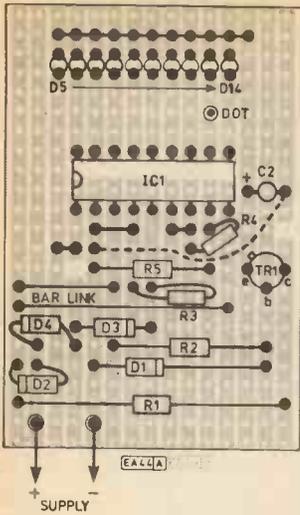


Fig. 10. Alternative Component layout using stripboard (21 track cuts)

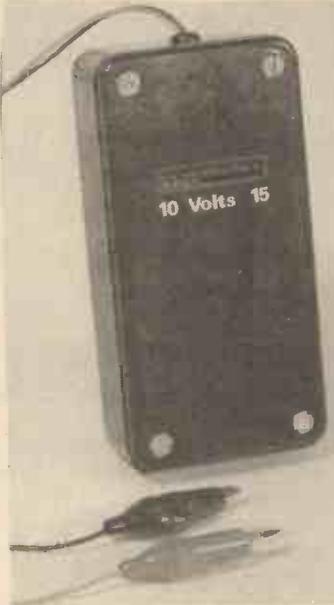

COMPONENTS . . .

Resistors

R1	27Ω	½W	5%
R2	2k2		
R3	1k		
R4	1k		
R5	3k3		

All resistors ½W 5% unless otherwise stated.

Capacitors

C1	2μ2	10V
C2	2μ2	25V

Semiconductors

D1	BZY88C5V8
D2	1N4001 or similar
D3	1N914 or similar
D4	BZY88C9V1
D5-14	10 off l.e.d.s to constructor's requirements
TR1	2N3053/BFY50 or similar
IC1	LM3914

Miscellaneous

- Case
- Printed Circuit Board (or Veroboard)

CONSTRUCTOR'S NOTE

Printed circuit boards, etc., are available from Howard Associates, 59, Oatlands Avenue, Weybridge, Surrey KT13 9SU. S.a.e. for details.

VARIATION OF DISPLAY BRIGHTNESS

The basic display module (Fig. 7) is designed to run the l.e.d.s at a nominal current of 12.5mA each when illuminated. The authors have found this to be a useful compromise value, appropriate to a wide variety of l.e.d. sizes and colours in a range of varied applications. There will, however, be many instances where the requirement of the individual constructor is not satisfied by this compromise value. This section is intended to describe how the basic circuit in Fig. 7 may be modified to suit the application.

The internal reference source develops a nominal 1.25V between the REF OUT (pin 7) and REF ADJ (pin 8) terminals. The current drawn out of the REF OUT terminal determines the l.e.d. current and approximately 10 times this current will be drawn through each illuminated l.e.d. The l.e.d. current will be relatively constant despite supply voltage and temperature fluctuations.

Table 1: L.e.d. illumination voltages in two circuit arrangements.

L.e.d. number	Illumination Supply Voltage	
	D3=short circuit D=BZY88C9V1	D3=1N914 D4=BZY88C9V1
5	9.3	9.8
6	9.9	10.45
7	10.5	11.1
8	11.1	11.7
9	11.7	12.25
10	12.25	12.85
11	12.85	13.45
12	13.35	14.05
13	13.85	14.6
14	14.55	15.2



In the circuit of Fig. 7 the l.e.d. current is:

$$I_{LED} = 12.5/R4$$

The full-scale indication value is:

$$V_{FSI} = 1.25 (1 + R5/R4)$$

The adjustment of the l.e.d. current programming resistor R4 will thus affect the full-scale indication voltage, and must be compensated by a corresponding change to R5. A table of suitable values for R4 and R5 for different l.e.d. currents is given in Table 2. Values of R4 and R5 are nearest preferred values, and R5 may need to be trimmed to give the required full-scale indication (see later). An alternative arrangement using variable resistors is shown in Fig. 11. The adjustment procedure is as follows. Connect the instrument to a variable d.c. supply and adjust VR1 to give the required l.e.d. brightness. Now adjust the supply to give 5.0V at pin 5, and vary VR2 such that D14 is just illuminated. Adjustment is

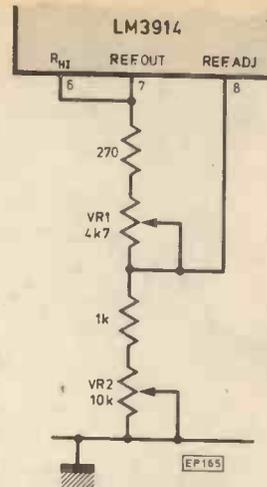


Fig. 11. Variation of l.e.d. brightness

Table 2: Values of R4 and R5 for differing l.e.d. currents.

L.e.d. current	R4(Ω)	R5(Ω)
1.2	10k	33k
2.7	4k7	15k
5.7	2k2	6k8
12	1k	3k3
17	750	2k2
22	560	1k8
27	470	1k5
32	390	1k2

now complete. In applications where an l.e.d. current in excess of 12mA is required, the maximum allowable regulator power dissipation will be exceeded for a fully-illuminated bar display. In such cases it is recommended that the discrete regulator (TR1, R1, R2, D1 and C1) is replaced with an i.c. 5V regulator mounted on a small heatsink. In dot mode the power consumption should not be a problem, as the maximum dissipation will be only 10 per cent of the bar mode display. The LM3914 has a maximum dissipation of 660mW. ★

NEXT MONTH: engine r.p.m. counter



Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS. Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for.....(amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss

ADDRESS


POSTCODE

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53626. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

USING Your FREE I.C. REMOVAL TOOL

Now you can get them out! Back in May we gave you a free I.C. Insertion Tool—these are still available from the editorial office for £1 each inclusive—now you can have its companion the I.C. Removal Tool, perhaps even more useful, and again extras are available for 50p each inclusive.

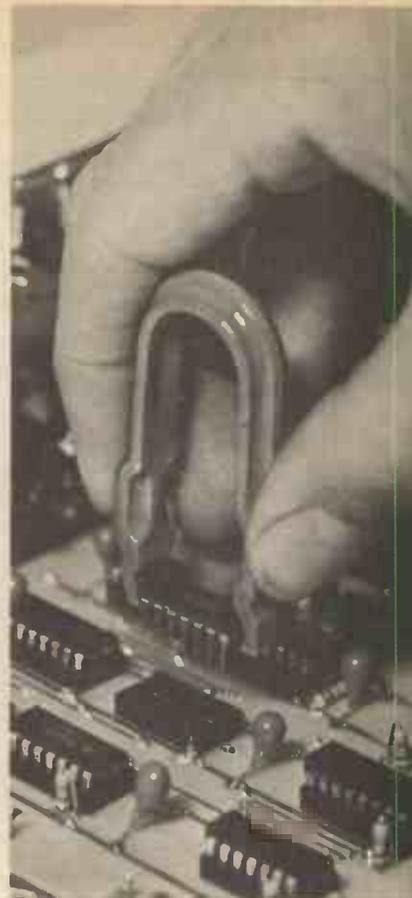Simply place the tool over the ends of 8, 14 or 16 pin d.i.l. i.c.s. and pull them out—it's that easy now!



News Briefs

ELECTRONICS CLUB AT MARGATE

A NEW electronics club has been started, called *Thanet Electronics Club*. Meetings are held every Thursday at the Quarter Deck, Margate, from 7.30 p.m. Other activities include camps, shows and visits. For youth (especially girls!!), it says in their literature. Further details: Ken Smith, The Electronics Laboratories, University of Kent, Canterbury CT2 7NT.

ON COURSE

SOUTH London College. A short course (ten lectures) will run on microprocessors, their hardware/software and applications, commencing October 2, 1979, and every following Tuesday at 6.30–8.30 p.m. A knowledge of digital principles is assumed. Course fee is £7.

Applications for *Microprocessors and their applications*, to Mr. A. A. Rowlands (course organiser), South London College, Knights Hill, London SE27 0TX.

AUTOMATIC FARE COLLECTION

WESTINGHOUSE are to design new ticket machines, gates and the communications network for the London Underground. Implementation is planned for the mid 1980's.

Fraud estimated at £8m a year should be virtually eliminated.

A Compendium of Electronic Erudition

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At £2.85 inc. VAT and postage (£3.45 overseas) they are obtainable from:

Post Sales Department, IPC Magazines Ltd.
Lavington House, 25 Lavington Street
London SE1 0PF

I enclose P.O./cheque value for binders at
£2.85 each (£3.45 overseas) for *Practical Electronics*
Vol. No's

Name

Address

Date

PE

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIER POWER AMPLIFIER



CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < 0.05% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 65dB; slew-rate 3V/μS; T.H.D. 20Hz–20kHz < 0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 × 80 × 20mm. Supply to be ± 15 volts.

MC 1—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

X02 : X03 — ACTIVE CROSSOVERS

X02 — two way, X03 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS

It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically -01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μS; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 × 80 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120–240 primary and single bolt fixing (includes capacitors/bridge rectifier).

PRE-AMPLIFIER KIT

This includes all metalwork, pots, knobs etc. to make a complete pre-amp with the CPR 1 (S) module and the MC 1 (S) if required.



ACTIVE CROSSOVERS

X02 £15.16 X03 £23.58

POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35v £19.52

CE 1004 100W/4 ohms 35-0-35v £23.02

CE 1008 100W/8 ohms 45-0-45v £25.96

CE 1704 170W/4 ohms 45-0-45v £31.00

CE 1708 170W/8 ohms 60-0-60v £33.97

TOROIDAL POWER SUPPLIES

CPS1 for 2 × CE 608 or 1 × CE 1004 £16.56

CPS2 for 2 × CE 1004 or 2/4 × CE 608 £18.80

CPS3 for 2 × CE 1008 or 1 × CE 1704 £19.75

CPS4 for 1 × CE 1008 £17.12

CPS5 for 2 × CE 1708 £24.18

CE 1708 £25.53

HEATSINKS

Light duty, 50mm, 2°C/W £1.44

Medium power, 100mm, 1-4°C/W £2.35

Disc/group, 150mm, 1-1°C/W £3.04

Fan, 80mm, state 120 or 240v £19.70

Fan mounted on two drilled 100mm heatsinks, 2 × 4°C/W, 65°C max. with two 170W modules. £31.05

THERMAL CUT-OUT, 70°C.. £1.54

Pre-amp Kit

£38.07

POWER AMP KIT

£35.03

PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPRI £31.85

CPRIS £40.87

MCI £21.28

MCIS £33.17

POWER SUPPLY

REG1 £8.90

TR6 £1.97

BRIDGE

DRIVER, BDI

Obtain up to 340W using 2 × 170W amps and this module BDI £5.75

CRIMSON ELEKTRIK

1A STAMFORD STREET,

LEICESTER, LE1 6NL

Tel: (0533) 653508

U.K.—please allow up to 21 days for delivery.

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

BADGER SOUND SERVICES LTD.
46 WOOD STREET, LYTHAM ST. ANNES,
LANCASHIRE FY8 1QG
"MINIC TELEPRODUKTER"
BOX 12935: S-750 12
UPPSALA 12, SWEDEN"


Guess who builds this great



Logic Probe... YOU! for only £11.92

With this easy-to-build Logic Probe Kit from CSC and just a few hours of easy assembly—thanks to our very descriptive step-by-step manual—you have a full performance logic probe.

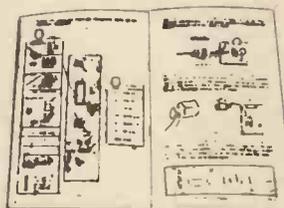With it, the logic level in a digital circuit is indicated by light from the Hi or Lo LED; pulses as narrow as 300 nanoseconds are stretched into blinks of the Pulse LED, triggered from either leading edge. You'll be able to probe deeper into logic with the LPK-1, one of the better tools from CSC.



Complete, easy-to-follow instructions help make this a one-night project.

CONTINENTAL SPECIALTIES CORPORATION



EUROPE, AFRICA, MIDEAST: CSC UK LTD. Dept. 5Z
Shire Hill Industrial Estate Units 1 and 2
Saffron Walden, Essex CB 11 3AQ
Telephone: SAFFRON WALDEN (0799) 21682
TLX 817477

CONTINENTAL SPECIALTIES CORPORATION, DEPT. 5Z
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____

Address _____

Inc P&P and 15% VAT

LPK-1 £14.86

I enclose cheque/

PO for £ _____

FREE Catalogue

tick box

Phone your order with Access. Barclaycard

or American Express

Card No. _____

Expiry date _____

DIGITAL TEMPERATURE CONTROLLER

D. COUTTS & P. MCALLISTER

TO date there have been many circuits produced to measure temperature and display it, either in analog form, or, more recently, in digital form using seven segment displays. Temperature control on the other hand has been left largely to the mechanical bimetallic strip. This suffers from restricted control range on one hand and coarse setting on the other. Even electronic systems using pots to set the temperature suffer from similar problems. However, a new chip from G.I. Microelectronics has been designed to combine the functions of digital temperature display and measurement with accurate control over wide range using digital switches (BCD encoded) to set up the desired temperature.

This project describes a system, using this chip, suitable for use in photography, home brewing, aquariums or even just simple room heating.

CONTROLLER DESCRIPTION

Externally the controller has the following format. All controls and the display are mounted on the front panel. The desired temperature is set up on the two digit BCD switch. The four seven segment leds are used as follows:

1. The left hand digit displays a C when the cooler is switched on and a minus sign (segment g) when the temperature is negative.
2. Two centre digits show the actual temperature from 0 to 90°C. The right hand digit displays an H when the heater is on.

Mounted on the back panel are two mains outlets, one to which a heater may be connected, and the other a cooler; an outlet for the temperature sensor, which consists of four diodes, and the mains inlet and three fuse holders.

DRIVE CIRCUIT

The relay drive circuit is necessary only because the chip cannot sink enough current to operate the relay. In the heater circuit, TR3 sinks the relay current while TR4 inverts the signal from the chip to drive TR3. Diodes D1 and D2 are necessary to protect TR1 and TR3 from the back e.m.f. generated by the relay coils when they turn off. Switches S1 and S2 are to enable either the heater or cooler to be manually turned on. Diodes D3, D4, D5, and D6 allow the on position of either S1 or S2 to over-ride the control signals from the chip. Thus if the cooler is on and then the heater is switched on using the manual switch (S2) the cooler will go off, and stay off (unless S1 is also turned on) until S2 is switched off again (Fig. 2).

CONTROLLER CIRCUIT

The controller circuit is best described by giving a brief description of the function of the circuitry to each pin out (Fig. 1).

Pins 21-27 drive the units digit, while pins 29-35 drive the tens digit. Pin 40 drives the sign indicator. Pin 17 drives the cooler relay circuit, and pin 18 the heater relay circuit.

Pins 14, 15 and 16 form the bridge network which does the temperature measurement and sensing. Before describing this further a few words about the use of a diode as a temperature sensor.

The voltage drop across a diode when current flows through it in the forward direction depends on the magnitude of the current and its temperature, so that to achieve a voltage across the diode varying only with temperature a constant current is put through it. Note that the value of this



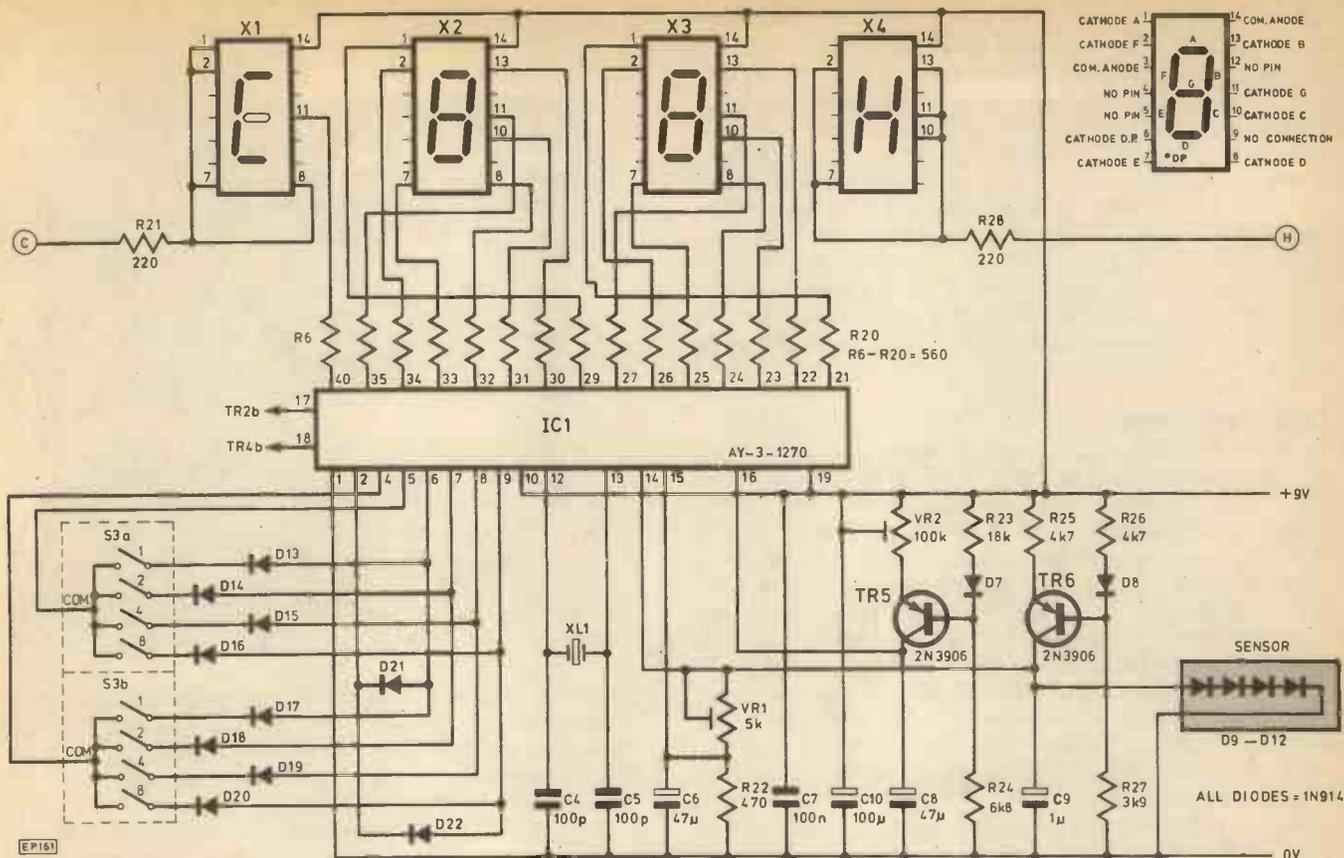


Fig. 1. Circuit of controller

current is chosen so that the diode is well passed the knee of its turn on characteristic, but not so high that a significant amount of self heating occurs. Under the above conditions the voltage across the diode varies approximately linearly by about 2mV/°C. To operate correctly the chip requires a change at its input of at least 5mV/°C hence it was decided to use four diodes in series to ensure sufficient voltage change.

R25, R26, R27, D8 and TR6 form the constant current source driving the diode sensor network, D9 to D12; the junction of TR6 and D9 providing the temperature dependant voltage to the input pin 14 of IC1. Pin 15 is connected to

a reference voltage, provided by VR1 and R22. This is adjusted to give the same voltage out as the sensor network at 0°C. Pin 16 is connected to a linear ramp, generated by the constant current source VR2, R23, R24, D7 and TR5 charging capacitor C8. IC1 measures the time that the ramp takes to travel between the voltage at pin 14 and the voltage at pin 15. Since these voltages are the same at 0°C, and the voltage on pin 15 varies linearly with temperature; time is also proportional to temperature. Suitable adjustment of VR2 enables the display reading to represent °C. If the voltage on pin 15 is less than that on pin 14, the minus sign comes on.

COMPONENTS . . .

Semiconductors

TR1-TR4	BC337 (4 off)
TR5-TR6	2N3906 (2 off)
IC1	AY-3-1270 (Marshall's)
IC2	7805 (with heatsink)
D1-D2	1N4004
D3-D22	1N914
D23	BZY88-3.9V Zener
REC1	1A bridge rectifier

Capacitors

C1	1,000µ	25V
C2-C3	100n	30V disc ceramic
C4-C5	100p	30V disc ceramic
C6	47µ	16V tantalum
C7	100n	30V disc tantalum
C8	47µ	16V tantalum
C9	1µ	16V tantalum
C10	100µ	16V tantalum

Switches

S1-S2	SPST 250V, 10A rocker (2 off)
S3	2 decade thumbwheel edge switch

Relays

RLA, RLB	12V, 205Ω two pole changeover (contacts 5A, 250V) (2 off)
----------	---

Displays

X1-X4	0.3in, 7 segment green l.e.d.s (common anode) (4 off) Bezel to suit 4 displays
-------	---

Potentiometers

VR1	5k 20 turn trimmer
VR2	100k 20 turn trimmer

Miscellaneous

XL1	560 kHz ceramic resonator
SK1, SK2	205 x 140 x 75mm case (Marshall's) 3 way sockets (2 off)

Resistors

R1	560
R2-R5	6k8 (5 off)
R6-R20	560 (15 off)
R21	220
R22	470
R23	18k
R24	6k8
R25-R26	4k7
R27	3k9
R28	220
All ¼W 10% carbon	

OSCILLATOR


XL1, C4 and C5 form the oscillator circuit. (XL1 is a ceramic resonator). The diode matrix connected to pins 4-9 determine the actual temperature to which the temperature is controlled. Diode D22 selects l.e.d. drive mode (if this diode is left out, the chip produces a.c. output signals for driving l.c.d.s). Diode D21 sets the controller output hysteresis to 2°C. In other words, when the desired temperature equals the displayed (actual) temperature, the heater (or cooler) will go off. The heater will not come on again until the temperature has dropped by 2°C. Likewise the cooler will not come on unless the temperature rises by two degrees. This prevents excessive switching on and off of the relays.

CONSTRUCTION

Mount and secure the panel components to the box. Note that to simplify wiring to the front panel, diodes D13-D20 are mounted on the back of their respective BCD switches, on the terminals marked 1, 2, 4, and 8. Now make and drill the p.c.b. and base of the box so that it may be easily mounted after the components are inserted. It is a good idea to hold the p.c.b. in position on the box while drilling to ensure perfect alignment of the holes. Now mount the remaining components on the p.c.b. as illustrated in Fig. 3.

The wiring to the front panel should now be carried out. The connections to be made are shown in Fig. 4. Note, that in order to accommodate the heatsink, which must be flattened in order to fit in, the terminals on S1 and S2 require shortening.

When wiring the back panel it is essential to keep in mind the electrical rating of the components being used to ensure they can safely handle the current and voltage of the appliance being controlled. First make sure the mains flex is rated to carry the current the heater/cooler requires. The live should go straight to the three fuses. FS1 then supplies the transformer; FS2 and FS3 each go to one set of relay contacts. The relay contacts are rated at 5A, 250V each. Since there are two contacts in each relay, used in parallel

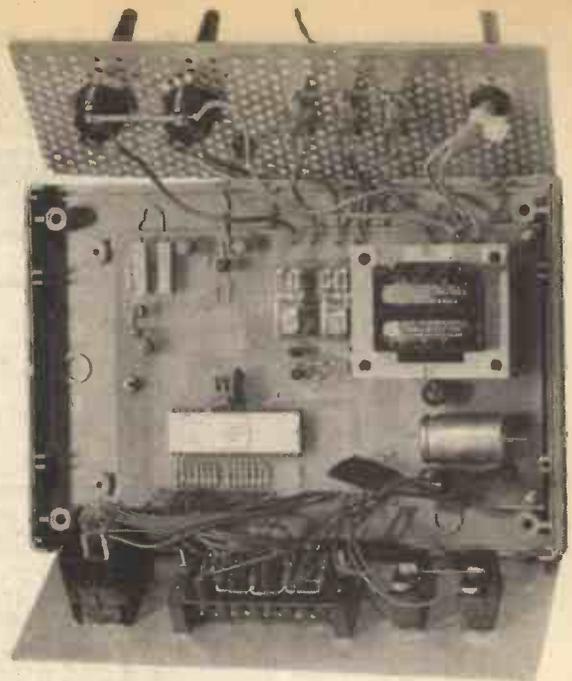

in this circuit, each relay may switch 10A. Inductive loads, such as motors, cause faster contact wear hence these should be limited to appliances with a rating of about 1A. With resistive loads, such as heaters, the full 10A rating may be used.

It is also unlikely that the p.c.b. track will carry such large current, hence it should be reinforced by soldering thick copper or tinned mains wire along the length of the current carrying tracks to and from the relay contacts. The outlet sockets take their neutral and earth straight from the mains input and their live from the relay switch. The sockets suggested are rated at 250V 1.5A. If this is insufficient use higher rated sockets, or alternatively wire the appliance permanently to the appropriate relay.



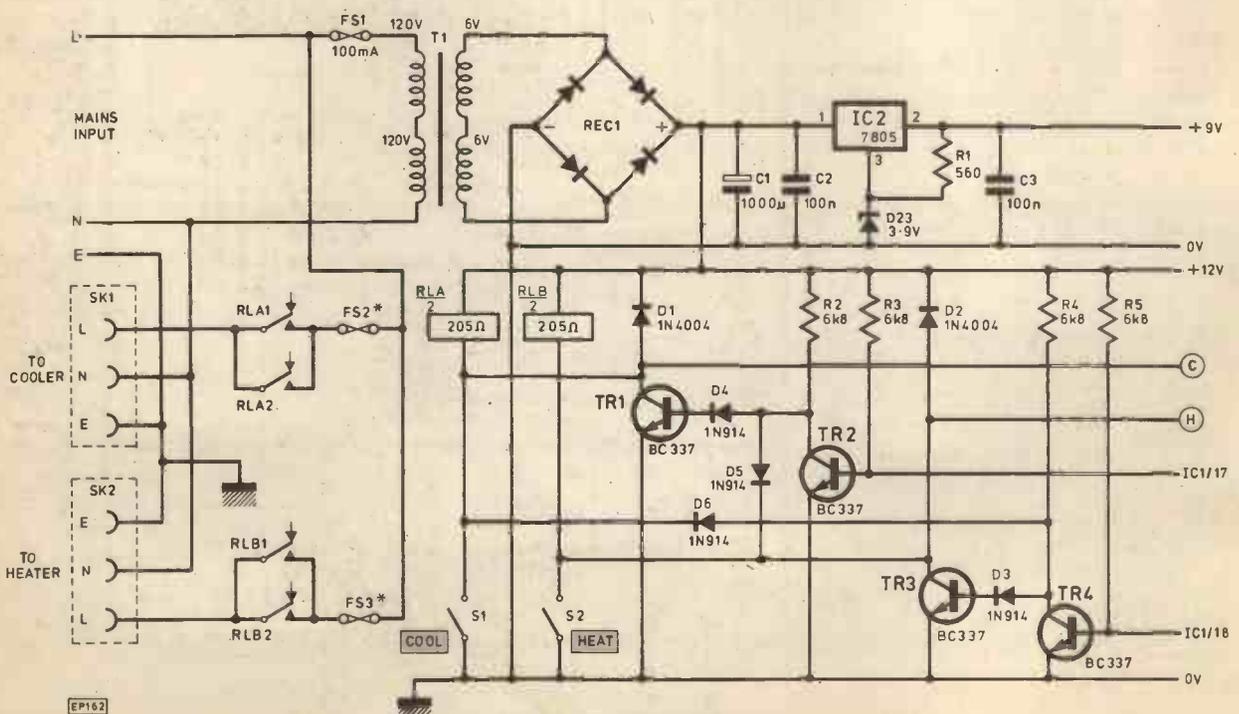
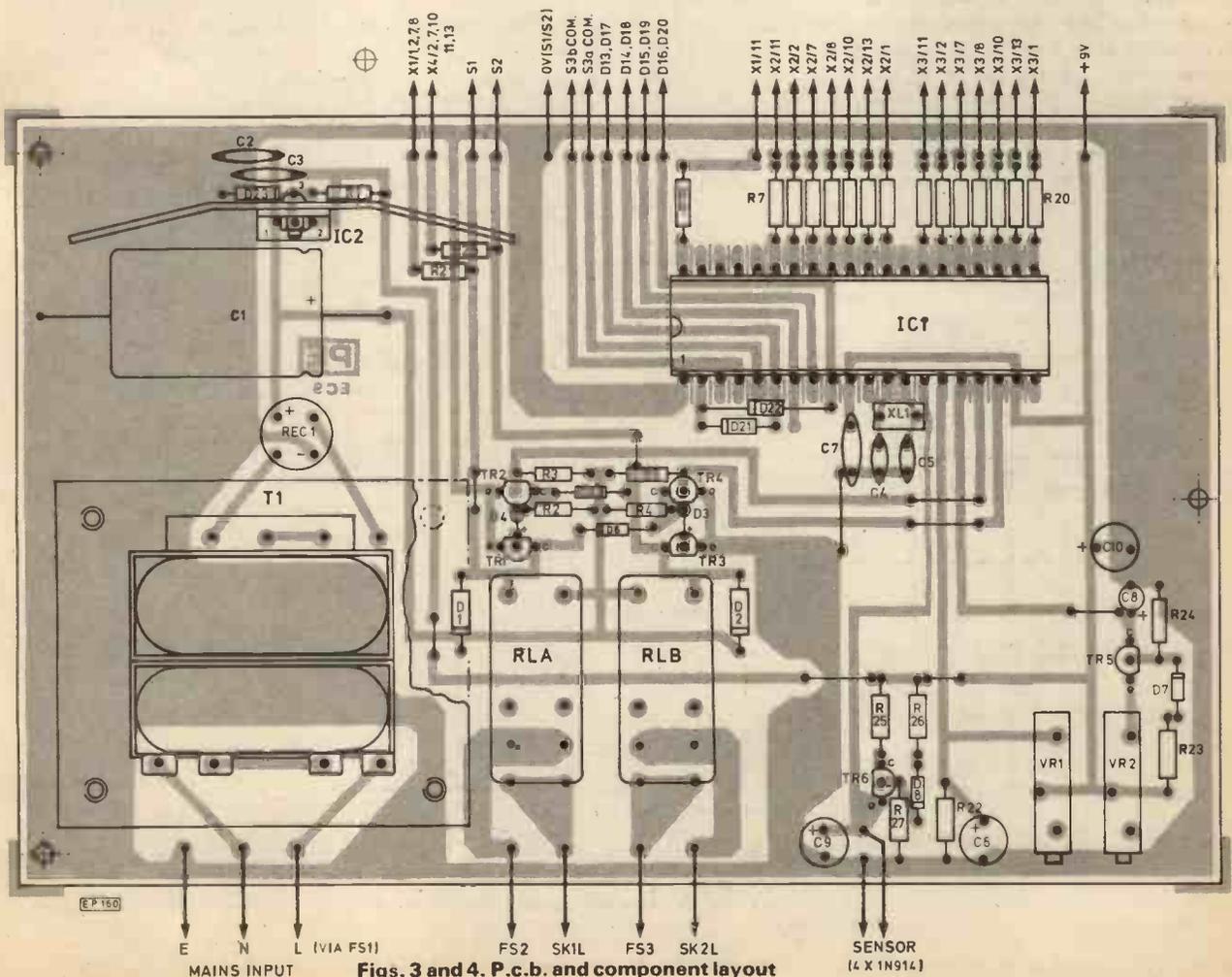


Fig. 2. Relay drive circuit and p.s.u.

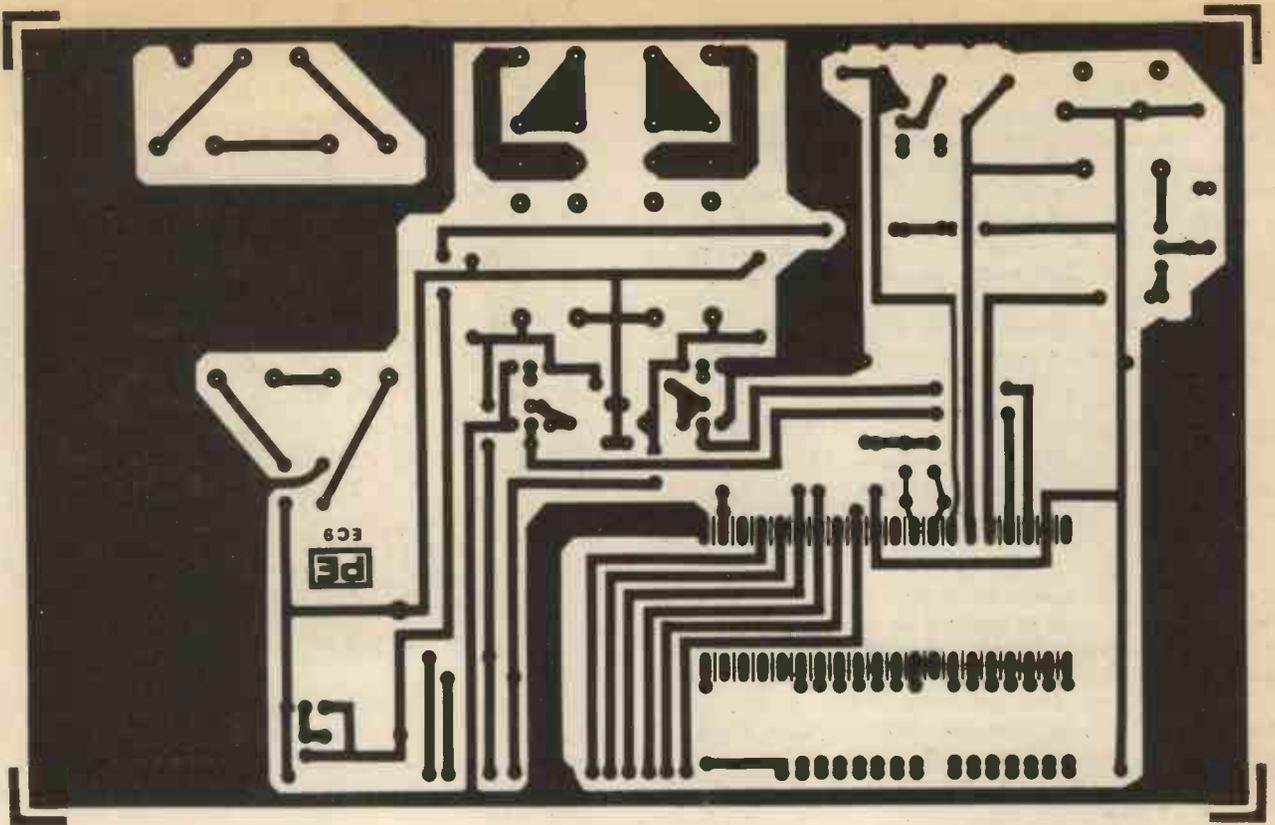

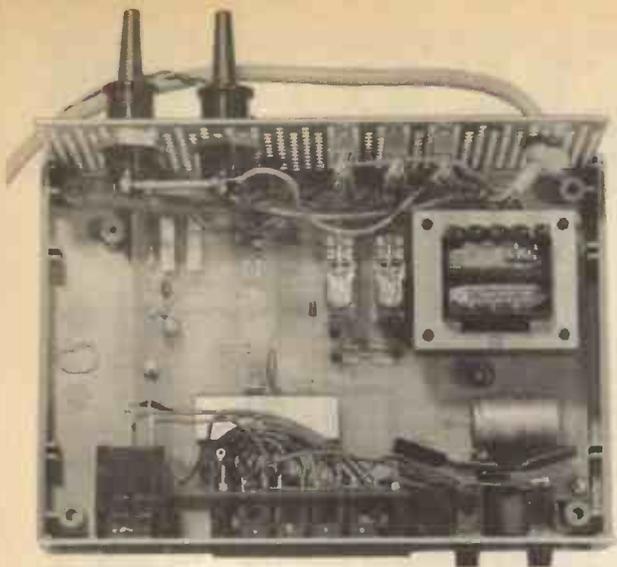Figs. 3 and 4. P.c.b. and component layout





Finally the diodes D9-D12 which form the sensor should have their leads cut short and be soldered together then insulated so that there is no danger of a short circuit by encapsulating in epoxy for example. The sensor diodes should then be connected to the controller via a length of wire, sufficient to place them far enough away from the

controller so as not to be affected by the heat coming from it. Don't forget to check the diodes polarity before connecting up. The circuit should now be ready for bolting into the box and fixing on the lid.

MODIFICATIONS AND ADJUSTMENTS

Hysteresis can be set to 2°C or 4°C by connecting diode D21 either between pins 2 and 6 or between pins 2 and 7 on IC1.

Before applying power to the circuit set VR1 and VR2 to mid positions, and do not short out VR2 when calibrating. To calibrate put the sensor in melting ice. After about 30 seconds adjust VR1 until the display reads zero. Now put the sensor in boiling water—when the display reading has settled adjust VR2 until the display reads 99 then zero—this represents 100°C, the “one” display being on the unused pins 36-38 of IC1. The calibration procedure should be repeated.

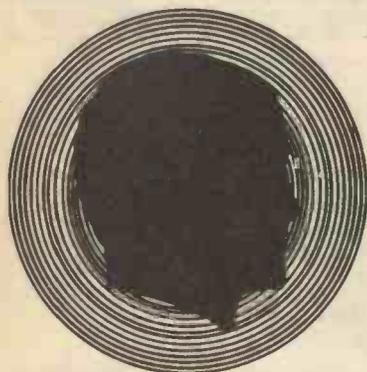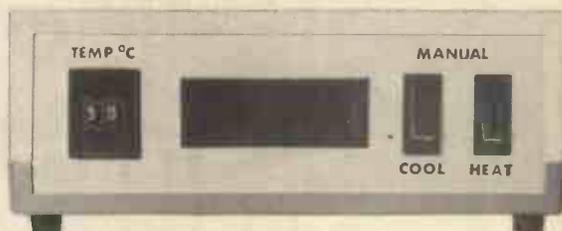

INGENUITY UNLIMITED

BATTERY MONITOR

MOST published designs for battery condition indicators light an l.e.d. when the battery nears exhaustion. However, a light may easily be overlooked if continuous and a significant improvement may be made by running the l.e.d. from an oscillator at 1 or 2Hz.

This circuit accomplishes this by employing an inexpensive dual op-amp as both a comparator and an oscillator. Half


of the supply voltage is derived from R2 and R3, and this is compared with a Zener reference; so when the battery voltage lowers, the output of IC1a becomes positive. R4 and R5 apply hysteresis.


IC1b forms an oscillator with a frequency of 1Hz. With the output of IC1a high, D1 flashes with a peak current of about 5mA. When IC1a output is low, the l.e.d. cannot light. D1 protects the l.e.d.

from reverse voltage breakdown in this condition.

Because of the low current consumption of IC1, only 2mA are drawn from the battery. With a 9V battery, the values are as shown, but for a larger battery voltage, D3 and R8 should be increased in proportion. Maximum supply voltage is 32V.

D. P. Akerman,
Coventry.

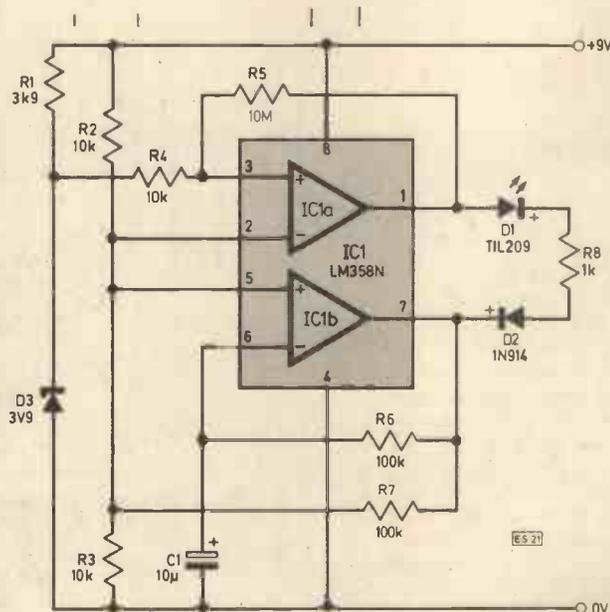

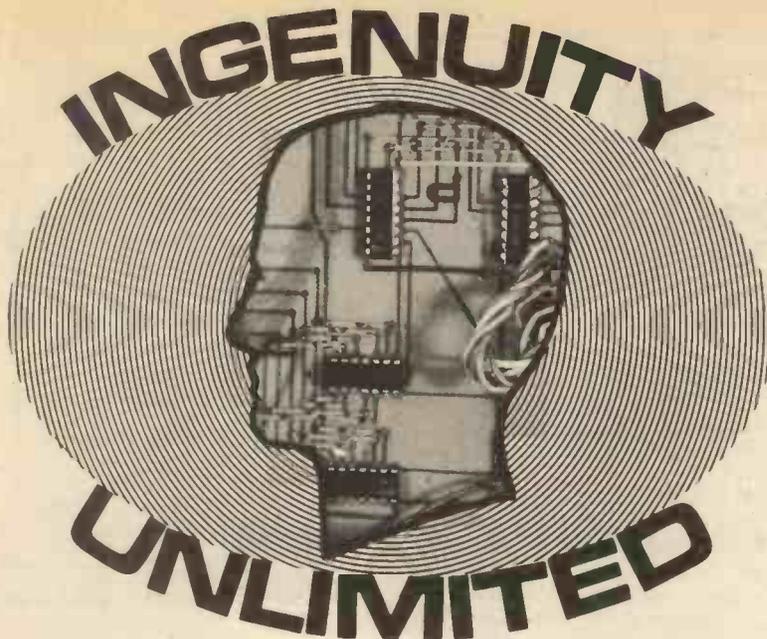

A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.


Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

FREEZER TEMPERATURE ALARM

THIS circuit was designed to give an audible alarm if, for any reason, the cabinet temperature of a deep freeze should rise above -10°C , thus giving time to take action to save the contents of the deep freeze from defrosting. Due to the high cost and low reliability of batteries, a mains powered unit was required. In order to eliminate the possibility of a power cut going unnoticed and ruining the contents of the freezer, the circuit was arranged such that loss of mains power would also trigger the alarm, the power being obtained from a standby battery.

The heart of the unit is the 748 op amp which acts as a comparator of a set voltage obtained from VR1 and VR2 against a voltage dependent on the resistance of R3. As the temperature rises the resistance of the thermistor falls and the voltage at the inverting input falls thus turning on TR2 and the alarm formed around IC2.

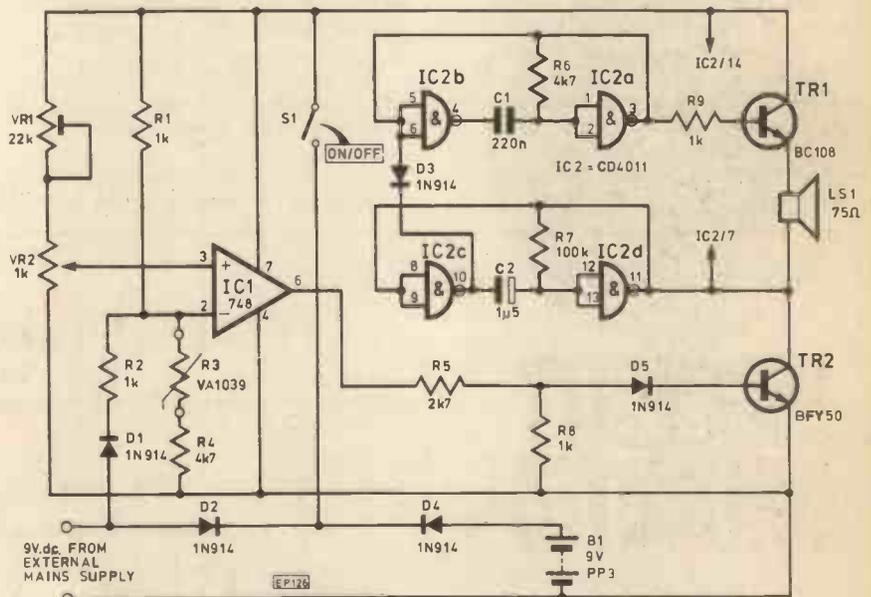
IC2a, IC2b, C1 and R6 form a high frequency oscillator. IC2c, IC2d, C2 and R7 form a low frequency oscillator. The two oscillators are linked by the diode, D3. The tone obtained from the speaker is thus a modulated high frequency tone or bleep, this sound being very noticeable with a very modest current consumption.



While mains power is available, the battery is isolated by the reverse biased D4, and no power is drawn from it. The two $1\text{k}\Omega$ resistors, R1 and R2, are effectively connected in parallel thus giving a total resistance of 500Ω to the inverting input from the +ve supply. When mains power is lost diode D4 will be forward biased and the battery will power the circuit. However, D1 will be reverse biased and so R2 will be out of circuit, and the effective resistance to the inverting input will rise to $1\text{k}\Omega$. Thus the voltage at this input will fall and the alarm will sound.

The only adjustment necessary is to calibrate VR1 and VR2 so that the alarm is just triggered at -10°C . A freezing mixture of ice and salt may be used for this. The state of the internal battery may be periodically tested by depriving the unit of mains power and listening for the alarm. The normal defrosting of the freezer is adequate for the testing of the rest of the circuit.

A. M. Smithers,
Tangmere,
Sussex.

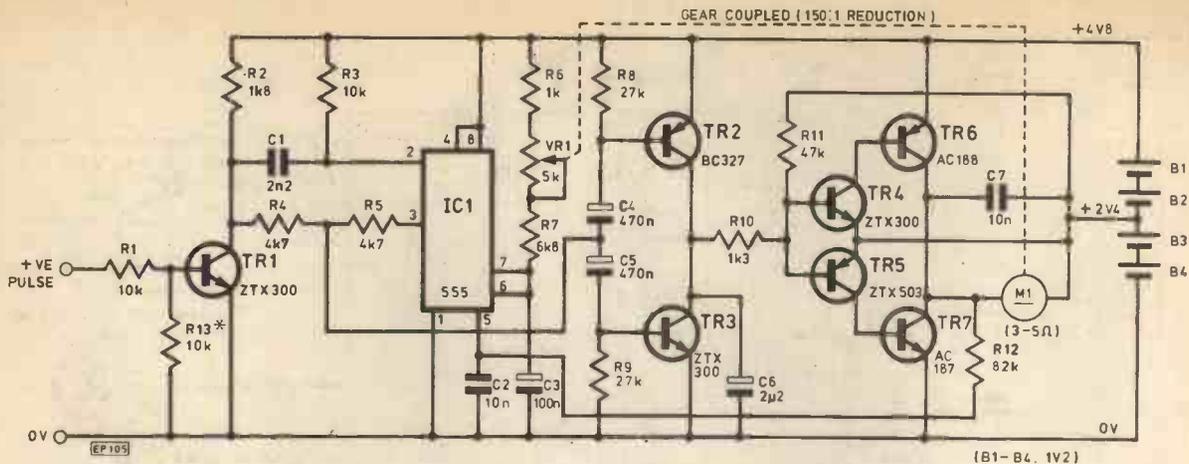

DIGITAL SERVO AMPLIFIER

THIS servo amplifier was developed for one reason—minimum component count. This has been achieved by the use of a 555 timer used as a one shot or monostable. This has the advantage of saving transistors and diodes for the normal monostable arrangement. Also, although many op-amps can perform this function the 555 has the advantage of being able to work down to $-4V$, and has the ability to have its pulse-widths modified by applying a control voltage to pin 5. Fortunately, the normal position for deriving this voltage is of the correct sense ($-ve$ feedback). The selection of R12 to $82k\Omega$ depends on control pulse neutral;

servo mechanics and the degree of under/over shoot which is acceptable for a loss in amplifier gain and hence speed of the servo and its torque. R6, VR1 and R7 and C3 control the pulse width range of the monostable. R6 should be fixed, but if the feedback potentiometer value is not $5k\Omega$ then R7 and C3 can be adjusted to give the desired centre (mechanical) and range of monostable widths.


The values of VR1, R7 and C3 have been adjusted here for 1.5ms neutral and a range of 1ms (i.e. 1 ms minimum and 2ms maximum).

The value of R7 and C3 are interlinked and some trial and error is needed to ob-

tain the correct centre (mechanical) and pulse width range (servo travel). No problems with the ultra stable pulse widths produced by the NE555 have been encountered and hence servo drift, when clocked by a battery driven encoder (subject to pulse width changes with battery voltage falling). For $-ve$ pulse systems remove TR1 and associated R1, R2 and R13 and apply $-ve$ pulses to C1+R4 junction.

If room is available fit R13 ($10k\Omega$) in. $+ve$ going systems.

G. Pike,
Co. Antrim,
N. Ireland

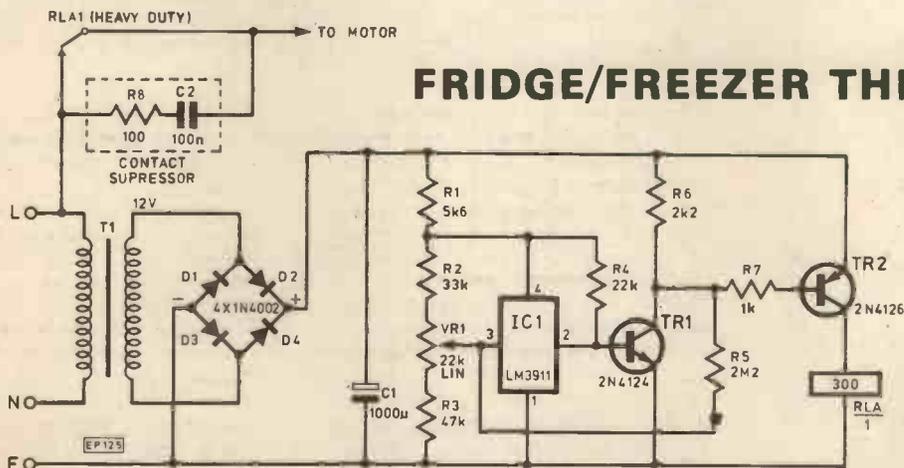

FRIDGE/FREEZER THERMOSTAT

THE circuit is built around the LM3911 temperature control i.c. and is designed as a cheap electronic replacement for the mechanical thermostats fitted to fridges and freezers.


Resistor R1 provides a positive voltage to the i.c. internal stabiliser, pin 4. R2, VR1 and R3 provide a present reference voltage to the i.c., pin 3. The output, pin 2, is taken to TR1 base and controls the relay via TR2.

The i.c. is mounted on a piece of Veroboard in a suitable probe box in the freezer. As the probe temperature rises above the level set by VR1, the i.c. output drops below 0.7 volt. Transistor TR1 switches off and switches TR2 off. The relay releases and the break contacts close, starting the freezer motor. When the temperature has dropped sufficiently the i.c. output volts rise above 0.7 volt and the relay operates, stopping the motor.

Resistor R5 provides positive feedback to ensure a rapid switching of the relay and to provide a temperature difference between switch on and switch off.

The motor is controlled via the relay break contact so that in the event of a circuit failure, the relay will release and the motor will run continuously.

B. C. James,
Wilford,
Nottingham.

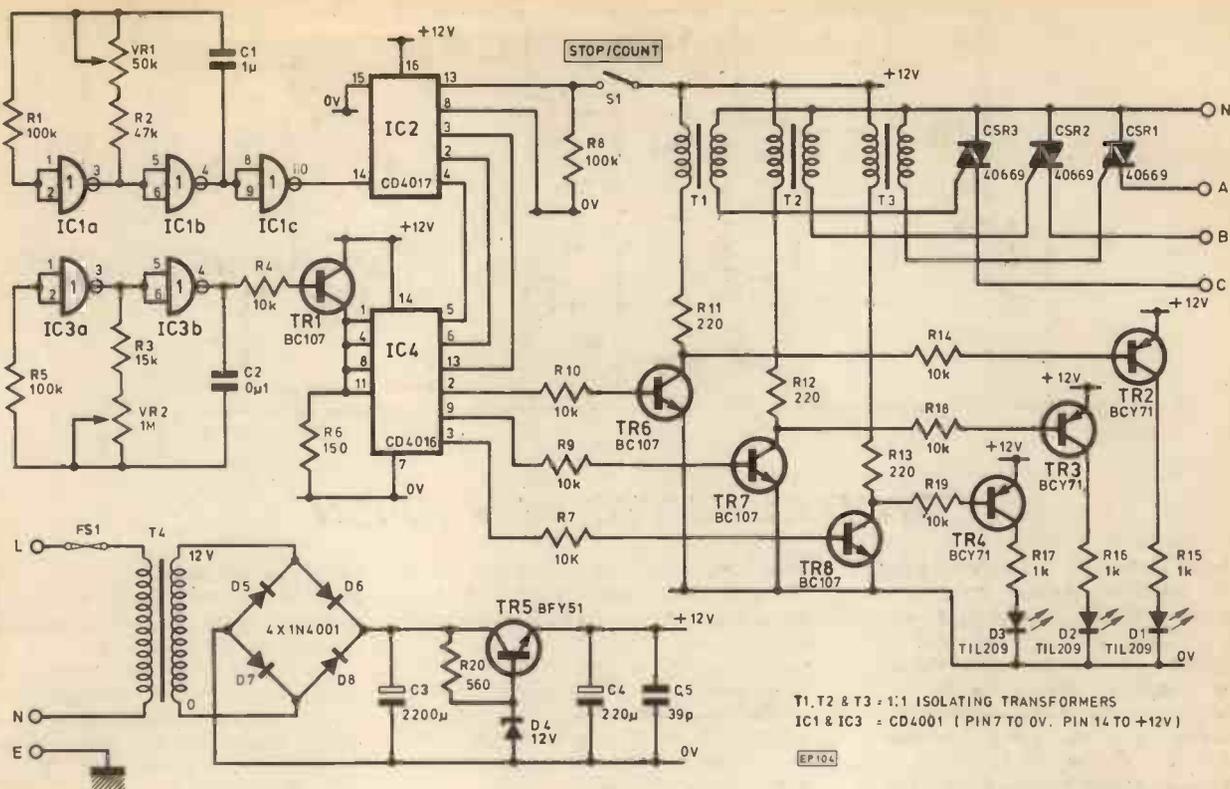

SEQUENTIAL LIGHT CHASER

THE design requirement for this light chaser was to have three channels but be capable of accepting up to ten. The circuit shown satisfies these conditions.

IC1 can be either a CD4001 or a CD4011 as can IC2 as the gates in these are used with their inputs joined. IC1a and IC1b form a slow running oscillator which can be varied by use of VR1. This potentiometer controls the speed at which the outputs switch. IC1c shapes the pulses from the oscillator before they are fed into a decade counter (CD4017). The outputs from the CD4017 are low until pulsed at which point the appropriate output goes high.

In the circuit only the outputs '0', '1' and '2' are shown, with output '3' being used to trigger the counter reset. A switch is included so that the count may be frozen at a desired point e.g. to check bulbs. For use with more outputs the reset would be connected to the 'Carry Out' pin, which

pulses only after each tenth input pulse.

IC3a and IC3b form a second oscillator running considerably faster than the first. This is buffered by a single BC107 transistor stage to provide enough current if more output stages are required. The output from the buffer is taken to the inputs of bilateral switches contained in the CD4016. The trigger voltage for these switches is provided by the outputs of the CD4017 which allows bursts of high frequency from IC1 oscillator to be passed to the triac firing circuits. VR2 in the second oscillator allows an interesting strobing effect to be produced in the output lamps.

The high frequency bursts are amplified by BC107 transistors which have 1:1 ratio insulation transformers in series with resistors in their collector lines. The transformers used had a breakdown voltage of 1.5kV and can be obtained cheaply, although they can be made by winding two layers of 26s.w.g. enamelled


copper wire on a one inch piece of ferrite rod with a layer of p.v.c. tape between each winding. Each winding to have 30 turns.

One side of the secondary is connected to neutral and the other to the gate of the output triacs. The triacs specified handle at least 5A, but others may be chosen to suit individual applications.

A set of mimic lights are included, but these could be omitted to reduce cost. A simple regulated p.s.u. is shown which supplies 12V. It should be noted that the control side of the unit is *not* connected to the mains. This makes it very much easier to work on the electronics whilst switched on. The outputs of the triacs (A, B, C) go to the load which in turn is connected to mains live. The inputs of all unused gates must be connected to 0V or +12V.

N. R. Negus,
Upton-on-Severn,
Worcs.

MOTION DETECTOR

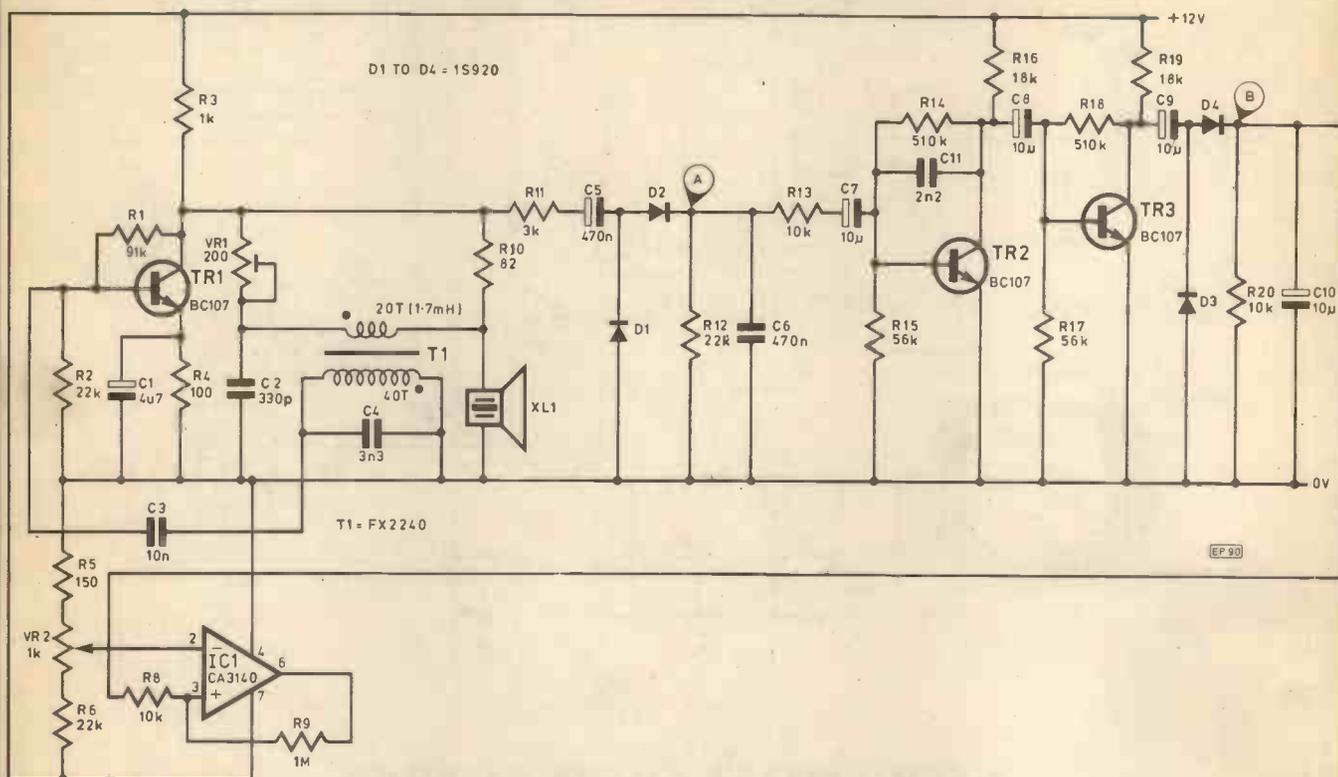

THIS circuit was designed as a motion detector, but it can be used as a level, proximity, air and gas flow switch; and in some cases as a gas leakage detector. Heart of the circuit is a 40kHz ultrasonic transducer.

One of the standard ways of detecting motion is by taking doppler shift measurements, but then one needs to use two transducers, one as a transmitter and the other as a receiver. But the circuit overcomes this disadvantage and is fairly simple to construct.

The transducer is used in series resonance as part of the oscillator, so that it determines the frequency of oscillation.

It is used in a bridge circuit. Here the voltage ratio between R10, and the impedance of the transducer at series resonance, determines the feedback voltage for oscillation. In this case, the frequency is about 40kHz.

This feedback ratio will vary depending on amplitude and phase of the transmitted signal reflected back to transducer, thereby modulating the amplitude of the oscillator. The output from the oscillator is rectified by diodes D1 and D2, to give a low frequency signal. Amplitude of this signal will depend on the distance between transducer and reflector.

If a reflector is placed quite close to the transducer, so that the reflected signal is large and 180° out of phase. The feedback voltage will decrease to a value below that required to keep the circuit oscillating. This characteristic of the circuit makes it possible for it to be used as a level switch by sampling the output at D1 and D2.

The low frequency a.c. signal at D1 and D2 is further amplified by transistors TR2 and TR3.

The output from transistor TR3 is rectified and filtered to give a d.c. voltage.

A CA3140 operational amplifier is used as a comparator, with a small amount of hysteresis, and an adjustable reference, so that one can adjust the sensitivity at a given distance from the transducer. It was possible to detect a person crossing at a distance of 3 metres from the transducer using the prototype.

All one needs to align it is a high impedance d.c. voltmeter. The voltage at point A is adjusted to one volt by potentiometer VR1. Have somebody move at the maximum distance you are interested in, and adjust the comparator reference VR2 accordingly.

If one is interested in using it as a burglar alarm, one can feed from point B to an R-S flip flop.

S. Choudhari,
Trondheim,
Norway

Now, the complete MK 14 micro-computer system from Science of Cambridge

VDU MODULE. £33.75

(£26.85 without character generator) inc. p & p.

Display up to ½K memory (32 lines x 16 chars, with character generator; or 4096 spot positions in graphics mode) on UHF domestic TV. Eurocard-sized module includes UHF modulator, runs on single 5 V supply. Complete ascii upper-case character set can be mixed with graphics.


POWER SUPPLY. £6.10 inc. p & p.

Delivers 8 V at 600 mA from 220/240 V mains – sufficient to drive all modules shown here simultaneously. Sealed plastic case, BS-approved.

CASSETTE INTERFACE MODULE.

£7.25, inc. p & p.

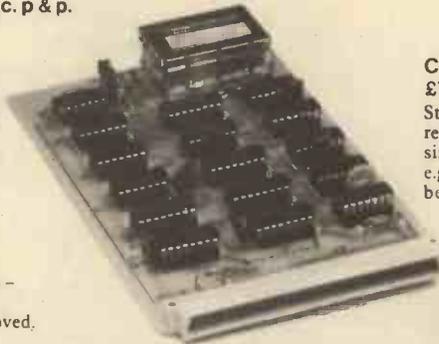Store and retrieve programs on any cassette recorder. Use for serial transmission down single line at up to 110 baud (teletype speed), e.g. over telephone line, and to communicate between two or more MK 14s.



MK 14 MICROCOMPUTER KIT

£46.55 inc. p & p.

Widely-reviewed microcomputer kit with hexadecimal keyboard, display, 8 x 512-byte PROM, 256-byte RAM, and optional 16-lines I/O plus further 128 bytes of RAM.

Supplied with free manual to cover operations of all types – from games to basic maths to electronics design. Manual contains programs plus instructions for creating valuable personal programs. Also a superb education and training aid – an ideal introduction to computer technology.

Designed for fast, easy assembly; supplied with step-by-step instructions.

PROM PROGRAMMER.

£11.85 inc. p & p.

Use to transfer your own program developed and debugged on the MK 14 RAM to PROM (74S571) to replace SCI0S monitor for special applications, e.g. model railway control. Software allows editing and verifying.

To order, complete coupon and post to Science of Cambridge for DELIVERY WITHIN 14 DAYS. Return as received within 14 days for full money refund if not completely satisfied.

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me:

MK 14 standard kit @ £46.55.

Extra RAM @ £4.14 per pair.

RAM I/O device @ £8.97.

VDU module including character generator @ £33.75.

VDU module without character generator @ £26.85.

Cassette interface module @ £7.25.

PROM programmer @ £11.85.

Power supply @ £6.10.

Full technical details of the MK 14 System, with order form.

All prices include p and p.

I enclose cheque/MO/PO for £ _____ (total).

Name _____


Address (please print) _____

Delivery within 14 days.

PE/10/79

Science of Cambridge Ltd

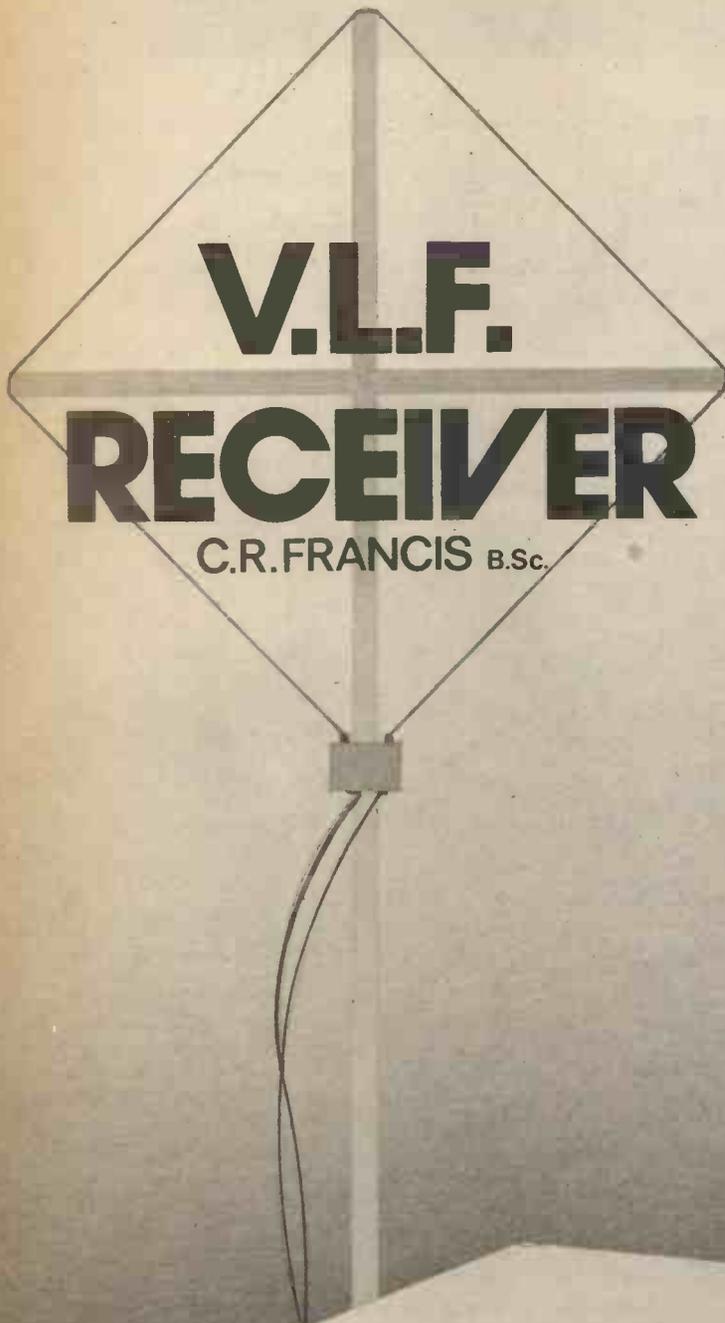6 Kings Parade, Cambridge, CAMBS., CB2 1SN.
Tel: 0223 311488.



THE ELF and VLF (extremely low and very low frequency) bands of the radio spectrum, which lie in the frequency range 300Hz to 30kHz, contain a number of interesting signals which are both man-made and naturally occurring. These were described in some detail in the September issue of PE, and are summarised in Fig. 1.

A portable receiving system which will enable these signals to be picked up will be described here. In designing such a system, careful attention has to be paid to interference problems. The signals of interest are on the whole rather weak, while the field strength due to mains electricity in a typical house is, by contrast, at a fairly high level. In the UK moreover, there is a very powerful VLF transmitter at Rugby, called GBR, which transmits at 16kHz and whose signal saturates the entire country. This signal is modulated by frequency shift keying, and non-linearities in the receiver may cause demodulation of this, producing interference. Signals from broadcast transmitters may also cause interference in the same way.

In this receiver these problems have largely been alleviated, but one or two sources of interference still remain, and they put constraints on the operating conditions. The first of these is interference from TV sets; this may be partially overcome by careful orientation of the aerial, but the best solution is to wait until transmissions have ceased in the evening. Many natural signals may only be received at night anyway, since they must penetrate the ionosphere. Another source is motor vehicles, and again this problem will often disappear after midnight. Next, proximity to broadcast transmitters gives rise to very high field strengths, so that the attenuation at RF built into the receiver may be insufficient. This also applies to the signal from Rugby and in some cases RF interference may prove to be a serious obstacle, though usually the problem will again disappear when the transmissions cease in the evening. Finally, nearby electricity substations will generate continuous interference. The only solution here is to take the receiver elsewhere.

THE RECEIVING SYSTEM

A block diagram of the receiving system is shown in Fig. 2. The aerial is a multi-turn loop, screened at RF. At VLF such an aerial appears as an inductance to the receiver, and we may therefore use a transformer to match the impedance of this to the high value presented by the front-end of the receiver. This has a further advantage in that the voltage of the signal is increased.



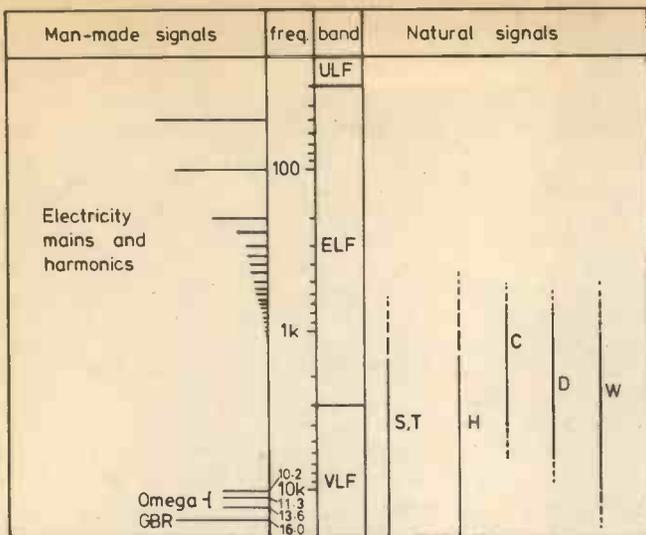


Fig. 1. Approximate frequency ranges of ELF/VLF signals. S: Sferics; T: Tweeks; H: Hiss; C: Chorus; D: Discrete emissions; W: Whistlers

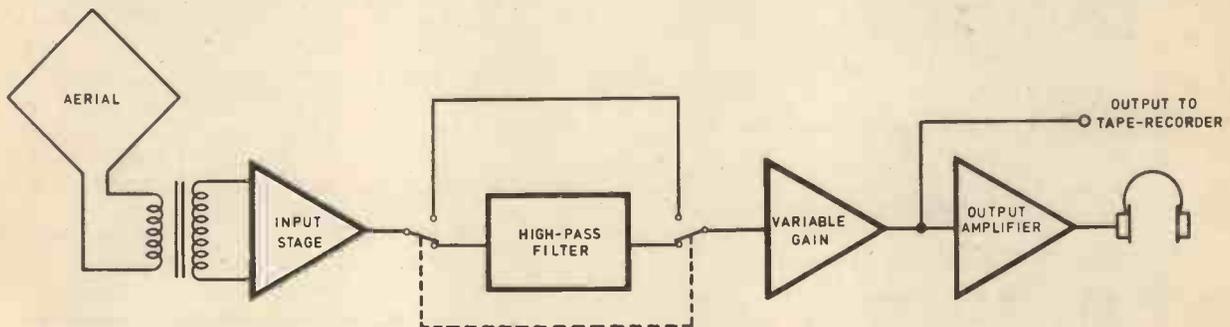


Fig. 2. Block diagram of the receiving system

The gain of the front-end is not defined by the use of negative feedback, and so will depend on the individual transistors used. It is, however, of the order of 40dB. The frequency response of this stage has been limited to 10kHz, to reduce the effect of the GBR signal. This filtering must be carried out as early as possible to minimise the chance of demodulating the GBR signal.

The signal then passes via a buffer stage to a passive high-pass filter, to remove the effect of mains and other low-frequency interference. This filter (and its buffer) may be switched out of the circuit, since the receiver may be used in remote areas where there is little interference. The next stage is a variable gain amplifier; the gain may be varied from 0dB to 60dB. The signal level is now high enough to drive a tape-recorder or other external equipment, and an internal output stage is also provided. This is completely separate; it is on a separate board and has its own power-supply to try to minimise the effects of unintentional positive feedback. There is, after all, a large amount of gain in the receiver. The output stage may be switched off if necessary, and it may of course be omitted entirely.

INPUT STAGE

The circuit diagram of the input stage is shown in Fig. 3. The input transformer, T1, has a turns-ratio of 100, and C1 is included to shunt RF signals. Part of the load for TR1, R3, is bootstrapped by C4, while C2 shunts this at frequencies above 10kHz.

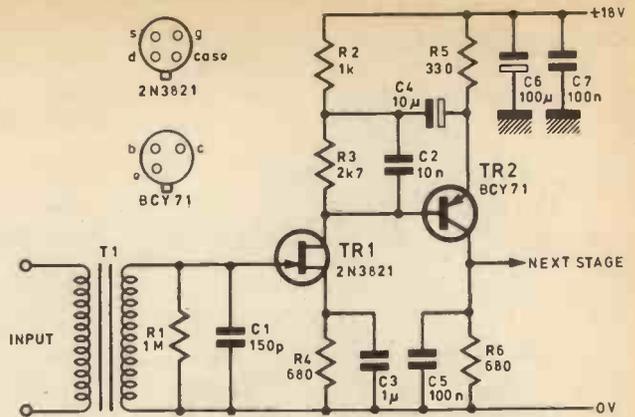


Fig. 3. Circuit diagram of the input stage

The input FET, TR1, gives the input stage a reasonably good noise performance since it is a fairly low noise device and provides useful gain. High gain in the input stage is essential in a low-noise receiver, so that the noise of following stages is negligible. Feedback is not used to limit the gain of this stage, so that the maximum gain is available.

PASSIVE FILTER

Fig. 4 shows the passive high-pass filter and its input buffer. This stage can be bypassed by the switch S1. The filter, comprising C9, C10, C11, L1 and L2 is a five element Tchebycheff high-pass, designed to have 0.28dB ripple in the passband. The cut-off frequency is about 1500Hz and the roll-off about 40dB per octave. For ideal operation the source and load impedance of this filter should be 220 ohms. IC1 is acting as a voltage follower, and has a very low output impedance; R7 therefore sets the source impedance. The load impedance is set by the parallel combination of R8 with the impedance between C11 and the virtual

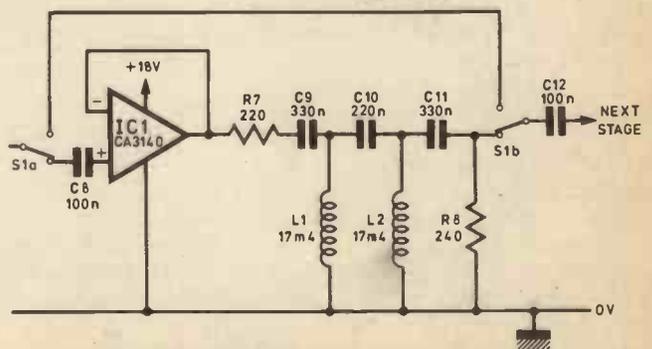


Fig. 4. Circuit diagram of the passive filter stage

earth at the inverting input of IC2. For a characteristic impedance of exactly 220 ohms, the values of the capacitive and inductive elements should be $C9$ and $C11 = 323\text{nF}$, $L1$ and $L2 = 17.4\text{mH}$ and $C10 = 206\text{nF}$. However the error introduced by using the preferred values for capacitance is acceptable.

OUTPUT STAGES

The next stage is shown in Fig. 5; it is a stage with variable gain. Negative feedback is varied by VR1, from 0dB to 60dB and since the bandwidth here is 10kHz, a 741 has adequate performance. The tape output is taken from this stage, via C13.

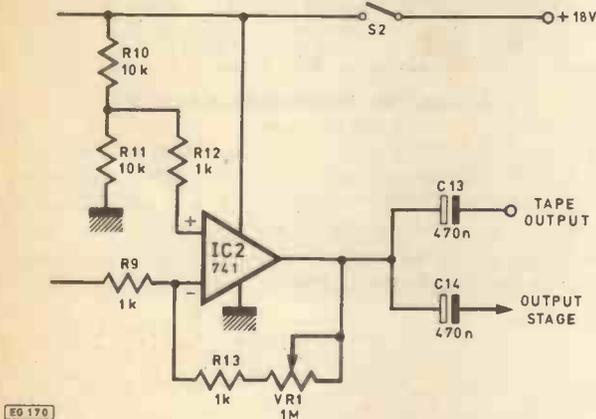


Fig. 5. Circuit diagram of the output stage

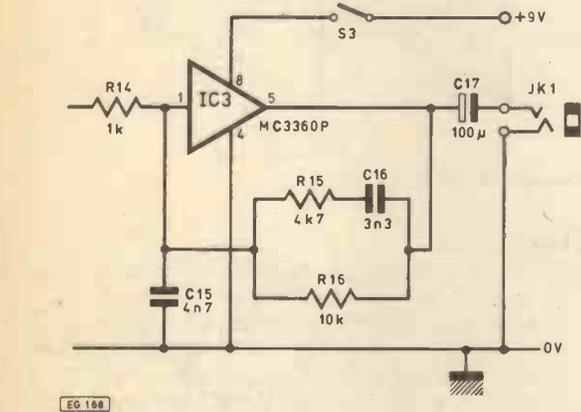


Fig. 6. Circuit diagram of the amplifier stage

The internal output amplifier is shown in Fig. 6. This is based on the Motorola MC3360P $\frac{1}{4}$ watt audio amplifier i.c. The power to this stage comes from a separate 9V battery and may be switched off independently from the receiver, by S3. The ground line of this stage is of course a common ground with the other circuitry.

THE AERIAL

A multi-turn loop aerial is used, made from a length of 15-core screened cable. A 5m length of this is adequate, though of course a longer piece or a larger number of cores will make a more sensitive aerial. It is unwise, however, to make an aerial of vastly different dimensions from those suggested without giving thought to matching the input transformer primary winding, and to possible resonances due to the combination of the loop inductance with its stray capacitance. Fig. 7 shows the main constructional features; the cores are connected by means of a piece of tagboard,

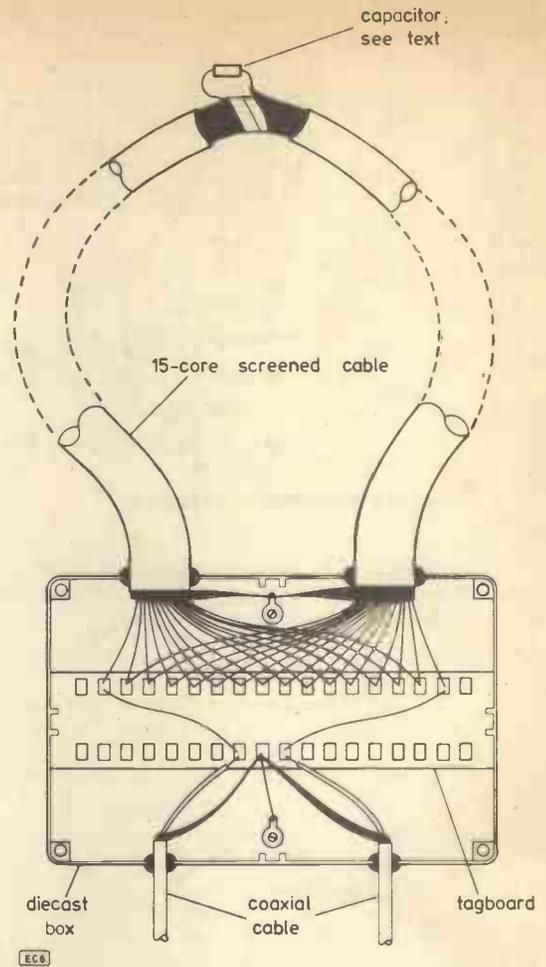


Fig. 7. Construction of the multi-turn aerial

within a metal box. Take care to produce one continuous wire with 15 turns, rather than, say, 15 separate single turns. This may be achieved by selecting a colour, say black, and soldering this to the first tag. Then solder the other end of the black to the brown at the next tag, the other brown end to the red, etc. The screen, and the screen of the output cables should be connected to the box.


In theory the screen should be cut at some point and linked by a capacitor, as indicated in Fig. 7, so that the screen is complete at RF, but broken at VLF. While trying to reduce RF interference, however, the author has found that the gap may in fact be absent. Individual experiment may be needed here, and it is suggested that the aerial be first constructed with the screen intact.

Co-axial cable should be used for the output leads, and any good quality co-ax connectors may be used (BNC types were used in the prototype), since the low impedance of the aerial at VLF will not match any particular type of cable or connector.

The aerial should be fitted onto a frame consisting of two, five to six foot lengths of wood fitted together to form a cross. The diecast case can be fitted to the base of the frame and the aerial loop spread out around the frame to form a diamond shape.


CONSTRUCTION

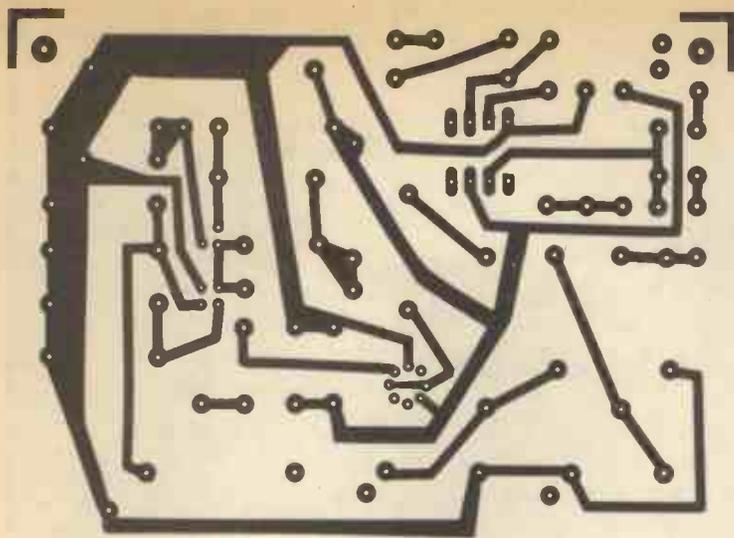The receiver circuitry is carried by two printed circuit boards; the main receiver is shown in Figs. 8 and 9, while Figs. 10 and 11 show the output stage. Three coil assemblies are required, T1, L1 and L2. Pads have been provided on




PE
EG174

Fig. 8. P.c.b. design for the receiver circuit

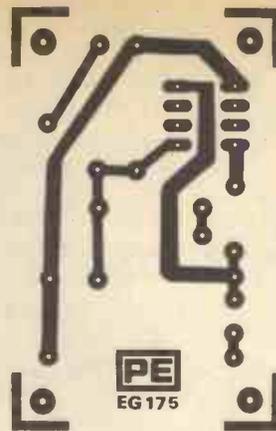


PE
EG175

Fig. 10. P.c.b. design for the amplifier circuit

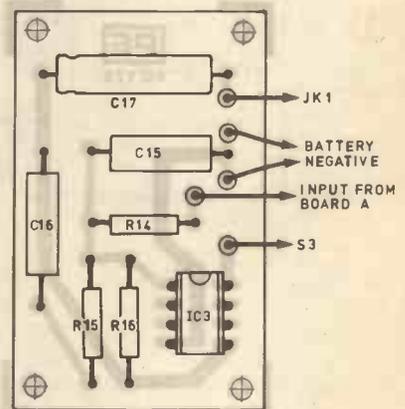

EG176

Fig. 11. Component layout for the amplifier circuit

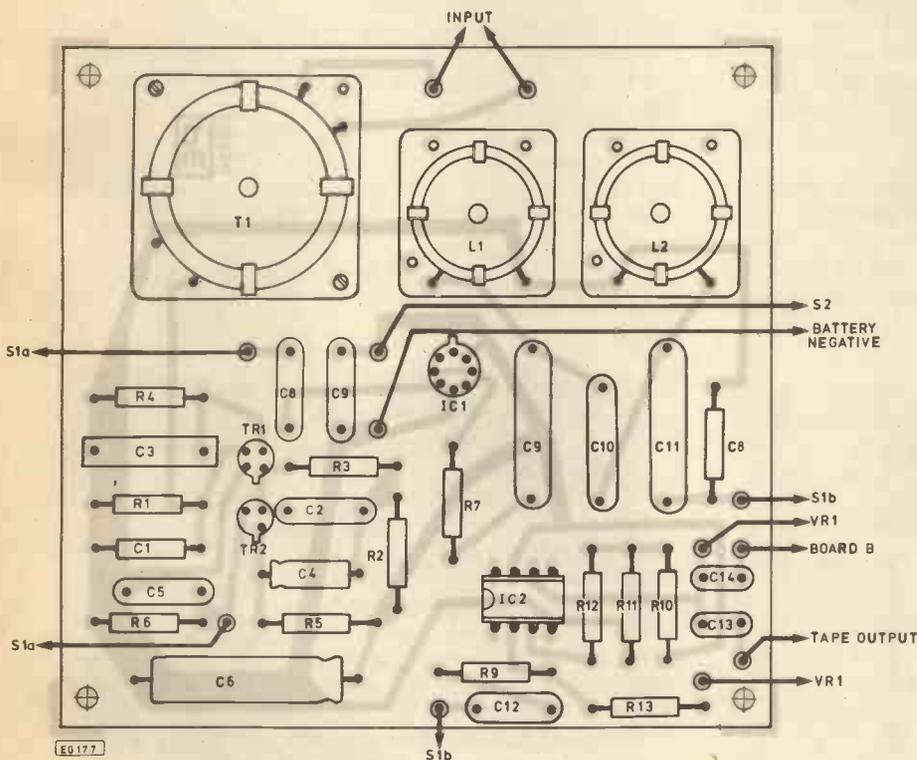


EG177

Fig. 9. Component layout for the receiver circuit

the receiver to suit the Mullard p.c.b. mountings for these cores; in the prototype receiver, however, steel cans (also manufactured by Mullard) were used, and the assemblies bolted to the case. Details of both of these alternatives are shown in the layout diagram, Fig. 12. Note that the use of a metal case is strongly advised; a diecast box was used for the prototype.

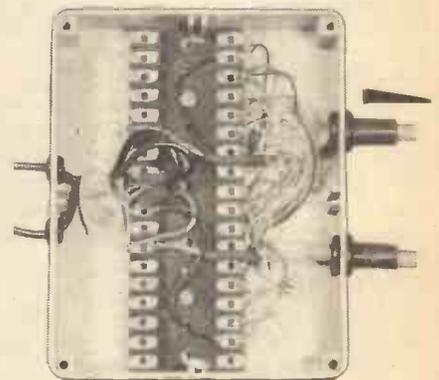The input transformer core is the FX2240, a 25mm core.



Internal view of the aerial case

The primary, 5 turns of 34 s.w.g. enamelled copper wire, is wound on the bobbin first. The secondary windings, 500 turns of 35 s.w.g. are then wound on top of the primary. Although this is well below the manufacturers' quoted minimum number of turns to fill the bobbin, care should be taken in winding to keep the turns tight, otherwise there may not be room.

Inductors L1 and L2 are identical. They consist of 230

COMPONENTS . . .

Resistors

R1*	1M
R2*, R9, R12, R13, R14	1k (5 off)
R3*	2k7
R4*, R6*	680 (2 off)
R5*	330
R7	220
R8	240
R10, R11, R16	10k (3 off)
R15	4k7

* These resistors should preferably be metal film or thick film.

Capacitors

C1	150p
C2	10n
C3	1 μ
C4	10 μ elect
C5, C7, C8, C12	100n (4 off)
C6, C17	100 μ elect (2 off)
C9, C11	330n (2 off)
C10	220n
C13, C14	470n tant (2 off)
C15	4n7
C16	3n3

Semiconductors

TR1	2N3821
TR2	BCY71
IC1	CA3140T
IC2	741
IC3	MC3360P

Inductors

L1, L2	17.4mH (see text)
--------	-------------------

Miscellaneous

- VR1, 1M log.
- T1, transformer (see text)
- S1, double pole changeover switch
- S2, S3, s.p.s.t. switch (2 off)
- JK1, $\frac{1}{4}$ in. jack socket (see text)
- Output socket to tape recorder
- Battery clips for PP7 battery
- Battery clips for PP3 battery (2 off)
- Tagboard
- 2 diecast boxes
- 5m 15-core screened cable
- 4m co-axial cable
- Co-ax plugs and sockets (2 off of each)
- Grommets

turns of 36 s.w.g. enamelled copper wire in an LA1226 18 mm pot core. Again, be sure to keep the turns tight.

The use of metal film resistors for the input stage (R1 to R6) is recommended, since these have better noise characteristics than other types. This is particularly important for the input resistor, R1. All the components in fact should be of high quality, in the interests of low noise.

If stereo headphones are to be used with the receiver, then a stereo headphone jack socket may be used. It should be made of plastic so that all the contacts are isolated from the case and wired up as shown in Fig. 6. This will put the two drive elements in series, since the output stage should not drive a load of less than 15 ohms.

TESTING AND USE

There is no setting up to be done. As an initial test, plug in a pair of headphones, and connect a short length of cable between the input sockets (or short out the primary winding of the transformer internally) and switch on. Noise from the input stage should be clearly audible. Without the short across the transformer oscillation may occur, but it is

unnecessary to try it! If oscillation occurs with the transformer shorted out, then positive feedback is to blame. Try reducing the gain control, switching off the internal amplifier and monitoring through an external amplifier, changing the layout or searching for an electrical fault.

If all is well, try the aerial. The best orientation for this is in the vertical plane; a light framework which will enable it to rotate about a vertical axis is advised, as this will enable interference sources to be nulled out. Plug the two coax cables from the aerial into the input sockets, switch the filter out of the circuit, set the gain to the lowest setting, and again switch on. It is more than likely, unless the hour


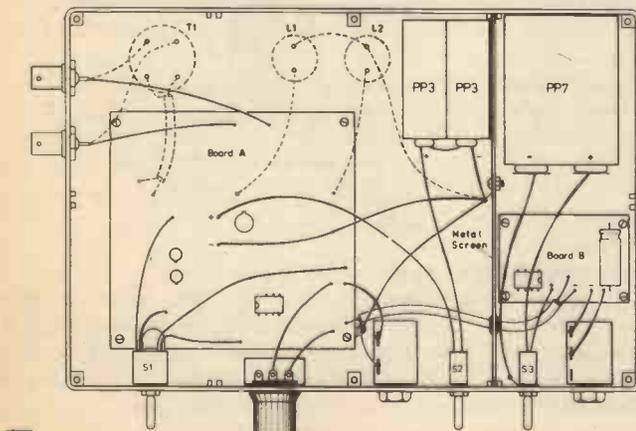


Fig. 12. Assembly of the receiver

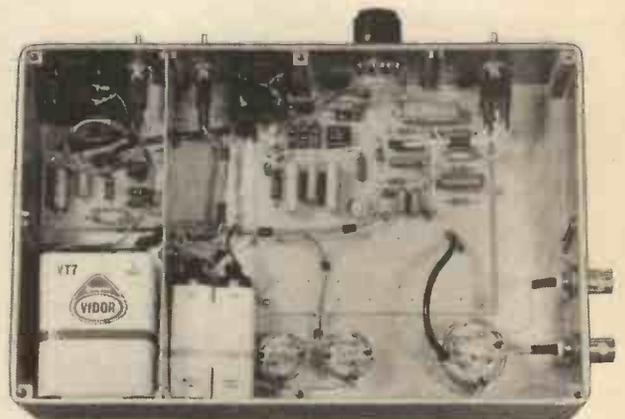

is late, that all that will be heard is a loud hum from mains or TV pickup. Check that the filter reduces this. You would be well advised now to wait until fairly late in the evening, or of course to drive out to a remote site in the countryside.

In the meantime, the frequency response of the input stage of the receiver and the passive filter are shown in Fig. 13. Notice that the response is peaked near 1kHz, falling off by about 10dB at 10kHz. The relevance of this will become clear when the receiver is finally switched on once

the interference has reached acceptable levels, for one of the most distinctive signals which may be heard are the Omega transmissions near 10kHz. These are a series of tones, of length one second each, which repeat at 10 second intervals.

The aerial should be rotated so that the best interference compromise is reached. This operation can be quite tricky, since it will rapidly become apparent that the receiving system is quite capable of picking up signals radiated from the drive coils in the headphones, giving rise to unpleasant howls of positive feedback. Perhaps the best idea is to push the aerial around with a long stick! It is, incidentally, possible to pick up signals radiated from loudspeaker coils at some distance, even though their design should minimise such radiation. Furthermore, the receiver is microphonic; slight taps on the case will be readily audible, since they cause the transformer to vibrate.


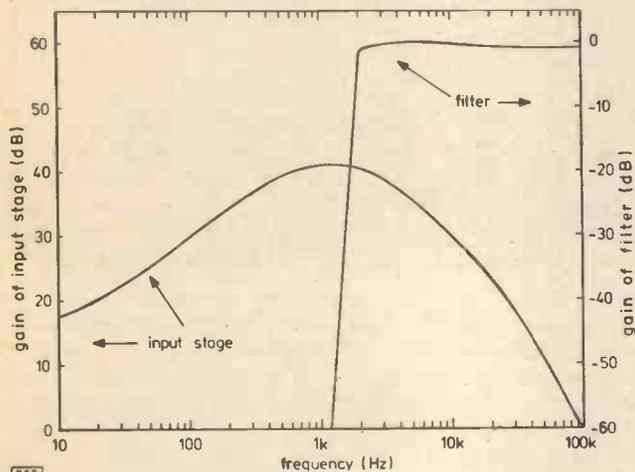


Fig. 13. Frequency response of the input stage and the passive high-pass filter

The signals which may be received have been described before, but a few words on their rate of occurrence in the UK would be in order. Sferics will almost always be heard, since lightning discharges from such an enormous area are being detected; and the virtually continuous nature of the crackling gives a vivid impression of the size of this area. They are, however, more frequent in the summer, and at this time will often limit the lowest intensity of whistler which may be detected.

Tweaks may be expected once or twice a minute, when there are many sferics, though this figure is variable and they are often not present at all.

Whistler rates depend on a number of factors. The geomagnetic latitude of the UK is favourable for whistler occurrence, but there are temporal factors. Whistlers tend to occur in groups lasting $\frac{1}{2}$ hour to about $2\frac{1}{2}$ hours; they tend to occur between the hours of midnight and dawn, and they are more common in winter than summer. The blanketing effect of sferics partially accounts for this seasonal effect, though seasonal variations in thunderstorm occur-

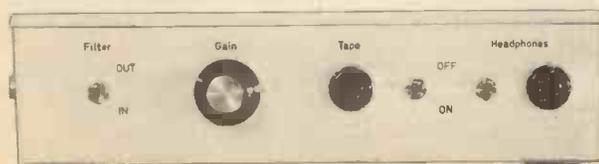

Front panel annotation

rence are also important. An average rate in the UK, over a year, is about one or two whistlers per minute.

Chorus, hiss and discrete emissions are rather more rare, since they tend to be higher latitude phenomena. They can be received in our latitudes, however, and they contribute much to the interest of listening to the strange sounds of natural VLF signals.

SIGNAL LEVELS

The signal strengths of whistlers vary greatly, and extend down to the background noise level. This is determined, in the absence of man-made interference, and at our latitudes, by sferics. In the winter the steady background of distant sferics has a field strength of about $20\mu\text{V/m}$, while in the summer numerous sferics from relatively nearby thunderstorms raise this to 200 to $700\mu\text{V/m}$. The upper limit of whistler signal strengths is a few mV/m .

The voltages these signals produce in the prototype aerial are approximately:

winter background noise:	$0.01\mu\text{V}$
summer background noise:	up to $0.5\mu\text{V}$
whistlers:	anything up to about $2\mu\text{V}$

TABLE 1

Now the random motions of the electrons in conductors give rise to noise, called Johnson noise, or thermal noise. The Johnson noise generated in the aerial is, for our 10kHz bandwidth, about $0.06\mu\text{V}$. Clearly, therefore, this defines the lowest signal we may detect (given a perfect receiver), and is higher than the background noise in the winter. Increasing the size of the aerial and/or reducing its d.c. resistance would improve this performance limitation, but the prototype aerial was considered to be a satisfactory compromise.

The input transformer, with its turns ratio of 100 brings these signals up to the following levels at the input to the receiver:

winter background:	$1\mu\text{V}$
summer background:	up to $50\mu\text{V}$
whistlers:	up to 0.2mV
Johnson noise in aerial:	$6\mu\text{V}$

TABLE 2

The noise generated in the receiver is equivalent to an input noise voltage of about $3\mu\text{V}$; this is not the best that can be achieved, but it ensures that the sensitivity of the receiving system is defined solely by the sensitivity of the aerial.

Incidentally, if you are wondering about the Johnson noise generated in R1; the noise generated by an open circuit 1M resistor is about $12\mu\text{V}$ under our conditions. However, R1 is effectively in parallel with the d.c. resistance of the secondary winding of T1, and the Johnson noise of this combination is negligible.

FURTHER READING

The definitive book on natural VLF signals is *Whistlers and Related Ionospheric Phenomena*, by R. A. Helliwell, published by Stanford University Press in 1965. Though this book has some fairly technical sections, it contains a fascinating atlas of natural VLF signals. Since it is the standard work in the field, most libraries should be able to obtain it. ★



MORE ABOUT JUPITER

The exploration of space is proceeding at such a pace that it seems to produce almost daily updating of information. The data on Jupiter is in such quantity that it is rather like zooming in on the planet with the result that detail is ever increasing. Pioneer 10 and Pioneer 11 added a new vista to the horizon and changed some of the old ideas yet also confirming that at least the thinking was in the right direction. Now Voyager 1 and Voyager 2 have added their astounding contribution. At the passage of the Pioneer 10 and 11 spacecraft much was learned about the magnetic field and other parameters. Voyager 1 and Voyager 2 have already transformed ideas of the atmosphere of the planet. For example Voyager 1 resolved the question of the coloured bands and the various changing spots particularly the Great Red Spot. Voyager 1 showed that the bands were caused by the effect of the high axial rotation speed of the planet. The action appears to be, that as the tops of clouds appear above the bulk of the atmosphere, they are immediately elongated along the main atmospheric surface. The reason, so simple that it should have been recognised before, for rapid rotation of the planet on its axis offered a clue. This rotation period is a few minutes less than 10 hours. The diameter of Jupiter is 142,700km at the equator (88,700m) this gives a figure of some 27,000 m.p.h. for the peripheral boundary of the atmosphere and the emerging clouds.

It is easy to accept that the spots are the constantly changing energy dissipation of the variable density clouds. During the period of four months that elapsed between the flypast of Voyager 1 and that of Voyager 2 considerable permanent changes appeared in the appearance of the area around the Red Spot (incidentally the so called Red Spot is a pale pink) also some of the first conclusions were the subject of some re-thinking. In the past, before the probes, there were a number of theories about the Red Spot.

One in particular was that of the 'Taylor' column. It was suggested that the Red Spot was the top of a supporting column of gas formed by dynamic wave conditions within the atmosphere of the planet. The first pass by Voyager 1 disposed of this and of all the previous thoughts because it appeared that in fact the Red Spot was an enormous cyclone type of activity some 21km in length east to west. This area between the pass of Voyager 1 and Voyager 2 four months later showed many changes including a reversal of movement of the peripheral activities. In the light of some of these findings there is a leaning again toward the idea of a more extensive connection with the lower atmosphere of the planet. The 'Taylor' column becomes again a possible. From the many thousands of drawings made by amateurs, particularly those of Jupiter Section of the British Astronomical Association, for the last 80 years or more, some useful correlation could be obtained. The requirement is for noticeable changes of the features over periods which could be correlated with photographs and their extensive detail.

While the drawings will give general shapes and outlines, those shapes will be easily interpreted in terms of the photographs. Cyclic changes whether from the immediate area of the planet or whether from solar effects would be visible. Observationally in spite of difficulties an enormous amount of data is available and even if the drawings are but 50 per cent accurate there is much to be gained. Indeed it could well be that this is a time when the efforts of amateurs throughout the world could be enlisted. There is no reason why sets of coded photographs should not be available for this purpose. Reference to the book *The Planet Jupiter* by Bertram M. Peak published in 1958, an outstanding classic in the literature by a former Director of the Jupiter Section of the BAA who personally observed directly over a period of 25 years, is very rewarding.

INTERESTING IO

The complication of the innermost satellites are of great interest especially Io. When the decametre radiations were first noted by Burke and Franklyn in America during 1955 a new wave of interest in the world of radio astronomy arose. Though only a small number of people took part in these activities (the writer included) the first ideas were that these radiations came from certain spots of the surface of the planet. A period of rotation was assigned which was slightly different from the axial rotation. Three areas were designated as being the origin. Beyond recognising these radiations no conclusions were really possible. As a participant in a National Aeronautics Space Agency contract the writer did not subscribe to the view that the radiations came from the planet but postulated a mechanism involving some sort of link with an ionised condition. This subsequently proved to be the case. It was put forward by Bigg an Australian meteorologist in 1964 that Io was responsible for a mechanism. This proved to be partly true as was found during a study in 1965 and 1966. In the meantime a link by current sheet or ionised bridge was put forward (by several of us) in relation to Io as an explanation. Pioneer 10 and 11 gave rather negative results

in this respect. However it has been now established by the Voyager missions that there is a torus of ionised material out at the orbit of Io. One other possibility is that Amalthea has some effect and more so now that it is known to be an elongated body whose axial rotation if any has not been established. It could be a possible trigger for the aurorae that has been observed.


The finding of a ring of small particles is of special interest. Like that of Uranus the ring is much more tenuous and does not extend as far out as those of Saturn. Its appearance to probes is not perhaps surprising because Jupiter is itself so bright that the possibility of actually seeing it from Earth is very remote even if an eclipsing disk was used in the telescope. The particles are so small that they may well be primordial dust or this is another activity of Jupiter in cleaning up the debris of the solar system.

GALILEAN SATELLITES

The satellites, that is the Galilean satellites, seem to have a special individuality. Io is volcanic and in continuous activity and is unique in the solar system. Many years were spent in the observation of Io by optical astronomers from Earth based instruments but no clue about any activity was ever seen. Not until the probes came did knowledge of the satellites become possible. It is being suggested that the volcanic activity is perhaps less than a million years old. The reason for this being the case is not clear. A suggestion that the pull of the planet Jupiter as opposed to the two Galilean satellites Europa and Ganymede may account for the heating of Io. However it is not 'hot' in the sense of that of the Earth's interior. The 'hot spot' on Io is a mere 20 degrees compared with the -140 degrees of its surface. There are therefore no signs of molten material around its craters. Europa was a puzzle until the probes went by. It was found that Europa is also unique for it is 'bald'. It is probably composed mainly of ice, very thick, perhaps as much as 100km. Voyager 1 has shown that the surface is probably slushy ice so the surface changes are obliterated from the viewpoint of the probe. Ganymede the third of the Galilean satellites is different again from the others. It appears to be mostly water. It has a low density. There are abrupt divisions between the types of surface. Some areas are very dark and heavily cratered while others appear to be lighter and perhaps made up of ice in ridges. The state of the cratering suggests that this satellite is about the age of the Earth. Finally the fourth of the Galilean group and the outermost is Callisto.

This body is the most cratered body so far observed in the Solar System. The surface is so cratered that it will take 20 years to count them up. It would seem that this moon also is made up largely of water and belongs to the early period of 4000 million years. The observations of Jupiter have gone on for some 11 months and the amount of data to be analysed is formidable and while the probes go on their way to Saturn the first real work on the Jupiter results will begin. The exciting beginning can only result in the re-shaping of many current ideas.

The hobby electronics show

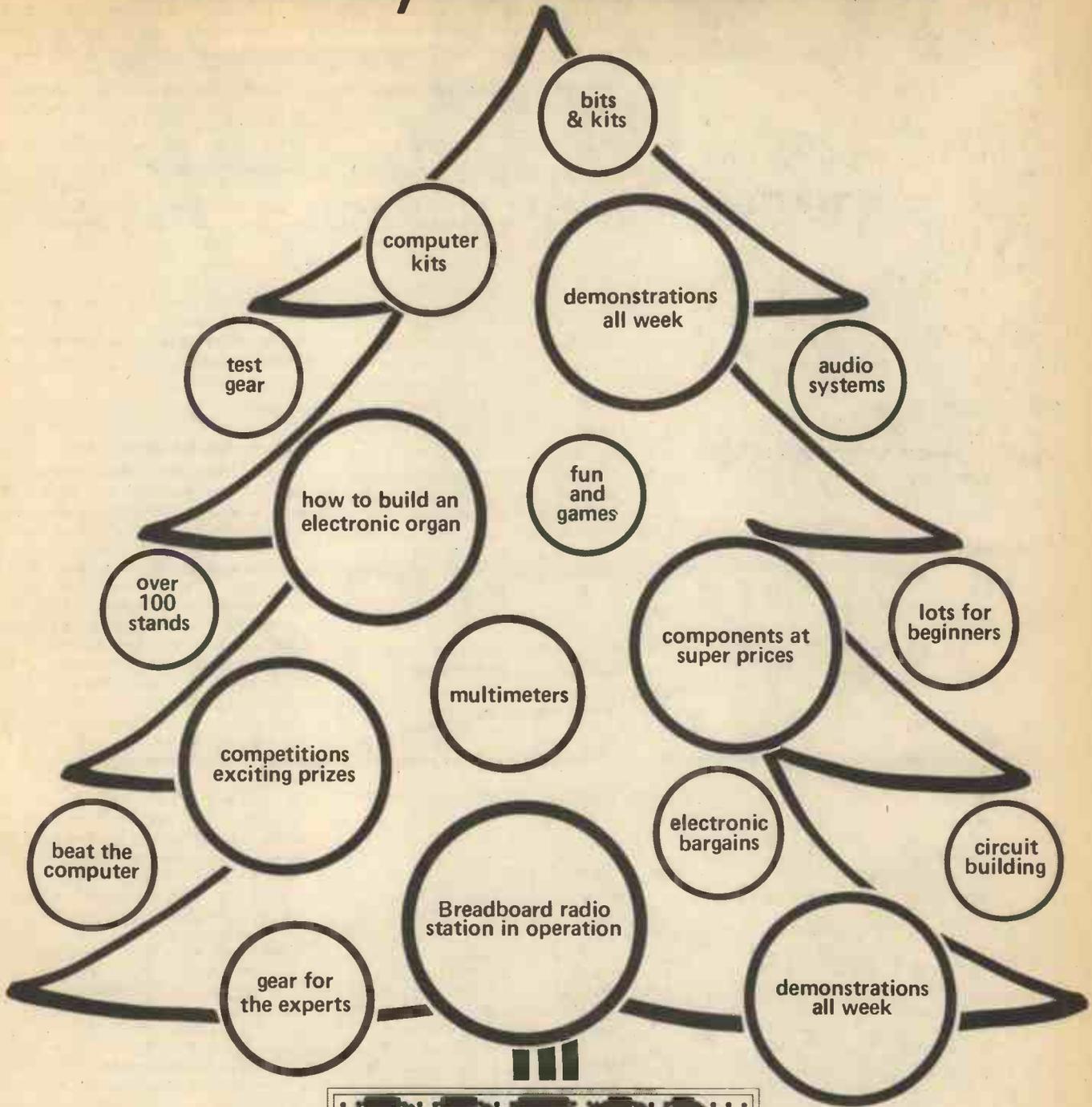

**BREAD
BOARD**

December 4-8th
1979

Admission £1
(students 70p)

1979

Royal Horticultural Halls
Elverton Street
Westminster SW1

6 CHANNEL MIXER

S.R.W. Grainger & C.R. Harding Part 2

In this final part board construction together with interwiring and final setting up will be detailed.

CONSTRUCTION

For the prototype printed circuit boards were used on the input channel amplifiers, this method was adopted because of the need to reproduce six identical circuits. However there is no reason why Veroboard (or similar) could not be used for construction providing dimensions are similar.

This involves the use of a two pole change-over interlocking push button switch system, however this can be replaced by a rotary selector switch as shown in Fig. 1.

All wiring in the mixer should be kept as neat as possible and all low level signal connections should be made with screened cable with the screen connected at one end only (this applies to the wiring of the 1kHz oscillator also). Connections to the bass and treble controls can be made with ordinary unscreened wire, providing the leads are kept

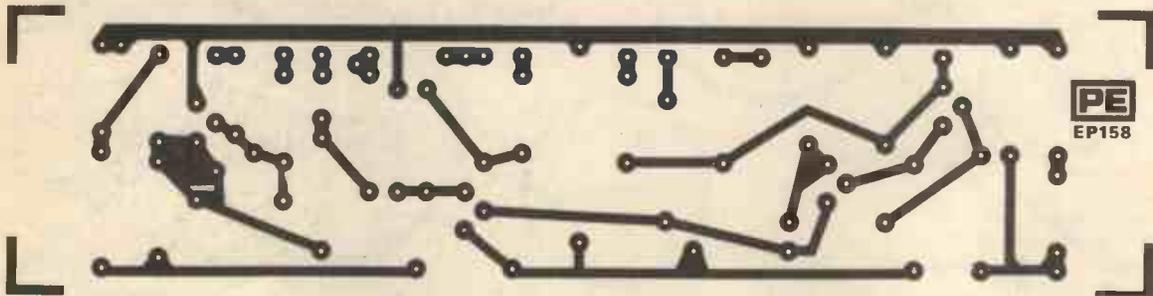


Fig. 10. Input channel amplifiers—six are required

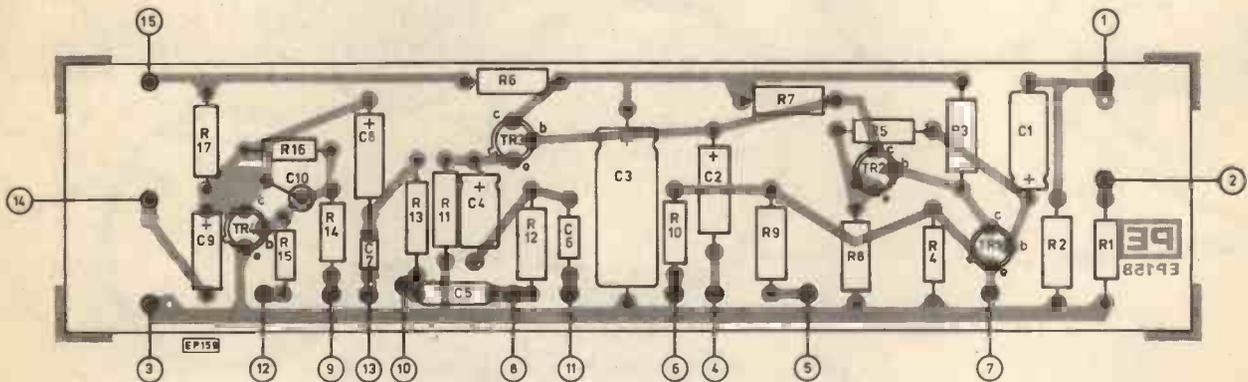


Fig. 11. Component layout for input amplifiers

The p.c.b. and component layout for the input channels is shown actual size in Fig. 10 and Fig. 11.

All the other circuits were constructed on Veroboard of 0.1in. matrix. The headphone amplifiers, output amplifiers, overload indicator, VU meter drive amplifiers and echo send amplifier and test oscillator were all built on one piece of Veroboard. The layout and track cutting diagram for this is given in Fig. 12. The power supply is built on a separate Veroboard as shown in Fig. 13.

The connections for the p.c.b. controls and gain switches on the input channels are shown in Fig. 16. The switching arrangement for pfl function switches is shown in Fig. 15.


short. The transformer and power supply should be mounted as far away from the input channel boards as possible.

The input channel boards are mounted on their long edge, which leaves the connection pins accessible. They are held in position by use of a piece of slotted plastic which is sprung, the springs being attached to two pots by solder tags (or brackets).

The output boards can be mounted on the base panel of the mixer and wires run from the miniature looms bound with "Spirowrap" or similar.

A control panel cut-out guide is shown in Fig. 14. The control panel was made from 14 s.w.g aluminium which

Fig. 12. Main board that includes headphone amplifiers, output amplifiers, overload indicator, VU meter amplifier and test oscillator. This should be attached to the bottom panel as shown in the prototype layout in Part 1

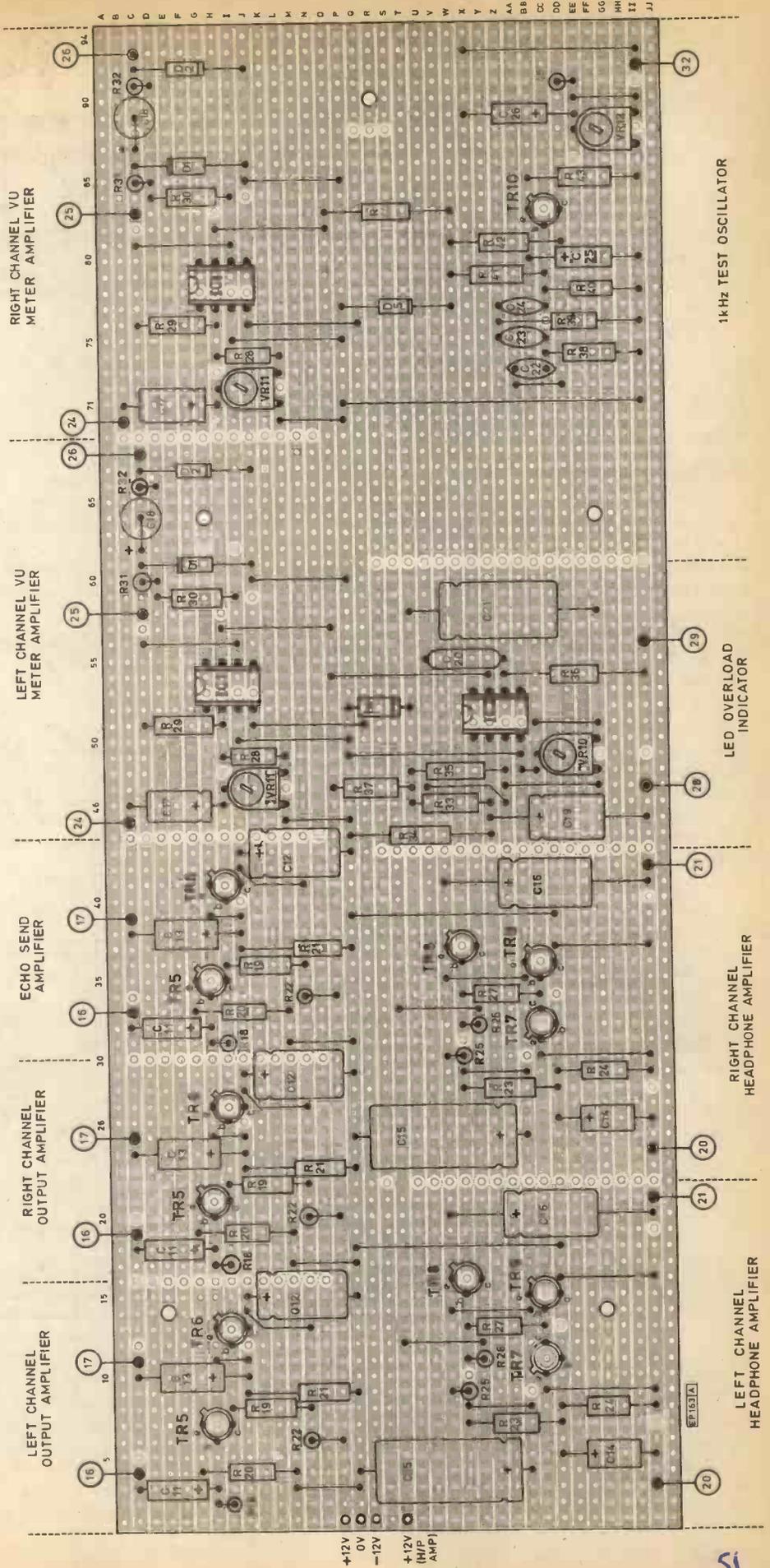

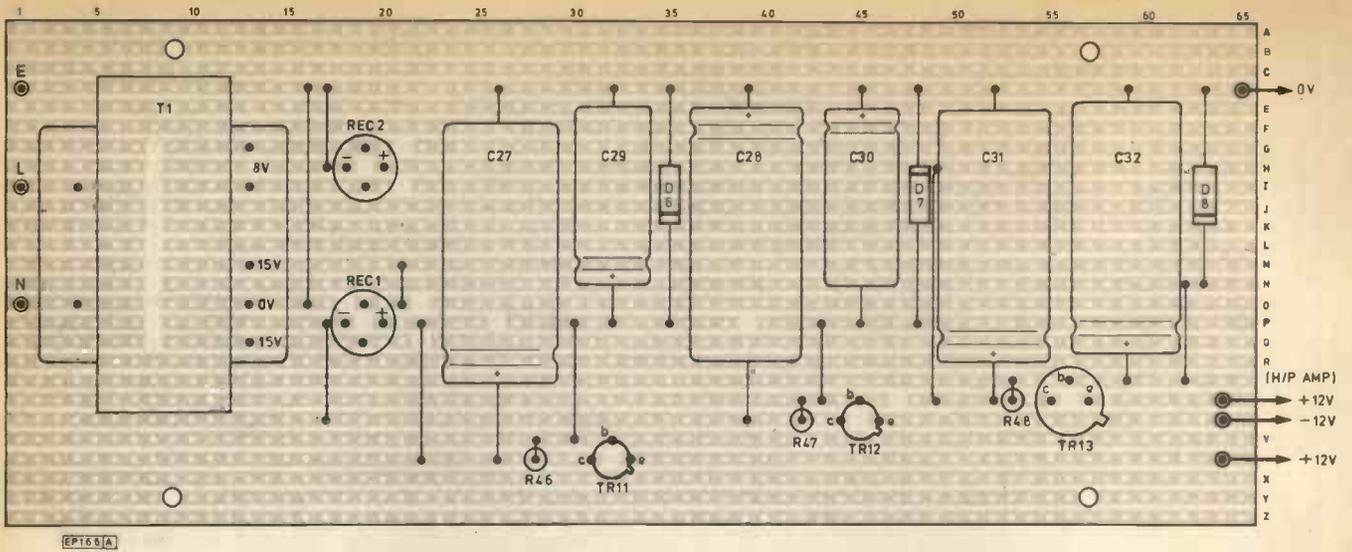


Fig. 13. P.s.u. board

provides adequate support and is easy to drill and file. Some hole sizes are omitted as these are to suit parts which are available to the constructor. These panel cut dimensions will need to be larger if slider pots are used on the input channel faders. The front was sprayed black (matt) and lettered with Letraset or similar and then given several coats of protective lacquer.

No details are given of the front and back panel drilling details, as these are to suit the input and output sockets used by the constructor. The front and back panels were made from 12 s.w.g. aluminium and attached to the side panels ($\frac{1}{2}$ in. solid teak) by $\frac{1}{2}$ in. angled aluminium.

A colour coding was adopted for the control knobs as follows:

- | | |
|---------------------------------|----------|
| Impedance and gain selector | — white |
| Pan control | — yellow |
| Bass control | — blue |
| Treble control | — red |
| Input channel echo send control | — green |
| Echo send master control | — black |
| Echo return master control | — black |
| Headphone volume control | — black |

These knobs were black with coloured inserts and for a contrast the channel faders used a different style of knobs, and the slider pots used the most readily available knobs.

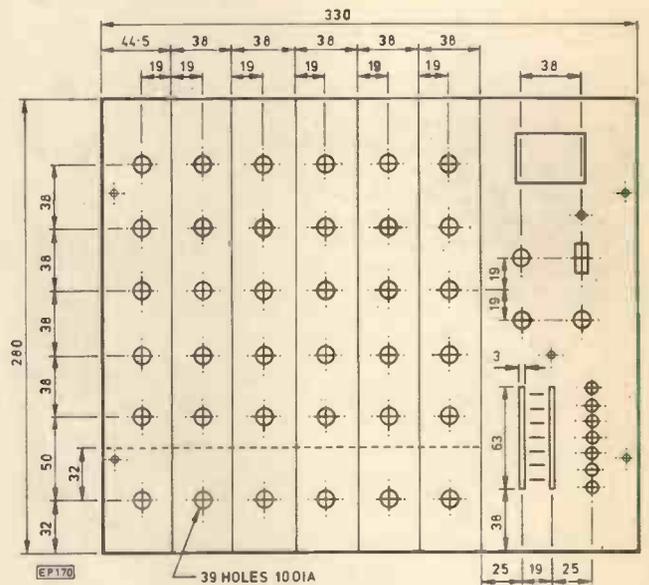


Fig. 14. Panel cut-out guide

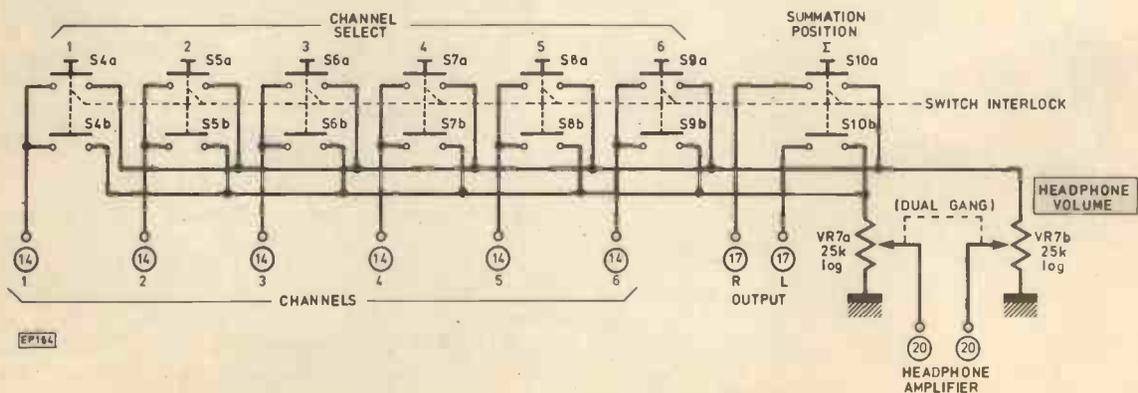


Fig. 15. Circuit for p.f.i. interlocking push switches


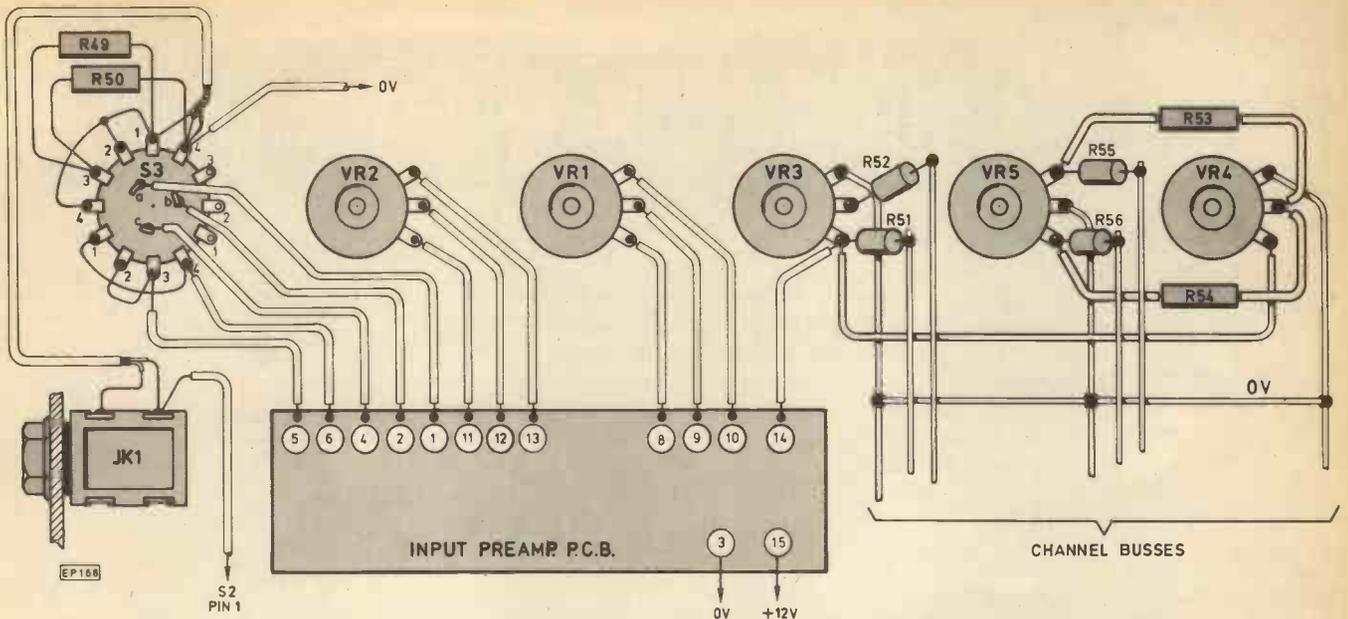


Fig. 16. Single channel control wiring to input amplifier

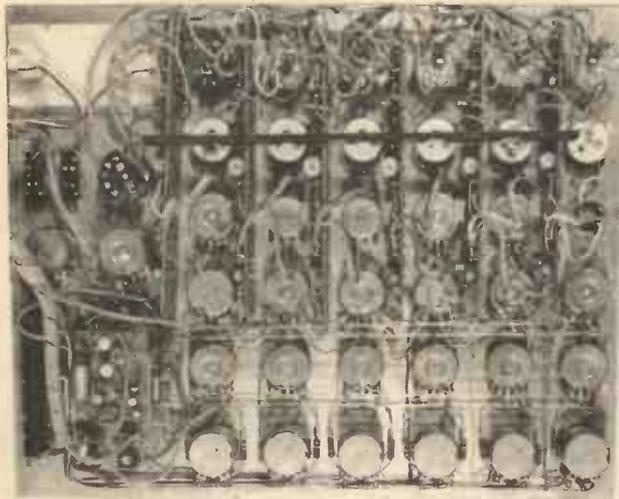

(Above) Prototype control panel layout. In the modified design the limiter switch is excluded. (Below) Headphone outlet is on the front panel with inputs to the rear

SETTING UP

1 KHz oscillator

The only adjustment required on this is that the output level on pin 32 should be set to 10mV. This should be done using an a.c. millivoltmeter or an oscilloscope, by adjustment of VR12. If an oscilloscope is available the shape of the sine wave can be seen, and should be observed to be fairly pure (distortion less than 10 per cent).

L.e.d. overload indicator

To set this circuit up an a.c. signal of 12mV peak-to-peak should be applied to one of the input amplifiers. The gain of this amplifier should then be set to 100 (using S3) and the output should measure 1.2V peak-to-peak, if this is not the case adjust the input signal level until it does. The preset pot on the overload indicator (VR10) should then be adjusted so that the l.e.d. just lights. This calibration will then suffice for all input channels.

VU meters

To calibrate these a signal from the 1kHz oscillator should be applied to one of the input channels via test selector switch and the gain adjusted to 100 and impedance 50 kilohms. The pan control on that channel should then be moved fully over to the left and the left master fader should be adjusted until the left output reads 1V r.m.s. on an a.c. millivoltmeter or oscilloscope. The calibration pot (VR11) on the VU meter amp should then be adjusted so that the meter reads 0dB. The procedure is then carried out for the right hand channel but with the pan pot fully over to the right.

All circuits should function first time in the mixer, with wide component tolerances, unless there has been a component failure or a mistake in the wiring. Care should be taken to select the correct input impedance and sensitivity (600 ohm input impedance is useful when using long microphone cables) but any overload of signal should be indicated by the overload indicator. The headphone monitoring facility provides useful quiet listening but can be routed to an external amplifier and speakers via an attenuator.





Associated Commodore dealers:

BIRMINGHAM
Camden Electronics 021-773 8240
CPS (Data Systems) 021-707 3866
Taylor Wilson Systems Knowle 6192

BOLTON
B & B Consultants 0204-26644

BOURNEMOUTH
Stage One Computers 0202-23570

BRADFORD
Ackroyd Typewriter & Adding Machine Co 0274-31835

BRENTWOOD
Direct Data Marketing 0277-229379

BRISTOL
Bristol Computer Centre 0272-23430
Sumlock Tabdown 0272-26685

CAMBRIDGE
Cambridge Computer Store 0223-68155

CARDIFF
Sigma Systems 0222-21515

COLCHESTER
Dataview 0206-78811

DERBY
Davidson Richards 0332-366803

DURHAM
Dyson Instruments 0385-66937

EDINBURGH
Micro Centre 031-225 2022

EXETER
A. C. Systems 0392-71718

GRIMSBY
Allen Computers 0472-40568

HEMEL HEMPSTEAD
Data Efficiency 0442-57137

HOVE
Amplicon Electronics 0273-720716

LEEDS
Holdene 0532-459459

LIVERPOOL
Aughton Automation 051-548 6060
Cortex Computer 051-263 5783
Dams Office Equip. 051-227 3301

LONDON E2
Ragnarok Elec Sys 01-981 2748

LONDON EC1
Sumlock Bondain 01-253 2447

LONDON N14
Micro Computation 01-882 5104

LONDON NW4
Da Vinci Computers 01-202 9630

LONDON SW14
Micro Computer Centre 01-876 6609

LONDON W5
Adda Computers 01-579 5845

LONDON WC1
Euro Calc 01-405 3113

LONDON WC2
TLC World Trading 01-839 3893

MANCHESTER
Cytek (UK) 061-832 7604
Executive Reprographic 061-228 1637
Sumlock Elec Svs 061-834 4233

MATLOCK
Lowe Electronics 0629-2817

MORLEY W. Yorks
Yorkshire Elec Svs 0532-522181

NORWICH
Sumlock Bondain 0603-26259

NOTTINGHAM
Betos (Systems) 0602-48106

OXFORD
Orchard Electronics 0491-35529

PLYMOUTH
JAD Integrated Svs 0752-62616

PRESTON
Preston Computer Ctr 0772-57684

READING
CSE Computers 0734-61492

SOUTHAMPTON
Business Electronics 0703-738248
Symtec 0703-37731
Xitan Systems 0703-38740

SUNDERLAND
Tripont Ass Systems 0783-73310

WOKING
P.P.M. Brookwood 80111
Petalect 04862-69032

YEOVIL
Computerbits 0935-26522

NORTH SCOTLAND
Thistle Computers Kirkwall 3140

NORTHERN IRELAND
Medical & Scientific Lisburn 77533

A computer range from £500

The number one micro-computer in Britain today, selling more than 1,000 per month!

The Commodore Pet computer range is versatile and affordable. Programs can be written in Basic, the easiest computer language to learn. There is also machine language accessibility for professionals.

The Pet is a fully expandable system, peripherals being available for many specialist applications, (peripherals such as dual drive floppy discs and printers).

There are already over 300 standard programs,

tested and in use in commercial, scientific, educational and many other applications throughout Britain. The Pet is a portable and professional computer that operates by plugging into a normal 13 amp mains. Service and advice is readily available through the nationwide network of dealer outlets.

For a demonstration contact your local dealer—some of whom are shown here. In case of difficulty contact

Consumer Information Dept (PE),
Commodore Systems,
360 Euston Road,
London NW1.



commodore
We made small computers big business.

COMPUKIT UK 101

SINGLE BOARD COMPUTER

PART 3 A.A. BERK B.Sc. Ph.D.



ERROR CODES

IF DURING the execution of a program, the computer encounters a word it does not understand, or is asked to perform an impossible calculation, it *may* detect an error of a recognisable type and so inform the user. Some errors are undetectable and simply produce wrong answers or bizarre behaviour. If it does recognise a *standard* error, it will print up one of the standard error codes listed in the table.

This *self-checking* activity makes computer programs easier to debug, but there are pitfalls, because sometimes, though an error of a particular type has been flagged, it may be the consequence of a more subtle error elsewhere in the program. Experience is the only answer!

Table 3.1. ERROR CODES

Code	Definition
O /	Double dimension: variable dimensioned twice. Remember subscripted variables default to Dim. 10.
F /	Function call error: parameter passed to function out of range.
I /	Illegal direct: INPUT cannot be used in immediate mode.
N \	NEXT without FOR.
O /	Out of data: more READs than DATA.
O 7	Out of memory: program too big or too many nested GOSUBs, FOR NEXT loops or variables.
O ⚡	Overflow: result of calculation too large for BASIC.
S J	Syntax error: typing mistakes etc.
R \	RETURN without GOSUB.
U ✓	Undefined statement: attempt to jump to non-existent line-number.
/ Δ	Division by zero.
C J	CONTINUE errors: inappropriate attempt to CONT after BREAK or STOP.
L ✓	LONG string: string longer than 255 characters.
O ✓	Out of string space: same as O7.
S S	String temporaries: string expression too complex.
T 7	Type mismatch: string variable mismatched to numeric variable.
U \	Undefined function.

EDITING

The program may be edited by writing further lines or rewriting existing ones.

Try typing the following (to be added to last program):

15 PRINT "BYE"

Typing LIST will insert this new statement between lines 10 and 20. Similarly, typing:

10 PRINT "THIS"

will *overwrite* line 10. Typing 10 followed only by RETURN will simply wipe out line 10 altogether. If a mistake is made in typing a character, it may be deleted by pressing the RUB OUT key, which if pressed several times will delete that number of previous characters. Try the following correction:

PRINT "HELLL (press RUB OUT) O"

The third L will be deleted and the VDU will show:

HELLO

The entire current line being typed may be deleted *before* RETURN is pressed, by pressing (SHIFT) P, which displays an @ sign and places the cursor on the next line to await further instructions.

USE OF CASSETTE

Check that pin 10 of J2 is connected to the earphone output, and pin 9 (or 7) to the auxiliary or microphone input, and pin 8 and/or 11 to the Earth of the cassette machine. Any ordinary cassette recorder should be suitable, but the very cheapest cassette *tapes* are prone to giving continual errors. The best volume setting is found by trial and error for playback. Recording may be on automatic level or manual. A machine having a tape counter is preferable.

PLAYING BACK A PROGRAM

(a) Rewind tape to "leader" or blank area before program starts.

(b) Place computer in command mode and type NEW (and RETURN).

(c) Type LOAD but *do not* press RETURN, to avoid spurious "noise" being interpreted as data and loaded to the computer.

(d) Switch recorder to PLAY.

(e) Wait for a second or two—or for the "leader" to pass through, then press RETURN.

Some random noise characters may still be printed on the screen, and if one of these is a number, it could be interpreted as a program line. However, without this unlikely event the program is printed on the screen line by line. When playback is complete, pressing SPACE and then RETURN returns the machine to BASIC and the new program is resident for listing or running.

RECORDING A PROGRAM

This assumes a BASIC program is stored in the Computer ready for saving on cassette.

- (a) Rewind tape to blank noise-free portion of tape.
- (b) Type SAVE (RETURN).
- (c) Type LIST but do not RETURN.
- (d) Switch cassette to RECORD and allow "leader" to pass, plus a further 5 seconds to allow settling to constant speed, then press RETURN. The program will list on the screen as it is being recorded.
- (e) When recording is complete, wait a few seconds, turn off tape recorder and type LOAD (press RETURN), then press SPACE and RETURN.

USING THE MACHINE IN BASIC

After
OK

appears, the machine is said to be in the Command Mode. At this point, two types of data may be entered, *always terminated by pressing RETURN*.

- (i) COMMANDS
- (ii) BASIC Statements

These are described below:

N.B.

Spaces are always ignored in Commands and BASIC Statements (except in *literals* and *string* arguments).

If you make a typing error, press RUB OUT.

(1) COMMANDS

CLEAR This causes all variables (numeric or string) to be set to zero (or null)

LIST This can be used in several forms as detailed below:

LIST Causes the whole stored BASIC program to be listed line by line until either the listing is complete or CONTROL C is pressed.

LIST n Will list that line only

LIST n- Will list all lines from n to the end of the program

LIST -n Will list all lines up to n

LIST n-m Will list from line n to line m. This allows any part of a program to be viewed at will

NULL n Inserts n null before sending data to serial I/O devices

RUN Starts program execution from the first line with all variables cleared

RUN n As above but starts program at line n

NEW Wipes out current program

CONT Continues execution of program after Control C, or after a STOP statement encountered within the program

LOAD
SAVE } Cassette commands dealt with elsewhere

CONTROL C

This is effected by pressing the "CTRL" key, and (with CTRL pressed) typing a "C". It suspends Computer activity and prints a message to give the line number at which the break occurred. The Computer then returns to COMMAND MODE. Many BASIC Statements may also be used as commands if unaccompanied by a line number—for instance:

GOTO n

would cause the Computer to begin executing from line number n without clearing all the variables. Similarly, many of the above may be used in programs—thereby causing a program to command the machine.

(ii) BASIC Statements

There are two modes of use of the BASIC language when using an *interpreter* such as this. These will be called:

- (a) Immediate Mode
- (b) File Mode.

IMMEDIATE MODE

If a BASIC statement is typed while in the Command mode, it is executed immediately a RETURN is encountered, and lost after execution. In this mode the Compukit, with its fast powerful floating-point calculation ability is able to act as a super calculator. For instance, answers to such calculations as:

$$X = \frac{15.7 \times 13^{\sin(0.781)}}{87 \times 10^4}$$

are found immediately. In this case, the user would type:

PRINT 15.7 * 13 ↑ SIN (0.781)/87E4

to get the answer:

1.09796E-04

The immediate-mode use of the machine allows instant indication of remaining program space, by typing:

PRINT FRE (N)

The answer (after RESET) on an 8K machine should be 7420.

An important use of this mode is for program debugging. The last values of the variables are retained when a program stops. Type:

PRINT A, B, C, etc.

where A, B, C are the variables whose values are required. Quite complex immediate-mode programming may be written by employing colons to separate the various statements. In order to write and *retain* a program, the File Mode must be employed.

FILE MODE

To retain a program line for *later* execution, a line number must precede the instructions.

This numbered program line must not be confused with a display line. The computer accepts a maximum of 71 characters on a program line, and depending upon the Terminal Width set up after a system reset, the program line may occupy up to around four and a half lines of VDU display (if terminal width is 16).

Table 3.2. COMPUKIT MEMORY MAP

0000—00FF	Page Zero
0100—01FF	Stack
0130	NMI Vector
01C0	IRQ Vector
0200—0221	BASIC Flags & Vectors
0203	LOAD Flag
0205	SAVE Flag
0218	Input Vector
021A	Output Vector
021C	Control C Check Vector
021E	Load Vector
0220	Save Vector
0222—02FA	Unused
0300 end of RAM	BASIC Workspace
A000—BFFF	BASIC-in-ROM
D000—D3FF	Video RAM
DF00	Polled Keyboard
F000—F001	ACIA Serial Cassette Port
F800—FBFF	ROM
FC00—FCFF	ROM—Floppy Bootstrap
FD00—FDFF	ROM—Polled Keyboard Input Routine
FE00—FEFF	ROM—65V Monitor
FF00—FFFF	ROM—BASIC Support
FFFA	NMI Vector
FFFC	Reset Vector
FFFE	IRQ Vector

MACHINE CODE MONITOR

The machine code monitor program provides a simple but adequate method of loading and running machine code routines, including loading from cassette. To prevent these routines being overwritten by BASIC, MEMORY SIZE? (After RESET) must be answered with a number restricting the BASIC's use of RAM. The number n, thus typed, restricts BASIC according to the following map.

Address in Decimal	Use
0	Page Zero
255	
256	Scratch-pad RAM used by BASIC and system monitor
768	
769	BASIC workspace
n-1	
n	protected against use by BASIC
End of RAM	

It is clear from the above that n must be at least greater than 769. In a 4K machine, the end of RAM occurs at memory location 4095, and 8K finishes at 8191.

After RESET, the machine code monitor is entered by pressing M. The display:

0000 4C

then appears.

The first four characters form the address field, and the second two represent data (all in *hexadecimal* notation). Typing any hex characters at this point will load the address field; the data field is kept constantly updated as the address changes. Mistakes may be corrected by typing further characters, as these will continue to be loaded into the right hand position and then rotated left as further entries are made.

The following commands are available:

- / Changes to data mode to allow data to be loaded. RETURN then opens the next location.
- . Changes back to address mode.
- G (Used after setting up an address with .). This jumps to the address showing on the screen and begins execution.
- L Transfers control to cassette—loading 00FB with 00 transfers control back to the keyboard.

After L, the monitor is in data mode and simply accepts all its commands from cassette instead of the keyboard. Thus the cassette tape must have a series of commands, stored as ASCII codes from BASIC, to control the Monitor. To load a program from cassette, it must be stored byte by byte, separated by RETURNS and ending with:

.00FB/00

This loads 00FB with 00 which is the flag to switch the monitor back to accepting commands from the keyboard. The program can be run from cassette, if desired, by ending with G after setting up the start of the routine in the address field.

The following gives a list of important address locations in the machine code monitor.

Starting address	Effect of jumping to address shown
FE00	Restart location. Ending machine-code programs with a jump to this location has the same effect as pressing M after D/C/W/M?
FE0C	Bypasses UART and Stack Pointer initialisation as well as clearing decimal mode, but still clears screen.
FE43	Enters directly into address mode. Bypasses initialisation and screen clearing.
FE77	As last, but for data mode.

The following are *subroutines* which may be of use in user programs.

Starting address	Effect of jumping to subroutine
FE80	Inputs an ASCII character from the cassette UART.
FE93	Returns stripped ASCII number if 0-9 or A-F otherwise returns FF.
FEED	Inputs an ASCII character from the keyboard.

To test the machine-code monitor, the message program used to illustrate USR (last month) may be adapted as follows.

Place the monitor in address mode either by pressing RESET followed by M, or by pressing *full stop* if already in the monitor. Enter the characters 0500 followed by / to access data. Type in the following pairs of digits—each pair separated by pressing RETURN.

```
A2 00 BD 00 06 C9 5F F0
07 9D E5 D1 E8 18 90 F2
4C 43 FE
```

This ends with a jump to location FE43 which places the monitor in address mode after the message has been displayed, thus preventing the clear screen routine in the monitor from erasing the message immediately after its appearance.

The following pairs of hex digits are ASCII codes for the characters of the message. The list may be of any length but must start at 0600 and end with the pair 5F.

Press *full stop* and the n type 0600 followed by / and the following pairs separated by RETURNS:

```
43 4F 4D 50 55 4B 49 54 5F
```

To run the program, type

.0500G

This will display the message for which the ASCII codes are given above, and leave the machine code monitor in address mode for further use. Memory size need not be specified unless BASIC is to be entered and the above protected against being overwritten.

GRAPHICS

Character resolution graphics are used by the CompuKit whereby 255 different graphic characters are available to fill any given character slot. To view the available characters, the BASIC function CHR\$ may be used by typing, for example:

PRINT CHR\$(24)

followed by pressing RETURN. This causes a £ sign to be

printed. Each number between 1 and 255 inclusive, corresponds to a character, as 24 does to £. (0 corresponds to a null character).

Two of these numbers correspond to *non-printing* commands for the print head (whose position is continuously shown by the cursor).

PRINT CHR\$(10)

causes a line-feed, i.e. the cursor jumps to the next line and the screen scrolls upwards.

PRINT CHR\$(13)

causes a carriage return.

The rest of the numbers correspond to ASCII characters, special characters and graphic characters.

The ASCII characters start at 32 (SPACE) and finish at 127. These are all accessible from the keyboard. The uppercase is set with SHIFT-LOCK down, and lower case with SHIFT-LOCK up.

The other characters are inaccessible from the keyboard directly, and they must be printed using CHR\$(I). These general graphic characters are best seen by writing a program to print them on the screen. This will be given later.

The following is a list of special (as distinct from *graphic*) characters, with their corresponding numbers:

number	character	number	character
0	null	244	δ
10	line-feed	245	ψ
13	carriage-return	246	Ω
24	£	247	μ
32	Space	248	π
179	⇒	249	ε
180	⇐	250	λ
211	✓	251	φ
212	∫	252	β
241	α	253	ε
242	β	254	γ
243	ω	255	χ

In order to select a particular graphic character, a list of those available may be displayed on the screen with corresponding number next to each one. The following program achieves this by allowing the user to specify which block of characters are to be displayed; there are too many to appear at once! The instructions for the program are as follows.

The program is loaded and run. The words:

WHICH BLOCK?

appear. Answer with a number between 1 and 4 inclusive followed by a RETURN. The numbers 1 and 2 display the graphic characters available, 3 shows the special characters already shown, and 4 displays the ASCII set.

To exit the program, just press RETURN instead of a number.

The line numbers chosen for the program put it well above any other program you may be working on. If the program under development ends with an END, then the following program will never be entered by the command RUN, and so RUN 10000 will be necessary. This allows the graphic program to remain in memory as a reference for use as necessary. It will be lost if NEW is typed or if RESET is pressed followed by C.

The Program Listing

(Spaces may be omitted, and PRINT may be typed as ?)

```

10000 INPUT "WHICH BLOCK"; B : B = FL = 0
10010 IF B = 1 THEN S = 1 : F = 31 : GOTO 10060
10020 IF B = 2 THEN S = 128 : F = 219 : GOTO 10070
10030 IF B = 3 THEN S = 220 : F = 255 : GOTO 10060
10040 IF B = 4 THEN S = 32 : F = 127 : GOTO 10070
10050 GOTO 10000
10060 FL = -1
10070 FOR I = S TO F
10080 IF I = 10 OR I = 13 THEN GOTO 10110
10090 PRINT I; CHR$(I); : H = I + 3
10100 IF INT(H/7) = H/7 THEN PRINT : IF FL THEN PRINT
10110 NEXT
10120 PRINT
10130 GOTO 10000
  
```


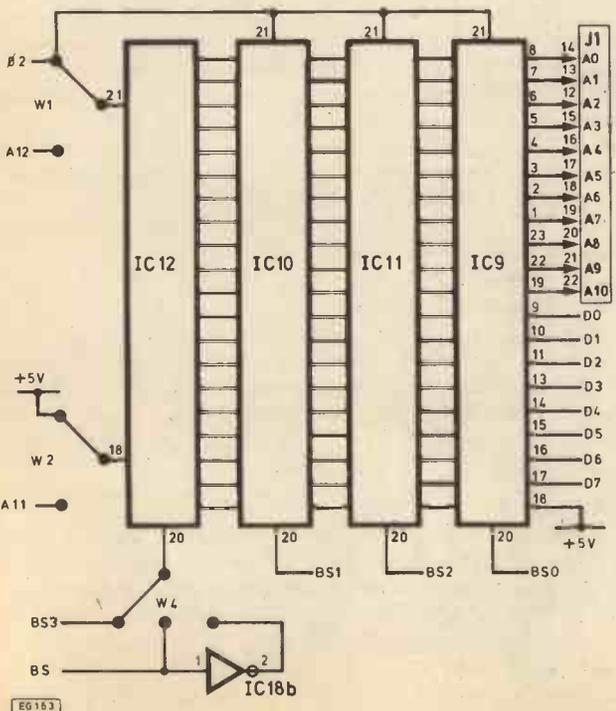


Fig. 3.1 (left). BASIC ROMs

Fig. 3.2 (below). Monitor ROM

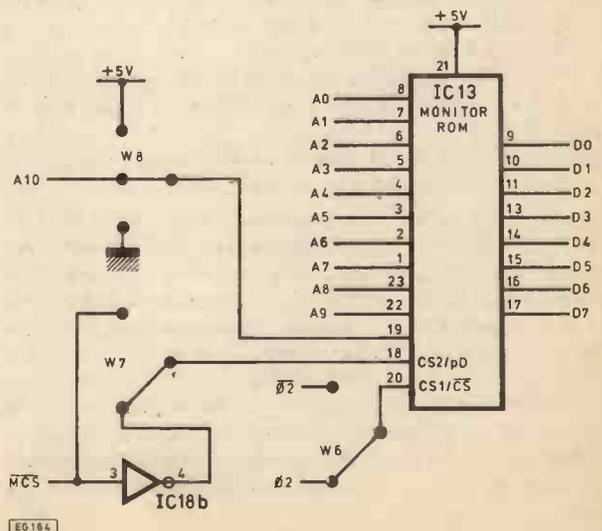

When Block 2 is requested, some of the vertically adjacent symbols run into each other. Use CHR\$ in the immediate mode to inspect individual characters, e.g. :

PRINT CHR\$(161)

reveals that this character fills the entire character slot.

The fact that characters run into each other in this manner allows the user to build up quite complex graphic patterns as well as graphs and bar-charts, etc. The user may find it useful to store the above program on cassette tape for future reference.

HARDWARE—BINARY COUNTING CHAINS

The clocking requirements for the system are supplied by the crystal oscillator and binary counting chains (see Fig. 2.5). Two gates of IC58, plus X1, form an 8MHz oscillator buffered by a further gate in IC58, and divided by 8 (IC29, which has a spare $\div 2$). Before IC29's $\div 8$ function, the CLK line feeds the Dot clock of the VDU with 8MHz. This governs the length of time available for displaying one of the dots of a character on the TV screen. Given the speed with which the electron beam strobos across the screen and the Dot time, the width of a dot may be calculated. A frequency of 8MHz gives a dot size sufficiently small to fit about 48 characters across the screen (each 8 dots wide), while of low enough frequency to pass easily through the UHF modulator and IF stages of a TV set.

The D output of IC29 (at 1MHz) then feeds the ϕ in line of the MPU, the C0 line of the VDU, and the counting chain of 74163's (or 74161's) IC59-61 and IC30. The constraints on the counting chain are that it must produce ripple-count outputs for C1-C6 in between line-sync pulses separated by 64 μ s. Note: $2^6 =$ maximum of 64 characters per line. There must be three outputs (C8-C10) for the row inputs to the character generator, and a further four outputs (C11-C14) for the 16 horizontal lines of characters. The entire picture must then be repeated at 50 times a second with a suitable frame-sync pulse. The final count output from the bottom of the chain is then inverted, and fed to load the chain elements.

Capacitor C3 is used to set the BAUD rate for the Cassette and serial interface via a further counter, IC57, and some decoding logic IC63 and IC58.

THE VDU


The block diagram of Fig. 1.2 shows the basic parts of the VDU and the circuit diagram (Fig. 2.2) gives the details referred to below.

The VDU RAM holds a screen full of characters (1024 in all). Through IC53-IC55 the RAM address lines (VA0-VA9) are either fed from the counter chain, or the MPU Address Bus, depending upon the state of \overline{VA} (VDU Access). When \overline{VA} is at "1", C1-C6 and C11-C14 are connected through to VA0-VA9, and when \overline{VA} is at "0", the MPU busses have direct Read/Write access to the VDU RAM. Reading or writing of data is controlled by the bi-directional buffers IC24 and IC25, which also disconnect the VDU RAM from the MPU Data Bus when the counter chain is supplying addresses to VA0-VA9. Thus when \overline{VA} is in the zero state, the VDU RAM acts just like any other block of Read/Write memory, here based at location address D000 hex. This allows the screen to be read or written to during a program. With \overline{VA} at "1", the ten VDU RAM addresses are derived from the counters sequentially. The RAM is in the READ condition when not selected by the MPU, and the contents of the RAM locations are sent to the character generator for interpretation into bit patterns forming characters on the screen

Each character in the Character Generator (IC41) is stored as an 8 x 8 matrix of white and black dots. White is stored as a "1". The characters appear on the outputs of IC41 (D0-D7) one row at a time, see Fig. 3.3. Here an "E" is being displayed on one of the 16 lines of text on the TV screen. C8, C9 and C10 from the counter chain determine which row (R0-R7) is being output at any time. The sequence of events is as follows: C1-C6, C11-C14 contain an address of a location in VDU RAM and hence of a character on the screen. The contents of this location (8 bits in parallel) are fed to IC41 which then parallel outputs the 1's and 0's (white and black dots) of one row of the character along D7-D0. Here, five 1's and three 0's are output to form the top row of the "E". IC42 serialises this parallel information at 8MHz, and sends it out in a stream to IC70 to be mixed with TV sync. information, etc. displayed along a TV line as the electron beam strobos across the screen. This takes 1 μ s, and each successive 1 μ s sees IC42 loaded with another character-row for the same treatment. Note: LD is fed from C0 to 1MHz via a monostable (half of IC71) to give a short negative going pulse, and CLK is at 8MHz. This is the Dot clock, so named because each cycle displays one of the 8 dots of a character on the screen. After the top row of the "E" has been displayed, the top row of the next character on that line must be fetched. Again, C8, C9, C10 will not change, but C1-C6 will, hence selecting the next VDU RAM location, and so on until C1-C6 have displayed one row of 64 characters. Some of these are lost at the end of the line, as the Dot clock is only at 8MHz. When C1-C6 have finished rippling through, C7 changes and the whole is repeated. C6 synchronises the TV line (at 64 μ s intervals) and thus starts a new line via IC65 on its downward edge. C7 is not used in the process and thus C1-C6 must count through twice before C8, 9, 10 increment to a new row of the character; this causes each row of dots to occupy two TV lines as shown in Fig. 3.3.

As C8, 9, 10 increment, the complete set of 16 TV lines builds up a row of text. The next step is to increment C11-C14 to address the next row of characters stored in the VDU RAM. The complete frame of 256 TV lines is built up as C1-C14 count through. Normally, in TV transmissions, another frame slightly different from this, is interlaced in the

Fig. 3.3 Dot structure of an ASCII Character on the VDU screen

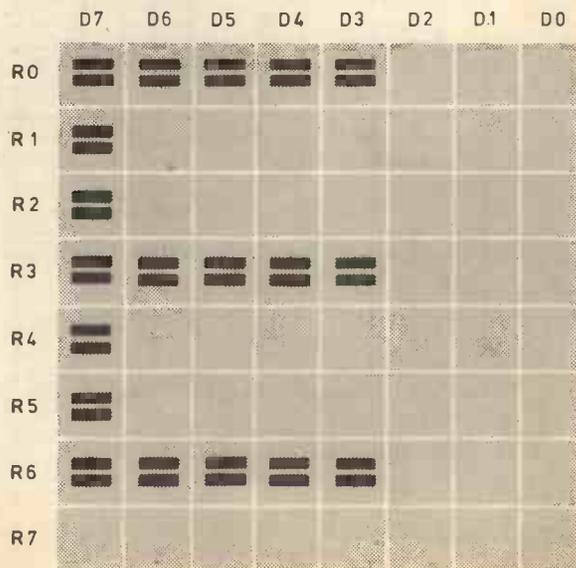

spaces between the lines of the first frame. Also, each half frame is composed of more lines. Here, C15, via IC71, provides a frame-sync. pulse to the TV, and the above process repeats exactly—each line occupying its previous position. The resolution thus obtained is not as high as a normal TV picture, but is more than adequate for 16 lines of VDU information.

The frame-sync. is delayed by half of IC65 to allow the TV picture to be moved up the screen, and hence prevent the bottom left character from being lost. This is the most important character slot on the screen and must be displayed clearly. The value of R33 and C8 may be adjusted to ensure its readability on any TV.

About 48 characters are able to be displayed on a normal TV, and hence about 16 characters are lost from the edges of the screen. At least 5 are missing from the start of the line and the rest from the end. The software of the COMPUKIT thus uses just those slots from the 6th to the 54th to prevent loss of information. The others are available to the user, however, and may be forced into display by adjusting a TV or monitor to "underscan". The RAM locations are still perfectly valid and may be used as normal.

A note about graphics should be made at this point. Since an 8 x 8 matrix of dots is used for characters in general and only a 7 x 5 matrix is used for the ASCII characters, spaces of varying sizes are left between text characters, both horizontally and vertically. However, the COMPUKIT's character generator is very rich in blocks, lines and special patterns which use the full 8 x 8 array of dots. By this means, adjacent graphic characters may be chosen to run into each other, and graphs, large patterns, block diagrams, etc. may all be constructed from basic components. Also, some extra characters are included such as £, π, ♦ etc. for a very full variety of uses.

ADDRESS DECODING AND MEMORY

Address decoding is performed via 74138's and 74139's with some extra gating. The address map defines the operation of this block and it is described here in full electrical detail. A TTL data book will provide all the information necessary to understand how this block works. RS0–RS7 are *selects* for the RAM (8 blocks of 1K, each

comprising two 2114's). BSO–BS3 select the BASIC ROMs, and MCS selects the monitor ROM. ACS selects the ACIA for the cassette. RKB and WKB are Read and Write selects for the keyboard and WVE and RVE for the VDU.

The RAMs are addressed so that IC31 and IC45 are at the lowest addresses and hence form the first 1K block of RAM (based at 0000). Addresses increase from right to left in pairs (the 2114 being arranged as 1K by four bits), IC32 and IC42 are next and so on. The ROMs are arranged to allow other options. When the 64K bit ROM is available, the four BASIC ROMs may occupy one package. A11 and

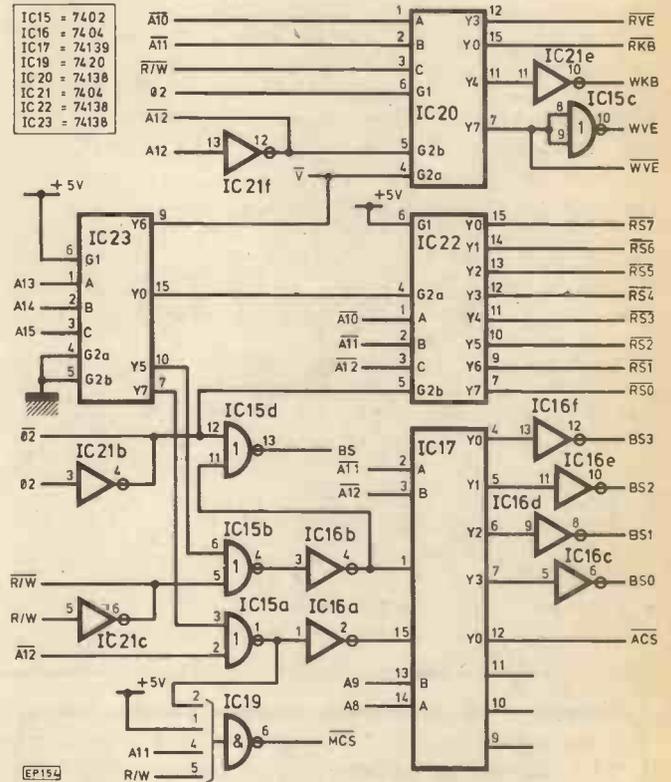


Fig. 3.5 (above). Address decoding

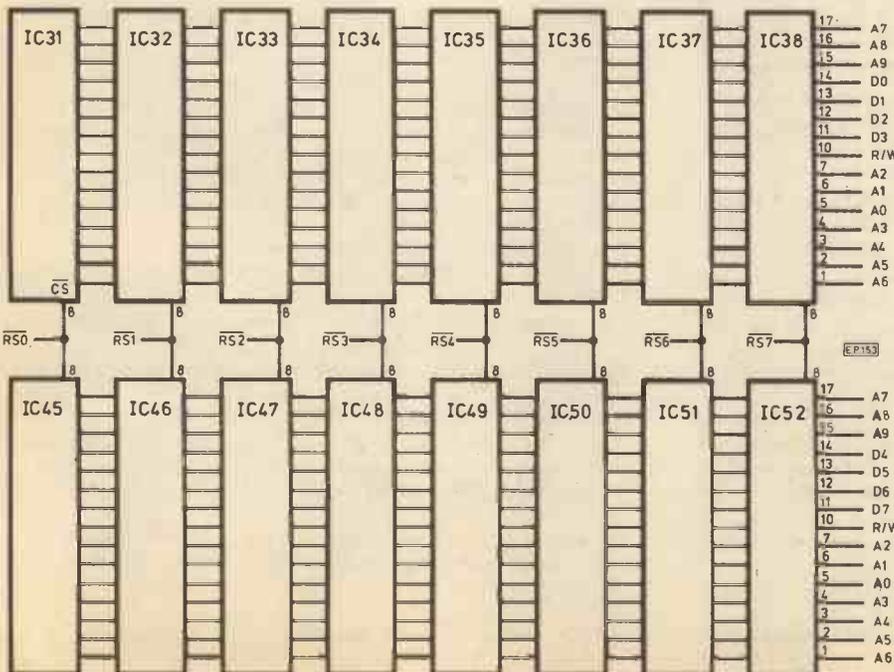


Fig. 3.4 (left). RAM configuration for 8K bytes

A12 will be needed and an address decoded line to select it. This already exists on the COMPUKIT; BS supplying the necessary address decoding. W1, W2 and W4 are pads next to the ROMs bringing these lines in. When this option is available, there will be three spaces free for ROMs or EPROMs of the user's choice. The COMPUKIT even allows for an active high or low BS line via IC18.

The Monitor ROM also has some flexibility in packaging and this is catered for, as shown.

PROCESSOR AND EXPANSION SOCKET J1


The processor is shown (Fig. 2.4) feeding all the Busses and control lines internally as well as externally, via J1, whose data lines are fully buffered by IC6 and IC7. External devices decide the direction of data flow through these buffers by DD. This socket allows any external logic to overtake the MPU system via interrupts and can easily be extended to control anything. External memory may be added via the socket; disc storage, S100 Bus expansions, etc. may all be plugged in directly.

SERIAL AND CASSETTE INTERFACE

The serial interface is controlled by IC14 (ACIA). This is primarily to drive a cassette interface. However, sockets and pads are provided for extra components to allow the ACIA to drive an RS232 interface if required. This will not be described here but is shown in the diagram.

The ACIA receives its clock from C3 of the counting chain via IC57, IC63 and IC58. Options exist, as shown, to separate the Tx and Rx clocks. In addition, driving the clock from C2, C1 or C0 will increase and BAUD rate from 300 by a factor of 2, 4 or 8 respectively.

The ACIA's Tx and Rx data lines are fed to the cassette interface as shown. The transmitter uses a 7476 (IC64) to present a high or low tone to the recorder as a "1" or "0" to be recorded. This follows the usual Kansas City recording format.

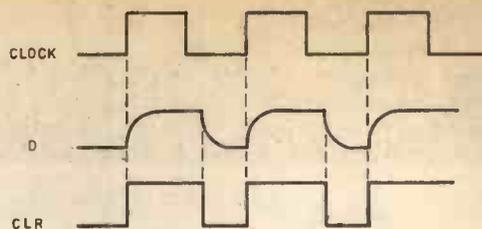

EO 178

Fig. 3.6 Timing diagram

Receiving depends upon the time-constant of a monostable. IC66 and IC62 are used to convert the sine-wave input, from cassette, to a square-wave suitable for the monostable IC69, and the clock input of a D-type flip-flop (IC63). While the tone is high, the 74123's time-constant is set such that the Q-output has no time to reset to zero before the next positive edge at B forces it high again. D and CLR of IC63 thus remain high, as Q does, and Rx DATA presents a constant "1". When a low tone arrives, the cycles arriving at B are long enough to allow Q to reset, after its positive-going timing pulse, before B encounters a further positive-going edge forcing Q high again. This gives the timing diagram shown in Fig. 3.6 for IC63.

The leading edge of D is slowed by R62 and C55. The zero on CLR now sets Q to zero and, because D's rising edge is slowed down, IC63 sees a zero on D when the clock goes high, thus preserving the zero on Q, and hence the circuit decodes a constant zero for as long as the low tone continues.

This sort of circuit is quite reliable at 300 BAUD and any instability will be due either to a large variation in tape speed, or to the value of R53 and C11 having been incorrectly chosen, thus allowing the negative-going edge on D to arrive too soon.

NEXT MONTH: Conclusion of series

Countdown

Organisers: Please send details of exhibitions and other events to Mike Abbott at least six weeks in advance. Inclusion will be subject to space etc.

Racalex '79—October 2-4. Royal Lancaster Hotel, London. Details: Racial Electronics Ltd., Western Road, Bracknell, Berks. RG12 1RG.

Eltro Hobby '79—October 3-7, Killesberg Exhibition Grounds, Stuttgart. Details: 01-236 0911.

Internecon UK '79—October 16-18. Metropole, Brighton.

Retailing in the 80's—Automation for Profit—October 23, 24, 1979. International Press Centre, London. Conference taking a broad view of the relationship between the retail manager and computer. Details: Online Conferences Ltd. Tel: Uxbridge (0895) 39262.

Satellite Communications (conference)—October 30, 31. London Press Centre. Will "tele-conferencing" replace business travel? Who will finance this expanding technology, and how should outer space be shared between the nations? Details: Online Conferences Ltd. Tel: Uxbridge (0895) 39262.

Personal Computer World Show—November 1-3. West Centre Hotel, London.

Compec—November 6-8, 1979. Grand Hall, Olympia, London. Details: Iliffe Promotions Ltd. Tel: 01-261 8437/8.

Professional Viewdata Exhibition '79—November 7 & 8. West Centre Hotel, London.

Technical Innovation In The Service Of The Elderly and Disabled—Markets And Needs (symposium)—November 19-21. Berlin. Details: H. S. Wolff, Clinical Research Centre, Watford Road, Harrow, Middlesex.

Electronics '79—November 20-23. Olympia, London. Details: 021-705 6707.

Breadboard '79—December 4-8. Royal Horticultural Halls, Westminster. Details: Trident International Exhibitions. Tel: 0822 4671.

IEA/Electrex—February 25-29, 1980. National Exhibition Centre, Birmingham. Details: Industrial and Trade Fairs Ltd. Tel: 021-705 6707.

Viewdata '80—March 26-28. Wembley Conference Centre, London. Conference and exhibition. Details: Online Conferences Ltd. Tel: Uxbridge (0895) 39262.

Computer-Aided Design (conference and exhibition)—March 31-April 2, 1980. Metropole, Brighton. Details: Organisers, CAD 80. Tel: 0483-31261.

Communications '80—April 14-18. National Exhibition Centre, Birmingham. Details: ITF Exhibitions. Tel: 021-705 6707.


Electronic Test and Measuring Instrumentation—April 22-24, 1980. Wythenshaw Forum, Manchester. Details: Trident.

International Conference On The Electronic Office—April 22-25, 1980. London Penta Hotel. Organised principally by the Institute of Electronic and Radio Engineers, 99 Gower St., London WC1E 6AZ.

All-Electronics Show (1980)—April 29-May 1, Grosvenor House, London. Details: 0799-22612.

The Mersey Micro Show—April 30, May 1, 2, 1980. Adelphi Hotel, Liverpool. Exhibition and seminars, with the cooperation of Liverpool University. Details: Online Conferences Ltd. Tel: Uxbridge (0895) 39262.

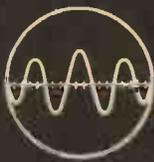IBC 80—September 20-24. Metropole Centre, Brighton, UK. Details: Secretariat, IEE, Savoy Place, London WC2R 0BL.



TUAC


TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE

correct at 17.8.79

TO ORDER BY POST

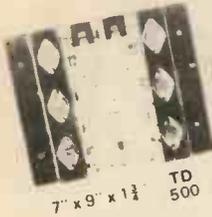Make cheques/P.O.s payable to TUAC LTD. or quote
Access/Barclaycard No. and post to TUAC LTD. 121
Charlmont Road, London SW17 9AB. We accept phone numbers
from Access/Barclaycard Holders, Phone 01-672 9080.



7" x 9" x 1 1/2" TD 500


NEW FROM TUAC ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS

Featuring
Electronic Short Open & Thermal Overload Protection.

Brief Spec.
Input Sensitivity 0.775v. R.M.S. (O.D.B.) at 25 K Ohms
Frequency Response 20 Hz-20 KHz
Hum & Noise 100 dB Relative full output

T.H.D. at full power 0.1%	
T.D. 500 300W into 2 Ohms	
220W into 4 Ohms	
140W into 8 Ohms	£47.95
Power supply P.S. 300	£31.95
T.D. 150 150W into 4 Ohms	
100W into 8 Ohms	£27.95
Power supply P.S. 150	£21.00
T.D. 150.60 Version 60W into 8 Ohms	
40W into 15 Ohms.	£21.00
Power supply P.S.60	£16.50

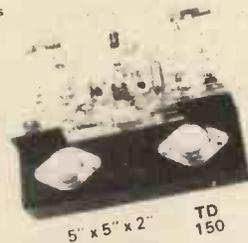
Note P.S. 300 will drive 2 T.D. 150 amplifiers



5" x 5" x 2" TD 150

All output ratings are R.M.S. continuous sine wave output.

AMPLIFIER MODULES

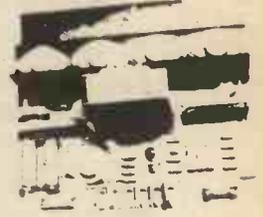

SPEC. INPUT
SENSITIVITY 60 mV
for full output
Frequency response
20 Hz-20 KHz
HUM & NOISE 70dB

TL30 5" x 5" x 2" * 35 watt 10 amp output transistors	£15.00
TL60 5" x 5" x 3" * 60 watt R.M.S. continuous sine wave output * 2 R.C.A. 110 watt 15 amp output transistors	£19.75
TL100 5" x 5" x 3" * 100 watt R.M.S. continuous sine wave output * 2 R.C.A. 150 watt 15 amp output transistors	£22.95
TP125 7" x 6" x 3" * 125 watt R.M.S. continuous sine wave output * 4 R.C.A. 150 watt 15 amp output transistors	£29.95



4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1

- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£22.95

Model 501 500W per channel as above without sound triggering

£14.95

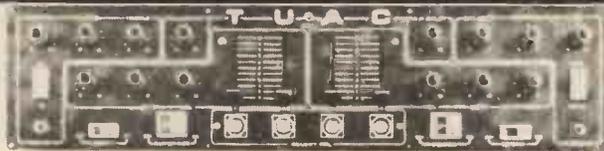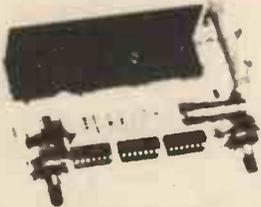

STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A.A. comp) 1 Flat 50mV at 1kHz. Bass controls - 18dB at 60Hz. Treble controls - 18dB at 15kHz.

OUTPUT: Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz - dB.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

Size 25in long x 6in high x 3in deep

Manual Disco Mixer with autotfade £55.50


£189.00

3 CHANNEL LIGHT MODULATOR SILMB

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£22.95

POWER SUPPLIES

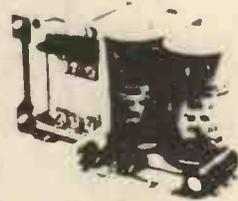

Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply:

PS250 for supplying 2 TP125s	£31.95
PS200 for supplying to TL100s	£31.95
PS60/60 for supplying 2 TL60s	£31.95
PS125 ± 45 volts for TP125	£21.00
PS100 ± 43 volts for TL100	£19.50
PS60 ± 38 volts for TL60	£16.50
PS30 ± 25 volts for TL30	£12.75
PSU 2 for supplying disco mixer	£8.00

STOCKISTS—CALLERS ONLY

A1 Music, 88, Oxford Street, Manchester (Tel 061-236 0340)
Geo. Mathews, 85/87, Hurst St., Birmingham (Tel 021-622 1941)
Soccold, 9, The Friars (Tel. Canterbury 60948)
Cookies Disco Centre, 125/128, West Street (Tel Crewe 4739)
Garland Bros. Ltd., Deptford Broadway, London 01-692 4412
Luton Disco Centre, 88, Wellington Street, Luton (Tel Luton 411733)
Session Music, 163, Mitcham Road, Tooting (Tel 01-672 3413),
Mon-Sat 10am to 6pm. Closed Wed.
Electrosure Ltd., Four St., Exeter. Tel. 56687.
Salcogen Ltd., 43 Borough Rd., Cleveland, Middlesbrough.
(Tel. 242851).
Menhouse Ltd., 82, St. Mary St., Southampton. (Tel 28028)
Electra Centre, 58 Lancaster Road, Preston (Tel. Preston 58488)

TRADE & EXPORT ENQUIRIES 01-672 3137

FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)
as illustrated



For SILMB £9.75
Size 8" x 4 1/2"



4LSM1 £7.75
Size 6 1/2" x 4 1/2"



FUZZ LIGHTS
Red, Green, Blue,
Amber. £25.95



SILMB £10.00
Combined with 3SDM1
Size 9" x 4 1/2"

ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1

£17.50

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE

Romane Electronics

PRESENT A SPECIAL INTRODUCTORY OFFER: LOW POWER SCHOTTKY TTL EX STOCK

Device	Price	Device	Price	Device	Price	Device	Price
74LS00	13p	74LS40	21p	74LS136	32p	74LS221	120p
74LS01	14p	74LS47	80p	74LS138	70p	74LS244	200p
74LS02	13p	74LS48	92p	74LS139	70p	74LS245	250p
74LS03	14p	74LS49	95p	74LS151	55p	74LS247	92p
74LS04	15p	74LS73	29p	74LS153	55p	74LS248	92p
74LS05	25p	74LS74	32p	74LS155	80p	74LS249	90p
74LS08	16p	74LS75	38p	74LS156	94p	74LS251	85p
74LS09	20p	74LS76	36p	74LS157	55p	74LS273	200p
74LS10	16p	74LS78	40p	74LS158	55p	74LS279	85p
74LS11	21p	74LS83	90p	74LS160	110p	74LS283	70p
74LS12	23p	74LS85	75p	74LS161	74p	74LS290	68p
74LS13	34p	74LS86	31p	74LS162	118p	74LS293	88p
74LS14	70p	74LS90	42p	74LS163	70p	74LS298	90p
74LS15	22p	74LS93	51p	74LS164	95p	74LS352	98p
74LS20	15p	74LS95	75p	74LS173	90p	74LS353	98p
74LS21	22p	74LS107	36p	74LS174	90p	74LS365	95p
74LS22	22p	74LS109	36p	74LS175	92p	74LS366	95p
74LS26	24p	74LS112	38p	74LS190	88p	74LS367	95p
74LS27	25p	74LS113	38p	74LS191	88p	74LS368	95p
74LS28	30p	74LS114	38p	74LS192	100p	74LS374	160p
74LS30	19p	74LS123	60p	74LS193	100p	74LS386	30p
74LS32	24p	74LS125	40p	74LS195	110p	74LS670	170p
74LS37	22p	74LS126	40p	74LS196	80p		
74LS38	25p	74LS132	70p	74LS197	100p		

We are holding substantial stocks of the devices listed. All orders, large and small, will be dealt with in strict rotation. Add 15% to all orders plus 30p P&P. Export orders no V.A.T., but postage at cost. Air/surface. Prompt delivery on all orders.

Full range of Breadboards, I.C. Test Clips, Ribbon Cable Assemblies (mostly ex-stock). Send large SAE for Catalogue and price lists.

Cheques, POs, Money Orders to be made payable to:-

ROMANE ELECTRONICS,
Sales Dept.,
64 Newlyn Drive,
Sale, Cheshire.
M33 3LE
Tel 061-962-2606

LOW PROFILE DIL SOCKETS BY TEXAS

8 PIN	13p	18 PIN	25p	24 PIN	33p
14 PIN	14p	20 PIN	27p	28 PIN	43p
16 PIN	16p	22 PIN	28p	40 PIN	53p

What's new from Heathkit?



IM 2212 - Auto Ranging DMM



IO 4105 - Single Beam 5 MHz Oscilloscope



IM 5217 - Portable Multimeter

Plus

- * GD 1290 - VLF Metal Locator
- * HX 1681 - CW Transmitter
- * IR 5201 - XY Recorder
- * CI 1525 - Car Temperature Indicator

These brand new self-assembly kits are designed to the highest specification. The step-by-step instructions make them easy to build at your leisure in your own home.

And first class quality makes them excellent value for money.

Details of the full Heathkit range are available in the Heathkit catalogue. Send for your copy now.



IM 2215 - Hand-held DMM

Soldering
Iron offer
FREE

To: Heath (Gloucester) Limited, Dept. (PE 10), Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.

Name _____

Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

When you receive your catalogue you will get details of this free offer.



There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451).

HEATHKIT

Next Month...

FREE!

IN OUR NOVEMBER ISSUE

MARSHALL'S 60 PAGE CATALOGUE

*Worth
50p*

PE DIAMATIC



PROGRAMMABLE A.V. UNIT

An up-to-the-minute development for the enthusiast in colour slide photography which allows controllable dissolve of images between two projectors.

Features include rapid slide alternation or superimposition of two images and cue-in commentary or musical sound track for creative sequences.

Solid State Car Instruments...

No.2 Rev. Counter

PRACTICAL

ELECTRONICS

SPECIAL OFFER—CSC PROTO BOARD KIT

OUR NOVEMBER ISSUE WILL BE ON SALE FRIDAY 12 OCTOBER 1979

C.B.



...in the U.K.

Dr. MARK SAWICKI

ONE MAN'S VIEWS ON THE PRESENT SITUATION

IN Holland, despite strong local opposition to Citizens Band Radio, the Dutch Government recently succumbed to public pressure and announced new legislation for the legal introduction of CEPT—22 channel standard in the 27MHz band. The new legislation was announced on January 22 by the media. In the eyes of the users this is a victory of the individual, in the form of public pressure, over the system.

As one can see, this type of problem often arises in the early underground stages of mass illegal use of CB, and has forced governments (Australia and Holland) to accept the fact that the thousands of users just cannot be ignored. The barometer swings from simple observation and monitoring of CB through enforced restriction on use, to eventual capitulation that it is just not feasible to track down or squash all opposition and CB users. So common sense prevailed in Holland, with the introduction of a 27MHz legal band, allowing thousands of users to crawl out of their burrows into the open air and talk, talk, talk.

Until January, the Dutch government had imposed heavy legislation against CB'ers—to the extent that it was possible to be prosecuted for possession. Naturally legalisation has brought out into the open all those underground users, and does pose a dilemma of whether they should be prosecuted for possession (if proved) before the Act was introduced.

The Dutch analogy is very similar to the CB situation in the UK, and I doubt whether anyone is so naive as to think otherwise. One only has to note the numerous reports that appear from the "authorities", quite apart from the many articles that have been appearing in a variety of magazines, and even the public debates over the radio.

ILLEGAL USERS

To ignore the existence of the ever increasing number of illegal CB users in the UK would be plain stupidity—it is a fact of life and as such should be recognised. The public, the press and others are becoming bolder—witness the articles that are appearing on subjects of pirate radio stations and CB rigs.

On a general basis, CB users in the UK could be divided into two groups; either professional, and these are mainly lorry drivers, or non professional—the CB hobbyists. The first group—the drivers—can use CB completely legally when travelling in many parts of Europe (on the 27MHz band) and not only does it alleviate the boredom of a long haul, it can in many instances be beneficial to road users.

CB is not a new thing, it has been particularly well tried and tested in the USA, and is an extremely important factor in improving communications from base or mobile stations in large towns, in the countryside or indeed, anywhere. The arguments for the other side, i.e. those opposed to the idea of legalisation look weak in the light of the fact that 19 countries have already welcomed CB users into their fold.

Sooner or later CB should become legal here, if the percentage of users keeps growing at the present rate, no government will be in a position to track them down or even control the 27MHz band. So basically all the rhetoric and academic discussion will serve no purpose except to delay the inevitable introduction of legislation and prolong interference caused by poor equipment being used illegally.

Once again it seems that the UK will be the last one to have her foot in the door. In the meantime, people will get caught for illegal use and suffer the consequences.

The CB Association's President, Mr. James Bryant sent an open letter to the then Prime Minister—Mr. Callaghan (January 12th) pointing out the rapid growth in the illegal use of CB radio in this country and urged him to legalize CB radio in Britain. Perhaps the most significant point made in this letter was the estimation by The Citizen Band Association that there were then about 15,000 illegal users in the country and that their number is increasing by roughly 2,000 per month. One does not need to be a mathematician to work out, that if this premise is true, then by the end of the summer holiday period there will be around 30,000 CB'ers in Britain, and that is no small number!

RADIO CONTROL

What about the actual legislation—it is worth considering one point—that recently the Society of Model Aeronautical Engineers have made a request to the Home Office for the use of a Radio Control band at 35MHz.

When one considers that 21 years have passed since CB was introduced by the US government—in 1958—to fill a need for a low-cost communication system available to everyone and requiring no technical skill, the attitude of the UK government seems old fashioned and wary. CB radio in the States was operated on 23 channels initially but in 1977 positive practice culminated in the addition of new channels making up a total number of 40, used by private citizens for personal or business communication on frequencies between 26.965MHz to 27.28MHz with the 27.065MHz channel used solely for emergency communications involving road safety, personal safety and property safety, and communications necessary to render assistance to motorists.

Lack of any legislation in the UK means that the type and quality of equipment will vary enormously—power output and number of channels etc.—and as such may interfere with legal emergency services, which obviously is to be avoided. An associated problem for CB'ers is that underground conditions force camouflage on mobile units, so one will find people driving around with completely unsuitable types of aerials, often generating signal harmonics and thus theoretically interfering with legal radio equipment users.

Radiomodellers on the other hand also face problems with the possibility of interference whilst working on 27.12MHz band. A conversation with an experienced radiomodeller who "flies" every Sunday in the Richmond area, shows that many modellers are not opposed to CB, however, there have been recent cases where expensive models crashed or were sent out of control. Naturally it is not possible to prove that these accidents were a result of CB rigs working in the area. The fact is that illegally operated CB rigs could theoretically affect radio-controlled equipment such as flying models. The consequences of this fact are serious, bearing in mind possible speeds of 120 miles per hour and model weight of up to a few kilos, especially when many radio modellers operate in public parks at weekends.

EQUIPMENT

There is a variety of different equipment in the potential reach of people determined enough to operate illegally on the 27MHz band. It seems to be exceptionally easy to buy CB equipment and associated CB accessories in London, both as second hand gear or brand new. Price ranges vary from about £40/£50 for a portable unit up to £260 for a high quality (69 channel s.b.) unit.

In 1976, the FCC estimated in excess of 10 million CB users in the USA and naturally American made equipment dominates both the legal and illegal CB market in Europe. There are also many European manufacturers on the scene from Switzerland, Belgium, Denmark, West Germany, Italy and Spain. Both European and American equipment is designed to operate on 27MHz, with variations in the number of channels, power output etc. As a result it is easy to see that the number of designs on the world market is large and many companies are rushing into CB production.

As no licence is required in the States to listen to the 27MHz band, a whole range of

CB convertors has been recently introduced as they have proved extremely useful for listening to CB traffic reports, weather and road conditions. In some cities Channel 9 (emergency) and Channel 14 (communication) are monitored by volunteer CB patrols who provide concerned citizens with a communication line to local police for reporting suspicious or criminal activity. Indeed the idea is widely accepted all around the world and called "React International"—emergency monitoring services (Channel 9—27.165MHz). "React" teams are active on a 24 hour basis in over 12 countries and their work has already saved the lives of victims of traffic accidents and freak weather conditions such as snow storms or typhoons.

CODE

Citizens band Radio operators have largely adopted the APCO 10 Code—developed originally by the police for their standard questions and answers, the code is easy to learn and useful in bad radio conditions. The CB subculture in the USA has taken things further, producing a bulk of speciality CB magazines and technical CB services. They have even developed a CB slang—which seems to be "double-dutch" to any outsiders.

Whatever ones feelings are about CB any technical or social discussion will produce good and bad aspects of the phenomena but my personal feelings are that the positive points outweigh the negative ones.

APCO 10 CODE

10- 1 Signal weak	10-18 Urgent
10- 2 Signal good	10-19 (In) Contact
10- 3 Stop transmitting	10-20 Location
10- 4 Affirmative (OK)	10-21 Call . . . by phone
10- 5 Relay (to) . . .	10-22 Disregard
10- 6 Busy	10-23 Arrived at scene
10- 7 Out of service	10-24 Assignment completed
10- 8 In service	10-25 Report to (meet) . . .
10- 9 Say again	10-26 Estimated time of arrival
10-10 Negative	10-27 License/Permit information
10-11 On duty	10-28 Ownership information
10-12 Stand by (stop)	10-29 Records check
10-13 Existing conditions	10-30 Danger/Caution
10-14 Message/Information	10-31 Pick Up . . .
10-15 Message delivered	10-32 Units needed: Specify
10-16 Reply to message	10-33 Help me quick
10-17 Enroute	10-34 Time

EDITORIAL NOTE

We believe the Home Office is revising its attitude on CB and understand that at a recent meeting between a Minister of state at the Home Office and an all party delegation of M.P.s, agreement was reached on the availability of frequency space and that the introduction of CB would not require new legislation.

Apparently the M.P.s expect the Home Office to come up with a programme for the introduction of CB for discussion at their next meeting in November. The all party group is advocating a service basically similar to the proposals of the Citizens Band Association—a VHF FM system with built in station identification.

Unfortunately, it is apparent that the Home Office still does not recognise the urgency of the situation if the illegal use is to be kept down, we believe this to now be crucial. Might we suggest that those who are in favour of CB in the UK, and particularly anyone who may suffer from the illegal use of 27MHz, write to the Home Secretary Mr. William Whitelaw M.P., House of Commons, London SW1 0AA, in support of the adoption of a VHF service as a matter of urgency. This we believe is now the only way to protect the 27MHz band from illegal use, and probably a way of achieving the best possible CB system for the UK.

It is known that the Prime Minister is in favour of CB and it would now seem to be a few belligerent civil servants in the Home Office that have to be overcome.

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas often come from readers working on their own systems, and payment will be made for any contribution featured.

THIS month's Micro-Bus compares the speed of four micros on a simple programming task: the conversion of a number from binary to decimal. The techniques involved in optimising the execution time of a machine code program are illustrated for the four micros, and the differences between them are discussed for the benefit of readers unfamiliar with their instruction sets. One of the micros is the new 6809, and another reason for performing this comparison is to see if the 6809 lives up to Motorola's claim that it is the "fastest 8-bit microprocessor".

Obviously one benchmark cannot give a representative idea of the performance of a

micro. The binary-to-decimal routine was chosen for the comparison because, while being interesting due to the need for indexed addressing in two different areas of memory, it does not favour the quirks of any particular instruction set.

BINARY TO DECIMAL

The binary-to-decimal routine converts a 16-bit unsigned binary number into its decimal equivalent. The routine is supplied with the number to be converted in a suitable register (or registers), and with the address of where the result should be stored. The result can be anywhere in memory, and occupies five suc-

cessive locations, one decimal digit per location. The routine, as given in many programming handbooks, is represented by the flowchart in Fig. 1. The variable N is the original binary number, and the five digits of the result are DIGIT(4) to DIGIT(0); D is a temporary counter for the digits.

The program works as follows: the first digit, DIGIT(4), is the number of tens of thousands, and so is obtained by counting how many 10,000s can be subtracted from N before it goes negative. Then the number of thousands is found by repeatedly subtracting 1,000, and so on, finally subtracting 1 to find the units.

SPEED OPTIMISATION

It is said that in most programs 90 per cent of the time is spent executing 10 per cent of the instructions, and the first step in optimising the speed of a program is to identify the time-consuming 10 per cent, which is normally the innermost loop of the program. The next step is to make this section of the program execute as fast as possible. The innermost loop in the flowchart of Fig. 1 begins at LOOP 2, and consists of a double-byte subtraction, a test, and an increment. This loop is executed once for each power of ten subtracted; in other words, the number of iterations is the sum of the decimal digits of the number being converted. The slowest number will be 59.999, needing 5+9+9+9+9 or 41 iterations.

An immediate improvement can be made by realising that the last digit is just the remainder after calculating the first four digits, so there is no need to repeatedly subtract 1 from it. This futile calculation can be removed from the program, reducing the number of iterations to 32. A second, less obvious, saving is gained by noticing that to implement the inner loop of Fig. 1, two branch (or jump)

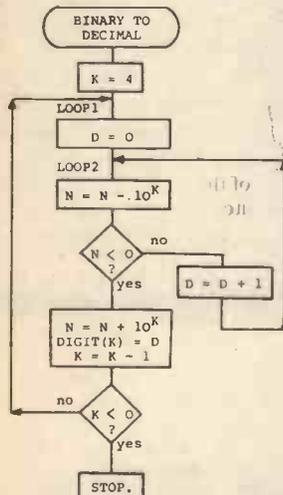


Fig. 1. Flowchart for a routine to convert a binary number N into decimal.

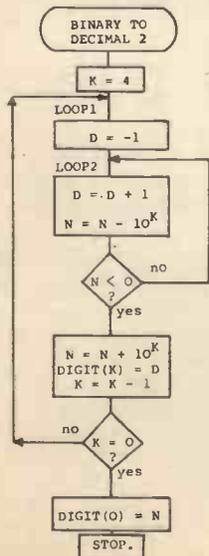


Fig. 2. Flowchart for an improved version of the binary-to-decimal routine.

instructions will be needed: one to test if N is negative, and one to jump back to the start of the loop after incrementing D. The second of these can be dispensed with by incrementing D at the start of the loop, and then either jumping over the increment instruction the first time round the loop, or counting from -1.

All the programs presented here incorporate these two improvements, and the optimised flowchart is shown in Fig. 2. Other methods used for trimming off cycles from the four programs depend on the idiosyncracies of each micro's instruction set, and are described for the four conversion routines.

6800

The binary-to-decimal conversion routine for the 6800 is shown in Fig. 3. In the 6800, direct (zero-page) addressing is the fastest mode, so rather than using indexed addressing each time round the inner loop, the power of

```

* BINARY TO DECIMAL FOR 6800
* NUMBER IN A, B
* RESULT STORED AT X
0000 0005 RESULT RMB 5
0005 0002 DIGITS RMB 2
0007 0002 XTENS RMB 2
0009 0002 POWER RMB 2
000B 2710 KIOTAB FDB 10000
000D 03E8 FDB 1000
000F 0064 FDB 100
0011 000A FDB 10

0013 86 EA BINDEC LDA A, ESEA A, B=59999
0015 C6 5F LDA B, E5FF FOR TEST
0017 CE 0000 LDX E, RESULT
001A DF 05 STX DIGITS SAVE X
001C CE 000B LDX KIOTAB
001F DF 07 LOOP1 STX XTENS
0021 EE 00 LDX O, X
0023 DF 09 STX POWER
0025 DE 05 LDX DIGITS
0027 6F 00 CLR O, X
0029 20 02 BRA NOINC
002B 6C 00 LOOP2 INC O, X
002D 0A 0A NOINC SUB B, POWER+1
002F 92 09 SBC A, POWER
0031 24 F8 BCC LOOP2
0033 DB 0A ADD B, POWER+1
0035 99 09 ADC A, POWER
0037 08 INX X
0038 DF 05 STX DIGITS
003A DE 07 LDX XTENS
003C 08 INX X
003D 08 INX X
003E 8C 0013 CPX KIOTAB+8
0041 26 DC LOOP LDX LOOP
0043 DE 05 LDX DIGITS
0045 E7 00 STA B, O, X
0047 39 RTS
    
```

Fig. 3. Binary-to-decimal routine for the Motorola 6800.

```

* BINARY TO DECIMAL FOR 6502
* NUMBER SUPPLIED IN A, X
* RESULT STORED AT (PNO)
0000 LO =, #020 FOR ACORN
0020 HI =, #+1 NUMBER BEING CONVERTED
0021 HI =, #+1 DITTO
0022 PNO =, #+2 ADDRESS OF RESULT
0028 27 PLOTAB .BYTE $27, $03, $00, $00
0028 10 .BYTE $10, $E8, $64, $0A

002C A9 EA BINDEC LDA ESEA A, X=59999
002E A2 5F LDX E5FF
0030 85 21 STA HI
0032 86 20 STX LO
0034 D8 CLD
0035 A0 00 LDX #0 FOR BINARY
0037 A2 FF LOOP1 LDX E5FF
0039 38 SEC COUNTER
003A E8 20 LOOP2 INX LO
003B A5 20 LDA LO
003D F9 28 00 SBC PLOTAB+4, Y
0040 85 20 STA LO
0042 A5 21 LDA HI
0044 F9 24 00 SBC PLOTAB, Y
0047 85 21 STA HI
0049 80 EF BCS LOOP2
004B A5 20 LDA LO
004D 78 28 00 ADC PLOTAB+4, Y
0050 85 20 STA LO
0052 A5 21 LDA HI
0054 79 24 00 ADC PLOTAB, Y
0057 85 21 STA HI
0059 8A TXA
005A 91 22 STA (PNO), Y
005C C8 BNE INY
005D C0 04 CPV E4
005F D0 D6 BNE LOOP1
0061 A5 20 LDA LO
0063 91 22 STA (PNO), Y
0065 60 RTS
    
```

Fig. 4. Binary-to-decimal routine for the MOS Technology 6502.

ten is first stored at POWER so that direct addressing can be used for the subtract operations with a saving of 4 cycles.

The 6800 routine differs from the flowchart of Fig. 2 in that the digit locations are incremented directly, eliminating the need for a temporary counter; although the indexed increment instruction costs an extra cycle in the inner loop, there turns out to be a net

saving. This is not a very flattering program for the 6800 as it very clearly shows up the disadvantages of having only one index register.

6502

In the 6502 all arithmetic operations use the accumulator, so for double-byte arithmetic the accumulator must be repeatedly loaded from memory and stored to memory, making the program of Fig. 4 relatively long. Since the 6502 does not have any 16-bit registers, the address of the result must be held in memory, and the digits are stored using post-indexed indirect addressing. An extra saving is gained by splitting the table of powers of ten into two halves so that the Y index register can be used for indexing both the powers of ten and the digits of the result; the X register is then free for use as the digit counter.

```

; BINARY TO DECIMAL FOR 6502
; NUMBER IN HL - RESULT AT IX
; FOR RESULT
0000 0005 DEC: DEFS 5
0005 10 27 KIOTAB: DEFV 10000
0007 EB 03 DEFV 1000
0009 64 00 DEFV 100
000B 0A 00 DEFV 10

000D 21 5F EA BINDEC: LD HL, 59999 ; TO TEST IT
0010 DD 21 00 00 LD IX, DEC
0013 FD 21 05 00 LD IX, KIOTAB
0018 3E FF LOOP1: LD A, OFFH ; GET POWER
001A FD 5E 00 LD E, (IX) ; OF TEN
001D FD 56 01 LD D, (IX+1) ; CLEAR CARRY
0020 87 OR A
0021 ED 52 LOOP2: SBC HL, DE
0023 3C INC A
0024 D2 21 00 JP NC, LOOP2
0027 19 ADD HL, DE ; STORE DIGIT
0028 DD 77 00 JUMP: LD (IX), A ; NEXT DIGIT
002B DD 23 INC IX ; NEXT POWER
002D FD 23 INC IX ; OF TEN
002F FD 23 INC IX
0031 7B LD A, E
0032 FE 0A CP 10
0034 C2 18 00 JP NZ, LOOP1
0037 DD 75 00 LD (IX), L ; REMAINDER
003A C5 RET ; FINISHED
    
```

Fig. 5. Binary-to-decimal routine for the Zilog Z80.

Z80

The program for the Z80, Fig. 5, closely follows the flowchart of Fig. 2. The OR A instruction, which at first sight achieves nothing, is used to clear the carry bit. Because it is rather awkward to test the value of the index register to determine when four digits have been completed, as in the other routines, this program checks to see if the lower byte of the power of ten, E, is equal to 10. It is a pity that the Z80's indexed addressing instructions need an extra byte prefix, because this reduces the speed advantage of using them.

6809

The Motorola 6809 is the newest of the four processors discussed here, and the chips are only just becoming available. It is an upgraded version of the 6800, and is compatible with the 6800 at the level of source code, which means that the routine for the 6800 in Fig. 3 could be re-assembled straight into 6809 instructions. However, the 6809 contains so many new addressing modes, registers, and additions to the 6800 instruction set that it is worth writing the routine from scratch.

The "ADDD .X+" instruction illustrates the power of the instruction set: this instruction performs a double-byte addition of the bytes pointed to by X into the 16-bit D register, and then increments X twice. It therefore replaces four of the instructions in the 6800 version. The provision of a Y index register in the 6809 makes it possible to eliminate from the 6800 version a further seven instructions that were needed to load and store the X register between uses.

* BINARY TO DECIMAL FOR 6809 *
* NUMBER IN D - RESULT AT Y *

```

0000 0005 RESULT RMB 5
0005 2710 K1OTAB FDB 10000
0007 03E8 FDB 1000
0009 0064 FDB 100
000B 000A FDB 10

000D CC EASP 3 BINDEC LDD $59999 FOR TEST
0010 BE 0005 3 LDX K1OTAB
0013 10BE 0000 4 LDR ERESULT
0017 6F A1 6 LOOP1 CLR O,Y
0019 20 02 3 BRA NOINC
001B 6C A4 6 LOOP2 INC O,Y
001D A3 84 6 NOINC SUBD O,X
001F 24 FA 3 BCC LOOP2
0021 31 21 5 PRN5 LEAY 1,Y T.E. INY
0023 E3 81 9 ADDD ,X++
0025 BC 000D 4 CMF K1OTAB+8
0028 26 ED 3 BNE LOOP1
002A E7 A4 4 STB O,Y REMAINDER
002C 39 5 RTS RETURN

```

Fig. 6. Binary-to decimal routine for the Motorola 6809.

The resulting program for the 6809, Fig. 6, is half the length of the 6800 version, and is the neatest of the programs presented here. It is a direct translation of the flowchart of Fig. 2 into instructions, without the need for any tricks, temporary locations, or extra operations.

PROGRAM EXECUTION TIMES

Each program can be divided into three parts. First there is the inner loop beginning at the label LOOP 2 which, as explained above, is executed 32 times for a worst-case number of 59,999. Then there is the outer loop beginning at LOOP 1 which is executed once for each digit, or a total of four times. Finally there are the remaining instructions, at the start and end of the programs, which are executed only once. The number of cycles for each of these sections of each program is shown in Table 1, together with the total number of cycles for the whole routine.

	6800	6502	Z80	6809
INNER LOOP (x 32)	17	25	29	15
OUTER LOOP (x 4)	75	62	159	39
REST (x 1)	30	28	67	19
TOTAL CYCLES	874	1076	1631	655
TOTAL TIME (secs)	57	71	53	43

TABLE 1

The bottom row of Table 1 gives the time, in seconds, for each routine to convert the number 59,999 a total of 65,536 times (a convenient loop count). These times are for a Z80 running with a 2MHz clock, and for the other three processors running at 1MHz, to allow for the different way the Z80 handles instruction timing. This seems fairer than comparing the processors running with the same clock rate, because the clock rate used by a system will normally be determined by the speed at which the memory will run, this tending to be a more expensive part of the system than the processor itself.

The 6800, 6502 and 6809 all access memory for one machine cycle, whereas in the Z80 the shortest memory access, the op-code fetch, lasts for two machine cycles: the Z80 can therefore run with twice the clock rate on the same memory as the other micros.

The result of the comparison is that the 6809 wins the race, followed by the Z80 and 6800, and the 6502 follows closely behind. Anyone writing a faster version of any of these routines should set up a loop to execute the routine 65,536 times, and check that the time taken agrees with the prediction from counting the number of cycles. If any substantially better routines are received, they will be presented in a future Micro-Bus.

EIGHT EIGHTS SOLUTION

August's Micro-Bus gave a program for the Mk14 microprocessor kit and posed the following problem: with the program running on an Mk14, what is the shortest sequence of key-presses that will cause eight eights to light up on the displays? Despite the apparent simplicity of the program, shown in Fig. 7, the problem is extremely tantalising and can only be solved by the following sequence of 45 keys:

```

0 2 3 2 4 2 3 2 5
2 3 2 4 2 3 2 6 2
3 2 4 2 3 2 5 2 3
2 4 2 3 2 7 2 3 2
4 2 3 2 5 2 3 1 0

```

This solution is unique, except that the order of the 0 and 1 at the end can be reversed, and other keys can be exchanged for the 1 key.

Although this solution looks complicated, there is an underlying pattern that yields to a little scientific investigation. Some experimentation with the program soon reveals the following rules about its behaviour:

- (1) Only the keys 0 to 7 need be considered. (All the other number keys just do the same as key 1.)
- (2) Every time a key is pressed one display is alternately illuminated with an "8", and blanked.
- (3) Numbering the displays 0 to 7 from right to left, keys 0, 1, and 2 always operate the corresponding display.
- (4) Keys 3 to 7 only operate the corresponding display if the display immediately to the right is on and all the other displays to the right are off; otherwise they operate display 1.

With these rules established it is then fairly simple to produce the desired result. First observe that since 0, 1 and 2 can be switched on at any time (rule 3) they are better left off for the moment, so press 0 as a first move to get all the displays blank. Now, to get 3 on we must first get 2 on by itself (rule 4) by pressing 2. Having operated 3 there are two options: operate 3 again, getting back to the previous state, or operate 2, getting to a new state. We choose the latter and continue in this way, always pressing the key that gets to a new state of the displays. The results of the first few steps are shown:

```

Key: Display: 7 6 5 4 3 2
Start      0 0 0 0 0 0
2          0 0 0 0 0 1
3          0 0 0 0 1 1
2          0 0 0 0 1 0
4          0 0 0 1 1 0
2          0 0 0 1 1 1
3          0 0 0 1 0 1
2          0 0 0 1 0 0
5          0 0 1 1 0 0

```

The state "111111" (displays 2 to 7 on) is reached after 42 key-presses. In addition there is the key-press at the start to get 0 off, and two at the end to get 0 and 1 on, making the 45-key sequence given above.

GRAY CODE

The sequence of states of the displays 2 to 7 may be familiar as a binary Gray code for the numbers 0 to 41. The Gray code was invented in the 1940's by Frank Gray, a

research physicist at the Bell Telephone Labs, to prevent errors in pulse-code modulated signals. In binary Gray codes each number differs from its neighbours by the alteration of only one bit, and they are now widely used in encoding applications where a normal binary code might give a false reading when changing between two adjacent states.

PROGRAM OPERATION

A fully commented version of the Eight Eights program is given in Fig. 7. The program

```

; EIGHT EIGHTS PROBLEM
0185 KYBD = X'0185 ;IN MONITOR
0080 = X'02 ;EXTENSION AS OFFSET
007F EIGHT = X'7F ;SEGMENT CODE FOR '8'
0000 OF18 = -OF18

OF18 C484 ; BEGIN: LDI L(KYBD)-1
OF1A 33 ; XPAL 3
OF1B C40F ; LDI H(DISBUF)
OF1D 36 ; XPAL 2
OF1E C401 ; BACK: LDI H(KYBD)
OF20 37 ; XPAL 3
OF21 01 ; XAE
OF22 C440 ; RIGHT: LDI L(DISBUF) ;E = P3H
OF24 32 ; XPAL 2 ;POINT P2 TO
OF25 C47F ; LDI EIGHT ; DISPLAY BUFFER
OF27 E280 ; XOR E(2) ;CHANGE STATE OF
OF29 C480 ; ST E ; DISPLAY E
OF2B SHOW: LDI E ;DISPLAY ROUTINE
OF2C 90FD ; JMP SHOW ;COMMAND KEY RETURN
OF2E 03 ; SCL ;NUMBER KEY RETURN
OF2F C402 ; LDI 2
OF31 7E ; CAL
OF32 94EE ; JP ;RIGHT
OF34 C601 ; LOOP: LD R1(2) ;IF SO-CHANGE DISPLAY
OF36 98FC ; JZ LOOP ; FIND FIRST NON-BLANK
OF38 32 ; XPAL 2 ; DISPLAY
OF39 60 ; XRE ;GET DISPLAY NUMBER
OF3A D40F ; ANI X'0F ;15 NUMBER = KEY 7
OF3C 98E4 ; JZ RIGHT ;IF SO-CHANGE DISPLAY
OF3E 90DE ; JMP BACK ;ELSE-CHANGE NUMBER 1
OF40 0000 ; ; DISPLAY BUFFER - STARTS ALL BLANK
DISBUF: BYTE 0,0,0,0,0,0,0,0

0000 ; .END

```

Fig. 7. SC/MP program for the Eight Eights problem posed in the last Micro-Bus.

makes use of the display routine KYBD in the Mk14 monitor: this routine displays the segment codes stored in the eight bytes pointed to by P2, and returns after a key-press with the value of the number key in the E register. In the Eight Eights program the eight bytes OF40 to OF48 are displayed, since P2 is set up to contain OF40. The segment codes X'00 and X'7F are stored in those locations to display either a blank or an "8" respectively.

A jump to the label RIGHT changes the state of display number E, where E represents the contents of the extension register. Alternatively, a jump to BACK sets E to the top byte of P3. Initially this will be zero, so when the program is first run display 0 is illuminated; on subsequent times round the loop the top byte of P3 will contain X'01 and so a jump to BACK will change display 1. Each time a key is pressed the program decides whether to jump to RIGHT and change the display corresponding to the key number, or to jump to BACK and change display 1. A jump to RIGHT is only allowed if the key number, E, is less than 2, or if display E is on and all those to the right of E are off (i.e. zero).

From this information, and the program listing, it should be clear how the program works. The names of the winners of the three VDU kits will be announced in the next Micro-Bus.

SELF-REPLICATION AGAIN

In the June 1979 Micro-Bus a nine-statement BASIC program was presented that would list a copy of itself at the terminal. Mr. Langdon Proctor, of Denmark, has pointed out that any BASIC program can be made self-replicating by including a LIST command as of the statements. The program '10 LIST' is thus a one-line solution to the original problem!

readout

... from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope.
Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Faster than light?

Sir—In your May issue of "Practical Electronics" referring to *Industry Notebook* there was mention of the Tektronix 7104 oscilloscope. The trace writing speed is described as "... an almost incredible 20cm/ns." This is a remarkably apt description since the speed of light, 300×10^6 metres/s., is 30cm/ns. by my maths. The combination of forward speed and deflection must put the beam velocity after deflection very close to the velocity of light indeed.

Assuming the stated bandwidth of 1GHz is the 6dB point, the deflection amplifiers should still have some response at 2GHz, requiring a writing velocity above the speed of light. I had always believed that it was, theoretically, impossible to exceed the speed of light but I am now beginning to wonder.

B. Page,
Southend-on-Sea,
Essex.

The extraordinary 7104 is in fact capable of spot velocities exceeding the speed of light even though at this setting the bandwidth specification would have to be exceeded by 500MHz at 3dB.

But Einstein can rest easy as his law has not been violated since the cathode is a continuous source of electrons reaching the swept spot at different points in time, not one electron moving across the scope screen at 30cm/ns.—Ed.

CB suggestions

Sir—I refer to your Editorial in the August issue on the subject of CB radio.

While I believe that those people wishing to use CB are as entitled to a part of the spectrum as anyone else, including the commercial interests, I doubt very much whether any allocation of frequencies, or licence conditions will be found to apply to those so lacking in social conscience as to put at hazard many thousands of pounds' worth of radio-controlled models, and cause interference to other users of the spectrum who have as much right as they to its use.

Having said that, I believe that there are two model control bands, one of which is at UHF, around the 450MHz area. While it will not be compatible with other CB equipment on 27MHz, it will satisfy the object of CB, which I understood in the USA to be "short range person to person communication". I have not seen any equipment for the higher band commercially available, so I could be wrong about this allocation.

The other possibility is to set a final date

for the phasing out of TV transmissions in the 41MHz band (405 line system), and put in a CB allocation, effective on the final date. Secondly, in view of the interference possibility, it could be made a condition of the licence that successful completion of the licence regulations and transmitter interference section of the Radio Amateur's Exam (suitably modified on licence regulations) be proved. Further, that the name and address of purchasers of CB equipment be noted by the seller, as is the case with much Amateur equipment. Of course, the people who are lacking in the consideration for other users mentioned above, will then set up a protest about too many regulations, but having listened to CB USA style, it would surely be preferable to the usual idiocy and sometimes obscenities one hears.

Finally, I would suggest that the address of the Post Office interference investigation department be made widely available, and that a requirement of the complaint be a tape recording of the interference; which should ensure that the offender is known about and found.

Peter J. Brent,
Fareham,
Hampshire.

Sir—In my opinion the reason that CB has not been legalised here is because of the mess left by previous administrations ignoring the CB issue from its inception.

What can Mr Whitelaw do? Conform with the rest of the world and legalise CB on 27MHz, to the wrath of aero modellers who have a great deal of capital tied up in 27MHz equipment. This frequency also has DX problems. Or he could decide to put CB on 230–232MHz, an unused band which would give an excellent service but would create anomalies between the UK and the rest of the world, plus inherent customs difficulties. Which ever way he turns, this is his dilemma; not CB, but where CB.

A few ignorant cranks are still opposed to CB, the sacred cow brigade, who want to hear only their own voices.

I do not believe that a man like Mr Whitelaw feels that the UK citizen is less fit than an Italian, German, Frenchman or Dutchman, to name a few, to operate profitably a CB network in terms of lives saved, property protected and fuel saved.

One thing is certain, CB will flourish within the law or outside it. With proper control CB can start to serve the community like nothing since sliced bread.

Nigel Longbotham,
Cramlington,
Northumberland.

Logical software

Sir—In the August issue of PE a letter—Logical software—by Mr H. S. Lynes expressed the views of many of my friends and myself. This being the use of software to 'replace' lots of hard wired logic for projects like Intelligent House Alarm, Heating Controller, etc.

Microprocessors together with plug-in PROMs (with necessary programs) could "look after" various systems, via interfaces. Appropriate PROMs could be selectable by switches on a PROM card connected to say UK101 via an expansion socket. A cheap PROM programmer could also be interfaced. Using PROMs obviates the need to load programs from cassettes.

I think logical software for UK101 plus hardware would generate interest among your readers who could contribute as well.

That would be making a practical use of a microprocessor rather than using it as an expensive toy for "Star Wars" and "Noughts and Crosses" (after all UK101 costs £219+VAT).

B. Jani,
Tufnell Park,
London.

We hope to be able to publish a good PROM programmer soon after the CompuKIT UK101 series. This will be useful with almost any computer and will plug into COMPUKIT.—Ed.

Newbear 77-68

Sir—I was pleased to see P. Birnie's excellent review of the 77-68 system.

In his review he is critical of the fact that Newbear do not provide BUG 2 in ROM. In fact Newbear provide an alternative monitor board MON 2 which was not mentioned. This board supports MIKBUG or similar monitors in ROM or EPROM.

An alternative to MIKBUG has been developed by Terry Cassell called T-BUG. This monitor, while maintaining MIKBUG compatibility, contains code to drive the VDU board as a scrolling display as well as various useful additions to the MIKBUG range of commands.

The advantage of MON 2 with T-BUG, or even MIKBUG, is that a vast amount of readily available M6800 software may be run, in most cases, unaltered.

My post bag often contains comments from users concerning the difficulty of getting available code to run under a MON 1 board as it has a completely different memory map to MIKBUG.

In my opinion the principal advantage of 77-68 over products such as NASCOM, TRITON and COMPUKIT is that it is very extendable having a backplane/board construction with the bus being well buffered. It turns out to be an eminently modifiable system and most systems are tailored by the constructor in one way or another.

Dr. P. Bryant,
Hon. Editor 77-68 Newsletter,
The Bumbles,
Well Meadow,
Shaw, Newbury.

DUE TO THE SUCCESS OF THIS SPECIAL OFFER METAC ARE REPEATING IT

SPECIAL OFFER!

L.C. DIGITAL ALARM CHRONO

£22.95

Including VAT Postage and Packing

A quality watch at an unbelievable price.

This Lambda l.c.d. alarm chronograph comes with complete instructions, and a worldwide one year guarantee and service network booklet. It is shown full size on this page and has the following functions.

Hours, minutes, seconds; date; day of the week; am/pm indication; stopwatch with 1:10 second readout, split time with automatic reset after six seconds and up to 13 hour capability; flashing stopwatch indication if time is displayed while stopwatch is running; beeping 24 hour alarm which sounds for one minute, continuously cancelled, the display flashes while the alarm is sounding; alarm set indication; simple, "to the second", time and date setting; second watch including seconds, date, day of week and am/pm indication for displaying time in another zone; nightlight; screw section in back to enable quick, simple d.i.y. battery replacement; stainless case and black/stainless bracelet; fully adjustable bracelet to fit wrists from 130mm (5 1/4 in) to 200mm (7 7/8 in) circumference without removal of links.

The alarm is loud enough to wake most people and the dual time zone facility is very useful for foreign phone calls, whilst travelling or just on holiday.

We have been careful with the choice of this watch and have tested it for three months, since we anticipate heavy demand please allow a maximum of 21 days for delivery—more if you live outside the U.K.



Please complete both parts of the coupon in BLOCK CAPITALS

To: METAC Electronics and Time Centre (P.E. Offer)
67 High Street, Daventry, Northants. Tel. 032 72 76545.

Mail order only

Please send me watch/es at £22.95 each

I enclose P.O./Cheque No. Value

Name

Address

Please allow 21 days (maximum) for delivery (more for overseas orders)

Name

Address

From: METAC Electronics and Time Centre (P.E. Offer)
67 High Street, Daventry, Northants.

SCHMITT TRIGGER CIRCUITS

D. F. BOWERS B.Sc.

It is often required, especially in the field of digital control, that a circuit should provide information as to whether an analogue signal is above or below a certain threshold. Where the threshold is fixed, the circuit used is known as a comparator and where the threshold alters in opposition to the circuit output, the circuit is said to have hysteresis. Because such circuits normally switch rapidly (in comparison to the rate of change of input voltage) they have also been classed under the general heading of trigger circuits.

HYSTERESIS

Hysteresis is often required in trigger circuits for one of two main reasons:

- (i) Because available comparator circuits have finite gain, inputs close to the threshold voltage can produce indeterminate outputs or even oscillation. Hysteresis ensures that as signals begin to cross the threshold, the latter itself moves to make the output more decisive.
- (ii) If a relatively slowly changing input is noisy or has ripple superimposed upon it, multiple triggering at the threshold may occur. Adding hysteresis can remove this.

The amount of hysteresis required is dependent on the comparator gain in case (i) and on the ripple magnitude in case (ii).

IDEAL TRIGGER

The ideal trigger can be visualised as a 'black box' as shown in Fig. 1, together with its transfer characteristics.

The output has two distinct states, controlled by the voltage on input. When the input voltage rises above a certain threshold value (V_{ON}) the output assumes the 'on' state and when the input falls below a certain value (V_{OFF}) the output assumes the 'off' state. The value $V_{ON} - V_{OFF}$ is called the hysteresis of the trigger. The input characteristic can thus be specified either by quoting V_{ON} and V_{OFF} or by quoting the mean of these values together with the hysteresis value.

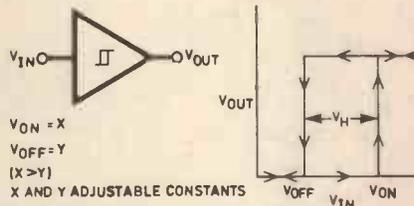


Fig. 1. Ideal trigger with associated transfer characteristic

The latter is sometimes specified as a percentage of the mean threshold.

The output states should correspond to levels compatible with following circuitry, and the input should draw as little current as possible. The threshold values should be both predictable and easily adjustable, and also exhibit high stability. The trigger should switch in as short a time as practicable.

PRACTICAL TRIGGERS

One of the first papers on this subject was presented by Otto H. Schmitt. His trigger circuit had a fixed lower threshold and an adjustable upper threshold, and was basically a long-tailed triode pair with positive feedback. The circuit switched comparatively slowly by present day standards ($\approx 10\mu s$) but was of course much faster than electromagnetic relays which were commonly used instead. Replacing Schmitt's triodes with bipolar switching transistors can speed up the operation ($< 200ns$) and a typical circuit is shown in Fig. 2.

TRANSISTORISED TRIGGER

Assuming TR1 is turned off (V_{IN} low), the base of TR2 is biased at approximately +6.8 volts by the voltage divider R1, R3 and R4. The emitters of both transistors are then at 6.2 volts due to the V_{bc} of TR2. If V_{IN} approaches 6.8 volts, a critical voltage is reached where TR1 begins to conduct and regeneratively turns off TR2. If the input voltage is now lowered below another critical value ($< 5.2V$) TR2 will again switch on.

The present tendency is to refer to all trigger circuits with this type of characteristic as Schmitt Triggers, even if different principles of operation are

employed. Other configurations have f.e.t.s instead of bipolar transistors, or sometimes use complementary devices. Often, a speed up capacitor is included across R3.

DISADVANTAGES

The circuit described has the advantage that the hysteresis level is substantially independent of temperature, but unfortunately is dependent on V_{CC} . The actual thresholds also include a V_{bc} term which is dependent on temperature, and another problem is that the output low voltage is always greater than VR_5 .

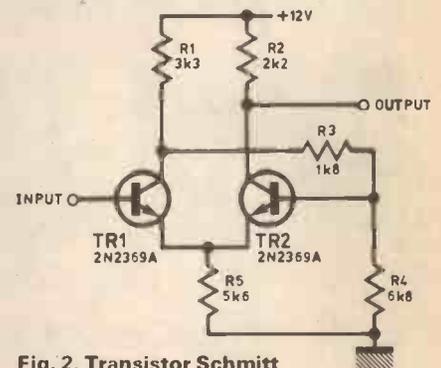


Fig. 2. Transistor Schmitt

The input characteristics are also far from ideal, since the input transistor draws considerably more base current when turned on than when turned off. A resistor is sometimes included in series with V_{IN} to limit this current if V_{IN} rises much above the 'on' threshold.

Added to the fact that the precise thresholds are quite difficult to ascertain, these disadvantages make this configuration somewhat awkward to implement, except in non-critical applications.

All these problems, except perhaps the hysteresis dependence on V_{CC} , can be

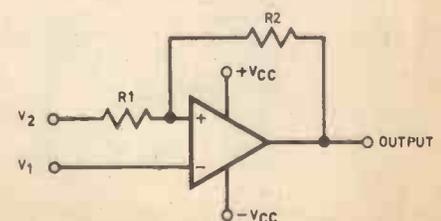


Fig. 3. Op amp Schmitt

alleviated by using operational amplifiers as the active switching element, but switching will generally be slower, since many operational amplifiers can only slew at around $70V/\mu s$, even if uncompensated, and have relatively long propagation delays.

OP AMP TRIGGERS

The use of operational amplifiers greatly simplifies trigger design, especially if the maximum output voltages can be accurately determined. Uncompensated operational amplifiers can generally be used directly and switch much faster than compensated types.

The basic configuration is shown in Fig. 3, and can be used to provide triggers of the inverting, non-inverting or differential type. The voltage at the non-inverting input will be:

$$\frac{R_1}{R_1 + R_2} V_{OUT} + V_2$$

and since the feedback is positive, the output will switch high if:

$$V_2 > V_1 - \frac{R_1}{R_1 + R_2} V_{OUT}(\text{low})$$

and will switch low if:

$$V_2 < V_1 - \frac{R_1}{R_1 + R_2} V_{OUT}(\text{high})$$

So clearly the hysteresis level is given by:

$$V_H = \frac{R_1}{R_1 + R_2} [V_{OUT}(\text{high}) - V_{OUT}(\text{low})]$$

and is symmetric of about the threshold if $V_{OUT}(\text{high}) = -V_{OUT}(\text{low})$ and one of V_1, V_2 is zero. Since most operational amplifiers run off symmetrical supply rails, and can swing very close to them, the formula for a ground referenced trigger becomes:

$$V_{\text{threshold}} = 0V, V_H = \frac{2R_1}{R_1 + R_2} V_{CC}$$

where $V_{CC} = \pm$ supply voltage.

In the inverting mode, V_2 will be grounded and in the non-inverting mode V_1 will be grounded, but note that in the latter case the drive impedance of V_2 should be low compared to $(R_1 + R_2)$ to prevent loading by the output. A Zener clamped output may be used where V_H must be accurately defined (see Fig. 4) and the Zener voltage

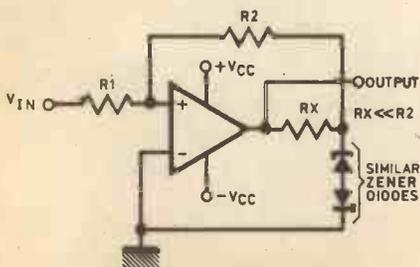


Fig. 4. Trigger with clamped output

plus the Zener forward voltage drop ($\approx 0.7V$) should replace V_{CC} in the hysteresis calculation. In the case of asymmetric output voltages, graphical techniques can greatly ease calculations.

COMPARATORS AS TRIGGERS

It is often desirable to use voltage comparators as triggers, since generally they switch faster than operational amplifiers. Indeed, with some comparators a small amount of hysteresis (1-5mV) is advised because of the finite gain problem mentioned previously.

The same treatment can broadly be given to comparators as for operational amplifiers bearing in mind that many have asymmetric (logic compatible) outputs and occasionally open collector (or emitter) outputs, where the pull-up (or down) resistor comes into the R_2 term in the threshold calculation, in the high (or low) state respectively. Problems also sometimes arise with the propagation delay, which effectively disconnects the positive feedback for the delay period, giving rise to possible instability.

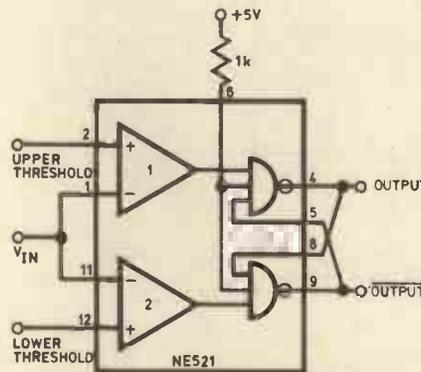


Fig. 5. I.c. programmable trigger

A neat trigger design using a dual comparator is shown in Fig. 5. This circuit enables the upper and lower thresholds to be accurately fixed by external reference voltages, making the trigger very versatile. The two gated outputs of the NE521 are arranged to form an R-S latch, set by comparator 1 and reset by comparator 2. The resulting output thus goes high when the input rises above the upper threshold, and goes low when the input falls below the lower threshold. (This configuration actually forms part of the internal circuitry for the popular 555 timer i.c. which can be used without modification to provide a Schmitt trigger with upper and lower thresholds of $\frac{2}{3} V_{CC}$ and $\frac{1}{3} V_{CC}$ respectively.) Replacing the R-S latch by an external J-K flip-flop ensures that the output only changes in synchronism with a clock pulse, which is often a useful feature. With an external flip-flop, naturally other comparators can be used instead of the 521.

TRIGGERS WITHIN LOGIC DESIGNS

An important application of trigger circuits is in logic interfacing where the signals presented to the logic must conform to specifications regarding level and risetime. Analogue signals from photocells, thermistors, etc., are clearly unusable directly, for both reasons. Quite often any trigger used will be required to operate from the logic supply voltage and preferably use as few discrete components as possible, especially where many triggers are used for mundane applications (such as R-C switch debouncing). The two most common logic systems (CMOS and TTL) will be considered here.



Fig. 6. Trigger formed from CMOS inverters

CMOS LOGIC TRIGGERS

Since CMOS gates have a very high input impedance and reasonable gain, it is possible to use them as switching elements in Schmitt triggers, in much the same manner as operational amplifiers are used. A common (non-inverting) configuration is shown in Fig. 6, using two CMOS inverters. Positive feedback is applied via R_1 , and the typical hysteresis obtained is tabulated in Fig. 7. The actual threshold is dependent on the switching point of the first inverter ($\frac{V_{DD}}{2} \pm 40\%$)

and is thus somewhat indeterminate, although reasonably stable with changes in temperature. The hysteresis tends to act symmetrically about the threshold provided this is fairly close to V_{DD} . The threshold can be shifted by means of a resistor connected between the input to the first inverter and V_{DD} or ground.

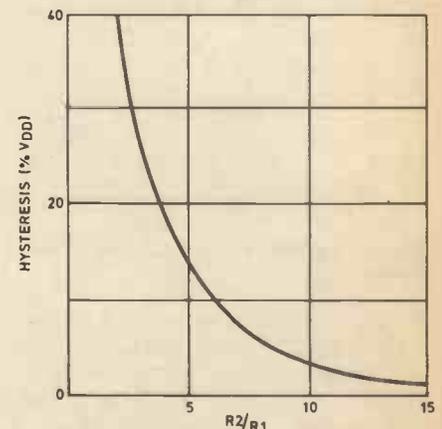


Fig. 7. Graph of hysteresis

Another method of using gates as triggers (Fig. 8) utilises the interdependence of switching characteristics between inputs of a multiple input gate. Varying

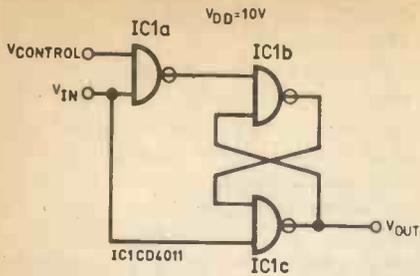


Fig. 8. Trigger utilising interdependence of CMOS gate inputs

$V_{Control}$ alters the input characteristics of gate I, which determines the upper switching point is determined by the input characteristics of IC1c, and is independent of $V_{Control}$. Thus varying $V_{Control}$ alters the hysteresis, typical values being shown in Fig. 9. Similar remarks about the threshold apply as for the previous example, but in this case the hysteresis acts asymmetrically, tending to raise the threshold. Replacing the NAND gates with NOR gates causes the hysteresis to lower the threshold. Note the similarity of this configuration to the circuit of Fig. 5.

INTEGRATED CMOS TRIGGERS

The CMOS logic families include several Schmitt triggers all intended for interface of noisy or slowly changing input signals. In general, these triggers feature very high noise immunity, unconditional input stability, and very high input impedance. On the black side, all have relatively long propagation delays (up to 600ns for the CD4093B) and poor threshold stability with respect to supply voltage.


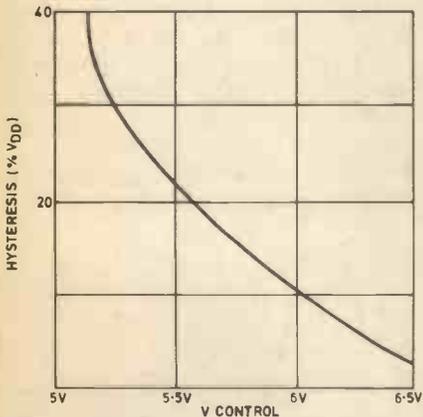


Fig. 9. Varying hysteresis with control voltage

Typical fixed-threshold triggers are the CD40106 and CD4093B. The CD40106 is a hex-inverting trigger (Fig. 10) featuring good threshold and hysteresis stability with changes in temperature. Fig. 11 shows typical threshold values for three different supply voltages for each individual trigger. The CD4093 is a quad trigger each of which has two inputs, functionally equivalent to a NAND gate. The threshold

levels are the same as for the CD40106 provided one input is tied to V_{DD} , but are raised slightly if both inputs are used. Typical hysteresis remains unchanged.

Another interesting trigger is the MC14583, which obtains its trigger effect using three resistors to control the transfer characteristics of an inverter. By varying these three resistors the threshold can be externally controlled. The 14583 comes in a dual package and also features non-inverting, inverting tri-state and EXCLUSIVE OR-ed outputs, making it especially useful as a transmission line receiver.

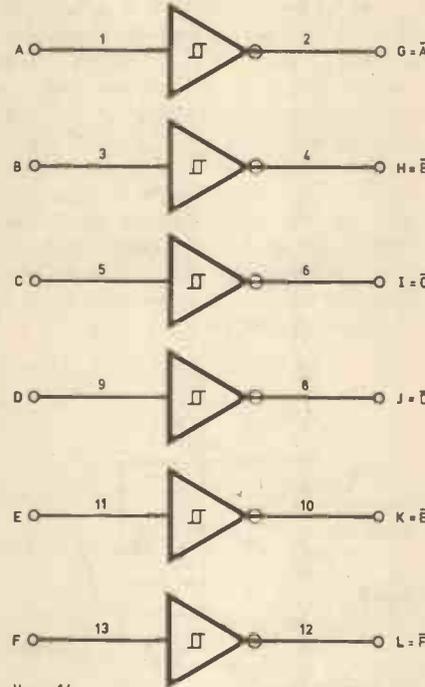

$V_{DD} = 14$
 $V_{SS} = 7$

Fig. 10. CD40106 hex inverting Schmitt trigger

V_{DD} (V)	5	10	15
V_{ONMAX}	3.6	7.1	10.8
V_{ONMIN}	2.2	4.6	6.8
V_{OFFMAX}	2.8	5.2	7.4
V_{OFFMIN}	0.9	2.5	4.0
V_{HMAX}	1.6	3.4	5.0
V_{HMIN}	0.3	1.2	1.8

Fig. 11. Switching characteristics for the CD40106

TTL SCHMITT TRIGGERS

The TTL 7400 series features three Schmitt triggers, all three available in standard and low power Schottky versions, and one (74S132) available in standard Schottky. Additionally, several other TTL i.c.s feature Schmitt characteristic inputs for reasons mentioned below. All these triggers feature temperature compensated hysteresis (typically less than 2% variation over the military temperature range). Propagation delay is around 15ns for the standard and low-power Schottky versions, and around 8ns for

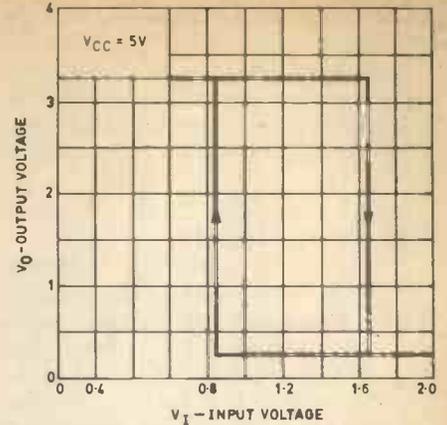


Fig. 12. Switching characteristics for the 7400 Schmitt trigger family

the Schottky versions, making them fairly fast devices. The 7414 (74LS14) is a hex inverting trigger, the 7413 (74LS13) is a dual 4-input NAND trigger and the 74132 (74LS132), is a quadruple 2-input NAND trigger.

All have the typical switching characteristic shown in Fig. 12, and have the usual TTL input current source characteristics, making them low input impedance circuits.

OTHER TTL DEVICES

A fairly common use of Schmitt triggers is as digital line receivers, where line capacitance and interference produces poor signal edges and noisy information. As a result, many line receivers have intrinsic hysteresis to sharpen up signal edges and to eliminate spurious noise signals. Some examples are the 74LS242 transceiver from the 7400 series, 75152 dual receiver (with adjustable hysteresis) from the 7500 series, and also the AMD 1489 (quad) and N8T37 (hex) line receivers.

Other functions occasionally incorporate Schmitt triggers, an example being the 74221 dual monostable multivibrator which will thus trigger reliably from inputs with transition rates as slow as 1 volt/second.


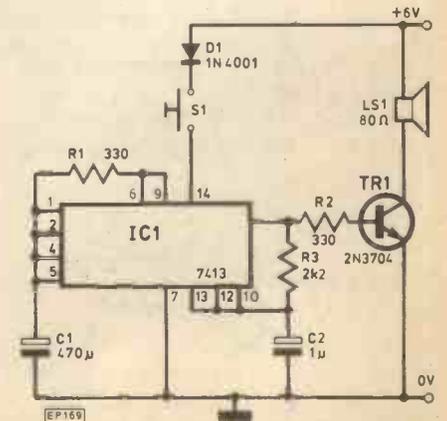


Fig. 13. Doorbell circuit employing dual Schmitt triggers

Three Trumps from Acorn

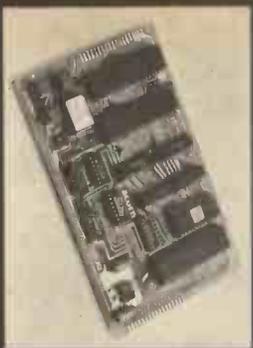


Acorn Controller

Designed as an industrial controller module, it is based on the 6502 CPU with 2K Eprom, 1.25K Ram and 32 I/O lines. In eurocard format it is provided with an onboard monitor (2 x 74SS571) giving comprehensive development and debugging facilities. Also available in minimum configuration for low cost DEM applications.

The Acorn Microcomputer

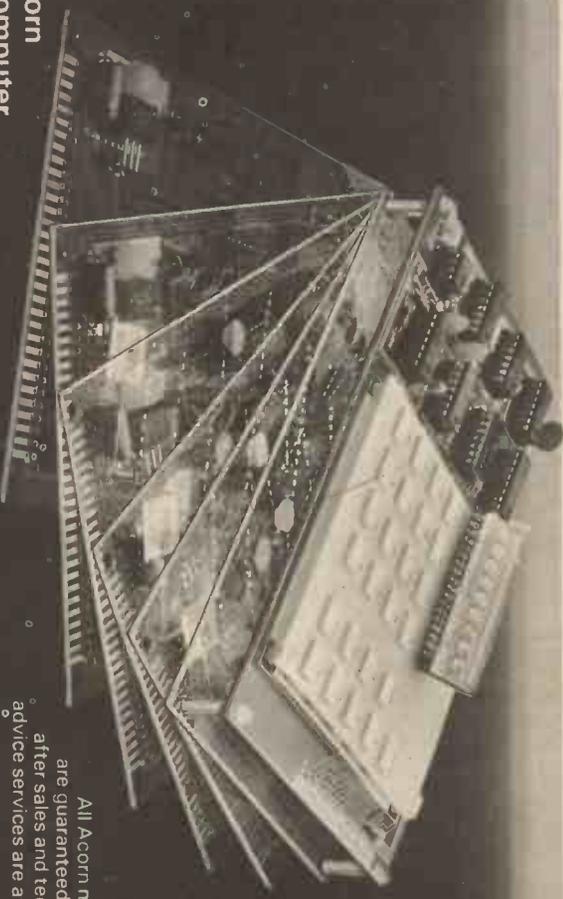The Acorn controller module mounted beneath a matching eurocard with hex keyboard, 8 digit seven segment display and CUTS tape interface requires only a single unswitched power supply to form the powerful Acorn microcomputer.



Although designed for expandability the Acorn Microcomputer is a complete development system for the Acorn controller and together with the Acorn Users Manual provides the perfect introduction to hex programming; the carefully optimised monitor has the following functions:

- System Program
- Set of sub-routines for use in programming
- Powerful de-bugging facility displays all internal registers
- Tape load and store

All Acorn modules are guaranteed and full after sales and technical advice services are available.

Acorn Memory

The first in our series of expansion cards is the Acorn 8K + 8K "state of the art" memory module. On a matching eurocard it provides 8K of ram (2 1 1 4) and 8K of Eprom (2 7 3 2) or 4K of Eprom (2 7 1 6). It requires a single 5V rail, is designed for direct connection via a 3.2 way edge connector to the Acorn bus and is fully buffered for wiring into any system. Two onboard sockets provide independent positioning of Eprom and ram.



ACORN COMPUTERS LTD.

4A Market Hill, Cambridge, Cambs.

Order form

- Send to: Acorn Computers Ltd, 4A Market Hill, Cambridge, Cambs.
- (qty) Acorn Microcomputer(s) in kit form at £65.00 plus £9.75 VAT
 - (qty) Acorn Microcomputer(s) assembled and tested at £75.00 plus £11.25 VAT
 - (qty) Acorn controller(s) (minimum configuration) at £35.00 plus £5.25 VAT
 - (qty) Acorn Memory(s) assembled and tested at £95.00 plus £14.25 VAT
- N.B. Price shown is for full 8K of ram, prices for smaller memory options and Eprom additions available on request.
- I enclose a cheque for £..... made out to Acorn Computers Ltd.


Name _____

Address _____

P.E. 10 _____



Regd No
1403810

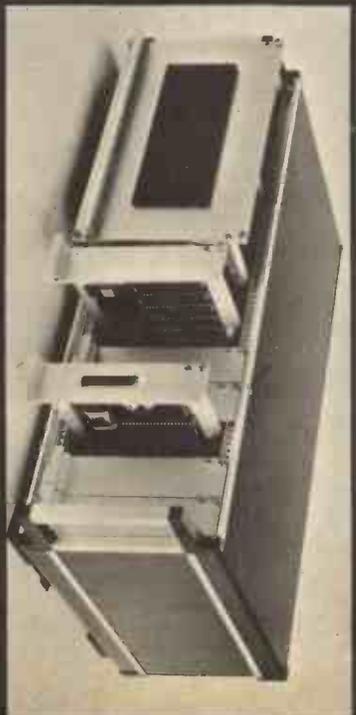

Software available soon includes 4K Editor-Assembler-Disassembler, 4K Proprietary Fast Basic, Disc operating system with full file handling.

Although a standard strip of

veroboard is all that is required for a full backplane, a racking system can be made available by Acorn Computers. The rack shown includes the VDU interface, two memory cards and dual floppy disc interface.

Just a little bit more... NASCOM-2



Compare its features:

- *Z-80A 4MHz. CPU: The most powerful 8-bit processor on the market.
- *8K Basic: resident on board, MICROSOFT Basic, the industry standard, with extensions for on-screen editing, graphics, machine code interfacing. Optimised for speed (see benchmarks below).
- *Full 57 Key Licon solid state keyboard: switch mechanisms are contactless, high reliability professional units for long trouble free life. Keyboard is mounted separately to avoid straining main P.C.B.
- *Total of 20K on-board memory: 2K monitor (Nas-Sys 1), 1K Video RAM, 1K Work space RAM, 8K Microsoft Basic, 8K user RAM.
- *Kansas City cassette interface: for reliable storage of programs and data at 300 or 1200 baud, with full checksum error detection.
- *Nas-sys monitor: A powerful 2K machine code monitor provides an ideal environment for learning about and developing machine code programs. Nas-sys uses a blinking non destructive cursor, with 22 commands. ASCII terminals are fully supported via the serial interface; users can add their own I/O drivers via the system I/O vector table to support other devices.

Nas-sys commands are:

- | | |
|-------------------------------------|-----------------------------|
| A—Hex arithmetic | N—return to normal |
| B—set breakpoint | O—Output to P.I.O. |
| C—Copy | Q—Query input port |
| E—Execute | R—Read tape |
| G—Generate | S—Single step |
| H—Operate as half duplex, terminal. | T—Tebulate memory |
| I—Intelligent copy | U—activate user I/O drivers |
| J—Execute at FFA | V—Verify tape |
| K—set keyboard options | W—Write tape |
| L—load from tape | X—set external device |
| M—Memory modify | Z—execute at FFD |

- *On board P.I.O. — An uncommitted P.I.O. (MK 3881) giving 16 programmable I/O lines with handshake.
 - *On board RS-232C Will interface directly into any standard teletype — allowing use of BASIC or Nas-sys from the teletype.
 - *Full on-screen editing: a complete screen editor with cursor movement (UP, DOWN, LEFT, RIGHT), insert and delete, backspace etc.
- Screen display of 16 lines x 48 characters: Stable, clear display to British televisual standards. Full 128 ASCII character set; option for further 128 graphics characters.
- *Fully buffered NASBUS compatible: Well defined bus structure with a range of expansion cards; including (shortly) a floppy disc system with CP/m — the industry standard operating system.

	Nett	Vat	Total
Nascom-2	295.00	44.25	339.25
Power supply	24.50	3.68	28.18

PERSONAL COMPUTER WORLD BENCHMARK TESTS

	Nett	Vat	Total
Nascom-2	295.00	44.25	339.25
Power supply	24.50	3.68	28.18
10 C15 cassettes	4.44	0.66	5.10
Z-80 Programming manual (Mobotek)			5.10
Z-80 Microcomputer handbook			6.95
Practical microcomputer programming the Z-80			20.00
Sargon-8K Z-80 Chess program (book)			9.50

	1.5	1.1	1.4	1.7
BM 1	1.5	1.1	1.4	1.7
BM 2	3.2	5.4	6.5	9.9
BM 3	7.3	11.1	13.2	18.4
BM 4	7.2	11.6	13.9	20.4
BM 5	6.9	12.6	15.0	21.7
BM 6	18.6	19.3	22.3	32.5
BM 7	28.2	27.6	31.8	50.9
BM 8		5.2	6.2	12.3



MICRODIGITAL

25 Brunswick Street, Liverpool L2 0BJ
Tel: 051-236 0707 (Mail Order) 051-227 2535 (All other Depts)

PE

ASTRA-PAK

92 GODSTONE ROAD
WHYTELEAF SURREY CR3 0EB

VAT must be added at 15% to all prices shown. P&P 25p + VAT. Send SAE for full catalogue including books, resistors, capacitors, vero, etc.

7400	0.10	7483	0.58	74166	0.78	4021	0.80	4160	1.05	LINEAR		16 pin	0.12
7400	0.23	7484	0.88	74187	2.00	4022	0.80	4161	1.05	CA3045-14	0.40	18 pin	0.16
7401	0.11	7485	0.68	74170	1.50	4023	0.15	4162	1.05	CA3046-14	0.50	20 pin	0.18
7402	0.11	7486	0.22	74172	6.30	4031	0.50	4163	1.05	LM309-14	0.85	22 pin	0.22
7403	0.11	7489	0.42	74173	1.15	4025	0.15	4164	1.05	LM381N-14	1.40	24 pin	0.24
7404	0.11	7489	1.65	74174	0.85	4026	1.16	4174	1.05	LM710-14	0.30	28 pin	0.26
74M04	0.23	7490	0.32	74175	0.60	4027	0.42	4175	0.98	LM711N-14	0.30	40 pin	0.37
7405	0.12	7491	0.64	745175	1.00	4028	0.65	4194	1.05	MC130P-14	0.88	81LS89	1.25
74M05	0.23	7492	0.36	74176	0.58	4029	0.76	4404	0.48	NE555-8	0.20	81LS89	1.25
7406	0.22	7493A	0.30	74177	0.58	4030	0.46	4412	0.19	NE558-14	0.50	81LS97	1.25
7407	0.22	7494	0.72	74178	1.80	4031	1.85	4428	0.38	LM339-14	0.80	81LS97	1.25
7408	0.13	7495	0.50	74179	1.50	4032	0.60	4445	0.90	SN75110N	0.40	MICROPROCESSOR	
7409	0.13	7496	0.48	74180	0.85	4033	1.25	4449	0.19	SN76003N	1.60	CRYSTALS	
7410	0.11	7497	1.90	74181	0.58	4034	1.15	4501	0.18	SN76013N	1.25	FREQUENCY	
74M10	0.23	74100	0.85	74182	0.70	4035	1.00	4502	0.80	SN76023N	1.25	Mhz	
74M11	0.17	74104	0.39	745182	1.50	4036	2.70	4503	0.68	SN76033N	1.60	0.100	3.50
74M12	0.15	74105	0.38	74H183	0.75	4037	0.85	4506	0.50	SN76077N	2.50	0.252	3.50
7413	0.24	74107	0.26	74184	1.30	4038	0.95	4507	0.50	TA5550B	0.32	0.300	3.50
7413	0.24	74109	0.32	74185A	1.30	4039	2.75	4508	2.50	TA6618	0.88	1.000	3.25
7414	0.50	74110	0.36	74186	5.00	4040	0.58	4510	0.82	TBA120S	0.66	1.008	3.25
74H15	0.23	74111	0.58	74188	2.70	4041	0.72	4511	0.82	TBA641A	1.50	1.8432	3.50
7418	0.23	74113	0.30	74190	0.58	4042	0.67	4512	0.82	TBA800	0.78	2.000	3.25
7417	0.23	74116	1.50	74191	0.88	4043	0.80	4513	1.85	TBA810S	0.75	2.097	3.25
7420	0.11	74118	0.80	74192	0.82	4044	0.80	4514	2.30	TBA820S	0.88	2.457	3.25
7421	0.20	74119	0.50	74193	0.82	4045	1.25	4515	2.60	TC27050	1.60	3.278	2.60
7422	0.16	74120	0.95	74194	0.62	4046	1.05	4516	0.99	TOA2020	3.00	3.579	2.60
7423	0.21	74121	0.25	74195	0.80	4047	0.85	4517	3.75	ZN414	0.80	3.932	2.60
7425	0.23	74122	0.39	74196	0.72	4048	0.48	4518	0.90	VOLTAGE	4.000	2.60	
7428	0.23	74123	0.38	74197	0.58	4049	0.33	4519	0.90	REGULATORS	4.433	2.60	
7427	0.74	74125	0.32	74198	1.00	4050	0.40	4520	0.95	LM300M-T099	0.75	4.315	2.60
7428	0.26	74126	0.35	74199	1.20	4051	0.72	4521	2.20	LM309K-T03	1.30	5.000	2.60
7430	0.11	74128	0.75	74221	1.30	4052	0.72	4522	1.25	uA723-1.4	0.32	5.068	2.60
AS330	0.23	74130	0.50	74273	2.05	4053	0.72	4526	1.25	7805-T0220	0.70	5.185	2.60
7432	0.22	74132	0.55	74278	1.65	4054	1.00	4527	1.40	7812-T0220	0.70	5.875	2.60
7433	0.30	74134	0.38	74279	1.10	4055	1.05	4528	0.82	7815-T0220	0.70	6.000	2.60
7437	0.21	74135	0.70	74283	1.65	4060	1.00	4529	1.30	7824-T0220	0.70	6.144	2.60
7438	0.21	74136	0.52	74284	3.40	4061	0.48	4530	0.78	7905-T0220	0.78	6.553	2.60
7440	0.12	74137	0.80	74293	1.30	4067	3.25	4531	0.99	7912-T0220	0.78	8.000	2.60
7441	0.50	74141	0.55	74298	1.80	4068	0.20	4532	1.20	7915-T0220	0.78	8.867	2.60
7442	0.40	74142	1.95	74390	1.75	4069	0.17	4534	5.20	LOW PROFILE	10.000	2.60	
7443	0.70	74143	2.50	74393	1.25	4070	0.17	4538	3.80	OIL SOCKETS	13.000	2.60	
7444	0.70	74144	2.50	CMDS		4071	0.17	4539	1.25	8 pin	0.09	12.516	2.60
7445	0.52	74195	0.55	4000	0.13	4072	0.45	4539	0.99	14 pin	0.11	18.000	3.25
7446	0.60	74147	1.40	4001	0.15	4073	0.17	4541	1.95	LED'S			
7447	0.48	74148	1.25	4002	0.15	4075	0.17	4543	1.50	RED	0.25"	0.2"	
7448	0.56	74150	0.58	4006	0.85	4076	0.84	4549	3.92	RED	0.85	0.09	
7450	0.11	74151	0.48	4007	0.16	4077	0.21	4553	3.60	RED	0.14	0.14	
7451	0.11	74153	0.48	4008	0.78	4078	0.18	4554	1.25	GREEN	0.14	0.14	
7452	0.23	74154	0.82	4009	0.40	4079	0.17	4555	0.75	GREEN	0.25	0.35	
7453	0.11	74155	0.50	4010	0.40	4082	0.18	4556	0.75	LED clip			
7454	0.11	74156	0.50	4011	0.15	4085	0.63	4557	3.25	TMS 4030 4096 BIT DYNAMIC RANDOM ACCESS (2107A) MEMORY 21 PIN DIL			
7460	0.11	74157	0.50	4012	0.15	4086	0.63	4558	1.25	300ms max. access time. 470ns max. read or write cycle time. TTL compatibility on all inputs. No pull up resistors needed. Low power dissipation. 350mV operating 0.3mA standby. Single low capacitance clock. Data sheet available			
7470	0.25	74158	0.68	4013	0.40	4089	1.35	4559	3.85	2.40 each - 4-10% 8-20%			
7472	0.22	74159	1.90	4014	0.78	4093	0.80	4560	1.98				
7473	0.25	74160	0.60	1165	0.70	4094	1.88	4561	0.72				
7474	0.25	74161	0.58	4018	0.60	4095	0.50	4562	5.50				
7474	0.42	74162	0.62	1017	0.72	4096	0.90	4566	1.42				
7475	0.30	74163	0.82	4018	0.75	4097	0.30	4568	2.50				
7476	0.26	74164	0.68	4019	0.42	4098	0.95	4569	1.60				
7480	0.43	74165	0.68	4020	0.88	4099	1.40	4580	4.98				

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln. LN2 1JF. TEL: 20767

- TUBULAR TANTALUM CAPACITORS 4-7uf 10v.w., 6 for 25p.
- MOULDED TRAP POTENTIOMETERS 1K or 10K Lin at 20p each.
- UNIUNION TRANSISTORS 2N 4871 • 22p, 2N 6028 • 25p, 2N 6029 • 25p, MEU 21 • 22p, MU 4894 • 22p, TIS 43 Type • 22p, 4JD5E29 • 22p.
- SILICON BRIDGES 100 PIV 1 amp • 20p, 200 PIV 4 amp • 60p, 50 PIV 20 amp • £1.30.
- IRON CORE I.F. CHOKE 2 M.H. 4 amp • 50p. (P&P 20p).
- ALLOY DIE CAST BOXES 8" x 3-3/4" x 2" • £1.18, 6" x 4" • £2.85.
- LOUDSPEAKERS 3" 150 ohm • £1.10, 1 1/2" 8 ohm • 85p.
- THYRISTORS (S.C.R.'s) 10 Amp Type 100 PIV • 25p, 800 PIV • 60p, 800 PIV • 60p.
- MYLAR CAPACITORS -0.1uf or -1uf 50v.w. Both 22p doz.
- 50- OC 71 TRANSISTORS untested for 75p.
- 10 ASSORTED PUSH BUTTON BANKS less knobs for £1.30.
- 10 ASSORTED SLIDER POTENTIOMETERS for £1.
- 50 1 AMP S.C.R.'s T05 case untested • £1.
- 25 STUD MOUNTING 10 AMP DIODES untested • 60p.
- 50 2 WATT ZENERS assorted untested • 60p.
- 10 20 AMP STUD MOUNTING DIODES untested • 60p.
- 25 THYRISTORS (S.C.R.'s) 5 amp type untested for 75p.
- 3 PIN PLUG-SOCKET European type with 2 mtrs. of cable • 75p.
- SUB-MINIATURE 24 VOLT 2 POLE CHANGE OVER RELAY • 60p.
- CLOSE TOLERANCE CAPACITORS 1288pf, 1670pf, 5979pf, 15669pf. All 1% at 5p, -0.1uf 2%, -1uf 1%. Both 8p.
- MULLARD TYPE 424-41103 -0.11uf 63v.w., 5% at 20p doz.
- HIGH SPEED SILICON DIODES BAW 62 • 12 for 35p.
- METAL FILM RESISTORS all 0-5% tolerance, 100R, 150R, 910R, 1K, 3K, 10K, 150K, 200K, 600K. All 8p each.
- TRANSISTORS ARRAY CA 3046 at 40p each.
- WIRE ENDED DIODE 50 PIV 2 1/2 amp • 7p, 6 for 25p.
- TV S.A.W. FILTERS untested. 3 for 35p.
- MOB PRE-AMP LIFERS 1 i.c. with data TAA 320 • 35p.
- POLYESTER CAPACITORS -1uf 400v.w. at 25p doz.
- 50 BC 107-8-9 TRANSISTORS assorted untested • 60p.
- 50 PLASTIC NPN-PNP TRANSISTORS untested • 60p.
- 50 PLASTIC ZTX NPN SERIES untested for 60p.
- SILICON SOLAR CELLS -5 volt 5mA • 40p.
- TANTALUM CAPACITORS -1uf 35v.w., -22uf 35v.w., -33uf 35v.w., -47uf 35v.w., 1uf 35v.w., 2-2uf 35v.w., 3-3uf 16v.w., 4-7uf 35v.w., 6-8uf 35v.w., 10uf 10v.w., 10uf 25v.w., 22uf 16v.w., 33uf 10v.w., 33uf 25v.w., all at 9p each. 100uf 10v.w., • 25p.
- STUD MOUNTING DIODES 100 PIV 10 amp • 15p, 100 PIV 20 amp • 25p.
- 50 NPN 100 VOLT 800mA TRANSISTORS type 2N 657 • 25p.
- WIRE WOUND POTENTIOMETERS 2 watt, 2K or 10K, 4 watt 100K

Cambridge Learning Enterprises

SELF-INSTRUCTION COURSES

UNDERSTANDING DIGITAL ELECTRONICS

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

The Algorithm Writer's Guide


explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

NEW from Cambridge Learning Enterprises

O - LEVEL ENGLISH LANGUAGE

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on COMPREHENSION, Book 2 covers SUMMARY, PUNCTUATION & SPELLING, and Book 3 coaches you in the principles of COMPOSITION. Size: 3 A4 volumes totalling 250 pages.

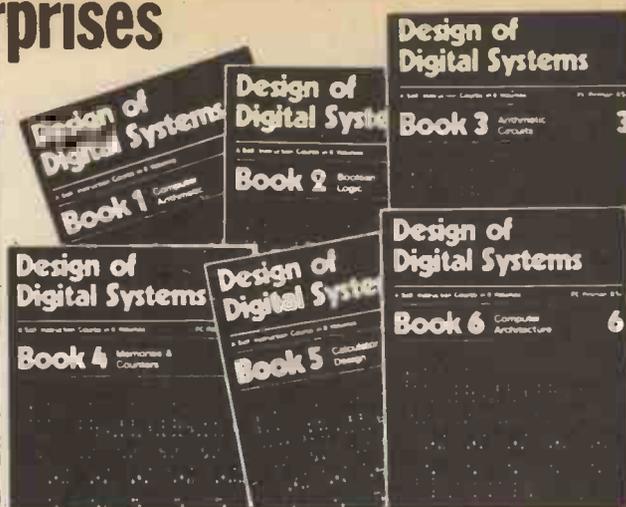CAMBRIDGE LEARNING ENTERPRISES, UNIT 23 RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND
 TELEPHONE: ST. IVES (0480) 67446.
 PROPRIETORS: DAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES
 REGD. IN ENGLAND No. 1328762



Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Four volumes Digital Computer Logic & Electronics at £6.50 inc
 Six volumes Design of Digital Systems at £10.50 inc p & p
 Three volumes O-Level English Language at £6.50 inc p & p
 The Algorithm Writer's Guide at £3.40 inc p & p

If your order exceeds £14 deduct £2 from your payment

Price includes surface mail anywhere in the world, airmail extra
GUARANTEE If you are not entirely satisfied your money will be refunded
 Please allow 21 days for delivery

Cambridge Learning Enterprises, Unit 23 Rivermill Site,
 FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR,
 England.

Please send me the following books:
 sets Digital Computer Logic & Electronics at £6.50, p & p
 sets Design of Digital Systems at £10.50, p & p included
 O-Level English Language at £6.50 p & p included
 The Algorithm Writer's guide at £3.40, p & p included

Name
 Address

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number

Signature *delete as appropriate.
 Telephone orders from credit card holders accepted on 0480-67446 (Ansafo). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

PE23

AITKEN BROS

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729



EXP300



P86 Kit

EXP300

550 contacts with two 50-point BLIS bars. Size 152x53mm. £6.95.
PROTO-BOARD 6 KIT
630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10.98.

CSC LOGIC PROBES

LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. £20.95.

LP-1 Memory Probe £38.65
LP-3 High Speed Memory Probe £56.75

CSC catalogue available. Please send S.A.E.

CALSCOPE SUPER 6 £186-30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1μs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

TE20D TECH R.F. SIGNAL GENERATOR

Accurately covers 120 KCS to 500 MCS in 6 bands. Directly calibrated. Variable RF attenuator 240 VAC. Size 140x215x170mm.

Price £52-50 (£50-58 to callers).

TE22D TECH AUDIO GENERATOR

Sine & square wave audio generator. Sine wave range -20 cps to 20K cps in four bands.

Square wave range 20 cps to 15K cps in four bands 240V A.C. Size 140x215x170mm.

Price £63-31 (£61-31 to callers).

TMK 500 MULTIMETER 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts. 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50μa, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to +56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included.

PRICE £25-95.

CSC EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.



SINCLAIR DM350 £79-95
SINCLAIR DM450 £114-95

Size 255x148x40mm.
DM350 3 1/2 digit display DM450 4 1/2 digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (100μV on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

Sinclair PMM200 frequency meter
Size 157x76x32mm.
Range 20Hz to 200MHz. Accessories and illustration as for PDM35 above. £67-95.

SINCLAIR PDM35 DIGITAL POCKET MULTIMETER
DC volts (4 ranges) 1MV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £34-95. AC Adaptor £3-95 de luxe padded carrying case £3-50 MN 1604 Battery £1-14. Size 157x76x32mm.

SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER.
DC volts (4 ranges) 1MV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1μa to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. PRICE £57-95. Carrying case £9-95. AC adaptor/charger. £4-50. Rechargeable Battery Pack. £9-70. Size 255x148x40mm.


PANEL METERS
DIMS 60MM x 45MM. 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac. 'S', 'VU', 50-0-50μa, 100-0-100μa, 500-0-500μa. PRICE £5-95.

DESOLDERING TOOL SUCTION PUMP. £8-45

Education Establishment Orders Accepted.
PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10.
ALL PRICES INCLUDE POSTAGE AND VAT.

ELECTROVALUE

Your leading direct suppliers for

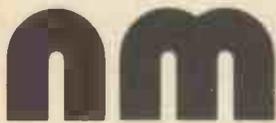

NASCOM MICROCOMPUTERS AND FULL SUPPORTING RANGE OF ITEMS TO ENABLE YOU TO WORK AT PROPER PROFESSIONAL LEVELS

- ★ Appointed Nascom stockists
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

We are also appointed distributors for the fine products of:

SIEMENS, ISKRA, RADIOHM, VERO AND MANY OTHER FAMOUS MANUFACTURERS

It's a good deal better from

ELECTROVALUE LTD

Dept. PE10, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.
Phone: Egham 3603. Telex 264475.
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

- We pay postage
in U.K. on orders list value £5 or over. If under, add 27p handling charge.
- We give discounts
on C.W.O. orders, except for a few items marked Net or N in our catalogue price list.
5% on orders, list value £10 or more
10% on orders list value £25 or more.
Not applicable to Access or Barclaycard orders.
- We stabilise prices.
by keeping to our printed price lists which appear but three or four times a year.
- We guarantee all products brand new, clean and to maker's spec. No seconds, no surplus.
- WE WILL SEND YOU OUR 120-PAGE PRINTED CATALOGUE No. 9 FREE ON REQUEST.
Comprehensive, informative, very well produced. Write, phone or call for your free copy, together with latest price list. (Available separately).

MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250 MA.

1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY 90p. 3 for £2.20.

1000 uf, 100V, Radial, 1 1/2" x 2". ONLY 70p. 3 for £1.50.

BD131's 4 for £1.00

<p>Don't Let Your Environment Dehydrate You! Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive. 1/8" shaft. 250V, 3.75A Contacts. Ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 90p ea. 3 for £2.</p>	<p>SMOKE AND GAS DETECTOR Uses TGS 105 plug in sensor, housed in neat 3 1/2" die cast box, led indicator. 24V, (12V by altering 3 component values). Will operate lamp or relay, with date and circuit. £8.95 Relays for above £1 ea. state voltage</p>
<p>CASSETTE MOTORS Self Regulating, will operate 6-12V Ideal for models, mechanical switching etc. 2000 R.P.M. approx. 80p ea.</p>	<p>TRANSISTOR PACKS 100. Full spec. new and marked includes BC148, BC184L, MED412, BF274, BC154 etc. etc. £4.95 200 as above and includes AC128, 2N3055, BFY50, BD131, BF200 etc. £9.95 Buy bulk and save money, these packs are worth at least double.</p>
<p>ULTRASONIC TRANSDUCERS Transmitter and receiver, 40 kHz 14 mm diam. £4.25 pair.</p>	<p>P/B SWITCH BANKS These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi point etc etc. Can be modified. Can't be repeated. 3 Banks for £1</p>
<p>6 x 6 POLE REED RELAYS ON BOARD 12V ideal for burglar alarms, model railways etc. £2.45</p>	<p>BULK BARGAINS. STOCK UP FOR SUMMER 300 mixed 1/4 & 1/2 watt resistors £1.50 150 mixed 1 & 2 watt resistors £1.50 300 mixed capacitors, modern, most types £3.30 100 mixed ceramic and plate caps £1.20 400 mixed 7 1/2m resistors £2.95 100 mixed polystyrene caps £2.20 25 pots and presets £1.50 25 presets, skeleton etc. £1.20 20 VDRs and thermistors £1.20 100 Hi-wattage resistors wirewound etc. £2.20 100 electrolytics, nice values £2.20 300 printed circuit resistors £1 300 printed circuit components £1.50</p>
<p>100 MINIATURE REED SWITCHES We are the cheapest! £3.30</p>	<p>100K MINIATURE THUMBWHEEL SLIDER POTS Very neat, can be banded side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1 100K STEREO SLIDER POTS Good quality, 25p ea. 5 for £1</p>
<p>G.E.C. UHF TRANSISTOR TV TUNERS Rotary type with slow motion drive, leads and aerial socket. £1.50 3 for £3.50</p>	<p>MINIATURE LEVEL/BATT. METERS 200μA F.S.D. as fitted to many cassette recorders 60p</p>
<p>MAKE CHEAP BATTERY ELIMINATORS Fully shrouded mini mains transformers. 240V in 0-0-8V at 100 MA out. Complete with mains lead and plug, as new equip. 80p</p>	
<p>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS Includes 150 sq. ins. copper clad F/G. board, 1 lb ferric chloride, 1 dolo etch resist pen. Abrasive cleaner, Etch tray plus instructions. Special Price £4.95 1 lb FE. C1. To mil spec. £1.25 5 lb FE. C1. To mil spec. £5.00 150 sq. in. Single sided board £2.00 150 sq. in. Double sided board £3.00</p>	

40p P & P on all above items. Cheque or P.D. with order to:

SENTINEL SUPPLY, DEPT. P.E.
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch. Very slim, only 6mm thick.



M1

SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins, secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

QUARTZ LCD 11 Function

SLIM
CHRONO

6 digit, 11 functions. Hours, mins, secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins., Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price



£10.65 Thousands sold! Guaranteed same day despatch. M3

QUARTZ LCD ALARM 7 Function

Hours, mins, secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

MULTI ALARM 6 Digits 10 Functions

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65



M5

FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet. Guaranteed same day despatch



£22.65

M6

SOLAR QUARTZ LCD Chronograph with Alarm

Dual Time Zone Facility
6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec., steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.



£27.95

M7

ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£29.65



M8

SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins, secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65

Guaranteed same day despatch.



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDEX glass. List Price £130.00

METAC PRICE

£105.00



M10

SEIKO MEMORY BANK

Calendar watch M354
Hours, mins., secs. Month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display month, year and all dates for any selected month over 80 year period. Memory bank function. Any desired dates up to 11 can be stored in advanced. 2 year battery life. Water resistant. List Price £130

Metac Price **£79.50** M11



M11

SEIKO-STYLE Dual time-alarm Chronograph

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

£35.00



M12

HANIMEX Electronic LED Alarm Clock



Features and Specification:
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

£9.65 Thousands sold!

Mains operated.

Guaranteed same day despatch.

M13

HANIMEX portable LCD clock radio



- Time set & alarm controls.
- Snooze & sleep controls.
- Wake to music or alarm.
- AM/PM indicator.
- Battery operated. No plug required.
- Receives all standard AM radio broadcasts.
- Drawstring carrying case included.
- Back-light.
- Batteries supplied free. **£17.95**
- Quartz crystal controlled. M14

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£9.95

Guaranteed same day despatch.



M15

Price breakthrough only £18.95



OUTSTANDING FEATURES

- DUAL TIME. Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
 - CALENDAR FUNCTIONS include the date and day in each time zone.
 - CHRONOGRAPH/STOPWATCH displays up to 12 hours, 59 minutes, and 59.9 seconds.
 - On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
 - ALARM can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch. M16

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

MICRO CHIMES

FROM THE INVENTORS
OF MICROPROCESSOR
MUSICAL CHIMES

New price for the
original

CHROMA- CHIME KIT

24 tune model!

Due to the fantastic
success of this product right
across the World we are able to offer it at

only **£9.95 + 75p p&p**


Comes complete with:

- * TMS1000 Micro
- * Superb cabinet
- * All R's & C's
- * Switches & pots
- * Fully prepared PCB
- * All semiconductors
- * Loudspeaker
- * Socket & Hardware

TMS 1000N - MP0027A Micro-
computer chip available separately if
required. Full 24 tune spec device
supplied with data sheet and fully
guaranteed.

New low price only **£4.95 inc. p&p**
(Only present 24 tune repertoire currently available.)

A COMPLETE KIT FOR THE NEW MICRO CHIME

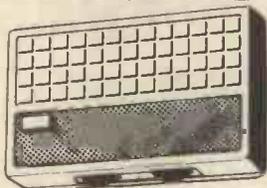

This easy to
build kit includes:

- * TMS1000 Custom MPU Chip
- * Special purpose designed case
- * Fully drilled and legended PCB
- * All transistors, Resistors and Capacitors
- * Full set of mechanical parts
- * Smart fascia labels
- * IC Socket and Loudspeaker
- * Really Low Price!

only **£8.95 + 55p p&p**

CHROMATRONICS RIVER WAY HARLOW ESSEX U.K. ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me: PE1
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX, UK.

NAME _____
ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

ZENER DIODES 2.40mW 2.7V to 33V 8p	OPTO/DISPLAY ORP12 70p DL704 110p DL707 110p	NE556 60p NE566 140p TBA641 200p TBA800 75p ZNA14 100p ZNI034 200p	74121 26p 74122 36p 74123 37p 74125 37p 74126 37p 74132 48p 74141 50p 74142 192p 7400/1 11p 7402/3 11p 7404/5 13p 7408/7 26p 7408/9 13p 7410 13p 7411 16p 7412 16p 7413 27p 7414 48p 7416 25p 7417 25p 7420 13p 7421 21p 7422 16p 7427 22p 7428 26p 7432 20p 7433 30p 7437 19p 7438 19p 7440 12p 7441 29p 7442 43p 7443 60p 7446 50p 7447 53p 7448 53p 7450 13p 7451 13p 7453 13p 7480 13p 7470 25p 7472 21p 7473 20p 7474 22p 7475 26p 7478 26p 7480 40p 7486 20p 7490 26p 7491 30p 7492 30p 7493 26p 7494 45p 7495 35p 7498 46p 74100 80p 74105 47p 74107 27p 74109 27p 74110 42p	NE555 60p NE566 140p TBA641 200p TBA800 75p ZNA14 100p ZNI034 200p	TTL 7400/1 11p 7402/3 11p 7404/5 13p 7408/7 26p 7408/9 13p 7410 13p 7411 16p 7412 16p 7413 27p 7414 48p 7416 25p 7417 25p 7420 13p 7421 21p 7422 16p 7427 22p 7428 26p 7432 20p 7433 30p 7437 19p 7438 19p 7440 12p 7441 29p 7442 43p 7443 60p 7446 50p 7447 53p 7448 53p 7450 13p 7451 13p 7453 13p 7480 13p 7470 25p 7472 21p 7473 20p 7474 22p 7475 26p 7478 26p 7480 40p 7486 20p 7490 26p 7491 30p 7492 30p 7493 26p 7494 45p 7495 35p 7498 46p 74100 80p 74105 47p 74107 27p 74109 27p 74110 42p	AD077 32p AD078 46p AD029 54p AD030 32p AD035 107p AD041 78p AD042 58p AD043 64p AD044 12p AD047 85p AD048 48p AD049 27p AD050 27p AD059 38p AD085 13p AD070 14p AD071 14p AD072 14p AD073 17p AD081 14p AD082 14p AD088 65p AD089 65p AD091 65p AD092 65p AD093 65p AD094 65p AD095 65p AD096 65p AD097 65p AD098 65p AD099 65p AD100 65p AD101 65p AD102 65p AD200 65p	BC213 11p BC214 11p BC237 11p BC301 18p BC303 18p BC328 18p BC338 18p BC547 12p BC548 12p BC549 13p BC557 13p BC559 26p BCY70 16p BCY71 18p BD115 50p BD121 90p BD123 90p BD124 100p BD131 38p BD132 38p BD133 38p BD135 38p BD136 38p BD137 42p BD138 42p BD139 42p BD140 42p BF167 30p BF180 27p BF181 8p BF184 21p BF185 25p BF194 10p BF196 10p BF197 10p BF200 32p BF224 20p BF339 27p BFR40 27p BFR75 27p BFR80 30p BFX29 27p BFX85 32p AF239 45p BC107/9 10p BC117 18p BC142 32p BC147 8p BC149 8p BC157 10p BC158 10p BC159 10p BC171 12p BC172 12p BC173 4p BC182 10p BC184 10p BC186 21p BC187 26p BC207 13p BC212 11p	BC213 11p BC214 11p OC28 86p OC35 86p OC71 9p OC72 34p OC84 30p TIP29 35p TIP29B 40p TIP30 35p TIP30B 40p TIP31 40p TIP32 40p TIP33 64p TIP33A 80p TIP35C 200p TIP35A 220p TIP41A 70p TIP42A 70p TIP2955 74p TIP3055 55p TIP3055 13p ZX108 13p ZX109 13p ZX100 18p ZX500 16p ZX706 14p ZX1132 26p ZX1302 38p ZX1304 55p ZX1305 35p ZX1306 40p ZX1308 53p ZX1711 23p ZX1893 34p ZX2129 23p ZX2389 17p ZX2484 30p ZX2905 23p ZX2926 11p ZX3053 22p ZX3055 54p ZX3102 11p ZX3704 11p ZX2706 11p ZX3707 11p ZX3772 180p ZX3866 70p ZX3904 20p
--	---	---	--	---	--	--	--	---

SAE for complete list.
Add 25p for p & p.
PRICES VAT INCLUSIVE
DELTA TECH
UNIT 4
62 NAYLOR ROAD
LONDON N20 0HN

CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,
WOOD GREEN, LONDON,
N22 4SJ (MAIL ORDER DEPT.) **888-3206**

FLIP
Push Button
Heads or Tails.
Complete kit
and full
instructions
supplied.
A pocket game. Easy to build and great to
play. Kit price £5.25 + 78p VAT.
Post free.

**3 KILOWATT PSYCHEDELIC
LIGHT CONTROL UNIT**
1000W lighting per channel, max.
A 3 channel sound to light unit housed in a
robust metal case, with a sensitivity control
for each channel i.e. Bass, middle and treble.
Full instructions make this unit easy to
connect to your present amplifier.
S.A.E. for spec. sheet.
Still only **£20.00 +£3 VAT.**

PANEL METERS.
Dims:- 80 x 47 x 33mm.
Require 38mm dia. cut out

T22	0-100µA
T23	0-500µA
T24	0-1 M/A
T25	0-5 M/A
T26	0-10 M/A
T27	0-50 M/A
T28	0-100 M/A
T30	0-1 AMP
T31	0-2 AMP
T36	VU Meter
T43	0-30 V.DC
T36	"S" Meter

£5.50 + 83p VAT.

**SWR50
SWR/POWER METER £21**
+ **£3.15 VAT** Measures SWR and power.

SWR:-	1:3 1:1
Power:-	0 1KW + 20%
Impedance:-	52 ohms
Frequency range:-	3.5 to 150 MHZ
Dims:-	145 x 76 x 57mm

SIRENS

S1 Siren 125mm diameter gold coloured horn
with fixing plate. Emits high-pitched wailing
note of varying frequency - 16 cyc. per
minute. 12 volts DC.

S2 As above but rapid noise frequency change
- 160 cyc. per minute.

PRICE = £11.50p including VAT.

**SWR9
SWR and FS METER**
£12.50 + £1.87 VAT

For antenna adjustment. Has conven-
ient relative field strength
meter built-in.

SWR:-	1:1 3:1
Accuracy:-	5%
Impedance:-	50 ohms
Frequency range:-	3 150 MHZ
Dims:-	120 x 50 x 55mm

U.S.A CO-AXIAL PLUG SOCKETS AND ADAPTORS

PL259	Standard co-axial male plug.	PRICE, EACH
SO239	Chassis mounting socket.	inc. VAT. 50p
SO239SH	Panel mounting, one hole fixing socket.	60p
PL259	Double ended female coupler.	20p
NC555	Reducer for PL259 plug (Small)	20p
NC556	Reducer for PL259 plug (Large)	20p
M359	Right angle coupler. PL259/SO239	£1.20p

Access **BARCLAYCARD**
"P&P" orders up to £5, Add 30p.
Orders £5-£10, Add 50p.
All orders over £10 post free!
Please add V.A.T. as shown.
S.A.E. with all enquiries please.

Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.
also 13 SOUTH MALL, EDMONTON GREEN, EDMONTON



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS. 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/4" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility.

£31.90
£3.00 p&p

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4 to 15 ohms speakers.

£31.50 p&p
£3.00

SPECIAL OFFER

30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge.

£57.00
+ p&p £6.00

EMI SPEAKER BARGAIN

Stereo pair 350 bt. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£15.25
Per stereo pair
£3.65 p&p



BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device.

£25.50
p&p £2.60

A.D.C. QLM 30 Mk III Magnetic Cartridge to suit

£7.95



BSR Manual single play record deck with auto return and cueing lever, lined with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use.

OUR PRICE £11.25 p&p
£2.75

GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.


£8.15 p&p £2.05 Size 12" x 8 1/2"



UNIT AUDIO STAND

Can be used with TV (to fit) Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors.

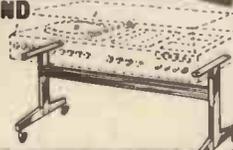£3.95 p&p £1.50
24" x 12 1/2" x 11 1/2" approx.



BARGAIN FOR PERSONAL SHOPPERS ONLY

Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones

complete with speakers. **£35.75**

Micro Cassette Recorder

Pocket size—home or office use or when travelling.

£14.25

Battery operated fluorescent camping lamp.

Runs off 8 U2 batteries.

£4.80

Mullard

AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE

PRICE & AT OVER **25** PER PACK SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.

OUR PRICE p&p **£5.00**

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.

illus. OUR PRICE p&p **£7.65**

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

Size approximately 9 1/4" x 8 3/4" x 4" p&p **£12.25**



ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance **£3.00**

plus **£1.50** p&p

Two Way Speaker Kit

Comprising of two 8" x 5" approx. 8 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£4.05**

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT. per stereo pair plus **£1.55** p&p



BARGAINS FOR PERSONAL SHOPPERS

LCD Solar 5 function with backlite stainless steel finish case and strap £7.40

LCD Solar Chrono 9 function with backlite stainless steel finish case and strap £9.55

Chrono stop watch 9 function with back lite stainless steel finish case and strap. £8.95

Solar Alarm LCD stainless steel case and strap. £21.95

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer £12.20

100 Watt Power Amp Module £14.25

Mains power supply for above unit £3.60

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers £20.45

VIDEOMASTER Super Score TV Game with pistol mains operation £15.95

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock. LW, MW, SW, VHF mains/battery operation £42.90

ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. £24.50

100 WATT MONO DISCO AMP

Size approx. 14" x 4 1/2" x 10 1/2"

Brushed aluminium fascia and rotary controls.

Five vertical slide controls, master volume, tape level, mc level, deck level, L PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to b.No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak

p&p **£4.05** **£66.45**



50 WATT MONO DISCO AMP

£30.60

p&p **£2.70**

Size approx. 13 1/2" x 5 1/4" x 6 1/4" 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches independent bass and treble controls and master volume.



FOR PERSONAL SHOPPERS ONLY

DUO II SPEAKERS

Attractive teak finish, modern design incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx. tweeter 45 to 1800 Hz Impedance 8 ohms. Power 15 watts RMS

18 1/2" x 13 1/2" x 7 1/4" Per stereo pair approx **£16.50**



FOR PERSONAL SHOPPERS ONLY

STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**

Size approximately 47" x 15 1/2" x 15"



323 EDGWARE ROAD, LONDON W2 218 HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers

ALL PRICES INCLUDE VAT AT 15%

All items subject to availability. Prices correct at 1.8.79 and subject to change without notice


NOTE: Persons under 16 years not served without parent's authorisation.

The latest kit innovation!

from **Sparkrite**

*Sparkrite -
was featured by Shaw Taylor
in "DRIVE IN"*

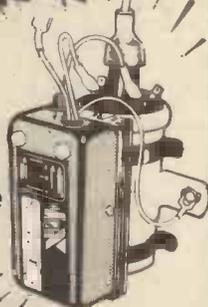the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE — Vehicles with current Impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £4.25 inc. VAT, post & packing UK only.

Electronics Design Associates, Dept. PE 10, 82 Bath Street, Walsall, WS1 3DE. Phone: Walsall 614791

Electronics Design Associates, Dept. PE10
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D.

Send SAE if brochure only required.

I enclose cheque/PD's for

X4 KIT £17.95

TACHOPULSE SLAVE UNIT £4.25

£

Cheque No. _____

Please state polarity pos or neg earth.

Access or Barclaycard No. _____



Wilmslow Audio

THE firm for speakers!

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

- AUDAX ● AUDIOMASTER ● BAKER
BOWERS & WILKINS ● CASTLE ● CELESTION
CHARTWELL ● COLES ● DALESFORD
DECCA ● EMI ● EAGLE ● ELAC ● FANE
GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON
JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER
McKENZIE ● MONITOR AUDIO ● PEERLESS
RADFORD ● RAM ● RICHARD ALLAN ● SEAS
SHACKMAN ● STAG ● TANGENT ● TANNY
VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.E.)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street

Tel.: Wilmslow 529599 for Speakers

Tel.: Wilmslow 526213 for Hi-Fi

FLADAR TRANSFORMERS

PRIMARY 0-240V 50Hz


IF YOUR REQUIREMENT IS NOT FEATURED BELOW
SEND FOR OUR TRANSFORMER CATALOGUE PRICE 40p

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
06FE06	6+6	0.5A EACH	1.82	60p	60FE24	24+24	1.2A EACH	4.58	102p
08FE06	6+6	0.6A EACH	2.19	80p	80FE24	24+24	1.5A EACH	5.66	120p
12FE06	6+6	1A EACH	2.43	72p	50FE28	28+28	0.75A EACH	3.74	84p
20FE06	6+6	1.6A EACH	3.06	84p	60FE28	28+28	1.1A EACH	4.58	102p
50FE06	6+6	3A EACH	3.74	84p	80FE28	28+28	1.4A EACH	5.66	120p
60FE06	6+6	4A EACH	4.58	102p	20FE30	30+30	0.35A EACH	3.06	84p
06FE09	9+9	0.3A EACH	1.82	60p	50FE30	30+30	0.75A EACH	3.74	84p
08FE09	9+9	0.5A EACH	2.19	80p	60FE30	30+30	1A EACH	4.58	102p
12FE09	9+9	0.75A EACH	2.43	72p	80FE30	30+30	1.2A EACH	5.66	120p
20FE09	9+9	1A EACH	3.06	84p	MULTITAP RANGE VOLTAGES AVAILABLE 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30				
50FE09	9+9	2.5A EACH	3.74	84p					
60FE09	9+9	3A EACH	4.58	102p	30FE30		1A	4.00	84p
06FE12	12+12	0.25A EACH	1.82	60p	60FE36		2A	4.80	102p
08FE12	12+12	0.3A EACH	2.19	60p	80FE36		3A	5.88	120p
12FE12	12+12	0.5A EACH	2.43	72p	CENTRE TAP SECONDARY				
20FE12	12+12	0.8A EACH	3.06	84p					
50FE12	12+12	1.8A EACH	3.74	84p	06FE30	6-0-6	1.80A	1.80	60p
60FE12	12+12	2.5A EACH	4.58	102p	08FE40	9-0-9	1A	2.18	60p
80FE12	12+12	3A EACH	5.66	120p	12FE50	12-0-12	1A	2.40	72p
06FE15	15+15	0.2A EACH	1.82	60p	20FE80	20-0-20	1A	3.00	84p
08FE15	15+15	0.25A EACH	2.19	80p	50FE80	20-0-20	2A	3.70	84p
12FE15	15+15	0.4A EACH	2.43	72p	60FE100	28-0-28	2.2A	4.50	102p
20FE15	15+15	0.6A EACH	3.06	84p	80FE70	24-0-24	3A	5.66	120p
50FE15	15+15	1.5A EACH	3.74	84p	90FE50	15-0-15	6A	8.80	120p
80FE15	15+15	2A EACH	4.58	102p	90FE80	30-0-30	3A	5.86	120p
80FE15	15+15	3A EACH	5.66	120p	100FE26	26-0-26	3.5A	6.05	138p
06FE20	20+20	0.15A EACH	1.82	60p	100FE28	28-0-28	3.5A	6.05	138p
12FE20	20+20	0.25A EACH	2.43	72p	100FE30	30-0-30	3A	6.05	138p
20FE20	20+20	0.5A EACH	3.06	84p	100FE36	36-0-36	3A	6.05	138p
50FE20	20+20	1.2A EACH	3.74	84p	150FE15	15-0-15	7A	7.47	150p
60FE20	20+20	1.5A EACH	4.58	102p	150FE26	26-0-26	5A	7.47	150p
80FE20	20+20	2A EACH	5.66	120p	150FE30	30-0-30	4A	7.47	150p
48FE12	0-6-12	4A	4.58	102p	150FE36	36-0-36	4A	7.47	150p
60FE12	0-6-12	5A	5.30	102p	150FE42	42-0-42	3A	7.47	150p
70FE12	0-6-12	8A	5.66	120p	250FE28	28-0-28	8A	8.60	175p
90FE12	0-6-12	8A	6.75	138p	250FE30	30-0-30	7A	8.60	175p
12FE24	24+24	0.2A EACH	2.43	72p	250FE42	42-0-42	5.5A	8.60	175p

FLADAR ELECTRIC
P.O. BOX 19
WESTCLIFF-ON-SEA
ESSEX. 0702-613314

TRADE ENQUIRIES
WELCOME

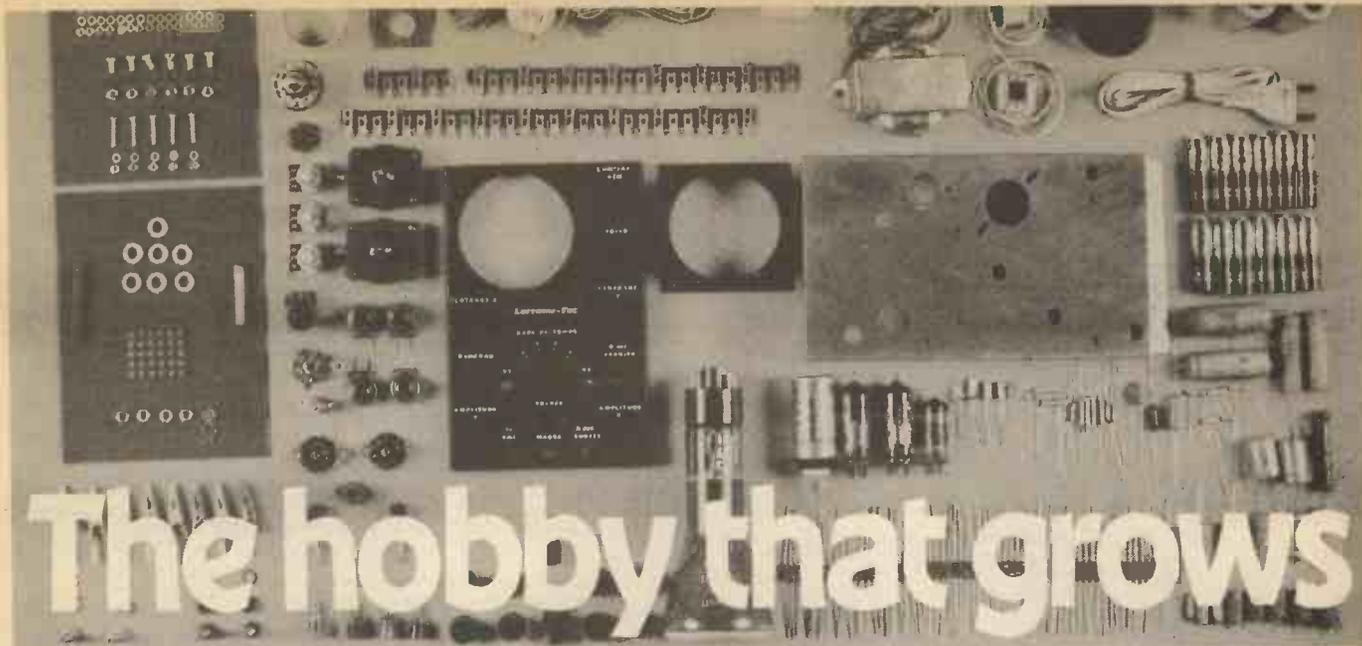PAYMENT TERMS:
C.V.O. Cheques,
Postal Orders
All Prices include 15% V.A.T.



What you see above is a kit of parts that builds into a fully working oscilloscope.

No toy, this vital piece of functional equipment can be found in any professional electronics workshop. It is a valuable instrument of true professional quality.

By building the oscilloscope you will be taking the first steps to a rewarding hobby that knows no bounds.

Each constructional stage is a complete lesson

in the basics of electronics practice and carefully designed to be understood by those with no previous knowledge. Once built, this instrument can be used to complete a course of practical study and experimentation that will reveal the secrets of printed circuitry, testing and servicing of T.V. and radio and the vast majority of electronic equipment.

Invaluable knowledge that pays big dividends. Send today for the free colour brochure and start growing a new hobby.

and grows.

1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.



4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



Free 32 page
Colour Booklet.

PEH 10

NAME.....

ADDRESS

Block Caps Please

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO and
ELECTRONICS SCHOOL**

P.O. Box 156, Jersey,
Channel Islands.

TRANSFORMERS

30 VOLT RANGE
Pri 220/240 sec 0-12-15-20-24-30V
12, 15, 18, 20, 24, 30V or 12V-0-12V
and 15V-0-15V.

Ref	VA	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.93	1.10
3	2.0	6.35	1.10
20	3.0	6.82	1.31
21	4.0	7.19	1.31
51	5.0	10.98	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.89	1.89
90	12.0	21.09	2.24
91	15.0	24.19	2.39
92	20.0	32.40	O.A.

CONTINUOUS RATINGS

EX-STOCK—

+ VAT 15%

**TRANSFORMERS
END OF LINE OFFERS**

Ref	VA	Price	P & P
30-Isolator 240V:240V	200VA	£4.54	£1.04
62-Isolator 240V:240V	250VA	£5.62	£1.04
63-Isolator 240V:240V	500VA	£11.50	£2.15
6-250-0-250 @ 100ma 1)	Sec 6-3V @ 3-5A 2)	Sec	£3.20 78p
0-5V, 6-3V @ 2/1 amp			
7-350-0-350V @ 100ma 1)	Sec 6-3V @ 3-5A 2)	Sec	£4.10 96p
0-5V, 6-3V @ 2/1 amp			
220-410-0-410V @ 180ma 1)	Sec 6-3V @ 4 amp CT 2)		
Sec 6-3V @ 2A 5V @ 2 amp			
M184 - To match EL84 15W		£1.62	32p
M616 - 0-240V: Screen 1)	13-0-13 1A, 2)	12V 150ma	£2.10 60p

M489 - 0-240V: 1400V @ 150ma, 6-3V @ 4A	£5.50	£1.04
M708 - 6K to 3KΩ matching transformer 5W	90p	40p
M679 - 120V x 2: 36V 1-6A	£3.00	78p
M865 - 100V Line to 4Ω 10 watts	£1.90	60p
M973 - 100V Line to 8Ω 40 watts	£2.90	60p
M1015 - Choke 8A @ 5mH 150A Surge	£1.50	45p
M1020 - 0-240V 12-0-12V @ 50ma	97p	41p
M1126 - 120/240V: 9-0-9V @ 1A	£2.40	71p
M1130 - 0-240 4500V @ 10ma	£4.86	£1.08
M1185 - 0-115-240V: 14V 50ma	75p	30p
M624 - 0-380V: 110V @ 13-6A	£10.70	£1.40

P.W. Purbeck oscilloscope transformer 250-0-250 6-3V: 12-9V £7.51 90p

Antex Soldering Irons 15W, 25W £4.58 Safety Stand £1.75 P & P 52p each

Solderless bread boarding U. Dec B for ICs etc. £6.99 P & P 40p VAT 15%

12 OR 24V OR 12-0-12V
Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0.5	0.25	2.42	0.82
213	1.0	0.5	2.90	0.90
71	2	2	4.46	1.10
18	4	2	4.46	1.10
85	5	2.5	6.16	1.10
70	6	3	6.99	1.10
108	8	4	8.16	1.31
72	10	5	8.93	1.31
116	12	6	9.89	1.52
17	16	8	11.79	1.52
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

AUTO TRANSFORMERS

Ref	VA	(Watts)	£	P&P
113	15	0-115-210-240	2.73	0.81
64	75	0-115-210-240	4.41	1.10
4	150	0-115-200-220-240	5.70	1.10
67	500	0-115-200-220-240	12.09	1.91
84	1000	0-115-200-220-240	20.84	2.39
93	1500	0-115-200-220-240	25.61	O.A.
95	2000	0-115-200-220-240	38.31	O.A.
73	3000	0-115-200-220-240	65.13	O.A.
80S	4000	0-10-115-200-220-240	84.66	O.A.
57S	5000	0-10-115-200-220-240	98.46	O.A.

High Quality Amplifier Modules

10W (AL30)	£3.75
25W (AL60)	£4.95
35W (AL80)	£7.79
125W (AL250)	£18.74

F.M. Tuner-4 push buttons £23-60
Pre-Amps & Power Supplies available. P & P 35p. VAT 15%

ABS PLASTIC BOXES inset brass nuts, internal slots to take P.C. cards, flush fitting lid.

PB1 150mm x 62 x 40	65p
PB2 100mm x 75 x 40	73p
PB3 120mm x 100 x 45	87p
PB4 215mm x 130 x 85	£2.54*

*P & P 33p. VAT 15% *P & P 46p

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V and 25V-0-25V.

Ref	VA	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.87	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	3.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	31.79	O.A.

MAINS ISOLATORS (SCREENED)
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.84	0.91
149	60	7.37	1.10
150	100	10.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
156	750	32.03	O.A.
155	1000	40.82	O.A.
157	1500	56.82	O.A.
158	2000	67.99	O.A.
159	3000	96.33	O.A.

*Pri 0-220-240V Sec 115 or 240V. State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	6.88	1.03	56W
75	8.80	1.31	64W
150	11.00	1.61	4W
200	12.08	1.67	65W
250	12.82	1.67	69W
500	20.13	1.89	67W
1000	30.87	2.65	84W
1500	28.82	O.A.	93W
2000	84.97	O.A.	95W

AVO TEST METERS
AVO 8 MK5 £88-10
AVO 71 £38-00
AVO 73 £48-70
AVO MM5 minor £32-95
Vee Megger £74-25
TT169 in circuit transistor tester £39-53
EM272 316 KΩ 1 volt £57-80
DA116 digital £108-30
BMT Megger £51-76
Clamp Meter to 300A £51-90
P & P £1-32 15% VAT

U4315 Budget Meter
20KΩ/V Ranges to 1000V, 2-5A AC/DC
500KΩ Res. In steel case £15-85 P & P £1-32
VAT 15%

SPECIAL OFFER Multimeter (20KΩ/V with combined audio/L.F. test oscillator at 1KHz, and 465 KHz AC/DC to 1000V, DC current to 500 mA resistance to 1KΩ size 160x97x40mm) £8-60. P & P £1-00, VAT 15%

ELECTROSIL metal oxide low noise resistors.

ELECTRONIC CONSTRUCTION KIT
Home electronics teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. Full instructions and clear diagrams.
Price £8.29 P & P £1-10. VAT 15%

PANEL METERS
43mm x 43mm 82mm x 78mm
0-500A 6-20 0-500A 6-70
0-500A 6-95 0-500A 6-70
0-1mA 5-95 0-1mA 6-70
0-30V 5-95 0-30V 6-70
VU Ind. Panel 48mm x 45mm 2-60
VU Ind. Edge 54 x 14mm 250µA F.S.D. 2-60
Carriage 76p. VAT 15%

NEW RANGES VAT 15%

Pri 0-220, 240V Sec 0-36-48 twice. To give 36-0-36, 48-0-48 72V or 96V.

Ref	£	P & P
3 amp	16.17	1.70
5 amp	20.65	2.47
5 amp	29.30	2.47

18V Range
0-C Tap (7.5V-0-7.5V)

171 500mA	2.30	0.52
172 1A	3.26	0.92
173 2A	3.98	0.90
174 3A	4.13	0.99
175 4A	6.30	1.10

PLUG IN SAVE BATTERIES
Fits into a 13A skt. 3-6-9-12V multipug outlet £4-00 P & P 55p. VAT 15%

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238 200	3-0-3		2.83	0.63
212 1A, 1A	0-6-0-6		3.14	0.90
13 100	0-6-0-6		2.35	0.43
235 330, 330	0-9-0-9		2.19	0.43
207 500, 500	0-8-0-8-9		3.05	0.82
208 1A, 1A	0-8-0-8-9		3.88	0.90
236 200, 200	0-15-0-15		2.19	0.43
214 300, 300	0-20-0-20		3.08	0.43
221 700(DC)	20-12-0-12-20		3.75	0.43
206 1A, 1A	0-15-0-15-20		5.09	1.10
203 500, 500	0-15-27-0-15-27		4.39	1.10
204 1A, 1A	0-15-27-0-15-27		6.64	1.10
239 50	12-0-12		2.88	0.43

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL ST

SINCLAIR PRODUCTS
PFM200 £52-89, case £3-40, adaptor £3-40, connector kit £11-27. Microvision TV UK model £91-44, mains adaptor £6-88.
PM35 £23-76, mains adaptor £3-40 case £3-40. 30Kv probe £20-13. DM350 £71-82. DM460 £102-17. DM235 £52-66. Accessories for all 3 models:- rechargeable batteries £7-99, mains adaptor/charger £3-94, case £9, 30kV probe £20-13. Enterprise prog calculator with accessories £23-37.
New 10 MHz scope p.o. £67

CALSCOPE OSCILLOSCOPES
Send sse for details or see the Calscope advert in this magazine. Super 6:- 6MHz single beam 60ns rise time £185. Super 10:- 10MHz dual trace 35ns rise time £251.

COMPUTER GAMES
Star Chess £82. Chess champion 6 £94. Chess challenger 7 £91. Chess challenger 10 £152-50. Voice challenger p.o.a. Checker challenger 2 £46. Checker challenger 4 £88. Atari video computer £147, cartridges £14-32.

CONTINENTAL SPECIALITIES PRODUCTS
EXP300 £6-61. EXP350 £3-62. EXP325 £1-84. EXP600 £7-24. EXP650 £4-14. EXP48 £2-64. P86 £10-58. P8100 £13-57. LM1 £32-99. LP1 £35-85. LP2 £20-70. MAX100 £89-18.

TV GAMES
Tank battles kit £6-34. AY-3-8500 chip £5-27. kit £4-26. stunt cycle AY-3-8760 chip £12-46. kit £4-26. 10 game paddle 2 AY-3-8610 chip £9-48. kit £7-03. racing car chip AY-3-8603 £9-48. modified shoot kit £5-28. rifle kit £5-27. colour generator kit £9-05. joystick 220K £1-80.

MAINS TRANSFORMERS
6-0-6V 100ma 76p, 1 1/2 £2-50. 6-3V 1 1/2 £2-01. 9-0-9V 75ma 76p, 1a £2-12. 2a £2-77. 12-0-12V 50ma 76p, 100ma 92p, 1a £2-65. 12V £1-01. 15-0-15V 1a £2-97. 30-0-30V 1a £3-82.

JC12 AND JC20 AMPLIFIERS
Integrated circuit audio amplifier chips supplied with free data and printed circuits. JC12 8 Watts £2-08. JC20 10 Watts £3-14. We also stock a range of matching preamp and power kits.

FERRANTZ N414
Ic radio chip £1-12. extra parts and pcb for radio £4-10. case £1-06.

PRINTED CIRCUIT MATERIALS
PC etching kits:- economy £2-32. standard £4-36. 40 sq ins pcb 64p. 1lb FeCl £1-20. etch resist pens:- economy 48p, dalo 84p. drill bits 1/32 ins or 1mm 25p each. etching dish 72p. laminate cutter 80p.

S-DECS AND T-DECS
S-DeC £4-05. T-DeC £4-28. u-DeCa £4-69. u-DeCb £7-16. 16 dil adaptor with socket £2-31.

BATTERY ELIMINATORS
4-way types with switched output and 4 way multi-jack:- 3/4/6V 100ma £2-89. 6/7/9V 300ma £3-14. 100ma radio types with press-stud connectors 9v £3-57. 6v £3-57. 4 1/2v £3-57. 9+9v £4-79. 6+6v £4-79. 4 1/2+4 1/2v £4-79. cassette recorder mains unit 7A 100ma with 5 pin din plug £3-67. fully stabilised type 3/6/7/9V 400ma £5-64. car converters 12v dc input, output 9v 300ma £1-60. output 7 1/2v 300ma £1-60. output 3/4/6/7/9/12V 800ma £2-66.

BATTERY ELIMINATOR KITS
100ma radio types with press-stud connectors 4 1/2v £1-49. 6v £1-49. 9v £1-49. 4 1/2+4 1/2v £1-92. 6+6v £1-92. 9+9v £1-92. cassette type 7 1/2v 100ma with din plug £1-49. heavy duty 13 way types 4 1/2/6/7/8 1/11/13/14/17/21/25/28/34/42v 1A £4-95. 2A £7-72. transistor stabilised 8-way types for low htm 3/4/6/7/9/12/15/18V 100ma £2-98. 1 amp £6-81. variable voltage stabilised models 2-18v 100ma £2-98. 2-30v 1A £7-40. 2-30v 2A £11-66. car converter 12v dc input. Output 9 1/2v 1A stabilised £1-44.

BI-PAK AUDIO MODULES
AL30 £4-04. PA12 £7-77. PS12 £1-42. TS38 £2-70. S450 £24-03. AL60 £4-97. PA100 £17-33. SP80 £4-57. 8MT80 £6-08. Stereo 30 £20-57. MA60 £36-23.

COMPONENTS
1N4148 1-4p. 1N4002 3-1p. 741 8 dil 18p. 723 14 dil 31p. NE555 8 dil 25p. bc 182b, bc183b, bc184b, bc212b, bc213b, bc214a, bc47, bc548, bc549 5p. bp315, bp2bc 28p. 1p1c, dip4c 46p. bd131, bd136 33p. plastic electrolytic bc107 5p. fuses 20mm x 5mm cartridge -15, -25, -5, 1, 2, 3, 5 amp quickblow 1p. anti-surge 3-6p. resistors 5% 1/4W E12 10R to 10M 1p. 0-8p for 50+ of one value. polyester capacitors 250v -015, -068, -1m 15p. -01, -033, -33mf 2-8p. -022, -.047mf 3-3p. -.22, -.47mf 4-9p. polystyrene capacitors E12 63v 10 to 1000pf 3p, 1n2 to 10n 4p. ceramic capacitors 50V E6 22pf to 47n 2p. electrolytic capacitors 250v -5, -1, 2mf 5p, 25v 5, 10 5p, 16v 22, 33, 47, 88mf 5p, 100mf 6p, 220mf 7 5p, 330, 470mf 9p, 1000mf 9p. zeners 400mW E24 2v7 to 33v 7p, preset pots subminiature 0-1W horiz or vert 100 to 4M7 7-2p. potentiometers 1/4W 4K7 to 2M2 log or lin single 27p, dual 78p. LEDs 9-7p. IC Sockets 8 dil 8-6p, 14 dil 10-1p, 16 dil 12p.

SWANLEY ELECTRONICS Official credit orders welcome
DEPT PE, 32 Goldael Rd., Swanley, Kent BR8 8EZ.
Mail order only. Please add 30p to the total cost of the order for postage.
Prices include VAT. Lists 20p post FREE. Overseas customers deduct 13%.

L.C.D. DIGITAL WATCHES



ALARM MODEL (illustrated)
* Constant 6 digit display shows Hours, Minutes, Seconds or Date.
* 24-hour alarm with on/off indication.
* Night Light.
* Matching adjustable stainless steel strap.
£12.50 inclusive

SLIM 11 FUNCTION CHRONOGRAPH
Time, Date, 1/100 second stopwatch.
£11.50 inclusive

All products carry full 7 day money back reassurance plus 12 month guarantee.

Please add further 50p for spare battery if required (£1 for No. 4.)

ALARM CHRONO WITH DUAL TIME
All functions of alarm model with 1/10 second stopwatch and dual time.
£18.00 inclusive

SOLAR ALARM CHRONO
As above but solar assisted.
£24.00 inclusive

LADIES 5 FUNCTION
Hours, Minutes, Seconds, Month and Date.
£7.95 inclusive

SAE for more details of large range of digital watches, clock/radios, clocks, car stereos, headphones etc.

SPARKS DEVELOPMENTS, 53 North Street, Melbourne, Derbyshire DE7 1FZ.

STEVENSON


Electronic Components

TTL			
7400	10p	7473	20p
7401	10p	7474	22p
7402	10p	7475	25p
7404	12p	7476	20p
7406	22p	7485	55p
7408	12p	7486	20p
7410	10p	7489	135p
7413	22p	7490	25p
7414	39p	7493	30p
7420	12p	7494	45p
7427	20p	7495	35p
7430	12p	7496	45p
7432	18p	74121	25p
7442	38p	74122	35p
7447	45p	74123	38p
7448	50p	74125	35p
7454	12p	74126	35p

CMOS			
4001	13p	4020	50p
4002	13p	4022	50p
4007	13p	4023	13p
4009	30p	4024	40p
4011	13p	4025	13p
4012	13p	4026	90p
4013	28p	4027	28p
4015	50p	4028	45p
4016	28p	4029	50p
4017	47p	4030	50p
4018	55p	4031	50p

FULL DETAILS IN CATALOGUE!

SKTS

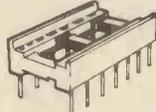

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

Soldercon pins: 100:50p 1000:370p

PCBS

VEROBOARD

Size in.	0.1in.	0.15in.	Vero
25 x 1	14p	14p	Cutter 80p.
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	

Single sided pins per 100 40p 40p

Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.

'Data' pens. 75p each.

Five mixed sheets of Alfac. 145p per pack.

OPTO

LED's	0.125in.	0.2in.	each	100+
Red	TIL209	TIL220	9p	7.5p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p

Clips 3p 3p

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:

0.25W	each	100+	1000+
0.5W	1p	0.9p	0.8p
	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (850 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability, low noise rated at ¼W 1%. Available from 51ohms to 330k in E24 series. Any mix:

0.25W	each	100+	1000+
	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER OVER 2500 STOCK ITEMS.

TRANSISTORS

AC127	17p	BCY72	14p	ZTX500	16p
AC128	16p	BD131	35p	2N697	12p
AC176	18p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BD140	35p	2N3055	50p
BC107	8p	BFY50	15p	2N3442	135p
BC108	8p	BFY51	15p	2N3702	8p
BC108C	10p	BFY52	15p	2N3703	8p
BC109	8p	MJ2955	98p	2N3704	8p
BC109C	10p	MPSA06	20p	2N3705	9p
BC147	7p	MPSA56	20p	2N3706	9p
BC148	7p	TIP29C	60p	2N3707	9p
BC177	14p	TIP30C	70p	2N3708	8p
BC178	14p	TIP31C	65p	2N3819	15p
BC179	14p	TIP32C	80p	2N3820	44p
BC182	10p	TIP2955	65p	2N3904	8p
BC182L	10p	TIP3055	55p	2N3905	8p
BC184	10p	ZTX107	14p	2N3906	8p
BC184L	10p	ZTX108	14p	2N4058	12p
BC212	10p	ZTX300	16p	2N5457	32p
BC212L	10p			2N5459	32p
BC214	10p			2N5777	50p
BC214L	10p				

DIODES

1N914	3p	1N4006	6p
1N4001	4p	1N5401	13p
1N4002	4p	BZY88 ser.	8p
1N4004	4p		
4TT Full spec. product.			
1N4148	-£1.40/100. £11/1000		

LINEAR

THIS IS ONLY A SELECTION!

709	35p	LM350	80p	NE531	98p
741	16p	LM301AN	26p	NE555	23p
747	45p	LM308	60p	NE566	60p
748	30p	LM318N	75p	NE567	100p
7106	850p	LM324	45p	RC4136	100p
7107	900p	LM339	45p	SN76477	230p
CA3046	55p	LM378	230p	TBA800	70p
CA3080	70p	LM379S	410p	TBA810S	60p
CA3130	90p	LM380	75p	TDA1022	220p
		LM3900	50p	TL081	45p
		LM3909	65p	TL084	125p
		LM3911	100p	ZN414	80p
		MC1458	32p	ZN425E	390p
		MM57160	590p	ZN1034E	200p

CAPACITORS

TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

MYLAR FILM

0.001, 0.01, 0.022, 0.032, 0.047, 0.068, 0.1	3p
	4p

POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
						7p
						13p
						20p
25V	10	22	33	47		5p
						8p
						10p
						15p
						23p

CONNECTORS

JACK PLUGS AND SOCKETS

	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	18p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p

Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
Crystal earpiece including 3.5mm plug. 30p each

TRANSFORMERS

All 240V Primary.

0 - 6, 0 - 6 @ 0.5A or 0 - 9, 0 - 9 @ 0.4A.	175p
0 - 12, 0 - 12 @ 0.5A or 0 - 15, 0 - 15 @ 0.4A	235p
0 - 9, 0 - 9 @ 1.2A or 0 - 12, 0 - 12 @ 1A.	345p
0 - 12 - 15 - 20 - 24 - 30V @ 1.5A.	455p
0 - 20 - 25 - 33 - 40 - 50V @ 1A.	455p
0 - 20 - 25 - 33 - 40 - 50V @ 2A.	585p
0 - 20 - 25 - 33 - 40 - 50V @ 3A.	715p

Miniature type
6 - 0 - 6, 9 - 0 - 9, 12 - 0 - 12 @ 100mA. 95p

SOLDERING IRONS

ANTEX X25 (25W) or ANTEX CX (17W) 390p each
Reel of solder (39.6M) 240p each

POTENTIOMETERS

Single gang Log or Lin 5K - 2M2 28p each
Dual gang Log or Lin 5K - 2M2 80p each
Presets, sub min. type hor. or vert. 100Ω - 2M2 6p each

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



SWITCHES

Subminiature toggle. SPDT 70p. DPDT 80p.
Standard toggle. SPST 34p. DPDT 48p.



Slide switches (DPDT) miniature or standard 15p.
Push to make switch. 15p. Push to break switch. 20p.
Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

BOXES

Folded construction complete with screws.

3 x 2 x 1	52p	4 x 3 x 2	70p	6 x 4 x 3	95p
4 x 3 x 2	64p	6 x 4 x 2	77p	8 x 6 x 2	125p




We now offer one of the widest ranges of components at the most competitive prices in the UK. See catalogue for full details. We welcome callers at our shop in College Road, Bromley, from Mon - Sat, 9am - 6pm (8pm on Weds. and Fridays). Special offers always available.

We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements.

TEL: 01-464 2951/5770

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.

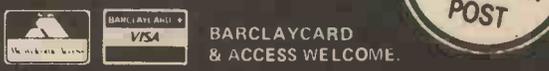

Mail orders to: STEVENSON (Dept PE)



76 College Road, Bromley, Kent BR1 1DE.

ALL PRICES INCLUDE 15% V.A.T.

**Measure Resistance to 0.01Ω ...
At a Price that has no resistance at all**

New **ELENCO PRECISION** Digital Multimeter M1200B
USA

ONLY £55 (£3 p&p + VAT £8.70 = £66.70)

*FULLY GUARANTEED
FOR 2 YEARS

*METAL CASE

*EX STOCK DELIVERY



**THE ULTIMATE IN PERFORMANCE —
MEASURES RESISTANCE TO 0.01 OHMS,
VOLTAGE TO 100 MICROVOLTS, CURRENT
TO 1 MICROAMPS AT LOWEST EVER PRICE!**

FEATURES

- 3½ digits 0.56" high LED for easy reading
- 100μV, 1μA, 0.01Ω resolution
- High input impedance 10 Megohm
- High accuracy achieved with precision resistors, not unstable trimpots
- Input overload protected to 1000V (except 200mV scale to 600V)
- Auto zeroing, autopolarity
- Mains (with adaptors not supplied) or battery operation—built-in charging circuitry for NiCads
- Overrange indication
- Hi Low power ohms, Lo for resistors in circuit, Hi for diodes

SPECIFICATIONS:

DC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1% ± 1 digit, Resolution .1mV Overload protection 1,000 volts max
AC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1.5% ± 2 digits, Resolution .1mV Overload protection 1000V max, 200mV scale 600V
DC Current	Range 2mA, 20mA, 200mA, 2amp. Accuracy 1% ± 1 digit, Resolution 1 Microamp Overload protection — 2 amp fuse and diodes
AC Current	Range 2mA, 20mA, 200mA, 2 amp Accuracy 1.5% ± 2 digits, Resolution 1 Microamp Overload protection — 2 amp fuse and diodes
Resistance	Range 20, 200, 2K, 20K, 2 Meg, 20 Meg. Accuracy 1% ± 1 digit, Resolution .01 ohms
Environmental	Temp coefficient 0° to 30°C ± .025%°C Operating Temp 0° to 50° C Storage — 20° to 60° C
General	Mains adaptor: 6 - 9 Volts @ 200mA (not supplied) 4C size batteries (not supplied) Size 8¼ x 5¼ x 2¼ Weight 2½ lbs.

To: Maclin-Zand Electronics Ltd
1st Floor, Unit 10, East Block
38 Mount Pleasant, London WC1X OAP

PE10

Please send me DMM M1200B
@ £66.70 inc. p&p + VAT (overseas £60)
I enclose cheque/PO/Bank Draft for £

Name

Address

(BLOCK
LETTERS
PLEASE)

ELENCO PRECISION Sole UK Distributor



Maclin-Zand Electronics Ltd
38 Mount Pleasant, London WC1XOAP

© N Zand

Tel. 01-837 1165
Telex. 8953084 MACLING

OUR 1979 CATALOGUE
including the first edition of

STOP PRESS

(Send S.A.E. for copy)

- ★ Latest low prices
- ★ Fascinating new items
- ★ Special offers — a bargain on their own
- ★ Lowest prices ever for TTL
- ★ Free 45p worth of vouchers

RAM
2102A-2
1024 x 1 250ns
£1.33
16 for £18.95

RAM 4116
16K x 1 250ns
£10.36
8 for £75.36

C.P.U.
8080
£5.84

CATALOGUE
40p

E. PROM
2708
£8.38

E. PROM
1702
£5.93

CHROMASONIC electronics

DEPT. 16, 56 FORTRIS GREEN ROAD
MUSWELL HILL, LONDON N10 3HN
TELEPHONE: 01-883 3705/2289



**USE OUR "ORDER
RING" LINES**



VAT INCLUSIVE PRICES P&P 25p

Codespeed Electronics ELECTRONIC MAIL
ORDER SPECIALISTS
PO BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH,

New, Full Spec. Devices P03 5BJ

- WRISTWATCH LCD'S A high contrast 3½ digit wristwatch LCD with centre colon. Supplied with polarizers and data. Only £1.00 Cat. No. 202
- MM5314 CLOCK CHIP A super value digital clock chip for only £1.99. With data. Cat. No. 207
- 4 DIGIT LCD A high contrast, easy to solder, display with four 0.5" high non-multiplexed digits. £8.95 each with data. Cat. No. 206
- DIGITAL ALARM CLOCK MODULE Complete with giant 0.84" LED display. Add transformer and switches for complete clock. With data only £5.50 Cat. No. 205
- SLIDE SWITCHES A miniature slide switch with two pole change-over contacts. All brand new. 16p each. Cat. No. 702
- MOMENTARY SWITCHES Miniature spring loaded push button switches with one normally open contact. Super value 15p each. Cat. No. 703
- POLARIZING FILTER MATERIAL 0.006" thick plastic film. Any size cut — even 1 sq. inch. Max. width 19", any length. Only 2p per sq. inch. Cat. No. 701
- PROGRAMMABLE UNJUNCTIONS Four MEU21.PUTS (similar to 2N6027). Makes long delay timers, oscillators etc. With data and applications sheet. 4 for 50p. Cat. no. 402
- MINI 6 DIGIT LED DISPLAY 6 digit 7 segment display from Texas. Common cathode, multiplexed, with 0.1" digits. £1.00. Cat. No. 306
- DMM CHIP MM5330 dvm chip. Builds into high accuracy dvm or panel meter. Requires additional circuitry. Supplied with data and circuit. Only £3.95. Cat. No. 404
- GIANT LED DISPLAY Common cathode, non-multiplexed super 4 digit LED clock display. Lots of other uses too. Only £3.95 each. Cat. No. 204
- MINIATURE DIODES 25 mini 1N3470 germanium diodes (35v, 600mA). Excellent value. 25 for 50p. Cat. No. 401
- 20 KEY KEYBOARDS Calculator keyboards, excellent key action. 20 keys per board. 2 keyboards for £1.00. Cat. No. 101
- 1½ DIGIT DISPLAY Bright orange gas discharge display. 1½ digits 0.25" high. With data only 50p. Cat. No. 304
- MATRIXED SWITCHING DIODES 23 diodes on each 14 pin chip. Supplied with data sheet. 5 chips for 50p. Cat. No. 504
- HIGH SPEED DIODES 1N4151 high speed switching diodes. Similar to 1N4148. 10 diodes for 35p. Cat. No. 403
- 10 HYBRID CIRCUITS 8 resistors and 8 capacitors built into each hybrid circuit. Ideal values for semiconductor circuits. Excellent for minimizing PCB component space. 10 Hybrids for 50p. Cat. No. 801

Untested Items

- LED DISPLAYS (Untested — no guarantees) 10 seven segment LED displays. 0.127" digits common cathode. 10 for £1.00. Cat. No. 311
- 30 MIXED IC'S (Untested — no guarantees) Could include anything Linear or Digital. You test. Good value for £1.00. Cat. No. 503
- REJECT CALCULATORS Production line rejects. Yields lots of goodies when stripped down (not much wrong with some we tested) Only £2.50 each. Cat. No. 104

A full refund guarantee on all items. Post and Packing please add 35p (Overseas orders add 90p). Lots more goodies in our catalogue. Send medium sized SAE for your free copy.

Marshall's

Head Office and Mail Order to Dept. P.E.,
A. Marshall (London) Ltd.,
Kingsgate House, Kingsgate Place,
London NW6 4TA. Tel: 01-624 0805.
Telex: 21492.


Retail Sales: London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 ALSO 325 Edgware Road, W2. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133 AND Bristol: 108A Stoke's Croft, Bristol. Tel: 0272 426801

BRIDGE RECTIFIERS

Type	Rating	Price	Type	Rating	Price
W005/			S005		
T1001	1A 50V 0.28	PW01	6A 100V 0.95	S01	2A 100V 0.44
W01	1A 100V 0.30	PW02	6A 200V 0.97	S02	2A 200V 0.48
W02	1A 200V 0.40	PW03	6A 400V 1.06	S04	2A 400V 0.60
W04	1A 400V 0.40	PW06	6A 800V 1.18	S06	2A 800V 0.74
W06	1A 600V 0.50	PW08	6A 100V 1.28	S08	2A 600V 0.84
W08	1A 800V 0.60	PW10	6A 1000V 1.60	S10	2A 1000V 1.35
VM18	1A 100V 0.44	K005	25A 50V 2.20	B40C1500	1.5A 100V 0.53
VM28	1A 200V 0.48	K01	25A 100V 2.37	B40C3200	3.2A 100V 1.20
VM45	1A 400V 0.50	K02	25A 200V 2.75	B40C1500	1.5A 200V 0.82
BY16	1A 120V 0.75	K04	25A 400V 3.40	B40C3200	3.2A 200V 1.25
BY179	1A 800V 0.70	K06	25A 600V 3.99	PW005	6A 50V 0.90

SINGLE IN LINE PLUGS AND SOCKETS

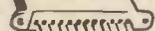Providing a simple and economical alternative to edge connectors for bringing cable into a pcb.
12 Way £0.90, 24 Way £1.20



New-SIEMENS TURN-SLIDE SWITCHES

This new version of the rotary switch is especially suitable for setting programs. The rotary switch is of 1 element no stop.
Voltage rating $\leq 60V$
Current rating $\leq 0.5A$
fixed contacts gold-plated. £2.65

TTL (see catalogue for full range)

SN74405N	0.60	74LS75N	0.58	74LS194N	0.70	74LS490N	0.90
SN74410N	0.55	74LS76N	0.42	74LS195N	0.70	74LS670N	1.90
SN74411N	0.55	74LS78N	0.42	74LS196N	0.80	SN74S00N	0.77
SN74420N	0.55	74LS83AN	0.90	74LS197N	0.80	SN74S01N	0.77
SN74421N	0.55	74LS85N	0.95	74LS221N	0.80	SN74S04AN	0.94
SN74430N	0.55	74LS86N	0.44	74LS224N	1.50	SN74S10N	0.77
SN74440N	0.55	74LS90N	0.42	74LS241N	1.50	SN74S20N	0.77
SN74451N	0.55	74LS91N	1.20	74LS242N	1.25	SN74S40N	0.77
SN74453N	0.55	74LS92N	0.70	74LS243N	1.25	SN74S46AN	0.77
SN74454N	0.55	74LS93N	0.64	74LS244N	1.50	SN74S65N	1.70
SN74455N	0.55	74LS95AN	0.90	74LS245N	1.65	SN74S101N	1.70
SN74460N	0.55	74LS96N	1.35	74LS247N	1.09	SN74S114N	1.70
SN74462N	0.55	74LS107N	0.42	74LS248N	1.09	SN74S140N	0.77
SN74470N	0.55	74LS109N	0.42	74LS249N	1.09	SN74S141N	0.77
SN74480N	0.55	74LS112N	0.42	74LS251N	1.00	SN74S188N	2.70
SN74481N	0.55	74LS113N	0.42	74LS252N	1.00	SN74S189N	1.81
SN74482N	0.55	74LS114N	0.42	74LS253N	1.00	SN74S189N	1.81
SN74474N	0.30	74LS114N	0.42	74LS257N	1.00	SN74S200N	3.50
SN74477N	0.30	74LS122N	0.62	74LS258N	1.00	SN74S201N	3.71
SN74485N	2.62	74LS123N	0.83	74LS259N	1.55	SN74S262N	12.50
SN74493N	2.60	74LS124N	1.70	74LS261N	3.25	SN74S287N	2.95
SN74500N	0.26	74LS125N	0.50	74LS266N	0.44	SN74S288N	2.70
SN74501N	0.26	74LS126N	0.50	74LS273N	1.30	SN74S289N	1.81
SN74502N	0.26	74LS126N	0.85	74LS275N	3.20	SN74S300N	5.06
SN74503N	0.26	74LS136N	0.42	74LS279N	0.58	SN74S301N	3.71
SN74504N	0.29	74LS138N	0.65	74LS280N	1.65	SN74S387N	3.05
SN74505N	0.29	74LS139N	0.65	74LS283N	1.20	SN74S470N	5.06
SN74508N	0.26	74LS156N	1.30	74LS289N	3.74	SN74S471N	5.06
SN74509N	0.26	74LS157N	1.30	74LS290N	1.00	SN74S472N	13.48
SN74510N	0.26	74LS158N	1.35	74LS293N	1.00	SN74S473N	13.48
SN74511N	0.26	74LS151N	0.58	74LS295N	1.35	SN74S474N	13.48
SN74512N	0.26	74LS153N	0.58	74LS298N	1.35	SN74S475N	13.48
SN74513N	0.58	74LS154N	1.45	SN74S299N	2.95	SN74S490AN	0.36
SN74514N	0.75	74LS155N	0.80	74LS323N	3.50	SN74S491AN	0.60
SN74515N	0.26	74LS156N	0.80	74LS324N	1.85	SN74S492N	0.36
SN74520N	0.26	74LS157N	0.60	74LS325N	2.95	SN74S493N	0.36
SN74521N	0.26	74LS158N	0.65	74LS326N	2.70	SN74S494N	0.90
SN74522N	0.26	74LS160N	0.80	74LS327N	2.55	SN74S495N	0.76
SN74526N	0.32	74LS161N	0.85	74LS348N	1.10	SN74S498N	0.54
SN74527N	0.26	74LS162N	0.80	74LS352N	1.07	SN74S497N	1.95
SN74528N	0.29	74LS163N	0.85	74LS353N	0.77	SN74S410N	0.24
SN74529N	0.26	74LS164N	1.10	74LS354N	1.10	SN74S4107N	0.24
SN74532N	0.27	74LS165N	1.15	74LS366N	0.55	SN74S118N	0.95
SN74533N	0.29	74LS166N	1.65	74LS367N	0.55	SN74S119N	1.40
SN74537N	0.32	74LS168N	1.45	74LS368N	0.55	SN74S121N	0.28
SN74538N	0.32	74LS169N	1.45	74LS373N	0.85	SN74S122N	0.55
SN74540N	0.26	74LS170N	1.10	74LS374N	0.85	SN74S123N	0.55
SN74542N	0.80	74LS173N	1.10	74LS375N	0.60	SN74S124N	0.20
SN74547N	1.09	74LS174N	0.75	74LS377N	1.30	SN74S125N	0.45
SN74548N	1.00	74LS175N	0.75	74LS378N	1.00	SN74S141N	0.56
SN74549N	1.05	74LS181N	2.75	74LS379N	1.25	SN74S145AN	1.95
SN74551N	0.26	74LS183N	2.70	74LS380N	0.84	SN74S148N	0.35
SN74554N	0.26	74LS186N	3.74	74LS381N	1.00	SN74S150N	0.90
SN74555N	0.26	74LS189N	1.00	74LS393N	0.50	SN74S151N	0.76
SN74563N	1.26	74LS191N	1.00	74LS395N	1.50	SN74S159N	0.65
SN74574N	0.42	74LS192N	0.95	74LS398N	1.90	SN74S154N	1.20
SN74579N	0.42	74LS193N	0.95	74LS399N	1.65	SN74S155N	0.70

TRANSISTORS (see catalogue for full range)

2N235	0.30	2N708	0.30	2N1420	0.55	2N2219	0.38	40081	1.20	AC188	0.54	BC118	0.22	BCY33A	1.10	80140	0.43	BF157	0.48
2N388	0.80	2N718	0.30	2N1483	1.85	2N2219A	0.39	40232	0.60	AD188K	0.65	BC119	0.33	BCY34A	1.10	80142	0.70	BF159	0.37
2N389A	0.77	2N718A	0.50	2N1485	2.20	2N2220	0.39	40233	0.70	AD136	2.75	BC122	0.61	BCY38	2.20	80X14	1.32	BF160	0.40
2N398	0.80	2N720A	0.35	2N1501	0.35	2N2221	0.25	40234	0.65	AD142	1.45	BC123	0.65	BCY40	1.95	80X18	1.90	BF161	0.33
2N456	2.20	2N721	1.05	2N1524	0.60	2N2221A	0.25	40237	0.85	AD143	1.45	BC125	0.62	BCY42	0.85	80X32	2.67	BF168	0.44
2N489	4.90	2N722	0.45	2N1553	1.50	2N2222	0.25	40242	0.66	AD149	2.85	BC132	0.33	BCY43	0.76	80Y11	3.30	BF167	0.37
2N489A	5.40	2N727	0.50	2N1613	0.30	2N2222A	0.25	40251	1.15	AD150	3.10	BC134	0.22	BCY54	2.40	80Y17	3.30	BF170	0.76
2N489B	5.90	2N744	0.35	2N1637	0.72	2N2223	0.27	40254	0.96	AD161	1.00	BC135	0.22	BCY58	0.27	80Y18	3.30	BF173	0.35
2N490	4.99	2N753	0.35	2N1638	0.70	2N2223A	0.28	40264	0.95	AD162	1.00	BC138	0.21	BCY59	0.27	80Y20	1.10	TPF90	0.85
2N490B	6.50	2N760	0.35	2N1711	0.30	2N2224	0.48	40260	3.90	AF105	0.60	BC137	0.22	BCY68	2.20	80Y23	2.45	TP30A	0.54
2N490C	6.90	2N869	0.35	2N1889	0.30	2N2303	1.54	40309	0.60	AF108	0.82	BC138	0.44	BCY67	2.70	80Y24	2.85	TP30C	0.70
2N491A	5.75	2N914	0.38	2N1890	0.30	2N2368	0.27	40310	0.85	AF114	0.70	BC140	0.30	BCY70	2.01	80Y25	2.85	TP31A	0.54
2N491B	6.25	2N916	0.33	2N1893	0.30	2N2369	0.27	40311	0.55	AF115	0.70	BC141	0.32	BCY71	0.26	80Y38	1.10	TP31C	0.72
2N491	7.50	2N917	0.38	2N1907	0.55	2N2369A	0.27	40312	0.99	AF116	0.70	BC142	0.32	BCY72	0.18	80Y54	1.55	TP32A	0.59
2N492	6.25	2N918	0.45	2N1974	0.58	2N2405	0.66	40313	1.38	AF117	0.70	BC143	0.32	BCY77	0.70	80Y55	1.90	TP32C	0.59
2N492A	6.75	2N929	0.37	2N1990	0.45	3N81	3.50	40315	0.60	AF118	0.70	BC152	0.38	BCY78	0.43	80Y56	2.10	TP33A	0.86
2N492B	7.25	2N930	0.37	2N1991	0.45	3N82	3.25	40316	0.95	AF126	1.45	BC153	0.65	BCY79	0.41	80Y57	5.90	TP33C	1.18
2N492C	6.90	2N930A	0.37	2N20670	1.00	3N128	3.50	40317	0.60	AF125	0.70	BC154	0.30	BCY87	5.35	80Y58	5.50	TP34A	0.87
2N493A	7.99	2N930A	0.95	2N2102	0.50	3N139	1.60	40324	0.95	AF126	0.70	BC160	0.38	BCY88	3.99	80Y60	1.65	TP34C	1.13
2N493B	8.76	2N1131	0.32	2N2147	1.55	3N140	1.10	40325	1.35	AF139	0.75	BC161	0.38	BCY89	3.80	80Y61	2.75	TP35A	2.20
2N494	6.90	2N1132	0.35	2N2160	1.55	3N141	0.95	40326	0.48	AF172	0.70	BC175	0.43	80Y115	0.80	80Y62	2.75	TP36A	2.00
2N494A	7.65	2N1204	1.65	2N2192	0.58	3N142	0.70	40327	0										

BAKER "BIG-SOUND" SPEAKERS Post £1.60 each

'Group 100'	'Group 35'	'Group 50/15'
12 inch 100 watt	12 inch 40 watt	15 inch 75 watt
£29	£15	£35
8 or 16 ohm	4 or 8 or 16 ohm	8 or 16 ohm

BAKER LOUDSPEAKER, 12 INCH, 60 WATT.
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.
FULL RANGE PROFESSIONAL QUALITY.
RESPONSE 30-16,000 CPS
MASSIVE CERAMIC MAGNET
WITH ALUMINIUM PRESENCE CENTRE DOME. **£23**

4 CHANNEL TRANSISTOR MONOMIXER
Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£7.50**
Two channel stereo version - £9.

HEATING ELEMENTS WAFER THIN
Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or similar. ALL POST PAID - Discounts for quantity.
ONLY 40p EACH (FOUR FOR £1.50)

MINI MODULE BAFFLE KIT Post 75p
EMI 15 x 8 1/2 in. 3-way Loudspeaker System 5in. Bass 5in. Middle 3in Tweeter with 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response=60 to 20 000 C.P.S. 12 watt RMS. 8 ohms. £10.95 per kit. Two kits £20.
Suitable Bookshelf Cabinet £9.50 each.



SINGLE RECORD PLAYER
Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable Size 7in. diameter a.c. mains 240V 3 speeds plays all size records. **£7.95**
Two for £16. Post 75p.

NEW BSR SINGLE PLAYER £24.50
Model P182 3-speeds flared aluminium turntable. Post £1. "S" shaped arm, cueing device, stereo ceramic cartridge.
B.S.R. De-Luxe Autochanger with stereo cartridge, plays all size records. P. & P. £1. **£20.00**

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER
Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music 4 way mixing.
Output 4/8/16 ohm, a.c. Mains 240V.
Separate treble and bass controls.
100 volt line model £14 extra. **£85** Post £1.60

BAKER COMPACT 50 WATT AMPLIFIER
IDEAL FOR DISCOS, GROUPS, PUBLIC ADDRESS
Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£63** Post £1.60

R.C.S. SOUND TO LIGHT DISPLAY MK II
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. **KIT = £18.00**

R.C.S. 10 WATT AMPLIFIER KIT
This kit is suitable for record players, tape play back, guitars electronic instruments or small PA systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume bass and treble controls. Spec. 10W output into 8 ohms 7W into 16ohms. Response 20c to 20Kc. Input 100mV. high Imp. Size 9 1/2 x 3 x 2 1/2 in. A/C mains operated
Mono kit **£12.50** Stereo kit **£20** Post 45p
Easy to build. Full instructions supplied

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 40V 60p; 25V 42p; 2500mF 50V 62p. 3000 mF 25V 47p; 50V 65p; 2700mF 76V £1. 4700mF 63V £1.20. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p. 5600mF 76V £1.76. 1200mF 76V 60p.

HIGH VOLTAGE ELECTROLYTICS
8/350V 22p 8+8/450V 50p 50+50/300V 50p
18/350V 30p 8+16/450V 50p 32+32/450V 75p
32/500V 75p 16+16/450V 50p 100+100/275V 65p
50/350V 50p 32-32/350V 50p 160+200/275V 70p
MANY OTHERS IN STOCK

TINTEO PLASTIC COVERS ONLY
Sizes: 14 1/2 x 12 1/2 x 4 1/2 in. £3. 16 x 14 x 3 1/2 in. £5. 15 1/2 x 13 1/2 x 4 in. £4. 17 1/2 x 9 1/2 x 3 1/2 in. £3. 14 1/2 x 14 1/2 x 2 1/2 in. Rosewood sides £4. 18 x 13 1/2 x 3 in. £6. 18 x 12 1/2 x 3 in. £6.
Ideal for record decks, tape decks, etc. Post £1.60

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £2.95
All parts and instructions with Zener diode printed circuit. rectifiers and double wound mains transformer input 200 240V a.c. Output voltages available 6 or 7, 5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required. Post 45p

ELECTRO MAGNETIC PENDULUM MECHANISM 95p Post 30p
1.5V d.c. operation over 300 hours continuous on SP2 battery fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome. strobe. etc

MAINS TRANSFORMERS ALL POST 75p each

250-0-250V 70mA 6 3/2A	£3.45
250-0-250 80mA. 6 3V 3 1A	£4.60
350-0-350 80mA. 6 3V 3 5A. 6 3V 1A	£9.00
300-0-300 120mA 2 + 6 3V 2A C.T.	£8.50
220V 45mA. 6-3V 2A	£1.78
HEATER TRANS 6 3V 3A £2 1/2 amp	£2.20
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at	
2A 3. 4. 5. 6. 9. 10. 12. 15. 18. 24 and 30V	£6.00
1A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£8.00
2A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£9.50
3A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£12.50
5A. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60	£16.00
5. 8. 10. 16V 1A £2.80 12V 100mA £1.30 12V 300mA £1.30.	
12V 750mA £1.60. 40V 2A tapped 10V or 30V £3.60.	
10-0-10V 2A £3. 40V 2A £3.80. 30V 5A 2A ct. £4.00.	
2 x 18V 6A £11. 12-0-12V 2 amp £3.50. 25-0-25V 2 amp £4.80.	
20-0-20V 1A £3.60. 30V 1A £3.30. 20V 1A £3.	
9V 3 amp £3.60. 60V. 40V. 20V or 20V. 1A £4.	
30-0-30 2A £8. 9V 250mA £1.50. 30V 2 amp £3.80.	
AUTO TRANSFORMERS 115V to 230V or 230ohm to 115V	
150W £7; 250W £8; 400W £9; 500W £10.	
CHARGER TRANSFORMERS Input 200/250V for 6 or 12V	
1 1/2A £4.25; 4A £7.25.	
FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs	
1 1/2A £5; 4A £1.60. HALF WAVE 12V 1 1/2A 38p.	

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. 6 x 4 in. 95p; 8 x 6 in. £1.40; 10 x 7 in. £1.85; 14 x 9 in. £1.90; 16 x 6 in. £1.85; 12 x 3 in. £1.20; 16 x 10 in. £2.20, 12 x 8 in. £1.70.
ALUMINIUM PANELS. 18 s.w.g. 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 5 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1.18; 10 in. £1.18.
ALUMINIUM ANGLE BRACKET. 6 x 1 1/2 x 3 in. 20p.
ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK
4 x 2 x 2 in. 85p; 3 x 2 x 1 in. 65p; 6 x 4 x 2 in. 95p; 9 x 6 x 3 in. £1.80; 9 x 4 x 4 in. £1.70; 10 x 7 x 3 in. £2.00; 12 x 8 x 3 £2.00.
THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes, and all sizes of tape reels a.c. mains 200/240V **£6.00**
Leaflet SAE. Post 50p.
Head demagnetiser **£5.00**


RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K.

Minimum post 30p. Access and Barclaycard Same day despatch Radio Books and Components Lists 20p Open 9-6 Sat. 9-5 (Closed Wednesday all day). Tel. 01-684 1665

Electronics

Make a job~or hobby~of it.....

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market. We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .

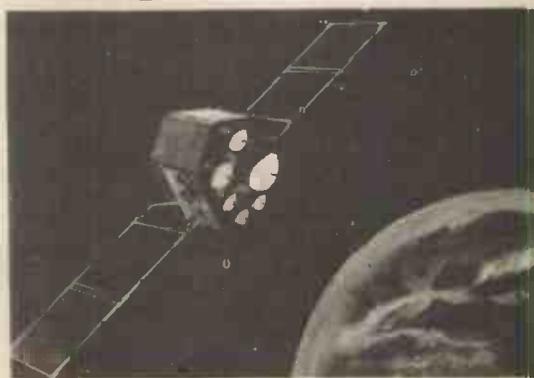

Free! Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

Block caps please


BIMENCLOSURES



ALL METAL BIMCASES
Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.
BIM 3000
(250x167.5x68.5mm) £15.52



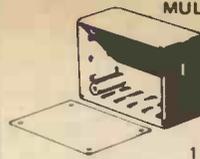MINI DESK BIMCONSOLES
Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied. 1mm Grey Aluminium panel sits recessed with fixing screws into integral brass bushes.
BIM 1005 (161 x 96 x 58mm) £2.48
BIM 1006 (215 x 130 x 75mm) £3.48





MULTI PURPOSE BIMBOXES
Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes. 1.8mm pcb guides incorporated and 4 BIMFEET supplied.
BIM 4003 (85x56x28.5mm) £1.34
BIM 4004 (111x71x41.5mm) £1.84
BIM 4005 (161x96x52.5mm) £2.48

ALL METAL BIMCONSOLES



All aluminium, 2 piece desk consoles with either 15° or 30° sloping fronts, sit on 4 self-adhesive non-slip rubber feet. Ventilation slots in base and rear panel for excellent cooling. See latest catalogue for new styles and sizes

15° Sloping Panel		30° Sloping Panel		Colour Code	Top Panel	Base
BIM7151 (102x140x51[28] mm)	BIM7301 (102x140x76[28] mm)	£11.36	A	OffWhite	Blue	
BIM7152 (165x140x51[28] mm)	BIM7302 (165x140x76[28] mm)	£12.28	B	Sand	Green	
BIM7153 (165x216x51[28] mm)	BIM7303 (165x183x102[28] mm)	£13.43	C	Satin Black	Gold	
BIM7154 (165x211x76[33] mm)	BIM7304 (254x140x76[28] mm)	£14.83				
BIM7155 (254x211x76[33] mm)	BIM7305 (254x183x102[28] mm)	£16.36				
BIM7156 (254x287x76[33] mm)	BIM7306 (254x259x102[28] mm)	£17.71				
BIM7157 (356x211x76[33] mm)	BIM7307 (356x183x102[28] mm)	£18.83				
BIM7158 (356x287x76[33] mm)	BIM7308 (356x259x102[28] mm)	£19.92				

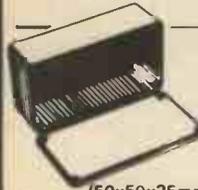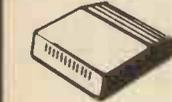


ABS & DIECAST BIMBOXES

6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue, Black or Grey. Diecast Aluminium in Grey Hammertone or Natural. All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).

	ABS		Diecast		Hammertone	Natural
(50x50x25mm)	N/A		BIM5001/11	£1.54	£1.23	
(100x50x25mm)	BIM2002/12	£1.09	BIM5002/12	£1.66	£1.32	
(112x62x31mm)	BIM2003/13	£1.27	BIM5003/13	£2.24	£1.70	
(120x65x40mm)	BIM2004/14	£1.51	BIM5004/14	£2.81	£2.11	
(150x80x50mm)	BIM2005/15	£1.72	BIM5005/15	£3.19	£2.72	
(190x110x60mm)	BIM2006/16	£2.69	BIM5006/16	£4.94	£3.96	

Also available in Grey Polystyrene with no slots and self-tapping screws
BIM 2007/17 (112x61x31mm) £1.06

LOW PROFILE BIMCONSOLES

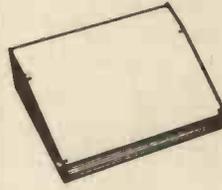

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes. 4 BIMFEET supplied.

BIM 6005 (143 x 105 x 55.5 [31.5] mm)	£2.76
BIM 6006 (143 x 170 x 55.5 [31.5] mm)	£3.58
BIM 6007 (214 x 170 x 82.0 [31.5] mm)	£4.83

EUROCARD BIMCONSOLES



Orange, Blue, Black or Grey ABS body accepts full or 1/2 size Eurocards, with bosses in the base for direct fixing. 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied. 1mm Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.

BIM 8005 (169x127x70[45]mm)	£4.71
BIM 8007 (243x187x103[66]mm)	£6.70

BIMTOOLS + BIMACCESSORIES



MAINS BIMDRILLS


Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks. Drills brass, steel, aluminium and pcb's. Under 250g, off load speed 7500 rpm. Orange ABS, high impact, fully insulated body with integral on/off switch £11.21

Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burrs and 2.4mm collet £2.64

Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burrs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £23.57

BIMDAPTORS

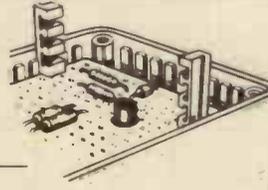Allows pcb's to be flat mounted sandwich fashion in BIMBOXES, BIMCONSOLES, and all other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snapped off to length. £1.15 per pack of 25.



BIMFEET

11mm dia. 3mm high, grey rubber self-adhesive enclosure feet. £0.81 per pack of 24.

12 VOLT BIMDRILLS

2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia. £ 8.62
Major BIMDRILL with 4 collets up to 3mm dia. £14.49

Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £16.10, Major Kit 1 - £20.70. Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains-12V dc adaptor. Mini Kit 2 - £36.22, Major Kit 2 - £41.97. Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £48.30, Major Kit 3 - £54.05.

BIMPUMPS

2 all metal desoldering tools provide high suction power and have easily replaceable screw in Teflon tips. Primed and released by thumb operation with in-built safety guard and anti-recoil system.
BIMPUMP Major (180mm long) £8.51
BIMPUMP Minor (150mm long) £7.24



BIMIRONS


Type 30 General Purpose 27 watt iron with long life, rapid change element, screw on tip, stainless steel shaft and clip on hook. Styled handle with neon. £4.37
Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip on hook. £4.71



BIMBOARDS



DIL COMPATIBLE BIMBOARDS

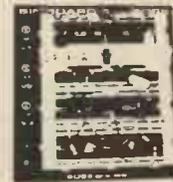

Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LEDs. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple

units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1	£ 8.23
BIMBOARD 2	£19.99
BIMBOARD 3	£29.07
BIMBOARD 4	£38.14

DESIGNER PROTOTYPING SYSTEM

1, 2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (±5 to ±15Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

DESIGNER 1	£58.65
DESIGNER 2	£64.97
DESIGNER 3	£71.30



...FROM **BOSS** INDUSTRIAL MOULDINGS LIMITED

All orders please state L.F.M. and include Postage. Please quote V.A.T. Terms and conditions apply with order unless you have authorized B.O.S.S. account. For details of data sheets or other forms contact your local B.O.S.S. distributor and stamped and addressed 4 x 8 envelope.

2 Herne Hill Road London SE24 0AU
Telephone 01 737 2383
Telex 919693 Answer Back LITZEN G
Cables & Telegrams LITZEN LONDON SE24



VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS
MAIL ORDER SERVICE**

AA119	0-12	BCY70	0-17	MPSU01	0-41	1N914	0-06	7405	0-18
AA30	0-31	BCY71	0-20	MPSU06	0-53	1N916	0-08	7406	0-46
AA32	0-48	BCY72	0-15	MPSU66	0-56	1N4001	0-07	7407	0-46
AA33	0-21	BCZ11	1-72	NE555	0-52	1N4002	0-07	7408	0-23
AA35	0-39	BD115	0-52	NKT401	2-30	1N4003	0-08	7409	0-23
AA37	0-31	BD121	1-38	NKT403	1-99	1N4004	0-08	7410	0-18
AC107	0-69	BD123	1-38	NKT404	1-99	1N4005	0-09	7411	0-30
AC125	0-23	BD124	1-50	OA5	1-09	1N4006	0-09	7413	0-37
AC126	0-23	BD131	0-40	OA7	0-63	1N4007	0-10	7416	0-37
AC127	0-23	BD132	0-44	OA10	0-74	1N4009	0-17	7417	0-37
AC128	0-23	BD135	0-39	OA47	0-16	1N4148	0-07	7420	0-20
AC141	0-29	BD136	0-39	OA70	0-38	1N5400	0-15	7422	0-23
AC141K	0-40	BD137	0-40	OA79	0-35	1N5401	0-15	7423	0-37
AC142	0-23	BD138	0-46	OA81	0-36	1S44	0-05	7425	0-35
AC142K	0-38	BD139	0-49	OA85	0-35	1S920	0-08	7427	0-35
AC176	0-23	BD140	0-51	OA90	0-09	1S921	0-08	7428	0-49
AC187	0-23	BD144	2-30	OA91	0-09	2G301	1-15	7430	0-20
AC188	0-23	BD181	1-26	OA95	0-09	2G302	1-15	7432	0-35
ACY17	0-98	BD182	1-36	OA200	0-10	2G306	1-27	7433	0-37
ACY18	0-92	BD237	0-46	OA202	0-10	2N404	1-15	7437	0-37
ACY19	0-86	BD238	0-63	OA211	1-15	2N696	0-29	7438	0-37
ACY20	0-80	BDX10	1-05	OAZ200	1-15	2N697	0-29	7440	0-21
ACY21	0-86	BDX32	2-30	OAZ201	1-15	2N698	0-35	7441A	0-97
ACY39	1-72	BDY20	1-44	OAZ206	1-15	2N705	1-38	7442	0-83
AD149	0-80	BDY60	1-72	OAZ207	1-15	2N706	0-17	7447A	1-04
AD181	0-40	BF115	0-40	OC16	2-30	2N708	0-23	7450	0-37
ASZ15	1-44	BF129	0-21	OC20	2-88	2N930	0-23	7451	0-21
AF106	0-52	BF153	0-23	OC22	2-88	2N1131	0-30	7453	0-21
AF114	0-86	BF154	0-20	OC23	3-16	2N1132	0-30	7454	0-21
AF115	0-86	BF159	0-26	OC24	3-45	2N1302	0-40	7460	0-21
AF116	0-86	BF160	0-18	OC25	1-04	2N1303	0-40	7470	0-40
AF117	0-86	BF167	0-23	OC26	1-04	2N1304	0-40	7472	0-38
AF139	1-38	BF173	0-28	OC28	2-30	2N1305	0-52	7473	0-41
AF186	1-38	BF177	0-28	OC29	2-30	2N1306	0-58	7474	0-46
AF239	0-52	BF178	0-28	OC35	1-73	2N1307	0-58	7475	0-62
AFZ11	3-16	BF179	0-29	OC36	1-73	2N1308	0-63	7476	0-46
AFZ12	3-16	BF180	0-35	OC41	0-92	2N1309	0-63	7480	0-63
ASY26	0-46	BF181	0-35	OC42	0-86	2N1613	0-25	7482	0-86
ASY27	0-46	BF182	0-35	OC43	2-59	2N1671	1-73	7483	1-04
ASZ15	1-44	BF185	0-29	OC44	0-89	2N1893	0-29	7484	0-15
ASZ16	1-44	BF184	0-29	OC45	0-63	2N2147	2-02	7486	0-40
ASZ17	1-44	BF185	0-29	OC71	0-63	2N2148	1-89	7490	0-60
ASZ20	1-72	BF194	0-10	OC72	0-63	2N2218	0-29	7491A	0-92
ASZ21	2-30	BF195	0-10	OC73	1-15	2N2219	0-28	7492	0-69
AU110	2-30	BF196	0-12	OC74	0-74	2N2220	0-21	7493	0-69
AU113	1-96	BF197	0-14	OC75	0-74	2N2221	0-21	7494	0-92
AU110	1-96	BF200	0-31	OC76	0-63	2N2222	0-21	7495	0-83
BA145	0-15	BF224	0-23	OC77	1-38	2N2223	3-16	7496	0-92
BA146	0-15	BF244	0-32	OC81	0-74	2N2368	0-20	7494	3-45
BA154	0-10	BF257	0-28	OC812	1-38	2N2369A	0-24	74100	1-73
BA155	0-12	BF258	0-30	OC82	0-74	2N2484	0-23	74107	0-52
BA156	0-12	BF259	0-37	OC83	0-74	2N2546	0-63	74109	0-81
BAW62	0-06	BF336	0-35	OC84	0-74	2N2904	0-29	74110	0-58
BAX13	0-07	BF337	0-35	OC122	1-73	2N2905	0-29	74111	0-81
BAX16	0-10	BF338	0-36	OC123	2-02	2N2906	0-24	74116	2-02
BC107	0-14	BFS21	4-55	OC139	2-59	2N2907	0-24	74118	1-15
BC108	0-14	BFS28	2-56	OC140	3-16	2N2924	0-24	74119	1-73
BC109	0-15	BFS51	0-24	OC141	3-74	2N2925	0-25	74120	0-95
BC113	0-18	BFS98	0-23	OC170	1-15	2N2926	0-16	74121	0-46
BC114	0-15	BFW10	0-74	OC171	1-15	2N3053	0-29	74122	0-69
BC115	0-16	BFW11	0-74	OC200	1-73	2N3054	0-58	74123	1-15
BC116	0-17	BFX84	0-25	OC201	2-02	2N3055	0-81	74125	0-63
BC117	0-20	BFX85	0-26	OC202	2-02	2N3440	0-89	74126	0-63
BC118	0-12	BFX87	0-24	OC203	2-02	2N3441	0-92	74128	0-63
BC125	0-18	BFS98	0-24	OC204	2-88	2N3442	1-26	74132	0-81
BC126	0-23	BFY50	0-30	OC205	2-88			74136	0-63
BC135	0-16	BFY51	0-30	OC206	2-88	2N3614	1-73	74141	0-92
BC136	0-17	BFY52	0-30	OC207	2-02	2N3702	1-73	74142	2-65
BC137	0-17	BFY64	0-30	OCP71	1-44	2N3703	0-15	74143	2-88
BC147	0-10	BFY90	1-44	ORP12	1-15	2N3704	0-18	74144	0-52
BC148	0-12	BSX19	0-24	R2008B	2-02	2N3705	0-15	74145	1-04
BC149	0-10	BSX20	0-23	R2009	2-59	2N3706	0-15	74147	2-30
BC157	0-10	BSX21	0-23	R2010B	2-02	2N3707	0-15	74148	2-02
BC158	0-09	BT106	1-44	T1C44	0-35	2N3708	0-12	74149	1-84
BC159	0-12	BTY79/4	3-67	T1C226D	1-38	2N3709	0-15	74151	0-97
BC167	0-14	BU205	2-02	T1L209	0-23	2N3710	0-12	74154	0-97
BC170	0-12	BU206	2-59	T1P28A	0-47	2N3711	0-12	74155	0-97
BC171	0-12	BU208	2-30	T1P30A	0-48	2N3771	2-02	74158	0-97
BC172	0-12	BY100	0-52	T1P31A	0-51	2N3772	2-30	74157	0-86
BC173	0-14	BY126	0-16	T1P32A	0-55	2N3773	3-45	74159	2-42
BC177	0-17	BY127	0-19	T1P33A	0-79	2N3819	0-41	74170	2-65
BC178	0-16	BZK61	0-21	T1P34A	0-84	2N3820	0-52	74172	5-06
BC179	0-18	Series	1-44	T1P41A	0-72	2N3823	0-63	74173	1-81
BC182	0-13	BZY88	0-15	T1P42A	0-81	2N3866	0-83	74174	1-73
BC183	0-12	Series	1-44	T1P2955	0-77	2N3904	0-15	74175	1-04
BC184	0-13			T1P3055	0-64	2N3905	0-15	74176	1-26
BC122	0-15	CRS1/40	0-69	T1S43	0-52	2N3906	0-15	74178	1-44
BC123	0-14	CRS3/40	0-86	ZS140	0-29	2N4048	0-16	74179	1-44
BC124	0-17	CRS3/60	1-04	ZS170	0-24	2N4059	0-12	74180	1-32
BC237	0-10	GEX66	1-73	ZS178	0-62	2N4060	0-14	74180	1-73
BC238	0-14	GEX541	2-02	ZS271	0-26	2N4061	0-14	74191	1-73
BC301	0-29	GJ3M	0-86	ZS278	0-65	2N4062	0-15	74192	1-55
BC303	0-28	GJ5M	0-86	ZTX107	0-13	2N4124	0-17	74193	1-85
BC307	0-12	GL7M	2-02	ZTX108	0-14	2N4125	0-17	74194	1-15
BC308	0-29	HM03/78A	0-86	ZTX109	0-13	2N4286	0-23	74195	1-85
BC327	0-23	KS100A	0-52	ZTX300	0-14	2N4288	0-25	74196	1-38
BC328	0-21	MJE340	0-92	ZTX301	0-15	2N4289	0-28	74197	1-26
BC337	0-21	MJE370	1-35	ZTX302	0-17	2N5457	0-40	74198	2-59
BC338	0-20	MJE371	0-60	ZTX303	0-20	2N5458	0-40	74199	2-59
BCV30	1-15	MJE520	1-63	ZTX311	0-14	2N5459	0-40	76013N	2-02
BCV31	1-15	MJE521	0-44	ZTX314	0-23				
BCV32	1-15	MJE2955	0-66	ZTX304	0-22				
BCV33	1-04	MJE3055	0-86	ZTX500	0-15				
BCV34	1-04	MPF102	0-35	ZTX501	0-16				
BCV39	3-45	MPF103	0-35	ZTX502	0-18				
BCV40	1-15	MPF104	0-35	ZTX503	0-20				
BCV42	0-29	MPF105	0-28	ZTX504	0-23				
BCV43	0-29	MPSA06	0-28	ZTX531	0-23				
BCV58	0-18	MPSA6	0-30	ZTX550	0-18				

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7
Quotations for any types not listed S.A.E.
Post and Packing 30p per order
All prices include VAT Telex 946708

AURA SOUNDS FOR WERSI KITS

14/15 ROYAL OAK CENTRE
BRIGHTON ROAD,
PURLEY, SURREY.
01-668 9733

SEE THE


"SOUND COMPUTER"

THE LATEST "STATE-OF-THE-ART"
ADDITION TO WERSI ORGANS

Send £1 for our 104 page full colour
Catalogue and Price List.

AURA SOUNDS
17 UPPER CHARTER ARCADE
BARNLEY, YORKSHIRE
0226 5248

STORAGE CABINETS

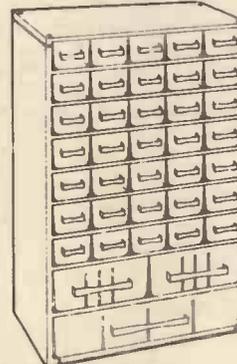

Metal Cabinets 12" wide x 5 3/4"
deep, finished blue with trans-
parent plastic drawers.

Type	H (ins)	No. of Drawers	Price
1118	11	15 2 1	£9-85
1633	16	30 2 1	£12-75
1838	18	35 2 1	£14-95
2236	22	30 4 2	£16-85
2260	22	60 - -	£16-95


Prices include VAT and Post. Cheque/P.O. to:

Millhill Supplies (Tools),
35 Preston Crowmarsh, Benson,
Oxon OX9 6SL.

PROGRESSIVE RADIO 31, CHEAPSIDE, LIVERPOOL L2 2DY
SEMICONDUCTORS. C106D 400V 2-5A SCR 20p. TB800 80p. 741 8 PIN 22p. NE555 24p. 1M3400 40p.
723 14 PIN REGS. 38p. AD181/2 MATCHED PAIRS 70p. 2N3055 38p. 1N4005 10 FOR 35p. BD238 28p.
BD438 28p.
MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY. 6-0-8 100mA. 9-0-9 75mA. 12-0-12 50mA
all 78p each. 12-0-12 100mA 95p. 12V 500mA 20p. 0-8V-0-8V 280mA

Simply ahead!

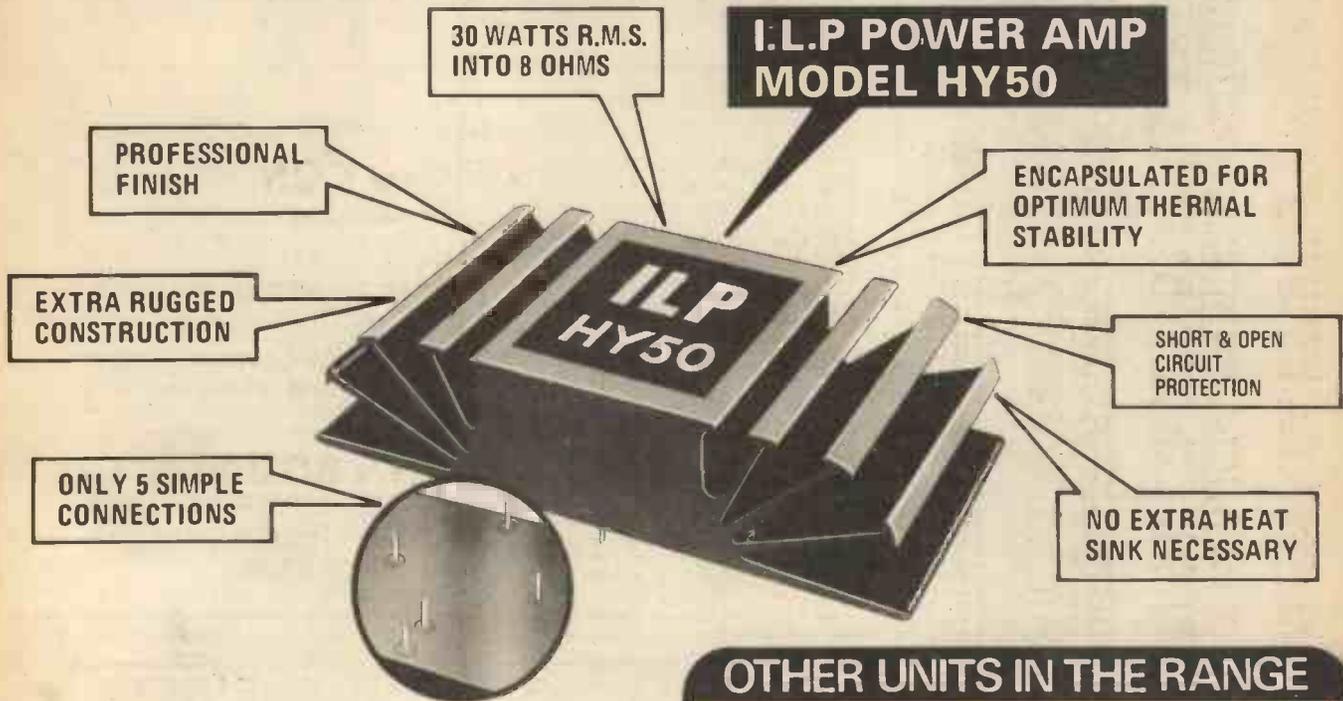**HIGH PERFORMANCE MODULAR UNITS
BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE**



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build or up-grade a hi-fi system, run a small high quality P.A. system, amplify a musical Instrument (say for practise or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make HY50 the ideal all-purpose quality power amp – and it is unconditionally guaranteed for five years. Tens of thousands are in use throughout the world.

... and a spec that means just what it says!

Encapsulated power amp with integral full-rated heatsink.
Input – 500mV
Output 30 watts RMS/8 Ω
Load Impedance – 4 to 16Ω
Distortion – 0.04% from 100mW to 25 watts at 1KHz/8Ω
Supply Voltage – ±25V. Size 105 x 50 x 25mm
Inc. V.A.T. and postage in U.K.

£8.33

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership for I.L.P. Now we have up-graded output ratings and down-graded prices to bring I.L.P. within easier reach of all who want the best.

New production techniques enable us to reduce prices apart from VAT by an average of 20%, making I.L.P. a better buy than ever.

Guaranteed 7 days despatch on all products

USE OUR FREE POST SERVICE for sending your orders, requests for information sheets etc. Simply address envelope.


NO STAMPS REQUIRED.



FREEPOST 2
Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP
Phone (0227) 54778 Telex 965780

OTHER UNITS IN THE RANGE

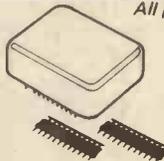
All prices inc. V.A.T. & Postage in the U.K.



HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps. and P.S.U.'s. In a single pack, needs external pots and switches. Multi-function equalization. 5 inputs, High overload margin. Active tone controls, 500 mV out. Distortion at 1 KHz – 0.01%.


Two connect easily for stereo. **£5.34**

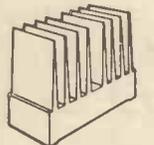

THE POWER AMPS

With heatsinks, full load line and thermal protection. Distortion typically 0.05% at 1 KHz.

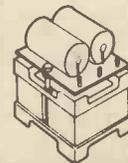HY120 60 Watts RMS/8Ω 114 x 50 x 85mm **£17.48**
HY200 120 Watts RMS/8Ω 114 x 50 x 85mm **£21.21**
HY400 240 Watts RMS/4Ω 114 x 100 x 85mm **£31.83**



THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power amps and HY5)

PSU50 for 1 or 2 x HY50 **£9.32**
PSU70 for 1 or 2 x HY120 **£16.85**
PSU90 for one HY200 **£15.85**
PSU180 for one HY400 or 2 x HY200 **£26.47**

Information sheets on application –
Use our FREEPOST Service.

★ NOW-PRICES DOWN BY 20%

Please supply
Total Purchase Price
I Enclose Cheque Postal Orders
Please debit my Access/Barclaycard Account number
Name
Address
Signature

Reg. Bus. No. 1032630 Eng.

FP 2/9



RECEIVERS AND COMPONENTS

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

ELECTRONIC COMPONENTS. Send S.A.E. for List. Special Offers monthly. Radnor Supplies, 23 Arbury Road, Nuneaton, Warwicks.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
 0.47 - 1.0 - 2.2 - 4.7 - & 10 Mds. — 5p.
 22 & 47 — 5p. (50V — 6p). 100 — 7p. (50V — 8p).
 220 — 8p. (50V — 10p). 470 — 11p. (40V — 16p).
 1000/15V — 15p. 1000/25V — 18p. 1000/40V — 35p.
 Subminiature bead Tantalum electrolytics.
 0.1 - 0.22 - 0.47 - 1.0 & 35V, 4.7 & 6.3V — 10p.
 2.2/35V, 4.7/25V — 11p. 10/25V, 15/16V — 14p.
 22/16V, 33/10V, 47/6V, 68/3V & 100/3V — 18p.
 15/25V, 22/25V, 47/10V — 24p. 47/16V — 32p.
 Subminiature Ceramic Caps. E12 Series 100V,
 2%, 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.
 10% 390 pf. to 4700 pf. — 4p.

Vertical Mounting Ceramic Plate Caps. 50V.
 E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.
 Polystyrene E12 Series 63V. Horizontal Mntg.
 10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.

Miniature Polyester 250V Vert. Mtg. E6 Series.
 .01 to .068 — 4p. .1 — 5p. 15, 22 — 6p. 33, 47 — 10p.
 .68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

Mylar (Polyester) Film 100V Vertical Mounting.
 .001, .002, .005 — 3p. .01, .02 — 4p. .04, .05 — 5p.

Miniature Film Resistors Highstab. E12 Ser. 5%.
 0.125W mixed carbon/metal 10Ω to 1MΩ — 1p.
 0.25W Carbon 1Ω to 10MΩ (10% over 1MΩ) — 1p.

(E24 Series av. in 3W C. Film 1Ω to 5M60).
 0.25W, 0.5W & 1.0W Metal Film 10Ω to 2M2Ω — 2p.
 1N4148 — 2p. 1N4002 — 4p. 1N4006 — 8p. 1N4007 — 7p.

8C107/8/9, 8C147/8/9, 8C157/8/9, 8F154 & 7 — 10p.
 8 Pin I.C.'s 741 Op. amp — 18p. 555 Timer — 24p.

Di. Holders 8 pin — 9p. 14 pin — 12p. 16 pin — 14p.
 LED's 3 & 5mm. Red — 10p. Green & Yellow — 14p.

Grommets for 3mm. — 1p. 2 pce. holders 5mm. — 2p.
 20mm. Q.B. Fuses .15, .25, .5, 1, 2, 3 & 5A — 3p.
 20mm. Anti Surge 100mA. to 5.0A — 8p.

20mm. Fuseholders P.C. or Chassis Mtg. — 5p.
 Solid A.I. knobs 15mm. — 25p. 25mm. — 35p. 30mm. — 50p.
 400mW Zener diodes E24 series 2V7 to 33V — 8p.

Prices VAT Inclusive Post 10p. (Free over £4).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

TUNBRIDGE WELLS COMPONENTS, Ballards, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquires S.A.E.

SURPLUS stocks of Electronic Components at less than wholesale prices. SAE brings free lists. Bardwell Ltd., 212 Stubby Lane, Dronfield-Woodhouse, Sheffield, S18 5YP.

COMPONENTS AT SILLY PRICES! Mixed Resistors: 250 £1.20, 1000 £3.60. Capacitors: 100 £1.00, 500 £3.20. Transistors: BC108, BC214 10 70p. 100 £5.80. Mixed Components, Hardware, Boards 10lbs £3.50. S.A.E. Lists. W.V.E.3, Craig Farm, Tintern, Gwent.

P.C.B.s Paxillon 10 1/4" x 4 1/4" 4-£1.30. 12" x 9 1/2" 85p. 16" x 11 1/4" £1.40. D.S. 10" x 8 1/2" 85p. Fibre Glass 12" x 7 1/2" £1.80. D.S. 10 1/2" x 7" £1.35. 8" x 7" £1.15. Unit with 8 silicon diodes 600V 20 amp, 8 SCRs 400V 16 amp, 6 Vinkors, W.W. resistors etc. £6.75. 300 small components, trans. diodes £1.55. 7 lbs. assorted components £3.75. List 15p refundable. Post 20p. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

ELECTRONIC COMPONENT. Quick delivery, wide range from stock. Catalogue on request. J. R. Hartley Electronic Components, 78B High Street, Bridgnorth, Salop, WV16 4DY.

100 MIXED COMPNDENTS £2.75, 10 LEDS 90p Lists 15p. Sole, 37 Stanley Street, Ormskirik, Lancs. L39 2DH.

SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

Publishers Announcement

Due to increases which may have taken effect since this issue went to press, we strongly advise readers to check with advertisers the prices shown, and availability of goods, before purchasing.

EDUCATIONAL

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. M272 Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. M272 Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. M272 Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

CAPACITY AVAILABLE

PRINTED CIRCUIT BOARDS. Quick deliveries, competitive prices, quotations on request, speciality small batches, larger quantities available. Contact: Mr. J. K. Harrison, Jamieson Automatics Ltd., 1/5 Westgate, Bridlington, North Humberside. Tel: (0262) 74738/77877.

AERIALS

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.
 B45-UHF TV, B11-VHF Radio. B11A-2 metre radio. For next to the set fitting.
 Price £5. S.A.E. for leaflets.

ELECTRONIC MAILORDER LTD,
 62 Bridge Street,
 Ramsbotton, Bury, Lancs, BLO 9AG.

TAPE EXCHANGES

RECORDER owners (cassette/reel) can now speak to the world! All ages... every interest. Send stamp: WORLDWIDE TAPETALK, 35 The Gardens, Harrow.

LADDERS

LADDERS. Varnished 25 1/2" ext. £40.34. Carr. £3. Leaflet. Callers Welcome. Ladder Centre (PEE5) Halesfield (1). Telford 596644.

FOR SALE

MK 14 Working, improved keyboard and revised monitor, extra PROM'S & Programmer kit, extra KEMITRON programming manual £60.00. Baguley, St. Leonards House, Ashtree Close, Worlingham, Nr. Beccles, Suffolk.

ITT 9099X Dual JK Flip Flops Brand New IO for £1. 50 for £4.50. Add 20p Post. Simpson, 2 Neville Street, Norwich, Norfolk.

NEW BACK ISSUES OF "PRACTICAL ELECTRONICS" available 70p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

QUARTZ Quality Battery Clock Movement to make your own clock, with straight or serpentine hands, £5.75 + 30p P&P. Mosswood Supplies, 6 St. Helens Crescent, Benson, Oxford.

CHART RECORDER "Matushita" Twelve Range - Six Speed £135 ono. 10 Weston Court, Eaton Socon, Cambs. 0480-215 824.

RECORD ACCESSORIES

STYL! Cartridges for MUSIC CENTRES, &c. FREE List No.29 for S.A.E. includes Leads, Mikes, Phones &c. FELSTEAD ELECTRONICS, (PE), Longley Lane, Gatley, Cheshire, Ches. SK8 4EE.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

WANTED

WANTED - C. R. Tube - For D43 Tequipment Scope. Type GEC - 1074H. Phone weekends. 0254 885672.

BOOKS AND PUBLICATIONS

COMPLETE REPAIR information any requested T.V. £5 (With diagrams £5.50). Any requested service sheet for £1. plus SAE. SAE brings newsletter + special offers - service sheets from 50p, bargain vouchers, unique publications.

AUS (PE) 76 Church Street, Larkhall, Lanarkshire

ROMANIAN ELECTROGRAPHY, tobioscopes, electrokinesis, biogravity, hallucinophotography, dermooptics, psychotronic generators, Kirlianography. SAE 4" x 9". PARALAB, Downton, Wilts.

TTL DESIGN CONSIDERATIONS

A booklet packed with information on TTL circuit building. Debouncing, decoupling, fan out, floating, buffers, open collector gates, regulators, race hazards, clocking, sinking, ground planes, cascading, simple interfacing, and much more. If you use TTL this has got to be helpful - well illustrated. 75p inclusive of P&P, etc.

PAWBROOKS

117 Blenheim Road, Deal, Kent.

**P.C. BOARDS
FOR INDUSTRY 'and' THE AMATEUR**

- One off or production runs
- Assembly of P.C.Bs or kits
- Expert hand soldering
- Design service if required
- Artwork & Photography

SEAHOSE ELECTRONICS LTD.
Unit 2 Picow Farm Road
Service Industry Estate,
Runcorn, Cheshire.
(09285) 75950

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P & P.
Dataplus Developments, 81 Cholmeley Road, Reading,
Berks.

**HIGH QUALITY
PCB's**

From your own artwork master negative or positive
maximum 12" x 12"
Manufactured in glass fibre tinned and drilled
Express service for prototypes and small production runs
Small contract circuit boards assembled
Gold plating for reliability where edge connectors
are used
**ANODISED SELF ADHESIVE FASCIA PANELS
WITH LEGENDS**
Manufactured from your own artwork master
Various colours available brushed and satin finish
Express service and competitive prices
Send artwork or phone for prices
.125W 5% C.F. Resistors £12 Series 1p each
IN4148 Diodes 2p each
Ecoscope Instruments Ltd.,
Clyde Workshops, Fullarton Road, Glasgow G32
01-641 7863

P.C.B's from P.E. DESIGNS


in high quality glass fibre flux varnished & drilled
Dec. 78 Guitar Multiproc. Set £9.35; Jan. 79 O & X Set £6.22
Feb. 79 Pulse Gen £1.35; Mar. 79 H/L Warning £1.38
Apr. 79 Phaser £1.36; Sequencer PSU £1.12; Bleeper 75p
May 79 Autorange Multimeter set £5.85; Sound switch 90p
Jul. 79 Micro Eval I/O unit 74p
Aug. 79 Chimesonic Main board £1.85; Melody Module 65p
For latest prices ring (0254) 73755.
Quotations for p.c.b's from customers' artworks send S.A.E. to
P.M., W.K., & I. Yates, 22, Ambleside Drive,
Darwen Lancs. BB338G
Terms CWO 25p P&P on orders less than £10

**GUITAR/PA/
MUSIC AMPLIFIERS**

100 watt superb treble/bass overdrive. 12 months guarantee.
Unbeatable at £44; 60 watt £37; 200 watt £59; 100 watt
twin channel sep. treble/bass per channel £58; 60 watt £48;
200 watt £72; 100 watt four channel sep. treble/bass per
channel £75; 200 watt £92; slaves: 100 watt £32; 200 watt
£50; fuzz boxes, great sound £9.50; bass fuzz £9.50; over-
drive fuzz with treble and bass boosters £15.50; 100 watt
combo superb sound overdrive, sturdy construction, castors,
unbeatable £90; twin channel £100; bass combo £100;
speakers 15in. 100 watt £35; 12in. 100 watt £23; 60 watt
£15.00; microphones Shure Unidyne B £26.
Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield, Cheshire.
Tel: 061-344 5007 or 061-308 2064

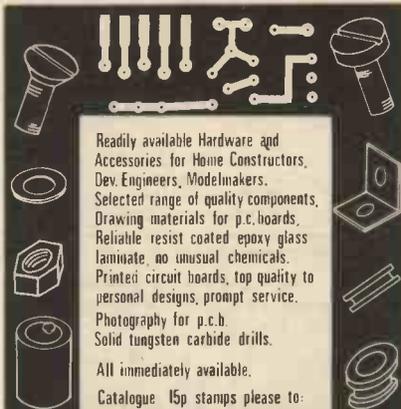SOLAR CELLS, Batteries, Panels, Thermoelectric Generators,
heat pipes, books etc., Details; Edcombe Ltd., 34
Nathans Road, N. Wembley, Middx. HA0 3RX.



Readily available Hardware and
Accessories for Home Constructors,
Dev. Engineers, Modelmakers.
Selected range of quality components.
Drawing materials for p.c. boards.
Reliable resist coated epoxy glass
laminates, no unusual chemicals.
Printed circuit boards, top quality to
personal designs, prompt service.
Photography for p.c.b.
Solid tungsten carbide drills.
All immediately available.
Catalogue 15p stamps please to:

**RAMAR CONSTRUCTOR
SERVICES,**
Masons Rd. Stratford on Avon
Warwks. CV37, 9NF 0789-4879

CABINET FITTINGS

FOR
Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Strap & Recess Handles, Feet, Castors,
Jocks & Sockets, Cannons, Bulgin 8 ways, Reverb Troys,
Locks & Hinges, Corners, Trim, Speaker Bolts etc.
Send 2 x 9p Stamps for samples and illustrated catalogue
ADAM HALL (P.E. SUPPLIES)
Unit 3, Carlton Court, Gralinger Road
Southend-on-Sea, Essex.

CLEARING LABORATORY. Scopes, recorders, testmeters,
bridges, audio, R.F. generators, turntables, tapeheads,
stabilised P.S.U.s, sweep generators, test equipment, etc.
Lower Beeding 236.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Trans-
mitter-Receiver Kit. Only £10.25 plus 25p P. & P.
'Brain-Freeze' 'em with a MINI-STROBE Elec-
tronics Kit, pocket-sized 'lightning flashes', vari-
speed. for discos and parties. A mere £4.50 plus 25p
P. & P. Experiment with a psychedelic DREAM
LAB, or pick up faint speech/sounds with the BIG
EAR sound-catcher; ready-made multi-function
modules. £5 each plus 25p P. & P.
LOTS MORE! Send 25p for lists. Prices include
VAT.

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

**RECHARGEABLE
BATTERIES**

TRADE ENQUIRIES WELCOME
FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for
Booklet "Nickel Cadmium Power" plus Catalogue. Write or
call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE,
SUTTON COLDFIELD, WEST MIDLANDS. 021-354 9764,
or see them at TLC, 32 Craven Street, Charing Cross,
London WC2.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

Send to: Classified Advertisement Manager
PRACTICAL ELECTRONICS
GMG, Classified Advertisements Dept., Room 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846
Rate:
20p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

"Stop Press UK 101 Compatible!"

COLOUR YOUR NASCOM!



DAZZLING COLOUR GRAPHICS FOR NASCOM 1

Genuine bit-addressable "pixel" system for straight-forward programming of pictorial or mathematical functions.

8 Colour display plus 8 colour independent background facility. Full documentation with FREE SOFTWARE: powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems — send us diagrams etc of your b & w video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.

NOW AVAILABLE FOR LIMITED PERIOD AT **£45** Inclusive of VAT and postage.

**WILLIAM
STUART
SYSTEMS Ltd**

Dower House, Billericay Road,
Herongate, Brentwood,
Essex CM13 3SD.
Telephone: Brentwood (0277) 810244

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gardens.

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2oz
10 to 19	2.83	1.55	.80	.64
20 to 29	3.03	1.76	1.00	.75
30 to 34	3.25	1.86	1.07	.80
35 to 40	3.60	2.08	1.22	.89
41 to 43	4.84	2.71	2.07	1.38
44 to 46	5.37	3.25	2.29	1.80
47	8.37	5.32	3.19	1.91
48 to 49	15.96	9.58	6.38	3.51

SILVER PLATED COPPER WIRE

14, 16, 18	4.30	2.39	1.53	1.00
20 & 22	5.32	3.03	1.85	1.13
24 & 26	6.06	3.57	2.13	1.30
28 & 30	7.00	4.10	2.50	1.53

Fluxcore 60/40 Solder 22 swg 65 ft 90p
18 swg 22 ft 80p

Tinned Copper Wire 6 mm 23 swg 1 lb £4.00 10 lbs £20

Wire Wrapping Wire 30 swg 82 ft £1.10

Wire Wrapping Tool & 4 Reels £6.00

CABLES

			Per Meter
2 WAY	13/2 mm	2.5 amp	13p
2 WAY	16/2 mm	2.5 amp	15p
3 WAY	24/2 mm	6 amp	24p
3 WAY	32/2 mm	10 amp	32p
3 WAY	14/2 mm	2.5 amp	16p
4 WAY	14/1 mm	.75 amp	30p
4 WAY	7/2 mm	1.4 amp	30p
6 WAY	14/2 mm	2.5 amp	45p
10 WAY	7/2 mm	1.4 amp	60p
1 CORE	7/2 mm	Screened	12p
2 CORE	7/2 mm	Each Screened	16p
2 CORE	7/2 mm	Screened	14p
4 CORE	7/2 mm	Screened	30p
LO LOSS	Co-Axial		25p

Prices include P & P and VAT. Dealer enquiries welcome.
Orders under £2 please add 20p.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers — Starter pack (5 sheets, lines, pads, i.c. pads) £1.55. Large range of single sheets in stock at 32p per sheet.
Ferric Chloride — 1 lb bags 80p (P&P 50p)*
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.30.
S.A.E. lists and information. P&P 25p/order except*

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation. Each cassette are type C90.
Morse by light system available. Morse Key and Buzzer unit for sending practice.
Prices each cassette (including booklets) £4.75. Morse Key and Buzzer £6.50.
Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. PE)
12 Longshore Way, Milton,
Portsmouth PO4 8LS.



**£26.75
INC. FLAME
TIPS**

Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size, adjustable to 5,000°F. Cuts metals, welds, brazes and solders gold, silver. Ideal modelling, electricians, opticians, dentists, silversmiths, jewellery, clockmakers, electronic and computer servicing. Up to 30 minutes use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder £2.45 + 30p p&p extra. Only £26.75 + £1.45 p&p. Access accepted.

JOHN DUDLEY & CO. LTD. (Dept. PE19)
Carolyn House, Water Road, Wembley, Middx.
(Mail Order)
Tel. 01-435 5456, before noon

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade.
BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancashire, LA 6LT.

RYDER ORGAN SYSTEM

(Wireless World)


A classical design with full-size keyboards. Couplers, capture, etc., can be included.

Cassette. p.c. boards, data, from:

HIKON LTD. (P),
Woodsale Croft, Ladybridge Lane,
Bolton BL1 5ED.

BUILD A SYNTHESISER!

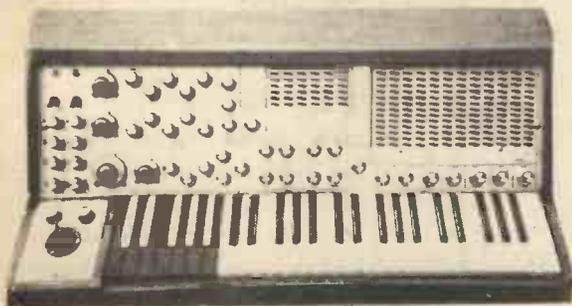**NO SPECIAL SKILLS
SPECIAL EQUIPMENT REQUIRED**



Using **Dewtron (Reg'd)**
PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR


FOR YOUR GUIDANCE VALUE ADDED TAX

In view of changes affecting V.A.T. at the time of going to press, readers should ensure that they have added the correct amount of V.A.T. before ordering.

Export orders are not subject to the addition of Value Added Tax.

Clef Kits —

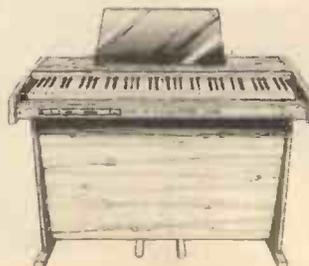Designer approved quality kits for Electronic Musical Instrument Construction.



JOANNA 72 & 88 PIANOS
Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. A new physical layout has been adopted to simplify construction.

P.E. STRING ENSEMBLE
The only kit available to the proven A. J. Boothman Design for this versatile String Machine. Specialists in all sizes of Square Front Keyboards. Send S.A.E. to:

Clef Products (Dept P.E.) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU

INTERLOCKING PLASTIC STORAGE DRAWERS




Neatest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

As supplied to Post Office, Industry and Government Departments.
SINGLE UNITS (1D) (5in x 2½in x 2½in) £3.50 DOZEN.
DOUBLE UNITS (2D) (5in x 4½in x 2½in) £5.50 DOZEN.
TREBLE (3D) £5.50 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £7.90 for 8.
EXTRA LARGE SIZE (6D1) £6.90 for 8.

PLUS QUANTITY DISCOUNTS

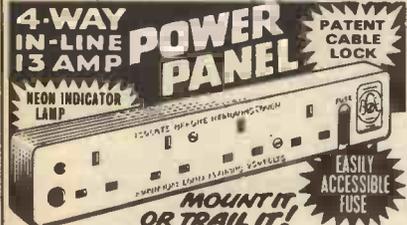Orders over £20, less 5%. Orders over £60, less 7½%. PACKING/POSTAGE/CARRIAGE: Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage. QUOTATIONS FOR LARGER QUANTITIES. Please add 15% V.A.T. to total remittance. All prices correct at time of going to press.



Modern, slim-line power panel, countless uses in home, office, factory, showrooms. Perfectly safe, unbeatable. Can be mounted on wall or trailed anywhere in room. Neat rubber base. Smart PVC outer cover. **Black £3.90, White £3.70, P & P 60p.**

FLAIRLINE SUPPLIES (P.E.10)
 124 Cricklewood Broadway, London N.W.2
 Telephone 01-450 4844

- MICROPROCESSORS AND MICROCOMPUTERS**
 Their Use and Programming
 by E. Huggins Price: **£5.60**
- IC CONVERTER COOKBOOK**
 by W. G. Jung Price: **£8.90**
- A SIMPLE GUIDE TO HOME COMPUTERS**
 by S. Ditlea Price: **£4.00**
- OPERATIONAL AMPLIFIERS 2nd ed.**
 by G. B. Clayton Price: **£10.00**
- RADIO & ELECTRONICS FOR TECHNICIAN ENGINEERS**
 by D. A. Jacobs Price: **£4.50**
- MICROCOMPUTER-BASED DESIGN**
 by J. B. Peatman Price: **£5.50**
- UNDERSTANDING DIGITAL ELECTRONICS**
 by G. McWhorter Price: **£3.90**
- MICROPROCESSOR INTERFACING TECHNIQUES**
 by A. Lesea Price: **£8.00**
- MICROPROCESSORS FROM CHIPS TO SYSTEMS**
 by R. Zaks Price: **£8.00**
- PROGRAMMING THE 6502**
 by R. Zaks Price: **£9.00**

ALL PRICES INCLUDE POSTAGE

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

INDEX TO ADVERTISERS

Acorn Computers	75	Kay & Co.	6
Adam Hall (P.E. Supplies)	93	L & B Electronics	11
Aitken Bros	78	Maclin-Zand	86
Astra Pak	76	Maplin Electronics	Cover IV
Aura Sounds	90	Marshall A. (London) Ltd.	87
A.U.S.	92	Metac	71, 79
Barrie Electronics	84	Mhel Electronics	94
Bi-Pak	4, 5	Microdigital	78
Bi-Pre-Pak	12	Mill Hill Supplies	90
Birkett J.	76	Modern Book Co.	95
Boffin Projects	93	Monolith	12
Boss Industrial	89	Newtronics	12
Breadboard	49	Noble Electronics	12
Brewster S.R.	3	P.H.W.K. & I. Yates	93
British National Radio & Electronics School	7, 83, 88	P.K.G. Electronics	94
Calscope	8	Pawbrooks	92
Cambridge Learning	77	Phonosonics	10, 11
Chromasonic	86	Progressive Radio	90
Chromatronics	80	Proto Design	94
Clef Products	94	Radio Component Specialists	88
Codespeed	86	Ramar Constructor Service	93
Commodore Business Machines	55	R.S.T. Valve Mail Order	90
Computer Components (Teleplay)	Cover II	Radio & T.V. Components	81
Continental Specialties Corporation U.K. Ltd	31	Romane Electronics	64
Crescent Radio	80	Sandwell Plant Ltd.	93
Crimson Elektrik	31	Saxon Entertainments	9
Crofton Electronics	8	Science of Cambridge	41
C.R. Supply Co.	92	Scientific Wire Co.	94
Delta Tech	80	Seahorse Electronics Ltd.	93
Digisound	6	Sentinel Supply	78
Dudley & Co. Ltd., John	94	Service Trading	Cover III
Ecoscope Instruments Ltd.	93	Sparks Developments	84
E.D.A.	82	Squires, Roger	3
Electronic Mail Order Ltd.	92	Stevens Electronic Components	85
Electrovalue	78	Sumico Ltd.	8
Fladar	82	Swanley Electronics	84
Flairline Supplies	95	Tandy	15
Fringewood Electronics	11	T.K. Electronics	14
Heathkit	64	Technomatic	96
Hiykon Ltd.	94	Tempus	95
Home Radio	14	Transam Components	13
H.S.B.C.	8	T.U.A.C.	63
I.C.S. Intertext	14, 92	Watford Electronics	2, 3, 16
I.L.P. Electronics	91	William Stuart Systems Ltd	94
Jayen Developments	6	Williamson Amplification	93
J.W.B. Radio	92	Wilmslow Audio	82

BUYING TIME?

Make sure it's CASIO

New Lithium batteries outlast most solar watches. From Casio's New Collection comes one of the most sophisticated executive watches available today,

THE 81CS-36B ALARM CHRONOGRAPH

LC Display of hours, minutes, seconds, day; And with day, date, month and year perpetual automatic calendar.

4-5 YEAR BATTERY

1/100 second chronograph to 7 hours. Net, lap and first & 2nd place times. User optional 12 or 24 hour display. 24 hour alarm. User optional hourly chime. Backlight. Mineral glass. Stainless steel case. Water resistant to 100 ft (3 at.)



£35.95

CASIO F-8C 3 YEAR BATTERY

8 digit display of hours, minutes, seconds and date, with day & am/pm. Auto calendar. Backlight. Resin case and matching strap. Mineral glass. Water resistant to 66 ft (2 at.) RRP £12.95 Real quality and value for money



£10.95

CASIO F-200

Sports chrono
 Hours, minutes, seconds, am/pm; and with day, date and month auto calendar. 1/100 sec chrono to 1 hour. Net, lap and 1st & 2nd place times. Resin case and matching strap. Mineral glass. Water resistant to 66 ft (2 at.) Silver oxide battery. RRP £17.95



£15.95

NEW LOWER PRICES

- Casio 95QS-31B chronograph **£23.95**
- Casio 95CS-31B chronograph **£29.95**
- MELODY 80** Now only **£23.95**

ISN'T IT WORTH PAYING A LITTLE MORE FOR QUALITY AND RELIABILITY?

Fully guaranteed for 12 months.

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of quality watches and calculators.

Price includes VAT and P & P. Send your Company order, cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:—

TEMPUS

Dept. PE, Beaumont Centre, 164-167 East Rd., Cambridge CB1 1DB Tel: 0223 312866

TTL by TEXAS 7400 11p 7401 12p 7402 12p 7403 12p 7404 12p 7405 12p 7406 32p 7407 32p 7408 19p 7409 19p 7410 15p 7411 24p 7412 20p 7413 30p 7414 60p 7415 90p 7416 27p 7417 27p 7418 27p 7419 27p 7420 17p 7421 17p 7422 22p 7423 34p 7424 34p 7425 30p 7426 40p 7427 34p 7428 36p 7429 36p 7430 17p 7431 50p 7432 30p 7433 40p 7434 35p 7435 35p 7436 17p 7437 40p 7438 60p 7439 112p 7440 112p 7441 93p 7442 93p 7443 60p 7444 80p 7445 80p 7446 93p 7447 60p 7448 80p 7449 17p 7450 17p 7451 17p 7452 17p 7453 17p 7454 17p 7455 17p 7456 17p 7457 36p 7458 36p 7459 36p 7599 36p 7600 36p	93 SERIES 9301 160p 9302 175p 9308 316p 9310 275p 9311 275p 9312 275p 9399 275p 9400 275p	VEROBOARD 0.1 0.15 (copper clad) 2 x 3 49p 33p 3 x 5 49p 45p 3 x 3 49p 45p 3 x 5 56p 60p 3 x 5 17 180p 150p 3 x 17 225p 190p 4 x 17 340p - Plat of 35 pins 30p Spot face cutter 85p Pin insertion 99p VERO WIRING PEN Plus spool 325p Spool spool 100p Wire 80p Combes 7p each NE561B 425p NE565 130p NE566 130p NE567 175p NE567 175p NE571 425p RC4151 400p SAD1024A 1250p SFF9364 1150p SN76023N 175p SN76013N 175p SN76013ND 120p SN76023N 140p ICL7106 850p ICL8038 340p SN76477 250p SP8515 75p TAA121 275p TBA614B11 225p LM311 120p LM318 120p TBA800 90p LM319 200p LM324 75p LM339 75p LM347 95p TCA4500A 250p TD1A004A 300p TD1A008 320p TD1A010 225p TD1A022 60p TD1A024 120p TD1A034B 250p TD1A170 250p TD2A020V 325p TD2A020 320p TL071 60p TL072 60p TL074 150p TL082 90p TL084 130p TL170 50p UDN6118 320p UDN6184 320p ULN2003 100p KR2206 350p 5101 110p 6810 350p KR2216 675p KR2240 400p ZNA14 700p LM319 90p ZN424E 135p ZN425E 400p IN1034E 200p 95H90 800p	TRANSISTORS *BF881 25p *AC127/28 25p *AC176/28 25p *AC187/28 25p *AF16/7 30p *AD149 70p *AD161/2 45p *AU107 250p *BC107/8 11p *BC109 11p *BC117 12p *BC149 10p *BC157/8 10p *BC159 12p *BC166 12p *BC177/8 17p *BC179 17p *BC182/3 11p *BC184 11p *BC185 11p *BC192 12p *BC193 12p *BC197 12p *BC198 12p *BC199 12p *BC814 12p *BC815 12p
---	--	--	---

SERVICE TRADING CO

RELAYS SIEMENS, PLESSEY, etc.

RELAYS WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock phone or write in your enquiries

FT3 NEON FLASH TUBE

High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50, P. & P. 25p (£2.01 inc. VAT) 3 for £3, P. & P. 50p (£4.03 inc. VAT & P.).

RODENE INSULATOR TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding mixing, etc. Price £6, P. & P. 60p (£7.59 inc. VAT & P.).

WHY PAY MORE?

MULTI RANGE METER TYPE MF15A a.c. d.c. volts 10 - 50, 250, 500, 1000. Ma 0-5, 0, 10, 0-100. Sensitivity 2000V 24 range, diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.63 inc. VAT & P.).

METERS (New) - 90 mm DIAMETER

A.C. Amp. Type 62T2, 0.1A, 0.5A, 0-20A, A.C. Volt, 0-100V, 0-300V, 0-500V, 0-1000V, D.C. Amp., Type 65C5, 0-2A, 0-10A, 0-20A, 0-50A, 0-100A

D.C. Volt, 0-15V, 0-30V, All types £3.50 ea. P. & P. 50p (£4.60 inc. VAT), except 0-50A, 0-100A, D.C., price £5.00 + 50p P. & P. (£6.33 inc. VAT).

HEAVY DUTY SOLENOID

Magnetic Devices, 240V, A.C. Intermittent operation. Approx. 20 lb. pull at 1.25 in. Ex-equip. Tested. Price: £4.75 + 75p P. & P. (£6.33 inc. VAT & P.).

A.C. SOLENOID p/e other type 176/2

240 A.C. Approx 1lb at 1/2 inch, intermittent rating. Price £1 p&p 20p (£1.38 inc VAT + P.).

WESTOIL TYPE MMB Model 2, 240V A.C. Approx 1 1/2 lb pull at 1/2 inch. Rating 1. Price £1.50 p&p 20p (£1.96 inc. VAT + P.).

18-24V, D.C. 70 ohm Coil Solenoid. Push or Pull. Adjustable travel to 3/16 in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25mm. Price: £3.40 + 30p P. & P. (min. 3 off). (£3.11 inc. VAT & P.).

MINIATURE UNISELECTOR

12 volt, 11-watt, 4 bank (3 non-bridging 1 homing) £3.00.

P. & P. 35p (£3.85 inc. VAT & P.). N.M.S.

240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet/outlet. Precision made. British mfg. Price: £3.50 Post 50p (£4.60 inc. VAT & P.).

MICRO SWITCHES

Sutl. min. Honeywell roller m/s type 3115m 9061. 10 for £2.50 post paid. (£2.88 inc. VAT).

LEVER OPERATED 20 amp C/O Mfg. by Unimax USA 10 for £4, P. & P. 50p (min. order 10) (£5.18 inc. VAT).

D.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total inc. VAT £2.93 (min 10).

MERCURY SWITCH

Size 27mm x 5mm, 10 for £5.00 (inc. VAT £6.12) min quantity 10. 30p P. & P.

Heavy duty type, size 38 x 16 x 10mm, minimum quantity 10. £7.50 post paid (£8.63 inc. VAT & P.).

2-CAM PROGRAMMER

Crouzet 1 rpm, 115V, A.C. Motor operating 2 Roller Micro switches (4 mm). Can be used on 240V, A.C. with either 0.25 mfd 250V, Condenser or 5-6K wirewound Resistor 7 watt. (not supplied). Price: £2.50 + 50p P. & P. (£3.45 inc. VAT & P.).

A.E.G. CONTACTOR

Type L56/L11. Coil 240V 50 Hz. Contacts - 3 make: 600V; 20amp, 1 break: 600V; 20 amp. Price: £5.50 + 50p P. & P. (£6.90 inc. VAT & P.).

TORIN BLOWER

16" 022 220 240V A.C. Aperture 10 x 4 1/2cm overall size 16 x 14cm. Price: £3.75 P. & P. 75p (inc. VAT £5.18).

Other types available. S.A.E. for details

24 volt, D.C. BLOWER UNIT

Precision 24 volt, D.C. 0-8 amp Blower that works well on 12V 0-4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P. & P. 75p (inc. VAT £6.04). N.M.S.

INSULATION TESTERS NEW!

Test to IEE Spec Rugged metal construction suitable for bench or field work constant speed clutch Size L Bin W 4in H 6in weight 6lb, 500V, 500 megohms, £49. Post 80p (£57.27 inc. VAT & P.). 1,000V, 1,000MΩ, £55, Post 80p (£64.17 inc. VAT & P.). S.A.E. for leaflet.

Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors. 10 for £1.50 p&p 50p. (£2.30 inc. VAT + p&p) (Min 10) N.M.S.

230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2 in. or 4 blade 3 in. aluminium fan. Price £3.00, P. & P. 65p. (£4.20 inc. VAT & P.).

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp inc. a.c. voltmeter £14.50
0.5 KVA (2 1/2 amp MAX) £17.00
1 KVA (5 amp MAX) £22.50
2 KVA (10 amp MAX) £37.00
3 KVA (15 amp MAX) £45.50
5 KVA (25 amp MAX) £74.00
10 KVA (50 amp MAX) £168.00
15 KVA (75 amp MAX) £260.00



CARRIAGE PACKING & VAT EXTRA

LT TRANSFORMERS

0-10-15V at 3 amp (lex new equip) £2.50 P. & P. 50p (£3.45 inc. VAT)
13-0 13V at 1 amp £2.50 P. & P. 50p (£3.45 inc. VAT)
25-0-25V at 2 1/2 amp £4.50 P. & P. 75p (£6.04 inc. VAT & P.)
0.4V/6V/24V/32V at 12 amp £18.50 P. & P. £1.90 (£23.48 inc. VAT & P.)
0.6V/12V at 20 amp £14.70 P. & P. £1.50 (£18.63 inc. VAT)
0-12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£15.53 inc. VAT & P.)
0-6V/12V at 10 amp £8.25 P. & P. £1.25 (£10.93 inc. VAT)
0-6V/12V/17V/18V/20V at 20 amp £19.00 P. & P. £1.50 (£23.58 inc. VAT & P.)
0-10V/17V/18V at 10 amp £10.50 P. & P. £1.50 (£13.80 inc. VAT)
Other types in stock, phone for enquiries or send see for leaflet.

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit: 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many Iso (called 4 Joule) strobes. Price £19.00. Post £1 (£23.00 inc. VAT & P.). Specially designed case and reflector for Hy-Light £8.80. Post £1 (£11.27 inc. VAT & P.).

XENON FLASHGUN TUBES

Range available from stock S A E for details



ULTRA VIOLET BLACK LIGHT

FLUORESCENT TUBES

4ft. 40 watt £10.00 (callers only) 2ft. 20 watt £8.20. Post 75p. (£7.99 inc. VAT + P.) (For use in stan bin-pin fittings) Mir 12 in. 8 watt £2.80. Post 35p. (£3.62 inc. VAT + P.). 9 in. 6 watt £2.25. Post 35p. (£2.99 inc. VAT + P.). 6 in. 4 watt £2.25. Post 35p. (£2.99 inc. VAT + P.).

Complete ballast unit, for either 6", 9" or 12" tube 230V AC op. £3.50. Post 45p. (£4.54 inc. VAT + P.). Also available for 12V DC op. £3.50. Post 45p. (£4.54 inc. VAT + P.).

400 watt UV lamp and ballast complete £31.50. Post £3. (£39.68 inc. VAT + P.). 400 watt UV lamp only £11.25. Post £1.20 (£14.32 inc. VAT + P.).

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. S.A.E. (foolscap) for further details. Price £60.00 p&p 70p (£69.81 inc. VAT + P.).



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details.

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/500/1kΩ/1.5kΩ, £2.40. Post 20p (£2.99 inc. VAT & P.).

50 WATT 25/50/100/250/500/1kΩ/1.5kΩ, £3.62 inc. VAT & P.).

100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ, £5.90 p. & p. 35p (£7.19 inc. VAT).

Black, Silver, Skirted knob calibrated in Nos 1-9 1 1/2 in. dia. brass bush. Ideal for above Rheostats 24p each.



SPECIAL OFFER

BERCO type L. RHEOSTAT

85 ohm 300 watt 1-86 amp. £7.50 p. & p. 50p. (Total: £9.20 inc. VAT). N.M.S.

RELAYS

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.96 inc. VAT & P.).

T.E.C. open type 3 c/o. 10 amp £1.10 (£1.50 inc. VAT & P.).

Omron or Keyswitch 1 c/o. 7 amp £1.00 (+20p P&P. Inc. VAT £1.38).

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 inc. VAT & P.). Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.38 inc. VAT & P.). Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.67 inc. VAT & P.). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.78 inc. VAT & P.). 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.78 inc. VAT & P.). (lamps = contact rating). P&P on any Relay 20p.

Other types available - phone for details. N.M.S.

Very Special Offer: 9-12V D.C., 2 make contacts, new I.T.T., 3 for £1.75 +25p P&P. (inc. VAT £2.30).

Diamond H heavy duty A.C. relay 230/240V a.c. two C/O contacts 25 amps res at 250 a.c. £2.50 p&p 50p. (£3.45 inc. VAT + p&p). Special base 50p. (inc. VAT 58p) N.M.S.

GEARED MOTORS

4 1/2 rpm, 115V a.c. 50 cycle, mf. SIGMA Inst. Ltd. U.S.A. Price: £7.50 + 75p P. & P. (£9.49 inc. VAT), supplied with transformer. N.M.S.

7 1/2 rpm, 115V a.c. 50 cycle approx. 25lb. mf. KLAXON.

28 rpm, 115V a.c. 20lb. in. reversible.

Price of either 2 Motors £4.75 each + 75p P. & P. (£6.33 inc. VAT). N.M.S. Any of above 3, supplied with Transformer for 240V operation: £7.25 x £1.00 P. & P. (£9.49 inc. VAT).

19 rpm FHP 220/240V, a.c. reversible torque 14.5kg. Gear ratio 144:1. Brand new including capacitor, mf. CITENCO. Price: £14.25 + £1.25 P. & P. (£17.83 inc. VAT). N.M.S.

30 rpm 230/240V a.c. 50lb. in. mf. PARVALUX. Price: £15.00 + £1.50 P. & P. (£18.98 inc. VAT). N.M.S.

56 rpm 240V a.c. 50lb. in. 50Hz 0.7 amp. Shaft length 35mm. Dia. 16mm. Wt. 6kg. 600g mf. FRACMO. Price: £15.00 + £1.50 P. & P. (£18.98 inc. VAT). N.M.S.

100 rpm, 110V, a.c. 115lb. in. 50Hz 2.8 amp. single phase split capacitor. Immense power. Continuously rated. Totally enclosed. Fan-cooled. In-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm, length 145mm. Tested. Price: £12.00 + £1.50 P. & P. (£15.53 inc. VAT). R. & T. Suitable Transformer for 230/240V operation. Price £8.00 + 75p P. & P. (£10.06 inc. VAT).

200 rpm, 35 lbs. in. 115V, 50Hz. Price: £16.00 + £1.50 P. & P. (£20.13 inc. VAT). N.M.S. Suitable Transformer for 230/240V a.c. Price: £8.00 + £1.00 P. & P. (£10.35 inc. VAT). N.M.S.

500 rpm, 230/250V a.c. 3 1/2 in. 2 right-angled spindles. Mf. PARVALUX. Price: £11.00 + £1.00 P. & P. (£13.80 inc. VAT). N.M.S.

6/9V. D.C. Miniature Geared Motor, precision built, incredibly powerful for size - approx. speed 6V. - 60 rpm 40 ma. approx. speed 9V. - 80 rpm 50 ma.

Size: 27mm dia., 30mm length, 55gr. weight, drive spindle 5 x 3mm dia.

Price: £2.50 post paid (£2.88 inc. VAT). N.M.S.

12V, D.C. type SD2. Shunt 1/2 ph continuously rated 4000 rpm. Mf. PARVALUX. Price: £11.00 + £1.00 P. & P. (£13.35 inc. VAT). N.M.S.

1rpm 230/240V, a.c. Synchronous geared Motor, mf. HAYDON. 2 rpm 230/240V, a.c. Synchronous geared Motor, mf. CROUZET. Either type £2.90 + 30p P. & P. (£3.68 inc. VAT). N.M.S.

1.400 rpm 115V, a.c. Motor, HP continuously rated. Fitted with anti-vibration cradle mounting. Mf. FRACMO. Supplied complete with Transformer for 230/240V, a.c. operation. Price: £10.00 + £1.00 P. & P. (£12.65 inc. VAT). N.M.S.

1.600 rpm, 230V, a.c. reversible Motor, 0-25 a, complete with anti-vibration mounting bracket and capacitor. O/A size: 110 x 90mm. Spindle 1/2 dia. reverse. Mf. GENERAL ELECTRIC, R. & T. Price: £3.00 + 50p P. & P. (£4.03 inclusive).

REDUCTION DRIVE GEAR BOX.

Ratio 72:1. Input spindle 1/2 x 3/8 In. Output spindle 3/8 x 3 in. long. Overall size approx: 120 x 98 x 68 mm. All metal construction. Ex-equip. tested. Price: £2.00 + 50p. (inc. VAT £2.88).

ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon Vane oil-less, 100/115V, A.C. 1/12 h.p. motor 50/60 cycle 2875/3450 rpm, 20" vacuum

1-25 cfm, 10 p.s.i. (approx. figures) mft. by Gast Co. Fraction of maker's price. £14.00 p. & p. £1.00 (Total: £17.25 inc. VAT). Suitable Transformer. £3.50 p. & p. 50p. (Total: £4.60 inc. VAT) N.M.S.

BLOWER VACUUM PUMP

English Electric 3 phase a.c. motor 220/250V Or 380/440V, 1.425 r.p.m. 1/2 h.p. continuously rated. Direct coupled to William Allday & Co Alcosa carbon vane blower/vacuum pump 0.9 cfm 8.H.G. Price £22 p&p £2 (£27.60 inc. VAT + p) N.M.S.

Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £9.00. P. & P. 75p (£11.22). R. & T.

SANGAMO WESTON TIME SWITCH

Type S251 200/250V a.c. 2 on/2 off every 24 hours 20 amps contacts with override switch. dia. 4 x 3 price £8.00 P & P 50p inc. VAT £9.78. Also available with Solar. dia. R. & T.

MINIATURE 24-HOUR TIMESWITCH

(German mfr.). 240V, A.C. operation. Spring Reserve. 10 amp contacts, one-on-off every 24 hours. Calibrated in two hour steps. Minimum on-off period 6 hours. Day Omission. Unusual feature with these Switches is that trips may be removed at will enabling individual days to be programmed as required. Size only 3" x 4". Depth 2 1/2". Price: £8.50 + 50p. p. & p. (£8.05 inc. VAT & P.).

KEY: N.M.S. New Manufacturers Surplus R. & T. Reconditioned and Tested

SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01 995 1650

ACCOUNT CUSTOMERS MIN. ORDER £10.00

All Mail Orders Callers Ample Parking Space Showroom open Mon-Fri.

Personal callers only Open Saturdays 9 Little Newport Street, London WC2H 7JJ Phone 01-437 0576

MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £18.38 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

MAPLIN

ELECTRONIC SUPPLIES LTD

Post this coupon now for your copy of our 1979-80 catalogue price 70p. Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____

PE 1079



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.