

PRACTICAL

ELECTRONICS

DECEMBER 1979

55p

Seiko
**WATCH
OFFER!**



... Saves you £45 ... Full Details Inside

Ultrasonic
**BURGLAR
ALARM**



SPECIAL

Supplement...

SOLID STATE

CAR INSTRUMENTS

AS SEEN IN
P.E. AUGUST, SEPTEMBER
OCTOBER 1979

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER —
JUST CHECK THE SPEC'S.


SAMPLE TAPE
WITH EXTENDED
MACHINE CODE MONITOR
AND DISSASSEMBLER
INCLUDED FREE

COMPUKIT UK101

LOW COST SUPERBOARD IN KIT FORM

The CompuKit UK101 has everything a one board 'superboard' should have.

- ★ Uses ultra-powerful 6502 microprocessor.
- ★ 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- ★ 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs.
- ★ Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen.
- ★ Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF
- ★ Fully stabilised 5V power supply including transformer on board.
- ★ Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder.
- ★ 4K user RAM expandable to 8K on board £49 extra.
- ★ 40 line expansion Interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible).
- ★ 6502 machine code accessible through powerful 2K machine code monitor on board
- ★ High quality thru plated P.C.B. with all I.C.'s mounted on sockets.
- ★ Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software.

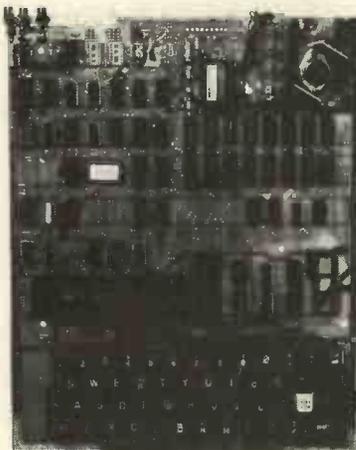

Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

KIT ONLY **£219** + VAT including RF Modulator & Power supply. Absolutely no extras.

Available ready assembled and tested, ready to go for **£269** + VAT

*8K Microsoft Basic means conversion to and from Pet, Apple and Sorcerer easy. Many compatible programs already in print. SPECIAL CHARACTERS

@ Erases line being typed, then provides carriage return, line feed.

CR Carriage Return — must be at the end of each line.

• Separates statements on a line. CONTROLIC Execution or printing of a list is interrupted at the end of a line.

"BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.

CONTROLIO No outputs occur until return made to command mode. If an input statement is encountered, either another CONTROLIO is typed, or an error occurs.

? Equivalent to PRINT

FUNCTIONS

ABS(X)	ATN(X)	COS(X)	EXP(X)
LOG(X)	PEEK(I)	POS(I)	RND(X)
SPC(I)	SQR(X)	TAB(I)	TAN(X)

FRE(X)	INT(X)
SGN(X)	SIN(X)
USR(I)	

STRING FUNCTIONS

ASC(X\$)	CHR\$(I)	FRE(X\$)	LEFT\$(X\$,I)
RIGHT\$(X\$,I)		STR\$(X)	
LEN(X\$)	MID\$(X\$,I,J)		
VAL(X\$)			

COMMANDS
CONT LIST NEW NULL RUN
STATEMENTS
CLEAR DATA DEF DIM END FOR
GOTO GOSUB IF.GOTO IF.THEN INPUT LET
NEXT ON.GOTO ON.GOSUB POKE PRINT REAC
REM RESTORE RETURN STOP
EXPRESSIONS
OPERATORS
+ * / % ^ NOT.AND.OR. >< <> >= <= RANGE 10⁻³² to 10⁺³²
VARIABLES
A,B,C...Z and two letter variables
The above can all be subscripted when used in an array
String variables use above names plus \$.e.g. A\$

COLOUR ADD-ON CARD AVAILABLE SOON

Enables you to choose your foreground the background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form.

THE ATARI VIDEO COMPUTER SYSTEM £138 + VAT



Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges!

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous.

You'll have thrill ater thrill, whether you're in the thick of a dogfight, screeching around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on color TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.


Cartridges now available All at £13.90 each + VAT

Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle Codebreaker*, Miniature Golf

Extra Paddle Controllers—£14.90 + VAT
*Keyboard Controllers—£16.90 + VAT

video 100

12" BLACK & WHITE
LOW COST VIDEO
MONITOR

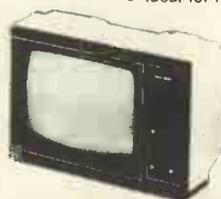

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

Only **£79** + VAT

SHORT C12 CASSETTES FOR COMPUTER PROGRAMMES 10 for £4.00



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CARD or AMERICAN EXPRESS number.

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G

Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday

★ NOW OPEN ALL DAY SUNDAY — For Shop Sales Only ★

Close to New Barnet BR Station — Moorgate Line.

COMP COMPUTER COMPONENTS

(Part of the Compshop Ltd. Group)



PRACTICAL ELECTRONICS

VOLUME 15 No. 12 DECEMBER 1979

CONSTRUCTIONAL PROJECTS

- EPROM PROGRAMMER—1** by *A. A. Berk B.Sc., Ph.D.*
Memory-mapped peripheral for the 2708 family 24
- ULTRASONIC BURGLAR ALARM** by *Gilbert Davies*
Versatile movement detection system 34
- DIAMATIC—2** by *J. R. W. Ames B.Sc. and W. L. Blyth B.Sc.*
Programmable Audio Visual Unit, construction and setting up 40
- COST-A-CALL CALCULATOR** by *A. P. Donleavy*
Keep a check on your phone bill 65

GENERAL FEATURES

- SEMICONDUCTOR UPDATE** by *R. W. Coles*
Z8000 7110 AY-3-1350 23
- MICROBUS** by *D.J.D.*
Seven programs/variations for Mk 14 68
- INGENUITY UNLIMITED**
Audio Millivoltmeter—Hex Keyboard For SC/MP—Tele-Games Mod—DC/DC Voltage Multiplier 72

NEWS AND COMMENT

- EDITORIAL** 17
- MARKET PLACE**
- New Products 18
- COUNTDOWN** 29
- POINTS ARISING**
- Digital Temperature Controller—6 Channel Mixer 29
- PATENTS REVIEW**
- Precipitation Sensor—Liquid Magnet 30
- SPACEWATCH** by *Frank W. Hyde*
- UKIRT—Shuttle Schedule 39
- INDUSTRY NOTEBOOK** by *Nexus*
- What's happening inside industry 47
- SEIKO WATCH OFFER** 61
- READOUT**
- A selection of readers' letters 62
- NEWS BRIEFS**
- Prestel testing the international market 70
- INDEX FOR VOLUME 15** 78

SPECIAL SUPPLEMENT

- SOLID STATE CAR INSTRUMENTS** by *Michael Tooley B.A. and David Whitfield B.A., M.Sc.* 48
- No. 3 Ammeter—No. 4 Temperature Gauge—No. 5 Dwell Meter—Hazard Warning and Cascading**

OUR JANUARY ISSUE WILL BE ON SALE FRIDAY, 14 DECEMBER 1979
(for details of contents see page 33)

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER. CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TELEPHONE ORDERS BY ACCESS NOW ACCEPTED (Minimum order £10.00). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 30p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: (Axial Lead Type)
400V: 1nF, 1.5n, 2n, 3n, 4n, 6n, 10n, 15n, 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 330n 13p; 470n 12p; 680n 18p; 1µ 22p 13p; 2.2µ 34p.
100V: 10nF, 15n, 22n 24p; 33n, 47n 41p; 68n 48p; 1µF 64p; 2.2µ 82p.
160V: 10nF, 12n, 33n, 100n, 150n, 220n 11p; 330n, 470n 19p; 680n, 1µF 22p; 2.2µF 32p; 4.7µF 36p.
1000V: 10n, 15n 20p; 22n 22p; 47n 26p; 100n 38p; 470n 53p; 1µF 175p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10n, 15n, 22n, 27n 5p; 33n, 47n, 68n, 100n 7p; 150n 9p; 220n, 330n 13p; 470n 12p; 680n 18p; 1µ 22p 13p; 2.2µ 34p.
ULTRASONIC TRANSDUCERS
40KHz 350p pr.

ELECTROLYTIC CAPACITORS: Axial lead type. Values are in µF.
500V: 10µ, 47µ, 68µ; 250V: 100µ, 65µ, 33µ, 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22, 33, 47, 50µ; 100V: 10µ, 22µ, 33µ, 50µ, 100, 220, 250µ; 47µ 32p; 1000 50p; 40V: 2.2, 3.3µF 8p; 100 12p, 220, 330, 500 8p; 4700 98p; 35V: 10, 33, 7p; 330, 470 32p; 1000 50p; 25V: 10, 22, 47, 68p; 80, 100, 180 8p; 220, 250 13p; 470, 640 25p; 1000 50p; 1500 30p; 2200 45p; 3300 52p; 4700 74p; 16V: 10, 47, 68, 7p; 100, 125 8p; 220, 330 14p; 470 16p; 1000, 1500 20p; 2200 34p; 10V: 10, 40, 6p; 640 12p; 1000 14p.

TAG-END TYPE: 450V: 100µF 180m; 70V: 4700 165p; 64V: 2500 98p; 3300 130p; 50V: 2200 99p; 3300 105p; 40V: 15,000 399p; 4700 120p; 4000 92p; 3300 93p; 2500 85p; 2200 85p; 2000 + 2000 120p; 30V: 4700 90p; 25V: 6400 105p; 4700 85p; 3300 80p; 2200 60p.

TANTALUM BEAD CAPACITORS
35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2µF, 3.3, 4.7, 6.8, 8.2V: 1.5, 10, 20V: 1.5µ, 16V: 10µF 13p each.
16V: 15µ, 22 25p; 47, 100, 220 40p.
100V: 15µ, 22, 33, 50µF; 100 35p; 6V: 47, 68, 100 30p; 33, 50µ 20p.

MYLAR FILM CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01, 0.01µF 6p
0.015, 0.02, 0.03, 0.04, 0.05, 0.05µF 7p
0.1µF, 0.2 10p. 50V: 0.47µF 12p

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF 4p
15nF, 22nF, 33nF, 47nF 5p 100nF 6p

POLYSTYRENE CAPACITORS:
10pF to 1nF, 6p. 1.5nF to 47nF 10p.

SILVER MICA (pF)
3-3, 4.7, 6.8, 8.2, 10, 12, 15, 22, 27, 33, 39, 47, 50, 68, 75, 82, 85, 100, 120, 150, 180, 200, 220 9p.
250, 270, 300, 330, 360, 390, 470, 500 & 820pF 10p each.
1000, 2000pF 20p

TRIMMERS miniature
2.5pF, 3-10pF;
3-30pF, 3-50pF 22p
2-25pF, 65pF 88pF 30p

COMPRESSION
3-40pF; 10-80pF 30p
25-200pF 35p
100-500pF 43p
1250pF 58p

RESISTORS - Erie meke 5% carbon
Resistor High Stability, Low Noise
RANGE Value 1-99 100+
0.25W 202-4-M7 E24 1-5p
0.5W 202-4-M7 E12 2-1p
1W 202-10M E12 5p 3p
2W Metal Film 100-1M 6p 4p
1% 0.5W 51D-1ME24 8p 6p
100 - price applies to Resistors of each type
not mixed values.

POTENTIOMETERS (AB or EGEN)
Carbon Track, 0-25W Log & 0-5W
Linear
500Ω, 1K & 2K (LIN ONLY) Single 27p
5KΩ-2MΩ single gang 27p
5KΩ-2MΩ single gang D/P switch 65p
5KΩ-2MΩ dual gang stereo 78p

SLIDER POTENTIOMETERS
0-25W log and linear values 60mm track
5KΩ 500KΩ Single gang 70p
10KΩ 500KΩ Dual gang 80p
Self-Strip graduated Alum. Bezels 25p

PRESET POTENTIOMETERS
0-15W 500-2M Mini. Vert. & Horiz. 7p
0-25W 1000-3MΩ Horiz. larger 10p
0-25W 2500-4.7MΩ Vert. 10p

TRANSISTORS

AC107	28	BC327	15	8FY51	P	TIP35C	P	2N1671B	215
AC125	20	BC328	15	8FY52	P	TIP36A	220	2N2219A	22
AC126	20	BC329	15	8FY56	45	TIP36C	256	2N2204A	26
AC127	20	BC331	15	8FY64	40	TIP41A	66	2N2221A	23
AC128	20	BC332	15	8FY71	20	TIP41B	66	2N2222A	23
AC141	24	BC337	25	8FY81	90	TIP42A	64	2N2369A	15
AC142	24	BC351E	48	85X20	18	TIP42B	82	2N2646	48
AC187	24	BC517	48	85X29	45	TIP142	195	2N2784	55
AC188	24	BC547	12	85Y95A	18	TIP147	199	2N2904	22
AC176	40	BC548	12	85Z26	78	TIP295E	65	2N2905A	22
ACY17	40	BC549C	12	85Z35	140	TIP305	75	2N3422	146
ACY18	40	BC557	15	BU205	190	TIS44	34	2N2907A	22
ACY19	40	BC558	20	BU208	225	TIS55	45	2N2826G	10
ACY20	40	BC559	20	MD8001	158	TIS45	45	2N3052	20
ACY21	35	BC570	18	MJ491	160	TIS88A	40	2N3054	55
ACY28	40	BC572	20	MJ255	105	TIS90	20	2N3055	48
ACY39	78	BD121	78	MJ340	54	TIS91	24	2N3056	48
AD149	70	BD121	78	MJE370	58	TIX07	12	2N3504	55
AD161	42	BD123	98	MJE371	60	ZTX108	12	2N3663	26
AD162	42	BD124	115	MJE2955	105	ZTX109	14	2N3702	11
AF114	50	BD131	45	MJE3055	70	ZTX122	28	2N3703	11
AF115	50	BD132	45	MPF102	68	ZTX300	13	2N3704	11
AF116	50	BD133	43	MPF103	36	ZTX301	25	2N3705	11
AF117	50	BD135	38	MPF104	36	ZTX302	20	2N3706	11
AF118	65	BD136	36	MPF105	36	ZTX303	25	2N3707	11
AF139	35	BD137	36	MPF106	40	ZTX304	24	2N3708	11
AF149	70	BD138	50	MPSA05	25	ZTX314	24	2N3709	11
8C107	10	BD139	40	MPSA06	25	ZTX320	30	2N3710	16
8C107B	12	BD140	30	MPSA12	40	ZTX311	40	2N3711	16
8C108	12	BD144	198	MPSA55	25	ZTX312	20	2N3822	130
8C108B	12	BD145	198	MPSA56	25	ZTX500	15	2N3771	233
8C108C	12	BD205	110	MPSU02	58	ZTX501	15	2N3772	195
8C109	12	BD378	65	MPSU05	50	ZTX502	19	2N3773	288
8C109B	12	BD517	65	MPSU06	58	ZTX503	15	2N3819	22
8C109C	12	BD517	65	MPSU07	65	ZTX504	25	2N3820	45
8C140	35	BD695A	65	MPSU55	55	ZTX511	25	2N3823	95
8C142	30	BD696A	65	MPSU56	60	ZTX520	25	2N3866	90
8C143	30	BDV56	156	OC23	170	40250	85	2N3903	20
8C144	30	BDV115	34	OC26	170	40251	97	2N3904	18
8C147B	10	BF172	20	OC28	150	40311	60	2N3905	18
8C148	8	BF177	24	OC30	150	40312	60	2N3906	18
8C148B	10	BF178	25	OC35	130	40315	55	2N4037	52
8C148C	10	BF179	30	OC41	48	40316	85	2N4058	17
8C149	8	BF180	35	OC42	48	40317	52	2N4061	17
8C150	11	BF194	12	OC43	55	40319	71	2N4062	17
8C151	11	BF195	12	OC44	55	40320	56	2N4063	17
8C152	27	BF196	12	OC45	28	40407	52	2N4922	55
8C157	10	BF197	14	OC70	28	40406	65	2N4829	65
8C158	11	BF198	18	OC71	28	40407	52	2N4922	55
8C159	11	BF199	18	OC72	45	40408	70	2N5135	42
8C160	42	BF200	32	OC73	55	40411	295	2N5136	42
8C167A	11	BF201	32	OC74	55	40412	295	2N5137	42
8C168C	12	BF244A	28	OC81	50	40467	95	2N5172	25
8C169C	14	BF244B	30	OC82	50	40494	90	2N5179	60
8C170	18	BF256	50	OC83	44	40595	98	2N5180	80
8C171	11	BF257	50	OC84	44	40603	65	2N5191	70
8C172	11	BF258	50	OC85	44	40604	65	2N5192	70
8C173	12	BF259	30	OC110	110	40594	90	2N5306	40
8C177	18	BF274	18	OC170	85	40595	98	2N5307	40
8C178	16	BF336	35	OC200	85	40636	125	2N5459	32
8C179	18	BF354	40	TIP29	43	40673	65	2N5485	35
8C181	21	BF359	38	TIP29A	44	40697	25	2N5642	750
8C182	9	BF360	38	TIP29B	44	40698	25	2N5777	45
8C183	9	BF369	25	TIP29C	66	40699	54	2N5778	40
8C184	9	BF370	25	TIP30	47	40706A	18	2N6109	50
8C182L	11	BF441	28	TIP30A	50	40708	19	3N128	112
8C183L	10	BF479	28	TIP30B	64	40714	32	3N140	112
8C184L	28	BF480	28	TIP30C	65	40716	27	40715	795
8C187	28	BF481	28	TIP30D	62	40718	40	40719	280
8C212	10	BF482	105	TIP31C	85	40719	22	40720	280
8C212L	11	BF483	105	TIP31D	58	2N1132	22	40721	280
8C213	12	BF484	26	TIP32C	75	2N1303	50	40722	280
8C213L	12	BF485	26	TIP33A	85	2N1304	50	40723	280
8C214	13	BF486	28	TIP33C	105	2N1305	28	40724	280
8C214L	13	BF487	28	TIP33D	115	2N1307	50	40725	280
8C307B	20	BF488	28	TIP34C	115	2N1308	46	40726	280
8C308B	20	BF500	20	TIP35A	185	2N1670	50	40727	280

ANTEX

Soldering Irons

C15W 360
CX17W 370
CCN15W 380
X25W 370

Spare bits 46
Iron stand 150

HEAT sink

T03 24
T0220 24
T05 12
T018 12
T092 9

Insulation Mica & Bushes 2

SPECIAL OFFER

741 17
555 20
2114 449
2708 675



CMOS (CONT.)

4093 78
4094 190
4095 105
4096 105
4097 372
4098 110
4099 145
4100 109
4101 109
4102 109
4200 109

LINEAR

LF356	90	NE567V	170
LM10	450	NE570	395
LM301A	30	NE5	

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the normal.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.

Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE EVERYTHING NEEDED

Die pressed case, Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE1279
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PD's for

X5KIT £16.95

ACCESS OR BARCLAY CARD No

£

Cheque No.

Send SAE if brochure only required

S. & R. BREWSTER LIMITED

WHY PAY MORE?

for Miniature Soldering Irons & Accessories		PRICE EACH	P & P EXTRA EACH
S.R.B. 18 watt Soldering Iron available in 12, 110 & 240 Volts, fitted with No. 20 bit		£4.43	+ 24p
SPARE BITS	No. 19 size 1.5mm or No. 20 size 3 mm or No. 21 size 4.5 mm or No. 22 size 6 mm	52p	—
	No. 78, I.C. Desoldering Bit	£1.04	+10p
	No. 1920L Long Life Bit	£1.12	10p
SAFETY STAND		£4.23	+ 70p
SOLDER	Savbit 20'	61p	+ 9p
	Savbit 10'	32p	+ 5p
	Lowmelt 10'	76p	+10p

INDUSTRIAL/RETAIL ENQUIRIES WELCOME FOR THE ABOVE

We also Offer & Recommend for Mail Order & Personal Callers Only

	PRICES EACH including V.A.T. and P & P
Oryx 50 Temperature Controlled Soldering Iron	£11.75
Spare tips for above	£1.39
Isotip quick charge rechargeable Soldering Iron	£24.60
Spare tips for above	£3.42
Cable 7/0.2 11 Colours 100 meter reel	£2.40
0.1 Veroboard 3/4" X 11 1/2"	£2.00
0.1 Veroboard 4/4" X 18"	£4.50
Copper Clad board single sided	75p
Watchmakers Side Cutters	£5.85
Watchmakers Pliers	£4.75
Transformer 100VA 2 X 12V 4.1A	£11.20

OTHER ITEMS ALSO AVAILABLE ASK FOR LIST S.A.E.

MAIL ORDER DEPT.
86-88 Union Street, Plymouth
PL13HG Tel:(0752) 65011



Please Quote your Number when ordering



MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4-5V-0-4-5V at 250 MA.
1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY 90p. 3 for £2.20.

1000 uf, 100V, Radial, 1 1/2" x 2". ONLY 70p. 3 for £1.50.

BD131's 4 for £1.00

<p>Don't Let Your Environment Dehydrate You! Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive. 1/2" shaft. 250V 3.75A Contacts ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 90p ea. 3 for £2.</p>	<p>SMOKE AND GAS DETECTOR Uses TGS 105 plug in sensor, housed in neat 3 1/2" die cast box, led indicator, 24V (12V by altering 3 component values). Will operate lamp or relay, with data and circuit. £8.95 Relays for above £1 ea. state voltage</p>
<p>CASSETTE MOTORS Self Regulating, will operate 8-12V. Ideal for modelers, mechanical switching etc. 2000 R.P.M. approx. 90p ea.</p>	<p>TRANSISTOR PACKS 100. Full spec. new and marked. Includes BC148, BC184L, ME0412, BF274, BC154 etc. etc. £4.95 200 as above and includes AC128, 2N3065, BFY50, BD131, BF200 etc. £9.95 Buy bulk and save money, these packs are worth at least double.</p>
<p>ULTRASONIC TRANSDUCERS Transmitter and receiver, 40 kHz 14 mm diam. £4.25 pair.</p>	<p>P/B SWITCH BANKS These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole c/o etc. Can be modified. Can't be repeated. 3 Banks for £1</p>
<p>6 x 6 POLE REED RELAYS ON BOARD 12V ideal for burglar alarms, model railways etc. £2.45</p>	<p>BULK BARGAINS. STOCK UP FOR SUMMER 300 mixed 1/2 & 1/4 watt resistors £1.50 150 mixed 1 & 2 watt resistors £1.50 300 mixed capacitors, modern, most types £3.30 100 mixed ceramic and plate caps £1.20 400 mixed 7 1/2m resistors £2.95 100 mixed polystyrene caps £2.20 25 pots and presets £1.50 25 presets, skeleton etc. £1.20 20 VDRs and thermistors £1.20 100 Hi-wattage resistors wirewound etc. £2.20 100 electrolytics, nice values £2.20 300 printed circuit resistors £1 300 printed circuit components £1.50</p>
<p>100 MINIATURE REED SWITCHES We are the cheapest! £3.30</p>	<p>100K MINIATURE THUMBWHEEL SLIDER POTS Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1</p>
<p>G.E.C. UHF TRANSISTOR TV TUNERS Rotary type with slow motion drive, leads and aerial socket £1.50 3 for £3.50</p>	<p>100K STEREO SLIDER POTS Good quality. 25p ea. 5 for £1</p>
<p>MAKE CHEAP BATTERY ELIMINATORS Fully shrouded, mini mains transformers. 240V in 8-0-8V at 100 MA out. Complete with mains lead and plug, ex new equip. 90p</p>	<p>MINIATURE LEVEL/BATT. METERS 200µA F.S.D. as fitted to many cassette recorders 80p</p>
<p>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS Includes 150 sq. ins. copper clad F/G board, 1 lb ferric chloride, 1 dato etch resist pen, Abrasive Cleaner, Etch tray plus instructions. Special Price £4.95 1 lb FE. C1. To mil. spec. £1.25 5 lb FE. C1. To mil. spec. £5.00 150 sq. in. Single sided board £2.00 150 sq. in. Double sided board £3.00</p>	

40p P & P on all above items. Cheque or P.D. with order to:

SENTINEL SUPPLY, DEPT. P.E.
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

Britain's Best Breadboard Buy at Breadboard '79

**FREE
ENTRY TICKET
WORTH £1.00
WITH EVERY PURCHASE**

All over Britain, hobbyists are discovering Britain's Best Breadboard Buys. At the London Breadboard exhibition '79 on Stand Nos. F1, F2 and G1, G2, CSC will be exhibiting their full range of breadboards.

Here is your chance to obtain a special ticket for Breadboard '79 worth £1.00 absolutely FREE.

Cut out the coupon below and take it along to one of our listed dealers, and make a purchase of any of our breadboards and receive your special FREE ticket — see you at Breadboard '79.

Take the coupon to any of these main dealers:

LONDON

Rastra Electronics Ltd., 279-281 King Street, Hammersmith, London W6

Cubegate Ltd., Audio Electronics, 301 Edgware Road, London W2 1BN

Technomatic Ltd., 17 Burnley Road, London NW10 1ED

Precision Instrument Labs., Instrument House, 727 Old Kent Road, London SE15

MANCHESTER

Shudehill Supply Co., 53 Shudehill, Manchester M4 4AW

BUCKINGHAMSHIRE

West Hyde Development, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET

Best Electronics (Slough) Ltd., Unit 4 Farnburn Ave., Slough, Bucks SL1 4XU

KENT

Lawtronics, 13a High Street, Edenbridge, Kent TN9 5AX

NEWCASTLE

Aitken Bros., 35 High Bridge, Newcastle upon Tyne

SCOTLAND

Marshalls, 85 West Regent Street, Glasgow G2

F. Brown & Co., 45 George IV Bridge, Edinburgh EH1 1E3

LEEDS

Leeds Amateur Radio Club, Cookridge Street, Leeds 1

HERTFORDSHIRE

BI-PAK, 3 Baldock Street, Ware, Herts.


CONTINENTAL SPECIALTIES CORPORATION



CSC UK LTD. EUROPE, AFRICA, MIDEAST

Dept 5CC2 Shire Hill Industrial Estate Units 1 and 2, Saffron Walden, Essex CB11 3AQ

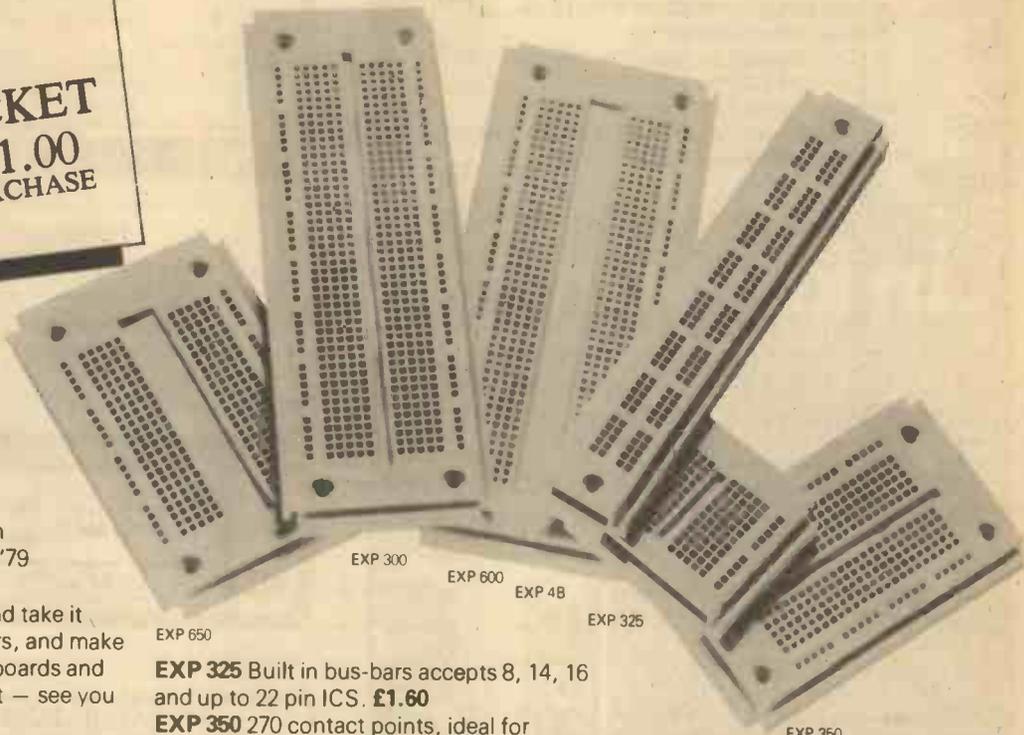Tel: Saffron Walden (0799) 21682. Telex: 817477



EXP 650
EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. **£1.60**
EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**
EXP 650 For microprocessor chips. **£3.60**
EXP 4B An extra 4 bus-bars in one unit. **£2.30**
EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**
EXP 600 6" centre channel makes this the Microprocessor Breadboard. **£6.30**
PB6 Professional breadboard in easily assembled kit form. **£9.20**
PB100 Kit form breadboard recommended for students and educational uses. **£11.80**

The above prices do not include P&P and 15% VAT

The Experimentor System

4 ways to order Experimentor Systems

1. EXP 300PC which includes one item.
A matchboard pre-drilled PCB — £1.32
2. EXP 302 which includes three items.
Three 50-sheet scratchboard workpads — £1.68
3. EXP 303 which includes three items.
Two matchboards and an EXP 300 solderless breadboard — £8.60
4. EXP 304 which includes four items.
Two matchboards and EXP 300 breadboard and a scratchboard workpad — £9.30

This coupon entitles the holder to a free ticket worth £1.00 to Breadboard '79, with the purchase of any listed breadboards

1. EXP 325 £2.70	Qty. Req'd.	2. EXP 350 £4.48	Qty. Req'd.
3. EXP 650 £5.00	Qty. Req'd.	4. EXP 4B £3.50	Qty. Req'd.
5. EXP 300 £7.76	Qty. Req'd.	6. EXP 600 £9.35	Qty. Req'd.
7. PB6 £11.73	Qty. Req'd.	8. PB 100 £14.72	Qty. Req'd.

Experimentor System

1. EXP 300PC £2.36	Qty. Req'd.	2. EXP 302 £2.79	Qty. Req'd.
3. EXP 303 £11.04	Qty. Req'd.	4. EXP 304 £11.85	Qty. Req'd.

Boxed prices include P&P and 15% VAT

If no dealer in your area contact CSC direct.

Continental Specialties Corporation, (U.K.) Limited, Dept 5CC2

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex Tel: (0799) 21682

NAME

ADDRESS

FREE catalogue tick box

I enclose cheque/PO for £
or debit my Barclaycard, Access, American Express card

No. Exp. date
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

Romane Electronics

LOW POWER SCHOTTKY TTL EX STOCK

Device	Price	Device	Price	Device	Price	Device	Price
74LS00	13p	74LS40	23p	74LS136	45p	74LS221	110p
74LS01	14p	74LS47	80p	74LS138	75p	74LS244	250p
74LS02	13p	74LS48	130p	74LS139	80p	74LS246	260p
74LS03	14p	74LS49	130p	74LS151	65p	74LS247	150p
74LS04	15p	74LS73	40p	74LS153	65p	74LS248	150p
74LS05	25p	74LS74	40p	74LS155	96p	74LS249	90p
74LS08	30p	74LS75	38p	74LS156	96p	74LS251	100p
74LS09	30p	74LS76	38p	74LS157	65p	74LS273	200p
74LS10	16p	74LS78	43p	74LS158	83p	74LS279	85p
74LS11	23p	74LS83	120p	74LS160	118p	74LS283	92p
74LS12	25p	74LS85	120p	74LS161	100p	74LS290	92p
74LS13	36p	74LS86	40p	74LS162	130p	74LS293	100p
74LS14	75p	74LS90	50p	74LS163	130p	74LS298	100p
74LS15	25p	74LS93	90p	74LS164	100p	74LS352	170p
74LS20	27p	74LS95	110p	74LS173	90p	74LS353	170p
74LS21	26p	74LS107	40p	74LS174	90p	74LS365	95p
74LS22	25p	74LS109	50p	74LS175	92p	74LS366	95p
74LS26	35p	74LS112	50p	74LS190	120p	74LS367	95p
74LS27	25p	74LS113	50p	74LS191	120p	74LS368	95p
74LS28	40p	74LS114	50p	74LS192	120p	74LS374	160p
74LS30	19p	74LS123	80p	74LS193	110p	74LS386	50p
74LS32	27p	74LS125	40p	74LS195	110p	74LS870	200p
74LS37	32p	74LS126	40p	74LS196	100p		
74LS38	39p	74LS132	70p	74LS197	120p		

LOW PROFILE DIL SOCKETS BY TEXAS

8 PIN	13p	18 PIN	25p	24 PIN	33p
14 PIN	14p	20 PIN	27p	28 PIN	43p
16 PIN	16p	22 PIN	28p	40 PIN	53p

VERD PRODUCTS Vero wiring Pen 290p. 2 x Spare Spools 100p. Spot Face Cutters 95p. Veroblock Breadboards 325p. Veroboard PCB's - 2.5" x 5" 65p. 2.5" x 3.75" 55p. 2.5" x 17" 195p. 3.75" x 5" 72p. 3.75" x 17" 262p.

MEMORIES 2214 500p. TMS 2516 Single Supply £27.00.

76477 Sound Generator Chip 210p.

LIGHT EMITTING DIODES

Color	0.122"	Price	0.2"	Price
RED	TIL209	13p	TIL220	15p
YELLOW	TIL212	22p	TIL224-1	20p
GREEN	TIL232	20p	TIL234-1	20p

All orders, large and small, will be dealt with IN STRICT ROTATION. Please add 15% V.A.T. to all orders plus 30p for P & P (P & P £1 for Poweraces). Export orders no V.A.T. but postage at cost air/surface. Prompt delivery on all orders.

Cheques, POs, Money Orders to be made payable to:-

ROMANE ELECTRONICS,
Sales Dept.,
64 Newlyn Drive,
Sale, Cheshire.
M33 3LE
Tel 061-962-2606

I.C. TEST CLIPS 10% discount for 25+ clips, 15% for 100+.

8 Pin £4.50, 14 Pin £2.73, 16 Pin £2.88, 18 Pin £6.06, 20 Pin £7.00, 22 Pin £7.43, 24 Pin £8.41, 28 Pin £9.24, 36 Pin £12.09, 40 Pin £12.73.

ALL CIRCUIT EVALUATORS Breadboards plus power supplies.

POWERACE 101 5-15VDC @ 600mA plus 0-15V meter. Price £68.55p.

POWERACE 102 +5VDC @ 1A plus 3 logic indicators & pulse detector, logic switches, data switches, clock generator and one shot. Price £92.75p.

POWERACE 103 +5VDC @ 750mA plus +15VDC @ 250mA & -15VDC @ 250mA. Also meter (15-0-15VDC), 2 logic indicators, 2 logic switches and 2 data switches. Price £99.80p.

SUPERSTRIP BREADBOARDS 840 solderless, plug-in tie points. Accommodates up to 9 14 pin DIPS. Price £10.07p with 10% discount for 10 superstrips or 15% discount for 25+.

Full range of breadboards, I.C. test clips, ribbon cable assemblies available (mostly ex-stock). Send large SAE for catalogue and price lists.

Now, complete your system!



Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £89.70.

The ultimate range of speakers

We carry a good selection of high quality chasis for the DIY speaker constructor: 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.80, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W. (No X over required) and cost only £6.32 each.



Projectors

Come and see our specially selected projectors from: £50.60 (Square Multifect 150) to £83.37 (Tutor 11E DDU) plus the widest array of projector attachment and effects that you'll ever see: on continuous demonstration.



Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive ONLY £28.75



Ropelights

Great effect at discos. 7 metres long. Multiway connectors. 4 channel. £46.00 (inc pack of spare bulbs)

Bulgian Octal plugs and sockets

There's always hundreds of Bulgian Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.69 P551 PLUG £1.72.

Multiway Cables
4 core (6A) 630p/metre
5 core (6A) 780p/metre
6 core (6A) 920p/metre

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

ALL SHOPS OPEN TUE.SAT
LATE NIGHT WED.
(UP TO 8 PM)

PERSONAL CALLERS ONLY

Roger Squire's

LONDON 176 Juno Iron Road, N19. 50yds Trafal Park Tube Station. Tel: 01 272 7474
BRISTOL 125 Church Road, Redfield (Near St. George's) 15 mins from City Centre
MANCHESTER Tel: 0272 550950
GLASGOW 251 Deansgate, 3.15 mins from City Centre
1 Queens Mansions Road (off Queen Margaret Drive) Kelvinside 20. just behind the BBC. Tel: 041 946 3303

ADVENTURES with ELECTRONICS

ADVENTURES WITH ELECTRONICS



UNILAB KIT

A complete Kit, including S-Dec, wire & battery, for the 16 projects described in Tom Duncan's book 'Adventures in Electronics' published by John Murray. No soldering. Adopted for class use in many schools; and a welcome gift for ages 11 upwards.

With book, £20.08 including postage and 15% VAT.

Without book, £18.58 including postage and 15% VAT.

Clear pictorial instructions for making the following: RAIN DETECTOR, INTERCOM, MORSE BUZZER, BURGLAR ALARM, 3 TYPES OF RADIO, PARKING LIGHT, FLASHING LAMP, ELECTRONIC ORGAN, METRONOME, SIREN, TIMER, COUNTER, FIRE ALARM.

And available shortly:

ADVENTURES WITH MICROELECTRONICS

A similar Kit based on 'Bimboard' and Integrated Circuits. Suitable for the complete beginner, or those who have already enjoyed 'Adventures with Electronics'.

With book, £31.80 including postage and 15% VAT.

Without book, £29.80 including postage and 15% VAT.

Conversion Kit: With book, £25.58 including postage and 15% VAT.

Without book, £23.58 including postage and 15% VAT.

Cash or cheque with order, please, to

UNILAB UNILAB LTD. Clarendon Road, Blackburn, BB1 9TA, England. Telephone (0254) 57643

Prices are correct at time of going to press.

MAPLIN

ELECTRONIC SUPPLIES




PRINTED CIRCUIT DRILLS

Miniature 12V DC drills designed for drilling pcb's. Small drill. Order as BW03D Price £6.75
Large drill. Order as BW02C Price £10.63



ANTI-STATIC MAT & GUN

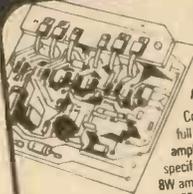Turntable mat removes static from discs while they are playing. Order as LX10L Price £2.95
Gun removes static charge from discs. After use dust no longer clings and may be easily brushed off. Order as LX04E Price £4.99



AMP KITS

Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications. 8W amp kit. Order as LW36P Price £3.83

50W amp kit. Order as LW35D Price £13.73
150W amp kit. Order as LW32K Price £14.89



HEADPHONES

High quality stereo headphone with large padded headband and slider volume controls. Order as WF14Q Price £7.99



CONDUCTIVE PAINT

Repair pcb's, car demisters, etc., with this silver paint. Phial contains 3gm. Order as FY72P Price £2.59



MCKENZIE POWER SPEAKERS

High quality, high power speakers. 12in. 50W 8Ω Order as XQ79L Price £18.79
12in. 50W 16Ω Order as XQ80B Price £18.79
12in. 80W 8Ω Order as XQ81C Price £26.92
12in. 80W 16Ω Order as XQ82D Price £26.92
15in. 150W 8Ω Order as XQ83E Price £57.00
15in. 150W 16Ω Order as XQ84F Price £57.80



MINIATURE VICE

Small modellers vice in tough plastic with metal jaws. Clamps to bench. Jaws width 41mm, maximum opening 30mm. Order as FY53H Price £2.78



20,000 OHM/VOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to -220dB. Complete with test leads, battery and instruction leaflet. Order as YB83E Price £13.70



ELECTRET MICROPHONES

Super quality genuine electret microphones operating on 1.5V battery (HP7-type) supplied. Cassette type with miniature jack plugs. Order as YB33L Price £3.84
Omnidirectional low-cost with standard jack plug. Order as YB34M Price £3.76
Unidirectional 600Ω with standard jack plug. Order as YB35Q Price £9.76
Unidirectional 600Ω/150kΩ dual with standard jack plug (pictured). Order as WF34M Price £16.77



WIRING TOOLS

Miniature box-jointed wiring pliers with insulated handles and return spring. Order as BR69A Price £4.52
Miniature box-jointed side cutters with insulated handles, return spring and precision cutting edges. Order as BR70M Price £4.45
End-action wire strippers, fully adjustable, insulated handles. Order as BR76H Price £5.85



CLOCK MODULE

Module requires only transformer and two push switches to operate 4 digit, 0.7in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue. Order as XL14Q Price £8.41



MEGAPHONE

High quality megaphone with differential microphone. Requires eight HP11 batteries (not supplied). Shoulder strap for portable operation. Order as XQ72P Price £47.61



DEMAGNETISER

Tape head demagnetiser with curved probe ideal for cassette tape heads. Cures hiss due to permanently magnetised heads. Amazing low price. Order as FQ62S Price £4.15



CAR AERIAL BOOSTER

High gain car aerial booster for long, medium, short and VHF bands. Negative earth cars only. Very easy to fit - just plugs in plus one wire to +12V. We have measured gains of 20dB at 90MHz! Order as XQ37S Price £5.95



TEACH YOURSELF ELECTRONICS

There is no better way of learning basic electronics than by practical experience and this set of books is undoubtedly the very best basic course for doing just that. Set of five Basic Electronics books. Order as XX10L Price £7.89



MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt. DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A. Resistance 5k, 50k, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet. Order as YB87U Price £39.30



TURNTABLES

Autochanger complete with stereo ceramic cartridge and circuit to make a complete low cost record player ideal for the young pop fan. Order as XQ80A Price £16.30
Single play rim-drive turntable with stereo ceramic cartridge. Order as XB23A Price £24.79
Single play belt-drive turntable S-shaped tone arm. Order as XB25C Price £30.63



TRANSISTOR TESTER

Accurate transistor tester measures dynamic gain, identifies unknown transistors, also ideal for matching transistors into pairs. Order as LM05F Price £12.28



QUICKTEST

A safe and quick way to connect to the mains. Just snap the wires under the sprung keys and close the lid. Completely safe both open and closed. Order as YB21X Price £6.29

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until January 11th 1980. Export customers deduct 13% and export postage will be charged extra at cost.

Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER.

MAPLIN


ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000.

A new edition from **Newnes Technical Books**

Questions and Answers Integrated Circuits Second Edition

R. G. Hibberd

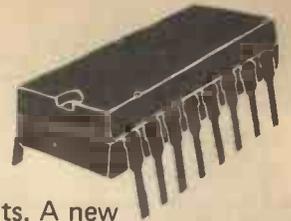

Covers in easy-to-follow Q & A format, all main types of integrated circuits. A new chapter on microprocessors and their application has been added for this new edition.

1979

108 pages

£1.55

(US \$3.50)

In the same series

Q & A Electronics, Clement Brown

Q & A Hi-Fi, Clement Brown

Q & A Radio Repair, Les Lawry-Johns

Q & A Radio and Television – Fourth Edition, H. W. Hellyer and I. R. Sinclair

£1.55 each (US \$3.50)


For further information please send for a free colour brochure describing these and many other publications.



Newnes - Butterworths

Borough Green, Sevenoaks, Kent TN15 8PH. Tel: (0732) 884567

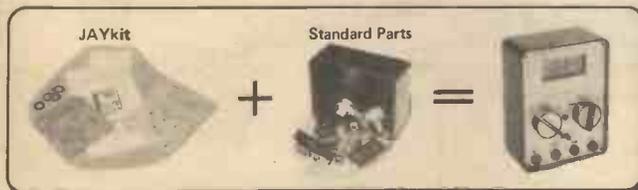Butterworths have companies in Australia, Canada, New Zealand, South Africa and the USA, where local prices apply



DM-2



DIGITAL
MULTIMETER

- ★ DC Volts 1mV to 1000V
- AC Volts 1V to 500V
- DC Current 0.1mA to 0.2A
- Resistance 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery Indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult pieces of hardware such as screws, washers etc. are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments
21 Gladeside, Bar Hill
Cambridge CB3 8DY
Tel: (0954) 80285

Name _____

Address _____

Please send:

- DM-2 @ £5.45
 FG-1a @ £4.95
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

P.E.11

JAYkits

Great new Crofton double!

Self contained
**MONITOR
PCB**



- Compact size, 5" x 7"
- Complete with power and video plugs, plus leads
- Scan coil assembly as standard supplied
- Transformers, tubes, and surrounds available
- 15v Mains or 12v DC power
- Ideal for O.E.M. use

self contained **10"**
MONITOR



- Totally enclosed
- All transistorised
- Suitable for analogue signals or alphanumeric
- Operable on 220v Mains or 12v DC power
- Comparable to wire frame monitors

ONLY **£35.50** ONLY **£85.00**

EX VAT AND P&P

Crofton Electronics

Crofton Electronics Limited, 35 Grosvenor Road,
Twickenham, Middlesex. Tel.: 01 891 1923



20 x 20 WATT STEREO AMPLIFIER
 Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/2" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility. **£31.90** p&p £3.00

30x30 WATT AMPLIFIER IN KIT FORM
 For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak For use with 4 to 15 ohms speakers. **£31.50** p&p £3.00

SPECIAL OFFER
30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge. **£57.00** + p&p £6.00

EMI SPEAKER BARGAIN
 Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround. 2 1/2" approx. Audaux tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max 8 ohm impedance. **£18.25** Per stereo pair £3.65 p&p

BSR P200
 Belt drive chassis turntable unit semi-automatic, cueing device. **£25.50** p&p £2.60
 A.D.C. QLM 30 Mk III Magnetic Cartridge to suit. **£7.95**

BSR Manual single play record deck with auto return and cueing lever. fitted with stereo ceramic cartridge 2 speeds, with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **OUR PRICE £11.25** £2.75

GARRARD DECK MODEL CC 10A
 Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth. **£8.15** p&p £2.05 Size 12" x 8 1/2"

UNIT AUDIO STAND
 Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors. **£3.95** £2.25 p&p 24" x 12 1/2" x 11 1/2" approx.

BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System
 Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones complete with speakers. **£35.75**

Micro Cassette Recorder
 Pocket size—home or office use or when travelling. **£14.25**

Battery operated fluorescent camping lamp.
 Runs off 8 U2 batteries. **£4.80**

Mullard

AUDIO MODULES IN BARGAIN PACKS
CURRENT CATALOGUE

PRICE £ AT OVER 25 PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £5.00** p+p £1.00


2 PACK 2. 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE £7.65** p+p £1.00

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit. Size approximately 9 1/4" x 8 1/4" x 4" **OUR PRICE £12.25** p&p £2.25



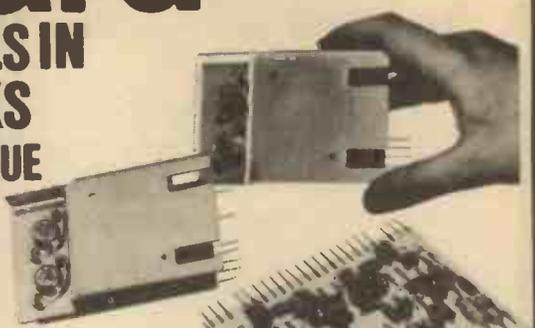ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.



ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance **£3.00** plus £1.50 p&p

Two Way Speaker Kit
 Comprising of two 8" x 5" approx 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors **£4.05** per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT.

BARGAINS FOR PERSONAL SHOPPERS

LCO Solar 5 function with backlite stainless steel finish case and strap **£7.40**

LCO Solar Chrono 9 function with backlite stainless steel finish case and strap **£9.55**

Chrono stop watch 9 function with back lite stainless steel finish case and strap. **£8.95**

Solar Alarm LCO stainless steel case and strap. **£21.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£12.20**

100 Watt Power Amp Module **£14.25**

Mains power supply for above unit **£3.60**

OECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3A" approx tweeter inc crossovers **£20.45**

VIDEOMASTER Super Score TV Game with pistol mains operation **£15.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock, LW, MW, SW, VHF mains/battery operation **£42.90**

ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. **£24.50**

100 WATT MONO DISCO AMP

Size approx 14" x 4" x 10 1/4"
 Brushed aluminium fascia and rotary controls
 Five vertical slide controls, master volume, tape level mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2 or vice versa Pre fade level control (PFL) lets YOU hear next disc before fading it in VU meter monitors output level. Output 100 watts RMS 200 watts peak **OUR PRICE £66.45** p&p £4.05

50 WATT MONO DISCO AMP

£30.60 p&p £2.70
 Size approx. 13 1/4" x 5 1/4" x 6 1/2"
 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

FOR PERSONAL SHOPPERS ONLY

DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 speaker units—8" approx woofer and 2 1/2" approx tweeter 45 to 1800 Hz Impedance 8 ohms Power 15 watts RMS 18 1/2" x 13 1/2" x 7 1/4" Per stereo pair approx **£16.50**

FOR PERSONAL SHOPPERS ONLY

STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. **Price £10.95**
 Size approximately 47" x 15 1/2" x 15"



323 EDGWARE ROAD, LONDON W2
 21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers


ALL PRICES INCLUDE VAT AT 15%

All items subject to availability. Prices correct at 1.10.79 and subject to change without notice

NOTE: Persons under 16 years not served without parent's authorisation

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

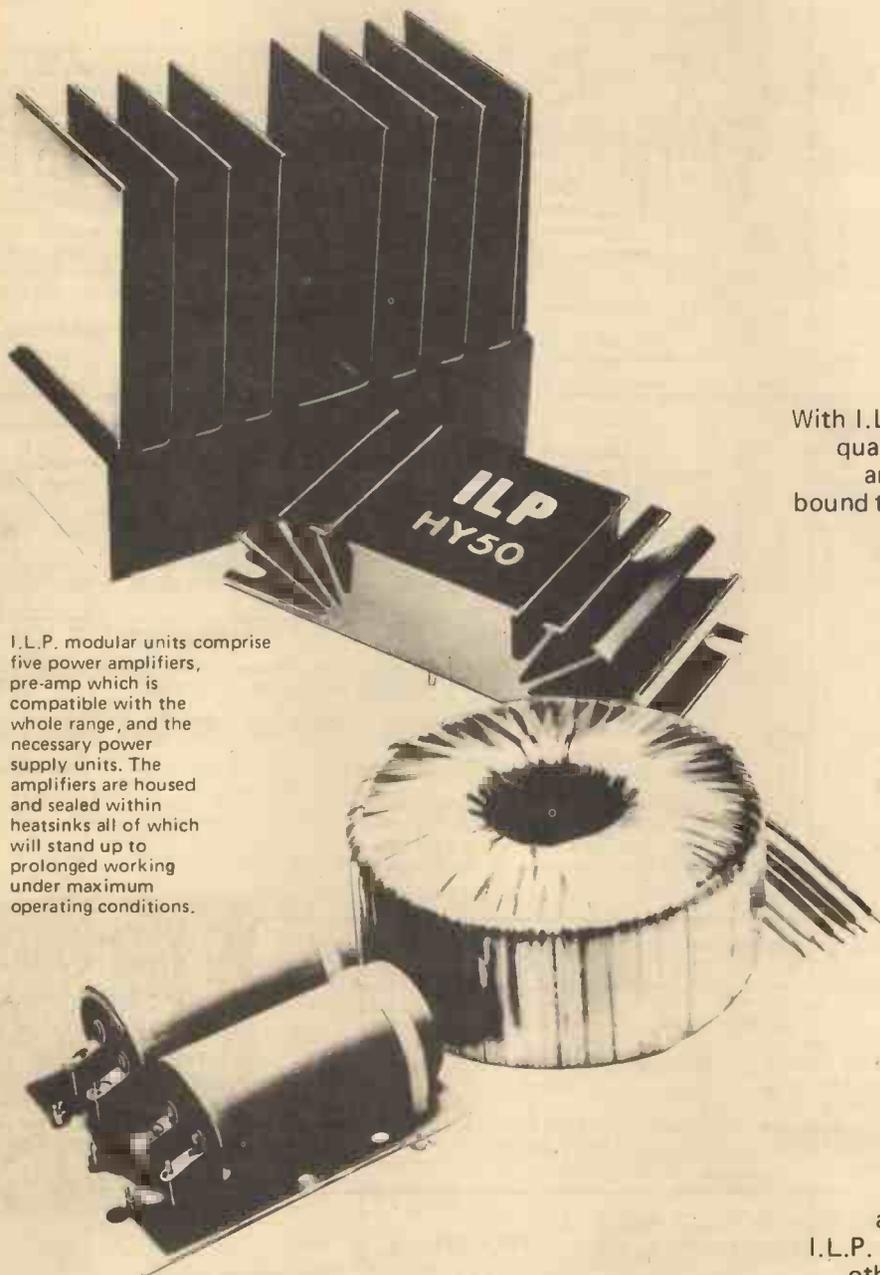

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.

With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance

— and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain

— the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance.

These have stood the test of time far longer than normally expected from

ordinary commercial modules. So we have concentrated on

improvements whereby our products will meet even more stringent demands such, for example, as

those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of

which can prove merciless to an indifferent amplifier system.



I.L.P. modules are for laboratory and other specialised applications too.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

and staying there

PERFORMANCE MODULAR UNITS



HY5 PRE-AMPLIFIER

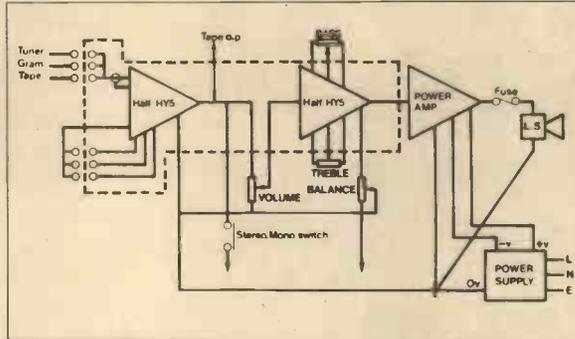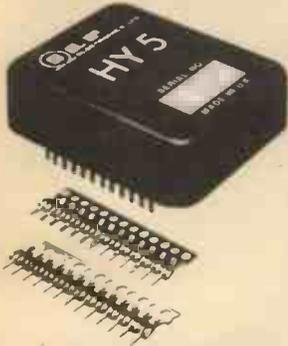

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz-0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

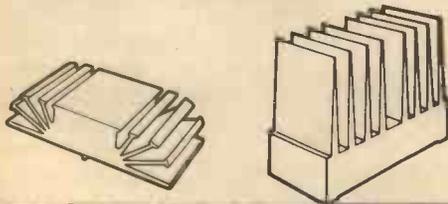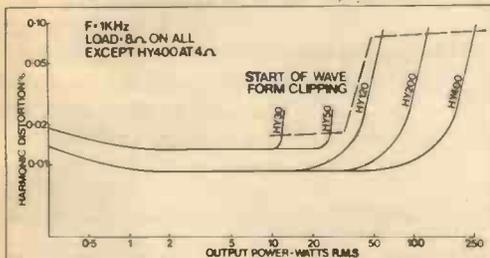

Model	Output Power R.M.S. into 8 Ω	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W	0.02%	80dB	-20 -0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W	0.02%	90dB	-25 -0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W	0.01%	100dB	-35 -0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W	0.01%	100dB	-45 -0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W	0.01%	100dB	-45 -0 +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4 - 16 Ω
 Input sensitivity - all models 500 mV
 Input impedance - all models 1.00 KΩ
 Frequency response - all models 10Hz - 45KHz - 3dB

THE POWER SUPPLY UNITS

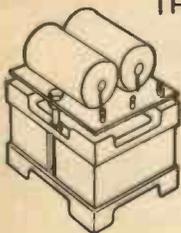

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled transformer the other with toroidal transformer having half the weight and height of its conventional laminated types.

PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT
PSU 30	± 15V at 100ma to drive up to: five HY5 pre-amps	£4.50 + 68p VAT

NO QUIBBLE
5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BUILT-IN PROTECTIVE CIRCUITRY
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE
 - see below

ALL U.K. ORDERS DESPATCHED POST PAID HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.

OLP
ELECTRONICS LTD.
 FREEPOST 2 Graham Bell House, Roper Close,
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 Telex 905780

Please supply

..... Total purchase price £.

I enclose Cheque Postal Orders International Money Order

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

Are your meters good enough?

If your recordings are spoilt by uneven levels and overloads—install Soundex professional PPM's now.



See us on Stand 609 at Electronics '79, Olympia, November 20-23rd where the full Soundex range will be on display.

The Soundex PPM 402 priced at £34.95 (plus VAT), has a closely specified electrical performance with a meter scale that has been developed from the BBC and VU scales providing high clarity and accuracy of indication. Special Features include: —

- Bipolar rectification
- Closed loop meter drive
- Wide frequency response
- Low current consumption
- Amplitude dependant amplifier
- Attack and decay circuits

Send for technical literature on the new 402

FREE
LINE-UPOSCILLATOR
WORTH NEARLY £5
WITH ALL ORDERS
PLACED BY
NOVEMBER
23RD '79

Bulgin Electronics

One of the Bulgin Group of Companies. **Soundex Ltd**
Park Lane, Broxbourne, Herts, Tel: Hoddesdon 64455

CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,
WOOD GREEN, LONDON,
N22 4SJ (MAIL ORDER DEPT.)

888-3206

FLIP

Push Button
Heads or Tails.

Complete kit
and full
instructions
supplied.

A pocket game. Easy to build and great to play. Kit price £5.25 + 78p VAT. Post free.



3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max. A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier. S.A.E. for spec. sheet. Still only £20.00 + £3 VAT.

PANEL METERS.

Dims:- 60 x 47 x 33mm.
Require 38mm dia. cut out

T22 0-100µA
T23 0-500µA
T24 0-1 M/A
T25 0-5 M/A
T26 0-10 M/A
T27 0-50 M/A
T28 0-100 M/A
T30 0-1 AMP
T31 0-2 AMP
T36 VU Meter
T43 0-30 V.DC
T35 "S" Meter
£5.50 + 83p VAT.



SWR50

SWR/POWER METER £21

+ £3.15 VAT Measures SWR and power.

SWR:- 1:3 1:1
Power:- 0-1KW ± 20%
Impedance:- 52 ohms
Frequency range:- 3.5 to 150 MHZ
Dims:- 145 x 75 x 57mm



SWR9

SWR and FS METER

£12.50 + £1.87 VAT

For antenna adjustment. Has convenient relative field strength meter built-in.
SWR:- 1:1 3:1
Accuracy:- 5%
Impedance:- 50 ohms
Frequency range:- 3-150 MHZ
Dims:- 120 x 50 x 55mm



SIRENS

S1 Siren. 125mm diameter gold coloured horn with fixing plate. Emits high-pitched wailing note of varying frequency - 16 cyc. per minute. 12 volts DC.
S2 As above but rapid noise frequency change - 160 cyc. per minute.
PRICE = £11.50p Including VAT.

U.S.A. CO-AXIAL PLUG SOCKETS AND ADAPTORS

	PRICE. EACH inc. VAT.
PL259 Standard co-axial male plug.	50p
S0239 Chassis mounting socket.	50p
S0239SH Panel mounting, one hole fixing socket.	60p
PL258 Double ended female coupler.	£1.30p
M358 "T" connector female/male/female	80p
NC563 Double in-line male adaptor (PL259 x 2)	£1.20p
M369 Right angle coupler. PL259/S0239	£1.20p

'P&P' orders up to £5. Add 30p.

Orders £5-£10. Add 50p.

All orders over £10 post free!

Please add V.A.T. as shown.

S.A.E. with all enquiries please.



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.
also 13 SOUTH MALL, EDMONTON GREEN, EDMONTON



Wilmslow Audio

THE firm for speakers!

SEND 30p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER
BOWERS & WILKINS ● CASTLE ● CELESTION
CHARTWELL ● COLES ● DALESFORD
DECCA ● EMI ● EAGLE ● ELAC ● FANE
GAUSS ● GOODMANS ● I.M.F. ● ISOPHON
JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER
McKENZIE ● MONITOR AUDIO ● PEERLESS
RADFORD ● RAM ● RICHARD ALLAN ● SEAS
SHACKMAN ● STAG ● TANGENT ● TANNOY
VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.E.)

SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street

Tel.: Wilmslow 529599 for Speakers


Tel.: Wilmslow 526213 for Hi-Fi

TRANSDAM

COMPUTER PRODUCTS

TRITON SINGLE PERSONAL COMPUTER

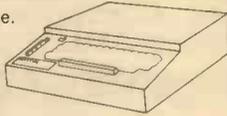Three new exciting expandable systems designed for ease of construction and flexibility. Kits come complete with case, power supply, full keyboard, PCB. All components available separately. See catalogue. Full hardware & programming manual available. The system is easy to expand and is well supported. Features:- 2, 2.5 or 7k basic in Eprom (See catalogue)



- Single board
- Holds up to 8k memory
- UHF or video output
- Cassette interface
- Three firmware options
- Basic in eprom
- 64 graphic characters
- Plug in expansion boards

From **£286** +VAT

EXPANSION MOTHERBOARD

TRITON. Expand your Triton simply and easily with our new 8-slot motherboard complete with its own P.S.U. takes 8 plug-in Euro cards. Plug-in 8k RAM card and Eprom cards now available. Kit complete with PSU & 1 set connectors.




8 SLOT
Uses standard 64-way DIN CON.

£50 +VAT

8K RAM CARD

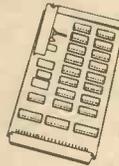
Triton 8k static Ram card. Kit uses 2114 Low power 4k. Static Rams. On board regulation, memory jump select. PCB only **£16** Rams **£5.50** each. Kit less Rams **£35** incl. all sockets & components.



Compl. kit **£97** +VAT

8K EPROM CARD

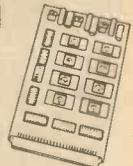Triton 8k Eprom card kit. Designed to take up to 8x2708 Eprom (1kx8)



PCB only **£15**
Kit less Eproms **£31**
Eproms (blank) **£9**
Plus VAT

Complete kit **£97** +VAT

BI DIRECTIONAL MATRIX PRINTER £595 +VAT

The BD80 is a low cost, 80 column line printer with microprocessor control to provide excellent reliability and performance.

- 5x7 Dot matrix
- 10 char per inch
- 6 lines/inch
- 400 char buffer
- Full asch char set
- 10 lines/adv
- paper advance
- 112 char/sec
- 84 lines per minute
- Self test
- Fully cased



A **UNIQUE PRINTER**
FAST AND RELIABLE

Switch selectable baudrate from 110 to 9600 on a standard V24 and R5232 interface. Send SAE for further details. Ideal printer for Triton or any system requiring high speed reliable hard copy. We can supply consumables.


\$100 boards

8k Static RAM board (450ns)	£123.75
8k Static RAM board (250ns)	£146.25
Z80 cpu board (2MHz)	£131.25
Z80 cpu board (4MHz)	£153.75
2708/2716 EPROM board	£63.75
Prototype board (bare board)	£18.75
Video display board (64 x 16, 128U/L Ascii)	£108.75
Disk controller board	£131.25
K2 disk operating system	£56.25
Assemble/z Macro Assm	£37.50

ITHACA DPS1

Pascal/z

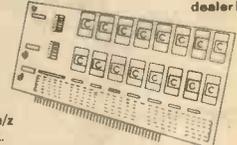Build your own Pascal Micro Development system. IEEE-S100 bus system using DPS1 mainframe. Supports K2, assemble/z and pascal/z on 8" disk.




your London dealer!

We stock the full range of ITHACA products.

PCB CONNECTORS

Edge connectors, gold contact double sided PCB connectors

Size	Price	156"	Price
1"	£3.20	6/12	£1.25
22/44	£3.20	12/14	£1.50
25/50	£3.60	10/20	£2.00
28/56	£3.90	15/30	£2.20
30/60	£4.15	18/36	£2.38
35/70	£4.60	22/44	£2.65
36/72	£4.75	28/56	£3.30
40/80	£5.00	36/72	£3.90
43/86	£5.50	43/82	£4.60
50/100	£5.80	(S100 BUS)	Plus VAT

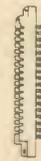

TRAP!

Triton resident assemble language package. Links via the L6-1 monitor and new scientific basic to make Triton a stand alone development system. Trap is an 8k package in EPROM and resides on our EPROM card. Set of 8x2708 only **£80** including document.

- EDITOR
- ASSEMBLER
- DISASSEMBLER
- SYMBOL TABLE
- CREATE
- BREAKPOINT
- SINGLE STEP
- TRACE
- PROGRAMME LOAD
- MONITOR

See catalogue for further details.

COMPONENTS 74LSXX

SN74LS00N	10	SN74LS40N	25	SN74LS113N	44	SN74LS165N	170	SN74LS248N	136
SN74LS01N	10	SN74LS42N	70	SN74LS114N	44	SN74LS166N	176	SN74LS249N	130
SN74LS02N	20	SN74LS47N	85	SN74LS122N	70	SN74LS168N	185	SN74LS251N	145
SN74LS03N	10	SN74LS48N	85	SN74LS123N	90	SN74LS169N	195	SN74LS252N	125
SN74LS04N	20	SN74LS49N	100	SN74LS124N	150	SN74LS170N	250	SN74LS257N	140
SN74LS05N	20	SN74LS54N	21	SN74LS125N	85	SN74LS173N	220	SN74LS258N	85
SN74LS08N	20	SN74LS55N	21	SN74LS126N	85	SN74LS174N	115	SN74LS259N	145
SN74LS09N	22	SN74LS56N	150	SN74LS127N	75	SN74LS175N	105	SN74LS260N	38
SN74LS10N	10	SN74LS57N	35	SN74LS128N	38	SN74LS176N	275	SN74LS261N	350
SN74LS11N	20	SN74LS58N	40	SN74LS129N	40	SN74LS177N	175	SN74LS262N	38
SN74LS12N	25	SN74LS59N	40	SN74LS130N	40	SN74LS178N	175	SN74LS263N	185
SN74LS13N	55	SN74LS60N	35	SN74LS131N	120	SN74LS179N	120	SN74LS264N	220
SN74LS14N	80	SN74LS61N	35	SN74LS132N	175	SN74LS180N	175	SN74LS265N	175
SN74LS15N	25	SN74LS62N	115	SN74LS133N	85	SN74LS181N	189	SN74LS266N	180
SN74LS16N	20	SN74LS63N	110	SN74LS134N	80	SN74LS182N	185	SN74LS267N	180
SN74LS17N	20	SN74LS64N	40	SN74LS135N	160	SN74LS183N	120	SN74LS268N	180
SN74LS18N	20	SN74LS65N	40	SN74LS136N	125	SN74LS184N	120	SN74LS269N	220
SN74LS19N	80	SN74LS66N	125	SN74LS137N	120	SN74LS185N	120	SN74LS270N	180
SN74LS20N	35	SN74LS67N	80	SN74LS138N	125	SN74LS186N	125	SN74LS271N	220
SN74LS21N	20	SN74LS68N	80	SN74LS139N	125	SN74LS187N	125	SN74LS272N	180
SN74LS22N	20	SN74LS69N	80	SN74LS140N	220	SN74LS188N	220	SN74LS273N	180
SN74LS23N	20	SN74LS70N	80	SN74LS141N	190	SN74LS189N	220	SN74LS274N	180
SN74LS24N	20	SN74LS71N	80	SN74LS142N	190	SN74LS190N	220	SN74LS275N	255
SN74LS25N	20	SN74LS72N	175	SN74LS143N	185	SN74LS191N	220	SN74LS276N	255
SN74LS26N	30	SN74LS73N	30	SN74LS144N	210	SN74LS192N	210	SN74LS277N	135
SN74LS27N	20	SN74LS74N	30	SN74LS145N	210	SN74LS193N	210	SN74LS278N	135
SN74LS28N	20	SN74LS75N	30	SN74LS146N	210	SN74LS194N	210	SN74LS279N	135
SN74LS29N	20	SN74LS76N	30	SN74LS147N	210	SN74LS195N	210	SN74LS280N	135
SN74LS30N	20	SN74LS77N	30	SN74LS148N	210	SN74LS196N	210	SN74LS281N	135
SN74LS31N	20	SN74LS78N	30	SN74LS149N	210	SN74LS197N	210	SN74LS282N	135
SN74LS32N	20	SN74LS79N	30	SN74LS150N	210	SN74LS198N	210	SN74LS283N	135
SN74LS33N	20	SN74LS80N	30	SN74LS151N	210	SN74LS199N	210	SN74LS284N	135
SN74LS34N	20	SN74LS81N	30	SN74LS152N	210	SN74LS200N	210	SN74LS285N	85
SN74LS35N	20	SN74LS82N	30	SN74LS153N	210	SN74LS201N	210		
SN74LS36N	20	SN74LS83N	30	SN74LS154N	210	SN74LS202N	210		
SN74LS37N	20	SN74LS84N	30	SN74LS155N	210	SN74LS203N	210		
SN74LS38N	20	SN74LS85N	30	SN74LS156N	210	SN74LS204N	210		

MEMORY AND SUPPORT CHIPS (Prices exclude VAT)

SUPPORT	220	TMS8011	5.00	4118	20.00	LINEARS	LM748CN-8	45	7815K	1.50	1M56011	6.00
8212	2.20	81LS95	1.80	280P10	10.00	LM301AH	LM748CN	45	7824K	1.50	MC14411	12.00
8216	2.28	81LS98	1.80	280 CTC	10.00	LM301AH-8	LM1458N	72	7905K	1.10	MC14412	12.90
8224	2.80	81LS97	1.80	280A P10	14.00	(Min Dip)	LM1458N-8	40	7912	1.10	95364	10.95
8226	2.20	81LS98	1.80	280A CTC	14.00	LM309K	LM14880	05	7915	1.10		
8228	4.20	RAMS				LM309K	LM1490	05	7924	1.10	CPU'S	
8238	4.20	2101	2.32	1702	6.00	(TOS)	LM1490AD	1.25	7905K	1.00	8080	6.33
8245	11.00	2102L-4	1.20	5204	6.00	LM311N	LM1495N-14	05	7912K	1.00	6800	10.00
8246	11.00	2111	2.32	5204	6.00	LM318N	LM1332N	05	7915K	1.50	280	10.00
8251	5.00	2112	2.46	2709	6.00	LM323K	LM1340N	05	7924K	1.89	280A	15.00
8253	11.00	2114	2.80	2516	28.00	LM324N	LM1390N	05	7924K	1.89	280B	12.85
8255	5.00	5810	4.08	2718	22.80	LM339N	LM1390N	54	DIL SOCKETS		6805	6.00
8257	11.00	8154	1.10			LM555N	75 TL080CP	1.40	8 DIL	14	SCM711	10.00
8259	12.50	2114	5.50			LM555N	75 TL081CP	05	18 DIL	17	6802	13.85
8264	11.00	2102L-3	1.50			LM555N	75 TL082CP	1.85	18 DIL	24	9900	30.00
8265	11.00	74C920	11.00	74S267	4.00	LM7080N	75 TL083CP	1.80	20 DIL	27		
8267	4.50	74C921	11.00	74S472	12.00	LM7090N	75 TL084CP	1.80	20 DIL	27	W/WRAP SKTS	
8268	4.50	74C922	11.00	74S473	12.00	LM7230N	75 TL085CP	1.80	28 DIL	30	8 DIL	20
8269	4.80	74C923	11.00	74S474	12.00	LM7230N	75 TL086CP	1.80	28 DIL	30	14 DIL	35
8271	5.50	4027	6.00	74S473	12.00	LM7230N	75 TL087CP	1.80	28 DIL	30	14 DIL	42
8272	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL088CP	1.80	28 DIL	30	14 DIL	42
8273	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL089CP	1.80	28 DIL	30	14 DIL	42
8274	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL090CP	1.80	28 DIL	30	14 DIL	42
8275	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL091CP	1.80	28 DIL	30	14 DIL	42
8276	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL092CP	1.80	28 DIL	30	14 DIL	42
8277	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL093CP	1.80	28 DIL	30	14 DIL	42
8278	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL094CP	1.80	28 DIL	30	14 DIL	42
8279	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL095CP	1.80	28 DIL	30	14 DIL	42
8280	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL096CP	1.80	28 DIL	30	14 DIL	42
8281	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL097CP	1.80	28 DIL	30	14 DIL	42
8282	5.50	4027	6.00	74S474	12.00	LM7230N	75 TL098CP	1.80	28 DIL	30	14 DIL	42
8283	5.5											

Quality audio modules and accessories for

S450

STEREO FM TUNER
Fitted with phase lock-loop

£26.73
+ 40p p&p



FREQUENCY RANGE	88-108 Mhz
SENSITIVITY	3.0 µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm × 110mm × 32mm

The S450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage, Vari-Cap diode tuning, Switched AFC LED Stereo Indicator.

Stereo 30

COMPLETE AUDIO CHASSIS

£22.06
+ 66p p&p



7 + 7w R.M.S.

OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dBs
tone CONTROL RANGE	± 12 dBs at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V.A.C. rated at 1A
DIMENSIONS (Less controls and panel)	200mm × 130mm × 33mm

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results. This unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.

AL60

AUDIO AMPLIFIER MODULE
25 Watts RMS

£5.39 + 35p p&p



25w R.M.S.

OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz × 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm × 64mm × 15mm

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

AL80

AUDIO AMPLIFIER MODULE
35 Watts RMS

£8.54 + 35p p&p



35w R.M.S.

OUTPUT POWER	35 Watts RMS
SUPPLY	40-60 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz × 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm × 64mm × 15mm

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

AL250

POWER AMPLIFIER

£20.49 + 76p p&p



125w R.M.S.

OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50-80 V
LOADS	4-16 ohms
FREQUENCY RESPONSE	25 Hz to 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS O/P AT 1 kHz	450 mV
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	50 WATTS into 4 ohms 0.1% 50 WATTS into 8 ohms 0.06%

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

AL30A

AUDIO AMPLIFIER MODULES

£4.36 + 35p p&p



10w R.M.S.

MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .25%
LOAD IMPEDANCE	8-16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	50 Hz-25 kHz ± 3 dBs
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm × 63mm × 28mm

These low cost 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

SPM80

STABILISED POWER SUPPLY
£5.06 + 35p p&p



INPUT A.C. VOLTAGE	33-40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	10 mA-1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm × 63mm × 30mm

Designed to power two AL60s at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

PA100

STEREO PRE-AMPLIFIER

£18.46
+ 46p p&p



FREQUENCY RESPONSE	20 Hz to 20 kHz × 1 dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY	1. TAPE 100 mV/100 K ohms } For an 2. RADIO TUNER 100 mV/100 K ohms } output 3. MAGNETIC P.U. 3.5 mV/50 K ohms } 250 mV
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10-20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All Inputs)
INPUT OVERLOAD	Better than 26 dBs (All Inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300 × 90 × 33mm (less controls)

A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution to the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

MPA30

MAGNETIC CARTRIDGE PRE-AMPLIFIER



£3.43

+ 35p p&p

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

SENSITIVITY	3.5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V—re earth
DIMENSIONS	110 × 50 × 25mm (inc DIN socket)

PA12

STEREO PRE-AMPLIFIER



£8.95

+ 35p p&p


The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL 20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

FREQUENCY RESPONSE	20 Hz-20 kHz (—3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	-60 dB
SIGNAL/NOISE RATIO	-85 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm × 84mm × 25mm

PS12 POWER SUPPLY MODULE

Power supply for AL20A-30A, PA12, S450, etc.
Transformer T538.

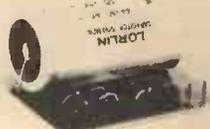Input A.C. Voltage 15-20V.
Output D.C. Voltage 22-30V approx. (Dependent upon input.)
Output Current 800mA maximum.
Dimensions 60 × 43 × 26mm.



£1.73

+ 35p p&p.

BP124 SIREN ALARM MODULE

American Police siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes.



ONLY £4.03

+ 35p p&p.

5 WATTS —

STA15 STEREO AMPLIFIER KIT

Build your own top quality amplifier, save yourself pounds. The STA15 kit comprises the following BI-kits modules, 2x AL60 amps, 1x PA100 pre-amp, 1x SPM80 stab. power supply, 1x BMT80 transf. giving 15 watts RMS per channel STEREO. All modules covered by the BI-PAK satisfaction or money back guarantee. Details of the above modules are in this ad.
Price £40.68 + 62p p&p.

STA15 ACCESSORY KIT

A beautifully designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. Front & Back Panels, Knobs, Chassis, Fuses, Sockets, Nuts, etc. Ideal for the MA60. Size: 425mm × 290mm × 95mm.
Price £21.94 + 86p p&p. Order No. 2240.

TRANSFORMERS

T538 For use with S.450 AL30A MPA30
Order No. 2036 Price: £3.68 + 55p p&p.
T2050 For use with Stereo 30
Order No. 2050 Price: £3.74 + 55p p&p.
BMT80 For use with AL60 SPM80
Order No. 2034 Price: £6.21 + £1.00 p&p.
BMT250 For use with AL250
Order No. 2035 Price: £7.30 + £1.10 p&p.
2040, For use with AL60
Order No. 2040 Price: £5.98 + 80p p&p.
2041, For use with AL80, AL120 and AL250
Order No. 2041. Price: £7.82 + 86p p&p.

CASES

TEAK 30, 32 × 23 × 8cm, designed mainly for use with our stereo 30 Audio System but has proved very helpful to home constructors. Fitted with solid uncut front and back. o/n 139. £6.27, p&p 70p.

TEAK 60, 42 × 29 × 9cm, for use with AL60/MK60 Audio Kit. Useful for the home constructor requiring an amplifier sleeve — has no front or back panel. o/n 140. £8.63, p&p 85p.

Professionals and Enthusiasts from BI-PAK

AL120

AUDIO AMPLIFIER
(With integral heat sink and short-circuit protection).

£13.74

+ P. & P. 35p

Introduced to fulfill the demand for a fully protected power amp., capable of driving high quality speaker systems at up to 50w., with distortion levels below 05%. Ideal for domestic use. Discos, P.A. systems, electronic organs etc. The generously rated components ensure continuous operation at high output levels.



50W
R.M.S.

OUTPUT POWER	50 Watts R.M.S.
SUPPLY	70 Watts
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	05% Max. (Typically 02%)
FREQUENCY RESPONSE	±1dB 25Hz-20KHz
SENSITIVITY	500mV
MAX HEAT SINK TEMP	45 deg. C
DIMENSIONS	192 x 89 x 49 mm

SPM120

STABILISED POWER SUPPLIES

SPM120/45
SPM120/55
SPM120/65

£6.67

+ P. & P. 35p



AC INPUTS	
SPM120/45	40-48v
SPM120/55	50-55v
SPM120/65	60-65v
OUTPUT CURRENT	2.5A
RIPPLE	1A 100mV 2A 150mV

SPM120 is a fixed voltage stabiliser available with an output voltage of either 45v, 55v, or 65v. Designed primarily for use in audio applications, the stabiliser which provides output currents up to 2.5A., operates direct from a mains transformer requiring only the addition of 2 electrolytic capacitors to complete the s/c protection.

GE100 Mk2.

10 CHANNEL MONOGRAPHIC EQUALISER

£23.00

+ P. & P. 35p



Control Range	±12dB
Dynamic Range	110dB
Maximum Output	+15dB
Frequency Response	30Hz-20KHz (±1dB)
Power Supply	15-0-15v.
Voltage Handling Input	3v R.M.S.
T.H.D.	-.05%

Only 155mm x 65mm x 50mm including the 10 x 10K 1in slider potentiometers and knobs which are mounted on a board positioned above the circuitry. In the frequency range of 31Hz to 20KHz you can cut and boost ±12dB with the 10 sliders, each of which has its frequency marked on the circuit board. The GE100 has numerous uses including mixers, P.A. systems and discos. It will also greatly improve the sound reproduction of your existing audio equipment. Power Supply for GE100, o/d SG30 £3.80.

VPS30

REGULATED VARIABLE STABILISED POWER SUPPLY

£8.74

+ P. & P. 35p



AC Input Maximum	25v
Voltage Regulation	2-30v
Regulated Current	0-2A
Incorporating short circuit protection	

This NEW variable Regulated Variable Stabilised Power Supply with short circuit protection and current limiting, is a must for all electronics enthusiasts. It incorporates adjustable voltage from 2v-30v, with a current limiting range of 0-2A. With this module there is no need to build a separate power supply for each of your projects, with the simple addition of a transformer (o/d 20331, 0-1ma (o/d 1310 or 1305), plus a suitable shunt, a voltmeter (o/d 1311 or 1306), a 470ohm pot (o/d 1896), a 4K7 pot (o/d 1899), it can be used again and again as a self-contained bench, power supply, eliminating the use of batteries and thus saving ££!

PA200

STEREO PRE-AMPLIFIER

£18.61

+ P. & P. 40p



FREQUENCY RESPONSE	20Hz to 20kHz x 1dB
TOTAL HARMONIC DISTORTION	Less than 1% (Typically .70%)
SENSITIVITY	1. TAPE 100mV/100 K ohms For an output 500mV
INPUTS	2. RADIO TUNER 100mV/100 K ohms
	3. MAGNETIC P.U. 3.5mV/50 K ohms
EQUALISATION	Within ±1dB from 20Hz to 20kHz
BASS CONTROL RANGE	±15dBs at 75Hz
TREBLE CONTROL RANGE	+10-20dBs at 15kHz
SIGNAL/NOISE RATIO	Better than 65dBs (All inputs)
INPUT OVERLOAD	Better than 26dBs (All inputs)
SUPPLY	35 to 70V
DIMENSIONS	300 x 90 x 33mm (less controls)

The PA200 is basically our popular PA100. Modifications have been made to make it compatible with the higher output AL120 and AL250 amplifiers.

HEADPHONES

A top quality headphone with cushioned earpads and headband. Separate balance/volume controls. Stereo or Mono switch. Impedance: 8 ohms. Frequency: 30-18,000Hz. o/n 884. £10.01. p&p 70p.

A brilliant compromise between price and performance. Superb stereo reproduction for the newcomer to Hi-Fi. Impedance 8 ohms. Frequency: 30-15,000Hz. o/n 885. £6.06. p&p 50p.

METERS

Miniature Balance & Tuning Meter
Miniature moving-coil meter for stereo balance indicator, tuning indicator for FM or similar application. Pointer at centre indicates zero or null position. Robust construction. Sensitivity: 100 0 1000UA. Dimensions: 23 x 22 x 26mm. o/n 1318. £2.24. p&p 35p.



Balance and Tuning Meter
Clear view edge-wise meter. Centre zero application. Sensitivity: 100 0 1000UA. Dimensions: 45 x 22 x 34mm. o/n 1319. £2.30. p&p 35p.



Miniature Level Meter
Moving coil, for accurate level indication for tape recorders, amplifiers etc. Neat design, rugged construction will withstand five times rated value. Sensitivity FSD 200UA OdB 130UA Dimensions: 23 x 22 x 26mm. o/n 1320. £3.22. p&p 35p.



Vu Meter
Calibrated 20 to +3 and 0 100%, making it suitable for use as a recording level meter or as a power output indicator. Sensitivity 130UA. Dimensions: 40 x 29mm. o/n 1321. £2.30. p&p 35p.



ADAPTORS

AC-DC enables a large range of battery powered radios, recorders, calculators to be run off the mains. (220-240v AC). Switchable for 3-6-9-12 volts. Current rating 300mA. Polarity reversing switch. Universal plug incorporated. o/n 137. £4.14. p&p 35p.

DC-DC for use in all cars, boats etc., with pos. or neg. earth for a regulated output of 6, 7.5 or 9 volts DC at 300mA. For radios, recorders etc. o/n 138. £3.22. p&p 35p.

CROSSOVER NETWORKS

2-WAY channels for high and low frequencies to correct speakers - high to tweeters, low to woofers. Complete with instructions. Frequency: 3,000Hz. o/n 1904. £1.73. p&p 35p.

2-WAY for 8 ohm speakers up to 30 watts. Frequency: .3KHz. o/n 1905. £2.65. p&p 35p.

3-WAY for 8 ohms speakers up to 30 watts. Frequency: 800Hz and 4.5KHz. o/n 1906. £4.60. p&p 35p.

MICROPHONES

DYNAMIC CASSETTE

For equipment requiring a high quality microphone. Sturdy, solid moulded body in black with neat chrome surround. Pick-up pattern is omnidirectional. On/Off switch, 1 metre of tough lead with floating 2.5 and 3.5mm plugs. Matching moulded strut. Impedance: 200 ohms. Sensitivity: 90dB. Frequency: 90-10,000Hz. Size: 20mm dia x 120mm. o/n 1326. £1.84. p&p 35p.

DYNAMIC MICROPHONE

Superior quality portable cassette recorder mike built-in remote control switch and lead fitted with 5-pin 240F DIN plug (remote switch) and 3-pin DIN plug (microphone). Provides a direct replacement for those supplied with recorders. With detachable stand. Omnidirectional. Impedance: 200 ohms. Freq. response: 100 to 10,000Hz. Sensitivity: 79dB at 1,000Hz. o/n 1327. £3.05. p&p 35p.

RE-317 DYNAMIC MICROPHONE

Highly sensitive, high-grade desk or hand mike suitable for use with many popular cassette decks. Incorporates On/Off switch and 1 metre lead with moulded standard jack plug. Complete with desk stand. Omnidirectional. Impedance: 5,000 ohms. Freq. response: 100 to 12,000Hz. Sensitivity: (-7dB at 1,000Hz). o/n 1336. £6.29. p&p 35p.

OMNIDIRECTIONAL CARDIOID

Powered by a 1 1/2 battery located within the aluminium body. Satin silver finish with front disk protection to the diaphragm housing. On/Off switch. Also with "Busby" type windshield. "U" bracket and stem and extremely supple cable. Consumption: 0.2mA from 1 1/2 battery providing approx. 8-10,000 hours continuous life. Impedance: 600 ohms. Sensitivity: 70dB. Frequency: 30-16,000Hz. Size: 23mm dia x 267mm. o/n 1328. £14.72. p&p 35p.

UNIDIRECTIONAL CARDIOID

Dual imp. 600 and 50,000 ohms. Response 50 to 14,000Hz. Sensitivity 54dB at 50K/ohms. Size 1 1/2" dia x 6 1/2" long. Weight approx., 190gm. o/n 1328. £12.69. p&p 35p.

STANDS

GOOSENECK CHROME FLEXIBLE HOLDERS

Length 320mm. o/n 1333. £2.99. p&p 35p.

Length 515mm. o/n 1334. £4.03. p&p 35p.

FLOOR STAND Heavy chrome. Stow-away feet with rubber ends for maximum stability. Draws to a height of 5' maximum. o/n 1335. + £12.31. p&p 85p.

BOOM ARM for use with the above stand. Heavy chromed metal. It gives 30" reach from the stand. o/n 1337. £10.58. p&p 70p.

WINDSHIELD COVERS

o/n 1331. Medium per pair £1.38. p&p 35p. o/n 1332. Large per pair £2.30. p&p 35p.

AUDIO LEADS

- 107 FM Indoor Ribbon Aerial £0.09
- 113 5mm Jack plug to 3.5mm jack plug Length 1.5m £0.86
- 114 5 pin DIN plug to 3.5mm. Jack connected to pins 3&5. Length 1.5m £0.98
- 115 5 pin DIN plug to 3.5mm. Jack connected to pins 1&4 Length 1.5m £0.98
- 116 Car aerial extension. Screened insulated lead. Fitted plug & socket £1.44
- 117 AC mains connecting lead for cassette recorders & radios. 2 metres £0.78
- 118 5 pin DIN phono plug to stereo headphone jack socket £1.21
- 119 2 - 2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m £1.04
- 120 Car stereo connector. Variable geometry plug to fit most car cassette, 8 track cartridge & combination units. Supplied with inline fused power lead and instructions. £0.89
- 123 6.5m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK £1.73
- 124 3 pin DIN plug to 3 pin DIN plug Length 1.5m £0.86
- 125 5 pin DIN plug to 5 pin DIN plug Length 1.5m £0.86
- 126 5 pin DIN plug to Tinned open end. Length 1.5m £0.86
- 127 5 pin DIN plug to 4 Phono Plugs. £1.80
- 128 All colour coded. Length 1.5m £1.92
- 129 5 pin DIN plug to 5 pin DIN socket. Length 1.5m £1.21
- 130 5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m £1.21
- 131 2 pin DIN plug to 2 pin DIN inline socket. Length 5m £0.78
- 131 5 pin DIN plug to 3 pin DIN plug 1&4 and 3&5. Length 1.5m £0.95
- 132 2 pin DIN plug to 2 pin DIN socket. Length 10m £1.13
- 133 5 pin DIN plug to 2 phono plugs. Connected pins 3&5 Length 1.5m £0.86
- 134 5 pin DIN plug to 2 phono sockets. Connected pins 3&5 Length 2.3cm £0.78
- 135 5 pin DIN socket to 2 phono plugs. Connected pins 3&5 Length 2.3cm £0.78
- 136 Coiled stereo headphone extension lead. Black Length 6m £2.01
- 178 AC mains lead for calculators etc. £0.54

All prices are inclusive of VAT. Barclaycard & Access accepted. Giro A/C No.: 3887006

BI-PAK
DEPT. PE12, P.O. Box 6,
13 Baldock Street, Ware, Herts.

Just a little bit more...

NASCOM-2


Compare its features:

- * Z-80A 4MHz CPU: The most powerful 8-bit processor on the market.
- * 8K Basic: resident on board, MICROSOFT Basic, the industry standard, with extensions for on-screen editing, graphics, machine code interfacing. Optimised for speed (see benchmarks below).
- * Full 57 Key Ucon solid state keyboard: switch mechanisms are contactless, high reliability professional units for long trouble free life. Keyboard is mounted separately to avoid straining main P.C.B.
- * Total of 20K on-board memory: 2K monitor (Nas-Sys 1), 1K Video RAM, 1K Work space RAM, 8K Microsoft Basic, 8K user RAM.
- * Kansas City cassette interface: for reliable storage of programs and data at 300 or 1200 baud, with full checksum error detection.
- * Nas-sys monitor: A powerful 2K machine code monitor provides an ideal environment for learning about and developing machine code programs. Nas-sys uses a blinking non-destructive cursor, with 22 commands. ASCII terminals are fully supported via the serial interface; users can add their own I/O drivers via the system I/O vector table to support other devices.

Nas-sys commands are:

- | | |
|-------------------------------------|-----------------------------|
| A—Hex arithmetic | N—return to normal |
| B—set breakpoint | O—Output to P.I.O. |
| C—Copy | Q—Query input port |
| E—Execute | R—Read tape |
| G—Generate | S—Single step |
| H—Operate as half duplex, terminal. | T—Tabulate memory |
| I—Intelligent copy | U—activate user I/O drivers |
| J—Execute at FFA | V—Verify tape |
| K—set keyboard options | W—Write tape |
| L—load from tape | X—set external device |
| M—Memory modify | Z—execute at FFD |

- * On board P.I.O. — An uncommitted P.I.O. (MK 3881) giving 18 programmable I/O lines with handshake.
- * On board RS-232C Will Interface directly into any standard teletype — allowing use of BASIC or Nas-sys from the teletype.
- * Full on-screen editing: a complete screen editor with cursor movement (UP, DOWN, LEFT, RIGHT), insert and delete, backspace etc.
- * Screen display of 16 lines x 48 characters: Stable, clear display to British television standards. Full 128 ASCII character set; option for further 128 graphics characters.
- * Fully buffered NASBUS compatible: Well defined bus structure with a range of expansion cards; including (shortly) a floppy disc system with CP/m — the industry standard operating system.

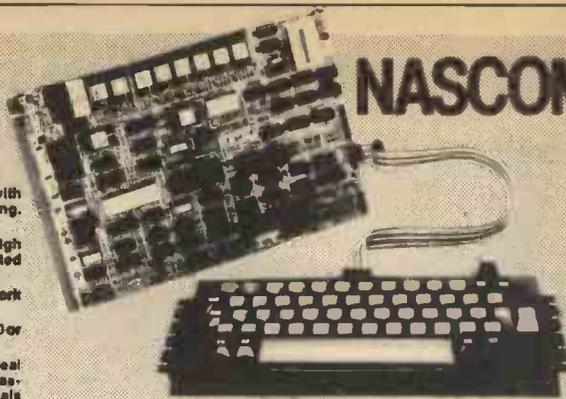

	Nett	Val	Total
Nascom-2	295.00	44.25	339.25
Power supply	24.50	3.68	28.18
10 C15 cassettes	4.44	0.66	5.10
Z-80 Programming manual (Mostek)			4.50
Z-80 Microcomputer handbook			6.95
Practical microcomputer programming the Z-80			20.00
Sargon-8K Z-80 Chess program (book)			9.50

PERSONAL COMPUTER WORLD BENCHMARK TESTS

	APPLE II		RM. 380Z	PET
BM 1	1.5	1.1	1.4	1.7
BM 2	3.2	5.4	6.5	9.9
BM 3	7.3	11.1	13.2	18.4
BM 4	7.2	11.6	13.9	20.4
BM 5	8.9	12.6	15.0	21.7
BM 6	16.6	19.3	22.3	32.5
BM 7	28.2	27.6	31.8	50.9
BM 8		5.2	6.2	12.3



25 Brunswick Street, Liverpool L2 0BJ
Tel: 051-236 0707 (Mail Order) 051-227 2535 (All other Depts)

What's new from Heathkit?



IM 2212—Auto Ranging DMM



IO 4105—Single Beam 5 MHz Oscilloscope



IM 5217—Portable Multimeter

Plus

- * GD 1290—VLF Metal Locator
- * HX 1681—CW Transmitter
- * IR 5201—XY Recorder
- * CI 1525—Car Temperature Indicator

These brand new self-assembly kits are designed to the highest specification. The step-by-step instructions make them easy to build at your leisure in your own home.

And first class quality makes them excellent value for money.

Details of the full Heathkit range are available in the Heathkit catalogue. Send for your copy now.



IM 2215—Hand-held DMM

To: Heath (Gloucester) Limited, Dept. (PE 12), Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.

Name _____

Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

Soldering Iron offer FREE

When you receive your catalogue you will get details of this free offer.



There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451).



THE COUNTRY

EVEN in the face of a Government paper, which basically reports that the microprocessor revolution will create more employment in the foreseeable future, and the recent Labour Party commitment to microelectronics at its conference, some bodies are still spreading gloom over the electronics industry and the country. Even if there are sound arguments behind such pessimistic views, we are pleased to report that at last we are beginning to stop procrastinating and get on with the job in hand.

Many component distributors have been reporting an increase of up to 60 per cent in sales, this increase started back in August—normally a quiet month in the industry. The boom is generally attributed to the employment of m.p.u.s in new designs and equipment causing a market expansion, especially in demand for memories. The problem is that we are now years behind the Americans and our industry has been so slow to react to the new technology that a very high percentage of the newly developed equipments are being imported because, as yet, there are no British competitors.

It seems to us that, as a nation, we excel at the investigation and discussion of possible social problems and both management and workers—usually for very different reasons—are initially set against the speedy introduction of new techniques and technology. Both the lengthy strikes at *The Times* and ITV have had much to do with new technology. Unless our basic attitudes to progress change we will suffer a lower standard of living and new technology *will* cause unemployment—because we refuse to allow it to be used. We must all be prepared to change our views and retrain ourselves if necessary; if we do and if we move quickly we will ultimately all prosper.

THE HOBBYIST

Unfortunately the present buying spree by industry is creating component supply problems and once again we suspect the hobbyist is beginning to suffer. There has been a world shortage of ROMS and this has affected the supply of parts for home computers. Delivery dates are again lengthening and sometimes being broken by manufacturers, so have some sympathy

with your component retailer if he is out of stock and says it could be a month or two before a certain device is again available—very often he can only pass on information from the manufacturer and that information has, in the past, sometimes proved to be unreliable.

These problems also have a bearing on the projects we bring you. Recently we have been investigating the possibility of publishing a constructional design for one of the latest devices, only to discover that no mask-programmed single chip processors, suitable for our purpose, were available in less than six months. Steps are now being taken to circumvent the problem with the use of a PROM—this alternative will cost slightly more but the six months gained will be worth it. However, the supply of PROMS and RAMS is now under some strain so we must also watch that position carefully. The time problem is not because we are small hobbyist buyers—we have been discussing a device costing about £6,000 to get into production with one of the world's largest suppliers.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

ADVERTISEMENT MANAGER

D. W. B. Tilleard

SECRETARY

Christine Pocknell

01-261 6676

AD. SALES EXEC.

Alfred Tonge 01-261 6819

CLASSIFIED MANAGER

Colin Brown 01-261 5762

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £3.75 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perryment Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Market Place


Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by
**Alan
Turpin**

and
**David
Shortland**

HUNTRON TRACKER

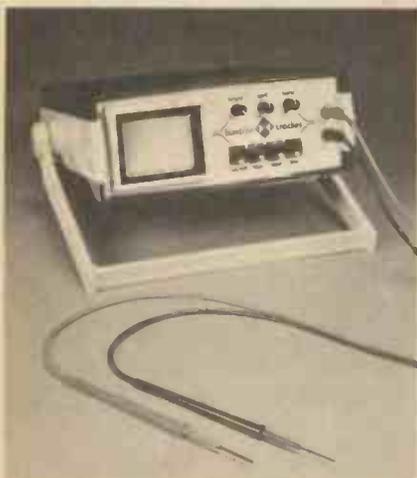The Huntron Tracker is a versatile instrument for trouble-shooting solid state circuits. The unit is capable of in-circuit testing of a number of discrete components: i.c.s, transistors, FETs, diodes, l.e.d.s, Zeners, UJT's, electrolytic capacitors and gate controlled devices.




The Tracker uses a scope display, two non-polarised leads and three impedance ranges. The scope display show the condition of the device under test indicating "shorts", "opens" and "leaks". Both the forward and reverse response of the component can be displayed on the scope screen.

The price of the Tracker will be around £500. MTL Microtesting Limited, 1-15 Butts Road, Alton, Hants. GU34 1EN (0420 88022).

DTL/TTL, CMOS PROBE

The 3300A logic probe which has a 1 Megohm input impedance is supplied with two i.c. clips (a single pole and a 16 pole), carrying case and operating instructions.

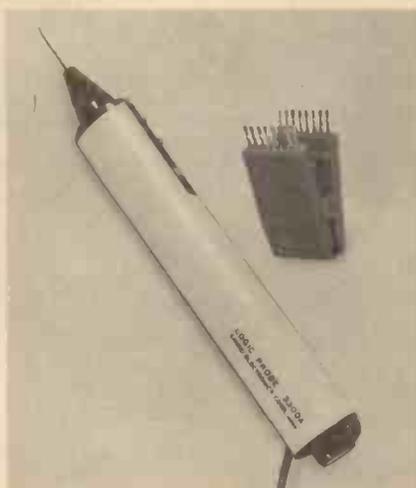The instrument operates on voltages from 5V to 18V d.c. and is protected against reverse p.s.u. connections and input over voltage.



Two l.e.d.s are used to detect high and low logic levels with the TTL threshold being $2.2V \pm 0.2V$ for logic '1' and $0.6 \pm 0.2V$ for logic '0'. The CMOS threshold is 70 per cent of the supply voltage $\pm 0.5V$ (logic '1') and 30 per cent of the supply voltage $\pm 1.0V$ (logic '0').

The price of the 3300A is £14.50 plus VAT and p&p. Watford Electronics, 33/35 Cardiff Road, Watford, Herts. WD1 8ED (9023 40588).

NEW CASES

Three new cases have been added to Vero Electronics range of moulded enclosures.

A desk top case (228 x 216mm) which is ideal for control equipment and keyboards is available in two versions, one with a raised top unit for digital readouts, encoders and other switches. Both have a base section moulded with an integral rear panel to accommodate connectors and plugs. Six mounting bosses are also provided in the base with holes to take self-tapping screws. Top and base sections screw together and the kit comes complete with aluminium front panels and fixing screws.




The other case, 150 x 85 x 45 mm high, has a front panel for identification and controls, which is protected by a raised edge all round. Assembly of components and connections to the front panel is simple as, with the case cover removed, components are accessible from all sides. The front panel is connected to the base by moulded posts and retained by the case cover. P.c.b. mounting pillars are moulded into the base, and a raised end surface is provided for cable grommets or components.

The price of the three cases are £9.50, £7.60 and £4.60 respectively.

Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hants SO5 3ZR (042 15 69911).

DRILL AND DE-BURR

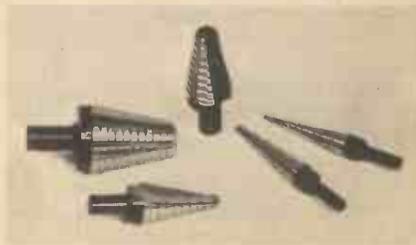The step configuration of these Unibits allows drilling and simultaneous de-burring of a range of holes with one bit. Five bits cover holes from 4mm to 34mm in 1mm or 2mm



steps. Unibits are said to cope with sheet steel, brass, aluminium, copper, plastic and wood. Price from £7.38 inc. VAT, exc. p&p.

Toolrange Ltd., Upton Road, Reading RG3 4JA (0734 29446).


HP-41C

The latest programmable calculator from Hewlett Packard has a 12-character liquid crystal display, alpha-numeric keyboard and a memory which can retain data and programs after the calculator has been switched off. The type of memory can be selected from 448 bytes or 63 data storage registers or any blend of bytes and registers required.

The HP-41C has a total of 130 mathematical, scientific and statistical functions which are identified on the keyboard or can be used by either spelling the name of the function or assigning it to a particular key replacing a function which is not needed in the calculation. Two overlays are provided to enable users to re-label the keyboard with the functions they use most.

For problems in specialised areas such as engineering, aviation, finance, surveying etc. plug in modules are available together with handbooks. Any created programs should be assigned a name and then keyed in and whenever the program name is entered the program is automatically carried out.

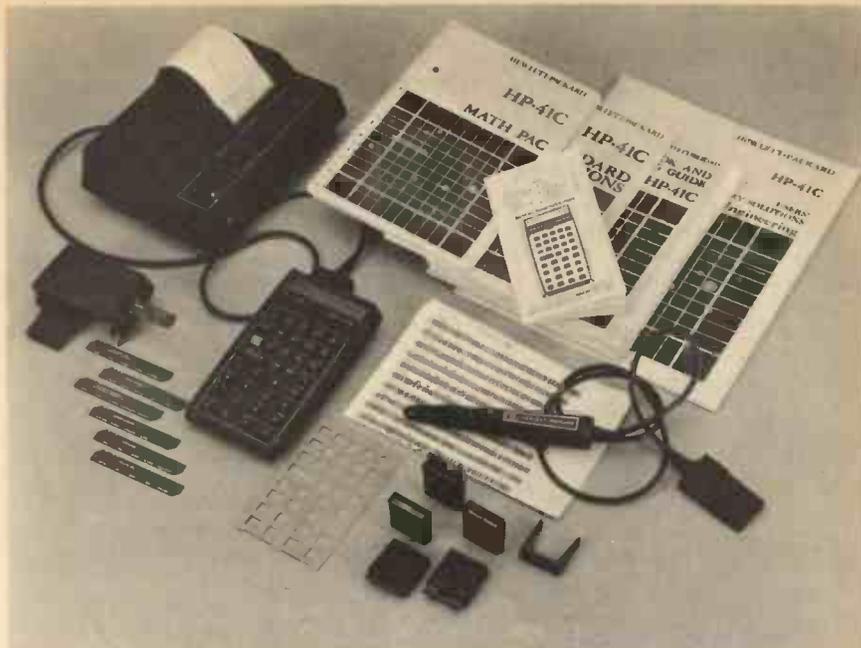Peripheral devices available for use with the HP-41C include: memory modules, magnetic card readers, plotting printer and an optical reader for bar codes. The card reader can be used to record programs which on replay become part of the calculator's memory. The programs on the card can also be instructed




only to execute the program and not allow alterations. The thermal printer can print numbers, letters (upper and lower case), special characters, graphics and produce high resolution plots from data of programs.

The price of the HP-41C is £190, the card reader £135 and the printer £260 plus VAT and p&p.

Hewlett-Packard Ltd., King Street Lane, Wokingham, Berks. (0734 784774)

US CRAZE

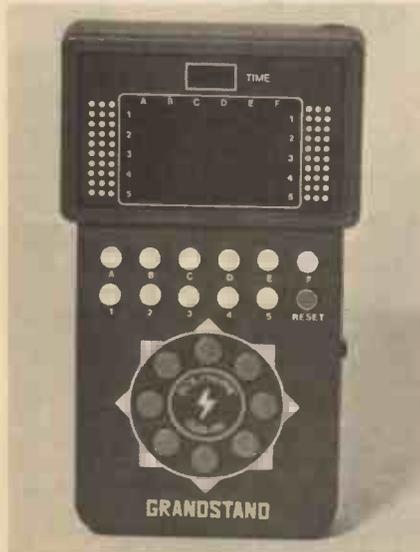As one of the latest crazes in the US at the moment is hand held computer games you won't be surprised to hear that many manufacturers are predicting this Christmas



as the start of the "craze" period for these games over here. Tempus are offering a range of games which includes Digits, a variation of Mastermind or Codebreaker where the player must guess a hidden number in as few attempts as possible.

Amaze-A-Tron which is a maze game for two players who must find their way through a maze using coloured pegs on a 25 key matrix board. There are eight game variations and over one million different mazes available.

The U.F.O. Master Blaser Station is a game in which you shoot down as many U.F.O.s as

possible before they reach your station. The U.F.O.s can change course, disappear or descend in pairs and you can increase the difficulty by increasing the speed of descent.

A hand held version of Solitaire is also available in which you must clear all the lights except one on the display panel by process of elimination. Each game is timed and two speeds are available.

The price of these games vary from £13.95 to £22.50 ex. VAT and p&p. Tempus 19-21 Fitzroy Street, Cambridge CB1 1EH.

PLUG-IN TIMERS

A new range of plug-in timers introduced by Adonis Instruments can be used to time intervals between 1 sec and 100 hours.



Both "delay on energise" or "interval delay" types are available and all types have the facility for "external start" from a remote signal. A range of voltage types are stocked, varying between 12V and 240V with each timer having 2-pole changeover contacts rated at 10A/250V.

Protection against mains transients and reverse polarity connection are built into the

timers and the time period can be set either with the control on top of the case, or fixed and adjusted with an external control.

Each timer fits into standard octal or 1-pin bases and are compatible with many existing types. The price range of the timers is from £15.50 to £18.00 excluding VAT and p&p.

A.I., 70 Broomfield Road, Chelmsford, Essex CM1 1SW (0245 68459).

3½ DMM

The latest DMM from Lascar Electronics is claimed to be the first l.c.d. multimeter with an indefinite "digital hold" facility.

The instrument which is housed in an ABS case with an adjustable carrying handle will give over 2000 hours life from a single battery.



The 0.5 l.c.d. has a built-in battery low indicator.

With a basic accuracy of 0.1 per cent the DMM features 10 voltage, 10 currents and 5 resistance ranges with resolutions of 0.1 mV, 0.1µA and 0.1 ohms. Inputs are via 4mm connectors which are protected against overloads and transients.

The multimeter is supplied complete with battery and operating instructions at a cost of £69.00 plus VAT and p&p.


Lascar Electronics Limited, Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex, SS13 1LH (0268 727383).

CRYSTAL SET

For anyone trying to find a Christmas present suitable for young children that will be both educational and interesting then the answer could be a crystal set. Many of us had our first introduction to electronics through such a set and Home Radio are hoping they will be able to addict youngsters to the hobby with their crystal set which is easy to build and requires no soldering. The price of the set is £2.50 including VAT and p&p. **Home Radio (Components) Ltd., 234-240 London Road, Mitcham, Surrey CR4 3HD (01-648 8422).**

BIMBOARD BUS-STRIP

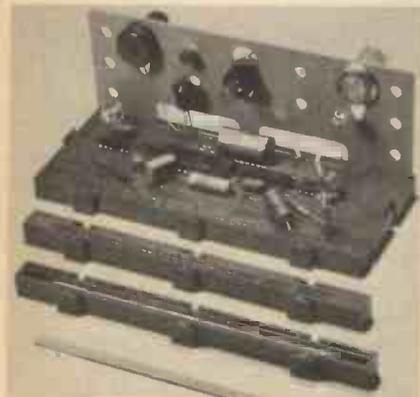To augment their existing range of 0.1in breadboards, Boss Industrial Mouldings have introduced a 2 line Bus-Strip for use where two existing integral rails of a Bimboard are



insufficient for a particular circuit design. The price of the bus is £1.92 excluding VAT and p&p. **Boss Industrial Mouldings Ltd., 2 Herne Hill Road, London SE24 0AU.**

OPTOELECTRONIC SHORTFORM

Optron, the US specialist manufacturer of optoelectronic devices whose products are handled exclusively in the UK by Norbain Electro-Optics Division has just brought out a new shortform catalogue giving details of its latest optoelectronic emitters and sensors. They range from phototransistors, infrared light emitting diodes, and matched emitting diodes and phototransistors to photodarlingtons and photodiodes.

Norbain, Electro-Optics Division, Norbain House, Arkwright Road, Reading, Berkshire RG2 0LT (0734 864411).

NEOSID

Neosid Limited have recently established a new outlet to cater for the amateur constructor.

A broad selection of the parent company's products are included in their new Small Order Catalogue, which covers a full range of ferrite components i.e. beads, screw cores, rods, E, I and U cores, also coil assemblies, plastics formers and trimming tools.

The catalogue is available free of charge from **Neosid Small Orders, P.O. Box 86, Welwyn Garden City, Herts, AL7 1AS.** (Please send stamped addressed envelope.)

PANEL TIME

Have you ever wanted an l.c.d. clock to mount on the front panel of a project, amateur transceiver, teletext control box?

Ambit International are now stocking a miniature panel clock that can display time,



day and date. The unit is quartz controlled, has a back light, and an alarm function to drive a bleeper or other indicator. Running consumption is 6µA, accuracy is within ± 2.5 minutes per year, and height of the characters is up to 0.5in. The display shown has a character height of 0.25in. Price is £10.60 inc. VAT and p&p.

Ambit International, 2 Gresham Road, Brentwood, Essex, CM14 4HN.

FREQUENCY SYNTHESISER


The FS-1B is a frequency synthesiser control unit module, comprising input prescalers, swallow counter, programmable divider, switchable filters and clock buffer.

It is programmed from a three line connection (clock/data/enable) with a 15 bit word that determines the reference frequency and output frequency of the VCO connected in the phase locked loop.

Frequencies in the range 20kHz to 200MHz may be programmed in conjunction with either discrete switch entry, hardwiring or simple computer control. A simple BASIC program

CSC CASE

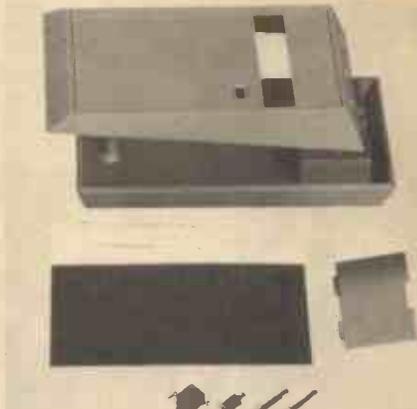The new hand-held case from CSC has been designed to house small, portable electronic systems such as calculators, counters, remote control units, communications devices and portable meters etc.



Measuring 76 x 152 x 38mm the case comes complete with assembly screws, antenna connector, red plastic front fascia panel, sub-miniature jack connected to a battery snap connector and a battery compartment. There is sufficient room for keyboards, speakers, microphones or controls on the front panel.

The price of the case is £3.00 ex. VAT and p&p. **CSC, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.**

exists to provide facilities for LF/MF/HF/VHF tuning options, so that owners of NASCOM, PET and similar systems may readily operate the module in conjunction with a voltage tuned radio having a buffered local oscillator output.

Various reference frequencies are available, both in conjunction with an on-board selection in the data control, and the use of different frequency crystals.

Priced at £24.95 in one-off quantities, the FS-1B is available from **Ambit International, 2 Gresham Road, Brentwood, Essex CM14 4HN (0277 227050).**

PE AT BREADBOARD

'79

**DECEMBER 4th-8th AT ROYAL
HORTICULTURAL HALLS, ELVERTON ST.,
WESTMINSTER**

We will be exhibiting a range of projects and hope to include: Ultrasonic Alarm; Solid State Car Instruments; EPROM Programmer; Ultrasonic Cleaner; Teletext; Digital Frequency Meter; Compukit UK101 with peripherals; Short Range Communication Transmitter and Receiver; Modem; Pushbutton Car Radio; PE Diamatic and perhaps a few more forthcoming attractions. Interested? Then come along and see for yourself.



A computer range from £500

The number one micro-computer in Britain today, selling more than 1,000 per month!

The Commodore Pet computer range is versatile and affordable. Programs can be written in Basic, the easiest computer language to learn. There is also machine language accessibility for professionals.

The Pet is a fully expandable system, peripherals being available for many specialist applications, (peripherals such as dual drive floppy discs and printers).

There are already over 300 standard programs,

tested and in use in commercial, scientific, educational and many other applications throughout Britain. The Pet is a portable and professional computer that operates by plugging into a normal 13 amp mains. Service and advice is readily available through the nationwide network of dealer outlets.

For a demonstration contact your local dealer—some of whom are shown here. In case of difficulty contact Consumer Information Dept (PE2),



commodore
We made small computers big business.

Commodore Systems,
360 Euston Road,
London NW1.

Associated Commodore dealers:

BIRMINGHAM

Camden Electronics 021-773 8240
CPS (Data Systems) 021-707 3866
Taylor Wilson Systems Knowle 6192

BOLTON

B & B Consultants 0204-26644

BOURNEMOUTH

Stage One Computers 0202-23570

BRADFORD

Ackroyd Typewriter & Adding
Machine Co 0274-31835

BRENTWOOD

Direct Data Marketing 0277-229379

BRISTOL

Bristol Computer Centre

0272-23430

Sumlock Tabdown 0272-26685

CAMBRIDGE

Cambridge Computer Store

0223-68155

CARDIFF

Sigma Systems 0222-21515

COLCHESTER

Dataview 0206-78811

DERBY

Davidson Richards 0332-366803

DURHAM

Dyson Instruments 0385-66937

EDINBURGH

Micro Centre 031-225 2022

EXETER

A.C. Systems 0392-71718

GRIMSBY

Allen Computers 0472-40568

HEMEL HEMPSTEAD

Data Efficiency 0442-57137

HOVE

Amplicon Electronics 0273-720716

LEEDS

Holdene 0532-459459

LIVERPOOL

Aughton Automation

051-548 6060

Cortex Computer 051-263 5783

Dams Office Equip. 051-227 3301

LONDON E2

Ragnarok Elec Sys 01-981 2748

LONDON EC1

Sumlock Bondain 01-253 2447

LONDON N14

Micro Computation 01-882 5104

LONDON NW4

Da Vinci Computers 01-202 9630

LONDON SW14

Micro Computer Centre 01-876 6609

LONDON W5

Adda Computers 01-579 5845

LONDON WC1

Euro Calc 01-405 3113

LONDON WC2

TLC World Trading 01-839 3893

MANCHESTER

Cytek (UK) 061-832 7604

Executive Reprographic

061-228 1637

Sumlock Elec Svs 061-834 4233

MATLOCK

Lowe Electronics 0629-2817

MORLEY W. Yorks

Yorkshire Elec Svs 0532-522181

NORWICH

Sumlock Bondain 0603-26259

NOTTINGHAM

Betos (Systems) 0602-48106

OXFORD

Orchard Electronics 0491-35529

PLYMOUTH

JAD Integrated Svs 0752-62616

PRESTON

Preston Computer Ctre 0772-57684

READING

CSE Computers 0734-61492

SOUTHAMPTON

Business Electronics 0703-738248

Symtec 0703-37731

Xitan Systems 0703-38740

SUNDERLAND

Tripoint Ass Systems 0783-73310

WOKING

PPM. Brookwood 80111

Petalect 04862-69032

YEOVIL

Computerbits 0935-26522

NORTH SCOTLAND

Thistle Computers Kirkwall 3140

NORTHERN IRELAND

Medical & Scientific Lisburn 77533

**SOLAR QUARTZ
ALARM CHRONO**

6 digits, 5 flags
22 functions.
Solar panel with
battery back-up,
6 basic functions,
Stop watch to 12 hrs.
69.9 secs. in 1/10 sec.
steps.
Split and lap timing
modes,
Dual time zone,
Alarm, Back light,
Fully adjustable bracelet



VT11
7mm thick

ONLY £19.95
(inc. VAT & P&P)

Same as special offer

TELENG SYSTEM - £89.95
COMP CARTRIDGES - £12.95
PHILIPS G7000 - £149.95
11 Videopack - £12.95 each
ATARI VCS - £159.95
21 Game Program £14.95 each
MATTEL INTELEVISION
builds into Computer £179.95
Cartridges - £15.95 each



**BIGGEST
RANGE
OF VIDEO
GAMES
- EX STOCK**
FULL
DETAILS
ON
REQUEST
**RADOFIN
TELETEXT
DECODER
£199.95**

**SEIKO MEMORY
BANK**

Calendar watch M354
Hours, mins., secs..
Month, day, date in
12 or 24 hr. format
all indicated continuously
Monthly calendar display
month, year and all dates
1 or any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advance.
2 year battery life.
Water resistant
List Price £130



ONLY £74.95
(inc. VAT & P&P)

**LCD
ALARM
with Snooze**

24hr alarm,
Hours, mins, secs,
day, month, date,
back light,
auto calendar,
adjustable
s/s bracelet.



VT10

ONLY £12.95
(inc. VAT & P&P)

Same day despatch

**LAMBDA ALARM
CHRONOGRAPH**

(same as PE offer)
6 basic functions
stop watch to
12 hours 59.9 secs.
in 1/10 sec. steps.
Split and lap
timing modes.
Dual time zones.
Alarm



VT14

ONLY £19.95
(inc. VAT & P&P)

Same day despatch

BELTIME-PICOQUARTZ

Microprocessor
Alarm Chrono

2 alarms,
2 chronos,
Hourly chimes,
Mineral glass,
12 or 24hr. clock,
5 languages for day,
1/100th sec. chrono,
Countdown alarm,
Back light.



VT1B

ONLY £37.95
(inc. VAT & P&P)

**MUSICAL ALARM
CHRONO - plays
melody on alarm**

6 digit, 11 function,
Count down alarm,
Dual time zone,
1/100th sec. chrono,
2 piece s/s bracelet



VT20
8mm thick

ONLY £25.95
(inc. VAT & P&P)

Same day despatch

Ladies Cocktail Watches - £12.95 Boys 5F LCD - £7.95



12 month guarantee. Cheques or P.O.'s or telephone Card no. to
DETAILS ON REQUEST. EXCHANGE ON CARTRIDGES.
CARTRIDGES SAME DAY DESPATCH. MONEY BACK GUARANTEE
OFFERS SUBJECT TO AVAILABILITY.
ALLOW 7 DAYS FOR DELIVERY

VIDEOTIME Products
56 QUEENS RD, BASINGSTOKE, HANTS. RG21 1RER
TEL. (0256) 56417 & 26620 TELEX 858747

Beckman 3020 The multimeter that defies competition



This is not just another new multimeter. Backed by over 40 years' experience and worldwide sales, it set out to beat the competition on virtually every count. To whet your appetite, here are just a few of the features that set it apart.

Accuracy—long term high accuracy ensured by a highly stable band gap reference element and thin-film resistors.

Reliability—total number of electronic parts reduced to less than 40 to give real reliability.

Portability—easy to hold, stand or hang, it weighs only 453 g (16 oz).

Continuity check—continuity can be checked in less than 100 milliseconds.

10A current range—up to 10A ac or dc without special adaptors.

Overload protection—voltage inputs and resistance ranges comprehensively protected.

Long battery life—9V transistor battery provides up to 2000 hours continuous operation, two years typical use.

Send for the full technical specification and see how the 3020 defies comparison—pound for pound—with any other multimeter on the market.

BECKMAN

Beckman Instruments Ltd
Sales and Marketing Organisation
Queensway, Glenrothes, Fife, Scotland, KY7 5PU.
Telephone: (0592) 753811 Telex: 72135

Semiconductor UPDATE...

FEATURING

Z8000

7110

AY-3-1350

R. W. Coles

CAPTAIN ZILOG

Zilog would like to draw your attention to their brand new microprocessor, the 16 bit Z8000.

Interesting electronics engineers or hobbyists in yet another new microprocessor will probably be difficult, and the fact that a comparable device from Intel, the 8086, has been around for several months won't make things any easier.

Technically, the Zilog Z8000 is a big leap forward, with the power of a minicomputer and an address range of up to 8 megabytes. It is probably more powerful than the Intel competition, but it seems that it will soon itself be upstaged by an even more powerful device from Motorola, the 68000. All this has put Zilog in the awkward position of not being the first and not being the best either, a situation which called for an expensive publicity campaign to broadcast the news about the Z8000 before all those sockets are gobbled up by other 16 bit devices.

Now, one way to tackle the publicity task would be to commission some technical articles and advertisements extolling the virtues of the Z8000 architecture, but Zilog wanted to get all electronics engineers interested and there's only one way to do that, isn't there? Yes of course, they gave the Z8000 its very own comic book! Enter Captain Zilog, alias systems designer Nick Stacey, who is given the gift of "Zilog power" by an extra terrestrial being who hauls him bodily through his VDU screen.

Moulded in the fine tradition of Superman and Captain America, Captain Zilog hurls himself into adventures such as "The doom of Doctor D" and "Battle beneath the architecture" in a desperate (and of course successful) attempt to foil the dastardly plans of Doctor Diabolicus who intends to conquer Earth with the aid of his super main-frame computer. Liberally laced with comments such as: "Stick it in your Index Register Diabolicus" or "Dancin' data" and "Leapin' logic", the new Zilog comic book is a must, if you can get one!

This is certainly a novel way to publicise a new device, being less distracting than the "sex" alternative, and much less boring than a ten page sheet! I found after reading the comic book that I knew quite a lot about the Z8000.

BIG BUBBLE

The future bulk memory requirements of the Zilog Z8000 and all the other fourth generation microprocessors will probably not be satisfied by present floppy disc systems because their electro-mechanical

technology is bulky, fragile, and likely to get more expensive rather than less as time goes by. The advantages of solid-state memory are self evident, and the bulk memory requirement will soon be satisfied by magnetic bubble memory chips which are compact and have no moving parts.

Bubble memories rely on the non-volatile storage and propagation of magnetic domains within a synthetic garnet substrate, and are thus quite different in their operation to conventional semiconductor RAM devices. Despite the differences in operation, bubble memories are made using the same basic techniques which have been developed for the other LSI technologies, and this has attracted many of the biggest semiconductor manufacturers including Intel, Texas Instruments, Rockwell, and Plessey in the UK.

Bubble memories are essentially serial in operation (like shift registers) rather than parallel (like RAM devices) and the speed at which the bit domains can be moved is limited to a few tens of kilohertz. Together, these factors make the access time to a particular location very much larger than the few hundred nanoseconds of today's RAM chips, but this is more than made up for by the huge amounts of data which can be stored by a single device. One of the latest bubble memory chips, the 7110 from Intel, stores 1 megabit, or looked at another way, 128 kilobytes, just think how many RAM chips you would need to handle that!

To speed up the access to any particular location, the 7110 is organised internally as 4096 separate shift registers, each of 256 bits. Two registers are used together to form a 512 bit page and on-chip processing treats each page as 64 8 bit bytes to achieve an average random access time of 40 milliseconds. That may be a lot slower than a conventional RAM but it's faster than a floppy disc and a lot more compact and reliable. A single 7110 could replace a complete mini-floppy drive in many applications.

RING-A-DING-DONG

A new single-chip tunes synthesiser, which can be programmed to generate up to 28 different tunes, has been introduced by General Instrument Microelectronics Limited.

Designated the AY-3-1350, the 28-lead NMOS device operates from a single 5V power supply, and is suitable for use in toys, musical boxes, doorchimes and other "novelty" products.

The standard circuit is pre-programmed with 25 short tunes plus 3 simple chimes,

but this may be altered to suit the application. It is possible for instance, to program just a single tune consisting of up to 251 notes. The chip does offer great flexibility to designers, as it can also generate tunes from data held in external PROMs.

In addition to its programming options, the AY-3-1350 may operate in a number of different modes, making it suitable for a wide variety of different applications. In a doorchime for instance, it can be connected to play any one of 25 pre-selected tunes from the front door bell push, with one of 5 tunes from the back door. In addition a third bell push can be wired to play a simple chime. All the tunes would be selected by switches or matrix board inside the chime cabinet.

A further possibility is to connect the circuit to a number of different bell pushes on each door. This might be useful for telling which different tradesmen are calling, or which member of the family is required at the door. Mother, father, brothers and sisters could each have their own particular "call" tune. In addition further variations could be made for back door, side door, or even a bell push for alarm purposes in an apartment used by an elderly relation.

Applications exist in low cost paging systems, where key personnel are each allocated one tune. A brief tune played over loudspeakers in a noisy factory would be much easier to recognise than a spoken name.

The circuitry may be connected so that there is virtually no power consumption when in the stand-by condition. When any bell push is activated the circuit plays a tune and then automatically powers down again to conserve batteries—even if the visitor keeps his finger on the bell push. Releasing the button and repressing would cause either the same tune to play again, or the next tune to be selected, depending on the precise operational mode of the device. Alternatively, the circuit may be wired to replay tunes over again until the button is released.

With the addition of an external ROM or PROM the standard AY-3-1350 will play almost any tune or tunes desired. These could be 28 tunes averaging 8 notes each or one tune of up to 251 notes. This would provide about 1-2 minutes worth of music.

The pitch, tone and speed of tunes played may be independently set by simple external components. These may be either preset or brought out as potentiometers as a user control. Either switch closures may be used to trigger the device or a capacitive touch switch using a few external interface components.

EPROM PROGRAMMER

PART 1

A.A. BERK B.Sc. Ph.D.

THE EPROM programmer is a memory-mapped peripheral for the 2708 family of Erasable Programmable Read Only Memories (EPROM's) and programs at about the maximum possible speed (around 2 minutes). The p.c.b. contains its own power supply giving +12V, -5V, +27V, and only requires +5V and a 9-0-9 volt transformer. On board, there is 1K of RAM for storing information to be transferred to the EPROM. The EPROM may be read before or after programming for verification, and used *in-situ* as a normal 1K block of Read Only Memory. The programmer thus effectively expands the host system by 2K of memory (1K of EPROM and 1K of RAM), with the added facility of being able to reprogram the EPROM section. Connection of the machine is simple and almost identical to the PE VDU connections.

Eleven Address Bus Lines (A0-A10), eight Data Bus Lines (D0-D7), a Read/Write line and some address decoding logic is all that is required. Interface to the COMPUKIT UK 101 and many other machines requires just a couple of d.i.l. plugs. The COMPUKIT would allow the necessary routines to be written in BASIC. A minimal MPU system containing the machine is shown in Fig. 1.

Use of the programmer is restricted to writing the desired target program or data into the 1K of on-board RAM, running and checking it, and then switching on the programmer which then takes around two minutes to copy the RAM contents onto EPROM. The machine automatically hands EPROM and RAM back to the MPU system.

EPROM THEORY

Each individual cell within the 2708 contains a "floating gate", which is able to collect a charge from a "pumping" pulse-train produced by a programmer. When sufficient charge has been accumulated within this completely insulated storage element, the cell, initially showing a "one", will return a "zero" along its data line when read.


The 2708 family members have a quartz window in the upper surfaces of their packages. Through this, a strong ultra-violet light may penetrate to knock the electrons in the storage elements out of their shallow energy levels and allow them to leak away via the substrate.

This clears the cell back to a "one". The organisation of the 2708 causes 8 cells (one byte) to be read and programmed at a time, hence requiring normal Address and Data lines.

To program the EPROM, the programmer produces a succession of addresses along A0-A9, and, for each, presents the data to be programmed along D0-D7. The EPROM thus starts, after erasure, with FF (8 "ones") in each location.

The requirements of the 2708 family demand that *all* locations be presented with data a large number of times during the programming sequence. The number of such complete addressing cycles is determined by the speed of operation.

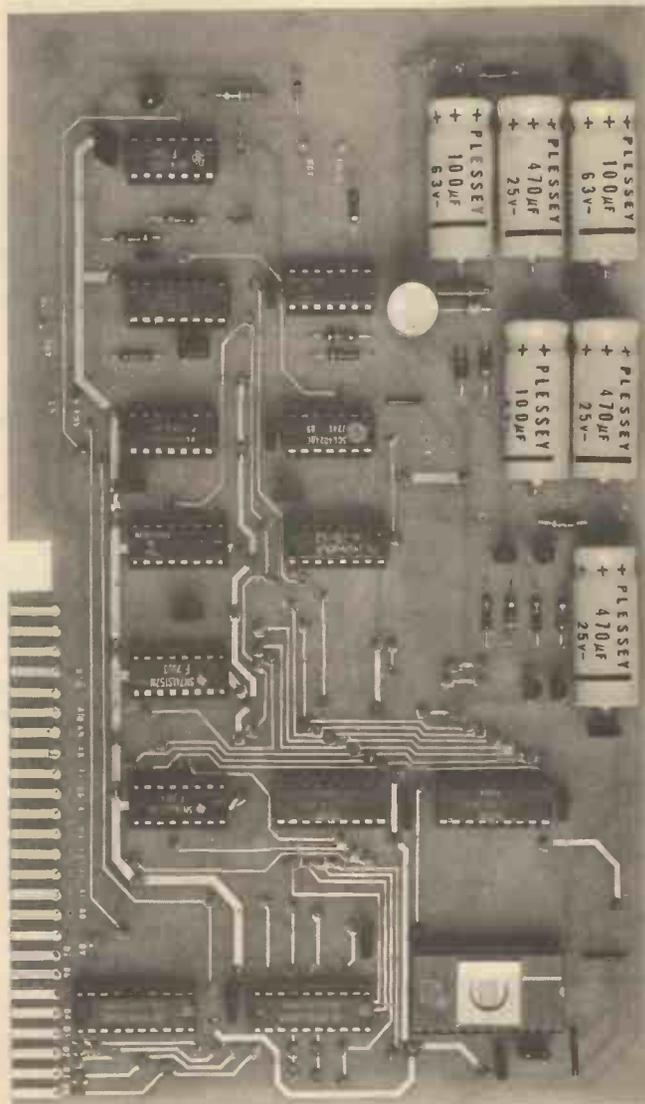The Block and Connections diagram shows a typical Read Only Memory device with the addition of a Programming pin. This pin is pulsed up to +27 volts during programming.



The \overline{CS}/WE pin is a normal chip select except when programming, when it is held at +12 volts. The timing Diagram (Fig. 3), shows the signals necessary to program the 2708. It should be emphasised that the programming cycle consists of cycling through all 1024 memory locations *N* times and presenting the data to be stored over and over again. The sequence is as follows. \overline{CS}/WE is switched to +12V, the first address and data are presented and $>10\mu S$ later, pin 18 is pulsed up to +27V. These conditions are held for 0.1 to 1ms (0.5ms for the machine presented here) and then pin 18 drops to zero and the next address and data loaded. The cycle from address 0 to address 1023 thus takes a little more than half a second.

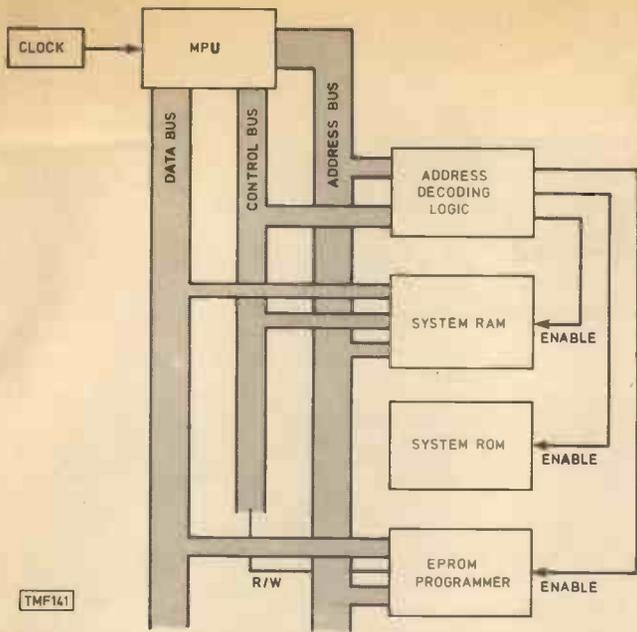


Fig. 1. Minimal system containing EPROM Programmer


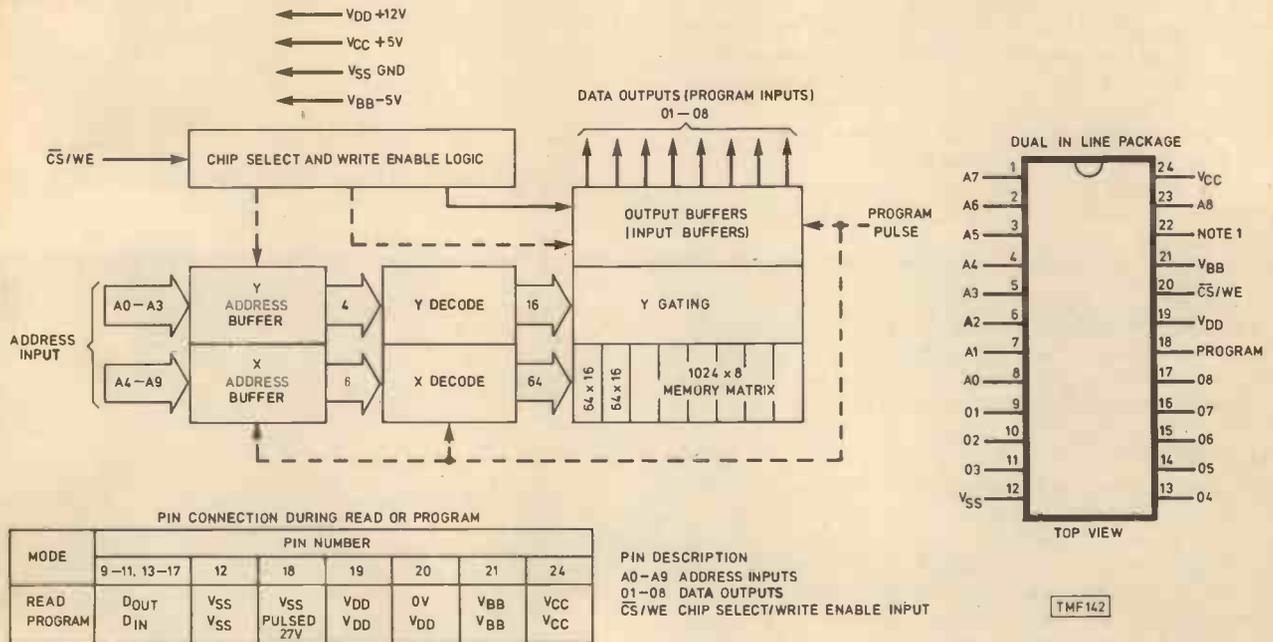


Fig. 2. The 2708 EPROM

Fig. 3. Program timing diagram

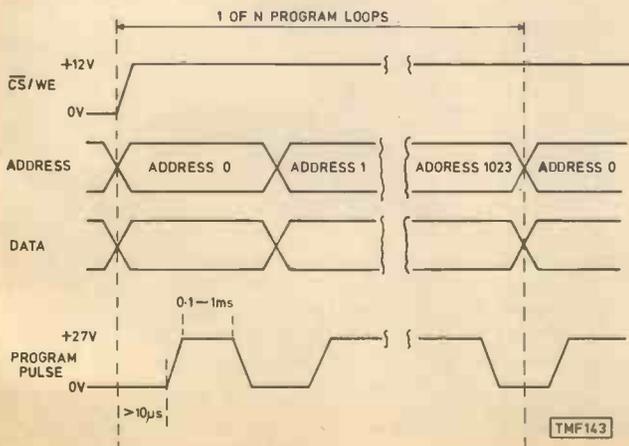

TMF143

This entire sequence is then repeated a number of times. The total number, N , of such loops is between 100 and 1000 (possibly more) depending upon the width (t_p) of the program pulse (+27 volts). The formula for determining N is: $N \times t_p > 100\text{ms}$. Thus, for 0.5ms, N is a minimum of 200. The total programming time for this number is slightly over 100 seconds.

The EPROM starts with its locations containing FF, thus if the programmer presents just FFs to the EPROM, it will retain its "erased" state. Even though each memory location must be accessed during programming (many times in fact), those presented with FF will remain untouched. Thus, a block of the EPROM may be programmed selectively without affecting the rest of the device. In fact, this is true of an EPROM already containing any other block of information. Contents of that block, whatever they may be, remain unaffected by the programming procedure as long as FF is presented to each of its locations during the cycles.

Indeed, a single bit in any given location can be set to zero selectively by presenting 1's everywhere else during programming.

It should be noted that the machine described here is *not* suited to the *single supply* 2716, nor types of EPROM other than 2704, 2708 and the multi-supply 2716. The reason for this is that the cycle-timing diagram requirements are quite unique to this family.

Fig. 4 shows the hardware set-up of the programmer. The heart of the device is in the timing control block. It is here that the cycles of sequentially presented addresses are produced, as well as the correct repetition rate and number of complete loops necessary.

The counter-produced addresses are switched over to the RAM and EPROM by the Address Bus switch after a Program Request signal is received. A Ready line, and i.e.d. on the p.c.b., signals when the programming cycle is in progress.

The RAM is held in the READ state, and the Counter addresses RAM and EPROM sequentially. The RAM (which holds the desired program) places the data on the Data Bus and hence onto the input pins of the EPROM. The timing control then waits a few microseconds and switches the 27 volt level on to the Program pin of the EPROM for 0.5ms.

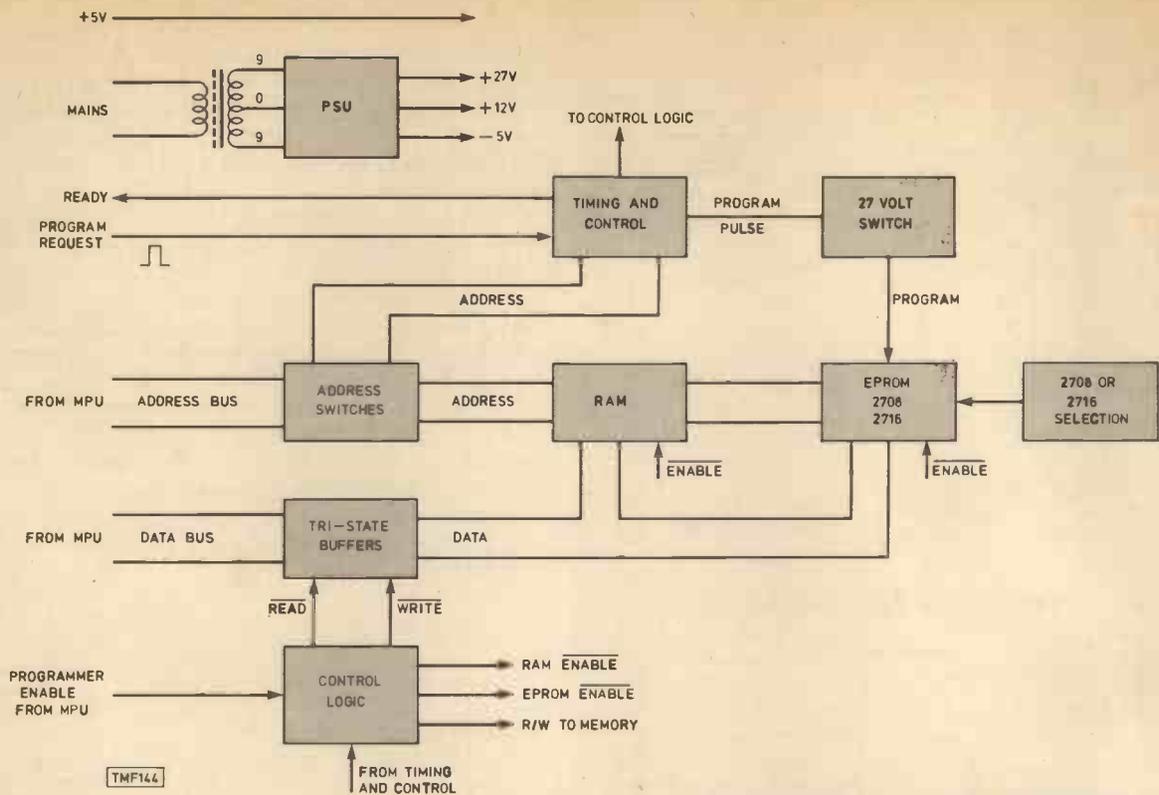


Fig. 4. Block diagram of EPROM Programmer

COMPONENTS . . .

Resistors

R1	1k ½W
R2	1k
R3	47
R4	150
R5	100
R6, R9	2k2 (2 off)
R7	15k
R8	8k2
R10, R12	10k (2 off)
R11	33k

All resistors ¼W 5% unless otherwise stated.

Capacitors

C1, C2, C4	470µF/25V elect (3 off)
C3, C5, C6	100µF/63V elect (3 off)
C7	1n ceramic
C8	100n ceramic
C9	10n ceramic
C10	33µ elect
C11 upwards	100n Supply decoupling

Transistors and Diodes

D1-D4	1N4004 (4 off)
D5, D6	1N914 (2 off)
D7	27V/1W Zener
D8	Any i.e.d.
TR1, TR3	BC549 (2 off)
TR2	BC559

Integrated Circuits

IC1	7474
IC2	4024
IC3	4040
IC4	2708 or 2716 EPROM
IC5, IC6	2114 (2 off)
IC7, IC14	74LS244 (2 off)
IC8, IC13	7400 (2 off)
IC9	74123
IC10-IC12	74LS157 (3 off)
IC13	79L05
IC14	78L12

Sockets

14 pin	4 off
16 pin	5 off
18 pin	2 off
20 pin	2 off
24 pin	1 off

Miscellaneous

T1	Mains transformer. Sec. 9-0-9V at 1A
S1	Double pole single throw
	Pins for through-board connection
	Double sided 0.156in. pitch 50-way edge socket
	Printed circuit board

Constructor's Note

Kit of parts, including double-sided, drilled and tinned p.c.b. (not plated-through), is available from: **Modus Systems Ltd., Dept. EP, 29a East Cheap, Letchworth, Herts. SG6 3DA. £37.30 VAT + p.p. inc. P.c.b. £8.45 inc.**

The kit excludes T1, S1, IC4 and edge socket, but sockets are included for all i.c.s.

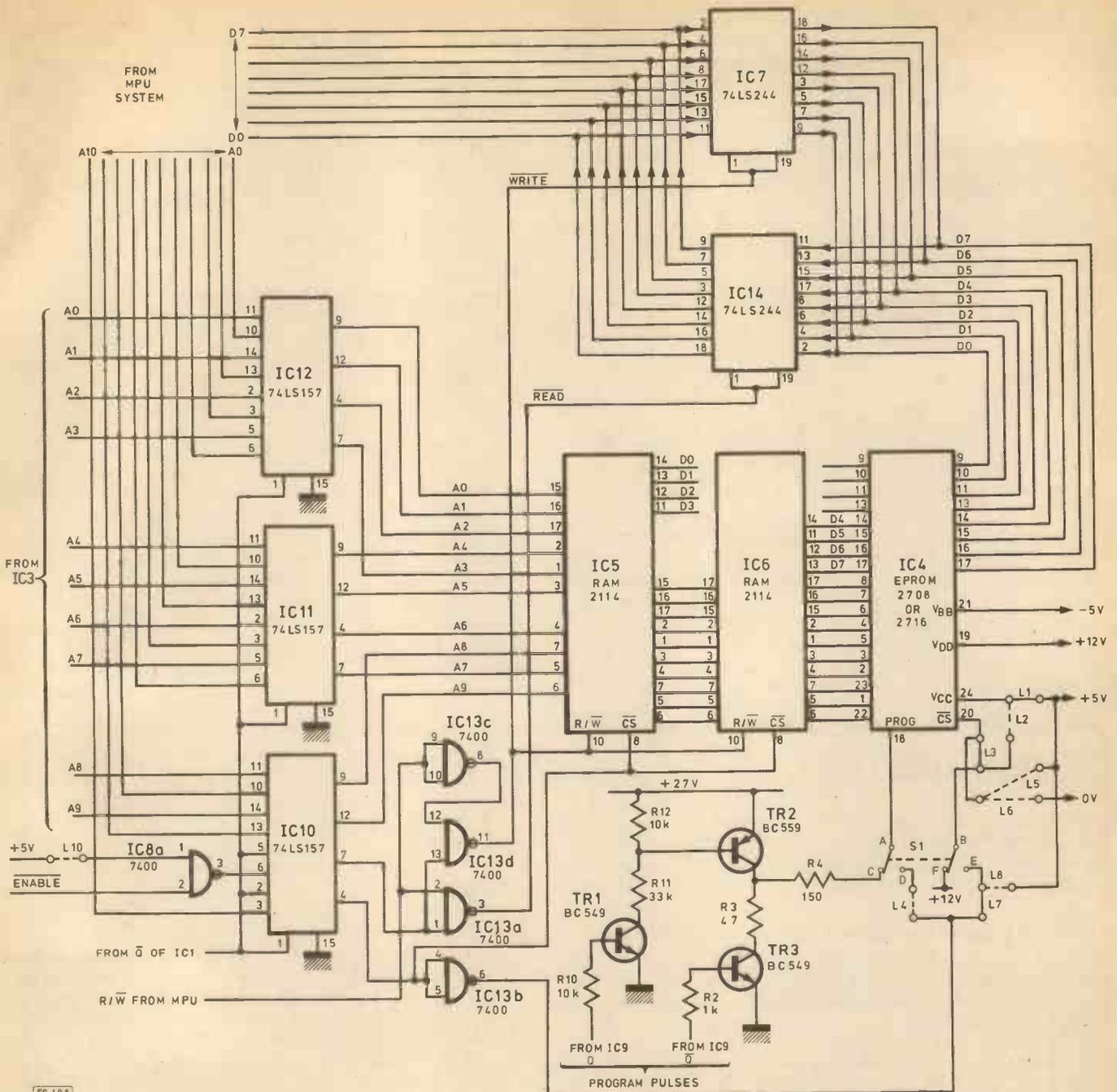


Fig. 5. Memory and switching of the Programmer. S1 is in the "Program" position. Links are shown connected for 2708

The cycles continue until complete and the EPROM and RAM are then handed back to the MPU system for normal use.

It should be clear then, that the role of the MPU system hosting the process is to provide for the RAM, programs or data to be "burned" into EPROM. To this effect, the RAM should be filled with FFs beforehand, so that any unused RAM space does not affect the EPROM.

The RAM and EPROM form a normal part of the MPU's address map, such that programs and data may be stored in either or both for running and use *in-situ*. The only time the memory is not available to the MPU is *during* programming. When the tri-state buffers are switched off, the data Bus of the MPU system is disconnected from the machine.

Last month, in the final part of the COMPUKIT UK 101 article, "plug-in" methods of expanding the machine utilising the upper part of the 2114 memory were described. This is the most convenient method of attaching a programmer and is described next month.

POWER SUPPLY


The Power Supply Unit (Fig. 6) gives all necessary power levels except for the +5V which is usually available from the MPU system. An external transformer with a secondary of 9-0-9 volts at 1 Amp is necessary for the PSU and may be purchased from Modus Systems Ltd., who can also supply the p.c.b. and full kit.

As a final note on the above, it is possible to perform the setting of RAM to FF by hardware. All the facilities for stepping through memory exist on the programmer, and it is just a question of keeping the EPROM disabled, the RAM in the write-state, the Bus buffers tri-state and all Data lines to a logic "one". This will fill the RAM with 1s as IC3 cycles through once.

Next month, the final part covers the rest of the hardware, p.c.b. layout, construction and hardware interfacing to your system.



Fig. 8. Flow diagram to fill the RAM with FFs

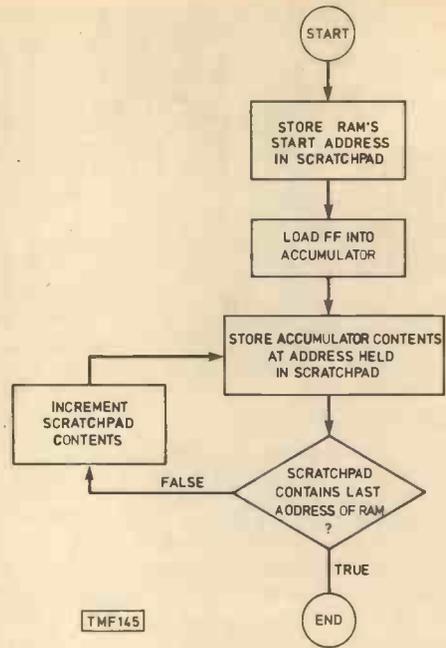

The EPROM Programmer may be run from the UK101

Countdown

Organisers: Please send details of exhibitions, club open days and other events to Mike Abbott at least six weeks in advance. Inclusion will be subject to space etc.

- Electronics 79**—Nov. 20-23. Olympia, London. ☎ 021 705 6707.
- Video Rights 79** (conference)—Nov. 26, 27. Cafe Royal, London. Details: Nord Media ☎ 01-629 9381.
- Breadboard 79**—Dec. 4-8. Royal Horticultural Halls, Westminster. Details: Trident International Exhibitions. ☎ 0822 4671.
- IBM Hardware Selection**—Dec. 5, 6. Skyline Hotel, London Airport. Details: Online.
- BEX** (Business Equipment Exhibition)—Feb. 6-7. Queens Hall, Leeds. Details: Douglas Temple Studios. ☎ 0202-20533.
- BEX**—Feb. 20-21. The Pavilion, Bournemouth. Details: Douglas Temple Studios.
- IEA/Electrex**—Feb. 25-29, 1980. National Exhibition Centre, Birmingham. Details: Industrial and Trade Fairs Ltd. ☎ 021-705 6707.
- Viewdata '80**—March 26-28. Wembley Conference Centre, London. Conference and exhibition. Details: Online Conferences Ltd. ☎ Uxbridge (0895) 39262.
- Computer-Aided Design** (conference and exhibition)—March 31-April 2, 1980. Metropole, Brighton. Details: Organisers, CAD 80. ☎ 0483 31261.
- Seminex**—April 14-18. Dept. Physics, Imperial College, London.

- Communications '80**—April 14-18. National Exhibition Centre, Birmingham. Details: ITF Exhibitions. ☎ 021-705 6707.
- Electronic Test and Measuring Instrumentation**—April 22-24, 1980. Wythenshaw Forum, Manchester. Details: Trident.
- International Conference On The Electronic Office**—April 22-25, 1980. London Penta Hotel. Organised principally by the Institute of Electronic and Radio Engineers. 99 Gower St., London WC1E 6AZ.
- All-Electronics Show (1980)**—April 29-May 1, Grosvenor House, Liverpool. Exhibition and seminars, with the co-operation of Liverpool.
- The Mersey Micro Show**—April 30, May 1, 2, 1980. Adelphi Hotel, Liverpool. Exhibition and seminars, with the cooperation of Liverpool University. Details: Online.
- The 1980 Microcomputer Show**—July 10-12. Royal Lancaster Hotel, London. Details: Online.
- IBC 80**—Sept. 20-24. Metropole Centre, Brighton. Details: Secretariat, IEE, Savoy Place, London WC2R 0BL.

POINTS ARISING

SIX CHANNEL MIXER (September 1979)

Switch S3b, terminal 4, should be connected to terminal 4 of switch S3a and not to 0V.

DIGITAL TEMPERATURE CONTROLLER (October 1979)

The values for C8 and C9 should be transposed in the circuit and components list.


PATENTS REVIEW...

Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent

Price 95p each


PRECIPITATION SENSOR

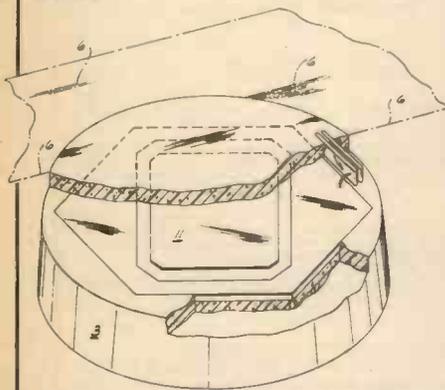British patent application 2010486 from Surface Systems Inc. of Missouri, USA (applied for under the new laws and dating back to December 1977) describes a module for automatically sensing wet and icy conditions on a road or airport runway surface.



The module can trigger a visible or audible alarm, for instance light up a danger sign, when a surface becomes slippery and dangerous; or a series of sensors can provide air traffic control with a continuous readout of airport runway conditions.

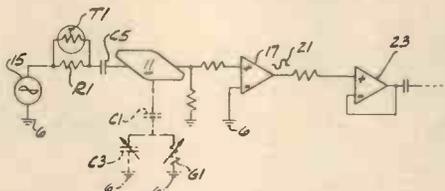A block 3 of epoxy resin material, with silica glass or sand filler for strength and resistance to wear, is embedded in the surface 6 to be monitored. A square electrode 11 of metallic foil is encapsulated in the block thereby providing both capacitance and conductance paths to surface 6.



In the circuit diagram the capacitance path is represented by phantom capacitors C1 and C3, and the conductance path by phantom resistor G1. A constant-voltage oscillator 15 and capacitor C5 supply electrode 11 with a sine wave signal at a

frequency of around 5kHz. The signal is applied via resistor R1 and thermistor T1 to compensate for any small change in the value of capacitor C1 caused by temperature. Because a relatively low frequency sine signal is used, oscillator 15 can be placed up to 500 feet from sensor electrode 11 without significant loss.

Whenever there is water or ice precipitation the sensor surface is connected capacitively and conductively to the surface 6. This causes a significant loss of current from electrode 11 to surface 6. The amplitude of the signal appearing at the input of amplifier 17 is thus a function of the change in the capacitance and conductance between sensor electrode 11 and surface 6. The output of amplifier 17 therefore decreases as precipitation accumulates on the sensor. Precipitation circuit 23 provides an indicator or alarm trigger signal when the output signal 21 of amplifier 17 falls to a predetermined level.

In one modification of the invention a delay circuit is incorporated to ensure that the temporary removal of ice or water from the sensor block by passing vehicles does not affect the overall reading.

LIQUID MAGNET

British patent application 2009414 from the French company Societe Nationale D'etude et de Construction de Moteurs D'aviation was filed under the new patent laws and dates back to November 1977.

Although the invention is concerned primarily with a magnetic means of measuring the thickness of passageways inside gas turbine blades, it is clear that the principle described has much wider applications. The specific aim of the invention is to check that

the cooling passages inside a turbine blade are accurately formed, with adequately thick walls. To achieve this the passages are temporarily filled with ferro-magnetic fluid.

This material, which was developed (like so many others) for use in space, is a suspension of magnetic particles in liquid which behaves like a fluid magnet. Because ferro-magnetic fluid is expensive, it is introduced into the passageways and withdrawn after use by a simple piston and cylinder arrangement.



A probe 11, like a metallic pencil, is wound with a coil 12 on a core 13. This coil forms one branch of an a.c. bridge 14, of which the other branches are formed by potentiometers 15, 16 and 17. The bridge is supplied at a first diagonal by a.c. from generator supply 18, 19 and a measuring

apparatus 20, for instance a meter, is connected across a second diagonal to read any dis-equilibrium of the bridge. Compensation winding 21 is identical to, and in parallel, with the winding 12, but wound in the opposite direction.

Equilibrium of the bridge is achieved with the probe against the part to be measured. When the probe is subsequently moved over the part, any irregularities in the passages containing the fluid cause a visible change at the meter 20 because the fluid governs the impedance of winding 12.

It is interesting to note in passing that the American firm Teledyne Acoustic Research already has what appears to be a master patent on use of ferro-magnetic fluid to fill the gap between the voice coil and magnet of a loudspeaker. Indeed many Acoustic Research loudspeakers now have fluid filled gaps of this type. The claimed advantage is that the fluid helps conduct heat away from the voice coil to the magnet pole piece in the manner of a heat sink and provides friction-free radial support for the coil former.

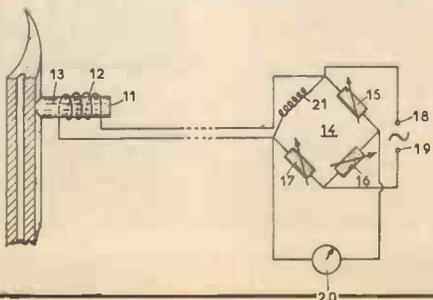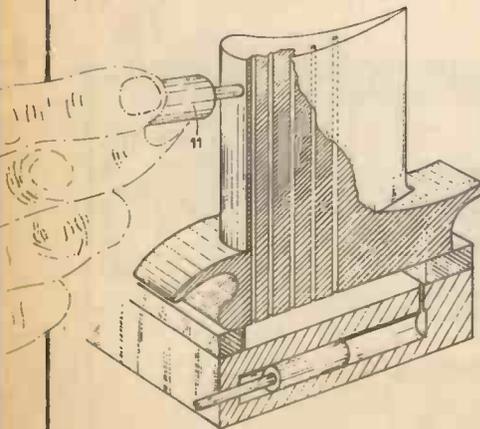The Acoustic Research patent was granted under the old British laws (BP 1542266) and cites US patents 3612630 and 3734578 as describing basic forms of ferro-magnetic fluid *per se*.



SERVICE TRADING CO

RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock phone or write in your enquiries
FT3 NEON FLASH TUBE
 High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50. P. & P. 25p (£2.01 inc. VAT) 3 for £3. P. & P. 50p (£4.03 inc. VAT & P.).

RODENE UNISEL TYPE 71 TIMER

0-60 sec 230V a.c. operation Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding, mixing, etc. Price £8. P. & P. 60p. £7.89 inc. VAT & P. & P.



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

200 watt (1 amp inc. ac. voltmeter)	£14.50
0.5 KVA (2 amp MAX)	£17.00
1 KVA (5 amp MAX)	£22.50
2 KVA (10 amp MAX)	£37.00
3 KVA (15 amp MAX)	£45.50
5 KVA (25 amp MAX)	£74.00
10 KVA (50 amp MAX)	£168.00
15 KVA (75 amp MAX)	£260.00



CARRIAGE PACKING & VAT EXTRA

LT TRANSFORMERS

0-10-15V at 3 amp (ex new equip)	£2-50 P. & P. 50p (£3-45 inc. VAT)
13-0-13V at 1 amp	£2-50 P. & P. 50p (£3-45 inc. VAT)
25-0-25V at 2 amp	£4-50 P. & P. 75p (£6-04 inc. VAT & P.)
0-4V/6V/24V/32V at 12 amp	£18-50 P. & P. £1-90 (£23-46 inc. VAT & P.)
0-6V/12V at 20 amp	£14-70 P. & P. £1-50 (£18-63 inc. VAT)
0-12V at 20 amp or 0-24V at 10 amp	£12-00 P. & P. £1-50 (£15-53 inc. VAT & P.)
0-6V/12V at 10 amp	£8-25 P. & P. £1-25 (£10-93 inc. VAT)
0-6V/12V/17V/20V at 20 amp	£19-00 P. & P. £1-50 (£23-58 inc. VAT & P.)
0-10V/17V/18V at 10 amp	£10-50 P. & P. £1-50 (£13-80 inc. VAT)

Other types in stock; phone for enquiries or send sae for leaflet.

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Hy-Light Strobe Kit Mk IV. Post £1-50 (£2-20 + £1 P. & P. inc. total £2-45). Specially designed case and reflector for Hy-Light £8-80. Post £1 (£11-27 inc. VAT & P.). Super Hy-Light Strobe Kit. Price £33-00 + £1-50 P. & P. (incl. total £39-68).

XENON FLASHGUN TUBES

Range available from stock SAE for details

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 Watt £8-70 inc. VAT £10-00 (callers only) 2ft. 20 watt £6-20. Post 75p. (£7-99 inc. VAT & P.) (For use in stan bi-pin fittings) Mirr 1 1/2m 8 watt £2-80. Post 35p. (£3-62 inc. VAT & P.). 9 in. 6 watt £2-25. Post 35p. (£2-99 inc. VAT & P.). 6 in. 4 watt £2-25. Post 35p. (£2-99 inc. VAT & P.). Complete ballast unit for either 6", 9" or 12" tube 230V AC op. £3-50. Post 45p. (£4-54 inc. VAT & P.). Also available for 12V DC op. £3-50. Post 45p. (£4-54 inc. VAT & P.). 400 watt UV lamp and ballast complete £31-50. Post £3. (£39-88 inc. VAT & P.). 60 watt UV lamp only £11-25. Post £1.20 (£14-32 inc. VAT & P.).

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free.

S.A.E. (foolscap) for further details. Price £60-00 p&p 70p (£69-81 inc. VAT & P.).

WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details.

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/500/1k/1k/1.5k/1.5k/2.0k	Post 20p (£2-99 inc. VAT & P.)
50 WATT 250/1k/2.0k	Post 25p (£3-62 inc. VAT & P.)
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k	£5-90 p. & p. 35p (£7-19 inc. VAT)

SPECIAL OFFER

BERCO type L RHEOSTAT 85 ohm 300 watt 1-86 amp. £7-50 p. & p. 50p. (Total: £9-20 inc. V.A.T.). N.M.S.

RELAYS

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1-50 (£1-96 inc. VAT & P.). T.E.C. open type 3 c/o. 10 amp £1-10 (£1-50 inc. VAT & P.).

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1-00 (£1-38 inc. VAT & P.). Sealed 12V 1 c/o 7 amp octal base £1-00 (£1-38 inc. VAT & P.). Sealed 12V 2 c/o 7 amp octal base £1-25 (£1-87 inc. VAT & P.). Sealed 12V 3 c/o 7 amp 11-pin. £1-35 (£1-78 inc. VAT & P.). 24V. Sealed 3 c/o 7 amp 11-pin £1-35 (£1-78 inc. VAT & P.). (amps = contact rating). P&P on any Relay 20p. Other types available - phone for details. N.M.S. Very Special Offer: 9-12V D.C., 2 make contacts, new I.T.T., 3 for £1-75 +25p P&P. (inc. VAT £2-30). Diamond H heavy duty A.C. relay 230/240V a.c., two C/O contacts 25 amps res at 250 a.c. £2-50 p&p 50p. (£3-45 inc. VAT & p&p). Special base 60p. (incl. VAT 58p) N.M.S.

GEARED MOTORS

4 1/2 rpm. 115V. a.c. 50 cycle. mf. SIGMA Inst. Ltd. U.S.A. Price: £7-50 + 75p. P. & P. (£9-49 inc. VAT). supplied with transformer. N.M.S.

7 1/2 rpm. 115V. a.c. 50 cycle approx. 25lb. mf. KLAXON. 28 rpm. 115V. a.c. 20lb. in. reversible. Price of either 2 Motors £4-75 each + 75p. P. & P. (£6-33 inc. VAT). N.M.S. Any of above 3, supplied with Transformer for 240V. operation: £7-25 + £1-00 P. & P. (£9-49 inc. VAT).

19 rpm FHP 220/240V. a.c. reversible, torque 14.5kg. Gear ratio 144-1. Brand new including capacitors. mf. CITENCO. Price: £14-25 + £1-25 P. & P. (£17-83 inc. VAT). N.M.S. 30 rpm. 230/240V. a.c. 50lb. in. mf. PARVALUX. Price: £15-00 + £1-50 P. & P. (£18-98 inc. VAT). N.M.S.

56 rpm. 240V. a.c. 50lb. in. 50Hz 0-7 amp. Shaft length 35mm. Dia 16mm. Wdg. 6000. mf. FRACMO. Price: £15-00 + £1-50 P. & P. (£18-98 inc. VAT). N.M.S.

100 rpm. 110V. a.c. 115lb. in. 50Hz. 2.8 amp. single phase split capacitor. Immense power. Continuously rated. Totally enclosed. Fan-cooled. In-line gear-box. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm. length 145mm. Tested. Price: £12-00 + £1-50 P. & P. (£15-53 inc. VAT). R. & T. Suitable Transformer for 230/240V. operation. Price £8-00 + 75p. P. & P. (£10-06 inc. VAT).

200 rpm. 35 lbs. in. 115V. 50Hz. Price: £16-00 + £1-50 P. & P. (£20-13 inc. VAT). N.M.S. Suitable Transformer for 230/240V. a.c. Price: £8-00 + £1-00 P. & P. (£10-35 inc. VAT). N.M.S.

500 rpm. 230/250V. a.c. 3 1/2 lb. in. 2 right-angled spindles. Mf. PARVALUX. Price £11-00 + £1-00 P. & P. (£13-80 inc. VAT). N.M.S.

6/9V. D.C. Miniature Gearing Motor, precision built, incredibly powerful for size - approx. speed e 6V. - 60 rpm 40 ma. approx. speed e 9V. - 80 rpm 50 ma. Size: 27mm dia., 30mm length, 55gr. weight, drive spindle 5 x 3mm dia. Price: £2-50 post paid (£2-88 inc. VAT). N.M.S.

12V. D.C. type SD2. Shunt 3 ph continuously rated 4000 rpm. Mf. PARVALUX. Price: £10-00 + 75p. P. & P. (£12-35 inc. VAT). N.M.S.

1rpm 230/240V. a.c. Synchronous geared Motor, mf. HAYDON. 2 rpm. 230/240V. a.c. Synchronous geared Motor, mf. CROUZET. Either type £2-80 + 30p. P. & P. (£3-68 inc. VAT). N.M.S.

1,400 rpm 115V. a.c. Motor. HP 1/4 continuously rated. Fitted with anti-vibration cradle mounting. Mf. FRACMO. Supplied complete with Transformer for 230/240V. a.c. operation. Price: £10-00 + £1-00 P. & P. (£12-65 inc. VAT). N.M.S.

1,600 rpm. 230V. a.c. reversible Motor. 0-25 a. complete with anti-vibration mounting bracket and capacitor. O/a size: 110 x 90mm. Spindle 3/4 dia. reversing. Mf. GENERAL ELECTRIC. R. & T. Price: £3-00 + 50p. P. & P. (£4-03 inclusive).

REDUCTION DRIVE GEAR BOX. Ratio 72:1. Input spindle 1/2 x 1/2 in. Output spindle 3/4 x 3 in. long. Overall size approx: 120 x 98 x 68 mm. All metal construction. Ex-equip. tested. Price: £2-00 + 50p. (incl. VAT £2-88).

ROTARY VACUUM AIR COMPRESSOR & PUMP
 Carbon Vane oil-less. 100/115V. A.C. 1/12 h.p. motor 50/60 cycle 2875/3450 rpm. 20" vacuum 1-25 c.f.m. 10 p.s.i. (approx. figures) mft. by Gast Co. Fraction of maker's price. £14-00 p. & p. £1-00 (Total: £17-25 inc. VAT). Suitable Transformer. £3-50 p. & p. 50p. (Total: £4-60 inc. VAT). N.M.S.

BLOWER VACUUM PUMP
 English Electric 3 phase A.C. motor 220/250V. Or 380/440V. 1.425 r.p.m. 1/2 h.p. continuously rated. Direct coupled to William Alday & Co. Alcosa carbon vane blower/vacuum pump 0.9 cfm 8.H.G. Price £22 p&p £2 (£27-60 inc. VAT & p) N.M.S.

Time Switch
 Vanner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any mutually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £9-00. P. & P. 75p (£11-22). R. & T.

SANGAMO WESTON TIME SWITCH
 Type S251 200/250V. a.c. 2 on/2 off every 24 hrs. 20 amps contacts with override switch dia. 4 x 3 price £8.00 P & P 50p inc. VAT £9.78. Also available with Solar dial. R. & T.

GERMANY 24-HOUR TIMESWITCH
 (Miner mfr.). 240V. A.C. operation. Spring Reserve. 10 amp contacts, one on-off every 24 hours. Calibrated in two hour steps. Minimum on-off period 6 hours. Day Omission. Unusual feature with these Switches is that trips may be removed at will enabling individual days to be programmed as required. Size only 3" x 4". Depth 2 1/2". Price: £8-50 + 50p. p. & p. (£8-05 inc. VAT & P.).

KEY: N.M.S. R. & T. New Manufacturers Surplus Reconditioned and Tested

All Mail Orders Callers Ample Parking Space Showroom open Mon-Fri.

SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01 995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10.00

Personal callers only Open Saturdays
 9 Little Newport Street, London WC2H 7JJ
 Phone 01-437 0576

24 TUNE DOOR CHIMES

DOOR TUNES £17.13 + VAT.

Waddington's Videomaster announce a doorbell that doesn't go Brrringgg, Ding-Dong or Bzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



T.V. GAMES

PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES:

ROAD RACE - £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

SUPER WIPEOUT - £3.17 + VAT.

10 different games of blasting obstacles off the screen.

STUNT RIDER - £12.16 + VAT.

Motorcycle speed trials, jumping obstacles, leaving various rows of up to 24 buses etc.

NON-PROGRAMMABLE TV GAMES

6 Game - COLOURSCORE II - £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS

STAR CHESS - £56.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 - £86.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, en passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.



ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT.

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 18 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE

CHESS CHAMPION - 6 LEVELS £47.39 + VAT.

CHESS CHALLENGER - 10 LEVELS - £138.70

+ VAT.

BORIS - MULTI-LEVEL TALKING DISPLAY £163.04


+ VAT.

DRAUGHTS COMPUTERS

CHECKER CHALLENGER 2 LEVELS £43.00 + VAT. 4 LEVELS £78.00 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

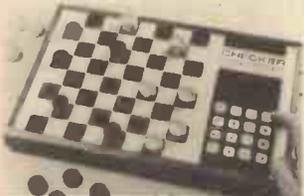PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER




FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on. Callers welcome at our shop in Welling demonstrations daily open from 9am-5.30pm Mon-Sat 10am-1pm Wed. To order by telephone please quote your name, address and Access/Barclaycard number. Postage and Packing FREE.

AJD DIRECT SUPPLIES LIMITED, Dept. PE12 102 Bellegrove Road, Welling Kent DA16 3DD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

PROOPS

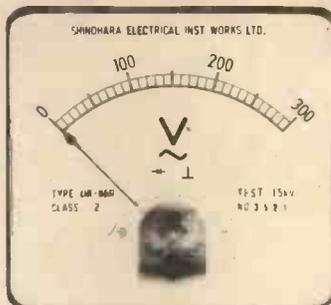BROTHERS LIMITED
Special purchase of Shinohara's SEW Panel meters at fantastic low prices



SEW RANGE - DC MOVING COIL TYPE

(Accuracy ± 2%)

MR 85P (110 x 120mm) x 47mm £3.50

±DC 50uA	±DC 1mA	DC 1A	AC 10A	DC 150V
±DC 100uA	DC 5mA	DC 5A	AC 20A	DC 300V
DC 200uA	DC 10mA	DC 15A	AC 30A	AC 15V
DC 500uA	DC 50mA	DC 30A	DC 10V	AC 300V
±DC 500uA	DC 100mA	AC 1A	DC 20V	VU
DC 1mA	DC 500mA	AC 5A	DC 50V	S METER

MR 45P (50 x 50mm) x 34mm £1.50

±DC 100uA	DC 100mA	DC 500mA	AC 15V
DC 10mA	DC 200mA	DC 1A	AC 300V
DC 50mA	DC 300mA	AC 1A	

MR 52P (60 x 60mm) x 40mm £2.50

DC 50uA	DC 500mA	AC 5A	AC 30A
±DC 50uA	DC 1A	AC 10A	DC 300V
±DC 100uA			
DC 5mA			

MR 38P (42 x 42mm) x 32mm £1.50

±DC 500uA	DC 150mA	DC 15V	DC 750V	AC 300V
±DC 1mA	DC 200mA	DC 150V	AC 15V	AC 500V
DC 2mA	DC 500mA	DC 300V	AC 50V	S METER
DC 50mA	DC 3V	DC 500V	AC 150V	

SW 100 (80 x 100mm) x 37mm £3.00

±DC 50uA	DC 1A	DC 20V	DC 300V
±DC 100uA	DC 5A	DC 50V	AC 150V
DC 100uA			
DC 500uA			

MR 65P (78 x 86mm) x 41mm £3.00

±DC 50uA	DC 500mA	DC 20A	DC 150V	AC 500V
±DC 1mA	AC 50mA	DC 30A	AC 15V	S METER
DC 5mA	AC 200mA	AC 50A	AC 50V	
DC 50mA	AC 500mA	DC 10V	AC 150V	

SD 830 (82.5 x 110mm) x 36mm £3.00

DC 5mA	5DC 500mA	DC 300V
DC 50mA	DC 50V	AC 15V

S - 80 (80 x 80mm) x 39mm £3.00

DC 50uA	DC 500mA	DC 20V	DC 300V
±DC 50uA	DC 1A	DC 50V	AC 300V

SD 460 (46 x 59.5mm) x 33mm £1.50

DC 5mA	DC 50mA	DC 300V	AC 300V
DC 10mA	DC 500mA	AC 15V	

SD 640 (63.5 x 85mm) x 33.5mm £2.50

DC 5mA	DC 1A	DC 10V	AC 15V
DC 10mA	DC 10A	DC 300V	AC 300V

Prices inclusive of VAT. Plus 30p per item carriage and packing.

RECHARGE YOUR BATTERIES FROM THE SUN

WITH MINIATURE SOLAR CELLS

A bank of five cells complete with a diode that prevents the battery discharging in the dark. Overall size of cell bank 15mm x 13mm. Output is two volts at 1.8 milliamps.

Price £2.00 plus 10p for postage and packing.



Barclaycard & Access Accepted - Order by phone or post.

Mail Orders to Proops Bros. Limited, Dept PE8

The Hyde Industrial Estate, Edgware Road,

London, NW9 6JS. Tel. 01-205 8006


Personal Shoppers: 52 Tottenham Court Road, London, W1P 0BA. 9-6 Mon-Sat.

NEXT MONTH



SCRATCH & RUMBLE FILTER...

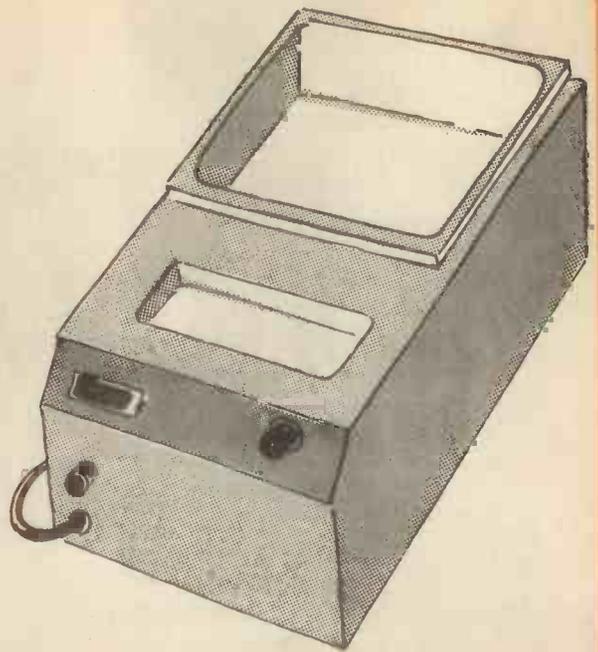Reduce the scratch noise from your favourite records, the rumble from a worn turntable or the noise of record warps and pressing imperfections, with this straightforward stereo design.



ULTRASONIC CLEANER

We do not believe an Ultrasonic Cleaner has ever been published as a constructional design. Why? Because the transducer and tank pose buying problems. A kit supplier has solved these problems for us and next month we will bring you a design for half the cost of a commercial unit.

SOFTY *Review*

Softy is a general development tool for MPUs and next month our contributor, Dr. A. A. Berk, reviews this new line in the micro scene.

PRACTICAL ELECTRONICS

JANUARY ISSUE ON SALE FRIDAY DECEMBER 14

Ultrasonic BURGLAR ALARM

GILBERT DAVIES

THIS ultrasonic burglar alarm is a two unit system: a Movement Detector and a Control Unit. The Movement Detector, which contains the ultrasonic transmitter (X1) and receiver (X2), will detect movement within a room and then send an alarm signal to the control board. The Control Unit contains the keyswitch for on/off control of the system, the delay circuits, and the relay for controlling the alarm as well as the battery back up circuit in case of mains failure.

which can be higher or lower than 40kHz); these will combine to produce a beat note. The frequency of this audio or sub-audio beat note will be the difference between the two ultrasonic frequencies. This beat frequency is then amplified, filtered and used to operate the alarm.

MOVEMENT DETECTOR

The circuit diagram of the Movement Detector is shown in Fig. 1. If constructors wish to use the Detector Unit on its own the relay RLA and D15 (shown in the shaded area) should be fitted and the value of C13 increased to 22 micro farads. If both units are to be used the two wire links shown on the Movement Detector board should be fitted. The 18V output from the transformer (T1) is fed to the bridge rectifier formed by D11 to D14, smoothing capacitor C15 and the voltage regulator (IC2) to obtain a stabilised 12V supply.

The 555 timer (IC3) is connected as a variable square wave generator the output of which (pin 3) is fed to the ultrasonic transmitter (X1). The transmitted signal from X1 is


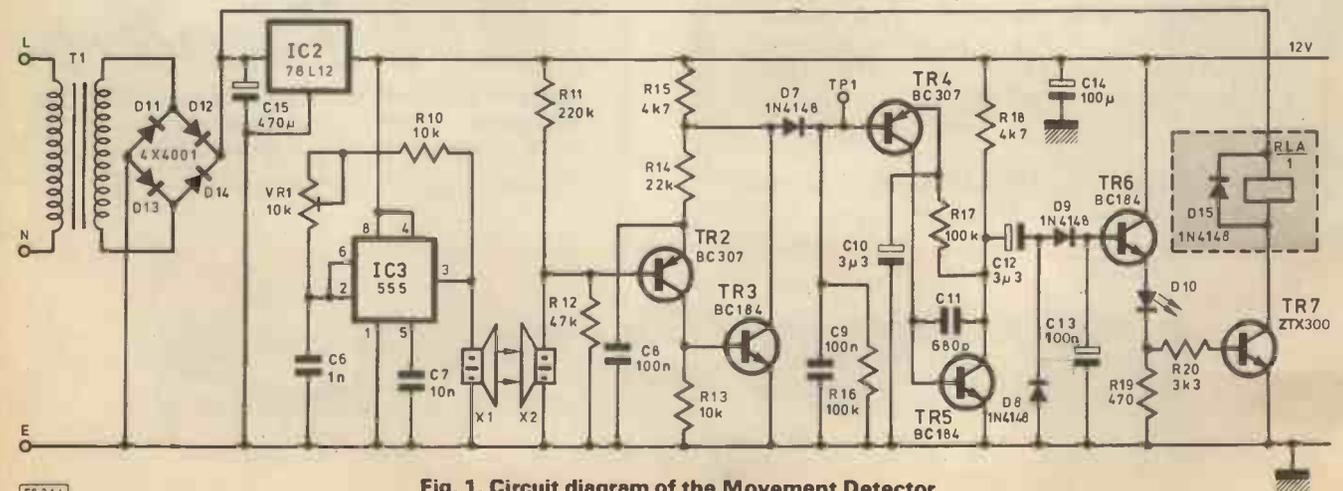


Fig. 1. Circuit diagram of the Movement Detector

picked up by the receiver X2 and amplified by TR2 and TR3 with resistor R14 providing 100 per cent feedback making this stage very stable. The a.c. gain of the stage is determined by C8 which shunts the high frequency signals in the feedback path therefore increasing the gain of the stage 50 times the input voltage at 40kHz.

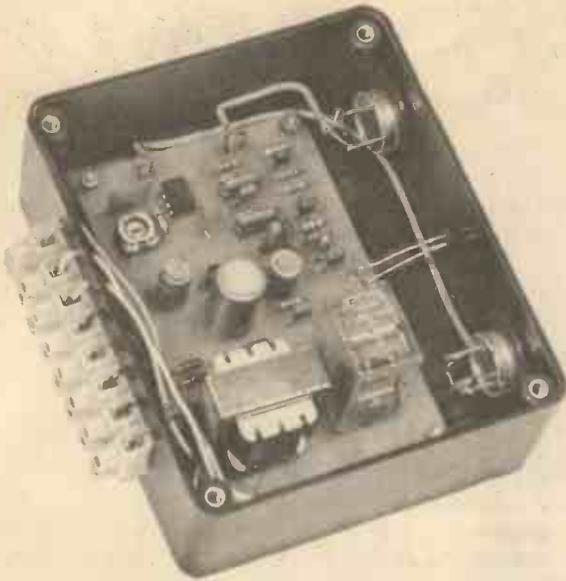As only the positive going signal is required at the output of this stage the bias is offset from the normal half supply rail to provide a better operating working voltage for the diode detector as well as a greater overload margin for the input stage.



Internal view of the Movement Detector. Note that the relay RLA has been included

The output from TR3 collector passes through the envelope detector D7 and the CR network C9, R16 which removes the 40kHz signal. The signal from TR3 collector varies the d.c. level across C9 and provides both the bias and the signal for the next stage. This stage is basically the same as the first stage with the exclusion of the load resistor for TR4 collector.

SPECIFICATION

- 0.5 sec alarm function test at switch on.
- 2 sec delay to suppress invalid movement.
- 20 sec delay at switch on — to prevent alarm operation on leaving room.
- 20 sec delay on entry — to allow the alarm to be cancelled.
- 2 min alarm before cancelling (alarm is pulsed at 2 Hz).
- Quiescent current 25µA at 12V d.c.
- 18V battery back up in the event of a mains failure.

The capacitor C11 limits the HF response by applying negative feedback to TR5 so that the ultrasonic component of the signal is not amplified. R17 and C10 were chosen to provide a suitable bandwidth for Doppler shift frequencies.

The output from TR5 is fed to the diode pump network (D8, D9) via C12 which rectifies the signal and charges C13 to convert the beat note to a steady voltage. When the voltage across C13 reaches 2.6V, TR6 turns on and the l.e.d. (D10) is illuminated. TR7 is also turned on via R20 and the collector voltage of TR7 falls to zero. This fall in collector

voltage is passed to the control unit via the wire link and the common output of RLA on the Movement Detector Board.

However if the relay RLA is used the falling collector voltage of TR7 is used to energise the relay from the un-stabilised 18V supply, whilst D15 suppresses any spikes generated by the relay coil. The collector of TR7 remains low until C13 discharges through TR6 turning off both TR6 and TR7 and switching the collector voltage of TR7 high.

COMPONENTS . . .

Resistors

R1, R3, R7, R14	22k (4 off)
R2, R11	220k (2 off)
R4, R5	2M2 (2 off)
R6	10M
R9, R10, R13	10k (3 off)
R8	470k
R12	47k
R15, R18	4k7 (2 off)
R16, R17	100k (2 off)
R19	470
R20	3k3

All resistors ¼W 10% carbon

Potentiometers

VR1	10k min. hor.
-----	---------------

Capacitors

C1, C4	4µ7 25V tant (2 off)
C2, C3, C5	10µ 25V tant (3 off)
C6	1n ceramic
C7	10n ceramic
C8, C9	100n polyester (3 off)
C10, C12	3µ3 16V tant (2 off)
* C13	100n or 22µ 16V elect
C11	680p ceramic
C14	100µ 16V elect
C15	470µ 25V elect

Semiconductors

D1 to D6, D7 to D9, D15	1N4148 (10 off)
D11 to D14	1N4001 (4 off)
D10	TIL 209
TR1, TR7	ZTX300 (2 off)
TR2, TR4	BC307 (2 off)
TR3, TR5, TR6	BC184 (3 off)
IC1	4093
IC2	78L12
IC3	NE555

Miscellaneous

X1	Transmitter MA 40 LIS
X2	Receiver MA 40 LIR
T1	Transformer 18V 75 mA
* RLA	Varley VP2 700 ohms
RLB	12V 1640Ω open type (RS 349 — 131)
B1, B2	Battery PP9 (2 off)
S1	Keyswitch
P.c.b.s.	(2 off)
Battery clips	(2 off)
ABS case 115 x 95 x 45mm	(2 off)
Grommets	
Terminal block	
Keyswitch	
* Piezoelectric transducer	1TT U2 — 50 RHA
* See text	

Constructor's Note

Printed circuit boards and other components are available from **G.J.D. Electronics, 105 Harper Fold Road, Radcliffe, Manchester.**

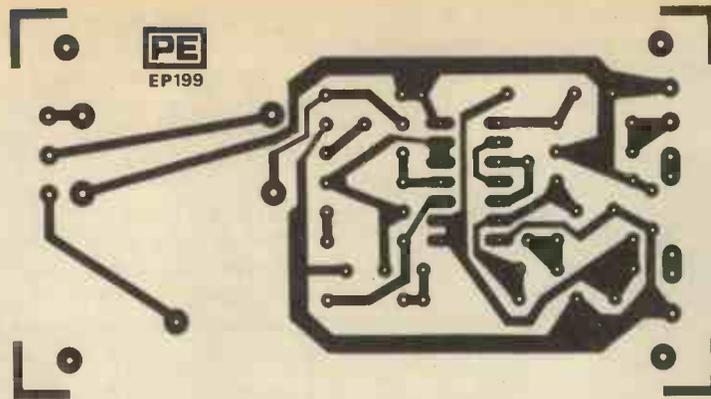


Fig. 5. P.c.b. design for the Control Unit

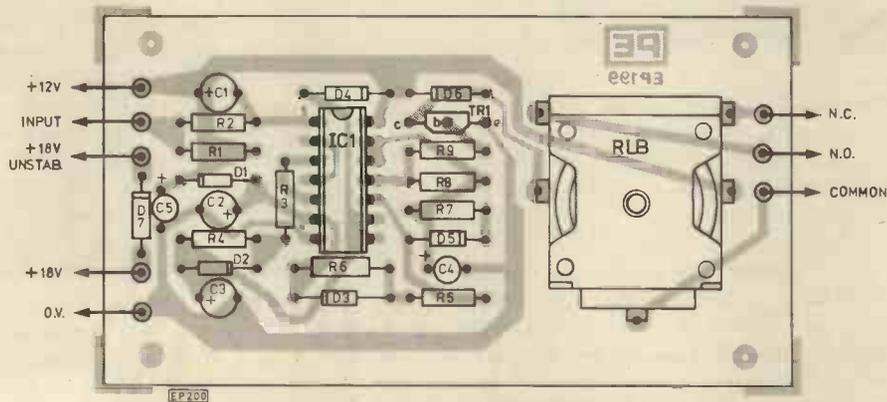


Fig. 6. Component layout of the Control Unit

for 0.5 sec to provide an alarm test every time the system is switched on.

When movement is present for more than 2 secs the input of gate "a" goes low setting the bistable with the output of gate "a" going high charging C3 through R3, R4. This allows the input to gate "c" to go high and its output low releasing the input of gate "d". Gate "d" forms a 2Hz Schmitt oscillator, the frequency being determined R8, C4. The output from gate "d" passes through R9 driving TR1 and energising RLB. D6 suppresses the back e.m.f. from the relay coil.

The output of gate "c" also discharges C2 which after 2 mins resets the bistable and cancels the alarm. D1 and D4

discharge C2 and C3 at switch off.

Diode D7 has the battery voltage connected to its anode and the un-stabilised 18V to its cathode. Because the un-stabilised voltage will be higher the diode is turned off. When the main voltage falls the diode will conduct and the battery voltage will be applied to the system. When the main supply is re-established the diode D7 automatically switches off the battery voltage.

CONSTRUCTION

In the prototype system the movement detector and the control unit were mounted into two separate ABS boxes.


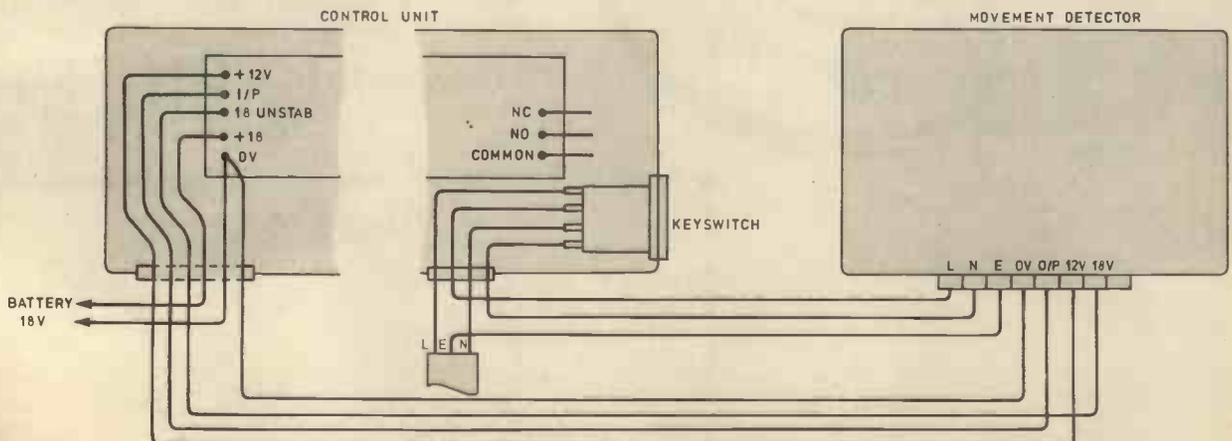


Fig. 7. Wiring interconnections for the two units

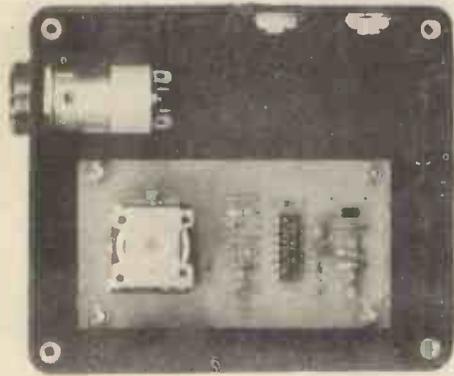The transducers are mounted inside grommets on the front panel with the indicator l.e.d. mounted mid way between them. If the l.e.d. is not required on the front panel it can be placed inside on the p.c.b.



Internal layout of the Control Unit

The p.c.b. design for the Movement Detector is shown in Fig. 3 with the component layout in Fig. 4. After the board has been soldered and checked it can be mounted into the case and connected to the terminal block. The transducers should be soldered to the board using screened leads.

The p.c.b. design and component layout for the Control Unit are shown in Figs. 5 and 6. After soldering and checking, the p.c.b. should be mounted into the case together with the keyswitch. The two PP9 batteries were mounted outside the case on the prototype although if a larger case is used they could be mounted inside. The two units should be wired together as shown in Fig. 7.

ALARM OPTIONS

The system can be fitted with an external piezo electric transducer which can directly replace RLB and D6, driven from the collector of TR1.

If an external alarm is used it can be connected via the contacts of RLB and either a mains or 12V d.c. buzzer used.

INSTALLATION

The detector is prone to both vibration and air currents therefore the points shown in Table 1 should be observed to avoid false triggering of the alarm.

TABLE 1	
a)	Do not place the unit on a vibrating surface.
b)	Close doors and windows.
c)	Do not point the unit at a wall with a radiator or convector heater.
d)	Objects should not be placed within 5 feet of the unit as this will limit its sensitivity.
e)	The external alarm should be far enough away from the unit so as not to produce vibration.
f)	Cats, dogs and other household pets should be taken into consideration.
g)	If more than one unit is used care should be taken to ensure the two ultrasonic "fields" do not interact the alarm to trigger.

SETTING UP


The variable resistor VR1 should be adjusted for the maximum d.c. level at TP1. The sensitivity of the unit can be checked by moving in front of the ultrasonic transmitter and receiver and noticing the l.e.d. movement indicator. Finely adjust VR1 until the maximum sensitivity is obtained ★

A real bind

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL ELECTRONICS logo. Gold letraset supplied for self blocking of volume numbers and years.

Price £3.75 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to:— IPC Magazines Ltd, Post Sales Dept, Lavington House, 25 Lavington St, London, SE1 0PF.

it's easy with **EASIBIND**

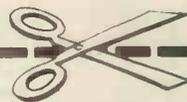

Order Form

PRACTICAL ELECTRONICS
 I enclose P.O./cheque valuefor binders
 Years required
 (BLOCK LETTERS PLEASE)
 Name
 Address

 Date



FRANK W. HYDE

THE LARGEST INFRA RED TELESCOPE

A triumph of engineering skill has added a fourth member to a group of telescopes on the summit of Mauna Kea on the big island of Hawaii. The United Kingdom Infra Red Telescope (UKIRT) was inaugurated by His Royal Highness the Duke of Gloucester on the 10th of October.

In recent years there has been a very considerable expansion of activity in the field of Infra Red Astronomy, indeed it could now be said that it has paralleled advances made in other areas of the spectrum. New sources of radiation have been recorded and new mechanisms have been posed to account for physical processes that are taking place in remote regions of the Universe. For example it has been discovered that the nuclei of galaxies radiate an unexpectedly large amount of infra red energy. As yet the extent of the power involved is unknown.

There are massive clouds of interstellar dust and gases which appear to be the site of galaxy and star formation. These cradles of creation may hold the clues relating to the origin of the Universe. Solid matter in these areas provide the surfaces needed for hydrogen and other molecules to form. Of the different types of molecule identified, more than 50, all have specific emission or absorption at the infra red and radio frequencies. The extent of the complexity involved in the molecular processes was unsuspected a decade ago.

It may be possible now to set up a galactic distance scale using techniques involving magnitudes and measured velocity dispersions. At millimetre wavelengths the infra red telescope is the only means of studying the cosmic background radiation at 2.7 degrees. This is the temperature at which there should be remanent radiation from the processes that were in operation at the formation of the Universe.

Two British firms were involved in the development and construction of the 3.8 metre UKIRT. They are Grubb Parsons who have had so much experience in the design and development of telescopes over many decades and are now a unit of Northern Engineering Industries, together with Hadfields Ltd., famous for their original work on the 250ft diameter radio telescope at Jodrell Bank, Hadfields are now part of the Lonrho Group.

The UKIRT was commissioned by the Science Research Council in 1975. The contract went to the Special Projects Division of Hadfields Limited. Work commenced in the spring of 1975.

Modern telescopes and other instruments in use for astronomical purposes are now very much concerned with electronics. Control systems abound and astronomy cannot be seen now as an isolated activity for it is, by reason of the space industry involved, not only in the scientific experiments but in all systems involving navigation and the practical guidance of space vehicles. The infra red telescope by its very nature covers a wide field of technology. The mechanics are concerned with the elements such as control of a surface which is so sensitive that just tilting on its axis can set the mirror in a condition of distortion. Such conditions not only affect the performance of individual tasks but have long term possibilities in ageing and deterioration of the materials used. This is primarily where the control system depends on electronics.

The mirror was to be 3.8 metres in diameter and 29 centimetres in thickness. Now apart from the very critical parameters involved in the manufacture of such a mirror, its performance at all angles is prodigious. The final result must be such that distortion must be held to an almost impossible low level. The contours of the surface of the primary mirror is held by a special support of three rings with a total of eighty pneumatic cylinders. These are electronically controlled. The result has been to achieve subarc second performance under all normal operating conditions.

The material of the mirror is a glass ceramic called Cer-Vit. Normal glass would not be suitable for a mirror of this size and nor would it be able to resist thermal distortion which is one of the great hazards with large mirrors. Cer-Vit is not subject to this defect and indeed is almost unaffected by thermal changes. It should be noted here that even a minute distortion of the surface can result in a confused image at the focus and thereby nullify measurements.

The rest of the optical system consists of smaller mirrors all made of Cer-Vit. One of them is a plane mirror used in the Coudé beam. This has a major axis of 1.5 metres and a thickness of 3 centimetres. The mirror blanks were purchased from Owen's of Illinois and figured by Grubb Parsons.

The principle of operation is in a number of modes. Two of these will be described.

The primary mirror is at the "bottom" of the main structure. This receives the radiation from the sky and directs it on to a secondary mirror at the "top" of the structure. The radiation is then again returned toward the primary mirror. Different secondaries may be

used. In one case the radiation passes from the secondary mirror through a hole in the centre of the primary mirror to a point about one metre behind the primary. This is the Cassagrainian focus. At this point the radiation is recorded by instruments mounted on the frame of the telescope. Thus all instruments in a similar mode have to be mounted on the telescope since it traverses the sky and the instruments must follow. The amount of such instrumentation has a limiting factor. To overcome this, where the equipment for examining the radiation is large, another mode is adopted. By the use of plane mirrors another focus independent of the position of the main axis of the telescope is achieved. This is called the Coudé focus. By means of plane mirrors the beam from the system can be diverted so that it remains independent of the motion of the telescope itself. This enables large and bulky apparatus to be accommodated in a basement below the telescope.

The remainder of the telescope apart from the optical systems was designed and constructed by Hadfields of Sheffield. The whole completed telescope was built, tested, dismantled and conveyed to the final site there to be erected and put into operation by that Company under the guidance of the Royal Observatory Edinburgh.

COMPUTER CONTROL

Many of the mechanical and control systems are new concepts in control. A high proportion of this innovative design is found in the unique electronic control systems and computer control. The control computer is physically coupled systems employing the European CAMAC standard interface which provides almost unlimited expansion facilities. The control computer is of unique design due to Hadfields and provides time dependent data for telescope motions without frequency synthesis. This technique has been developed into an advanced form by software engineers from Imperial College, London and the Royal Observatory of Edinburgh.

In operation the telescope has a special device not used on ordinary optical telescopes. To be effective an infra red device must be able to separate the radiation from the body or area under study from the background radiation. This is provided by a special "rocking" secondary mirror. This allows the telescope to "see" the sky and the object alternately. The mirror is rocked at a rate of up to 30 cycles per second. The detector is therefore presented with a varying signal which the electronics record. Any British astronomer may apply for time to use the telescope. Application must be made to the Royal Observatory, Edinburgh who are responsible for the administration of their project.

SHUTTLE SCHEDULE

The first space shuttle schedule shows that between 1981 and 1984 all thirty-eight flights are already fully booked.

The customers are US business enterprises, foreign Governments, many departments of the US Government in which no less than 12 spacelabs are required each having many experiments aboard.

PE

DIAMATIC

Programmable Audio Visual Unit

PART 2 — J.R.W. Ames B.Sc. W.L.Blyth B.Sc.

In this final part board construction together with interwiring and final setting up will be detailed.

CONSTRUCTION

The authors' projectors are made largely of plastic with a metal lamp house which gets very hot so there is no suitable heatsink surface for the triacs. To get round this problem the prototype system, shown in the photographs, was built in two boxes. One houses the majority of the electronics while the other, which also doubles as a heatsink, is for the triacs. Two boxes were used so that the high current connections to the triacs could be kept short whilst leaving the control box free to be positioned in a convenient position when making a recording. Connection to each projector is via a short length (approx. 400mm) of heavy duty mains cable while a screened multi-core cable connects the triac drivers to the control box. Other constructors may have projectors with exposed cool metal surfaces in which case the triac housing can be eliminated and the projectors connected directly to the control box.

The price of the multi-way connectors used in this arrangement amounts to nearly £18—one third of the cost of the whole unit. Many constructors may therefore prefer to mount a heatsink on the side of their plastic bodied projectors thereby eliminating the need for expensive connectors. The connection from each projector to the control unit then comprises 5 light current signal leads plus earth so a DIN audio connector can be used, reducing the cost of connectors to no more than £2.

TRIAC HOUSING


Fig. 1 shows the circuit that is contained within this housing. Straight-through connections are provided for the slide change and power supply connections to each projector while additional inputs from the main control box trigger each triac. The connections to the control box carry only small currents and are made by a multi-core screened cable (to reduce radiation from the triac trigger pulses) terminated by a 15-way D-type plug and socket (PL2, SK2). D-type plugs and sockets are also used for the connections to the projectors. Each way of these connectors can carry a maximum of 5A and in this arrangement four pins are connected in parallel for each of the two load carrying connections.

The circuit is housed in an aluminium die-cast box which should be painted with matt black spray paint after drilling. Before mounting the triacs on the inside of the box make sure that all paint is removed from the area and apply a thin


film of heatsink compound to the mating surfaces. The specified triac has a mounting tab which is electrically isolated from all of its terminals. When using a substitute device without an insulated tab it will be necessary to mount it by means of a nylon nut and bolt and to use a mica insulating washer.

Fig. 14 shows the layout inside the box and the details of the connections to the plugs, shown from the solder side of each plug. It will be necessary to shorten the specified group-boards a little before they will fit in the box. About 400mm of 3 core 13A mains cable is used to connect the housing to each projector plug. The third core of the cable can be pulled out leaving a hole large enough to take the four 0.4mm dia. wires that connect to the slide change mechanism, the power supply and earth. Inside the box the conductors from each composite cable are connected to tags on the group-board. From the group-board stout wires are connected to the T_1 and T_2 connections of each triac while the cores of the multi-way connection to the control box are also terminated on the appropriate tags. Make sure that the earth wire from each of the projectors is connected through to the chassis tag and that the screen of the multi-core cable is connected to this tag also.

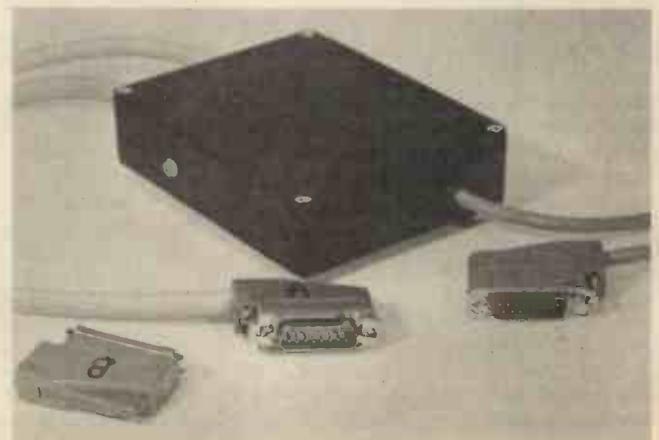It is not easy to solder the thick conductors of the load carrying cable to the pins of the projector plugs and it may be helpful to make the parallel connections between pins first using a piece of stiff wire (a resistor lead, for example). The heavy duty cable cores are then stripped back for only a short distance (approx. 4mm) and fanned out a little before



Triac housing

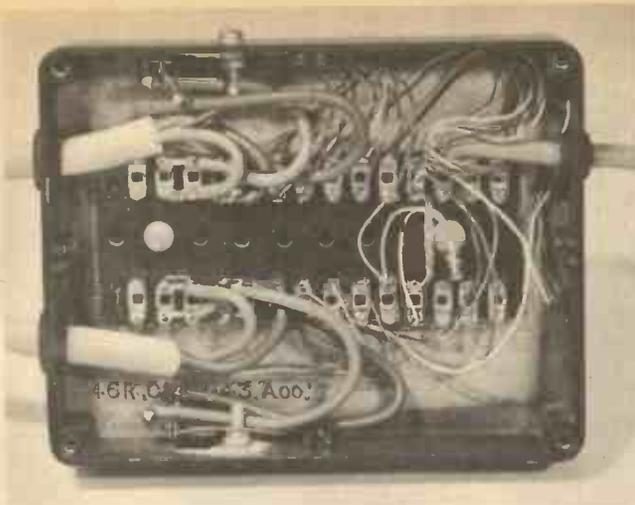

Interior wiring

being butt jointed to the stiff wire link which provides a large enough area to form a good soldered joint.

MAIN CONTROL CIRCUIT

The whole of the electronics is mounted on a single printed wiring board whose layout and component overlay are shown in Figs. 19 and 15. As a result the circuit is very easy to assemble even for the beginner or for someone whose main interest lies in photography! Installing a few components at a time work from one side of the board inserting the components and bending back their leads so that they do not drop out when the board is inverted. When a group of components have been fixed in this way invert the board and solder carefully using a clean miniature iron and miniature resin-cored solder. Apply only the minimum amount of solder to make a sound joint and then cut off the

component leads before repeating the operation. Continue in this way mounting all the wire-ended discrete components before others are inserted. R4, the power supply dropper resistor, gets fairly hot and should be stood away from the board by putting a U-bend in its leads.

Mount the skeleton preset potentiometers and sockets for the integrated circuits making sure that they are held securely home whilst soldering.

The specified cermet preset potentiometers should not be replaced by the cheaper s.r.b.p.-based types which have inferior mechanical and electrical characteristics. Use of sockets for the i.c.s is not a luxury—it is very difficult indeed to unsolder all 14 or 16 leads of a suspect "chip" without damaging the device or the board (or both), and it is very discouraging to undertake the task only to discover that it was not the i.c. that was causing the problem. Sockets allow easy substitution tests as well as ensuring that the devices are not damaged by excessive heat during soldering.

Finally, insert pins from the copper side of the board into the holes provided for off-board connections and push them firmly home using a hot soldering iron before fixing them with a small quantity of solder. In the same way that i.c. sockets are not essential to the project these pins can be omitted, but they make it much easier to make connections to the board without causing damage, and they make it possible to attach and remove external wires once the board is firmly mounted in the box.

TRANSFORMER

The pulse transformers, T101 and T102, are very easy to make and should not deter anyone from undertaking the project. Wind 100 turns of 38 swg wire on to one half of the sectionalised bobbin and twist the free ends of the wire together for a short distance to prevent them from unwinding. Repeat the operation for the secondary winding using 10 turns of 28 swg wire in the other half of the bobbin.

Now put the bobbin into one half of the pot core, line the other half of the core up on top and clip the whole assembly to the mounting board with the ring and clips as shown in Fig. 18. Solder the protruding wire ends to the pins on the base according to the layout in Fig. 15—the sense of the windings is not important as the triac will turn on with either positive or negative pulses applied to its gate. To prevent vibration and noise from the transformer when in use dip the whole assembly into household polyurethane varnish, giving it a good shake to remove surplus fluid on removal, and leave it to dry for 24 hours. Finally give the windings a check for d.c. continuity and insert the transformer into the printed wiring board before carefully soldering it into place.

THE BOX

First mount the two sockets SK1 and SK2 at the back of the box after carefully making the cut-outs.

The DIN socket SK1 is used to interconnect with the



Relative sizes of Diamatic pair

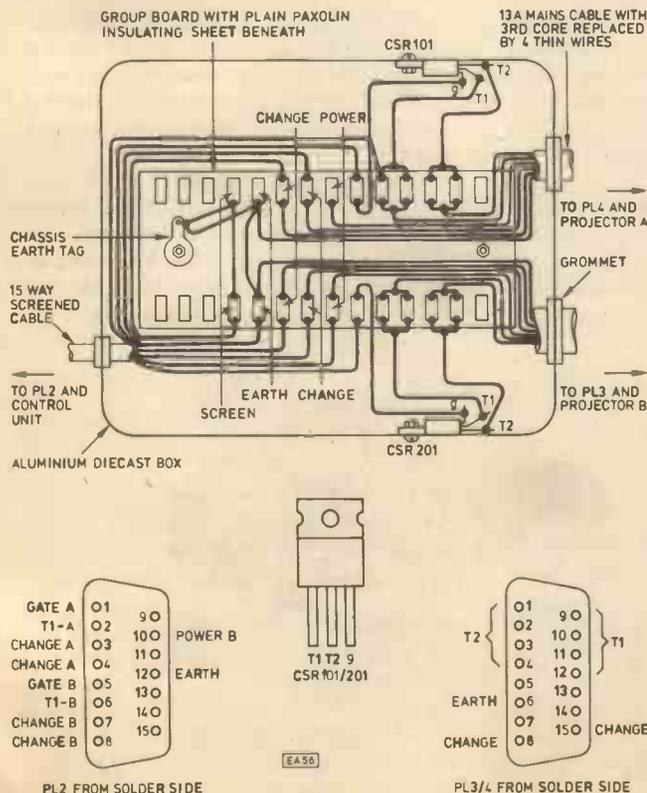


Fig. 14. Layout and plug connection

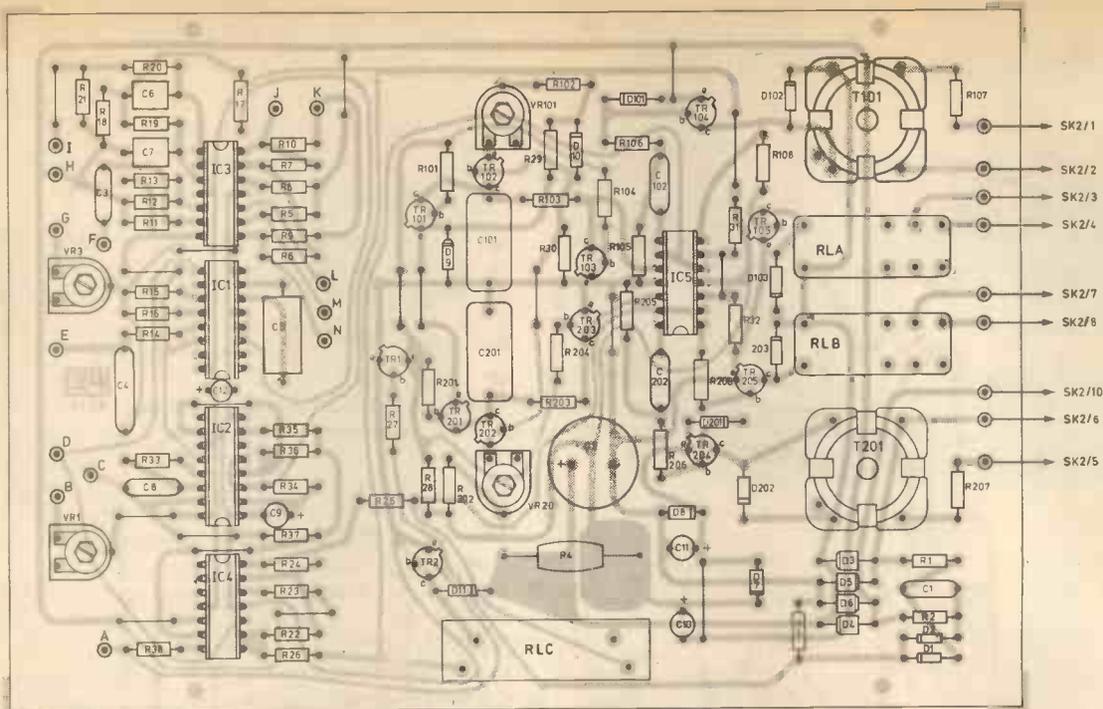


Fig. 15. Board component layout

tape recorder while the multi-way D-type socket, SK2, carries the connections to the triac housing. Fig. 20 shows the numbering of the socket connections from the interior of the box to assist in wiring. Solder leads of suitable lengths to the socket pins before mounting the printed wiring board in the box using four 3mm holes drilled to align with the mounting holes on the board. Group the wires neatly together and solder them to the appropriate pins on the board making sure that you leave enough wire to allow the board to be removed from the box to assist with later fault finding and debugging.

Fig. 16 shows the drilling details for the front panel. Mount the components where shown being careful not to damage the front surface of the panel and wire up the controls as shown in Fig. 17.

Group the wires from the front panel together remembering to leave enough wire to allow the panel to be removed for access.

When all the soldering is complete insert IC1-5 in their sockets noting that they do not all lie the same way round. It is very easy to insert an i.c. the wrong way round or to trap a pin underneath it so check carefully to avoid some tricky fault finding later.

AUDIO LEADS

The correct terminations for the DIN plug connection to the tape recorder are shown in Fig. 20 in which the left hand channel of the stereo pair has been chosen to carry the dissolve control tone. The connections to the plugs at both ends of the lead are identical. For right hand channel operation wire up the plug using pins 4 and 5 in place of

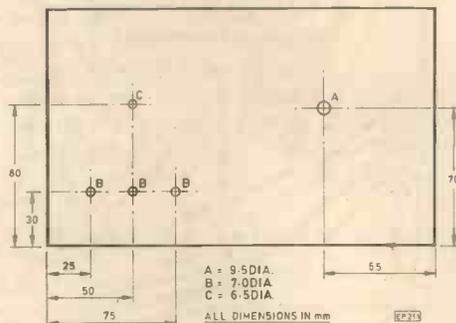


Fig. 16 Drilling detail of control panel

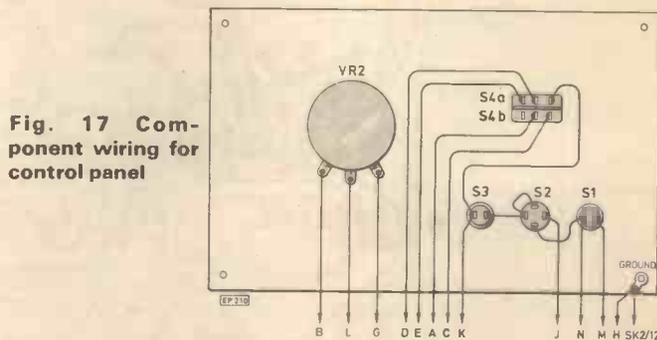


Fig. 17 Component wiring for control panel

1 and 3 respectively. If phono connections to the tape recorder are required wire up one DIN plug as shown and terminate the two free wires at the other end with standard phono plugs.

MODIFYING THE PROJECTORS

There are probably as many variations on the basic electrical circuit of a projector as there are manufacturers of this type of equipment so it is not possible to give modification instructions in great detail. We show in Fig. 21 the circuit diagram of a typical projector together with the modifications needed to enable it to work under control from the slide dissolve unit.

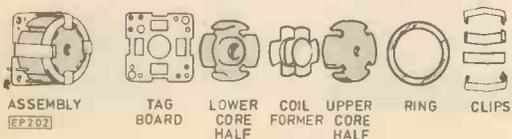


Fig. 18. Exploded detail of pulse transformer

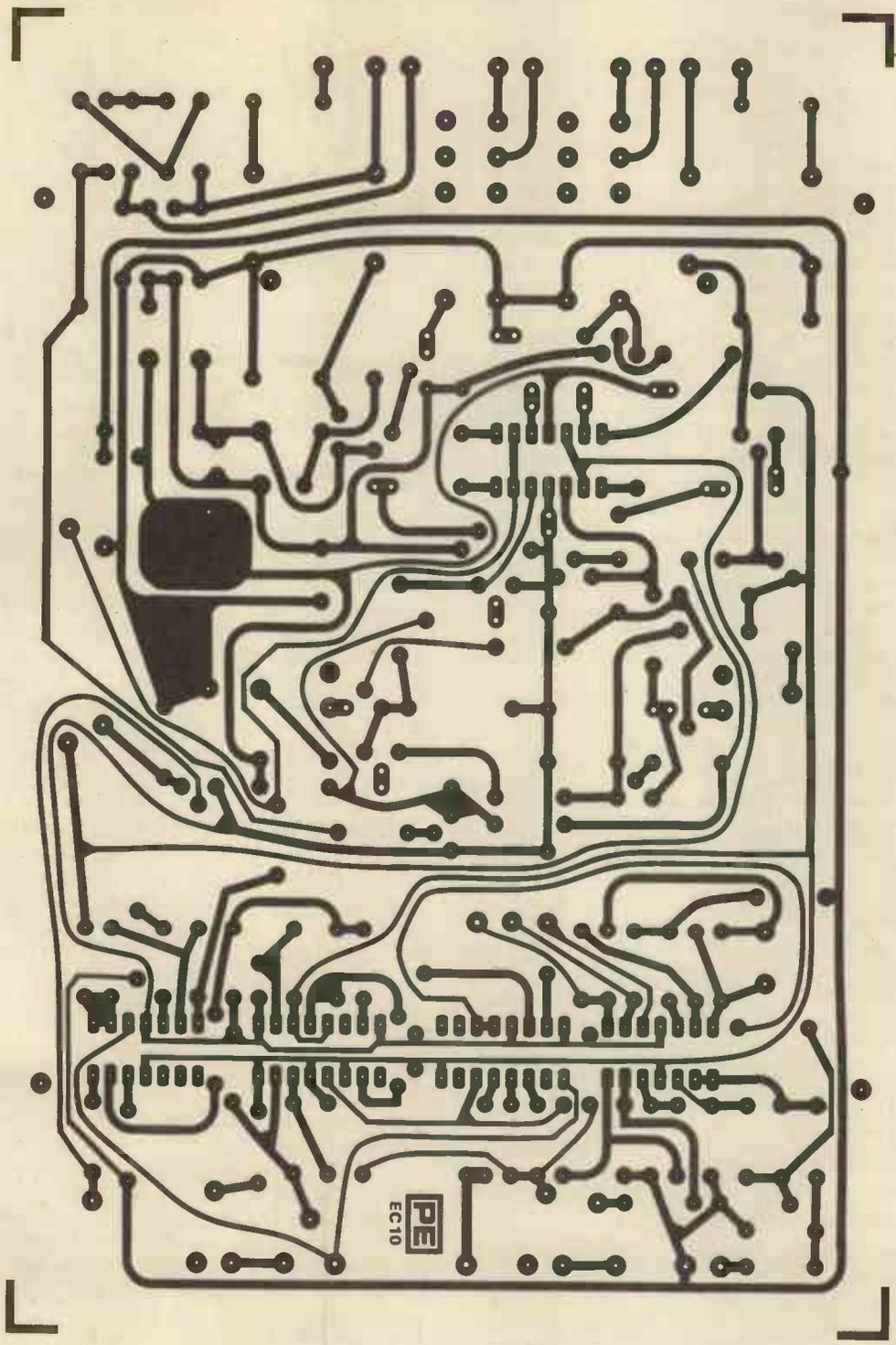


Fig. 19. Printed circuit board for Diamatic

The first and most obvious of the modifications involves interrupting the lamp circuit and bringing it out to a suitably placed D-type socket for connection to the triac housing. Also brought out to the socket is a connection in parallel with the slide change switch and a connection to the transformer secondary which completes the power supply circuit for the control electronics.

Not so obvious are the suppression components shown connected across the two solenoids. The change solenoid (SOL1) operates every time the change relay contacts make in the control unit and the slide direction solenoid (SOL2) will also operate if the direction switch on the projector remote control is set to "reverse". On release of the change relay the back e.m.f. across both of the solenoids causes arcing across the relay contacts which can interfere with the audio channel and disturb the operation of the control circuit. Suppression components are fitted across the coils of both the solenoids to prevent this problem.

First it is necessary to establish whether the solenoids involved (in many projectors there will be only one) are powered from an a.c. or d.c. supply. In the example shown (which is of a real projector) SOL1 is d.c. operated while SOL2 is powered by unrectified a.c. Across the d.c. solenoid we may connect a normally reverse biased rectifier diode that will conduct during the reverse swing of the back e.m.f. thereby preventing an arc from developing. This treatment is not possible for an a.c. solenoid so in this case a series combination of R/C is used to damp the back e.m.f. and reduce the intensity of the arc.

For operation as a normal projector without the dissolve control unit in circuit a dummy plug which shorts together the interrupted lamp connections is inserted in the multi-way socket and slide change is controlled in the usual way from the projector remote control.

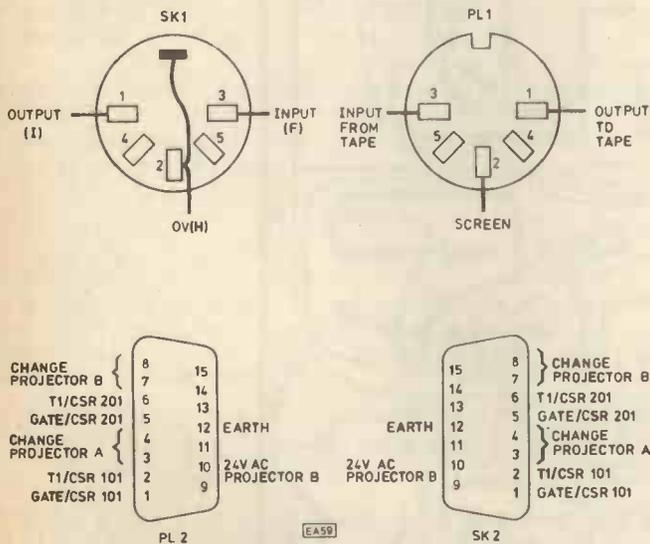


Fig. 20. Plug and socket connections

Constructors who build the triac into their projectors can revert to normal operation by connecting a resistor in series with a switch between T_2 and gate of the triac. With the switch open operation of the lamp circuit is controlled by the triac trigger pulses but when the switch is closed the triac is held in its conducting state and the lamp remains at full brightness.

SAFETY

An earth connection is shown in the circuit diagrams which connects the OV rail and all metalwork to mains earth via the projectors. It is important that this connection is

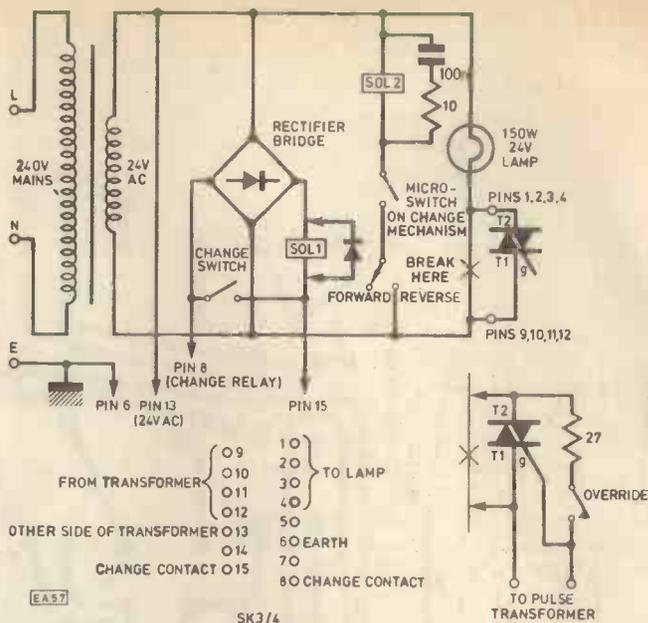


Fig. 21. Circuit diagram of projector with mods

made even if the projectors are double-insulated and do not have a ground connection because the control circuits and hardware are not protected by the double-insulation and could therefore become live in the event of a fault in either projector. If a two-core mains lead is fitted to either or both of the projectors replace it with a three-core 3A cable and connect the earth lead through to the control equipment via the multi-way connector as shown in the diagrams.

Do not rely on an earth connection made via audio equipment—if a hum loop results when separately earthed audio equipment is used remove the connection between the board (pin H) and the DIN connector (SK1, pin 2) to alleviate the problem but remember to replace it if isolated equipment is used at a later date.

ADJUSTMENTS

Only four adjustments are needed before the unit can be used. The object is to adjust the control circuit of each projector so that the lamp is just extinguished at one extreme of the range of the dissolve control knob and just at maximum brilliance at the other. This ensures that there is no "dead space" at either end of the control and that maximum brightness is achieved with no annoying residual image on the screen at the other extreme. Referring back to Fig. 3 we see that a projector is at maximum brilliance when its control voltage just reaches the bottom of the ramp signal (approximately $-2V$). The lower extreme of the ramp is fixed for both projectors by the common bias (set by R29/D9) to which C101 is discharged. Because this level is fixed it is necessary to adjust the control voltage at each end of its range to make certain that the bright projector is just at its brightest point. This adjustment is made with VR1 and VR3 which set the voltage seen by the wiper of VR2 at each end of its travel (Fig. 6).

Having set up the bright end of the range for each projector it is necessary to ensure that they just turn off at the other extreme of their range. A projector lamp is just extinguished when its maximum control voltage just exceeds the positive tip of the ramp. As we have already fixed the two extreme values of the voltage we must now adjust the peak value of the ramp at the dark end of the range for each projector. The adjustment is made by VR101 (VR102) which

varies the current generated by the source which charges C101 (C201) and therefore affects the slope of the ramp.

SETTING UP

The setting up procedure is as follows. First connect the two projectors to the triac housing via the heavy duty cables. It does not matter which projector is connected to each of the two cables as, although power is drawn from only one of the two projectors, both are wired up to supply power when connected to the appropriate lead. Next plug the multi-core connection from the triac housing into the control box, which should be switched to record with all preset adjustments set to mid range, and switch on the projectors. Check that operation of the dissolve control fades from one projector to the other although the adjustment of the lamps at each end of the range will almost certainly be wrong. With the control to the extreme of its travel at which projector A should be bright adjust the preset VR3 anti-clockwise until the projector will go no brighter and then reduce its setting until the lamp dims just perceptibly. Now increase the setting a little to reach maximum brightness. Set the dissolve control to its other extreme (B bright) and repeat the procedure using VR1 for the other projector. The adjustments of VR1 and VR3 interact so it will be necessary to repeat this sequence of events with the control set alternately at each end of its travel three or four times until no perceptible difference is found from one adjustment to the next.

When the bright end of the range is correct set the dissolve control to make A dark and adjust the current source preset VR101 until A is just extinguished. The best way of making this adjustment is to project a slide onto a screen in a darkened room and to adjust the preset until the image can just no longer be seen. When the setting is made in this way the projector lamp will be left with a dull orange glow which keeps it warm and speeds its response to rapid changes. Repeat the adjustment for projector B using VR201; the current source presets do not interact so it is only necessary to make one adjustment for each projector at opposite extremes of the dissolve control.

When the adjustments are complete check that the slide change control works at both ends of the dissolve control range, that the "twinkle" control swaps over the states of the two projectors and that the "superimpose" button forces them both to illuminate at half power. Finally, with the dissolve control set to either end of its range and with no audio input switch to play and check that the signal loss detector operates forcing both the projectors to switch on as if the "superimpose" button had been pressed.

You are now ready to make your first slide dissolve programme.

FREQUENCY SETTING

The adjustments already described are all that are required if the same unit is to be used both to record and to play your audio-visual presentations. Because the same VCO is used both during recording and during playback no adjustment of the VCO output frequency is needed. If, as may happen in a club for instance, different units are used for recording and playing back it is necessary to ensure that all the VCOs have the same brightness/frequency characteristic.

R15 and R16 control the frequency of the VCO at the upper and lower extremes of its control range. In order to make several units compatible with one-another it will be necessary to replace these resistors with pre-set potentiometers, possibly mounted so as to be accessible through the rear of the box.

In order to set up a group of units they should first be adjusted individually in the manner described in the previous section. One of the units is then nominated as "master" and its variable R15 and R16 set to mid-range. The output of this unit is then connected to each of the "slave" units in turn so as to carry out the adjustment of their VCO frequencies. With the "master" set to record and the "slave" set to play the master control potentiometer is set to the end of its range at which projector A is bright. R16 of the "slave" is then adjusted until its A projector is just at full brightness. R15 is next adjusted to set the brightness of "slave" projector B with the "master" control at the other extreme. The whole procedure must be repeated three or four times until no variation between successive adjustments is detected as the frequency setting controls will interact with one-another.

MAKING A RECORDING

The best recording technique to use will depend on the type of tape recorder involved. The output from the dissolve unit occupies one complete track of an audio tape recorder so those readers who, like the authors, do not possess a multi-track machine, will have to use one track of their stereo tape deck and record only mono sound. This is a limitation of course but the impact of a fully synchronised dissolve programme more than makes up for a lack of accompanying stereo sound.

Using a two-head machine (many cassette recorders are of this type) it will be necessary to record both the sound and the slide control tone simultaneously. The sound will first be assembled on an auxiliary tape machine if a number of sources (e.g. disc, tape, microphone) are to be mixed together and then played into the master recorder while the slide sequence controls are operated. With a relatively simple sound programme (e.g. disc only) it is possible to record sound and vision directly without the need for an extra tape recorder.

Three-head machines often allow you to play the contents of one track whilst recording on the other. In this case the sound programme can first be built up on one track, from a number of sources if required, and the visual control signal can later be added to the other track whilst listening to the sound.

Before making a recording it is vital to draw up a script indicating exactly how the intended sequence of dissolves, twinkles, etc. relates to the sound track. It is also helpful to practice by running through the programme several times



to check on timings and to learn to anticipate the operation of the controls.

To make a recording arrange the projectors so that their images are superimposed and load the slides alternately into each magazine with a black slide as the first in each set so that the screen is dark whichever projector is illuminated. With the black slide in each projector gate switch to record and adjust the dissolve control so that the projector that will show the first slide is *dark*, the other fully illuminated. Now switch on the tape recorder at least 30s before the first slide is due to appear and after about 15s press the slide change button to remove the black slide from the gate and replace it with the first one to be projected. When the slide is to appear fade it in with the dissolve control and as soon as it is fully illuminated press the change button to bring the second slide into the gate of the dark projector. Continue in this way alternately operating the dissolve control and the change button until the sequence is completed. It will probably be necessary to insert a black slide as the last in each projector so that the screen remains dark at the end of the presentation.

REPLAY

A smooth, efficient and unruffled beginning to a show adds greatly to the overall effect that it has on even the most uncritical of audiences so fumbling with projectors, wires and controls is best done before the viewers arrive.

The signal loss detector helps by allowing you to superimpose the images from the two projectors at half power simply by switching to "play" without an audio input applied. When the images are set correctly load the slides into the two projectors (making very sure that the right magazine

has been loaded into each projector) and bring the first (black) slide into the gate of each. Wind the tape to a position just after the beginning of the slide control tone and connect the output of the recorder to the control unit which is switched to "play".

When the moment arrives switch on the projectors and turn off the room lights. Now start the tape recorder and enjoy the show which will begin by first bringing a slide into the gate of the dark projector and then fading it up on to the screen.

We apologise for the omission of joint authorship and qualifications in Part 1. ★



Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for.....(amount).


PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss _____

ADDRESS _____

POSTCODE _____

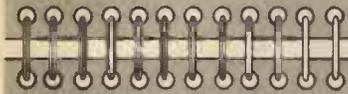Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53628. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.



INDUSTRY NOTEBOOK

By Nexus



Energy Saving

Among all the claims and counterclaims for energy saving systems, sane or crazy, it is refreshing to find a few hard facts and figures based on actual field experience.

The Italian company Telettra has recently published some details of a 2,000 mile national route network of microwave links they have engineered in co-operation with the New Guinea PTT Administration. The first links went in seven years ago and, taking advantage of the newest technology which allowed an extremely low power consumption of only 30W, the equipment was originally powered from dry cells needing replacement every six months. There was therefore no need for mains supply power lines or expensive diesel generation and, as New Guinea has a benign climate, no air conditioning was required. Despite the low power consumption of the repeater stations the capacity is 960 telephone channels plus TV.

Later expansion of the system also brought an up-date and the repeaters are now powered from solar cells with a secondary cell float. The system still demands a visit from a technician every six months to service the secondary cells and clean the solar panels, but over a five year period the cost of ten replacement sets of dry batteries is saved.

Drawing on this experience together with the falling cost of solar cells Telettra now say that the capital cost of a solar powered system breaks even with a diesel generator installation for local power up to 100W. In service the savings come from a nil fuel bill and no maintenance costs for diesel equipment. One of the great advantages of independent local power is that the equipment cabins can be sited anywhere. No approach roads are needed as would be the case for regular delivery to the site of diesel fuel, or the provision of overhead power lines or both.

Fine! But how about locations where temperature variations are such that the equipment needs an air conditioned environment? Conventional air-conditioning burns up more power than the equipment itself. Telettra says the answer lies in a new form of shelter exploiting the thermal characteristics of the materials from which it is constructed and the few watts of heat dissipation in the equipment itself. There are no moving parts and by changing the materials a passively conditioned shelter can be made to iron out temperature fluctuations in either tropical or arctic environments. For large installations the conditioning can be enhanced by natural circulation of fluids in a closed circuit.

Note the three-pronged systems approach. First, getting the power needs lower for a given function, second the development of a non-energy consuming conditioned shelter, third the timely application of solar cells as soon as the cost became economical. Telettra see a huge market for this type of equipment all over the world but especially in the vast undeveloped areas.

Augustine's Law

Norman R. Augustine, vice president technical operations, Martin Marietta Aerospace Corporation, following the example of Professor Parkinson, has established his own set of Laws. Augustine's are based on observation of trends in his own industry and projecting them into the future. The US defence budget increases yearly but so does the cost of tactical aircraft, the latter at a much greater rate. Extrapolating the figures Augustine suggests that by the year 2054 the total defence budget of the United States will buy only one tactical aircraft. Similarly, that before the tricentennial the US Government will employ more government workers than there are workers. Nonsense, of course, but with just that little grain of truth which makes you sit up and think.

Augustine ruefully reflects that in World War 2 all the technology was developed, built and applied and the war was won in just half the time it takes to develop a new military system today.

How Big?

GEC may be Britain's largest private employer (about 184,000 employees) as well as one of the best managed and consistently profitable. And annual turnover is now a healthy £2,500 million. But, as GEC management point out to their staff, there are much bigger fish in the sea. US General Electric (no connection) has nearly four times the turnover and Siemens of West Germany over three times. Matsushita and Toshiba of Japan are both much larger in turnover than GEC while French Thomson-Brandt and Brown Boveri of Switzerland and Germany are nudging from behind only barely short of GEC's sales performance.

Direct comparisons are, however, difficult because such conglomerates (including

GEC) have different interests. GEC, for example, unlike US GE, does not make aero engines or own coal mines. A more valid comparison is to try to separate out the various activities. Yet when we do this there is another shock. The whole of GEC's activities in electronics, automation and telecommunications accounts for only one fifth of group turnover. Take out the business in traffic lights, telephone exchanges and industrial automation and you might guess that in 'pure' electronics GEC is about level on turnover with Racal whose business is almost totally in professional electronics.

This is not to disparage GEC, clearly a powerful force in electronics world-wide, but it does impress on us the problem of comparability and that, after all, from this perspective some of the smaller British firms are relatively larger than we imagined.


It is now ten years since GEC swallowed up English Electric and AEL. Turnover was then less than £900 million. Today's £2,500 million turnover is achieved with 50,000 fewer employees, reflecting a mix of factory productivity gains and price inflation. Annual salary per employee is now averaging nearly £4,000, not far short of four times the 1970 figure which worked out, by present standards, at a lowly £21.80 per week—but you got more for your money in those days.

BPO Split

Apart from predictable adverse comment from union spokesmen on the postal side of the business, the Government's decision to split the present BPO into two corporations was generally welcomed. PO telecommunications can now romp ahead doing their own thing, and doing it well. Most people, users only of the domestic network, are unaware of the international aspects of the business, or of the immense capital sums involved.

Two recently announced projects are examples. TAT 7, due in service by 1983, will provide another 4,200 submarine cable channels between the UK and the USA. Britain has a 22 per cent share of the £100 million cost and ST&C will manufacture in the UK 2,700 miles of the cable at a cost of £30 million. Another £100 million project is INMARSAT providing by the mid-80s marine satellite communications for shipping. The BPO has an 11 per cent share in the project which will have its HQ in London. Yet another dish aerial is to be constructed at the Goonhilly complex to accommodate the new service. The BPO of course also has a major share in INTELSAT and is pressing ahead with international sales of the Prestel viewdata service.

Under the new arrangement, home and business subscribers will be able to use terminal equipment of their own choice provided it has no adverse technical effect on the public network. With the BPO monopoly of supply broken, there will be intense competition for the business providing a real challenge for home producers to exercise initiative. They have about two years in which to prepare. Failure means handing the bulk of the business to the Far East.

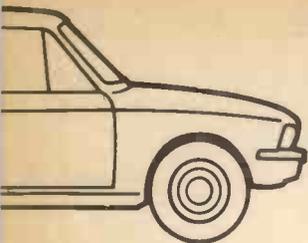

SPECIAL SUPPLEMENT

SOLID STATE CAR INSTRUMENTS

Ammeter - Engine Temperature Dwell Meter

Michael Tooley B.A. David Whitfield B.A. M.Sc.

No. 3 AMMETER

CONVENTIONAL moving iron ammeters usually offer poor calibration, whilst transient response is severely impaired due to the damping needed to prevent overshoot. These ammeters are often difficult to install since they require heavy duty leads (30A or more) from the battery.

The instrument described overcomes these limitations and provides linear response over a range of typically $\pm 25A$. Furthermore, the displayed current range is adjustable, thus permitting the user to preselect the actual range of indication to suit his particular needs. The module is basically a voltage measuring device with a high input impedance.

PRINCIPLE OF OPERATION

The usual arrangement of connections to a vehicle battery is shown in Fig. 1(a). A heavy duty copper braid links the negative terminal of the battery to the vehicle chassis. This earth strap has a very low resistance, typically 0.002Ω or less. The equivalent circuit of the battery connection, showing the earth strap resistance, is given in Fig. 1(b). The voltage drop developed across the earth strap resistance, R , is directly proportional to the current flowing in it. Furthermore, the polarity of this voltage will change according to whether the battery is being charged or discharged. The obvious disadvantages are that the resistance of the earth strap will vary from car to car, and the voltage developed is very small, typically 20mV for a current of 10A. Hence, in order to interface with the standard LM3914 display circuit, additional amplification is required, and the gain must be made variable to allow for variation in earth strap resistance from one vehicle to the next.


The obvious solution is to use a simple operational amplifier arrangement. There is, however, a problem associated with the fact that the input voltage (developed across the earth strap) varies in polarity about 0V (chassis potential). This is overcome by using a FET as a common source amplifier. See Fig. 2. The output voltage developed

No. 1 Battery Voltage Indicator, including a description of the LM3914, and No. 2 Rev' Counter appeared in *October* and *November*. This supplement incorporates the remaining three, plus details of warning and cascading.

across the drain load resistor, R_D , depends upon the drain current, I_D , and Fig. 3 shows how the drain current varies with the gate-source voltage, V_{GS} . By suitable choice of source resistor, R_S , the drain current will increase and decrease about a steady value according to whether the battery is being charged or discharged. Again, by appropriate choice of values, the drain voltage is made to be approximately half the supply voltage, and thus it will interface correctly with the operational amplifier stage which follows. The effects of supply voltage and temperature variations are reduced by using a balanced differential arrangement as shown in Fig. 4. An input protection circuit is necessary in the event of the earth strap ever becoming disconnected, since the excessive gate-source voltage would damage TR1. VR1 allows the circuit to be balanced and compensates for any difference in FET characteristics.

The complete circuit of the Ammeter is shown in Fig. 5. Input protection is provided by R3 and D1-D2. This ensures that the maximum input voltage excursion at the gate of TR1 is 600mV in either polarity. R5 and D13 provide a regulated supply for the differential stage and VR2 sets the voltage gain of the operational amplifier stage. D14 is used to remove the d.c. level from the output of the operational amplifier and allows correct interfacing with the display driver, which requires a 0 to 5V input signal. By suitable adjustment of VR1 and VR2 it is possible to produce a compatible signal at the input of IC2 over the desired current range.

NO HEAVY GAUGE WIRES
FAST RESPONSE
CLOSER CALIBRATION

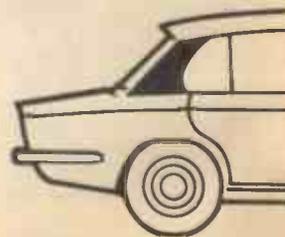

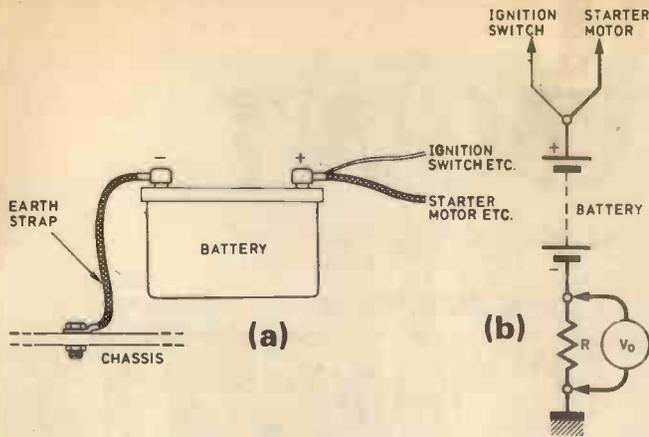


Fig. 1. (a) Conventional car battery connections; (b) Equivalent circuit of the battery earth strap

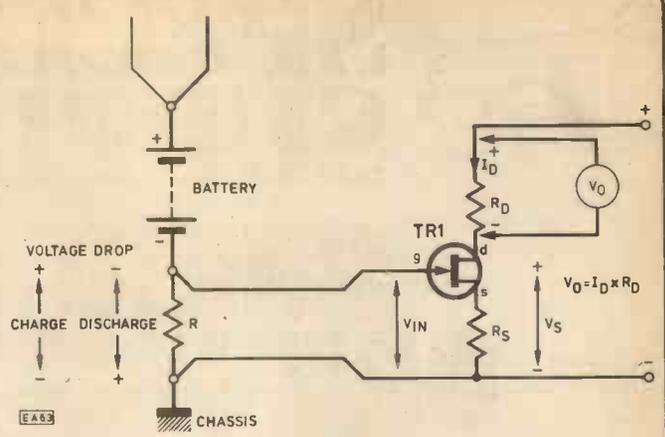


Fig. 2. Simple common source amplifier using an n-channel FET

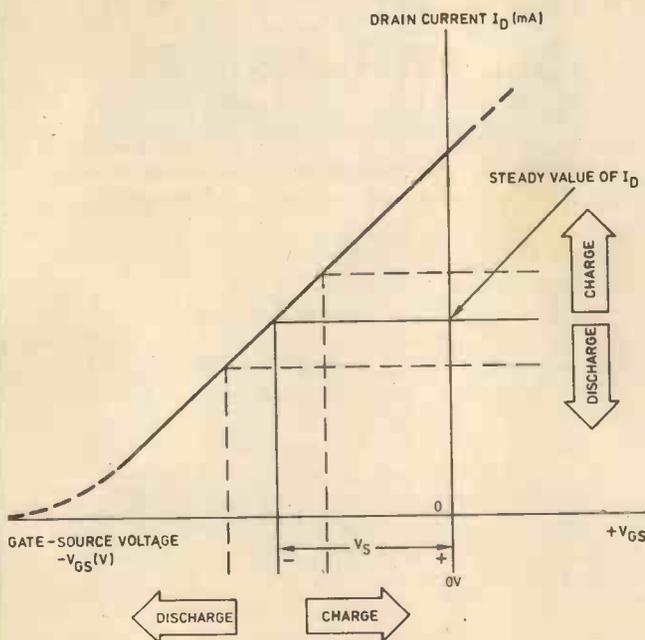


Fig. 3. Mutual characteristics $I_D/(V_{GS})$ of an n-channel depletion mode FET


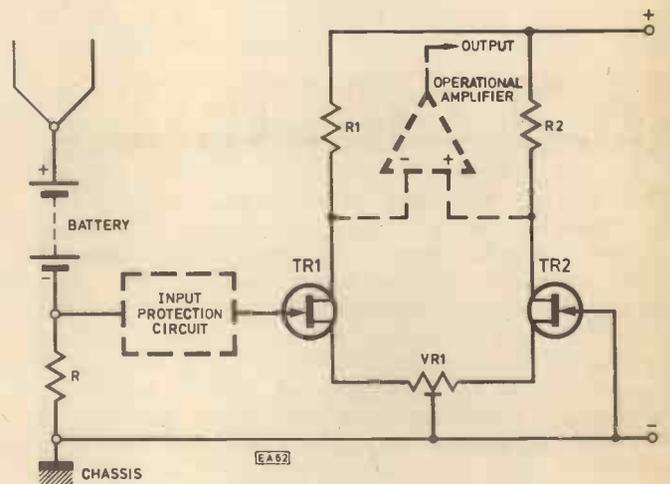


Fig. 4. Practical realisation of Fig. 2

Fig. 5. Circuit diagram of the Ammeter

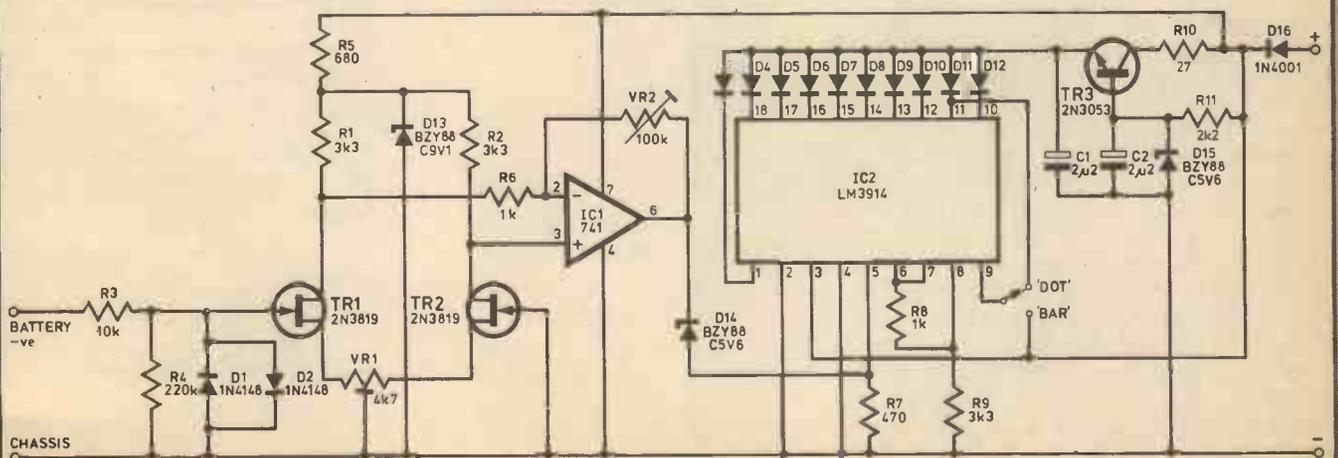

CONSTRUCTION

Two constructional examples are described. Individual constructors will most likely exercise their own preference as to the mechanical assembly of the instrument. The p.c.b. pattern is shown in Fig. 6 with the corresponding component layout given in Fig. 7. The printed circuit board is recommended for use when the instrument is for dashboard mounting in a rectangular "instrument pod". An alternative layout which uses 0.1 inch matrix stripboard is shown in Fig. 8. This method of construction is more appropriate when the instrument is to be of the hand-held type.

The pod mounted version uses standard 0.2 inch I.e.d.s whereas the hand-held instrument uses smaller TIL209 type devices. The MODE link in both layouts has been shown in the recommended DOT display position. The I.e.d.s may be colour coded to suit the constructor's preference and suggested colours are red for the five left-hand diodes (indicating discharge) and green for the five right-hand diodes (indicating charge).

TESTING AND CALIBRATION

Before installation it is recommended that the instrument is "bench checked" using the circuit in Fig. 9. This provides a variable input voltage of up to 100mV of either polarity. It thus simulates the approximate range of voltages that will appear across the earth strap, and constructors can check

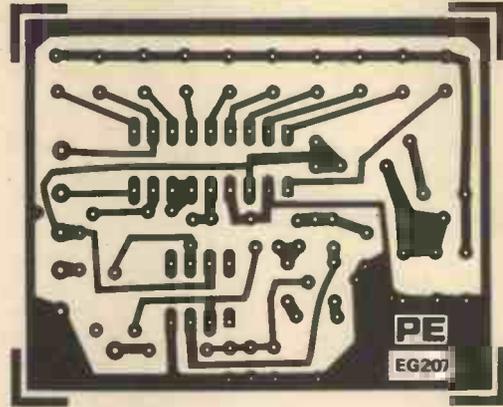
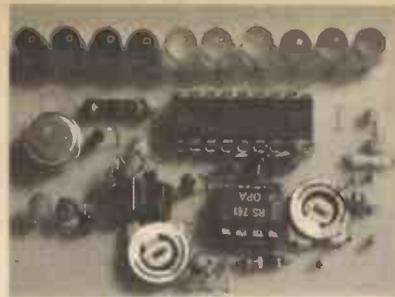


Fig. 6. Printed circuit layout (actual size)

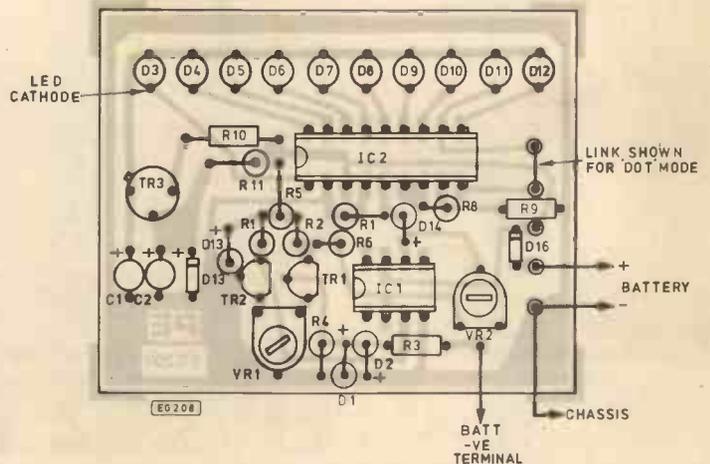


Fig. 7. Component layout

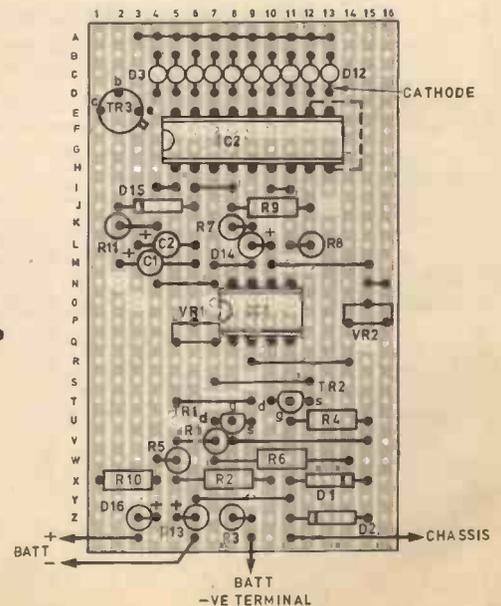


Fig. 8. Alternative stripboard layout

COMPONENTS . . .

Resistors

R1, R2, R9	3k3 (3 off)
R3	10k
R4	220k
R5	680
R6, R8	1k (2 off)
R7	470
R10	27 $\frac{1}{2}$ W 5%
R11	2k2
All resistors $\frac{1}{4}$ W 5% unless otherwise stated	

Potentiometers

VR1	4k7 miniature skeleton pre-set
VR2	100k miniature skeleton pre-set (Use horizontal pre-sets for PCB mounting, vertical for Veroboard mounting.)

Capacitors

C1, C2	2 μ 2 25V tantalum (2 off)
--------	--------------------------------

Transistors and Diodes

TR1, TR2	2N3819 (2 off)
TR3	2N3053
D1, D2	1N4148 (2 off)
D3-D12	10 off I.e.d.s—size and colour to suit
D13	BZY88 C9V1
D14, D15	BZY88 C5V6 (2 off)
D16	1N4001

Integrated Circuits

IC1	741
IC2	LM3914

Miscellaneous

Printed circuit board or stripboard
Moulded case as appropriate

that the circuit functions correctly before wiring to the vehicle. With the 1k variable resistor set to mid-position, VR1 should be adjusted so that D7 just extinguishes and D8 just becomes illuminated. Moving the variable in one direction should cause the green l.e.d.s (D8 to D12) to illuminate successively and in the other direction the red l.e.d.s (D3 to D7) should illuminate successively. VR2 should be adjusted so that the whole range is covered.

The instrument can now be fitted to the vehicle. Care should be taken to connect the input leads correctly (otherwise a reverse indication will result) using a length of two core cable which terminates at either end of the earth strap. Calibration in the vehicle can then follow, but it will first be necessary to know the power or current requirements of one or more items connected to the vehicle's electrical system.

With no electrical accessories operating and the ignition off, VR1 should be adjusted for centre zero indication as before. Now assume, for example, that two headlamps, each rated at 60W, are illuminated together with side lights and rear lights accounting for a further 60W. The total power from the battery (assuming that the engine is not running and no other accessories are connected) will be 180W which corresponds to a current of 180/12 or 15A. (In the example we have assumed that the battery is man enough to stand up to this load—in practice the terminal voltage of the battery would probably fall a little from the nominal 12V.) It is now merely a question of adjusting VR2 so that the third

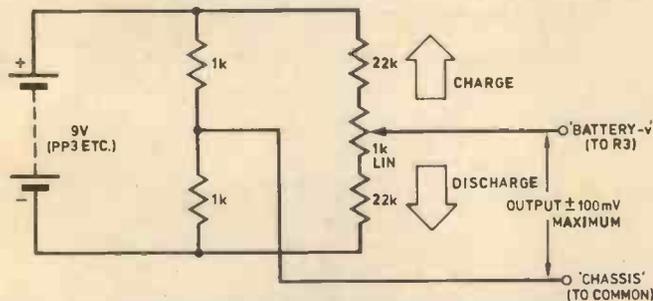


Fig. 9. Circuit for bench-checking the Ammeter

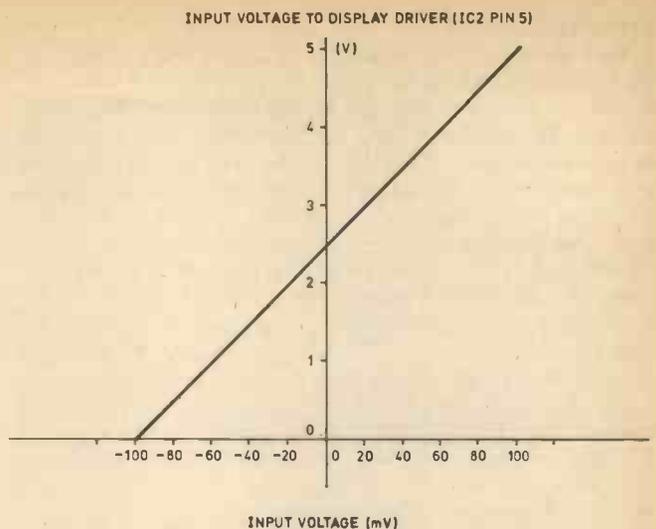


Fig. 10. Earth strap voltage versus display module input voltage — typical

red l.e.d. from the centre, D5, is illuminated (assuming calibration is 5A/LED or $\pm 25A$). If a different calibration is required it is simply a matter of adjusting VR2 accordingly. The setting of VR1 should now be checked once again and the car started. A momentary full scale discharge indication will be given as the starter motor is engaged. The charging indication should be checked. On most cars this will be between 5 and 15A. The following table gives a rough guide of the current consumption of various items:


Sidelights	3A
Rear stoplamps	5A
Rear screen heater	10A
Radio/cassette	less than 1A
Fan	3A
Interior light	$\frac{1}{2}$ A

No. 4 ENGINE TEMPERATURE

THE instrument described overcomes the accuracy limitations of conventional temperature gauges, and provides a linear response over a range of typically 0°C to 100°C. In addition, the response time is faster than with conventional gauges, and the displayed temperature range is adjustable, thus permitting the user to select a range of indication to suit his particular needs.

PRINCIPLE OF OPERATION

The transducer used is a general purpose silicon transistor. The base-emitter junction voltage, V_{BE} , which although normally quoted as approximately 600mV, varies with the junction temperature. Although the voltage change produced is rather small, it is a linear function of temperature and lies in the range from -2.0 to -2.5 mV/°C (ie, V_{BE} falls as the temperature increases). Over the desired 100°C temperature range the total change in V_{BE} will be approximately 225mV and, since the display module requires an input voltage of 0 to 5V, some additional amplification is necessary.

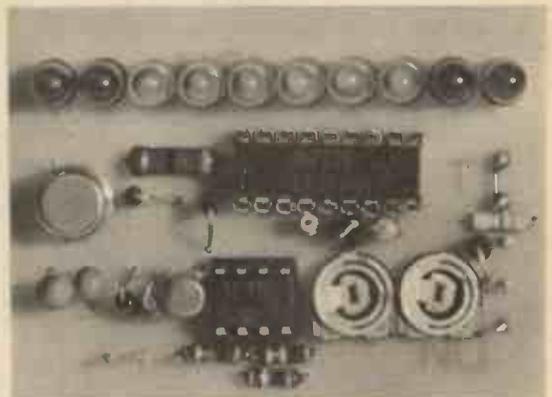

The basic temperature sensing arrangement is shown in Fig. 1. The base-collector voltage is fixed; a resistor is included in the emitter lead and, provided that the supply and bias voltages remain constant, V_{BE} gives an indication of the temperature of the transistor junction. An improved arrangement is shown in Fig. 2 where two transistors are connected

in a differential configuration. This is important in reducing the effects of supply voltage variation which in a vehicle can be as much as 25%. If the circuit is exactly balanced, with R_1 equal to R_2 and identical transistors, the output voltage will be zero, provided that the two transistors are at the same temperature. Any difference in temperature will cause an imbalance in the circuit and a corresponding output voltage. Ideally TR2 should be closely maintained at a constant temperature, however in practice the interior temperature of a vehicle is usually regulated to a comfortable and fairly constant level (between 20 and 25°C) by the driver. The temperature sensor, TR1, is mounted at some convenient point on the engine block and thus is kept at the working temperature of the engine.


Fig. 3 shows the practical realisation of Fig. 2. A Zener diode is used to stabilise the base-collector voltages of TR1 and TR2. The emitters of TR1 and TR2 are connected to the differential inputs of an operational amplifier. This responds to the difference in the two base-emitter voltages. The operational amplifier also provides the additional voltage gain necessary for interfacing with the display module. VR1 provides a means of balancing the circuit and compensating for any mismatch in transistor characteristics.

The complete circuit of the engine temperature indicator is shown in Fig. 4. The gain of the operational amplifier stage is made adjustable by means of VR2 and, since the output of the stage is at about half-supply potential (approximately 5V), a Zener diode, D2, is used to remove the d.c. level before the signal is applied to the display driver, IC2. By suitable adjustment of VR1 and VR2 it is possible to produce a compatible 0 to 5V signal at the input of IC2 over the desired temperature range.

CONSTRUCTION

As with the other instruments in this series, two constructional examples are described. Fig. 5 shows the printed circuit track pattern and Fig. 6 the corresponding component layout recommended for use in a dashboard instrument for mounting in a rectangular instrument pod. The alternative layout using 0.1 inch matrix stripboard which is suitable for a hand-held instrument is shown in Fig. 7. The pod mounted version uses standard 0.2 inch l.e.d.s whereas the hand-held instrument uses smaller TIL209 type devices. The wire MODE link in both layouts has been shown in the recommended Dot display mode. The l.e.d.s. may be colour coded,

Fig. 4. Circuit diagram of Engine Temperature Gauge. Note: D2 should be BZY88 C4V7

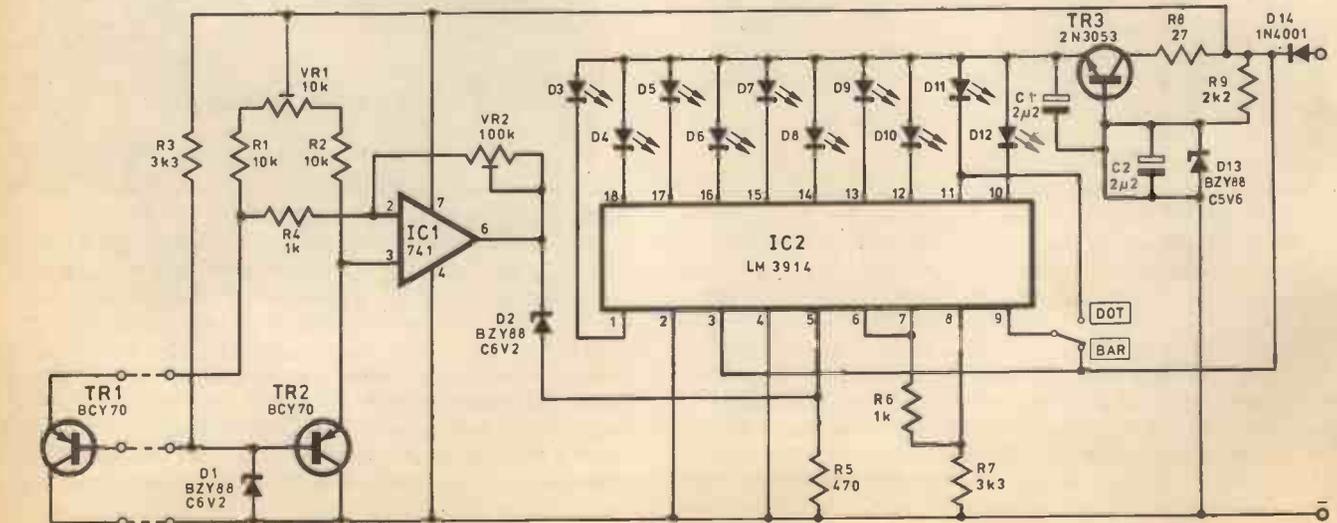

EG2.13

Fig. 1. Base-emitter voltage varies with temperature of transistor junction

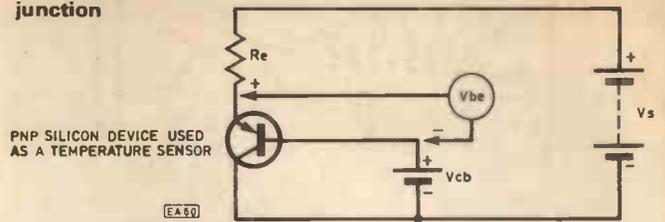


Fig. 2. Differential configuration to reduce the effects of supply and bias voltage variations


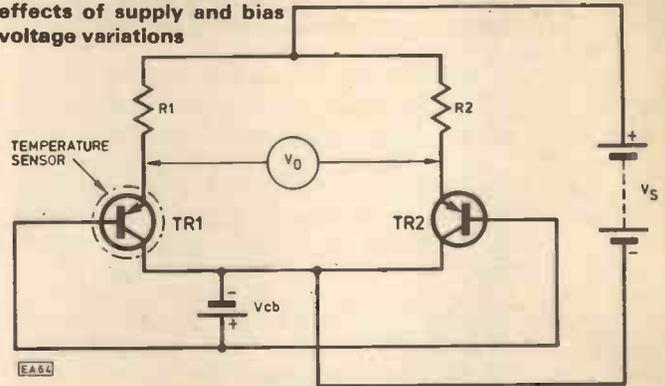


Fig. 3. Practical realisation of Fig. 2

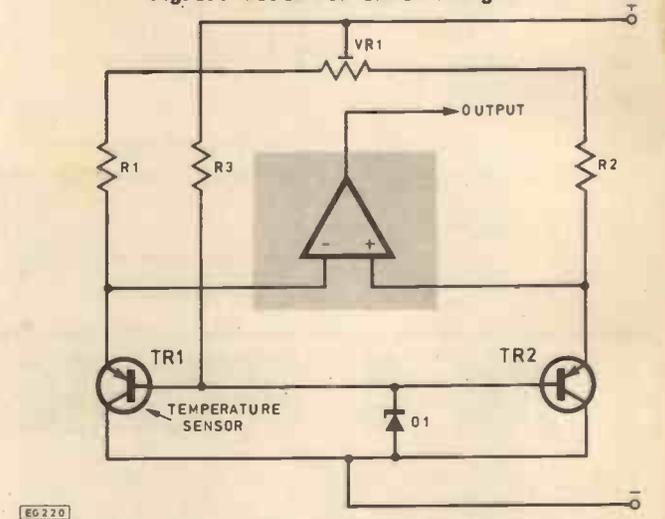

EG2.20

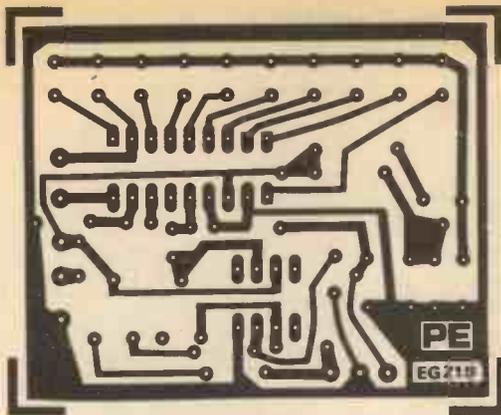


Fig. 5. Printed circuit layout (actual size)

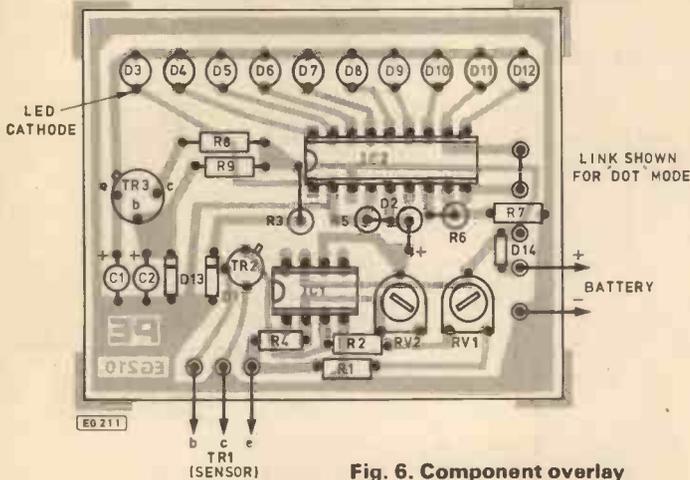


Fig. 6. Component overlay

sensor, TR1, should be placed in the ice taking care not to immerse the leads. VR1 is then adjusted until the extreme left hand i.e.d., D3, just extinguishes (leaving the rest of the display blank). TR1 should then be placed in a cupful of water that has just been boiling, again taking care not to immerse the leads. This will produce a temperature of around 90 to 95°C. (Do not use a kettle since the steam produced can cause condensation around the transistor leads.) VR2 is then adjusted so that the extreme right hand i.e.d., D12, is illuminated. The procedure should be repeated, again adjusting VR1 at one end of the range and VR2 at the other. The calibration can, of course, be checked using an accurate thermometer if available. Having completed the calibration, the instrument is ready for fitting to the vehicle.

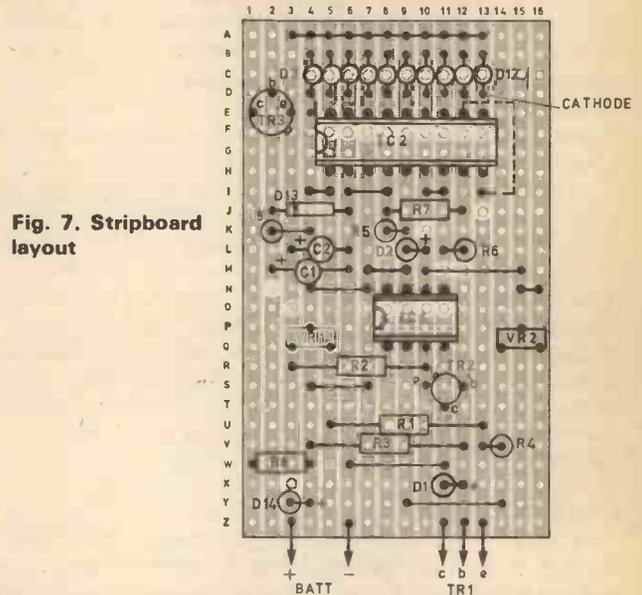


Fig. 7. Stripboard layout

COMPONENTS . . .

Resistors

R1, R2	10k (2 off)
R3, R7	3k3 (2 off)
R4, R6	1k (2 off)
R5	470
R8	27 ½W
R9	2k2
All resistors ½W 5% except where stated	

Potentiometers

VR1	10k	min. skel. pre-set
VR2	100k	min. skel. pre-set
(Use hor. pre-sets for p.c.b. mounting, vert. for stripboard mounting.)		

Capacitors

C1, C2	2µ2 25V tantalum
--------	------------------

Transistors and Diodes

TR1, TR2	BCY70
TR3	2N3053
D1	BZY88 C6V2
D2	BZY88 C4V7
D3-D12	i.e.d.s to suit (10 off)
D13	BZY88 C5V6
D14	1N4001

Integrated Circuits

IC1	741
IC2	LM3914

Miscellaneous

Printed circuit board or 63 x 40mm of 0.1 inch strip-board
Moulded case as appropriate

and suggested colours are red for the two i.e.d.s on either extreme and yellow for the others. Hence a red "warning indication" will be given when the engine temperature is outside the range 20°C to 80°C.

CALIBRATION

Calibration is quite simple and, if necessary, can be carried out without the aid of a thermometer. VR1 should be used to set the low temperature indication of the display and VR2 to adjust the range of display. An approximate calibration temperature of 0°C can be obtained using a cupful of crushed ice which is just on the point of melting. The temperature


CONNECTION TO THE VEHICLE

The temperature sensor, TR1, should be either bonded to the engine block using epoxy adhesive or held in place by a small metal clamp. The metal case of the transistor is connected to the collector and may thus safely be earthed to the chassis of the vehicle. Care should be taken to insulate the transistor leads and ensure a sound mechanical termination. A short length of three-core cable should be used to connect the temperature sensor to the instrument pod. Alternatively a length of two-core screened cable may be used in which case the earth/collector connection is the screen itself. ★

No. 5 DWELL METER

THE dwell angle of the contact breaker cam is of great importance to engine performance, particularly at higher rev's. The dwell angle is the angle through which the cam turns while the contact breaker points remain closed and depends upon the angular separation of the cam lobes on the distributor shaft, and the maximum gap between the points. It must be sufficiently large to enable the soft iron core of the ignition coil to become magnetically saturated to provide a good spark, yet not so large as to cause over-dissipation. Too small a dwell angle will result in a low spark voltage, and poor combustion. This may be caused by:

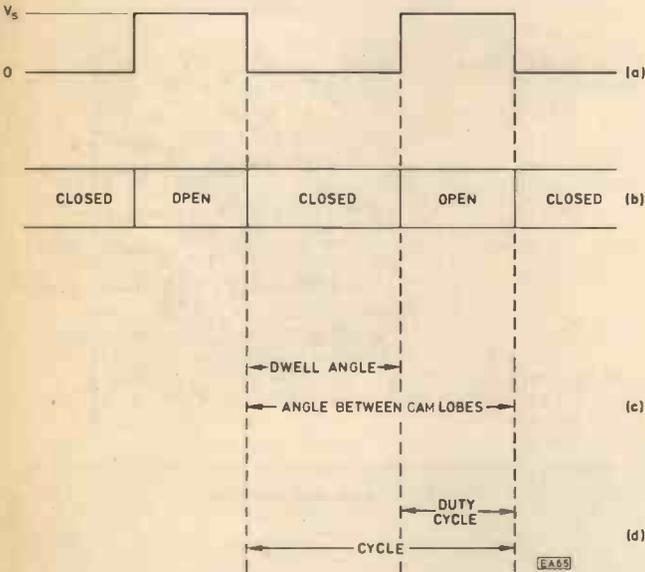- (a) The contact breaker gap being too large.
- (b) The cam being excessively worn.
- (c) The cam and shaft bearings being excessively worn.



Large dwell angles will result in overloading of the capacitor and burning of the contact breaker points at low speeds. Too large a dwell angle is usually due to the gap of the contact breaker being set too small.

The correct dwell angle for a particular vehicle will be found in the workshop manual. Generally, the dwell angle is usually slightly less than two-thirds of the angle between the cam lobes. In a 6-cylinder distributor, for example, the cam lobe separation is 60 deg and the dwell angle is about 36 deg (comparable figures for a 4-cylinder unit are 90 deg and 52 deg, respectively).

MEASUREMENT OF DWELL ANGLE

Measurement of the contact breaker dwell angle is most easily accomplished by observation of the voltage waveform across the contact breaker points. An idealised representation of this waveform is shown in Fig. 1(a).

A straightforward method of measuring dwell angle requires only a moving coil d.c. voltmeter and a calculator. The mean value of the waveform in Fig. 1(a) is given by:

$$V_{mean} = V_s \times \frac{\text{Angle between cam lobes} - \text{Dwell angle}}{\text{Angle between cam lobes}}$$

Fig. 1. (a) Breaker points voltage waveform. (b) Points condition; (c) Timing angles; (d) Duty cycle

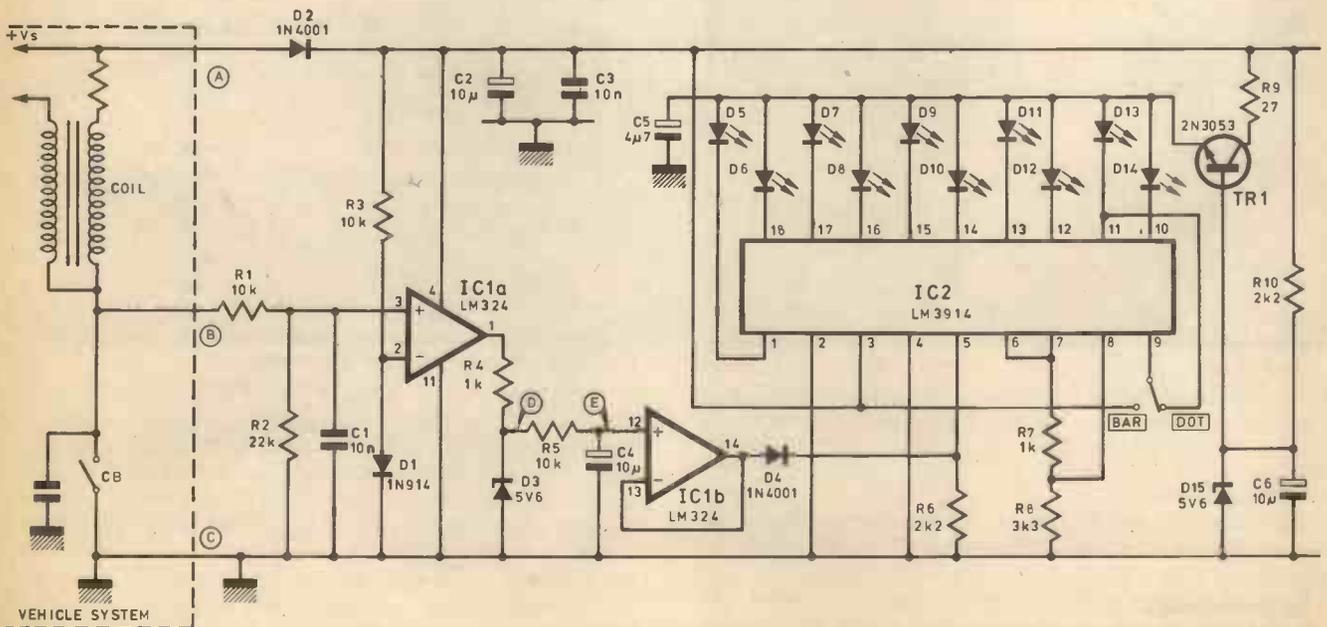


Fig. 2. Circuit diagram

The values of V_{mean} and V_s may be measured at the two ends of the ignition coil primary winding. The moving coil movement will average the waveform and the dwell angle may then be found from:

$$\text{Dwell angle} = \text{Angle between cam lobes} \times \frac{V_s - V_{mean}}{V_s}$$

This technique is tedious when repeated measurements are required.

Ideally, dependance upon the variable value of V_s should be eliminated, allowing a simple scaled meter to be used, whereby the *duty cycle* of the waveform, rather than the *voltage* is measured. The dwell angle is then:

$$\text{Dwell angle} = \text{Angle between cam lobes} \times \frac{100\% - \text{Duty cycle}}{100\%}$$

The calibration now depends only upon the angle between the cam lobes. This meter works on duty cycle and displays dwell on a scale which may be calibrated to 90 deg, 60 deg or 45 deg for distributors with 4, 6 or 8 cam lobes, respectively.

CIRCUIT DESCRIPTION

The circuit diagram is shown in Fig. 2. The contact breaker voltage waveform is sampled at point "B", and then filtered by R1, C1 and R2. The filtered signal is applied to the non-inverting input of op. amp. IC1a, which is arranged as a voltage comparator. The combination of R3 and D1 sets the switching threshold such that the voltage at point "B" must exceed approximately 1 volt to cause the output of the comparator to go "high".

COMPONENTS ...

Resistors

R1, R3, R5	10k (3 off)
R2	22k
R4, R7	1k (2 off)
R6, R10	2k2 (2 off)
R8	3k3
R9	27 1/2W
All 1/4W 5% unless otherwise stated	

Capacitors

C1, C3	10n ceramic (2 off)
C2, C4, C6	10µ/16V elect (3 off)
C5	4µ7/10V elect

Transistors and Diodes

D1	1N914 or similar
D2, D4	1N4001 (2 off)
D3, D15	BZY88 C5V6 Zener (2 off)
D5-D14	L.e.d.s to suit physical requirements (10 off)
TR1	2N3053, BFY50 or similar

Integrated Circuits

IC1	LM324
IC2	LM3914

Miscellaneous

Stripboard or p.c.b. Moulded case

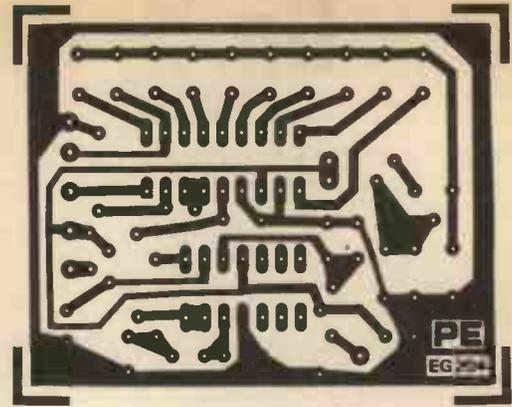


Fig. 3. Printed circuit layout (actual size)

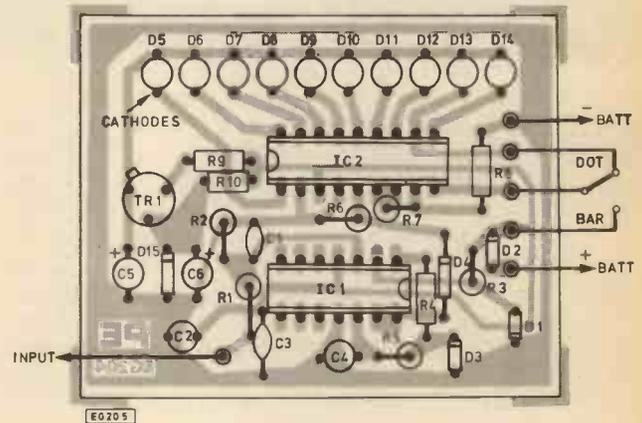


Fig. 4. Component overlay

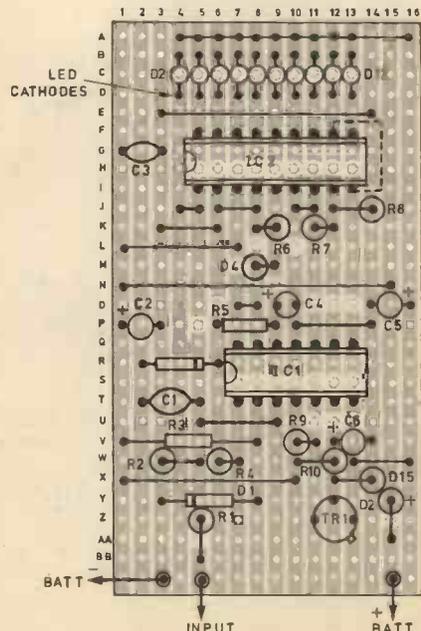


Fig. 5. Alternative stripboard layout

The comparator output is a rectangular waveform limited to the output saturation levels of the op. amp., which in this application are approximately 600mV and $(V_{\text{supply}} - 1.2)$ volts for the "low" and "high" states respectively. The dependence of the "high" level on the supply voltage is eliminated by the clipper circuit, R4 and D3, and the result is a signal between the levels of 600mV and 5.6 volts.

The average value of the signal at point "D" varies linearly between 600mV and 5.6 volts as the duty cycle varies between 0 and 100%. This average value is developed at point "E" by the integrator formed by R5 and C4, and is subsequently buffered by IC1d to minimise loading effects. The 600mV d.c. offset is removed by D4, and the voltage across R6 varies from 0 to 5V as the duty cycle at the input varies from 0 to 100 per cent to correspond to dwell angles from maximum (angle between the cam lobes) to zero, respectively.

The time constant of the display response is determined

by the integrator circuit of R5 and C4. The remainder of the circuit comprises the standard display module.

PRACTICAL DETAILS

The constructional details for the dwell meter closely follow those outlined for the earlier instruments in the series. A p.c.b. design is shown in Fig. 3, with a corresponding component layout in Fig. 4. A stripboard layout for a hand-held test instrument is shown in Fig. 5.

Both instrument variants are shown wired for dot mode display. The display scale should be calibrated $90^{\circ}-0^{\circ}$, $60^{\circ}-0^{\circ}$, $45^{\circ}-0^{\circ}$ for 4, 6, 8-cylinder distribution units respectively. The connections for use are the same as those for the tachometer (November), and are summarised again in Fig. 2. A higher resolution display of the dwell angle may be obtained by the use of additional display driver devices, described later.



HAZARD WARNING & CASCADING...

THERE are many occasions when it is imperative that the driver receives an immediate warning that all is not well under the bonnet. The two techniques described below illustrate methods of producing hazard warnings in sharp contrast to the normal indication given by the instrument concerned. The examples provided should enable constructors to modify any of the instruments previously described in the series for added hazard warning indications. The enthusiastic constructor will doubtless wish to further exploit the many features of the LM3914 and, in this case, the suggestions given will merely provide a starting point.

MODE SWITCHING

An obvious method of attracting the driver's attention to an instrument operating in Dot mode is to change the display to Bar mode whenever a pre-determined level is exceeded. In practical terms this involves switching the display mode input (pin 9 of the LM3914) electronically, and since the particular l.e.d. illuminated relates to the input level, it is possible to sense the voltage across the l.e.d. concerned and use this to activate an electronic changeover switch. If the voltage at the input of the standard display module (pin 5 of the LM3914) were to be increased slowly from 0 to 5V, and the last l.e.d. used for setting the display into Bar mode, then the display would operate in the normal Dot mode until the last l.e.d. became illuminated, at which level the display would change to Bar mode. In practice any one of the l.e.d.s could be used for determining the changeover point. For most applications it is suggested that either l.e.d. No. 8 or l.e.d. No. 9 is used to provide the changeover (corresponding respectively to 80% and 90% of full range).

Fig. 1 shows a simple practical arrangement which may be used in conjunction with the standard display module. The display mode is changed from Dot to 'bar' whenever D8 is illuminated. A reference voltage is provided by means of R3 and D9. This sets the potential at the emitter of TR1. When D8 is extinguished the voltage at pin 12 of the LM3914 is "high" and base current flows through R1, effectively saturating TR1 and thereby reducing the collector voltage and the mode input voltage at pin 9 of the i.c. to a low value. The display then operates in Dot mode. When D8 is illuminated the voltage at pin 12 of the LM3914 is

low (approximately 3V), and thus the base-emitter junction of TR1 is no longer forward biased. TR1 is therefore held off and the voltage at its collector rises to be almost equal to the supply (12V). Hence the mode input is made approximately equal to the supply voltage and the display operates in Bar mode. It is important to note that, if the display indication falls back below the hazard threshold determined by the particular l.e.d. selected, the display then reverts to the normal Dot mode of operation.

TR1 can be almost any n.p.n. silicon transistor having a current gain of 100 or more. A 3.3V Zener diode of at least 250mW rating should be used for D9. The additional components can readily be mounted on a small piece of stripboard and wired to the existing circuitry.

FLASHING BAR DISPLAY

Where a Bar mode display is used (as would normally be the case with a rev. counter, for example) an alternative technique for gaining the driver's attention must be used. In this case, probably the most dramatic method is to make the entire display flash on and off whenever a safe level is exceeded. Since the current drawn from the reference output (pin 7 of the LM3914) determines the brightness of the l.e.d.s in the display it is possible to turn off the display by reducing this current to zero. The circuit of Fig. 2 shows a simple arrangement for flashing the display whenever D8 is illuminated. The falling potential at the cathode of D8 when it first becomes illuminated is applied, by means of C1 and R2, to the reference output of the display driver. R3 is included to ensure that D8 becomes extinguished along with the other l.e.d.s in the display when the display is momentarily turned off. The LM3914 is programmed to produce a constant current in each of its l.e.d. loads and hence the additional resistor in series with D8 does not affect its brilliance. With the component values given the circuit operates at a rate of approximately 90 flashes per minute with a duty cycle of around 30%. It is important to note that, because the reference output is used to modulate the display, the top end of the resistive divider chain which feeds the non-inverting inputs of the ten comparators within the LM3914, must be supplied from a separate regulated supply. This can conveniently be derived from the supply rail which feeds the l.e.d.s (nominally 5V) however, since Bar

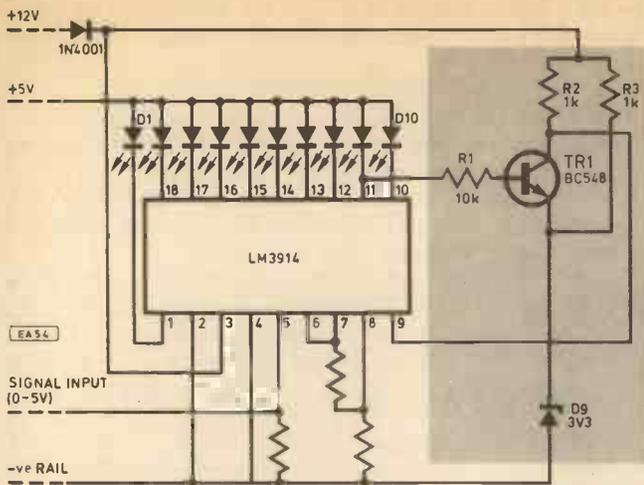


Fig. 1. Circuit to provide Dot-to-Bar mode changeover triggered by I.e.d. 8

mode is employed and a relatively high current is drawn from this rail, it is recommended that the simple discrete component series transistor regulator used with the standard display module be replaced with a conventional 5V integrated circuit regulator.

Where the flashing circuit is to be fitted to an existing circuit board it is recommended that the extra components are assembled using a small piece of stripboard. The regulator should be fitted with a suitable heatsink (19°C/W should be adequate) and capacitors C2 and C3 should be fitted as close as possible to the pins of the regulator. The existing transistor series regulator arrangement should be disabled by removing the transistor and associated components from the board. It will also be necessary to modify the board

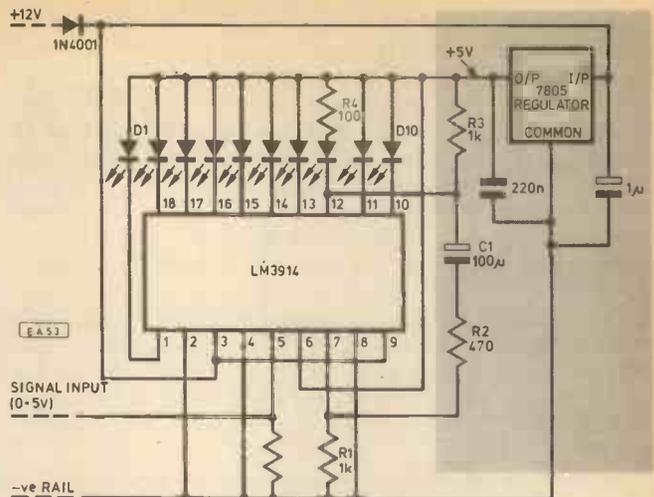


Fig. 2. Circuit to provide flashing bar display triggered by I.e.d. 8

wiring around pins 6 and 7 of the LM3914. R1 and R4 can conveniently be incorporated on the existing board and five connecting wires will be necessary.

DISPLAY RESOLUTION ENHANCEMENT

The basic display module described in this series makes use of a display consisting of 10 I.e.d.s. It is often desirable, however, to know the value of the measured parameter to finer limits than can be read from the basic display module. This means that a greater number of I.e.d.s must be used, for example, to display 0-6000 r.p.m. in steps of 200 r.p.m. requires 30 I.e.d.s.

The design of the LM3914 integrated circuit means that the display is conveniently increased in multiples of 10

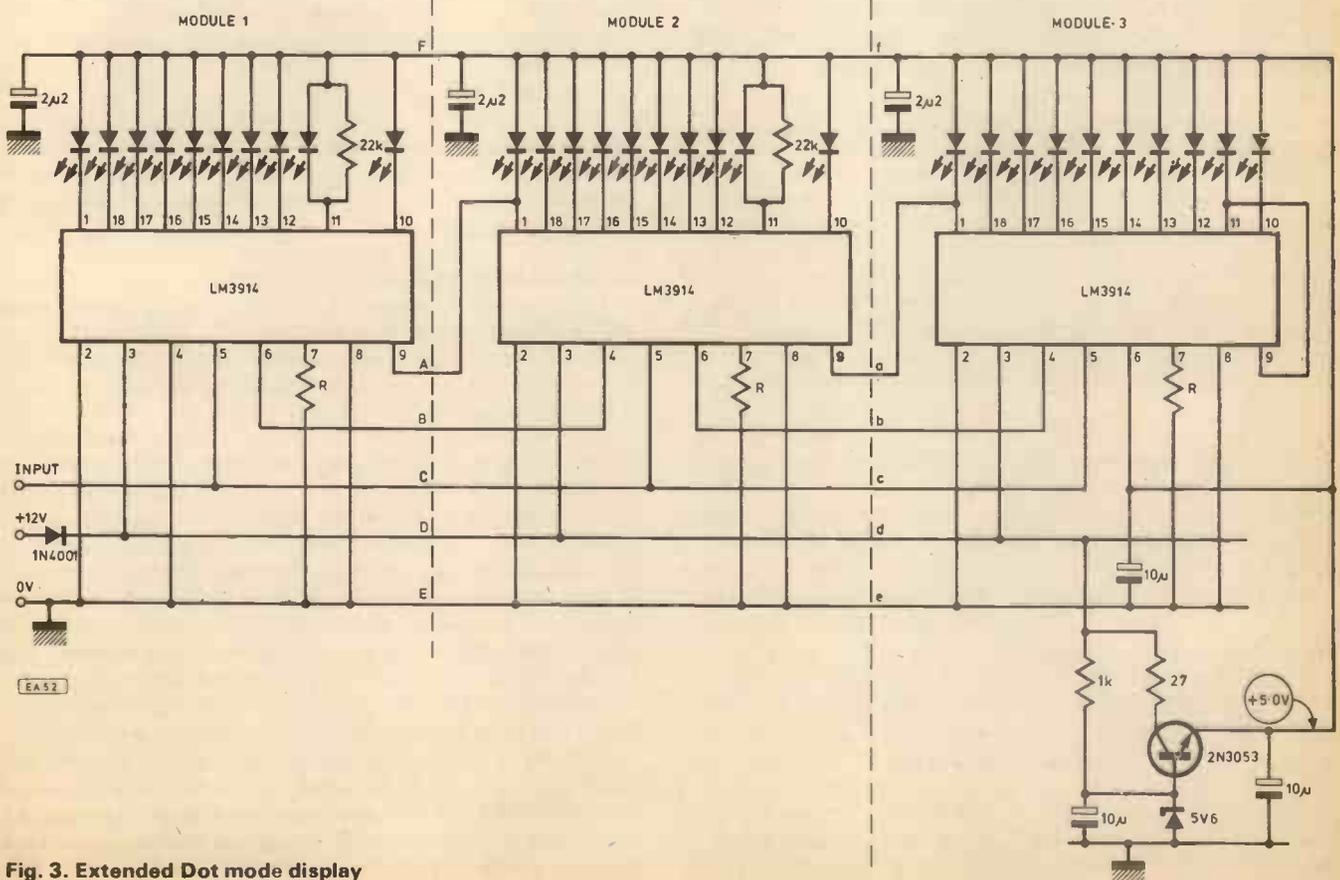


Fig. 3. Extended Dot mode display

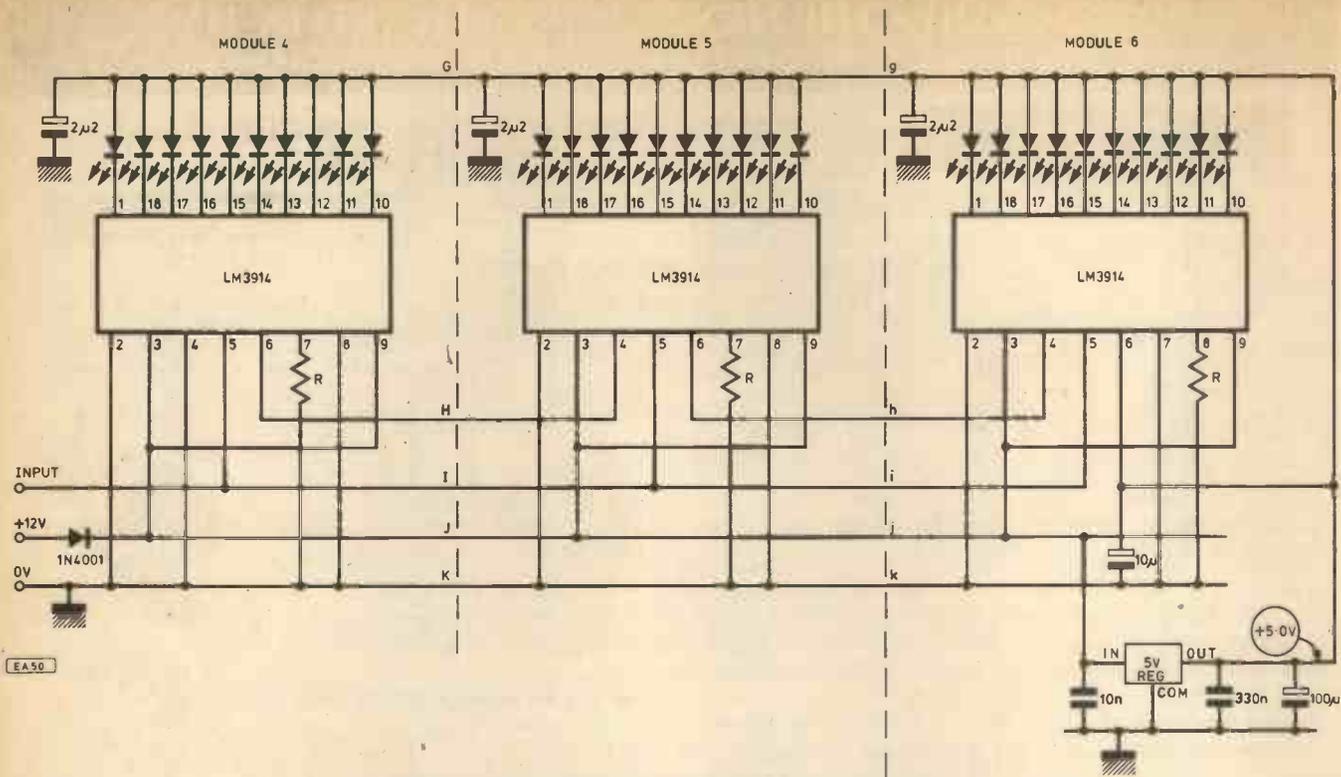


Fig. 4. Extended Bar mode display

I.e.d.s; with the precise circuit details varying slightly depending upon the choice of Dot or Bar mode for the display format. In this way the display may be extended up to 100 I.e.d.s.

EXTENDED DOT MODE DISPLAYS

The "chaining" of display devices to provide an extended Dot mode display employs some as yet unused characteristics of the Mode Select Amplifier in the LM3914. The Mode Select Amplifier looks at three inputs to decide whether to show a Dot display, a Bar display, or a Dot display using multiple LM3914 devices. The three inputs to the Mode Select Amplifier are from pin 9 (mode), pin 3 (V+), and from pin 11 (D9); the last two being connected internally.

Holding the mode pin to within 20mV of the voltage at pin 3 will cause a bar graph to be displayed. A dot mode display will appear if pin 9 is 200mV or more below the voltage at pin 3. If the mode pin is 900mV below the voltage at the anodes of the I.e.d.s, D10 will be turned off. This last feature is exploited in the extended dot mode displays to be discussed and is used to turn the last I.e.d. of one LM3914 off when the first I.e.d. of the next device up the chain is turned on.

The circuit diagram for a 30-I.e.d. dot mode display module is shown in Fig. 3. The I.e.d. current is set by the value of the resistors R, to a value given by:

$$I \approx \frac{12.5}{R} \text{ (R is typically 1 k}\Omega\text{)}$$

The full-scale calibration of the display module shown depends on the exact value of the 5 volt rail, i.e. the full-scale value is set by the voltage at pin 6 of the LM3914 in

module 3. A 22k resistor is also required in parallel with D9 in modules 1 and 2 to ensure correct operation of the Mode Select Amplifiers.

A 20-I.e.d. display may be constructed by omitting module 2 from the circuit of Fig. 3, and making direct connections A-a, B-b, C-c, D-d, E-e, and F-f. Alternatively, the display may be extended beyond 30 I.e.d.s. by breaking the links at A, B, C, D, E, and F, and inserting additional modules of type 2 as required.

EXTENDED BAR MODE DISPLAYS

Bar graph displays of 20 or more I.e.d.s are relatively simple to build. All that is required is that the mode pin of each LM3914 is connected to pin 3 of the same LM3914. The circuit diagram for a 30-I.e.d. bar graph display module is shown in Fig. 4.

As with the extended dot mode display, the full-scale input voltage for the module is set by the voltage at pin 6 of the LM3914 in module 6. The power dissipation of the regulator for the anode supply to the I.e.d.s requires careful consideration. A stable 5.0 volt output is required, with the regulator capable of dissipating the surplus power associated with a full-scale display. For example, a 100-I.e.d. display with $R = 1\text{ k}\Omega$ would involve a regulator dissipation of 8.75 watts when operated from 12V supply, (the individual I.e.d. current would be 12.5mA). It is recommended, therefore, that an integrated circuit regulator be used as shown in Fig. 4, and that adequate heat-sinking arrangements be made.

Displays of 20 I.e.d.s should omit module 5 from the circuit given in Fig. 4, and links should be inserted at G-g, H-h, I-i, J-j and K-k. For displays of more than 30 I.e.d.s, the links should be broken at G, H, I, J, and K, and additional modules of type 5 inserted as required.



FROM CASIO - THE NEXT STEP FORWARD IN TIME

Casio's new Lithium battery, lasting up to 5 years or more, totally eclipses most SOLAR watches.

Hand held COMPUTER GAMES

We have selected the best available
It's you against the computer...

GRANDSTAND

4-in-1
Calculator/Auto Race/
Code Breaker (as
Mastermind)/Blackjack.
Convenience - skill -
brainpower - luck.

£22.50

UFO MASTER BLASTER STATION

More sophisticated than Destroyer. Guide
missiles to destroy UFO's which may change
course or disappear!

£22.50

AMAZE-A-TRON

Over 1 million mazes to defeat! 1 or 2 players.
Electronic sound effects.

£17.25

GRANDSTAND DESTROYER

Protect your convoy from torpedoes.

£14.95

GRANDSTAND SOLITAIRE

Absorbing and challenging.

£14.95

DIGITS (As Mastermind)

Deduce four random numbers.

£13.95

MICROPROCESSOR

FAIRCHILD GRANDSTAND

Video Entertainment Computer

£74.95

19 plug-in
pre-programmed
memory cartridges
now available.

Each £12.50

NEW SCIENTIFICS With non-volatile memory

CASIO FX-2600
Ultra slim - 5/32in
6 + 2 digit LC Display.
43 scientific functions.
Non-volatile memory.
Auto power off 6 levels
parenthesis. Standard
deviations. R to P, P to R,
ENG, FIX, SCI, RND
and Random number keys.
5/32in x 2 1/4 x 4 1/4in.

£19.95

CASIO FX-3200
As above but 10 digits.

£21.95

CASIO FX-310
As FX-2600 but 50
scientific functions,
1/4 x 2 1/4 x 5 1/4in.

£17.95

CASIO FX-510
10 digit version of above.

£19.95

HAVE A FABULOUS TIME THIS CHRISTMAS - FROM TEMPUS

From CASIO's New Collection we present
some of the most sophisticated executive
watches available today.

ALARM CHRONOGRAPH

Displaying hours, minutes, seconds, date,
am/pm; or Hours, minutes, alpha day, date,
am/pm. With automatic 28, 30, 31 day calendar.

83SQ-27B

4 YEAR BATTERY.
1/10 second chrono to
12 hrs, measuring net,
lap and 1st and 2nd place
times. 24 hour alarm.

Hourly chimes.

Backlight. Mineral glass,
Stainless Steel encased,
Water resistant to 66 feet.
(£31.95) **£27.95**



Displaying hours, minutes, seconds, day; and
with day, date, month and year perpetual
automatic calendar.

Available soon:

81QS-33B

5 YEAR BATTERY
Chrome plated case
WR to 66 feet
(£31.95)

£27.95

1/100 second chrono to
7 hours.
Net, lap and 1st and
2nd place.
Selectable 12 or
24 hour display.



24 hour alarm.
Selectable hourly chime
facility. Backlight.
Mineral glass face.

81CS-36B

As above but:
Stainless steel case.
WR to 100 feet.
(£39.95)

£35.95



HONG-KONG WATCHES

Most low cost digital watches come from Hong
Kong. In our experience these are proving un-
reliable, particularly those with multi-function
modules, with very high failure rates. Repairs
can take as long as three months and replacement
parts are not always available even
replacement plastic glasses!

Compare this with Casio, Citizen and Seiko,
whose failure rate is typically under 1%. Casio's
service time of 2-3 weeks and comprehensive
spares and we ask you:-

**ISNT IT WORTH PAYING A LITTLE
MORE FOR QUALITY AND RELIABILITY?**

Fully guaranteed for 12 months.

Most CASIO products available from
stock. Send 25p for illustrated brochures
and membership of our **CHRISTMAS
CLUB. EXTRA DISCOUNTS** on many
items.

CASIO CHRONOGRAPHS

Constant LC display of hours, minutes,
seconds, am/pm and day (12 or 24 hour). Dual
time (12 or 24 hours). Automatic day, date,
month and year calendar. Chronograph
measures net, lap and 1st and 2nd place times
from 1/100 second to 7 hours. Backlight.
Mineral glass face.

Guaranteed water resistant to 66 or 100 feet.

NEW MODEL

95QS-32B

4 YEAR BATTERY.
Superbly styled brass
case heavily chrome
plated. Water Resistant
to 66 feet.

(RRP £27.95)

£23.95



95QS-31B

(left)
4 YR BATTERY
S/Steel jacket.
WR to 66 feet
(£27.95)

£23.95

95CS-31B

(Right)
5 YR BATTERY
Solid S/S case.
WR to 100 feet.
(£34.95)

£29.95



F-200 SPORTS CHRONO

Hours, minutes, seconds,
am/pm. Day, date, month
1/100 sec chrono to 1 hr.
Net, lap and 1st and 2nd
place times. Backlight.
Resin case/strap.
Mineral glass.
WR to 66 feet.
Silver oxide battery
(£17.95)

£15.95



F-8C Time/date

3 YEAR BATTERY
Hours, minutes, seconds,
date, day, am/pm. Auto
28, 30, 31 day calendar.
Backlight. Resin case/
strap. Mineral glass.
WR to 66 feet
(£12.95)

£10.95



LADIES MODELS (others available)
Hours, minutes, 10 seconds, am/pm. Automatic
calendar. Stainless steel, mineral glass. WR to
100 feet.



86QL-10B
£26.50

86QL-12B
£31.95

86CL-22B
£37.25

Price includes VAT, P&P. Send your cheque, P.O.
or phone your ACCESS or BARCLAYCARD
number to:-

TEMPUS

Dept. PE, Beaumont Centre, 164-167 East Rd.,
Cambridge CB1 1DB. Tel. 0223 312866



TUAC

TRANSISTOR UNIVERSAL
AMPLIFICATION CO LTD
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY
AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS


4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSMI

- Full wave control
- RCA BA Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£22.95

Model 501 500W per channel as above without sound triggering

£14.95

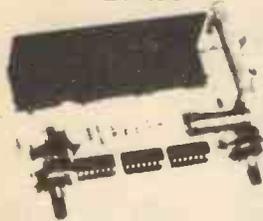

ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



3SDMI

- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

£17.50

FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)
as illustrated



For S1LMB £9.00
Size 8" x 4 1/2"



4LSM1 £7.75
Size 6 1/2" x 4 1/2"



FUZZ LIGHTS
Red, Green, Blue,
Amber. £25.00



S1LMB £10.00
Combined with 3SDMI
Size 9" x 4 1/2"

£22.95

PRICES INCLUDE VAT. P & P FREE

correct at 1.10.79

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD. 121 Charlmont Road, London SW17 9AB. We accept phone numbers from Access/Barclaycard Holders. Phone 01-672 9080.



HERE ARE JUST A FEW OF THE 1000 REASONS

which makes the Starchaser 4000 the finest 4 channel lighting unit available anywhere. *4 channels 750W each *over 1000 different sequence patterns and effects *3 alternative sound triggers *A.G.C. *simulated strobing *zero reference triac firing *superb TUAC quality and reliability **£99.00 inc. VAT.** Move into the 80's today by sending for further details to: TUAC Ltd., 119 Charlmont Road, S.W.17. Tel: 01-672 3137/9080.



TUAC Main Distributors (Callers Only)

A1 Music, 88 Oxford Street, Manchester (Tel: 236 0340). Cookies Disco Centre, 126/128 West Street, Crewe (Tel: 4739). Electra Centre, 58 Lancaster Road, Preston (Tel: 58488). Electrosure, Fore Street, Exeter (Tel: 56687). Garland Bros., Deptford Broadway, London (Tel: 01-692 4412). George Matthews, 85/87 Hurst Street, Birmingham (Tel: 622 1941). Luton Disco Centre, 88 Wellington Street, Luton (Tel: 411733). Memhouse, 82 St. Mary Street, Southampton (Tel: 28028). Salscoglen, 43 Borough Road, Middlesbrough (Tel: 242851). Soccidi, 9 The Friars, Canterbury (Tel: 60948). Session Music, 163 Mitcham Road, Tooting, London (01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE



Seiko
**WATCH
 OFFER...**

Saves you £45!

Seiko have done it again! This incredible new watch, which you will probably not find in the shops until next year, has both analogue and digital readout and—as has become their trademark—Seiko have presented it in a beautifully designed and finished stainless steel case, with matching bracelet.

The recommended retail price from Seiko is expected to be £125 and, believe us, this watch is worth every penny in looks alone. However, by arranging this exclusive offer we can save you £45 on that recommended price making the watch £79.75 including VAT and postage. To help spread the load we have also arranged for Access and Barclaycard payment.

The watch, shown full size on the front cover, is only 8mm thick and has a battery life of about 3 years. The following facilities are provided:

- Analogue watch —completely independent of other functions but quartz controlled.
- Digital watch —l.c.d. reading hours, minutes and seconds.
- Date —showing day, date and month; requires setting on leap years or after renewal of battery.
- Stopwatch —reading minutes, seconds and hundredths up to 20 minutes then hours, minutes and seconds (automatic changeover), includes lap and accumulated time functions and flags for lap, 1/100ths and stop.
- Counter —Single counter up to 9,999 or dual counter up to 99 on each button.
- Flags —Showing setting mode e.g. Stopwatch, Counter or Time, plus those for the stopwatch.
- Battery indication —When batteries run low the display flashes.

The watch is splash resistant, anti-magnetic and shock protected, it comes in a handsome black presentation case complete with a fully illustrated manual showing in a clear, concise manner how to set and use all the functions. The accuracy is better than 10 seconds per month at normal temperature range (-10°C to +60°C). The watch is covered by a one year guarantee.

Don't miss this exclusive offer—it closes on 29th Feb.

To: Practical Electronics
 Dept: PE1, Rochester X, Kent ME99 1AA
 Please send me the Seiko Watch(es) as indicated at £79.75 each, incl. p. & p.
 I enclose P.O./cheque No. Value

No. of watches required

Name

Address

Tel. No. (Home or Work)

I wish to pay by Access or Barclaycard.  
 My Number is:

Cardholder's Address

Signature

No. of watches required

Name

Address

From Practical Electronics,
 Dept: PE1, Rochester X, Kent ME99 1AA

CUT ROUND DOTTED LINE

Orders are normally despatched within 28 days but please allow time for carriage. You will be notified if a longer delay may be expected. Remittances may be by Access, Barclaycard, postal order or cheque (Name and address on back of cheques, please), crossed, and made payable to IPC Magazines Ltd. This offer is open to readers in England, Scotland, Wales, Northern Ireland and Channel Islands only. It is not available in Eire or overseas. Offer closes on 29th February, 1980. Please complete both parts of the coupon in BLOCK CAPITALS. If paying by Access or Barclaycard, please do not send your credit card.

readout

... a selection from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Compukit

Sir—Some time ago I think you asked for reader comments and I would like to say that in my view *PE* has improved very considerably over the years and particularly in recent times.

But I have a moan! The Compukit articles, who are they aimed at, the expert or the amateur? Right at the start the writer lists the amateur as a potential user, but the articles are written using computer jargon (the writer says as much in one place) which is pretty well unintelligible to the beginner in the computer world, however expert he may be in general electronics. In saying, this I am not referring to the BASIC dialect but to words such as "string function" (on page 43 of the pull-out, it is stated that a string can be 0 characters long which seems to have no meaning, and whence 255?), "the memory defaults", "arrays", "truncated integers", etc., and does the average amateur know his Boolean algebra?

With reference to the pull-out itself, does this refer particularly to the Compukit or to BASIC in general?

May I refer to the "Microprocessor Evaluation System" article in the May issue of *PE* in which the writer states several times that 377 octal is 255 binary, but 377 octal is equivalent to 255 decimal, there are no 2s and 5s in the binary system. As the writer makes the statement several times he presumably means something by it, but what? Lastly, to the beginner in the computing world (and that includes me) the charts on pages 20, 21 of the same article, are unintelligible in the form given.

The small booklet that you issued in May 1978 is not much use with reference to the above points, what about a reissue?

I was initially filled with enthusiasm for the Compukit but this is rapidly turning to frustration. Is there any chance of a short glossary being published as an addendum to the last article of the series?

A. Bray,
Potters Bar.

Thank you for your comments. This is a difficult area for PE because we have to optimise between encumbering every computer based article with the same mass of fundamental explanations, or keeping to the point but losing the beginner. This is why, in the Compukit article, we refer the reader to our Learn BASIC article which, we hope, will put the newcomer in the picture.

However, to briefly answer your questions: A string (\$\$) is a string of alphabetic characters. i.e. You may state A = 123 but not A = CAT, for this must be a string A\$ = "CAT". A

string of no characters is a null string, i.e. A = "". The maximum of 255 char's is governed by the highest number 8 binary bits may record.

When the machine is said to default to something, it is assuming a preset value in the absence of information to the contrary.

An array is a subscripted variable i.e. A(1) to A(10) is a dimensioned array with ten possible values.

Truncated Integer. This is to round-down, i.e. 2.76 becomes 2 etc.

To revise Boolean algebra is a prerequisite for any amateur embarking on computer work, and the pull-out describes the BASIC which Compukit is capable of only.

With reference to the binary and octal numbers in the Microprocessor Evaluation System article, the statement is technically incorrect. The number 255 represents the individual digits of the b.c.d. equivalent, not the strict binary equivalent—Ed.

Schottky

Sir,—In "Semiconductor Update" in September's issue of Practical Electronics, R. W. Coles states "There will be other new TTL families from manufacturers such as Fairchild..."

A few months ago Texas Instruments announced their AS and ALS range of advance TTL families. To date, only one part is obtainable, the 74ALS74.

One year ago, Fairchild announced fast: "Fairchild Advanced Schottky TTL". This range was not only announced several months before competing products: it is also considerably easier to obtain. Already the simple SSI building blocks are available, and MSI multiplexers, registers, counters and bus drivers are either available or will shortly be announced.

Fast is fast: 3ns per gate at one fifth the power of high speed standard Schottky.

A technical description of fast technology has already been published in *Electronics*, March 1979, pp. 111.

J. Summers,
Fairchild.

Recompense!

Sir—Re. your correspondence page in October issue and the article on CB. There is no doubt in my mind that most, if not all of this, is triggered off by people who wish to flog 27MHz imports. I have had a life-long interest in radio and have made no concerted effort to study, and yet recently I saw a paper used at the May RAE exam and could have passed it. This would give me access to equipment

designed for 144MHz costing less than the £260 quoted in Mark Sawicki's article. Study Morse for a few weeks and I can transmit world-wide! Much more interesting and just as useful in emergencies as CB probably is. In the States, I am told, it (CB) is abused more than used.

I suppose that the Government will eventually give in, they usually do, but if they take the soft option, 27MHz, then they are morally bound to recompense modellers financially, who have to change their equipment. I am not, by the way, an RC modeller.

T. D. Ray,
Derby.

Champ

Sir,—In the conclusion of the CHAMP series you mentioned possible further articles on programming or hardware designs, but nothing has been printed yet.

There must be many PE readers who have constructed CHAMP and have information to exchange.

I would be glad to exchange with any CHAMP enthusiasts hardware ideas, problems and even the occasional program.

J. Coyne,
BFPO 17.

CHAMP has been rather overtaken by new technology but it is not our intention to neglect those who have built it and we would welcome small programmes and hardware ideas for publication and for exchange to other CHAMP users—Ed.

P.E. COMPONENT STANDARD

Typical examples:

	Now	Before
Resistance	3k9	3.9kΩ
	1M5	1.5MΩ
	470	470Ω
	2Ω2	2.2Ω
Capacitance	680μ	680μF
	4μ7	4.7μF
	470n	0.47μF
	47n	0.47μF
	4p7	4.7pF
Inductance	3H4	3.4H
	800m	800mH
	2m6	2.6mH
	1m	1mH

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE

£6.95



6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less than ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Reg. 9V battery. 22-351. REG. PRICE

£79.95



MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megaohm. 0-100-1k-101C-100K-3 megaohms. Reg. 9V battery. 22-209.

REG. PRICE

£29.95



TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE **£9.95**



DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE **£19.95**



SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**



AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.

REG. PRICE **£229.95**



DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.

REG. PRICE **£9.95**



VARIABLE POWER SUPPLY

Power project boards. IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**



You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.




Access, Barclaycard and Trustcard welcome.

Prices may vary at individual stores.

ELECTRONI-KIT

DENSHI KITS— SPECIAL OFFER

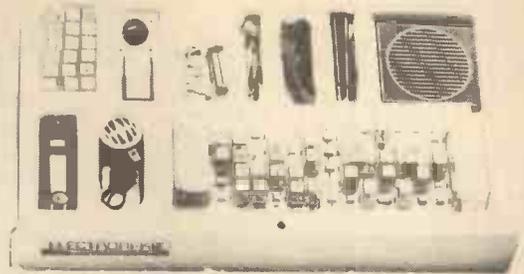

"... fun and entertainment
as well as education"—
(EVERYDAY ELECTRONICS mag.)

The SR-3A kit (over 100 circuits) and the SR-3A de luxe kit (over 105 circuits) are available again, at little more than their 1977 prices

Circuits are constructed by plugging the encapsulated components into the boards provided, following the instruction manual. Technical details are also given concerning each project. The components are used over and over again and you can design your own circuits too, or use the kit as a useful testing board.

No previous experience of electronics is required but you learn as you build—and have a lot of fun too. The kits are safe for anyone.

SR-3A KIT **£29.95**
(illustrated $16\frac{1}{2} \times 10 \times 2\frac{1}{2}$ ")

Build any of 100 projects including 3-TR reflex radio receiver, 3-TR radio receiver with RF amplifier, 2-TR reflex radio receiver, 3-TR amplifier for crystal mike, 3-TR amplifier for speaker mike, 3-TR signal tracer, Morse Code trainer, 2-TR electronic organ, electronic metronome, electronic bird, electronic cat, electronic siren, electronic gun, 2-TR sleeping aid, high voltage generator, discontinuity warning device, water supply warning device, photoelectric alarming device, 3-TR burglar alarm, 3-TR water supply warning device, 3-TR water level warning device, 3-TR photoelectric alarming device, Morse Code trainer with sound & light, discontinuity warning device with sound & light, water level warning device with sound & light, electronic metronome with sound & light, buzzer with sound & light, wireless mike, wireless telegraph set, wireless discontinuity warning device, wireless water level warning device, wireless water supply warning device, and wireless photoelectric warning device.

SR-3A de luxe KIT **£39.95**
($16 \times 14 \times 3\frac{1}{2}$ ")

Similar to SR-3A, more components including solar cell and additional Speaker unit plus sophisticated control panel.

All kits are guaranteed and supplied complete with extensive construction manuals PLUS Hamlyn's "All colour" 160 page book "Electronics" (free of charge whilst stocks last).

Prices include batteries, educational manuals, free book, VAT, p&p (in the UK), free introduction to the British Amateur Electronics Club.

Cheque P.O. Access Barclaycard
(or 16p. for illustrated literature) to DEPT. PE

ELECTRONI-KIT LTD.
RECTORY COURT, CHALVINGTON,
E.SUSSEX, BN27 3TD (032 183 579)


THE NEW

EUROSOLDERSUCKER

The 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £7.25 inc. VAT & P.P.

THE UNIQUE

EUROBREADBOARD

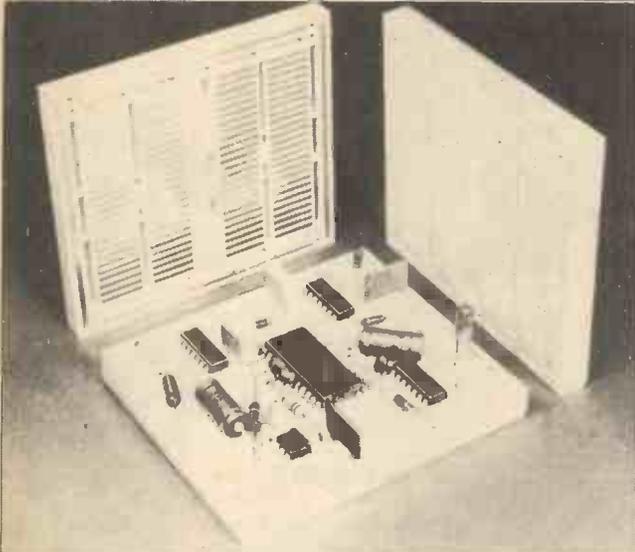

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £6.20 each or £11.70 for 2 – inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

PE12/79

Please send me 1 EuroSolderSucker @ £7.25 Please
or 1 EuroBreadBoard @ £6.20 Tick
or 2 EuroBreadBoards @ £11.70

(All prices are applicable from July 1st 1979 and include VAT & P.P, but add 15% for overseas order.)

Name

Company

Address

Tel. No.

Please make cheque/P.O.'s payable to David George Sales



COST • A • CALL

A.P. DONLEAVY

Calculator

Can be used to cost several calls

THE unit to be described will display directly the cost of a telephone call, taking into account the time of day, distance called, and length of time of a call. The unit can also be used to total the cost of several calls.

At the time of writing, the Post Office charges three pence for each unit of time of the duration of a telephone call. For a long distance call (over 56km) at peak rate, each ten seconds will cost three pence. A local call at peak rate costs three pence for two minutes. Table 1 gives the current rates (cost codes) presently charged by the Post Office.

For example with the instrument set to cost code (a) it will add three pence to the display every ten seconds.

CIRCUIT

Fig. 1 gives a block diagram of the system used. The period timer is a monostable with a timing period set for the appropriate cost code—10s, 15s, etc. The negative edge of the output pulse is fed to both the unit timer, which is also a monostable, and, in turn, the cost oscillator. The timing pulse of this is used to gate the cost oscillator.

The duration of this pulse and the frequency of the oscillator are chosen such that only thirty oscillations occur before the gating pulse stops the oscillator. These thirty pulses are fed to the counter/display system, and cause a 3 to be displayed. The unit timer pulse is also fed back to re-trigger the period timer, and start again the sequence of events.

IC1 contains two monostable oscillators (Fig. 2). IC1a is used to provide the period timing pulse. The length of this depends on which resistor R3—R11 is switched into the circuit and on the value of C3. VR1 is used to provide a control voltage to pin 3 which is used to make a fine adjustment to the timing pulse period. The length of this pulse is altered by VR2.

The output pulse is then fed to pin 12 of IC2. This is a four NAND gate CMOS chip. Three of these gates are connected as an oscillator. The oscillations are fed to pin 9, and only emerge at pin 11 of the gate if pin 12 is at logical 1, which is for the duration of the unit timer pulse.

Table 1: Cost Codes
Time in secs. for 3p. Costcode is in brackets

	Peak Rate	Standard	Cheap
Local	120 (f)	180 (g)	480 (h)
Up to 56km	30 (c)	45 (d)	180 (g)
Over 56km	10 (a)	15 (b)	60 (e)

The negative edge of the pulse is fed back via C5 to re-trigger IC1a. C4, R13 and C5, R12 are used to provide short input triggering pulses, since these must be of shorter duration than the output pulse, which would not be the case if the pulses were fed directly to the inputs.

S2 is a double pole switch arranged such that S2a is on when S2b is off. In this mode pin 4, the reset of IC1 is grounded and the output pin 5 is low. Switching S2b on immediately gives a negative pulse to pin 8 IC1b which triggers the monostable so that the instrument immediately displays the first unit of cost, and then proceeds to cost the rest of the call.

TIMING PERIODS

The values of C3 and R3—R11 are chosen to give a timing period of 10 seconds per 100k (using VR1 for a final calibration). Therefore to obtain the timing periods 10, 15, 30, 45, 60, 120 and 180 seconds, resistors of 100k, 150k, 300k, 450k, 600k, 1.2M and 1.8M, respectively are required.

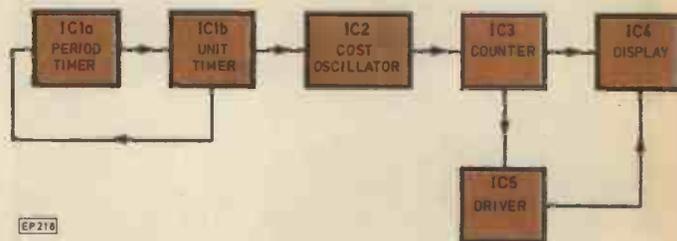


Fig. 1. Block diagram

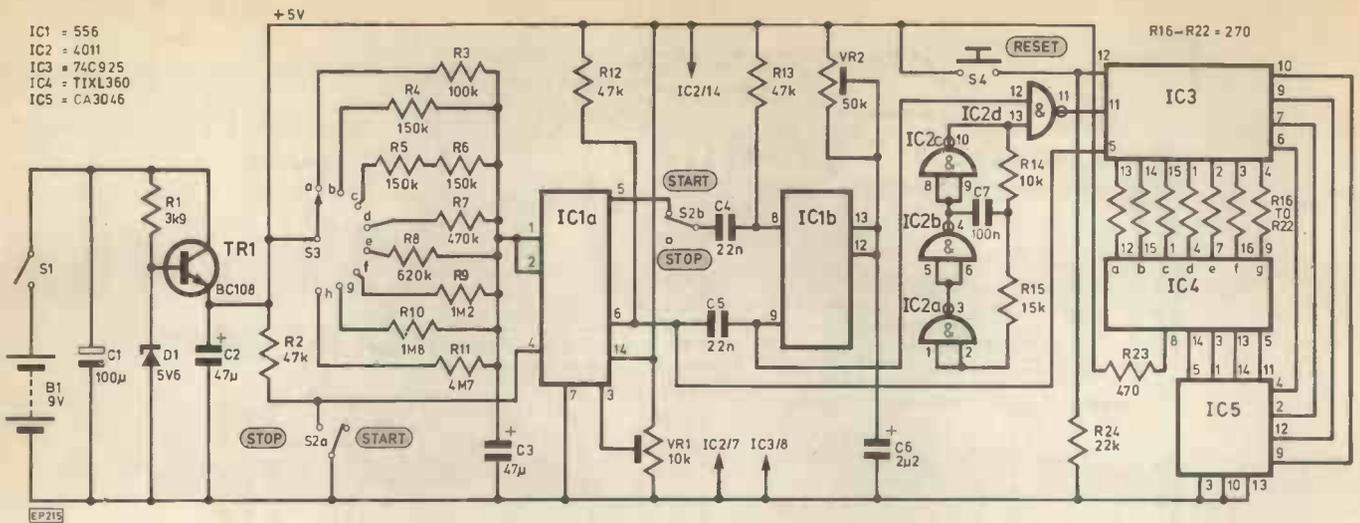


Fig. 2. Circuit diagram

300k resistor is obtained by two 150k in series and a 470k resistor is used instead of a 450k resistor, leading to a 5 per cent error in this timing interval. However, for domestic use this is not significant. Also R8 will need to be 620k. Varying VR1 changes all timing periods by the same percentage.

In the event of changes in telephone charges VR2 will recalibrate the unit cost of a call. Any changes in this period costing may be done with VR1, or else resistor changes may be required. This however is a simple job.

IC3 is a National CMOS MM 74C925 four digit counter/latch/driver, internally multiplexed. IC5 is a CA3046 chip containing five identical transistors, four of which are used to drive the display digits. The display is a TIXL306 calculator display with either four or six digits. Only four are used in this project.

The pulses from the oscillator are clocked into pin 11 of IC3 where they are then counted and displayed on IC4. S4 is depressed to zero the reading on the display.

The power supply regulation circuit is fairly simple and straightforward giving a line voltage of about five volts.

COMPONENTS

IC5 may be substituted by an LM3086, which is a pin for pin equivalent. IC4 may be substituted by any display if the appropriate adjustments are made to the printed circuit board. All that is required is that the segments a-g and digits be connected to IC3 as shown. Individual 0.3 in. displays may be used also. Again the constructor will need to make his own modifications.

The specified display fits into a 16 pin DIL socket making the mounting simple. It is recommended that DIL sockets be used for all the i.c.s, especially for the 74C925. Being CMOS it can be easily damaged by static electricity.

CONSTRUCTION

Figs. 3 and 4 give the printed circuit board and component layout. The display is mounted in a DIL 16 pin socket arranged on its edge, such that the display is perpendicular to the board. Bend the socket pins round 90° and solder them into the holes drilled in the board. Stiff wire is used to connect the remaining pins of the display to the board.

Drill the front panel of the case to take the switches. Cut a window in this panel suitable for viewing the display. Red clear plastic can be used as a filter. This can be glued to the inside of the panel.

S3 is mounted on the lid of the box. R3-R11 are soldered directly onto the terminals of this switch. The battery, if used, is stuck on the underside of the lid using a double sided sticky mounting tab. The printed circuit is held to the base using two screws into the mounting studs. The lettering on the box can be done using Letraset. To avoid extra circuitry for controlling the decimal points, the unwanted decimals are blanked off using a felt tipped pen.



COMPONENTS . . .

Semiconductors

D1	RZY88-5.6 Zener 400mW
TR1	BC108
IC1	556
IC2	4011
IC3	74C925
IC4	TIXL360
IC5	CA3046

Resistors

R1	3.9k
R2	47k
R3	100k
R4	150k
R5	150k
R6	150k
R7	470k
R8	620k
R9	1M2
R10	1M8
R11	4M7
R12	47k
R13	47k
R14	10k
R15	15k
R16-22	270
R23	470
R24	22k
All 1/4W 10% carbon	

Capacitors

C1	100µ elect 25V
C2	47µ tantalum
C3	47µ tantalum
C4	22n
C5	22n
C6	2.2µ tantalum
C7	100n

Switches



S1	On-off toggle
S2	Double pole double throw
S3	Single pole eight way rotary
S4	Press switch

Variable resistors

VR1	10k linear
VR2	50k multitrn trimpot

Miscellaneous

Verobox	153 x 84 x 39.5mm
---------	-------------------

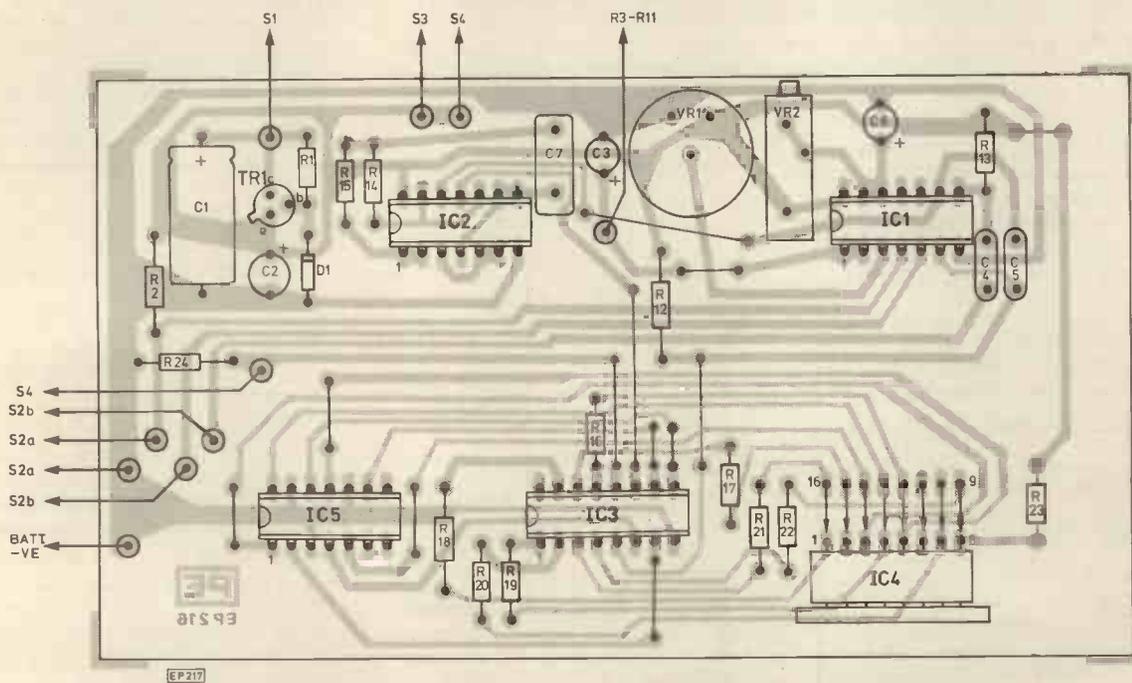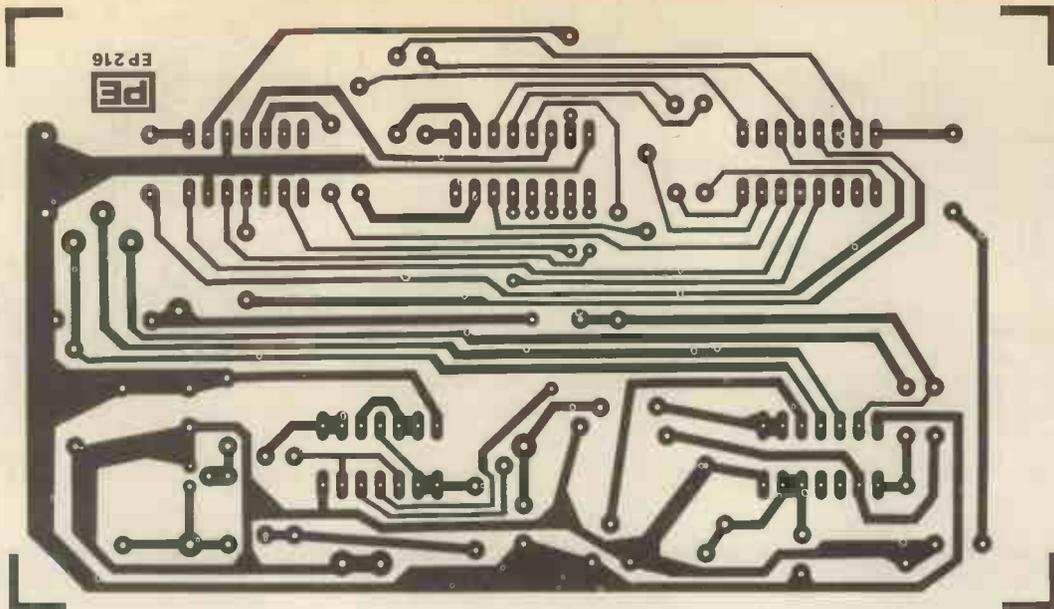

Figs. 3 and 4. P.c.b. and component layout. Arrows refer to display pin connections. For these see circuit

CALIBRATION

VR2 must first be adjusted so that the display increments by thirty each time. Switching S2 from stop to start will increment the display and speed up the calibration process.

Switch to cost code a, and adjust VR2 until the counter increments every 10 seconds. This roughly calibrates the period timer. Then switch to position g, and readjust VR2 so that the counter increments every three minutes. The unit is now calibrated.

TROUBLE SHOOTING

If the unit doesn't work on switching on, check power supply voltage and wiring. Also check the i.c.s are inserted the right way round.

If the four digits of the display light and S4 will zero any random number displayed when the instrument is turned on, then IC3, IC4, IC5 will be functioning. Attention can then be

turned to the remaining circuitry. Remove IC1 and the display should count continuously. Switching on/off may be necessary to start the oscillations. If the oscillator is working, attention can then be turned on IC1. Make sure that VR1 is not set to either end of its travel, and check the voltages on the various pins of the i.c.

USING THE INSTRUMENT

Switch on, set cost code. Put S1 to stop, press S4, then put S1 to start when the call starts. At the end of the call put S2 to stop.

The cost will then be displayed. If another call is to be made do not turn off the instrument. Press to start and the cost of this call will be added to the last call. The instrument could be permanently left on if required to total the cost of all calls (up to a limit of £9.99). However, a mains adaptor would be imperative in this case. ★

how the Mk14s display can be multiplexed from a user program. It displays a nine-letter message, making use of the ninth digit wired up as described above. The routine works by repeatedly copying the nine segment codes for the message to the addresses for the nine display digits; P1 points to the display and P2 to the message bytes, and the extension register is used as an offset. The routine formed part of a cassette interface system, submitted by *Colin C. Tredwell of London*, which displayed a file name after a program was loaded from tape; unfortunately there is not space to publish the whole program here.

AUTOMATIC OFFSET CALCULATOR

As anyone who has programmed a SC/MP micro will know, the hardest part of "hand

In the example of a program which loops around, decrementing a counter the address of the program to be processed (0F20 in this example) is put in 0FF9, 0FFA so that the monitor will set up P1 for us. Then the offset calculator program is run from 'ENTER', and will stop when it encounters 'A0'. It will have altered the program to:

```
0F20 B8FE
0F22 90FC
and the program is now ready to run."
```

PROGRAM OPERATION

"The SC/MP instruction set can be divided into three basic types:

- 1) Single byte instructions
- 2) Double-byte immediate or indexed instructions
- 3) Double-byte instructions with displacement.

```

; OFFSET CALCULATOR FOR SC/MP
0000      ; -OPRA
0F9A C501 ALTER: LD @1(1) ;SKIP 2-BYTE INSTRUCTION
0F9C C501 ENTER: LD @1(1) ;START EXECUTION HERE
0F9E 94FC JF ENTER ;NO CALCULATION
0F00 940F ANI OF ;ENDS IN ZERO
0F02 981E JZ NDO ;ENDS IN ZERO
0F04 C1FF LD -1(1) ;ENDS IN ZERO
0F06 D40F ANI OF ;ENDS IN ZERO
0F08 E808 XRI 08 ;ENDS IN EIGHT
0F0A 9821 JZ NDB ;ENDS IN EIGHT
0F0C C1FF LD -1(1) ;JFFZ
0F0E E494 XRI 074 ;JFFZ
0F10 9804 JZ JUF ;JUF
0F12 E408 XRI 08 ;NOT INZ.
0F14 9C64 JZ ALTR ;NOT INZ.
0F16 31 JUMP XPAL 1
0F18 01 XAE
0F1A 40 LDE
0F1C 31 JUMP 1 ;RESTORE P1
0F1E C501 LD @1(1) ;GET SECOND BYTE
0F20 02 CCL ;STORE DISPLACEMENT
0F22 78 CAE ;CONTINUE
0F24 C9FF ST -1(1) ;STORE DISPLACEMENT
0F26 90DA JNB ENTER ;CONTINUE
0F28 C1FF NDC: LD -1(1) ;STORE DISPLACEMENT
0F2A E490 XRI 090 ;STORE DISPLACEMENT
0F2C 982E JZ JUMP ;JMPZ
0F2E E43D XRI 03D ;JMPZ
0F30 9C07 JZ INC ;JMPZ
0F32 3F XPC 3 ;STOP AT A0 BYTE.
0F34 C1FF NDC: LD -1(1) ;STORE DISPLACEMENT
0F36 E198 XRI 098 ;JMPZ
0F38 98E3 JZ JUMP ;JMPZ
0F3A 8800 INC: ILD (1) ;MEMORY REFERENCE
0F3C 90DF JNB JUMP ;NO CALCULATION
0000      .END

```

Fig. 4. SC/MP program automatically calculates offsets for program-counter relative instructions

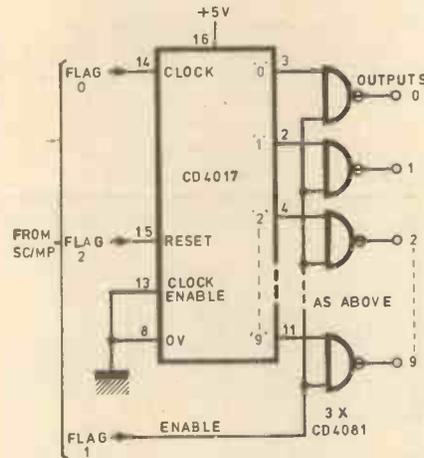


Fig. 5. Circuit uses a decade counter to add ten outputs to a SC/MP micro

gates provide control of the selected output.

"A small subroutine, Fig. 6, is run to address any particular output. Once addressed, the output can then be controlled on and off by the operation of flag 1. The contents of 0F27 determine which output will be enabled. If the addressed output is changed the original output will be disabled, but if necessary latches could be added to store the states of the outputs. The circuit was originally developed to connect a small robot to an Mk14."

SC/MP SUBROUTINE STACKER

"One of the problems of programming with SC/MP is how best to use the three 16-bit pointer registers. These can be used as stacks, subroutine addresses, or to address data, etc. but when you need to switch from one use to another it is easy to get into a mess."

```

; OUTPUT ADDRESSING ROUTINE
0006      ; OUTPUT = 6 ; OUTPUT 1 TO 10
0000      ;
0000      ; -OPIF
0F1F COUNT: LD -1 ;COUNT
0F20 C404 BEGIN: LD 04 ;PULSE RESET
0F22 07 CAS ;
0F24 C400 LD 00 ;
0F26 C406 LD ;
0F28 C8F6 ST ; WHICH OUTPUT?
0F2A C401 LOOP: LD 01 ;PULSE CLOCK
0F2C 07 CAS ;
0F2E D400 LD 00 ;
0F30 B8EE DLD ;
0F32 9CF6 JNZ COUNT ;FLAG PULSED
0F34 C402 LD 02 ; 'OUTPUT' TIMES?
0F36 07 CAS ;ENABLE OUTPUTS
0F38 3F XPC 3 ;RETURN
0000      .END

```

Fig. 6. Routine which selects an output—in this case 6—with Fig. 5

```

; SC/MP SUBROUTINE STACKER
0000      ;
0B00 3F EXIT: XPC 3 ; -OB00
0B01 01 ENTRY: XAE ;
0B02 C9FD ST -3(1) ;STORE ENTRY VALUE OF B
0B04 C280 LD 2(2) ;GET SUBROUTINE ADDS. HIGH
0B06 3F XPAH 3 ;
0B07 CDFP ST 0-1(1) ;RETURN ADDS. HIGH TO STACK
0B09 02 CCL ;INCREMENT E:
0B0A C401 LD 1 ;
0B0C 70 ADE ;
0B0D 01 XAE ;
0B0E C280 LD 2(2) ;SAME FOR LOW ADDS. BYTE
0B10 33 XPAL 3 ;
0B11 CDFP ST 0-1(1) ;
0B13 C1FF LD -1(1) ;RESTORE ORIGINAL E VALUE
0B15 01 XAE ;
0B16 90E8 JNB EXIT ;
0B18 C501 ENTRY2: LD 0+1(1) ;RETURN ADDS. LOW
0B1A 33 XPAL 3 ;
0B1B C501 LD 0+1(1) ;RETURN ADDS. HIGH
0B1D 3F XPAH 3 ;
0B1E 90E0 JNB EXIT
0000      .END

```

Fig. 7. Program implements a stack to simplify the use of subroutines

assembling" programs is calculating the offsets for program-counter relative jumps and addressing operations. The "offset calculator" program of Fig. 4, submitted by *Mr D. Love of Swansea*, eliminates the need to make these calculations by hand.

"The 'offset calculator' makes all the calculations automatically in one pass, thus speeding up writing programs and making them more likely to be free of errors. To use the offset calculator, programs are written as usual except that where instructions require a displacement, the low byte of the destination address is inserted as the second byte of the instruction instead of the displacement. The offset calculator makes the calculation when it passes over the program.

So writes *Mr N. E. H. Feilden of Suffolk*, and to remedy the situation he has written a routine for SC/MP to simulate the JSR and RTS instructions of other micros such as the 6502; see Fig. 7.

"A list of the subroutine addresses is stored in memory pointed to by P2. The appropriate one is selected by the value received in the accumulator by the stacker routine. Thus the calling program contains: 'LDI n, XPPC 3' (C4 nn 3F) as the equivalent of 'jump to subroutine'. The subroutine address is taken from locations P2+n (high byte) and P2+n+1 (low byte). The calling address is saved in a stack using P1, which should initially point to the top of a free area of RAM. Return is achieved using 'JMP 17(3)' (93 17) which causes a jump to the stacker routine at 'ENTRY 2'.

Pointer P3 should be set to the address 'EXIT' (0B00 in this case) before use. The routine is fully relocatable, so it can be put anywhere convenient in memory without modification. This version is fairly simple; it does

```

0F1F      COUNTER
0F20 B81F LOOP: DLD COUNTER
0F22 9020 JMP LOOP
0F24 A0 STOP CHARACTER
FOR OFFSET
CALCULATOR

```

EXTRA OUTPUTS FOR SC/MP

The basic SC/MP micro has three "flag" outputs which can be controlled from programs. The circuit of Fig. 5, sent in by *Steve Stamps of Avon*, shows a simple way of extending the number of outputs by using a CMOS decade counter, clocked by one of the flags, to select one of ten outputs. The AND

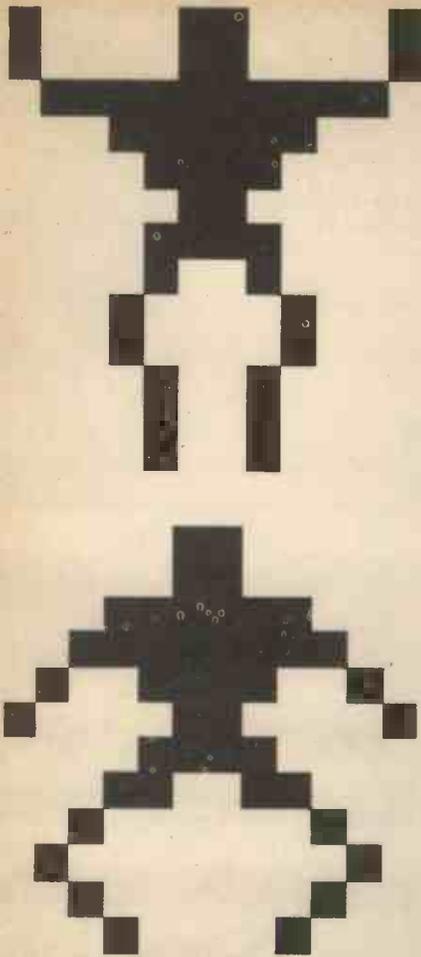


Fig. 8. Graphics generated by the falling-man program

```

; FALLING MAN DISPLAY
)
OF00 RAM = OF00 ;FOR VARIABLES
OB00 DESP = OB00 ;DISPLAY MEMORY
)
0002 J RAM OFFSETS:
0003 CNT = 3 ;COLUMN
0004 ROW = 4 ;COUNTER
;ROW COUNT

0000
0F20 C40F ENTER: LDI H(RAM)
0F22 37 XPAH 3
0F23 C400 LDI L(RAM)
0F25 33 XPAL 3 ;P3 TO VARIABLES
0F26 C40B BEGIN: LDI H(DISP)
0F28 35 XPAH 1
0F29 C406 LOOP: LDI 6
0F2B C802 ST COL(3)
0F2D 31 NEMMAN: XPAL 1 ;BEGIN NEW MAN
0F2E C40F LDI H(MAN)
0F30 36 XPAH 2
0F31 C47D LDI L(MAN)
0F33 32 XPAL 2 ;P2 TO MAN PATTERN
0F34 C413 LDI 19
0F36 C803 ST CNT(3)
0F38 C40F COPY: LDI 15 ;ROWS PER PICTURE
0F3A C804 ST ROW(3)
0F3C C401 NEMROW: LD 0(2)
0F3E C001 ST 0(1)
0F40 C601 LD 0(2)
0F42 C007 ST 0(1)
0F44 B804 DLD ROW(3) ;POINT TO NEXT ROW
0F46 9CF4 JNZ NEMROW ;PICTURE DONE?
0F48 C4B2 LDI 0-30(2) ;RESET P2
0F4A C590 LD 2-112(1) ;RESET P1 1 ROW DOWN
0F4C 8F40 DLY 040 ;WAIT...
0F4E B803 DLD CNT(3)
0F50 E404 XRI 4 ;4 SWEEPS TO GO?
0F52 9618 JI LAND ;YES = CHANGE PICTURE
0F54 E404 XRI 4 ;RESTORE CNT
0F56 9CE0 JNZ COPY ;FRESH SWEEP?
0F58 8FF7 DLY OFF ;LEAVE MAN STANDING
0F5A B802 DLD COL(3) ;NEXT MAN?
0F5C B802 DLD COL(3) ;SUBTRACT 2
0F5E 94CD JP NEMMAN ;ALL DONE?
0F60 C500 LDI 1 ;CLEAR SCREEN
0F62 31 CLEAR: ST 1
0F63 C400 LDI 0 ;BLANK
0F65 C001 ST 0(1)
0F67 31 XPAL 1
0F68 9CF8 JNZ CLEAR ;MORE TO DO
0F6A 908A JMP START ;REPEAT FOR EVER.
0F6C C43C LAND: LD 0+2(2) ;P2 TO STANDING MAN
0F6E 90C8 JMP COPY ;CONTINUE.

; BIT-PATTERNS FOR FALLING MAN
0F70 0000 MAN: .DBYTE X'0000,X'1308,X'4308
0F72 3FFD .DBYTE X'3FF0,X'0F00,X'0750
0F74 0300 .DBYTE X'0300,X'0780,X'0480
0F76 0840 .DBYTE X'0840,X'0840,X'0480
0F78 0480 .DBYTE X'0480,X'0480,X'0000

; BIT-PATTERNS FOR STANDING MAN
0F8E 0300 .DBYTE X'0300,X'0300,X'0FC0
0F90 1FED .DBYTE X'1FED,X'2790,X'4308
0F92 0780 .DBYTE X'0780,X'0C00,X'1020
0F94 2010 .DBYTE X'2010,X'1020,X'0840
0F96 0000 .DBYTE X'0000,X'0000

0000 .END

```

Fig. 9. Animation program for use with a Science of Cambridge VDU module

preserve the E register, but not the S. It could be adapted to handle interrupts since an 'XPPC 3' will always go to the stacker from anywhere outside the stacker. More complex schemes with two levels of indirection may be used to perform multiple tasks, for instance, in controllers."

FALLING MAN DISPLAY

The last in this month's series of applications for the Mk14 is a program donated by *Nick Toop*, designer of the Science of Cambridge VDU Module, to demonstrate some of the graphics possible with this VDU. The program generates a display of a man falling through space with his arms raised, and then landing with his arms lowered; see Fig. 8. He is then joined by three similar men, and the cycle repeats indefinitely. The animation is generated in half of the screen, 32 of the 64 possible rows, and uses the Mk14's extra RAM at OB00 for the display area. This memory is mapped to the display in rows of 64 dots, 8 bytes per row.

PROGRAM OPERATION

The falling-man program, Fig. 9, makes clever use of auto-indexing to keep it as short as possible. The bit patterns for the two positions of the man are stored after the program at "MAN". Each row of the man consists of 16 dots, specified by two bytes, and the whole man comprises 15 rows. The program writes the man to the display a total of 19 times, each time shifting the man down by one row to give the appearance of falling. For the first 15 sweeps of the man the picture of the falling man is used, and for the last 4 sweeps the standing man is used.

The resulting animation is pleasingly realistic, and should inspire owners of suitable systems to attempt more ambitious displays, such as a man walking across the screen.

EIGHT EIGHTS WINNERS

The winners of the Eight Eights competition, presented in the August Micro-Bus, were:

Mr D. Caballero of Ramsgate, Mr J. M. Brinton of Cheltenham and Mr E. Vyncke of Allur, Belgium.

News Briefs

PRESTEL TESTING THE INTERNATIONAL MARKET

BUSINESSMEN in seven countries will soon be able to take part in an international trial of Prestel, the British Post Office's world-leading viewdata system which gives users access to computer information banks by means of a simple TV type display terminal.

Invented at the Post Office Research Centre this system has already put Britain ahead of any other country in the mass marketing of electronic information. Now following the start of the world's first public viewdata service in London on March 27 Britain will score another world first when it begins experiments with an international viewdata service later this year.

The trial is designed to identify the kind of information today's

globe-trotting businessman, or government official, needs to know but which is often difficult to get quickly. With a Prestel international service it will be instantly available, literally at the user's fingertips.

The trial will be open to selected users in the UK and up to six countries—Australia, German Federal Republic, the Netherlands, Sweden, Switzerland, and the United States. It will offer a wide variety of up-to-the-minute business information drawn from many parts of the world—prices in the world's premier stock markets, currency exchange rates, schedules for the world's major airlines, the latest shipping news, as well as a variety of specialist information such as commodity prices, economic analyses and company management information.

The decision to go ahead with the trial follows a six-month evaluation of the potential market for such a service carried out for the Post Office by Logica Limited. This firm has now been commissioned to assist in implementing the trial which is expected to last one year. During the trial, a decision will be taken regarding a full-scale service.

Already discussions are under way with firms who might provide information needed for an international databank, part of which could be multi-lingual. Parallel talks are due to start soon with TV set manufacturers about supplying the few hundred terminals needed for the trial. The telecommunications authorities of the other countries involved are being invited to discuss the Post Office's plans.

The trial service will be using a dedicated Prestel computer in London which will become available after the full public service goes live in London.

STEVENSON

Electronic Components

CMOS			
4020	50p	4050	25p
4022	50p	4060	80p
4023	13p	4066	30p
4024	40p	4068	13p
4025	13p	4069	13p
4026	90p	4070	13p
4027	28p	4071	13p
4028	45p	4072	13p
4029	50p	4081	13p
4040	55p	4093	36p
4041	55p	4510	60p
4042	55p	4511	60p
4043	50p	4518	65p
4044	90p	4520	60p
4045	25p	4528	60p

FULL DETAILS IN CATALOGUE!


TTL			
7473	20p	74141	55p
7474	22p	74145	55p
7475	25p	74148	90p
7476	20p	74150	55p
7485	55p	74151	40p
7486	20p	74154	65p
7489	135p	74157	40p
7490	25p	74164	55p
7492	30p	74165	55p
7493	25p	74170	100p
7494	45p	74174	55p
7495	35p	74177	50p
7496	45p	74190	50p
74121	25p	74191	50p
74122	35p	74192	50p
74123	38p	74193	50p
74125	35p	74196	50p
74126	35p	74197	50p
74132	45p	74199	90p

OPTO			
LED's	0.125in. 0.2in	each	100+
Red	TIL209 TIL220	9p	7.5p
Green	TIL211 TIL221	13p	12p
Yellow	TIL213 TIL223	13p	12p
Clips	3p		

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

SKTS

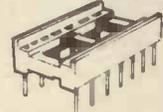

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

3 lead TO18 or TO5 socket. 10p each
Soldercon pins: 100:50p 1000:370p

PCBS

VEROBOARD

Size in.	0.1in. 0.15in.	Vero	
25 x 1	14p	Cutter	80p.
2.5 x 3.75	45p		
2.5 x 5	54p	Pin insertion	
3.75 x 5	64p	tool	108p
3.75 x 17	205p		

Single sided pins per 100 40p 40p
Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.
"Dalo" pens 75p each.
Five mixed sheets of Alfac. 145p per pack.

RESISTORS

Carbon film resistors. High stability. low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:

each	100+	1000+
0.25W	1p	0.8p
0.5W	1.5p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability. low noise rated at 1/2W 1% Available from 51ohms to 330k in E24 series. Any mix.

each	100+	1000+
0.25W	4p	1.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.

LINEAR

THIS IS ONLY A SELECTION!

LF356	80p	NE531	98p
LM301AN	26p	NE555	23p
LM308	60p	NE556	60p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	TBA800	70p
LM379S	410p	TBA810S	100p
LM380	75p	TDA1022	620p
LM3900	50p	TL081	45p
LM3909	65p	TL084	125p
LM3911	100p	ZN414	80p
MC1458	32p	ZN425E	390p
MM57160	590p	ZN1034E	200p

TRANSISTORS

AC127	17p	BCY72	14p	ZTX500	16p
AC128	16p	BD131	35p	2N697	12p
AC176	18p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BD140	35p	2N3055	50p
BC107	8p	BFY50	15p	2N3442	135p
BC108	8p	BFY51	15p	2N3702	8p
BC108C	10p	BFY52	15p	2N3703	8p
BC109	8p	MJ2955	98p	2N3706	9p
BC109C	10p	MPSA06	20p	2N3707	9p
BC147	7p	MPSA56	20p	2N3708	8p
BC148	7p	TIP29C	60p	2N3819	15p
BC177	14p	TIP30C	70p	2N3820	44p
BC178	14p	TIP31C	65p	2N3904	8p
BC179	14p	TIP32C	80p	2N3905	8p
BC182	10p	TIP2955	65p	2N3906	8p
BC182L	10p	TIP3055	55p	2N4058	12p
BC184	10p	ZTX107	14p	2N4557	32p
BC184L	10p	ZTX108	14p	2N5459	32p
BC212	10p	ZTX300	16p	2N5777	50p
BC212L	10p				
BC214	10p				

DIODES

BC214L	10p	1N914	3p	1N4006	6p
BC477	19p	1N4001	4p	1N5401	13p
BC478	19p	1N4002	4p	BZY88 ser.	8p
BC548	10p	ITT Full spec. product.			
BCY70	14p	1N4148	-£1.40/100. £11/1000		
BCY71	14p				

CAPACITORS

TANTALUM BEAD

each

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047	3p
0.068, 0.1	4p

POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

CERAMIC

Plate type 50V. Available in E12 series from 220F to 1000pF and E6 series from 1500pF to 0.047uF

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
			22	33	47	7p
						13p
			220			20p
25V	10	22	33	47		5p
	100					8p
		220				10p
			470			15p
						23p

CONNECTORS

JACK PLUGS AND SOCKETS

	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs 6p each Sockets. 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow Plugs 11p each Sockets 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

SOLDERING IRONS

ANTEX X25 (25W) or ANTEX CX (17W) 390p each
Reel of solder (39.6M) 240p each

LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p

Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
Crystal earpiece including 3.5mm plug. 30p each

SWITCHES

Subminiature toggle. SPDT 70p. DPDT 80p
Standard toggle. SPST 34p. DPDT 48p.



Slide switches (DPDT) miniature or standard 15p.
Push to make switch. 15p. Push to break switch. 20p.
Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow & black. 14p.



MISCELLANEOUS


Connection cable available in single or stranded packs of eight colours.

	Single	Stranded
8 metre pack	18p	18p
40 metre pack	85p	80p

BATTERY CLIPS

Battery clips for PP3 with lead. 6p each.
Battery clips for PP9 with lead. 10p each.
Miniature crocodile clips in red or black. 8p each.
Red or black probe clips. 20p each.

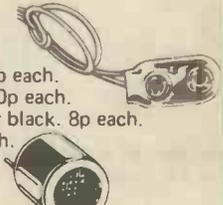Murata Ultrasonic Transducers. 180p each. 350p pair.



PANEL METERS

High quality 2" wide view meters. Zero adjustment. Back illumination wiring. Available in 50 uA, 100 uA, 500 uA, 1mA, 100mA, 500mA, 1A. £4.75 ea. VU meter similar style. £1.40 ea.



SLIDE POTENTIOMETERS

Good quality 60mm travel slider with 80mm fixing centres. Available from 5k - 500K in log and linear. 55p each. Suitable black knobs 6p ea. Coloured knobs 10p ea.



We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

ORDERS DESPATCHED BY RETURN POST


BARCLAYCARD & ACCESS WELCOME



Mail orders to: STEVENSON (Dept PE)



76 College Road, Bromley, Kent BR1 1DE.

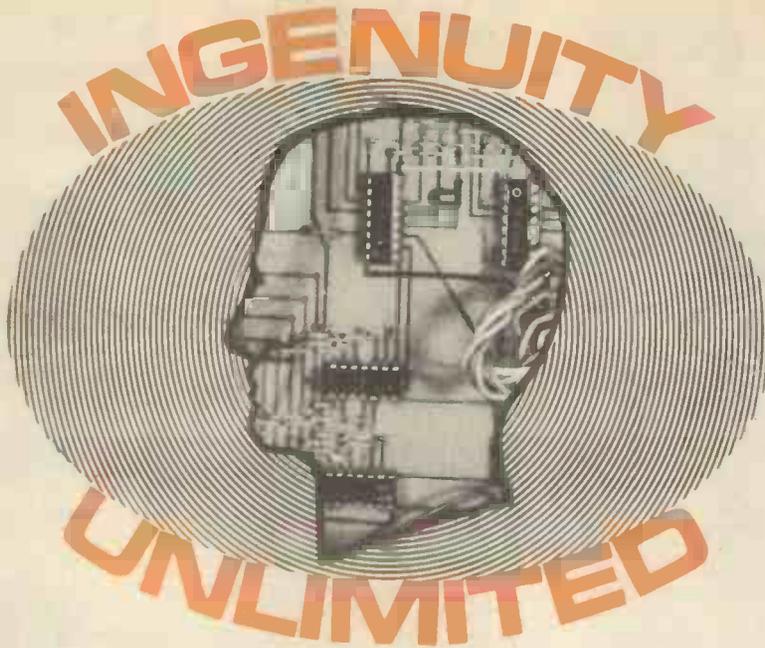


A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

AUDIO-MILLIVOLTMETER

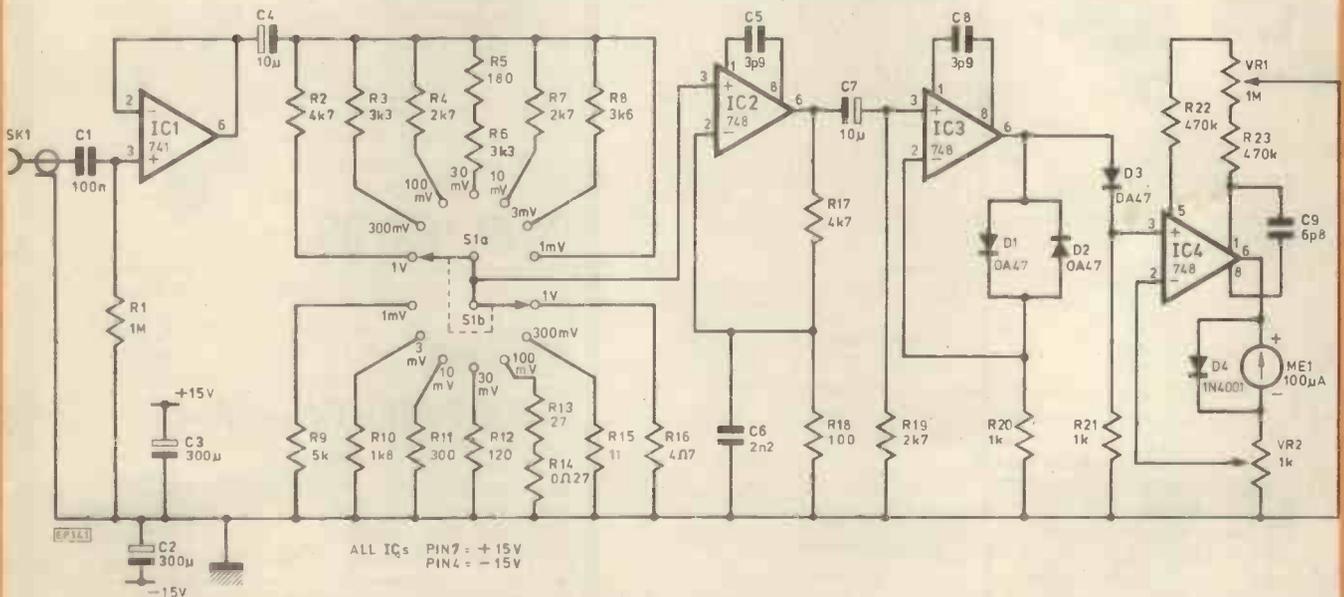

HAVING constructed the audio-millivoltmeter featured in the June '76 edition of *PE*, I discovered that circuit noise and main's hum caused a permanent deflection on the meter that was unacceptably large on the lowest range. To cure this I devised this circuit.

IC1 has unity gain and acts as a buffer amplifier for the input signal across R1. The signal is then fed through one of the voltage-dividers to IC2, which amplifies it and provides frequency compensation. The signal then passes to IC3 which duplicates

it across R4 and so produces a low-distortion half-wave rectified signal across R5 (it is important that R20 = R21 and that D1, D2 and D3 are identical). The rectified signal is d.c. and is amplified by IC4 to drive the meter. The gain of this stage is varied by VR2, allowing calibration, and the meter is zeroed by VR1. D4 protects it from damage.


The input impedance of the circuit is governed by R1, one megohm was found to be satisfactory. The frequency response is virtually flat up to and beyond 100kHz,

depending on the value of C2 which affects the frequency compensation of IC2. The circuit measures a.c. signals from 1mV to 1V in seven ranges using a 100µA f.s.d. meter with 0-3 and 0-10 scales.

The circuit is very sensitive and care should be taken in its construction and housing; all signal carrying leads, the selector switch, the input socket, and any sources of main's hum should be properly screened.

Kevin Cameron,
Melrose,
Roxburghshire.

TELE-GAMES MOD

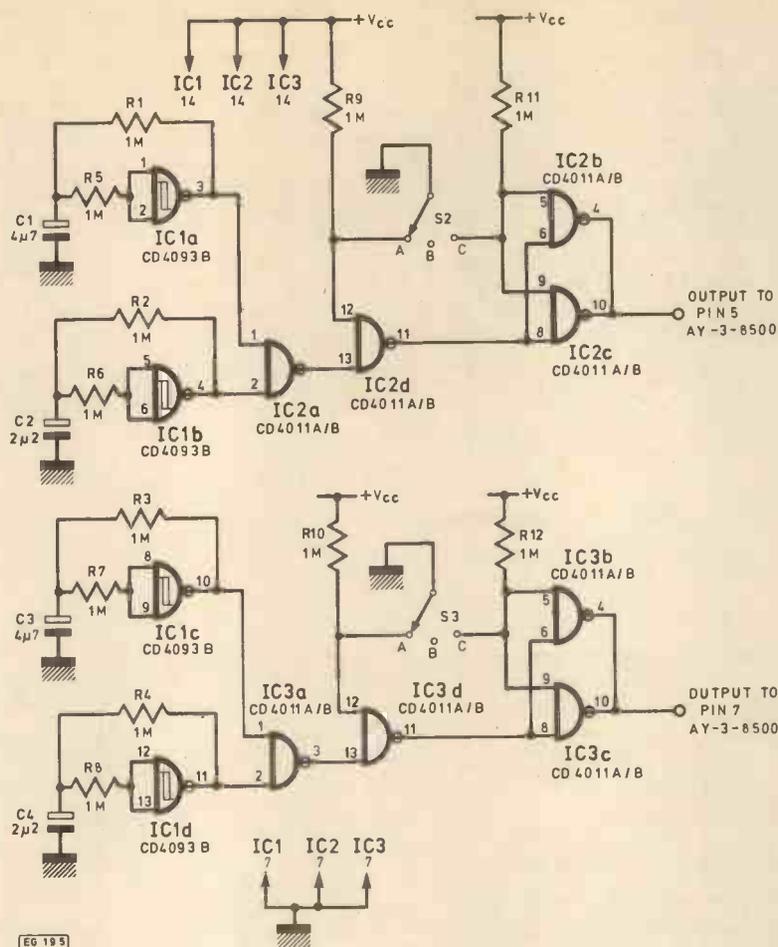

EG 193

THE introduction of the General Instruments, AY-3-8500 i.c. has produced a large number of almost identical tele-games circuits. It was while seeking some degree of variation from these circuits, while still maintaining the use of the AY-3-8500, that the following circuit was evolved, to introduce a certain amount of randomness to the game. In this way differences in ground texture (ball speed variation) and slight mis-hitting (angle at which the ball leaves the bat is uncertain) can be represented.

The circuit operation is very simple; consider the top section used for ball speed variation. Two slow oscillators are built around two NAND Schmitt triggers operated in the inverting mode. The speed of the oscillators is 0.3Hz and 1Hz using the quoted values. The resistor in series with the gate is to help protect the gate from

switch on surges. The two oscillators are then gated via IC2a to produce random pulses.

A SPDT centre off switch (S2) replaces the S2 in the original game. It can be seen that with S2 in position A the output of IC2c will be high, thus IC2bd will be low, giving a high ball speed. Similarly, with S2 in position C, IC2bd will be high, and so the ball speed will be low. However, with S2 in position B, both IC2c and IC2bd are enabled thus giving the random transitions at the output of IC2bd. The AY-3-8500 uses 100 kilohm pull up resistors, and although one gate drive will cope with the current drain, two may be used in parallel to ensure adequate speed.

An identical circuit is used to change the rebound options between 2 and 4 angles.

The circuit may be much simplified, by using only one oscillator and one drive gate, the circuit could then be built around one quad NAND Schmitt, but the full random nature is not available. It should also be possible to obtain speed changes every time a rebound occurs by using a monostable and latch on the sound output to alter the speed.

The connection to pins 5 and 7 of the AY-3-8500 may be made at the original switch points.

The oscillator gates must be Schmitt to ensure oscillation and the capacitors should be Tantalum types.

I. C. Lare,
Northwich,
Cheshire.

DC/DC VOLTAGE MULTIPLIER

SHOWN is an astable, symmetrical multivibrator working at about 1,000Hz. It has the special feature, that the ordinary collector resistors are replaced by *p.n.p.* silicon transistors. Even using small transistors, the output has a low impedance. When using supply voltages lower than 5-6 volts the base protection diodes may be omitted. It is advisable to use transistors with a nominal I_c maximum two or three times the input current; they need not match exactly.

The multivibrator has been tested with small power transistors BC328 as TR1-TR2; and BC338 as TR3-TR4. The base diodes are ordinary small signal silicon types.

The circuit works well with power transistors too: *p.n.p.* 2N2955, *n.p.n.* 2N3055

and base diodes 1N4001. With these it is necessary to decrease the base resistors and to keep the frequency, increase the capacitors proportionally.

It might seem unusual to use this type of converter instead of the popular transformer coupled type, which has somewhat higher efficiency, but this needs less space and is light weight. Thanks to the present cheap, high quality semiconductors, the total result is better than one might expect.

The circuits are interesting to the experimenter, and could certainly be improved.

The examples in the tables tell the rest of the story.



P. Poulsen,
Odense,
Denmark.

Circuit 1 + 2

Input:	1.5V 14mA	Output:	2-25V 2mA
	3.0V 50mA		3-0-3V 10mA
	6.0V 80mA		9-0-9V 20mA
	12.0V 250mA		16-0-16V 50mA

Circuit 1 + 3

Input:	3V 130mA	Output:	6-0-6V 15mA
	6V 100mA		23-0-23V 10mA
	6V 160mA		16-0-16V 15mA
	6V 280mA		15-0-15V 30mA
	6V 340mA		12-0-12V 50mA
	12V 680mA		28-0-28V 60mA
	12V 750mA		25-0-25V 80mA

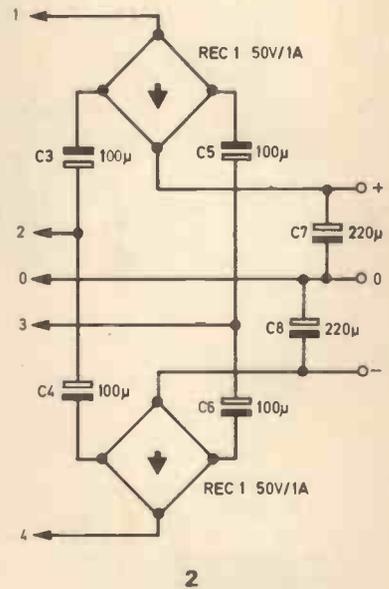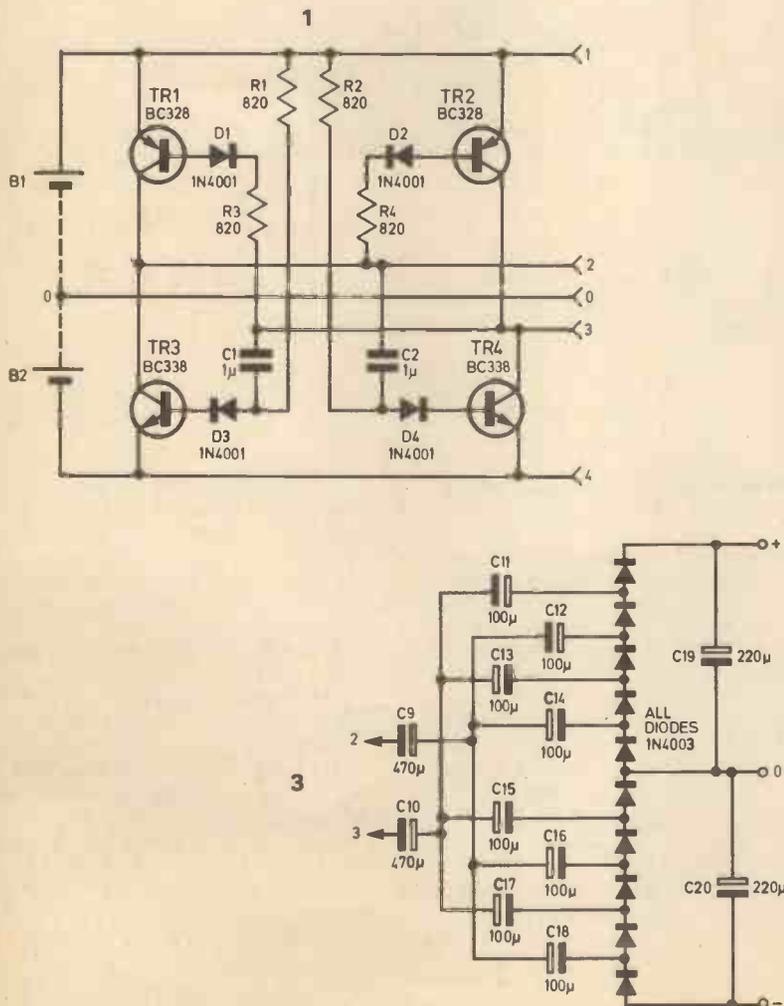

SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE EQUIPMENT AT INCOMPARABLE PRICES

STANDARD CENTAUR 100W

£309 incl. of carr. & VAT Deposit £62.00
12 months @ £24.47 or 24 months @ £14.19

SUPER CENTAUR 200W

£366 incl. of carr. & VAT Deposit £74.00
12 months @ £28.94 or 24 months @ £16.78

GXL 200W

With Twin 200 Watt Columns

£470 incl. of carr. & VAT Deposit £94.00
12 months @ £37.27 or 24 months @ £21.60

GXL WITH PDF BINS

£502 incl. of carr. & VAT Deposit £102.00
12 months @ £39.66 or 24 months @ £23.00

CUSTOM CENTAUR 400/600W WITH FOUR PDF 100A BINS

£833 incl. of carr. & VAT Deposit £167.00
12 months @ £66.03 or 24 months @ £38.28

CENTAUR STEREO DISCOS C/W LIGHT SHOW & DISPLAY TWIN LOUDSPEAKERS & LEADS 100W-600W

20% DEPOSIT CREDIT TERMS



GXL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Bass/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

JUST PLUG IN AND GO!!
SEND TODAY FOR YOUR FREE BROCHURE

MINI DISCO 100 WATT

MONO SYSTEM WITH LOUDSPEAKERS
£229.00 incl. of carr. & VAT Deposit £46.00
12 months @ £18.13 or 24 months @ £10.52

P.A. SYSTEMS

2 YEAR GUARANTEE
100 WATT incl. of carr. & VAT Deposit £207.00
12 months @ £16.35 or 24 months @ £9.49 £42.00

- ★ Four Mixing Inputs
- ★ Bass & Treble Controls
- ★ Twin Piezo Horn Columns

200 WATT incl. of carr. & VAT Deposit £309.00
12 months @ £24.47 or 24 months @ £14.19 £62.00

AMPLIFIER UNITS ONLY

AP100 AMPLIFIER £56.92 + Carr. £1.50 incl. of VAT
★ 4 Mixed Inputs
★ Bass/Treble Controls
★ Vynide Case
★ 100 Watts Output

AP200 AMPLIFIER £102.92 + Carr. £1.50 incl. of VAT
★ Six Mixed Inputs
★ Three Sets Bass/Treble
★ 200 Watts Output
★ Slave Socket



NEW SAXON KLAXON

UK Police Hawaii 50
US Police Destroyer

Four Sirens in one package £20.12 incl. of VAT
Individual Sirens £8.62



NEW SAXON SMASH

ALIEN VOICE SIMULATOR

Add a new dimension to your disco with this press button effect unit
Insert between mic & amp £8.62



PLUTO PROJECTORS

P140 £44.27
150 WATT
INC WHEEL



P5000 £102.92
250 watt Q.I. inc Cassette/Wheel
(Full range of wheels - ask for list)

AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers



SA30B 8 ohms 30W 45V £12.36
Supply for 2 modules £13.68
SA604 4 ohms 50V £16.67
Supply for 1 or 2 modules £17.19
SA608 8 ohms 60W 65V £17.82
Supply for 1 or 2 modules £17.19
SA1204 4 ohms 120W 75V £20.12
Supply for 1 module £17.19
SA1208 8 ohms 120W 95V £24.15
Supply for 2 modules £28.46

DISCO MIXERS - COMPLETE OR MODULAR



MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE:
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.

COMPLETE MIXERS (with case)
Mono mains £45.75 + £3.66
Stereo main £73.31

MODULES
Mono module £31.62
Stereo module £43.12
Panel £4.54
Kit of knobs/sockets etc £6.32

D.I.Y. MODULES FOR P.A. SYSTEMS MONO/STEREO

Input Modules
Mono PCB only £7.47
Stereo PCB only £12.07
Mono C/W Front panel £10.92
Stereo C/W Front panel £15.81
Mixer/Monitor-Modules
Mono PCB only £7.47
Stereo PCB only £12.07
Mono C/W Front panel £10.92
Stereo C/W Front panel £15.81

Power supply to suit £10.92
send for full details.



Make your own mixer
Mono/Stereo up to 20 channels accept all inputs available as PCB only or complete on front panels

SOUND-TO-LIGHT UNITS



3 CHANNEL - 3kW £33.92
 Operates from 1W upwards
 Bass/middle/treble/master controls + £1 carr. complete
Module only £22.71
Panel £3.39
4 CHANNEL - 4 kW SOUND-LIGHT SEQUENCER (illus) £46.57
 Dimmer on each channel
 Automatic sound light level
 Logic circuitry throughout
Module only £30.76 Panel £3.39

MOTOROLA PIEZO HORNS £5.46 YES!!

FUZZ LIGHTS Red, Blue, Yellow, Green £26.22

HEAVY DUTY SPOT BANKS - MATCHES LOUDSPEAKERS

3 way 600W £40.82 4 way 800W £47.72

100W SPOTS

Red - Blue - Amber - Green £1.72

CABINET FITTINGS

ICI Vynide 50" wide £4.02m
Kick-res grille 50" wide £4.02m
Netlon kick proof 24" wide £4.02m
Corners/feet-recess plates 17p
Recess handle 52p
Bar handles £2.87
Jack plugs/sockets 29p

LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) £50.60

Large 100W 1 x 12 (65 x 48 x 24) £62.67

P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24) £82.22

P.A. 2 x 12 200W (100 x 38 x 24) £119.60

Disco 2 x 12 200W (80 x 63 x 24) £103.50

PDF reflex bin (80 x 40 x 41) £115.00

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals

- Use with all types of mixer
- Pan and volume controls
- Send for details £155.25 Deposit £31.25

ABOVE PRICES INCL. OF CARR. & VAT

All prices are inclusive of 15% VAT. Shop premises open Tues to Sat 9 am - 5 pm. Lunch 12.30 - 1.30 pm. Mail order dept open Mon to Fri 10 am - 4 pm. Ring 01-684 6385.

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclaycard Number NOT THE CARD

By Phone You may order COD. Access or Barclaycard. Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS

327 Whitehorse Road, Croydon, Surrey.

All Enquiries Large SAE Please Brochures on request

MANCHESTER DISCO CENTRE, 237 DEANS GATE, MANCHESTER CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY


A Range of Performance from... ...HAMEG



PERFORMANCE AND RELIABILITY
ARE THE SEALS FIRMLY STAMPED
ON THE COMPLETE HAMEG RANGE
AND IT IS A COMPLETE RANGE

HM307	Single Trace DC-10MHz Plus Built-in Component Tester	£ 149
HM312	Dual Trace DC-20MHz, 5mV/cm, Full X-Y, 30MHz Trigger, Plus TV Trigger	250
HM412	Dual Trace DC-20MHz, 2mV/cm, X-Y, 40MHz Trigger, Plus Sweep Delay	350
HM512	Dual Trace DC-50MHz, 5mV/cm, X-Y, 70MHz Trigger Sweep Delay, Plus Single Shot, Sweep Delay and After Delay Trigger	580
HM812	Dual Trace as per HM512. Plus Storage, Automatic Storage and Variable Persistence	1325

Prices UK List ex VAT

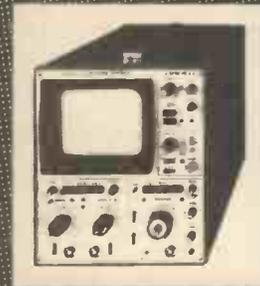

For FULL DETAILS and
DISTRIBUTOR LIST
Contact

Hameg Ltd.,
74-78 Collingdon St.,
Luton,
Beds.
LU1 1RX.

Tel: (0582) 413 174



Build any Project - Fast and Easy

It's the new deal for project builders from Lektrokit! A complete new range of breadboarding and testing devices. At prices anyone can afford. For any project anyone could want to build - from one-chip simplicity to 1,000-chip complexity.

It's fast and easy project building, too. You simply push components in and pull them out. No soldering, no de-soldering, no chance of heat damage. You can make design changes instantly, keeping full leads on components.

In fact, with Lektrokit, you can build a project as fast as you used to sketch a layout. And a lot more easily.

LEKTROKIT completes the circuit

Send for the name of your nearest dealer/mail order supplier - plus FREE catalogue.

To Lektrokit Limited, London Road, Reading, Berks, RG6 1AZ.

Tel: Reading (0734) 669116/7.

Please send me the name of my nearest Lektrokit dealer - plus FREE catalogue.

Name

Address

PE





HEX

KEYBOARD

FOR

SC/MP

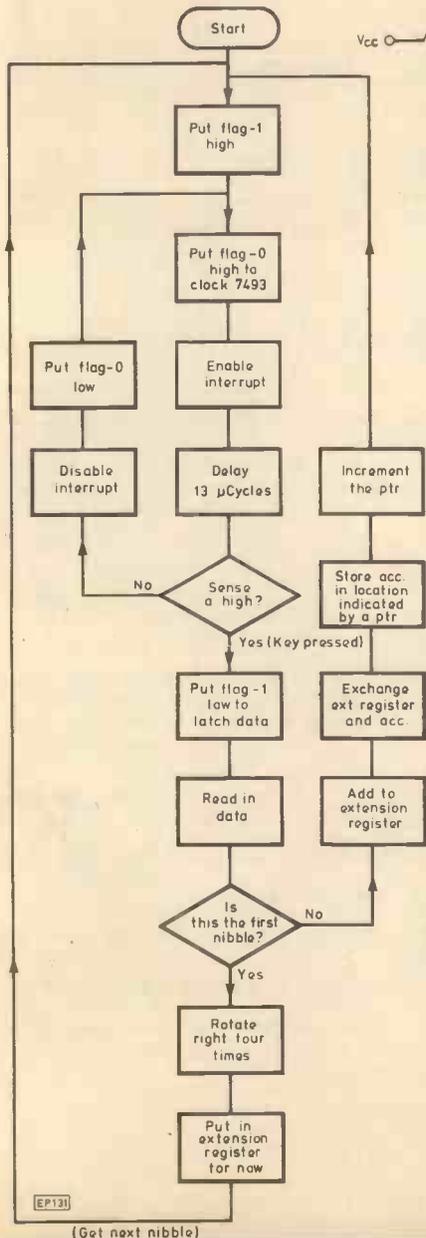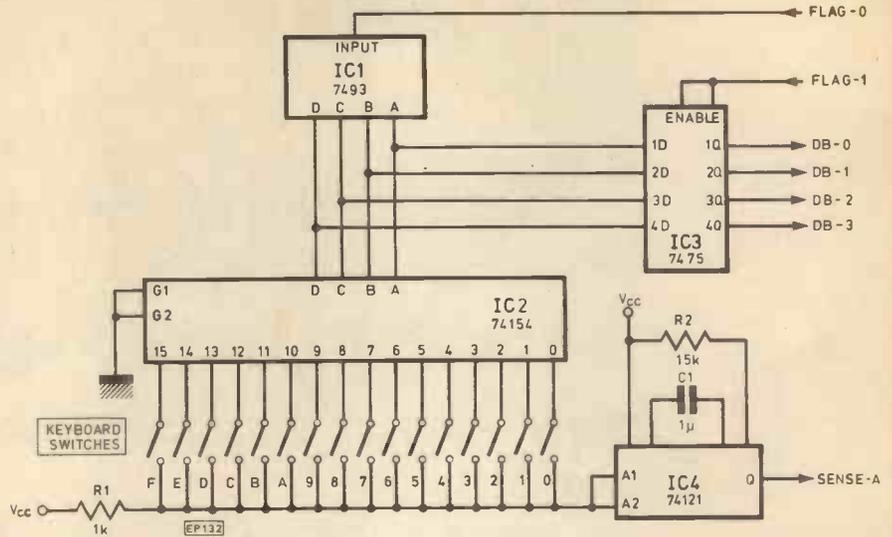

THIS circuit is for an experimental hexadecimal keyboard for use with National Semiconductor's SC/MP microprocessor. Using four popular TTL i.c.s it represents an interesting example of the hardware/software trade-off in MPU systems. If built with one of the surplus calculator-style keyboards advertised regularly in *P.E.*, total cost should be under £5. Use of 74LS series TTL is recommended.

It comprises a 7493 4-bit counter clocked by Flag-0 of SC/MP, feeding a 74154 4-16 line decoder. Outputs from this decoder go to the 16 keys of the keyboard, whose common line is debounced via a 74121 monostable.

SC/MP increments the counter by putting Flag-0 high. One of the 16 decoded lines corresponding to the resultant 7493 binary output now goes low. Suppose the key on that line is now depressed, causing the output of the 74121 to go high and an interrupt on the SC/MP. The MPU responds by halting the counting sequence, and by putting Flag-1 low to latch the 4-bit (hexadecimal) code using a 7475. Outputs of the 7475 are connected to the four least significant bits of SC/MP's data bus, which it now reads and stores after rotating right four times. The sequence is now repeated to get another hexadecimal character, which is added to the first to produce a single 8-bit byte. This can now be stored in a memory location pointed to by a Pointer Register; the Pointer Register is now incremented and the whole process is repeated to obtain the next byte.

A greater understanding of the above process may be obtained by studying the flowchart 2 shown left.

N. Rushton,
Northwood,
Kirkby.

INDEX

JANUARY 1979 TO DECEMBER 1979

VOLUME 15

CONSTRUCTIONAL PROJECTS

- A.D.S.R. Envelope Shaper by *D. J. Stephenson* Jan. 32, March 20
AF/RF Signal Generator by *J. Gerrard* Aug. 21
Alarm, Babycom Nov. 24
Alarm, Home Freezer Aug. 18
Alarm, Ultrasonic, Burglar Dec. 34
Ammeter by *M. Tooley B.A. and D. Whitfield B.A.* Dec. 48
Amplifier, Class A Headphone Aug. 62
Autoranging Multimeter by *Dr. M. Sawicki and A. Kowalewski* April 56, May 56, June 39, Aug. 70, Nov. 27
Babycom by *O. N. Bishop* Nov. 24
Battery Voltage Indicator by *M. Tooley B.A. and D. Whitfield B.A.* Oct. 24
Burglar Alarm, Ultrasonic Dec. 34
Car, Ammeter Dec. 48
Car Instruments, Solid State Oct. 24, Nov. 18, Dec. 54
Chimesonic by *P. Copeland* Aug. 66
Cine Speed Controller by *M. Yeomans* June 34
Class A Headphone Amplifier by *Stephen Price* Aug. 62
Compukit UK101 by *A. A. Berk B.Sc., Ph.D.* Aug. 24, Sept. 40, Oct. 56, Nov. 28
Control, Quizmaster Nov. 60
Control, Ultrasonic Remote June 50, Aug. 70
Controller, Digital Temperature Oct. 32, Dec. 29
Cost-A-Call by *A. P. Donleavy* Dec. 65
Counter, Rev Nov. 18
Diamatic by *J. R. W. Ames B.Sc and W. L. Blyth B.Sc.* Nov. 32, Dec. 40
Digital Darkroom Timer by *R. J. Morris* Nov. 66
Digital Enlarging Exposure Meter by *A. A. Luha, B.Sc.* March 34
Digital Temperature Controller by *D. Coutts and P. McAllister* Oct. 32, Dec. 29
Doorbell, Chimesonic Aug. 66
Doorbell, Novelty Bleeper April 38
Dwell Meter by *M. Tooley B.A. and D. Whitfield B.A.* Dec. 54
Engine Temperature Meter by *M. Tooley B.A. and D. Whitfield B.A.* Dec. 51
Envelope Shaper, A.D.S.R. Jan. 32, March 20
Environmental Thermometer by *M. Plant* Feb. 22
EPROM, Programmer Dec. 24
Evaluation System, Microprocessor May 18, June 42, July 43
Exposure Meter, Digital Enlarging March 34
Flash, Sound Triggered by *R. A. Penfold* July 18
Fuzz, Smooth Sept. 62
Game, Noughts and Crosses Jan. 46, March 20
Generator, Pulse Feb. 18
Generator, Waveform Sept. 28
Guitar, Phaser April 50, June 39
Guitar Processor by *Dr. M. Sawicki and A. Kowalewski* Jan. 18, Feb. 48, Aug. 70
Headlight Warning Device by *P. G. Wagstaff* March 62
Headphone Amplifier, Class A Aug. 62
High Impedance Unit, Metermate July 58, Aug. 70, Sept. 32
Home Freezer Alarm by *P. E. Chaplin* Aug. 18
Light, Sound to May 28, June 26
Logic Tester by *N. D. Jones* Jan. 63
Logiscope by *R. A. Penfold* March 18
Low Noise Pre-Amp by *J. Gerrard* May 54
Meter, Dwell Dec. 54
Meter, Engine Temperature Dec. 51
Metermate by *P. R. Spurgeon* July 58, Aug. 70, Sept. 32
Microprinter, PE Jan 38, Feb. 34, March 44, May 45
Microprocessor Evaluation System by *D. Coutts* May 18, June 42, July 43
Mixer, 6 Channel Sept. 18, Oct. 50, Dec. 29
Mixer, Stereo Feb. 62, April 64
Multimeter, Autoranging April 56, May 56, June 39, Aug. 70, Nov. 27
Noughts and Crosses Game by *Kenneth Amor* Jan. 46, March 20
Novelty Bleeper Doorbell by *D. J. Folwell* April 38
PE Microprinter by *Mark Simon* Jan. 38, Feb. 34, March 44, May 45
Phaser by *D. S. Gibbs and I. M. Shaw C.Eng., M.I.E.E.* April 50, June 39
Pre-Amp, Low Noise May 54
Processor, Guitar Jan. 18, Feb. 48, Aug. 70
Programmer EPROM by *A. A. Berk B.Sc., Ph.D* Dec. 24
P.S.U. Workshop June 56
Pulse Generator by *M. Tooley B.A. and D. Whitfield B.A.* Feb. 18
Quizmaster by *I. J. Nicolle* Nov. 60
Receiver, V.L.F. Oct. 42
Rev Counter by *M. Tooley B.A. and D. Whitfield B.A.* Nov. 18
Sequencer, 16 Note March 22, April 31, May 45, Sept. 32
Signal Generator, AF/RF Aug. 21

Smooth Fuzz by <i>D. S. Gibbs and I. M. Shaw</i> <i>C.Eng. M.I.E.E.</i>	Sept. 62	UK 101 Compukit.....	Aug. 24, Sept. 40, Oct. 56, Nov. 28
Sound Operated Switch by <i>M. Tooley B.A. and</i> <i>D. Whitfield B.A.</i>	May 46, Aug. 70	Ultrasonic Burglar Alarm by <i>G. Davies</i>	Dec. 34
Sound To Light by <i>Ben J. Duncan</i>	May 28, June 26	Ultrasonic Remote Control by <i>M. Plant and</i> <i>G. Hallam</i>	June 50, Aug. 70
Sound Triggered Flash by <i>R. A. Penfold</i>	July 18	V.L.F. Receiver by <i>C. R. Francis B.Sc.</i>	Oct. 42
Speed Controller, Cine.....	June 34	Voltage Indicator, Battery.....	Oct. 24
Stereo Mixer by <i>J. P. Macaulay</i>	Feb. 62, April 64	Warning Device, Headlight.....	March 62
Stroboscope by <i>G. Brown Ph.D.</i>	July 24	Waveform Generator by <i>M. Tooley B.A. and</i> <i>D. Whitfield B.A., M.Sc.</i>	Sept. 28
Switch, Sound Operated.....	May 46, Aug. 70	Workshop P.S.U. by <i>S. Hoare</i>	June 56
Switched Tone Treble Boost by <i>J. D. Rogers</i>	July 64	6 Channel Mixer by <i>S. R. W. Grainger and</i> <i>C. R. Harding</i>	Sept. 18, Oct. 50, Dec. 29
Telephone, Coster.....	Dec. 65	16 Note Sequencer by <i>Lyndsay Robinson</i>	March 22, April 31, May 45, Sept. 32
Tester, Logic.....	Jan. 63		
Tester, Logiscope.....	March 18		
Thermometer, Environmental.....	Feb. 22		
Timer, Digital Darkroom.....	Nov. 66		
Treble Boost, Switched Tone.....	July 64		

GENERAL FEATURES

Acorn Computer Review by <i>Mike Abbott</i>	Sept. 34	Logic Probe Injector by <i>D. P. Akerman</i>	July 40
Binaural Stereo Patents by <i>Adrian Hope</i>	March 28	Low Cost Thermometer by <i>B. J. Fowler</i>	June 65
Bubble Memories by <i>Dr. P. V. Cooper</i>	April 40	Meter For Electrolytics by <i>D. P. Akerman</i>	Aug. 48
Constant Current Sources by <i>D. F. Bowers B.Sc.</i>	March 54	MK 14 Review by <i>A. A. Berk B.Sc., Ph.D.</i>	May 50
Electric Vehicles by <i>Mike Abbott</i>	Jan. 52	Modification For The PE Sportscentre by <i>E. A. Parr</i>	July 41
Elf II Review by <i>A. A. Berk B.Sc., Ph.D.</i>	July 34	Motion Detector by <i>S. Choudhari</i>	Oct. 40
Home Computers by <i>R. W. Coles</i>	Feb. 28, March 46	Newbear 77-68 by <i>P. Birnie</i>	Aug. 38
INGENUITY UNLIMITED.....	Jan. 29, Feb. 44, March 66, April 22, May 68, June 65, July 40, Aug. 46, Sept. 24, Oct. 37, Nov. 52, Dec. 72	Novelty Doorbell by <i>P. R. Williams</i>	Feb. 46
A.D.S.R. Envelope Shaper by <i>P. V. Saduikis</i>	Sept. 24	Organ Rhythm Generator by <i>P. Gladdish</i>	April 25
A Peak Program Indicator by <i>D. R. G. Self</i>	Nov. 55	Parity For ASCII by <i>M. Williams</i>	Nov. 54
A Simple Thermometer by <i>J. D. Berryman</i>	Jan. 29	Programmable Divider by <i>J. Hogarth</i>	April 24
Audio Millivoltmeter by <i>K. Cameron</i>	Dec. 72	Sequential Light Chaser by <i>N. R. Negus</i>	Oct. 39
Auto Tape Switch by <i>A. Glover</i>	Jan. 30	Shorted Turns Detector by <i>R. D. Homerstone</i>	Aug. 47
Battery Monitor by <i>D. P. Akerman</i>	Oct. 36	Signal Injector by <i>D. P. Akerman</i>	April 23
Boat Speed Controller by <i>S. H. Allsop</i>	June 67	Simple Phaser by <i>T. P. Hopkins</i>	March 68
Car Intruder Alarm by <i>N. J. Bailey</i>	March 69	Simple TTL ROM by <i>J. E. Geary</i>	Nov. 56
Car Intruder Alarm by <i>C. J. Nother</i>	April 22	Sound Operated Flash by <i>P. R. Williams</i>	Aug. 47
Car Theft Alarm by <i>M. A. Robertson</i>	Sept. 25	Sound-To-Light-Preamp by <i>J. Little</i>	April 23
Cheap Thermometer by <i>P. R. Williams</i>	May 68	Sound-To-Light Sequencer by <i>R. Scott</i>	Nov. 54
CMOS Logic Probe by <i>D. P. Akerman</i>	May 69	Stereo Peak Detecting PPM by <i>P. R. Williams</i>	June 67
DC/DC Voltage Multiplier by <i>P. Poulsen</i>	Dec. 74	Tele-Games Mod by <i>I. C. Lare</i>	Dec. 73
DC Ringing for Intercoms by <i>R. A. Sudron</i>	Aug. 47	Tops and Tails by <i>T. Froggatt</i>	Jan. 31
Digital Servo Amplifier by <i>G. Pike</i>	Oct. 38	Touch Switches For Games Chip by <i>Olav Foldoy</i>	Nov. 52
Diode Tester by <i>N. Sunderland</i>	Sept. 25	Transducer Oscillator by <i>P. R. G. Reynolds</i>	Nov. 53
Display Tube/TTL Interface by <i>A. Langton</i>	Nov. 55	TTL Oscillator by <i>R. D. Homerstone</i>	Aug. 46
Electronic Doorbell by <i>P. R. Williams</i>	April 24	TV Alerts by <i>M. Plant</i>	Jan. 30
Envelope Shaper by <i>A. N. Oliver</i>	Feb. 45	Ultrasonic Proximity Detector by <i>D. P. Akerman</i>	March 67
Freezer Temperature Alarm by <i>A. M. Smithers</i>	Oct. 37	Variable Pulse Delay by <i>T. P. Hopkins</i>	March 66
Fridge/Freezer Thermostat by <i>B. C. James</i>	Oct. 38	Varitone Stylophone by <i>T. J. Barker</i>	May 70, July 48
Guitar Fuzz/Sustain Unit by <i>A. Niemi</i>	June 66	Versatile Timer by <i>D. P. Burton</i>	Feb. 44
Hazard Flasher Monitor by <i>J. B. Farmer</i>	March 67	4 Wire—8 Way Bell System by <i>C. P. Finn</i>	May 69
Heads or Tails by <i>D. J. Taylor</i>	Feb. 46	6-12V Converter by <i>D. Turner</i>	Feb. 45
Hex Keyboard for SC/MP by <i>N. Rushton</i>	Dec. 77	Learn BASIC This Way by <i>R. Ferguson</i>	Nov. 42
Kettle Whistle by <i>R. Wilds</i>	Jan. 31	MICROBUS by <i>D.J.D.</i>	Feb. 59, April 47, June 68, Aug. 42, Sept. 32, Oct. 67, Dec. 68
Lamp Dimmer by <i>M. A. McCabe</i>	June 66	Ohio Superboard II Review by <i>A. A. Berk B.Sc.,</i> <i>Ph.D.</i>	June 18
Lightning Chess Timer by <i>Y. H. Diamant</i>	Aug. 46	R.F.I. Suppression in P.S.U.s by <i>B. E. Taylor</i>	June 54
Livewire by <i>S. Kelly</i>	March 68	Schmitt Trigger Circuits by <i>D. F. Bowers B.Sc.</i>	Oct. 72


SEMICONDUCTOR UPDATE <i>by R. W. Coles</i> Jan. 60, Feb. 47, March 59, April 21, May 38, June 25, July 42, Aug. 45, Sept. 69, Oct. 23, Nov. 51, Dec. 23	Shottky 74AS 74ALS, Signetics 82S106-7, Intersil ICL7600-5 Sept. 69
Texas TMS 4164, AM 9511, Analog Devices AD509 Jan. 60	National MM 74C912, 74C917, 74C911, Intersil ICL 7611 Oct. 23
Motorola MC68488 MC3448, Intersil ICL 8211-2 Feb. 47	Ferranti ULA 2U000, Analog Devices AD7525, Signetics NE586 NE587 Nov. 51
Texas TL 496C, Intel 8202, International Rectifier IRF100 IRF305 March 59	Zilog Z8000, Intel 7110, General Instruments Microelectronics AY-3-1350 Dec. 23
A.M.I. S2600-1, Intel 2758 April 21	Solders and Soldering <i>by P. Dinsdale</i> Aug. 50
Mullard TDA1028 TDA1029, Texas MC3423 May 38	STRICTLY INSTRUMENTAL <i>by K. Lenton Smith</i> .. Jan. 36, May 36, Sept. 51
Thomson-C.S.F. FRED, Intersil IM7224-5, National DM8678 June 25	Tandy TRS80 Level II Review <i>by A. A. Berk B.Sc., Ph.D.</i> April 26, June 39
Intersil ICL 8063, Harris HA 5195, Mullard BB212 July 42	Vehicle Instrument Displays <i>by B. Shepherd C.Eng., F.I.E.E.</i> Nov. 24
National INS 8295, Mostek MK4816, Fairchild μ A78MGUIC Aug. 45	V.L.F. Signals and the Magnetosphere <i>by C. R. Francis B.Sc.</i> Sept. 52

NEWS AND COMMENT

BOOK REVIEWS Feb. 68, March 56, April 70, June 55, Aug. 70	Newbear 77-68 <i>by P. Birnie</i> Aug. 38
Breadboard Competition Results Feb. 68	NEWS BRIEFS Jan. 44, 45, Feb. 61, March 31, 41, 43, 53, 64, 70, April 39, May 45, 53, 55, June 38, 39, 55, July 33, 39, 48, 53, Aug. 53, 65, Sept. 37, 68, Oct. 30, Nov. 27, Dec. 70
CB in the UK <i>by Dr. M. Sawicki</i> Oct. 66	PATENTS REVIEW Jan. 68, Feb. 56, April 68, May 37, June 31, July 51, Aug. 54, Sept. 70, Oct. 54, Nov. 69, Dec. 30
COUNTDOWN Oct. 62, Nov. 31, Dec. 29	POINTS ARISING Jan. 50, Feb. 68, March 20, April 64, May 45, June 39, July 48, Aug. 70, Sept. 32, Nov. 27, Dec. 29
EDITORIAL .. Jan. 17, Feb. 17, March 17, April 17, May 17 June 17, July 17, Aug. 17, Sept. 17, Oct. 17, Nov. 17, Dec. 17	READOUT .. Jan. 59, Feb. 68, March 60, April 69, July 54, Aug. 58, Oct. 70, Nov. 70, Dec. 62
INDUSTRY NOTEBOOK <i>by Nexus</i> Jan. 67, Feb. 55, March 42, April 67, May 66, June 48, July 38, Aug. 57, Sept. 33, Oct. 22, Nov. 41, Dec. 47	SPACEWATCH <i>by Frank W. Hyde</i> Jan. 37, Feb. 43, March 21, April 54, May 44, June 32, July 52, Aug. 33, Sept. 38, Oct. 48, Nov. 59, Dec. 39
MARKET PLACE Jan. 24, Feb. 25, March 32, April 18, May 41, June 40, July 22, Aug. 34, Sept. 26, Oct. 18, Nov. 22, Dec. 18	
MK 14 Review <i>by A. A. Berk B.Sc. Ph.D.</i> May 50	
More To The Point Jan. 64	
Motorola Microcomputer Forum <i>by D.J.D.</i> Sept. 39	

SPECIAL SUPPLEMENTS

Special Offer—Dolomiti Multimeter July 57	Special Offer—Proto Board Nov. 71
Free Entry Competition Sept. 67	Using the I.C. removal tool Oct. 30
I.C. Insertion Tool May 65	Watch Offer (Digital) June 33
Solid State Car Instruments Dec. 48	Watch Offer (Seiko) Dec. 61

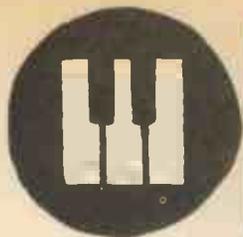

WERSI



AT

BREAD
BOARD

1979

AURA SOUNDS will again be showing the fabulous **WERSI ORGAN & AUDIO KITS**.

There will be a **FREE** competition to

WIN A STEREO MIXER KIT

AND CONTINUOUS DEMONSTRATIONS OF COMPLETED ORGANS

If you can't visit us at the exhibition, or visit one of our showrooms, then send for the Wersi 104-page full-colour catalogue.

AURA SOUNDS

14/15 Royal Oak Centre, Brighton Road,
Purley, Surrey. Tel: 01-668 9733.

17 Charter Arcade, Barnsley. Tel: 0226 5248.
(Next to W. H. Smith).

I enclose £1.00, please send the Wersi Catalogue & Information Pack (U.K. only).

NAME.....

ADDRESS.....

.....

Please send to our Purley address.

SEIKO MEMORY BANK

Calendar watch M354
Hours, mins, secs.
Month, day, date in
12 or 24 hour format
all indicated continuously.
Monthly calendar display
month, year and all dates
for any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advanced.
2 year battery life.
Water resistant.
Metac Price



£79.50

M11

SEIKO Alarm Chronograph

With WEEKLY Alarm.
Hours, mins, secs, month,
date, day, am/pm.
Weekly alarm - can be set
for every day at designated
time e.g. 8.30 am on Mon,
Wed and Friday.
Alarm set time displayed
above time of day.
Full stopwatch functions,
laptime, split etc.



£89.95

M10

SEIKO Melody Alarm Chronograph

Chiming Alarm,
plus chrono.
Hours, mins, secs, date,
day, 24 hour alarm, 12
hour chronograph, 1/10th
secs, Laptime, Back light,
Stainless steel, mineral
glass.



METAC PRICE

£92.95

M19

SEIKO Calculator Watch

Full specification
calculator with
memory, plus multi
function watch.
Hours, mins, secs,
day, date, backlight.
Automatic calendar.
Long life battery.



£99.95

M27

CASIO CHRONO 95QS-3LB

Stainless steel case,
water resistant to 66 feet.
Hours, mins, secs, am/pm,
year, month, date, day.
Auto-calendar
pre-programmed
until the year 2029.
12/24 hour. Stopwatch
function.
Range 7 hours. 1/100 sec.
(Mode) Net time/lap-time/
1st-2nd place times.
Dual time function.
Accuracy 15 secs per month.
Battery life approx 4 years.



£22.95

M22

CASIO LADIES 86CL-23B-1

Elegant slim line.
Stainless steel bracelet,
fully adjustable.
Hour, mins, 10 sec symbol
second by flash, am/pm.
Month, date, day.
Auto-calendar preprogrammed
for 28th day in Feb.
Accuracy per month 15 secs.
Battery life approx 15 months.



£29.95

M23

CASIO F-200 Sports Chrono

Attractive Mans watch
in black resin with
mineral glass.
Hours, mins, secs, am/pm.
Month, date,
alpha-numeric day.
Auto-calendar set
28th Feb.
Stopwatch working
range 1 hour,
units 1/100 sec. Mode,
Net Time/lap/time/
1st-2nd place times.
Accuracy approx 15 secs
per month.
Battery 12 months.



£14.95

M24

CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs, day,
and also day, month and year
perpetual automatic calendar.
100th sec chronograph to
7 hours.
Net time/lap/time/1st
and 2nd place times. User
optional 12/24 hr display, 24
Alarm. User optional,
hourly chime.
Backlight, mineral glass,
stainless steel.
Water resistant to
100ft.
Battery life approx 4 years.



£34.95

M25

BELTIME Chronograph

(9-Functions)
Hours, mins, secs,
day, date, month,
interchange feature,
automatic calendar,
backlight, Net
time/lap/time.
Stainless steel bracelet.
Battery life 1 year.



£14.95

M34

BELTIME Multi Alarm

29 Functions
Hours, mins, secs,
date, day.
Alarm, chronograph,
Light.
Watch 8 functions,
Alarm 4 functions,
chronograph 17
functions.
Stainless steel
bracelet.



£29.95

M35

CASIO F-8C 3 Year Battery life.

Hours, mins, secs,
am/pm, date, day.
Auto calendar set
28th Feb.
Stopwatch function.
Accuracy 15 secs per
month. 8 battery life
approx 3 years.



£9.95

M36

CASIO CALENDAR 200 47CS-23B-1 Black. Stainless steel.

Hours, mins, 10 second
symbol, second (by flash),
am/pm. Month, day, date.
Auto-calendar set from
1901 to 2009.
Full month calendar display,
Dual time function.
Accuracy 10 secs per
month. Battery life
approx 15 months.



£59.95 M37

MELODY Multi Alarm Chronograph

Hours, mins, secs,
Day, Date, Count-
down alarm,
Dual time zone,
1/100th sec
stopwatch.
Lap/split time,
1st and 2nd place
times, Melody test
function.



£26.95

M30

DUAL TIME-ALARM CHRONOGRAPH

Incorporating module
of world famous
Japanese watch
manufacture.
Hours, mins, secs,
days of week, month,
day and date,
24 hour alarm,
1/10th secs,
lap time, Back light,
stainless steel case
and bracelet,
Mineral glass,
Battery hatch,
long life battery.



£35.00

M12

PICOQUARTZ Microprocessor Alarm Chronograph

Multilanguage-day of
the week can be set
to English, French,
German, Italian or
Spanish.
Chime - every full
hour combined with a
response signal,
beeping at every
pressing of the
functions.
Can be switched off.
12-24 hour format.
Backlight.
Chrono - 1, full scale
chrono with lap,
counting hours upto
24 hrs. Mins, secs,
1/100th secs.
Two Alarm systems.
Two time zones.



£37.95

M32

SEIKO CHRONOGRAPH

Hours, mins, secs
and day of the week.
Month date and
day of the week.
Stopwatch display -
Hours, mins, secs
up to 12 hours
(mins, secs, 1/100 secs
up to 20 minutes).
Lap timing.
Continuous time
measurement of two
competitors.
Stainless steel,
mineral glass.



£56.00

M33

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins., secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

QUARTZ LCD 11 Function

SLIM
CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins., Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price



£10.65 Thousands sold!
Guaranteed same day despatch.

M3

QUARTZ LCD ALARM 7 Function

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

MULTI ALARM 6 Digits 10 Functions

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65

M5



FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags. 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet.

£22.65

M6



SOLAR QUARTZ LCD Chronograph with Alarm

6 digits, 5 flags. 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec., steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.



£27.95

M7

ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£29.65

M8



SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65

Guaranteed same day despatch.

M9



QUARTZ LCD Ladies Day Watch

Only 25 x 20mm and 8mm thick. Hours, minutes, seconds, day, date, backlight and auto calendar. Elegant metal bracelet in silver or gold fully adjustable to suit very slim wrists. State colour preference.

£9.95

Guaranteed same day despatch.

M15



QUARTZ LCD Ladies Fashion Watch

Elegant bracelet in bronze/gold finish or silver colour. Hours, mins, secs, day, date, backlight and auto calendar. Adjustable for the slimmest of wrists. State colour preference.

£14.95

Guaranteed same day despatch

M17



QUARTZ LCD Ladies Cocktail Watch

Highly functional watch which also suits those special occasions. Beautifully designed with a very thin bracelet which retains strength as well as elegance. Hours, mins, secs, day, date, backlight and auto calendar. Bracelet fully adjustable to suit slim wrists. State gold or silver finish.

£19.95

Guaranteed same day despatch

M18



HANIMEX Electronic LED Alarm Clock



Features and Specification:
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

£10.20 Thousands sold!

Mains operated.

Guaranteed same day despatch.

M13

EXECUTIVE ALARM WATCH

8 Functions plus Alarm: Conference signal, 5 minute snooze alarm. Conference signal sounds 4 secs., before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins., after main alarm and is always preceded by the conference signal.

£14.95

M60



MACY QUARTZ ANALOGUE

Automatic Calendar Day and Date infinite bracelet. This mans watch has elegance as well as the robust appearance provided by a watch with traditional features. Accuracy is provided by a quartz crystal powered by a long life miniature battery.

£24.95

M21



Metac price breakthrough for an Alarm Chronograph with Dual Time only

£18.95

- OUTSTANDING FEATURES**
- DUAL TIME. Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
 - CALENDAR FUNCTIONS include the date and day in each time zone.
 - CHRONOGRAPH/STOPWATCH displays up to 12 hours, 59 minutes, and 59.9 seconds.
 - On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
 - ALARM can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch. **M16**



HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

Metac Wholesale:

Trade enquiries - send for a complete list of prices for all the goods advertised plus many more not shown also minimum order details.

Telephone orders: Credit card customers can telephone orders direct to Daventry (03272) 76545 or Edgware Rd. 01-723 4753 24 hours a day.



Service Enquiries 03272-77659
CALLERS WELCOME Shops open 9-30am-6.00

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

MOTOR CYCLING

LIGHT IT

This time of year you'll have to light up more than ever. So here's all the fitting and wiring know-how you need to keep your auxiliary lights in tip-top condition.

CHECK IT

Your bike charging circuit.

TEST IT

Kawasaki's Z650SR, BMW's R100RT and Yamaha's DT100.

CHAIN IT

There's more to final drives than you think.

SERVICE IT

The proper way with the Fantic Fifty. Plus MICK GRANT—exclusive interview with Honda's GP rider. CHRISTMAS GOODIES—presents for a biker's best friend.

Do yourself a favour - get
MOTORCYCLING
December issue



OUT NOW 50p

HOME COMPUTING BARGAINS

All of this month's offers have full key boards, use your TV as a VDU and will read and write onto most cassette recorders:— Ohio Scientific Superboard II fully assembled, 8K basic, 4K ram £188 + VAT. Tandy TRS80 level II basic, converted to UK TV standard, includes modulator and PSU— with 4K ram £399 + VAT, with 16K ram £450 + VAT.

SINCLAIR PRODUCTS

PFM200 £52.69, case £3.40, adaptor £3.40, connector kit £11.27. Microvision TV £91.44, mains adaptor £6.88. PDM35 £29.76, mains adaptor £3.40, case £3.40. DM350 £71.92. DM450 £102.17. DM235 £52.66. Accessories for all 3 models:— rechargeable batteries £7.99, mains adaptor/charger £3.94, case £9. Enterprise prog calculator £23.27. New 10MHz scope £149.

COMPUTER GAMES

Chess challenger 7 £84. Chess challenger 10 £139.70. Voice challenger £229. Checker challenger 2 £46. Checker challenger 4 £84. Atari video computer £147. Cartridges £14-32. Star Chess £62. Chess champion £661.

CONTINENTAL SPECIALITIES PRODUCTS

EXP300 £6.61. EXP350 £3.62. EXP325 £1.84. EXP650 £4.14. EXP4B £2.64. LP2 £20.70.

TV GAMES

Tank battles kit £6.34. AY-3-8500 chip £5.27. kit £4.26. Stunt cycle AY-3-8760 chip £12.46. kit £4.26. 10 game paddle 2AY-3-8600 chip £10, kit £7.03. Racing car chip AY-3-8603 £13.03. Modified shoot kit £5.28. Rifle kit £8.27. Colour generator kit £9.05. Joystick 220K £1.80.

MAINS TRANSFORMERS

6-0-8V 100mA 76p. 1½ £2.60. 9-0-9V 75mA 76p. 1a £2.22. 2a £2.89. 12-0-12V 100mA 92p. 1a £2.75. 15-0-15V 1a £3.09.

JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 8 Watts £2.08. JC20 10 Watts £3.14.

FERRANTI ZN414

IC radio chip 85p. Extra parts and pcb for radio £4-10. Case £1.06.

PRINTED CIRCUIT MATERIALS

PC etching kits:— economy £2.32, standard £4.36. 40 sq. in pcb 66p. 1 lb FeCl £1.30. Etch resist pens:— economy 50p, dialo 84p. Drill bits 1/32" or 1mm 27p. Etching dish 85p. Laminata cutter 82p.

S-DECS AND T-DECS

S-Dec £3-79. T-Dec £4-59. u-DecA £4-69. u-DecB £7-16. 16 diil adaptor £2-31.

BATTERY ELIMINATORS

3-way types with switched output and 4-way multi-jack:— 3/4/6V 100mA £2-39. 6/7/9V 300mA £3-14. 100mA radio types with press stud connectors 9V £3-57. 6V £3-57. 4½V £3-57. 9+9V £4-79. 6+6V £4-79. 4½+4½V £4-79. Cassette recorder mains unit 7½V 100mA with 5 pin din plug £3-87. Fully stabilized type 3/6/7/9V 400mA £5-76. Car converters 12V dc input, output 9V 300mA £1-19. output 7½V 300mA £1-19. output 3/4/6/7/9/12V 800mA £2-66.

BATTERY ELIMINATOR KITS

100mA radio types with press-stud connectors 4½V £1-49. 6V £1-49. 9V £1-49. 4½+4½V £1-92. 6+6V £1-92. 9-9V £1-92. Cassette type 7½V 100mA with din plug £1-49. Heavy duty 13 way types 4/6/7/8/11/13/14/17/21/25/28/34/42V 1A £4-95. 2A £7-72. Car converter input 12V dc, output 6/7/9V 1A stabilised £1-35.

STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. 8-way types 3/4/6/7/9/12/15/18V 100mA £1-74 (£2-50), 1A £2-98 (£5-10). 2A £4-10 (£6-87). Variable voltage models: 2-18V 100mA £2-12 (£2-98). 1-30V 1A £2-98 (£6-95). 1-30V 2A £4-98 (£11-24).

BI-PAK AUDIO MODULES

AL30 £4-04. PA12 £7-77. PS12 £1-42. T538 £2-70. S450 £24-03. AL60 £4-97. PA100 £17-33. SPM80 £4-57. BMT80 £6-08. Stereo 30 £20-57. MA60 £36-23.

COMPONENTS

1N4148 0-9p. 1N4002 3-1p. 741 8 diil 16p. 723 14 diil 31p. NE555 8 diil 25p. bc183 8 bc113. bc547. bc549 4 2p. bc182. bc184. bc212. bc214. bc548 5p. lp31c. lp32c 30p. tip41c 39p. bd131. bd132 27p. Plastic equiv. bc107 5p. Fuses 20mmx6mm cartridge 15. 25. 5. 1. 2. 3. 5 Amp quickblow 1p. anti-surge 3-6p. Resistors 5% 1W E12 10R to 10M 1p. D-8p. for 50¢ of one value. Polyester capacitors 250V .015. .068. .1mf 1-5p. .01. .033. .33 2-8p. .022. .047mf 3-3p. .22. .47mf 4-9p. Polystyrene capacitors E12 63V 10 to 10000p. 1n2 to 10n 4p. Ceramic capacitors 50V E6 22pF to 47n 2p. Electrolytic capacitors 50V .5. 1. 2mf 5p. 25V 5. 10mf 5p. 16V 22. 33mf 5p. 47. 68mf 3 5p. 100mf 6p. 220mf 7-5p. 330. 470mf 9p. 1000mf 10p. Zeners 400mW £2.07V to 33V 7p. Preset pots subminiature 0-1W horiz or vert 100 to 4M7 6p. Potentiometers 1W 4K7 to 2M2 log or lin single 27p. dual 67p. 1 red LEDs 9-7p. IC sockets 6 diil 8-7p. 14 diil 10-1p. 16 diil 12p.

PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L2 2DY

SEMICONDUCTORS. C106D 400V 2-5A SCR 20p. TB800 80p. 741 8 PIN 22p. NE555 24p. 1M3400 40p. 723 14 PIN REGS. 35p. AD161/2 MATCHED PAIRS 70p. 2N3055 38p. 1N4005 10 FOR 38p. BD238 28p. BD438 28p.
MINIATURE MAINS TRANSFORMERS. All 240VAC PRIMARY. 6-0-6 100mA. 9-0-9 75mA. 12-0-12 50mA all 75p each. 12-0-12 100mA 95p. 12V 500mA 95p. 0-6V-0-6V 280mA £1.30p.
PULSE TRANSFORMERS. 1:1 (GPO type) 30p. 1:1 plus 1 min. P. C. mounting 80p.
MINIATURE SOLID STATE BUZZERS. 33X17X15MM. output at 3 feet 70db, only 15mA drain. 4 voltages available. 8-9-12 or 24VDC 80p each.
LOUD BUZZER. 8-12 volts 63p. GPO type adjustable buzzer 8-12 volts 27p.
POCKET MULTIMETER. MODEL NH68 2,000 ohms per volt. 1,000 volts AC/DC. 100mA DC current. 2 resistance ranges to 1 meg. £8.95p.
BOLDER SUCKER. High suction/telton nozzle. £4.99p.
MURATA TRANSDUCERS. 40KHz. REC/SENDER £3.60 pair.
MOTORS. 3V model type 22p. 12V model 5 pole 35p. Replacement 12VDC 8 track motors 85p. Ex. equip. 5-7 volt cassette motors 70p. Low rev. mains motor 240VAC motor with gearbox 2½ RPM 75p.
AMPHENOL COAX CONNECTORS. Plugs 47p. Sockets 42p. Elbows 80p. Reducers 13p.
TELEVISION OUTLET BOXES. Wall mounting; single 40p. double 75p. switched double 95p. low loss in line splitter 1 in 2 out 80p.
SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only £2.95p.
INTERCOM UNITS (can be used as baby alarm) supplied with approx 60' cable, call button, 2 way £25 pair, 3 way £7.25p. WIRELESS INTERCOM. 2 units both operate on 240VAC and mains connected. AM frequency 180KHz. £29.95p.
MINIATURE TIE PIN MICROPHONE. Omni, 1K imp., uses deaf aid battery (supplied) £4.95p. LOW COST CONDENSER MICROPHONE. Stick type Omnid, 800 ohms, on/off switch, standard jack plug only £2.95p. EM507 CONDENSER MICROPHONE. Highly polished metal stick mike, uni directional, 600 ohms, 30-18KHz, on/off switch only £7.95p. DYNAMIC STICK MIKE. CARDIOD, dual imp., 600 ohms or 20K. 70-15KHz, attractive black metal case only £7.75p.
PUBLIC ADDRESS HORN SPEAKERS. Suitable for outdoor use 5" round 8 watts, 8 ohms, adjustable bracket £4.95p. 6" 15 watts 8 ohms adjustable bracket £8.25p.
SPECIAL OFFER TAPE HEAD DEMAGNETISER, 240VAC with curved probe only £2.85p.
Cash with order please, official orders welcome from schools etc., please add 30p post and packing. VAT inclusive. SAE for latest illustrated stock list. ALL ORDERS DESPATCHED BY RETURN POST

SWANLEY ELECTRONICS

Dept. PE, 32 Goldsal Road, Swanley, Kent BR8 8EZ.

Mail order only. Please add 30p to the total cost of your order for postage. Prices include VAT unless stated. Lists 24p post free. Overseas customers deduct 13%. Official credit orders welcome.

QUALITY REEL TO REEL & CASSETTE TAPE HEADS

B12-01	MONO PLAYBACK	£1.89	E12-09	MONO/STEREO ERASE	£1.85
B12-02	MONO RECORD/PLAYBACK	£4.02	B22-02	TWIN HALF TRACK RECORD/PLBK	£5.97
B24-01	STEREO PLAYBACK	£3.30	C44RPS02	QUAD QUARTER TRACK REC/PLBK	£9.37
B24-02	STEREO RECORD/PLAYBACK	£6.86	C22ES02	TWIN HALF TRACK ERASE	£4.72
B24-RP	STEREO GLASS FERRITE REC/PLBK	£11.60		MAGNETIC TAPE HEADS CATALOGUE 25 PENCE	

AUDIO AND HI-FI CATALOGUE 180 PAGE FULL COLOUR 50 PENCE

MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER
ALL PRICES INCLUDE VAT



How to make a hobby

The opportunities in electronics, today, and for the future are limitless — throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics — especially for the servicing of radio, TV and all associated equipment — can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.


We give modern training courses in all fields of electronics — practical D.I.Y. courses — courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.

All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

and a career.

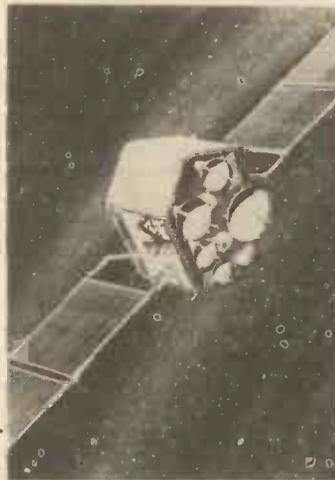- COURSES AVAILABLE
- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page Colour Booklet.



WE ARE AN INTERNATIONAL SCHOOL SPECIALISING IN ELECTRONICS TRAINING ONLY AND HAVE OVER 40 YEARS EXPERIENCE IN THIS SUBJECT.

PEA 12

NAME.....
ADDRESS.....

Block Caps Please

Post now, without obligation, to:-

BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

KITS FOR SYNTHESISERS, SOUND EFFECTS



COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. 128-NOTE PROGRAMMABLE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic component kits	KIT 76-5	£28.92
Set of PCBs & layout charts	KIT 76-6	£5.66
Set of text photocopies		£1.36

P.E. 16-NOTE PROGRAMMABLE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic component kits	KIT 86-3	£22.90
Set of PCBs	KIT 86-4	£5.09
Set text photocopies		£1.84

P.E. STRING ENSEMBLE

A multivoiced string instrument synthesiser.

Set of basic component kits	KIT 77-6	£68.70
Set of PCBs & layout charts	KIT 77-7	£24.19

P.E. JOANNA PLUS ORGAN VOICING

A modified version of the P.E. 5-octave piano that retains all the original facilities and also includes switchable organ voicing circuitry.

Set of basic component kits	KIT 71-5	£89.87
Set of PCBs & layout charts	KIT 71-6	£29.81
"Sound Design" booklet		£1.00

ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic components	KIT 80-6	£100.64
5-octave set of PCBs (as published)	KIT 80-7	£26.02
Additional 3-octave extension basic parts	KIT 80-5	£40.98
Additional 3 octave set of PCBs (as published)	KIT 80-8	£9.45
Set of text photocopies		£1.81

P.E. MINISONIC MK2 SYNTHESIZER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available)	KIT 38-23	£67.05
Set of PCBs (incl. layout charts)	KIT 38-24	£9.87
"Sound Design" booklet		£1.00

P.E. SYNTHESIZER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Main Unit basic component kits	KIT 23-27	£86.99
Main Unit set of PCBs & layout charts	KIT 23-28	£14.82
Keyboard Unit basic component kits	KIT 23-29	£52.07
Keyboard Unit set of PCBs & layout charts	KIT 23-30	£8.42
Main Unit set of text photocopies		£5.81
Keyboard Unit set of text photocopies		£2.30

ELEKTOR FORMANT SYNTHESIZER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic component kits	KIT 66-12	£193.66
Set of PCBs (as published)	KIT 66-13	£53.92
Set of text photocopies		£7.83

P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic parts with foot switches	KIT 42-1	£8.45
Basic parts with panel switches	KIT 42-2	£5.55
PCB & layout chart	PCB 43A	£1.57
Text photocopy		28p

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic component kit	KIT 78-1	£49.99
Main unit PCB (as published)	PCB 9913	£3.89
Extension unit basic component kit	KIT 78-2	£47.69
Extension unit PCB (as published)	PCB 78B	£1.16
Text photocopy		

ELEKTOR ANALOGUE REVERB UNIT

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set	KIT 83-1	£29.49
Additional Delay basic components	KIT 83-2	£20.07
PCB (as publ.) to hold both kits	PCB 9973	£4.31
Text photocopy		

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic component kits	KIT 85-3	£43.75
Set of PCBs & layout charts	KIT 85-4	£10.62
Set of text photocopies		£2.52

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Set of basic components, incl. PCB & chart	KIT 88-1	£10.14
Text photocopy		68p

ELEKTOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic components	KIT 70-1	£19.11
PCB & layout chart	PCB 70A	£2.58
Text photocopy		67p

P.E. PHASING UNIT

A simple but effective manually controlled phasing unit.

Set of basic components incl. PCB & chart	KIT 25-1	£3.52
Text photocopy		28p

PHASING CONTROL UNIT

For use with Phasing Kit 25 to automatically control rate of phasing.

Set of basic components incl. PCB & chart	KIT 36-1	£5.21
Text photocopy		10p

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Set of basic components, PCB & chart	KIT 89-1	£3.82
Text photocopy		78p

P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control of depth.

Set of basic components, PCB & chart	KIT 53-1	£2.76
--------------------------------------	----------	-------

ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic components	KIT 82-1	£16.61
PCB (as published)	PCB 9951	£3.29
Text photocopy		

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments.

Set of basic components	KIT 56-1	£7.87
PCB & layout chart	PCB 56A	£1.78
Text photocopy		88p

P.E. FUZZ UNIT

A simple fuzz unit. Slightly modified from the original.

Set of basic components, PCB & chart	KIT 55-1	£2.25
--------------------------------------	----------	-------

TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Set of basic components, PCB & chart	KIT 54-1	£3.23
--------------------------------------	----------	-------

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.

Set of basic components, PCB & chart	KIT 74-1	£4.97
Text photocopy		39p

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, foot switches, PCB & chart	KIT 75-1	£5.64
Basic components, panel switches, PCB & chart	KIT 75-2	£4.08
Text photocopy		38p

P.E. WAH-WAH UNIT

Can be controlled manually or by Integral automatic control.

Set of basic components, PCB & chart	KIT 51-1	£3.99
--------------------------------------	----------	-------

P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played.

Basic components, foot switches, PCB & chart	KIT 58-1	£8.43
Basic components, panel switches, PCB & chart	KIT 58-2	£5.31
Text photocopy		58p

ELEKTOR WAVEFORM CONVERTOR

Converts a saw-tooth waveform into sinewave, mark-space sawtooth, regular triangle, or square-wave with variable mark-space ratio.

Basic components, PCB & chart, but excl. sw's.	KIT 67-1	£9.24
--	----------	-------

P.E. VOLTAGE CONTROLLED FILTER

Extracted from P.E. Minisonic project.

Set of basic components, PCB & chart	KIT 65-1	£7.88
--------------------------------------	----------	-------

P.E. RING MODULATOR

Extracted from P.E. Minisonic project.

Set of basic components, PCB & chart	KIT 59-1	£6.05
--------------------------------------	----------	-------

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic components	KIT 87-1	£4.66
PCB (as published)	PCB 79040	£1.74
Text photocopy		38p

10% DISCOUNT VOUCHER (PE 70)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly coded, C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E.

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.30 each. Other goods: Under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 20p, other countries send 50p.

PHONOSONICS · DEPT PE70 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquires for list: Europe—send 20p; other countries—send 50p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50

4 Octave (49 notes) £32.25

5 Octave (61 notes) £39.75

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each KBD note:

Type GJ — SPCO 25½p ea. Type GA — 1 pr of contacts, normally open 24p ea. Type GB — 2 pr N/O 28½p ea. Type GC — 3 pr N/O 37½p ea. Type GE — 4 pr N/O 46½p ea. Type GH — 5 pr N/O 58½p ea. Type 4PS — 3 pr N/O plus SPCO 67p ea.

P.E. NOISE GENERATOR

Extracted from the P.E. Minisonic.

Set of basic components,

PCB & chart KIT 60-1 £4.00

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Set of basic components,

PCB & chart KIT 28-1 £4.68

Text photocopy 28p

P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.

Set of basic components,

PCB & chart KIT 44-1 £5.24

Text photocopy 49p

P.E. ENVELOPE SHAPER WITH VCA

Has an Integral Voltage Controlled Amplifier, and has full manual control over the A,D,S,R functions.

Set of basic components,

PCB & chart KIT 50-1 £7.34

Text photocopy 58p

P.E. GENERATOR

An ADSR envelope shaper without VCA, and additional providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Set of basic components KIT 63-1 £5.13

PCB & layout chart PCB 63A £2.00

Text photocopy 58p

P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphones etc., to be processed by synthesiser circuits.

Set of basic components,

PCB & chart KIT 81-1 £3.23

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic components,

PCB & chart KIT 46-1 £16.42

Power Supply components,

PCB & chart KIT 46-2 £6.90

Text photocopy 97p

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.

Set of basic components,

PCB & chart, but excl. sw. KIT 69-1 £8.19

Text photocopy 58p

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Set of basic components,

PCB & chart KIT 62-1 £5.03

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 5-digit counter for 1Hz to 55KHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Set of basic components KIT 79-1 £26.45

PCB (as published) PCB 79A £3.33

Text photocopy 78p

INTEGRATED CIRCUITS

301	48p
318	220p
320-15	195p
323	562p
324	87p
341-15	87p
356	101p
709	48p
723	51p
726	1005p
741	24p
748	57p
4001	15½p
4007	17½p
4011	17½p
4013	34p
4016	33p
4017	54p
4024	48½p
4046	96p
4049	37½p
4066	40½p
4069	18p
4081	16½p
4136	126p
AM2833	396p
AY-1-0212	617p
AY-1-1320	636p
AY-1-6721/6	188p
CA3046	71p
CA3080	63p
CA3084	209p
FX209	729p
M252	680p
MC3340	150p
MCM6810	670p
RC4195	117p
SAD1024	1762p
SG3402	282p
TDA1022	582p
TL074	120p
XR2207	420p
ZN425	375p
7400	20p
7402	20p
7404	18p
7413	31p
7420	15p
7447	72p
7472	22½p
7473	37½p
7474	31½p
7489	241p
7490	42p
7493	49½p
74121	53p
74123	55½p
7805	145p
7808	145p
7812	145p
7815	145p
7818	145p



TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____
Address _____

Age _____

ICS

To ICS, Dept. P273, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONONICS

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS

STEREO PRE-AMPLIFIER POWER AMPLIFIER



CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < 0.05% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/μS; T.H.D. 20Hz–20kHz < 0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ±15 volts.

MC 2—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

X02 : X03—ACTIVE CROSSOVERS

X02—two way, X03—three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS

It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically 0.1% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μS; signal to noise ratio 110dB; frequency response 10Hz–35kHz, –30dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120–240 primary and single bolt fixing (includes capacitors/bridge rectifier).

PRE-AMPLIFIER KIT

This includes all metalwork, pots, knobs etc. to make a complete pre-amp with the CPR 1 (S) module and the MC 1 (S) if required.



ACTIVE CROSSOVERS

X02.....£18-16 X03.....£23-58

POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35v £19-52

CE 1004 100W/4 ohms 35-0-35v £23-02

CE 1008 100W/8 ohms 45-0-45v £25-96

CE 1704 170W/4 ohms 45-0-45v £31-00

CE 1708 170W/8 ohms 60-0-60v £33-97

TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £18-56

CPS2 for 2 x CE 1004 or 2/4 x CE 608 £18-80

CPS3 for 2 x CE 1008 or 1 x CE 1704 £19-75

CPS4 for 1 x CE 1008 £17-12

CPS5 for 1 x CE 1708 £24-15

CPS6 for 2 x CE 1704 or 2 x CE CE 1708 £25-53

HEATSINKS

Light duty, 50mm, 2°C/W..... £1-44

Medium power, 100mm, 1-4°C/W..... £2-35

Disco/group, 150mm, 1-1°C/W £3-04

Fan, 80mm, state 120 or 240v... £19-70

Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules..... £31-05

THERMAL CUT-OUT, 70°C.. £1-54

Pre-amp Kit

£38-07

POWER AMP KIT

£35-03

PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1..... £31-85

CPRIS... £40-87

MCI..... £21-28

MCIS... £33-17

POWER SUPPLY

REG1..... £8-90

TR6..... £1-97

BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module BDI £5-75

CRIMSON ELEKTRIK

1A STAMFORD STREET,

LEICESTER, LE1 6NL

Tel: (0533) 553508

U.K.—please allow up to 21 days for delivery.

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

Distributors:
BADGER SOUND SERVICES LTD.
46 WOOD STREET, LYTHAM ST. ANNES,
LANCASHIRE FY8 1QG
MINIC TELEPRODUKTOR
BOX 12035: S-750 12
UPPSALA 12, SWEDEN

Codespeed Electronics

PO BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, PO3 5BJ
ELECTRONIC MAIL ORDER SPECIALISTS
New, Full Spec. Devices

LED WRISTWATCH I.C. Super value I.C. in 24 pin 'legless flatpack' style package for maximum space saving. With data. A snip at only 99p Cat. no. 208.

0.1" LED WRISTWATCH DISPLAY. Also in a 'legless flatpack' style package, this display matches the wristwatch I.C. shown above. With data. Only 99p Cat. No. 209.
★ CASH SAVER ★ Purchase one each of catalogue numbers 208 AND 209 for only £1-50.

POLARIZING FILTER MATERIAL 0-006" thick plastic film. Any size cut—even 1 sq. inch. Max. width 19", any length. Only 2p per sq. Inch. Cat. No. 701.

BRIGHT ORANGE DISPLAY 9 digit, 7 segment gas discharge display, 0-25" high digits. With data 75p. Cat. No. 310.

DMM CHIP MM5330 dvm chip. Builds into high accuracy dvm or panel meter. Requires additional circuitry. Supplied with data and circuit. Only £3-95. Cat. No. 404.

MINI 6 DIGIT LED DISPLAY 6 digit 7 segment display from Texas. Common anode, multiplexed, with 0-1" digits. £1-00. Cat. No. 306.

MM5314 CLOCK CHIP. A super value digital clock chip for only £1-99. With data. Cat. No. 207.

4 DIGIT LCD. A high contrast, easy to solder display with four 0-5" high non-multiplexed digits. £8-95 each with data. Cat. No. 206.

DIGITAL ALARM CLOCK MODULE. Complete with giant 0-84" LED display. Add transformer and switches for complete clock. With data only £6-50. Cat. No. 205.

GIANT LED DISPLAY. Common cathode, non-multiplexed super 4 digit LED clock display. Lots of other uses too. Only £3-95 each. Cat. No. 204.

WRISTWATCH LCD'S. A high contrast 3 1/2 digit wristwatch LCD with centre colon. Supplied with polarizers and data. Only £1-00. Cat. No. 202.

MEMORIES. MV2102 static 1024 bit memories. A snip at 99p each. With data sheet. Cat. No. 102.

20 KEY KEYBOARDS. Calculator keyboards, excellent key action. 20 keys per board. 2 keyboards for £1-00. Cat. No. 101.

PROGRAMMABLE UNJUNCTIONS. Four MEU21 PUTS (similar to 2N6027). Makes long delay timers, oscillators etc. With data and applications sheet. 4 for 50p. Cat. No. 402.

10 HYBRID CIRCUITS. 8 resistors and 8 capacitors built into each hybrid circuit. Ideal values for semiconductor circuits. Excellent for minimizing PCB component space. 10 Hybrids for 50p. Cat. No. 801.

25 germanium diodes 50p. 10 switching diodes 35p. Mini slider switches (2 pole change-over) 16p each. Momentary switches (spring loaded) with 1 n.o. contact 15p each. Mono jack sockets 23p each. Stereo jack sockets 25p each. Slide control knobs (state colour) 12p each. Rotary control knobs (push-on). Black with coloured cap (state colour) 20p each.

Untested Items

REJECT CALCULATORS. Production line rejects. Yields lots of goodies when stripped down (not much wrong with some we tested). Only £2-50 each. Cat. No. 104.

LED DISPLAYS. (Untested—no guarantees) 10 seven segment LED displays. 0-127" digits common cathode. 10 for £1-00. Cat. No. 311.

Postage and Packing please add 35p. (Overseas orders add 90p)

Satisfaction guaranteed or return for replacement or refund.

Send medium sized S.A.E. for your free copy of our new Autumn Catalogue (Issue No. 6).

Codespeed's Design, Development and Production teams are also at your service for quantity/batch production.

BUY an ELF II microcomputer for less than some TV games

KIT ONLY
£79-95
+ VAT.

ELF 11 BOARD WITH VIDEO OUTPUT FEATURING THE RCA 1802 COSMAC C.P.U.

ADD-ONS

- POWER SUPPLY (6.3V AC) for ELF 11 5.00
- ELF 11 DE LUXE STEEL CABINET (IBM Blue) 23.01
- GIANT BOARD KIT System/Monitor, Interface to/cassette—RS232, TTY etc 35.00
- 4K STATIC RAM board kits (requires expansion power supply) 69.44
- Expansion power supply (required when adding 4K Rams) 19.00
- ASC11 Keyboard Kits 96 printable characters etc 50.58
- ASC11 d/lux steel cab. (IBM Blue) 15.02
- KLUGE prototype board (build your own circuits) 12.83
- 86 pin Gold plated connectors (each) 4.00
- ELF Light pen writes/draws on TV screens 6.50
- Video graphics board 32/64 characters by 16 lines on TV/monitor screens 69.95
- ELF 11 Tiny basic on cassette 13.50
- ELF 11 Bug/monitor powerful systems monitor/editor 13.50
- T. PITMANS short course in programming manual (Nil VAT) 4.00
- T. PITMAN short course on tiny basic manual (Nil VAT) 4.00
- RCA 1802 users manual (Nil VAT) 4.00

† On cassette Text Editor: Assembler: Dissassembler (each) 16.95

SAVE 10% AND BUY ALL THREE TOGETHER

All units can be supplied wired and tested

Send S.A.E. for comprehensive brochure

NEW: GAMES ON TAPE send for list

Send s.a.e. for brochure and orders to:

P & P £2.00

DEALER ENQUIRIES WELCOME

Newtronics 138 Kingsland Road

London E2 8BY

Tel: 01-739 1582

DEPT. P.E.

SOLE U.K. AGENTS

CHROMASONIC electronics

your soundest connection in the world of components

The items shown in this advert are just a small selection taken from our 1979 Catalogue containing everything from Resistors to the latest in Microprocessors. Order your copy today FREE with all orders upon request or SAE

Dept PE 1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TEL: 01 883 3705 01 883 2289

TTL74	74LS	74LS290	1.05
7400 .11	74LS00 .17	74LS293 1.05	
7401 .11	74LS01 .17	74LS295 1.50	
7402 .11	74LS02 .17	74LS298 1.33	
7403 .13	74LS03 .17	74LS348 1.00	
7404 .14	74LS04 .18	74LS352 1.20	
7405 .16	74LS05 .22	74LS353 1.05	
7406 .24	74LS06 .21	74LS385 .54	
7407 .24	74LS07 .21	74LS366 .54	
7408 .14	74LS10 .21	74LS387 .54	
7409 .15	74LS11 .21	74LS368 .54	
7410 .13	74LS12 .21	74LS386 .61	
7411 .20	74LS13 .43	74LS393 .87	
7412 .15	74LS14 .75	74LS668 1.35	
7413 .22	74LS15 .21	74LS670 1.97	
7414 .48	74LS20 .21		
7416 .22	74LS21 .21		
7417 .20	74LS22 .21		
7420 .12	74LS26 .21		
7423 .21	74LS27 .21		
7425 .21	74LS28 .22		
7426 .21	74LS30 .21		
7427 .29	74LS32 .30		
7428 .33	74LS33 .30		
7430 .12	74LS37 .26		
7432 .21	74LS38 .26		
7437 .22	74LS40 .21		
7438 .22	74LS42 .75		
7440 .18	74LS47 .40		
7441 .53	74LS48 .93		
7442 .40	74LS49 .93		
7445 .84	74LS51 .21		
7446 .84	74LS52 .78		
7447A .48	74LS55 .21		
7448 .56	74LS73 .38		
7450 .12	74LS74 .31		
7451 .12	74LS75 .48		
7453 .12	74LS76 .31		
7454 .14	74LS78 .31		
7460 .12	74LS83 .30		
7470 .22	74LS85 .30		
7472 .20	74LS86 .31		
7473 .27	74LS90 .86		
7474 .23	74LS91 .112		
7475 .19	74LS92 .89		
7476 .20	74LS93 .89		
7482 .80	74LS95 .93		
7485 .104	74LS96 1.33		
7486 .10	74LS107 .37		
7489 .150	74LS109 .37		
7490 .28	74LS112 .37		
7491 .82	74LS113 .37		
7492 .33	74LS114 .37		
7493 .20	74LS122 .79		
7495 .40	74LS123 .83		
7496 .48	74LS124 1.60		
74107 .28	74LS125 .41		
74109 .36	74LS126 .41		
74121 .23	74LS132 .69		
74122 .33	74LS133 .46		
74123 .52	74LS136 .41		
74125 .45	74LS138 .67		
74126 .48	74LS139 .67		
74132 .82	74LS145 1.12		
74141 .48	74LS151 .83		
74145 .48	74LS153 .80		
74147 .136	74LS154 1.50		
74148 .99	74LS155 .83		
74150 .88	74LS156 .83		
74151 .48	74LS157 .85		
74153 .43	74LS158 .65		
74154 .88	74LS160 1.25		
74155 .46	74LS161 .80		
74156 .43	74LS162 1.33		
74157 .40	74LS163 .80		
74160 .57	74LS164 1.22		
74161 .58	74LS165 .83		
74162 .57	74LS166 1.80		
74163 .48	74LS168 1.87		
74164 .80	74LS169 1.87		
74165 .58	74LS170 1.98		
74166 .98	74LS173 .93		
74170 .150	74LS174 1.12		
74173 .121	74LS175 1.12		
74174 .58	74LS181 3.19		
74176 .58	74LS188 .51		
74177 .73	74LS189 2.39		
74178 .73	74LS190 .99		
74180 .43	74LS191 .99		
74181 .44	74LS192 1.20		
74182 .67	74LS193 1.20		
74184 .114	74LS194 .99		
74185 .121	74LS195 1.12		
74188 .316	74LS196 1.12		
74189 .250	74LS197 1.12		
74190 .52	74LS221 1.08		
74191 .48	74LS240 2.39		
74192 .50	74LS241 2.39		
74193 .51	74LS242 2.39		
74194 .44	74LS243 2.39		
74195 .70	74LS245 .80		
74196 .79	74LS247 1.25		
74197 .75	74LS248 1.25		
74198 .99	74LS249 1.25		
74199 .130	74LS251 1.10		
74221 .105	74LS253 1.00		
74247 .136	74LS257 1.00		
74251 .81	74LS258 1.00		
74273 .127	74LS259 1.00		
74283 .113	74LS261 1.30		
74285 .87	74LS266 .80		
74366 .57	74LS273 1.95		
74367 .57	74LS279 .65		
74368 .57	74LS283 1.25		
74390 .88	74LS289 .80		

LINEAR	AY-5-1224	2.85
CA3046 .77	LM381AN .77	1.77
CA3053 .71	LM382N .77	2.81
CA3075 .41	LM388N .77	1.36
CA3080 .42	LM387N .77	1.12
CA3081 .69	LM389N .40	1.06
CA3082 .35	LM725CN .40	2.96
741 8 pin .23	LM1303N .46	1.18
741 14 pin .42	LM1808N .96	2.22
741 1099 .46	LM1812N .46	6.48
747 14 pin .78	LM1820N .38	1.17
748 8 pin .38	LM3065N .120	1.23
748 14 pin .40	LM3900N .95	1.50
748 1099 .55	LM3905N .375	1.22
753 8 pin 1.99	LM3909N .75	2.15
AY-1-0212 .67	LM3911N .128	1.28
AY-1-5051 .187	LM3912N .85	0.87
AY-1-8721-6 2.24	M252-81-AA .28	9.20
	M253-81-AA .40	1.01
	MC1310P .51	1.28
	MC1312P .225	2.25
	MC1314P .347	3.47
	MC1315P .495	4.95
	MC1327P .115	1.15
	MC1330P .235	2.35
	MC1350P .123	1.23
	MC1351P .132	1.32
	MC1352P .60	6.00
	MC1456CP .232	2.32
	MC1458CP1 .56	5.60
	MC1495L .531	5.31
	MC1496P .350	3.50
	MC3302P .71	7.10
	MFC6000A .226	2.26
	NE555N .30	3.00
	NE568N .446	4.46
	NE569N .350	3.50
	NE561N .350	3.50
	NE562N .350	3.50
	NE565N .129	1.29
	NE566N .139	1.39
	NE567N .181	1.81
	SL414A .194	1.94
	SA1102A .395	3.95
	SA1102S .582	5.82
	SD8000V .346	3.46
	SN76001N .95	9.50
	SN76003N .232	2.32
	SN76008N .125	1.25
	SN76013N .155	1.55
	SN76013MD .136	1.36
	SN76018K .125	1.25
	SN76023ND .140	1.40
	SN76033N .232	2.32
	SN76532N .173	1.73
	SN76544N .920	9.20
	SN76680N .65	6.50
	SN76686N .78	7.80
	TA320A .80	8.00
	TA350A .270	2.70
	TA6120B .79	7.90
	TA6231 .288	2.88
	TBA5200 .98	9.80
	TBA51 .205	2.05
	TBA600 .92	9.20
	TBA810AS .85	8.50
	TBA820 .82	8.20
	TBA890Q .275	2.75
	TCA730 .425	4.25
	TC740 .71	7.10
	TC840 .226	2.26
	TDA1054 .80	8.00
	TDA2020 .350	3.50
	UAA170 .229	2.29
	UAA180 .228	2.28
	UAA190 .75	7.50
	UAA204 .115	1.15
	UAA237 .138	1.38
	UAA245E .410	4.10
	UAA252E .382	3.82
	UAA59CT .216	2.16
	ZN10346 .888	8.88
	ZN1040E .719	7.19
	ZN134 .3621	3.621

CMOS	DYNAMIC RAMS	STATIC RAMS	ROMS	VOLTAGE REGULATORS	CRYSTALS
4000 .15	4027 3.46	2102A(350ns) 1.33	2513(10C) 7.18	1 Amp +ve T0220	100kHz .395
4001 .17	4116(250ns) 7.75	4050(200ns) 2.87	2513(L) 7.18	-ve T0220	1.0MHz 3.45
4002 .15	4060 7.8	4050(300ns) 2.75	MM5230 5.31	5v 7808 .89	2.0MHz 3.45
4006 .78	4067 1.5	211A-(1500ns) 1.33	2102A 5.93	12v 7812 .89	2.097152MHz 3.45
4007 .15	4068 .62	211A-(21250ns) 1.33	1702A 7.20	15v 7815 .89	3-27880MHz 3.45
4008 .62	4009 .35	211A-(21250ns) 2.11	2708 29.59	18v 7818 .89	4-194304MHz 3.45
4009 .35	4010 .30	21L02(350ns) 1.33	2102A 5.93	24v 7824 .89	4-433615MHz 1.27
4010 .30	4011 .20	21L02(350ns) 1.33	MM5257 7.97		5-0MHz 3.45
4011 .20	4012 .15	MM5214 6.00	MM5214 6.00		10-0MHz 3.45
4012 .15	4013 .40	MM5217 6.00	MM5217 6.00		10-7MHz 3.45
4013 .40	4014 .67	MM5218 6.00	MM5218 6.00		
4014 .67	4015 .71	MM5219 6.00	MM5219 6.00		
4015 .71	4016 .32	MM5220 6.00	MM5220 6.00		
4016 .32	4017 .78	MM5221 6.00	MM5221 6.00		
4017 .78	4018 .67	MM5222 6.00	MM5222 6.00		
4018 .67	4019 .55	MM5223 6.00	MM5223 6.00		
4019 .55	4020 .72	MM5224 6.00	MM5224 6.00		
4020 .72	4021 .67	MM5225 6.00	MM5225 6.00		
4021 .67	4022 .71	MM5226 6.00	MM5226 6.00		
4022 .71	4023 .16	MM5227 6.00	MM5227 6.00		
4023 .16	4024 .58	MM5228 6.00	MM5228 6.00		
4024 .58	4025 .16	MM5229 6.00	MM5229 6.00		
4025 .16	4026 1.50	MM5230 6.00	MM5230 6.00		
4026 1.50	4027 .35	MM5231 6.00	MM5231 6.00		
4027 .35	4028 .60	MM5232 6.00	MM5232 6.00		
4028 .60	4029 .60	MM5233 6.00	MM5233 6.00		
4029 .60	4030 .60	MM5234 6.00	MM5234 6.00		
4030 .60	4031 .95	MM5235 6.00	MM5235 6.00		
4031 .95	4032 .95	MM5236 6.00	MM5236 6.00		
4032 .95	4033 1.30	MM5237 6.00	MM5237 6.00		
4033 1.30	4034 .31	MM5238 6.00	MM5238 6.00		
4034 .31	4035 .91	MM5239 6.00	MM5239 6.00		
4035 .91	4036 .69	MM5240 6.00	MM5240 6.00		
4036 .69	4037 .37	MM5241 6.00	MM5241 6.00		
4037 .37	4038 .60	MM5242 6.00	MM5242 6.00		
4038 .60	4039 .60	MM5243 6.00	MM5243 6.00		
4039 .60	4040 .75	MM5244 6.00	MM5244 6.00		
4040 .75	4041 .60	MM5245 6.00	MM5245 6.00		

kontite remote control switch


—Simple to install
even simpler to use.



The Receiver:
contains input and
output cables which
are connected to the
appliance to be
controlled.

The Transmitter:

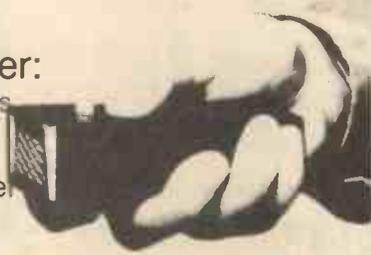is light and cordless
and housing the
battery. Simply,
point the transmitter
at the receiver to
turn on or off



Now available in the U.K. the 'Kontite' Remote Control unit switches electrical appliances and equipment on or off safely from distances of up to 35 feet.

Televisions, radios, hi-fi equipment, lighting, model trains etc. electric fans, electric fires (up to 2kw) and many other appliances are within its scope, providing that they have a power supply of 240/250 AC single phase. 50/60 Hz and a maximum 10 amp rating and also that the relevant safety regulations are applied.

The unit is ideal for use in the home, office, factory and hospital. Particularly useful as an aid to the disabled and invalid—wherever an electrical appliance is difficult to reach in the normal manner.

The Kontite Remote Control Switch
available now through
Electrical Component
Retailers.



If you have difficulty in locating a stockist please contact:

Kay & Co (Engineers) Ltd.

Acrsfield House, 15 Exchange Street, Bolton, Lancashire.
Telephone: Bolton 21041 Telex: 63186

ZENER DIODES (400 mW) 2.7V to 33V 8p	OPTO/DISPLAY ORP12 70p DL704 110p DL707 110p 1.25" & "2" LEDs: 2.5" x 5" 52p 2.5" x 5" 62p 3.75" x 5" 62p Red 10p Green 14p Yellow 14p	NE555 25p NE556 60p NE566 140p 74125/6 34p 74132 48p 74141 45p 74142 200p 74145 55p 74151 48p 74153 52p 7400/1 11p 7402/3 11p 7404/5 13p 7406 15p 7407 20p 7408/9 13p 7410 17p 7411 17p 7412 15p 7413 27p 7414 48p 7416/7 25p 7420 13p 7421 21p 7422 16p 7427 25p 7428 28p 7432 18p 7433 30p 7437/8 15p 7440 10p 7441 55p 7442 43p 7443 35p 7444 78p 7445 60p 7446 65p 7447 53p 7448 62p 7450 10p 7451/3 12p 7454 10p 7460 12p 7470 17p 7472 21p 7473/4 24p 7475 30p 7476 26p 7480 25p 7486 22p 7490 32p 7491 28p 7492 17p 7493 32p 7494 30p 7495 30p 7496 43p 74100 60p 74105 43p 74107 20p 74109 25p 74110 40p 74121 26p	22p 40p 34p 48p 45p 200p 55p 48p 52p 89p 54p 30p 62p 20p 50p 66p 85p 15p 27p 48p 70p 60p 53p 14p 12p 84p 32p 15p 32p 85p 63p 37p 57p 18p 68p 45p 92p 80p 85p 18p 47p 18p 47p 18p 54p 63p 48p 107p	4041 78p 4042 58p 4043 88p 4044/7 90p 4048 55p 4049 30p 4050 30p 4056 38p 4069 15p 4070 15p 4072/3 15p 4081/2 16p 4086 66p 4510 73p 4511 99p 4516 95p 4518 72p 4520 69p 4528 99p BR139 35p BU208 20p NJ2955 110p MJ3340 40p MJ2355 104p MJ3055 85p AC126 20p AC128 20p AC176 20p AC187 21p AC188 21p AD149 80p AD161 40p AD162 40p AF115 21p AF117 24p AF124 34p BC107/9 10p BC147 8p BC148 10p BC157 10p BC158 10p BC167 13p BC169C 13p BC178 16p BC179 18p BC182 10p BC183 24p BC184 32p BC209 11p BC212 11p BC214 14p BC241 34p BC477 23p BC478 23p BC479 23p BC547 12p BC549 13p BC557 13p BC558 13p BC559 15p BC70 16p BC71 19p BC772 18p BO131 38p	80132 38p 80135 to 35p 80140 24p 80180 24p 80194 10p 80195 10p 80196 10p 80197 10p 80244 18p 80248 18p 80252 18p 80253 18p 80254 18p 80349 18p 80350 18p	ZTX501 16p ZTX502 21p ZTX503 17p ZTX504 28p ZTX505 33p ZTX506 13p ZTX507 30p ZTX508 30p ZTX509 30p ZTX599 30p ZTX600 30p
--	---	--	--	---	--	--

SAE for complete list.
Add 25p for p & p.
PRICES VAT INCLUSIVE

DELTA TECH
UNIT 4
62 NAYLOR ROAD
LONDON N20 0HN

BOOKS·BOOKS·BOOKS

How to Build a Working Digital Computer	£4.60
How to Build a Computer Controlled Robot	£5.95
Illustrating Basic, Donald Alcock	£2.25
Basic Basic, J. Coan	£6.50
Advanced Basic, J. Coan	£6.00
Intro. to Micros, Vol.0, Osborne	£6.30
Intro. to Micros, Vol.1, Osborne	£6.30
Microprocessors, Chips to Systems, Zaks	£7.95
Microprocessors, Interfacing Tech., Zaks	£8.75
TTL Cookbook, Lancaster	£7.50
CMOS Cookbook, Lancaster	£7.95
TV Typewriter Cookbook, Lancaster	£7.50
Cheap Video Cookbook, Lancaster	£5.10
6800 Assembly Language Programming, Osborne	£6.30
8080A/8085 Ass. Language Prog., Osborne	£6.30
6502 Applications Book, Zaks	£8.95
Z80 Assembly Language Programming, Osborne	£6.95
Microprocessor Data Manual, Bursky	£5.50
Programming the 6502, Zaks	£7.95
How to Program Micros, W. Barden Jr.	£6.95

Phone in your Access/
Barclaycard No
0742 585490
or complete this
order form

Send s.a.e. for full list. Prices correct at
going to press. Add 12p insurance on
books if required.

Cromemco (ITT 2020 appls) **PET**
TEXAS INSTRUMENTS **na/com-1**

Please supply


I enclose: - £
Cheque/Postal Order No.
Barclaycard/Access No.
Name:
Address:

Datron Micro Centre, Latham House, 243 London Road,
Sheffield S2 4NF. Tel: 0742-585490

AITKEN BROS

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729

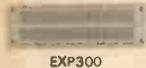

EXP300



P86 Kit

EXP300

550 contacts with two 50-point BUS bars. Size 152x53mm. £6-95.

PROTO-BOARD 6 KIT

630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10-98.

CSC LOGIC PROBES

LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds. 300 KΩ input impedance, tests circuits up to 1-5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. £20-95.

LP-1 Memory Probe

£36-65

LP-3 High Speed Memory Probe

£56-75

CSC catalogue available. Please send S.A.E.

CALSCOPE SUPER 6 £186-30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1µs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

TE20D TECH R.F. SIGNAL GENERATOR

Accurately covers 120 KCS to 500 MCS in 8 bands. Directly calibrated. Variable RF attenuator 240 VAC. Size 140x215x170mm.

Price £52-50 (£50-58 to callers).

TE22D TECH AUDIO GENERATOR

Sine & square wave audio generator. Sine wave range -20 cps to 20K cps in four bands.

Square wave range 20 cps to 15K cps in four bands 240V A.C. Size 140x215x170mm.

Price £63-31 (£61-31 to callers).

TMK 500 MULTIMETER 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50µa, 5mA, 50mA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to +56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included.

PRICE £25-95.

CSC EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.

SINCLAIR DM350

£79-95

SINCLAIR DM450

£114-95

Size 255 x 148 x 40mm.

DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10µV to 1200V (100µV on DM350) A.C. voltage 100µV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

Sinclair PMM200 frequency meter

Size 157 x 76 x 32mm.

Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. £57-95.

SINCLAIR PDM35

DIGITAL POKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200mA. Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £34-95. AC Adaptor £3-95 de luxe padded carrying case £3-50 MN 1604 Battery £1-28.

Size 157 x 76 x 32mm.

SINCLAIR DM235

BENCH-PORTABLE DIGITAL MULTIMETER.

DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1µa to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω.

PRICE £57-95. Carrying case £9-95. AC adaptor/charger. £4-50. Rechargeable Battery Pack. £9-70

Size 255 x 148 x 40mm.

PANEL METERS

DIMS 60MM x 45MM. 50µ amp, 100µ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, "S" "VU" 50-0-50µa, 100-0-100µa, 500-0-500µa. PRICE £5-95.



DESOLDERING TOOL

£6-45

SUCTION PUMP.

Education Establishment Orders Accepted.

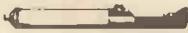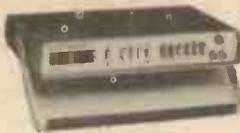PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10. ALL PRICES INCLUDE POSTAGE AND VAT.



J. BIRKETT

(Partners: J. H. Birkett, J. L. Birkett)

Radio Component Suppliers

25 The Strait, Lincoln. LN2 1JF

- 10 WATT STUD MOUNTING ZENERS 18v, 22v, 33v, 68v, 100 volt. All at 35p each.
- 10 AMP 2 POLE MAKE TOGGLE SWITCHES • 50p.
- CMOS CD 4518 • 75p each. 4 for £1.60.
- MINIATURE NON POLARISED CAPACITORS 1uf 63v.w. • 5p, 4.7uf 63v.w. • 10p, 10uf 63v.w. • 15p.
- ELECTROLYTIC CAPACITORS 5000+5000uf 25v.w. • 75p.
- MINIATURE BRIDGES 100 PIV 1 AMP • 20p, 200 PIV 4 AMP • 60p, 50 PIV 20 AMP • £1.30.
- 2N 657 100 VOLT 800mA NPN TO 5 TRANSISTORS • 25p each.
- THYRISTORS 10 AMP Type 100 PIV • 28p, 400 PIV • 55p, 800 PIV • 65p.
- UNIUNCTION TRANSISTORS 2N 4871 • 22p, 2N 802B • 25p, 2N 6029 • 25p, MEU 21 • 22p, MU 4894 • 22p, GE4JDE29 • 22p, TIS 43 Type • 22p.
- 12 WAY PLASTIC BARRIER STRIPS 5 Amp • 30p, 4 for £1.
- PRECISION METAL FILM RESISTORS 0.5% 68R, 100R, 121R, 150R, 240R, 274R, 332R, 360R, 365R, 562R, 619R, 750R, 820R, 909R, 910R, 1K, 2.15K, 2.2K, 2.21K, 3.01K, 3.9K, 5.1K, 6.2K, 10K, 18K, 75K, 150K, 200K, 392K, 597K, 600K, 1.21M. All at 6p each.
50. BC 107-8-9 TRANSISTORS Assorted Untested • 60p.
50. PLASTIC PNP TRANSISTORS Assorted Untested • 60p.
50. PLASTIC BC 107-8-9 TRANSISTORS Assorted Untested • 60p.
50. OC 71 TRANSISTORS Untested for 75p.
50. STUD MOUNTING 10 AMP DIODES Untested • 60p.
10. STUD MOUNTING 20 AMP DIODES Untested • 60p.
50. 2 WATT ZENERS Untested Assorted • 60p.
50. 1 AMP T05 S.C.R.'s Untested for £1.
25. 5 AMP STUD MOUNTING S.C.R.'s Untested • 75p.
10. ASSORTED PUSH BUTTON BANKS less Knobs for £1.30.
10. ASSORTED SLIDER POTENTIOMETERS for £1.
- ELECTROLYTIC CAPACITORS Screw Terminals. 880uf 160v.w. • 20p, 2400uf 150v.w. • £1, 2800uf 100v.w. • £1, 4700uf 40v.w. • 80p, 4700uf 63v.w. • £1, Tag Ended. 2350+2350uf 63v.w. • 75p, 3000uf 25v.w. • 40p, 5000uf 30v.w. • 50p, 6400uf 25v.w. • 50p.
- SPECIAL PAPER CAPACITOR 10uf 370 VAC • £1.50 each, 135uf 290 VACW • £6 each.
- 50 PIV 1½ AMP WIRE ENDED DIODES • 7p, 6 for 25p.
- P2102 1024 BIT FULLY DECODED STATIC RAM • £1.
- 10 ASSORTED MULTI-TURN TRIM POTENTIOMETERS • 65p.
- 12 WAY CERAMIC TAG STRIPS • 15p each.
- MINIATURE R.F. CHOKES 3 U.H., 5 U.H., 22 U.H., 27 U.H. All at 7p each.
- 400 mW ZENERS unmarked good. 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36 volt. All at 10 for 40p.
- MAINS TRANSFORMERS 240 volt Input. Type 1. 24 volt Tapped at 14 volt 1 amp • £1.30 (P&P 25p), Type 2. 30-0-30 volt 500mA • £1.30 (P&P 25p), Type 3. 45 volt 6 amp • £4.50 (P&P 95p), Type 4. 20 volt 1 amp Twice, 10 volt 1 amp Twice • £4.50 (P&P 95p).
- MULLARD .1uf 160v.w. POLYESTER CAPACITORS • 22p doz.
- OP-AMPS MC 1439G at 40p each. 3for £1.

Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas postage charged at cost.

ELECTROVALUE

LEADING DIRECT SUPPLIERS FOR



NASCOM MICROCOMPUTERS
AND FULL SUPPORTING RANGE
OF ITEMS TO ENABLE YOU TO
WORK AT PROPER
PROFESSIONAL LEVELS

- ★ Appointed Nascom stockists
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

We are also appointed distributors
for the fine products of:

SIEMENS, ISKRA, RADIOHM,
VERO AND MANY OTHER
FAMOUS MANUFACTURERS

It's a good deal better from

ELECTROVALUE LTD

Dept. PE12, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.
Phone: Egham 33603. (London, dial 87 first. STD 0784). Telex: 264475.
Northern Branch (Personal shoppers only), 680 Burnage Lane,
Burnage, Manchester M19 1NA. Phone (061) 432 44945.

Be among the very first to receive your

FREE CATALOGUE 10 (Ready shortly)

by sending your name and address NOW. (124 pages - packed with items, illustrations etc).

- We pay postage
- in U.K. on orders list value £5 or over. If under, add 27p handling charge.
- We give discounts
- on C.W.O. orders, except for a few items marked Net or N in our catalogue price list.
- on orders, list value 5% £10 or more
- on orders list value 10% £25 or more.
- Not applicable to Access or Barclaycard orders.
- We stabilise prices.
- by keeping to our printed price lists which appear but three or four times a year.
- We guarantee
- all products brand new, clean and to maker's spec. No seconds, no surplus.

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

. . . our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.Cs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including I.Cs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.




Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

Electronics Make a job~or hobby~of it.....

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market.

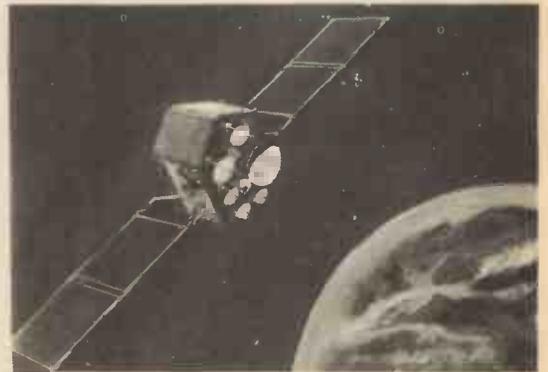We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .



Free!

Brochure without obligation to.

PEB/12

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

Block caps please

RT

VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS
MAIL ORDER SERVICE**

Ep	Ep	Ep	Ep	Ep	Ep
AA119	0-12	BCY70	0-17	MPSU01	0-41
AA130	0-31	BCY71	0-20	MPSU06	0-53
AA132	0-48	BCY72	0-15	MPSU56	0-56
AA213	0-21	BCZ11	1-72	NE555	0-52
AA215	0-39	BD115	0-52	NKT401	2-30
AAZ17	0-31	BD121	1-38	NKT403	1-99
AC107	0-69	BD123	1-38	NKT404	1-99
AC125	0-23	BD124	1-50	OA5	1-09
AC126	0-23	BD131	0-40	OA7	0-63
AC127	0-23	BD132	0-44	DA10	0-74
AC128	0-23	BD135	0-39	DA47	0-16
AC141	0-29	BD136	0-39	OA70	0-35
AC141K	0-40	BD137	0-40	OA78	0-35
AC142	0-23	BD138	0-46	OA81	0-36
AC142K	0-35	BD139	0-49	OA85	0-35
AC176	0-23	BD140	0-51	OA90	0-09
AC187	0-23	BD144	2-30	OA91	0-09
AC188	0-23	BD181	1-26	OA95	0-09
AC178	0-98	BD182	1-36	OAZ00	0-10
AC191	0-92	BD237	0-26	OAZ02	0-10
AC196	0-86	BD238	0-83	OAZ11	1-15
AC200	0-80	BDX10	1-05	OAZ200	1-15
AC21	0-86	BDX32	2-30	OAZ201	1-15
AC239	1-72	BDY20	1-44	OAZ206	1-15
AD149	0-80	BDY60	1-72	OAZ207	1-15
AD161	0-52	BF115	0-29	OC16	2-30
AD162	0-52	BF173	0-23	OC20	2-88
AF106	0-52	BF153	0-23	OC22	2-88
AF114	0-86	BF154	0-20	OC23	3-16
AF115	0-86	BF159	0-26	OC24	3-45
AF116	0-86	BF160	0-18	OC25	1-04
AF117	0-86	BF187	0-23	OC28	1-10
AF139	0-46	BF173	0-23	OC29	2-30
AF186	1-38	BF177	0-28	OC29	2-30
AF239	0-52	BF178	0-28	OC35	1-73
AFZ11	3-16	BF179	0-29	OC36	1-73
AFZ12	3-16	BF180	0-36	OC41	0-92
AS26	0-46	BF181	0-35	OC42	0-86
AS27	0-46	BF182	0-35	OC43	2-59
ASZ15	1-44	BF183	0-29	OC44	0-69
ASZ16	1-44	BF184	0-29	OC45	0-63
ASZ17	1-44	BF185	0-29	OC71	0-63
ASZ20	1-72	BF194	0-10	OC72	0-63
ASZ21	2-30	BF195	0-10	OC73	1-15
AU110	2-30	BF196	0-12	OC74	0-74
AU113	1-96	BF197	0-14	OC75	0-74
AU110	2-30	BF200	0-31	OC76	0-63
BA145	0-15	BF224	0-23	OC77	1-38
BA148	0-15	BF244	0-32	OC81	0-74
BA154	0-10	BF257	0-28	OC81Z	1-38
BA156	0-12	BF258	0-30	OC82	0-74
BA156	0-10	BF259	0-37	OC83	0-74
BAW62	0-06	BF326	0-35	OC84	0-74
BAW62	0-07	BF337	0-35	OC122	1-73
BAW62	0-10	BF338	0-36	OC123	2-02
BC107	0-14	BF321	4-56	OC139	2-59
BC108	0-14	BF328	2-56	OC140	3-16
BC109	0-15	BF351	0-24	OC141	3-74
BC113	0-14	BF358	0-23	OC170	1-15
BC114	0-16	BFW10	0-74	OC171	1-15
BC115	0-16	BFW11	0-74	OC200	1-73
BC116	0-17	BFX84	0-25	OC201	2-02
BC117	0-20	BFX85	0-28	OC202	2-02
BC118	0-12	BFX87	0-24	OC203	2-02
BC125	0-14	BFY50	0-24	OC204	2-88
BC125	0-23	BFY50	0-30	OC205	2-88
BC135	0-16	BFY51	0-30	OC206	2-88
BC136	0-17	BFY52	0-30	OC207	2-02
BC137	0-17	BFY64	0-30	OC271	1-44
BC147	0-10	BSX18	1-44	R20088	2-02
BC148	0-10	BSX19	0-24	R20088	2-02
BC149	0-10	BSX20	0-23	R2009	2-59
BC157	0-10	BSX21	0-23	R2010B	2-02
BC158	0-09	BT106	1-44	TC144	0-35
BC159	0-12	BTY79/4	3-67	TC226D	1-38
BC167	0-12	BU208	2-02	TL209	0-23
BC170	0-13	BU208	2-02	TP129A	0-47
BC171	0-12	BU208	2-30	TP30A	0-48
BC172	0-12	BY100	0-52	TP131A	0-51
BC173	0-14	BY126	0-16	TP132A	0-55
BC177	0-17	BY127	0-19	TP133A	0-78
BC178	0-18	Series	0-21	TP134A	0-78
BC179	0-18	Series	0-21	TP141A	0-72
BC182	0-13	BZY88	0-15	TP142A	0-81
BC183	0-12	Series	0-15	TIP2955	0-77
BC184	0-13	CRS1/40	0-69	TIP3055	0-64
BC212	0-16	CRS3/40	0-86	TS143	0-52
BC213	0-17	CRS3/60	1-04	ZS170	0-24
BC214	0-10	GEX66	1-73	ZS178	0-62
BC237	0-10	GEX66	2-02	ZS271	0-26
BC238	0-14	GEX541	0-86	ZS278	0-65
BC301	0-38	GJ3M	0-86	ZTX107	0-12
BC303	0-38	GJ5M	0-86	ZTX108	0-12
BC307	0-12	GL7MA	2-02	ZTX109	0-14
BC308	0-12	IM0378A	0-52	ZTX300	0-14
BC327	0-23	KS100A	0-92	ZTX301	0-15
BC328	0-21	MJE340	1-35	ZTX302	0-17
BC337	0-20	MJE370	0-60	ZTX303	0-20
BC338	0-20	MJE371	0-60	ZTX304	0-22
BCY30	1-15	MJE520	0-63	ZTX311	0-14
BCY31	1-15	MJE521	1-44	ZTX314	0-23
BCY32	1-04	MJE2955	0-86	ZTX500	0-15
BCY33	1-04	MJE3055	0-35	ZTX501	0-16
BCY34	1-04	MPE102	0-35	ZTX502	0-18
BCY39	3-45	MPE103	0-35	ZTX503	0-20
BCY40	1-15	MPE104	0-35	ZTX504	0-23
BCY42	0-29	MPSA05	0-28	ZTX531	0-23
BCY43	0-29	MPSA06	0-28	ZTX550	0-18
BCY58	0-18	MPSA56	0-30		

TUNE IN!

Build the World Famous CHROMA-CHIME



Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

**ONLY
£9.95
+ 75p p&p
UK ONLY**

* Save pounds on normal retail price by building yourself.

TMS 1000N - MP0027A Micro-

computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.



New low price only **£4.95 inc. p&p**

R/C MODELLERS - LISTEN FOR THE C.B. MENACE GET A 27MHZ MONITOR

- * Audibly confirm your channel's clear.
- * Tunes over whole 27mhz model band. (CB)
- * Receives normal broadcast AM/FM bands as well.
- * Sensitive with telescopic aerial.
- * Totally portable.
- * Runs on standard batteries.

**ONLY
£17.95
INC. V.A.T.
AND P. & P.**



This neat three band Superhet receiver not only provides an invaluable service, checking your channel and TX, but gives normal broadcast reception when you need it as well.

Costing less than a decent Servo, you'll find it cheap and reassuring insurance!

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE

PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____

or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7
Quotations for any types not listed S.A.E.

Post and Packing 30p per order
All prices include VAT Telex 946708

Prices correct
when going
to press

U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE

BAKER "BIG-SOUND" SPEAKERS Post £1.60 each

'Group 100-12' 'Group 45-12' 'Group 100-15'

12 inch 100 watt £29 12 inch 45 watt £15 15 inch 100 watt £35
8 or 16 ohm 4 or 8 or 16 ohm 8 or 16 ohm

BAKER LOUDSPEAKER, 12 INCH, 60 WATT.
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.
FULL RANGE PROFESSIONAL QUALITY.
RESPONSE 30 16 000 CPS
MASSIVE CERAMIC MAGNET
WITH ALUMINIUM PRESENCE CENTRE DOME. **£23**

4 CHANNEL TRANSISTOR MONOMIXER
Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£7.50**

Two channel stereo version **£9.**

HEATING ELEMENTS WAFER THIN
Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. All must be clamped between two sheets of metal or similar. ALL POST PAID - Discounts for quantity. **ONLY 40p EACH (FOUR FOR £1.50)**

MINI MODULE BAFFLE KIT Post £1.
EMI 15 x 8 1/2 in. 3-way Loudspeaker System 5in. Bass 5in. Middle 3in Tweeter with 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response=60 to 20 000 C.P.S. 12 watt RMS. B ohms. £10.95 per kit. Two kits £20. Suitable Bookshelf Cabinet **£9.50** each. Post **£1.60**.



SINGLE RECORD PLAYER
Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable Size 7in. diameter a.c. mains 240V 3 speeds plays all size records. **£7.95**

Two for £15. Post £1 one or two.

NEW BSR SINGLE PLAYER **£24.50**
Model P182 3-speeds flared aluminium turntable. "S" shaped arm, cueing device, stereo ceramic cartridge.
B.S.R. De-Luxe Autochanger with stereo cartridge, plays all size records. Post **£1.60**. **£20.00**

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER
Ideal for Groups, Disco, P.A. and Musical instruments. 4 inputs speech and music. 4-way mixing. Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£85** Post **£1.60**
100 volt line model **£14** extra.

BAKER COMPACT 50 WATT AMPLIFIER

IDEAL FOR DISCOS, GROUPS, PUBLIC ADDRESS
Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£65**. Post **£1.60**.

R.C.S. SOUND TO LIGHT DISPLAY MK II
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. **KIT = £18.00**

R.C.S. 10 WATT AMPLIFIER KIT
This kit is suitable for record players, tape play back, guitars, electronic instruments or small PA systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms 7W into 15ohms. Response 20c.s to 30K.c.s. Input 100mV. High imp. Size 9 1/2 x 3 x 2 in. A/C mains operated.
Mono kit **£12.50** Stereo kit **£20** Post **45p**
Easy to build. Full instructions supplied.

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 40V 80p; 25V 42p. 2500mF 50V 62p. 3000mF 25V 47p; 50V 85p. 2700mF 76V 11, 4700mF 63V £1.20. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p. 5600mF 76V £1.75. 1200mF 76V 80p.

HIGH VOLTAGE ELECTROLYTICS
8/350V 22p 8+8/450V 50p 50+50/300V 50p
16/350V 30p 8+16/450V 50p 32+32/450V 76p
32/500V 75p 16+16/450V 50p 100+100/275V 65p
50/500V £1.20 32+32/350V 50p 150+200/275V 70p
MANY OTHERS IN STOCK

TINTED PLASTIC COVERS ONLY
Sizes: 14 1/2 x 12 1/2 x 3in. £3.50. 16 x 14 x 3 1/2 in. £5. 15 1/2 x 13 1/2 x 4in. £4. 17 1/2 x 9 1/2 x 3 1/2 in. £3. 14 1/2 x 16 x 2 1/2 in. Rosewood sides £4. 18 x 13 1/2 x 3in. £6. 18 x 12 1/2 x 3in. £6. Ideal for record decks, tape decks, etc. Post **£1.60**

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS Post 45p **£2.95**
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200 240V a.c. Output voltages available 6 or 7, 5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/4 x 1 1/2 in. Please state voltage required.

ELECTRO MAGNETIC PENDULUM MECHANISM 95p Post 30p
1.5V d.c. operation over 300 hours continuous on SP2 battery fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome, scribe etc.

MAINS TRANSFORMERS ALL POST 75p each

250-0-250V 70mA 6 3 2A	£3.45
250-0-250 80mA 6 3V 3 5A 6 3V 1A	£4.80
300-0-300V 100mA 6 3V amp	£6.80
300-0-300 120mA 2 . 6 3V 2A C T . 6 3V 2A	£8.50
220V 45mA 6 3V 2A	£2.50
HEATER TRANS 6 3V 3A £2 1/2 amp	£2.20
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at	
2A 3 4 5 6 8 9 10 12 15 18 24 and 30V	£8.00
1A 6 8 10 12 16 18 20 24 30 36 40 48 60	£6.00
2A 6 8 10 12 16 18 20 24 30 36 40 48 60	£9.50
3A 6 8 10 12 16 18 20 24 30 36 40 48 60	£12.50
5A 6 8 10 12 16 18 20 24 30 36 40 48 60	£16.00
5 6 10 15V 1A £2.50 12V 100mA £1.30 12V 300mA £1.50.	
12V 750mA £1.75. 40V 2A tapped 10V or 30V £3.50.	
10-0-10V 2A £3. 40V 2A £3.50. 30V 5A + 34V 2A £4.	
2 x 18V 6A £11. 12-0-12V 2 amp £3.50. 25-0-25V 2 amp £4.80.	
20-0-20V 1A £3.50. 30V 1 1/2A £3.50. 20V 1A £3.	
9V 3 amp £3.50. 60V 40V 20V 1A £4.	
32-0-32V 6 1/2A £11. 5V 250mA £1.50. 30V 2 amp £3.50.	
AUTO TRANSFORMERS 115V to 230V or 230V to 115V	
150W £7; 250W £8; 400W £9; 500W £10.	
CHARGER TRANSFORMERS input 200/250V for 6 or 12V	
1 1/2A £4.25. 3 amp £4. 4A £7.25.	
FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs	
1 1/2A 85p; 4A £1.80. HALF WAVE 12V 1 1/2A 38p.	

BLANK ALUMINIUM CHASSIS, 18 a.w.g. 2 1/2 in. slides, 6 x 4 in. 95p; 6 x 6 in. £1.40; 10 x 7 in. £1.55; 14 x 9 in. £1.90; 16 x 6 in. £1.85; 12 x 3 in. £1.20; 16 x 10 in. £2.20, 12 x 8 in. £1.70. ALUMINIUM PANELS, 18 a.w.g. 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 3 in. 50p; 12 x 6 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1; 16 x 10 in. £1.16. ALUMINIUM ANGLE BRACKET, 6 x 1 1/2 in. 20p. ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK 4 x 2 x 2 in. 86p; 3 x 2 x 1 in. 66p; 6 x 4 x 2 in. 98p; 8 x 6 x 3 in. £1.80; 9 x 4 x 4 in. £1.70; 10 x 7 x 3 in. £2.20; 12 x 8 x 3 £2.90.

THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes, and all sizes of tape reels. a.c. mains 200 240V **£7.50**
Leaflet SAE. Post 75p.
Head demagnetiser **£5.00**

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K.

Minimum post 30p. Access and Barclaycard Same day despatch Radio Books and Components Lists 20p Open 9-8 Sat. 9-5 (Closed Wednesday all day). Tel. 01-684 1665

CLEF KITS

P.A.'s - SPEAKERS - CABINETS
Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

SUB-KITS
Reduce the cash outlay during the building process - details in lists.

KEYBOARDS
We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry soft plated contact springs.

49 NOTE C-C	£23.80
73 NOTE F-F	£37.00
88 NOTE A-C	£45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

NEW KITS
This space reserved for December release of Electronic Rotol! (See us at BREADBOARD '79.)

BUILDING SERVICE
We are specialists in Electronic Piano Manufacture and can build your Piano for you - see lists.

DEMONSTRATION CASSETTES
Please specify Ensemble or Piano at £1.50 each for ten minute content. Cost may be deducted from subsequent orders.

INFORMATION
Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & insurance.

VISITS
Are welcome by appointment, otherwise Mail Order Only.

EXPORT
Enquiries welcome - in Australia please contact JAYCAR (Sydney).

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS
Six and 7 1/2 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. Build this widely acclaimed professional Instrument, for either domestic or Stage use, from our top quality Component Kits.

SIX OCTAVES - £184
7 1/2 OCTAVES - £209

P.E. STRING ENSEMBLE
The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT - £164

Back up TELEPHONE advice is available from the Designer to supplement the clear instructions included with the above Kits.

CLEF PRODUCTS (ELECTRONICS) LIMITED
(Dept. PE) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU.
061-439 3297

AT BREADBOARD '79

ALCON PRESENT THE BIGGEST RANGE OF MULTIMETERS

and the new AMAZING MINI 20

a complete pocket multimeter at only £27.37 incl V.A.T.

PLUS MANY OTHER INCREDIBLE BARGAINS!! SEE YOU AT STAND C8


For details of this an other exciting Alcon instruments please write or phone:

ALCON Instruments Ltd.
19 MULBERRY WALK - LONDON SW3 6DZ - TEL: 01-352 1897 - TELE X: 918867

LIGHTING & AMPLIFIER MODULES FROM L&B

JUST LOOK AT THESE PRICES!

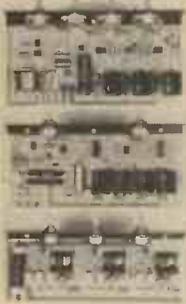SUPERIOR HIGH QUALITY LIGHTING CONTROL MODULES. ALL 1000 WATTS PER CHANNEL. NO POWER SUPPLIES NEEDED. ALL READY TO GO!



— LB31000SL —

3 channel Sound-Light. Zero switching, high sensitivity & input impedance. Excellent Separation. Excellent for disco's. **£18.90**

— LB41000LS —

4 channel sequencer. Suedo-random with two speed controls. Disco/band lighting effects. **£14.90**

— LB31000LD —

3 channel lamp dimmer. Control from full off to full on. Ideal for stage lighting. **£12.90**

NEW.

— LB11000LD —

Super tiny single channel lamp dimmer. For stage lighting. **£5.70**

— LB31000SLC —

All the advantages of the 31000SL, active filters & automatic chasing in the absence of a music input. **£28.90**

— LB81000LC —

8 channel chase. Chase rate & return speed controls. Optional foot switch trigger/trig o/p for module cascading. A breakthrough in modular technology. **£25.50**

— LB250 —

250W R.M.S. 4Ω
10Hz-20kHz
T.H.D. 0.3% 110dB
S/N

£29.50

— LB100 —

100W R.M.S. 4Ω
10Hz-25kHz
T.H.D. 0.4% 80dB S/N

£15.70

PREAMPLIFIERS

LBPA1 Stereo disc/tape **£14.50**

LBPA2. 4 channel gen. purpose mixer **£13.50**

LBPA3. Stereo disco with mic. **£27.00**



POWER SUPPLIES

LB25PS£10.00

LB100PS£12.20

LB250PS£21.20

— LB25 —

25W, RMS 4Ω
10Hz-50kHz
T.H.D. 0.1% 90dB S/N

£8.20

All prices include VAT. Add 50p p/packing. Quantity/trade and overseas inquiries welcome. For further information send a SAE to:

L&B

ELECTRONICS

45 WORTLEY ROAD, W. CROYDON
SURREY CR0 3EB. TEL: 01-689 4138

CALLING ALL RADIO ENTHUSIASTS

RADIO DATA SUPPLEMENT


A mine of reference information on building and using radio equipment for both amateur and broadcast bands enthusiasts.

New series RADIO CONTROL

More and more people are building radio-controlled model aircraft, boats and cars. You can obtain superb control with this easy-to-build proportional system featuring the latest developments in f.m. techniques.

SPECIAL XMAS OFFER

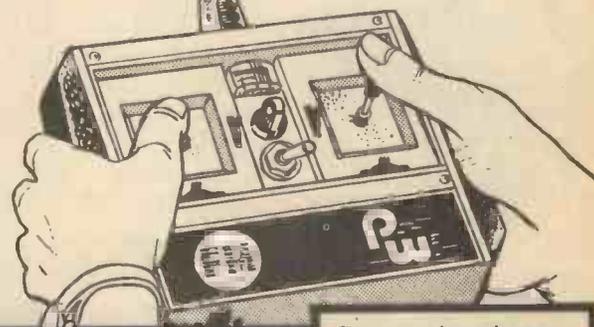Digital watch (liquid crystal display) with alarm, time and stopwatch capabilities.



December issue
55p

practical WIRELESS

Please phone for availability before ordering. All our prices include 15% VAT. Companies invited to send SAE for our up to date Wholesale price list.

WHOLESALE ELECTRIC COMPONENTS

	Stock	Price
AU113	183	.98
BC183A	2,000	.036
BC184L	7,000	.036
BC212A	4,000	.036
4v7 Zener	12,000	.02
3K Presets	20,000	.013
TBA800	6,000	.44
7448	1,600	.20
.01uF Disc	10,000	.01
16 Pin Dil	10,000	.08

We also buy large packages of Components.

STRUTT

ELECTRICAL AND MECHANICAL ENGINEERING LTD.
ELECTRONIC COMPONENT DISTRIBUTORS

3c, Barley Market St., Tavistock, Devon. PL19 05F
Tel: Tavistock (0822) 5439 Telex: 45263

FLADAR TRANSFORMERS

PRIMARY 0-240V 50Hz

IF YOUR REQUIREMENT IS NOT FEATURED BELOW
SEND FOR OUR TRANSFORMER CATALOGUE PRICE 40p

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
08FE06	6+6	0.5A EACH	1.82	60p	60FE24	24+24	1.2A EACH	4.58	102p
08FE06	6+6	0.6A EACH	2.19	60p	80FE24	24+24	1.5A EACH	5.66	120p
12FE06	6+8	1A EACH	2.43	72p	50FE28	28+28	0.75A EACH	3.74	84p
20FE06	6+6	1.6A EACH	3.06	84p	60FE28	28+28	1.1A EACH	4.58	102p
50FE06	6+6	3A EACH	3.74	84p	80FE28	28+28	1.4A EACH	5.66	120p
60FE06	6+6	4A EACH	4.58	102p					
06FE09	9+9	0.3A EACH	1.82	60p	20FE30	30+30	0.35A EACH	3.06	84p
08FE09	9+9	0.5A EACH	2.19	60p	50FE30	30+30	0.75A EACH	3.74	84p
12FE09	9+9	0.75A EACH	2.43	72p	60FE30	30+30	1A EACH	4.58	102p
20FE09	9+9	1A EACH	3.06	84p	80FE30	30+30	1.2A EACH	5.66	120p
50FE09	9+9	2.5A EACH	3.74	84p					
60FE09	9+9	3A EACH	4.58	102p					
06FE12	12+12	0.25A EACH	1.82	60p					
08FE12	12+12	0.3A EACH	2.19	60p					
12FE12	12+12	0.5A EACH	2.43	72p					
20FE12	12+12	0.8A EACH	3.06	84p					
50FE12	12+12	1.8A EACH	3.74	84p					
60FE12	12+12	2.5A EACH	4.58	102p					
80FE12	12+12	3A EACH	5.66	120p					
06FE15	15+15	0.2A EACH	1.82	60p					
08FE15	15+15	0.25A EACH	2.19	60p					
12FE15	15+15	0.4A EACH	2.43	72p					
20FE15	15+15	0.6A EACH	3.06	84p					
50FE15	15+15	1.5A EACH	3.74	84p					
60FE15	15+15	2A EACH	4.58	102p					
80FE15	15+15	3A EACH	5.66	120p					
06FE20	20+20	0.15A EACH	1.82	60p					
12FE20	20+20	0.25A EACH	2.43	72p					
20FE20	20+20	0.5A EACH	3.06	84p					
50FE20	20+20	1.2A EACH	3.74	84p					
60FE20	20+20	1.5A EACH	4.58	102p					
80FE20	20+20	2A EACH	5.66	120p					
CHANGER TRANSFORMERS									
48FE12	0-6-12	4A	4.58	102p					
66FE12	0-6-12	5A	5.30	102p					
70FE12	0-6-12	6A	5.66	120p					
90FE12	0-6-12	8A	6.75	138p					
12FE24	24+24	0.2A EACH	2.43	72p					

FLADAR ELECTRIC
P.O. BOX 19
WESTCLIFF-ON-SEA
ESSEX. 0702-613314

TRADE ENQUIRIES
WELCOME

PAYMENT TERMS:
C.W.O. Cheques,
Postal Orders
All Prices include 15% V.A.T.



Microcomputers are coming - ride the wave! Learn to program

Millions of jobs are threatened, but millions more will be created through the microcomputer revolution. Will YOU sink or swim? Be one of the people who welcomes computers and the end of boring jobs.

Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency - all you need to start with is a knowledge of simple arithmetic and the use of decimals. And you don't need a computer.

This unique course comes as four A4 books, written by three authors well-known in the fields of microcomputing, self-instruction and writing clear English. In 60 straightforward lessons you learn the five essentials: problem definition, flowcharting, coding the program, debugging, and preparing clear documentation.

Every lesson has thought-provoking questions and we never ask for mindless drudgery. You will know that you are mastering the material and feel a rare satisfaction. Harder problems are provided with a series of graded hints, a unique and really helpful approach. So you never sit glassy-eyed with your mind a blank. First time through, you may need to read most of the hints, but you will soon learn to tackle tough programming tasks - such as writing programs for computer games, preparing graphs on an output printer, calculating compound interest tables and estimating costs.

COMPUTER PROGRAMMING IN BASIC £7.50

Book 1 Computers and what they do well; READ, DATA, PRINT; powers, brackets, variable names; LET; errors; coding simple programs.
Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.
Book 3 Compilers and interpreters; loops, FOR...NEXT; RESTORE; debugging; arrays; bubble sorting; TAB.
Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

FORTRAN COLORING BOOK £5.40

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

A.N.S. COBOL £4.40

Covers the most widely used computer language in business today. It teaches how to write a COBOL program and compile it effectively, paying proper attention to spelling, punctuation, and format.

THE ALGORITHM WRITER'S GUIDE £3.40


FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions. *The Algorithm Writer's Guide* explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

Random Electronic

EASY DICE

Build your own 'EASY DICE' from the 5 intergrated circuits and full components supplied, including box and descriptive instructions.

Complete or Kit

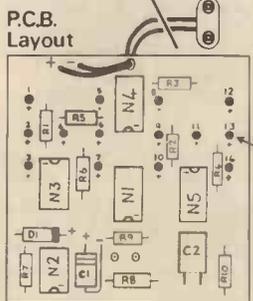

All you need is a soldering iron
TWO OICE FACES TOUCH CONTROL...

- a *Self Assemble Dice £3.95
- b *Ready built Dice £4.75 (INCL. P+P)

Order now from: **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk 0473-210151

Amount enclosed £ _____
Name _____
Address _____

please state amount required in appropriate box a b

Cambridge Learning Enterprises

Understand Digital Electronics

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £6.50

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

- Book 1 Binary, octal and decimal number systems; conversion between number systems.
- Book 2 AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables.
- Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates.
- Book 4 R-S and J-K flip flops; binary counters, shift registers and half adders.

DESIGN OF DIGITAL SYSTEMS £10.50


Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

- Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2 OR and AND functions; logic gates; NOT, exclusive-OR NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

O-LEVEL ENGLISH LANGUAGE £6.50

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on COMPREHENSION, Book 2 covers SUMMARY, PUNCTUATION & SPELLING, and Book 3 coaches you in the principles of COMPOSITION. Size: 3 A4 volumes totalling 250 pages.

SELF-INSTRUCTION COURSES

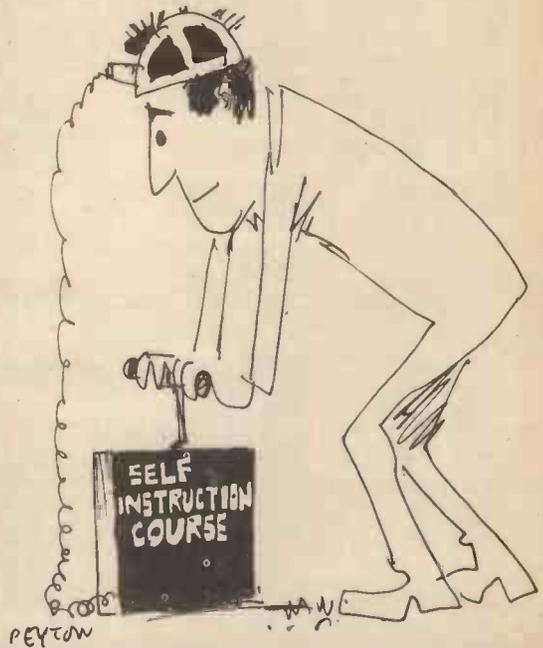

CAMBRIDGE LEARNING ENTERPRISES, UNIT 25, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS PE17 4BR, ENGLAND.
TELEPHONE: ST. IVES (0480) 67446

All prices include worldwide postage (airmail extra) if order comes to £15 or more, deduct £2
Please allow 21 days for delivery

GUARANTEE No risk to you.

If you are not completely satisfied your money will be refunded.

Please send me the following books:

- Computer Programming in BASIC (4 books) at £7.50
- The BASIC Handbook at £11.50
- FORTRAN Coloring Book at £5.40
- A.N.S. COBOL at £4.40
- Algorithm Writer's Guide at £3.40
- Digital Computer Logic & Electronics (4 books) at £6.50
- Design of Digital Systems (6 books) at £10.50
- O-Level English Language (3 books) at £6.50

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my

* Access/Barclaycard/Visa/Eurocard/Mastercharge/Trustcard
account no. (*delete where applicable)

Signature.....

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers (inc. Eire) should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

Name

Address

Cambridge Learning Enterprises, Unit 25, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England.

MICROPROCESSOR MULTI-ALARM/CHRONO WATCH.

£39.95 inc.

This 'BELTIME PICOQUARTZ' has more functions than any other watch we've seen.

- A. Normal display - hours, mins, secs, date, weekday in English, French, German, Italian or Spanish.
- B. Month and year - programmed up to year 2008 to cater for 28, 29, 30 or 31 day months.
- C. Choice of 12 or 24 hour mode. Back light.
- D. 2nd time zone with all above functions.
- E. Daily alarm facility for either time zone.
- F. 2nd alarm to remind you of appointments.
- G. Chronograph 1 - (1/100 sec) accumulative, split or lap modes. Records up to 24 hours. Optional alarm beep every 30 seconds.
- H. Chronograph 2 - Counts down from preset time to zero when it sounds alarm and starts chrono 1.
- J. Chime - Optional programming of hourly chime.

BELTIME ALARM/CHRONO

Advanced and accurate, this watch has a total of 29 functions. (8 time functions, 4 alarm functions and 17 chronograph functions.) World timer version illustrated but other styles available.

£19.95

All products carry full 7 day money back reassurance plus 12 month guarantee. Please add 50p for each spare battery required. SAE for illustrated details of other bargains.



DIGITAL CLOCK RADIO

£19.95 inc.

AM/FM/LW Radio. Green fluorescent display, snooze and sleep time facilities, dimmer, alarm, etc.

LADIES WATCHES

DRESS
£11.95

DAY
£8.95



5 function - Hours, mins, secs, day, date, back light, auto calendar. Only 6mm thick. Elegant matching metal bracelet. State preference for gold or silver colour.

ANALOGUE QUARTZ

Exceptionally good looking watch with conventional display but digital accuracy.

ONLY

£23

inc.



QUARTZ LCD Alarm/Chrono

22 function, 6 digit. Hours, mins, secs, date, day of week, stopwatch, split time, alarm, back light.


ONLY

£17.95

inc.

CREDIT CARD CALCULATOR

£8.65 inc.

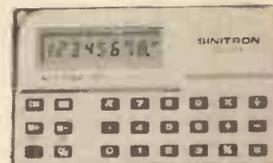

Very slim with standard 4 functions plus memory, percentage and sq. root. In mock leather wallet with credit card pocket.

SPARKS DEVELOPMENTS,
53 North Street, Melbourne,
Derbyshire DE17 1FZ.

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

DL1000K

This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.60



DLZ1000K

A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00
Optional Opto Input £1.60
DLA1



MINI KITS

These KITS form useful subsystems which may be incorporated into larger designs or used alone.

Kits include PCB short Instructions and all components.

TEMPERATURE CONTROLLER/THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. PCB (4 cm.sq.) potentiometer, plus all other components included with instructions. 500W £3.20 1KW £3.50

SOLID STATE RELAY

Ideal for switching motors, lights, heaters etc. from logic. Opto isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. £2.60

BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

DIGITAL VOLTMETER/THERMOMETER KIT



a single diode as the sensor. Requires a 3mA 9V supply. (PP3 battery) £20.75

LEDs

0.1" Red	9p	DL727 0.5" 2-digit display	£1.50
0.2" Red	9p	CA	
Green	12p	DL304 (pin compatible with DL704) 0.3" CC Red	70p
Yellow	12p	DL847/DL850 (pin compatible with DL747/750) 0.8"	£1.80
Square Red		CA/CC	
5x2.5x	20p	LIQUID CRYSTAL DISPLAY 0.5" 3 1/2 digit 40 pin dil.	£8.10
SPECIAL OFFER		SPECIAL	
25 off 0.2"		IL74 Opto Isolator	45p
Red	£1.50		
Green	£2.00		
Yellow	£2.00		

DISPLAYS

400V Plastic Case (Texas)	
3A	49p
15A	90p
8A	62p
20A	165p
12A	70p
25A	190p
6A with trigger	80p
8A isolated tab	82p
Disc	18p

TRIACS

400V Plastic Case (Texas)	
3A	49p
15A	90p
8A	62p
20A	165p
12A	70p
25A	190p
6A with trigger	80p
8A isolated tab	82p
Disc	18p

INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	18p
AY-5-1224 Clock	£2.60
AY-5-1230 Clock/Timer	£4.50
AY-5-1270 Thermometer Controller	£8.60
ICL7106 D.V.M. (I.C.D. Drive)	£7.50
TDA1024 Zero Voltage Switch	£1.20
LM3911 Thermometer	£1.20
LM3914 Dot/Bar Driver	£2.60
MM57160 (stac) Timer	£5.95
S566B Touchdimmer	£2.60
S9263 Touchswitch 16 way	£4.85
ZN1034E Timer	£1.80
All ICs supplied with data and circuits Data Sheets only 5p	



BARCLAYCARD

VISA

All components brand new and to specification. Add V.A.T. AT CURRENT RATE TO ABOVE PRICES PLUS 30p P.&P. Mail Order - Callers welcome by appointment.



T.K. ELECTRONICS (PE) 106 Studley Grange Road, London W7 2LX. Tel: 01-579 9794

KITS

Kits include components, printed circuit boards and instructions

Pools predictor (ZA44)	£7.30
Clap switch (ZA40)	£5.00
Ring Modulator (ZA39)	£6.70
Mini Short Wave Receiver (ZA33)	£8.00
Ioniser (ZA28)	£9.00
Telephone amplifier (ZA26)	£11.00
Touch dimmer (ZA21)	£6.50
Equaliser (ZA15)	£17.00
Parametric equaliser (ZA52)	£25.00
Audio analyser (ZA51)	£14.00
Automatic battery charger (ZA54)	£17.50
VHF/UHF T.V. modulator (ZA1)	£5.50
100W amplifier using 2 x LM391 I.C.'s (ZA3)	£15.50
Ultrasonic transmitter for headphones (ZA56)	£6.50
Ultrasonic receiver for headphones (ZA57)	£8.25

SPECIAL OFFERS

Assorted transistors BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197. 100 for £5.50

Murata ultrasonic transducers MA40 LIS 180p MA40 LIR 180p or 320p PR. Data 10p.

Reed inserts - 28mm. Normally open gold contacts. 10 for £1.00 100 for £7.50

5" oscilloscope tubes - SE5J. £15.00 (for callers only).

Assorted Giant Screw Packs Includes

Self tapping, self cutting screws, nuts, bolts, washers, eyelets etc. etc. Weight - 1kg (2.2lb). Approx 1400 items Only £1.80 (U.K. only).

ORDERS -

Add 25p post and packing Add 15% VAT to total order Minimum order £1.00. Barclay/Visa/Access cards accepted. Minimum Telephone orders £5.00.

T. POWELL,
306 St. Pauls Road, Highbury
Corner, London N1.

Tel: 01-226 1489

SHOP HOURS

Mon-Fri 9-5.30 pm
Sat 9-4.30 pm

TRANSFORMERS

30 VOLT RANGE
Pri 220/240 Sec 0-12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
73	1.0	3.93	1.10
3	2.0	6.25	1.10
20	3.0	6.82	1.31
21	4.0	8.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.39	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	20.0	32.40	O.A.

CONTINUOUS RATINGS

EX-STOCK—

+ VAT 15%

**TRANSFORMERS
END OF LINE OFFERS**

Ref	VA	Price	P & P
30-Isolator	240V:240V 200VA	£4.54	£1.04
62-Isolator	240V:240V 250VA	£5.62	£1.04
6-250-0-250	100ma 1) Sec 6-3V	3.5A 2) Sec 0-5V, 6-3V	2/1 amp £3.20 78p
7-350-0-350V	100ma 1) Sec 6-3V	3.5A 2) Sec 0-5V, 6-3V	2/1 amp £4.10 96p
M184	To match EL84 15W	£1.62	32p
M616	0-240V: Screen 1) 13-0-13 1A. 2) 12V 150ma	£2.10	60p

M489	0-240V: 1400V	150ma, 6-3V	4A £5.50	£1.04
M708	6K to 3KΩ	matching transformer	5W	90p 40p

M679	120V x 2: 36V 1.6A	£3.00	78p	
M865	100V Line to 4Ω	10 watts	£1.90 60p	
M973	100V Line to 8Ω	40 watts	£2.90 60p	
M1015	Choke 8A	5mH 150A Surge	£1.50 45p	
M1020	0-240V 12-0-12V	50ma	97p 41p	
M1130	0-240 4500V	10ma	£4.86	£1.08
M1165	0-115-240V: 14V 50ma		75p 30p	

Metal Oxide Resistors 1/4W 5% TR4 (Electrosil)
24K/470Ω/560Ω/1K/1K8/2K4/1K1/270K/1K6/82K/
20K/820Ω/16K/180K/390Ω/3K/510Ω/300K/
220K/2K/100K/22K/130K/47K/1K2/120K/110K
£1.50/100, VAT.

P.W. Purbeck	oscilloscope transformer 250-0-250	6-3V: 12-9V	£7.51	£1.04
--------------	------------------------------------	-------------	-------	-------

Antex Soldering Irons	15W, 25W	£4.58
Safety Stand		£1.75 P & P 52p each

Solderless bread boarding U. Dec B for ICs etc. £6.99
P&P 40p VAT 15%

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V and 25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	4.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	18.37	1.89
118	8.0	27.29	2.39
119	10.0	27.48	O.A.
109	12.0	31.79	O.A.

MAINS ISOLATORS (SCREENED)
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.84	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.81	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	58.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-220-240V Sec 115 or 240V.
State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	6.55	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
200	12.02	1.67	65W
250	12.55	1.67	69W
500	20.13	1.89	67W
1000	30.67	2.65	84W
1500	33.02	O.A.	93W
2000	38.97	O.A.	95W

12 OR 24V OR 12-0-12V
Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.86	0.90
18	4	2	4.48	1.10
85	5	2.5	6.16	1.10
70	6	3	8.99	1.10
108	8	4	8.16	1.31
72	10	5	8.83	1.31
116	12	6	9.69	1.52
17	16	8	11.79	1.52
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

AUTO TRANSFORMERS

Ref	VA	(Watts)	£	P&P
113	15	0-115-210-240	2.73	0-81
64	75	0-115-210-240	4.41	1-10
4	150	0-115-200-220-240	5.70	1-10
67	500	0-115-200-220-240	12.09	1-91
84	1000	0-115-200-220-240	20.64	2-39
93	1500	0-115-200-220-240	25.81	O.A.
95	2000	0-115-200-220-240	38.31	O.A.
73	3000	0-115-200-220-240	65.13	O.A.
80S	4000	0-10-115-200-220-240	84.55	O.A.
57S	5000	0-10-115-200-220-240	98.45	O.A.

High Quality Amplifier Modules

10W (AL30)	£3.75
25W (AL60)	£4.95
35W (AL80)	£7.75
125W (AL250)	£18.74

F.M. Tuner 4 push buttons £23.60
Pre-Amps & Power Supplies available. P&P 40p. VAT 15%

ABS PLASTIC BOXES inset brass nuts, internal slots to take P.C. cards, flush fitting lid

PB1	180mm . 62 . 40	80p
PB2	100mm . 75 . 40	90p
PB3	120mm . 100 . 45	£1.04
*PB4	215mm . 130 . 85	£2.88

P & P 33p. VAT 15% *P & P 46p

AVO TEST METERS

AVO 8 MK5	£91.50
AVO 71	£39.00
AVO 73	£50.78
AVO MM5 minor	£35.95
Wee Megger	£76.28
TT169 in circuit transistor tester	£41.53
EM272 316 KΩ 1 volt	£59.80
DA116 digital	£110.90
BM7 Megger	£53.76
Clamp Meter to 300A	£54.60

All Avos Meggers and accessories available
P&P £1.32 15% VAT

NEW RANGES VAT 15%

Pri 0-220, 240V Sec. 0-36-48 twice. To give 36-0-36, 48-0-48 72V or 96V.

Ref.	£	P & P
3amp	16.17	1.70
4amp	20.85	2.11
5amp	29.30	2.47

U4315 Budget Meter
20KΩ/V Ranges to 1000V. 2.5A AC/DC
500K Res. in steel case £15.85 P&P £1.32
VAT 15%

O-C Tap (7.5V-0-7.5V)

171	500mA	2.30	0.52
172	1A	3.26	0.82
173	2A	3.95	0.90
174	3A	4.13	0.99
175	4A	6.30	1.10

SPECIAL OFFER Multimeter (20KΩ/V with combined audio/I.F. test oscillator at 1KHz and 465 KHz. AC/DC to 1000 volts. DC current to 500 MA resistance to 1KΩ size 160x97x40mm EB-50, P&P £1.00, VAT 15%

PLUG IN SAVE BATTERIES
Fits into a 13A skt. 3-6-9-12V multipug outlet 300ma £4.60 P&P 55p. VAT 15%

ELECTROSIL metal oxide low noise resistors.

SCREENO MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0-3	2.83	0.63
212	1A, 1A	0-6, 0-6	3.14	0.90
13	1000	9-0-9	2.38	0.44
235	330, 330	0-9-0-9	2.19	0.44
207	500, 500	0-8-9, 0-8-9	3.05	0.85
208	1A, 1A	0-8-9, 0-8-9	3.88	0.90
236	200, 200	0-15-0-15	2.19	0.44
214	300, 300	0-20-0-20	3.08	0.90
221	7000CI	20-12-0-12-20	3.75	0.90
206	1A, 1A	0-15-20-0-15-20	5.09	1.10
203	500, 500	0-15-27-0-15-27	4.39	1.10
204	1A, 1A	0-15-27-0-15-27	6.64	1.10
239	50	12-0-12	2.88	0.43

ELECTRONIC CONSTRUCTION KIT
Home electronics teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. Full instructions and clear diagrams.
Price £8.29 P&P £1.10, VAT 15%

PANEL METERS

43mm . 43mm	6.20	82mm . 78mm	6.70
0 50MA	5.95	0 50MA	6.70
0 500MA	5.95	0 500MA	6.70
0 1mA	5.95	0 1mA	6.70
0 30V	5.95	0 30V	6.70

VU ind. Panel 48mm x 45mm
VU ind. Edge 54 . 14mm
250µA F SD . 2.60
Carriage 76p. VAT 15%

Barrie Electronics Ltd.
3, THE MINORITIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

PLEASE MENTION
PRACTICAL ELECTRONICS
WHEN REPLYING TO ADVERTISEMENTS

Amplifiers from HiAmp. All fully short circuit and open circuit protected with thermal limiting. Making these amplifiers indestructible from stress other than incorrect supply voltage.

- £5.19** 10 watts into 4 ohm .1% distortion max. 30Hz-80KHz, supply voltage ± 18v.
- £6.79** 20 watts into 4 ohm .1% distortion max. 30Hz-80KHz, supply voltage ± 22v.
- £15.79** 50 watts into 4 ohm .1% distortion max. 30Hz-80KHz, supply voltage ± 22v.
- £23.32** 100 watts into 4 ohm .1% distortion max. 30Hz-80KHz, supply voltage ± 32v.

All prices include P. P.
Make your own keyboards - ML-3 the reccapable switch, ML-3 individual keyboard switch with reccapable top allowing lettering by individual.

Only: 1-10 **30p** each 51-100 **25p** each
11-50 **27p** each P. & P. 30p.

JONES ELECTRONIC SUPPLIES
588 ASHTON ROAD, HATHERSHAW, OLDHAM, OL8 3HW
Tel: 061-652 9879 Telex: 668250

FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation second to none for our catalogue - and for the service that backs it up. Experience both for yourself. Just send £1.30 with the coupon and a catalogue will come by return of post.

● About 2,500 items clearly listed and indexed.
● Profusely illustrated throughout.
● 128 A-4 size pages, bound in full-colour cover.
● Bargain list of unrepeatable offers included free.
● Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.,
Dept. PE., 234-240 London Road, Mitcham, Surrey CR4 3HD

POST THIS COUPON
with cheque or P.O. for £1.30

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

HOME RADIO (Components) LTD., Dept. PE. (Regn. No
234-240 London Road, Mitcham, Surrey, CR4 3HD London 912966



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

NICAD RECHARGEABLE CELLS, replacement sizes (Sub-C) 1.2AH £1.99, U11 (C) 1.8AH £2.75, U2 4AH £3.00, Penlite £1.50. P&P 16p/Cell 12V-5A accumulators, Component packs 10p stamp for list. C.W.O. HARNETT SUPPLIES, 1 Harnett Cottage, Bogle, Lynsted, Sittingbourne, Kent. (Postal Only).

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.
22 & 47 — 5p. (50V — 6p). 100 — 7p. (50V — 8p).
220 — 8p. (50V — 10p). 470 — 11p. (40V — 16p).
1000/15V — 15p. 1000/25V — 18p. 1000/40V — 35p.
Subminiature bead Tantalum electrolytics.
0.1, 0.22, 0.47, 1.0, 35V, 4.7 & 6.3V — 14p.
2.2/35V, 4.7/25V — 18p. 10/25V, 15/16V — 15p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V — 20p.
15/25V, 22/25V, 47/10V — 20p. 47/16V — 36p.
Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.
10% 390 pf. to 4700 pf. — 4p.
Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.
Polystyrene E12 Series 63V. Horizontal Mtg.
10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.
Miniature Polyester 250V Vert. Mtg. E6 Series.
-01 to -068 — 4p. -1 — 5p. 15 — 22 — 6p. -33, -47 — 10p.
-68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.
Mylar (Polyester) Film 100V Vertical Mounting.
-001, -002, -005 — 3p. -01, -02 — 4p. -04, -05 — 5p.
Miniature Film Resistors Highstab. E12 Ser. 5%.
0.125W mixed carbon/metal 10Q to 1MΩ — 1p.
0.25W Carbon 1Q to 10MΩ (10% over 1MΩ) — 1p.
(E24 Series, av. in 1W C Film 1Q to 5MΩ).
0.25W, 0.5W & 1.0W Metal Film 10Q to 2MΩ — 2p.
1N414B — 2p. 1N4002 — 4p. 1N4006 — 6p. 1N4007 — 7p.
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7 — 10p.
8 Pin i.c.s. 741 Op. amp. — 18p. 555 Timer — 24p.
Dil Holders 8 pin — 9p. 14 pin — 12p. 16 pin — 14p.
LED's 3 & 5mm. Red — 10p. Green & Yellow — 14p.
Grommets for 3mm — 1 1/2p. 2 pcs. holders 5mm. — 2p.
20mm. O.B. Fuses 15, 25, 5, 1, 2, 3 & 5A — 3p.
20mm. Anti Surge 100mA. to 5.0A — 5p.
20mm. Fuseholders P.C. or Chassis Mtg — 5p.
Solid A1. knobs 15mm. — 25p. 25mm. — 35p. 30mm. — 50p.
400mV Zener diodes E24 series 2V7 to 33V — 8p.

Prices VAT Inclusive Post 10p. (Free over £34).

THE C.R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

100 7400 SERIES IC + 100 Diodes 4148 type. Marked and Unmarked. Untested. 100 + 100 £1.50. STE Ltd., Uni-Com Building, Edenbridge, Kent. TN8 6EW.

P.C.B.s Paxolin 10 1/2" x 4 1/2" 4-£1.30. 12" x 9 1/2" 85p. 16" x 11 1/2" £1.40. D.S. 10" x 8 1/2" 85p. Fibre Glass 12" x 8" £1.70. D.S. 10 1/2" x 7" £1.35. 8" x 7" £1.15. Unit with 8 silicon diodes 600V 20 amp, 8 SCRs 400V 16 amp, 6 Vinkors, W.W. resistors etc. £6.75. 300 small components, trans. diodes £1.85. 7 lbs. assorted components £3.75. List 15p refundable. Post 20p. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

TUNBRIDGE WELLS COMPONENTS, Ballards, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquires S.A.E.

SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

VHF CONVERTER. 45-220MHz (Varicap) 29-30MHz IF. Ideal feed HF receiver. Only £6.80. Ready built (PSU etc) in case. £24.50. £1.00 carr. SAE details. H. Cocks, Bre Cottage, Staplecross, Robertsbridge, Sussex. Tel: 058083-317.

COMPONENTS AT SILLY PRICES. 1000 mixed resistors £3.60. SAE Lists. W.V.E.3, Craig Farm, Tintern, Gwent.

CUT PRICE COMPONENTS

SL810C	RF Amplifier	£2.40
SL813C	Limiting wideband amplifier	£2.70
SL840C	Double balanced modulator	£3.00
SL680C	Crystal oscillator maintaining circuit	£1.50
LM340K-5.0 (7805)	1 amp 5 volt regulator in TO3 CAN	£1.20
78M06	1/2 amp 6 volt regulator in TO39 CAN	£0.70
XR4136CP	Quad 741 op. amp. 14 PIN DIL	£0.70
CA3080	Operational transconductance amp. 8 lead TO5 CAN	£0.60
709	Op. amp. 14 PIN DIL	£0.20
4016	CMOS quad bilateral fet switch	£0.25
4047	CMOS monostable/astable multivibrator	£0.80
1702A	256 by 8 BIT UV erasable prom	£4.50
VP5	Reliability Inc. derives isolated 5 volt supply from 5 volt DC input. Ideal for RAM's ROM's op. Amp's etc.	£6.00
5/12D	DC-DC converter derives ± 12 volts from single 5 volt DC input	£11.50

For orders less than £5 please add 25p Post. SEND TO:

J. PORTER

177, Brookdale Avenue, Greasby, Wirral, Merseyside L49 1SR

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

SURPLUS stocks of Electronic Components at less than wholesale prices. SAE brings free lists. Bardwell Ltd., 212 Studley Lane, Dronfield-Woodhouse, Sheffield, S18 5YP.

200 mixed components £4. Sole Electronics, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

100 ASSORTED COMPONENTS 115p, 100 Resistors assorted 1/2W 75p, 10 Mains Neons 50p, 20 Micro-switches 150p, 50 Reed switches 200p, 50 assorted capacitors 150p, add 25p P&P. Durrants, 9 St. Marys Street, Shrewsbury, Salop.

CAPACITY AVAILABLE

PRINTED CIRCUIT BOARDS. Quick deliveries, competitive prices, quotations on request, speciality small batches, larger quantities available. Contact: Mr. J. K. Harrison, Jamieson Automatics Ltd., 1/5 Westgate, Bridlington, North Humberside. Tel: (0262) 74738/77877.

RECORD ACCESSORIES

STYLII Cartridges for MUSIC CENTRES, &c. FREE List No.29 for S.A.E. includes Leads, Mikes, Phones &c. FELSTEAD ELECTRONICS, (PE), Longley Lane, Gately, Cheadle, Ches. SK8 4EE.

TAPE EXCHANGES

RECORDER OWNERS (Cassette/reel) can now speak to the World! All ages... every interest. Send stamp: WORLDWIDE TAPETALK, 35 The Gardens, Harrow.

SERVICE SHEETS

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

Publishers Announcement

Due to increases which may have taken effect since this issue went to press, we strongly advise readers to check with advertisers the prices shown, and availability of goods, before purchasing.

SITUATIONS VACANT

ELECTRONIC TECHNICIANS Grades 3 and 4 required to assist in the construction, modification and maintenance of electronic equipment for use in teaching and research carried out in the Psychology Dept. of U.C.L. The work is varied and interesting and covers a wide range of analogue and digital techniques. ONC, C. & G. or equivalent required. The Grade 3 technician could have an electrical/mechanical background. Salary in range Grade 4: £3432-3950. Grade 3: £3122-2553 plus £524 London Weighting (under review). Application form from Personnel Officer (Technical Staff CK3) University College London, Gower St. London WC1E 6BT.

EDUCATIONAL

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. P272 Intertech House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. P272 Intertech House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. P272 Intertech House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

AERIALS

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.
B45-UHF TV, B11-VHF Radio. B11A-2 metre radio. For next to the set fitting.
Price £6. S.A.E. for leaflets. ACCESS
ELECTRONIC MAILORDER LTD,
62 Bridge Street,
Ramsbottom, Bury, Lancs, BLO 9AG.

WANTED

WANTED CIRCUIT DESIGNER, to supply Schematics and P.C. board layout for mains powered 6 digit display controlled by clock I.C. with stand-by battery for clock chip. Send details of Fee required etc. To: T.S.C. P.O. Box 2216, Darwin N.T. 5794 AUSTRALIA.

WANTED P.E. Jonna in good condition for around £100. Ring Crawley 30174.

FOR SALE

NEW BACK ISSUES of "Practical Electronics" available 70p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

PRACTICAL ELECTRONICS June 1966 to February 1972. Offers. Leeds 691655.

ACORN MICROCOMPUTER Factory Built and Tested, including acorn power supply, manuals, circuit diagrams etc. £80.00 o.v.n.o. Phone Kettering 711644.

PRACTICAL ELECTRONICS, WIRELESS, TELEVISION, 146 copies: 1964-1968. Offers over £30. Phone Bedford 851010.

FOR SALE £100 PE Joanna completely built with cabinet, can be seen working, small problems on one board. Tel: Fareham 231538.

25000 RESISTORS Unused & Boxed all types & Values, some Wirewound. Offers. Phone 01-764 0264.

MK14 Working, improved Keyboard and revised monitor, extra RAM and spare RAM Chip, Kemtron programming manual and data sheets. PSU cooling Fan £60.00. Phone Rainham, Essex. 51164. Dave.

COMPUTER EQUIPMENT. Westrex Teletype ASR 33 vgc £150.00. Paper-Tape Reader 250 CH/SEC £100.00. Paper-Tape Punch £100.00. More Available: Bedford 57135.

BOOKS AND PUBLICATIONS

FREE. World-famous manufacturer's convenient, pocket-sized electronic construction guide (Nearly 200 full-colour illustrations). Limited period offer. Send S.A.E. now to **TECHNOCENTRE**, 54 Adcott Road, Middlesbrough.

ROMANIAN ELECTROGRAPHY, tobiscopes, electrokinesis, biogravity, hallucinophotography, dermoptics, psychotronic generators, Kirlianography. SAE 4"x9". **PARALAB**, Downton, Wilts.

TTL DESIGN CONSIDERATIONS

A booklet packed with information on TTL circuit building. Debouncing, decoupling, fan out, floating, buffers, open collector gates, regulators, race hazards, clocking, sinking, ground planes, cascading, simple interfacing, and much more. If you use TTL this has got to be helpful - well illustrated. 75p inclusive of P.&P. etc.

PAWBOOKS,
117 Blenheim Road, Deal, Kent.

ANY REQUESTED SERVICE SHEET £1 + Large S.A.E. Full repair data any named TV £5.30 (with circuits, layouts etc. £7). SAE brings newsletter, bargain offers, etc. **AUSPEL**, 76 Church St, Larkhall, Lanarks ML9 1HE.

LADDERS

LADDERS. Varnished 25 1/2" ext. £46.04. Carr. £3.50. Leaflets. Callers Welcome. Ladder Centre (PEES) Halesfield (1). Telford 596644.

MISCELLANEOUS

P.C. BOARDS FOR INDUSTRY 'and' THE AMATEUR

- One off or production runs
- Assembly of P.C.Bs or kits
- Expert hand soldering
- Design service if required
- Artwork & Photography

SEAHORSE ELECTRONICS LTD.
Unit 2 Picow Farm Road
Service Industry Estate,
Runcorn, Cheshire.
(09285) 7595

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerocol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper clad Fibreglass Board approx. 1mm thick £1.70 sq. ft. Post/packing 60p. **WHITE HOUSE ELECTRONICS**, P.O. Box 19, Castle Drive, Penzance, Cornwall.

GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable at £44; 60 watt £37; 200 watt £89; 100 watt twin channel sep. treble/bass per channel £58; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt £32; 200 watt £50; fuzz boxes, great sound £8-50; bass fuzz £9-50; over-driver fuzz with treble and bass boosters £15-50; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £90; twin channel £100; bass combo £100; speakers 15in. 100 watt £38; 12in. 100 watt £23; 60 watt £15-00; microphones Shure Unidyne B £26.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield, Cheshire.
Tel: 061-344 5007 or 061-308 2064

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

"Stop Press UK 101 Compatible!"
**COLOUR
YOUR
NASCOM!**



DAZZLING COLOUR GRAPHICS FOR NASCOM 1

Genuine bit-addressable "pixel" system for straightforward programming of pictorial or mathematical functions.

8 Colour display plus 8 colour independent background facility. Full documentation with **FREE SOFTWARE**: powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems - send us diagrams etc of your b & w video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.

NOW AVAILABLE FOR £45 inclusive of VAT and postage.

WILLIAM STUART SYSTEMS Ltd Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £1.55. Large range of single sheets in stock at 32p per sheet.
Ferric Chloride - 1 lb bags 80p (P&P 50p)*
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.30.
S.A.E. lists and information. P&P 25p/order except*

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE


SOLID STATE CAR INSTRUMENTS

AS FEATURED IN P.E. OCTOBER, NOVEMBER, AND DECEMBER 1979.

Send S.A.E. for component price lists to:-

HOWARD ASSOCIATES
59, Oatlands Avenue, Weybridge, Surrey KT13 9SU

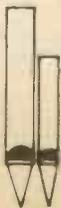PRINTED CIRCUIT BOARDS from your own or published designs, Glass fibre tinned or varnished, Panel and P.C.B. legend printing. S.A.E. for quotations. R. D. **ELECTRONICS**, 12 Whiteoaks Road, Oadby, Leicester. 0533 716273.



RYDER ORGAN SYSTEM (Wireless World)

A classical design with full-size keyboards. Couplers, capture, etc., can be included.

Cassette. p.c. boards, data, from:-
HIKON LTD. (P),
Woodside Croft, Ladybridge Lane,
Bolton BL1 5ED.

MSF CLOCK

NEW! Shows Date, Hours, Minutes, Seconds, 8 digit LED, also parallel BCD output, only 5 x 8 x 15cm. Time Signal accuracy always. £48.80.

60KHz MSF Receiver, serial data output. £13.70.

Still NO RADIO 4? Get all the NEWS with a 200KHz to Medium Wave Converter. £11.40.

SIG. GEN., 10Hz-200KHz, logic and variable sine and square wave outputs. £10.80.

Each fun-to-build kit includes all parts, printed circuit, case, postage, money back assurance so **SEND OFF NOW**.

CAMBRIDGE KITS

45 (FZ) Old School Lane, Milton, Cambridge.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS, 021-354 9764, or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

KITS, constructed by competent engineer, assembled and soldered professionally, any make of kit including the well known names of Heathkit, Jostykit, Sinclair, Hart, Ambit, etc, etc. High standard work throughout and a progress report on work after two weeks. Testing facilities also available. D. G. Harrington, 25 Poynter Road, Bush Hill Park, Enfield, Middx. EN1 1DN.

MINI-POWER DRILL KIT

ULTRA HIGH
SPEED
OVER
25,000 RPM



This mains operated Dremel Kit can grind, drill, polish, carve, sand, rout, engrave etc. Contains over 30 accessories inc. cutters, grinding wheels & points, brushes, polishing tips, sanding discs, drum sanders, sanding bands, mandrels, dressing stone, collet wrench etc. All you need for home, hobby and craft work, electronics, modelling and pattern making, gun-smithing, lapidary work-you name it, fitted case, £41.95 + £1.95 p&p. If required, 34 piece accessory kit, £15.75 + £1.50 p&p. Access accepted. Send Name, Address and No.

JOHN DUDLEY & CO. LTD. (Dept PE20)
Carolyn House, Water Road, Wembley, Middx.
(MAIL ORDER), 01-435 5456 (before noon)

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation. Each cassette are type C90.
Morse by light system available. Morse Key and Buzzer unit for sending practice.
Prices each cassette (including booklets) £4.75. Morse Key and Buzzer £4.75.

Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. PE)
12 Longshore Way, Milton,
Portsmouth PO4 8LS.

SOLAR CELLS, Batteries, Panels, Thermoelectric Generators, heat pipes, books etc., Details: Edenscombe Ltd., 34 Nathans Road, N. Wembley, Middx. HA0 3RX.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for fast charge HP7 (AA) £1-05 SUB C £1-36, HP11 (C) £1-98, HP2 (D) £3-02, PP3 £3-79, PP3 charger £5-40.

All the above nickel cadmium batteries are brand new and are guaranteed full spec. devices. All cells are supplied complete with solder tags (except PP3). Brand new full spec. **RECHARGEABLE SEALED LEAD ACID** maintenance free batteries suitable for burglar alarms etc. 1-2 amp hr. 6V £4-07. 2-6 amp hr. 6V £5-23.

Quantity prices available on request. Data and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type). Please add 10% P&P in orders under £10 - 5% over £10. VAT at the current rate should be added to total order. Cheques, Postal Orders, Mail order to:-

SOLID STATE SECURITY DEPT (PE), 10 Bradshaw Lane, Parbold, Wigan, Lancs. Tel: 02575 4726.

PE ULTRASONIC ALARM KITS

Designer Approved

All Kits Inc. all components, F/G PCB, ready drilled ABS box and hardware

ULTRASONIC DETECTOR KIT

(less relay) £12.75
CONTROL KIT (less relay, & keyswitch) £5.95

Relay £2.75 Keyswitch £3.95

Piezo Electronic Sounder (105dB @ 1mtr) £7.75

All prices inc. VAT P & P. SAE with enquiries.

UK Mail order only (CWO)

GJD ELECTRONICS 105 Harper Road, Radcliffe, Manchester M26 0RQ.

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, L.E.D.s, and Instructions. Available at £5.00 each (including P. & P.)


- Kit One - Gates
- Kit Two - Flip-Flops
- Kit Three - Shift Registers
- Kit Four - Counters
- Kit Five - Displays

S.A.E. for further details to:

AUTOMATED HOMES

69 High Street, Ryton, Coventry, CV8 3FJ.
(Mail Order).

SIGHT FOR SORE EYES

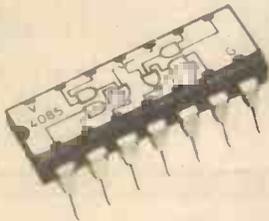

STICKIES are printed self-adhesive labels that stick to the top of ICs. They turn a board-full of ICs into a working circuit diagram! See at a glance where to place your soldering iron or test probe. Use **STICKIES** for building and de-bugging prototypes, fault-finding, experimenting, teaching - even designing PCB layouts.

STICKIES come in handy-size packs for 7400- or 4000-series ICs. Each pack contains a sensible mix of more than 60 different IC types. 120-label packs 80p.. 480-label packs £2.80, 2-10 packs £2.50 each. 11+ £2.20 each.

Prices include 15% VAT and first-class postage.

Please state whether TTL or CMOS required.

Official orders welcome.

Let others suffer the sore eyes - try a pack of **STICKIES** and see the difference.

For your **STICKIES** by return of post contact

CONCEPT ELECTRONICS, 8 Bayham Road, Sevenoaks, Kent, TN13 3XA (0293 514110).

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P&P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

PRACTICAL ELECTRONICS P.C.B.'s

Professional quality glass fibre Fry's roller tinned and drilled.

- Sept. 79 Waveform Generator EG161 £1.58
- Smooth fuzz EP134 75p.
- Oct. 79 Input Channel Amp EP158 set of 6 £5.61
- Dig Temp Controller EC9 £1.90
- VLF Receiver EG174/5 set of 2 £1.75
- Nov. 79 Diomatic £2.04. Digital darkroom timer £1.88.

For full list and current pcb's please send SAE. Pcb's also produced from customers own masters. Trade enquiries welcome. Please write for quote. CWO please. Postage - On orders less than £10 please add 25p postage.

PROTO DESIGN

14 Downham Road, Ramsden Heath
Billerica, Essex CM11 1PU
Telephone 0268-710722

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. **BAZELLI** (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster. LA 6LT.

CABINET FITTINGS FOR

Stage Loudspeakers and Amplifier Cabs
Fratchcloths, Coverings, Strap & Recess Handles, Feet, Castors, Jocks & Sockets, Cannons, Bulgin 8 ways, Reverb Trays, Locks & Hinges, Corners, Trim, Speaker Bolts etc.

Send 2 x 9p Stamps for samples and illustrated catalogue

ADAM HALL (P.E. SUPPLIES)

Unit 3, Carlton Court, Grainger Road
Southend-on-Sea, Essex.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10.70 plus 25p P. & P. 'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', variable speed, for discos and parties. A mere £4.50 plus 25p P. & P. Experiment with a psychedelic DREAM I.A.R. or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £3 each plus 25p P. & P. **LOTS MORE!** Send 25p for lists. Prices include VAT.

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E 4
Reg. Office 22 Coningsby Gardens.

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2oz
10 to 19	2.83	1.55	.80	.64
20 to 29	3.03	1.76	1.00	.75
30 to 34	3.25	1.86	1.07	.80
35 to 40	3.60	2.08	1.22	.89
41 to 43	4.84	2.71	2.07	1.38
44 to 46	5.37	3.25	2.29	1.80
47	8.37	5.32	3.19	1.91
48 to 49	15.96	9.58	6.38	3.51

SILVER PLATED COPPER WIRE

14, 16, 18	4.30	2.39	1.53	1.00
20 & 22	5.32	3.03	1.85	1.13
24 & 26	6.06	3.57	2.13	1.30
28 & 30	7.00	4.10	2.50	1.53

Fluxcore 60/40 Solder 22 swg 65 ft 90p
18 swg 22 ft 80p

Tinned Copper Wire .6 mm 23 swg 1 lb £4.00 10 lbs £20

Wire Wrapping Wire 30 awg 82 ft £1.10

Wire Wrapping Tool & 4 Reels £6.00

CABLES

			Per Meter
2 WAY	13/2 mm	2.5 amp	13p
2 WAY	16/2 mm	2.5 amp	16p
3 WAY	24/2 mm	6 amp	24p
3 WAY	32/2 mm	10 amp	32p
3 WAY	14/2 mm	2.5 amp	16p
4 WAY	14/1 mm	.75 amp	30p
4 WAY	7/2 mm	1.4 amp	30p
6 WAY	14/2 mm	2.5 amp	45p
10 WAY	7/2 mm	1.4 amp	60p
1 CORE	7/2 mm	Screened	12p
2 CORE	7/2 mm	Each Screened	16p
2 CORE	7/2 mm	Screened	14p
4 CORE	7/2 mm	Screened	30p
LO LOSS	Co-Axial		25p

Prices include P & P and VAT. Dealer enquiries welcome.
Orders under £2 please add 20p.

MEMORY MART

'UK 101' 'Superboard' 4K RAM

Memory Expansion £37.80

2114 1k x 4 each £4.70

2708 UV prom each £6.41

P & P and VAT included if cash with order.

C.O.D. 60p extra.

MEMORY MART

24 Ashleigh Estate, Crundale,
Haverfordwest, Dyfed, South Wales.

Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c. boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills. All immediately available. Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,

Masons Rd. Stratford on Avon
Warwks. CV37 9NF 0789-4879

PROFESSIONAL AND DIY BURGLAR ALARM EQUIPMENT

Send SAE for Pricelist and full details of our top quality items at competitive prices


SONIC INTRUDER ALARM SYSTEMS

19, Hope Street, Old Glossop, Derbyshire, SK13 9SB. Tel: (04574) 2858

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

INTER-LOCKING PLASTIC STORAGE DRAWERS

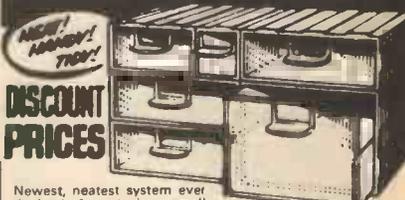

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2 1/2in x 2 1/2in) £3.70 DOZEN
DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in) £5.90 DOZEN
TREBLE (3D) £5.90 for 8.
DOUBLE TREBLE 2' drawers, in one outer case (6D2), £8.90 for 8
EXTRA LARGE SIZE (6D1) £7.90 for 8.

PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%. Orders over £60, less 7 1/2%. PACKING/POSTAGE/CARRIAGE: Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage. QUOTATIONS FOR LARGER QUANTITIES. Please add 15% V.A.T. to total remittance. All prices correct at time of going to press.

4-WAY IN-LINE POWER PANEL
13 AMP
NEON INDICATOR LAMP
PATENT CABLE LOCK
EASILY ACCESSIBLE FUSE
MOUNT IT, OR TRAIL IT!

Modern slim-line power panel, countless uses in home, office, factory, showrooms. Perfectly safe, unbeatable. Can be mounted on wall or tailed anywhere in room. Neat rubber base. Smart PVC outer cover. Black £3.70. White £3.90. P & P 60p. Cable 30p per yard.

FLAIRLINE SUPPLIES (P.E.12)

124 Cricklewood Broadway, London N.W.2
Telephone 01-450 4844

ASTRA-PAK

92 GODSTONE ROAD
WHYTELEAF SURREY CR3 0EB

VAT must be added at 15% to all prices shown. P&P 25p + VAT. Send SAE for full catalogue including books, resistors, capacitors, vero, etc.

7400 0.10	7483 0.58	74166 0.78	4021 0.80	4180 1.06	LINEAR	16 pin	0.12
7400 0.23	7484 0.88	74167 2.00	4022 0.80	4181 1.05	CA3045-14	0.40 18 pin	0.16
7401 0.11	7485 0.58	74170 1.50	4023 0.15	4182 1.05	CA3045-14	0.50 20 pin	0.18
7402 0.11	7486 0.23	74172 6.30	4024 0.50	4183 1.05	LM380N-14	0.85 22 pin	0.22
7403 0.11	7485RE 0.42	74173 1.15	4025 0.15	4184 1.05	LM381N-14	1.40 24 pin	0.24
7404 0.11	7489 1.85	74174 0.65	4026 1.15	4174 1.05	LM710-14	0.30 28 pin	0.26
7404 0.23	7490 0.32	74175 0.60	4027 0.42	4175 0.98	LM711N-14	0.30 40 pin	0.37
7405 0.12	7491 0.64	745175 1.00	4028 0.65	4194 1.05	MC1310P-14	0.88 81LS95	1.25
7405 0.23	7492 0.38	74176 0.58	4029 0.76	4404 0.48	NE555-8	0.20 81LS96	1.25
7406 0.22	7493A 0.30	74177 0.58	4030 0.46	4412 0.19	NE555-14	0.50 81LS97	1.25
7407 0.22	7494 0.72	74178 1.50	4031 1.95	4428 0.38	NE2501B-14	0.80 81LS98	1.25
7408 0.13	7495 0.50	74179 1.50	4032 0.88	4445 0.90	SN75110N	0.40 MICROPROCESSOR	
7409 0.13	7496 0.48	74180 0.85	4033 1.25	4449 0.19	SN76003N	1.60 CRYSTALS	
7410 0.11	7497 1.90	74181 0.58	4034 1.15	4501 0.18	SN76013N	1.25 FREQUENCY	
7410 0.23	74100 0.85	74182 0.70	4035 1.00	4502 0.80	SN76023N	1.25 Mhz	
7411 0.17	74104 0.38	745182 1.50	4036 2.70	4503 0.88	SN76033N	1.48 0.100	3.50
7411 0.23	74105 0.38	74H183 0.75	4037 0.85	4508 0.50	SN76477N	2.50 0.262	3.50
7412 0.15	74107 0.24	74184 1.30	4038 0.95	4507 0.52	TAAS50B	0.32 0.300	3.50
7413 0.24	74109 0.32	74185A 1.30	4039 2.75	4508 2.50	TAA661B	0.88 1.000	3.25
7414 0.50	74110 0.38	74186 5.00	4040 0.68	4510 0.92	TBA120S	0.66 1.008	3.25
7415 0.23	74111 0.58	74188 2.70	4041 0.72	4511 0.82	TBA41A	1.50 1.8432	3.50
7416 0.23	74112 0.30	74189 0.88	4042 0.87	4512 0.92	TBA800	0.78 2.000	3.25
7417 0.23	74116 0.50	74191 0.88	4043 0.80	4513 1.85	TBA810S	0.75 2.097	3.25
7420 0.11	74118 0.80	74192 0.62	4044 0.80	4514 2.30	TBA820S	0.68 2.457	3.25
7421 0.20	74119 1.50	74193 0.62	4045 1.26	4515 2.80	TCA270SD	1.60 3.276	2.60
7422 0.16	74120 0.95	74194 0.82	4046 1.05	4516 0.99	TCA2020	3.00 3.579	2.60
7423 0.21	74121 0.25	74195 0.60	4047 0.86	4517 3.75	ZM411	0.80 3.932	2.60
7425 0.23	74122 0.38	74196 0.72	4048 0.48	4518 0.90	VOLTAGE	4.000	2.60
7426 0.23	74123 0.38	74197 0.58	4049 0.33	4519 0.50	REGULATORS	4.433	2.60
7427 0.24	74125 0.32	74198 1.00	4050 0.40	4520 0.95	LM300H-T099	0.75 4.915	2.60
7428 0.26	74126 0.35	74199 1.20	4051 0.72	4521 2.20	LM309K-T03	1.30 5.000	2.60
7430 0.11	74128 0.75	74221 1.30	4052 0.72	4522 1.25	uA723-14	0.32 5.068	2.60
7430 0.23	74130 0.50	74273 2.05	4053 0.72	4526 1.25	7805-T0220	0.70 5.185	2.60
7432 0.22	74132 0.55	74278 1.65	4054 1.05	4527 1.40	7812-T0220	0.70 5.875	2.60
7433 0.30	74134 0.38	74279 1.10	4055 1.05	4528 0.92	7815-T0220	0.70 6.000	2.60
7437 0.21	74135 0.70	74283 1.65	4080 1.00	4529 1.30	7824-T0220	0.70 6.144	2.60
7438 0.21	74136 0.52	74284 3.40	4086 0.48	4530 0.78	7905-T0220	0.78 6.553	2.60
7440 0.12	74137 0.80	74293 1.30	4067 3.25	4531 0.99	7912-T0220	0.78 8.000	2.60
7441 0.50	74141 0.58	74298 1.80	4068 0.20	4532 1.20	7915-T0220	0.78 8.867	2.60
7442 0.40	74142 1.95	74390 1.76	4089 0.17	4534 5.20	LDW PROFILE	10.000	2.60
7443 0.70	74144 2.50	74393 1.28	4070 0.40	4535 3.80	DIL SOCKETS	12.000	2.60
7444 0.70	74144 2.50	CMOS	4071 0.17	4538 1.26	8 pin	0.09 13.518	2.60
7445 0.52	74145 0.55	4000 0.13	4072 0.17	4539 0.99	14 pin	0.11 18.000	3.20
7446 0.60	74147 1.40	4001 0.15	4073 0.17	4541 1.05	LED's	0.25" 0.2"	
7447 0.48	74148 1.25	4002 0.15	4075 0.17	4543 1.50	RED	6.85 0.09	
7448 0.56	74150 0.68	4006 0.85	4076 0.84	4549 3.92	YELLOW	0.14 0.14	
7450 0.11	74151 0.48	4007 0.16	4077 0.21	4553 3.80	GREEN	0.14 0.14	
7451 0.11	74153 0.48	4008 0.78	4078 0.18	4564 1.25	YELLOW	0.14 0.14	
7452 0.23	74154 0.82	4009 0.40	4081 0.17	4555 0.75	LED clip	0.25 0.35	
7453 0.11	74155 0.50	4010 0.40	4082 0.18	4556 0.75	TMS 4030 4096 BIT DYNAMIC RANDOM ACCESS (2107A) MEMORY 22 PIN DIL		
7454 0.11	74156 0.50	4011 0.15	4085 0.83	4557 3.25	300ms max. access time. 470ns max. read or write cycle time. TTL compatibility on all inputs. No pull up resistors needed. Low power dissipation. 350mW operating 0.3mW standby. Single low capacitance clock. Data sheet available.		
7450 0.11	74157 0.50	4012 0.15	4086 0.63	4558 1.26	2.40 each 4-10% 8-20%		
7450 0.25	74158 0.58	4013 0.40	4089 1.35	4559 3.95			
7472 0.22	74159 1.90	4014 0.78	4093 0.80	4560 1.98			
7473 0.25	74160 0.60	1015 0.70	4094 1.68	4561 0.72			
7474 0.25	74161 0.58	4018 0.40	4095 0.90	4562 5.50			
7474 0.42	74162 0.62	4017 0.72	4096 9.00	4566 1.42			
7475 0.30	74163 0.62	4018 0.75	4097 3.30	4568 2.50			
7475 0.25	74164 0.58	4019 0.82	4098 0.95	4569 1.50			
7480 0.43	74165 0.88	4020 0.88	4099 1.40	4580 4.98			

BUILD A SYNTHESISER!

NO SPECIAL SKILLS REQUIRED
SPECIAL EQUIPMENT



Using **Dewtron** (Reg'd)
PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

MICROELECTRONICS

Digital & Analog Circuits & Systems
by J. Millman Price: £7.80

SILICON CHIPS & YOU
by C. D. Renmore Price: £2.90

INTEGRATED CIRCUITS HOW TO MAKE THEM WORK
by R. H. Warring Price: £4.45

DIGITAL INTEGRATED CIRCUITS & COMPUTERS
by B. Woollard Price: £3.75

BEGINNER'S GUIDE TO HOME COMPUTERS
by M. Grosswirth Price: £3.00

CB BIBLE. THE COMPLETE GUIDE TO CITIZENS BAND 2-WAY RADIO
by P. Bibb Price: £4.25

ELECTRONIC FAULT DIAGNOSIS
by G. C. Loveday Price: £3.60

PROJECTS IN RADIO & ELECTRONICS
by I. R. Sinclair Price: £2.60

CLOSED CIRCUIT T.V. FOR TECHNICIANS VOL. I
by K. J. Bohlman Price: £5.10

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176



Closed Saturday 1 p.m.

INDEX TO ADVERTISERS

Acorn Computers ...	Cover III	E.D.A. ...	4	Phononics ...	86, 87
Adam Hall (P.E. Supplies) ...	102	Electroni-Kit ...	64	Porter J. ...	100
Aitken Bros. ...	91	Electronic Mail Order Ltd. ...	100	Powell T. ...	98
A.J.D. Supplies ...	32	Electrovalve ...	91	Progressive Radio ...	84
Alcon Instruments ...	94	Fladar ...	96	Proops Bros. ...	32
Astra Pak ...	103	Flairline ...	102	Proto Design ...	102
Aura Sounds ...	81	George, David Sales ...	64	Radio Component Specialists ...	94
Automated House ...	102	G.J.D. Electronics ...	101	Ramar Constructor Service ...	102
Barrie Electronics ...	99	Hameg ...	76	R.S.T. Valve Mail Order ...	93
Beckman Instruments ...	22	Heathkit ...	16	Radio & T.V. Components ...	9
BI-Pak ...	14, 15	Hlykon Ltd. ...	101	Romane Electronics ...	6
Birkett J. ...	91	Home Radio ...	99	Sandwell Plant Limited ...	101
Boffin Projects ...	102	Howard Associates ...	101	Saxon Entertainments ...	75
British National Radio & Electronics School ...	85, 92	I.C.S. Intertext ...	87, 100	Scientific Wire Co. ...	102
Brewster S.R. ...	4	I.L.P. Electronics ...	10, 11	Seahorse Electronics ...	101
Bulgin ...	12	Jayen Developments ...	8	Sentinel Supply ...	4
Butternorths ...	8	Jones Electronic Supplies ...	99	Service Trading ...	31
Cambridge Kits ...	101	Kay & Co. ...	90	Solid State ...	101
Cambridge Learning ...	96, 97	L & B Electronics ...	95	Sonic Intruder Alarm Systems ...	102
Chromasonic Electronics ...	89	Lektrokit ...	76	Sparks Developments ...	98
Chromatronics ...	93	Maplin Electronics ...	7, Cover IV	Squires, Roger ...	6
Clef Products ...	94	Marshall A. ...	92	Stevensons Electronic Components ...	71
Codespeed ...	88	Memory Mart ...	102	Strutt Electrical ...	95
Commodore Business Machines ...	21	Menocrest ...	96	Swanley Electronics ...	84
Computer Components (Teletype) ...	Cover II	Metac ...	82, 83	Tandy ...	63
Concept Electronics ...	102	Mhel Electronics ...	101	T.K. Electronics ...	98
Continental Specialties Corporation ...	5	Microdigital ...	16	Technomatic ...	104
U.K. Ltd. ...	12	Modern Book Co. ...	103	Tempus ...	59
Crescent Radio ...	5	Monolith ...	84	Transam Components ...	13
Crofton Electronics ...	8	Datron ...	90	T.U.A.C. ...	60
C.R. Supply Co. ...	100	Delta Tech ...	90	Unilab ...	6
Crimson ...	88	Design Engineering ...	103	Videotime ...	22
Design Engineering ...	103	J. Dudley & Co. Ltd. ...	101	Watford Electronics ...	2, 3
J. Dudley & Co. Ltd. ...	101	Newtronics ...	88	William Stuart Systems Ltd. ...	101
Pawbrooks ...	101	P.K.G. Electronics ...	101	Williamson Amplification ...	101
		Wilmslow Audio ...	12		

Four of a kind!

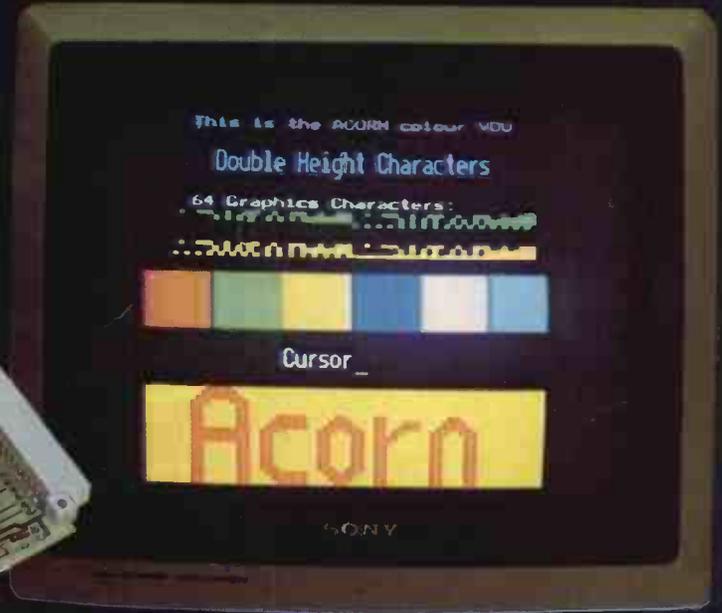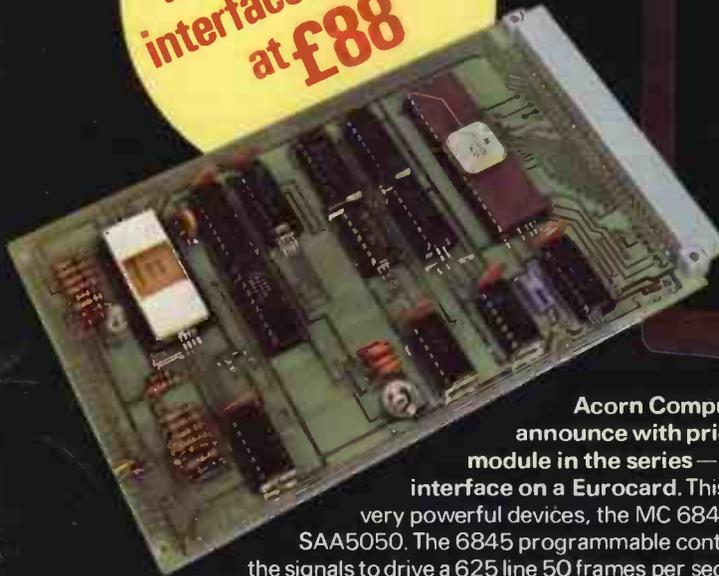The most advanced VDU interface available at £88




Acorn Computers announce with pride the fourth module in the series — a VDU

interface on a Eurocard. This unit uses two very powerful devices, the MC 6845 and the SAA5050. The 6845 programmable controller provides all the signals to drive a 625 line 50 frames per second VDU together with read addresses for the character RAM, the SAA5050 character generator then produces the necessary dot patterns to refresh the VDU. The SAA5050 produces standard teletext characters and graphics and has Red, Green and Blue outputs. This means that the Acorn system will be compatible with CEEFAX, ORACLE and PRESTEL transmissions.


The Acorn VDU module in kit form is complete with sockets and is supplied with listings for programs which set up the 6845, a miniature disassembler which displays 25 hex instructions (double or treble byte) and graphics programs. All these may be loaded and run using the Acorn system 1 monitor.

Options include:- VHF modulator for B.W. domestic T.V. and PAL colour encoder for domestic colour T.V.

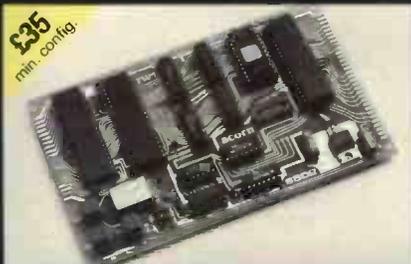- 40 characters per line
- 25 lines per page
- 7-colour graphics and characters
- Upper and lower ASC11
- Teletext graphics font
- Programmable cursor
- Hardware scroll
- Light pen facility
- Memory mapped
- Transparent access
- Single 5V supply



Acorn CPU

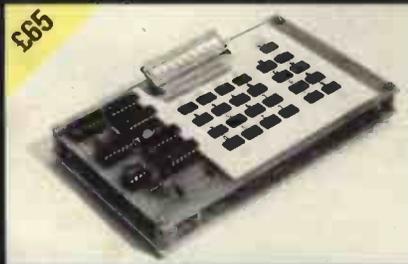

Acorn System 1



Acorn 8K Memory

Order form

Send to: Acorn Computers Ltd., 4a Market Hill, Cambridge, Cambs.

- Acorn controller @ £35.00 plus VAT 5.25
 Microcomputer @ £65.00 plus VAT 9.75
 Assembled
 Microcomputer @ £79.00 plus VAT 11.85
 Memory @ £95.00 plus VAT 14.25
 Memory assembled @ £100.00 plus VAT 15.00
 V.D.U. @ £88.00 plus VAT 13.20
 V.D.U. assembled @ £98.00 plus VAT 14.70
 V.H.F. Modulator to be announced
 Colour Encoder to be announced

Name _____

Address _____



ACORN COMPUTER

Acorn Computers Ltd., 4a Market Hill, Cambridge.
 Telephone 0223 312772

MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.

Breadboard 1979 is even bigger and better than last year. It's the one show no one should miss!

These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £15.92 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

MAPLIN

ELECTRONIC SUPPLIES LTD

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____


ADDRESS _____

P. E. 1279



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.

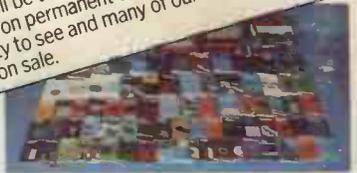Maplin will be there in force with all our projects on permanent demonstration. There will be plenty to see and many of our interesting lines will be on sale.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.