

Australia 95c

New Zealand \$1.10

South Africa 99c

Malaysia \$2.75

PRACTICAL

# ELECTRONICS

JANUARY 1980

55p

## ULTRASONIC CLEANER



*Also in this issue*

**SCRATCH & RUMBLE FILTER**

**SOFTY REVIEW**

AS SEEN IN  
P.E. AUGUST, SEPTEMBER  
OCTOBER 1979

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER —  
JUST CHECK THE SPEC'S.

# COMPUKIT UK101

SAMPLE TAPE  
WITH EXTENDED  
MACHINE CODE MONITOR  
AND DISSASSEMBLER  
INCLUDED FREE

## LOW COST SUPERBOARD IN KIT FORM

The CompuKit UK101 has everything a one board 'superboard' should have.

- ★ Uses ultra-powerful 6502 microprocessor
- ★ 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- ★ 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs
- ★ Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen
- ★ Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF
- ★ Fully stabilised 5V power supply including transformer on board
- ★ Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder
- ★ 4K user RAM expandable to 8K on board £49 extra
- ★ 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller (Ohio Scientific compatible)
- ★ 6502 machine code accessible through powerful 2K machine code monitor on board
- ★ High quality thru plated PCB with all IC's mounted on sockets
- ★ Professional 52 Key keyboard in 3 colours — soft ware polled meaning that all debouncing and key decoding done in software



\*8K Microsoft Basic means conversion to and from Pet, Apple and Sorcerer easy. Many compatible programs already in print.  
**SPECIAL CHARACTERS**  
@ Erases line being typed, then provides carriage return, line feed.  
Erases last character typed.  
CR Carriage Return — must be at the end of each line.  
: Separates statements on a line.  
CONTROL/C Execution or printing of a list is interrupted at the end of a line. "BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.  
CONTROL/O No outputs occur until return made to command mode. If an input statement is encountered either another CONTROL/O is typed, or an error occurs.  
? Equivalent to PRINT

Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

KIT ONLY **£219** + VAT including RF Modulator & Power supply.  
**Absolutely no extras.**

Available ready assembled and tested, ready to go for  
**£269** + VAT

**COMMANDS**  
CONT LIST NEW NULL RUN  
**STATEMENTS**  
CLEAR DATA DEF DIM END FOR  
GOTO GOSUB IF GOTO IF THEN INPUT LET  
NEXT ON GOTO ON GOSUB POKE PRINT REAC  
REM RESTORE RETURN STOP  
**EXPRESSIONS**  
**OPERATORS**  
+ \* / NOT AND OR >> << > < = > < = RANGE 10 32 to 10 + 32  
**VARIABLES**  
A B C Z and two letter variables  
The above can all be subscripted when used in an array. String variables use above names plus \$ e.g AS

**FUNCTIONS**  
ABS(X) ATN(X) COS(X) EXP(X)  
LOG(X) PEEK(I) POS(I) RND(X)  
SPC(I) SQR(X) TAB(I) TAN(X)  
FRE(X) INT(X)  
SGN(X) SIN(X)  
USR(I)  
**STRING FUNCTIONS**  
ASC(X) CHR\$(I) FRE\$(X) LEFT\$(X,I)  
RIGHT\$(X,I) STR\$(X)  
LEN\$(X) MID\$(X,I,J)  
VAL\$(X)

## COLOUR ADD-ON CARD AVAILABLE SOON

Enables you to choose your foreground the background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form.

## THE ATARI VIDEO COMPUTER SYSTEM £138 + VAT



Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges!

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous. You'll have thrill ater thrill, whether you're in the thick of a dogfight, screeching around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on color TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available. All at £13.90 each + VAT  
Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score\*, Space War, Sky Diver, Air Sea Battle Codebreaker\*, Miniature Golf

Extra Paddle Controllers—£14.90 + VAT  
\*Keyboard Controllers—£16.90 + VAT

## video 100

12" BLACK & WHITE  
LOW COST VIDEO  
MONITOR



- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Compatible with many computer systems
- Solid state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

Only **£79** + VAT

## SHORT C12 CASSETTES FOR COMPUTER PROGRAMMES 10 for £4.00



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CARD or AMERICAN EXPRESS number.  
CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G

Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday

★ NOW OPEN ALL DAY SUNDAY — For Shop Sales Only ★

Close to New Barnet BR Station — Moorgate Line.

**COMP** COMPUTER COMPONENTS

(Part of the Compsshop Ltd. Group)



# PRACTICAL ELECTRONICS

VOLUME 16 No. 1 JANUARY 1980

---

## CONSTRUCTIONAL PROJECTS

<b>SCRATCH AND RUMBLE FILTER</b> by <i>R. A. Penfold</i>	22
Reduce turntable and record surface noise	
<b>ULTRASONIC CLEANER</b>	41
Cavitation cleaning for small objects	
<b>SCINTILLATING PENDANT</b> by <i>Owen Bishop</i>	48
Electronic jewellery	
<b>R/C SERVO TESTER</b> by <i>C. R. Francis B.Sc.</i>	50
Provides 0.5A/5V for miniature servo testing	
<b>EPROM PROGRAMMER—2</b> by <i>A. A. Berk B.Sc., Ph.D.</i>	55
Construction and interfacing	

## GENERAL FEATURES

<b>SEMICONDUCTOR UPDATE</b>	26
8294, 2920, SL446A, SL441A	
<b>SOFTY REVIEW</b> by <i>A. A. Berk B.Sc., Ph.D.</i>	27
MPU development tool under the microscope	
<b>INGENUITY UNLIMITED</b>	35
Simple Autofade—R/C Servo—Car Burglar Alarm—Phased White Noise— Glow Plug Supply—Disco Cross-Fader—Low Pass Filter	
<b>WIEGAND EFFECT</b> — <i>B. Dance M.Sc</i>	39
New vehicle ignition technique	
<b>SWITCHING REGULATORS</b> by <i>D.L. H. Smith</i>	64
Theory and suggested circuits	
<b>CALCULATOR CHIPS AS LOGIC DEVICES</b> by <i>P. A. Birnie</i>	69
Circuits using the G.I. C683	

## NEWS AND COMMENT

<b>EDITORIAL</b>	17
<b>MARKET PLACE</b>	18
New products	
<b>SPACEWATCH</b>	32
Pioneer II, Magnetic Field, Tailpiece	
<b>SEIKO WATCH OFFER</b>	34
<b>INDUSTRY NOTEBOOK</b>	47
Inside industry	
<b>PATENTS REVIEW</b>	62
<b>READOUT</b>	63
A selection of readers' letters	
<b>NEWS BRIEFS</b>	66, 71
<b>COUNTDOWN</b>	71


OUR FEBRUARY ISSUE WILL BE ON SALE FRIDAY, 11 JANUARY 1980  
(for details of contents see page 33)

---

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.





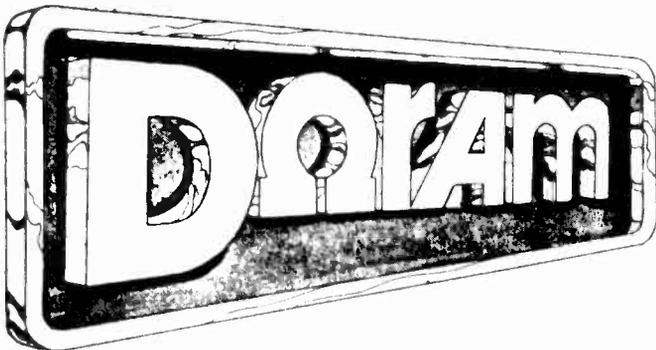

## BACK IN BUSINESS

DORAM ELECTRONICS LTD, a name well known in the home electronics market, are back in business under new management. We aim to combine our many years experience supplying components worldwide with personal service to our new customers.

### NEW PROJECT PACKS:

- + Universal Digital – This versatile unit can replace analogue meters with an fsd from 1 to 100 V or 10mA to 1 Amp. Three 7-segment LED display. **£14.65**
- + Touch Tuning – Can be used with most varicap tuned front ends to select up to 9 pre-set channels. Digital channel display. **£17.80**
- + DJ Killer – Detects the sound of a voice on the radio and cuts off the audio until music is transmitted. **£7.65**

*VAT inclusive prices. Postage add 40p*

**COMPONENTS** We stock a large range of TTL, CMOS, Linear and Microprocessor IC's, plus Transistors, Diodes, Resistors and Capacitors etc.

**PROJECT PACKS** We can supply 'Project Packs' containing all the electronic components, PCB and instructions for over 100 different magazine projects. These range from simple circuits suitable for the beginner to very advanced designs, like our user-programmable TV GAMES COMPUTER system.

**PRICE LIST** For our new Price List send a large SAE to :  
Doram Electronics Ltd., Dept PE, Fitzroy House, Market Place,  
Swaffham, Norfolk. PE37 7QH.  
Tel: Swaffham (0760) 21627. Telex: 817912

A DE BOER COMPANY

START 1980 WITH

# AURA SOUNDS

the **WERSI** specialist

Enjoy the long winter evenings with  
KITS KITS KITS KITS  
something for everyone

**ORGANS, PIANOS, MIXERS  
SYNTHESISERS, RHYTHM UNITS**

Visit one of our showrooms at  
**14-15 Royal Oak Centre, Purley  
(01 668 9733)**

OR

**17 Upper Charter Arcade, Barnsley  
(0226 5248)**

or send £1 for our literature

I enclose £1 for the WERSI literature

NAME.....

ADDRESS .....

.....

.....

.....

### PE PHASER UNIT P.E. APRIL 1979

A superb six stage phaser that really gives your guitar lift off. Equals the best commercial models. Uses latest FET op-amps. Glassfibre p.c.b.

COMPLETE KIT OF ALL PARTS AS SPECIFIED..... **£15.95\***

- Pack 1. All semiconductor devices..... **£6.00\***
- Pack 2. Resistors, capacitors & preset pot..... **£3.75\***
- Pack 3. Footswitch, jacks, pot, knob, printed circuit & hardware..... **£4.25\***
- Pack 4. Diecast box and feet..... **£2.00\***

Separate parts: TL062 80p, BF245B 50p, PCB £1.50, 8 pin sockets (not included in kit) 21p each.

DESIGNER  
APPROVED KITS

### PE SUSTAIN UNIT P.E. OCT. 1977

Superb quality, low noise, low distortion sustain unit equal to the very best commercial models. Suits all guitars. Glassfibre p.c.b.

COMPLETE KIT OF ALL PARTS AS SPECIFIED..... **£7.95\***

- Pack 1. Resistors, capacitors & p.c.b..... **£1.75\***
- Pack 2. All semiconductor devices..... **£1.75\***
- Pack 3. Footswitch, jacks, pot, knob, and battery clip..... **£2.75\***
- Pack 4. Diecast box and feet..... **£2.00\***

Separate parts: XC5053R 50p, RPY58A 75p, Printed circuit board 95p, Footswitch £1.50 each.

ORION  
AMPLIFIER

Complete set of semiconductors..... **£9.75**  
Quality glass fibre p.c.b., printed with component locations..... **£3.50**

PE TV SOUND  
SEPARATOR

Complete set of semiconductors..... **£2.30**  
High quality glass fibre p.c.b..... **£1.50**  
Murata filters: SFE6.0MA 50p, CDA6.0MC 50p.

### PE FUZZ UNIT

**STOP  
PRESS!**

This is the Fuzz unit you have been waiting for! Smooth, clean tone with low noise and low current drain. Uses glassfibre p.c.b. and latest FET op-amp.

COMPLETE KIT OF ALL PARTS AS SPECIFIED **£7.95**

POSTAGE & PACKING 15p per order. Orders over £5.00 post free.  
All devices are top grade, brand new and to full manufacturers spec.  
Send S.A.E. for our data sheet and price list of Ferranti semiconductors.

**PRICES DO NOT INCLUDE VAT.** Add 15% to all prices.

MAIL ORDER ONLY  
CALLERS BY APPOINTMENT

**DAVIAN ELECTRONICS**  
13 DEEPDALE AVENUE, ROYTON, OLDHAM OL2 6XD.

# SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE EQUIPMENT AT INCOMPARABLE PRICES

## STANDARD CENTAUR 100W

£309 incl. of carr. & VAT Deposit £62.00  
12 months @ £24.47 or 24 months @ £14.19

## SUPER CENTAUR 200W

£366 incl. of carr. & VAT Deposit £74.00  
12 months @ £28.94 or 24 months @ £16.78

## GXL 200W

With Twin 200 Watt Cabinets

£470 incl. of carr. & VAT Deposit £94.00  
12 months @ £37.27 or 24 months @ £21.60

## GXL WITH PDF BINS (illus)

£502 incl. of carr. & VAT Deposit £102.00  
12 months @ £39.66 or 24 months @ £23.00


## CUSTOM CENTAUR 400/600W WITH FOUR PDF 100A BINS

£833 incl. of carr. & VAT Deposit £167.00  
12 months @ £66.03 or 24 months @ £38.28

## CENTAUR

STEREO DISCOS  
C/W LIGHT SHOW & DISPLAY  
TWIN LOUDSPEAKERS & LEADS  
100W-600W

20% DEPOSIT CREDIT TERMS

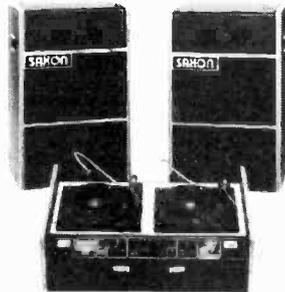

GXL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Bass/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

**JUST PLUG IN AND GO!!**  
SEND TODAY FOR YOUR FREE BROCHURE

## MINI DISCO 100 WATT

MONO SYSTEM WITH LOUDSPEAKERS  
£229.00 incl. of carr. & VAT Deposit £46.00  
12 months @ £18.13 or 24 months @ £10.52

## P.A. SYSTEMS

2 YEAR GUARANTEE  
100 WATT incl. of carr. & VAT **£207.00**

12 months @ £16.35 or 24 months @ £9.49 Deposit **£42.00**

- ★ Four Mixing Inputs
- ★ Bass & Treble Controls
- ★ Twin Piezo Horn Columns

200 WATT incl. of carr. & VAT **£309.00**

12 months @ £24.47 or 24 months @ £14.19 Deposit **£62.00**

## AMPLIFIER UNITS ONLY

AP100 AMPLIFIER **£56.92** + Carr. £1.50 incl. of VAT

- ★ 4 Mixed inputs
- ★ Bass/Treble Controls
- ★ Vynide Case
- ★ 100 Watts Output

AP200 AMPLIFIER **£102.92** + Carr. £1.50 incl. of VAT

- ★ Six Mixed inputs
- ★ Three Sets Bass/Treble
- ★ 200 Watts Output
- ★ Slave Socket



## NEW SAXON KLAXON

UK Police Hawaii 50  
US Police Destroyer  
Four Sirens in one package **£20.12** incl. of VAT  
Individual Sirens **£8.62**




## NEW SAXON SMASH

ALIEN VOICE SIMULATOR  
Add a new dimension to your disco with this press button effect unit  
Insert between mic & amp **£8.62**


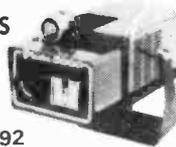
## PLUTO PROJECTORS

P140 **£44.27**  
150 WATT  
INC WHEEL  
P5000 **£102.92**  
250 watt Q.I. inc Cossette/Wheel  
(Full range of wheels - ask for list)



ELECTRECT MIC DI501 **£21.27**  
TOP QUALITY UNIT + VAT £2.31

ECM105 LOW COST ELECTRECT CONDENSER MIC + VAT 62p **£5.75**

MELOS CASSETTE ECHO-REVERB UNIT - Twin input VARIABLE SPEED & DEPTH **£74.75**

## AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers



SA308 8 ohms 30W 45V **£12.36**  
Supply for 2 modules **£13.68**  
SA604 4 ohms 50V **£16.67**  
Supply for 1 or 2 modules **£17.19**  
SA608 8 ohms 60W 65V **£17.82**  
Supply for 1 or 2 modules **£17.19**  
SA1204 4 ohms 120W 75V **£20.12**  
Supply for 1 module **£17.19**  
SA1208 8 ohms 120W 95V **£24.15**  
Supply for 2 modules **£28.46**

## DISCO MIXERS - COMPLETE OR MODULAR



### MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

### FEATURES INCLUDE:

Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.

COMPLETE MIXERS (with case)  
Mono mains **£45.75** + £3.66  
Stereo main **£73.31**

MODULES  
Mono module **£31.62**  
Stereo module **£43.12**  
Panel **£4.54**  
Kit of knobs/sockets etc **£6.32**

## D.I.Y. MODULES FOR P.A. SYSTEMS

### MONO/STEREO

Input Modules  
Mono PCB only **£7.47**  
Stereo PCB only **£12.07**  
Mono C/W Front panel **£10.92**  
Stereo C/W Front panel **£15.81**  
Mixer/Monitor Modules  
Mono PCB only **£7.47**  
Stereo PCB only **£12.07**  
Mono C/W Front panel **£10.92**  
Stereo C/W Front panel **£15.81**

Power supply to suit **£10.92**  
send for full details.



Make your own mixer Mono/Stereo up to 20 channels accept all inputs available as PCB only or complete on front panels

## SOUND-TO-LIGHT UNITS



3 CHANNEL - 3kW **£33.92**

- Operates from 1W upwards
- Bass/middle/treble/master controls + £1 carr. complete

Module only **£22.71**  
Panel **£3.39**

4 CHANNEL - 4 kW SOUNDLIGHT SEQUENCER (illus) **£46.57**

- Dimmer on each channel
  - Automatic sound light level
  - Logic circuitry throughout
- Module only **£30.76** Panel **£3.39**

## MOTOROLA PIEZO HORNS £5.46 YES!!

## FUZZ LIGHTS Red, Blue, Yellow, Green £26.22

## HEAVY DUTY SPOT BANKS - MATCHES LOUDSPEAKERS

3 way 600W **£40.82** 4 way 800W **£47.72**

## 100W SPOTS

Red - Blue - Amber - Green **£1.72**

## CABINET FITTINGS

ICI Vynide 50" wide **£4.02m**  
Kick-res grille 50" wide **£4.02m**  
Netlon kick proof 24" wide **£4.02m**  
Corners/feet/recess plates 17p  
Recess handle **52p**  
Bar handles **£2.87**  
Jack plugs/sockets **29p**

## LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) **£50.60**

Large 100W 1 x 12 (65 x 48 x 24) **£62.67**

P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24) **£82.22**

P.A. 2 x 12 200W (100 x 38 x 24) **£119.60**

Disc 2 x 12 200W (80 x 63 x 24) **£103.50**

PDF reflex bin (80 x 40 x 41) **£115.00**

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals

- Use with all types of mixer
- Pan and volume controls
- Send for details **£155.25** Deposit **£31.25**

ABOVE PRICES INCL. OF CARR. & VAT

All prices are inclusive of 15% VAT. Shop premises open Tues to Sat 9 am - 5 pm. Lunch 12.30 - 1.30 pm. Mail order dept open Mon to Fri 10 am - 4 pm. Ring 01-684 6385.

## TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclaycard Number NOT THE CARD.

By Phone You may order COD, Access or Barclaycard. Post & Packing 50p on all orders except where stated.

**SAXON ENTERTAINMENTS**  
327 Whitehorse Road, Croydon, Surrey CR0 2HS.

All Enquiries Large SAE Please Brochures on request

MANCHESTER DISCO CENTRE,  
237 DEANSGATE, MANCHESTER M3 4EN.  
CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY

# First the EuroBreadBoard Now the EuroSolderBoard

**World's best Breadboard buy** **Accepts all D.I.L. I.C. packages**

**Free!**

**Indispensible for the professional** **Ideal for the beginner**

## Design on a EuroBreadBoard — Install on a EuroSolderBoard

### First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2 including 1 or 2 EuroSolderBoards FREE

### Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's or FREE with every EuroBreadBoard)

### And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,  
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.

Please send me:—

- 1 EuroBreadBoard (plus 1 free EuroSolderBoard) @ £ 6.20  Please
- or 2 EuroBreadBoards (plus 2 free EuroSolderBoards) @ £11.70  Tick
- or 3 EuroSolderBoards @ £ 2.00
- or 1 EuroSolderSucker @ £ 7.25

All prices are applicable from Jan. 1st 1980 and include VAT & PP but add 15% for overseas orders.

Name . . . . .

Company . . . . .

Address . . . . .

. . . . .

Tel. No . . . . .

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

# Now, complete your system!



### Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system 4.6 ch mono inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU E89 70.


### The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor. 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £12.80. or our fabulous Pizzo Horns which handle a 5K - 20K frequency range in any PA system up to 100W (No X over required) and cost only £6.32 each.



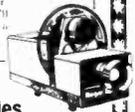
### Projectors

Come and see our specially selected projectors from E50.60 (Square Multi-flect 150) to E83.37 (Tutor IIE DDU) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



### Turntables

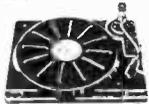

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive. ONLY £28 75

**Ropelights** Great effect at discos. 7 metres long. Multiway connectors. 4 channel £46.00 (inc. pack of spare bulbs)

### Buigin Octal plugs and sockets

There's always hundreds of Buigin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET. £0.69 P551 PLUG £1.72



### Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

Multiway Cables  
4 core (6A) 63p/metre  
5 core (6A) 78p/metre  
6 core (6A) 92p/metre

**Roger Squire's**

ALL SHOPS OPEN TUE-SAT. LATE NIGHT WED (UP TO 8 PM)

**PERSONAL CALLERS ONLY**

**DISCO CONIPLES**

176 Junction Road, N19, 50yds Tufnell Park Tube Station (Near St. George's) 1 mile from end of M32

125 Church Road, Rixfield (Near St. George's) 1.5 miles from City Centre

251 Deanshill, 3, 15 mins from City Centre


1 Queen Margaret Road (off Oxman Margaret Drive) Kelynside 20, just behind the BBC. Tel: 041 946 3303

LONDON Tel: 01 272 7474  
BRISTOL Tel: 0272 550550  
MANCHESTER Tel: 061 831 7676  
GLASGOW Tel: 041 946 3303

# BI-PRE-PAK

## NICKEL-CADMIUM BATTERIES AT LESS THAN HALF-PRICE

BY A WORLD  
FAMOUS  
MANUFACTURER

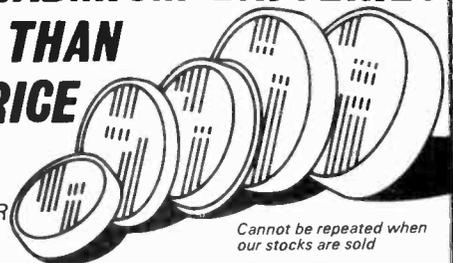

Cannot be repeated when our stocks are sold

Type	Capacity mAh	Voltage	Charge rate mA/12hrs	Dia. & thickness mm	Price inc. VAT
NC20	200	1.24	20	24.8 x 7.4	45p
NC28	280	1.24	28	34.4 x 5.3	60p
NC50	500	1.24	50	34.3 x 9.5	80p
NC90	900	1.24	90	50.5 x 8.3	1.20p
NC175	1,750	1.24	175	50.7 x 14.9	1.75p

- IDEAL POWER-SOURCE FOR MODELLERS, ETC.
- Brand new factory surplus stock
- Indefinite shelf life.
- Fully guaranteed.
- Supplied uncharged for safety.

High capacity for small size, wide operating temperature range and low internal resistance. Very simple charging circuit required.

### AND 2 SPECIAL PACK OFFERS

1. 100 mixed untested germanium and silicon PNP/NPN transistors (inc. P/P & VAT) £1.75
2. The famous LM380 (inc. P/P & VAT) 99p.

**TO ORDER: Cash with order. Minimum order for batteries value £3 plus 30p post & packing UK. Orders over £10 carriage paid UK. TO PAY BY ACCESS OR BARCLAYCARD just tell us your number.**

## BI-PRE-PAK LTD

(PE180) WEST RD., WESTCLIFFE-ON-SEA, ESSEX, SS0 9DF.  
Telephone 03708 5542

# MORE BIG VALUE FROM YOUR TANDY STORE

## 1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy:  $\pm 3\%$  full scale on DC ranges,  $\pm 4\%$  on AC ranges. Complete battery. 22-027. REG. PRICE

**£6.95**



## 6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then  $\pm 30$  Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Req. 9V battery. 22-351. REG. PRICE

**£79.95**



## MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1.3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-30 1C-1 megaohm. 0-100-1k-10 1C-100K-3 megaohms. Req. 9V battery. 22-209.

REG. PRICE  
**£29.95**



## TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE **£9.95**



## DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE **£19.95**



## SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**



## AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

## REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.

REG. PRICE **£229.95**



## DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.


REG. PRICE  
**£9.95**



## VARIABLE POWER SUPPLY

Power project boards, IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**

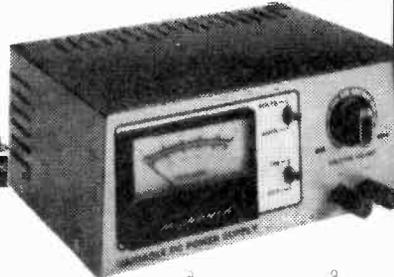

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

# TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.




## TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access, Barclaycard and Trustcard welcome. Prices may vary at individual stores.

# KITS FOR SYNTHESISERS, SOUND EFFECTS

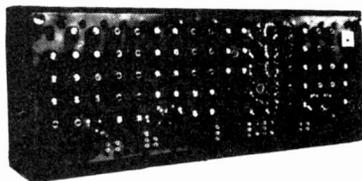

**COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

**LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

## P.E. 128-NOTE PROGRAMMABLE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic component kits	KIT 76-5	<b>£28.92</b>
Set of PCBs & layout charts	KIT 76-6	<b>£6.86</b>
Set of text photocopies		<b>£1.36</b>

## P.E. 16-NOTE PROGRAMMABLE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic component kits	KIT 86-3	<b>£22.90</b>
Set of PCBs	KIT 86-4	<b>£5.09</b>
Set text photocopies		<b>£1.84</b>

## P.E. STRING ENSEMBLE

A multivoiced string instrument synthesiser.

Set of basic component kits	KIT 77-6	<b>£68.70</b>
Set of PCBs & layout charts	KIT 77-7	<b>£24.19</b>

## P.E. JOANNA PLUS ORGAN VOICING

A modified version of the P.E. 5-octave piano that retains all the original facilities and also includes switchable organ voicing circuitry.

Set of basic component kits	KIT 71-5	<b>£90.36</b>
Set of PCBs & layout charts	KIT 71-6	<b>£29.81</b>
"Sound Design" booklet		<b>£1.00</b>

## ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic components	KIT 80-6	<b>£110.39</b>
5-octave set of PCBs (as published)	KIT 80-7	<b>£26.02</b>
Additional 3-octave extension basic parts	KIT 80-5	<b>£46.05</b>
Additional 3-octave set of PCBs (as published)	KIT 80-8	<b>£9.55</b>
Set of text photocopies		<b>£1.81</b>

## P.E. MINISONIC MK2 SYNTHESISER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available)	KIT 38-23	<b>£87.06</b>
Set of PCBs (incl. layout charts)	KIT 38-24	<b>£9.87</b>
"Sound Design" booklet		<b>£1.00</b>

## P.E. SYNTHESISER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Main Unit basic component kits	KIT 23-27	<b>£86.95</b>
Main Unit set of PCBs & layout charts	KIT 23-28	<b>£14.48</b>
Keyboard Unit basic component kits	KIT 23-29	<b>£62.06</b>
Keyboard Unit set of PCBs & layout charts	KIT 23-30	<b>£8.41</b>
Main Unit set of text photocopies		<b>£5.91</b>
Keyboard Unit set of text photocopies		<b>£2.30</b>

## ELEKTOR FORMANT SYNTHESISER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic component kits	KIT 66-12	<b>£193.88</b>
Set of PCBs (as published)	KIT 66-13	<b>£53.92</b>
Set of text photocopies		<b>£7.83</b>

## P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic parts with foot switches	KIT 42-1	<b>£8.45</b>
Basic parts with panel switches	KIT 42-2	<b>£5.55</b>
PCB & layout chart	PCB 42A	<b>£1.57</b>
Text photocopy		<b>28p</b>

## ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic component kit	KIT 78-1	<b>£49.99</b>
Main unit PCB (as published)	PCB 9913	<b>£3.69</b>
Extension unit basic component kit	KIT 78-2	<b>£47.69</b>
Extension unit PCB (as published)	PCB 78B	<b>£1.16</b>
Text photocopy		

## ELEKTOR ANALOGUE REVERB UNIT

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set	KIT 83-1	<b>£29.49</b>
Additional Delay basic components	KIT 83-2	<b>£20.07</b>
PCB (as publ.) to hold both kits	PCB 9973	<b>£4.31</b>
Text photocopy		

## P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic component kits	KIT 85-3	<b>£43.75</b>
Set of PCBs & layout charts	KIT 85-4	<b>£10.82</b>
Set of text photocopies		<b>£2.52</b>

## P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Set of basic components, incl. PCB & chart	KIT 88-1	<b>£10.14</b>
Text photocopy		<b>68p</b>

## ELEKTOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic components	KIT 70-1	<b>£19.11</b>
PCB & layout chart	PCB 70A	<b>£2.66</b>
Text photocopy		<b>67p</b>

## P.E. PHASING UNIT

A simple but effective manually controlled phasing unit.

Set of basic components incl. PCB & chart	KIT 25-1	<b>£3.52</b>
Text photocopy		<b>28p</b>

## PHASING CONTROL UNIT

For use with Phasing Kit 25 to automatically control rate of phasing.

Set of basic components incl. PCB & chart	KIT 36-1	<b>£5.21</b>
Text photocopy		<b>10p</b>

## P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Set of basic components, PCB & chart	KIT 89-1	<b>£3.82</b>
Text photocopy		<b>78p</b>

## P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control of depth.

Set of basic components, PCB & chart	KIT 53-1	<b>£2.76</b>
--------------------------------------	----------	--------------

## ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic components	KIT 82-1	<b>£16.61</b>
PCB (as published)	PCB 9951	<b>£3.29</b>
Text photocopy		

## P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments.

Set of basic components	KIT 56-1	<b>£7.67</b>
PCB & layout chart	PCB 56A	<b>£1.78</b>
Text photocopy		<b>68p</b>

## P.E. SMOOTH FUZZ

Set of basic components, PCB & chart	KIT 91-1	<b>£5.01</b>
--------------------------------------	----------	--------------

## TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Set of basic components, PCB & chart	KIT 54-1	<b>£3.23</b>
--------------------------------------	----------	--------------

## GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.

Set of basic components, PCB & chart	KIT 74-1	<b>£4.97</b>
Text photocopy		<b>39p</b>

## P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, foot switches, PCB & chart	KIT 75-1	<b>£5.84</b>
Basic components, panel switches, PCB & chart	KIT 75-2	<b>£4.08</b>
Text photocopy		<b>38p</b>

## P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control.

Set of basic components, PCB & chart	KIT 51-1	<b>£3.99</b>
--------------------------------------	----------	--------------

## P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played.

Basic components, foot switches, PCB & chart	KIT 58-1	<b>£8.43</b>
Basic components, panel switches, PCB & chart	KIT 58-2	<b>£5.31</b>
Text photocopy		<b>58p</b>

## ELEKTOR WAVEFORM CONVERTOR

Converts a saw-tooth waveform into sinewave, mark-space saw-tooth, regular triangle, or square-wave with variable mark-space ratio.

Basic components, PCB & chart, but excl. sw's.	KIT 67-1	<b>£9.24</b>
--	----------	--------------

## P.E. VOLTAGE CONTROLLED FILTER

Extracted from P.E. Minisonic project.

Set of basic components, PCB & chart	KIT 65-1	<b>£7.88</b>
--------------------------------------	----------	--------------

## P.E. RING MODULATOR

Extracted from P.E. Minisonic project.

Set of basic components, PCB & chart	KIT 59-1	<b>£6.05</b>
--------------------------------------	----------	--------------

## ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic components	KIT 87-1	<b>£4.66</b>
PCB (as published)	PCB 79040	<b>£1.74</b>
Text photocopy		<b>38p</b>

### 10% DISCOUNT VOUCHER (PE 70)

**TERMS:** Goods in current adverts & lists over £50 goods value (excl. P&P & VAT). Correctly coded, C.W.O. U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E. Does not apply to credit card orders.

### ADD: POST & HANDLING

U.K. orders: Keyboards add £2.30 each. Other goods: Under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

### ADD 15% VAT

(or current rate if changed). Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports.

**EXPORT ORDERS ARE WELCOME** but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 25p, other countries send 50p.

**PHONOSONICS · DEPT PE81 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH**

**TERMS: C.W.O. MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)**

# AND OTHER PROJECTS

**PHOTOGRAPHS** in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

**LIST**—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

**OVERSEAS** enquiries for list Europe—send 20p; other countries—send 50p.



## KIMBER-ALLEN KEYBOARDS AND CONTACTS

**KIMBER-ALLEN KEYBOARDS** as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) **£28.80**  
 4 Octave (49 notes) **£32.25**  
 5 Octave (61 notes) **£39.75**

### P.E. NOISE GENERATOR

Extracted from the P.E. Minisonic.  
 Set of basic components.  
 PCB & chart **KIT 60-1 £4.00**

### WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.  
 Set of basic components.  
 PCB & chart **KIT 28-1 £4.68**  
 Text photocopy **28p**

### P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.  
 Set of basic components.  
 PCB & chart **KIT 44-1 £5.24**  
 Text photocopy **49p**

### P.E. ENVELOPE SHAPER WITH VCA

Has an integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.  
 Set of basic components.  
 PCB & chart **KIT 50-1 £7.34**  
 Text photocopy **58p**

### P.E. GENERATOR

An ADSR envelope shaper without VCA, and additional providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.  
 Set of basic components **KIT 63-1 £5.13**  
 PCB & layout chart **PCB 63A £2.00**  
 Text photocopy **58p**

### P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphones etc., to be processed by synthesiser circuits.  
 Set of basic components.  
 PCB & chart **KIT 81-1 £3.23**

### P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.  
 Set of basic components.  
 PCB & chart **KIT 46-1 £16.42**  
 Power Supply components, **KIT 46-2 £6.90**  
 PCB & chart **Text photocopy 97p**

### P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.  
 Set of basic components.  
 PCB & chart, but excl. sw. **KIT 69-1 £8.19**  
 Text photocopy **58p**

### P.E. DYNAMIC RANGE LIMITER

Presets to automatically control sound output levels.  
 Set of basic components.  
 PCB & chart **KIT 62-1 £5.03**

### P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 5-digit counter for 1Hz to 55KHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.  
 Set of basic components **KIT 79-1 £26.45**  
 PCB (as published) **PCB 79A £3.33**  
 Text photocopy **78p**

## INTEGRATED CIRCUITS

301	48p
318	220p
320-15	195p
323	562p
324	87p
341-15	81p
356	101p
709	48p
723	51p
726	1005p
741	24p
748	57p
4001	151p
4007	171p
4011	171p
4013	34p
4016	33p
4017	54p
4024	461p
4046	96p
4049	371p
4066	401p
4069	18p
4081	161p
4136	126p
AM2833	396p
AY-1-0212	617p
AY-1-1320	636p
AY-1-6721/6	188p
CA3046	71p
CA3080	63p
CA3084	209p
FX209	729p
M252	680p
MC3340	150p
MCM6810	670p
RC4195	117p
SA01024	172p
SG3402	262p
TDA1022	582p
TL074	120p
XR2207	420p
ZN425	375p
7400	20p
7402	20p
7404	18p
7413	31p
7420	15p
7447	72p
7472	221p
7473	371p
7474	311p
7489	241p
7490	42p
7493	491p
74121	53p
74123	561p
7805	145p
7808	145p
7812	145p
7815	145p
7818	145p




**PHONOSONICS**

## 24 TUNE DOOR CHIMES

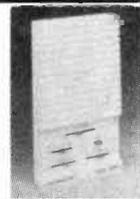**DOOR TUNES £17.13 + VAT.**

Waddington's Videomaster announce a doorbell that doesn't go Brrrring, Ding Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES

**PROGRAMMABLE £29.50 + VAT.**  
**COLOUR CARTRIDGE T.V. GAME.**

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



**EXTRA CARTRIDGES**

**ROAD RACE — £8.87 + VAT.**  
 Grand Prix motor racing with gear changes, crash noises  
**SUPER WIPEOUT — £9.17 + VAT.**  
 10 different games of blasting obstacles off the screen  
**STUNT RIDER — £12.16 + VAT.**  
 Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc  
**NON PROGRAMMABLE TV GAMES**

**6 Game — COLOURSCORE II — £13.50 + VAT.**  
**10 Game COLOUR SPORTSWORLD £22.50 + VAT.**

## CHESS COMPUTERS

**STAR CHESS — £56.09 + VAT.**  
**PLAY CHESS AGAINST YOUR PARTNER.**

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but also each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



**CHESS CHALLENGER 7 — £85.65 + VAT.**  
**PLAY CHESS AGAINST THE COMPUTER.**

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Castling, en passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button. Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.



**ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT.**

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

**OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE**


**CHESS CHAMPION — 8 LEVELS £47.39 + VAT.**  
**CHESS CHALLENGER — 10 LEVELS — £138.70 + VAT.**  
**BORIS — MULTI-LEVEL TALKING DISPLAY £163.04 + VAT.**

## DRAUGHTS COMPUTERS

**CHECKER CHALLENGER 2 LEVELS £43.00 + VAT.**  
**4 LEVELS £78.00 + VAT.**

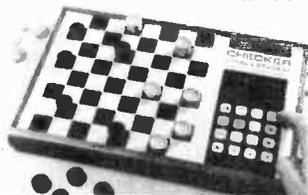**PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER**

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.



## FOR FREE BROCHURES — SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on. Callers welcome at our shop in Welling demonstrations daily - open from: 9am-5.30pm Mon-Sat 9am-1pm Wed. To order by telephone please quote your name, address and Access/Barclaycard number. Postage and Packing FREE.

**AJD DIRECT SUPPLIES LIMITED, Dept. PE12** 102 Bellegrave Road, Welling Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

### SEIKO MEMORY BANK

Calendar watch M354  
Hours, mins, secs.  
Month, day, date in  
12 or 24 hour format  
all indicated continuously.  
Monthly calendar display  
month, year and all dates  
for any selected month over  
80 year period.  
Memory bank function.  
Any desired dates up to 11  
can be stored in advanced.  
2 year battery life.  
Water resistant.  
Metac Price



£79.50

M11

### SEIKO Alarm Chronograph

With WEEKLY Alarm.  
Hours, mins, secs, month,  
date, day, am/pm.  
Weekly alarm - can be set  
for every day at designated  
time e.g. 6.30 am on Mon,  
Wed and Friday.  
Alarm set time displayed  
above time of day.  
Full stopwatch functions,  
laptime, split etc.



£89.95

M10

### SEIKO Melody Alarm Chronograph

Chiming Alarm,  
plus chrono.  
Hours, mins, secs, date,  
day, 24 hour alarm, 12  
hour chronograph, 1/10th  
secs, Laptime, Back light,  
Stainless steel, mineral  
glass.



METAC PRICE  
£92.95

M19

### SEIKO Calculator Watch

Full specification  
calculator with  
memory, plus multi  
function watch.  
Hours, mins, secs,  
day, date, backlight,  
Automatic calendar.  
Long life battery.



£99.95

M27

### CASIO CHRONO 95QS-3LB

Stainless steel case,  
water resistant to 66 feet.  
Hours, mins, secs, am/pm,  
year, month, date, day.  
Auto-calendar  
pre-programmed  
until the year 2029.  
12/24 hour, Stopwatch  
function.  
Range 7 hours, 1/100 sec.  
(Mode) Net time/lap-time/  
1st-2nd place times.  
Dual time function.  
Accuracy 15 secs per month.  
Battery life approx 4 years.



£22.95

M22

### CASIO LADIES 86CL-23B-1

Elegant slim line.  
Stainless steel bracelet,  
fully adjustable.  
Hour, mins, 10 sec symbol  
second by flash, am/pm.  
Month, date, day.  
Auto-calendar preprogrammed  
for 28th day in Feb.  
Accuracy per month 15 secs.  
Battery life approx 15 months.



£29.95

M23

### CASIO F-200 Sports Chrono

Attractive Mans watch  
in black resin with  
mineral glass.  
Hours, mins, secs, am/pm.  
Month, date,  
alpha-numeric day.  
Auto-calendar set  
28th Feb.  
Stopwatch working  
range 1 hour,  
units 1/100 sec. Mode,  
Net Time/lap/time/  
1st-2nd place times.  
Accuracy approx 15 secs  
per month.  
Battery 12 months.



£14.95

M24

### CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs, day,  
and also day, month and year  
perpetual automatic calendar.  
100th sec chronograph to  
7 hours.  
Net time/lap/time/1st  
and 2nd place times. User  
optional 12/24 hr display, 24  
Alarm, User optional,  
hourly chime.  
Backlight, mineral glass,  
stainless steel.  
Water resistant to  
100ft.  
Battery life approx 4 years.



£34.95

M25

### BELTIME Chronograph

(9-Functions)  
Hours, mins, secs,  
day, date, month,  
interchange feature,  
automatic calendar,  
backlight, Net  
time/lap/time.  
Stainless steel bracelet.  
Battery life 1 year.



£14.95

M34

### BELTIME Multi Alarm

29 Functions  
Hours, mins, secs,  
date, day.  
Alarm, chronograph,  
Light.  
Watch 8 functions.  
Alarm 4 functions,  
chronograph 17  
functions.  
Stainless steel  
bracelet.



£29.95

M35

### CASIO F-8C 3 Year Battery life.

Hours, mins, secs,  
am/pm, date, day.  
Auto calendar set  
28th Feb.  
Stopwatch function.  
Accuracy 15 secs per  
month. Battery life  
approx 3 years.



£9.95

M36

### CASIO CALENDAR 200

#### 47CS-23B-1 Black. Stainless steel.

Hours, mins, 10 second  
symbol, second (by flash),  
am/pm. Month, day, date.  
Auto-calendar set from  
1901 to 2009.  
Full month calendar display.  
Dual time function.  
Accuracy 10 secs per  
month. Battery life  
approx 15 months.



£59.95 M37

### MELODY Multi Alarm Chronograph

Hours, mins, secs,  
Day, Date, Count-  
down alarm,  
Dual time zone,  
1/100th sec  
stopwatch.  
Lap/split time,  
1st and 2nd place  
times, Melody test  
function.



£26.95

M30

### DUAL TIME-ALARM CHRONOGRAPH

Incorporating module  
of world famous  
Japanese watch  
manufacture.  
Hours, mins, secs,  
days of week, month,  
day and date,  
24 hour alarm,  
12 hour chronograph,  
1/10th secs,  
lap time, Back light,  
stainless steel case  
and bracelet,  
Mineral glass,  
Battery hatch,  
long life battery.



£35.00

M12

### PICOQUARTZ Microprocessor Alarm Chronograph

Multilanguage-day of  
the week can be set  
to English, French,  
German, Italian or  
Spanish.  
Chime - every full  
hour combined with a  
response signal,  
beeping at every  
pressing of the  
functions.  
Can be switched off.  
12-24 hour format.  
Backlight.  
Chrono - 1, full scale  
chrono with lap,  
counting hours upto  
24 hrs. Mins, secs,  
1/100th secs.  
Two Alarm systems.  
Two time zones.



£37.95

M32

### SEIKO CHRONOGRAPH

Hours, mins, secs  
and day of the week.  
Month date and  
day of the week.  
Stopwatch display -  
Hours, mins, secs  
up to 12 hours  
(mins, secs, 1/100 secs  
up to 20 minutes).  
Lap timing,  
Continuous time  
measurement of two  
competitors.  
Stainless steel,  
mineral glass.



£56.00

M33

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

### QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M1

### SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins., secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

### QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold!  
Guaranteed same day despatch.



M3

### QUARTZ LCD ALARM 7 Function

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

### MULTI ALARM 6 Digits 10 Functions

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65

M5



### FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags. 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet. Guaranteed same day despatch

£22.65

M6



### SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags. 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£27.95

M7



### ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs.
- in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£29.65

M8



### SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65

Guaranteed same day despatch.

M9



### QUARTZ LCD Ladies Day Watch

Only 25 x 20mm and 6mm thick. Hours, minutes, seconds, day, date, backlight and auto calendar. Elegant metal bracelet in silver or gold fully adjustable to suit very slim wrists. State colour preference.

£9.95

Guaranteed same day despatch.

M15



### QUARTZ LCD Ladies Fashion Watch

Elegant bracelet in bronze/gold finish or silver colour. Hours, mins, secs, day, date, backlight and auto calendar. Adjustable for the slimmest of wrists. State colour preference.

£14.95

Guaranteed same day despatch

M17



### QUARTZ LCD Ladies Cocktail Watch

Highly functional watch which also suits those special occasions. Beautifully designed with a very thin bracelet which retains strength as well as elegance. Hours, mins, secs, day, date, backlight and autocalendar. Bracelet fully adjustable to suit slim wrists. State gold or silver finish.


£19.95

Guaranteed same day despatch

M18



### HANIMEX Electronic LED Alarm Clock

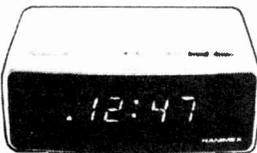

Features and Specification  
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm)  
Weight 1.43 lbs (0.65 kg) AC power 220V.

£10.20 Thousands sold!

Mains operated.

Guaranteed same day despatch.

M13

### EXECUTIVE ALARM WATCH

6 Functions plus Alarm: Conference signal, 5 minute snooze alarm. Conference signal sounds 4 secs., before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins., after main alarm and is always preceded by the conference signal.

£14.95

M60



### MACY QUARTZ ANALOGUE

Automatic Calendar Day and Date infinite bracelet. This mans watch has elegance as well as the robust appearance provided by a watch with traditional features. Accuracy is provided by a quartz crystal powered by a long life miniature battery.

£24.95

M21



Metac price breakthrough for an Alarm Chronograph with Dual Time only

£18.95

- OUTSTANDING FEATURES**
- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
  - **CALENDAR FUNCTIONS** include the date and day in each time zone.
  - **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
  - On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
  - **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch. M16



#### HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

#### Metac Wholesale:

Trade enquiries - send for a complete list of prices for all the goods advertised plus many more not shown also minimum order details.

Telephone orders: Credit card customers can telephone orders direct to Daventry (03272) 76545 or Edgware Rd. 01-723 4753 24 hours a day.



Service Enquiries 03272-77659

CALLERS WELCOME Shops open 9-30am-6.00

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

# All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

## ..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

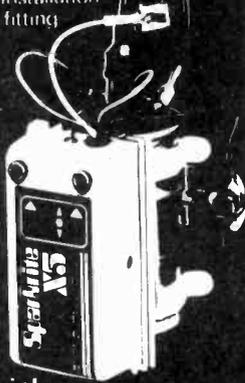There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems function light, and security changeover switch. Will work all rev counters.



**Fits all 12v negative earth vehicles with coil/distributor ignition up to 8 cylinders.**

THE KIT COMPRISES EVERYTHING NEEDED. Die pressed case. Ready drilled, aluminum extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

# Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE180  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name \_\_\_\_\_  
Address \_\_\_\_\_

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D

I enclose cheque/PO's for

X5KIT £16.95

£

Cheque No

ACCESS OR BARCLAY CARD No

Send SAE if brochure only required



From Kam  
Circuits  
a new p.c.b.  
battery  
operated  
Mini-Drill

Available with or without a portable stand this new powerful precision drill will enable you to drill holes in p.c.b.'s, metal, wooden panels or anywhere that small holes are needed. Bit sizes 0.6mm, 1.0mm and 1.5mm.

Power supply 4 x UM3 batteries.

Price without stand £19.02 (inclusive of p.p. and VAT).

Stand price £8.63 (inclusive of p.p. & VAT).

Write for technical brochure now:




Kam Circuits Limited

Porte Marsh Road, Calne, Wilts. SN11 9BW

Telephone: (0249) 815262 Telex: 444218

# ALCON

BRING YOU THE NEW CHINAGLIA

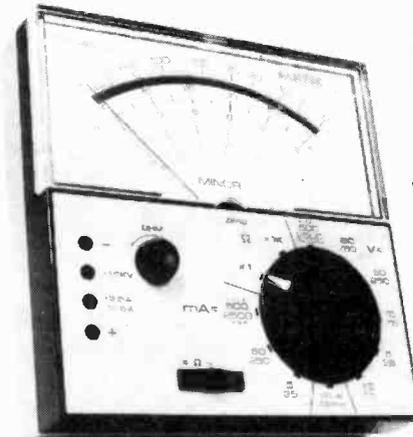

MINOR  
POCKET  
MULTIMETER

THE  
PROFESSIONAL  
SOLUTION  
TO  
GENERAL  
MEASUREMENT  
PROBLEMS

£32.50 inc. VAT.

The best instrument for the workshop, school, toolbox, T.V. shop and anywhere accurate information is needed quickly and simply.

IT OFFERS:

- ★ Single-knob range selection
- ★ 110° Full-view mirror scale and fine line pointer
- ★ Clear unambiguous scales
- ★ A well-damped cylindrical magnet movement with resilient bearings
- ★ 31 ranges providing coverage from 150mV to 1.5kV d.c.; 7.5V to 1.5kV a.c.; 50µA to 2.5A d.c.; 25mA to 12.5A a.c.; 10kΩ and 10MΩ resistance and six signal level ranges.
- ★ Accuracy ±2.5% d.c., ±3% a.c. and 2% resistance.

For details of this and other exciting Alcon Instruments please write or phone:-

# ALCON

 Instruments Ltd.

19 MULBERRY WALK, LONDON SW3 6DZ TEL: 01-352 1897

# STARCHASER


## THE NEW FOUR CHANNEL LIGHTING CONTROLLER FROM TUAC

# 4000




- 4 channels 750W each
  - over 1000 different sequence patterns and effects
  - 3 alternative sound triggers
  - A.G.C.
  - simulated strobing
  - zero reference triac firing
  - superb TUAC quality and reliability
- £99.00 inc. VAT.**
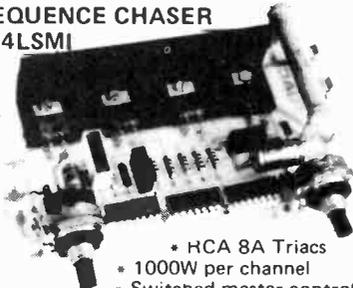
### 4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER — 4LSMI



- RCA 8A Triacs
  - 1000W per channel
  - Switched master control
- for sound operation from 1/2W to 125W • Speed control for fixed rate sequence from 8 per minute to 50 per second • Full logic integrated circuitry with optical isolation for amplifier protection. **£22.95**
- Model 501 500W per channel, as above without sound triggering. **£14.95**

### 3 CHANNEL LIGHT MODULATOR —SILMB

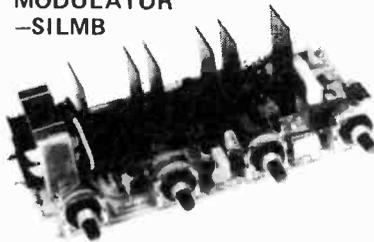

- RCA 8A Triacs
  - 1000W per channel
  - Each channel fully suppressed and fused
  - Master control to operate from 1W to 125W
  - Full Wave control
- £22.95**

### ADD SEQUENCE CHASING & DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR — 3SDMI



- Speed Control 3 per minute to 10 per second
  - Full logic integrated circuitry
  - Dimmer control to each channel
- £17.50**

Front panels for lighting effects modules (complete with switches, neons & knobs)



For S1LMB  
Size: 8" x 4 1/2"  
**£9.00**




4LSMI  
Size: 6 1/2" x 4 1/2"  
**£7.75**



Send for our free 28 page catalogue, please enclose a stamp.

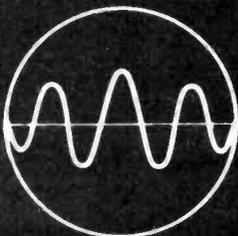S1LMB Combined with 3SDMI. Size: 9" x 4 1/2". **£10.00**



# TUAC

TUAC Ltd., 119/121 Charlmont Road, SW17.  
Tel: 01-672 3137/9080  
**PRICE INCLUDES VAT. P+P FREE (at 1.10.79)**

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD. 119/121 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders. Phone 01-672 9080.

### TUAC MAIN DISTRIBUTORS (Callers Only)

Birmingham, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).  
Canterbury, Socodi, 9 The Friars, (Tel: 60948).  
Crewe, Cookies Disco Centre, 126/128 West Street, (Tel: 4739).  
Exeter, Electrosure, Fore Street, (Tel: 56687).  
London, Garland Bros., Deptford Broadway, (Tel: 01-692 4412).  
London, Session Music, 163 Mitcham Road, Tooting, (Tel: 01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.  
Luton, Luton Disco Centre, 88 Wellington Street, (Tel: 411733).  
Manchester, A1 Music, 88 Oxford Street, (Tel: 236 0340).  
Middlesbrough, Salcoglen, 43 Borough Road, (Tel: 242851).  
Southampton, Memhouse, 82 St. Mary Street, (Tel: 28028).



Send your orders to:-

DEPT. PE1, PO BOX 6, WARE, HERTS. Tel: 0920-3182

Visit our NEW shop: 3 BALDOCK ST., WARE, HERTS. Telex: 817861

EXPERIMENTOR BREADBOARDS


FROM 

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size. All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


**EXP.325.** The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin IC's. **ONLY £1.70**



**EXP.350.** £3.73  
270 contact points with two 20-point bus-bars.

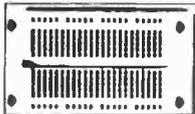

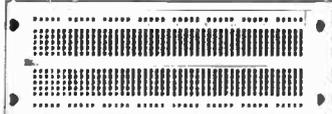**EXP.300.**  
550 contacts with two 40-point bus-bars. **£6.13**



**EXP.650** for Micro-processors. **£3.83**



**EXP.4B.**  
More bus-bars. **£2.45**



ALL EXP.300 Breadboards mix and match with 600 series.

ANTEX IRONS

- 1943 15 watt quality soldering iron with 3/32" bit **£4.88**
- 1947 Replacement element for 1943 **£2.18**
- 1944 Iron coated bit 3/32" for 1943 **£0.53**
- 1945 Iron coated bit 1/8" for 1943 **£0.53**
- 1946 Iron coated bit 3/16" for 1943 **£0.53**
- 1948 18 watt iron with iron coated bit **£4.59**
- 1952 Replacement element for 1948 **£2.18**
- 1949 Iron coated bit 3/32" for 1948 **£0.53**
- 1950 Iron coated bit 1/8" for 1948 **£0.53**
- 1951 Iron coated bit 3/16" for 1948 **£0.53**
- 1931 X25 25 watt iron, ceramic shaft and another shaft of stainless steel to ensure strength **£4.88**
- 1935 Replacement element for 1931 **£1.84**
- 1932 Iron coated bit 1/8" for 1931 **£0.57**
- 1933 Iron coated bit 2/16" for 1931 **£0.57**
- 1934 Iron coated bit 3/32" for 1931 **£0.57**
- 1953 SK1 soldering Kit - contains 15 watt soldering iron with 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to Solder' **£6.38**
- 1939 ST3 iron stand made from high grade bakelite chrom plated steel spring, suit all models - includes accommodation for six bits and two sponges to keep the iron bits clean **£1.86**
- 1724 Model MLX as X25 iron but 12 volts **£5.29**

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA110	£0.09	BY100	£0.25	BY211	£0.52	OA90	£0.11
AA120	£0.09	BY101	£0.25	BY212	£0.46	OA91	£0.11
AA129	£0.09	BY105	£0.25	BY213	£	OA95	£0.11
AA30	£0.10	BY114	£0.25	BY216	£0.47	OA182	£0.15
AAZ13	£0.17	BY124	£0.25	BY217	£0.41	OA200	£0.09
BA100	£0.11	BY126	£0.17	BY218	£0.41	OA202	£0.09
BA102	£0.37	BY127	£0.18	BY219	£0.41	SD10	£0.07
BA148	£0.17	BY128	£0.18	OA5	£0.69	SD19	£0.07
BA154	£0.14	BY130	£0.19	OA10	£0.40	IN34	£0.08
BA155	£0.16	BY133	£0.24	OA47	£0.09	IN34A	£0.08
BA173	£0.17	BY164	£0.58	OA70	£0.09	IN914	£0.07
BB104	£0.17	BY176	£0.86	OA79	£0.11	IN16	£0.07
BAX13	£0.08	BY206	£0.34	OA81	£0.11	IN4148	£0.07
BAX16	£0.09	BY210	£0.51	OA85	£0.11	IS44	£0.06
						IS920	£0.07

CASES AND BOXES

INSTRUMENT CASES in two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.72
156	11in	6in	3in	£2.92
157	6in	4 1/2in	1 1/2in	£1.79
158	9in	5 1/2in	2 1/2in	£2.43

ALUMINIUM BOXES made from bright all, folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.85
160	4in	4in	1 1/2in	£0.85
161	4in	2 1/2in	1 1/2in	£0.85
162	5 1/2in	4in	1 1/2in	£0.97
163	4in	2 1/2in	2in	£0.97
164	3in	2in	2in	£0.60
165	7in	5in	2 1/2in	£1.43
166	8in	6in	3in	£1.82
167	6in	4in	2in	£1.18

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front - strong construction easily accessible.

No.	Length	Width	Height	Bin	Price
163	2 1/2in	5 1/2in	2 1/2in	12in	£5.45
168	2 1/2in	7in	4in	16in	£8.21

VERO plastic case box. These boxes consist of top and bottom sections which include fixing points for horizontal mounting PC boards/chassis plates, the two sections are held together by four screws which enter through the base and are concealed by plastic feet.

No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4.14
171	140mm	75mm	205mm	£4.62
172	140mm	110mm	205mm	£6.00

SPECIAL OFFERS

MINIDRILL 12v hand held battery-operated mini drill, 7.500 r.p.m. Collet chuck. Ideal for drilling printed circuits or model making. No.1402. **£7.79**

TRANSFORMER 240v Primary 0-20v ± 2A Secondary. By removing 5 turns for each volt from the secondary winding, any voltage up to 20v ± 2A is obtainable. Ideal for the experimenter. No.2042 **£1.50 + 86p P & P**

ANTEX MLX Soldering Iron. Sturdy 25 watt iron complete with: 4 1/2 metres of 2-core cable. Works off a 12 volt battery. Ideal for Car. Boat, Caravan. No.1724. **£6.29**

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors assorted into the following groups:

16213	60 mixed 1/8w	100ohms-920ohms	£0.69
16214	60 mixed 1/8w	1Kohms-82Kohms	£0.69
16215	60 mixed 1/8w	10Kohms-830Kohms	£0.69
16216	60 mixed 1/8w	100Kohms-820Kohms	£0.69
16217	40 mixed 1/2w	100ohms-820ohms	£0.69
16218	40 mixed 1/2w	1Kohms-82Kohms	£0.69
16219	40 mixed 1/2w	10Kohms-82Kohms	£0.69
16220	40 mixed 1/2w	100Kohms-820Kohms	£0.69

CERAMIC PAKS

16160	24-3 or each value	22pf 27pf 33pf 39pf 47pf 68pf	£0.69
16161	24-3 of each value	100pf 120pf 150pf 180pf 220pf 270pf 330pf	£0.69
16162	24-3 of each value	470pf 560pf 680pf 1000pf 1500pf 2200pf 3300pf	£0.69
16163	24-3 of each value	4700pf 6800pf 01uf 015uf 022uf 033uf 047uf	£0.69

ELECTROLYTIC PAKS

16201	values from 47mfd - 10mfd	£0.69
16202	values from 10mfd - 100mfd	£0.69
16203	values from 100mfd - 680mfd	£0.69

COMPONENT PAKS

16164	200 resistors mixed value approx (count by weight)	£0.69
16165	150 capacitors mixed value approx (count by weight)	£0.69
16167	80 1/2w resistors mixed values	£0.69
16168	5 pieces assorted ferrite rods	£0.69
16169	2 tuning gangs MW LW VHF	£0.69
16170	1 pack wire 50 metres assorted colours single strand	£0.69
16171	10 reed switches	£0.69
16172	3 micro switches	£0.69
16173	15 assorted pots	£0.69
16175	30 paper condensers - mixed values	£0.69
16176	20 electrolytic trans. types	£0.69
16177	1 pack assorted hardware - nuts, bolts gromets etc	£0.69

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	40p
BP14	2nd book Transistor Equivs & Subs	£1.10
BP22	79 Electronic Novelty Circuits	75p
BP24	52 Projects Using IC741 (or Equiv)	75p
BP26	Radio Antenna Book Long Distance Reception & Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	60p
BP32	Build Metal & Treasure Locator	85p
BP34	Practical Repair/Renovation C/TV	95p
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	95p
BP36	50 Ccts use Germ/Sil/Zener Diodes	75p
BP37	50 Projects Using Relays/SCR/Triacs	£1.20
BP39	50 Field Effect Trans Projects	£1.15
BP40	Digital IC Equivs & Pin Connection	£2.50
BP41	Linear IC Equivs & Pin Connection	£2.75
BP42	50 Simple LED Circuits	75p
BP43	How to make Walki-Talkies	£1.25
BP44	IC 555 Timer Projects	£1.45
BP45	Projects on Opto-electronics	£1.25
BP46	Radio Circuits Using IC's	£1.35
BP47	Mobile Discotheque Handbook	£1.35
BP48	Electronics Projects for Beginners	£1.35
BP49	Popular Electronic Projects	£1.45
BP50	IC LM3900 Projects	£1.35
BP55	Radio Stations Guide	£1.45
BP160	Coil Design & Construction Manual	85p
BP202	Handbook of Integrated Circuits Equivalents & Substitutes	75p
BP205	1st Book Hi-Fi Speaker Enclosures	75p
BP213	Circuits for Model Railways	85p
BP215	Shortwave Circuits & Gear for Experiments & Radio Hams	85p
BP216	Electronic Gadgets & Games	85p
BP217	Solid State Power Supply Handbook	85p
BP221	28 Tested Transistor Projects	95p
BP222	Short-wave Receivers for Beginners	95p
BP223	50 Projects using IC CA3130	95p
BP224	50 CMOS IC Projects	95p
BP225	A Practical Intro to Digital IC's	95p
BP226	Build Advanced Short-wave Receivers	£1.20
BP227	Beginners Guide to Building Electronic Projects	£1.25

REGULATORS

Positive	Price	SILICON 1 amp	Type	No.	Price
uA7805 T0220	£0.85	50v RMS	BR1/50	£0.23	
uA7812 T0220	£0.85	100v RMS	BR1/100	£0.25	
uA7824 T0220	£0.85	200v RMS	BR1/200	£0.29	
uA7818 T0220	£0.85	400v RMS	BR1/400	£0.41	

Negative	Price	SILICON 2 amp	Type	No.	Price
uA7905 T0220	£0.92	50v RMS	BR2/50	£0.52	
uA7912 T0220	£0.92	100v RMS	BR2/100	£0.55	
uA7924 T0220	£0.92	200v RMS	BR2/200	£0.60	
uA7918 T0220	£0.92	400v RMS	BR2/400	£0.67	
72723 14 pin DN	£0.52	1000v RMS	BR2/1000	£0.78	
uA723C T099	£0.52				
LM309K TO3	£1.72				

CASSETTES

o/n.o.3193	30 min lettertape	£0.38
o/n.o. 301	Dindy C60 tape	£0.41
o/n.o. 302	Dindy C90 tape	£0.52
o/n.o. 303	Dindy C120 tape	£0.78

TRIACS

2 amp volts	TO5 case	Price	10 amp volts	Price	
100	TR12A/100	£0.38	100	TR110A/100	£0.88
200	TR12A/200	£0.59	200	TR110A/200	£1.06
400	TR12A/400	£0.82	400	TR110A/400	£1.29

ZENER DIODES

400 mw (Bz88) D007. Glass encapsulated range of voltages available: 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v. <b>No. Z4 10p</b>
1w-1.5w Plastic and metal encapsulated. Range of voltages available: 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v. <b>No. Z13 18p</b>
10w Metal stud type S010 case. Range of voltages available: 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v. <b>No. Z10 44p</b>

METAL FOIL CAPACITOR PAKS

16204 - Containing 50 metal foil capacitor like Mullard C280 series - Mixed values ranging from 01uf - 2.2uf. Complete with identification sheet **£1.38**




# A Range of Performance from... ...HAMEG

PERFORMANCE AND RELIABILITY  
ARE THE SEALS FIRMLY STAMPED  
ON THE COMPLETE HAMEG RANGE  
AND IT IS A COMPLETE RANGE



HM307	Single Trace DC-10MHz Plus Built-in Component Tester	£ 149
HM312	Dual Trace DC-20MHz, 5mV/cm, Full X-Y, 30MHz Trigger, Plus TV Trigger	250
HM412	Dual Trace DC-20MHz, 2mV/cm, X-Y, 40MHz Trigger, Plus Sweep Delay	350
HM512	Dual Trace DC-50MHz, 5mV/cm, X-Y, 70MHz Trigger Sweep Delay, Plus Single Shot, Sweep Delay and After Delay Trigger	580
HM812	Dual Trace as per HM512. Plus Storage, Automatic Storage and Variable Persistence	1325

Prices UK List ex VAT

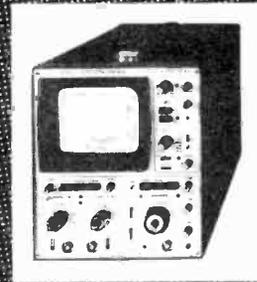

for FULL DETAILS and  
DISTRIBUTOR LIST  
Contact

Hameg Ltd.,  
74-78 Collingdon St.,  
Luton,  
Beds.  
LU1 1RX.

Tel (0582) 413 174

## The NEW Marshall's 79/80 catalogue is just full of components

*and that's not all . . .*

. . . our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.Cs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including I.Cs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

## REACTIVE TELLY

TO ANY that are hesitant at plunging into the depths of computer programming we would like to recommend them to it. The fascination of learning to think things through in a logical sequence and finding a TV to be a reactive medium after so many years of soap operas can be quite a revelation. Programming in itself probably accounts for hobby computing being such a fast growing pastime, it is most certainly addictive. Even if you find it difficult to dream up applications for the new toy don't be put off—they will probably take second place for a few months anyway.

The computer is, however, a hard task master, it does not tolerate sloppy work—even a journalist well used to checking copy can find the requirement for correctness in programming frustrating at first, no comma can be omitted. Once the basics (excuse the

pun) are mastered, these previously passive punctuation marks take on new meanings, together with a few rather odd words, a range of numbers, letters and characters, they are capable of captivating the mind.

It is a new experience to spend hours gazing at a TV screen and feel achievement and satisfaction at the end of a productive session.

At first the hobby tends to be hermit like and stunts conversation and other interests to a far greater extent than the latest American repeats on the other channels—you don't get the news either! However, after a few weeks of late nights and bleary eyes, not to mention a wife who still thinks that peek and poke sound rather ominous, one comes out of it and starts to swap programs and even make the computer pay for itself. Our Modem to be published next month should assist the swapping of the latest program or chips full of data.

## USEFUL?

Perhaps soon the step to becoming a useful tool will be taken by our office system—nicknamed Hal! At the present time Hal is rather a detraction, with a proliferation of new games being tried by all—apparently our Senior Illustrator is required in the Air Force, having excelled at Hectic; and we thought there was an age limit!

We hope that in due course all our indexing will be looked after by Hal. "He" will, we hope, help to lay out our issues, keep a check on the literary budget, write our standard letters, address hundreds of labels—even assist with project design and, most importantly, help us with our expenses. We could, of course, soon be receiving programs for *Microbus* from Hal via our Modem. It is just a start, but it is a start and we are all learning because of it.

Just don't expect any free time if you do invest!

*Mike Kenward*

## EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

## ADVERTISEMENT MANAGER

D. W. B. Tilleard

SECRETARY

Christine Pocknell

} 01-261 6676

AD. SALES EXEC.

Alfred Tonge 01-261 6819

CLASSIFIED MANAGER

Colin Brown 01-261 5762

### Editorial Offices:

Practical Electronics,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191

**We regret that lengthy technical enquiries cannot be answered over the telephone (see below).**

### Advertising Offices:

Practical Electronics Advertisements,  
King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Telex: 915748 MAGDIV-G

**Make Up/Copy Dept.: 01-261 6601**

## Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to **one published project only.**

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

## Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

## Binders

Binders for PE are available from the same address as back numbers at £3.75 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

## Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

# Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

## EXTRA EYE

Any constructors having problems seeing the new micro-technology will be interested in a highly efficient magnifier called the Handstand, it can be used as a hand-held magnifier or it may be inserted into a simple stand.



The lens, the wide rim protecting it and the flat handle are made as a single integral moulding from a high-grade acrylic material, which is shatter-resistant and has a better light transmittance than any glass lens. It has a diameter of 96mm (approx 4 inches), permitting both eyes to be used to view the work. Magnification is about 2 times.


The unit is available from large stores, optical accessory outlets, stationers, hobby and craft shops at about £4.40 including VAT.

Combined Optical Industries Ltd., 200 Bath Road, Slough SL1 4DW.
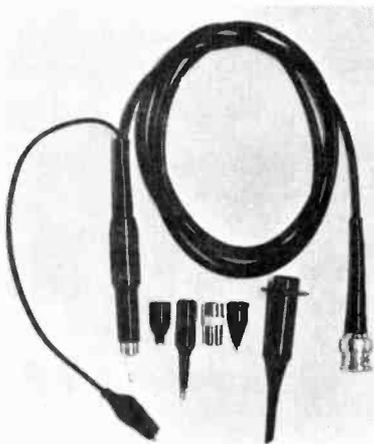
## SCOPE PROBES

A new range of scope probes designed for use with all popular makes of oscilloscopes is being launched by Electronic Brokers.

The probes are available in three different forms—model X1 or X10 and model X1X10



which is a switched probe. Each kit is supplied with a set of accessories, including a spring hook tip, i.e. tip, BNC adaptor and a trimmer tool. Model X10 has a bandwidth of 100MHz and the X1 a bandwidth of 20MHz. Maximum working voltage is 600V d.c., including peak a.c.


All three probes have a cable length of 1.5 metres and are supplied in a zip-up plastic wallet. Prices start from £9.00 a kit plus VAT and p&p.

For further information contact **Electronic Brokers Ltd., 49/53 Pancras Road, London NW1 2QB (01-837 7781).**
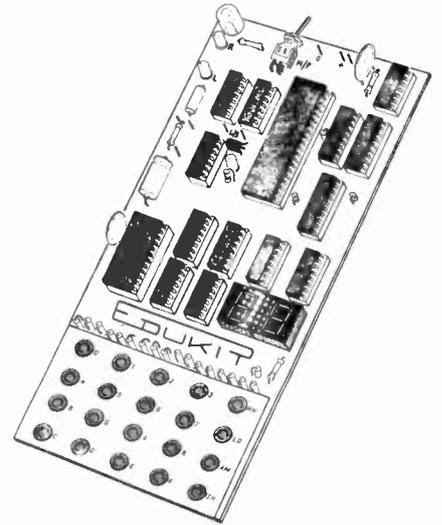
## THE EDUKIT

A new MPU system aimed at teaching about micros from scratch is to be launched by Modus Systems. The EDUKIT is believed to be the first machine available for under £30. It is based around the COSMAC processor and comes with a carefully written manual produced by the designer Dr. A. A. Berk.

Rather than reading a book, those wishing to extend their knowledge to include the micro revolution can buy this complete package and practice on their own machine at very low cost.



The manual is suitable for technical and non-technical people of all ages. As well as describing construction, use of machine-code, hardware control etc., it guides the user to bigger machines once the basics have been learned on the EDUKIT.

The machine has hex keypad and hex display, 256 bytes of RAM, runs from a 6 volt dry battery or a 5 volt supply and has special command keys for loading and running programs and correcting mistakes. Plenty of I/O lines are included to form the basis of a simple but powerful control device. Indeed, the COSMAC MPU is very well set up for exactly this application.

As a special introductory offer, the EDUKIT is available from **Modus Systems., 29A, Eastcheap, Letchworth, Herts., at £29.99 inc. VAT. plus 80p p&p.**

## BRAIN BANK

The Brainbank Electronic Information Centre represents a new generation of pocket companions following on from calculators and mini TVs. It is a learning aid, phrase book and translator for foreign languages; a library of general knowledge, education and entertainment topics; and a personal filing system combined.

The unit has a series of plug-in interchangeable memory cells, which provide this hand-held, machine with an infinitely variable store of information. This effective and novel learning laboratory for foreign languages has a powerful and immediate translation facility of up to three languages at a time.

Each language cell holds 1,200 of the most frequently used words which can be stored both in alphabetical order and by groups of

up to 50 in categories such as Travelling, Clothing, and Food.

Operation is via an A to Z keyboard, which includes numerals and punctuation. The unit is also programmed with 25 complete and 25 partial phrases which can be added to give full sentences, for example "May I introduce . . .", "I'd like to say . . .". Spelling mistakes are automatically corrected and a "phonetic" cell aids pronunciation.

Currently six language cells are available—English, French, German, Spanish, Italian and Portuguese, with Japanese and Arabic due in



the next few weeks. All the remaining major languages will be available during the next four months.

As an Information Centre, the unit has a built-in metric conversion facility, while memory cells containing comprehensive details on diet and nutrition programs. First Aid, Taxation and a Thesaurus are already complete.

The unit is housed in a robust case which measures  $7 \times 3 \times 1\frac{1}{2}$  in and weighs 14oz. It is powered by four standard alkaline penlight batteries which give ten hours continuous use, or by rechargeable nickel cadmium batteries. "Brainbank" is sold complete with mains adaptor and battery recharger and one free cell. The price is around £150 and additional cells cost under £20.

Further details **Ring Group, Gelderd Road, Leeds LS12 6NB. (0532 632421).**

## CATALOGUES

The latest catalogue from Ace Mailtronix is now available at a cost of 30p with a 30p voucher which is redeemable with orders over £5.00. Ace can also supply all RS stock items and have also helped many readers obtain particularly difficult to get components. So the next time you are looking for an awkward item try **Ace Mailtronix, Tootal Street, Wakefield, West Yorkshire WF15 JR.**

Also available now is the latest edition of **Ambit International's Tecknowledgey series** (the third) which follows the style of the other two with plenty of constructional circuits and component information. All three editions are available for £1.50 which includes p&p.

**Ambit International, 2 Gresham Road, Brentwood, Essex CM14 4HN (0277 216029).**

The latest **TK Electronics** catalogue contains a wide range of components and includes applications for triacs, UJT, timers and dimmers. The catalogue is available free of charge from **TK Electronics, 106 Studley Grange Road, London W7 2LX** (Please send a stamped addressed envelope). **Both TK and WATFORD ELECTRONICS can supply the chip (AY-3-1270) used in the Digital Temperature Controller (Oct. '79).**




## NEW SCOPE RANGE

Hameg is a new name in the high performance low cost oscilloscope market. Though until now relatively unknown in this country the company has established a dominant position in the West German market.

Their current range of products extends from the single trace HM307 10MHz instrument, which features a built-in component tester, up to the 50MHz dual trace HM812 with storage and sweep delay facilities.

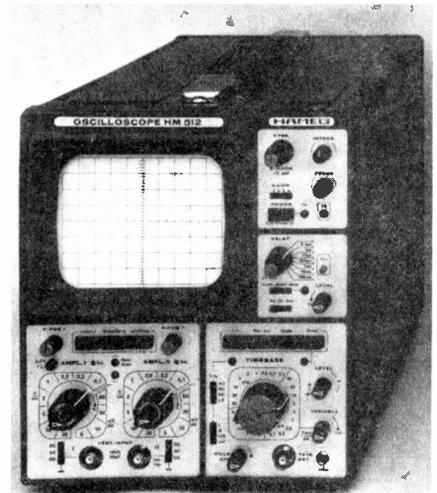The HM312 is a dual trace oscilloscope with a vertical amplifier bandwidth of dc-20MHz and 5mV/cm sensitivity. Full X-Y operation is achieved by switching channel 2 into the horizontal deflection system. This amplifier system is complemented by a wide



range calibrated timebase with 18 sweep speeds from 0.5µs-0.2s/cm.

The complete range and prices excluding VAT are as follows: HM 307-3 (£149), HM 312-8 (£250), HM 412-4 (£350), HM 512-8 (£580) and the HM 812-2 (£1,325).

For further information contact **Hameg Ltd., 74-78 Collingdon Street, Luton, Bedfordshire LU11 RX (0582 413174).**

## LOW COST MULTIMETER

The new MINI 20 multimeter from Alcon Instruments has been designed specifically to cover the needs of the lower end of the market.

Built in ABS plastic, with a full-view anti-static cover and the simplest of controls, this instrument is ideal for applications where simplicity is the keynote.

One rotary-switch selects any 27 ranges in a.c., d.c. (both V & I) or resistance. The scale used is provided with an anti-parallax mirror

Ranges extend from 100mV to 600V d.c., 15V to 1500V a.c., 50µA to 600mA d.c., 30mA to 3A a.c., and up to 2kΩ and 2MΩ on resistance. There are also five dB ranges corresponding to the five a.c. voltage ranges.

An internal battery provides power for the resistance ranges and protection is by both movement diode and fuse.

The instrument comes complete with case, leads and instructions at £27.37 including VAT.

**Alcon Instruments, 19 Mulberry Walk SW3 (01-352 1897)**



and clear calibrations to avoid ambiguity and error. The only other control is the ohms zero potentiometer, which projects from the right hand side of the instrument-case.

Only two terminations are used (4mm banana) so there is no possibility of confusion in selecting a wrong socket for a probe, and the ranges provided cover most situations.

Sensitivity is 20kΩ/V d.c. and 4kΩ/V a.c. Accuracy is 2 per cent on d.c. and on resistance, and 3 per cent on a.c.—sufficient for most professional uses and other applications.

## CASIO WATCHES

Four of the latest range of Casio watches are shown below. The F-8C has an eight digit readout of hours, minutes, seconds and date with a four year calendar. Both the F-8C and the F-200 sports have black resin cases and straps with the F-200 incorporating a stopwatch.




The 95QS-31B and 81CS-36B are stainless steel chronographs with six digit readouts and calendars pre-programmed to the year 2029. These models also have alarm and stop watch facilities. Prices F-8C (£10.95), F-200 (£15.95), 95QS-31B (£23.95) and the 81CS-36B (£35.95).

**Tempus, The Beaumont Centre, 164-167 East Road, Cambridge, CB1 1DB (0223 312866).**
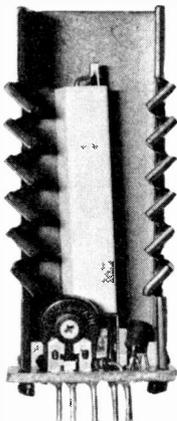
## LEDCo

The LEDCo company manufacture and market a wide range of replacement panels and modules for colour TVs.

A typical example is the CDA panel (colour-difference amplifier) fitted to the Pye 691, 693 and 697 chassis. The main problem with the board has been the heat generated by the four valves which have resulted in charred p.c.b.s and oxidation of valve pins and holder contacts. The new replacement panel, which



requires no soldering, is a solid state design and is available with details of setting-up procedure, expected voltage reading and a circuit diagram.

Another development is a solid state replacement for the PL802 which plugs right into the existing holder and requires no modifications.


For further information about these and other replacement panels. LEDCo, 189a Livingstone Road, Thornton Heath, Surrey, CR4 8JZ (01-653 7575).

## CHASERS

Two new modules have been introduced to the existing range of lighting control units from L&B Electronics.

The LB81000 & C is an eight channel chaser capable of controlling a substantial number of lights.

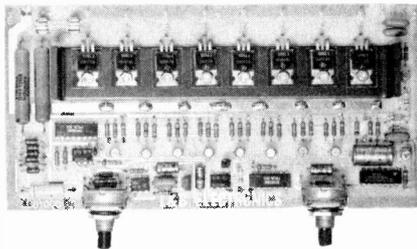A chase speed control allows a wide variation of chase rates whilst a second control allows a delay to be introduced between the




end of the chase cycle and the start of a new one. During this delay period, all the lamps remain off. Again the wide range enables this delay to be set to virtually zero, if required, so the sequence appears to start immediately after the finish of the last one. Both controls are mounted at the board edge, allowing easy presentation to your front panel.

Because the system logic allows only one channel of lamps to be powered at any given instant, the mains current consumption will
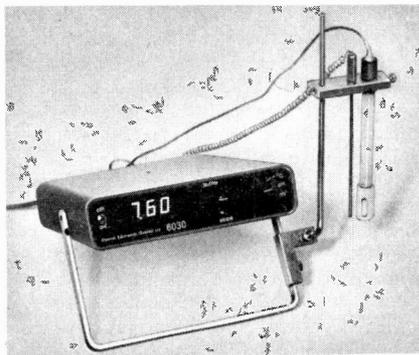
## pH METER

The 6030pH meter has been designed for the rapid and accurate determination of pH, millivolts and temperature values.

The unit measures over the range 0-14.00 pH to a resolution of 0.01pH and has completely automatic temperature compensation over the range 0-100°C. In the temperature measurement mode the instrument will measure from -149.9°C to 199.9°C to a resolution of 0.1°C. This is effected by the use of a high accuracy platinum resistance probe.




In the millivolt mode the instrument will measure over the range  $\pm 999\text{mV}$  to a resolution of 1.0mV.

A voltage output for each of the measuring modes is provided at the rear of the instrument and offers a 1mV per least significant digit output.

The Model 6030 is supplied complete with one plastic bodied, gell filled combination pH electrode, one PRT probe plus buffer powders. A convenient pH temperature compensation electrode holder is available which clamps to the front of the instrument.

never exceed the loading of one channel, ie, four amps max, although up to 8000 watts may be connected. This is a considerable advantage meaning that the module can be connected to a domestic mains supply, with a tremendous number of lamps (eighty 100W spots for instance). As each triac is triggered near to mains zero, no interference is produced on nearby amplifier equipment, and the use of heavy duty triacs and in-line fusing

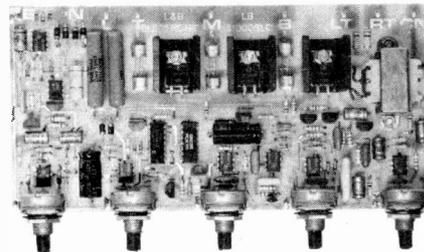

gives protection against overload. Full logic design, using CMOS i.c.s, means no additional power supplies are required, so connection remains simple.


Additional features allow the chaser to be footswitch triggered (ideal for band stage effects). In this mode, the module may be set to give one chase cycle per footswitch pulse, or can be triggered into continuous cycles from a single pulse. Further trigger output and input pulses allow modules to be connected in series,

The price of the 6030 is £199 plus VAT and p&p.

Channel Electronics (Sussex) Ltd., P.O. Box 58, Seaford, Sussex BN25 3JB (0323 894961).
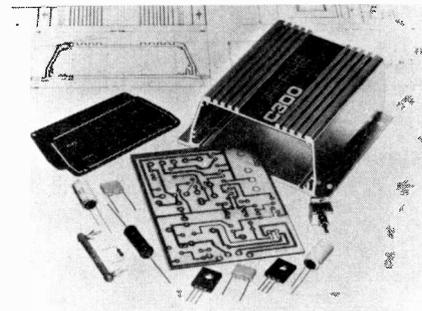
## TOP CDI SYSTEM AS KIT

Electronic ignition systems have the general advantage of greatly extending the life of contact breakers and plugs, also affording a fat spark for easy starting and obviating misfiring at high engine speeds.



Suretron Systems have for a number of years been marketing both the ES2000 and C3000 with the latter figuring very favourably against stern competition in "Which" magazine tests. Now, on special offer, this company provides the same electronics and therefore performance in kit form renumbered as the ES200 and C300. Purchasing either shows a considerable price saving, almost half the price of its completed counterpart. These are ES200—£13.95 and C300—£17.95 which includes VAT and postage.

Suretron Systems (UK), Ltd, Piccadilly Place, London Road, Bath, BA1 6PW.

to form 16, 24, 32, 40, etc., channels (there is no limit to the number), hence forming a line or tunnel of lamps, that may indeed be set to run as a continuous chase, or be footswitch controlled.

Each p.c.b. is fully assembled, tested, supplied with full wiring instructions, circuit diagram, and guaranteed for a year.

The LB31000SLC is a sound-to-light chaser. When fed. by a music source the module acts as a sound-to-light system, flashing three banks of lamps, bass, middle and treble. However, when the music signal ceases or becomes sufficiently low enough, the system automatically switches to a chase mode. Upon return of the music signal, the sound-to-light display is instantly resumed.

Five controls, mounted on the board, allow variation of chase speed, master volume for the sound input and individual bass, mid and treble settings for the perfectionist.

No additional components are required. The system is simply wired to the mains, the three banks of lights, and the music input (usually derived from across the speaker terminals). You will need a suitable case/panel.

Each board is thoroughly tested and inspected, guaranteed for a year and provided with wiring instructions and circuit diagram.

The price of the 81000LC is £25.50 and the 31000SLC is £28.90 including VAT, plus 50p postage and packing.

L&B Electronics, 45 Wortley Road, West Croydon, Surrey, CR0 3FB.


## LOW COST SCOPE

Manufacturers of the ST-45 claim to have reached the peak of performance-quality to price ratio with the introduction of the SAFGAN ST-45 oscilloscope.

This single trace oscilloscope with 5MHz bandwidth, 10mV/div sensitivity and a display area of 6.4cm x 8cm with a graticule ruling of 8 x 10 divisions. The vertical amplifier which has 1M $\Omega$  plus approx 22pf input impedance uses a FET input stage followed by stages consisting of transistor arrays in order to achieve minimal drift of the trace with temperature changes. Input attenuator stages are set for best-pulse shapes and has  $\pm 5$  per cent accuracy on all ranges. 50 $\Omega$  input impedance attenuator settings are useful for r.f. work.

Overall time base speed range from 250ms/div to 200ns/div including multiplier and x5 expansion facilities; all timebase speeds are calibrated to  $\pm 5$  per cent accuracy. External -x sensitivity is 1V/div with 500kHz bandwidth.

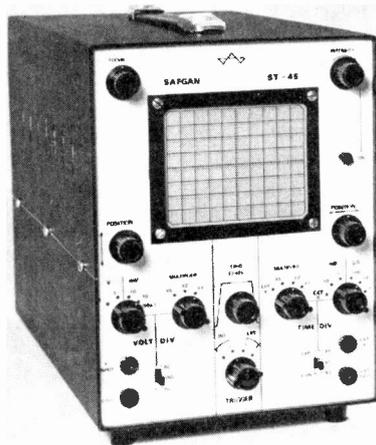Trigger level and +ve, -ve slope selection



on both internal and external trigger modes is also incorporated.

The instrument is mains powered with an approx power consumption of 10 watts.

Aluminium covers are black with p.v.c. finish and are fairly scratch proof.

The price of the ST-45 is £125.00 plus VAT.

Safgan Electronics Ltd., 56 Bishops Wood, St. Johns, Woking, Surrey GU21 2QB (04862 66836).


## NEW COMPONENT SUPPLIERS

Our cover subject this month is the product of a new component supplier. This company—WICCA Electronic Systems Ltd—have been able to source the transducer and tank in order to develop the Ultrasonic Cleaner and have had the coil and transformer specially wound and the cases made up to form a complete kit for the project. WICCA are also now supplying various other components including a new Sanyo dual 30W amplifier module (STK 463) and a sound to light unit, see their advertisement in this issue for more details. WICCA Electronic Systems Ltd., Orchard Works, Church Lane, Wallington, Surrey.


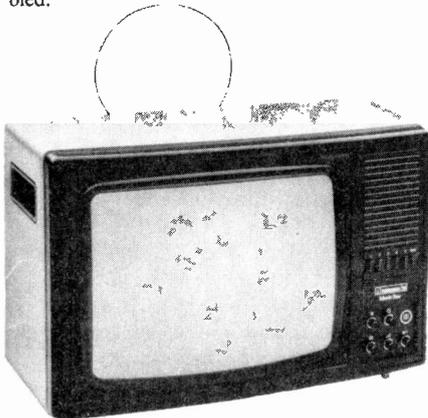
## FERGUSON TX9


The first TV to feature Ferguson's revolutionary TX9 single board chassis is now available. This new colour set is a 14 inch portable model called the Moviestar 3755 and Market Place recently had the opportunity to visit the production line at Gosport in Hampshire to see how the set is being assembled.



The 14in Moviestar model 3755.


When Ferguson decided to design a completely new TV they realised that to compete with foreign manufacturers the new set would have to be automatically assembled to a very large degree, using the most up-to-date techniques available. This decision involved the company in a massive £10 million plus investment programme which when finished will make the Gosport factory the most advanced automatic TV production line in the UK.

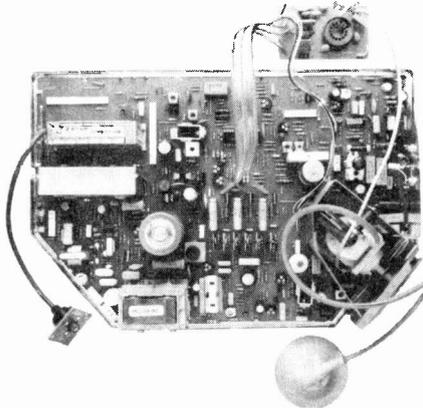The single board chassis has 70 per cent of its components automatically tested, inserted and soldered. After the rest of the components have been fitted the complete board is tested and assembled into the cabinet without the need for any further soldering.



The TX9 chassis.

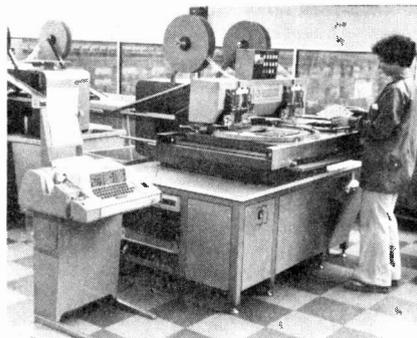Using automatic insertion techniques the component density of the p.c.b. can be greatly increased. Also as the number of components has been greatly reduced compared with their 9000 series chassis the overall effect is a




The automatic insertion system is computer controlled with the components being fed from a bandolier to the machine head where they are crimped into the p.c.b.

reduction in human errors and an increase in both performance and reliability in the set.

The 3755 model will be followed by 16in, 18in and 20in versions, each driven by the TX9 chassis without the need for any component or electrical changes. The TX9 also consumes less power than most other CTV's (50 per cent less than the 9000 series) and therefore generates less heat inside the receiver resulting in increased component life.

An optional 12 or 24V battery converter which has been designed for in-set installation is also available. Further developments will include Teletext, Viewdata and infra-red/ultrasonic remote control models.

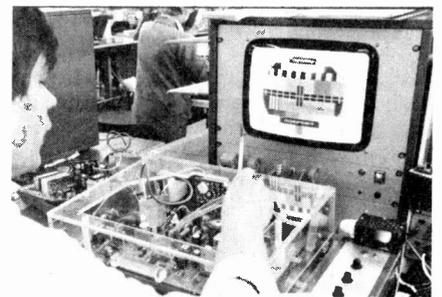One area where the 3755 will get a very good reception is servicing. If a set should need attention the engineer will find the chassis easily accessible and because it can be positioned vertically free access is available to both sides of the p.c.b. If the fault cannot be



After assembly the chassis is checked to assess picture alignment.

traced the chassis can be replaced in minutes.

Another advantage in using the same chassis in the 14in, 16in, 18in and 20in models is that the range of parts required for servicing is greatly reduced.

As TV production—like most areas of electronics—is a fiercely competitive business it is good to see a British company with the foresight and confidence to manufacture a well designed product to fill a definite market gap and using advanced production techniques to ensure a competitive price (around £250).

# Scratch & Rumble Filter

R.A. Penfold

A scratch filter can be very effective at reducing the noise generated when playing worn or dust impregnated records. This type of filter merely attenuates high frequency signals above about 6 or 7kHz, and the background "crackle" of surface noise consists mainly of frequencies above this level. Comparatively little of the programme signal will be in this high frequency range, and so the noise is considerably attenuated with little, although admittedly some, of the wanted signal being lost.

A rumble filter operates at the opposite end of the audio frequency spectrum, and rolls off the low frequency response of the system below about 50Hz. This can be used to reduce noise produced by record warps or pressing imperfections.

Again, there will obviously be some loss of the wanted signal, but this will only be minimal. Most of the frequency range affected by a rumble filter lies below the lower limit of the audio spectrum. It may seem to be pointless to attenuate noise which cannot be heard, but it is not necessarily superfluous to do so. Record warps can generate strong low frequency signals which will vary the amplifier's biasing either side of its normal central level. This can cause the main signal to be clipped on one set of half cycles when the low frequency signal is at or close to its peak positive or negative level. Even if clipping does not occur, intermodulation distortion can still cause audible phasing type effects to be produced.

Although some hi-fi amplifiers and receivers incorporate scratch and/or rumble filters, this is by no means a feature of all designs. Also, many amplifiers and receivers that do have these filters only have simple 6dB/octave types. These can be quite effective, but do not give a level of performance equal to that of a sophisticated filter having an attenuation rate of 12dB/octave or more. It is possible to use an add-on scratch and rumble filter with most hi-fi systems, and it is a high performance unit of this type that forms the subject of this article.

## BASIC FILTERS

Ideally a scratch filter would not attenuate frequencies below the turn-over frequency, and would eliminate all signals above this frequency. Similarly, an ideal rumble filter would not affect signals above the turn-over frequency, and would block signals below this frequency. Simple passive filters fall well short of this goal, and give an ultimate roll off rate of only about 6dB/octave as well as significant losses at frequencies well within the passband.

A basic R-C high pass filter uses the arrangement shown in Fig. 1(a). The component values are chosen so that the impedance of C is low in relation to that of R at pass frequencies, and the impedance of C is roughly equal to that of R at the desired cut off frequency. Thus, there is little attenuation at pass frequencies, and a loss of about 6dB at the cut off frequency, increasing by about 6dB/octave below this due to the losses produced by the increasing impedance of C.

A basic R-C low pass filter is shown in Fig. 1(b) and operates in much the same way as the high pass circuit. However, the capacitor and resistor have been swapped over so that as the impedance of C falls with increasing frequency, losses through R increase, as does the attenuation through the circuit.

The relatively slow roll off rate of these circuits can be greatly improved by using two or more filters in series. Unfortunately this still tends to leave significant losses at frequencies well below the cut off frequency.

## ACTIVE FILTERS

This problem can be overcome by using an active filter of the type outlined in Fig. 1(c) (high pass) and Fig. 1(d) (low pass).

Taking Fig. 1(c) first, the series capacitance of C1 and C2 forms a simple high pass filter in conjunction with R1. The output from this network is taken to a buffer amplifier, and bootstrapping resistor R2 introduces positive feedback between the output of the buffer amplifier and the junction of C1-C2.

Whereas the negative feedback normally employed in audio circuits has the effect of flattening any variations in frequency response, positive feedback has the opposite effect and tends to increase any such variations. This is desirable in this case since it produces a fast roll off rate.



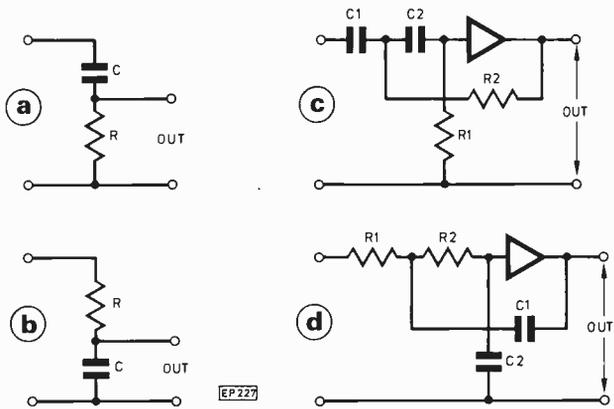


Fig. 1 (a) Basic R-C high pass filter (b) low pass filter (c) active high pass (d) active low pass

At pass frequencies R2 does not have any real effect on the circuit since any change in voltage at the junction of C1 and C2 will be matched by an identical change at the output of the buffer amplifier. No voltage is developed across R2, and it is effectively nonexistent.

If R2 has a suitable value, at frequencies where the circuits response is beginning to fall slightly it will tend to reinforce the input signal, flattening the response and preventing the very gradual initial roll off that occurs with passive filters. Filters of this type often actually have a small peak in the response just above the cut off frequency.

At frequencies where C1-C2 and R1 introduce significant losses, voltage changes at the left hand end of R2 will no longer be fully matched by a change in potential at the other end. This results in some of the input signal current flowing through R2, and this component then effectively forms a second high pass filter network in conjunction with C1. This increases the attenuation rate to about 12dB/octave.

Thus this type of circuit does not attenuate signals that are well below the cut off frequency, and has a fairly fast attenuation rate. By using two or more R-C networks at the input it is possible to obtain an extremely rapid roll off rate.

The low pass version of this filter configuration functions in the same basic manner as the high pass one, but the resistive and capacitive circuit elements are, of course, transposed in order to obtain the correct filter action.

## CIRCUIT

The complete circuit diagram of the scratch and rumble filter appears in Fig. 2.

The buffer amplifier for the rumble filter uses TR1 in the emitter follower mode. This has R6 as its emitter load and is biased by R4 and R5. Two sets of filter components are used at the input, the first consisting of C3, R1, C4, and R2, and the second one using C5, R3, C6, and the input impedance of the buffer amplifier. The latter is mainly determined by the

## COMPONENTS ...

Asterisked components should be repeated for a stereo channel

### Resistors

R1*	5.6k	R7*	4.7k
R2*	12k	R8*	4.7k
R3*	6.8k	R9*	4.7k
R4*	120k	R10*	4.7k
R5*	150k	R11*	3.9k
R6*	3.9k	R12*	330

All miniature 1/4 watt 5% carbon

### Capacitors

C1*	100n type C280
C2*	4.7μ 16V
C3*	470n type C280
C4*	470n type C280
C5*	470n type C280
C6*	470n type C280
C7*	6.8n polystyrene
C8*	3.3n polystyrene
C9*	10n polystyrene
C10*	680p polystyrene
C11*	10μ 25V electrolytic
C12	2,200μ 25V electrolytic
C13	330μ 16V electrolytic

### Semiconductors

TR1*	BC109
TR2*	BC109
TR3	BFY51
D1	1N4001
D2	1N4001
D3	BZY88C13V 400mW Zener

### Switches

S1-S3 Double pole rotary on/off switches (3 off)

### Transformer

T1 Standard mains primary, 12-0-12V secondary of 50 or 100mA rating

### Fuse

FS1 1 1/4 in 100mA

### Miscellaneous

Main printed circuit board, and P.S.U. printed circuit board  
 Case of metal construction and having dimensions of about 203 x 152 x 63mm (see text)  
 Three aluminium control knobs  
 Panel neon indicator having integral series resistor for mains operation  
 1 1/4 in in-line fuseholder  
 Phono input and output sockets (SK1 and SK2)  
 Wire, grommet, solder, etc

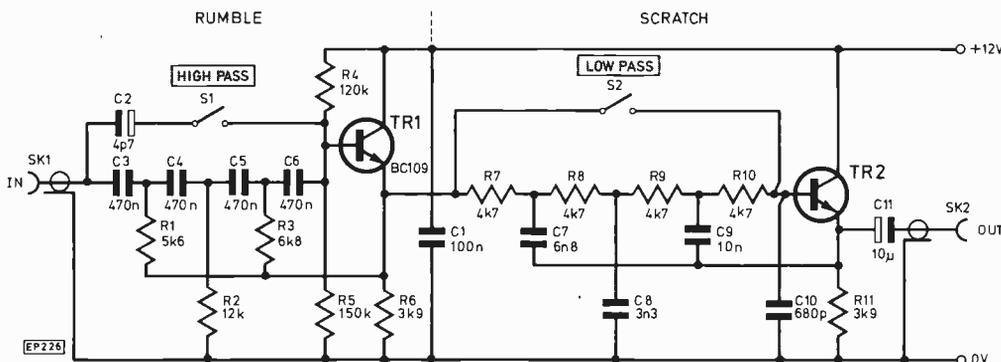


Fig. 2 Complete circuit

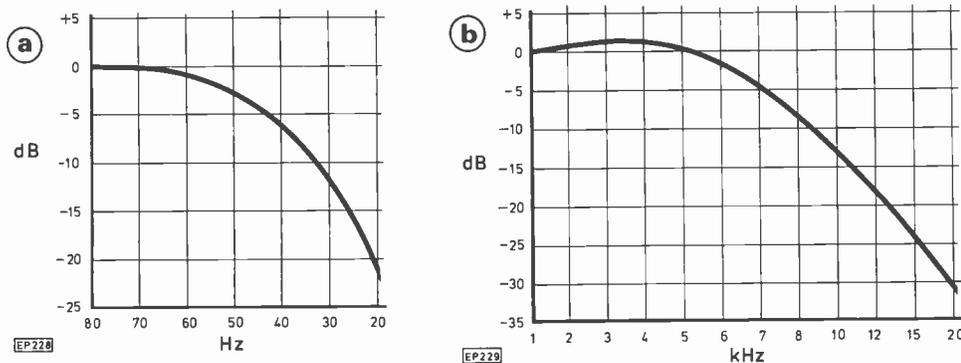


Fig. 3(a) Frequency response graph of rumble filter and (b) response of scratch filter

values of the two biasing resistors. S1 can be used to bypass the filter components and eliminate the filtering. C2 is merely a d.c. blocking capacitor.

As can be seen from the frequency response graph of Fig. 3(a), the rumble filter has a  $-6\text{dB}$  point at about 40Hz, and a roll off rate of approximately 18dB/octave.

TR2 is used in the emitter follower mode and is the buffer amplifier for the scratch filter. It has R11 as its emitter load resistor and is biased from the emitter of TR1 via filter resistors R7 to R10. C7 to C10 are the capacitive elements of the low pass filter, and again, two filter sections are used. When only the high pass filtering is required, S2 can be used to bypass the low pass filter networks. C11 provides d.c. blocking at the output.

The frequency response of the scratch filter is shown in Fig. 3(b). The  $-6\text{dB}$  point is reached at a little in excess of 7kHz, and the response then falls away at about 18dB/octave.

Negligible noise and distortion are introduced by the unit since both active stages have 100 per cent negative feedback.

### MAINS P.S.U.

The circuit has a current consumption of about 3mA from 12V, and will work well on any supply potential from about 9 to 18V. A 9V battery supply can be used, but the prototype is powered from the simple mains power supply circuit given in Fig. 5.

This uses a push-pull rectifier and smoothing circuit feeding a conventional emitter follower series regulator. This gives an extremely well smoothed output of approximately 12V. S3 is the on/off switch.

Note that if an alternative mains supply unit is used, this must have a low ripple output since any noise on the supply lines will be coupled into the main signal path by the biasing resistors in the main circuit.

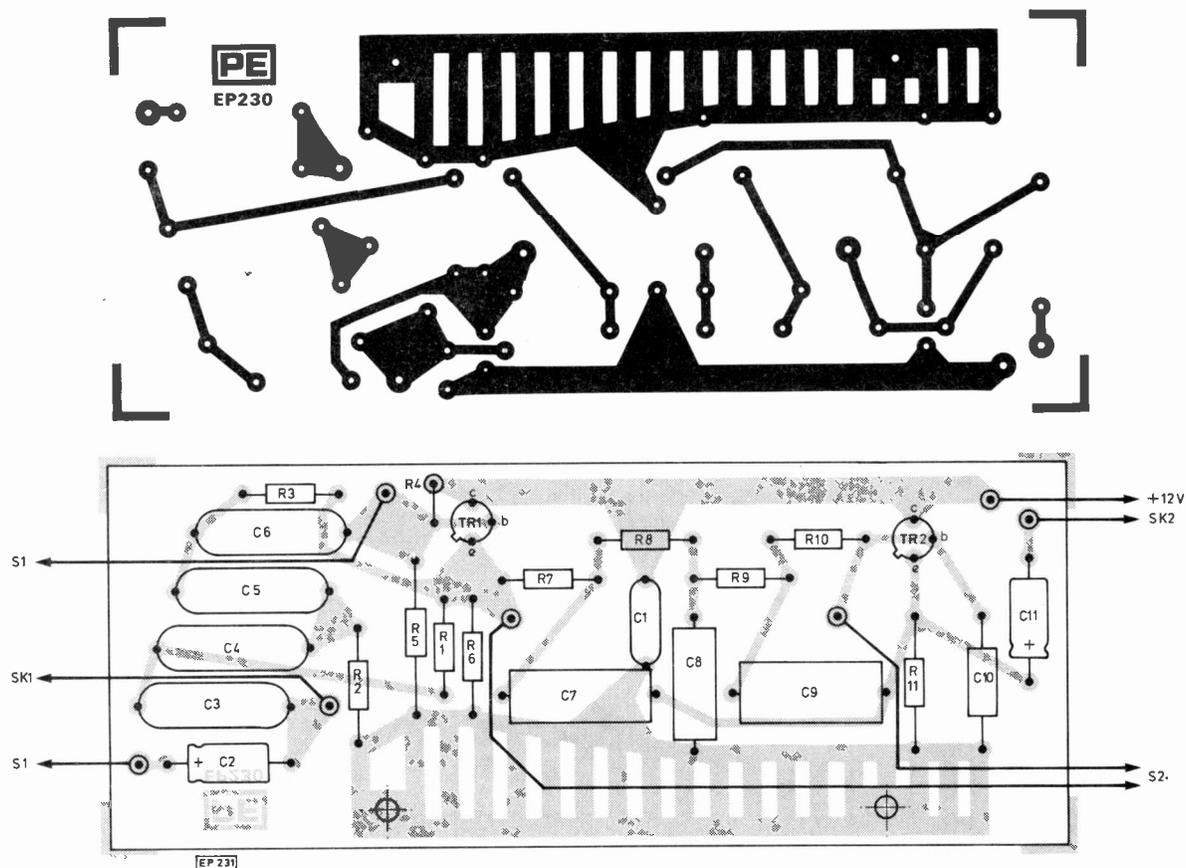


Fig. 4 P.c.b. and component layout

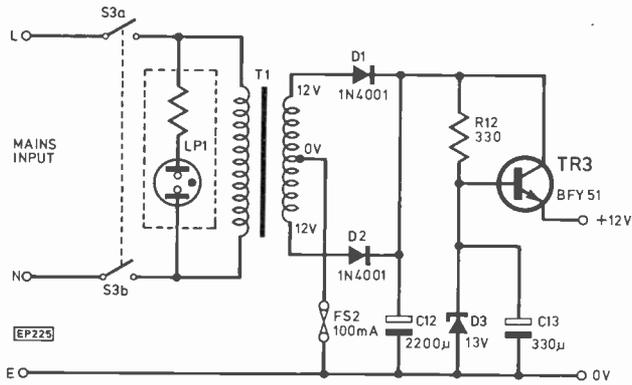


Fig. 5 Mains p.s.u.

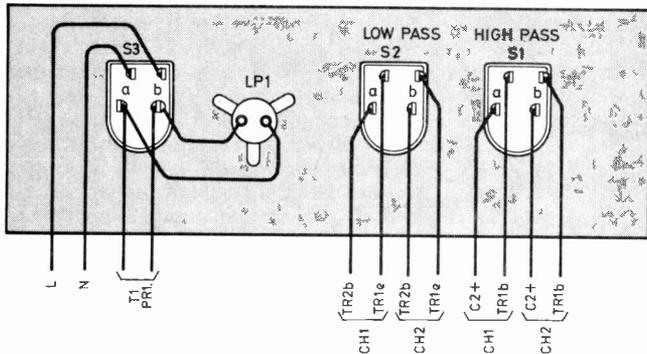
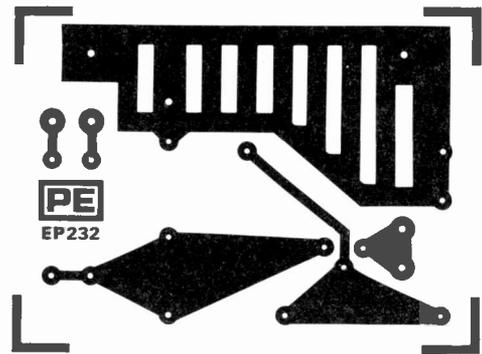


Fig. 7 P.c.b. and component layout for p.s.u.


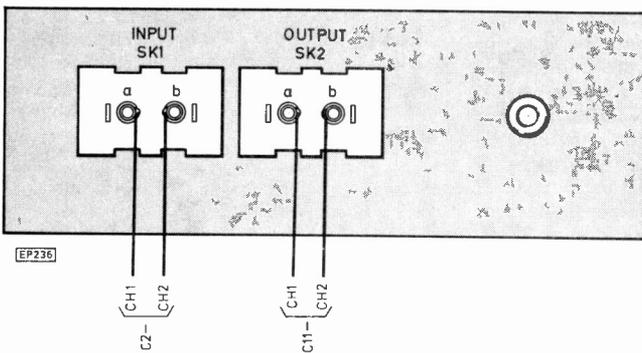


Fig. 6 Component assembly for panels

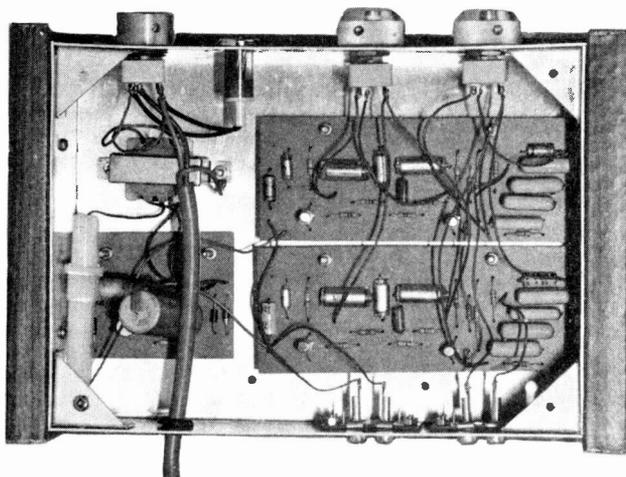

## CONSTRUCTION


The housing for the prototype consists of a 203 x 152 x 63mm chassis and base plate to which a wood grain finish for top and sides was added to give a better appearance.

The filter components are assembled on a printed circuit board using the copper backing pattern and component layout illustrated actual size in Fig. 4. Of course, for stereo operation it is necessary to make up two of these p.c.b. assemblies, one for each channel.

A separate printed circuit board is used to accommodate most of the power supply components. Details of this and the other power supply wiring are provided in Fig. 7. The negative supply rail, and the earthy connections to the input and output sockets, are all carried by the metal chassis plus the mounting bolts and spacers for the p.c.b.s.
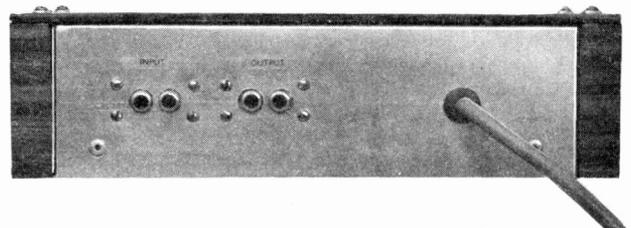
## USING THE UNIT

It is necessary to connect the filter between the pre-amplifier output and the power amplifier input. Many amplifiers have a "tape monitor" facility or something of this nature which enables this to be easily achieved. It is not really feasible to use the unit with equipment which does not have such a facility unless it is fitted with a suitable pre-amplifier to enable it to be connected between the record deck and a high level input of the amplifier. ★



# Semiconductor UPDATE...

FEATURING

8294

2920

SL446A

SL441A

R. W. Coles

## JAMES BOND CHIP

If I were 'M' I would send our Jim off to Intel for a crash course in microprocessor encryption techniques before that bunch from SMERSH and SPECTRE get there.

Gone forever, it seems, are the five letter groups and secret code books of yesterday's spy, and disappearing too is the need for rack sized encryption and decryption systems at the FO and the ACME Import/Export Co. Intel have spoiled all the fun by designing a chip to do both jobs and, horror of horrors, *anyone* can buy one!

The mathematics of code generation and code breaking reached their zenith during the second world war, and as we now know, we (the British) were much better at breaking codes than the Germans were at generating them. It became obvious with the dawn of the computer age that there could be no such things as an unbreakable code, and the effectiveness of a code is now judged not by whether it can or cannot be cracked but simply by how long it would take the fastest available computer to crack it! It is quite feasible to generate codes which would take hundreds of years to crack, but for most commercial purposes a code which will afford a few years, or even a few weeks protection is quite adequate. Think of the cost of tying up a mainframe computer for a few weeks just to crack one message.

Because more and more "sensitive" commercial data is being transmitted from computer to computer over telephone and satellite links and being carried around on magnetic tapes or discs, the US government has identified the need for a data encryption standard which can be used by anyone who requires this kind of security. An algorithm has been produced by the National Bureau of Standards which will generate codes secure enough for all but MI5 and the CIA, and to implement this algorithm, Intel has produced the **8294** data encryption/decryption device. The 8294 is used as a peripheral chip in a microprocessor based system using an 8080 or similar CPU chip, and is therefore as easy to use as, say, an 8251 USART device. The 8294 fits into a 40 pin package and runs from a single 5 volt supply. It accepts data in 64 bit (8 byte) blocks and encrypts or scrambles it at the rate of 640 bits per second using a 64 bit "key" supplied by the user. The 8294 is normally controlled by the microprocessor but data can be transferred to and from the 8294 either under software control or by means of the much faster Direct Memory Access (DMA) technique. With the chip initialised and an

eight byte key entered, encryption or decryption is achieved by simply entering eight data bytes and reading back the eight converted bytes. Simple, eh, Jim!

## ANALOGUE MICRO

It had to happen I suppose. All you die-hard analogue fans who still feel that microprocessors will never replace the 741 op-amp or those lovely tuned filters using rows of carefully wound inductors and precision capacitors, stand by for a few nagging doubts!

Intel have done it again, by introducing a radical new microprocessor chip with analogue inputs and analogue outputs, to challenge traditional linear circuit designs in some of their most hallowed sanctuaries.

Imagine a single 28 pin chip running from plus and minus five volt supplies. To the input of the chip you connect a wide-band audio signal, and from the output you get a filtered 1kHz tone whenever the input signal is in-band. Sounds like a conventional 1kHz bandpass filter circuit, but in this case it's the Intel **2920** analogue microprocessor, and you tune the filter not by means of precision RLC components but by means of software instructions! Fed up with a 1kHz bandpass filter? No problem. The 2920 program is stored in an on-chip erasable PROM memory, so just give it a dose of UV light and reprogram for 500Hz. Fed up with filters altogether? Why not program up a function generator, or a full-wave rectifier or a logarithmic amplifier or—well the mind boggles! Actually you can do even more, because the 2920 has *four* separate multiplexed analogue inputs, and eight separate sample-and-hold output amplifiers, some or all of which can be programmed as TTL compatible logic outputs (to indicate under or over frequency in the filter example, perhaps).

Take heart all you clever analogue circuit fans, because you still need the same skills as before to design a 2920 application program, only the hardware really changes. To describe a filter you require a mathematical function whether you use LC components or the 2920. When you use the 2920 however, instead of choosing component values to suit the mathematical function, you write a software program instead. You still have to be a bit of a clever-clogs to get the function correct in the first place of course, and there is really very little scope for suck-it-and-see tuning techniques when using the new approach!

Internally, the 2920 has an analogue to digital converter at its front-end and a digital to analogue converter to generate outputs. Each time the A to D takes a sam-


ple of the input signal, the 2920 executes its entire program of up to 192 instructions. The time it takes to do this determines the input sample rate and hence the bandwidth of the system. With the longest program possible, single input frequencies of up to 6.5kHz can be dealt with (13kHz sample rate).

The architecture of the 2920 is not comparable to any "normal" microprocessor because of the requirement for fast accurate computation and the lack of any external data or address bus needs. Instruction words are actually 24 bits wide, and the internal arithmetic unit uses 25 bit precision to reduce error accumulation. Because the 2920 is timed from a crystal controlled clock source, the time and temperature drifts of conventional low frequency components can be all but eliminated.

So there it is you linear fans, time to retrieve that microprocessor primer from the waste paper basket!
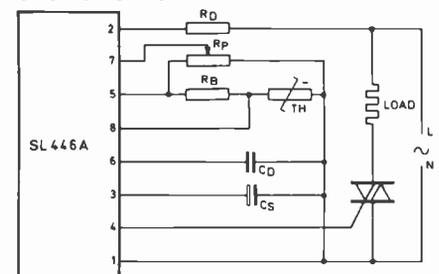
## ZERO VOLTAGE SWITCH

The **SL446A** from Plessey is a zero voltage switch intended for use in the on/off control of triacs and this device incorporates zero voltage point triggering in order to minimise radio interference.




Typical circuit for providing linear temperature control over a range of +5°C to 35°C.

Main applications are in switching resistive loads and replacing mechanical thermostats in central heating systems, washing machine heaters, water heaters and electric irons.

The device has a spike filter for reliable triggering and a pulse generator with a bistable arranged to eliminate half wave firing. A voltage sensing circuit inhibits the firing pulses when the supply is inadequate to guarantee proper circuit operation.

Another zero voltage switch in the same range is the **SL441A** which can be used to regulate a.c. power by varying the number of mains cycles applied to the load in a fixed timing period.



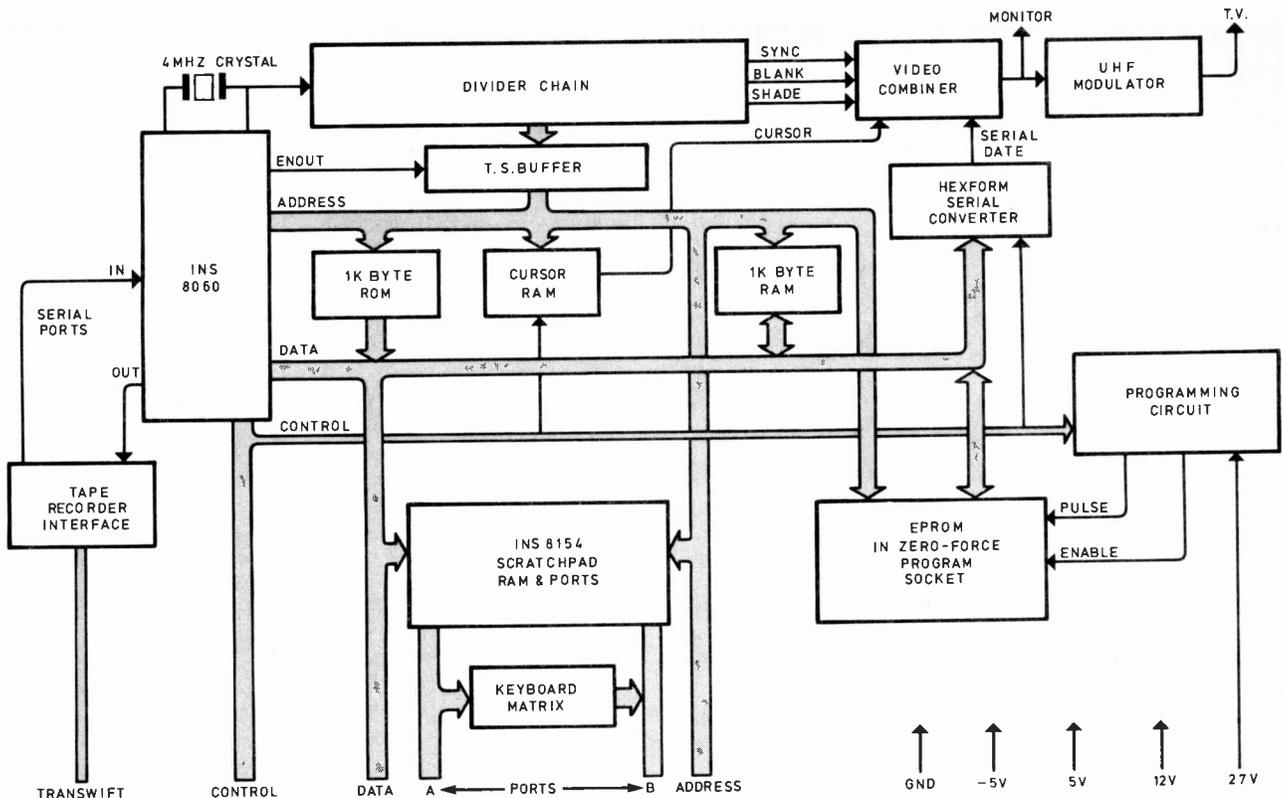

EO 250

## BLOCK DIAGRAM

Referring to the block diagram, a reasonably familiar overall pattern is discovered with bus lines, RAM, ROM, MPU, I/O ports, cassette etc. The details show some differences from the usual format; an EPROM burner is included, for instance, along with special RAM for the VDU cursor. The main difference is, however, in Softy's firmware itself. This is set up, basically, to manipulate the contents of three blocks of RAM — two  $\frac{1}{2}$ K pages and an area of 128 bytes of "scratchpad". Commands for the editing features as well as control of the ultra-fast cassette interface and EPROM burner are not typed in with alphanumeric characters but, instead, appear on the keys of the keyboard and are accessed via a "function" key, exactly as on a scientific calculator.

The VDU picture, as seen in the photographs, constantly displays 512 bytes in hexadecimal digit pairs. An area of reversed video (white characters on black) is also available at top and bottom of the TV picture—if your TV can show it. This is part of the 128 bytes of "scratchpad" RAM included in the INS 8154 RAM/IO chip. The screen itself is divided into four main areas of 128 bytes each, by shading, to assist the user in estimating the size and positioning of blocks of information. In addition, the user memory is used to store those posi-

tions on screen which are to be highlighted in a very bright shade for various purposes described below.

At the top of the screen four lines of reversed video may be displayed by adjusting the height control of one's set. Only the bottom one of these four is of major importance. It contains various useful bytes of information, such as current cursor address and contents of the SC/MP's registers. The meanings of these locations are shown in the annotated photograph.

The I/O ports of the 8154 device are used to scan the keyboard matrix, but may be utilised for hardware control and are brought out to the edge tracks below the keyboard—see the photograph of the p.c.b.

## EDIT COMMANDS AND POWER UP

As seen on the heading photo, most of the keyboard keys have a dual purpose—i.e. hex digits as well as commands accessed by first pressing the FN key.

After power-up, the RESET key is pressed, giving a random collection of bytes on the screen randomly highlighted by bright patches corresponding to 1's in the cursor memory. The FN key is pressed twice to clear the cursor memory with the exception of the bright patch over the top left byte. This patch denotes the write-cursor position—i.e. where the

next byte of information will appear if the keyboard keys are operated. To alter this byte, two hex digits must be keyed in, after which the user automatically moves onto the next location. The cursor may be stepped backward or forward by using the appropriate keys and hence any byte displayed may be altered—writing only occurring to the cursor position.

If the back or forward cursor keys are held down, the cursor moves a step at a time automatically until the 16th step when it will revert to stepping up or down the screen vertically one line at a time. When the cursor meets the top or bottom of the screen, the  $\frac{1}{2}$ K page displayed changes to the next adjacent—this may be the other half of the 1K of RAM or one of the two EPROM pages—if the user steps off the edge of the screen too many times (i.e. into a non-existent page), the machine aborts and must be reset before continuing. After reset, the cursor is at the top of the 1K of screen RAM and just below the user EPROM section. Thus, moving the cursor back takes it into the bottom of the lower  $\frac{1}{2}$ K page of EPROM. The contents of the EPROM placed in the zero-force EPROM socket may be copied into screen RAM by the "copy" command—accessed by pressing FN, followed by the "C" key. The full 1K is copied into the screen RAM by this process and may be altered by moving the cursor around and pressing hex keys

as described above. If required, the whole 1K may be stored on, or recalled from, cassette by the "RECORD", or "RECALL", Commands. Alternatively, an erased EPROM may be inserted into the zero-force socket and the 1K RAM contents burned into it by the "BURN" Command. In this way, EPROMS are very conveniently copied with or without modification in around 2 minutes.

Other text editing commands include a block shift. The cursor is positioned over the final member of a block to be shifted and the DEFINE Command pressed (after the FN key, of course). Backward shifts of the cursor leave behind highlighted bytes on the screen. When the complete block to be shifted (a maximum of 127 bytes) has been highlighted, the SHIFT Command is entered. This allows the back and forward cursor keys to shift the entire highlighted block one position at a time for 16 moves, followed by movements of one line at a time, throughout the 1K of screen RAM. This provides a very graphic and useful block manipulation facility.


In order to search for all occurrences of a given byte, the MATCH command is used followed by the byte to be matched. All occurrences are highlighted—yet another use for the cursor RAM. The extra highlights may be erased by pressing FN twice. This function has been used to highlight the word SOFTY on the screen photo.

The whole 1K of RAM may be filled with 1's (FF) by the CLEAR Command. This is used for selective block storage on EPROM. The erased EPROM contains just 1's—during programming some of these are turned into zero's according to the data presented. If a block of the EPROM is to be left unprogrammed, it must be presented with FF bytes only. Thus, the screen RAM may be filled with FF and a selected area written to by cassette or keyboard. The "BURN" Command will then store this block in the EPROM leaving the rest to be programmed at a later date.

The Softy firmware may be copied into RAM by the FIRM Command for modification by the user. This firmware comes on EPROM anyway and may thus be copied into RAM, modified and then blown into an erased EPROM for immediate use. Who says computers can't reproduce!
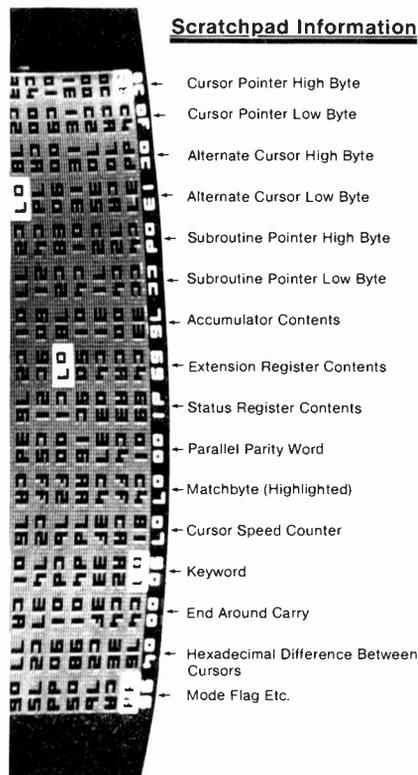
## PROGRAMMING COMMANDS

So far, screen editing and storage have been described without reference to the executing and testing of the routines being developed. As explained above, the heart of the Softy system is a SC/MP and routines for the SC/MP may be executed in screen RAM, EPROM or Scratch Pad



using various other commands on the keyboard—this facility is useful for developing programs for the SC/MP microprocessor without any extra hardware. The register contents are continuously displayed at the top of the screen, as indicated, and large numbers of uses can be envisaged for the machine as a controller.

There is a very graphic offset calculation facility included on the Softy, which is accessed via the FIX Command. This causes the current position of the cursor to be stored. The cursor may then be moved to any new position within the program under development. The offset between stored and current cursor locations is continuously displayed at the top of the screen, as are the absolute addresses of the two cursor locations. The current address location of the cursor is always displayed at top left of the screen, and screen RAM starts at address OCOO.

## DEVELOPING GENERAL SYSTEMS

Most of the above editing, storage and program writing facilities would be very useful for developing any MPU system and it is here that the Softy finds its most exciting application. The system is designed to look like a 2K block of intelligent memory. That is, it has data, address and control busses to fit into any system at any base address. While the target system is not processing and using

the busses, Softy may be used to Write a program into screen RAM using all its facilities for making the job easy. When finished, the program is automatically in the embryonic system's memory for running on the target's MPU, using the Softy VDU for output as necessary. No editing firmware or even RAM is necessary in the test system—Softy supplies it all.

The manufacturers, Videotime Products, have now produced an interface card with all the address and data bus lines fully demultiplexed, along with general address decoding to allow any bus-oriented MPU to be used. The designer sets up links on the interface p.c.b. to decide where in the MPU system's memory Softy will sit. All that is needed is an MPU with its own processor clock and RESET switch to develop a complete MPU system. The MPU Address and Data busses, plus R/W, are connected to the interface board and Softy takes over for program writing and hands back control to the external MPU for execution.

The final software is blown into EPROM and, along with some RAM etc., may be attached to the MPU system under development to complete the machine. The photograph of the whole system shows the interface board connected to a prototyped Z80 system. The prototype contains MPU, clock and RESET switch.



Videotime are hinting at producing a variety of such MPU p.c.b.'s, for different processors, to save the prototyper even the trouble of connecting Veroboard and ribbon cables to his favourite MPU!

## HARDWARE AND CONSTRUCTION

I did not have the opportunity to make up a kit from scratch and can only comment from an external viewpoint. The p.c.b. is covered with solder-resist and has a silk-screened component legend which should make construction easy. Tracks are no closer than usual, though components are a bit crammed around the DIN socket and a large Mylar capacitor did impede adjustments to the cassette interface pot quite considerably.

The keyboard is of the "click" calculator type and showed the usual tendency towards variation in performance but seemed adequate for the job.

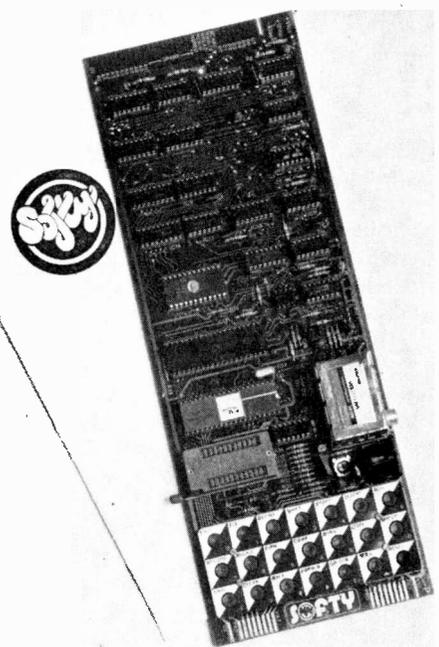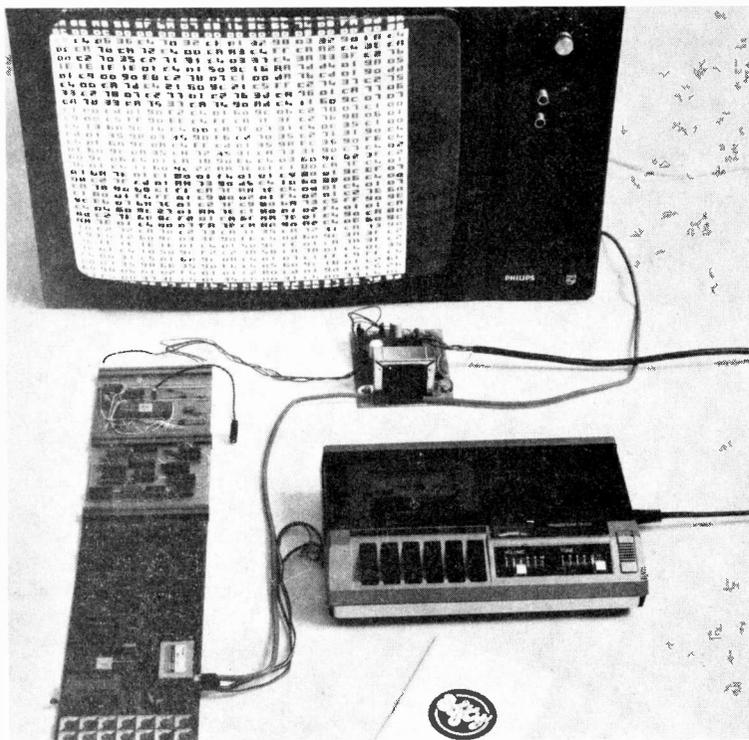My version was not through-plated and thus contained pins through the p.c.b.—perhaps a little disappointing on an article not made "down" to a price in most other ways—but again, in my experience, perfectly adequate. It was very nice to see a zero-force socket for the EPROM as standard, as well as u.h.f. modulator giving excellent TV performance.



The EPROM programmer will program both 2708's and multi-supply 2716's (in two halves) and these devices require several supply voltage levels. Videotime sell a small Power Supply Unit which proved adequate to power the complete system as shown in the photo—i.e. including a simple target system.

The EPROM burner is straightforward and controlled by a 555 timer to program at the maximum theoretical speed for the 2708 family of EPROMS (around 110 seconds). A 27 volt supply is included in the Videotime power supply unit for this purpose, but is left unconnected, for purposes of safety, until required.

The cassette interface is controlled by software and is little more than a couple of lines connected to serial-in and serial-out pins of the SC/MP processor. As a consequence, the "Transwift" system runs at over 2000 Baud (equivalent) and is considerably less prone to tape-speed variations than many other simple interfaces. The cassette plugs into a Din socket, just above the keyboard, which is wired to the international standard.

The cursor RAM is formed by a single bit by 1K 2102 chip. This is accessed by the VDU counter circuitry at the same time as the main VDU RAM and fed to the video mixing circuitry to brighten the VDU picture at the necessary locations as the electron beam strobes across the TV tube. While the SC/MP is not processing a program in user memory, it hands the Address and Data busses over to the VDU counters which address one of the four memory pages displayable.

The page selected depends upon the state of two I/O lines on the 8154 chip which are kept updated by the firmware. The memory map of the system is not given and this appears in Table 1.

The address map depends upon a 74LS42 decoder and could easily be changed if necessary—though what this would do to the firmware, I can't imagine! A system under development would see Softy mapped out as in Table 1, in its memory, but at a different base address from 0000 if required.

TABLE 1

Address	Memory selected
0000—03FF	SOFTY's 2708-based firm-ware
0400—07FF	RAM/IO (8154) with some addressing redundancy
0800—0BFF	2708 (or 2716) Socket for user's EPROM
0C00—0FFF	VDU RAM (workspace) in two ½K pages of display

The VDU, of course, is a very specialised binary data display device and has nothing to do, for instance, with displaying ASCII characters. It is a device for displaying the exact binary contents of 512 memory locations—in hexadecimal digits directly. Thus, a special character generator ROM is used. The VDU electronics presents the 8 bits from any memory location to the ROM as two 4 bit "nybbles", for conversion into hexadecimal characters on a TV screen. This obviates the necessity for the usual

software routines used to convert bytes into nybbles and nybbles into ASCII codes.


#### MANUAL AND SOFTWARE

As can be seen from the above, the software is thoughtful and very graphic. A few more traps against inappropriate commands could have been included, I feel, even though the whole thing is contained in just 1K of ROM. Try block shifting into the EPROM, for instance, and everything is lost—or, as mentioned, try shifting the cursor to a non-existent page and the machine locks completely.

A lot more description of the software itself would be of considerable use in modification and, most importantly, in using subroutines contained within the firmware. It is an excellent idea to include a special command for copying it to screen RAM—but of little use without, at least, an annotated listing.

The manual makes it clear from the beginning that Softy is a tool for those who know what they are doing. To this end it is very concise and makes reference to other literature, such as data sheets on specific devices. A reference table is given of the SC/MP instruction set, as well as an architecture diagram for both the SC/MP and the RAM/IO and a potted description of the RAM/IO's use as a parallel I/O port.

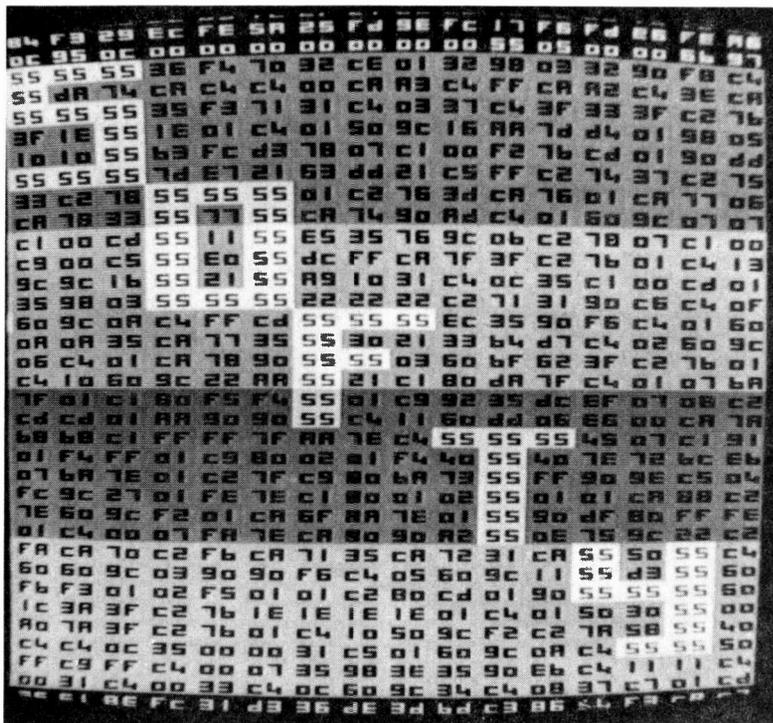The Softy circuit diagram is given in complete detail as well as an adequate explanation for anyone familiar with MPU engineering. This is most useful for those willing to take the basic tool and use or modify it in their own way.



Construction is hardly covered at all but should be quite clear due to the component position labelling on the p.c.b.—all component numbering starts at the top right of the p.c.b. and should save endless

hours of searching for a particular number of component.

Another section of the manual includes interfacing to the external system—though the SC/MP data sheet is essential

to a complete understanding of the device. Control signals and memory—select logic are mentioned as well as product and program development.

An interpretive language of a very simple nature is actually listed for use in development, along with a couple of elementary sample programs to help the user familiarise him or herself with the system. The final section of the manual explains the software (annotated listing included) for interfacing Softy with an ex-GPO BAUDOT code printer. A little more on hardware would be useful at this point, along with methods of attaching it to the more common 8-level ASCII machines.

Any well thought out tool can be made to perform wonders in the right hands. Think how a good engineer can extract complex information from an electrical device using just an oscilloscope. Softy is in this class—it is a well-constructed bench tool for anyone dealing with MPU products and requiring development and test facilities. It should not be placed in the lengthening string of hobbyist computers, each vying with the next for higher level languages and more photographic VDU displays.

#### Acknowledgement

The Softy was originally designed—hardware and software—by Barry Savage. Phil Morris, of Videotime Products, has updated the machine and designed the interface board for prototyping a general MPU system.



## Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

### PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for..... (amount).


PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

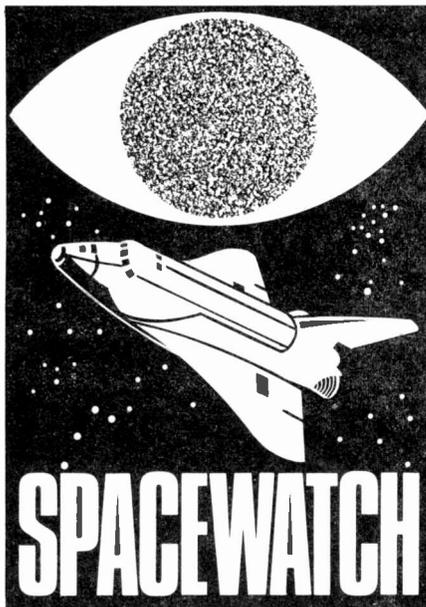Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53828. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.



**FRANK W. HYDE**

## PIONEER 11

Pioneer 11 is on its way out of the Solar system and into the Galactic space and none will know of its final fate. Its last encounter was the planet Saturn. At that time it had travelled more than 2,000 million miles from Earth, having started its journey in April 1973. The vehicle has more than justified the costs involved and is yet another tribute to the technology of space engineering. The first flypast was concerned with the planet Jupiter and opened the first chapter of a new view and model of the largest body in the Solar system. While Pioneer 11 continued its journey toward Saturn aided by the kick (gravitational) of the fastest rotating body, the Voyagers were to open the second chapter of the chronicle of Jupiter.

However all might well have been lost for there was a near case of disaster as Pioneer 11 approached Saturn's rings from the underside. The vehicle was at a distance from Saturn of 2.53 Radii 23 minutes, after crossing the plane of the ring system inside the orbit of Saturn's moon Janus, but not quite at the A ring. Calculations show that the spacecraft passed about 900 miles below and 1,500 miles slant distance to the "Pioneer Rock". It was discovered as a result of the change of behaviour of some of the on-board instruments. The charged particle instruments showed that during the time of the near encounter the flux of the 2-4MEV electrons dropped to a level a thousand times less over about 10 seconds.

The period of the drop-out indicates a body of the order of 124 miles in diameter. Earlier it had been thought that there was another body about this diameter. It is a 50-50 chance that this "Pioneer Rock" is that object. It would be unlikely that it could be discovered from earth based telescopes, being obscured by the ring

system. A further confirmation of the "new" moon came from the magnetometer data. The short time resolution instrument which showed a ten second oscillation at 15 seconds after the dip in the particle counts. Thus the conclusion was reached that this was a small body in the plane of the ring system, a body that was conductive.

The deflections of the path of the spacecraft have been studied. These are caused by the gravitational fields of three of the Saturnian satellites Iapetus, Rhea and Titan. The indications are that these three moons are of low density and made up of ices in the main with little rock or iron. These data also confirm that the flattening at the poles is as predicted but that the shape is not ellipsoidal as it would be if the planet was homogeneous. It would seem likely that there are extensive areas of inhomogeneities. Some depressions may be as much as 75 miles.

Nothing has so far come to light to cause rethinking of the present models of Jupiter or Saturn. That is that the interior core of Saturn is about the same size of that of the Earth but three times as dense and consists of rock and iron. Around this would be a layer of metallic hydrogen which probably extends to about 0.58 of radius of the planet. Above that a layer of liquid hydrogen and then the atmosphere a gaseous mixture about 200 miles deep. It is here that there may be some need for remodelling.

## MAGNETIC FIELD

The magnetic field is not so extensive as that of Jupiter. The magnetic field and the pulsating magnetosphere extended out to about a hundred Saturn radii before the spacecraft was free. This is half the distance found in the case of Jupiter. The magnetic field was very uniform which suggests that it is an uncomplicated dipole field. The dipole axis is within 0.1 degree of the spin axis. This fact is unique for the Solar system. The centre of the field does not coincide with the centre of the planet and is southbound at the equator. This is not unusual.

The magnetic field rotates with the planet at its rotational period of 10h 14m and this means that as it is faster than the orbiting satellites a "wake" is created in front of the satellites. The satellites would be subject, that is those inside the magnetosphere, to some disturbance. In fact a wavelike disturbance did appear when Pioneer 11 crossed Titan's orbit. A symmetry was observed in the stable inner region of the magnetosphere. This is partly responsible for the "cleaning up" of trapped radiation.

It had been anticipated that Saturn's ring would clear any charged particles in the inner area of the magnetosphere. It has been stated if this were not so Saturn would show strong radio emission. There is some confirmation of that in the writer's own experience. When observing Jupiter radiation in 1962 it was decided to use the 1,000 ft. radio telescope at Aricebo to "look" also at Saturn. No sign of radiation was observed. It was concluded that

Saturn did not radiate or there was a mechanism to stop the radiation. This shows the importance of the spacecraft missions.

Some of the preliminary results show some details of various conditions. For example the infra-red radiometer could not detect the unlit side of the planet's rings. Even the Sun side was indicating a temperature of 70K. Some readings were available to provide average values for the A and B rings. The temperature of Titan at the cloud tops was about 75K. It is not expected that day and night temperatures will be available.

A weak hydrogen glow was detectable throughout the saturn system. It was noted that the ultraviolet emission brightened when the scan crossed the ring plane. This indicates that hydrogen clouds are present. Also it was noted that in the north and south polar regions brightening also occurred but was absent in equatorial regions. Ultra violet was detected at Titan but it extended only a short distance from the moon. It is unlikely that hydrogen cloud filled the satellite's orbit. It seems that the temperature at the exosphere, 1,110K, is rather lower than that of Jupiter.

## ATMOSPHERE


A model of the atmosphere has been constructed which shows a surface pressure of about 15 atmospheres. Here the layer is hydrogen and helium at  $-65^{\circ}\text{F}$  this merges into clouds of water-ammonia at a temperature of  $45^{\circ}\text{F}$  succeeded by a layer of water ice clouds starting at  $9^{\circ}\text{F}$  and falling to  $-63^{\circ}\text{F}$ . The next layer is possibly ammonium hydrosulphide ice clouds falling to  $-135^{\circ}\text{F}$ . Then another layer of clear hydrogen and helium falling to  $-210^{\circ}\text{F}$  with ammonia ice clouds, above this a thin ammonia haze at  $-280^{\circ}\text{F}$  at a pressure now down to 1 atmosphere. Above this level very thin dust particles followed by the rest of the clear upper atmosphere again hydrogen and helium, at 0.1 atmosphere the temperature falls to  $-306^{\circ}\text{F}$  rising again to  $-240^{\circ}\text{F}$  at the level which has fallen to 0.01 atmosphere.

The satellite Iapetus exhibits a peculiar exterior appearance. It is about 900 miles in diameter and shows a wide difference in brightness very high one side and dark the other. The bright side is consistent with highly reflective material ice or snow but it is not possible to determine at this stage the composition of the dark side. Iapetus is the farthest satellite from its parent.

## TAILPIECE


There is evidence to show that the Sun is shrinking. The Sun has been measured at noon on every day since 1750. The disk is measured at high noon on the transit telescope. The mechanics are that as the limb crosses the fixed meridian wire the time is noted and when the trailing limb crosses the wire the time is noted once more. From these two timings the horizontal solar diameter is determined.

# ...all in Next Month's issue!

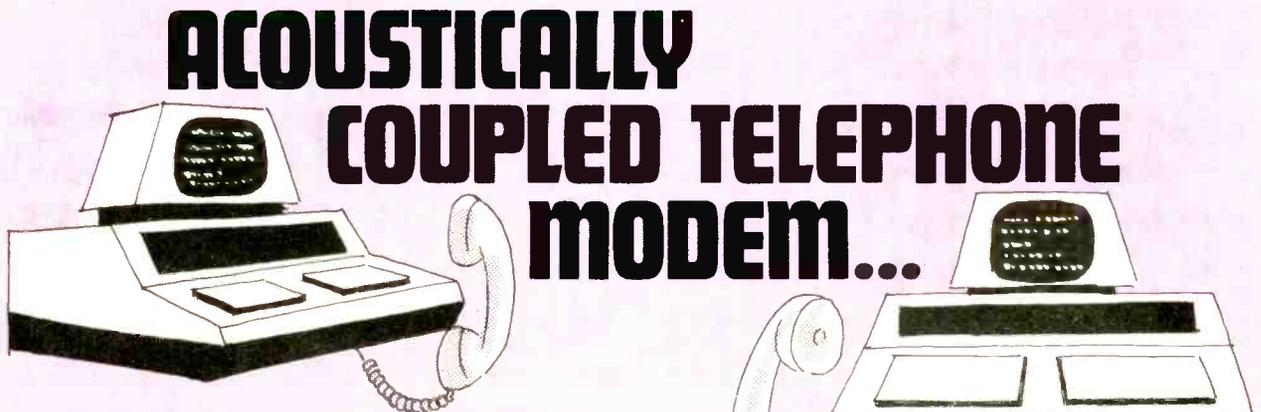
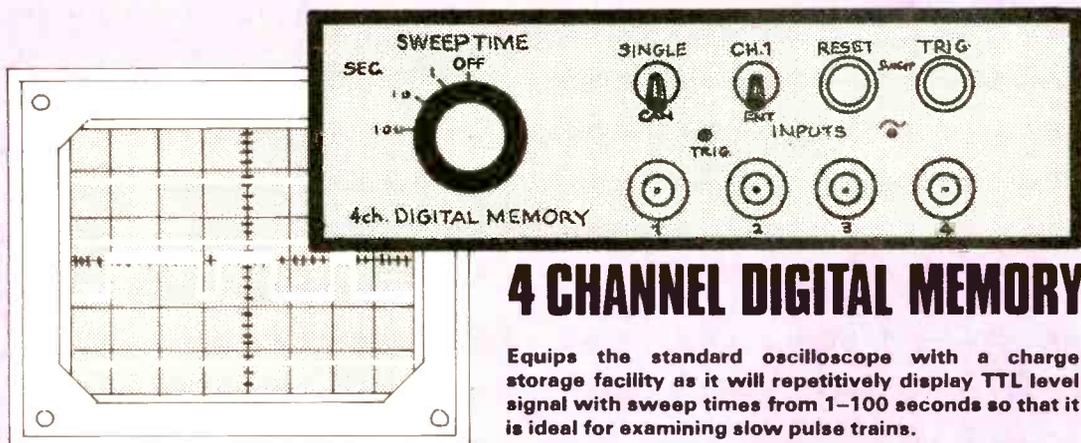
## ACOUSTICALLY COUPLED TELEPHONE MODEM...

If you have a telephone, then your computer can be coupled to any other computer—anywhere!!! Full "nuts n' bolts" constructional details and application notes are included. With your assistance, we shall also follow up with a Modem Users' Register.



### 4 CHANNEL DIGITAL MEMORY


Equips the standard oscilloscope with a charge storage facility as it will repetitively display TTL level signal with sweep times from 1-100 seconds so that it is ideal for examining slow pulse trains.

*Also...* **DYNAMIC NOISE LIMITER**  
(U.K. Mainland sales only).
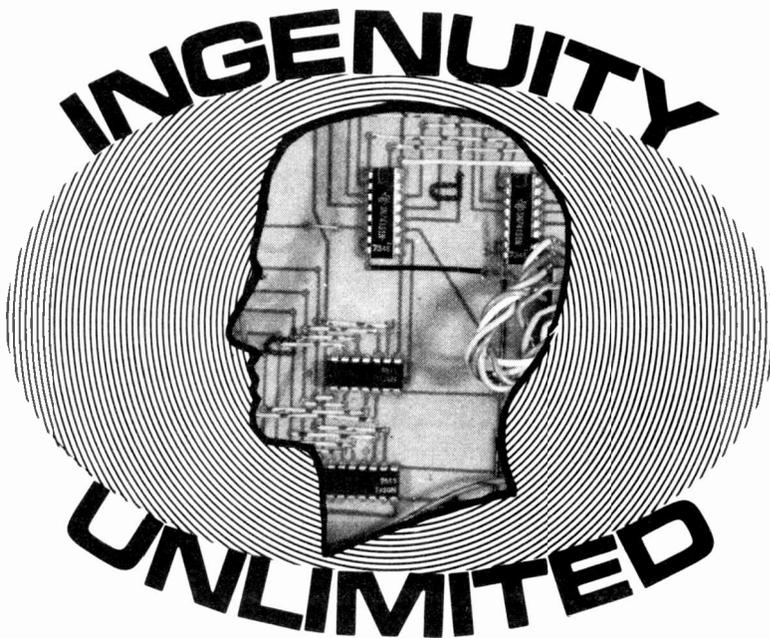
# PRACTICAL ELECTRONICS

OUR FEBRUARY ISSUE WILL BE ON SALE FRIDAY JANUARY 11 1980






A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

## SIMPLE AUTOFADE

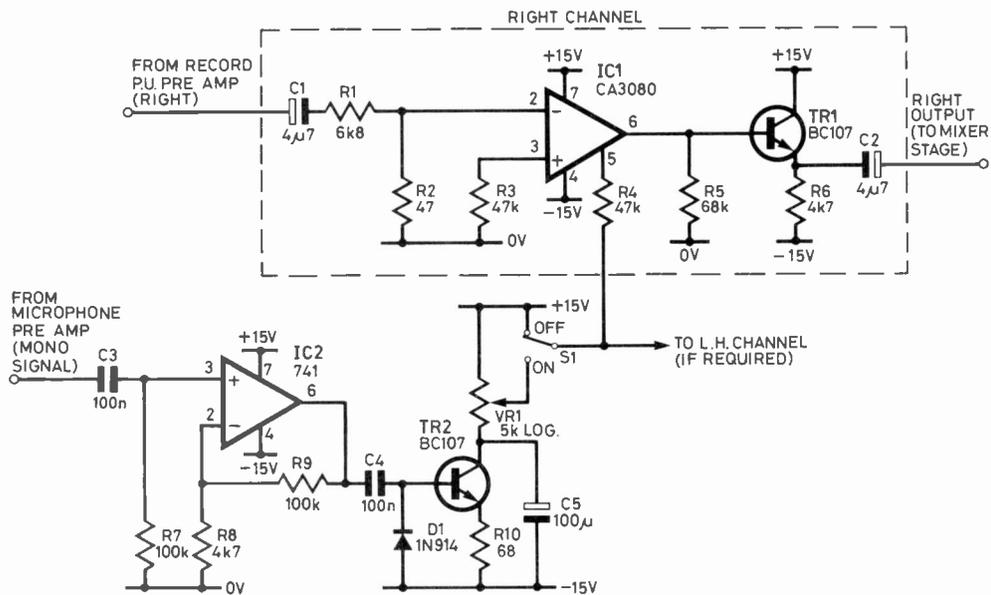

**T**HIS circuit automatically fades signals from one source (e.g. records or cassettes) when a signal is present from another source such as a microphone. This permits, for example, records to be faded whilst the DJ is speaking, and this facility is easily and cheaply added to most mono or stereo mixers.

The signal from, say, a record pick-up preamplifier is fed to a CA3080 operational transconductance amplifier, the gain of

which is controlled by the current into pin 5. The microphone pre-amp signal is amplified by IC2 and rectified by D1 and TR2, providing the control current for both channels. S1 enables the autofade action and VR1 adjusts the depth of fade required. C5 determines the attack and decay times (20ms and 500ms respectively), while R4 alters the nominal gain of the circuit (approximately 0dB).

Sensitivity at the microphone input is

about 35mV for full fade, and may be increased by reducing R8. Maximum input is 2V rms (more if R1 is increased), and fades of over 40dB are possible.

T. P. Hopkins,  
Haywards Heath,  
West Sussex.

## R/C SERVO

In the servo circuit shown in Fig. 1, ZTX300 and ZTX500 transistors are used throughout because of their small size. They are rated at 500mA which is more than sufficient for small modern servo motors.

The circuit works as follows: The 555 is connected as a monostable whose period is controlled by R5/C2 and the control voltage on pin 5. This voltage is derived from VR1, the servo feedback potentiometer and RA/RB. TR1 is a simple inverter. TR2 and TR3 are switched by TR1 and the output of the 555. Three possible conditions of the circuit can occur. (2a) shows the input pulse and the 555 period equal and both TR2 and TR3 cut off. (2b) shows the input pulse shorter than the 555 period. Now TR3 can switch on for a short while. This drives the motor via TR4, TR5, TR6. Similarly, in (2c), TR2 drives the motor via TR7, TR8, TR9. C3 and C4 smooth out the drive between pulses. The motor is connected by the servo gearing to the potentiometer, VR1. Thus the motor will move the potentiometer until the input and the 555 period are equal again.

Fig. 3 shows a simple servo tester circuit. This is simply a 555 connected as an astable to simulate the output of the decoder, i.e. a variable negative pulse of between one and two milliseconds every twenty or so milliseconds. Using this tester it is then useful for setting all them servos to the same neutral position which is very useful on a multi-channel system.

RA/RB should be selected to suit the servo used.

N. Roche,  
Willingdon,  
Sussex.

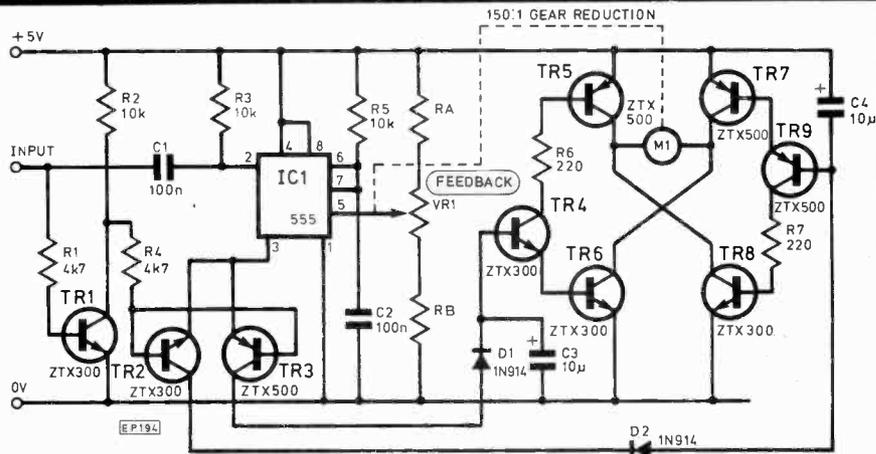


Fig. 1

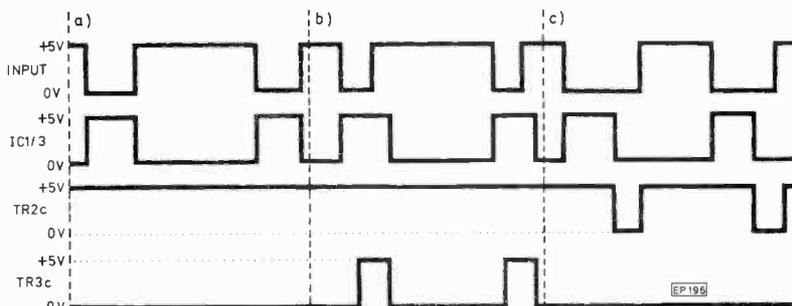


Fig. 2


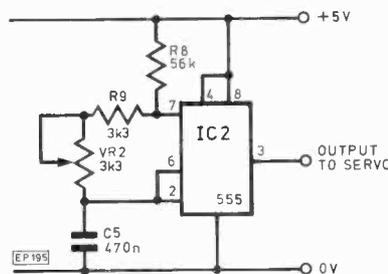


Fig. 3

## CAR BURGLAR ALARM

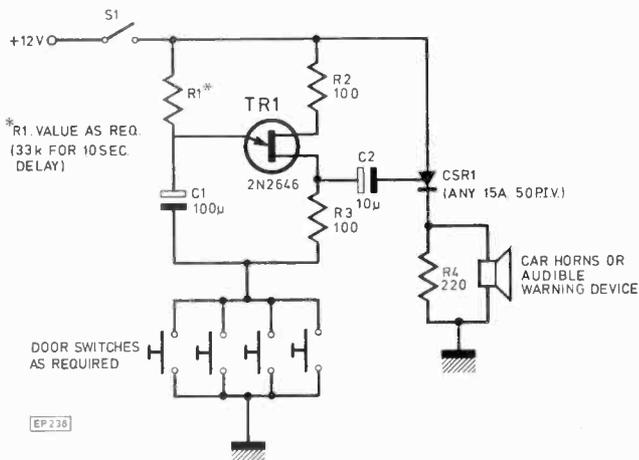


The unijunction TR1 is used as a time delay device with the switch-on time determined by R1/C1 (33 kilohms gives a switching delay of approximately 10 seconds). When the unijunction switches, the o/p pulse via C2 triggers CSR1 which activates either the car horn(s) or some external audible warning device.

R4 is used as a hold on path for SCR1 to prevent switch-off of the thyristor due to the interruptions of the car horn circuitry.

The circuit thus enables the driver to switch on the alarm internally before shutting the rear door, and vice versa when opening the door.

C. Guthrie,  
Hardgate,  
Clydebank.

## PHASED WHITE NOISE

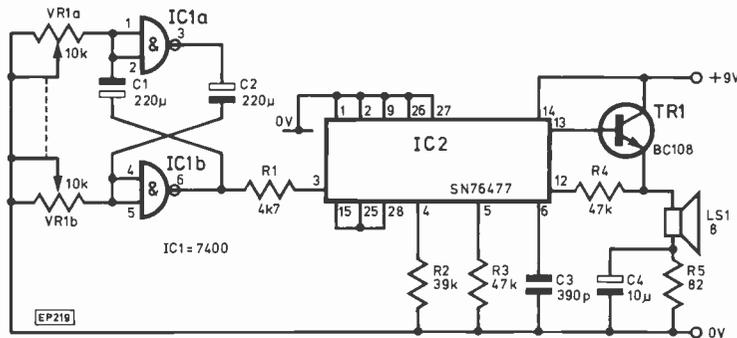

**T**HIS circuit, using the SN76477N sound effects chip, produces a phased white noise output when VR1 is rotated, such as would be obtained by a system using several phase shift stages being fed with an input from a conventional white noise generator. The white noise section comprises the LSI chip, together with its associated components, which provide the programming requirements.

A single BC108 transistor feeds an 8 ohm speaker, together with a series resistor, which provides an audio output. In many cases the audio output will be taken directly to an amplifier, mixer or tape recorder.

Pin 3 of the SN76477N is connected, via R1, to the output of an astable multivibrator constructed around  $\frac{1}{2}$  IC1 (7400). VR1a and VR1b (dual gang pot) control the astable's rate.

The phasing effect is produced because the SN76477N exhibits a kind of voltage controlled filter effect when a slow clocking oscillator is connected to pin 3 of the device. If the speed of the external clock is below that of the SN76477N's internal noise oscillator then the internal oscillator is overridden and external circuit takes over.


The circuit can be used to provide numerous special effects such as jet engines, rainstorm, thunder, wind, etc., in its present form. By connecting a 100nF capacitor from pin 21 to ground, a 1M pot from pin 20 to ground and re-programming pins 25, 26, 27 as follows: pin 25—logic 0, pin 26—logic 0, pin 27—logic 1.

A further range of aircraft, helicopter and train sound effects can be obtained by operating VR1. The circuit can be easily constructed on 0.1in Veroboard and its recommended that a 28 pin DIL socket be used for IC1.

If the speaker output is not required omit TR1, R3, speaker, R4 and C3 and connect a 47k resistor from pin 11 to ground, a 10k resistor between pins 12 and 13 and connect to external amplifier via a 2.2µF/10V (C6) electrolytic capacitor with +ve terminal to pin 13. It is hoped these notes will encourage experimentation with this interesting and versatile i.c.

R. Otterwell,  
Rochdale,  
Lancs.

## GLOW PLUG SUPPLY

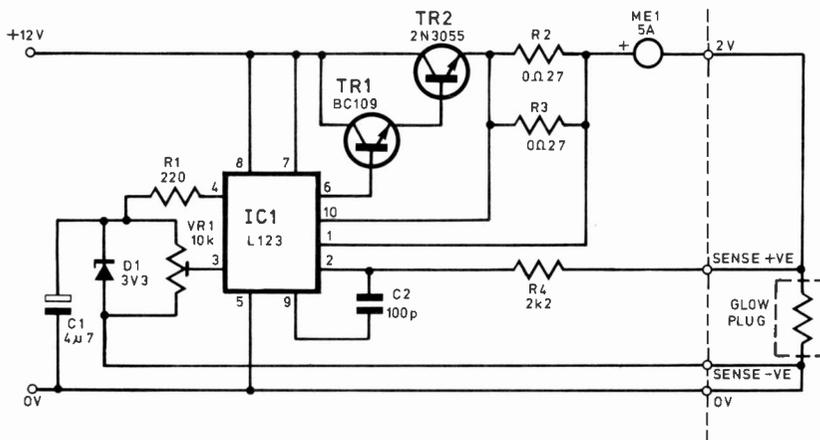

**T**HIS circuit provides a regulated 2V or 1.5V supply for glow plug engines and overcomes the problems of battery internal resistance and connecting lead resistance by sensing the voltage at the plug terminals.


The internally regulated voltage at pin 4 is divided down and applied to pin 3 as the reference input. If the voltage at the +ve sense input differs from this then the output from pin 6 varies inversely to compensate. The -ve sense input is effectively connected in series with the negative supply lead, any voltage drop due to this lead's resistance is reflected into pin 3 by the level changing action of D1, the preset across D1 allowing 2V or 1.5V plugs to be accommodated.

The circuit is current limited to 5A by R1, the meter indicating o/c or s/c plugs and also plugs wet with fuel oil by a higher than normal reading. The unit is operated from a 12V battery which is normal field equipment for use with electric starters etc. Heavy duty twin cable can be used as connecting leads, the outer conductor carrying the plug current and the inner the minute sensing current.

R. MacFarlane,  
Newtonhill,  
Aberdeen.

# A SEMI-AUTOMATIC

# DISCO CROSS-FADER

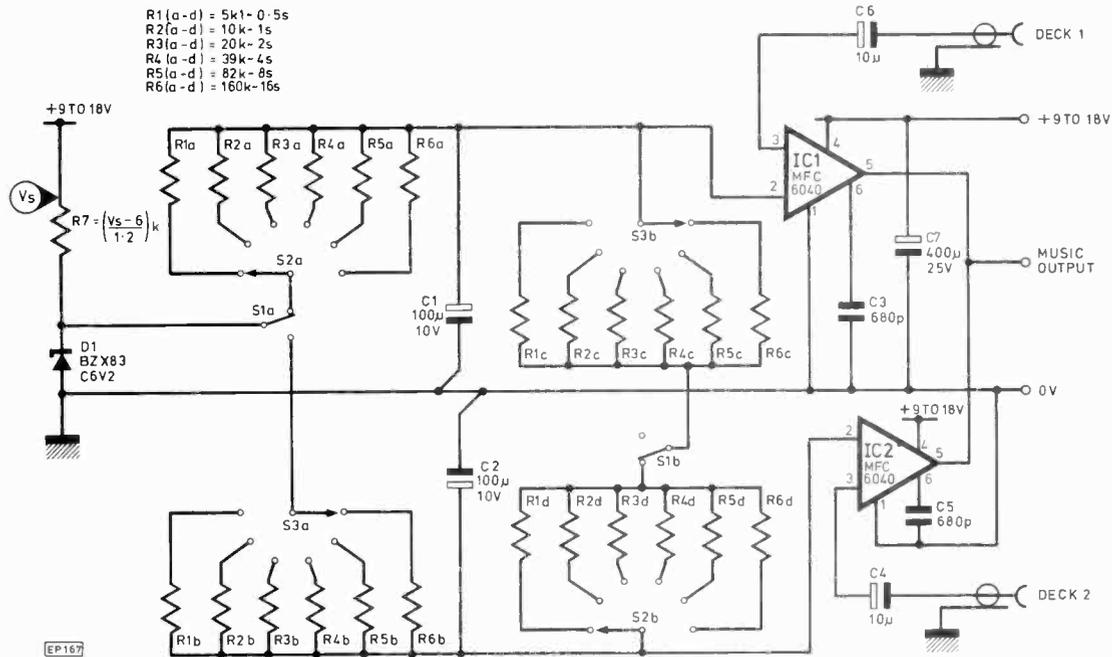

THE circuit shows a semi-automatic cross-fader for discotheque applications. A cross-fade is effected merely by operating a toggle switch.

The MFC 6040 electronic auto-attenuators are operated by mutually symmetrical control voltages. The resistors R1 (a-d)-R6 (a-d) are selected to give a range of time constants from 0.5 to 16 seconds for


the cross fading action. These are selected by two rotary switches, one for each deck, beforehand.

It is advisable to keep the signal inputs below 100mV to avoid excessive harmonic distortion. At 100mV this varies from 0.6 per cent ( $V_s = 9$ ) to 1 per cent ( $V_s = 18$ ). In any case, the i.c.s have a gain of 13dB (approx.).

C1 and C2 can be electrolytics, since leakage is not a critical factor, the charging current always being maintained on the relevant capacitor.

Ben Duncan,  
 Market Rasen,  
 Lincoln.

## LOW PASS FILTER

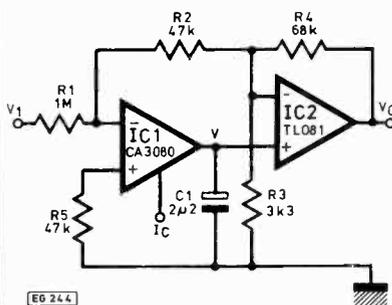

THIS filter is built around an operational transconductance amplifier, the CA3080, and is a simpler alternative to double integrator VCFs where only a low-pass function is required. The transconductance,  $k$ , of the 3080 is directly proportional to the control current,  $I_c$ , over a three decade range, allowing a similar variation in time-constant.

The circuit is basically an integrator with negative feedback which converts it into a low-pass filter. Because the output stage of the 3080 acts as a current source, it is important that there should be no load on it apart from the capacitor, especially if very long time-constants are required. This is achieved by buffering the output with an f.e.t. input operational amplifier, and connecting the feedback resistor, R2, to the inverting input of the buffer, which is held at the same voltage as the non-inverting input by op-amp action.

It can be shown that the transfer function of the filter

$$\frac{V_0}{V_1} = \frac{-R_2}{R_1} \frac{1}{1 + sC_1/k}$$

which is the expression for a low-pass filter with time constant of  $C_1/k$ . The time constant is inversely proportional to the control current,  $I_c$  and will vary between 1ms and 1s with the 2.2µF capacitor shown, for  $I_c$  in the range 0.1-100µA.


The main drawback of the 3080 in this application is that the peak output current is limited to the value of the control current. To allow a reasonable input range, the signal must be attenuated at the output of the 3080 by a factor  $G$  where:

$$G = \frac{R_1}{R_2} > 20 \frac{V_1}{V_{Peak}}$$

To restore the signal level at its output the buffer has a gain of  $G$ . For the circuit shown  $G$  is 20 so a peak input of 1V can be accommodated.

Applications for this circuit include an envelope generator for synthesizers, where the long time constants obtainable are particularly useful, and since all the parameters can be current/voltage controlled, the circuit lends itself to remote control.

J. J. Lambe,  
 Farnborough,  
 Hants.

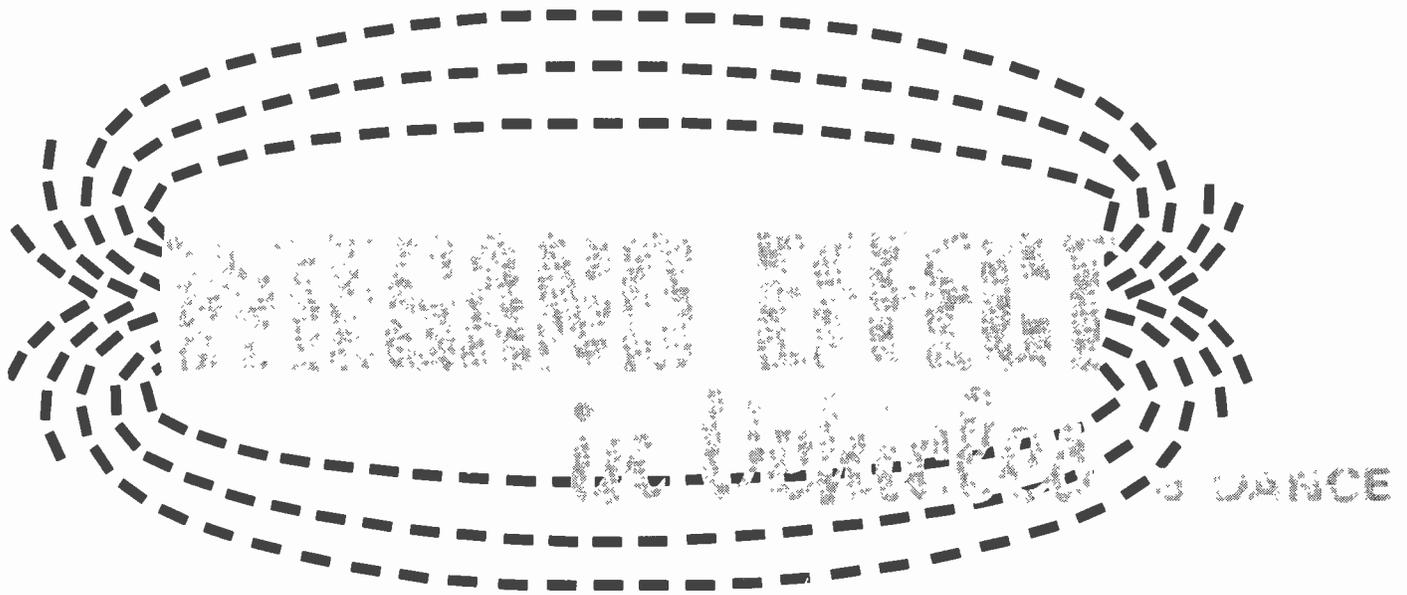

THE classical method of timing the ignition sparks in a vehicle requires a cam to open a pair of contacts, but most vehicle owners will be aware of the troubles which can occur when these points are not cleaned and set at regular intervals. Some of the simpler electronic systems employ a pair of contacts, but the ignition coil current does not flow through these contacts and the absence of sparking at the contacts greatly increases reliability. More advanced timing systems have employed magnetic and optical contactless sensors which produce pulses at the correct times. This article describes a new type of contactless magnetic sensor which enables considerably simpler circuits to be used than with other contactless systems and which is therefore considerably cheaper.

### WIEGAND WIRE

The new system employs a small, thin specially processed wire known as a Wiegand wire (after John R. Wiegand who discovered an unusual switching effect). A section diagram of a distributor using this technique is shown in Fig. 1. The Wiegand wire is located in the lower leg of a slotted structure which also carries two magnets. The permanent magnet in the upper leg provides a saturating flux to the Wiegand wire in the absence of a rotating vane.

The rotating vane is made of a soft magnetic material and has as many fingers as the number of cylinders in the vehicle. When one of these fingers passes through the slot between the saturating magnet and the Wiegand wire, it effectively provides a short circuit for most of the magnetic flux from the upper magnet so that the small magnet in the lower leg provides the flux required to reset the magnetic switching wire. This small magnet is orientated so that it provides a flux of the opposite polarity to that from the upper saturating magnet.

A coil of wire is wrapped around the Wiegand wire. Each time the magnetism in the wire is reset, a sharp pulse is produced across this sensing coil. The amplitude of the pulse is typically a few volts, so it can be used without further amplification to trigger an electronic ignition circuit. The low impedance of the coil avoids any troubles due to noise pick up. The pulse is very sharp, the width of the pulse at half the peak height being typically 20µs, so the timing can be made very accurate.



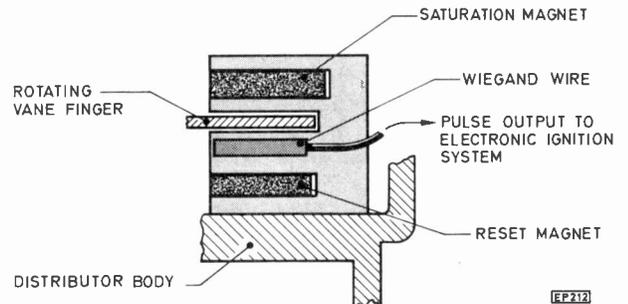


Fig. 1. A section of a distributor employing a Wiegand wire to generate the timing pulses

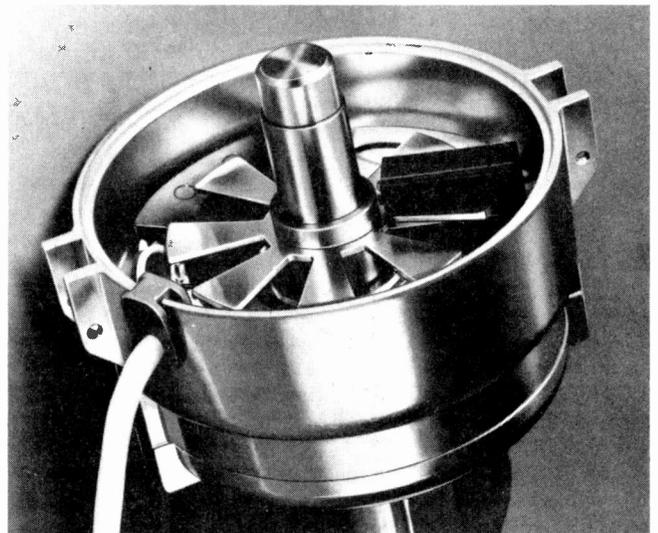

A Wiegand distributor; note the rotating vane made of a soft magnetic material

An advantage of the new technique is that no wires are required to carry any power to the sensing head. The two output leads from the coil (one of which can be earthed) are the only output connections required and this greatly simplifies the wiring.

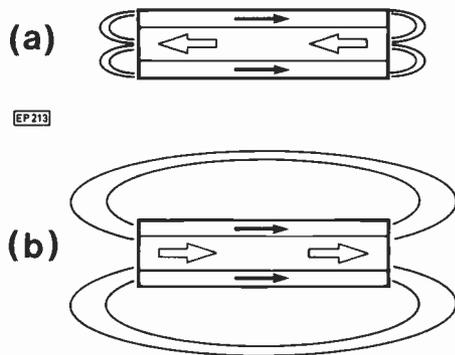

**Fig. 2. A Wiegand wire (a) with no external applied magnetic field and (b) with an applied field great enough to reverse the direction of magnetisation of the core. Note the external field from the wire is much greater in (b) than in (a)**

The time of switching of the Wiegand wire is a threshold effect determined by the level of the magnetic flux, so the pulses have the same amplitude and duration over the entire speed range of the vehicle from 'tick-over' to the maximum permissible engine revolution rate.

This type of ignition timing system can operate over a very wide temperature range with excellent stability. Indeed, the Wiegand wire is able to operate from  $-196^{\circ}\text{C}$  (liquid nitrogen temperature) up to more than  $260^{\circ}\text{C}$  where the insulation of the wire may fail. The magnetic flux required to produce switching is almost constant over the temperature range. The output pulse amplitude variation with temperature is less than 5 per cent over a wide temperature range.

The output pulse from the Wiegand sensing coil is passed to a transistor switching circuit which allows a tank capacitor to discharge through the ignition coil so as to produce the ignition spark at the correct time. It is claimed that maximum combustion efficiency can be ensured using this system which maintains the accuracy of the timing to 0.25 degree.


Wiegand systems are immune to the presence of dust, smoke, fuel or other vapours, vibration, dirt and moisture. There are no contact points to maintain and the system can provide a rate of engine revolution indication if required. A great advantage is the simplicity of the sensing unit and associated circuitry. The use of a Wiegand distributor will not alone improve the performance of a perfectly tuned engine, but it will normally improve considerably the reliability of racing cars under severe environmental conditions.

### THE WIEGAND EFFECT

The Wiegand Effect is exhibited by wires made of a ferromagnetic material which have been suitably worked at the correct temperatures. Initially a homogenous wire about 0.25mm in diameter and little more than 10mm in length is taken; this wire is cold worked by twisting and stretching it, after which it is thermally tempered at about  $300^{\circ}\text{C}$ .

The wire thus produced has a magnetically 'soft' inner core which is easily magnetised by a weak magnetic field, but this inner core is surrounded by a shell of magnetically 'hard' material which requires a much larger field to magnetise it.

In the absence of an external magnetic field, the field from the outer shell of the Wiegand wire will pass through the soft core material with the result that the total external field due to the core and outer shell will be negligible. If an asymmetrical field is now applied so that its polarity is essentially parallel to the shell of the wire, a sudden reversal of the polarity of the field of the core occurs as the external field reaches a certain threshold intensity known as  $H_{\text{set}}$ . The flux from the core and from the shell now re-inforce each other externally so that the external magnetic field is greatly increased.

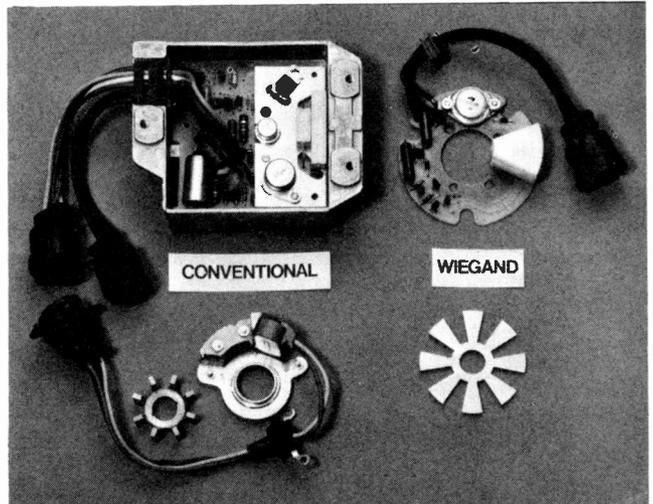

**The Wiegand electronic ignition system on the right hand side employs only 17 components against the 40 components used in the conventional magnetic pick up system**

When the external field falls and changes its polarity, the field in the core of the Wiegand wire switches back to its original direction. This occurs at an external field value  $H_{\text{reset}}$  which is much smaller than  $H_{\text{set}}$ .

In a typical system, a coil of perhaps 1000 turns on a short Wiegand wire will produce output pulses of well over 1V across a 2k load. The pulse amplitude can be increased to over 10V if required. The pulse of the opposite polarity is much smaller in the normal asymmetrical drive system. In some systems a stronger external field is used so that the polarity of the shell is reversed after the polarity of the core has been reversed; in this case the switching is symmetrical.

### OTHER USES

Apart from the use of the Wiegand Effect in vehicles for ignition timing and sensing the rate of engine revolution, it could also be used for sensing the rotation of each of the road wheels in anti-skid braking systems; when a wheel locks, the brake fluid pressure would be released for a fraction of a second before being re-applied so as to obtain the maximum braking effect automatically.

Wiegand sensors could also be used to provide data to a microprocessor which could control the ignition timing and the fuel/air mixture automatically so as to provide the best performance under all conditions.


Wiegand wires are also used in other applications, such as in plastic cards which control the access of people to certain areas or to railway stations, etc. and can be employed in electronic touch keys and for measurement of liquid flow. (Information on Wiegand products can be obtained from Sensor Engineering Co., Echlin Rd., Brandford, Connecticut 06405, U.S.A.) ★



latch, so the basic frequency is set at around 66kHz, the actual output after the divide by 2 latch being a square wave of frequency around 33 kHz, with a precise 50/50 duty cycle. R2, D1 and C3 derive a 9V supply for the CMOS i.c. The resistor R9 prevents damage to IC1 whilst connecting VR1.

The output of IC1 is amplified by transistors TR1 and TR2 to give a voltage swing at TR2's collector of 40Vpk-pk. The collector voltage of TR1 is held low by TR2 whose base voltage is maintained by R4, D2 and D3 at approx. 1.2V. This arrangement overcomes the problem of the collector base capacitance of TR1 limiting the maximum rate of rise of the output voltage. TR3 and TR4 provide current amplification to drive the primary of T2 via C4.

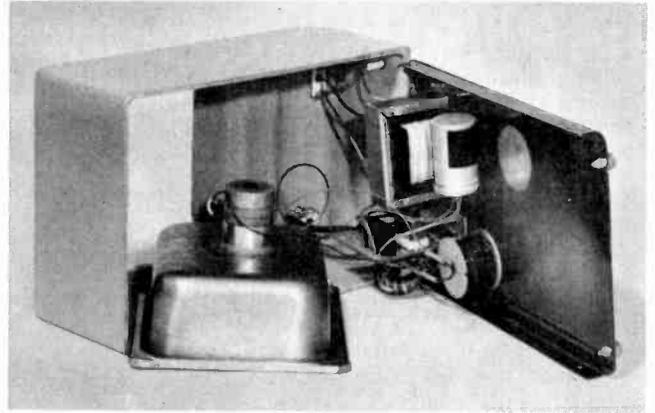The output of T2 is used to drive the output transistors TR5 and TR6 and R8 limits the maximum current. The reverse voltage helps to switch off the transistor quickly



Internal view of the Cleaner

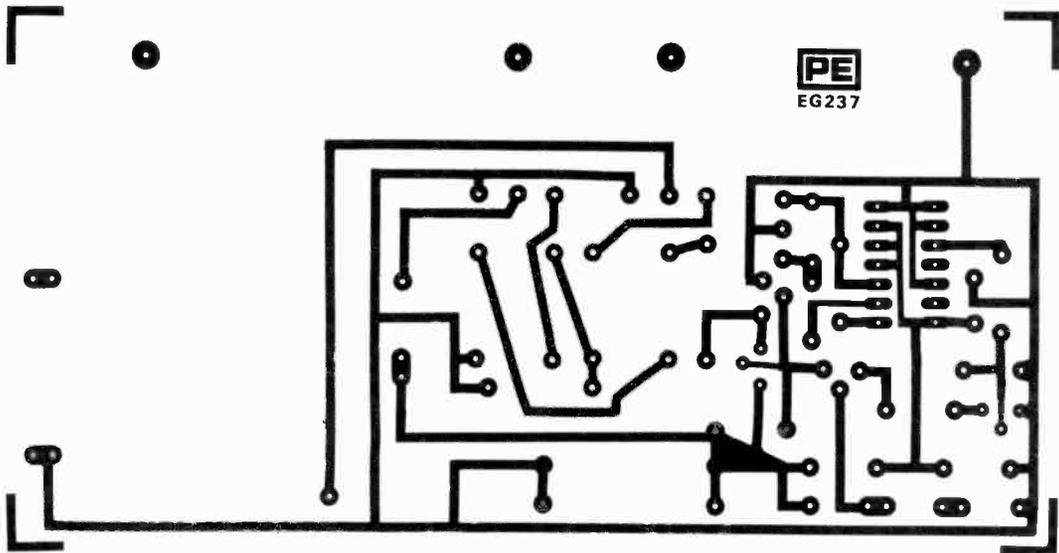


Fig. 2. P.c.b. design for the Cleaner.

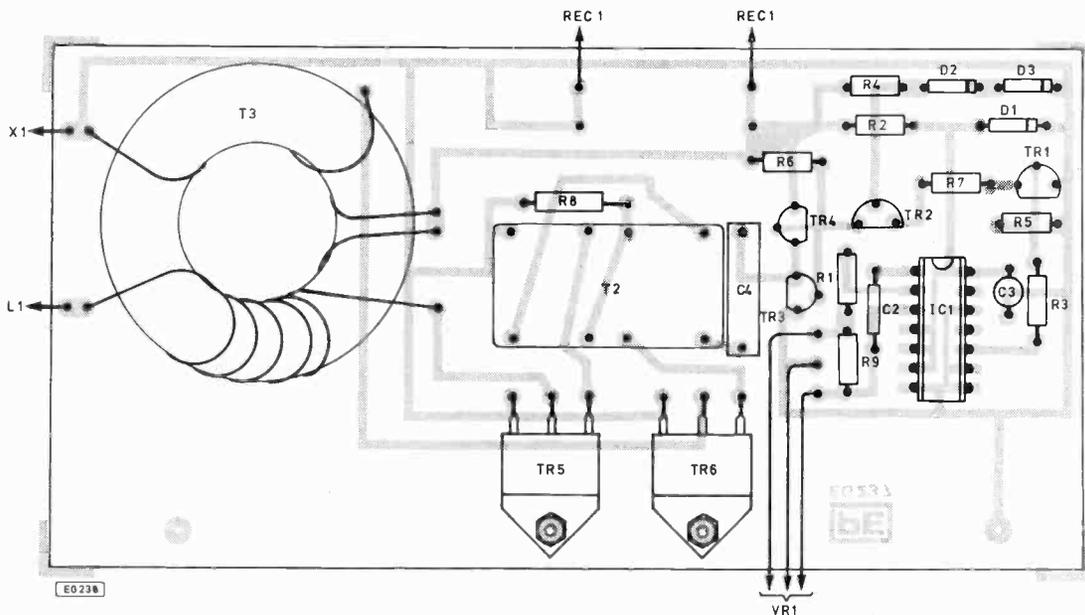



Fig. 3. Component layout.

which is the reason for using the drive transformer. L1 matches the parallel capacitance of the transducer to the secondary of T3 further improving the overall efficiency.

The power supply consists of transformer T1, bridge rectifier BR1, and smoothing capacitor C1. The fuse (FS1) and front panel mounted neon illuminated switch S1 complete the circuit.
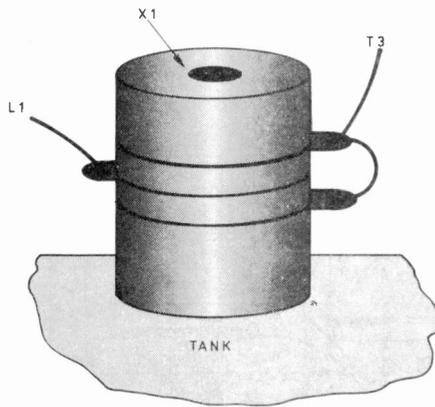
## CONSTRUCTION


The transducer should be glued to the tank bottom using Araldite. The quick setting type is not suitable. The surfaces to be stuck must be thoroughly cleaned using a de-greasing solvent and the tank bottom lightly abraded. The transducer should be stuck centrally on the tank bottom by the aluminium end, which has been shot blasted to help adhesion. The tank should be inverted over a 40W light bulb so that the adhesive heat cures. The transducer face should be coated with adhesive, applied to the pre-heated tank, and a length of tape used to keep the transducer in contact with



EO240 Fig. 4. Transducer (X1) wiring

the tank. This can be removed when the glue has hardened. The lamp should be left on for one hour after mounting the transducer and the tank should not be used until the glue has had at least 36 hours to set. This is critical to the final performance of the finished unit, and care should be taken to get best results.

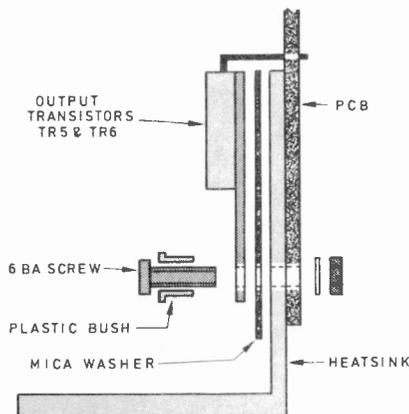The p.c.b. design of the Ultrasonic Cleaner is shown in Fig 2 and the component layout is shown in Fig 3. After soldering and checking the p.c.b. it can be mounted on the aluminium mounting bracket which doubles as a heatsink. The output transistors TR5 and TR6 must be isolated using mica mounting kits (Fig 5). The output transistors should be



EO239 Fig. 5. Heatsink mounting for TR5 and TR6

soldered after they are clamped down to the heatsink. Care should be taken soldering IC1 which should be put in last. An i.c. socket may be used if preferred.

## BASE PLATE

The base plate should be fitted into the cover of the unit and mounting holes drilled (two holes each side).

The components that mount onto the base plate are the mains transformer T1, the clip for capacitor C1, the p.c.b., inductor L1, the bridge rectifier and the four rubber feet. These components should be fitted to the base plate as shown in Fig. 7, taking care not to foul the tank. L1 should be glued to the base plate with araldite and must not be bolted through.

## COMPONENTS . . .

### Resistors

R1	43k
R2, R4	8k2 (2 off)
R3	10k
R5	3k3
R6	4k7
R7	27
R8	18 (2.5W)
R9	150k
VR1	10k

All resistors  $\frac{1}{2}$ W 5% carbon unless otherwise stated

### Capacitors

C1	4700 $\mu$ 40V
C2	15 $\mu$ polystyrene
C3	2 $\mu$ 2 tant 16V
C4	100n

### Semiconductors

D1	BZY 88C 9V1 Zener
D2, D3	1N4148 (2 off)
REC 1	BR1 8A
TR1	BC182A
TR2	2N5550
TR3	2N2904A
TR4	BFY50
TR5, TR6	TIP33C
IC1	4047

### Inductors

L1	(UTWEL 1)
T1	Mains transformer 80VA 2A sec (UTWET 1)
T2	(UTWET 2)
T3	(UTWET 3)

### Miscellaneous

Case & tank  
Fuse holder  
Fuse 1A  
Neon switch (S1)  
Two transistor mounting kits  
Heatsink  
Transducer X1

### Constructor's Note

A complete kit of parts for the Ultrasonic Cleaner can be supplied by WICCA ELECTRONIC SYSTEM LTD., ORCHARD WORKS, CHURCH LANE, WALLINGTON, SURREY.

The kit price is £68.00 plus VAT and £1.81 p&p.



to front left transformer mounting bolt. Mount VR1 on the tank body and screw the base plate to the body using four self tapping screws. The transducer should be wired as shown in Fig 4.

The tank can then be mounted into the cover and adhesive used to make a waterproof seal.

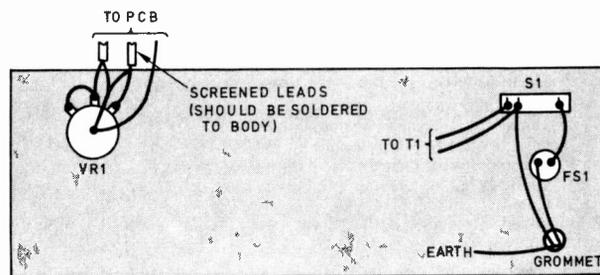


Fig. 6. Front panel wiring

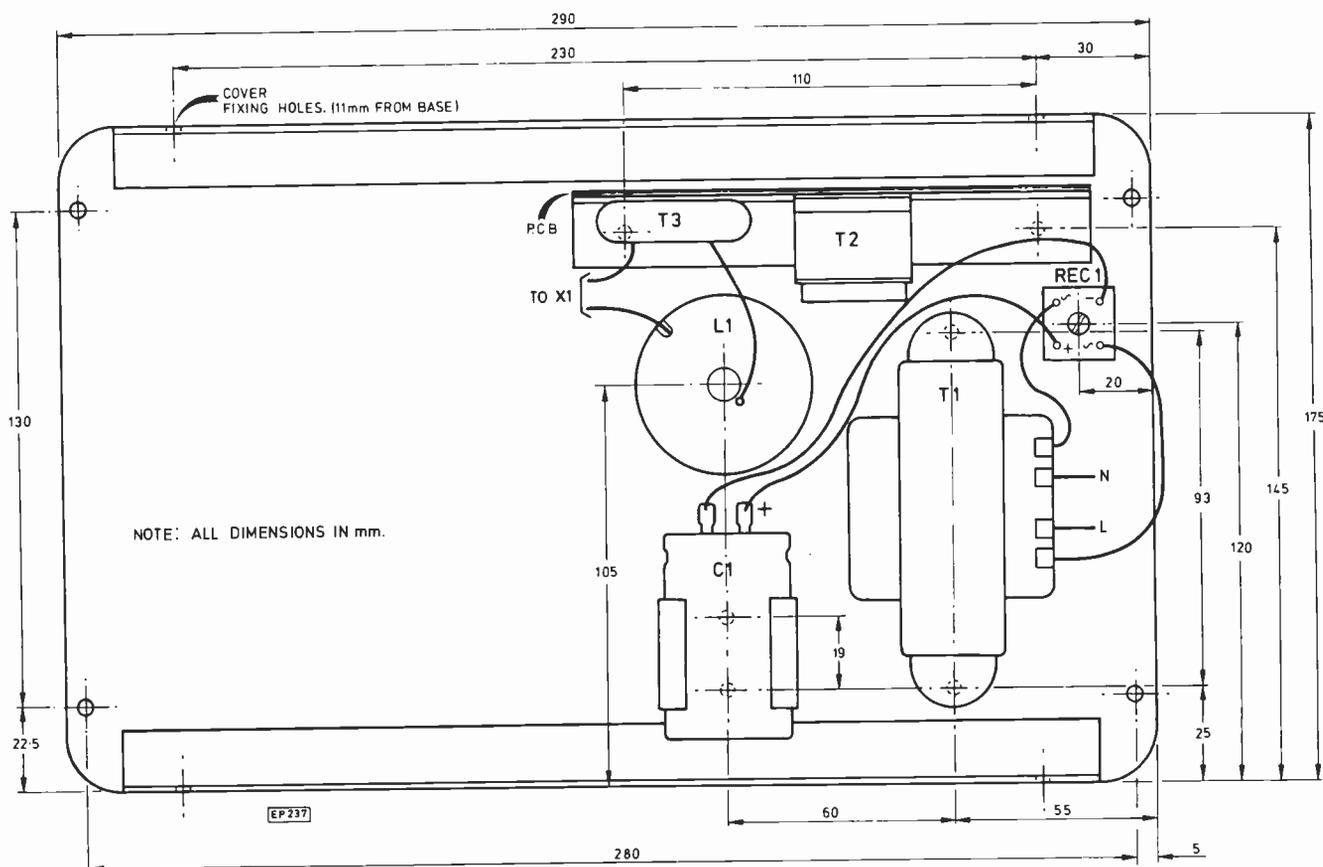


Fig. 7. Base plate wiring and drilling details

The mains switch, potentiometer VR1 and the mains fuse holder mount directly onto the fibre glass cover.

### WIRING UP

The mains lead to the fuse holder and switch should be wired next (Fig 6). A 4BA tag should be soldered to mains earth for clamping to one of the transformer mounting bolts and the leads from the switch to the transformer should be about 5" long. The wiring to the base plate components can be carried out next. VR1 is connected with screened leads to the p.c.b. and the screens at the pot end should be soldered to the pot body. After the leads from the switch to the tank cover and transformer have been wired clamp the earth lead

### TESTING

To test the unit fill the tank with water to within about an inch from the top and switch on, adjust VR1 until maximum activity is noted in the water. If a point cannot be found then recheck the p.c.b. for errors. The simplicity of the circuit should mean first time results.

Articles to be cleaned are suspended in the tank in the centre. If required wire holders can be made up to help support items. ★


*When the prototype unit was tested in the office an ink drawing pen, which had been blocked up and left for three years, was placed in the tank. The result was a completely cleaned and working pen in a couple of minutes.*

# Now, the complete MK 14 micro-computer system from Science of Cambridge
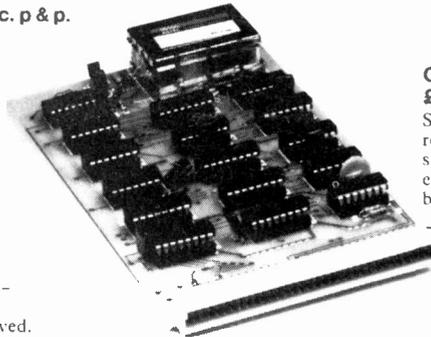
## VDU MODULE. £33.75

(£26.85 without character generator) inc. p & p.


Display up to 1/2K memory (32 lines x 16 chars, with character generator; or 4096 spot positions in graphics mode) on UHF domestic TV. Eurocard-sized module includes UHF modulator, runs on single 5 V supply. Complete ascii upper-case character set can be mixed with graphics.


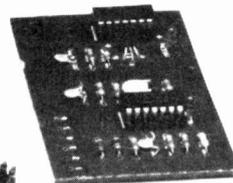
## CASSETTE INTERFACE MODULE.


£7.25, inc. p & p.

Store and retrieve programs on any cassette recorder. Use for serial transmission down single line at up to 110 baud (teletype speed), e.g. over telephone line, and to communicate between two or more MK 14s.


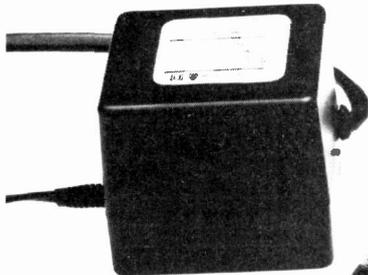
## POWER SUPPLY. £6.10 inc. p & p.

Delivers 8 V at 600 mA from 220/240 V mains - sufficient to drive all modules shown here simultaneously. Sealed plastic case, BS-approved.



## MK 14 MICROCOMPUTER KIT

£46.55 inc. p & p.


Widely-reviewed microcomputer kit with hexadecimal keyboard, display, 8 x 512-byte PROM, 256-byte RAM, and optional 16-lines I/O plus further 128 bytes of RAM.

Supplied with free manual to cover operations of all types - from games to basic maths to electronics design. Manual contains programs plus instructions for creating valuable personal programs. Also a superb education and training aid - an ideal introduction to computer technology.

Designed for fast, easy assembly; supplied with step-by-step instructions.
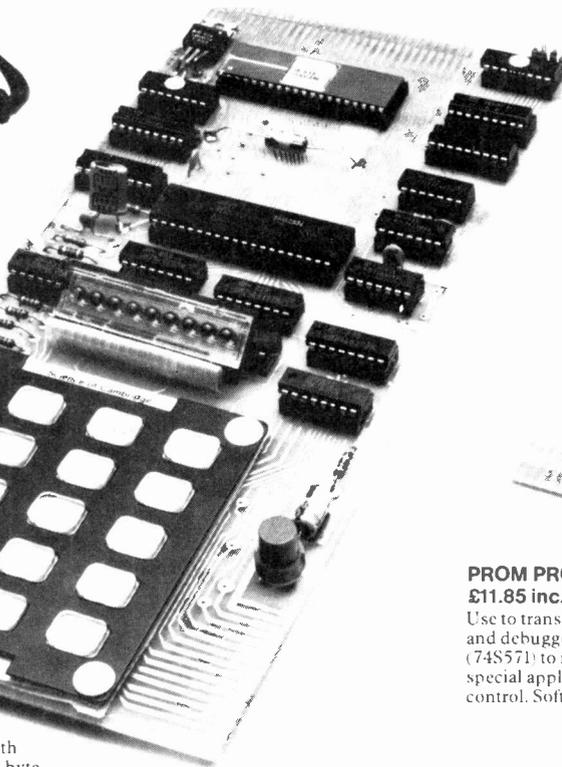
# Science of Cambridge Ltd


6 Kings Parade, Cambridge, CAMBS., CB2 1SN.  
Tel: 0223 311488.


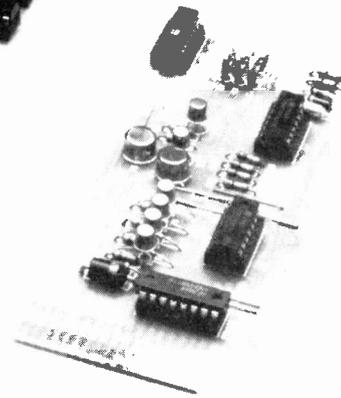
## PROM PROGRAMMER.

£11.85 inc. p & p.

Use to transfer your own program developed and debugged on the MK 14 RAM to PROM (74S571) to replace SC10S monitor for special applications, e.g. model railway control. Software allows editing and verifying.



To order, complete coupon and post to Science of Cambridge  
Return as received within 14 days for full money refund if not completely satisfied.

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me:

MK 14 standard kit @ £46.55.

Extra RAM @ £4.14 per pair.

RAM I/O device @ £8.97.

VDU module including character generator @ £33.75.

VDU module without character generator @ £26.85.

Cassette interface module @ £7.25.

PROM programmer @ £11.85.

Power supply @ £6.10.

Full technical details of the MK 14 System, with order form.

All prices include p+p and VAT.

I enclose cheque/MO/PO for £ \_\_\_\_\_ (total).

Name \_\_\_\_\_

Address (please print) \_\_\_\_\_

PE/1/80

# Romane Electronics

## LOW POWER SCHOTTKY TTL EX STOCK

Device	Price	Device	Price	Device	Price	Device	Price
74LS00	11p	74LS40	14p	74LS138	75p	74LS247	90p
74LS01	11p	74LS47	50p	74LS139	80p	74LS248	90p
74LS02	11p	74LS49	50p	74LS151	32p	74LS249	70p
74LS03	12p	74LS73	25p	74LS153	51p	74LS251	74p
74LS04	12p	74LS74	25p	74LS155	51p	74LS273	150p
74LS05	17p	74LS75	28p	74LS156	54p	74LS279	50p
74LS08	30p	74LS76	30p	74LS157	65p	74LS283	92p
74LS09	17p	74LS85	56p	74LS158	52p	74LS290	40p
74LS10	14p	74LS86	30p	74LS160	118p	74LS298	50p
74LS11	23p	74LS90	30p	74LS162	50p	74LS352	100p
74LS12	15p	74LS93	42p	74LS164	60p	74LS353	100p
74LS13	20p	74LS95	50p	74LS174	65p	74LS366	50p
74LS14	30p	74LS107	25p	74LS175	65p	74LS367	50p
74LS20	15p	74LS109	25p	74LS190	60p	74LS368	50p
74LS21	16p	74LS112	25p	74LS191	60p	74LS374	150p
74LS26	25p	74LS113	25p	74LS192	60p	74LS386	25p
74LS27	15p	74LS114	25p	74LS193	60p	74LS670	150p
74LS28	25p	74LS123	70p	74LS196	53p		
74LS30	14p	74LS125	30p	74LS197	53p		
74LS32	16p	74LS246	30p	74LS221	85p		
74LS37	20p	74LS132	46p	74LS244	190p		
74LS38	20p	74LS136	36p	74LS245	260p		

### LOW PROFILE DIL SOCKETS BY TEXAS

8 PIN	13p	18 PIN	25p	24 PIN	33p
14 PIN	14p	20 PIN	27p	28 PIN	43p
16 PIN	16p	22 PIN	28p	40 PIN	53p

### CALCULATORS

Textet 1500	£3.75	Brain Wave	£7.70
Textet 1800	£6.40	Trader	£9.00
Scientific 2001	£7.25	LCD 300	£9.40

(\*Phone for details)

All orders, large and small, will be dealt with in STRICT ROTATION.

Please add 15% VAT plus 30p P & P to all orders (Games 30p P & P each).

Export orders no VAT but postage at cost.

Prompt delivery on all orders.

Cheques, POs, Money Orders to be made payable to:-

**ROMANE ELECTRONICS,**  
Sales Dept.,  
64 Newlyn Drive,  
Sale, Cheshire.  
M33 3LE  
Tel 061-962-2606

### VERO PRODUCTS

Veroblock Breadboards	320p
Vero Wiring Pen	270p
2 x Spare Spools	85p
Spot face cutters	85p
Pin Insertion tool for 0.052" Pins	115p
Pin Insertion tool for 0.040" Pins	115p

### ELECTRONIC GAME (No TV required).

BLIP - Tennis Game	£9.00
COMPUTE-A-TUNE	£15.00
CODE NAME SELECTOR - Submarine Pursuit Game	£16.95
INTERCEPT - With Sounds and Lights of a Fighter Plane Attack	£12.85
DIGITS - Match Your Wits With a Computer	£12.95
UFO MASTER BLASTER STATION - Guide Your Missile and destroy the UFO, which may change course or even disappear!	£17.50
Terminal pins 0.052" full pin	per 100 39p per 1000 390p
Terminal pins 0.040" full pin	per 100 37p per 1000 360p

### Veroboard PCBs

0.1" Copper Clad	
2.5" x 5"	57p
2.5" x 3.75"	48p
2.5" x 17"	180p
3.75" x 5"	64p
3.75" x 17"	220p

### LIGHT EMITTING DIODES

	0.122"	Price
RED	TIL 209	13p
YELLOW	TIL 212	22p
GREEN	TIL 232	20p
	0.2"	Price
RED	TIL 220	15p
YELLOW	TIL 224-1	20p
GREEN	TIL 243-1	20p

A new book for the home electronics constructor

## Microprocessors for Hobbyists

Ray Coles

- \* An introduction to microprocessors based on two popular series in *Practical Electronics*
- \* Covers the architecture of microprocessor chips and systems, programming memory and input-output components
- \* Describes home computers together with a comparison of different models and the appropriate software
- \* A comprehensive glossary of terms is included to explain the 'buzz-words' of the micro-processor scene

1980

96 pages


£2.95 (US \$ 6.75)



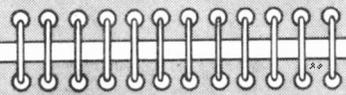**Newnes Technical Books**


Borough Green, Sevenoaks, Kent TN15 8PH. Tel: (0732) 884567

Butterworths have companies in Australia, Canada, New Zealand, South Africa and USA, where local prices apply



# INDUSTRY NOTEBOOK

By Nexus

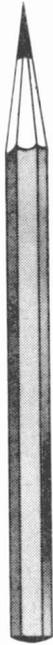

## Chaos Ahead?

Every 20 years the nations of the world get together to examine the international regulations on radio communications services. Are they working well? Is the available spectrum being used efficiently? Should power limitations be imposed on short wave broadcast propaganda stations? Should amateur radio be squeezed out in favour of more essential services? These and many other questions.

This great jamboree is called the World Administrative Radio Conference, abbreviated to WARC 79. It is held under the auspices of the International Telecommunications Union. Twenty years ago at WARC 59 there were 87 participating countries. The self-determination movement and further progress in decolonisation has boosted the number of countries to 140 and, not unnaturally, all the new members are extremely proud of their new status as independent self-governing nation states.

The old rules still apply, one nation one vote. Little Fiji with 580,000 population, for example, has the same voting power as the UK's 56 million, the USA's 215 million or the Soviet Union's 257 million. This is not to say that wisdom is proportional to population or that the big powers should bulldoze their own demands through the conference. What happens in practice, however, is that the less prosperous countries which, almost by definition, are less able to form fairly balanced technical judgements, tend to vote either in solidarity with their own blocs or to side with the more prosperous countries from which they are already receiving or hoping to receive aid. There is also an unfortunate, but again natural, trend for newly emergent nations to take a swipe at their former "oppressors" whatever the merits of a proposal put forward quite honestly on purely technical and operational grounds.

The first big squabble came with the appointment of the WARC 79 chairman. The first nominated was from New Zealand, rejected by the non-aligned countries. Next was one from India, not accepted by the Western Group. Surely nobody would object to a candidate from neutral Switzerland? Not so, this worthy individual being rejected by the non-aligned group and the Western group. Eventually, after much behind-the-scenes lobbying, an Argentinian, R.J.P. Severini emerged as chairman.

One fears that more so than ever before, WARC 79 has become a political more than a technical conference. Even though the numerous sub-committees working entirely at the technical level make sound decisions their work may well be frustrated by the national and international voting pattern.

Attending WARC are some 2,000 delegates if you include official "observers" with special interests who will be lobbying in the corridors. I hope they enjoy their long sojourn in Geneva. Originally scheduled as a 10-week event ending on November 30, I forecast that this conference will go down in history as WARC 79/80. But better to have an extended conference with sensible results than a hodge-podge of ill thought out decisions which can only lead to even more chaos on the radio waves in the years ahead.

## Telecom 79

Also in Geneva was the great Telecom 79 exhibition. This one for the world's telecommunications equipment manufacturers is staged every four years by the International Telecommunications Union, an agency of the United Nations. ITU's secretary-general M. Mili opened Telecom 79 by reminding us that there are some 400 million telephone lines today and that present projections indicate some 1,400 million by the end of the century. At today's prices this means the spending of an extra £1 trillion during the next 20 years.

No wonder this exhibition was chosen as the first launch platform for Britain's System X, the all-digital telephone system of the future. System X is a joint development between the British Post Office, Standard Telephones & Cables, Plessey and GEC. Overseas marketing is through a newly-formed consortium company, British Telecommunications Systems (BTS).

The BPO has endorsed the system (could it do otherwise?) by ordering the first nine System X exchanges which will go into service from 1981 onwards. BTS is not expecting quick results in exports but is taking the long-term view. System X cannot sell on technical merit alone. The big markets are in countries which have no indigenous telecommunications industry and they need financial support to invest in huge capital projects. They may also demand a share in the manufacture of equipment. So any negotiations tend to be complicated and lengthy.

At Geneva System X was one of the few digital systems demonstrated live—a great point in its favour against what is likely to become fearsome competition from the leading European and US manufacturers.

## MEDE 79

The Military Electronics Defence Expo '79 staged at Wiesbaden was a frightening showcase of ingenuity. Military electronics is one field in which the Japanese have, as yet, made no impact. Except that one could not fail to note that nearly all the audio-visual displays of missiles homing on to targets and other awesome scenes were using Sony VCR equipment. At least aiding and abetting if not participating directly!

There was in fact one Far Eastern exhibitor, Veterans Electronics Communications Incorporated, who make combat radio, manpacks and vehicle-mounted, in the Philippines. Their marketing arm is Vetrionix Inc. and the company slogan is "High technology aimed at low budget targets". Translated this means Asia, Africa and South America. Their appearance in Europe could well have been not so much to sell here as to look for new lines to manufacture under licence.

This trend, which I have commented on before, is steadily growing. Technology transfer, today's big business, is tomorrow's threat, that is unless you can stay ahead in technology. But looking over the prime exhibits from the USA and Europe there seemed little chance of the tiddlers in electronics ever catching up with the big fish. They haven't the technical design teams or the financial resources. Even in the West costs are becoming so prohibitive that joint ventures are ever more necessary.

One can argue that all military spending is waste but one is also forced to the conclusion that the United Kingdom would indeed be in a sorry state in terms of overseas trade balance and unemployment but for exports of defence equipment with the very high added value afforded by high technology. A single example illustrates the point. Plessey alone have already completed their first £100 million of sales on Clansman equipment and they are only one of four British contractors on the project.

An interesting point on design philosophy arose during the technical conference at MEDE. Surprisingly two different viewpoints were expressed from the same company, RCA, although the speakers were from different divisions of the company and talking on different topics.

Our speaker, a software orientated person, was singing the praises of standard hardware in which software changes could be rapidly made to accommodate new or different applications as the military need dictated. This is a commonly accepted doctrine.

A second RCA engineer took the opposite view pointing out that hardware costs are constantly falling while software costs are constantly increasing. The implication here is that versatile systems can be implemented more economically through plug-in hardware modules. This speaker went so far as to state, "Ten years ago it appeared that software-controlled processing in a general purpose computer would provide maximum flexibility at minimum costs. In fact real-time software has proven to be very expensive and inflexible".

# SCINTILLATING PENDANT



**T**HIS project was designed as a piece of jewellery for evening wear. It produces a scintillating light effect from an array of light emitting diodes and could equally well be made up as a pin-on brooch or as a bracelet. There can be many varieties on the original theme so that the final product can be unique in appearance and activity.

## CIRCUIT DESCRIPTION

The circuit is based on two CMOS i.c.s (Fig. 1). R1 is included for extra protection against static discharge. The CD4060B together with the timing capacitor C1 and resistors R2 and R3 provide an astable multivibrator and a 14-stage binary dividing chain. Outputs from stages 1, 2, 3 and 11 are not available. Reading from pin 7 down to pin 3 represents the multivibrator frequency divided by 16, 32, 64, 128, 256, 512, 1,024, 4,096, 8,192 and 16,384 respectively. These outputs, with the exception of that from pin 15 (+1,024) and pin 2 (not used) are fed to the CD4052 dual analogue multiplexer/de-multiplexer. The function of one half of this i.c. is illustrated in Fig. 2. In effect it is a 5-way switch, through which current can flow in either direction, just as in an ordinary mechanical switch, except that the path through the switch in positions 0 to 3 has a resistance of about 120 ohm. Though we are calling this a switch, for this is how it functions, in fact the i.c. contains a number of CMOS transmission gates, under the control of the inhibit and the two control inputs A and B. With inhibit input high, the switch is open-circuit. With inhibit input low, one channel becomes closed-circuit, or "ON":

Inputs		Channel On
B	A	
0	0	0
0	1	1
1	0	2
1	1	3

The two analogue switches of the i.c. are used to direct the outputs from IC1 to the five l.e.d.s D1 to D5. D6 is lit directly


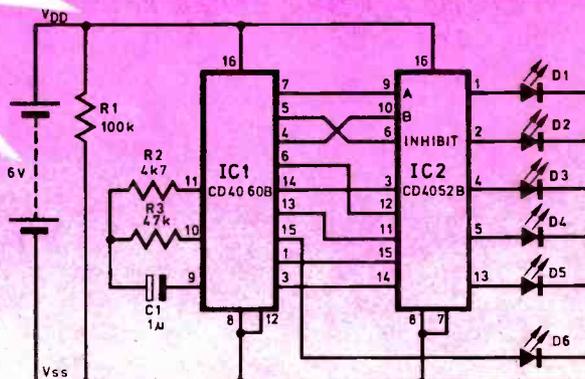


Fig. 1. Circuit diagram of the Pendant

EG234

Owen Bishop

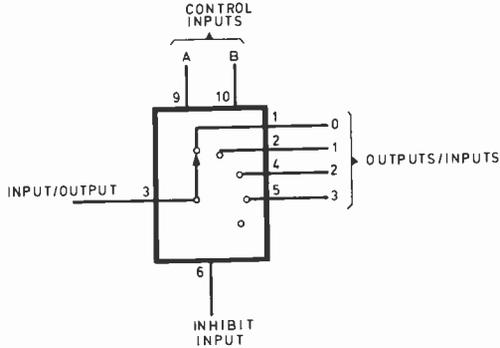from the output of pin 15, IC1. Four l.e.d.s D1 to D4 are connected so that they are illuminated in turn, depending on inputs to A and B, but only when the output of IC1, pin 14 is high. D5 is illuminated if one of the outputs it is connected to (pins 6, 13, 1 or 3 in turn) is high. The effect of this is to produce a sequence of illumination that is apparently



EG235 Fig. 2. Function diagram of IC2

random. The sequence is further complicated by the inhibiting action which cuts out some stages altogether. This action also ensures that for at least 50 per cent of operating time none of the l.e.d.s D1 to D5 are lit, so doubling battery life. D6 operates independently of IC2 and thus creates a further apparent randomness.

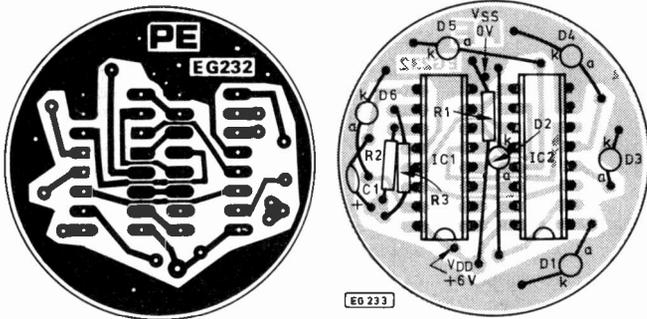


Fig. 3 and Fig. 4. P.c.b. design and component layout

The circuit has low current consumption (0.08 mA when no l.e.d.s are lit and about 10 mA per l.e.d. lit) so it will run for 10 hours or more from 4 button-cells. Though CMOS i.c.s and l.e.d.s can both be run from supplies of 3V, reduction of voltage increases the switch resistance and the intensity of light emission becomes too low for good effect.

## COMPONENTS . . .

### Resistors

R1	100k
*R2	4k7
*R3	47k
*See text	
All resistors 0.125W, 10%	

### Capacitor

C1	1 $\mu$	35V tantalum bead
----	---------	-------------------

### Semiconductors

D1 to D6	light-emitting diodes of constructors choice
IC1	CD4060BE
IC2	CD4052BE

### Miscellaneous

Materials for mounting, according to individual design. Plastic resin kit, necklace chain, button cells (4 off) type 675.



## CONSTRUCTION

The p.c.b. design and component layout are shown in Figs. 3 and 4. If it is intended to hang the pendant from a chain, the p.c.b. may be extended to form a projecting lug with a hole drilled through it for attachment. Constructors will have realized that there are many ways of connecting the two i.c.s, with each way producing its unique sequence of illumination. At this stage you may prefer to set up the circuit on a bread-board and try varying the connections to obtain different effects. Some modification of the p.c.b. pattern may then be decided upon. Select the values of C1 and R3 to obtain the rate preferred and alter R2 so that its value is about 10 per cent of R3. There is also a choice of l.e.d.s.

The l.e.d.s should be mounted as close as possible to the board, so that their tops project only slightly above the upper surfaces of the i.c.s.

## PRESENTATION

Here there is infinite scope for individuality and artistic ability. Some points have already been mentioned and it is important to work out these details fully before commencing construction. When the prototype circuit-board was complete and working, it was inverted in a cylindrical mould made from aluminium kitchen foil and cast into a disc-shaped block of clear resin. The front and edges of the disc were covered with irregularly shaped fragments of transparent plastic. Since the inner surface of each piece

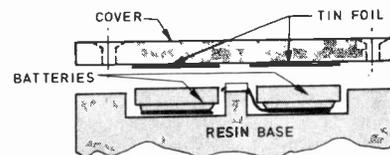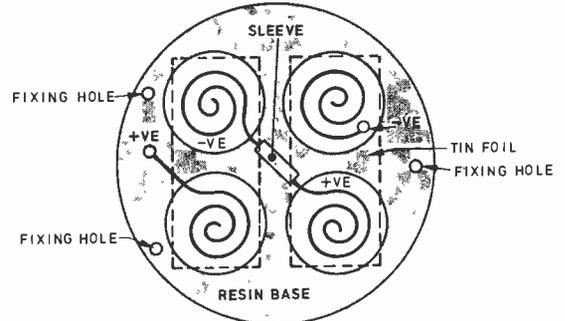

EG241


Fig. 5. Layout and connection of batteries

was corrugated, refraction caused the light from each l.e.d. to appear as a streak, its orientation depending on the orientation of the corrugations. A simple way of covering the l.e.d.s could be to cast the circuit in a disc of resin in a mould made from crumpled foil; the resin could be coloured red or any other shade by mixing in a few drops of pigment before pouring it into the mould. If you are really skilled you could contemplate mounting the circuit in an ornamental bezel, or perhaps cover it with a filigree network through which the l.e.d.s protrude. Alternatively, you could buy a ready-made mount and design the p.c.b. to fit it.

## BATTERY CONNECTION

In the prototype, a second resin disc was cast on the back of the p.c.b., leaving 4 circular pits to hold the button cells, and using wire and foil strips to make the connections to the terminal pins on the board, and between cells (Fig. 5). The pendant was backed with a thin disc of Formica. ★

# R/C SERVO TESTER

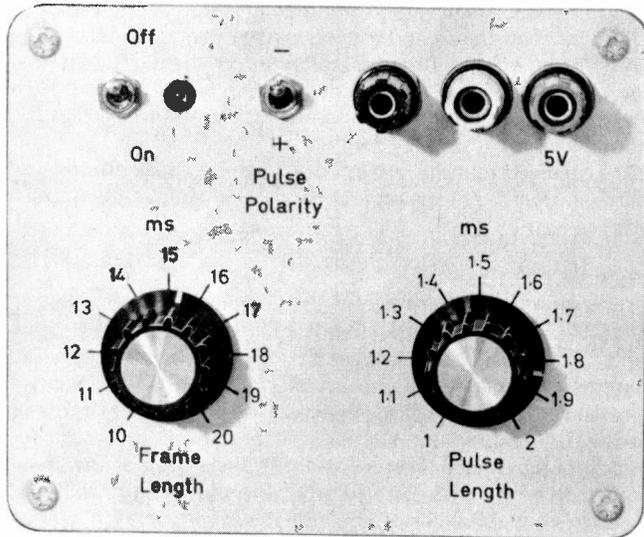


## C.R.FRANCIS B.Sc.Ph.D.


**M**ANY remotely controlled models operate very satisfactorily with simple on/off commands. The undercarriage of a model aircraft may be retracted or extended by this type of command for example, and similar applications abound. For more sophisticated control however, some form of proportional response is required. Imagine that we wish to steer a model car by some form of remote control, say radio control. By using two separate on/off commands we could arrange the wheels to be straight or hard left, or straight or hard right, and steering would be possible, if a little jerky. Using a proportional system the wheels could be made to imitate, or follow, the movements of a knob on the control set. The mechanical movements of the wheels would be carried out by connecting them to a servo-mechanism.

Now many proportional control systems may be used which do not involve electromechanical devices; such as voltage control of the frequency of a radio tuner through a varicap diode, or, more relevantly, control of an electric

**Fig. 1. Layout of a typical servo.** The potentiometer wiper is normally directly coupled to the output shaft, which is driven through reducing gear by the electric motor

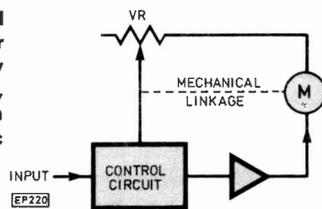

**Fig. 2. Block diagram of the servo tester**

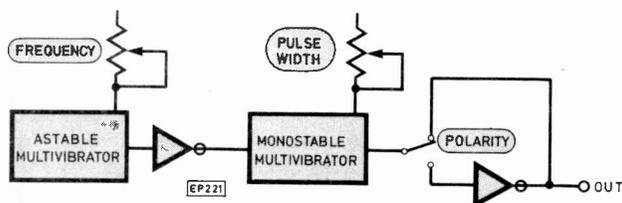

motor by pulse width modulation of the power supply. The most commonly used method in radio controlled models however, is the electromechanical servo mechanism, or servo.

### TYPICAL SYSTEM

A typical modern radio control system uses pulses of variable width to transfer information. A short pulse will cause the servo to move to one end of its travel, a long pulse makes it move to the other end and intermediate pulses result in an intermediate position. A typical servo will contain an electric motor to drive its movements, a potentiometer to monitor these movements, mechanical linkages between these two, and a control circuit. These are all shown in Fig. 1.

Typical characteristics for the control pulses are as follows:

Frame length (the interval between successive pulses)—20ms

Pulse length—1ms to 2ms for complete range of travel

Positive pulses

Many servos may be included in a system by interleaving the control pulses, so that proper decoding and routing of the pulses will give simultaneous control. It is often convenient to operate a servo in isolation from the rest of such a system, and in this case a servo tester is ideal.

### THE TESTER DESCRIBED

The servo tester to be described will control servos with the characteristics listed above, and furthermore the frame length is variable, from 10 to 20ms, and the pulses can be positive or negative going. Instructions will be given so that departures from these parameters may be accommodated. The tester can also supply up to 500mA at 5V to the servo under test. This should be adequate for most miniature servos, though electronic control of anything other than a small electric motor will require a more suitable power supply.

### BLOCK DIAGRAM

A block diagram of the servo tester is shown in Fig. 2 and we can see that it is very simple. An astable multivibrator produces pulses of fixed length (about half a millisecond) but variable repetition frequency; this defines the frame length. The inverter is necessary simply to achieve the correct polarity for the triggering of the next stage, a monostable multivibrator.

When triggered this produces an output pulse whose length is variable, between 1 and 2ms. These pulses may be inverted, or not, in the final stage, to produce negative or positive going pulses.

### CIRCUIT

A circuit diagram of the complete instrument is shown in Fig. 3. The astable multivibrator is built around a 555 timer; for convenience a 556 dual timer was used in the prototype, since another 555 is required for the monostable multivibrator. Although the 556 is specified in the circuit diagram and component list, two 555s may be used if preferred.

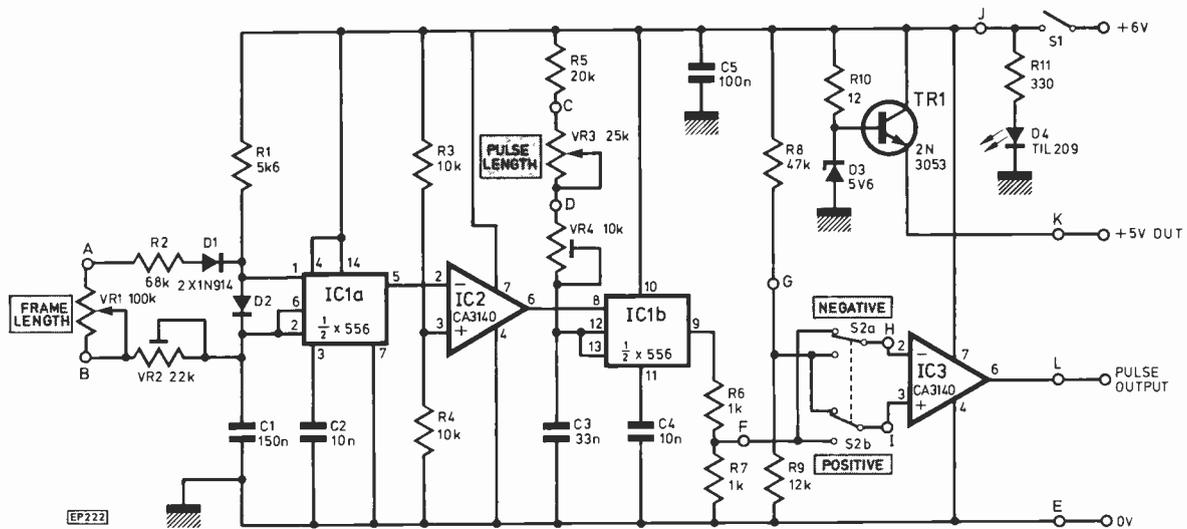


Fig. 3. Circuit diagram of the servo tester

When operating as an astable multivibrator the timer ic.1 monitors the voltage on the timing capacitor, C1, as it charges through R1 and D2. The output voltage is, at this time, high. When the voltage on C1 reaches 2/3 the supply voltage,  $V_{cc}$  the output voltage switches low and C1 starts to discharge through VR1, VR2, R2 and D1, into the discharge pin. When the voltage on C1 has dropped to 1/3  $V_{cc}$  the trigger pin is activated, which restarts the sequence.

The period when the output is high,  $t_1$ , is governed simply by R1 and C1. The low output period,  $t_2$ , is controlled by VR1, VR2, R2 and C1. The relationships are:

$$t_1 = 0.7 R_1 C_1$$

$$t_2 = 0.7 (VR_1 + VR_2 + R_2) C_1$$

R1 and C1 are chosen so that  $t_1$  is shorter than any of the pulses required from the monostable. A period of 500  $\mu$ s is suitable.


The second timer unit, IC1b, which is a monostable multivibrator, requires negative-going signals to trigger. Inversion is carried out by IC2, a CA3140, which is connected as a comparator. The output of IC1a is compared with a voltage of  $\frac{1}{2}V_{cc}$  and the output of IC2 is high or low, if this output voltage is less than or greater than  $\frac{1}{2}V_{cc}$  respectively. The output of IC1a is thus inverted. A CA3140 is used here (and for IC3) since the power supply is only 6V. A 741 will not operate reliably from such a supply.

The operation of a second timer as a monostable multivibrator is very straightforward. When a negative going signal is detected at the trigger pin its timing capacitor, C3, starts to charge via R5, VR3 and VR4, and the output goes high. When C3 charges to 2/3  $V_{cc}$  the output goes low and C3 rapidly discharges. The circuit is now ready to be re-triggered. The time for which the output remains high,  $t_3$ , is controlled by R5, VR3, VR4 and C3, as shown by the equation

$$t_3 = 1.1 (R_5 + VR_3 + VR_4) C_3$$

The output from this timer is a train of pulses with the required time characteristics. The remaining parts of the circuit give the voltage characteristics we have specified.

Fig. 4. Modification to the circuit to provide pulses of +5V

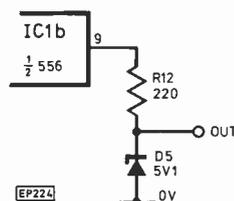

### SUPPLY

A 5V supply is provided for the servo under test, but the pulses are of only 4V, which will normally be satisfactory. This situation arises because the CA3140 which is used as a comparator in the output polarity switching stage can only swing up to 2V below  $V_{cc}$ . The voltages to be compared here are half the output from IC1b, and  $\frac{1}{4}V_{cc}$ . These are routed via S2 to the inputs of IC3, so that either the inverting or non-inverting action occurs.

If positive pulses only, of the full 5V, are required, then the modifications shown in Fig. 4 may be employed. Here the output is taken straight from the monostable stage, but is limited to 5.1V by the Zener diode, D5.

The 5V supply is provided by TR1. The emitter of this transistor is held about half a volt negative of its base, if sufficient current into the base is available. The 2N3053 is rated at 700mA maximum collector current, so the 500mA required for our supply is within its capabilities. At this level of collector current, quite a large base current is required to maintain the emitter about 0.5V negative of the base, so R10 has to have a low value. This means that with no load, D3 is also approaching its rated power dissipation if a 400mW type is used. To avoid trouble here a 1W type is recommended, though in the prototype a 400mW Zener was used without overheating.

Since D3 is a 5.6V Zener diode the emitter of TR1 should be held at about 5.1V, but remember Zener diodes are normally of 10 per cent tolerance. The output voltage is therefore only nominally 5V.

Veroboard was used in the construction of the prototype. A suitable layout is given in Fig. 5; note that the size of the piece of board was chosen so that it could be supported in slots in the plastic case. A heat dissipating clip was attached to TR1, though it is probably unnecessary. The wiring up of the various off-board components of the front panel, or lid, is illustrated in Fig. 6. Careful cable routing enables the board to be removed from the case easily for adjustments.

### ADJUSTMENTS

Only two adjustments are necessary. The frame length control, VR1, is calibrated 10ms to 20ms. Set the control to its mid-point, 15ms. Now adjust VR2 while observing the output on an oscilloscope, or with a frequency counter. Vary VR2 so that the period between successive leading edges of the pulse train is 15ms, or if a frequency counter is being used, until the frequency is 66.7Hz. Check now that at each

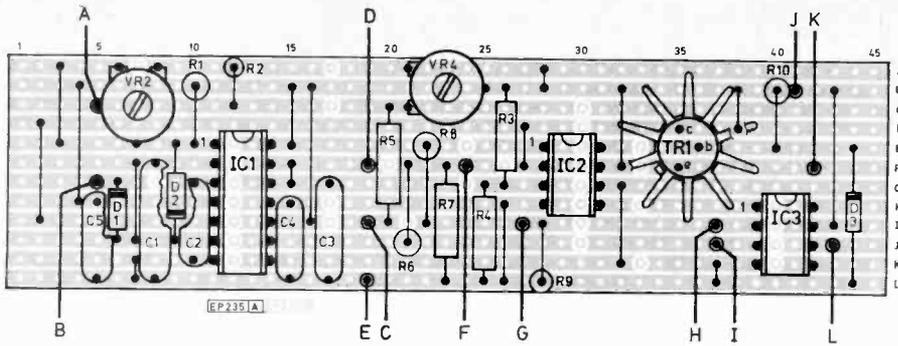


Fig. 5. Veroboard layout


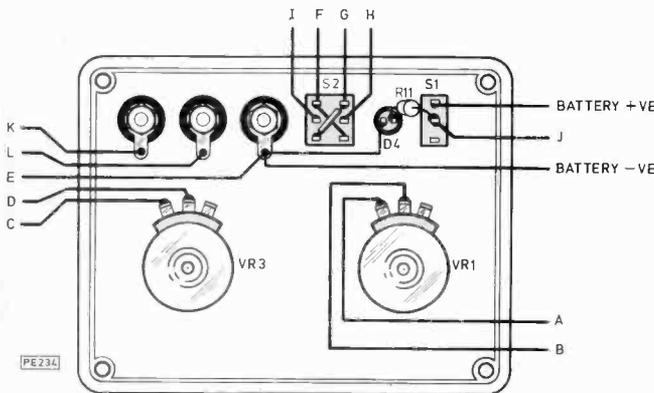


Fig. 6. Control panel wiring

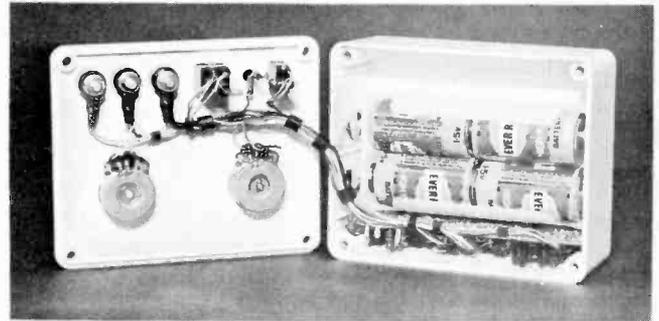

## COMPONENTS ...

### Resistors

R1	5k6
R2	68k
R3, R4	10k (2 off)
R5	20k
R6, R7	1k (2 off)
R8	47k
R9	12k
R10	12
R11	330
VR1	100k linear
VR2	22k preset
VR3	25k linear
VR4	10k preset

### Capacitors


C1	150n
C2, C4	10n (2 off)
C3	33n
C5	100n

### Semiconductors


IC1	556
IC2, IC3	CA3140 (2 off)
TR1	2N3053
D1, D2	1N914 or similar (2 off)
D3	5V6 Zener 1W (see text)
D4	TIL 209

### Miscellaneous

S1	On/off switch
S2	Double-pole changeover switch
Terminal posts (3 off)	
Veroboard	
Plastic case	
HP11 batteries (4 off)	
Battery box for the above	

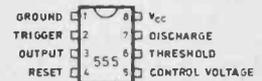

EP223

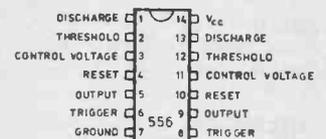

end of the scale the markings are correct. Be prepared to accept some inaccuracies, bearing in mind component tolerances.

Next VR4 is similarly adjusted so that the 1ms to 2ms scale on the pulse length control is correct. An oscilloscope should be used for this measurement.

If no oscilloscope is available, but accurate measurements of resistance and capacitance can be made, then the necessary adjustments can still be carried out. First measure the capacitance of the timing capacitors C1 and C3, the resistance of R2 and R5, and the range of VR1 and VR3. The equations

$$t_2 = 0.7 (VR1 + VR2 + R2) C1$$

$$\text{and } t_3 = 1.1 (VR3 + VR4 + R5) C3$$

may then be used to find the required value for VR2 and

VR4. A value is found for VR2 so that the extreme values of VR1 give values for  $t_2$  of 10ms and 20ms respectively. Similarly with VR4 and  $t_3$ .

These equations should also be used to choose suitable components if time characteristics different from those in the prototype are required. If a pulse length of about half a millisecond or less is required, then the astable multivibrator pulse length must be reduced to a value less than the shortest output pulse. This may be done by increasing R1 in accord with the equation

$$t_1 = 0.7 R1 C1$$

Do not reduce R1 much less than a kilohm. If a shorter time is then required, reduce C1 instead, but remember that R2, VR1 and VR2 will need changing to maintain  $t_2$ .





# NewBear Books



## INTRODUCTION TO MICROCOMPUTING

Volume 0 The Beginners Book	A. Osbourne . . .	£ 5.95
Volume I Basic Concepts	A. Osbourne . . .	£ 5.95
Volume II Some Real Products	A. Osbourne . . .	£18.95
Volume III Some Real Support Devices	A. Osbourne . . .	£11.95
Understanding Microcomputer & Small Computer Systems	Scelbi . . . . .	£ 7.56
An Introduction to Personal & Business Computing	R. Zaks . . . . .	£ 5.75
Getting Acquainted with Micros	. . . . .	£ 7.95
Getting Involved with your Own Computer, A guide for Beginners	. . . . .	£ 4.75
The First Book of Microcomputers	Moody . . . . .	£ 3.60
A Consumers Guide to Personal Computing and Microcomputers	. . . . .	£ 5.65
Peanut Butter & Jelly Guide to Micro's	. . . . .	£ 6.20

## BASIC BOOKS

Beginning Basic	P. E. Gosling . . .	£ 2.95
Introduction to Basic	P. J. Hartley . . .	£ 1.95
Some Common Basic Programmes Illustrated Basic	A. Osbourne . . .	£ 6.45
Learning Basic Fast	Alcock . . . . .	£ 2.25
The Basic Workshop	De Rossi . . . . .	£ 6.30
Discovering Basic	K. Schoman Jnr. .	£ 4.50
The User's Guide to North Star Basic	R. E. Smith . . . .	£ 4.90
Star Basic	R. Rogers . . . . .	£10.00
Basic with Business Applications	Hayden . . . . .	£ 5.56
Basic and the Personal Computer	Dwyer & Critchfield .	£10.36
A Guided Tour of Computer Programming in Basic	Dwyer/Kaurman . .	£ 4.16
Basic Basic	J. S. Coan . . . . .	£ 5.00
Advanced Basic	J. S. Coan . . . . .	£ 5.50

## PASCAL

Pascal: User Manual & Report	Springer-Verlag . .	£ 5.52
Problem. Solving Using Pascal	Springer-Verlag . .	£ 7.84
Programming in Pascal	P. Grogono . . . . .	£ 7.50
A Practical Introduction to Pascal	A. Addyman . . . . .	£ 3.50
An Introduction to Programming & Problem Solving with Pascal	Schneider . . . . .	£ 9.50
Introduction to Pascal	Welsh . . . . .	£ 6.95

## SC/MP

Guide to SC/MP Programming	. . . . .	£ 3.75
SC/MP Assembly Language Programming Manual	. . . . .	£ 6.45
A Guide to Kitbug. KEMITRON	. . . . .	£ 0.95

## COBOL

Cobol Programming	Nickerson . . . . .	£ 6.95
Learning Cobol Fast	De Rossi . . . . .	£ 6.20
Cobol with Style	Hayden . . . . .	£ 4.20

## 6800 BOOKS

6800 Programming for Logic Design	A. Osbourne . . . .	£ 5.95
6800 Assembly Language Programming	A. Osbourne . . . .	£ 6.95
Using the 6800 Microprocessor	. . . . .	£ 5.65
77-68 6800 Microprocessor Design Manual	. . . . .	£ 7.50
6800 Software Gourmet Guide	Scelbi . . . . .	£ 7.95
Practical Microcomputer Programming (6800)	Weller . . . . .	£14.95
The 6800 Microprocessor	. . . . .	£ 3.60
6800 Applications Manual	Motorola . . . . .	£10.50
Programming the 6800 Micro	Southern . . . . .	£ 8.00
6800 System Design Data	Motorola . . . . .	£ 2.00

## Z80 BOOKS

Z80 Programming for Logic Design	A. Osbourne . . . .	£ 5.95
Z80 Technical Manual	Zilog . . . . .	£ 4.00
Z80 PIO Technical Manual	Zilog . . . . .	£ 2.75
Z80 Programming Manual	Zilog . . . . .	£ 4.50
Z80 Microcomputer Handbook	W. Barden . . . . .	£ 6.95
Practical Microcomputer Programming (Z80)	Weller . . . . .	£19.55
Z8000 PLZ/ASM Manual	Zilog . . . . .	£11.50

## 8080 BOOKS

Practical Microcomputer Programming (8080)	Weller . . . . .	£17.56
8080A Bugbook	Larson . . . . .	£ 6.95
8080A/8085 Assembly Language Programming	. . . . .	£ 6.95
8080 Programming for Logic Design	A. Osbourne . . . .	£ 5.95
8080 Software Gourmet Guide Cook Book	Scelbi . . . . .	£ 7.95
8080/8085 Software Design	(Titus) . . . . .	£ 7.50
An Editor/Assembler for 8080/8085	. . . . .	£11.50

## 6502

The Best of Micro 6502 Journal	. . . . .	£ 5.99
6502 Applications Handbook	Zaks . . . . .	£ 8.95
First Book of Kim	. . . . .	£ 7.00
6500 Hardware Manual	. . . . .	£ 7.50
6500 Programming Manual	. . . . .	£ 7.50
Programming the 6502 SYBEX	Zaks . . . . .	£ 7.95
Programming a Micro. 6502	Caxton Foster . . . .	£ 7.95

## FORTRAN

Elementary Computer Programming Fortran IV	Boguslauskys . . . .	£ 6.30
--	----------------------	--------

## GAMES

32 Basic Programs for the PET COMPUTER	. . . . .	£ 9.95
101 Basic Computer Games	. . . . .	£ 5.50
Games, Trick & Puzzles for a Hand Calculator	W. Judd . . . . .	£ 2.49
Games with a Pocket Calculator	. . . . .	£ 1.75
Star Ship Simulation	. . . . .	£ 5.10
Game Playing with Basic	. . . . .	£ 4.10
Game Playing with Computers	D. Spencer . . . . .	£10.20
Game Playing with Basic	. . . . .	£ 4.20
SARGON-A Chess Computer Program in Z80 Assembly Language	. . . . .	£ 9.50
Chess & Computers	D. Levy . . . . .	£ 7.16
Chess Skill in Man & Machine	P. Frey . . . . .	£11.84
57 Practical Games & Programs in Basic	. . . . .	£ 6.40

## COOKBOOKS

Active Filter Cookbook	Lancaster . . . . .	£10.45
CMOS Cookbook	Lancaster . . . . .	£ 6.95
OP-AMP IC Cookbook	Jung . . . . .	£ 9.50
IC Timer Cookbook	Jung . . . . .	£ 7.50
TTL Cookbook	Lancaster . . . . .	£ 6.95
T.V. Typewriter Cookbook	Lancaster . . . . .	£ 7.50
Cheap Video Cookbook	Lancaster . . . . .	£ 4.30

## PROGRAMMING

Intro. to TRS80 Graphics	Inman . . . . .	£ 5.75
Design of Well Structured Programs	Alagic . . . . .	£10.00
Chemistry with a Computer	Cauchon . . . . .	£ 7.96
Top-Down Structured Prog. Techniques	McGowan . . . . .	£12.50
Computer Input Design	Woolridge . . . . .	£ 8.85
Computer Output Design	Woolridge . . . . .	£ 9.70

## MISC.

Microprocessor Data Manual	Bursky . . . . .	£ 4.80
Best of Byte	. . . . .	£ 8.50
Scelbi Byte Primer	Scelbi . . . . .	£ 9.95
The Best of Creative Computing Vol. 1	. . . . .	£ 6.95
The Systems Analyst	Atwood . . . . .	£ 6.60
Bipolar & CMOS Memory Databook	Harris . . . . .	£ 4.50

## Terms:

"INSTANT DESPATCH SERVICE"

SEND FOR FULL BOOKLIST.

Credit Sales (min. £10). Barclaycard and Access welcome.

All book prices include post and packing.

MAIL ORDER & CALLERS: 40 Bartholomew Street, Newbury, Berks. Tel: 0635 30505

CALLERS ONLY: 220-222 Stockport Road, Cheadle Heath, Stockport Tel: 061 491 2290

# WICCA



## Electronic Systems Ltd

### P.E. ULTRASONIC CLEANER



All the designer approved parts, including fibre glass case, to complete this exciting project as featured in this issue.


+p.p. £2.50 **£68.00**

## SANYO

### STK 463

Hybrid stereo power amp I.C. delivers 30W R.M.S into 8 ohms from each channel, all contained in one package approximate size as outline to this item. From one of the worlds leading manufacturers this new I.C. features only 0.5mV output noise and THD of .07% and IMD of .1% at 1W. Price includes P.C.B., data sheet and additional support components to complete. Just add pre-amp and power supply (not supplied) to build a high quality stereo amp.

**£15.80**

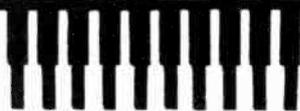

### PS463

Toroidal transformer, bridge rec and smoothing caps and instructions to make a suitable power supply for the STK 463 **£13.80** p.p. £2.00

### CPLM1

A versatile self contained sound to light unit comprising red, green and blue lamps in moulded cases that snap together to form columns on modulator. Extra snap together lamp cases to extend column or to construct extra lamp columns are available with lamps. Sockets on rear of unit enable up to 1000 watts of lamps to be connected to each channel. No need to connect to amplifier as modulator has a built in microphone, just connect to mains and its ready to go.

**£29.50**  
p.p. £2.50

extra lamp holders with lamps £4.50 p.p. £1.00 each.

Send large S.A.E. for further details of all our products.

Terms C.W.O. Add £1.00 p.p. unless stated. Prices do not include VAT, add 15% to total order and carriage price. Send order to

## WICCA ELECTRONIC SYSTEMS LTD

Orchard Works, Wallington, Surrey  
Phone: 01-669 6047

MAIL ORDER

CALLERS BY APPOINTMENT ONLY

## Electronic components in small quantities are our speciality



Our name is probably a new one to you, but we've been supplying technicians, workshops and hobbyists for a long time now. The personal service we give seems to have been appreciated, so we are now offering a component service nationally.

We don't give world shattering discounts, but our prices are very competitive; and our stock goes right through the range down to the most mundane plug or socket, which many suppliers don't even bother with. And if you only want one item - we'll sell you only one.

At GEAR you're known by your name and not a number, and any problems you have - just write or phone and our engineers are there to help. That's what personal service is all about.

**SEND SAE OR PHONE FOR FREE COMPONENT/PRICE LIST.**

**PRIC INCLUDE VAT & POST & PACKING - NO EXTRAS TO PAY.**

All components are manufacturers full spec. devices. (min. order by post £1.)

The Moor, Falmouth, Cornwall. Tel. 0326 312321.

# GEAR

## TV. & AUDIO SERVICE CENTRE

JAYkit



Standard Parts



+

=



DM-2



DIGITAL MULTIMETER

- ★ DC Volts . . . . . 1mV to 1000V
- AC Volts . . . . . 1V to 500V
- DC Current . . . . . 0.1mA to 0.2A
- Resistance . . . . . 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments  
21 Gladeside, Bar Hill,  
Cambridge CB3 8DY  
Tel: (0954) 80285

Name \_\_\_\_\_

Address \_\_\_\_\_

Please send:

- DM-2 @ £5.45  
 FG-1a @ £4.95  
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

# JAYkits

# EPROM PROGRAMMER

## PART 2 A.A. BERK B.Sc. Ph.D.

THE EPROM programmer is a straightforward device to add to any Bus-oriented MPU system, and this month an interface is described for the Compukit in particular, and other machines in general. A particularly simple machine to interface would be the KIM, for instance, since its "K" outputs provide 1K blocks of address decoding automatically. The only other connections are Data Bus, Address Bus and a single Read/Write line—again brought out to convenient external connections on the KIM.

Also, the rest of the hardware of the programmer is described along with Construction, Setting Up and Troubleshooting.

### MEMORY AND SWITCHING

As explained last month, IC3 provides the cycling addresses for RAM and EPROM while programming. During this time, the RAM places data to be "burned" on to the programmer's internal Data Bus. It is essential that none of this is allowed on to the MPU's Data Bus to cause a conflict. Tri-State buffers (IC7 & 14) perform this isolation when their ENABLE lines are held at a logic 1 by IC13 as explained below.

In addition, the MPU Address Bus must be disconnected from the EPROM and RAM while IC3 is cycling, and IC3's counter addresses must be allowed through. This function is performed by the selectors IC10, 11, and 12 when their pin 1's are held at a logic 0 by IC1. A zero from IC1 is also allowed through to pins 1, 4, 5, and 13 of IC13 during programming. This holds pins 11, 3 and 6 at logic 1. Pin 11 holds IC7 in its Tri-State mode and the RAM in its "READ" state to allow data out of the RAM. Pin 3 of IC13 holds IC14 Tri-State and pin 6 is unused in the program mode. The R/W line from the MPU is also ineffective during programming as IC13a and IC13d are held with their outputs "high" by the above. Finally, the Chip Select pins of the RAM are held "low" by IC1's  $\bar{Q}$  output via IC10.

While the machine is programming, IC9b produces 5 volt programming pulses to be converted to 27 volts for the EPROM. TR1, TR2 and TR3 perform this function. While  $Q$  and  $\bar{Q}$  of IC9b are at 1 and 0 respectively, TR1 is *on* forcing TR2 *on* and TR3 is *off*. This connects the program pin of IC4 (pin 18) to the 27 volt supply via R4, and TR2's "on" resistance. When the opposite condition holds, TR3 turns *on* and TR1 and TR2 *off* forcing pin 18 of IC4 to Ground through R4, R3 and TR3's *on* resistance.

Using p.n.p. and n.p.n. transistors (TR2 and TR3) in this mode ensures that almost all of the current supplied by the 27 volt supply is used by IC4 and very little sunk to Ground. At no time (theoretically) is the +27 volt supply connected to Ground via the output transistors. The only consistent path to Earth is via TR1, which, with R12 and R11 in series, will draw something of the order of half a milliamp from the 27 volt supply. This is, of course, apart from the normal leakage of TR2 and TR3 when *off*, and during the fast change over from *off* to *on*, which is at relatively low repetition rate.

### EPROM REQUIREMENTS

The 2708 specifications demand that, during programming,  $\bar{CS}$  (pin 20) be held at +12 volts. Thus, switch S1 is connected to supply this as well as the 27 volt program pulse to IC4. The difference between 2708 and 2716 are catered for by links L1-L8. The 2716 must receive +12 volts on pin 24 during programming instead of +5 volts, therefore L1 and L3 are replaced by L2. L7 is replaced by L8 so that when S1 is switched out of program mode, +5 volts is again applied to pin 24. Pin 20 is A10 and not  $\bar{CS}$  on the 2716, thus links L5 and L6 are used to apply a logic 1 or 0 to this pin, to select one or other 1K half of the 2716. Pin 18 doubles as the  $\bar{CS}$  and Program pin, and hence, out of the program mode, linking L4 supplies the ENABLE signal from IC13b.

Thus, during Program mode, the machine is disconnected from all external systems. Addresses are generated internally by the counters and fed to the EPROM and RAM. The latter, being in Read mode, places data to be programmed on the internal Data Bus which is collected by the EPROM and "burned in" over a number of program pulses.


When IC1 is reset, the machine re-enters its normal Read/Write mode.  $\bar{Q}$  of IC15 is at a "1" and hence pins 1 of IC10, 11 and 12 select the external Address Bus which is then allowed to communicate with the RAM and EPROM.

The ENABLE line (pin 2 of IC8) must be low to select the EPROM programmer, and the host microcomputer generates this signal as a normal part of its address decoding. The nature of the decoding decides which locations in memory the EPROM programmer occupies. When it is selected, the ENABLE must go "low" which, through IC8a and IC10, sets a logic 1 on pins 1 and 13 of IC13. This allows the R/W from the MPU system to gate a zero on WRITE or READ (to IC7 or IC14) depending upon whether it is performing a write or read operation respectively. During READ, R/W is "high" which, via IC13, places a zero on WRITE. This controls data direction through IC7 and IC14. If the RAM is to be selected, either the MPU system or the user must place a zero on the external A10 line—this becomes a zero on  $\bar{CS}$  to the RAM.


To select the EPROM, a logic one on A10 becomes zero (via IC13b) on the  $\bar{CS}$  pin of IC4 as long as S1 is in the non-program position. The MPU system may thus use the RAM and EPROM as normal blocks of memory. Programs may be written to, and run, in either.

### LED INDICATOR

While programming, the l.e.d. on IC8 is off, giving a positive indication of the state of the machine. If the l.e.d. is off after power up or at any time, a zero may be applied to the RESET line via IC1 and the programming cycle stops. A READY (and  $\bar{READY}$ ) signal is generated by the EPROM programmer and may be used by the MPU system to determine when the programmer is "BUSY". The positive-going "Program Initiate Pulse", via IC1, may also be generated by the MPU system, or a push switch operated by the user.

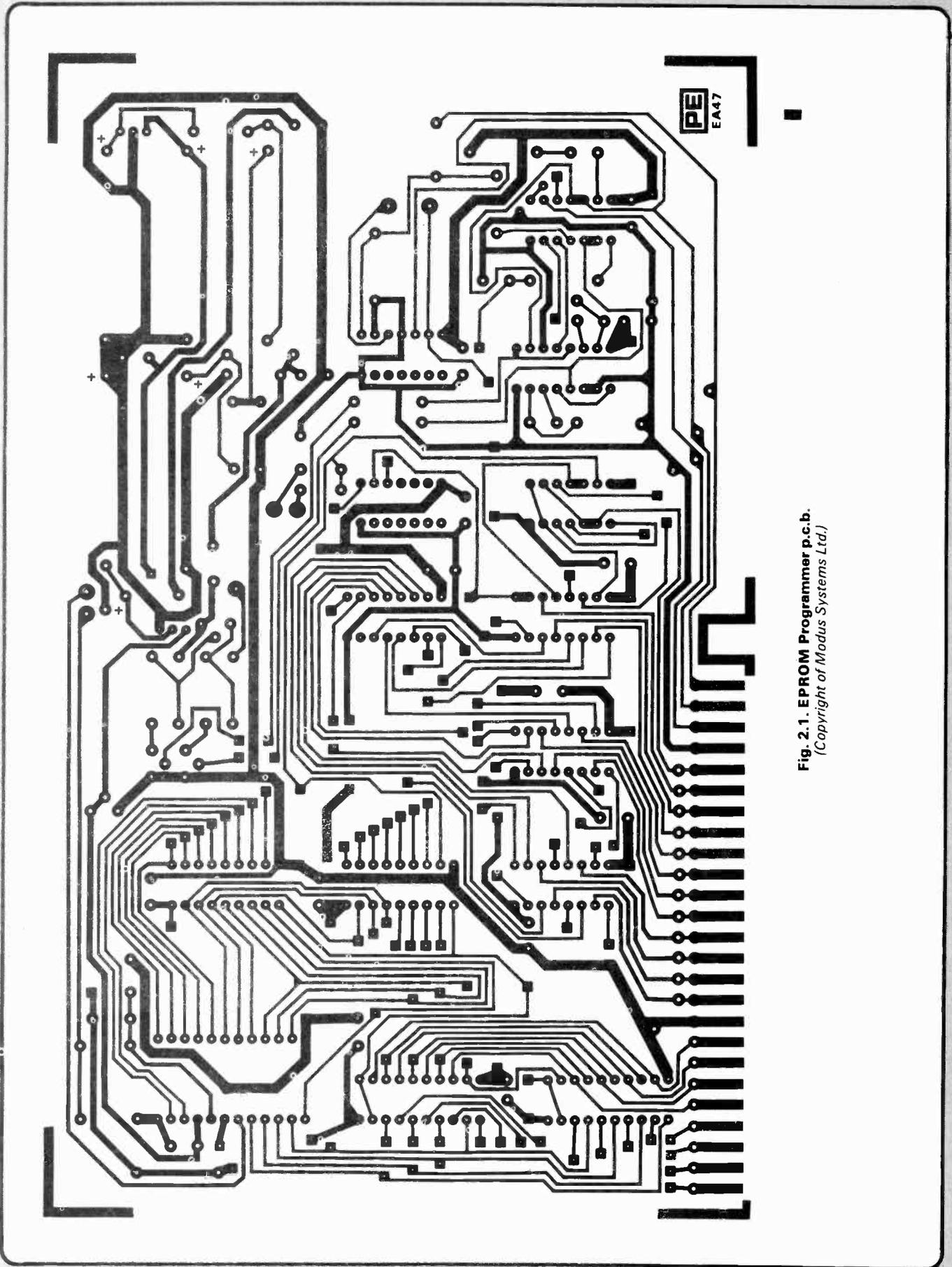

**Fig. 2.1. EPROM Programmer p.c.b.**  
*(Copyright of Modus Systems Ltd.)*

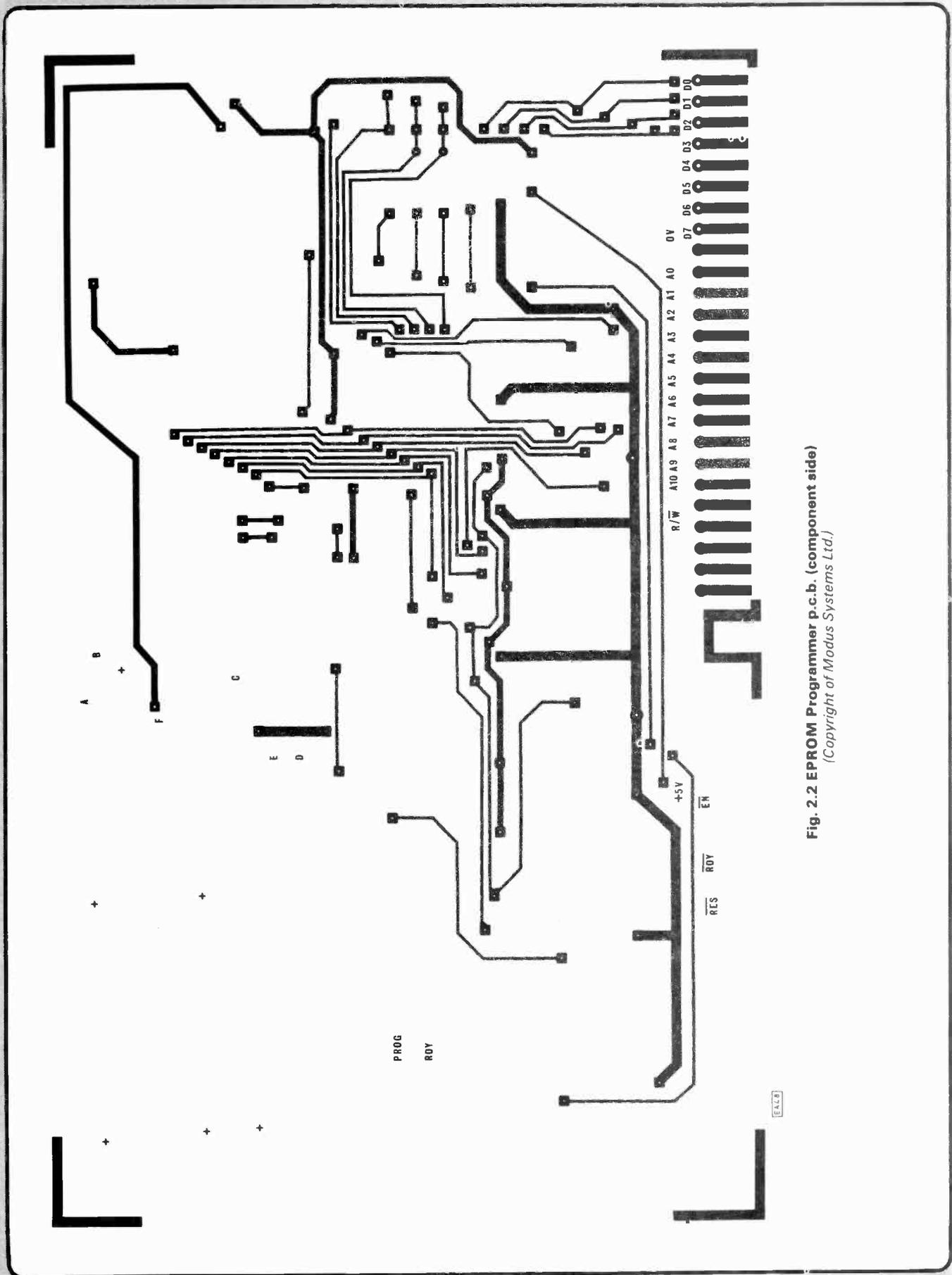

**Fig. 2.2 EPROM Programmer p.c.b. (component side)**  
*(Copyright of Modus Systems Ltd.)*

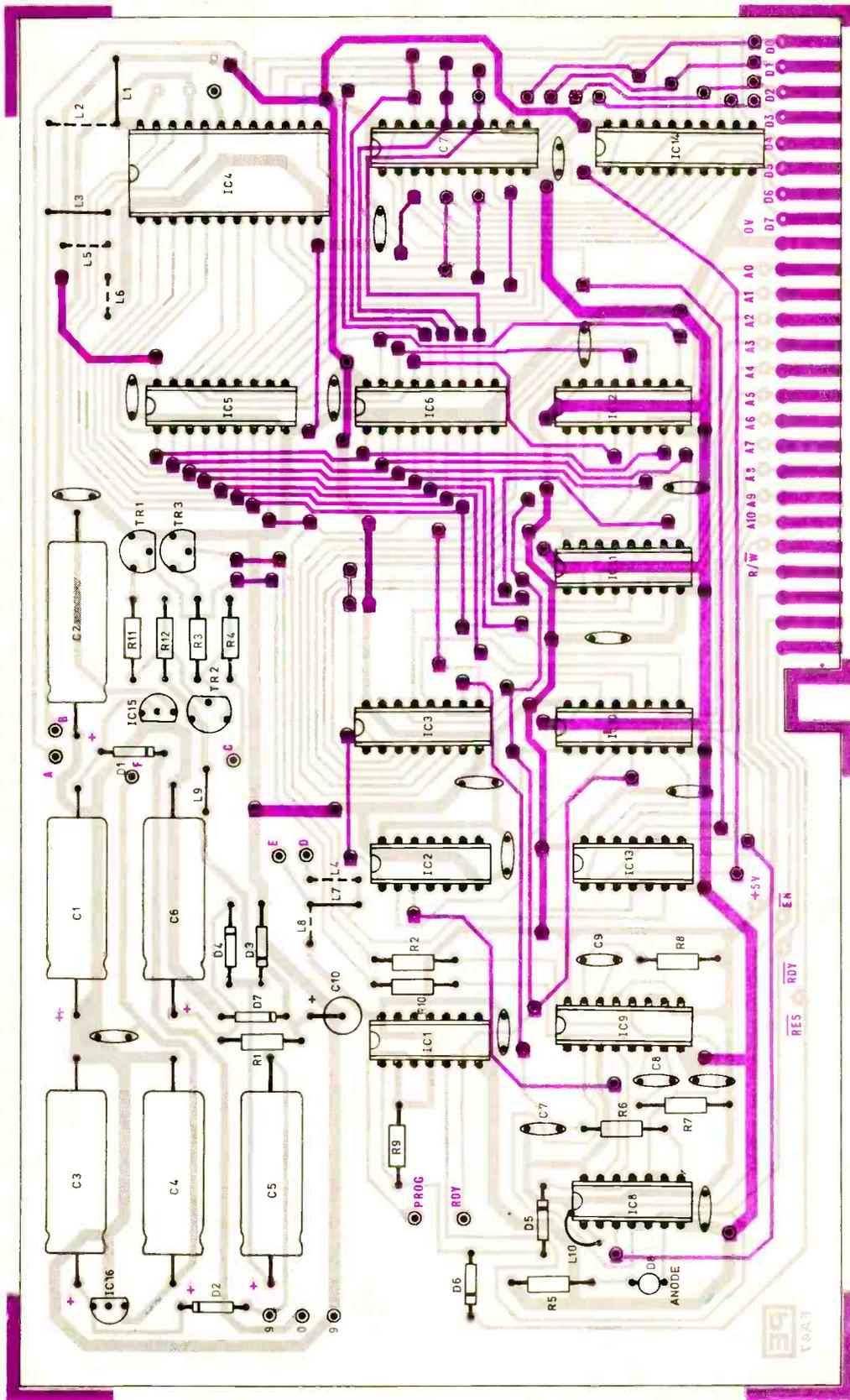


Fig. 2.3. Component layout. Note: R5 is 390Ω, and S1 is a d.p.d.t. Last month's components list is incorrect on these two points

## CONSTRUCTION

The machine has been designed for ease of construction. All connections are made to the bottom of the board, except for through-pins, and the odd discrete component whose lead may act as a through-pin. All i.c.s point the same way and all external connections are labelled on the p.c.b.'s upper surface. See Figs. 2.1, 2.2 and 2.3.

External wire links appear on the p.c.b. only insofar as they provide flexibility of options as described in the text, and they may well be replaced by switches for convenience.

A good plan is to through-pin the board first. In general pins will not push right through the board and they should not be forced to do so. Push enough of the pin through to connect the two sides of the p.c.b., solder both sides and clip off the excess pin length. This produces a very neat aspect to the board. The exception is for the externally connected pins which may be left unclipped to facilitate solder or crocodile clip connection.

The i.c. sockets should be inserted and soldered next, followed by the discrete components. Make sure that regulators, diodes, transistors and capacitors are connected up correctly as shown in the component overlay diagram, or permanent damage will result. The correct positioning of transistors and i.c. regulators is indicated on the p.c.b.'s upper surface. Finally, insert the i.c.'s and turn to the set-up and testing section.

## INTERFACE

Interfacing is a question of physically connecting wires for Data, Address and Read/Write lines, and arranging the address decoding.

A general interface with full MPU control of all lines is quite possible but is a little inappropriate for the majority of users, hence Fig. 2.4 suggests a simple interface where control is mostly directed by switches.

A two-bit I/O port on the MPU system could easily be utilised to provide 1's and 0's for  $\overline{\text{RES}}$  (Reset) and  $\text{PROG}$  (program initiate). A further line could accept the  $\overline{\text{READY}}$  signal from the EPROM programmer. However, most systems will require an EPROM programmer reasonably rarely and special software would be required for a fully MPU-controlled machine.

Thus, the EPROM programmer reset line is connected to a Ground switch and pull-up resistor, and the Program-Initiate pin to a +5V switch and pull-down resistor for hand use. A power-up reset is also suggested with a capacitor across the Reset switch. A 1K Address-Decode line is assumed here, thus only A0-A9 are fed to the programmer and A10, again, is set by hand to select RAM or EPROM. If a 2K or larger Address Decode line is available this may be connected to  $\overline{\text{ENABLE}}$  and the programmer's A10 connected to the MPU's A10 line: RAM and EPROM are then addressable together.

If two separate 1K decode lines are available (as with KIM and COMPUKIT), then Fig. 2.5 suggests how they may be connected to achieve the same result. Here, a zero on  $\overline{\text{D1}}$  or  $\overline{\text{D2}}$  forces  $\overline{\text{ENABLE}}$  to zero via nand gates a and b. If  $\overline{\text{D1}}$  is low, then  $\overline{\text{D2}}$  must be high and gate c receives two '1's, forcing A10 low which selects the RAM. If  $\overline{\text{D2}}$  is low and  $\overline{\text{D1}}$  high, then c receives a logic 1 and a 0. This forces A10 high, selecting the EPROM. A later section deals with interfacing directly to the COMPUKIT.

## SETTING UP AND TESTING

Assuming the EPROM programmer has been connected to the MPU system via Data Bus, Address Bus,  $\overline{\text{ENABLE}}$  and R/W lines, the correct links should be inserted for the EPROM type chosen. Table 1 describes all the link options

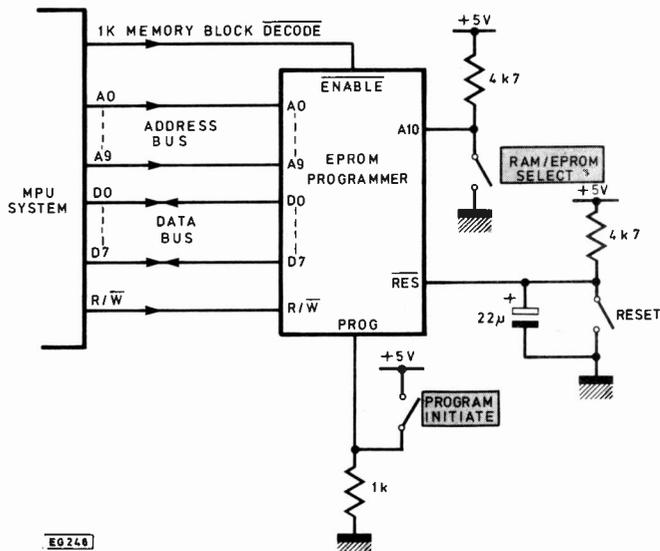


Fig. 2.4 Simple interface

on the board. Of course, any or all of the links could be replaced by appropriate switches if the links are to be changed frequently.

L5 and L6 must not both be connected simultaneously, even momentarily, as the power supply will be shorted. By using L5 and L6, each half of the 2716 is programmed separately, since the RAM holds just 1K of data and the 2716 has 2K. Connecting L1, L3, L7, excludes L2, L4, L8 and vice-versa. L9 is connected only for programming and a switch in this position (as for L5 and L6 if 2716's are to be used) would be most advantageous.

L10 should always be in place unless pin 1 of IC8 is required as a further  $\overline{\text{ENABLE}}$  input. This can be used to simplify Address Decoding in some systems. In this case, L10 is left unconnected and pin 1 of IC8a connected to a top-side pad of the edge connector for external connections via the edge socket. L10 is assumed connected in the following.

Certain checks are worth making when first using the machine. Make sure, before applying mains, that the secondary windings of the mains transformer are connected correctly—centre tap to the centre pin.

## AT SWITCH-ON

When first switching on, leave the EPROM out and L9 unlinked. Check the -5V and +12V supplies at the EPROM socket. Check +27V at L9.

The 12 volt regulator may become very hot during use. This can be replaced by a 1 Amp device at a very small cost if the overheating is excessive. Similarly, R1 dissipates some heat, and this can be replaced by two 1/2W 2K resistors in parallel or a 1W 1K resistor if the problem is excessive.

TABLE 1

LINKS	OPERATION
L1, L3, L7	2708
L2, L4, L8	2716
L5	Selects lower half of 2716
L6	Selects upper half of 2716
L9	Supplies 27 volts to Program Pulse switches
L10	Places a '1' on pin one of IC8. This is normally connected—but see text.

Neither of these modifications proved necessary on the prototype, even after many hours of use.

If the l.e.d. is off after switch-on, short **RESET** to zero momentarily. If the light remains off, check the +5V supply and then refer to the Troubleshooting section. Assuming everything is okay, check that the RAM is working, by Reading and Writing to it using the MPU system's monitor. The RAM must be selected by connecting A10 to zero if the MPU system does not perform this action automatically (see the section on interfacing). A small memory test program may be written to check that information can be written to, and read from, each location in the RAM.

If the RAM operation is satisfactory, check that S1 is in the non-program position and plug the EPROM into its socket. The EPROM should then be selected by ensuring that A10 is at "one". A test may be performed without sacrificing the contents of the EPROM in the following manner. The RAM should be filled with random data and either the EPROM absent or S1 in the non-program position. Set the programming cycle going by applying a positive pulse to the PROGRAM line. The Address lines to EPROM should be oscillating with A0 (pin 8) changing the most rapidly, A1 (pin 7) at half that speed and so on up to A9 (pin 22). At the same time, D0-D7 should all be oscillating and R4 should be applying 0.5 ms pulses at 27 volts to pin C of S1 with L9 linked. These are all necessary conditions for the correct working of the system.

## PROGRAMMING

Ideally, the sequence of operation is as follows. 2708 or 2716 links should be selected as in Table 1, with L5 or L6 in place if a 2716 is being used. A zero is placed on A10 and the RAM contents changed to the selected data for programming into the EPROM. If necessary, the contents of RAM may be checked—perhaps by running a program in the RAM block. Parts of the EPROM which are to remain unchanged must be presented with FF during programming and the corresponding blocks in RAM should contain FF, as explained in Part 1 last month.

Check that S1 is in the program position, link L9 and apply a logic 1 to the program line on IC1. The l.e.d. should switch off for about two minutes. During this time, the EPROM is being programmed. When the programming cycle is over, switch S1 back, take A10 to a "one" and check that the contents of the EPROM have been altered correctly. This may be done in several ways. A very convenient method of such verification is to write a program which compares the EPROM contents byte for byte with the contents of the RAM, or some "mirror" of the RAM contents in the MPU's RAM. An Error message could signal any disparities which may arise. Alternatively, if a program has been stored, it may be run *in-situ* in the EPROM.

L9 should be removed for safety, as soon as programming has finished.

## TROUBLESHOOTING

The test given in the above section is a good one for checking that counters, address switches and the 27 volt switch are all working, as well as the RAM itself.

If reading from RAM and EPROM or writing to RAM is not occurring, check connection between MPU and pins of IC10, 11, 12, 7 and 14 with a continuity tester and check that, while out of program mode, address information is passing through to Address pins of RAM and EPROM. A similar check may be made for data on IC7 and 14. An oscilloscope is helpful in troubleshooting, and will normally narrow down the fault very quickly to a poorly-soldered joint, missing component or a solder bridge.

IC13's connections, particularly, should be checked very carefully throughout the system with a continuity tester, as this component forms a major link in the control of the machine.

If the programming cycle is not even starting, check that IC1 can be turned on and off by PROG and RESET. Check the connections to IC9, where all the clocking information is generated, and check for appropriate length pulses on pins 13 and 5. Do not be alarmed if the 20µs turns out to be 30µs or the 0.5 ms is ±10 or 15%.

If the cycling is occurring but never stops, check that IC8c is connected correctly and read through last month's explanation of the working of the Program Timing and Control sections.


The usual theme for troubleshooting is to start at the clock, make that work and follow it right through the system. Again, a scope and a continuity tester are very important.

## COMPUKIT INTERFACE

The EPROM programmer has been designed, in part, to be plug-compatible with the CompuKit, and this section describes the actual connection necessary.

As in Fig. 2.4, connections for the Data Bus, Address Bus (A0-A9), the R/W Line and ENABLE line must be provided for the interface. The first three groups are quite straightforward. The ENABLE line, however, varies from system to system.

The EPROM programmer, illustrated in Fig. 2.4 acts like a 1K block of RAM or EPROM, depending upon the state of A10. That block of memory must be inserted into the memory map of the MPU system and only enabled for the appropriate 1K of Memory Addresses. The KIM has a set of outputs (called K outputs) used specifically for this purpose of "slotting in" external blocks of memory.

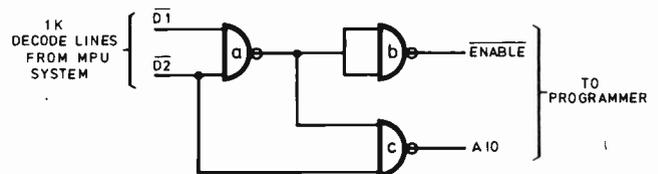

EG247

Fig. 2.5 Enable decode for CompuKit and Kim

If a machine does not provide those external address-decoding lines, it is usually possible to replace an internal 1K block of Memory with the external block by using the internal block's dedicated Address Decoding line. This technique is used on the CompuKit. IC38 and IC52 on the CompuKit are removed from their sockets and the EPROM programmer plugged into their place. This places the memory of the programmer in the address block: 1C00 → 1FFF. Of course, any of the 1K blocks from 0400 onwards may be used, but this will restrict the BASIC workspace. 0000 → 03FF may not be used as this provides scratchpad for the COMPUKIT's monitor program. Fig. 2.5 shows the Connection diagram for the above interface.

The Programmer's +5V power may be supplied by a CompuKit with improved regulator heat-sinking. Two d.i.l. plugs and ribbon cable are most convenient for this link up and the cable may be soldered to an edge-connector socket which is plugged into the programmer's edge-connector surface. This forms a very neat job and allows instant unplugging of the devices when not in use.

The Address Decoding RS7 is supplied by IC38's socket in Fig. 2.6, as is the R/W line and Address Bus. Only half of the Data Bus is available at IC38's socket, hence the connection to IC52's socket. Use of the machine is quite simple. A10 is set to a low level to select the RAM and the program switch is off. RESET is brought low if the l.e.d. is off and the machine is ready for use. (Check that L10 is connected).

If some of the EPROM is to remain unprogrammed, a short BASIC program is written to fill addresses 1C00-1FFF with FF before the RAM is filled with a block of information to be stored in the EPROM. A program is given below for this process. The only point to remember is that all addresses and data are in *decimal* in BASIC.

```
10 FOR I = 7168 TO 8191
20 POKE I, 255
30 NEXT
```

This can be checked by replacing line 20 by:

```
20 IF PEEK(I) < >255 THEN PRINT I
```

Any locations not containing FF (255 in decimal) will be found and their addresses printed out on the screen. The erased EPROM may be checked by taking A10 "high" (which selects EPROM) and running this program.

The RAM may now be filled with binary information either by resetting the Compukit and using "M" to enter the machine code monitor, or by using the Compukit's powerful extended machine code monitor.

To program the EPROM, L9 is connected, the program switch (S1) thrown, and PROG brought high momentarily. When the l.e.d. comes on again, switch S1 back, remove S9, bring A10 to a high level and read the EPROM through to check the contents.

If Fig. 2.5 has been used to replace the upper 2K of memory with the programmer, the EPROM and RAM may be read and compared directly by the Compukit to verify EPROM contents. The connections for this would require IC37 and IC51 to be removed and RS6 (pin 8 of either socket) would be connected to  $\overline{D2}$  (Fig. 3).  $\overline{D1}$  would be connected to RS7 (pin 8, of IC38). The RAM would then reside at addresses 1C00-1FFF and the EPROM at addresses 1800-1BFF (DECIMAL 6144-7167).


The following program would check EPROM against Ram:

```
10 FOR I = 0 TO 1023
20 IF PEEK (6144 + I) < > PEEK (7168 + I)
   THEN PRINT (6144 + I)
30 NEXT
```

This will print out those addresses in EPROM which disagree with the RAM contents.

**TABLE 2**

Special EPROM programmer signals	Function
A10	HIGH level selects EPROM LOW selects RAM
RESET	LOW pulse stops programming cycle
PROG	HIGH pulse initiates programming cycle
ENABLE	LOW level selects RAM or EPROM depending upon A10
READY (output)	LOW level output from here implies programming cycle has stopped— i.e.d. in ON condition
READY (output)	Inverse of READY line

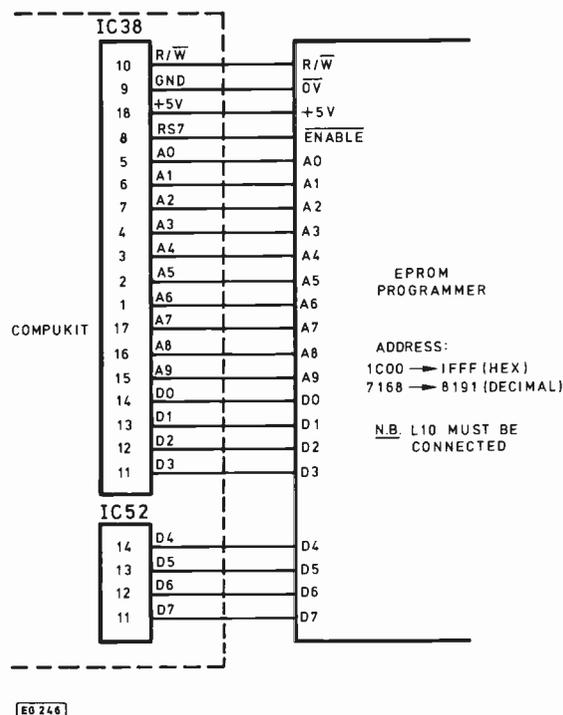

**Fig. 2.6 Interface for Compukit**

If this occurs, the RAM should be checked through for correct data and the EPROM reprogrammed. If a few unrelated locations remain unprogrammed, then either the EPROM was not fully erased or the chip is faulty. If many locations are incorrect, the programmer's operation must be suspected.

Adding the programmer to the Compukit, as in Fig. 2.6, does not in any way restrict the Compukit's memory, as 1K of RAM is still available in the programmer for normal use. This 1K of RAM, however, has the added advantage that its contents may be stored permanently.

### ERASING

Erasure of the EPROM consists of shining a strong Ultra Violet light through the transparent quartz window in the package's upper surface. Short wave UV is required (around 2500 Angstrom units) and exposure time varies from 8 minutes to one hour or more, depending mainly upon UV intensity. A medicinal "sunray" light has been found to perform erasure quite effectively, and some experimentation for erasure time is essential.


Erasers may also be purchased and several are advertised in this magazine. In addition, PE has published an EPROM eraser (June 1978) as part of the CHAMP articles and this would be an excellent inexpensive alternative.

### CONCLUSION

For many years, the problem of non-volatile memory storage has been solved by media such as paper-tape, disc and cassettes. These media are still important for mass storage. However, the coming of Micros has led to the need for permanent *alterable* storage of small capacity. This need is satisfied by the 2708 family and the EPROM programmer described here in an inexpensive, but highly flexible manner.

In addition, anyone attempting the development of an MPU system from scratch, may use another system plus the programmer to produce the all-important and previously elusive System Monitor required by any machine when first powered up. ★

# PATENTS REVIEW...

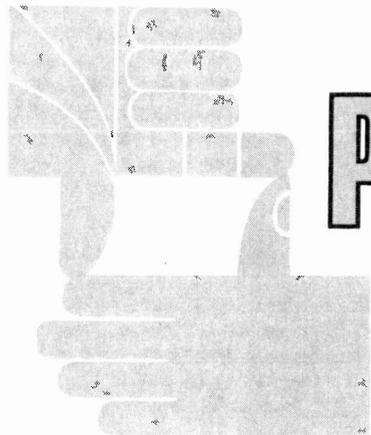

Copies of Patents can be obtained from :  
the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

## TOUCH SENSITIVE CONTROLS

Two recently published British patent applications disclose proposed improvements in touch sensitive controls. Application number 2013032 (filed under the new laws and dating back to July 1977) describes an idea by Jacques Lewiner and Claude Henion of France. The aim is to provide a touch-sensitive electret suitable for use as a multiple key keyboard, for instance in a musical instrument. But according to the inventors the same principle can be adopted for the construction of sound and shock wave sensors.

Fig. 1 shows a touch sensitive electret which is already known. A sandwich is formed from outer electrodes 1 and 2, inner electret 4 and rigid spacers 6. The electret is of conventional dielectric foil with a permanent electric charge on at least one face F. In practice the electrode 1 is often formed by metalisation of a flexible electret 4 to give a combined thickness of less than 100 microns. When pressure is applied the charged face F moves temporarily closer to the electrode 2 and a small current flows in circuit 3. The spacers provide essential limiting of the electret movement but, being rigid, prevent the contacting areas of the electret from contributing any signal. This reduces overall efficiency.

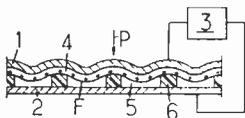


Fig. 1

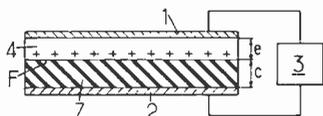


Fig. 2

Fig. 2 shows the invention. The rigid spacers 6 are omitted and an elastic layer 7 of elastomer is sandwiched between the electret 4 and electrode 2. The elastomer is more flexible, or softer, than the electret and has very high electrical resistivity, in the order of  $10^{15}$  ohms/cm to  $10^{17}$

ohms/cm. Because of its deformability the elastomer layer offers relatively little physical resistance to movement of the electret, but because of its high resistivity, prevents the formation of an inter-electrode conduction path. The inventors suggest that a silicon-based compound, for instance siloxane, is ideal. Impedance adaptation circuits are suggested to make the response more linear with pressure and frequency.

Thorn of Upper St. Martin's Lane, London, have filed a British patent application (2 013 984) which dates back to January 1979 and claims touch sensitive controls for electrical circuitry, particularly a domestic liquidiser or blender. The claim to a patent monopoly is very broad and doubtless readers will have their own views on whether Thorn's ideas were, or were not, new in early January 1979 when the application was filed. (The legal procedures open to readers who believe that ideas are not as new as inventors claim were detailed on page 68 of *Practical Electronics* April 1979).

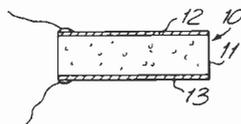


Fig. 3

Thorn proposes a strip of conductive foam of which the electrical resistance changes with finger pressure to produce an analogue control signal. This signal is used to govern the speed and duration of operation of a drive motor for a liquidiser. One foam touch control increases motor speed, another decreases motor speed, a third increases duration of the motor operating cycle and the other decreases the cycle duration. Fig. 3 shows one type of foam control. A strip of conductive foam 11 is sandwiched between flexible contact 12 and rigid contact 13. Pressure on contact 12 compresses the foam to decrease the resistance between contacts 12, 13. Another type of control is shown in Figs. 4 and 5. Foam strip 211 carries contacts 212, 213 and is supported by insulators 214, 215. Parallel conductors 216, 217 extend along the underside of the strip. A

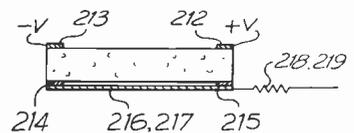


Fig. 4

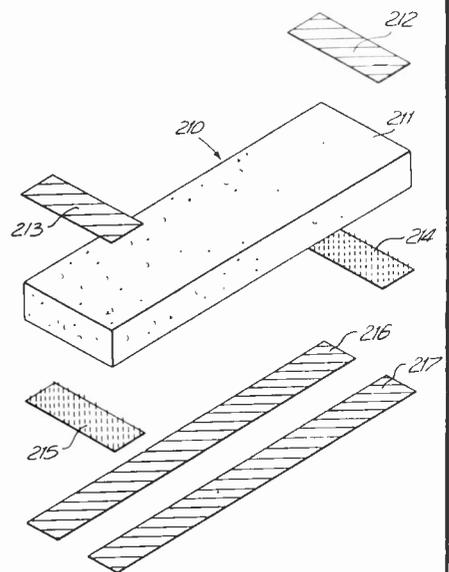


Fig. 5

voltage is applied across contacts 212, 213 to create a potential gradient along the strip and pressure on the foam causes the conductors 216, 217 to assume the potential existing at the pressed point. Hence the voltage appearing at 216, 217 is independent of actual pressure.

Thorn suggest digital circuitry on which the analogue control signals operate. Essentially this relies on a clock pulse generator and divide by 16 counters with lines of l.e.d.s which are gated to display the desired time of motor operation as a bar of lights whose length varies with selected time. The l.e.d.s also indicate selected speed in a similar manner. A motor interface circuit uses a triac/diac combination to govern speed by phase control.

# Readout...

## A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

### Public Radio Facility

Sir, I am pleased to read the positive comments in your editorial addendum (on p. 67 Oct '79 P.E.) following the article *CB in the UK* by Dr. Mark Sawicki. The writer of the article did not refer to the many overwhelming disadvantages of the present useage in the 27MHz spectrum using amplitude modulation and in fact ignored the more than probable granting of v.h.f. or u.h.f. Public Radio Facility. Possibly frequencies in the 420-430MHz part of the u.h.f. spectrum will be granted, being eminently suited to local portable, mobile and base useage. Narrow-band f.m. will of course be used for a variety of technical reasons.

Not only is the present Trans-Atlantic lingo-apeing an insult to anyones intelligence but the propogation characteristics in the 27MHz region combined with aerial inefficiencies and proneness to interference combine to make that part of the spectrum the most unsuited to the task for which the public require it i.e. local personal communications. Pity the poor person stuck up on a mountainside with a 1 watt (a very enthusiastic rating more than likely!) hand-held unit with short whip aerial trying to get 20 miles or more with racous foreign interference to contend with. On u.h.f. there could be a community based repeater made avaiable for an emergency channel with built-in automatic scanning in all units to lock into such emergency transmissions.

Even now some users on 27MHz are trying to boost their range through the use of so-called linears which are very efficient at producing harmonics, especially when used by non-technical persons. Already some of the few users here in Ireland (illegal of course) have managed by using mistuned aerials or amplifiers to be heard on 2nd, 3rd and 4th harmonics, in addition to causing interference with their high power fundamental to paging and model control users. Advertising in the newspapers and shop-windows is open and blatant, and the whole situation is fast getting out of control.

Hopefully the Personal Radio Service will shortly be announced on v.h.f. or u.h.f on a basis similar to that being advocated by the C.B.A. (Citizens' Band Association). There is some reluctance by the authorities however as to the possible release of frequencies for private communications.

The low price of some 27MHz units now being made available is I am sure due to massive over production and subsequent cash-flow problem. Dealers have to empty warehouses quickly. Let us hope that the resultant flow of equipment on to the market does not influence the introduction of an out-

dated and technically inferior service. British technology and production can rise to the challenge of a good v.h.f. or u.h.f. f.m. service.

Those who support 27MHz must not have had experience of the quality of v.h.f. otherwise they must want to join the nest of furtive clandestine operators trying to "work the skip", just a cult. I look forward to the announcement in British Parliament of an enquiry into the possible granting of a Public Radio Service.

D. Walsh, Co. Tipperary.

### ROMs

Sir, Our ROMs have arrived! Our Compukit is working! But what a gruelling experience it has been. We saw the prototype on April 2nd and, under the impression that we were amongst the privileged few to have heard of it at this early stage, ordered immediately for delivery in about "ten weeks"—i.e. June 11th. By the time of the Chancellor's speech, delivery was promised for the end of June or "early July" so we paid in full while VAT was still 8 per cent. We collected the kit on July 5th with the ROMs promised for "two or three weeks", then "definitely August 15th". On the 15th it was again "two or three weeks"; three weeks later on September 5th it was "they are at Heathrow". On September 8th we got more impatient as term was approaching and we had already proved our Compukit worked (with Superboard ROMs), but we were satisfied with "We'll have them early next week and will post them to you by first class post on Tuesday or Wednesday". The following Thursday, the 13th, it was "Yes, we've sent them all off today". On Saturday 15th it was "I'm not sure at the moment but I'll check the files and if we haven't sent yours off already we'll send them off first thing on Monday . . . We posted them all off on Thursday and Friday".

On Tuesday 18th things changed: "You'll get yours next week—we sent 800 off last week to those who ordered their kits when it was announced in February and March". February? We saw nothing in print about the kit until May, and I have still not discovered where this "announcement" was made.

On Thursday 27th: Actually it was 500 . . . or 460 . . . sent off last week. The next batch of 1,000 is "at Heathrow" due to arrive on Saturday and to be posted to us "next week". By October 10th I had written three letters to COMPshop (ne'er any reply) and located Compukit owners with and without ROMs (the one with had ordered his kit three months after us). By the 18th we were told that two sets posted to us must have "got lost in the

post" so another set was posted on the 19th by recorded delivery and this arrived on the 20th. More than four months late—but for the last six weeks we had been led to expect delivery almost every day. Perhaps we have wronged COMPshop—could the Post Office have lost all their replies as well as the two earlier sets of ROMs?

Incidentally, have you tried giving a "Memory size" of 20 or 30 thousand bytes? You will get a pleasant surprise! It is also interesting to compare strings in immediate mode, and to find how soon the random number generator recurs (it's after 1861 calls). However, we do find the Compukit to be excellent value for money and would now be building our second if we thought we could trust the supplier—but now we are waiting eagerly for the Nascom 2 we ordered an hour before the ROMs arrived!

C. C.H. Dawkins, Felsted School, Essex.

*Unfortunately, as you are aware, the problems have affected many readers. At least Comp. now have kits (with ROMs) in stock.*

### Computerised

The purpose of my letter is to give profuse praise for the newest of my project completions—i.e. COMPUKIT UK 101 by Dr. Berk. After excruciating—and obviously unavoidable—delays in obtaining the BASIC ROMs, my computer worked first time and it has delighted and astonished me since that first magic moment. I am totally impressed and already, in my field of secondary education, it has proved to be a boon, and unforeseen uses loom. Exciting possibilities are glimpsed and oh! how I wish I were more capable of programming my ideas. My ineptness in this respect is a barrier, which, in middle years, is slow in being absorbed. I have great visions and moderate expertise to make them manifest.

I offer some suggestions for future consideration and the very fact that I take the trouble to write to you about them should add emphasis to my concern:

1. A "feed-back" column with short snippets.
2. This is the most important request: An article on graphics. I really would appreciate a structured article on the use of POKE and PEEK and their use in producing diagrams etc.
3. Your last article showed that POKE 530, 1 disables the CONTROL C use. What other facilities are there available hidden away in the ROM's? For example: I would like to write messages in immediate mode—more than one line produces SYNTAX ERROR. If I use the SHIFT P @ line feed I am left with @ which I do not want. Am I able to disable the @ sign but still obtain a new line?

I hope my letter conveys my real pleasure and appreciation and I hope my suggestions are constructive.

J. W. Coulthard, York.

We will be starting a "Computing Corner"—possibly next month—with some of the ideas you sent in. We will also look at your other suggestions.

# Switching Regulators

D.L.H. Smith B.Sc.

**T**HE SWITCHING regulator is a relatively new circuit for the control of d.c. voltages. It takes the place of a normal series regulator in a power supply. The basic problem with series regulators is that, because of the voltage drop across the pass transistor, they tend to be very inefficient. The ratio of output power to input power is typically in the range of 30–40 per cent in good conditions.

Because in switching regulators the regulating transistor is either switched on or off, very little power is dissipated in it, and efficiencies in the order of 70–80% are possible.

Apart from the obvious advantage of higher efficiency, the switching regulator has other advantages. Because of the nature of operation, a switching regulator can not only convert voltages down, but can also convert them up, and even invert the polarity. Consequently they have a wide use as unisolated d.c. to d.c. converters.

## HOW THEY WORK

The basic switching-down regulator circuit is shown in Fig. 1. This consists basically of the following elements: switching transistor TR, storage inductor L, smoothing capacitor C, commutation diode D, and a controlling circuit (which will be discussed later).


When the input voltage  $V_{in}$  is applied to the circuit, the control circuitry senses that the output voltage  $V_{out}$  is low, and switches the transistor on at time  $t_1$ . A current  $I_L$  flows through the inductor L into the load. The current in L reaches a peak value  $I_{peak}$ , and the transistor is switched off at time  $t_2$ . The inductor is now storing an energy equal to  $0.5 L I_{peak}^2$ . The current now flows into the capacitor C, the diode D completing the circuit. So energy is transferred from the inductor L to the capacitor C. The energy stored in the capacitor is equal to  $0.5 C V_{out}^2$ , and provided that the energy dissipated in diode D is small, we can say that  $0.5 C V_{out}^2 \approx 0.5 L I_{peak}^2$ .

Now that C is charged up, it can supply current to the load. As the voltage across C falls due to the load, the control circuitry senses this and the transistor is turned on once again at time  $t_3$ , repeating the cycle. If the load takes little current from the output, the interval between the transistor switching on and off is large, and if more current is taken, the interval between switching is much shorter, and capacitor C is charged up more often, thus providing more current. These conditions are clearly illustrated by the two waveform diagrams Figs. 2 and 3.


The control circuitry consists basically of a voltage comparator, which compares the output voltage with a reference level. This feeds a voltage controlled oscillator, which then drives an output transistor. All these functions are normally included on one i.c.
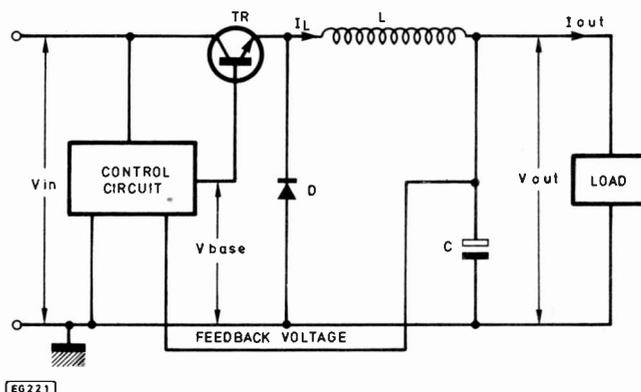
## SWITCHING-UP AND INVERTING REGULATORS

Since the switching regulator circuit works by the transference of the energy in the storage inductor to the capacitor, there is no reason why we cannot make the output



E0222

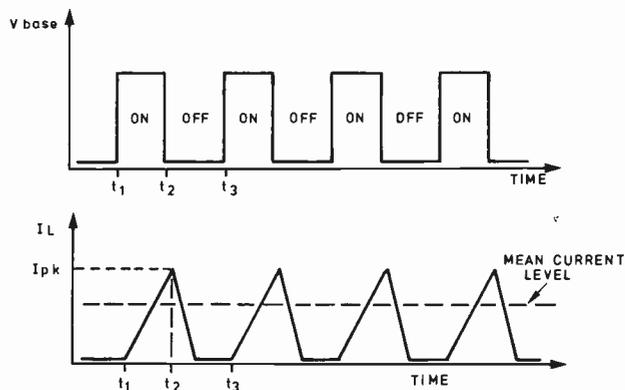

E0223

Fig. 3. As above but for high load current

voltage higher than the input voltage, provided we decrease the output current. However, we need to change the position of the commutation diode to prevent the smoothing capacitor from discharging back to the lower voltage input. The new circuit configuration is shown in Fig. 4.

When the transistor T turns on, the current in inductor L increases up to a peak current, storing energy as before. When the transistor is turned off, the only way the current from the inductor L can flow is through the diode D, transferring its stored energy to the capacitor C.

By using yet another circuit configuration, it is possible to invert the input voltage, so where the input voltage is positive with respect to ground, the output voltage is negative with respect to ground. In this case, it is possible for the magnitude of the output voltage to be greater than or less than the value of input voltage. The circuit used is shown in Fig. 5. It works in a similar way to the previous circuit, with a few changes, as explained here. The transistor TR is first turned on, the current through

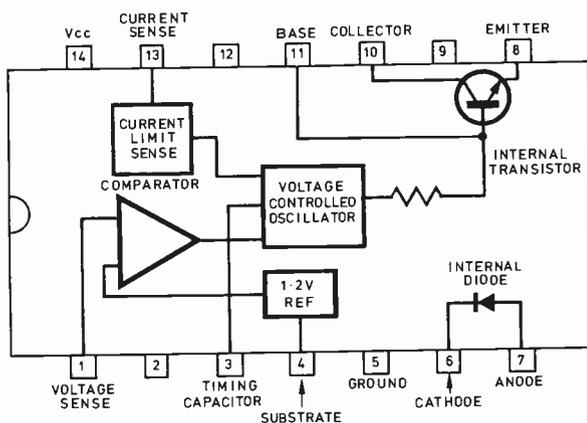
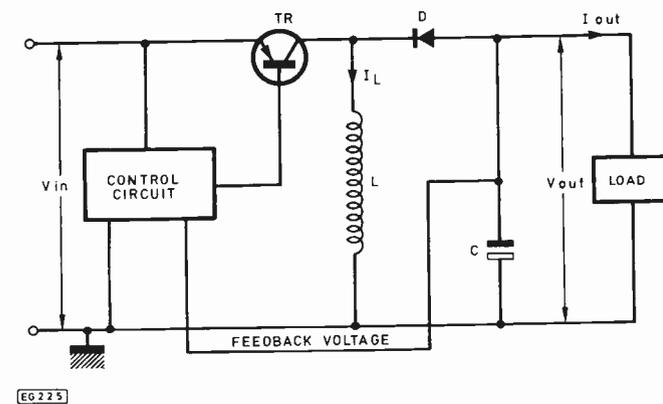
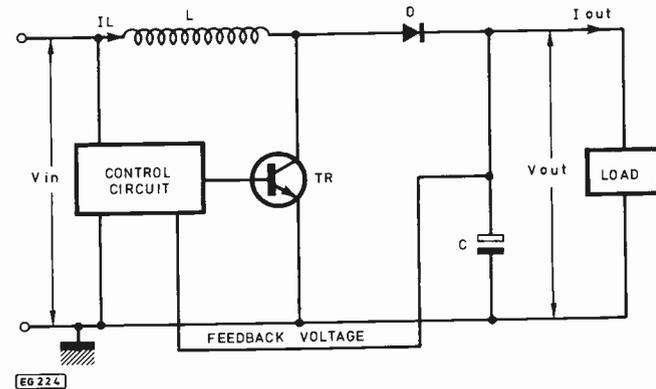


Fig. 6. Internals of the TL497. Pins 9 and 12 are N.C.

the inductor L again rises to a peak value. When the transistor is turned off, the current in the inductor flows into the capacitor C, charging it up. Again, the commutation diode D completes the circuit, but it is now in the opposite direction, charging the capacitor C negatively, which provides the negative output voltage.

## CONTROL CIRCUITRY

One i.c. that provides all of the necessary functions for the circuits described is the Texas Instruments TL497. A block diagram of the i.c. is shown in Fig. 6.

For low output power circuits, the internal transistor and diode can be used as the switching transistor and commutation diode.

Operation of the i.c. is as follows: Pin 1 senses the output voltage (suitably divided down) and compares it with the internal 1.2 volts reference. If the output voltage is too low, the comparator voltage increases and drives the oscillator faster. The oscillator then switches the internal transistor. The current limit senses the voltage between pins 14 and 13 (across which there is normally a low value resistor). If the current flowing is too great, the oscillator is disabled.

Pin 4, the substrate, must be connected to the most negative voltage point in the circuit. This is so that the voltage appearing at pin 1 is of correct polarity. Pin 2 is always connected to ground.

In the case of higher output power circuits, the internal transistor is used to switch an external transistor, and an external diode is used, normally a fast switching type.

## PRACTICAL EXAMPLES

Three practical examples are considered:

- (i) Switching-down regulator, with an input of 11–15 volts, and an output of 5 volts at 1 Amp (Fig. 7).
- (ii) Switching-up regulator, with an input of 11–15 volts, and an output of 24 volts at 300mA (Fig. 8).
- (iii) Inverting-regulator, with an input of +12 volts, and an output of –12 volts with respect to ground (Fig. 9).


All of these circuits have quite high peak inductor currents, and hence need inductors which can handle this current at the required frequency. These can be wound on ferrite cores. Mullard type LA4348, or similar, with an inductance-per-turn factor ( $A_L$ ) of 100.

In all of these designs an input capacitor C1 is included. This provides a charge store, to prevent current spikes occurring in the input leads. Capacitor C2 is the timing capacitor, which determines the length of the transistor conduction time (and hence peak), and the maximum operating frequency.

The resistor dividing chain R4 and R5 attenuates the output voltage to 1.2 volts so that it can be compared with the TL497's internal 1.2 volts reference. Capacitor C4 is included in the switching-down regulator circuit to improve the stability of the attenuated 1.2 volts signal.


Resistor R1 is the circuit current sensing element. Current sensing performs two functions: (i) When switched on, the current sensing circuitry "soft-starts" the unit. This means that a large initial inrush of current through the transistor, which might damage it, is prevented. (ii) If too much output current is drawn, the current sense circuitry will limit it, preventing any damage. The current sense circuitry operates when the voltage across R1 increases above one transistor Vbe drop (about 0.6 volts).

In the circuits shown in Figs. 7 and 9, a T1P 42 p.n.p. main switching transistor is used. When the TL497's internal transistor switches on, the T1P 42's base is connected to ground via R3, the base current limit resistor, and hence is turned on. R3 was chosen as 27Ω, so that the T1P 42 base current ( $I_{base}$ ) would be great enough for the equation  $\beta I_{base} > I_{peak}$ , the

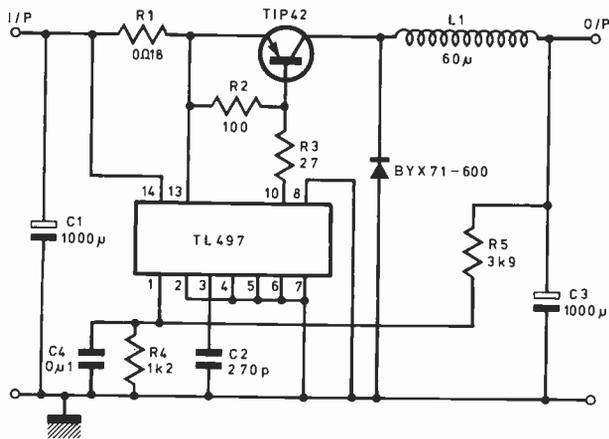


EO228

Fig. 7. Switching-down regulator. Coil: 25 turns of 20 SWG on Mullard LA4348 ferrite

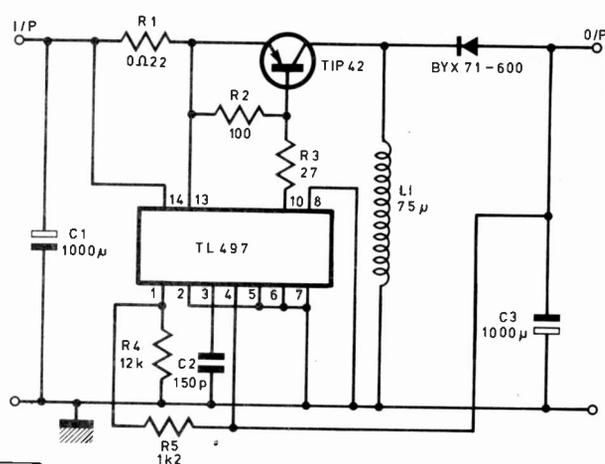

EO230

Fig. 9. Inverting regulator. Coil: 27 turns of 20 SWG on LA4348

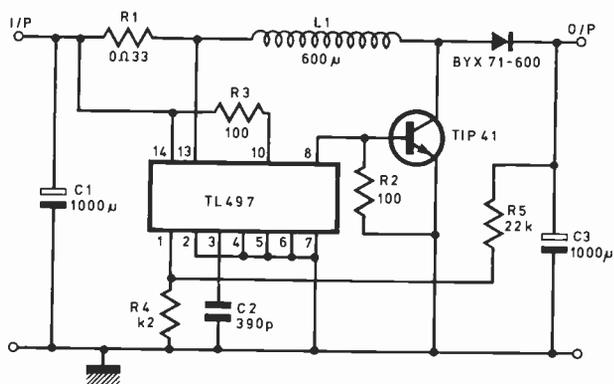

EO229

Fig. 8. Switching-up regulator. Coil: 77 turns of 26 SWG on LA4348

peak transistor current (where  $\beta$  is the transistor current gain). In the switching-up circuit (Fig. 8), a TIP 41 n.p.n. main switching transistor is used. When the internal TL497 transistor is switched on, current flows via R3 through it into the TIP 41 base, turning it on. The base current limit resistor is chosen for the same reasons already discussed.

The base-emitter resistor, R2 in all of the circuits acts as a stored-charge damping resistor. This rapidly removes the stored charge in the transistor's base, enabling faster switching and hence higher circuit efficiencies.

## News Briefs

### NEW ASSOCIATION

AT A meeting in London recently an association was formed for computer retailers, which, it is hoped will be the end user's best guarantee of service and support. Called the "Computer Retailers' Association", it is also anticipated that every reputable firm in the industry will become a member.

The purpose of the Association is to maintain and improve standards within the industry and represent the industry to the outside world, government and press etc.

Companies willing to subscribe to the Association's code of practice should apply to Ms. Heather Hodgson, 47 Creswell Road, Newbury, Berks. Tel. Newbury 42486.

Finally, consideration must be given to the commutation diode. Normal rectifier diodes are very inefficient at these high frequencies. This is because they have a relatively high forward voltage drop, and a long reverse-recovery time (the time taken to switch from the conducting state to the non-conducting state). An ideal diode for these circuits is the BYX 71-600 fast switching diode.

The i.c. connections for the different types of circuit are shown in the following practical examples, Figs. 7, 8 and 9. Notes on construction: The current sense resistor between pins 13 and 14 should be at least a 2.5 watt resistor. The switching transistor and the BYX 71-600 should both be mounted on a heatsink insulated with mica washers and bushes.

All of these practical circuits have a peak inductor current of between 2 and 3 Amps and an overall efficiency of about 70 per cent.

### CONCLUSION

Switching regulators do have some disadvantages; they tend to cost more than simple series regulators and have a larger output ripple voltage, in the region of 100-200mV. However, this is not much of a problem for many of the applications in which they are used.

Switching regulators are a relatively new type of circuit, which have been made possible by the introduction of low-priced control i.c.'s and fast switching diodes. They are beginning to find widespread use in industry, especially where efficiency is important.

### BACK AGAIN!

DORAM Electronics Ltd. is to be relaunched under the ownership of the Dutch "De Boer" Group, who will run mail order for both kits and components based on the current Dutch catalogue rather than the previous Doram range. However, warranties for goods purchased during the Electrocomponents ownership will be honoured.

### RAIBC

THE NEW address of the Radio Amateur Invalid and Blind Club is 9 Rannoch Court, Adelaide Road, Surbiton, Surrey KT6 4TE.

The RAIBC, which last year celebrated its Silver Jubilee, comprises invalid and blind amateur radio enthusiasts, and local representatives who assist with visits, repairs and advice. The sole condition of membership is an annual subscription of £1 minimum for "Radial" the club newsletter, issued every six weeks. Details from the secretary, Mrs. F. E. Woolley.

# STEVENSON

## Electronic Components

CMOS			
4020	50p	4050	25p
4022	50p	4060	80p
4023	13p	4066	30p
4024	40p	4068	13p
4001	13p	4025	13p
4002	13p	4026	90p
4007	13p	4027	28p
4009	30p	4028	45p
4011	13p	4029	50p
4012	13p	4040	55p
4013	28p	4041	55p
4015	50p	4042	55p
4016	28p	4043	50p
4017	47p	4046	90p
4018	55p	4049	25p


FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	7475	25p
7401	10p	7476	20p
7402	10p	7485	55p
7404	12p	7486	20p
7406	22p	7489	135p
7408	12p	7490	25p
7410	10p	7492	30p
7413	22p	7493	25p
7414	39p	7494	45p
7420	12p	7495	35p
7427	20p	7496	45p
7430	12p	74121	25p
7432	18p	74122	35p
7442	38p	74123	38p
7447	45p	74125	35p
7448	50p	74126	35p
7454	12p	74132	45p

OPTO			
LED's	0.125in.	0.2in.	each 100+
Red	TIL209	TIL220	9p 7.5p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips		3p	

DISPLAYS			
DL704	0.3 in CC		130p 120p
DL707	0.3 in CA		130p 120p
FND500	0.5 in CC		100p 80p

### SKTS

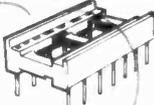

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

3 lead T018 or T05 socket. 10p each  
Soldercon pins: 100:50p 1000:370p

### PCBS

VEROBOARD			
Size in.	0.1in.	0.15in.	Vero
25 x 1	14p	-	Cutter 80p.
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 4.7	205p	185p	

Single sided pins per 100: 40p 40p  
Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.  
'Dalo' pens. 75p each.  
Five mixed sheets of Alfac. 145p per pack.

### RESISTORS

Carbon film resistors. High stability, low noise 5%  
E12 series. 4.7 ohms to 10M. Any mix:  
each 100+ 1000+

0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

#### METAL FILM RESISTORS

Very high stability, low noise rated at 1%  
Available from 50ohms to 330k in E24 series. Any mix:  
each 100+ 1000+

0.25W	4p	3.5p	3.2p
-------	----	------	------

*Add 30p Post*

**WE WISH ALL OUR CUSTOMERS A MERRY CHRISTMAS AND A HAPPY NEW YEAR**

### LINEAR

THIS IS ONLY A SELECTION!

LF356	80p	NE531	98p
LM301AN	26p	NE555	23p
LM308	60p	NE566	60p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	TBA800	70p
LM379S	410p	TBA810S	100p
LM380	75p	TD1022	620p
LM390	50p	TL081	45p
LM3909	65p	TL084	125p
LM3911	100p	ZN414	80p
MC1458	32p	ZN425E	390p
MM57160	590p	ZN1034E	200p

### TRANSISTORS

AC127	17p	BCY72	14p	ZTX500	16p
AC128	16p	BD131	35p	ZN697	12p
AC176	18p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BD140	35p	2N3055	50p
BC107	8p	BFY50	15p	2N3442	135p
BC108	8p	BFY51	15p	2N3702	8p
BC108C	10p	BFY52	15p	2N3703	8p
BC109	8p	MJ2955	98p	2N3704	8p
BC109C	10p	MPSA06	20p	2N3705	9p
BC147	7p	MPSA06	20p	2N3706	9p
BC148	7p	TIP29C	60p	2N3707	9p
BC177	14p	TIP30C	70p	2N3708	8p
BC178	14p	TIP31C	65p	2N3819	15p
BC179	14p	TIP32C	80p	2N3904	8p
BC182	10p	TIP2955	65p	2N3905	8p
BC182L	10p	TIP3055	55p	2N3906	8p
BC184	10p	ZTX107	14p	2N4058	12p
BC184L	10p	ZTX108	14p	2N4547	32p
BC212	10p	ZTX300	16p	2N4549	32p
BC212L	10p			2N5777	50p
BC214	10p				
BC214L	10p				
BC477	19p	1N914	3p	1N4006	6p
BC478	19p	1N4001	4p	1N4001	13p
BC548	10p	1N4002	4p	BZY88 ser.	8p
BCY70	14p	ITT Full spec. product.			
BCY71	14p	1N4148	- £1.40/100		

### DIODES

1N914	3p	1N4006	6p
1N4001	4p	1N4001	13p
1N4002	4p	BZY88 ser.	8p
ITT Full spec. product.			
1N4148	- £1.40/100		

### CAPACITORS

#### TANTALUM BEAD

each

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1.8, 2.2uF @ 35V	8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V @ 47 @ 6V, 100 @ 3V	16p

#### MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1	3p
	4p

#### POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

#### CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF

63V	0.47	1.0	2.2	4.7	10	5p
			22	33	47	7p
			100			13p
			220			20p
25V	10	22	33	47		5p
			100			8p
			220			10p
			470			15p
			1000			23p

### CONNECTORS

#### JACK PLUGS AND SOCKETS

2.5mm	screened	unscreened	socket
3.5mm	9p	13p	7p
Standard	9p	14p	8p
Stereo	16p	30p	15p
	23p	36p	18p

#### DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

#### 1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

#### 4mm PLUGS AND SOCKETS


Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

#### PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p
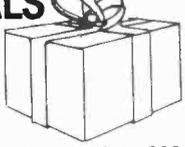
### CHRISTMAS SPECIALS

A range of special offer items valid during December. All orders placed for these items must be received during December.



Murata Ultrasonic Transducers, per pair	350p	280p
PCB etch kit. Contents: 5 assorted sheets Alfac. Pound of Ferric Chloride. Dalo pen. Fibre glass PCB.	375p	325p
Resistor Development Pack. 10 off, each 1/4W value from 4.7Ω to 1M	570p	470p
Polyester Development Pack. 5 off, each value from 0.01uF to 2u2.	620p	480p
Texas sockets. Must be in multiples of 100.		
8 pin, per 100		750p
14 pin, per 100		900p
16 pin, per 100		1000p
Pack of 10 x NE555	230p	200p
Pack of 10 x PP3 clips	60p	45p
Pack of 10 crocodile leads (20 clips)	115p	90p
Pack of 6 x C106D thyristors	270p	220p
Pack of 70 x 1N4148	140p	100p
Expo Reliant drill	665p	550p
Expo Titan drill	1030p	890p
LEDs, Pack of 10 x 0.2 Red		
10 x 0.2 Green		
10 x 0.2 Yellow	350p	290p
AY51013P UART	360p	325p
2114 Low Power 300ns	535p	450p
2708 EPROM	750p	590p
SS-2 Breadboards	1085p	990p

### PANEL METERS



High quality 2" wide view meters. Zero adjustment. Back illumination wiring. Available in 50 uA, 100 uA, 500 uA, 1 mA, 100 mA, 500 mA, 1A. £4.75 ea. VU meter similar style. £1.40 ea.

### SLIDE POTENTIOMETERS



Good quality 60mm travel slider with 80mm fixing centres. Available from 5k - 500k in log and linear. 55p each. Suitable black knobs 6p ea. Coloured knobs 10p ea.

We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



BARCLAYCARD & ACCESS WELCOME

**ORDERS DESPATCHED BY RETURN POST**

**76 College Road, Bromley, Kent BR1 1DE.**

Mail orders to: STEVENSON (Dept PE)



# Handy size Reels & Dispensers

**OF THE WORLD'S FINEST CORED SOLDER TO DO  
A PROFESSIONAL JOB AT HOME**

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

**SAVBIT**  
handy solder dispenser

Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.  
**Size 5 78p**

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits.  
**PC115 92p**  
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.  
**Size 19A 83p**



handy size reels of **SAVBIT, 40/60, 60/40 & ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. mm.	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£3.22
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£3.22
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£3.22
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£3.22

**WIRE STRIPPER & CUTTER**

Easily adjustable for most sizes of flex and cable. Fitted with extra strong spring for automatic opening. Easy grip handles and handle locking device.  
Ref 9  
**£2.48 inc. VAT.**

**MULTICORE WICK**  
for solder removal and desoldering.

Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watts soldering iron. Quick and easy to use. Non-corrosive.

**Size AB10 £1.29**

Sole UK Sales Concessionaires:  
**Bib Hi-Fi Accessories Limited,**  
Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

Prices shown are recommended retail inc. VAT. From Electrical and Hardware Shops. In difficulty send direct, plus 20p P&P. Prices and specifications subject to change without notice.

## MICRODIGITAL BOOKS BEST SELECTION-BEST PRICES-BEST SERVICE

25 Brunswick Street, Liverpool 2 Tel 051-236 0707 (Mail Order) 051-227 2535 (All Other Depts)

Accounts Payable & Accounts Receivable, Poole/Boichers £9.95	Byz Book of Computer Music, Morgan £7.00	Computers for the Physicians Office £15.50	Fundamentals of Digital Computers £7.25	Introductory Experiments In Digital Electronics Vol. 1 £8.75	Microprocessor Basics £7.60
Advanced Basic, Coan £4.00	Beginners Glossary and Guide £5.75	Computerisation for Small Business £9.95	Fortran Programming £6.75	Introductory Experiments In Digital Electronics Vol. 2 £7.75	Microprogrammed API Implementation £14.75
Algorithms & Data Structure Equations, With £15.00	Best of Byte Vol. 1 £8.45	Computer Quiz Book £5.45	Fortran Fundamentals £3.45	Introduction To TRS-80 Graphics Instructor's Manual For Fortran Programming £6.95	Mos Memory Data Book £2.80
Anatomy of a Compiler, Lee £15.00	Basic - a Unit for Secondary Schools £4.45	Computer Programs That Work In Basic £2.95	Fun With Computers & Basic £5.35	Illustrating Basic £2.95	Microprocessor Encyclopaedia Vol. 2 £7.45
Art of Computer Programming Vol. 1, Knuth £16.45 H/B	Basic Printer, Waite & Parsce £6.95	Computer Programs That Work In Basic £2.55	50 Circuits Using 7400 Series IC's £7.50	IC Oupamp Cookbook £8.25	9900 Family Systems Design & Data Book, Texas Instr £7.95
Art of Computer Programming Vol. 2, Knuth £16.45	Charging for Computer Services, Bernard £8.00	Computer Music £7.00	Fortran Fundamentals A Short Course £2.95	Introduction To Microprocessors & Computing £2.40	Book, Texas Instr £7.95
Art of Computer Programming Vol. 3, Knuth £16.45	Cheap Video Cookbook, Lancaster £4.30	Computer Data Directory £3.98	Game Playing With Basic, Spencer £5.50	Num 1 - Users Manual £5.00	1976 US Comp Chess £6.95
Assembly Level Programming For Small Computers, Weller £12.76	Chemistry with a Computer, Cauchon £7.95	Computer Rage (a board game) £5.60	Getting Involved With Your Own Computer, Solomon Int £4.75	First Book Of Kim £7.00	NCR Basic Electronics £7.15
Analysis and Design of Digital Circuits and Computer Systems £16.40	Chess and Computers, Levy £7.95	Content Addressable Parallel Processors £11.00	Games, Tricks & Puzzles For A Hand Calculator £2.49	Linear Control Circuits Data Book, Texas Instruments £2.40	NCR Data Communications £7.15
Appl. Implementation £14.75	Chess Skills in Man and Machine, Frey Ed £11.50	Designing With TTL Integrated Circuits, Texas Instruments £24.80	How To Build A Computer Controlled Robot, Loof Bourque £5.95	Link 68 - An M6800 Linking Loader, Grappel/Hemenway £5.50	NCR Data Processing £6.35
Accent on Basic £4.95	Clos Cookbook, Lancaster £7.50	Design Of Well Structured Programs, Alagic £10.00	How To Profit From Your Personal Comp., Lewis £5.50	Little Book Of Basic Style, Nevison £4.75	Nascom 1 - Hardware Notes £1.50
About Computers £6.95	Collection of Programming Problems and Techniques, Maurer-Williams £12.00	Dictionary of Microcomputing, Boyce £10.00	How To Program Microcomputers, Barden £7.50	Math Elements For Computer Graphics, And Projects, E. M. Noll £7.16	Nascom 1 - Seminar Notes £1.50
Active Filters £6.45	Computer Crime, Bequa I £12.00	Dr. Dobbs Journal Vol. 1, Edit. Warren £10.00	How You Can Learn To Live With Computers, Kienburg £7.00	Math Elements For Computer Graphics, Adams £7.16	Optoelectronics Data Book, Texas Instr £2.80
Analog/Digital Experiments £7.15	Computer Data Directory, Staff £3.98	Digital IC Equivalents & Pin Connections, BP-10 £1.25	How To Buy & Use Minis & Micros, W. Barden £7.50	Microcomputer - Based Design, Peatman £8.00	Osborne Updated Subscriptions Vol. 2 (6 issues) £18.95
A Guided Tour of Computer Programming In Basic £4.16	Computer Lib/Dream machines, Nelson £5.95	Digital IC Equivalents & Pin Connections, BP-11 £1.25	How To Build A Working Digital Computer £4.60	Microcomputer Handbook, Sippl £15.96	Osborne Updated Subscriptions Vol. 3 (6 issues) £18.95
A Quick Look at Basic £4.45	Computer Models of Thought and Language, Edit Shank £17.00	Designing M/Computer Systems, Udo W. Posch £5.40	How To Package Your Software £27.50	Microelectronics £3.25	Osborne Updated Subscriptions Vol. 4 (6 issues) £18.95
Apple II Operators Manual £5.50	Computer Power and Human Reason, Weizenbaum £4.76	Editor/Assembler Systems for 8080/8085 Based Systems, Weller £11.96	Home Computer Revolution, T.H. Nelson £2.75	Micro Problem Solving Using Pascal, Bowles £7.50	Osborne Updated Subscriptions Vol. 5 (6 issues) £18.95
Apple II Integer Basic Manual £3.55	Computer Resource Book Algebra, Dwee & Creechfield £4.00	8080 Programmer Pocket Guide, Sedha £1.95	Home Computers: A Beginners Glossary And Guide, M. Miller £4.95	Microprocessor Interfacing techniques, Zaks £7.95	Osborne Updated Subscriptions Vol. 6 (6 issues) £18.95
Apple II AppleSoft Extended Basic Manual, J. Raskin £5.75	Computer Science a First Course, Forsythe £15.00	8080 A Bugbook, Rony Et Al £7.65	Hobby Computers Are Here £3.95	Microprocessor Lexicon, Sybes £2.00	Osborne Updated Subscriptions Vol. 7 (6 issues) £18.95
Advanced Business, Billing, Inventory, Investments, Payroll £26.95	Computer Science Programming in Fortran IV, Forsythe £7.80	8080 Programming for Logic Design, Osbourne £5.95	Incredible Secret Money Machine, Lancaster £4.75	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 8 (6 issues) £18.95
An Introduction to Your New Pet Bar Code Loader, Budnick £1.60	Computer Science Projects and Study problems, Forsythe £8.75	8080/8085 Assembler Language Programming, Leventhal £6.95	Interface Circuits Data Book, Texas Instr £2.80	Microprocessor From Chips To Systems, Zaks £7.50	Osborne Updated Subscriptions Vol. 9 (6 issues) £18.95
Bases, Warme £5.60	Concurrent Pascal Compiler, Hartmann Ed. £6.40	8080/8085 Software Design £7.65	Introduction To Artificial Intelligence, Jackson £14.80	Mind Appliance, Lewis £4.75	Osborne Updated Subscriptions Vol. 10 (6 issues) £18.95
Basic A Hands On Method, Pockham £6.50	Conference Proceedings of the 1st West Coast Computer Fair, Warren Ed £9.56	8080 Machine Language Programming For Beginners, R. Santore £5.10	Introduction To Basic Interfacing With The 8255 PPI Chip, Goldsborough & Rony £8.00	Modern Operational Circuit Design, Smith £18.60	Osborne Updated Subscriptions Vol. 11 (6 issues) £18.95
Basic and the Personal Computer, Dwyer/Critchfield £10.00	Conference Proceedings of the 2nd West Coast Computer Fair, Warren Ed £9.56	8080/8085 Based Computers, W.J. Weller £11.96	Microcomputers At A Glance £6.45	Modern Operational Circuit Design, Peter £23.50	Osborne Updated Subscriptions Vol. 12 (6 issues) £18.95
Basic Basic, Coan £4.80	Conference Proceedings of the 3rd West Coast Computer Fair, Warren Ed £9.56	8080 Standard Monitor £9.95	Micro/Computer Interfacing With The 8255 PPI Chip, Goldsborough & Rony £8.00	Microprocessor Data Manual £5.50	Osborne Updated Subscriptions Vol. 13 (6 issues) £18.95
Basic Computer Games Micro, AHL £5.50	Consumer Guide-Personal Computers & Micros, Freiberger/Chew £5.00	8080 Standard Editor £9.95	Microcomputer Primer, Waite £6.35	Microprocessors £3.25	Osborne Updated Subscriptions Vol. 14 (6 issues) £18.95
Basic From The Ground Up, Simon £7.00	Content Addressable Parallel Processors, Foster £11.20	8080 Standard Assembler £9.95	Microelectronics £3.25	Micro Problem Solving Using Pascal, Bowles £7.50	Osborne Updated Subscriptions Vol. 15 (6 issues) £18.95
Basic Microprocessors and the 6800, Bishop £7.20	Computer Dictionary (Sams) £6.95	57 Practical Programs, Tracton £6.40	Microprocessor Handbook, Sippl £15.96	Microprocessor Interfacing techniques, Zaks £7.95	Osborne Updated Subscriptions Vol. 16 (6 issues) £18.95
Basic With Business Applications, Lott £8.40	Computer Dictionary & Handbook £11.95	Fortran Colouring Book, Kaufman £7.00	Microprocessor Lexicon, Sybes £2.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 17 (6 issues) £18.95
Basic With Style/Programming Proverbs, Nagin & Ledgrad £3.60	Computer & Prog. Guide for Engineers, D. Spencer £9.45	Fundamentals of Data Structures, Horowitz & Sanni £5.56	Microprocessor System Design, Kingman £14.00	Microprocessor From Chips To Systems, Zaks £7.50	Osborne Updated Subscriptions Vol. 18 (6 issues) £18.95
Basic Workbook, Schoman £3.70	Computer Lib £2.95	Fundamentals of Computer Algorithms, Horowitz & Sanni £15.00	Microprocessor System Design, Kingman £14.00	Mind Appliance, Lewis £4.75	Osborne Updated Subscriptions Vol. 19 (6 issues) £18.95
Best of Creative Computing Vol. 1, AHL Ed £6.95	Consumer Guide-Personal Computers & Micros, Freiberger/Chew £5.00	Fundamentals and Applications of Digital Logic, Libes £6.00	Microprocessor System Design, Kingman £14.00	Modern Operational Circuit Design, Peter £23.50	Osborne Updated Subscriptions Vol. 20 (6 issues) £18.95
Best of Creative Computing Vol. II, AHL Ed £6.95	Content Addressable Parallel Processors, Foster £11.20	From The Counter To The Bottom Line, Warren & Miller £8.75	Microprocessor System Design, Kingman £14.00	Microcomputers At A Glance £6.45	Osborne Updated Subscriptions Vol. 21 (6 issues) £18.95
	Computer Dictionary & Handbook £11.95		Microprocessor System Design, Kingman £14.00	Micro/Computer Interfacing With The 8255 PPI Chip, Goldsborough & Rony £8.00	Osborne Updated Subscriptions Vol. 22 (6 issues) £18.95
	Computer & Prog. Guide for Engineers, D. Spencer £9.45		Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 23 (6 issues) £18.95
	Computer Lib £2.95		Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 24 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 25 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 26 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 27 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 28 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 29 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 30 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 31 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 32 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 33 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 34 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 35 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 36 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 37 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 38 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 39 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 40 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 41 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 42 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 43 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 44 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 45 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 46 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 47 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 48 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 49 (6 issues) £18.95
			Microprocessor System Design, Kingman £14.00	Microprocessor System Design, Kingman £14.00	Osborne Updated Subscriptions Vol. 50 (6 issues) £18.95

**WELCOME**  
Prices include Postage and Packing anywhere in the UK.

# Calculator Chips as Logic Devices

P.A. Birnie

POCKET calculators have now become a familiar part of life to most people and their price has dropped to a very low level—£4 for a standard 4 function machine being about average. This acceptance of calculators has not, surprisingly, extended to the most important part of the machine—the calculator chip itself which has been totally ignored by constructors as a very versatile and cheap device capable of performing a wide range of functions. A typical example is the General Instruments C680 series calculator chips, typified by the C-683, an 8 digit 4 function plus percent device which costs only £3.00 (one off) and with the addition of a few components will perform 8 digit up/down count with display decode and drive and other functions normally found in more expensive devices. The C-683 also operates on a nominal 9 volt supply making it CMOS compatible.

## CALCULATOR OPERATION

For those unfamiliar with calculator operation, it is essential that the method of keying in information and display driving is thoroughly understood. Due to the requirement to limit the number of pins on the packages of calculator chips, it is essential that multiplex techniques are used and the "standard" display

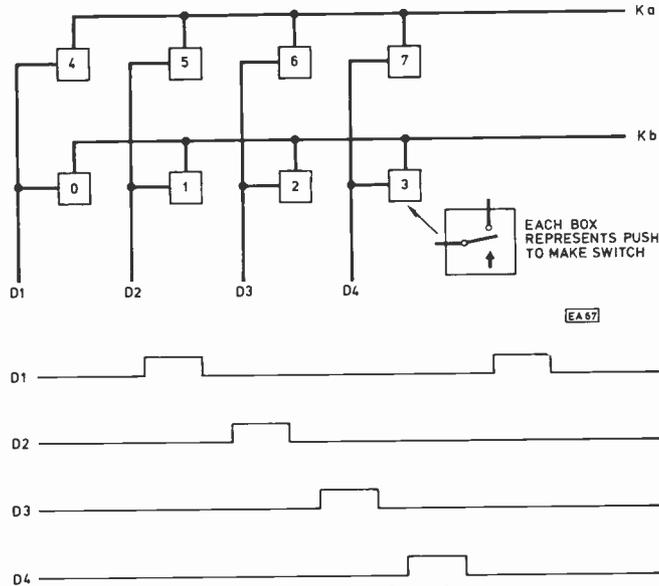


Fig. 1. Multiplexed keyboard system

multiplexing method is without exception adopted. The chip outputs seven segment drives and 9 digit drives plus a decimal point "segment" drive with one digit of the display having its digit driver enabled for a short period (a few hundred microseconds) and the segment drives then turn on the appropriate segments for that particular digit. Then the next digit of the display has its digit driver enabled for a similar period, segment drives as required for this digit being applied. Thus each digit driver is enabled in turn and it should be clear that if, say, all segments "a" in each display are commoned to a segment drive

output (and b, c.....g), then by controlling the seven segment drive outputs and the nine digit drive outputs, the nine digit display can be operated using only 16 connections. The alternative approach where each segment is driven continuously requires 63 connections for the segments plus one for the common return.

## KEYBOARD

Turning now to the keyboard, for a basic calculator, keys 0-9, + - x ÷ % · = C/CE are needed, 18 in all and these could be individually wired to the calculator chip. Instead of this, the keyboard itself is operated in a multiplexed mode as illustrated in Fig. 1. For simplicity, an eight digit keyboard is

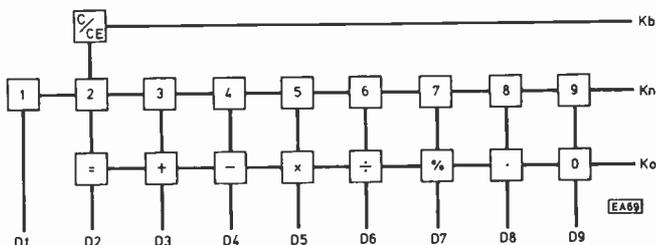


Fig. 2. Key matrix for the C-683

shown, although in practice many keys are interconnected in this type of matrix to reduce interconnections to a minimum. If we have four waveforms D1, D2, D3, D4 as shown and these are applied to the key matrix, then when say button 2 is depressed, the D3 waveform will appear at Kb. By simple gating, it would be possible to tell that button 2 was the one that was depressed as only this button will produce the 'high' pulse at this time i.e. in phase with D2. If the key matrix for the C-683 is studied (Fig. 2), then it can be seen that the number of wires from keyboard to chip is reduced from 19 to 12. Now comes the clever trick—the display drive circuitry produces digit drive waveforms, nine in all to enable, one at a time, the display digits. If these are applied to the D1-D9 keyboard connections then the keyboard only needs a further three connections to the chip.

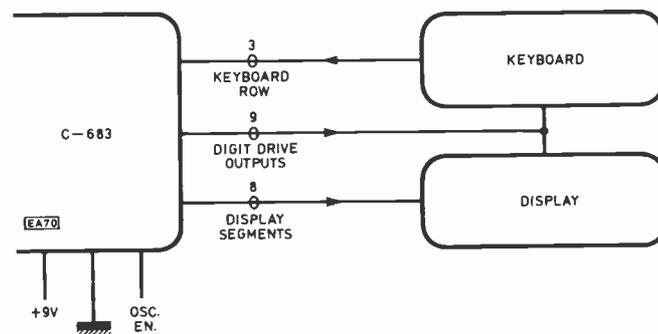


Fig. 3. Keyboard and display drive connections

Internal circuitry as before can detect which key has been depressed by detecting the phase of the signal received on one of the three keyboard "row" outputs. Thus in Fig. 3, a block diagram shows the keyboard and display drive connections required and by referring to Fig. 4, the pin-out diagram for the C-683, the purpose of most of the pins on the i.c. can be seen. Other pins are an oscillator enable pin, pin 14 which is tied to ground by a 470k resistor for normal operation and supply and ground connections. In the G1 calculator chip range, all the chips in the family have common keyboard and display pinout for ease of printed circuit board stocking by the calculator manufacturer. More complex calculators such as the C-596 15 function scientific use the spare pins (9, 10, 11) to extend the keyboard to more rows, giving a greatly increased number of functions.

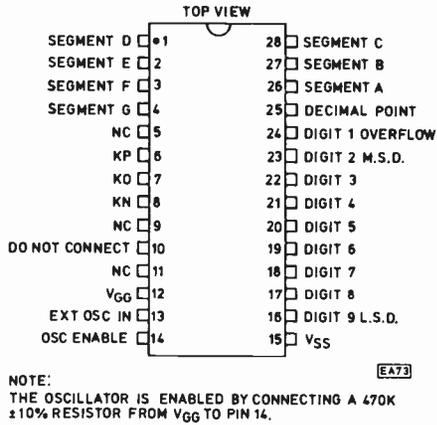


Fig. 4. Pin-out diagram for the C-683

### CIRCUIT FUNCTIONS

Now that the theory of operation of the calculator chip has been established, it is necessary to investigate how, in practice, it can be made to perform a circuit function. Let us assume that we want to perform simple addition of a pulse stream, with the ability to count up or down. Some intelligent probing round the chip reveals that to perform multiple addition, the operations + 1 = need to be performed each time a pulse is to be added to the total in the calculator chip registers. Normally this would be performed by key depressions but when the chip is performing

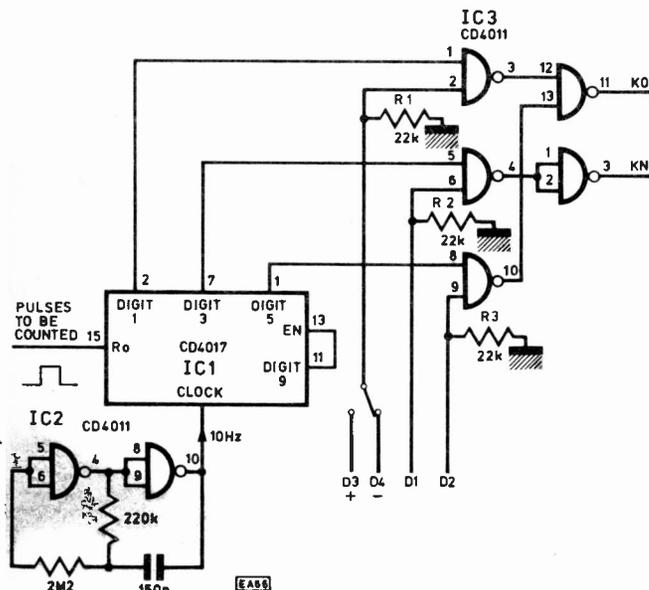


Fig. 5. Circuit to simulate key depression

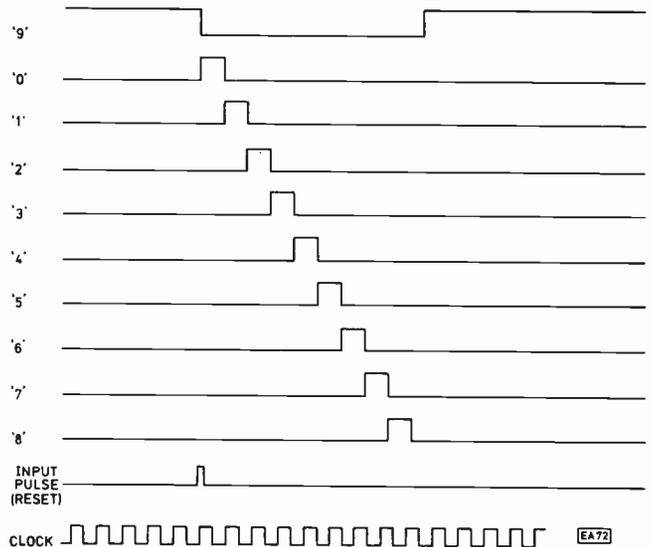


Fig. 6. Output waveforms of Fig. 5

an "in-circuit" function, it is obviously necessary to use logic to simulate switch closures. The circuit shown in Fig. 5 can be used to generate the necessary waveforms in the following manner. The fully decoded decade counter CD4017 is clocked by a free-running oscillator with a period of about 50 ms and by connecting the 9th output of the counter to the clock inhibit input (pin 13), the counter will normally be in the halted state with output 9 high and all other outputs low. If a short positive going pulse is now applied to the reset pin, the counter will be reset and immediately start to count up to 9 again. Fig. 6 shows the waveforms associated with this device. Outputs 1, 3 and 5 are now used to simulate keyboard operations +, 1 and = respectively by means of IC2 and IC3. Thus for a + input, the calculator chip expects to see its D3 signal connected to Ko and this is performed by NANDing D3 with the digit 1 output (pin 2) of IC1, and using part of IC3 to OR this signal into the Ko input of the calculator chip. Similarly D1 is NANDed with digit 3 and fed to the Kn input after inversion by part of IC3, and D2 is NANDed with digit 5 and OR'd to the Ko input. Alternative digit outputs from the decade counter must be used to simulate the gap between pressing keys and the frequency of the drive oscillator must be such as to allow the calculator chip time to perform its keyboard input validation function and arithmetic operations before the next signal is input. The use of an oscillator period of 50 ms or greater appears satisfactory for addition and subtraction but longer periods of about 200 ms are necessary for multiplication and division. In the basic circuit shown in Fig. 5, S1 allows either D3 or D4 to be the first signal connected to Ko, D3 causing an addition to take place and D4 a subtraction. The resistors R1 to R3 are necessary to act as pull-down elements on the calculator chip digit drive leads since these are open drain outputs which can source current, but do not actually switch a logical level.

### UP/DOWN COUNTER

Using the circuit shown in Fig. 5, an up/down counter of up to 8 digits can be constructed and with the addition of a display and a few associated components, (Fig. 7) a four digit counter display module can be made at very low cost.

The addition of other components can allow the multiplication and division functions of the C-683 to be used, but this does introduce some complications as it is necessary to input the numbers, not as say binary but as a 1 out of 10. This can be done by using some decoder chips and an outline circuit is shown in Fig. 8. The CD4067 is a 16:1 multiplexer which is used here to select digit drive outputs from the calculator chip

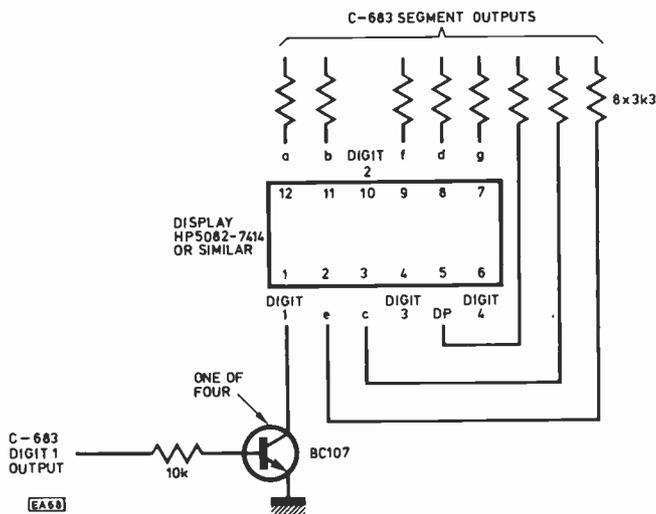


Fig. 7. Circuit diagram of a four digit counter display

according to the binary address applied. Thus for a binary address 0101, digit drive D5 is routed to the Kn input on the C-683, causing a "5" to be entered into the calculator chip—since 0101 represents 5 in 8421—b.c.d. code, the circuit clearly enters our "A" number. The next operation involves the digit 3 output of the CD4017, this being gated with D5 and then routed to the Ko input of the calculator chip causing the function multiply to be performed. If D6 was routed, divide would be performed. When the digit 5 output of the CD4017 occurs, it causes the quad 2:1 data selector—CD4019, to select the "other" input number and this is applied in b.c.d. form to the 16:1 multiplexer as before to cause the second number to be input to the

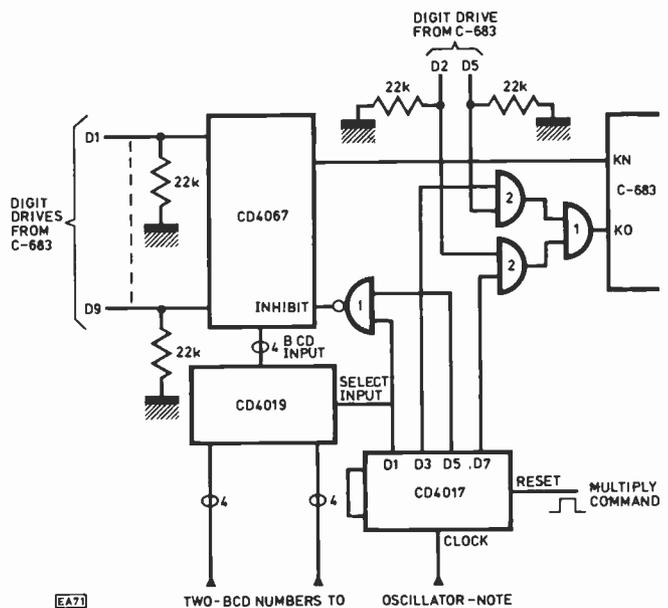


Fig. 8. Outline circuit for multiplication and division

calculator. Finally digit 7 output from the CD4017 is used to gate D2 from the C-683 into Ko on the same chip, causing the equals function to be performed and the answer to be displayed.

The description so far given illustrates only simple applications and with a little thought, circuitry can be constructed to say accumulate pulses over a period of time, divide the total by a fixed factor and then cancel the display to allow the process to be performed again.

# Countdown

**Organisers:** Please send details of exhibitions, club open days and other events to Mike Abbott at least six weeks in advance. Inclusion will be subject to space etc.

- BEX (Business Equipment Exhibition) Feb. 6-7. Queens Hall, Leeds. K
- BEX Feb. 20-21. Pavilion, Bournemouth. K
- IEA/Electrex Feb. 25-29. National Exhibition Centre, Birmingham. I
- Viewdata March 26-28. Wembley Conference Centre, London. O
- Computer-Aided Design (conference & exhibition) March 31-April 2. Metropole, Brighton. Details: CAD 80/0483-31261
- Seminex April 14-18. Dept. Physics, Imperial College, London. H1
- Communications 80 April 14-18. National Exhibition Centre. I
- Electronic Test & Measuring Information April 22-24. Wythenshaw Forum, Manchester. T
- International Conference On The Electronic Office April 22-25. London Penta Hotel. Organised principally by the Institute of Electronics & Radio Engineers. 99 Gower St., London WC1E 6AZ
- North Midlands Mobile Rally April 27. Drayton Manor Park, Tamworth, Staffs. Details: Norman Gutteridge, 68 Max Rd., Quinton, Birmingham.
- All-Electronics Show April 29-May 1. Grosvenor House, London. E
- The Mersey Micro Show April 30-May 2. Adelphi Hotel, Liverpool. O
- Compec Europe May 6-8. Centre International Rogier, Brussels. L
- Great British Electronics Bazaar June 20-22. Alexandra Palace. Many improved features this year, to enhance the unique atmosphere of the "Ally Pally". There will be free "bring-and-buy" sales for all visitors. E
- Intel Fair June 24. Wembley Conference Centre, London. U
- Tempcon July 1-3. Wembley Conference Centre. Exhibition devoted to temperature control & measurement. T
- Transducer July 1-3. Wembley Conference Centre. T
- The 1980 Microcomputer Show July 10-12. Royal Lancaster Hotel, London. O

- E Evan Steadman, 34-36 High st., Saffron Walden, Essex. £ 0799 22612
- H1 Seminec Ltd., 79 High st., Tunbridge Wells, Kent. TN1 1XZ. £ 0892 39664/5
- I Industrial Trade Fairs, Radcliffe Ho., Blenheim Court, Solihull, W. Midlands B91 2BG. £ 021-705 6707
- K Douglas Temple Studios, 1046 Old Christchurch Rd., Bournemouth, Dorset BH1 1LR. £ 020 20533
- L Iliffe Promotions, Dorset Ho., Stamford St., London SE1 9LU. £ 01-261 8437/8
- O Online Conferences, Cleveland Rd., Uxbridge, Middx. UB8 2DD. £ 0895 39262
- T Trident International Exhibitions, Abbey Mead Ho., 23a Plymouth Rd., Tavistock, Devon PL19 8AU. £ 0822 4671
- U Brian Crank Associates, 58 London Rd., Southborough, Kent. £ 0892-31812 38414

# News Briefs

## ON THE BUTTON


BA has just awarded a £16M contract for the high power u.h.f. transmitters needed to launch ITV's fourth channel in November 1982.

Divided, roughly equally, between Marconi and Pye, the contract covers the supply and installation of equipment necessary to transmit to 80 per cent of the entire population at the inauguration date of the new channel.

The fourth channel will be the first programme service to open in the UK where virtually all viewers already have receivers and aerials for a new entertainment dimension at no extra cost. A little initial aggravation in band searching will be inevitable but at last that unused button will have meaning.

# Simply ahead . . .

## ILP'S NEW GENERATION OF HIGH

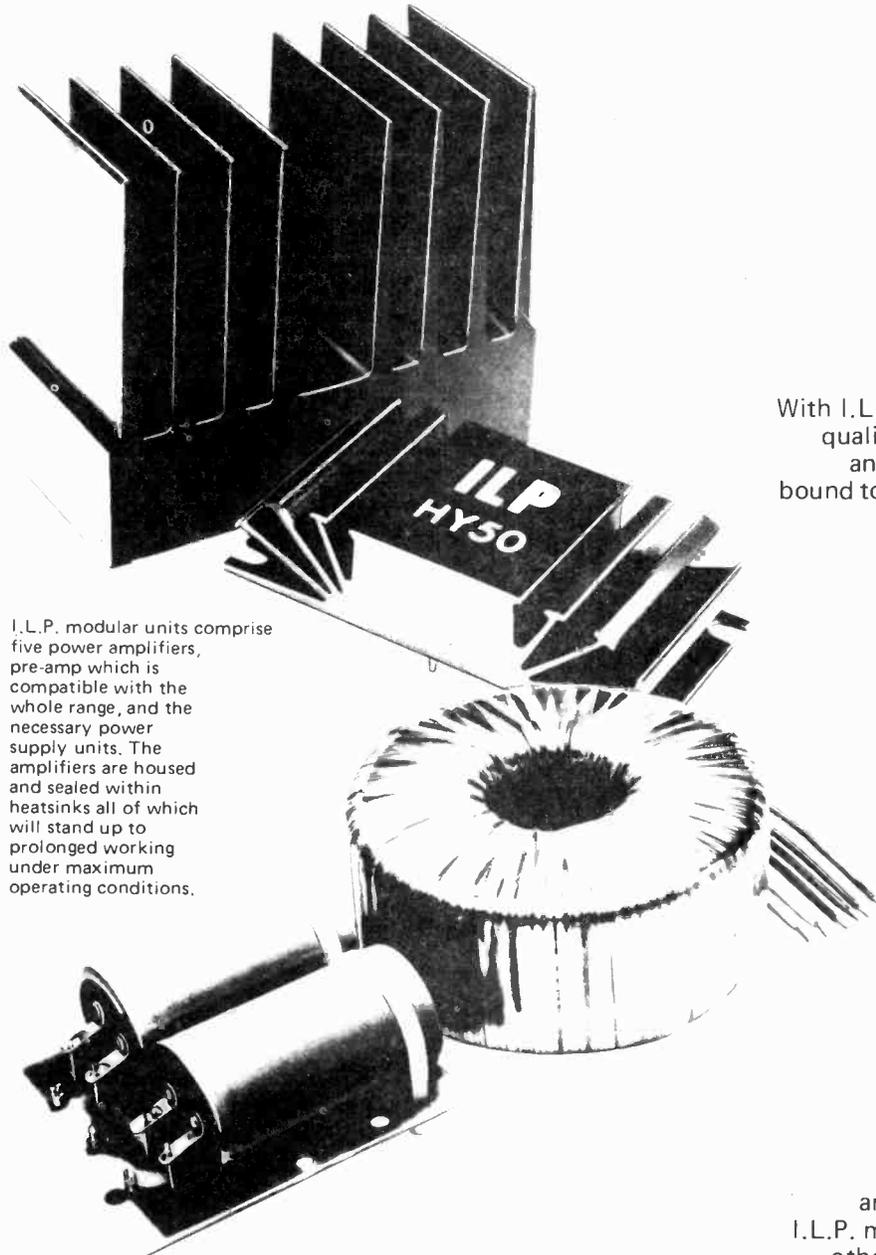

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.

With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance – and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain – the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.



**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS  
IN ELECTRONIC MODULAR DESIGN**

*ALSO AVAILABLE FROM SELECTED STOCKISTS*

# and staying there

## PERFORMANCE MODULAR UNITS

### HY5 PRE-AMPLIFIER

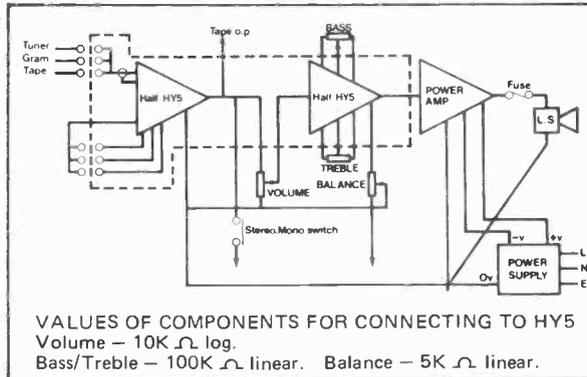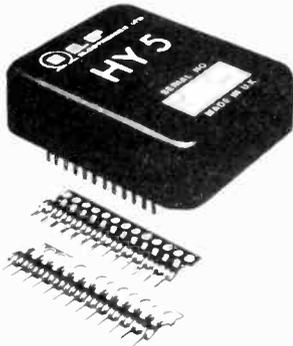


VALUES OF COMPONENTS FOR CONNECTING TO HY5  
 Volume — 10K  $\Omega$  log.  
 Bass/Treble — 100K  $\Omega$  linear. Balance — 5K  $\Omega$  linear.

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm, and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


### THE POWER AMPLIFIERS

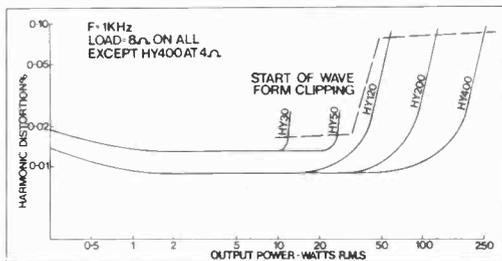

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 $\Omega$	0.02%	80dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 $\Omega$	0.02%	90dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 $\Omega$	0.01%	100dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 $\Omega$	0.01%	100dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 $\Omega$	0.01%	100dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance — all models 4 - 16  $\Omega$   
 Input sensitivity — all models 500 mV  
 Input impedance — all models 100K  $\Omega$   
 Frequency response — all models 10Hz - 45Hz - 3dB

### THE POWER SUPPLY UNITS

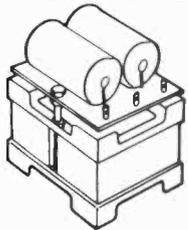

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	$\pm 15V$ at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU 180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

**NO QUIBBLE  
 5 YEAR GUARANTEE  
 7-DAY DESPATCH ON  
 ALL ORDERS  
 INTEGRAL  
 HEATSINKS  
 BRITISH DESIGN AND  
 MANUFACTURE  
 FREEPOST SERVICE  
 —see below**

#### ★ ALL U.K. ORDERS DESPATCHED POST PAID HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



**L.P. ELECTRONICS LTD.**  
 FREEPOST 2 Graham Bell House, Roper Close,  
 Canterbury, Kent CT2 7EP.  
 Telephone (0227) 54778      Telex 965780

Please supply .....

..... Total purchase price £ .....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Account/Barclaycard Account No. ....

NAME .....

ADDRESS .....

Signature .....

# TRANSFORMERS

### 30 VOLT RANGE

Pri 220/240 sec 0.12-15.20-24-30V  
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.93	1.10
3	2.0	6.35	1.10
20	3.0	6.82	1.31
21	4.0	8.79	1.31
51	5.0	10.88	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.89	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	20.0	32.40	O.A.

### 50 VOLT RANGE

Pri 220/240V Sec 0.20-25-33-40-50V  
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V and 25V-0-25V

Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	31.79	O.A.

### MAINS ISOLATORS (SCREENED)

PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.84	0.91
149	60	7.37	1.10
150	100	9.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

\*Pri 0.220-240V Sec 115 or 240V  
State sec. volts required

### CASED AUTO TRANSFORMERS

240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	8.55	1.03	56W
75	8.50	1.31	65W
150	11.00	1.31	4W
200	12.02	1.67	55W
250	12.55	1.67	69W
300	20.13	1.89	67W
1000	30.67	2.65	84W
1500	33.02	O.A.	93W
2000	34.97	O.A.	95W

## CONTINUOUS RATINGS + VAT 15%

### 60 VOLT RANGE

Pri 220/240V Sec 0.24-30-40-48-60V  
Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V

Ref	Amps	Price	P & P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	2.12
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.
189	12.0	37.47	O.A.

## TRANSFORMERS END OF LINE OFFERS

Ref	VA	Price	P & P
30-Isolator	240V:240V 200VA	£4.54	£1.04
62-Isolator	240V:240V 250VA	£5.62	£1.04
M489	0-240V: Screen 1) 13-0-13 A. 2) 12V 150ma	£2.10	60p
M708	6K to 3KΩ matching transformer 5W	£5.50	£1.04
M679	120V x 2.36V 1 6A	90p	40p
M865	100V Line to 4Ω 10 watts	£3.00	78p
M973	100V Line to 8Ω 40 watts	£2.90	60p
M1015	Choke 8A x 5mH 150A Surge	£1.50	45p
M1020	0-240V 12-0-12V x 50ma	75p	41p
M1126	120-240V 9-0-9V x 1A	£1.79	71p
M1130	0-240 4500V x 10ma	£4.86	£1.08
M1165	0-115 240V: 14V 50ma	75p	30p
	0-240V 9V 3Amp	£2.20	60p

**Metal Oxide Resistors 1/4W 5% TR4 (Electroil)**  
390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2  
1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/  
100K/110K/120K/130K/180K/220K/270K/300K  
£1.50/100 VAT

**Antex Soldering Irons 15W, 25W £4.58**  
Safety Stand £1.75 P & P 52p each

### 12 OR 24V OR 12-0-12V

Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.86	0.90
85	5	2.5	4.46	1.10
70	6	3	6.99	1.10
108	8	4	8.16	1.31
72	10	5	8.93	1.31
116	12	6	9.89	1.52
117	16	8	11.79	1.52
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

### Bridge Rectifiers

Ref	Amps	Price	P&P
100V	25A	£2.10	
200V	4A	.45	
400V	4A	.85	
400V	6A	£1.25	
500V PM7A6 12A		£2.85	

P & P 17p VAT 15%

### 20,000 ohm/V Multimeter

mirror. Scale ranges AC/DC to 1000V DC current to 250mA. Resistance to 3 M Ohms  
5" x 3 1/2" x 1 1/2" £14.36, P & P £1.00, VAT 15%

### Panel Meters

Ref	VA	Price	P & P
0.50VA	6.20	0.50VA	6.70
0.500VA	5.95	0.500VA	6.70
0.1mA	5.95	0.1mA	6.70
0.30V	5.95	0.30V	6.70
43mm - 43mm		82mm - 78mm	
3mm ind. Panel 48mm x 45mm			2.60
50mA A.S.D 54 - 14mm			2.60
Carriage 76p			VAT 15%

### AUTO TRANSFORMERS

Ref	VA	(Watts)	£	P&P
113	15	0-115-210-240	2.73	0.81
34	75	0-115-210-240	4.41	1.10
4	150	0-115-200-220-240	5.70	1.10
67	500	0-115-200-220-240	12.09	1.91
104	1000	0-115-200-220-240	20.64	2.39
93	1500	0-115-200-220-240	25.61	0.41
95	2000	0-115-200-220-240	38.31	0.41
73	3000	0-115-200-220-240	65.13	0.41
805	4000	0-115-200-220-240	84.55	0.41
575	5000	0-115-200-220-240	98.45	0.41

### AVO TEST METERS

Ref	Price	P&P
AVO 8 Mk5	£91.50	
AVO 71	£38.00	
AVO 73	£50.78	
AVO MMS minor	£35.95	
Wee Megger	£76.28	
TT169 in circuit transistor tester	£41.53	
EM272 316KΩ - Volts	£59.80	
DA116 digital	£110.90	
BM7 Megger	£53.76	
Clamp Meter to 300A	£54.60	

All Avos Meggers and accessories available  
P & P £1.32 15% VAT

### U4315 Budget Meter

20KΩ/Q Ranges to 1000V. 2.5A AC/DC  
500K Res. In steel case £15.85 P & P £1.32

**SPECIAL OFFER Multimeter (20KΩ/V with combined audio/F. test oscillator at 1KHz, and 465 KHz AC/DC to 1000 volts. DC current to 500 mA resistance to 1KΩ size 160x97x40mm £8.50, P & P £1.00, VAT 15%**

**Split Bobbin Type - 0-12-15-20-24-30V.**  
Ref 009 - 1 Amp £2.98, P & P £1.10  
Ref 010 - 2 Amp £4.65, P & P £1.10 open frame fixing. Other split bobbin types available.

### ELECTRONIC CONSTRUCTION KIT

Home electronics teacher. Start simply and progress to a TRF radio or electronic organ. No soldering. All parts included in presentation box. Full instructions and clear diagrams.  
Price £8.29 P & P £1.10, VAT 15%

### High Quality Amplifier Modules

Ref	Price
10W (AL30)	£3.75
25W (AL60)	£4.95
35W (AL80)	£7.79
50W (AL120)	£11.95
125W (AL250)	£18.74

F.M. Tuner 4 push buttons £23.60  
Pre Amps & Power Supplies available. P & P 40p. VAT 15%

### P.W. Purbeck oscilloscope transformer

250-0-250V  
6.9V-12.9V £7.51, P & P £1.04

### NEW RANGE TRANSFORMERS

2 windings - 0.36V-48V/36V 0.36V  
48V-0.48V 72V or 96V.

Amps	Ref	Price	P & P
0.5	430	4.88	0.76
1.0	431	8.12	0.99
2.0	432	13.35	1.31
3.0	433	16.17	1.40
4.0	434	20.65	2.11
5.0	435	29.30	2.47
6.0	436	36.69	O.A.
8.0	437	40.03	O.A.

### MAINS ELIMINATOR

Fits into a 13A skt. 3-6-9-12V multipig outlet  
300ma £4.60 P & P 55p, VAT 15%

### SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	2.83	0.63
212	1A	0-6-0-6	3.14	0.90
13	100	9-0-9	2.35	0.44
235	330	330-0-9-9	2.19	0.44
207	500	500-0-8-9-0-8-9	3.05	0.85
208	1A	0-8-9-0-8-9	3.88	0.90
236	200	0-15-0-15	2.19	0.44
214	300	0-20-0-20	3.08	0.90
221	700DCI	20-12-0-12-20	3.75	0.90
206	1A	0-15-20-0-15-20	5.09	1.10
203	500	0-15-27-0-15-27	4.39	1.10
204	1A	0-15-27-0-15-27	6.84	1.10
239	50	12-0-12	2.88	0.43

## Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: AFGATE & LIVERPOOL ST

### DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

**DL1000K**  
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.60

**DL21000K**  
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00  
Optional Opto Input DL-1A 60p

### MINI KITS

These KITS form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB short instructions and all components.

**TEMPERATURE CONTROLLER/THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. PCB (4 cm sq.) potentiometer, plus all other components included with instructions.  
500W £3.20 1KW £3.50

**SOLID STATE RELAY**  
Ideal for switching motors, lights, heaters etc. from logic. Opto isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. £2.60

**BAR/ODT DISPLAY**  
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

**BURST FIRE/PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the TDA1024 Zero Voltage Switch this kit contains all the components required to make a 'burst fire' power controller or a 'proportional temperature' controller enabling the temperature of an enclosure to be maintained to within 0.5°C.  
1.5KW £5.25 3KW £6.55

### DIGITAL VOLTMETER/THERMOMETER KIT

Based on the ICL 7106. This Kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3Ma 9V supply. (PP3 battery) £20.75

### LEDs

Ref	Price
0.1" Red	9p
0.2" Red	9p
Green	12p
Yellow	12p
5x2.5	18p
9mm	20p

**SPECIAL OFFER**  
2.5 off 0.2" Red £1.50  
Green £2.00  
Yellow £2.00

### DISPLAYS

Ref	Price
DL727 0.5" 2-digit display	CA £1.50
DL304 (pin compatible with DL704) 0.3" CC Red	70p
DL847/DL850 (pin compatible with DL747/750) 0.8" CA/CC	£1.80

**LIQUID CRYSTAL DISPLAY** 0.5" 3 1/2 digit 40 pin dill. £3.10  
**SPECIAL**  
IL74 Opto Isolator 45p

### TRIACS

Ref	Price
400V Plastic Case (Texas)	
3A	49p
8A	57p
12A	70p
6A with trigger	82p
8A isolated tab	82p
Diac	18p

### INTEGRATED CIRCUITS

Ref	Price
555 Timer	21p
741 Op. Amp	18p
AY-5-1224 Clock	£2.80
AY-5-1220 Clock/Timer	£4.50
AY-3-1270 Thermometer Controller	£8.60
ICL7106 D.V.M. (L.C.D. Drive)	£7.50
TOA1024 Zero Voltage Switch	£1.20
LM3911 Thermometer	£1.20
LM3914 Dot/bar Driver	£2.60
MM57180 (stac) Timer	£5.95
S566B Touchdimmer	£2.85
S9263 Touchswitch 16 way	£4.85
TN1034E Timer	£1.80

All ICs supplied with data and circuits  
Data Sheets only 5p

### PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L3 2DY

**SEMICONDUCATORS.** C106D 400V 2.5A SCR 20p. 16A800 50p. 741 B PIN 22p. NE555 24p. LM3400 40p. 723 14 PIN REGS 35p. AD1672 MATCHED PAIRS 70p. 2N3055 38p. 1N4005 10 FOR 35p. BD238 28p. 8D438 28p. MPU131 P.U.T.s. 40V, 200mA, 375mA/W 15p each

**MINIATURE MAINS TRANSFORMERS.** ALL 240V AC PRIMARY. 6-0-6 100mA, 9-0-9 75mA, 12-0-12 50mA all 75p each. 7250VA £1.10p. 0-10V-0-10V 280mA £1.30p

**PULSE TRANSFORMERS:** 1:1 IGPO type 30V, 1.5A, 1.5m. P.C. mounting 60p.

**MINIATURE SOLID STATE BUZZERS.** 33X17X15MM, output at 3 feet 70db, only 15mA drain, 4 voltages available, 6-9-12 or 24VDC 80p each.

**LOUD BUZZER.** 6-12 volts 83p. GPO type adjustable buzzer 6-12 volts 27p.

**POCKET MULTIMETER, MODEL NH55** 2,000 ohms per volt, 1,000 volts AC/DC, 100mA DC current, 2 resistance ranges to 1 meg. £8.95p.

**SOLDER SUCKER.** High suction/reflow nozzle. £4.95p.

**MURATA TRANSFORMERS.** 40KHz, REC/SENDER £3.60p.

**MOTORS.** 3V model type 22p. 12V model 5 pole 38p. Replacement 12VDC 8 track motors 55p. Ex equip. 5-7 volt cassette motors 70p. Low rev. mains motor 240VAC motor with gearbox 2 1/2 RPM 75p.

**ALPHENOL COAX CONNECTORS:** Plug 47p, Sockets 42p, Elbows 50p, Reducers 13p.

**TELEVISION OUTLET BOXES.** Wall mounting; single 40p, double 75p, switched double 95p, low loss in line splitter 1 in 2 out 90p.

**SPECIAL OFFER STEREO HEADPHONES.** 8 ohms, adjustable, standard stereo plug only £2.95p.

**INTERCOM UNITS** (can be used as baby alarm) supplied with approx. 60' cable, call out. 2 way £5.25 pair, 3 way £7.25. **WIRELESS INTERCOM.** 2 units both operate on 240VAC & mains connected. AM frequency 180KHz. £28.95p.

**MINIATURE TIE PIN MICROPHONE.** Omni, 1K imp., uses deaf aid battery (supplied) £4.95p. **LOW COST CONDENSER MIKE.** Stick type, Omni, 600 ohms, on/off switch, standard jack plug only £2.95p. **EM607 CONDENSER MICROPHONE.** Highly polished metal stick mike, uni directional, 600 ohms, 30-18KHz., on/off switch only £7.95p. **DYNAMIC STICK MIKE.** CARDIOD, dual imp., 600 ohms or 20K, 70-15KHz., attractive black metal case only £7.75p.

**PUBLIC ADDRESS HORN SPEAKERS.** Suitable for outdoor use. 5" round 8 watts, 8 ohms, adjustable bracket £4.95p. 6" 15 watts 8 ohms adjustable bracket £8.25p.

**SPECIAL OFFER TAPE HEAD DEMAGNETISER,** 240VAC with curved probe only £2.65p.

Cash with order please, official orders welcome from schools etc., please add 30p post and packing. VAT inclusive. SAE for latest illustrated stock list. ALL ORDERS DESPATCHED BY RETURN POST

Amplifiers from HiAmp. All fully short circuit and open circuit protected with thermal limiting. Making these amplifiers indestructible from stress other than incorrect supply voltage.


- 1) £5.19 10 watts into 4 ohm .1% distortion max. 30Hz-80KHz, supply voltage ± 18v.
- 2) £6.79 20 watts into 4 ohm .1% distortion max. 30Hz-80KHz, supply voltage ± 22v.
- 3) £15.79 50 watts into 4

# TRANSDAM

## COMPUTER PRODUCTS
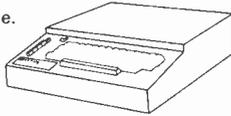
### TRITON SINGLE BOARD PERSONAL COMPUTER

Three new exciting expandable systems designed for ease of construction and flexibility. Kits come complete with case, power supply, full keyboard, PCB. All components available separately. See catalogue. Full hardware & programming manual available. The system is easy to expand and is well supported. Features:- 2, 2.5 or 7k basic in Eprom (See catalogue)



- Single board
- Holds up to 8k memory
- UHF or video output
- Cassette interface
- Three firmware options
- Basic in eprom
- 64 graphic characters
- Plug in expansion boards

From **£286** +VAT

**NOW! - Resident Pascal**

### BI DIRECTIONAL MATRIX PRINTER £595 +VAT

The BD80 is a low cost, 80 column line printer with microprocessor control to provide excellent reliability and performance.

- 5x7 Dot matrix
- 10 char per inch
- 6 lines/inch
- 400 char buffer
- Full asch char set
- 10 lines/sec
- paper advance
- 112 char/sec
- 84 lines per minute
- Self test
- Fully cased




A UNIQUE PRINTER FAST AND RELIABLE

Switch selectable baudrate from 110 to 9600 on a standard V24 and R5232 interface. Send SAE for further details. Ideal printer for Triton or any system requiring high speed reliable hard copy. We can supply consumables.
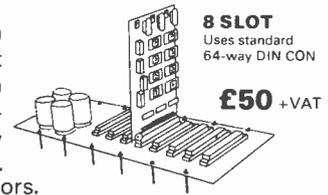
### EXPANSION MOTHERBOARD

**TRITON.** Expand your Triton simply and easily with our new 8-slot motherboard complete with its own P.S.U. takes 8 plug-in Euro cards. Plug-in 8k RAM card and Eprom cards now available. CP/M disc interface available. Kit complete with PSU + 1 set connectors.



**8 SLOT**  
Uses standard 64-way DIN CON

**£50** +VAT

### 8K RAM CARD


Triton 8k static Ram card. Kit uses 2114 Low power 4k. Static Rams. On board regulation, memory jump select. PCB only **£15** Rams **£5.50** each. Kit less Rams **£35** incl. all sockets & components.



Compl. kit **£97** +VAT
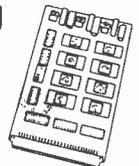
### 8K EPROM CARD

Triton 8k Eprom card Kit. Designed to take up to 8x2708 Eprom (1kx8)



PCB only **£15**  
Kit less Eproms **£31**  
Eproms (blank) **£9**  
Plus VAT

Complete kit **£97** +VAT


### \$100 boards

8k Static RAM board (450ns) **£123.75**  
8k Static RAM board (250ns) **£146.25**  
Z80 cpu board (2MHz) **£131.25**  
Z80 cpu board (4MHz) **£153.75**  
2708/2716 EPROM board **£63.75**  
Prototype board (bare board) **£18.75**  
Video display board (64 x 16, 128U/L Ascii) **£108.75**  
Disk controller board **£131.25**  
K2 disk operating system **£66.25**  
Assemble/z Macro Assm **£37.50**
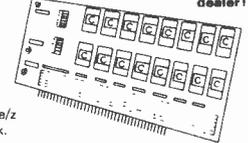
### ITHACA DPS1

Pascal/z

Build your own Pascal Micro Development system. IEEE-S100 bus system using DPS1 mainframe. Supports K2, assemble/z and pascal/z on 8" disk.




your London dealer!

We stock the full range of ITHACA products

### PCB CONNECTORS

Edge connectors, gold contact double sided PCB connectors

Size	Price	156" Price
1"	22/44	6/12
22/44	<b>£3.20</b>	12/14
25/50	<b>£3.60</b>	10/20
28/56	<b>£3.90</b>	15/30
30/60	<b>£4.15</b>	18/36
35/70	<b>£4.60</b>	22/44
36/72	<b>£4.75</b>	28/56
40/80	<b>£5.00</b>	36/72
43/86	<b>£5.50</b>	43/82
50/100	<b>£6.50</b>	<b>£100 BUS</b>

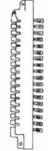

### TRAP!

Triton resident assembly language package

Links via the L6-1 monitor and new scientific basic to make Triton a stand alone development system. Trap is an 8k package in EPROM and resides on our EPROM card. Set of 8x2708 only **£80** including document.

- EDITOR
- ASSEMBLER
- DISASSEMBLER
- SYMBOL TABLE
- CREATE
- DEVELOPMENT SYSTEM
- BREAKPOINT
- SINGLE STEP
- TRACE
- PROGRAMME LOAD
- MONITOR

### COMPONENTS 74LSXX

SN74LS00N	10	SN74LS04N	25	SN74LS113N	44	SN74LS195N	170	SN74LS248N	136
SN74LS01N	10	SN74LS042N	78	SN74LS114N	44	SN74LS196N	175	SN74LS249N	130
SN74LS02N	20	SN74LS047N	85	SN74LS122N	78	SN74LS198N	185	SN74LS251N	145
SN74LS03N	10	SN74LS048N	85	SN74LS123N	89	SN74LS199N	185	SN74LS253N	126
SN74LS04N	20	SN74LS049N	100	SN74LS124N	150	SN74LS200N	250	SN74LS257N	140
SN74LS05N	28	SN74LS054N	21	SN74LS125N	85	SN74LS201N	220	SN74LS258N	85
SN74LS06N	20	SN74LS055N	21	SN74LS126N	85	SN74LS202N	115	SN74LS259N	146
SN74LS09N	22	SN74LS063N	150	SN74LS132N	76	SN74LS203N	105	SN74LS280N	30
SN74LS10N	18	SN74LS073N	35	SN74LS133N	39	SN74LS204N	275	SN74LS281N	350
SN74LS11N	28	SN74LS074N	40	SN74LS138N	75	SN74LS206N	39	SN74LS282N	39
SN74LS12N	25	SN74LS075N	48	SN74LS139N	40	SN74LS207N	175	SN74LS283N	185
SN74LS13N	55	SN74LS076N	35	SN74LS145N	128	SN74LS208N	145	SN74LS284N	79
SN74LS14N	88	SN74LS078N	35	SN74LS146N	176	SN74LS209N	175	SN74LS285N	175
SN74LS15N	25	SN74LS083AN	115	SN74LS151N	85	SN74LS210N	180	SN74LS286N	180
SN74LS16N	20	SN74LS085N	110	SN74LS153N	80	SN74LS211N	85	SN74LS287N	180
SN74LS17N	28	SN74LS088N	40	SN74LS154N	180	SN74LS212N	180	SN74LS288N	180
SN74LS18N	28	SN74LS089N	85	SN74LS155N	125	SN74LS213N	220	SN74LS289N	220
SN74LS19N	28	SN74LS091N	80	SN74LS156N	125	SN74LS214N	125	SN74LS290N	220
SN74LS20N	35	SN74LS092N	90	SN74LS157N	80	SN74LS215N	220	SN74LS291N	180
SN74LS21N	35	SN74LS093AN	120	SN74LS160N	115	SN74LS216N	190	SN74LS292N	255
SN74LS22N	27	SN74LS098N	175	SN74LS161N	115	SN74LS217N	185	SN74LS293N	255
SN74LS23N	38	SN74LS107N	38	SN74LS162N	115	SN74LS218N	210	SN74LS294N	135
SN74LS24N	28	SN74LS109N	38	SN74LS163N	80	SN74LS219N	280	SN74LS295N	150
SN74LS25N	28	SN74LS112N	38	SN74LS164N	150	SN74LS220N	125	SN74LS296N	85

### MEMORY AND SUPPORT CHIPS (Prices exclude VAT)


SUPPORT	TMS6011	500	4118	2080	LINEARS	LM748CN-8	45	7915K	150	CMOS-FULL RANGE IN STOCK		
8212	2.20	81LS95	1.80	280P10	10.00	LM3013AH	30	LM748CN	45	7824K	1.50	
8216	2.20	81LS98	1.80	280 CTC	10.00	LM3013AN-8	10.00	LM1458H	72	7905	1.50	
8224	2.80	81LS97	1.80	280A P10	14.00	(Mini Dip)	30	LM1458M-8	48	7912	1.10	
8226	2.20	81LS98	1.80	280A CTC	14.00	LM308N	90	LM1488D	85	7915	1.10	
8228	4.20	RAMS				LM309K	145	LM1489AD	125	7905K	1.00	
8238	4.20	TIMERS				(TDS)	1.45	LM1495N-14	85	7912K	1.00	
8245	11.00	2101	2.32	1702	8.00	LM311N	128	LM1495N-14	85	7912K	1.00	
8246	11.00	2102L-4	1.20	5204	8.00	LM318N	2.25	LM3302N	85	7915K	1.50	
8251	5.00	2111	2.32	2708	8.00	LM323X	8.00	LM3401N	85	7924K	1.80	
8253	11.00	5810	4.08	2516	28.00	LM324N	78	LM3402N	120	8085	12.95	
8295	5.00	5814	4.08	2716	22.00	LM339N	54	LM3500N	84	8085	8.00	
8297	11.00	8154	11.95	2532	68.00	LM555N	30	TLO80CP	1.48	8 DIL	.14	
8298	12.50	2114	5.50	ROMS		LM556N	75	TLO81CP	.05	14 DIL	.17	
8299	18.00	2102L-3	1.60	74S287	4.00	LM7909CN	37	TLO82CP	1.28	18 DIL	.17	
8299	18.00	74CS20	11.00	74S287	12.00	LM7909CN	38	TLO83CN	1.85	20 DIL	.27	
6820P	4.50	74CS21	11.00	74S472	12.00	LM7909CN	38	TLO84CN	1.80	24 DIL	.27	
6821P	4.50	74CS29	11.00	74S470	5.00	LM723CH	5.00	LM741CN-S	25	2824	3.00	
6850P	4.50	4027	9.00	74S474	12.48	LM723CH	48	LM741CN-S	25	2824	3.00	
6852P	5.50	4044	9.00	74S471	12.48	LM733CN	1.30	VOLT REGS	80	28 DIL	.30	
AY-5-2376	11.50	4045	9.16	I/O	5.50	LM739CN	1.30	7805	30	48 DIL	.38	
MC14411	12.00	4050	8.16	I/O	7.50	LM741CH-14	33	7812	30	14 DIL	.42	
M57109	12.43	4080	7.80	2513	7.50	LM741CN-S	25	7815	30	CRYSTALS	18 DIL	.80
M57180	10.00	2107	7.00	98384	10.85	LM747CN-14	78	7824	30	100K	3.00	
M57161	10.00	4116	8.00	14412	12.00	LM747CH	1.10	7805K	1.50	200K	3.78	
								7812K	1.50	1MHZ	3.00	

### TRITON DOCUMENTATION

Available separately as follows Prices include P&P  
Triton manual. Detailed circuit description and constructional details and user documentation on level 4-1 monitor and basic **£5.70**  
L4-1 Listing listing of 1k monitor 2k tiny basic **£4.20**  
L5-1 User documentation on level 5-1 firmware **£1.20**  
L5-1 Listing listing of 1-5k monitor and 2-5k basic **£5.50**  
L6-1 User documentation on 7k basic interpreter **£1.80**  
Motherboard, 8k Ram and 8k Eprom constructional details **£5.00**  
User group newsletter subscription **£4** per annum. Triton software send SAE for list of programs available for Triton.
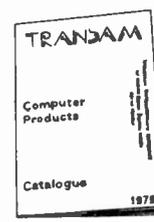
### HOME COMPUTING CATALOGUE

If you're in town, visit our showroom in Chapel Street, next to Edgware Road tube station. We have Tritons on display plus a comprehensive range of components and accessories, specifically for personal computer users. Books, mags, tapes, data, cables plus much more. Showroom open 6 days a week. (Half day Thurs., from 1.30).



**NEW**  
A4 size catalogue filled with our latest products

**40p** +SAE

All prices exclude VAT





4 1/2 in x 3 1/2 in **METER**. 300µA, 50µA or 100µA, **£6.40**. 25p P.&P.

**MICROPHONES FOR TAPE RECORDERS**  
DM228R 200 ohm with 3 5 and 2 5mm Jack Plugs **£1.70**  
DM229R 50K with 3 5 and 2 5mm Jack Plugs **£2.25**  
DM18D 200 ohm with 5 and 3 pin Din Plugs **£1.99**  
Postage on above microphones 17p



**CARDIOD DYNAMIC MICROPHONE**

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. **£8.02**. 33p P. & P.

2in x 2in meters 500µA, **£4.14**  
17p P.&P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, **£6.16**, 17p P.&P.

6V BUZZERS, 50mm diameter 30mm high, 52p. 15p. P. & P.

**MULTI-METER**

7N 360TR  
20,000 ohm/volt  
RESISTANCE  
RANGES  
X1, X10, X1K,  
X10K  
**£13.30**  
P.&P. 60p



**TRANSFORMERS Primary 240V**  
6-0-6V 100mA **£0.75**  
9-0-9V 75mA **£0.75**  
12-0-12V 50mA **£0.85**  
12-0-12V 100mA **£1.05**  
Post on above transformers 45p.  
9-0-9V 1A **£1.80**  
12-0-12V 1A **£2.15**  
15-0-15V 1A **£2.51**  
30-0-30V 1A **£3.10**  
6 3V 1 1/2A **£1.80**  
6-0-6V 1 1/2A **£2.20**  
Post on above transformers 60p.

All above prices include V.A.T. Send 40p for new fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

**M. DZIUBAS**

158 Bradshawgate · Bolton · Lancs. BL2 1BA

**ASTRA-PAK**  
92 GODSTONE ROAD  
WHYTELEAF SURREY CR3 0EB

VAT must be added at 15% to all prices shown. P&P 25p - VAT. Send SAE for full catalogue including books, resistors, capacitors, vero, etc.

7400	0.10	7483	0.58	74166	0.78	4021	0.80	4180	1.05	LINEAR	16 pin	0.12	
7400	0.23	7484	0.88	74167	2.00	4022	0.80	4181	1.05	CA3045-14	0.50	0.18	
7401	0.11	7485	0.58	74170	1.50	4023	0.15	4182	1.05	CA3046-14	0.20	0.18	
7402	0.11	7486	0.22	74172	6.30	4024	0.50	4183	1.05	LM380N-14	0.85	0.22	
7403	0.11	7488	0.42	74173	1.15	4025	0.15	4184	1.05	LM381N-14	1.40	0.24	
7404	0.11	7489	1.65	74174	0.65	4026	1.15	4174	1.05	LM710-14	0.30	0.28	
7404	0.23	7490	0.32	74175	0.60	4027	0.42	4175	0.98	LM711N-14	0.30	0.36	
7405	0.12	7491	0.64	745175	1.00	4028	0.65	4194	1.05	MG1310P-14	0.88	0.11	
7405	0.22	7492	0.36	74176	0.58	4029	0.76	4404	0.48	NE555-8	0.25	0.12	
7406	0.22	7493A	0.30	74177	0.58	4030	0.46	4412	0.19	NE556-14	0.50	0.11	
7407	0.22	7494	0.72	74178	1.50	4031	1.95	4428	0.38	NE2501B-14	0.80	0.11	
7408	0.13	7495	0.50	74179	1.50	4032	0.88	4445	0.90	SN75110N	0.40	0.11	
7409	0.13	7496	0.48	74180	0.85	4033	1.25	4449	0.19	SN76003N	1.60	0.11	
7410	0.11	7497	1.90	74181	0.58	4034	1.15	4501	0.18	SN76013N	1.25	0.11	
7410	0.23	74100	0.85	74182	0.70	4035	1.00	4502	0.80	SN76023N	1.25	0.11	
7411	0.17	74104	0.39	745182	1.50	4036	2.70	4503	0.68	SN76033N	1.60	0.10	
7411	0.23	74105	0.38	74183	0.75	4037	0.85	4506	0.50	SN76477N	2.50	0.262	
7412	0.15	74107	0.24	74184	1.30	4038	0.95	4507	0.52	TA6550B	0.32	0.300	
7413	0.24	74109	0.32	74185A	1.30	4039	2.75	4508	2.50	TA6551B	0.88	1.000	
7414	0.50	74110	0.36	74186	5.00	4040	0.58	4510	0.92	T8A120S	0.66	1.008	
7415	0.23	74111	0.30	74187	0.60	4041	0.72	4511	0.92	T8A641A	1.50	1.8432	
7416	0.23	74113	0.30	74190	0.68	4042	0.57	4512	0.92	T8A800	0.78	2.000	
7417	0.23	74116	1.50	74191	0.68	4043	0.80	4513	1.85	T8A810S	0.75	2.097	
7420	0.11	74118	0.80	74192	0.62	4044	0.80	4514	2.30	T8A820S	0.68	2.457	
7421	0.20	74119	1.50	74193	0.62	4045	1.25	4515	2.60	TC4270S0	1.60	3.276	
7422	0.16	74120	0.95	74194	0.62	4046	1.05	4516	0.99	TD4200	3.00	35.79	
7423	0.21	74121	0.25	74195	0.60	4047	0.85	4517	3.75	ZN414	0.80	3.332	
7425	0.23	74122	0.39	74196	0.72	4048	0.48	4518	0.90	VOLTAGE	4.000	2.60	
7426	0.23	74123	0.38	74197	0.58	4049	0.33	4519	0.50	REGULATORS	4.433	2.60	
7427	0.24	74125	0.32	74198	1.00	4050	0.40	4520	0.95	LM300H-1099	0.75	4.915	
7428	0.26	74126	0.35	74199	1.20	4051	0.72	4521	2.20	LM305H-703	1.30	5.000	
7430	0.11	74128	0.75	74221	1.30	4052	0.72	4522	1.25	UA723-14	0.32	5.068	
7433	0.23	74130	0.50	74273	2.05	4053	0.72	4526	1.25	7805-10220	0.70	5.185	
7432	0.22	74132	0.55	74278	1.65	4054	1.00	4527	1.40	7812-10220	0.70	5.875	
7433	0.30	74134	0.38	74279	1.10	4055	1.05	4528	0.92	7815-10220	0.70	6.000	
7437	0.21	74135	0.70	74283	1.65	4060	1.00	4529	1.30	7824-10220	0.70	6.144	
7438	0.21	74136	0.52	74284	3.40	4066	0.48	4530	0.78	7805-10220	0.78	6.553	
7440	0.12	74137	0.80	74293	1.30	4067	3.25	4531	0.99	7912-10220	0.78	8.000	
7441	0.50	74141	0.55	74298	1.80	4068	0.70	4532	1.20	7915-10220	0.78	8.867	
7442	0.40	74142	1.95	74390	1.75	4069	0.17	4534	5.20	LOW PROFILE	10.000	2.60	
7443	0.70	74143	2.50	74393	1.25	4070	0.17	4536	3.60	DIL SOCKETS	12.000	2.60	
7444	0.70	74144	2.50	CMOS	4071	0.17	4538	1.25	8 pin	0.09	13.516	2.60	
7445	0.52	74145	0.55	4000	0.13	4072	0.17	4539	0.99	14 pin	0.11	18.000	3.20
7446	0.60	74147	1.40	4001	0.15	4073	0.17	4541	1.05	16 pin	0.11	18.000	3.20
7447	0.48	74148	1.25	4002	0.15	4075	0.17	4543	1.50	LED'S			
7448	0.56	74150	0.68	4006	0.85	4076	0.84	4549	3.92	RED	0.25"	0.2"	
7450	0.11	74151	0.48	4007	0.16	4077	0.21	4553	3.60	GREEN	0.14	0.14	0.09
7451	0.11	74153	0.48	4008	0.78	4078	0.18	4554	1.25	LOW	0.14	0.14	0.09
74452	0.23	74154	0.82	4009	0.40	4081	0.17	4555	0.75	LED clip	0.25	0.35	
7453	0.11	74155	0.50	4010	0.40	4082	0.18	4556	0.75	TMS 4030 4096 BIT DYNAMIC RANDOM ACCESS (2107A) MEMORY	2.70	2.60	
7454	0.11	74156	0.50	4011	0.15	4085	0.63	4557	3.25	300ms max. access time 470ns max. read			
7460	0.11	74157	0.50	4012	0.15	4086	0.63	4558	1.25	Inputs No. on pull up resistors needed. Low			
7470	0.25	74158	0.68	4013	0.40	4089	1.35	4559	3.95	1.42 power dissipation. 350mW operating 0.3mW standby. Single low capacitance clock.			
7472	0.22	74159	1.90	4014	0.78	4093	0.60	4560	1.98	Data sheet available			
7473	0.25	74160	0.60	1015	0.70	4094	1.68	4561	0.72	2.40 each 4-10% 8-20%			
7474	0.25	74161	0.50	4016	0.40	4095	0.90	4562	5.50				
74574	0.42	74162	0.62	4017	0.72	4096	0.90	4566	1.42				
7475	0.30	74163	0.62	4018	0.75	4097	3.30	4588	2.50				
7476	0.25	74164	0.68	4019	0.42	4098	0.95	4569	1.60				
7480	0.43	74165	0.68	4020	0.88	4099	1.40	4580	4.98				



**Microcomputers are coming - ride the wave! Learn to program**

Millions of jobs are threatened, but millions more will be created through the microcomputer revolution. Will YOU sink or swim? Be one of the people who welcomes computers and the end of boring jobs.

Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency - all you need to start with is a knowledge of simple arithmetic and the use of decimals. And you don't need a computer.

This unique course comes as four A4 books, written by three authors well-known in the fields of microcomputing, self-instruction and writing clear English. In 60 straightforward lessons you learn the five essentials: problem definition, flowcharting, coding the program, debugging, and preparing clear documentation.

Every lesson has thought-provoking questions and we never ask for mindless drudgery. You will know that you are mastering the material and feel a rare satisfaction. Harder problems are provided with a series of graded hints, a unique and really helpful approach. So you never sit glassy-eyed with your mind a blank. First time through, you may need to read most of the hints, but you will soon learn to tackle tough programming tasks - such as writing programs for computer games, preparing graphs on an output printer, calculating compound interest tables and estimating costs.

**COMPUTER PROGRAMMING IN BASIC £7.50**

- Book 1** Computers and what they do well: READ, DATA, PRINT; powers, brackets, variable names; LET; errors; coding simple programs.
- Book 2** High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.
- Book 3** Compilers and interpreters; loops, FOR...NEXT; RESTORE; debugging; arrays; bubble sorting; TAB.
- Book 4** Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

**THE BASIC HANDBOOK £11.50**

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

**FORTRAN COLORING BOOK £5.40**

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others-this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

**A.N.S. COBOL £4.40**

Covers the most widely used computer language in business today. It teaches how to write a COBOL program and compile it effectively, paying proper attention to spelling, punctuation, and format.

**THE ALGORITHM WRITER'S GUIDE £3.75**

FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

**The Algorithm Writer's Guide** explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.



# Cambridge Learning Enterprises

## Understand Digital Electronics

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

## DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

- Book 1** Binary, octal and decimal number systems; conversion between number systems.
- Book 2** AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables.
- Book 3** Positive ECL; De Morgans Laws; designing logic circuits using NOR gates.
- Book 4** R-S and J-K flip flops; binary counters, shift registers and half adders.

## DESIGN OF DIGITAL SYSTEMS £11.50

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates; NOT, exclusive OR NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

## O-LEVEL ENGLISH LANGUAGE £7.00

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on COMPREHENSION, Book 2 covers SUMMARY, PUNCTUATION & SPELLING, and Book 3 coaches you in the principles of COMPOSITION. Size: 3 A4 volumes totalling 250 pages.

## SELF-INSTRUCTION COURSES



**CAMBRIDGE LEARNING ENTERPRISES, UNIT 26, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS PE17 4BR, ENGLAND. TELEPHONE: ST. IVES (0480) 67446**

All prices include worldwide postage (airmail extra)  
If order comes to £15 or more, deduct £2  
Please allow 21 days for delivery

### GUARANTEE No risk to you.

If you are not completely satisfied your money will be refunded when books are returned in good condition.

Please send me the following books:

- .....Computer Programming in BASIC (4 books) at £7.50
- .....The BASIC Handbook at £11.50
- .....FORTRAN Coloring Book at £5.40
- .....A.N.S. COBOL at £4.40
- .....Algorithm Writer's Guide at £3.75
- .....Digital Computer Logic & Electronics (4 books) at £7.00
- .....Design of Digital Systems (6 books) at £11.50
- .....O-Level English Language (3 books) at £7.00

I enclose a \*cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my >(\*delete where applicable)

\*Access/Barclaycard/Visa/ Eurocard/Mastercharge/Trustcard  
Diners Club. Account No. ....

Signature .....

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers (inc. Eire) should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

Name .....

Address .....

Cambridge Learning Enterprises, Unit 26, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England.



*"Once upon a time the oscilloscope was adequate for most development Engineers."*

**With the advent of micro's this is not enough !!**

**What you now need is ...**



*(as reviewed in this issue)*

**...the complete visual development system.**

Softy Development Kit - £99.95 + VAT

Softy Built - £119.95 + VAT

**CAN YOU AFFORD TO BE WITHOUT ONE ?**

## **SUPERBOARD II**

**£188  
plus VAT**

**(4k RAM)**



**NO FLICKER - NOW 50Hz**

- |   |               |
|---|---------------|
| Plastic Case                                      | - £26 + VAT   |
| G10 Ram expansion with 8k                         | - £188 + VAT  |
| IP FD Floppy Disc Drive                           | - £312 + VAT  |
| Additional 4k Ram (8x2114)                        | - £35 + VAT   |
| PAL Colour Graphics Card                          | - TBA         |
| Software Cassettes from<br>(Range of 65 programs) | - £5.50 + VAT |

**PLEASE NOTE, OHIO SOFTWARE WILL ONLY RUN ON OHIO PRODUCTS.**

## **THE RADOFIN**

The Radofin Teletext Decoder comes complete with remote controller and will operate with most colour or black and white television sets.


The Radofin Teletext Decoder enables you to use your present TV set to receive all Teletext transmissions in your area. It is not necessary to buy or rent another TV set. You merely plug your aerial into the Radofin Teletext Decoder and a simple connection between the Decoder and your TV set gives you the full Radofin Teletext service. With Teletext you get instant visual information on the news, the weather and a mass of other subjects. And because it does not depend on the sound it is of great benefit to the deaf.

This 'State of the Art' Teletext Decoder incorporates the very latest technology and includes the following features:

- Double height character facility*
- Resolution doubled for easier viewing*
- True PAL colour for faithful reproduction*
- Meets latest broadcast specifications by BBC and IBA*
- Push button channel change*
- Unnecessary to remove the unit to watch normal TV programmes*
- Silent keys to remote controller-tone tells you a new entry is being made*
- Gold plated circuit board for long life and high reliability*
- Stylish cabinet to suit all decors*

*Dimensions: Main Cabinet-400mm length, 205mm depth, 105mm height.  
Remote controller-112mm depth, 63mm width, 20mm height (average)  
Input voltage: 240 volts AC 50Hz*

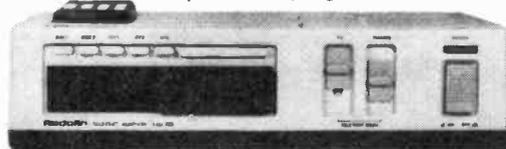**Ready built to plug into aerial £185 plus VAT**



12 month guarantee. Cheques or P.O.'s or telephone Card no. to  
DETAILS ON REQUEST.  
MONEY BACK GUARANTEE


ALLOW 7 DAYS FOR DELIVERY

**VIDEOTIME Products**  
**56 QUEENS RD, BASINGSTOKE, HANTS. RG21 1RER**  
**TEL. (0256) 56417 & 26620 TELEX 858747**

# TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

—WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS—

## STEREO PRE-AMPLIFIER POWER AMPLIFIER

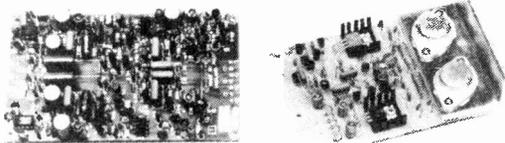

### CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/μS; T.H.D. 20Hz—20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 × 80 × 20mm. Supply to be ±15 volts.

### MC 1—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

### X02 : X03 — ACTIVE CROSSOVERS

X02 — two way, X03 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

### REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

### POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μS; signal to noise ratio 110dB; frequency response 10Hz-35kHz, —3dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 × 80 × 25mm.

## POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120–240 primary and single bolt fixing (includes capacitors/bridge rectifier).
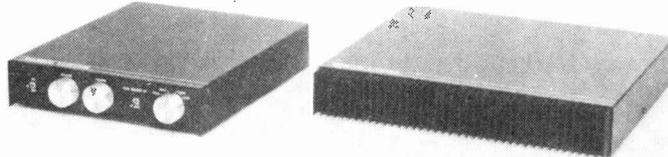
## PRE-AMPLIFIER KIT

This includes all metalwork, pots, knobs etc. to make a complete pre-amp with the CPR 1 (S) module and the MC 1 (S) if required.



### ACTIVE CROSSOVERS

X02 ..... £16-18 X03 ..... £23-58

### POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35v ..... £19-52

CE 1004 100W/4 ohms 35-0-35v ..... £23-02

CE 1008 100W/8 ohms 45-0-45v ..... £26-96

CE 1704 170W/4 ohms 45-0-45v ..... £31-00

CE 1708 170W/8 ohms 60-0-60v ..... £33-97

### TOROIDAL POWER SUPPLIES

CPS1 for 2 × CE 608 or 1 × CE 1004 ..... £16-56

CPS2 for 2 × CE 1004 or 2/4 × CE 608 ..... £18-80

CPS3 for 2 × CE 1008 or 1 × CE 1704 ..... £19-75

CPS4 for 1 × CE 1008 ..... £17-12

CPS5 for 1 × CE 1708 ..... £24-15

CPS6 for 2 × CE 1704 or 2 × CE 1708 ..... £25-53

### HEATSINKS

Light duty, 50mm, 2°C/W ..... £1-44

Medium power, 100mm, 1-4°C/W ..... £2-35

Disco/group, 150mm, 1-1°C/W ..... £3-04

Fan, 80mm, slate 120 or 240v ..... £19-70

Fan mounted on two drilled 100mm heatsinks, 2 × 4°C/W, 65°C max. with two 170W modules ..... £31-05

THERMAL CUT-OUT, 70°C. .... £1-54

### Pre-amp Kit

..... £38-07

### POWER AMP KIT

..... £35-03

### PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1 ..... £31-85

CPRIS ..... £40-87

MCI ..... £21-28

MCIS ..... £33-17

### POWER SUPPLY

REG1 ..... £6-90

TR6 ..... £1-97

### BRIDGE DRIVER, BDI

Obtain up to 340W using 2 × 170W amps and this module BDI ..... £5-75

## CRIMSON ELEKTRIK

1A STAMFORD STREET,  
LEICESTER. LE1 6NL

Tel: (0533) 553508

U.K.—please allow up to 21 days for delivery.

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.


### Distributors:

**BADGER SOUND SERVICES LTD.**  
46 WOOD STREET, LYTHAM ST. ANNES,  
LANCASHIRE FY8 1QG  
**MINIC TELEPRODUKTOR**  
BOX 12035: S-750 12  
UPPSALA 12, SWEDEN

## Great new Crofton Treble

Self contained

### MONITOR PCB

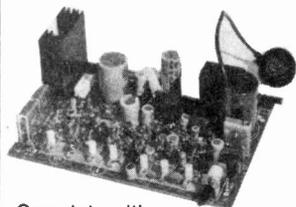

Complete with all leads and scan coil assembly. Tubes and transformers available separately from stock.

£35.50



Self contained  
10" MONITOR

The unbeatable 10" Aztec, complete and ready to go.

£85.00

THE SOUGHT AFTER

## ★ OHIO SUPERBOARD II ★

(All prices ex VAT and P&P)

Fully constructed at £188.00

# CROFTON ELECTRONICS

Crofton Electronics Limited, 35 Grosvenor Road,  
Twickenham, Middlesex. Tel: 01 891 1923

## Mail Order Protection Scheme

The Publishers of 'Practical Electronics' are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with 'Practical Electronics' within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence. For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.



# ELECTROVALUE CATALOGUE 10

Ready early December

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

## FREE

(You don't even have to pay postage)

### IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

- **We give discounts**  
on C.W.O. orders, except for a few items market Net or N in our price lists.  
**5%** on orders, list value £10 or more  
**10%** on orders list value £25 or more.  
*Not applicable on Access or Barclaycard purchase orders.*
- **We stabilise prices.**  
by keeping to our printed price lists which appear but three or four times a year.
- **We guarantee**  
all products brand new, clean and maker's spec. No seconds, no surplus.
- **We pay postage in U.K.**  
on C.W.O. orders list value £5 or over. If under, add 30p handling charge.
- **Appointed distributors for**  
SIEMENS, VERO, ISKRA, NASCOM and many others.

#### OUR NEW CATALOGUE No 10

Over 120 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

## ELECTROVALUE LTD

#### HEAD OFFICE (Mail Orders)

28(B) St. Judes Road, Englefield Green, Egham, Surrey  
TW20 0HB. Phone: 33603 (London prefix 87. STD 0784) Telex 264475.

#### NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA  
Phone: (061) 432 4945.

#### HOME COMPUTING BARGAINS

Full keyboard, cassette interface, use your TV as a VDU. Chip Scientific Superboard II fully assembled, 8K basic, 4K ram, special offer price now includes free power supply and modulator kit £188 + 15% VAT. Tandy TRS80 level 2 basic, 16K ram, includes modulator and psu £450 + 15% VAT.

#### SINCLAIR PRODUCTS

FM200 £51.95, case £3.40, adaptor £3.40, connector kit full £11.27. Microvision TV £91.44, mains adaptor £6.88. PDM35 £29.76, mains adaptor £3.40, case £3.40. DM350 £71.82. DM450 £102.17. DM235 £52.66. Accessories for all 3 models:- rechargeable batteries £7.99, mains adaptor/charger £3.94, case £9. Enterprise prog calculator £23.27. New 10MHz scope £145.

#### COMPUTER GAMES

Chess challenger 7 £84. Voice challenger £229. Checker challenger 2 £46. Checker challenger 4 £84. Atari video computer £147. Cartridges £14.32. Star Chess £62. Chess champion 6 £49.95.

#### CONTINENTAL SPECIALITIES PRODUCTS

EXP300 £6.61. EXP350 £3.62. EXP325 £1.64. EXP650 £4.14. EXP4B £2.64. LP2 £20.70.

#### TV GAMES

Tank battles kit £6.34. AY-3-8500 chip £5.27, kit £4.26. Stunt cycle AY-3-8760 chip £13.63, kit £4.00. 10 game paddle 2 AY-3-8600 chip £10.25, kit £7.03. Racing car chip AY-3-8603 £13.63. Modified shoot kit £5.28. Rifle kit £5.27. Colour generator kit £9.05. Joystick 220K £1.80.

#### MAINS TRANSFORMERS

6-0-6V 100ma 76p, 1½ £2.60. 9-0-9V 75ma 76p, 1a £2.22, 2a £2.89. 12-0-12V 100ma 92p, 1a £2.75. 15-0-15V 1a £3.09.

#### JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 Watts £2.08. JC20 10 Watts £3.14.

#### FERRANTI ZN414

IC radio chip 85p, extra parts and pcb for radio £4.10, case £1.06.

#### PRINTED CIRCUIT MATERIALS

PC etching kits:- economy £2.32, standard £4.36. 40 sq ins pcb 66p. 1 lb FeCl £1.30. etch resist pens:- economy 50p, dalc 84p. drill bits 1/32" or 1mm 27p. etching dish 89p. laminate cutter 82p.

#### S-DECS AND T-DECS

S-Dec £3.79. T-Dec £4.59. u-DecA £4.69. u-DecB £7.16. 16 dil adaptor £2.31.

#### BATTERY ELIMINATORS

3-way types with switched output and 4 way multi-jack:- 3/4/6V 100ma £2.39. 6/7/9V 300ma £3.14. 100ma radio types with press stud connectors 9v £3.57. 6v £3.57. 4½ + 4½v £4.79. cassette recorder mains unit 7½V 100ma with 5 pin din plug £3.57. fully stabilized type 3/6/7/9V 400ma £5.76. car converters 12v dc input, output 9v 300ma £1.19. output 7½v 300ma £1.19. output 3/4/6/7/9/12v 800ma £2.66.

#### BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4½v £1.49. 6v £1.49. 9v £1.49. 4½ + 4½v £1.92. 6 + 6v £1.92. 9 + 9v £1.92. cassette type 7½v 100ma with din plug £1.49. heavy duty 13 way types 4½/6/7/8½/11/13/14/17/21/25/28/34/42v 1A £4.95. 2A £7.72. car converter input 12v dc, output 6/7/9V 1A stabilized £1.35.

#### STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. 8-way types 3/4/6/7/9/12/15/18v 100ma £1.74 (£2.50). 1A £2.98 (£5.10). 2A £4.10 (£6.87). variable voltage models 2-18V 100ma £2.12 (£2.98). 1-30v 1A £2.98 (£5.35). 1-30v 2A £4.98 (£11.24).

#### BI-PAK AUDIO MODULES

AL30A £4.08. PA12 £8.38. PS12 £1.58. T538 £2.70. S450 £25.06. AL60 £5.06. PA100 £17.33. SPM80 £4.74. BMT80 £6.08. Stereo 30 £21.57. MA60 £38.27.

#### COMPONENTS

1N4148 0.9p. 1N4002 3.1p. 741 8 dil 18p. 723 14 dil 31p. NE555 8 dil 25p. bc183, bc213, bc547, bc549 4.2p. bc182, bc184, bc212, bc214, bc548 5p. tip31c, tip32c 30p. tip41c 39p. bd131, bd132 27p. plastic equiv bc107 5p. fuses 20mm x 5mm cartridge 15, 25, 5, 1, 2, 3, 5 Amp quick-blow 1p. anti-surge 3.6p. resistors 5% ½W £12 10R to 10M 1p. 0.8p for 50 + of one value. polyester capacitors 250v 0.15, .068, 1mf 1.5p, .01, .033, .33 2.8p. .022, .047mf 3.3p. .22, .47mf 4.9p. polystyrene capacitors £12 63v 10 to 1000pf 3p. 1n2 to 10n 4p. ceramic capacitors 50V £6 22pf to 47n 2p. electrolytic capacitors 50v, 5, 1, 2mf 5p. 25v 5, 10mf 5p. 16v 22, 33mf 5p. 47, 68mf 3.5p. 100mf 6p. 330, 470mf 9p. 1000mf 10p. zeners 400mw E24 2v7 to 33v 7p. preset pots subminiature 0.1W horiz or vert 100 to 4M7 6p. potentiometers ½W 4K7 to 2M2 log or lin 31p. dual 6p. 7 red LEDs 9.7p. ic sockets 8 dil 8.7p. 14 dil 10.1p. 16 dil 12p.

### SWANLEY ELECTRONICS

DEPT PE, 32 Goldsrd Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 30p to the total cost of your order for postage. Prices include VAT unless stated. Lists 24p post free. Overseas customers deduct 13%. Official credit orders welcome.

The new all British designed single board

MICROCOMPUTER

## SEMEL-ABACUS

IN KIT FORM

- ★ Supplied with 16K of RAM
- ★ Uses the powerful Z-80 Microprocessor
- ★ Space for upto 32K RAM on board
- ★ 8K Full Basic
- ★ VDU Memory Mapped
- ★ 64 Characters by 16 Lines
- ★ Tape Interface
- ★ Single Board Construction
- ★ RS 232 Printer Interface
- ★ Plugs into a standard TV set
- ★ Full alphanumeric Characters plus 64 User Definable Graphics

**£376.50**

**+ VAT**

#### OPTIONAL

- ★ Colour Graphics
- ★ Expansion board to full 64K Memory
- ★ Analogue Interface



## STRUTT

ELECTRICAL AND MECHANICAL  
ENGINEERING LTD.

3C, BARLEY MARKET ST., TAVISTOCK, DEVON. PL19 05F  
Tel: TAVISTOCK (0822) 5439 Telex: 45263

# U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

## BSR DE LUXE AUTOCHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13 1/2" x 11 1/4". 3 speeds. Above motor board 3 3/4". Below motor board 2 1/2". With Ceramic Stereo cartridge.



£20 Post £1 60

## HEAVY METAL PLINTHS ONLY

Cut out for most BSR or Garrard decks. Silver grey finish. Model 'A' Size 14 1/2" x 12 1/2" x 3in.

Post £1 60  
£3.50  
£4.50


## TINTED PLASTIC COVERS ONLY

Sizes 14 1/2" x 12 1/2" x 3in. £3.50 each  
14 1/2" x 12 1/2" x 3in. £3.50 each  
15 1/4" x 13 1/4" x 4in. £6.  
17 1/4" x 9 1/2" x 3 1/2in. £3.18 x 12 1/2" x 3in. £6.  
14 1/2" x 14 1/4" x 2 1/2in. Rosewood sides £4.

Post £1 60
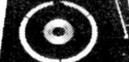
## BSR SINGLE PLAYER

Ideal replacement or disco deck with cueing device and stereo ceramic cartridge. 3 speeds. Large turntable, modern design.



£21 Post £1 60

## TWO-SPEED BUDGET DESIGN £15.

BSR P182 3 speeds flared aluminium turntable 'S' shape arm, cueing device, ceramic cartridge £24. Post £1 60. BSR MP60/P128 Stereo Ceramic, balanced arm, cueing device. Bias compensator £28. Magnetic £5 extra.

## GARRARD HI-FI MINI CHANGER

Model 2025  
3-speed stereo cartridge £8.95  
Cueing devices Post £1 60



## B.S.R. P163 BELT DRIVE QUALITY DECK

Manual or automatic play. Two speeds. Precision balanced arm. Slide in head, cueing device. Bargain price.



£30 Post £1 60  
Suitable magnetic cartridge £6.50.

## ELAC HI-FI SPEAKER 8in. TWIN CONE

Large ceramic magnet. 50-16,000 c/s. Bass resonance 40 c/s. 8 ohm impedance. 10 watts RMS. 20 watt woofer bass unit only.



£5.95 Post 75p  
£7.95 Post 75p

## LOW VOLTAGE POWER PACK FOR MODELS

Ready made. Famous make. Will supply 10 volts D.C. at 400mA. With terminals and mains lead.

£2.75 Post 50p

## POTENTIOMETERS

5kΩ to 2MΩ. LOG or LIN. L/S 35p. DP 60p. Stereo L/S 85p. DP. Edge Pot 5K SP. 45p.

## 80 Ohm Coax

FRINGE LOW LOSS 15p yd. PLUGS 10p. SOCKETS 10p. LINE SOCKETS 25p. OUTLET BOXES 80p. 300 ohm FEEDER 5p yd.

## EMI 1 1/2 x 8in. LOUSPEAKERS

With tweeter and crossover 10 watt 3 or 8 ohm.

Bass woofer only 8 ohm 15 watt.

£9.95 Post 75p

£10.95 Post 75p

Bass woofer only 15 ohm 20 watt.

£11.95 Post 75p

## Suitable Bookshelf Cabinet

Teak finish. For EMI 1 1/2 x 8 speakers. Size 16 x 11 x 8 inches approximately.

£9.50 Post £1 60

## THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S A E. Will also demagnetise small tools.



Head Demagnetiser only £5.00 Post 50p

## RELAYS. 12V DC 95p. 6V DC 85p. 24V AC 95p.

BLANK ALUMINIUM CHASSIS. 6 x 4-95p; 8 x 6-£1.40; 10 x 7-£1.55; 12 x 8-£1.70; 14 x 9-£1.90; 16 x 6-£1.85; 16 x 10-£2.20. ANGLE ALI. 6 x 3/4 x 4in-20p. ALUMINIUM PANELS. 6 x 4-24p; 8 x 6-38p; 14 x 3-40p; 10 x 7-54p; 12 x 8-70p; 12 x 5-44p; 16 x 6-70p; 14 x 9-84p; 12 x 12-£1; 16 x 10-£1.16. PLASTIC AND ALI BOXES IN STOCK. MANY SIZES VARICAP FM TUNER HEAD with circuit & connections. Some technical knowledge required £4.95. TAG STRIP. 28-way 12p. TAPE OSCILLATOR COIL. Valve type. 35p. BRIDGE RECTIFIER. 200V PIV 1/2 amp 50p. 8 amp £2.50. TONGLE SWITCHES SP 30p. DPST 40p. DPDT 50p. MANY OTHER TOGGLES IN STOCK. Please enquire. PICK-UP CARTRIDGES ACOS, GP91 £2.00. GP94 £2.50. SONOTONE 9TAHC Diamond £3.75. V100 Magnetic £6.50. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p. CASSETTE MOTOR. 6 volt £1.00. CASSETTE MECHANISM. Mono heads no motor £3.00.

## MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V AC Mains F.M./A.M. Stereo Tuner Covering M.W., A.M. 540-1605KHz. V.H.F., F.M. 88-108MHz. Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Indicator. Built-in Pre-amps with variable output adjustable by pre-set control. Max. o/p Voltage 600mV R.M.S. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/4in wide, 4in high x 9 1/2in deep approx.

Only £28 Post £1 60

## RCS SOUND TO LIGHT KIT Mk. 2

Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. Suitable for home or disco. Easy to build. Full instructions supplied. Cabinet £4.50 extra. Will operate from 200MV to 100 watt signal.

£18 Post 50p

## RCS "MINOR" 10 watt AMPLIFIER KIT

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available. Mono. £12.50; Stereo. £20. Post 45p. Specification 10W per channel, input 100mV, size 9 1/2" x 3 x 2in approx. SAE details. Full instructions supplied. AC mains powered. Input can be modified to suit guitar.


R.C.S. STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel. With volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95 Post 35p

## MAINS TRANSFORMERS

250 0 250V 70mA 6.5V 2A	£3.45
250 0 250V 80mA 6.3V 3.5A 6.3V 1A	£4.60
350 0 300V 100mA 6.3V 3.5 5 amp	£5.80
300 0 300V 120mA 2x6 3V 2A CT 5V 2A	£5.80
220V 45mA 6.3V 2A	£2.50
HEATER TRANSFORMER 6.3V 1/2 amp	£2.00 3 amp
GENERAL PURPOSE LOW VOLTAGE Tapped outputs available	£2.20
12 amp 3 4 5 6 8 9 10 12 15 18 25 and 30V	£6.00
1 amp 6 8 10 12 16 18 20 24 30 36 40 48 60	£9.50
2 amp 6 8 10 12 16 18 20 24 30 36 40 48 60	£12.50
3 amp 6 8 10 12 16 18 20 24 30 36 40 48 60	£16.00
5 amp 6 8 10 12 16 18 20 24 30 36 40 48 60	£19.00
12V 100mA	£1.30
12V 250mA	£1.75
10 0 10V 2amp	£3.00
30V 5 amp and 17V 0.17V	£4.00
2 amp	£2.50
0.5 8 10 16V 1/2 amp	£3.50
9V 3 amp	£4.50
25 0 25V 2 amp	£4.50
30V 2 amp	£3.50
30V 1 1/2 amp	£3.50
20V 40V 60V 1 amp	£3.50
12V 3 amp	£3.00
10V 30V 40V 2 amp	£3.50
40V 2 amp	£3.50
20V 1 amp	£3.00
20V 0.20V 1 amp	£3.00
30V 0.30V 2 amp	£6.00
2 of 18V 6 amp each	£11.00
12 0 12V, 2 amp	£3.50
9V 1/2 amp	£3.00
AUTO TRANSFORMERS 115V to 230V 230V to 115V 150W	£7.00
250W £8.00 400W £8.00 500W £10.00	
FULL WAVE BRIDGE CHARGER RECTIFIERS	
6 or 12V outputs 2 amp 75p. 4 amp £4 25	
CHARGER TRANSFORMERS 1 1/2 amp £1.60. 3 amp £4.00 4 amp £6.50	
12V 1 1/2 amp Half Wave Selenium Rectifier	25p
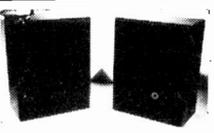
## COMPACT SPEAKERS

Teak 4 or 8 ohm. White 4 ohm only. 13 x 10 x 6in approx. 50 to 14,000 cps. 10 watts. £16 pair Post £1 60



## EXTENSION SPEAKERS £3.95 ea.

Globe shaped cases in high gloss mouldings of red or green, are finished with chrome frontal trim. In addition, 2 1/2 metres of twin lead already fitted with phono plug is supplied.



Full Range Quality Frequency Response Impedance: 8 ohms Power Peak: 5 watts

## LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 15p; 25V 20p; 50V 30p; 420mF 50V £1.30.  
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.  
2000mF 6V 25p; 25V 42p; 40V 60p; 1200mF 76V 80p.  
2500mF 50V 82p; 3000mF 25V 47p; 50V 65p.  
4500mF 64V £2; 4700mF 63V £1.20. 2700mF/76V £1.  
5000mF 35V 85p. 5600mF/76V £1.75.

## HIGH VOLTAGE ELECTROLYTICS

8/350V 22p 8+8/450V 50p 50+50/300V 50p  
16/350V 30p 8+16/450V 50p 32+32/450V 75p  
32/500V 75p 16+16/450V 50p 100+100/275V 65p  
50/500V £1.20 32+32/350V 50p 150+200/275V 70p

## MANY OTHER ELECTROLYTICS IN STOCK

SHORT WAVE 100pf air spaced gangable tuner. 85p.  
TRIMMERS 10pF 30pF. 50pF. 5p. 100pF. 150pF. 15p.  
CERAMIC, 1pf to 0.01mF. 5p. Silver Mica 2 to 5000pf. 5p.  
PAPER 350V/0.1 7p; 0.15p; 1mf 150V 20p; 2mf 150V 20p.  
20p; 50V 0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.  
MICRO SWITCH SINGLE POLE CHANGE OVER 20p.  
SUB-MIN MICRO SWITCH, 25p. Single pole change over  
TWIN GANG, 385 + 385pf 80p; 500pf slow motion 75p.  
365 + 365 + 25 + 25pf. Slow motion drive 85p. 120pf 50p.  
TRANSISTOR TWIN GANG, 50p.  
NEON PANEL INDICATORS 250V. Amber or red 30p.  
ILLUMINATED ROCKER SWITCH, single pole. Red 65p.  
RESISTORS. 100 to 10M. 1/4W, 1/2W, 1W, 20% 2p; 2W, 10p.  
HIGH stability. 1/2W 2% 10 ohms to 1 meg. 12p.  
Ditto 5%. Preferred values 10 ohms to 10 meg. 5p.

## ELECTRO MAGNETIC PENDULUM MECHANISM 95p

Post 30p. 1.5V DC operation over 300 hours continuous on SP2 battery. Fully adjustable swing and speed. Ideal displays. teaching electro magnetism or metronome, strobe, etc.

## BAKER SUPERB 12in 25 watt

Post £1 60

Quality loudspeaker, low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register. Bass resonance 25 c/s. Useful response 20-17,000 c/s. 8 or 16 ohms models.



## BAKER "BIG-SOUND" SPEAKERS. Post £1 60

'Group 100'	'Disco 100'	'Group 50/15'
12 inch 100 watt	12 inch 100 watt	15 inch 75 watt
8 or 16 ohm	8 or 16 ohm	8 or 16 ohm

## BAKER LOUDSPEAKER, 12 INCH. 60 WATT.

GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER FULL RANGE PROFESSIONAL QUALITY RESPONSE 30-16,000 CPS MASSIVE CERAMIC MAGNET WITH ALUMINIUM PRESENCE CENTRE DOME. Post £1 60

## TEAK VENEERED HI-FI SPEAKER CABINETS

For 13x8in or 8in speaker £9.50 Post 1 00. For 6 1/2in speaker and tweeter £8.50 Post 75p. Many other cabinets in stock. Phone your requirements. SPEAKER COVERING MATERIALS. Samples Large S A E LOUDSPEAKER CABINET WADDING 18in wide 20p ft

## R.C.S. 100 watt VALVE AMPLIFIER CHASSIS



Four inputs. Four way mixing. master volume. treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, PA. where high quality power is required. 5 speaker outputs. AC mains operated. Slave output socket. Produced by demand for a quality valve amplifier. 100V line output to order. £10 extra. Send for leaflet. Suitable carrying cab £21. Price £105. Carr £6 00

## GOODMANS TWIN AXIOM 8 inch dual cone loudspeaker 8 ohm, 15 watt hi-fi unit £10.50.

## CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps. £2.20.

## LOUDSPEAKERS PM 3 OHM 7x4in £1.50; 6 1/2in £1.95; 8x5in. £1.90; 8in. £2.50.

## SPECIAL OFFER: 8 ohm, 2 1/2in 2 1/2in 35 ohm, 3in 25 ohm, 2 1/2in 3in 5x3in 7x4in 8 ohm, 2 1/2in 3in 3 1/2in 5in 15 ohm, 3 1/2in dia 6x4in 7x4in 5x3in 3 ohm, 2 1/2in 2 1/2in 3 1/2in 5in dia £1.50 each.

## PHILIPS LOUDSPEAKER, 8in, 4 ohms, 4 watt £2.50.

## RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in diameter 4W £2.50. 10in diameter 5W £3.50; 12in diameter 6W £4.50. 3/8/15 ohms, please state.

## MOTOROLA PIEZO ELECTRIC HORN TWEETER. £6.50

Handles up to 100 watts. No crossover required.

## BLACK PLASTIC CONSTRUCTION BOX with brushed aluminium face. Sturdy job. Size 6 1/4 x 4 1/4 x 2in £1.50

## BAKER 150 WATT PROFESSIONAL MIXER AMPLIFIER



All purpose transistors. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 4/8/16 ohms A.C. Mains. Separate treble and bass controls. Master volume control. 100 volt line model. £85. £1 60 carr.

## BAKER 50 WATT AMPLIFIER



£65 Post £1 60

Superior quality ideal for Halls/PA systems. Disco s and Groups. Two inputs with Mixer Volume Controls. Master Bass. Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets. 4 8 16 ohm AC 240V (120V available). Blue wording on black cabinet.

## GOODMANS RUBBER SURROUND BASS WOOFER

Standard 12in diameter fixing with cut sides 12 x 10 14 000 Gauss magnet. 20 watts RMS. 4 ohm imp. Bass resonance = 30 c/s. Frequency response 30-8000 c/p s. £9.85 each Post £1 60.



## ALUMINIUM HEAT SINKS. FINNED TYPE.

Sizes 5" x 4" x 1" 95p. 6 1/2" x 2 1/2" x 1" 45p.

JACK PLUGS Mono Plastic 25p; Metal 30p.

JACK PLUGS Stereo Plastic 30p; Metal 35p.

JACK SOCKETS Mono Open 20p; Closed 25p.

JACK SOCKETS Stereo Open 25p; Closed 30p.

FREE SOCKETS - Cable end 30p.

2.5mm and 3.5mm JACK SOCKETS 15p.

2.5mm and 3.5mm JACK PLUGS 15p.

DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 10p. Free Sockets 10-pin, 5-pin 25p.

Plugs 3-pin 20p; 5-pin 25p.

PHONO PLUGS and SOCKETS ea. 10p.

Free Socket for cable end ea. 15p.

Screened Phono Plugs ea. 15p.

TV CONVERGENCE POTS 15p each.

Values = 5, 7, 10, 20, 50, 100, 200, 250, 470, 2000 ohms

## MONO PRE-AMPLIFIER. Mains operated solid state pre-amplifier unit designed to complement amplifiers with low level phono and tape input stages. This free-standing cabinet incorporates circuitry for automatic R.I.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Phono sockets for input and output.

£5 Post 50p

# RADIO COMPONENT SPECIALISTS

Radio Books and Components Lists 20p. (Minimum posting charge 30p.) Access or Barclaycard please. Telephone: 01-884 1665 for same day despatch.


## 337 WHITEHORSE ROAD, CROYDON

Open 9-6. Closed all day Wed. Open Sat. 9-5.

Open 9-6. Closed all day Wed. Open Sat. 9-5.

# AITKEN BROS

35, High Bridge, Newcastle upon Tyne  
Tel: 0632 26729

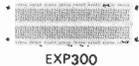

EXP300



PB6 Kit

**EXP300**  
550 contacts with two 50-point BUS bars. Size 152x53mm. **£6-95.**  
**PROTO-BOARD 6 KIT**  
630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. **£10-98.**

## CSC LOGIC PROBES

### LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. **£20-95.**

LP-1 Memory Probe **£36-85**  
LP-3 High Speed Memory Probe **£56-75**

CSC catalogue available. Please send S.A.E.

### CALSCOPE SUPER 6 £186-30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1μs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

### CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

### TE20D TECH R.F. SIGNAL GENERATOR

Accurately covers 120 KCS to 500 MCS in 6 bands. Directly calibrated. Variable RF attenuator 240 VAC. Size 140x215x170mm.

Price **£52-50 (£50-58 to callers).**


### TE22D TECH AUDIO GENERATOR

Sine & square wave audio generator. Sine wave range -20 cps to 20K cps in four bands.

Square wave range 20 cps to 15K cps in four bands 240V A.C. Size 140x215x170mm.


Price **£63-31 (£61-31 to callers).**

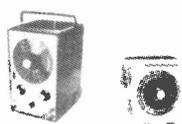**TMK 500 MULTIMETER** 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50μa, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size. 160 x 110 x 55MM. Batteries & leads included.  
**PRICE £25-95.**


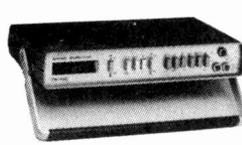
## CSC EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.



**SINCLAIR DM350 £79-95**  
**SINCLAIR DM450 £114-95**

Size 255x148x40mm.  
DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (100μV on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

### Sinclair PFM200 frequency meter

Size 157x76x32mm.  
Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. **£67-95.**

### SINCLAIR PDM35 DIGITAL POCKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £34-95.** AC Adaptor **£3-95** de luxe padded carrying case **£3-50** MN 1604 Battery **£1-28.** Size 157x76x32mm.

### SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER.



DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1μa to 1000MA Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £57-95.** Carrying case **£9-95.** AC adaptor/charger. **£4-50.** Rechargeable Battery Pack. **£9-70.** Size 255x148x40mm.

### PANEL METERS

DIMS 60MM x 45MM. 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, "S", "VU" 50-0-50μa, 100-0-100μa, 500-0-500μa. **PRICE £5-95.**
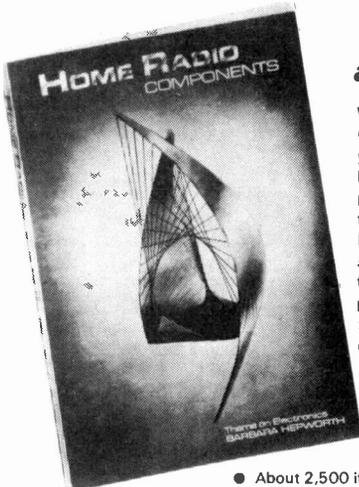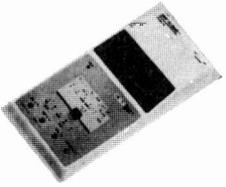
### DESOLDERING TOOL SUCTION PUMP. £6-45

Education Establishment Orders Accepted.  
PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10.  
ALL PRICES INCLUDE POSTAGE AND VAT.



## FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation *second to none* for our catalogue - and for the service that backs it up. Experience both for yourself. Just send £1.30 with the coupon and a catalogue will come by return of post.

### TREAT YOURSELF for XMAS!

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.,

Dept. PE., 234-240 London Road, Mitcham, Surrey CR4 3HD  
Phone 01-648 8422

Please write your Name and Address in block capitals


NAME.....

ADDRESS.....

HOME RADIO (Components) LTD., Dept. PE  
234-240 London Road, Mitcham, Surrey. CR4 3HD (Regn. No London 912966)



## - CLEF KITS -

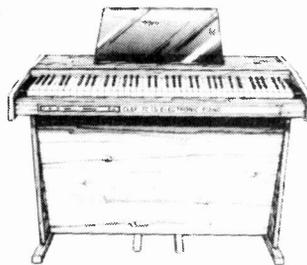

**P.A.'s - SPEAKERS - CABINETS**  
Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

**SUB-KITS**  
Reduce the cash outlay during the building process - details in the lists.

**KEYBOARDS**  
We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyboard hardware including the industry standard soft plated contact springs.

49 NOTE C-C **£23.80**  
73 NOTE F-F **£37.00**  
88 NOTE A-C **£45.00**

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

**NEW KITS**  
This space reserved for December release of Electronic Rotor! (See us at BREADBOARD 79.)

**BUILDING SERVICE**  
We are specialists in Electronic Piano Manufacture and can build your Piano for you - see lists.

**DEMONSTRATION CASSETTES**  
Please specify Ensemble or Piano at £1.50 each for ten minute content. Cost may be deducted from subsequent orders.

**INFORMATION**  
Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & insurance.

**VISITS**  
Are welcome by appointment, otherwise Mail Order Only.

**EXPORT**  
Enquiries welcome - in Australia please contact JAYCAR (Sydney).

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

**JOANNA 72 & 88 PIANOS**  
Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. Build this widely acclaimed professional instrument, for either domestic or Stage use, from our top quality Component Kits.

SIX OCTAVES - £184  
7½ OCTAVES - £208

**P.E. STRING ENSEMBLE**  
The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT - £164

Back up TELEPHONE advice is available from the Designer to supplement the clear instructions included with the above Kits.

## CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. PE) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU.  
061-439 3297

POST THIS COUPON with cheque or P.O. for £1.30



# How to make a hobby.

The opportunities in electronics, today, and for the future are limitless – throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics – especially for the servicing of radio, TV and all associated equipment – can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.

We give modern training courses in all fields of electronics – practical D.I.Y. courses – courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.


All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

# and a career.

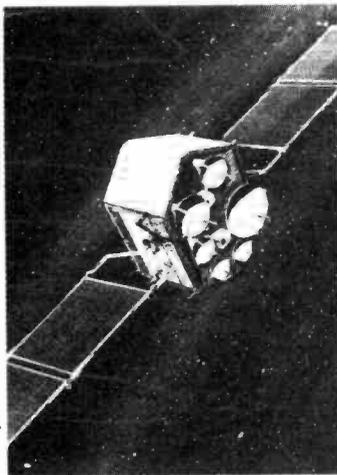
## COURSES AVAILABLE:-

- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page Colour Booklet.

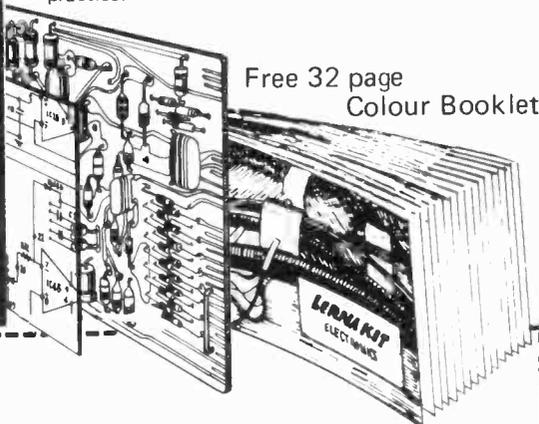

WE ARE AN INTERNATIONAL SCHOOL SPECIALISING IN ELECTRONICS TRAINING ONLY AND HAVE OVER 40 YEARS EXPERIENCE IN THIS SUBJECT.

PE A/1/80

NAME.....  
ADDRESS .....

Block Caps Please

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL**  
P.O. Box 156, Jersey, Channel Islands.

# RST

**VALVE MAIL ORDER CO.**  
 Climax House  
 Fallsbrook Road, London SW16 6ED  
**SPECIAL EXPRESS  
 MAIL ORDER SERVICE**

Ep	Ep	Ep	Ep	Ep	Ep
AA119	0.12	BCY70	0.17	MPSU01	0.41
AA130	0.31	BCY71	0.20	MPSU06	0.53
AA132	0.48	BCY72	0.15	MPSU56	0.56
AA133	0.21	BCZ11	1.72	NE555	0.52
AA135	0.39	BD115	0.52	NK7401	0.50
AA137	0.31	BD121	1.50	NK7403	1.99
AC107	0.69	BD123	1.50	NK7404	1.99
AC125	0.23	BD124	1.50	OA5	1.09
AC126	0.23	BD131	0.40	OA7	0.63
AC127	0.23	BD132	0.44	OA10	0.74
AC128	0.23	BD135	0.39	OA47	0.18
AC141	0.29	BD136	0.39	OA70	0.35
AC141K	0.40	BD137	0.40	OA79	0.35
AC142	0.23	BD138	0.46	OA81	0.36
AC142K	0.36	BD139	0.49	OA85	0.35
AC176	0.23	BD140	0.51	OA90	0.09
AC187	0.23	BD144	2.30	OA91	0.09
AC188	0.23	BD181	1.26	OA93	0.09
AC187	0.98	BD182	1.38	OA200	0.10
AC188	0.92	BD237	0.46	OA202	0.10
AC189	0.86	BD238	0.63	OA211	1.15
AC190	0.86	BD239	1.05	OA220	1.15
AC191	0.86	BD240	2.30	OA201	1.15
AC192	0.86	BD241	1.44	OA205	1.15
AC193	0.86	BD242	0.72	OA206	1.15
AD149	0.52	BF115	0.29	OC16	2.30
AD162	0.52	BF152	0.21	OC20	2.88
AF106	0.52	BF153	0.23	OC22	2.88
AF114	0.86	BF154	0.20	OC23	3.16
AF115	0.86	BF159	0.26	OC24	3.45
AF116	0.86	BF160	0.26	OC25	1.04
AF117	0.86	BF167	0.23	OC26	1.04
AF139	0.46	BF173	0.23	OC28	2.30
AF186	1.38	BF177	0.28	OC29	2.30
AF239	0.52	BF178	0.28	OC35	1.73
AF211	3.16	BF179	0.29	OC36	1.73
AF212	3.16	BF180	0.29	OC41	0.92
AS226	0.46	BF181	0.35	OC42	0.86
AS227	0.46	BF182	0.35	OC43	2.89
AS215	1.44	BF183	0.29	OC44	0.69
AS216	1.44	BF184	0.29	OC45	0.63
AS217	1.44	BF185	0.29	OC71	0.63
AS220	1.72	BF244	0.10	OC72	0.63
AS221	2.30	BF195	0.10	OC73	1.15
AU110	2.30	BF196	0.12	OC74	0.74
AU113	1.96	BF197	0.14	OC75	0.74
AU110	2.30	BF200	0.31	OC76	0.63
BA145	0.18	BF224	0.23	OC77	1.38
BA146	0.18	BF244	0.32	OC81	0.74
BA154	0.10	BF257	0.28	OC81Z	1.38
BA155	0.12	BF258	0.30	OC82	0.74
BA156	0.10	BF259	0.37	OC83	0.74
BAW62	0.06	BF336	0.35	OC84	0.74
BAX13	0.07	BF337	0.35	OC122	1.73
BAX16	0.07	BF338	0.35	OC123	2.02
BC107	0.14	BFS21	4.55	OC139	2.89
BC108	0.14	BFS28	2.86	OC140	3.16
BC109	0.14	BFS51	0.23	OC141	3.74
BC113	0.14	BFS98	0.23	OC170	1.15
BC114	0.14	BFW10	0.74	OC171	1.15
BC115	0.14	BFX11	0.24	OC200	1.73
BC116	0.14	BFX14	0.26	OC201	2.02
BC117	0.20	BFX85	0.26	OC202	2.02
BC118	0.12	BFX87	0.24	OC203	2.02
BC125	0.18	BFX88	0.24	OC204	2.88
BC126	0.23	BFY50	0.30	OC205	2.88
BC135	0.16	BFY51	0.30	OC206	2.88
BC136	0.16	BFY52	0.30	OC207	2.02
BC137	0.17	BFY64	0.30	ORP17	1.44
BC147	0.10	BFY90	1.44	ORP12	0.86
BC148	0.09	BSX119	0.24	R2008B	1.15
BC149	0.10	BSX20	0.23	R2009	2.89
BC157	0.10	BSX21	0.23	R2010B	2.02
BC158	0.10	BT106	1.44	T1C44	0.56
BC159	0.12	BTY79/4	3.67	T1C226D	1.38
BC167	0.14	BU205	2.02	T1L209	0.23
BC170	0.13	BU206	2.59	T1P29A	0.47
BC171	0.12	BU208	2.30	T1P30A	0.48
BC172	0.12	BY100	0.82	T1P31A	0.61
BC173	0.12	BY126	0.38	T1P32A	0.56
BC177	0.17	BY127	0.19	T1P33A	0.79
BC178	0.16	BZK61	0.21	T1P34A	0.84
BC179	0.18	Series	1.15	T1P41A	0.72
BC182	0.13	BZY88	0.15	T1P42A	0.81
BC183	0.12	Series	1.15	T1P2955	0.77
BC184	0.13	Series	1.15	T1P3055	0.84
BC212	0.16	CRS1/40	0.69	T1S43	0.52
BC213	0.14	CRS3/40	0.86	ZS140	0.29
BC214	0.17	CRS3/60	1.04	ZS170	0.24
BC237	0.10	GEX66	1.73	ZS178	0.62
BC238	0.14	GEX541	1.73	ZS271	0.26
BC301	0.38	GJ3M	0.86	ZS278	0.65
BC303	0.38	GSM	0.86	ZTX107	0.13
BC307	0.12	GL7M	0.86	ZTX108	0.12
BC308	0.12	GM0378A	2.02	ZTX109	0.14
BC327	0.23	K100A	0.52	ZTX300	0.14
BC328	0.21	MJE340	0.92	ZTX301	0.15
BC337	0.20	MJE370	0.71	ZTX302	0.17
BC338	0.20	MJE371	0.71	ZTX303	0.20
BCY30	1.15	MJE520	0.60	ZTX304	0.22
BCY31	1.15	MJE521	0.63	ZTX311	0.14
BCY32	1.15	MJE2955	1.44	ZTX314	0.23
BCY33	1.04	MJE3055	0.86	ZTX500	0.15
BCY34	1.04	MPE102	0.35	ZTX501	0.16
BCY39	3.45	MPE103	0.35	ZTX502	0.18
BCY40	1.15	MPE104	0.35	ZTX503	0.20
BCY42	0.29	MPE105	0.35	ZTX504	0.23
BCY43	0.29	MPSA06	0.28	ZTX531	0.23
BCY58	0.18	MPSA56	0.30	ZTX550	0.18

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.  
 Valves, Tubes and Transistors - Closed Saturday  
 Terms C.W.O. only - Tel. 01-677 2424-7  
 Quotations for any types not listed S.A.E.

Prices correct  
 when going  
 to press

Post and Packing 30p per order  
 All prices include VAT Tel: 046708

# MICROSYSTEMS'80

A Conference and Exhibition to help you come to terms with the Second Industrial Revolution



at the WEMBLEY CONFERENCE CENTRE  
**JANUARY 30-FEBRUARY 1** from 9.30 am each day

CONFERENCE SESSIONS enable you to share the experience of experts in the microtechnology field.

A BUYERS' FORUM helps you to establish effective criteria for selection of goods and services.

A PROFESSIONAL DEVELOPMENT SEMINAR introduces managers to the use of microprocessors in business and industry.

AN EXHIBITION where you can talk personally with the suppliers of microtechnology products and services.

Admission to the exhibition is free. You may book in on the spot for conference sessions, or obtain further details of fees and a booking form from:

**MICROSYSTEMS CONFERENCE** Room 821, Dorset House, Stamford Street, London, SE19LU.

## J. Birkett

Radio Component Suppliers

25 The Stait, Lincoln LN2 1JF. Tel: 20767

- PAPER CAPACITORS 10uf 270V A.C.W. 5 1/2 x 2 1/2 x 1 1/2 £1.50.
- VHF-UHF FETS BF 256C @ 4 for 75p, E 304 @ 4 for £1.
- HIGH SPEED CMOS HEF4518BF @ 55p, 5 for £1.
- 50 BC 107-B TRANSISTORS untested for 60p.
- 50. PLASTIC BC 107-B TRANSISTORS untested for 60p.
- 50. PLASTIC PNP TRANSISTORS untested for 60p.
- 50. ASSORTED 2 WATT ZENERS untested @ 80p.
- 50. T05 1 AMP S.C.R.'s untested for £1.
- 25. 5 AMP STUD MOUNTING S.C.R.'s untested @ 75p.
- 10. 20 AMP STUD MOUNTING DIODES untested @ 60p.
- 20. 10 AMP STUD MOUNTING DIODES untested @ 60p.
- 10. ASSORTED PUSH BUTTON BANKS less knobs @ £1.30.
- 1000pf 6 K. V.W. DISC CERAMICS at 6 for 20p.
- POLYESTER CAPACITORS 1uf 63v.w. @ 5p, 4.7uf 63v.w. @ 10p, 10uf 63v.w. @ 15p.
- FETS N CHANNEL 2N 3819 @ 20p, 2N 4092 @ 15p, 2N 4093 @ 15p, 2N 4118A @ 15p, 2N 4302 @ 15p, 2N 4392 @ 15p, 2N 4869A @ 15p, E111 @ 10p, E113 @ 15p, VHF-UHF E300 @ 25p, W309A @ 25p, P CHANNEL Type 3177 @ 20p.
- 300 To 75 ohm BALUM TRANSFORMERS @ 20p each.
- ELECTROLYTIC CAPACITORS 2000uf 450v.w. 5 1/2 x 3" @ £2.25.
- TEXAS BRIDGES 100 PIV 1 amp @ 20p, 200 PIV 4 amp @ 60p.
- TOGGLE SWITCHES 250 volt 10 amp 2 Pole Make @ 50p.
- ELECTROLYTICS 2350 + 2350uf 63v.w., 5000 + 5000uf 25v.w., both @ 75p.
- MULLARD POLYESTER CAPACITORS 1uf 160v.w. @ 20p doz.
- UNIUNIONS 2N 4871 @ 22p, 2N 6028 @ 25p, 2N 6029 @ 25p, MEU 21 @ 22p, M114804 @ 22p, 4JD5E29 @ 22p, TIS 43 Type @ 22p.
- TANTALUM CAPACITORS .1uf 35v.w., .22uf 35v.w., .33uf 35v.w., .47uf 35v.w., 1uf 35v.w., 2.2uf 35v.w., 3.3uf 16v.w., 4.7uf 16v.w., 4.7uf 35v.w., 6.8uf 35v.w., 10uf 10v.w., 10uf 25v.w., 22uf 16v.w., 33uf 10v.w., 33uf 25v.w., all at 25p ea. 100uf 10v.w., 150uf 10v.w., both 25p.
- MOS PRE-AMPLIFIER I.C. TAA 320 with circuits @ 35p.
- MULLARD PRE-AMPLIFIER I.C. TAA 435 with data @ 30p.
- WIRE WOUND POTENTIOMETERS 2 watt type 2K or 10K, 4 watt 5K or 10K. All 25p.
- 3 PIN PLUG AND SOCKETS with 2 metres of cable as fitted to Hi-Fi @ 75p.
- MAINS TRANSFORMERS 240 volt input. Type 1, 24 volt tapped at 14 volt 1 amp @ £1.30 (P&P 25p). Type 2, 30-0-30 volt 500mA @ £1.30 (P&P 25p). Type 3, 45 volt 6 amp @ £4.50 (P&P 95p). Type 4, 20 amp 1 amp Twieem 10 volt 1 amp Twice @ £4.50 (P&P 95p). Type 5, 45 volt 2 amp 45 volt 500mA @ £3.50 (P&P 85p). Type 6, 16 volt 2 amp @ £1.60 (P&P 25p). Type 8, 30 volt 1 amp @ £1.60 (P&P 25p).
- S.C.R.'s 10 amp type 100 PIV @ 28p, 400 PIV @ 55p, 800 PIV @ 65p.
- PARMEKO TRANSFORMER type 5082/1 ratio 1 to 4.2 @ 40p (P&P 15p).
- TRANSFORMER 240 volt input, output 26 volt 332 mA @ 75p (P&P 25p).
- METAL FILM RESISTORS all 0.5% tol. 100, 150, 360, 619, 750, 820, 910, 1K 2.2K, 3.9K, 5.1K, 6.2K, 10K, 18K, 75K, 150K, 200K, 392K, 597K, 600K. All at 6p each.


Please add 20p for post and packing on U.K. orders under £2, unless otherwise stated. Overseas postage charged at cost.

# Electronics
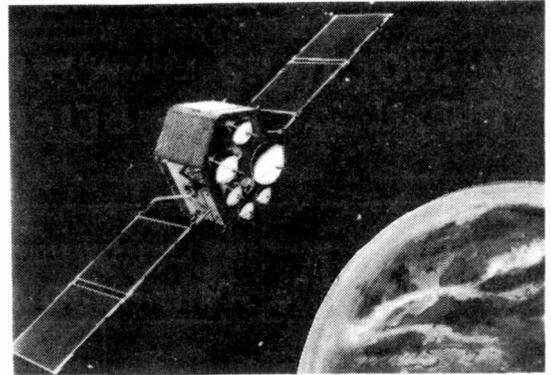
## Make a job~or hobby~of it.....

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market.

We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .



FEB 1/80

Brochure without obligation to.

## British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Block caps please

### MAINS INTERCOM



**NO BATTERIES  
NO WIRES**

**ONLY  
£32.99  
PER PAIR  
+ VAT £4.95**

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/2 mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. £1.25.

### 4-STATION INTERCOM

**£27.95  
+ VAT £4.19**

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs) in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A Battery and other accessories. P. & P. £1.25.

### NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



**£17.95  
+ VAT £2.70  
+ P&P 99p**

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £19.95 + VAT £3.00. P. & P. 99p.

### DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Surface/Mortice reversible latch locks), mains power unit, cable (8-way) 50 ft and wiring diagram. Price £49.95 + VAT £7.50 + P. & P. £1.50. Kit with two Telephones £59.95 + VAT £9.00 + P. & P. £1.75.

10-day price refund guarantee on all items.

WEST LONDON DIRECT SUPPLIES (PE1)  
169 KENSINGTON HIGH STREET, LONDON, W8

KITS Kits include components, printed circuit boards and instructions	SPECIAL OFFERS																														
<table style="width: 100%; border-collapse: collapse;"> <tr><td>Pools predictor (ZA44)</td><td style="text-align: right;">£7.30</td></tr> <tr><td>Clap switch (ZA40)</td><td style="text-align: right;">£5.00</td></tr> <tr><td>Ring Modulator (ZA39)</td><td style="text-align: right;">£6.70</td></tr> <tr><td>Mini Short Wave Receiver (ZA33)</td><td style="text-align: right;">£8.00</td></tr> <tr><td>Ioniser (ZA28)</td><td style="text-align: right;">£9.00</td></tr> <tr><td>Telephone amplifier (ZA26)</td><td style="text-align: right;">£11.00</td></tr> <tr><td>Touch dimmer (ZA21)</td><td style="text-align: right;">£6.50</td></tr> <tr><td>Equaliser (ZA15)</td><td style="text-align: right;">£17.00</td></tr> <tr><td>Parametric equaliser (ZA52)</td><td style="text-align: right;">£25.00</td></tr> <tr><td>Audio analyser (ZA51)</td><td style="text-align: right;">£14.00</td></tr> <tr><td>Automatic battery charger (ZA54)</td><td style="text-align: right;">£17.50</td></tr> <tr><td>VHF/UHF T.V. modulator (ZA1)</td><td style="text-align: right;">£5.50</td></tr> <tr><td>100W amplifier using 2 x LM391 I.C.'s (ZA3)</td><td style="text-align: right;">£15.50</td></tr> <tr><td>Ultrasonic transmitter for headphones (ZA56)</td><td style="text-align: right;">£6.50</td></tr> <tr><td>Ultrasonic receiver for headphones (ZA57)</td><td style="text-align: right;">£8.25</td></tr> </table>	Pools predictor (ZA44)	£7.30	Clap switch (ZA40)	£5.00	Ring Modulator (ZA39)	£6.70	Mini Short Wave Receiver (ZA33)	£8.00	Ioniser (ZA28)	£9.00	Telephone amplifier (ZA26)	£11.00	Touch dimmer (ZA21)	£6.50	Equaliser (ZA15)	£17.00	Parametric equaliser (ZA52)	£25.00	Audio analyser (ZA51)	£14.00	Automatic battery charger (ZA54)	£17.50	VHF/UHF T.V. modulator (ZA1)	£5.50	100W amplifier using 2 x LM391 I.C.'s (ZA3)	£15.50	Ultrasonic transmitter for headphones (ZA56)	£6.50	Ultrasonic receiver for headphones (ZA57)	£8.25	<p>Assorted transistors BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197. 100 for <b>£5.50</b></p> <p>Murata ultrasonic transducers MA40 LIS <b>180p</b> MA40 LIR <b>180p</b> or 320p PR. Data 10p.</p> <p>Reed inserts - 28mm. Normally open gold contacts. 10 for <b>£1.00</b> 100 for <b>£7.50</b></p> <p>5" oscilloscope tubes - SE5J. <b>£15.00</b> (for callers only).</p>
Pools predictor (ZA44)	£7.30																														
Clap switch (ZA40)	£5.00																														
Ring Modulator (ZA39)	£6.70																														
Mini Short Wave Receiver (ZA33)	£8.00																														
Ioniser (ZA28)	£9.00																														
Telephone amplifier (ZA26)	£11.00																														
Touch dimmer (ZA21)	£6.50																														
Equaliser (ZA15)	£17.00																														
Parametric equaliser (ZA52)	£25.00																														
Audio analyser (ZA51)	£14.00																														
Automatic battery charger (ZA54)	£17.50																														
VHF/UHF T.V. modulator (ZA1)	£5.50																														
100W amplifier using 2 x LM391 I.C.'s (ZA3)	£15.50																														
Ultrasonic transmitter for headphones (ZA56)	£6.50																														
Ultrasonic receiver for headphones (ZA57)	£8.25																														
<h3 style="text-align: center;">Assorted Giant Screw Packs Includes</h3> <p>Self tapping, self cutting screws, nuts, bolts, washers, eyelets etc. etc. Weight - 1kg (2.2lb). Approx 1400 items Only <b>£1.80</b> (U.K. only).</p>	<h3 style="text-align: center;">ORDERS -</h3> <p style="text-align: center;"><i>Add 25p post and packing Add 15% VAT to total order Minimum order £1.00. Barclay/Visa/Access cards accepted. Minimum Telephone orders £5.00.</i></p>																														
<h2 style="margin: 0;">T. POWELL,</h2> <p style="margin: 0;"><b>306 St, Pauls Road, Highbury Corner, London N1.</b></p> <p style="margin: 0;">Tel: 01-226 1489</p>																															
<h3 style="margin: 0;">SHOP HOURS</h3> <p style="margin: 0;">Mon-Fri 9-5.30 pm Sat 9-4.30 pm Closed from 22nd Dec to 28th Dec.</p>																															



**All you need for listening!**

Every month

**PRACTICAL HI-FI**

Listen with the complete hi-fi magazine



# Wilmslow Audio

**THE firm for speakers!**

SEND 30p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

AUDAX • AUDIOMASTER • BAKER  
 BOWERS & WILKINS • CASTLE • CELESTION  
 CHARTWELL • COLES • DALESFORD  
 DECCA • EMI • EAGLE • ELAC • FANE  
 GAUSS • GOODMAN'S • I.M.F. • ISOPHON  
 JR. • JORDON WATTS • KEF • LEAK • LOWTHER  
 MCKENZIE • MONITOR AUDIO • PEERLESS  
 RADFORD • RAM • RICHARD ALLAN • SEAS  
 SHACKMAN • STAG • TANGENT • TANNOY  
 VIDEOTONE • WHARFEDALE • YAMAHA

**WILMSLOW AUDIO (Dept. P.E.)**  
 SWAN WORKS, BANK SQUARE, WILMSLOW,  
 CHESHIRE SK9 1HF

Discount HI-FI, etc. at 5 Swan Street

Tel.: Wilmslow 529599 for Speakers

Tel.: Wilmslow 526213 for Hi-Fi

ZENER DIDDIES (400 mW)	2.7V to 33V 8p	NE555 25p	74122 22p	4041 78p	BD132 38p	ZTX501 16p
VERO BOARDS (0.1" Copper)	2.5" x 5" 52p	NE556 60p	74123 40p	4042 58p	BD135 10	ZTX502 21p
3.75" x 5" 62p	MAN72 110p	NE566 140p	74125/6 34p	4043 83p	BD140 35p	ZTX503 17p
LEDs:-	MAN74 110p	TBA641 200p	74132 48p	4044/7 90p	BF180 24p	ZTX504 28p
Red 10p	2N414 100p	TBA800 75p	74141 45p	4048 55p	BF194 10p	ZN696 33p
Green 14p	2N1034 200p	UA710 33p	74142 200p	4049 30p	BF195 10p	ZN697 13p
Yellow 14p	7407 34p	TTL 7400/1 11p	74145 48p	4050 30p	BF196 10p	ZN698 30p
RESISTORS (1/4 Watt E12)	7408 15p	BRIDGE 7402/3 11p	74154 89p	4055 38p	BF197 10p	ZN814 34p
10 ohms 1-5p	7409 14p	RECTIFIERS 7404/5 13p	74155 54p	4066 18p	BF244B 35p	ZN818 38p
to 10 Mohms 1-5p	7410 13p	1A/50V 22p	74156 30p	4069 18p	BF248 35p	ZN1302 38p
PRESETS (horizontal)	7411 17p	1A/400V 34p	74157 52p	4072/3 18p	BF299 32p	ZN1303 60p
100 ohms	7412 15p	2A/50V 40p	74160 64p	4081/2 18p	BF299 32p	ZN1303 60p
to 2 Mohm 8p	7413 27p	2A/400V 55p	74161 50p	4086 66p	BF299 32p	ZN2389 17p
POTENTIAL	7414 48p	DIODES 0A47 8p	74162/3 66p	4086 66p	BF299 32p	ZN2484 30p
OMETERS (carbon)	7415 15p	0A91 8p	74164 66p	4086 66p	BF299 32p	ZN2484 30p
1 Mohm to 2 Mohm	7416/7 25p	0A202 9p	74165 45p	4086 66p	BF299 32p	ZN2484 30p
CERAMIC CAP (50V)	7417 21p	1N4148 4p	74166 85p	4086 66p	BF299 32p	ZN2484 30p
22pF to 50nF 2p	7418 16p	1N916 5p	74167 70p	4086 66p	BF299 32p	ZN2484 30p
POLYSTYRENE CAP (E12 50V)	7419 17p	1N4002 4p	74170 50p	4086 66p	BF299 32p	ZN2484 30p
10pF to 1nF 5p	7420 13p	1N4004 6p	74171 53p	4086 66p	BF299 32p	ZN2484 30p
POLYESTER CAP (E12 100V)	7421 21p	1N5400 13p	74172 53p	4086 66p	BF299 32p	ZN2484 30p
1nF to 1uF 5p	7422 16p	1N5404 16p	74173 70p	4086 66p	BF299 32p	ZN2484 30p
15, 22, 33 6p	7423 30p	VOLTAGE REGULATORS 7440 10p	74174 50p	4086 66p	BF299 32p	ZN2484 30p
47, 68 10p	7424 43p	7441 5p	74175 60p	4086 66p	BF299 32p	ZN2484 30p
1-0uF 12p	7425 25p	7442 43p	74176 60p	4086 66p	BF299 32p	ZN2484 30p
2-2uF 20p	7426 28p	7443 35p	74177 53p	4086 66p	BF299 32p	ZN2484 30p
3-0uF 24p	7427 18p	7444 78p	74178 53p	4086 66p	BF299 32p	ZN2484 30p
4-7uF 28p	7428 18p	7445 60p	74179 70p	4086 66p	BF299 32p	ZN2484 30p
ELECTROLYTIC CAP (25V)	7429 18p	7446 65p	74180 50p	4086 66p	BF299 32p	ZN2484 30p
1uF to 50uF 8p	7430 30p	7447 53p	74181 99p	4086 66p	BF299 32p	ZN2484 30p
68uF, 100uF 6p	7431 15p	7448 82p	74182 30p	4086 66p	BF299 32p	ZN2484 30p
150uF 9p	7432 18p	7449 10p	74183 30p	4086 66p	BF299 32p	ZN2484 30p
220uF 10p	7433 30p	7450 10p	74184 66p	4086 66p	BF299 32p	ZN2484 30p
500uF 13p	7434 30p	7451 10p	74185 45p	4086 66p	BF299 32p	ZN2484 30p
1,000uF 20p	7435 30p	7452 10p	74186 85p	4086 66p	BF299 32p	ZN2484 30p
DIL SOCKETS	7436 30p	7453 10p	74187 70p	4086 66p	BF299 32p	ZN2484 30p
8 pin 11p	7437 30p	7454 10p	74188 50p	4086 66p	BF299 32p	ZN2484 30p
14 pin 13p	7438 30p	7455 10p	74189 64p	4086 66p	BF299 32p	ZN2484 30p
18 pin 14p	7439 30p	7456 10p	74190 75p	4086 66p	BF299 32p	ZN2484 30p
18 pin 18p	7440 30p	7457 10p	74191 70p	4086 66p	BF299 32p	ZN2484 30p
22 pin 22p	7441 5p	7458 22p	74192 50p	4086 66p	BF299 32p	ZN2484 30p
24 pin 24p	7442 43p	7459 32p	74193 64p	4086 66p	BF299 32p	ZN2484 30p
28 pin 28p	7443 35p	7460 12p	74194 80p	4086 66p	BF299 32p	ZN2484 30p
40 pin 40p	7444 78p	7461 22p	74195 85p	4086 66p	BF299 32p	ZN2484 30p
	7445 60p	7462 28p	74196 80p	4086 66p	BF299 32p	ZN2484 30p
	7446 65p	7463 30p	74197 40p	4086 66p	BF299 32p	ZN2484 30p
	7447 53p	7464 24p	74198 60p	4086 66p	BF299 32p	ZN2484 30p
	7448 82p	7465 10p	74199 80p	4086 66p	BF299 32p	ZN2484 30p
	7449 10p	7466 12p		4086 66p	BF299 32p	ZN2484 30p
	7450 10p	7467 17p		4086 66p	BF299 32p	ZN2484 30p
	7451 10p	7468 25p		4086 66p	BF299 32p	ZN2484 30p
	7452 10p	7469 32p		4086 66p	BF299 32p	ZN2484 30p
	7453 10p	7470 17p		4086 66p	BF299 32p	ZN2484 30p
	7454 10p	7471 21p		4086 66p	BF299 32p	ZN2484 30p
	7455 10p	7472 21p		4086 66p	BF299 32p	ZN2484 30p
	7456 10p	7473/4 24p		4086 66p	BF299 32p	ZN2484 30p
	7457 10p	7475 30p		4086 66p	BF299 32p	ZN2484 30p
	7458 22p	7476 28p		4086 66p	BF299 32p	ZN2484 30p
	7459 32p	7477 28p		4086 66p	BF299 32p	ZN2484 30p
	7460 12p	7478 28p		4086 66p	BF299 32p	ZN2484 30p
	7461 22p	7479 28p		4086 66p	BF299 32p	ZN2484 30p
	7462 28p	7480 25p		4086 66p	BF299 32p	ZN2484 30p
	7463 30p	7481 25p		4086 66p	BF299 32p	ZN2484 30p
	7464 24p	7482 17p		4086 66p	BF299 32p	ZN2484 30p
	7465 10p	7483 32p		4086 66p	BF299 32p	ZN2484 30p
	7466 12p	7484 24p		4086 66p	BF299 32p	ZN2484 30p
	7467 17p	7485 22p		4086 66p	BF299 32p	ZN2484 30p
	7468 25p	7486 22p		4086 66p	BF299 32p	ZN2484 30p
	7469 32p	7487 22p		4086 66p	BF299 32p	ZN2484 30p
	7470 17p	7488 22p		4086 66p	BF299 32p	ZN2484 30p
	7471 21p	7489 32p		4086 66p	BF299 32p	ZN2484 30p
	7472 21p	7490 32p		4086 66p	BF299 32p	ZN2484 30p
	7473/4 24p	7491 28p		4086 66p	BF299 32p	ZN2484 30p
	7475 30p	7492 17p		4086 66p	BF299 32p	ZN2484 30p
	7476 28p	7493 32p		4086 66p	BF299 32p	ZN2484 30p
	7477 28p	7494 30p		4086 66p	BF299 32p	ZN2484 30p
	7478 28p	7495 30p		4086 66p	BF299 32p	ZN2484 30p
	7479 28p	7496 42p		4086 66p	BF299 32p	ZN2484 30p
	7480 25p	7497 42p		4086 66p	BF299 32p	ZN2484 30p
	7481 25p	7498 42p		4086 66p	BF299 32p	ZN2484 30p
	7482 17p	7499 42p		4086 66p	BF299 32p	ZN2484 30p
	7483 32p	7500 42p		4086 66p	BF299 32p	ZN2484 30p
	7484 24p	7501 42p		4086 66p	BF299 32p	ZN2484 30p
	7485 22p	7502 42p		4086 66p	BF299 32p	ZN2484 30p
	7486 22p	7503 42p		4086 66p	BF299 32p	ZN2484 30p
	7487 22p	7504 42p		4086 66p	BF299 32p	ZN2484 30p
	7488 22p	7505 42p		4086 66p	BF299 32p	ZN2484 30p
	7489 32p	7506 42p		4086 66p	BF299 32p	ZN2484 30p
	7490 32p	7507 42p		4086 66p	BF299 32p	ZN2484 30p
	7491 28p	7508 42p		4086 66p	BF299 32p	ZN2484 30p
	7492 17p	7509 42p		4086 66p	BF299 32p	ZN2484 30p
	7493 32p	7510 48p		4086 66p	BF299 32p	ZN2484 30p
	7494 30p	7511 48p		4086 66p	BF299 32p	ZN2484 30p
	7495 30p	7512 28p		4086 66p	BF299 32p	ZN2484 30p
	7496 42p			4086 66p	BF299 32p	ZN2484 30p
	7497 42p			4086 66p	BF299 32p	ZN2484 30p
	7498 42p			4086 66p	BF299 32p	ZN2484 30p
	7499 42p			4086 66p	BF299 32p	ZN2484 30p
	7500 42p			4086 66p	BF299 32p	ZN2484 30p
	7501 42p			4086 66p	BF299 32p	ZN2484 30p
	7502 42p			4086 66p	BF299 32p	ZN2484 30p
	7503 42p			4086 66p	BF299 32p	ZN2484 30p
	7504 42p			4086 66p	BF299 32p	ZN2484 30p
	7505 42p			4086 66p	BF299 32p	ZN2484 30p
	7506 42p			4086 66p	BF299 32p	ZN2484 30p
	7507 42p			4086 66p	BF299 32p	ZN2484 30p
	7508 42p			4086 66p	BF299 32p	ZN2484 30p
	7509 42p			4086 66p	BF299 32p	ZN2484 30p
	7510 48p			4086 66p	BF299 32p	ZN2484 30p
	7511 48p			4086 66p	BF299 32p	ZN2484 30p
	7512 28p			4086 66p	BF299 32p	ZN2484 30p
	7513 42p			4086 66p	BF299 32p	ZN2484 30p
	7514 42p			4086 66p	BF299 32p	ZN2484 30p
	7515 42p			4086 66p	BF299 32p	ZN2484 30p
	7516 42p			4086 66p	BF299 32p	ZN2484 30p
	7517 42p			4086 66p	BF299 32p	ZN2484 30p
	7518 42p			4086 66p	BF299 32p	ZN2484 30p
	7519 42p			4086 66p	BF299 32p	ZN2484 30p
	7520 42p			4086 66p	BF299 32p	ZN2484 30p
	7521 42p			4086 66p	BF299 32p	ZN2484 30p
	7522 42p			4086 66p	BF299 32p	ZN2484 30p
	7523 42p			4086		

## BUILD A SYNTHESISER!

**NO SPECIAL SKILLS REQUIRED  
SPECIAL EQUIPMENT**



Using **Dewtron** (Reg'd)  
**PROFESSIONAL MODULES**

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!


**D.E.W. LTD.**

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR
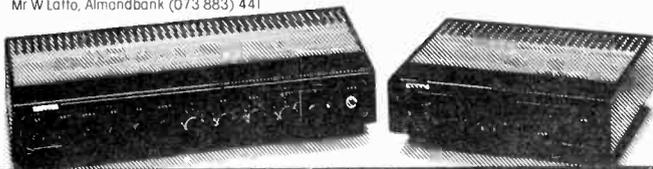
## McLAREN AUDIO BY POST AT DISCOUNT PRICES.


20w per channel Amplifier only **£52.95** Post Free

McLaren, Scotland's leading audio manufacturer, offer a fully guaranteed 20w per channel stereo amplifier direct from the factory for just **£52.95 post free**. Features base, treble, volume balance controls and push button selectors for P/U, Radio, Auxiliary, Tape, Mono, Hi-filter and On/Off. Harmonic distortion better than 0.05% at -3dB of full rated output. Superb black finish with wood surround. Send cheque or P.O. to **GR International Electronics, Almondbank, Perthshire PH1 3NQ**. Goods sent by security delivery within 21 days of receipt. Full money back guarantee if not satisfied. For further information or details of cassette players, 8 tracks, matched record deck or speakers, write or phone Mr W Lallo, Almondbank (073 883) 441


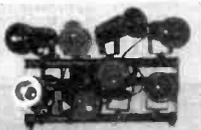
## SUPER SPOT DISCO SYSTEM 2

- ★ Fully enclosed drive unit ★ 8A triacs ★ Fused ★ Suppressed
- ★ Expandable using slave units connected via 9 way socket
- ★ Stand takes 16 Spots ★ Regd. Design
- ★ 450 watt/channel ★ Sequence, auto or audio drive
- ★ Fully adjustable ★ Fully isolated audio input and output sockets ★



	Built & tested	Kit	Slave	Slave kit
3 Ch. 3 Spots	<b>£64.95</b>	<b>£48.95</b>	<b>£39.95</b>	<b>£37.95</b>
3 Ch. 6 Spots	<b>£78.95</b>	<b>£63.95</b>	<b>£59.95</b>	<b>£56.95</b>
4 Ch. 4 Spots	<b>£75.95</b>	<b>£59.95</b>	<b>£54.95</b>	<b>£41.95</b>
4 Ch. 8 Spots	<b>£89.95</b>	<b>£75.95</b>	<b>£67.95</b>	<b>£62.95</b>
4 Ch. 16 Spots	<b>£117.95</b>	<b>£102.95</b>	<b>£95.95</b>	<b>£90.95</b>

Price includes: Spot stand, Swivel spot holders, Coloured spot lamps, Sequence drive, or slave unit, Fitting kit for ceiling hung & surface or wall mounting V.A.T. Post & Packing and Guarantee.

**NOBLE ELECTRONICS (PW)**  
26 Lloyd Street, Altrincham, Cheshire WA14 2DE.  
Tel: 061-941 4510

Trade enquiries welcome

# TRAIN FOR SUCCESS

**in Radio, Television & Electronics**

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

### Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

### City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

### Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical engineering, Installations & Contracting

### Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE BOOK**

Post this coupon or 'phone today for free ICS careers guide.

Name \_\_\_\_\_


Address \_\_\_\_\_

Age \_\_\_\_\_

**ICS**

To ICS, Dept. Q273, Intertext House,  
London SW8 4UJ  
or telephone 01-622 9911 (all hours)

### SUPERSOUND 13 HI-FI MONO AMPLIFIER

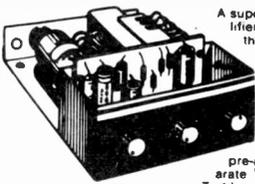

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep AC 200/250V

PRICE £18.40 P. & P. £1.20.

### HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminum front escutcheon. For AC mains operation 200/240 volts. Size approx 12 1/2in wide x 5in high x 7 1/2in deep. Special introductory price £29.00 + £2.50 carriage and packing.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2in x 14 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £8.90 each + P. & P. (one 90p, two £1.10). Now available in 8in round version. 10 watts R.M.S. 60Hz-20kHz £6.30 + P. & P. (one 65p, two 75p.).

### MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200.240V Mains operated Solid State F M A M Stereo Tuner Covering M W A M 540-1605kHz V H F F M 88-108MHz Built-in Ferrite rod aerial for M W Full AFC and AGC on A M and F M Stereo Beacon Lamp Indicator Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV R M S into 20k. Simulated Teak 4in high x 9in deep approx.

Limited number only at £29.00 + £1.50 P. & P.

**STEREO MAGNETIC PRE-AMP** Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ.  $\pm$  1dB from 20Hz to 20kHz. Input impedance 47k. Size 1 1/2in x 2 1/2in x 1 1/2in H. £3.20 + 20p. P. & P. Mullard LP1159 RF-IF module 470 kHz. £2.50 + P. & P. 20p. Full specification and connection details supplied. Five VHF FM Tuner Head covering 88-108 MHz 10.7 MHz i.f. output. 7.8V + earth. Supplied pre-aligned, with full circuit diagram with precision-ganged F.M. gang and 323PF + 323PF A.M. Tuning gang only £3.40 + P. & P. 35p.

### 10/14 WATT HI-FI AMPLIFIER KIT

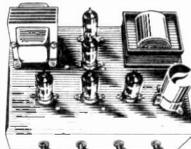

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15W speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 60p + S.A.E. (Free with parts). All parts sold separately. ONLY £18.40 P. & P. £1.40. Also available ready built and tested £22.50 P. & P. £1.40.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS esp. 54 in. wide. Our price £2.30 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design. All parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminum front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification, Power output 14 watts R M S per channel into 5 ohms. Frequency response  $\pm$  30dB 12-30,000Hz. Sensitivity better than 80mV into 1 M $\Omega$ . Full power bandwidth  $\pm$  3dB 12-15,000Hz. Bass boost approx to  $\pm$  12dB. Treble cut approx to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A. Overall size 12in wide x 8in deep x 2 1/2in high.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S A E

AMPLIFIER KIT (Magnetic input components 33p extra) £14.95 P & P 80p

POWER PACK KIT £6.20 P & P 95p

CABINET £6.20 P & P 95p

SPECIAL OFFER—only £25.80 if all 3 items ordered at one time plus £1.25 P. & P.

Full after sales service Also available ready built and tested £32.20 P & P £1 50

### HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec. play socket are mounted on the printed circuit panel. Size approx 9 1/2in x 2 1/2in x 1in max depth. Supplied brand new and tested with knobs, brushed anodised aluminum 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10.40 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £2.15 + 40p P. & P. If required. Full connection details supplied.

### STEREO DECODER

SIZE 2" x 3" x 1" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £8.20 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice.

## HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 MERTON HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station


(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.
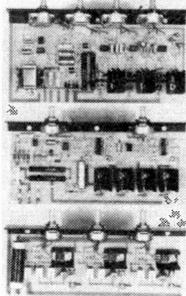
## LIGHTING & AMPLIFIER MODULES FROM L&B

JUST LOOK AT THESE PRICES!

SUPERIOR HIGH QUALITY LIGHTING CONTROL MODULES. ALL 1000 WATTS PER CHANNEL NO POWER SUPPLIES NEEDED. ALL READY TO GO!



#### — LB310008L —

3 channel Sound-Light. Zero switching, high sensitivity & input impedance. Excellent Separation. Excellent for disco's. £18.90

#### — LB410008L —

4 channel sequencer. Suedo-random with two speed controls. Disco/band lighting effects. £14.90

#### — LB310008LD —

3 channel lamp dimmer. Control from full off to full on. ideal for stage lighting. £12.90

#### NEW.

#### — LB110008LD —

Super tiny single channel lamp dimmer. For stage lighting. £5.70

#### — LB310008LC —

All the advantages of the 310008L, active filters & automatic chasing in the absence of a music input. £28.90

#### — LB810008LC —

8 channel chase. Chase rate & return speed controls. Optional foot switch trigger/trig o/p for module cascading. A breakthrough in modular technology. £25.50

#### PREAMPLIFIERS

LBPA1 Stereo disc/tape £14.50

LBPA2. 4 channel gen. purpose mixer £13.50

LBPA3. Stereo disc with mic. £27.00



#### — LB25 —

25W. RMS 4Q 10Hz-50kHz T.H.D. 0.1% 90dB S/N £8.20

#### POWER SUPPLIES

LB25PS.....£10.00

LB100PS.....£12.20

LB250PS.....£21.20

#### — LB250 —

250W R.M.S. 4Q 10Hz-20kHz T.H.D. 0.3% 110dB S/N £29.50

#### — LB100 —

100W R.M.S. 4Q 10Hz-25kHz T.H.D. 0.4% 80dB S/N £15.70

All prices include VAT. Add 50p p/packing. Quantity/trade and overseas inquiries welcome. For further information send a SAE to:

**L&B**

ELECTRONICS

45 WORTLEY ROAD, W. CROYDON SURREY CR0 3EB. TEL: 01-689 4138

## Codespeed Electronics

PO BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, PO3 5BJ  
ELECTRONIC MAIL ORDER SPECIALISTS  
New, Full Spec. Devices

LED WRISTWATCH I.C. Super value I.C. in 24 pin 'legless flatpack' style package for maximum space saving. With data. A snap at only 99p Cat. no. 208.

0.1" LED WRISTWATCH DISPLAY. Also in a 'legless flatpack' style package, this display matches the wristwatch I.C. shown above. With data. Only 99p Cat. No. 209. \* CASH SAVER \* Purchase one each of catalogue numbers 208 AND 209 for only £1.80.

POLARIZING FILTER MATERIAL 0.006" thick plastic film. Any size cut - even 1 sq. inch. Max. width 19", any length. Only 2p per sq. inch. Cat. No. 701.

BRIGHT ORANGE DISPLAY 9 digit, 7 segment gas discharge display. 0.25" high digits. With data 75p. Cat. No. 310.

DMM CHIP MMS330 dvm chip. Builds into high accuracy dvm or panel meter. Requires additional circuitry. Supplied with data and circuit. Only £3.95. Cat. No. 404.

MINI 6 DIGIT LED DISPLAY 6 digit 7 segment display from Texas. Common anode, multiplexed, with 0.1" digits. £1.00. Cat. No. 306.

MMS314 CLOCK CHIP. A super value digital clock chip for only £1.99. With data. Cat. No. 207.

4 DIGIT LCD. A high contrast, easy to solder display with four 0.5" high non-multiplexed digits. £8.95 each with data. Cat. No. 206.

DIGITAL ALARM CLOCK MODULE. Complete with giant 0.84" LED display. Add transformer and switches for complete clock. With data only £8.50. Cat. No. 205.

GIANT LED DISPLAY. Common cathode, non-multiplexed super 4 digit LED clock display. Lots of other uses too. Only £3.95 each. Cat. No. 204.

WRISTWATCH LCD'S. A high contrast 3 1/2 digit wristwatch LCD with centre colon. Supplied with polarizers and data. Only £1.00. Cat. No. 202.

MEMORIES. MM2102 static 1024 bit memories. A snap at 99p each. With data sheet. Cat. No. 102.

20 KEY KEYBOARDS. Calculator keyboards, excellent key action, 20 keys per board. 2 keyboards for £1.00. Cat. No. 101.

10 HYBRID CIRCUITS. 8 resistors and 8 capacitors built into each hybrid circuit. Ideal values for semiconductor circuits. Excellent for minimizing PCB component space. 10 Hybrids for 60p. Cat. No. 801.

25 germanium diodes 500 10 switching diodes 35p. Mini slider switches (2 pole change-over) 18p each. Momentary switches (spring loaded) with 1 n.c. contact 15p each. Mono jack sockets 23p each. Stereo jack sockets 25p each. Slide control knobs (state colour) 12p each. Rotary control knobs (push-on). Black with coloured cap (state colour) 20p each.

#### Untested Items

REJECT CALCULATORS. Production line rejects. Yields lots of goodies when stripped down (not much wrong with some we tested). Only £2.80 each. Cat. No. 104.

LED DISPLAYS. (Untested - no guarantees) 10 seven segment LED displays. 0.127" digits common cathode. 10 for £1.00. Cat. No. 311.

Postage and Packing please add 35p. (Overseas orders add 90p)

Satisfaction guaranteed or return for replacement or refund.

Send medium sized S.A.E. for your free copy of our new Autumn Catalogue (Issue No. 6).

Codespeed's Design, Development and Production teams are also at your service for quantity/batch production.

# THE NEXT STEP FORWARD IN TIME

CASIO MEANS DIGITAL – New Lithium batteries lasting up to 5 years or more, totally eclipse most SOLAR watches

**FOR THE EXECUTIVE WHO DOESN'T WANT HANDS ON HIS TIME**

★ **THIS YEAR'S STAR BUY** ★

## THE NEW 83QS – 27B ALARM CHRONOGRAPH

Optional display of hours, minutes, seconds, date, am/pm; or alternatively: Hours, minutes, alpha day, date, am/pm. The automatic calendar is set for 28 days in February. Casio's new Lithium battery lasts up to 4 YEARS or more. The chronograph times in 1/10 second units up to 12 hours, measuring net, lap and first and second place times. An indicator shows the chronograph is running when normal time is displayed. The 24 hour alarm can be set very easily to 1 minute intervals with an indicator to show the alarm is set. In addition the watch can be set to chime every hour, on the hour, with a separate indicator to show this function is on. A micro light illuminates the display at night time. This superb watch is stainless steel encased, has a mineral glass face and is guaranteed water resistant to 66 feet (2 at).



RRP £31.95 **£27.95**

## COMPUTER GAMES

**Fairchild Grandstand** (Microprocessor). Video Entertainment Computer. (Special offer) **£69.50**  
**UFO Master Blaster Station**. Guide missiles to destroy UFO's. Score against the clock. **£22.50**  
**Grandstand 4-in-1**. Calculator/Auto Race/Code Breaker (as Mastermind)/Blackjack. **£22.50**  
**Grandstand Adam**. Tune Memory/Pathfinder/Ditto (as Simon Says)/Bounce. **£22.50**  
**Amaze-A-Tron**. Over 1 million mazes. 8 games. 1 or 2 players. Electronic sound effects. **£17.25**  
**Grandstand Solitaire**. Absorbing. **£14.95**

## CASIO CALCULATORS

**AQ-2000**. Clock, calendar, 2 alarms, stopwatch, time memory, countdown alarm. **£24.95**  
**MQ-11**. Micro version of above. **£26.95**  
**CQ-82**. Clock. 4 alarms, snooze, light. **£19.95**  
**HQ-21**. Quartz clock and calculator. **£10.95**  
**Scientifics with non-volatile memory**  
**FX-310** (8 digits) 50 sci functions. **£17.95**  
**FX-510** (10 digits) 50 sci functions. **£19.95**  
**FX-2600** (8) 43 sci funct. Ultra slim **£19.95**  
**FX-3200** (10) 43 sci funct. Ultra slim **£21.95**  
 Others: **FX-80** £15.95. **FX-68** £19.95

**Non-volatile Programmables**  
**FX-501P** £54.95 **FX-502P** £74.95  
**FA-1** Adaptor/Cassette interface 19.95

**There is no present like the time**

## CASIO LADIES WATCHES

Superbly styled stainless steel cases, with mineral glass face, water resistant to 100 feet, LC display of hours, minutes, 10 seconds, seconds by flash, am/pm; and with day, date and month.



86QL-10B  
**£26.50**

86QL-12B  
**£31.95**

26CGL-20L  
Gold plated  
**£53.25**

## SUPER VALUE CHRISTMAS PRESENT

**HQ-21** 6 digit clock and calculator with full memory, %. Two AA batteries last 1 year.  $\frac{1}{2} \times 3 \times 5\frac{1}{2}$  inches. **ONLY £10.95**

You cannot fight against the future  
Time is on our side. *W. E. Gladstone*

## 81CS-36B

LC Display of hours, minutes, seconds, day; And with day, date, month and year calendar pre-programmed to 2029.

## 4-5 YEAR BATTERY

1/100 second chronograph to 7 hours.

Net, lap and first & 2nd place times.

User optional 12 or 24 hour display.

24 hour alarm.

User optional hourly chime.

Backlight.

Mineral glass.

Stainless steel case.

Water resistant to

100ft (3 at.)

RRP £39.95 **£35.95**



WE ARE NEVER KNOWINGLY UNDERSOLD AND WILL TRY AND MATCH OR BEAT ANY OTHER ADVERTISED PRICE PROVIDING THE ADVERTISER HAS STOCKS

IF YOU WANT A WATCH WITH

Chrome plating that may wear off after a few months. A plastic glass that will scratch and scuff and you may not be able to replace.

A module with around 25% failure rate, that may take weeks to repair.

A dubious or non-existent spares service.

If you want a watch that the manufacturer doesn't put his name on

THEN DON'T BUY A CASIO

## GET THE MIDAS TOUCH BEFORE YOUR FRIENDS DO

### SUPERSWITCH Midas Touch Dimmer

The softest touch on the brushed aluminium panel of this beautifully styled control is all that is required to switch lights on and off and to vary lighting brilliance.

Touch Midas with the fingertips and the light is on. Touch again and it's off. Allow the finger to rest on the panel and the light intensity changes smoothly through a cycle from bright to dim and back again. Removing the touch during the cycle sets the lighting at the level required. Once set, this brightness level will be maintained during normal on/off operations.

Meets latest BS for R.F. interference.

**£14.95**

## CASIO CHRONOGRAPHS

Constant display of hours, minutes, seconds, am/pm and day (12 or 24 hour) Dual time (12 or 24 hour). Automatic day, date, month, year calendar pre-programmed to 2029. Chronograph measures net, lap and 1st and 2nd place times from 1/100 second to 7 hours. Backlight. Mineral glass face. Guaranteed water resistant to 66 or 100 feet.

## NEW MODEL 95QS-32B

4 YEAR BATTERY Superbly styled brass case heavily chrome plated.

Water resistant to 66 feet.

(RRP £27.95)

**£23.95**



## 95QS-31B

(Left)

4 YEAR BATTERY S/S jacket. W.R. to 66 feet.

(£27.95)

**£23.95**



## 95CS-31B

(Right)

5 YEAR BATTERY Solid S/S case. W.R. to 100 feet.

(£34.95) **£29.95**

Time never stands still with Casio

## F-200 SPORTS CHRONO

Hours, minutes, seconds am/pm. Day, date, month, 1/100 sec.

chrono to 1 hour. Net, lap and 1st and 2nd place times. Backlight.

Resin case/strap. Mineral glass, W.R. to 66 feet. Silver oxide battery.

(£17.95) **£15.95**



## F-8C time/date 3 YEAR BATTERY

Hours, minutes, seconds, date, day, am/pm. Auto 28, 30, 31 day calendar. Backlight. Resin case/strap. Mineral glass. W.R. to 66 feet.

(£12.95) **£10.95**

NB. This watch does not have a stopwatch.



Most CASIO products available from stock. Send 25p for illustrated brochures and membership of our CHRISTMAS CLUB. EXTRA DISCOUNTS on many items.

Price includes VAT, P&P. Send your cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:-

# TEMPUS

Dept. PE, Beaumont Centre, 164-167 East Rd., Cambridge CB1 1DB. Tel. 0223 312866



## RECEIVERS AND COMPONENTS

**SURPLUS** stocks of Electronic Components at less than wholesale prices. SAE brings free lists. Bardwell Ltd., 212 Studley Lane, Dronfield-Woodhouse, Sheffield, S18 5YP.

**BRAND NEW PCB's**, slightly imperfect due to error in Silk Screen Printing, various sizes and layout plus a few very large boards with components. Please send SAE. Portbuild Ltd., 57 Amberwood Rise, New Malden, Surrey.

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
 0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.  
 22 & 47—5p. (50V—6p). 100—7p. (50V—8p).  
 220—8p. (50V—10p). 470—11p. (40V—10p).  
 1000/15V—15p. 1000/25V—18p. 1000/40V—35p.  
**Subminiature bead tantalum electrolytics.**  
 0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.  
 2.2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.  
 22/16V, 33/10V, 47/6V, 68/3V & 100/3V—30p.  
 15/25V, 22/25V, 47/10V—35p. 47/16V—60p.  
**Subminiature Ceramic Caps. E12 Series 100V.**  
 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.  
 10% 330 pf. to 4700 pf.—4p.  
**Vertical Mounting Ceramic Plate Caps. 50V.**  
 E12 22 pf. to 1000 pf. E8 1500 pf. to 47000 pf.—2p.  
**Polystyrene E12 Series 63V, Horizontal Mtg.**  
 10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.  
**Miniature Polyester 250V Vert. Mtg. E8 Series.**  
 .01 to .068—4p. .1—5p. 15, 22—6p. 33, 47—10p.  
 .68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.  
**Mylar (Polyester) Film 100V Vertical Mounting.**  
 .001, .002, .005—3p. .01, .02—4p. .04, .05—5p.  
**Miniature Film Resistors Highestab. E12 Ser. 5%.**  
 0.125W mixed carbon/metal 100 to 1MΩ—1p.  
 0.25W Carbon 1Ω to 10MΩ (10% over 1MΩ)—1p.  
 (E24 Series as in 3W C. Film 1Ω to 5MΩ).  
 0.25W, 0.5W & 1.0W Metal Film 100 to 2MΩ—2p.  
 1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.  
 6C107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—10p.  
 8 Pin I.C.s. 741 Op. amp.—18p. 555 Timer—24p.  
 DIL Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.  
 LED's. 3 & 5mm. Red—10p. Green & Yellow—14p.  
 Grommets for 3mm.—11p. 2 pce. holders 5mm.—21p.  
 20mm. Q.B. Fuses .15, .25, .5, 1, 2, 3 & 5A—3p.  
 20mm. Anti Surge 100mA. to 5.0A—8p.  
 20mm. Fuseholders P.C. or Chassis Mtg.—5p.  
 Solid A.I. knobs 15mm.—25p. 25mm.—35p. 30mm.—50p.  
 400mW Zener diodes E24 series 2V7 to 33V—8p.  
 Prices VAT Inclusive Post 10p. (Free over £4).

**THE C. R. SUPPLY CO.**

127, Chesterfield Rd., Sheffield S8 0RN.

**100 7400 SERIES IC + 100 Diodes** 4148 type. Marked and Unmarked. Untested. 100 + 100 £1.50. STE Ltd., Uni-Com Building, Edenbridge, Kent. TN8 6EW.

**COMPONENTS AT SILLY PRICES.** 1000 mixed resistors £3.60. SAE Lists. W.V.E.3, Craigo Farm, Tintern, Gwent.

**TUNBRIDGE WELLS COMPONENTS,** Ballard's, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquires S.A.E.

P.C.B.s Paxolin 10 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ " 4-£1.30. 12" x 9 $\frac{1}{2}$ " 85p. 18" x 11 $\frac{1}{2}$ " £1.40. D.S. 10" x 8 $\frac{1}{2}$ " 85p. Fibre Glas 12" x 8" £1.70. D.S. 10 $\frac{1}{2}$ " x 7" £1.35. 8" x 7" £1.15. Unit with 8 silicon diodes 600V 20 amp, 8 SCR's 400V 18 amp, 6 Vinkors, W.W. resistors etc. £6.75. 300 small components, trans. diodes £1.55. 7 lbs. assorted components £3.75. List 15p refundable. Post 20p. Insurance add 15p.

### J.W.B. RADIO

2 Bamfield Crescent, Sale, Cheshire M33 1NL

**100 ASSORTED COMPONENTS** 115p, 100 Resistors assorted  $\frac{1}{4}$ W 75p, 10 Mains Neons 50p, 20 Micro-switches 150p, 50 Reed switches 200p, 50 assorted capacitors 150p, add 25p P.&P. Durrants, 9 St. Marys Street, Shrewsbury, Salop.

**200 mixed components** £4. Sole Electronics, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

**T & J ELECTRONIC COMPONENTS** - Quality Components - sensible prices. Same day service. Send a stamped addressed envelope for full list. 98 Burrow Road, Chigwell, Essex. IG7 4HB.

# SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

**VHF CONVERTOR,** 45-220MHz 29-30MHz IF. Ideal feed HF receiver. £6.80, SAE details, lists other items. H. Cocks, Bre Cottage, Staplecross, Robertsbridge, Sussex. Tel: 058083-317.

## CUT PRICE COMPONENTS

SL610C RF Amp £2.40, SL613C limiting Amp £2.70. SL640C D.B. modulator £3.00. SL680C crystal osc. maintaining circuit £1.50.  
 74154 TTL £0.80.  
 78M06 6 volt regulator £0.70.  
 XR4136CP quad 741 14 pin DIL £0.70.  
 CA3080AS op. transconductance amp. 8 pin TO5 £0.80.  
 SN72709DN op. amp (709) 14 pin DIL £0.20.  
 CMOS: 4016 £0.25, 4047 £0.80.  
 VP5 5 volt DC-DC converter £6.00.  
 Cermet pots  $\frac{3}{4}$ " square 10K (top adjust) £1.50, 20K (side adjust) £1.50.  
 AX121B-4 14 pin DIL relay 10 watts, 5 volt nominal coil voltage £1.12.  
 For orders less than £5 please add 25p P.&P.  
 Send to:

**WIRRAL SEMICONDUCTORS,**  
 177 Brookdale Ave.,  
 Greasby, Wirral, Merseyside L49 1SR.

**TURN YOUR SURPLUS** Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

## BOOKS AND PUBLICATIONS

**WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS.** A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated Manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED,** as the Manual covers in 13 Chapters, where to obtain all the work you need, materials required, all instructions rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4.00 plus 30p P. & P. UK CWO, to INDUSTRIAL SUPPLIES, 102 Parrswood Rd., Withington, Manchester 20, Dept. PE.

**ROMANIAN ELECTROGRAPHY,** tobiscopes, electrokinesis, biogravity, hallucinophotography, dermoptics, psychotronic generators, Kirlianography. SAE 4"x9": PARALAB, Downton, Wills.

## TTL DESIGN CONSIDERATIONS

A booklet packed with information on TTL circuit building. Debouncing, decoupling, fan out, floating, buffers, open collector gates, regulators, race hazards, clocking, sinking, ground planes, cascading, simple interfacing, and much more. If you use TTL this has got to be helpful - well illustrated. 75p inclusive of P.&P. etc.

**PAWBOOKS,**  
 117 Blenheim Road, Deal, Kent.

**ANY REQUESTED SERVICE SHEET** £1 + Large S.A.E. Full repair data any named TV £5.30 (with circuits, layouts etc. £7). SAE brings newsletter, bargain offers, etc. AUSPEL, 76 Church St, Larkhall, Lanarks ML9 1HE.

## SERVICE SHEETS

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, Tv, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

**SERVICE SHEETS** from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

## NOTICE TO READERS

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.*

## BUSINESS OPPORTUNITIES

**IN VIEW OF** current Government moves towards free enterprise in the sale of telephones and their installation we may be presented with the largest instant growth industry opportunity of the decade. We are the largest reproduction telephone manufacturers and importers in the U.K. We wish to grasp these opportunities. You are interested in handling sales and/or installation of a wide variety of decorative telephones. You wish to grasp these opportunities. Please write for details, enclosing 2x10p stamps for a brochure of our telephones if required, and enclosing relevant details about yourself which will be held in strict confidence. **CONVERSATION PIECES,** 55 Swindon Road, Cheltenham, Glos. Cheltenham 35707.

## RECORD ACCESSORIES

**STYLII** Cartridges for MUSIC CENTRES, &c. **FREE** List No.29 for S.A.E. includes Leads, Mikes, Phones &c. **FELSTEAD ELECTRONICS,** (PE), Longley Lane, Gatley, Cheshire, Ches. SK8 4EE.

## AERIALS

## AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.

B45-UHF TV, B11-VHF Radio. B11A-2 metre radio. For next to the set fitting.

**Price £6.** S.A.E. for leaflets. **ACCESS**

**ELECTRONIC MAILORDER LTD,**  
 62 Bridge Street,  
 Ramsbottom, Bury, Lancs, BLO 9AG.

## ACCESSORIES

**INSTRUMENT CASE** Steel with  $\frac{1}{4}$ " Alum. Heat sink moulded front panels 9 items C.K.D. £1.50 P.P. C.W.O. Tenxex Ltd., Stock Road, Industrial Estate, Southend 68608.

## FOR SALE

**MK14 MICROCOMPUTER,** working, with P.S.U., Keyboard, and Tape interface. £45. 0704-34085.

**HEATHKIT 'IM-36'** Transistor - Tested, scarcely used. (Not Home-Built). £35. AVO Model '8' MK V. As New, £60. 051-355 2833.

**MK14** with P.E. Cassette interface, extra RAM, Auxilliary Keyboard, loudspeaker £35. 0934-832025. (Weston-S-Mare).

**ISSUE 2 MK14,** Cassette interface, no power supply, £24. Hinds, 109 Summerland Lane, Newton, Swansea.

**COMPUKIT UK101** in full working order with extra 4K R.A.M. £355 O.N.O. Tel: 01-675 0855.

**NEW BACK ISSUES** of "Practical Electronics" available 70p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

## EDUCATIONAL

# TELEVISION & VIDEO SYSTEMS SERVICING

**18 MONTHS full-time Diploma course to include a high percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES TELETEXT
- COMPUTER & MICROPROCESSORS

Shortened courses for applicants with suitable electronics background.

Next session starts January 7th.

(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

## LONDON ELECTRONICS COLLEGE

Dept. PEA1, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Q272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Q272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Q272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### MISCELLANEOUS

**NORTHERN IRELAND.** Build your own Computer. Nascom-1 Microcomputer kits. From P&O Computers (N.I.). 81 Dublin Road, Belfast, BT2 7HF. Tel: 22010. Evenings. Donaghmore 312 Belfast 621706.

## P.C. BOARDS FOR INDUSTRY 'and' THE AMATEUR

- \* One off or production runs
- \* Assembly of P.C.Bs or kits
- \* Expert hand soldering
- \* Design service if required
- \* Artwork & Photography

**SEAHORSE ELECTRONICS LTD.**  
Unit 2 Picow Farm Road  
Service Industry Estate,  
Runcorn, Cheshire.  
(09285) 7595

**CLEARING LABORATORY.** Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.



### RYDER ORGAN SYSTEM (Wireless World)

A classical design with full-size keyboards. Couplers, capture, etc., can be included.

Cassette. p.c. boards, data, from:  
**HIKON LTD. (P),**  
Woodside Croft, Ladybridge Lane,  
Bolton BL1 5ED.

### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state **Transmitter-Receiver Kit**. Only £10.70 plus 25p P. & P. 'Brain-Freeze' 'em with a **MINI-STROBE** Electronics Kit, pocket-sized 'lightning flashes', variable, for discos and parties. A mere £4.50 plus 25p P. & P. Experiment with a psychedelic **DREAM** I.A.B. or pick up faint speech/sounds with the **BIG EAR** sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P. **LOTS MORE!** Send 25p for lists. Prices include VAT.

### BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh Ewell, Surrey (P.E.)

**SUPERB INSTRUMENT CASES BY BAZELLI**, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. **BAZELLI** (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton-caster, LA 6LT.

### MAKE YOUR OWN PRINTED CIRCUITS

**Etch Resist Transfers**—Starter pack (5 sheets, lines, pads, I.C. pads) £1.60. Large range of single sheets in stock at 34p per sheet.

**Ferric Chloride**—1 lb bags 80p (P&P 50p)\*  
**Master Positive Transparencies** from P.C. layouts in magazines by simple photographic process. Full instructions supplied, 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.30.

S.A.E. lists and information. P&P 25p/order except\*

**P.K.G. ELECTRONICS**  
OAK LODGE, TANSLEY, DERBYSHIRE

**SOLAR CELLS**, Batteries, Panels, Thermoelectric Generators, heat pipes, books etc., Details: Edenscombe Ltd., 34 Nathans Road, N. Wembley, Middx. HA0 3RX.

### PRACTICAL ELECTRONICS P.C.B.'s

Professional quality glassfibre, Fry's roller tinned and drilled.  
May 79 Auto ranging multimeter. Set of 5 pcb's £8.27  
Aug. 79 Door chime EG140/3. Set of 2 pcb's £1.98  
Sept. 79 Waveform generator EG161 £1.58  
Input channel amp EP155. Set of 5 pcb's £5.61  
Digital temp controller EC9 £1.90  
Nov. 79 Diatomic EC10 £2.28  
Digital dark room timer EG199 £1.55  
Dec. 79 Ultrasonic burglar alarm EP200 EG126. Set of 2 pcb's £2.06  
Cost a call EP216 £1.38  
Car solid state EG192, 205, 208, 211 & EA46  
Set of 5 pcb's £4.45. Individual pcb's 96p  
For full list and current pcb's please send SAE. Pcb's also produced to customers own masters. Trade enquiries welcome. Please write for quote. CWO Please.  
Postage—Please add 25p postage and packing to complete order.

### PROTO DESIGN

14 Downham Road, Ramadon Heath  
Billericay, Essex CM11 1PU  
Telephone 0268-710722

## MSF CLOCK

**NEW.** Shows continuous Date, Hours, Minutes, Seconds, 8 digit LED—larger digits for Hours and Minutes, also parallel BCD output, auto-reset after power failure, auto GMT/BST and leap year, only 5x8x15cm, built-in 60KHz antenna, 1000Km range, all parts, case, printed circuit, instructions, postage etc. money back assurance, send £48.80 for the RIGHT TIME—NOW.

**CAMBRIDGE KITS**  
45 (FA) Old School Lane, Milton, Cambridge.

**ULTRASONIC TRANSDUCERS.** £2.85 per pair + 25p P&P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

### P.C.B.'s FROM P.E. DESIGNS.

in high quality glass fibre drilled & tinned April 79 Phaser 90p. May 79 Sound op Switch 84p.  
Autoringing Multimeter set £5.60.  
August 79 Chimesonic set of 2 £1.70.  
Sept 79 Smooth Fuzz 70p. Waveform Generator £1.20.  
October 79 VLF Receiver Set £1.80.  
Digital temp controller £2.00 mixer £1.00.  
For latest prices ring (0254) 73755. Quotations for P.C.B.'s from customers artworks send SAE, to  
**P. A., W. K., & I. YATES.**  
22 Ambleside Drive, Darwen, Lancs. BB3 3BG.  
Terms CWO. 25p P&P on orders less than £10.

## BOOST YOUR CAR RADIO WITH THIS ASTONISHING HIGH GAIN ELECTRONIC AERIAL



For every car owner who wants the best in radio reception in fringe areas, along streets walled by high rise buildings, where there are hills, mountains. Highly sensitive car antenna with built-in amplifier suitable to receive AM/FM/SW/LW signals. Adjusts any angle fore and aft. Non-glare construction with staff in black coated brass.

**IDEAL FOR ROOF MOUNTING OR ELSEWHERE**

It's really terrific and very well made. ONLY £8.35 POST PAID.

**STARPARTS (PE1)**

Wynnstay Road, Colwyn Bay, North Wales

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer—now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass Board approx. 1mm thick £1.70 sq. ft. Post/packing 60p. **WHITE HOUSE ELECTRONICS**, P.O. Box 19, Castle Drive, Penzance, Cornwall.

### CABINET FITTINGS

FOR

**Stage Loudspeakers and Amplifier Cabs**  
Fretcloths, Coverings, Strop & Recess Handles, Feet, Costors, Jocks & Sockets, Cannons, Bulgin 8 ways, Reverb Troys, Locks & Hinges, Corners, Trim, Speaker Bolts etc.  
Send 2 x 9p Stamps for samples and illustrated catalogue

**ADAM HALL (P.E. SUPPLIES)**

Unit 3, Carlton Court, Grainger Road  
Southend-on-Sea, Essex.

**SEEN MY CAT?** 5000 Odds and ends. Mechanical. Electrical. Cat. free. Whiston Dept. PRE. New Mills, Stockport.

### USE A REAL KEYBOARD

**BRAND NEW, BUILT & TESTED. PROFESSIONAL QUALITY.**

60 KEYS INCLUDING CURSOR CONTROL. STEPPED ROWS, TYPEWRITER STYLE. AUTO REPEAT. UC + LC ASCII CODED.

£44.75 (£53.19 inc. p. & p. and VAT).

**S.A.E. for details.**

**TIMEDATA Ltd.**

57 Swallowdale, Basildon, Essex.

HIGH QUALITY  
PCB's

From your own artwork master negative or positive maximum 12" x 12"  
Manufactured in glass fibre tinned and drilled  
Express service for prototypes and small production runs  
Small contract circuit boards assembled  
Gold plating for reliability where edge connectors are used  
**ANODISED SELF ADHESIVE FASCIA PANELS WITH LEADS**

Manufactured from your own artwork master  
Various colours available brushed and satin finish  
Express service and competitive prices  
Send artwork or phone for prices  
125W 5% C.F. Resistors E12 Series 1p each  
IN4148 Diodes 2p each  
Ecoscope Instruments Ltd.,  
Clyde Workshops, Fullarton Road, Glasgow G32  
041 641 7863

**THE SCIENTIFIC WIRE COMPANY**  
PO Box 30, London E.4  
Reg. Office 22 Coningsby Gardens.

**ENAMELLED COPPER WIRE**

SWG	1 lb	8 oz	4 oz	Zoz
10 to 19	2.83	1.55	.80	.64
20 to 29	3.03	1.76	1.00	.75
30 to 34	3.25	1.86	1.07	.80
35 to 40	3.60	2.08	1.22	.89
41 to 43	4.84	2.71	2.07	1.38
44 to 46	5.37	3.25	2.29	1.80
47	8.37	5.32	3.19	1.91
48 to 49	15.96	9.58	6.38	3.51

**SILVER PLATED COPPER WIRE**

14, 16, 18	4.30	2.39	1.53	1.00
20 & 22	5.32	3.03	1.85	1.13
24 & 26	6.06	3.57	2.13	1.30
28 & 30	7.00	4.10	2.50	1.53

Fluxcore 60/40 Solder 22 swg 65 ft 90p  
18 swg 22 ft 80p  
Tinned Copper Wire .6 mm 23 swg 1 lb £4.00 10 lbs £20  
Wire Wrapping Wire 30 awg 82 ft £1.10  
Wire Wrapping Tool & 4 Reels £6.00

**CABLES**

			Per Meter
2 WAY	13/2 mm	2.5 amp	13p
2 WAY	16/2 mm	2.5 amp	16p
3 WAY	24/2 mm	6 amp	24p
3 WAY	32/2 mm	10 amp	32p
3 WAY	14/2 mm	2.5 amp	16p
4 WAY	14/1 mm	.75 amp	30p
4 WAY	7/2 mm	1.4 amp	30p
6 WAY	14/2 mm	2.5 amp	45p
10 WAY	7/2 mm	1.4 amp	60p
1 CORE	7/2 mm	Screened	12p
2 CORE	7/2 mm	Each Screened	16p
2 CORE	7/2 mm	Screened	14p
4 CORE	7/2 mm	Screened	30p
LO LOSS	Co-Axial		25p

Prices include P & P and VAT. Dealer enquiries welcome.  
Orders under £2 please add 20p.

**NICKEL CADMIUM BATTERIES**

Rechargeable and suitable for fast charge HP7 (AA) £1.05  
SUB C £1.36, HP11 (C) £1.98, HP2 (D) £3.02, PP3 £3.79,  
PP3 charger £5.40.

All the above nickel cadmium batteries are brand new and are guaranteed full spec. devices. All cells are supplied complete with solder tags (except PP3). Brand new full spec. RECHARGEABLE SEALED LEAD ACID maintenance free batteries suitable for burglar alarms etc. 1.2 amp hr. 6V £4.07. 2.6 amp hr. 6V £5.23.

Quantity prices available on request. Data and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type). Please add 10% P&P in orders under £10 - 5% over £10. VAT at the current rate should be added to total order. Cheques, Postal Orders. Mail order to:-

**SOLID STATE SECURITY DEPT (PE), 10 Bradshaw Lane, Parbold, Wigan, Lancs. Tel: 02575 4726.**

**I.C. EXPERIMENTER'S KITS**

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, L.E.D.s, and Instructions. Available at £5.00 each (including P. & P.)

Kit One -Gates Kit Two-Flip-Flops  
Kit Three-Shift Registers  
Kit Four-Counters Kit Five-Displays

S.A.E for further details to:

**AUTOMATED HOMES**

69 High Street, Ryton, Coventry, CV8 3FJ.  
(Mail Order).

**MORSE CODE TUITION AIDS**

Cassette A: 1-12 w.p.m. for amateur radio examination.  
Cassette B: 12-24 w.p.m. for professional examination preparation. Each cassette are type C30.  
Morse Key and Buzzer unit for sending practice.  
Prices each cassette (including booklets) £4.75. Morse Key and Buzzer £4.75.  
Prices include postage etc., Overseas Airmail £1.50 extra.

**MHEL ELECTRONICS (Dept. PE)**  
12 Longshore Way, Milton,  
Plymouth PL4 8LS.

**GUITAR/PA/  
MUSIC AMPLIFIERS**

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable at £44; 80 watt £37; 200 watt £89; 100 watt twin channel sep. treble/bass per channel £58; 80 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt £32; 200 watt £50; fuzz boxes, great sound £8.50; bass fuzz £9.50; over-driver fuzz with treble and bass boosters £18.50; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £90; twin channel £100; bass combo £100; speakers 15in. 100 watt £35; 12in. 100 watt £23; 60 watt £15.00; microphones Shure Unidyne 8 £28.

Send cheque or P.O. to:

**WILLIAMSON AMPLIFICATION**  
62 Thorncliffe Avenue, Dukinfield, Cheshire.  
Tel: 061-344 5007 or 061-308 2064

**NEW QUALITY KITS FROM DENMARK**

Easy-to-build, sure-fire kits with full English instructions  
Latest IC circuit designs

JK01 AF Amp	£6.75	JK06 27MHz Xtal TX	£9.85
JK02 Mic Amp	£6.75	JK07 Tone Decoder	£9.85
JK03 Sig. Gen	£9.85	JK08 Triac Control	£6.95
JK04 FM Tuner	£9.95	JK09 Birdie Bleeper	£5.95
JK05 27MHz Xtal RX	£10.50	HF61 Beginners radio	£6.50

Prices include VAT

Add 50p for post and packing

Stocks limited due to world-wide demand

ORDER NOW

SAE for FREE Kit Guide

Full money back guarantee

Mail order

**TECHNOCENTRE LTD**

54 Accott Road  
Middlesbrough TS5 7ES

PLEASE  
MENTION  
PRACTICAL  
ELECTRONICS  
When replying  
to  
Advertisements

**QUALITY ELECTRONIC COMPONENTS AT LOW PRICES**

Write or telephone for free pamphlet to:

**HARRISON BROS.**

Dept. P.E. Box 55, Westcliff-on-Sea,  
Essex SS0 7LQ.  
Telephone: Southend-on-Sea 32338

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Practical Electronics for .....

insertions. I enclose Cheque/P.O. for £ .....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME .....

ADDRESS .....

.....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager

**PRACTICAL ELECTRONICS**

GMG, Classified Advertisements Dept., Room 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5846

Rate:

20p per word, minimum 12 words. Box No. 60p extra.

# POSITRON COMPUTERS LTD

## 6800 SPECIALIST SUPPLIERS

MC 6800 Microprocessing Unit	£6.95
MC 6802 MPU + 128 Bytes RAM + Clock	£10.95
MC 6810 128 x 8 Static RAM	£3.50
MC 6821 Peripheral Interface Adaptor	£4.40
MC 6850 Asynchronous Communications Interface Adaptor	£4.40
MC 6852 Synchronous Serial Data Adaptor	£4.90
MC 68A00 1.5 MHz Microprocessing Unit	£9.90
MC 68B00 2.0 MHz Microprocessing Unit	£10.90
MK 4118 1024 x 8 Static RAM 250ns	£23.95

### MOTOROLA 6800 D2 EVALUATION KIT

This highly professional kit is an excellent introduction to the 6800 system, for the beginner. The kit comes complete with a detailed assembly guide, description of circuit operation, programming examples, and book of data sheets for the 6800 family devices. Requires only a 5V power supply. **£179**


Prices include Post and Packing. Please add VAT at 15%

Cheques or P.O. with order to Dept. MC (PE), Positron Computers Ltd., 39 Wigan Rd., Ashton-in-Makerfield, Nr. Wigan, Lancs. WN4 9AR.

PLEASE  
MENTION  
**PRACTICAL  
ELECTRONICS**  
WHEN REPLYING TO  
ADVERTISEMENTS

## MORE SCOPE FOR YOUR MONEY

### ELMAC 4810 4" CRT 5MHz SCOPE

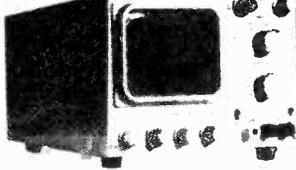


#### AS RECOMMENDED BY ELECTRONICS TODAY INTERNATIONAL SPECIFICATIONS

**ELECTRICAL DATA VERTICAL AXIS (Y) Deflection** Sensitivity — 100mV/division Bandwidth (between 3 dB points) — DC — 5MHz Input Attenuator — (calibrated) — 9 step 0.1 0.2 0.5 1 2 5 10 20 50/div Input impedance — 1 Meg 40 pF inshunt Input Voltage — Max — 600V P.P. **HORIZONTAL AXIS(X) Deflection Sensitivity** — 0.400mV/division Bandwidth (between 3 dB points) — 1Hz 350KHz Gain Control — Continuous when time bases in EXT position Input impedance — 1 Meg Input Voltage — Max — 500V P.P. **TIME BASE Sweep Range (calibrated)** — 100msec/div to 1µsec/div in 5 steps **FINE Control** — Variable between steps — includes time-base calibration position Blanking — Internal on all ranges

**SYNCHRONISATION Selection** — Internal external Synchronisation Level — Continues from positive to negative **POWER SUPPLY** Input voltage — 115 200V AC — 10% at 50 60Hz Power Dissipation — 18W **CRT DATA** — 4in — flat face single beam — Maximum high voltage — 1.5kV — Fitted with 8x10 division blue filter graticule **PHYSICAL DATA** Dimensions — 15cm(h) x 20.5cm(w) x 28cm(d) Weight — 4.3Kg (approx) Stand — 2 position flat and inclined Case — Steel epoxy enamelled Front panel — Aluminium enamelled epoxy printing

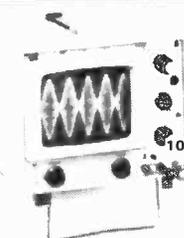**Cash with order Test leads available £2.00. £120 (+£16.35 VAT) Barclay and Access SINCLAIR MINISCOPE SC110 @ £159.85**

SAE for Brochure. Open from Mon-Fri. Closed Sat. Open Sun by appoint.



**RADAT 3106C 5" CRT 10MHz SCOPE**  
SAE for further details

#### As recommended by Practical Wireless

**SPECIFICATION**  
Display: 8 x 10cm with 1cm graticule squares  
Tube: 130BE P31  
EHT: 1.6kV

**VERTICAL AMPLIFIER**  
Sensitivity: 10mV/cm to 50mV/cm in 12 steps  
Bandwidth: 10MHz — 3dB  
Risetime: 55ns  
Input Impedance: 1MΩ and 30pF  
Input: 400V max

**HORIZONTAL AMPLIFIER**  
Sensitivity: 720mV/cm to 50V/cm  
Bandwidth: DC to 1.5MHz — 3dB  
X-Y Phase Shift: 5 d.c. to 50kHz

**TIMEBASE**  
Range: 0.5µs/cm  
Magnifier: x5 (100ns/cm fastest sweep speed)  
Calibration: 5%  
Vermer: 12.1 continuous

**Trigger Sensitivity:** 1cm deflection 10Hz to 8MHz  
**Power Supplies:** 100 to 135V and 200 to 265V 48.440Hz 15W

**Dimensions:** 182 x 200 x 405mm 4.5kg  
**Accessories:** Main test prods and leads Hand book

**Price: £189.96 inc 15% VAT and carriage**  
**Probes: x 1 £8.50 x 10 £10.50**

Please send me Radat 3106C 10MHz Scope  
I We enclose Elmac 4810 5MHz Scope

Please send me details of 5MHz + 6MHz, 10MHz, 15MHz 5" CRT scopes YES NO  
Name \_\_\_\_\_  
Address \_\_\_\_\_

KRAMER & CO., 9 OCTOBER PLACE, LONDON, N.W.4. Tel: 01-203 2473

# INDEX TO ADVERTISERS

Adam Hall (P.E. Supplies) 93	Fladar .....	78	Positron Computers .....	95
Aitken Bros. .... 84			Powell T. .... 87	
A.J.D. Supplies .... 9	Gear T.V. Audio Centre .....	54	Progressive Radio .....	74
Alcon Instruments .... 12	George, David Sales .....	6	Proto Design .....	93
Astra Pak .....	G.R. International .....	89		
Aura Sounds .....			Radio Components	
Automated Homes .....			Specialists .....	83
	Hameg .....	16	R.S.T. Valve Mail Order .....	86
Barrie Electronics .....	Harrison Bros. .... 94		Radio & T.V.	
Bib Hi-Fi Accessories .....	Harversons .....	90	Components .....	Cover III
Bi-Pak .....	Hiykon Ltd. .... 93		Romane Electronics .....	46
Bi-Pre-Pak .....	Home Radio .....	84		
Birkett J. .... 86			Saxon Entertainments .....	5
Boffin Projects .....	I.C.S. Intertext .....	89, 93	Science of Cambridge .....	45
British National Radio & Electronics School .....	I.L.P. Electronics .....	72, 73	Scientific Wire Co. .... 94	
Butterworths .....			Seahorse Electronics .....	93
	Jayen Developments .....	54	Sentinel Supply .....	78
Cambridge Kits .....	Jones Electronic Supplies .....	74	Solid State Security .....	94
Cambridge Learning .....	J.W.B. Radio .....	92	Squires, Roger .....	6
Chromasonic Electronics .....			Star Parts .....	93
Clef Products .....	Kam Circuits .....	12	Stevensons Electronic	
Codespeed .....	Kramer & Co. .... 95		Components .....	67
Computer Components (Teletype) .....			Strutt Electrical .....	82
Crimson Elektrik .....	L & B Electronics .....	90	Swanley Electronics .....	82
Crofton Electronics .....	London Electronics College .....	93		
C.R. Supply Co. .... 92	Maplin Electronics .....	Cover IV	Tandy .....	7
	Marshall A. .... 16		T.K. Electronics .....	74
	Metac .....	10, 11	Technomatic .....	96
	Mhel Electronics .....	94	Tempus .....	91
Davian Electronics .....	Microdigital .....	68	Transam Components .....	75
Delta Tech .....	Microsystems .....	86	T.U.A.C. .... 13	
Design Engineering .....	Modern Book Co. .... 95			
Doram Electronics .....			Vero .....	3
Dziubas .....	Newbear .....	53	Videotime .....	79
	Noble Electronics .....	89		
			Watford Electronics .....	2, 3
Ecoscope Instruments Ltd. .... 93			West London Direct Supplies .....	87
E.D.A. .... 12			Wicca Electronics .....	54
Electroni-Kit .....	P.A.W.K. & I. Yates .....	93	Williamson Amplification .....	94
Electronic Mail Order Ltd. .... 92	Pawbrooks .....	92	Wilmslow Audio .....	88
Electrovalue .....	Phonosonics .....	8, 9	Wirral Semiconductors .....	92

## MICROELECTRONICS

**Digital & Analog Circuits & Systems**  
by J. Millman Price: **£7.80**

**SILICON CHIPS & YOU**  
by C. D. Renmore Price: **£2.90**

**INTEGRATED CIRCUITS HOW TO MAKE THEM WORK**  
by R. H. Warring Price: **£4.45**

**DIGITAL INTEGRATED CIRCUITS & COMPUTERS**  
by B. Woollard Price: **£3.75**

**BEGINNER'S GUIDE TO HOME COMPUTERS**  
by M. Grosswirth Price: **£3.00**

**CB BIBLE. THE COMPLETE GUIDE TO CITIZENS BAND 2-WAY RADIO**  
by P. Bibb Price: **£4.25**

**ELECTRONIC FAULT DIAGNOSIS**  
by G. C. Loveday Price: **£3.60**

**PROJECTS IN RADIO & ELECTRONICS**  
by I. R. Sinclair Price: **£2.60**

**CLOSED CIRCUIT T.V. FOR TECHNICIANS VOL. I**  
by K. J. Bohman Price: **£5.10**

★ ALL PRICES INCLUDE POSTAGE ★

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

**19-21 PRAED STREET LONDON W2 1NP**

Phone 01-402 9176

Closed Saturday 1 p.m.





### 20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS. 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/2" x 3" x 10" approx. **NEW** feature—units now include a built-in four channel stereo sound facility.

**£31.90**  
p&p £3.00

### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV but with 30x30 output 60x60 watts peak. For use with 4 to 15 ohm speakers.



**£31.50** p&p £3.00


### SPECIAL OFFER

**30 x 30 WATT AMPLIFIER KIT** with BSR P200 belt drive deck and Shure M75 cartridge.

**£57.00**  
+ p&p £6.00
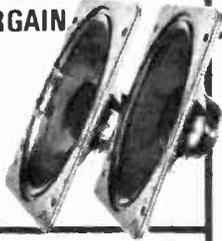
### EMI SPEAKER BARGAIN

Stereo pair 350 hr. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 kHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.



**£18.25** per stereo pair  
£3.65 p&p

### BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device.

**£25.50** p&p £2.60

A D C QLM 30 Mk III Magnetic Cartridge to suit

**£7.95**



**BSR** Manual single play record deck with auto return and cueing level. Fitted with stereo ceramic cartridge. 2 speeds with 45 / 33 rpm spindle adaptor ideally suited for home or disco use.

**OUR PRICE £11.25** p&p £2.75

### GARRARD DECK MODEL CC 10A


Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

**£8.15** p&p £2.05 Size 12" x 8 1/2"
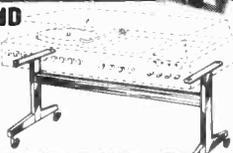
### UNIT AUDIO STAND

Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors.

**£3.95** £2.25 p&p 24" x 12 1/2" x 11 1/2" approx.



**BARGAIN FOR PERSONAL SHOPPERS ONLY**  
**Altone UA4 Stereo System**

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones.

complete with speakers. **£35.75**

### Micro Cassette Recorder

Pocket size—home or office use or when travelling.

**£14.25**

### Battery operated fluorescent camping lamp.

Runs off 8 U2 batteries.

**£4.80**

# Mullard

## AUDIO MODULES IN BARGAIN PACKS


CURRENT CATALOGUE  
PRICE **£25** AT OVER  
PER PACK

### SEE OUR PRICES

**1** PACK 1 2 x LP1173 10w RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.  
**OUR PRICE p+p £1.00** **£5.00**

**2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.

**illus. OUR PRICE p+p £1.00** **£7.65**

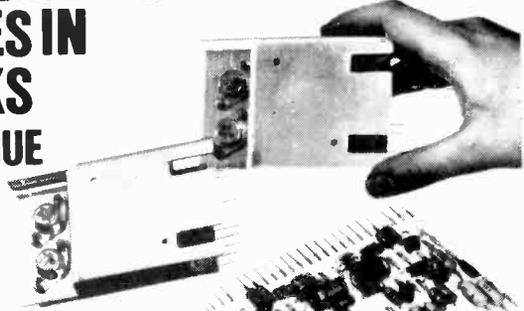

### ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance.

**£3.00** plus £1.50 p&p

Two Way Speaker Kit

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid range tweeter with two cross-over capacitors.


**£4.05**

per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT
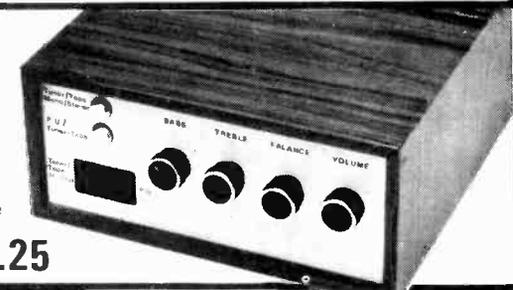
### 10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire and an easily assembled wrap around cabinet to house the finished unit.



Size approximately 9 1/4" x 8 1/4" x 4" p&p £2.25 **£12.25**

### BARGAINS FOR PERSONAL SHOPPERS

LCD Solar 5 function with backlite stainless steel finish case and strap **£7.40**

LCD Solar Chrono 9 function with backlite stainless steel finish case and strap **£9.55**

Chrono stop watch 9 function with back lite stainless steel finish case and strap **£8.95**

Solar Alarm LCD stainless steel case and strap **£21.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£12.20**

100 Watt Power Amp Module **£14.25**

Mains power supply for above unit **£3.60**

DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc crossovers **£20.45**

VIDEOMASTER Super Score TV Game with pistol mains operation **£15.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW MW SW VHF mains/battery operation **£42.90**

ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop **£24.50**

### 100 WATT MONO DISCO AMP

Size approx 14" x 4" x 10" Brushed aluminium fascia and rotary controls.

Five vertical slide controls: master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2 or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

p&p £4.05 **£66.45**

### 50 WATT MONO DISCO AMP

**£30.60** p&p £2.70

Size approx 13 1/2" x 5 1/4" x 6 3/4" 50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

### BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00.

**OUR PRICE £11.95**

P. & P. £2.50



323 EDGWARE ROAD, LONDON W2  
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
**ALL PRICES INCLUDE VAT AT 15%**  
All items subject to availability. Prices correct at 1.10.79 and subject to change without notice.

NOTE: Persons under 16 years not served without parent's authorisation.

# MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.

**Breadboard 1979 is even bigger and better than last year. It's the one show no one should miss!**

These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £750. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £18.38 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

# MAPLIN

**ELECTRONIC SUPPLIES LTD**


Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PE 180

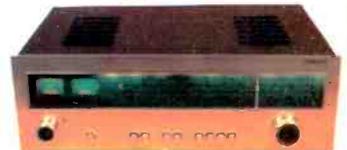

A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.

Maplin will be there in force with all our projects on permanent demonstration. There will be plenty to see and many of our interesting lines will be on sale.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road, Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554000.