

PRACTICAL

125414  
**ELECTRONICS**

SEPTEMBER 1980

55p

**DISCO  
DESK.**

Part 1

**SPECIAL OFFER**  
**Autorangeing Dmm**

**COMPURIT SOUND BOARD**

# EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

## COMPUKIT UK101

★ 6502 based system — best value for money on the market. ★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Disassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for CompuKit expansion **£8.50 + VAT**

Build, Understand and Program your own Computer for only a small outlay

**KIT ONLY £179 + VAT**  
**NO EXTRAS NEEDED**

Available ready assembled, tested & ready to go **£229 + VAT**

### NEW MONITOR FOR COMPUKIT UK101

● In 2K Eprom 2716 ● Allows screen editing ● Saves data on tape ● Flashing cursor ● Text scrolls down **£22.00 + VAT**

### FOR THE COMPUKIT

Assembler/Editor **£14.90**  
Screen Editor Tape **£5.90**

### Game Packs

1. Four Games **£5.00**  
2. Four Games **£5.00**  
3. Three Games 8K only **£5.00**

Space Invaders **£5.00**  
Chequers **£3.00**  
Real Time Clock **£3.00**  
Case for CompuKit **£29.50**

All Prices exclusive VAT

**only £349 + VAT**



**TRS80 LEVEL 2 16K**

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals UK Power Supply — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available.

Interface to Centronics Parallel for TRS80 **£75.00 + VAT**

**only £295 + VAT**

Expand your TRS80 by 32K

**32K TRS80 EXPANSION INTERFACE**

32K Memory on board Centronics parallel port Disk controller card Real time clock. Requires Level II Basic. Interface for 2 cassette decks. complete with power supply.

## THE ATARI VIDEO COMPUTER GAMES SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!

**£79.00** + VAT

Most Cartridges only **£13.90 + VAT**  
Prices may vary with special editions Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score\*, Space War, Sky Diver, Air Sea Battle, Codebreaker\*, Miniature Golf.

Extra Paddle Controllers **£14.90 + VAT**  
Keyboard Controllers **£16.90 + VAT**

**SPACE INVADERS NOW IN STOCK £25**

### SPECIAL—ONCE IN A LIFETIME OFFER!

16K **£399**  
32K **£449**  
48K **£499**  
+ VAT

## EXIDY SORCERER

For Personal or Business Use.  
32K or 48K memory. 8K Microsoft Basic in ROM. Dual Cassette I/O, RS232 I/O. Parallel I/O (Centronics). Expansion available through optional extra \$100 Motherboard. 69 Key keyboard including 16 key numeric pad.

**video 100**

12" BLACK & WHITE LOW COST VIDEO MONITOR

**only £79 + VAT**

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum
- Central 80% of CRT; 550 Lines Minimum beyond central 80%.

### SPECIAL OFFER

We will part exchange your Sinclair ZX80 for any of our products.

Refurbished ZX80's—fully guaranteed **£69.90** + VAT  
(Supply dependant upon stocks).

### NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.

**MINI KIT** — PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. **£14.90 + VAT**  
**OR PCB** **£2.90** MAIN LSI **£8.50** Both plus VAT

We have one of the largest collections of Computer Books under one roof, along with racks of software for the PET and TRS80. **Come and see for yourself.**

### WE ARE NOW STOCKING THE APPLE II EUROPLUS AT REDUCED PRICES

16K **£599**  
32K **£649**  
48K **£690** + VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:

- BASIC — The Language that Makes Programming Fun.
- High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays.
- Sound Capability that Brings Programs to Life.
- Hand Controls for Games and Other Human-Input Applications.
- Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package.
- Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

### EXATRON STRINGY FLOPPY FOR TRS80

(Expansion interface not needed)  
**only £169 + VAT**

High Speed storage medium that is cheap and reliable. Includes 20 wafers - M/C monitor - BUS EXPN cable. **£169**

### NEW REDUCED PRICES

8K **£399**  
16K **£499**  
32K **£599** + VAT

RRP £795 for 32K

**The PEDIGREE PETS** Very popular for home & business use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard. All with green screen. Cassette Deck **£55** extra. Full range of software available. Interface PET IEEE — Centronics Parallel. Not decoded **£49.00 + VAT** Decoded **£77.00 + VAT**

We give a full one year's warranty on all our products.

We now have in stock demonstration models of the Atari 800 and Texas 99/4. **Come and see them**

### NASCOM-2

WITH FREE POWER SUPPLY & 16K RAM B BOARD  
**only £305 + VAT**

Subject to Availability

### NASCOM 2 DISC DRIVES

Add a powerful, double density, mini floppy disc to your Nascom system.

- Disc Controller Card (includes Nasbus 6 S100 interface)
- Will control 4 Drives.
- CPM operating system.
- Extended Disc Basic Compiler.
- Power supply included

One Disc System — **£499 + VAT**  
Additional Disc Unit — **£299 + VAT**

### SPECIAL SCOOP GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

**only £349 + VAT**

Full Pet Graphics including cables. Ready to go **EX-STOCK.**

Please add VAT to all prices — including delivery. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G

OPEN - 10 am - 7 pm — Monday to Saturday  
Close to New Barnet BR Station — Moorgate Line.

★ **NOW IN IRELAND** at: 80 Marlborough St., Dublin 1. Tel: Dublin 749933  
★ **COMP SHOP USA**, 1348 East Edinger, Santa Ana, California, Zip Code 92705. Telephone: 0101 714 5472526

**COMP SHOP LTD.** "Europe's Largest Discount Personal Computer Store"

**COMP COMPUTER COMPONENTS**  
(Part of the Compshop Ltd. Group)

# PRACTICAL ELECTRONICS

VOLUME 16 No. 9 SEPTEMBER 1980

---

## CONSTRUCTIONAL PROJECTS

<b>DISCO DESK Part 1</b> by Ben J. Duncan	24
A mobile control console for high power, h.f. sound systems	
<b>PROGRAMMABLE SOUND GENERATOR</b> by D. Coutts	32
An almost unlimited range of sound effects for your Compuikit	
<b>PE TELETEXT Part 2</b> by David Shortland	42
Tuner and Decoder circuits	
<b>PE MAGNUM Part 2</b> by Andy Flind	52
Final construction and setting up	
<b>CLASS "A" AMPLIFIER</b> by K. Garwell	58
30W Stereo Design	

## GENERAL FEATURES

<b>SEMICONDUCTOR UPDATE</b> by R. W. Coles	20
NSC 800 74LS610 MA 537	
<b>UK 101 TELEPRINTER INTERFACE</b> by J. J. Trevillion	38
A simple alternative to an on-line printer	
<b>MICRO PROMPT</b>	40
Another batch of original ideas	
<b>INGENUITY UNLIMITED</b>	66
Alarm Clock Weekend Lockout—Four Digit to Six Digit Clocks—Quiz Win Indicator— Function Generator—Slave Flash Controller—Battery Check	

## NEWS & COMMENT

<b>EDITORIAL</b>	17
<b>MARKET PLACE</b>	18
New Products	
<b>COUNTDOWN</b>	21
<b>POINTS ARISING</b>	21
Digital Tachometer—Compuikit Update—PE DMM—Micro Prompt—Constant Current Sources	
<b>INDUSTRY NOTEBOOK</b> by Nexus	23
Keeping up to date on the Electronics Industry	
<b>PATENTS REVIEW</b>	51
New ideas from around the world	
<b>SPECIAL OFFER—AUTORANGING DMMS</b>	57
<b>NEWS BRIEFS</b>	62
<b>SPACEWATCH</b> by Frank W. Hyde	64
News from Russia, and more details of the Satellite Power System	
<b>CASIO WATCH OFFER CORRECTION</b>	65

**OUR OCTOBER ISSUE WILL BE ON SALE FRIDAY, 12 SEPTEMBER 1980**  
(for details of contents see page 63)

---

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

# WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum order £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 40p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

## VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.  
We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/B.R. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

## POLYESTER CAPACITORS: (Axial Lead Type)

400V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 3p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 48p; 1uF 84p; 2uF 82p; 4uF 85p; 10uF: 10n, 15n 20p; 22n 22p; 47n 26p; 100n 38p; 470n 53p; 1uF 175p.

## POLYESTER RADIAL LEAD CAPACITORS: 250V:

10n, 15n, 22n, 33n, 47n, 68n, 100n, 150n, 220n, 330n, 470n, 1uF 22p; 2uF 34p.

## ELECTROLYTIC CAPACITORS: (Values are in µF)

5000V: 105p; 47 78p; 250V: 100 68p; 0.1, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8p; 10, 15, 22 11p; 32, 47 50 12p; 63, 100, 270p; 50V: 50, 100, 220 26p; 470 32p; 1000 60p; 40V: 22, 33µF 8p; 100 12p; 220, 330 85p; 4700 98p; 35V: 10, 33 7p; 330, 470 32p; 25V: 10, 22, 47, 100 8p; 160, 220, 250 16p; 470 26p; 640, 1000 35p; 1500 40p; 2200 45p; 3300 7p; 4700 85p; 16V: 10, 20, 40, 47 7p; 100, 125 8p; 200, 330 14p; 470 20p; 1000, 1500 30p; 2200 36p.  
TAG-END TYPE: 450V: 100µF 180p; 70V: 4700 165p; 64V: 2500 110p; 3300 150p; 50V: 2200 95p; 3300 135p; 40V: 4700 130p; 4000 95p; 3300 98p; 2500 2200 90p; 2000 + 2000 120p; 30V: 4700 110p; 25V: 15,000 195p; 6400 120p; 4700 100p; 330 85p; 2200 60p.

## TANTALUM BEAD CAPACITORS

35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 1.5, 2u2, 3µ3, 4u7, 25V: 10, 20V: 6u8, 16V: 2u2, 4u7, 10 20n each

18V: 22µ 32p; 47, 100 58p; 220 75p; 1000 15p; 22, 33µF: 100, 40p; 6V: 47µF, 80µF: 100 32p; 3V: 100 30p.

## MYLAR FILM CAPACITORS

100V: 0.001, 0.01, 0.05, 0.1µF 6p; 0.015, 0.02, 0.03, 0.04, 0.05, 0.056µF 7p; 0.1µF 8p; 50V: 0.47µF 12p.

## CERAMIC CAPACITORS: (50V)

Range: 0.5pF to 10nF 4p; 15nF, 22nF, 33nF, 47nF 5p; 100nF 7p; 220nF 8p.

## POLYSTYRENE CAPACITORS:

10pF to 1nF 8p; 1-5nF to 47nF 10p.

## SILVER MICA (pF)

2, 3.3, 4.7, 6.8, 8.2, 10, 12, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180, 200, 220, 11p each

250: 270, 300, 330, 360, 390, 470, 600, 800 & 820pF 16p each

1000, 1200, 1800, 2000 26p each

## TRIMMERS miniature

2.5pF: 3-10pF: 28p; 3-30pF: 3-50pF: 35p; 5-25pF: 65pF 88pF: 28p

## COMPRESSION

2.5-40pF: 10 80pF: 30p; 100-500pF: 45p; 400-1250pF: 58p

## POTENTIOMETERS (AB or EGEM)

Carbon Track, 0-25W Log & 0-5W Linear values.

500Ω, 1K & 2K (LIN ONLY) Single 29p

5KΩ-2MΩ single gang 29p

5KΩ-2MΩ single gang D/P switch 29p

5KΩ-2MΩ dual gang stereo 88p

1W Wire-wound 500-20K 105p

## SLIDER POTENTIOMETERS

0-25W Log and linear values 60mm track

5KΩ 500KΩ Single gang 80p

10KΩ 500KΩ Dual gang 80p

Self-Stick graduated Alum. Bezels 33p

## PRESET POTENTIOMETERS

0.1W 500-2.2M Min. Vert. & Horiz. 7p

0.25W 100Ω-3.3MΩ Horiz. larger 10p

0.25W 250Ω-4.7MΩ Vert. 10p

Precision Cermet 1W 100Ω-100K 90p

## RESISTORS—Erie make 5% carbon

Miniature High Stability, Low Noise

RANGE Val. 1-99 100p

0-25W DQ2-4-M7 E24 2p 1p

0-5W DQ2-4-M7 E12 2p 1p

1W 2MΩ Film 100-1E 2p 4p

1% 0.5W 510-1ME24 8p 6p

100 - price applies to Resistors of each type not mixed values.

## TRANSISTORS

AC107	28	BC307B	14	BFX86	28	PIP33C	78	2N1132	24
AC125	35	BC308B	12	BFX87	28	PIP34A	78	2N1303	50
AC126	25	BC328	12	BFX88	28	PIP34C	84	2N1304	50
AC127	22	BC348	12	BFY50	21	PIP35A	170	2N1305	35
AC128	20	BC431	30	BFY51	21	PIP35C	160	2N1307	50
AC141	27	BC461	30	BFY52	21	PIP36A	185	2N1308	46
AC142	28	BC477	35	BFY56	32	PIP36C	199	2N1670	150
AC187	24	BC478	35	BFY64	40	PIP41A	55	2N1671B	215
AC176	25	BC517	35	BFY81	99	PIP41B	60	2N2219A	22
ACY17	60	BC547	10	BRY39	39	PIP42A	64	2N2220A	26
ACY18	60	BC548	7	BSX20	20	PIP42B	64	2N2221A	29
ACY20	60	BC549C	10	BSX29	45	PIP42C	90	2N2222A	29
ACY21	60	BC557	15	BSY50A	18	PIP121	90	2N2369A	15
ACY22	60	BC559	15	BU105	170	PIP141	120	2N2646	48
ACY28	60	BCY70	14	BU205	170	PIP142	126	2N2784	55
ACY39	80	BCY71	18	BU208	215	PIP147	195	2N2904	24
AD161	42	BD127	20	E421	250	PIP255	60	2N2905A	22
AD162	42	BD128	20	M0800U	225	PIP265	60	2N2906	22
AF114	75	BD133	40	MJ491	78	TIS43	40	2N2907A	22
AF115	75	BD134	40	MJ2955	98	TIS44	35	2N2926G	10
AF116	75	BD135	40	MJ340	98	TIS45	45	2N3053	19
AF117	95	BD136	40	MJ340A	98	TIS88A	30	2N3054	55
AF118	95	BD137	40	MJ350	98	TIS90	30	2N3055	55
AF119	40	BD138	40	MJ350A	98	TIS91	32	2N3056	140
AF178	75	BD139	40	MJ355	98	UC734	66	2N3504	55
BC107	10	BD140	40	MPF102	66	ZTX107	11	2N3663	14
BC108	10	BD141	40	MPF103	66	ZTX108	11	2N3702	10
BC109	10	BD142	40	MPF104	66	ZTX109	11	2N3703	10
BC109B	12	BD143	40	MPF105	66	ZTX110	11	2N3704	10
BC109C	12	BD144	40	MPF106	66	ZTX111	11	2N3705	10
BC140	26	BD145	175	MPSA05	22	ZTX301	18	2N3706	10
BC142	26	BD146	175	MPSA06	24	ZTX302	20	2N3707	10
BC143	26	BD147	175	MPSA12	29	ZTX303	26	2N3708	11
BC147	9	BD148	175	MPSA15	29	ZTX304	24	2N3709	11
BC147B	10	BD149	175	MPSA18	29	ZTX305	24	2N3710	11
BC148	10	BD150	175	MPSA29	30	ZTX306	24	2N3711	10
BC148C	10	BD151	175	MPSA38	30	ZTX307	24	2N3712	10
BC149	9	BD152	175	MPSA48	30	ZTX308	24	2N3713	10
BC149C	10	BD153	175	MPSA52	30	ZTX309	24	2N3714	10
BC153	20	BD154	175	MPSA55	30	ZTX310	24	2N3715	10
BC157	10	BD155	175	MPSA58	30	ZTX311	24	2N3716	10
BC158	10	BD156	175	MPSA68	30	ZTX312	24	2N3717	10
BC159	11	BD157	175	MPSA72	30	ZTX313	24	2N3718	10
BC160	28	BD158	175	MPSA75	30	ZTX314	24	2N3719	10
BC167	11	BD159	175	MPSA78	30	ZTX315	24	2N3720	10
BC167B	11	BD160	175	MPSA82	30	ZTX316	24	2N3721	10
BC169C	10	BD161	175	MPSA85	30	ZTX317	24	2N3722	10
BC170	11	BD162	175	MPSA88	30	ZTX318	24	2N3723	10
BC171	11	BD163	175	MPSA92	30	ZTX319	24	2N3724	10
BC172	11	BD164	175	MPSA95	30	ZTX320	24	2N3725	10
BC173	11	BD165	175	MPSA98	30	ZTX321	24	2N3726	10
BC174	11	BD166	175	MPSA102	30	ZTX322	24	2N3727	10
BC175	11	BD167	175	MPSA105	30	ZTX323	24	2N3728	10
BC176	11	BD168	175	MPSA108	30	ZTX324	24	2N3729	10
BC177	11	BD169	175	MPSA112	30	ZTX325	24	2N3730	10
BC178	14	BD170	175	MPSA115	30	ZTX326	24	2N3731	10
BC179	15	BD171	175	MPSA118	30	ZTX327	24	2N3732	10
BC181	10	BD172	175	MPSA122	30	ZTX328	24	2N3733	10
BC182	10	BD173	175	MPSA125	30	ZTX329	24	2N3734	10
BC183	10	BD174	175	MPSA128	30	ZTX330	24	2N3735	10
BC184	10	BD175	175	MPSA132	30	ZTX331	24	2N3736	10
BC184C	10	BD176	175	MPSA135	30	ZTX332	24	2N3737	10
BC182L	10	BD177	175	MPSA138	30	ZTX333	24	2N3738	10
BC183L	10	BD178	175	MPSA142	30	ZTX334	24	2N3739	10
BC184L	10	BD179	175	MPSA145	30	ZTX335	24	2N3740	10
BC187	25	BD180	175	MPSA148	30	ZTX336	24	2N3741	10
BC187B	25	BD181	175	MPSA152	30	ZTX337	24	2N3742	10
BC122L	9	BD182	175	MPSA155	30	ZTX338	24	2N3743	10
BC213	9	BD183	175	MPSA158	30	ZTX339	24	2N3744	10
BC213L	9	BD184	175	MPSA162	30	ZTX340	24	2N3745	10
BC214	10	BD185	175	MPSA165	30	ZTX341	24	2N3746	10
BC214L	10	BD186	175	MPSA168	30	ZTX342	24	2N3747	10
BC237	14	BD187	175	MPSA172	30	ZTX343	24	2N3748	10
BC238	15	BD188	175	MPSA175	30	ZTX344	24	2N3749	10
BC238B	15	BD189	175	MPSA178	30	ZTX345	24	2N3750	10
BC238C	15	BD190	175	MPSA182	30	ZTX346	24	2N3751	10
BC238D	15	BD191	175	MPSA185	30	ZTX347	24	2N3752	10
BC238E	15	BD192	175	MPSA188	30	ZTX348	24	2N3753	10
BC238F	15	BD193	175	MPSA192	30	ZTX349	24	2N3754	10
BC238G	15	BD194	175	MPSA195	30	ZTX350	24	2N3755	10
BC238H	15	BD195	175	MPSA198	30	ZTX351	24	2N3756	10
BC238I	15	BD196	175	MPSA202	30	ZTX352	24	2N3757	10
BC238J	15	BD197	175	MPSA205	30	ZTX353	24	2N3758	10
BC238K	15	BD198	175	MPSA208	30	ZTX354	24	2N3759	10
BC238L	15	BD199	175	MPSA212	30	ZTX355	24	2N3760	10
BC238M	15	BD200	175	MPSA215	30	ZTX356	24	2N3761	10
BC238N	15	BD201	175	MPSA218	30	ZTX357	24	2N3762	10
BC238O	15	BD202	175	MPSA222	30	ZTX358	24	2N3763	10
BC238P	15	BD203	175						



# Enter the 80's with SAXON

**£30 FREE!**

## STEREO DISCO SYSTEMS

WITH LIGHT SHOW & DISPLAY

### STANDARD CENTAUR 100W

£299 incl. VAT Deposit £60  
12 mth = £24 or 24 mth = £14

### SUPER CENTAUR 200W

£399 incl. VAT Deposit £80  
12 mth = £32.03 or 24 mth = £18.75

### GXL 200W with PDF BINS (illus)

£489 incl. VAT Deposit £99  
12 mth = £39.16 or 24 mth = £22.91

### CUSTOM CENTAUR 400/600W

with four PDF 100A Bins

£899 incl. VAT Deposit £167  
12 mth = £72.19 or 24 mth = £42.25

### MINI DISCO 100W

MONO

£249 inc. carr. & VAT Dep. £50  
12 mth = £19.98 or 24 mth = £11.70

**JUST PLUG IN AND GO!!**

AP100 AMPLIFIER £67.50  
AP200 AMPLIFIER £119



- Headphone monitor/cue light
- Full mixing/crosstape
- Tape & mic inputs
- Top Quality
- 4 channel soundlight

CARRIAGE ON COMPLETE SYSTEMS  
IN U.K. £19

**20% DEPOSIT CREDIT TERMS**

All systems complete with loudspeakers, leads, & 2 years warranty

100 WATT £229 inc. VAT  
Dep. £46  
or 12 mth = £18.38  
or 24 mth = £10.76

- Four mixing inputs & master
- Bass & treble controls
- Sturdy construction
- Twin Piezo cabinets

200 Watt £348.15 inc. VAT Dep. £70.15  
• Twin 200W cabinets 12 mth = £27.92  
• Six inputs—three channels 24 mth = £16.34



P.A SYSTEMS  
C/W LOUDSPEAKERS



Vouchers with our new catalogue over 200 items of disco systems, lighting and accessories. Send £1.00 now.

### EXAMPLES:

Fuzz lights £26.75  
Projectors from £55.50  
Strobes £35-£220  
Rope lights 8 mt £59  
Disco stands £29.75  
Echo chambers from £77.50  
100W speaker £29.50  
10 way chaser £199  
100W twin horn £125  
800W spot bank £55

Mixers, mics, amplifiers, goosenecks, light units, bubble machines, mirror balls, helicopters, bins, consoles, and much more.

**AND IF WE HAVEN'T GOT IT - WE'LL GET IT!**

Full range of Pluto, D.J. Lightomation products in stock  
Send £1 now for your catalogue - worth £30!!!

SAXON  
ENTERTAINMENTS  
333 WHITEHORSE ROAD  
CROYDON  
SURREY CR0 2HS  
Tues-Sat 9am-5pm

ALL MAIL & CREDIT ENQUIRIES TO  
CROYDON TO ORDER  
Send cheque/crossed POS or Telephone (01) 684 6385  
Access/Barclaycard. Telephone orders accepted  
For Credit Sales & Enquiries Ring  
SUE ABEGG ON (01) 684 8007/0098

ERSIN

**Multicore**  
5 CORE SOLDER

## Handy size Reels & Dispensers

OF THE WORLD'S FINEST CORED SOLDER TO DO  
A PROFESSIONAL JOB AT HOME

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.



**SAVBIT**  
handy solder dispenser

Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.  
Size 5 90p

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits. PC115 £1.15  
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.  
Size 19A 97p



handy size reels of **SAVBIT, 40/60, 60/40 & ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. mm.	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£3.91
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£6.00
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£3.91
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£3.91



**WIRE STRIPPER & CUTTER**

Easily adjustable for most sizes of flex and cable. Fitted with extra strong spring for automatic opening. Easy grip handles and handle locking device.  
Ref 9  
£2.48 inc. VAT.

### MULTICORE WICK

for solder removal and desoldering.

Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watts soldering iron. Quick and easy to use. Non-corrosive.



Size AB10 £1.38


Sole UK Sales Concessionaires:

**Bib Hi-Fi Accessories Limited,**

Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

Prices shown are recommended retail inc. VAT. From Electrical and Hardware Shops. In difficulty send direct, plus 40p P&P. Prices and specifications subject to change without notice.
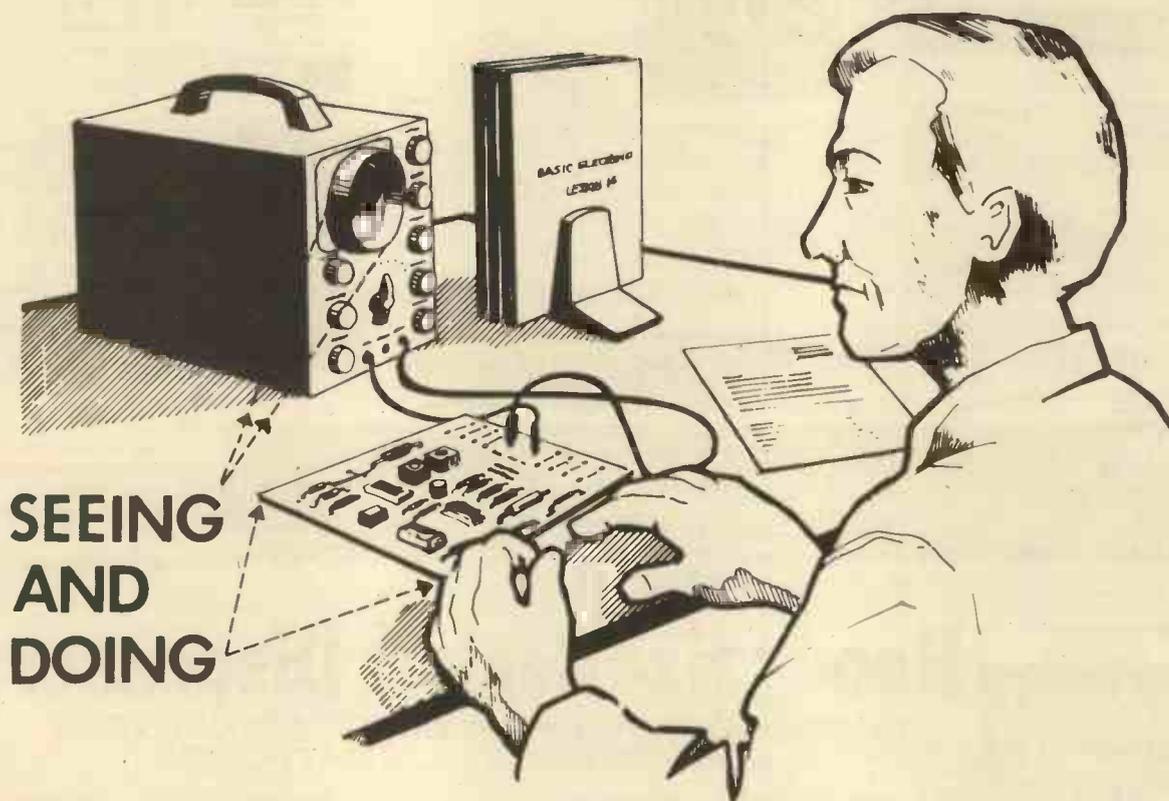
# Master Electronics the new Practical way.



SEEING  
AND  
DOING

## Conquer the 'Chip' – Easy-Fast-Exciting !

AND MASTER ALL THE NEW TECHNIQUES  
IN MODERN ELECTRONICS.

- Build an Oscilloscope.
- Carry out over 40 full experiments including work on Digital Electronic Circuits.
- Recognition of Electronic Components.
- Understand and draw Circuit Diagrams.
- Experience with handling Solid State Circuits and "Chips".
- Testing and Servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

Colour Brochure – without any obligation. Post to :-

PE/9/812

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**  
4 Cleveland Road, Jersey, Channel Islands.

Name .....

Address .....

.....

BLOCK CAPS PLEASE

**FREE**

# D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



**BASIC COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

**LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

## P.E. MINISONIC MK2 SYNTHESIZER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available) and PCBs (incl. layout charts)

KIT 38-25 £80.12

"Sound Design" booklet £1.00

## P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic comps, PCBs and charts

KIT 76-7 £35.56

Set of text photocopies £1.36

## P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic comps, PCBs and charts

KIT 86-5 £33.60

Set text photocopies £1.84

## P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser.

Set of basic comps, PCBs & charts

KIT 77-8 £107.86

## ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic comps and PCBs (as publ.)

KIT 80-9 £146.66

Additional 3-octave extension and basic parts and PCBs (as published)

KIT 80-10 £56.36

Set of text photocopies £1.81

## ELEKTOR FORMANT SYNTHESIZER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.)

KIT 66-14 £255.45

Set of text photocopies £7.83

## ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.)

KIT 78-3 £55.40

Extension unit basic comps and PCB (as publ.)

KIT 78-4 £52.77

Text photocopy 86p

## ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set

KIT 83-1 £29.49

Additional Delay basic components

KIT 83-2 £20.07

PCB (as publ.) to hold both kits

PCB9973 £4.52

Text photocopy 67p

## ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic comps & PCB (as publ.)

KIT 87-2 £6.84

Text photocopy 38p

## NEW KITS

### ELEKTOR CHOROSYNTH

A 2 $\frac{1}{2}$ -octave Chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage.

Basic comps, PCBs and charts but excl. sw's

KIT 100-8 £44.39

Text photocopy 70p

### ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.)

KIT 101-1 £22.53

Text photocopy 60p

### ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music signals.

Basic comps, PCB (as publ.)

KIT 99-1 £9.60

Text photocopy 40p

### ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.)

KIT 98-1 £5.48

Text photocopy 20p

### P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart

KIT 102-3 £17.58

Text photocopy 65p

### P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart

KIT 96-1 £3.98

### DISCO-CROSS FADER

The cross-fade between 2 decks is switch-initiated and can be preset on the panel for a cross fade rate of between about  $\frac{1}{2}$  sec & 24 secs. Basically a stereo unit but may be used in mono.

Basic comps, PCB & chart

KIT 94-1 £11.83

### P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic comps, PCBs & charts (excl. SWs)

KIT 85-5 £54.56

Set of text photocopies £2.52

### P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic components, PCB & chart

KIT 88-1 £10.89

2-Notch extension, PCB & chart

KIT 88-2 £6.36

Text photocopy 68p

### ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart

KIT 70-2 £21.67

Text photocopy 67p

## ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic comps, & PCB (as publ.)

KIT 82-2 £22.45

Text photocopy 57p

## P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart

KIT 42-3 £10.37

Text photocopy 28p

## P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic components, PCB & chart

KIT 56-3 £11.22

Text photocopy 64p

## P.E. SMOOTH FUZZ

Basic components, PCB & chart

KIT 91-1 £6.40

Text photocopy 55p

## TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Basic components, PCB & chart

KIT 54-1- £3.74

## GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.

Basic components, PCB & chart

KIT 74-1 £5.19

Text photocopy 38p

## P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, PCB & chart

KIT 75-1 £6.73

Text photocopy 38p

## P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control.

Basic components, PCB & chart

KIT 51-1 £4.93

## P.E. AUTO-WAH UNIT

Automatically gives Wah or Swell sounds with each note played.

Basic components, PCB & chart

KIT 58-1 £9.68

Text photocopy 53p

## ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space sawtooth, regular triangle, or square-wave with variable mark-space.

Basic comps, PCB & chart, but excl. sw's

KIT 67-1 £9.24

## P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses

Basic components, PCB & chart

KIT 89-1 £4.34

Text photocopy 78p

## P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control depth.

Basic components, PCB & chart

KIT 53-1 £2.92

## P.E. SYNTHESIZER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Basic comps, PCBs & charts

KIT 23-33 £167.57

Set of text photocopies £8.21

### 10% DISCOUNT VOUCHER (PE 83)

TERMS: Goods in current adverts & lists over £50 goods value (excl. P&P & VAT). Correctly coded, C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E. Does not apply to credit card orders.

### ADD: POST & HANDLING

U.K. orders: Keyboards add £2.70 each. Other goods: Under £5 add 50p, under £20 add 75p, over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

### ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 35p, other countries send 75p. Note that we do not offer a C.O.D. service and that our terms are payment in advance.

PHONOSONICS · DEPT PE88 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

# AND OTHER PROJECTS

**PHOTOGRAPHS** in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

**LIST**—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

**OVERSEAS** enquiries for list Europe—send 35p; other countries—send 75p.



## KIMBER-ALLEN KEYBOARDS AND CONTACTS

**KIMBER-ALLEN KEYBOARDS** as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50 4 Octave (49 notes) £32.25 5 Octave (61 notes) £39.75

**CONTACT ASSEMBLIES** (gold-clad wire) — 1 required for each KBD-note:  
Type GJ — SPCO 33p ea. Type GB — 2 pr N/O 37½p ea.

### P.E. V.C.F.

A voltage controlled filter extracted from P.E. Minisonic project.  
Basic comps, PCB & chart KIT 65-1 £8.45

### P.E. RING MODULATOR

Extracted from P.E. Minisonic project.  
Basic comps, PCB & chart KIT 59-1 £6.35

### WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.  
Basic comps, PCB & chart KIT 28-1 £4.84  
Text photocopy 28p

### P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.  
Basic comps, PCB & chart KIT 44-1 £5.73  
Text photocopy 49p

### P.E. ENVELOPE SHAPER WITH VCA

Has an Integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.  
Basic comps, PCB & chart KIT 50-1 £8.03  
Text photocopy 58p

### P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.  
Basic comps, PCB & chart KIT 63-2 £7.82  
Text photocopy 58p

### P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.  
Basic comps, PCB & chart KIT 81-1 £3.90

### P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.  
Set of basic components, incl. power supply, PCBs & charts KIT 46-3 £23.32  
Text photocopy 97p

### P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.  
Basic components, PCB & chart, but excl. sw. KIT 69-1 £8.19  
Text photocopy 58p

### P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.  
Basic comps, PCB & chart KIT 62-1 £5.31

### P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.  
Basic components, PCB & chart KIT 79-4 £31.35  
Text photocopy 78p

### P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances.  
Basic components, (excl. sw's.) and set of PCBs and charts. KIT 90-8 £61.25  
Extra 2-channel set with PCB KIT 90-9 £11.82  
Set of Text photocopies £1.50

### STEREO HEADPHONE AMPLIFIER

Extracted from P.E. 6-channel mixer.  
Basic components, PCB & chart KIT 92-1 £5.68

### DIGITAL EXPOSURE UNIT

Controls up to 750 watts in ½ second steps up to 10 minutes, with built-in audio alarm.  
Basic components, PCBs & charts KIT 93-3 £23.27  
Text photocopy £1.20

### P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation, and with extra audio input.  
Basic components, PCB & chart KIT 57-2 £25.12  
Text photocopy 78p

### RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, 128 beat almost infinite pattern, and pre-programmed 15 pattern using either M252 or M253 rhythm chips. A selection of effects instrument circuits is also available.

### P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for discos.  
Basic components, PCB & chart KIT 30-1 £4.37  
Text photocopy 28p

### P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.  
Basic components, PCB & chart KIT 97-1 £8.07  
Text photocopy 75p



# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

### Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

### City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, T.V. Electronics Technicians,  
Radio Amateurs  
Electrical Installation Work

### Diploma Courses

Colour T.V. Servicing  
CCTV Engineering  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations & Contracting

### Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE BOOK**

Post this coupon or 'phone today for free Electronics careers guide.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_


**ICS**

To ICS, Dept. Y273, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

PRICES ARE CORRECT AT TIME OF PRESS.  
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.


**PHONOSONICS**

# Pure ind

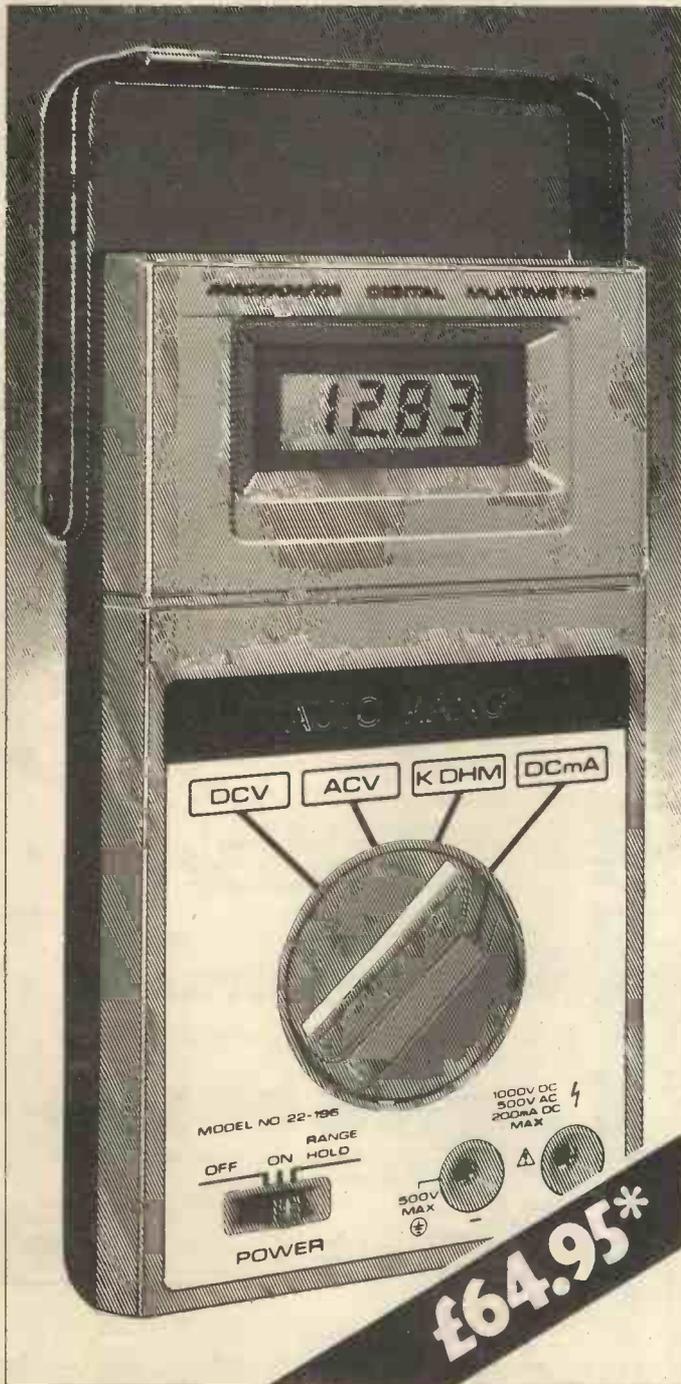

**Micronta Auto Range Multimeter** Gives you correct polarity, range and measurement — every time. Single function switch lets you choose DC 4 ranges; AC 4 ranges; DC current resistance. 4 ranges. LCD readout. Exclusive range hold facility. 22-196

**£64.95\***

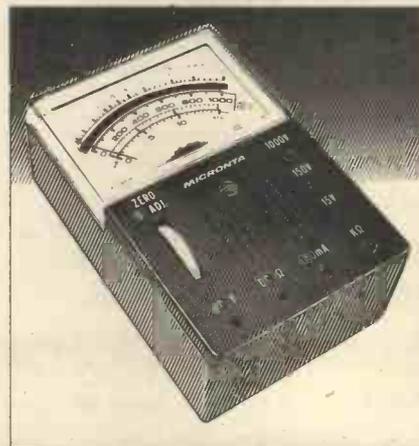

**£6.95\***

**Micronta 1000 Ohms/Volt Multitester** Very compact at 89 x 59 x 32 mm. Easy to read colour meter, pin jacks for all 8 ranges. Reads AC V, DC current and ohms. Mirrored scale. 20-027



**£9.95\***

**Micronta Transistorized Signal Tracer** Spot circuit troubles, check RF, IF and audio signals from aerial to speaker on all audio equipment. It has built in 5 cm speaker with volume control. 50 x 143 x 38 mm. 22-010



**£9.95\***

**Micronta Dynamic Transistor Checker** Shows current gain and electrode open and short circuit. Tests low medium or high power PNP or NPN types. Go/no-go tests from 5-50 mA on power types. "Quick-check" sockets. 22-024

# Intelligence.

Realistic Direct Entry Programmable Scanning Receiver Hear real-life drama on six exciting bands. With direct access to all frequencies, you can punch in actual frequencies for monitoring, storing in the computer's memory or just exploring. Big fluorescent display. Phase locked loop security. 20-9111

TRS-80 Model I C.P.U.'s Ready to run from your TV monitor. Plug in and start computing. Contains 4096 bytes of user memory and can be expanded to 16K. 26-9051



**ACCRINGTON**  
37 Union Street  
**ALDRODGE**  
15 Central Area Development  
**BARNESLEY**  
56 Market Street  
**BASHINGSTONE**  
27 London Street  
**BIRKENHEAD**  
Kwik Save Centre, Prenton  
**BRADFORD COMPUTER CENTRE**  
2/4, Forster Square  
**BIRMINGHAM AREA**  
**BULL RING**  
526 Bridge Link  
Shopping Centre  
**CAPE HILL**  
44-46, Cape Hill  
**CITY CENTRE**  
57/58 Dale End  
**CORPORATION STREET**  
80, Corporation Street  
**DALE END**  
57-58, Dale End  
**EDGECASTON COMPUTER CENTRE**  
Edgebaston Shopping Centre  
**ERDINGTON**  
218 High Street  
**HALESOWEN**  
5-7 Queensway  
**NORTHFIELD**  
749 Bristol Road South

**PERRY BARR**  
20 Lynton Square  
**SHELDON**  
2268 Coventry Road  
**SMETHWICK**  
44/46 Cape Hill  
**WARD END**  
887 Washwood Heath Road  
**WEDNESBURY**  
Bilston Road  
**BOLTON**  
5 Nelson Square  
**BOSCOMBE**  
548 Christchurch Road  
**BOURNEMOUTH**  
132/4 Commercial Road  
**BRADFORD**  
9 Petergate  
**BRIGHTON**  
70 London Road  
**BRISTOL AREA**  
**BISHOPSTON**  
13 Gloucester Road  
**BRISTOL COMPUTER CENTRE**  
Colston Centre  
**CLIFTON**  
146 Whiteladies Road  
**DOWNEND**  
5 Badminton Road  
**KNOCKLE**  
Broadwalk Shopping Centre  
**YATE**  
4 North Parade

**BROMSGROVE**  
6/8 St. John Street  
**BROWNHILLS**  
60 High Street  
**BURY (Lancs)**  
91 The Rock  
**CARDIFF**  
9 Wood Street  
**CHELTENHAM**  
31 Cambray Place  
**CHESTER**  
Kwik Save Centre  
**COVENTRY**  
Sealand Road  
**CREWE**  
12 Market Street  
**DARLINGTON**  
15/16 Priestgate  
**DERBY**  
33 Victoria Street  
**DONCASTER**  
32/34 Kingsgate  
**DUDLEY**  
Trindle Road Roundabout  
**EASTBOURNE**  
Langley Shopping Centre  
**EXETER**  
13 Paris Street  
**GRIMSBY**  
Riverhead Centre  
**KNOWLE**  
Broadwalk Shopping Centre  
**LONDON AREA**  
8/10 North Street  
**BATSWATER**  
The Colonnades  
**POCHESTER ROAD**  
34 Oxford Street

**HUDDERSFIELD**  
Packhorse Shopping Centre  
**HULL**  
Status City, Cough Road  
**LEAMINGTON SPA**  
53 Warwick Street  
**LEEDS**  
77 Merrion Centre  
**LEEDS**  
3 Eastgate  
**LEICESTER**  
Market Street  
**LETCHEWORTH**  
25 Commerce Way  
**LINCOLN**  
High Street  
**LIVERPOOL AREA**  
**ALLERTON**  
50 Allerton Road  
**BOOTLE**  
New Strand Precinct  
**OLD SWAN**  
648 Prescott Road  
**ST. JOHN'S PRECINCT**  
168 Market Way  
**LONDON AREA**  
8/10 North Street  
**BATSWATER**  
The Colonnades  
**POCHESTER ROAD**  
34 Oxford Street

**BECKENHAM**  
144 High Street  
**CATFORD**  
23 Catford Broadway  
**CHESHURT**  
92 Turners Hill  
**CHINGFORD**  
3 Hall Lane  
**CLAPHAM**  
84 Clapham High Street  
**BOLTON**  
COLLIER ROW  
**CRUICK END**  
42 The Broadway  
**DAGENHAM**  
297 Heathway  
**EDDWARE**  
23, North Mall  
**EDMONTON**  
142/4 King Street  
**HAMMEPSMITH**  
10 Colman Parade  
**HENDON**  
24 Sentinel Square  
**ORPINGTON**  
5 The Walnuts  
**PALMERS GREEN**  
379 Green Lanes  
**ROMFORD**  
27 Collier Row Road  
**SEACOL LANE**  
1/2, Seacool Lane

**STREATHAM**  
254 Streatham High Road  
**TOTTENHAM**  
455 High Road  
**WALTHAMSTON**  
123 High Street  
**WALWORTH**  
239 Walworth Road  
**WANDSWORTH**  
107/9 High Street  
**WELLING**  
7 Embassy Court  
**WIMBLEDON**  
124/6 The Broadway  
**LITTON**  
157 Dunstable Road  
**MANCHESTER AREA**  
**ARNDALE**  
Unit 71, Arndale Centre  
**BIRMIHALL**  
14/15 The Centre  
**CHADDERTON**  
67 High Street  
**CHEADLE**  
67 High Street  
**DEANSGATE COMPUTER CENTRE**  
36, Market Place, Hyde  
**HYDE**  
4-8 The Mall  
**RADCLIFFE**  
25 Blackburn Street  
**SALE**  
The Mall

**CITY CENTRE**  
Annals Centre  
**STRETFORD**  
Arndale Centre  
**NEWBURY**  
14 Bartholomew Street  
**NORTHAMPTON**  
Weston Favel Shopping Centre  
**NOTTINGHAM AREA**  
**ARNOLD**  
126/8 Front Street  
**BEESTON**  
30 The Square  
**NUJEATON**  
1 Church Street  
**OXFORD**  
9/10 St. Clements  
**PAIGINTON**  
35 Hyde Road  
**PLYMOUTH**  
54 Royal Parade  
**PORT TALBOT**  
Aberafan Centre  
**READING**  
18 The Butts Shopping Centre  
**RUGBY**  
25 Church Street  
**RUNCORN**  
120 Runcorn Shopping City  
**SCUNTHORPE**  
140 High Street

**SHREWSBURY**  
20 Shop Latch  
**SITTINGBOURNE**  
20 The Forum Shopping Centre  
**SLOUGH**  
293 High Street  
**SOUTHAMPTON**  
East St. Centre  
**STAFFORD**  
6 Sheridan Shopping Centre  
**ST. HELENS**  
Fingerpost Centre  
**STOKE-ON-TRENT**  
Hanley 16 Charles Street  
**SUNDERLAND**  
4 Fawcett Street  
**SURREY**  
206 High Street (Surrey)  
**TORQUAY**  
134 Union Street

**TYNE AND WEAR AREA**  
**NEWGATE**  
23 Newgate Centre  
**SHEFFIELD**  
19-20, Hillsborough Shopping Centre  
**SHIELDS ROAD**  
184/6 Shields Road  
**WASHINGTON NEW TOWN**  
Galleries  
**SHOPPING CENTRE**  
**WAKEFIELD**  
Kirkgate Shopping Centre  
**WALSALL**  
74 Bradford Street  
**WALLASEY**  
The Precinct  
**WORCESTER**  
8 St. Nicholas Street  
**WORKOP**  
7/9 Bridge Place  
**YORK**  
5 Church Street

Offers subject to availability. Instant credit available in most cases. Prices may vary in individual stores. Access. Barclaycard and Trustcard welcome. Most items also available at Tandy Dealers. Look for this sign on your store.



\*All prices include VAT.

# IT'S POSSIBLE, ONLY AT Tandy

## Better Equipment. Lower Prices. No Middlemen.

# DorAm

a de boer company

Buying one of our PROJECT PACKS will save you the frustration of tracking down those evasive components that hold up the completion of your project. Our packs include Printed Circuit Board, all the components listed in the article together with sockets and solder. Cases, knobs etc can be supplied as extra items if required. Ask for more information ... !

## cars.80

- **Battery protection (80109).** Forgetting to turn off the headlights need no longer be a motorist's nightmare. This project is designed to monitor the battery voltage and switch off the lights automatically in all kinds of motor vehicles. **£5.15**
- **Transistor ignition (80084).** A system which combines the most significant advantages of other systems including the conventional system! **£20.45**
- **A dip-stick probe (80102).** There are all kinds of indicators and warning lights in modern cars, but an oil temperature indicator is rarely included. The easiest way to add this type of indicator to an existing car is to mount a temperature sensor in the dip-stick. Project without dip-stick **£3.65**  
Dip-stick with indicator (short) **£11.00**  
Dip-stick with indicator (long) **£11.45**
- **Intelligent wiper delay (80086).** This wiper delay only needs to be told once what is required of it. It will then carry out your orders until you change them, which you can at any time, instantly. **£15.85**
- **Active car aerial (80018-1+2).** If there is one place to use a good aerial it is in a car. **£13.85**
- **Stop thief! (80097).** There are all sorts of systems for protecting cars, but this one is unusual; it is deception, rather than protection ... **£4.20**
- **Battery voltage indicator (80101).** Only a few components are needed to obtain an optional indication of the battery condition: a single lamp that changes colour as the battery goes into the danger area. **£6.85**



### HOW TO ORDER

Send a cheque or postal order to Doram Electronics Ltd, Fitzroy House, Market Place, Swaffham, Norfolk PE37 7QH. All prices INCLUDE VAT, please add 40p for postage and packing. 24 Hour Answering Service available for ACCESS orders.

Telephone: Swaffham (0760) 21627. Telex 817912 Doram G.

## a de boer company

# Make sure of your Heathkit catalogue... write now.



Keep up to date with the world's finest electronic kits—with the Heathkit catalogue.

48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers.

Heathkit make it easy to build, easy on your pocket, and, as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (PE 9), Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue.

I enclose 25p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_

Soldering  
Iron offer  
FREE

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.

# HEATHKIT

HEATH  
KIT

# PRIME COMPONENTS LOW PRICES

All our micro chips are at micro prices. Don't be fooled by low prices. We do not offer for sale sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of P&P and VAT - please refer to "Ordering Information" before ordering. Official orders from Schools, Colleges, Universities and Gov. Authorities accepted.

DTL		MEMORIES		CPUS	
930	55p	4028	75p	6502	795p
935	65p	4029	80p	6504	795p
937	55p	4030	50p	6505	795p
944	65p	4033	143p	6800	695p
946	65p	4035	104p	6802	995p
947	55p	4036	290p	8080A	525p
962	55p	4037	110p	8088A	1095p
9099	90p	4039	290p	280	795p
		4040	99p	280A	995p
		4041	75p	28001	12500p
		4042	75p	28002	9500p
		4043	86p	WD9000B	19900p

7400		EPROMS		VOLTAGE REGULATORS	
7400	11p	1702A	450p	7805/7812	55p
7401	12p	2708 450 NS	425p	7905/7912	65p
7402	15p	2716 5V 450 NS	995p	78H05CC	575p
7403	13p	2532 32K 450 NS	2995p	78HGKC	625p
7404	17p				
7405	17p				
7409	18p				
7410	16p				
7412	18p				
7413	14p				
7420	16p				
7430	18p				
7432	25p				
7440	16p				
7442	89p				
7448	75p				
7473	32p				
7474	40p				
7476	40p				
7480	35p				
7492	50p				
7493	50p				
7496	45p				
74121	35p				
74123	45p				
74154	90p				
74157	55p				
74122	45p				
74125	50p				
74195	100p				
74196	100p				
74231	140p				
74290	120p				
74365	90p				
74366	90p				

74LS		CHARACTER GENERATOR		BIPOLAR PROMS	
74LS00	18p	RO-3-2513 UC	450p	93448 512x8 40 NS	p.o.a.
74LS01	12p	KEYBOARD ENCODER		93453 1kx4 40 NS	p.o.a.
74LS04	15p	AY-5-2376	795p	93451 1kx8 45 NS	p.o.a.
74LS08	20p	FLOPPY DISK CONTROLLERS		93511 2kx8 50 NS	p.o.a.
74LS10	19p	FD1793 8-01	2995p		
74LS11	30p	FD1791 8-01	2995p		
74LS12	30p	D/D Inverted Bus	4995p		
74LS14	60p	FD1792 8-01	3495p		
74LS15	35p	S/D Inverted Bus	4995p		
74LS20	19p	D/D True Bus	5495p		
74LS30	19p	FD1794 8-01	3495p		
74LS32	25p	S/D True Bus	3495p		
74LS40	26p	FD1795 8 D/D Inverted Bus, side select	5995p		
74LS42	56p	FD1797 8 D/D True Bus, side select	5995p		
74LS47	75p	SUPPORT DEVICES			
74LS48	85p	5620	495p		
74LS49	95p	6822	795p		
74LS53	30p	6532	895p		
74LS54	30p	6551	1095p		
74LS57	39p	6820	325p		
74LS58	39p	6821	425p		
74LS90	40p	6850	425p		
74LS107	40p	8212	395p		
74LS123	89p	8216	395p		
74LS132	70p	8224	395p		
74LS138	69p	8228	395p		
74LS151	75p	8251	495p		
74LS153	75p	8253	1125p		
74LS155	65p	8257	1050p		
74LS163	90p	8259	1325p		
74LS194	75p	MC 144 12VL	797p		
74LS196	75p	Z80 P10	595p		
74LS198	75p	Z80 CTC	595p		
74LS199	75p	Z80 P10	695p		
74LS184	90p	Z80A CTC	695p		
74LS168	190p	Z80 DMA	1995p		
74LS174	99p	Z80 DMA	2495p		
74LS175	99p	Z80 S10/0	2995p		
74LS195	77p	Z80 S10/1	3495p		
74LS221	110p	Z80 S10/2	2995p		
74LS244	175p	Z80 S10/2	3495p		
74LS245	325p				
74LS251	120p				
74LS257	110p				
74LS290	95p				
74LS293	120p				
74LS366	57p				
74LS373	170p				
74LS374	170p				
74LS375	140p				
74LS377	188p				
74LS393	135p				
74LS490	140p				

74LS		KEYBOARD ENCODER		FLOPPY DISK CONTROLLERS	
74LS00	18p	AY-5-2376	795p	FD1793 8-01	2995p
74LS01	12p			FD1791 8-01	2995p
74LS04	15p			D/D Inverted Bus	4995p
74LS08	20p			FD1792 8-01	3495p
74LS10	19p			S/D Inverted Bus	4995p
74LS11	30p			D/D True Bus	5495p
74LS12	30p			FD1794 8-01	3495p
74LS14	60p			S/D True Bus	3495p
74LS15	35p			FD1795 8 D/D Inverted Bus, side select	5995p
74LS20	19p			FD1797 8 D/D True Bus, side select	5995p
74LS30	19p				
74LS32	25p				
74LS40	26p				
74LS42	56p				
74LS47	75p				
74LS48	85p				
74LS49	95p				
74LS53	30p				
74LS54	30p				
74LS57	39p				
74LS58	39p				
74LS90	40p				
74LS107	40p				
74LS123	89p				
74LS132	70p				
74LS138	69p				
74LS151	75p				
74LS153	75p				
74LS155	65p				
74LS163	90p				
74LS194	75p				
74LS196	75p				
74LS198	75p				
74LS199	75p				
74LS184	90p				
74LS168	190p				
74LS174	99p				
74LS175	99p				
74LS195	77p				
74LS221	110p				
74LS244	175p				
74LS245	325p				
74LS251	120p				
74LS257	110p				
74LS290	95p				
74LS293	120p				
74LS366	57p				
74LS373	170p				
74LS374	170p				
74LS375	140p				
74LS377	188p				
74LS393	135p				
74LS490	140p				

74LS		SUPPORT DEVICES	
74LS00	18p	5620	495p
74LS01	12p	6822	795p
74LS04	15p	6532	895p
74LS08	20p	6551	1095p
74LS10	19p	6820	325p
74LS11	30p	6821	425p
74LS12	30p	6850	425p
74LS14	60p	8212	395p
74LS15	35p	8216	395p
74LS20	19p	8224	395p
74LS30	19p	8228	395p
74LS32	25p	8251	495p
74LS40	26p	8253	1125p
74LS42	56p	8257	1050p
74LS47	75p	8259	1325p
74LS48	85p	MC 144 12VL	797p
74LS49	95p	Z80 P10	595p
74LS53	30p	Z80 CTC	595p
74LS54	30p	Z80 P10	695p
74LS57	39p	Z80A CTC	695p
74LS58	39p	Z80 DMA	1995p
74LS90	40p	Z80 DMA	2495p
74LS107	40p	Z80 S10/0	2995p
74LS123	89p	Z80 S10/1	3495p
74LS132	70p	Z80 S10/2	2995p
74LS138	69p	Z80 S10/2	3495p
74LS151	75p		
74LS153	75p		
74LS155	65p		
74LS163	90p		
74LS194	75p		
74LS196	75p		
74LS198	75p		
74LS199	75p		
74LS184	90p		
74LS168	190p		
74LS174	99p		
74LS175	99p		
74LS195	77p		
74LS221	110p		
74LS244	175p		
74LS245	325p		
74LS251	120p		
74LS257	110p		
74LS290	95p		
74LS293	120p		
74LS366	57p		
74LS373	170p		
74LS374	170p		
74LS375	140p		
74LS377	188p		
74LS393	135p		
74LS490	140p		

74LS		LINEAR IC'S	
74LS00	18p	AY-3-1350	795p
74LS01	12p	AY-3-8910	825p
74LS04	15p	709	30p
74LS08	20p	723	33p
74LS10	19p	741	18p
74LS11	30p	ICL7106	595p
74LS12	30p	ICL7107	695p
74LS14	60p	ICL8038	295p
74LS15	35p	ICM7216A	1875p
74LS20	19p	ICM7216B	1675p
74LS30	19p	ICM7555	80p
74LS32	25p	LM301AM	50p
74LS40	26p	LM311	50p
74LS42	56p	LM318	75p
74LS47	75p	LM324	45p
74LS48	85p	LM339	45p
74LS49	95p	LM380	85p
74LS53	30p	LM496	115p
74LS54	30p	LM1871	550p
74LS57	39p	LM1872	550p
74LS58	39p	LM3900	50p
74LS90	40p	LM3914	225p
74LS107	40p	LM3915	225p
74LS123	89p	LM13600	125p
74LS132	70p	NE555	18p
74LS138	69p	NE556	18p
74LS151	75p	RC4136	85p
74LS153	75p	SN76477N	175p
74LS155	65p	TB8810DAS	85p
74LS163	90p	TLO71	130p
74LS194	75p	TLO82	75p
74LS196	75p	TLO84	110p
74LS198	75p	TL490	175p
74LS199	75p	XR2206	325p
74LS184	90p	ICL2207	375p
74LS168	190p		
74LS174	99p		
74LS175	9		



**Freeport E**  
**Birmingham**  
**B19 1BR**  
**021-233-2400**

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C.MOS (BUFFERED)				LINEAR				SEMICONDUCTORS			
HEF4036	23	HEF4044	105	HEF4512	136	IC3046	84	IN618	5	BC162L	12
HEF4001	22	HEF4046	133	HEF4516	127	CA3080E	77	IN4001	6	BC184	11
HEF4002	22	HEF4047	109	HEF4517	476	CA3130E	99	IN4002	5	BC184L	12
HEF4009	119	HEF4049	67	HEF4518	118	CA3140E	48	IN4004	7	BC212	11
HEF4007	22	HEF4050	57	HEF4519	69	CA3180E	260	IN4007	9	BC212L	12
HEF4008	100	HEF4051	87	HEF4520	119	LM301AN	34	IN4148	4	BC214	11
HEF4011	22	HEF4052	90	HEF4521	225	LM339N	78	IN4542	15	BC214L	12
HEF4012	22	HEF4053	90	HEF4522	124	LM3800N	104	2N2169	21	BC2547	33
HEF4013	57	HEF4056	62	HEF4522	150	LM3818N	198	2N2646	48	BC548	11
HEF4014	105	HEF4067	475	HEF4534	438	LM3900N	75	2N2926G	13	BC549	12
HEF4015	100	HEF4068	100	HEF4539	138	MC330P	156	2N3055	19	BC557	15
HEF4016	57	HEF4069	27	HEF4585	122	NE531	231	2N3054	55	BC568	15
HEF4017	100	HEF4070	22	HEF4274	214	NE536T	259	2N3055	55	BCY70	15
HEF4018	100	HEF4071	23	HEF4007	112	NE565A	28	2N3702	9	BCY71	15
HEF4019	58	HEF4093	23	HEF4009E	92	NE566E	86	2N3704	9	BD131	39
HEF4020	112	HEF4073	23	HEF40106	78	NE566N	171	2N3705	10	BD132	39
HEF4021	107	HEF4075	23	HEF40140	149	NE570N	485	2N3773	297	BD139	39
HEF4022	103	HEF4076	110	HEF40192	149	NE571N	505	2N3819	22	BD140	39
HEF4023	22	HEF4077	22	<b>Voltage Regulators</b>				RC4136	146	2N3820	39
HEF4024	76	HEF4078	23	LM309DAIK1	119	TA8120S	88	2N3904	9	8F X85	233
HEF4025	22	HEF4081	23	UA723CM	42	TA8142Z	73	2N4357	38	8F Y50	117
HEF4026	244	HEF4082	23	UA7805CU	78	TA81034B	239	2N4659	38	8F Y51	17
HEF4027	57	HEF4085	80	UA7812CU	78	TLO81CP	84	40673	88	8R Y39	50
HEF4028	89	HEF4086	80	UA7815CU	78	TLO84CH	156	8C107	14	8R X20	21
HEF4029	113	HEF4091	62	UA7818CU	78	UA7818CN	20	8C108	14	8R Y50	117
HEF4030	58	HEF4094	219	UA7819CU	78	UA7819CT	47	8C108C	18	8R Y51	17
HEF4031	250	HEF4094	219	UA7819CU	78	Zener	BC109	14	8R Y52	54	
HEF4032	138	HEF4095	114	UA7819CU	78	Diodes	BC109C	20	8R Y53	76	
HEF4033	109	HEF4095	114	UA7819CU	78	400mV CAVT.C33	8C148	10	8R Y54	75	
HEF4041	94	HEF4508	200	UA7819CU	78	82Y88/82X79	8C158	10	8R Y55	60	
HEF4042	83	HEF4510	135	UA7819CU	38	* Voltage	8C177	17	T543	36	
HEF4043	100	HEF4511	157	UA7819CU	38						



**PE PHASER UNIT** P.E. APRIL 1979  
A superb six stage phaser that really gives your guitar lift off. Equals the best commercial models. Uses latest FET op-amps. Glassfibre p.c.b.  
**COMPLETE KIT OF ALL PARTS AS SPECIFIED..... £16.50**  
Pack 1. All semiconductor devices..... £8.00  
Pack 2. Resistors, capacitors & preset pot..... £3.75  
Pack 3. Footswitch, jacks, pot, knob, printed circuit & hardware..... £4.76  
Pack 4. Diecast box and feet..... £2.50  
Separate parts: TL062 80p, BF2458 50p, PCB £1.50, 8 pin sockets (not included in kit) 21p each.



**DESIGNER APPROVED KITS**  
**PE SUSTAIN UNIT** P.E. OCT. 1977  
Superb quality, low noise, low distortion sustain unit equal to the very best commercial models. Suits all guitars. Glassfibre p.c.b.  
**COMPLETE KIT OF ALL PARTS AS SPECIFIED..... £8.50**  
Pack 1. Resistors, capacitors & p.c.b..... £1.75  
Pack 2. All semiconductor devices..... £1.75  
Pack 3. Footswitch, jacks, pot, knob, and battery clip..... £3.25  
Pack 4. Diecast box and feet..... £2.50  
Separate parts: XC053R 50p, RPY58A 75p, Printed circuit board 95p, Footswitch £1.80 each.



**ORION AMPLIFIER**  
Complete set of semiconductors..... £9.75  
Quality glass fibre p.c.b., printed with component locations..... £3.50



**PE TV SOUND SEPARATOR**  
Complete set of semiconductors..... £2.30  
High quality glass fibre p.c.b..... £1.60  
Murata filters: SFE6.0MA 50p, CDA6.0MC 50p.

**P.E. SMOOTH FUZZ UNIT**  
(P.E. September 1979)  
This is the Fuzz unit you have been waiting for! Smooth, clean tone with low noise and low current drain. Uses glassfibre p.c.b. and latest FET op-amp.  
**COMPLETE KIT OF ALL PARTS AS SPECIFIED..... £8.50**

POSTAGE & PACKING 25p per order. Orders over £10.00 post free.  
All devices are top grade, brand new and to full manufacturers spec.  
**PRICES DO NOT INCLUDE VAT. Add 15% to all prices.**  
MAIL ORDER ONLY  
CALLERS BY APPOINTMENT  
**DAVIAN ELECTRONICS**  
13 DEEPDALE AVENUE, ROYTON, OLDHAM OL2 6XD.

**GMT SELL PA. EQPT.**

CAPACITORS				Polyester Radial Leads				Electrolytic Radial Leads			
Electrolytic Axial	Order Code	Cap. 0.022 µF	Cap. 0.047 µF	Dipped Type, C280/352 Style	Order Code	Cap. 330 µF	Cap. 330 µF	±10% to +50% Tol.	Order Code	Cap. 0.22 µF	Cap. 0.47 µF
1.0	10	25	40	1.0	10	25	40	1.0	10	25	40
1.5	9	9	9	1.5	9	9	9	1.5	9	9	9
2.2	9	9	9	2.2	9	9	9	2.2	9	9	9
3.3	9	9	9	3.3	9	9	9	3.3	9	9	9
4.7	9	9	9	4.7	9	9	9	4.7	9	9	9
5.6	9	9	9	5.6	9	9	9	5.6	9	9	9
10	9	9	9	10	9	9	9	10	9	9	9
15	8	9	11	15	8	9	11	15	8	9	11
22	8	9	11	22	8	9	11	22	8	9	11
33	8	9	11	33	8	9	11	33	8	9	11
47	8	9	11	47	8	9	11	47	8	9	11
68	8	9	11	68	8	9	11	68	8	9	11
100	9	10	13	100	9	10	13	100	9	10	13
150	9	10	13	150	9	10	13	150	9	10	13
220	13	20	36	220	13	20	36	220	13	20	36
330	13	20	40	330	13	20	40	330	13	20	40
470	10	22	32	470	10	22	32	470	10	22	32
680	21	30	38	680	21	30	38	680	21	30	38
1000	26	30	59	1000	26	30	59	1000	26	30	59
1500	35	38		1500	35	38		1500	35	38	
2200	42			2200	42			2200	42		

RESISTORS				Skeletal Presets, Miniature			
Carbon Film, Fixed	Order Code	Rev. RD1	Rev. RD4	0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting	8	Min. Preset V	Order Code
0.25W, E24 Values, 10R-10M, 5% Tol.	2 each			0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8	Min. Preset V	
0.5W, E12 Values, 10R-4M7, 10% Tol.	3 each			0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting	11	Std. Preset V	
Metal Film, Fixed	Order Code	Rev. RD30	Rev. RD52	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11	Std. Preset V	
0.5W, E24 Values, 5R-10M, 2% Tol.	8 each			Potentiometer, Rotary			
2.5W, E12 Values, 10R-27K, 5% Tol.	16 each			0.5W, E3 Values, 1K-2M2 Lin.	39	Ro Pot Lin	
Metal Glaze, Fixed	Order Code	Rev. VR37		0.25W, E3 Values, 4K7-2M2 Log.	39	Ro Pot Log	
0.5W, E24 Values, 1M-33M, 5% Tol.	16 each			Potentiometer, Slider			
0.1W, E24 Values, 10R-10M, 5% Tol.	16 each			0.5W, E3 Values, 2K2-4K7, Lin.	45	S Pot Lin	
0.1W, E24 Values, 10R-10M, 5% Tol.	16 each			0.25W, E3 Values, 1K0-1M0 Log.	48	S Pot Log	

**SEND A LARGE SAE. FOR OUR 'FLOG LIST' & OTHER INFO.**

MAINS TRANSFORMERS				Plastic Boxes - Boss Industrial Mouldings			
Secondaries may be connected in series or parallel to give wide voltage range				Moulded Box and Close Fitting Flanged Lid			
Primaries 0-270, 240V				ABS Box, C/W Brass Bushes, and Lid In Orange			
BVA - Clamp Type Construction	235 each			L112 W82 D31	90	Case B1M2003 OR	
Approx. 18% Regulation F.C. 54, H36, W35				L150 W80 D50	121	Case B1M2005 OR	
0-4.5V, 0-4.5V Secondaries	9	Trans 6VA		L190 W110 D80	223	Case B1M2008 OR	
0.5V, 0.5V				Plastic Boxes with Metal Lids			
0.12V, 0.12V				Recessed Top Box			
0.15V, 0.15V				ABS Box, C/W Brass Bushes, In Orange			
0.175V, 0.175V				Trim Aluminium Top Panel Finished Grey			
0.20V, 0.20V				L85 W58 D28	112	Case B1M4003 OR	
20V A - Clamp Type Construction	360 each			L111 W71 D42	150	Case B1M4004 OR	
Approx. 16% Regulation F.C. 70, H48, W46				L181 W98 D53	208	Case B1M4005 OR	
0-4.5V, 0-4.5V Secondaries	9	Trans 20VA		Diast Boxes			
0.5V, 0.5V				Diast Box and Flanged Lid			
0.12V, 0.12V				Aluminium Box and Lid In Natural Finish			
0.15V, 0.15V				L112 W82 D31	126	Case B1M5003 NA	
0.175V, 0.175V				L152 W82 D50	215	Case B1M5005 NA	
0.20V, 0.20V				L182 W113 D81	334	Case B1M5008 NA	

VERO ELECTRONICS PRODUCTS				SWITCHES			
2.5" x 5" 11" pitch Veroboard	71	200-21069J		Miniature Toggle - Honeywell			
3.75" x 5" 11" pitch Veroboard	79	200-21072D		SPDT			
2.5" x 11" 11" pitch Veroboard (SI)	85/Pack	200-21076E		SPDT C/O/F	67	SW 8A1011	
3.75" x 11" 11" pitch Plain Board	65	200-21078H		SPDT Double Box To Centre	81	SW 8A1021	
5.82" x 2.9" 11" pitch V-DIP Board	135	200-21084E		DPDT	90	SW 8A2011	
Spot Face Cutter	107	200-21013A		DPDT C/O/F	111	SW 8A2021	
Pin Insertion Tool for .040 type pin	147	200-21015E		Miniature Push - C & K			
DS Pins .040 (100)	44/Pack	200-21087G		SP Push To Make, Momentary	62	SW 8531	
55 Pins .040 (100)	44/Pack	200-21017H		SP Push To Break, Momentary	82	SW 8533	
Verobase Kit (100, 2-wire, 75-comb)	484/Kit	200-21041D					
Verobase Combs (24)	109/Pack	200-21339F					
Verobase Woz (2)	109/Pack	200-21340G					

G.M.E. ELECTRONICS KITS			
FLUX THERMIST KIT			£199.00
TELETYPE JITTERER - REMOTE CONTROL KIT			£12.90
PAL VIDEO MODULATOR KIT			£22.90
DOPPLER RADAR ALARMS KIT			£44.90
1 T. POWER AMPLIFIER OUTPUT MODULE KIT			£220.00
ONE AMP POWER SUPPLY MODULE KIT - FIVE VOLTS			£54.00
TWO AMP POWER SUPPLY MODULE KIT - FIVE VOLTS			£72.00
MODEL INERTIA CONTROLLER FOR R.F. JET ENGINE			£30.00
MODEL INERTIA CONTROLLER FOR R.F. TRAIN HAND UNIT			£29.00
MODEL INERTIA CONTROLLER FOR R.F. CONSOLE UNIT			£29.00

**GMT ELECTRONICS, P.O. BOX 290, HAMPTON STREET, BIRMINGHAM B19 3JR**

**Be an ELECTRONIC ENGINEER**

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.  
Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.  
You risk nothing! We promise to get you through your chosen course-or, refund your fee!  
So, join the thousands who have built a new future through home study Engineering courses.

- Courses in
- C & G Elect. Technicians
  - C & G Elect. Installations
  - Telecomms. Technicians Exams
  - Television Servicing
  - Radio Maint. & Repairs (BIET)
  - Pract. Radio & Electronics
- Plus over 60 other home study courses.

**POST COUPON FOR FREE 44 PAGE GUIDE**

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Aldermaston Court, Dept. TPE06, Reading RG7 4PF.

NAME (Block capitals please) \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
POSTCODE \_\_\_\_\_  
Other Subjects \_\_\_\_\_ AGE \_\_\_\_\_  
Accredited by CACC Member of ABCC

1

**GENTS QUARTZ LCD.** 5-function. Hours, minutes, secs, month, date, backlight. **ONLY £4.95**

2

**GENTS QUARTZ LCD.** SAME AS 1 - Alternative style. **ONLY £4.95**

3

**QUARTZ LCD Slim Chronograph.** 11-function. Hours, mins, secs, 6 digit-month, date, day of week, 1/100 sec stopwatch, split and lap modes, backlight. **ONLY £7.95**

4

**QUARTZ LCD ALARM.** 6 digit, hours, mins, secs, day, date. 24-hour alarm with on/off indicator. **ONLY £8.95**

5

**QUARTZ LCD Alarm/Chronograph.** 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split and lap modes, 12 and 24 hour modes, 24 hour alarm. **ONLY £12.95**

We don't believe you can find better value combined with quality, than these - our special introductory prices. Compare the savings we offer and order now.




6

**QUARTZ LCD Musical Multi-Alarm/Chronograph.** 6-digit. Hours, mins, secs, day, date, 1/100 second stopwatch, split and lap modes, 24 hour alarm, dual time zone. **ONLY £13.45**

14

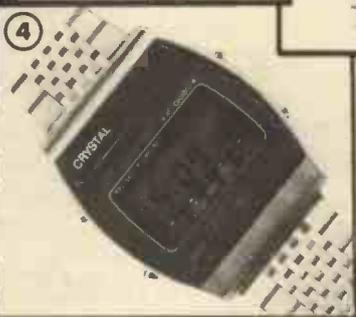**CREDIT CARD CALCULATOR.** Very slim with standard 4 functions plus memory, percentage and square root. Complete with a mock leather wallet with credit card pocket. **ONLY £6.95**



5



6



7

**SINCLAIR PROGRAMMABLE SCIENTIFIC CALCULATOR**

Genuine programmable model using micro processor technology, this amazing device is more like a computer than a calculator. Complete with programme library book containing approx. 370 programmes for ELECTRONICS, MATHS, PHYSICS, ENGINEERING ETC. Limited quantity available.

**ONLY £7.95**  
+ 75p carriage.

13

**BELTIME 29F. Alarm/Chrono.** Advanced and accurate, this watch has 8 time functions, 4 alarm functions and 17 chronograph functions. Complete with backlight and stainless steel bracelet. **ONLY £19.95**



8




8

**LADIES QUARTZ LCD.** 5-function as Gents No. 1. Available with black or white face. **ONLY £5.95**

12

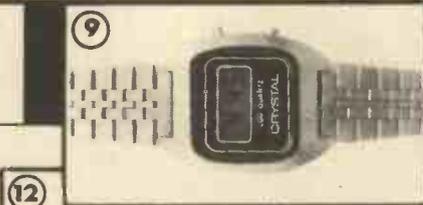**GENTS ANALOGUE QUARTZ.** Conventional display, accuracy normally associated with digital watches. Automatic calendar, elegant and robust. **ONLY £19.95**



10



9

**LADIES QUARTZ LCD.** SAME FUNCTIONS AS 8. - Alternative style. Available with black or white face. **ONLY £5.95**

11

**LADIES QUARTZ LCD SAME AS 10.** Alternative "Round" shape. Available in gold or silver colour. **ONLY £8.95**



13



All watches have fully adjustable, matching stainless steel straps, and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required.

10

**LADIES QUARTZ LCD.** 5 functions. Dress Style. Functions same as 1. Available in gold or silver colour. **ONLY £8.95**



14



All products carry a Full 7-Day Money-Back Reassurance, plus 12-Month Guarantee. Prices include VAT.

Send stamped addressed envelope for Colour Brochure of 120 other bargains.

**BEELMOOR LTD**

**78 CASTLE STREET,  
MELBOURNE, DERBY,  
DE7 1DY**

Please send me items..... (list numbers)

I enclose cheques/P.O.s for £.....

NAME.....

ADDRESS.....

Please add 35p P/P per item

PE4

# Britain's first com puter kit.

## The Sinclair ZX80.

# £79.95

Price breakdown  
ZX80 and manual: £69.52  
VAT: £10.43  
Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

### 'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); *everything!*

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done; connect it to your TV... link it to an appropriate power source\*... and you're ready to go.

#### Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be **SAVED** and **LOADED** on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

#### Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

\*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

### The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:


- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing: Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions. USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

### Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines. And Benchmark tests show that the ZX80 is faster than all other personal computers.

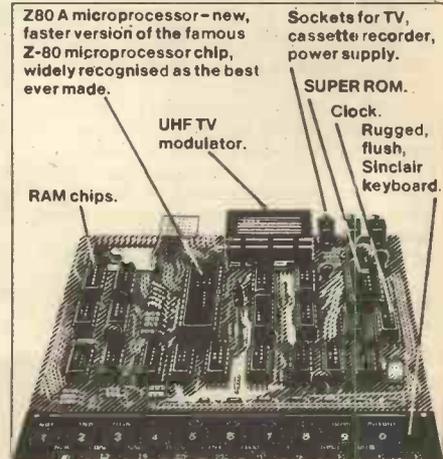No other personal computer offers this unique combination of high capability and low price.





# CONSTRUCTORS PACK 7

## ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

**\* EASY TO BUILD \* 5 PUSH BUTTON TUNING \* MODERN STYLING DESIGN \* ALL NEW UNUSED COMPONENTS \* 6 WATT OUTPUT \* READY ETCHED & PUNCHED P.C.B. \* INCORPORATES SUPPRESSION CIRCUITS**



The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue.

The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia.

The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit.

The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

**£10.50** p&p £1.75

**CONSTRUCTORS PACK 7A**  
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

**£1.95** Per Pack, p & p £1.00.  
Pack 7A may only be purchased at the same time as Pack 7.

**NOTE:** Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

**A FEATURED PROJECT IN PRACTICAL ELECTRONICS**



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.  
21B HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm  
Closed Thursday

### NEW 12+12

#### AMPLIFIER KIT

An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 3/4" x 4" approx. **£13.95** p&p £2.55

**TWO WAY SPEAKER KIT** To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65.

Available only to first time purchasers of the 12 + 12 kit.

### 50WATT MONO

#### DISCO AMP

**£30.60**  
p&p £3.20

Size approx 13 1/4" x 5 1/4" x 6 1/4"  
50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infra-red push-pull switches. Independent bass and treble controls and master volume.

### NOW AVAILABLE

#### 30 + 30 WATT STEREO AMPLIFIER

Vacuum TV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/4" x 3 1/4" x 10" approx. **£32.90** p&p £3.30

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

## Mullard

### AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

**£25 PER PACK** SEE OUR PRICES

**1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input **OUR PRICE** p&p £1.10 **£5.00**

**2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs **illus. OUR PRICE** p&p £1.15 **£7.65**

**ACCESSORIES** Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

**Two Way Speaker Kit** Comprising of two 8" x 5" approx. 4ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p **£4.05**

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS

**£76.00** p&p £4.00  
**100 WATT MONO DISCO AMP**

Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10 1/4"  
Five vertical slide controls, master volume, tape level, mic level, deck level.  
**PLUS INTER DECK FADER** for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak

### EMI SPEAKER BARGAIN

Stereo pair 350 lt. System consists of 13" x 8" approx woofer with rolled surround, 3 1/4" Goodman speaker crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

**£18.25**  
Per stereo pair p&p £4.20

### BSR P200

**£25.50**

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00  
Shure M75 6 Magnetic Cartridge to suit. **£7.95**



**BSR** Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use. **OUR PRICE** p&p £2.75 **£12.25**

### PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY.

### BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. **OUR PRICE** p&p £2.50 **£11.95**



323 EDGWARE ROAD, LONDON W2  
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
**ALL PRICES INCLUDE VAT AT 15%**  
All items subject to availability. Prices correct at 8.7.80 and subject to change without notice.  
All enquires Stamped Addressed Envelope.

**NOTE:** Persons under 16 years not served without parent's authorisation.

## VALUE

**N**EXT month your copy of PE will cost 65p. Value for money? We think so, but we are operating in one of the few areas of technology which has been characterised by falling prices over the years.

Back in November 1964 (Vol. 1 No. 1) PE was 2/6d or 12½p in modern terms. Next month PE will cost more than five times that price. An Armstrong AM-FM Tuner Amplifier advertised in that first issue cost just £37.10.0 and 37 feet of solder was 5/-; no VAT to add on in those days! So, although the price of technology has fallen, a five times increase on the cover price does not seem wildly out. Add to that the fact that the issues were then a smaller size and yes, we do still think PE is good value.

Fortunately, it would appear that many of you concur with our views as PE has been privileged to boast the highest total sales of any British electronic constructors' magazine for the past three years; we still hold that position. This boast is based on Audit

Bureau of Circulation figures of total copies sold.

## OFFERS

As we have pointed out in the past, we believe our special offers give excellent value for money; this issue carries a double autoranging multimeter offer (page 57) and a corrected re-run of our Casio watch offer. There were some errors in the original Casio offer so we have published corrections and re-run it. If you took advantage of the previous offer, or if you are interested in a Casio watch at discount, turn to page 65.

## FREE

Next month you will also get a free *Transistor Identichart* (see page 63) with your issue and November will carry another free chart. We have plenty of exciting projects planned for future issues and are anticipating other special giveaways and offers.

As we have said, PE is number one and we intend to stay there.

## RECESSION

The country may be in a period of recession but we believe that this will only increase activity in the hobby electronics field. If you can build a project for half the cost of a commercial unit, it could make all the difference. To those that read more than do, perhaps being forced into something by economics will prove to be very enjoyable.

Even in these dark days when we are regularly fed on the alarming jobless figures and listen with dismay to reports of school leavers without jobs, the electronics industry in general continues to thrive. It is interesting to note that recent issues of such publications as *Computer Weekly* continue to be fat with job advertisements. There is much to encourage youngsters to take up electronics!

*Mike Kenward*

## EDITOR

**Mike Kenward**

**Gordon Godbold** ASSISTANT EDITOR

**Mike Abbott** TECHNICAL EDITOR

**David Shortland** PROJECTS EDITOR

**Jasper Scott** PRODUCTION EDITOR

**Jack Pountney** ART EDITOR

**Keith Woodruff** ASSISTANT ART EDITOR

**John Pickering** SEN. TECH. ILLUSTRATOR

**Isabelle Greenaway** TECH. ILLUSTRATOR

**Colette McKenzie** SECRETARY

### Editorial Offices:

Practical Electronics,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191

**We regret that lengthy technical enquiries cannot be answered over the telephone (see below).**

### Advertising Offices:

Practical Electronics Advertisements,  
King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Telex: 915748 MAGDIV-G

**Make Up/Copy Dept.: 01-261 6601**

## ADVERTISEMENT MANAGER

**D. W. B. Tilleard**

SECRETARY **Christine Pocknell**

} 01-261 6676

AD. SALES EXEC. **Alfred Tonge** 01-261 6819

CLASSIFIED MANAGER **Colin Brown** 01-261 5762

## Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

## Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

## Binders

Binders for PE are available from the same address as back numbers at £4.30 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

## Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

# Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by  
**David Shortland**

## FABULOUS FRED

A new electronic entertainments centre which looks as if it will be fun for adults as well as children is now available from Optim Toys.

Fabulous Fred incorporates ten different electronic games which use a sound generator as well as a visual display. The nine-note keyboard can be used as a simple organ, and the memory allows tunes of up to 50-note length to be keyed in and played back.



Other games include 'Space Attack', 'Submarine Hunt', and 'Catch the Comet'. 'Baseball' and 'Roulette' are more complicated and involve the use of a board and betting chips.

Fabulous Fred should be available from many toy shops at around £25.

## DIRECT TO WIRE

A new Direct to Wire Kit which offers 1,000 connections has been introduced by Verospeed.

Based on the GTH contact patented by BICC-Burndy, the kit includes eight types of

and  
**Jasper Scott**

connector interlinked with M100 10 way ribbon cable, supplied on two reels, and a selection of pre-stripped ribbon cable in various lengths. Gas tight connections are achieved by direct insertion of tinned, stranded or solid conductors into the contact assemblies, thus precluding the use of noble metals and making considerable cost savings.




The kit offers the Research and Development Engineer the ability to incorporate the same products that are used in production and eliminates the need for value engineering.

Verospeed stock all replacement parts, which are also available individually. The kit is priced at £39.95, and is available direct from: Verospeed Ltd., Stansted Road, Boyatt Wood, Eastleigh, Hants. SO5 42Y (0703 618525).
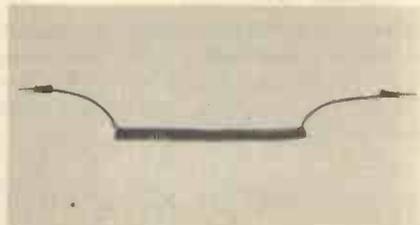
## COILY JUMPERS

The range of EZ test hooks, with their 'hypodermic' finger action, has been further extended by coil jumper leads.

To allow greater flexibility of movement, when making test connections, EZ Hooks are being introduced joined by a p.v.c. coil cord—gauge 22SWG 26 x 36—which will expand



from closed position of 180 to 900mm. The various size Hooks (44, 57 and 127mm) are all available in ten colour-coded colours connected by self-coloured cord. Further information on the entire range of EZ Hooks is available from: British Central Electrical Co. Ltd. (International Division), Unit 10, Carvers Industrial Estate, Southampton Road, Ringwood, Hants. BH24 1JS (04254 4617).

## COMPUTER ACCESSORIES

A new microcomputer case which is suitable for the UK101, Superboard and Nascom 2 has just been introduced by Microtype. Known as the Model 3, it succeeds Microtype's previous model and is considerably larger than other cases on the market, with space for expansion boards, fan ventilation or other additions. Made in black ABS plastic, the Model 3 can be sprayed with cellulose based car paints if a different colour is required. A pre-cut keyboard panel is available for UK101, Superboard and Nascom 2 and a blank panel is available for those with 'homebrew' computers.



The price for the Model 3 is £29.90 including VAT and postage.

Also available from Microtype is their Stak-Pak, a very neat cassette filing and storage system which should solve your program storage problems. The Stak-Pak consists of drawer sections in black plastic which lock together to form miniature cabinets of almost any height. Each drawer holds two cassettes and comes complete with index cards as well as two cassettes each loaded with 12 minutes of Agfa tape.

The price for five Stak-Pak drawer sections is £6.60 including VAT & postage.

Microtype, PO Box 104, Hemel Hempstead, Herts. HP2 7QZ.

## RECHARGEABLE BATTERIES

If you're fed up with constantly having to replace the batteries in your portable radio or electric shaver, you may be interested to know that a range of rechargeable cells from the Furukawa Battery Co. is now available from Marshalls, together with a range of constant current chargers made by Friemann & Wolf.


The Nickel-Cadmium cells which are of the sealed sintered-plated type come in three different sizes, equivalent to HP7, HP11, and HP2 dry batteries. In normal use, a life of roughly 500 charge/discharge cycles may be expected.

The Friemann & Wolf (FRIWO) chargers are available in two basic types, both being double insulated and meeting SEMCO, NEMCO and DEMCO standards. The smaller of the two, the Penlight 4, accommodates up to four HP7 size cells, and maintains a charge rate of 50mA nominal. All three sizes of cell can be charged using the larger Combibox FW611, and the charge current can be switched from 50mA to 120mA to give overnight recharging for each size.

Prices for the cells and chargers are as follows: S101 (HP7)—£0.98; sub C (HP11)—£1.75; sub D (HP2)—£1.95; Penlight 4—£5.50; Combibox FW611—£13.25. Further information is available from: A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA.
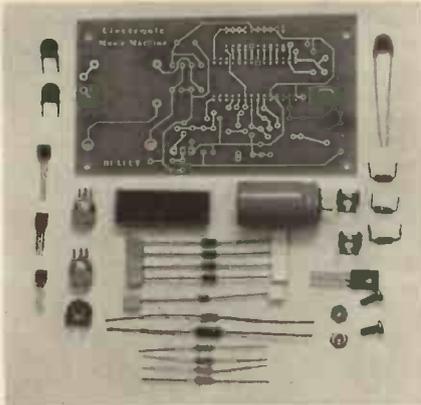
## MACLIN ZAND

Two new kits from Maclin Zand feature an electronic music generator and a sound effects unit. The music generator which can be used as a doorbell, toy or music box is pre-programmed to play 25 songs and three chime sequences. The song memory is an integral part of the chip and therefore cannot be re-programmed.



The sound effects board has been designed around the SN76477 sound generator and includes a noise generator, VCO, noise filter, mixer, attack/decay circuit, audio amplifier and control circuitry. A prototype area is provided on the p.c.b. for experiments and among the many sounds available are one-shot controls for gun shots, explosions etc., bird sounds, sirens, race car crashes, steam trains, etc.,


The music generator is priced at £9.95 and the sound effects board is £14.99. Both prices exclude VAT and p&p.

Maclin Zand Ltd., 38 Mount Pleasant, London WC1X 0AP.
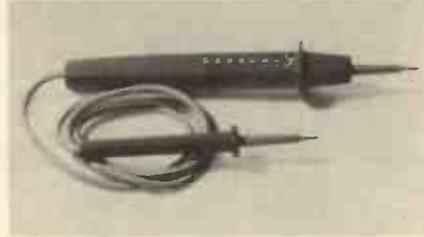
## DOUBLE POLE TESTER

A range of pocket sized double pole testers is now available from Branco Tools Ltd.

The cheapest of the range is the Volt Check, which indicates a.c. and d.c. voltages between 4.5V and 415V and indicates d.c. polarity. In the middle of the range is the Multi Check which checks continuity between 0 and 20k $\Omega$  and the direction of semiconductors, as well as indicating voltages within the same range as that of the Volt Check.




Pictured above is the Master Check, which measures d.c. and a.c. voltages in seven steps from 6V to 415V and indicates polarity. Prices range from £4.30 for the Volt Check to £14.24 for the Master Check. Further information on the whole range of testers is available from:

Branco Tools Ltd., 7 Birchway, Prestbury, Cheshire SK10 4BD (0625 828478).
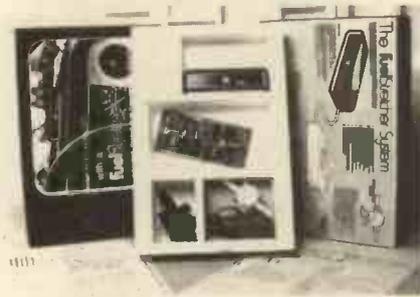
## FUEL METERS

Two new petrol consumption meters are now available from Enviro-Systems in kit form. The FSX20 provides a system which will give an instantaneous digital readout of MPG, with a choice of two update frequencies to suit individual driving conditions, automatic clear-down under idling and simple owner calibration facility, which means the system is suitable for most vehicles with carburettor fuel systems and cable driven speedometer. A petrol injection option is available to compensate for fuel returned to the tank.



The FSX10 provides a total gallons used read-out, and the overall fuel consumed with the average MPG. This kit requires a fuel sensor input only.


Both kits are suitable for 12V negative earth vehicles only and come complete with digital transducers, p.c.b.s and all components. Construction and installation instructions are provided and a technical back-up service is available.

The FSX20 is priced at £47.50, the FSX10 is £34.80 and the petrol injection option is £65.90.

Enviro-Systems, Hampsfell Road, Grange-over-Sands, Cumbria LA11 6BE.
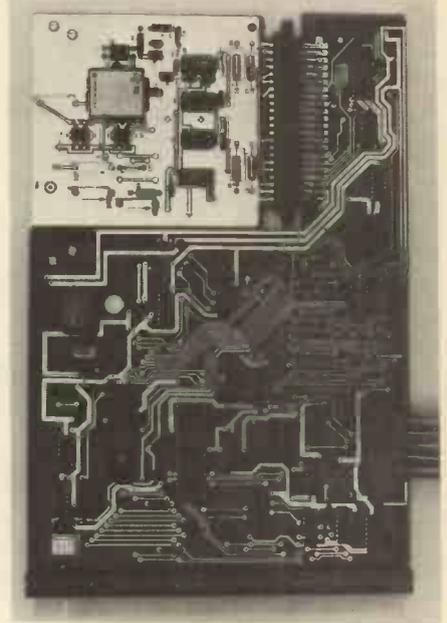
## NASCOM MEMORY

Microdata Computers are now offering a combined bubble memory and real time clock board which can be plugged into the standard 77-way NASBUS. The capacity is 92,304 bits and the initialisation routines and operating system are supplied in a 2708 EPROM. They may be relocated anywhere within the RAM area and will operate with the NAS-SYS, T2, T4 and B-Bug monitors. Organised as 144 minor loops of 641 bits each, the average access time to the first bit of data is 4 milliseconds.



The real time clock has a deac battery back up, the capacity is sufficient to power the CMOS clock chip for approximately 12 months in the absence of system power.

The price of the complete board is £750 excluding VAT and p&p.

Microdata Computers Limited, Belvedere Works, Bilton Way, Pump Lane, Hayes, Middlesex.

## SUPERPET

Commodore's new '8000 Series' system which has been nick-named the SUPERPET, consists of an 80-column version of the popular 32K PET. Text editing and report formatting are faster and easier with the new wide screen display and the 8032 provides a resident operating system with expanded commands and functions for arithmetic, editing and disk management. For data input/output applications, an 8-bit parallel Port and an IEEE-488 instrumentation bus are provided. The 8032 includes a 73-key full business style keyboard and is priced at £895 plus VAT.

Also available is the new 8050 dual drive floppy disk which has been designed to complement the 8032. The 8050 incorporates all the existing features of the current disk unit, but provides more powerful software capabilities and a one megabyte capacity.

The 8050 which is priced at £895 plus VAT utilises five 1/4" diskettes and Micropolis drives.

Commodore Business Machines Limited, Information Centre, 360 Euston Road, London (01-388 5702).

# Semiconductor UPDATE...

FEATURING NSC800 74LS610 MA537

R. W. Coles

## COMPATIBLE MICRO (NSC 800)

All you microprocessor fans who have plumped for the Intel 8080 family as your "pin-up" chip, need not worry about the obsolescence of all that hardware and software knowledge you have amassed. Many of you may have already upgraded to the Z80 processor from Zilog, and gained those by now well-known benefits of a more powerful instruction set, more CPU registers, and on-chip refresh for dynamic memories. Going from the 8080 to the Z80 is easy because the 8080 instructions are a sub-set of the Z80 codes and most 8080 programs will run immediately on the Z80 with no alterations, an important advantage while system software is costing more than system hardware in many situations.

Intel's own improved 8080, the 8085, takes a different line by keeping an almost identical instruction set with only limited enhancements while reducing system hardware complexity and the need for peripheral devices by providing more "on-chip" functions such as clock oscillator, bus controller, serial I/O, and several levels of direct-vector interrupt inputs. The 8085 also runs from a single 5 volt supply, like the Z80 but unlike the 8080, and it runs faster than both the 8080 and the Z80. The extra on-chip functions provided by the 8085 need extra pins which are not normally available within the limitations of a 40 pin package. Intel solved this problem by multiplexing the 8 data bus lines so that they also carry the 8 low order address bits during certain sections of an instruction cycle, as flagged by the ALE (Address Latch Enable) output. The L in ALE means, of course, that the availability of address information on the bus for only a limited period has to be overcome by latching this information externally. This need is normally satisfied by the use of special 8085 peripheral chips such as the 8155 RAM/I/O/TIMER chip, and the 8355 ROM/I/O chip which have internal address latches.

In short, you have a choice for 8080 upgrade. Choose either the big system power of the Z80 or the compact simplicity of the 8085 and its multiplexed bus.

Well, anyway, you *did* have to choose until recently, before National introduced the NSC800, a chip which must make all '80 fans drool with anticipation! Taking compatibility one stage further, National have made their new processor emulate both the 8085 and the Z80 by combining

the power of Z80 instruction set with the simplicity of the 8085 bus. As if that in itself were not sufficient, National have also made other improvements to rectify some of the deficiencies of it's ancestors.

The most fundamental change is in the semiconductor technology used, NMOS for the 8080, Z80, and 8085 and a new CMOS process called P<sup>2</sup>CMOS for the NSC800. The advantage here is the wide supply voltage range possible (3 to 12 volts) and the very low power consumption which makes battery operation a real possibility. Despite its low power consumption the new chip will run as fast as the Z80 even to the extent of having a 4MHZ high speed version, the NSC800A which equates to the Z80A.

One problem with the Z80 is that the useful on-chip refresh for dynamic memories has only a 7-bit counter, and this makes it difficult to use with the coming generation of 64K RAMs which need 8 bits. The NSC800 overcomes this shortcoming by providing the eighth bit.

So far as I know, this device is not widely available yet, but when it is, it must surely become the eighth bit standard for future designs.

## MAP CHIP

Still on the subject of microprocessors, it seems that the 64K address space of most micros, which has always seemed so huge that one could never imagine having the funds to fill it, is about to become *too small!*

The reason is that memory is getting cheaper and cheaper, and soon it will take just eight 16 pin chips to give a system all the memory it can address, thanks to the 64K dynamic RAM devices now becoming available from Motorola, Texas Instruments and others. The effects this plentiful memory will have on system software and programming in general will be far-reaching, but down at the hardware level there will be the problem of how to address more than that restrictive 64K.

One possible solution is now available from Texas instruments in the form of a family of "Memory-mapper" devices which can be used to increase the memory space of, say, a 6800 or 8080 microprocessor to an incredible 16 megabytes! Now even if 64K RAM chips drop in price to £10 each, a quick sum reveals that to fill that space you would need to raise over £20,000 for memory alone, so it seems likely that the problem has been solved for all time!

The new devices, part of the Low Power Shottky TTL family and coded 74LS610 to 74LS613, provide an extra eight bits of addressing to give a total of 24 for most micros. Address expansion is achieved by using the top four bits of the standard address bus to select one of sixteen twelve bit registers within the map chip. The contents of the selected register provide twelve further address bits to give the total of twenty-four required, effectively splitting the memory map up into 4096 pages each of 4096 words. The registers within the mapper have to be loaded under software control of course, and this makes the expansion scheme less "transparent" to the programmer than a conventional twenty-four bit address counter. Since most programmers interact with their system via system software, however, this need not be a problem in day to day usage. A likely technique would be to load the registers with the addresses of consecutive 4K blocks to provide a single 64K 'Environment'. When more memory is needed, for a second user for example, system software would reload the registers to access further 64K blocks. A total of 256 blocks are available, although it is most unlikely that all this space would be needed in any practical system.

The attraction of these devices is really that they will allow the upgrading of an "old fashioned" eight bit system to suit future system software. Whether it will be better to throw the old eight bit chips away and go for one of the new sixteen bit devices such as the Z8000 or the 8086 which can already access more memory via an expanded address counter, remains to be seen.

The new devices run from standard TTL supplies and are housed in forty pin packages.

## BIG IMAGE (MA537)

I realize that my offerings so far this month are not the sort of devices which the average reader is likely to be able to (or want to!) rush out and buy just yet. My final offering is even more exotic I am afraid, but nevertheless it does provide a fascinating glimpse of the capabilities of a British electronics firm, and a hint of what the future holds for us. After all, today's exotic device is tomorrow's 'jelly-bean' part!

The device in question is made by GEC and coded the MA537, and it is a complete solid state TV image sensor in a very tiny package. On the face of it, it appears that this device opens the door to tiny video

cameras no bigger than, say, an instamatic, with full 625 line capability and a performance approaching that of conventional camera tubes. Combine a device such as with the LED and LCD image displays currently under development, and it seems likely that the whole concept of television and home video recording will be revolutionised within the next decade.

The MA537 is a CCD or 'Charge Coupled Device' image sensor which has an 8.5mm by 6.4mm sensor surface covered with an array of 576 by 385 photo detectors, all on one chip of silicon. The chip is split into two

roughly equal sections, one being used for image sensing and the other half for storage. The image sensor provides a basic 288 line picture, with each line resolvable into 385 'pixels' or picture points, but by means of an ingenious trick with the clocking of the CCD image registers the number of lines is effectively doubled to provide compatibility with the interlaced 575 line image used in the so-called 625 line system. (The other lines are never displayed and form part of the field blanking interval.) The store half of the array is also photo sensitive but is normally shielded from any il-

lumination and used as a buffer to aid the transfer of data out of the device. Left unshielded, however, it can be used to provide a full-frame mode for enhanced resolution in special applications. In the normal mode, line image information is shifted out via a 400 element CCD analogue shift register, the extra 15 elements being available to provide a black reference level for each line.

The MA537 is packaged in a 30 pin flat-pack and would probably cost an arm and a leg at present, but come the revolution...

Nice try G.E.C., but now how about a colour version?

## Countdown

**Edtech** Aug. 19-21. Holland Park School, London. **C1**  
**Personal Computer World Show** Sept. 4-6 Cunard Hotel, Hammersmith, London. **M**

**Laboratory** Sept. 9-11. Grosvenor Ho., Park Lane, London. **E**

**Intron 80** Sept. 9-11. RDS, Simonscourt Pavilion, Dublin. **V**

**West of England Electronics Exhibition** Sept. 9-11. Bristol Exhibition Centre. **Q**

**Electrathon** (Lucas battery vehicle race) Sept. 13, 1980. Fashioned on last year's event, this "whispering Grand Prix" is a contest for home made electric vehicles. It will again be held at Donington Park Race Circuit, nr. Derby. Details: £ 021-554 5252.

**Avionics** (symposium) Sept. University of Surrey. **S1**

**Emix** (Electronic Measuring Instruments Exhibition) Sept. 30, Oct. 1-2. Post House Hotel, Southampton. **I**

**BEX** (Business Equipment Exhibition) Oct. 1-2. The Guildhall, Plymouth. **K**

**Emix** Oct. 7-8. Centre Hotel, Newcastle. **I**

**Emix** Oct. 14-15. Guildhall, Cambridge. **I**

**Drive Electric** October 14-17. Wembley Conf. Centre, London. organiser: £ 01-834 2333.

**BEX** Oct. 15-16. Assembly Rooms, Edinburgh. **K**

**Engineering Ireland** Oct. 15-18. Leopardstown Exhibition Centre. **V**

**Testmex** (exhibition and conference) Oct. 28-30. Wembley Conference Centre. **T**

**Viewdata Exhibition for Professional & Business People** Oct. 29-31.

West Centre Hotel, London. **Z1**

**Compec** Nov. 4-6, Olympia. **Z1**

**BEX** Nov. 5-6. Sophia Gardens, Cardiff. **K**

**Semiconductor International 80** Nov. 25-27. Metropole Convention Centre. **T1**

**Breadboard** Nov. 26-30. Royal Horticultural Halls, Westminster. **T**

**Microsystems 81** (exhibition and conference) March 11-13, Wembley Conference Centre, London. **Z1**

**Inspex 1981** March 16-20. NEC Birmingham. **Z1**

**Computer Graphics 1981** April 28-30. The Barbican Centre, London **O**

**Entertainment 81** May 9-17 (weekly mornings trade only). NEC Birmingham. **B2**

**Components 81** (Electronic Components Industry Fair) June 9-12, 1981. Earls Court, London. This show will alternate yearly with *Electronics*, now the IEA amalgamation with Electrex has ceased. **I**

**Solar Energy Exhibition** Aug. 23-28, 1981. Brighton. **M**

**International Business Show 1981** October 20-29. NEC Birmingham. **A2**

**Electronics 82** (formerly IEA, but now sub-titled International Electronics, Control and Instruments Exhibition) May 24-28, 1982. NEC. This show will alternate yearly with *Components* now that the IEA/Electrex amalgamation has ceased. **I**

**E** Evan Steadman. £ 0799 22612

**I** ITF. £ 021-705 6707

**K** Douglas Temple Studios, 1046 Old Christchurch Rd., Bournemouth.

**M** Montbuild. £ 01-486 1951

**O** Online Conferences. £ 0895 39262

**Q** Exhibitions For Industry Ltd. £ 08833-4371

**T** Trident International Exhibitions. £ 0822 4671

**V** SDL Exhibitions, 68 Fitzwilliam Square, Dublin, Ireland.

**C1** Stereoscopic Television Ltd., 41/43 Charlbert St., St. John's Wood, London NW8 6JN. £ 01-722 4139

**S1** Society of Electronics & Radio Technicians, 57-61 Newington Causeway, London SE1 6BL. £ 01-403 2351

**T1** Kiver Communications U.K., Millbank House, 171/185 Ewell Road, Surbiton, Surrey KT6 6AX

**Z1** IPC Exhibitions Ltd., 40 Bowling Green Lane, London EC1R 0NE. £ 01-837 3636

**A2** Hart Browne & Curtis Ltd., 29 Sackville Street, Piccadilly, London W1X 1DB. £ 01-439 8556

**B2** Brintex Exhibitions Ltd., 178-202 Great Portland Street, London WIN 6NH. £ 01-637 2400

## POINTS ARISING

### ACORN REVIEW (August 1980)

Acorn Computers Limited are the suppliers of the Acorn modular system, peripherals and software reviewed last month. Science of Cambridge are not connected with this product and were incorrectly referred to. We apologise for any inconvenience caused.

### COMPUKIT UPDATE (June 1980)

There is an error in Fig. 1 showing the software Baud rate circuit around IC57. RTS from IC14, pin 5, should go to IC57 pin 5 and *not* pin 4. On IC57, pins 3, 4 and 6 go to 0V.

### P.E. DMM (July 80)

In Fig. 5 the component overlay shows R6, 7, 8 (lower left) incorrectly numbered. They should be R9, 10, 11 respectively.

### MICROPROMPT (July 1980)

Line 40 in Le Passe-Temps should read: **DIMS (44)**, etc., Line 830 should read: **T(I) = T(I) + etc.**

### CONSTANT CURRENT SOURCES (August 1980)

There are some omissions in Fig. 4. D9 and D13 are BZY 88s, D10 is a BZY 88 5V1. TR2 is a 2N3055 and C4 is 100n.

# THREE FOR FREE FROM CSC

**NEW PROJECTS**

Electronics by Numbers  
Projects No 7, No 8, No 9

Available from selected stockists  
**ELECTRONICS BY NUMBERS**

**No. 7 DIGITAL DICE**

Roll the dice – the electronic way! The digital dice gives you an instant score randomly chosen from 1 to 6, every time you press the button. No losing this under the table!


**No. 8 QUIZ MASTER**

Play your own 'Sale of the Century'! Up to four contestants pit their wits; the first one to get the answer lights up his 'win' light, and stops anybody else from having a go.

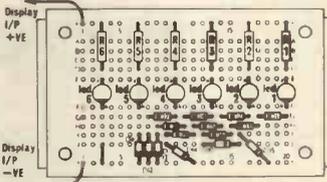**No. 9 MOVING TARGET GAME**

Test your reactions! A moving 'line of light' travels along from left to right, over and over again. You've got to 'fire' at just the right moment to score a hit. Fun for all the family!

Want to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph:



You will need; One EXP 300 or EXP 350 breadboard, 15 silicon diodes, 6 resistors, 6 Light Emitting Diodes.

Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components, connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

For full detailed instructions and layouts of Projects, 7, 8 and 9, simply take the coupon to your nearest CSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you missed projects, 1, 2 and 3, or 4, 5 and 6, please tick the appropriate box in the coupon.


**PROTO-BOARDS**

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

**PROTO-BOARD 6 KIT £9.20**

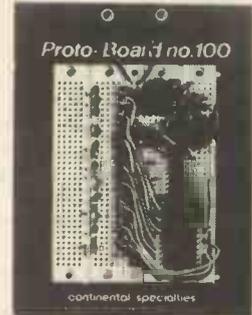

PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

**PROTO-BOARD 100 KIT £11.80**

**EXPERIMENTOR BREADBOARDS**


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B.

**EXP 325 £1.60** The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



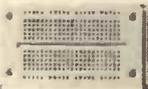**EXP 350 £3.15** Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.




**EXP 300 £5.75** The most widely bought bread-board in the UK.

With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.



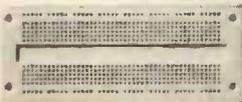
**EXP 600 £6.30** Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.



**EXP 650 £3.60** Has 6" centre spacing so is perfect for MICROPROCESSOR applications.



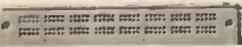**EXP 4B £2.30** Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

**THE CSC 24 HOUR SERVICE TELEPHONE (0799) 21682**

With your Access, American Express, Barclaycard number and your order will be in the post immediately

**CONTINENTAL SPECIALTIES CORPORATION**



C.S.C. (UK) LTD Dept. 5PP  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Tel: Saffron Walden (0799) 21682 Telex: 817477

**IT'S EASY WITH C.S.C.**  
TO RECEIVE YOUR FREE COPY OF PROJECTS 7, 8 and 9

**Just clip the coupon**

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

**For immediate action**

The C.S.C. 24 hour, 5 day a week service. Telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN DIP.	UNIT PRICE INC P&P & 15% VAT	Qty req.
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.48	
EXP 300	550	6	£ 7.76	
EXP 600			£ 8.30	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus-Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	

**PROTO BOARDS**

PB6	630	6	£11.73	
PB100	760	10	£14.72	

C.S.C. (UK) Ltd. Dept. 5PP Unit 1 Shire Hill Industrial Estate Saffron Walden Essex CB11 3AQ

Tel: Saffron Walden (0799) 21682. Telex: 817477

NAME .....

ADDRESS .....

I enclose cheque/P.O. for £.....

Debit my Barclaycard, Access,


American Express card No. ....

Expiry date .....

If you missed project No's

1, 2, 3, 4, 5, and 6, tick box.

For Free catalogue tick box

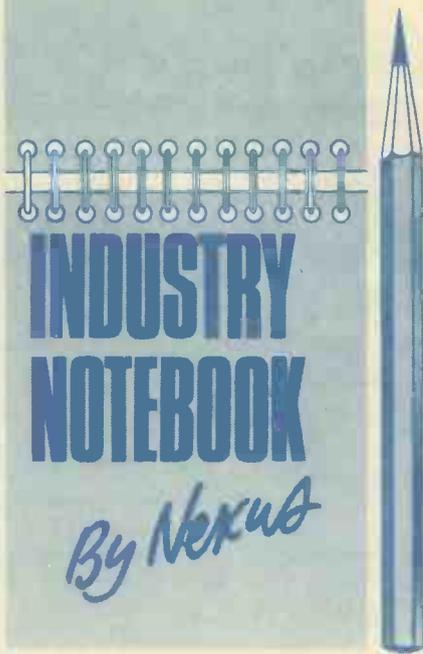

## Climatic Change

After more than a year of Conservative government led by Mrs Thatcher there is still plenty of opportunity and, indeed, reason for vigorous debate in her economic policy and where it is leading. And not least in industry in general and the electronics industry in particular.

Electronics companies are having mixed results. Some are doing well, some less well. But this has always been the case whatever government has been in power. Of course trading conditions are tough and are likely to worsen. All the more reason to work harder to succeed. It is fact, not fancy, that hard working companies staffed by well motivated people have succeeded through good times and bad, and under Labour as well as Conservative governments. Racal and GEC are two prime examples.

What Mrs Thatcher and her colleagues are attempting is to change the attitude of organisations and people. To encourage them to face a real world rather than a dream world. Of course it is a tough policy and very unpleasant medicine.

It may not succeed. There are plenty of people about who hope it won't, some actively working against the policy. There are signs, however, that despite the nasty medicine and its direct and side effects, the majority believe it needs taking in the hope of a cure.

## Subsidies

One of the attitudes which the Government is attempting to change is that of the begging bowl. It has long been my conviction that the practice of direct government hand-outs has done more harm than good to the electronics industry. It has always encouraged sloth. Why spend your own time and money on developing a new product when a government has promised to support it?

So the long delays start, fatal in a fast-moving industry like electronics. First the debate on the amount, then the allocation of funds (too little, too late is always the industry response), the formation of committees, further debate, the start of the programme, the work put in hand, by which time the market has been missed.

This is not to say that private venture, putting your money where your mouth is, is universally successful. There is the sad story of Martello, the privately developed long range three-dimensional defence radar from Marconi Radar Systems. This was a contender for the NATO installations in Scotland. The NATO nations in this case were paymasters and, looking for the best buy, chose a US General Electric system as meeting all the technical requirements at the lowest cost. Marconi investment in Martello has been reported as being £10 million and, as Martello sales prospects are now bleak, it looks as if Marconi Radar will lose money as well as prestige on the project.

The reaction was predictable. Cries of 'foul' from Marconi Radar. Hidden subsidies were suggested from the US Government who had largely or totally paid for the radar development and had already ordered similar models to equip a US Air Force radar chain in Alaska.

And yet within the same GEC-Marconi Electronics group of companies there is brisk overseas trade with, for example, the Clansman military radio funded entirely in its development and early production phases by the British taxpayer through the Ministry of Defence. There are plenty of other Ministry-funded projects in the Group which will be offered at attractive prices to overseas buyers. Even a version of the new air interception radar now in an advanced development stage for the Royal Air Force air-superiority F2 Tornado fighter.

When we look at Plessey we find not only more Clansman radios of Plessey manufacture going overseas but also versions of multi-million pound Parnigan military truck radio and Wavell data processing systems on offer, all funded from public money.

The fact is that we all play the same games and you can't win 'em all. Martello was a private gamble that so far hasn't come off.

In respect of subsidies in general the so-called 'hidden' subsidy of defence equipment funding has been of great benefit to the electronics industry. Defence electronics has always been the forcing ground for advanced technology since the initiation of radar development in the late 1930s. Anyone privileged to see the avionics fit of the Tornado aircraft, or the Mk2 maritime reconnaissance Nimrod or airborne early warning (AEW) Nimrod can see this is as true today as ever it was.

Such projects, distasteful as they may be in some circles, keep the Marconi's, Plesseys, Ferrantis and Cossors in the forefront of electronic skills and large scale project management and are a far more effective way of supporting the industry than the direct subsidy. At the end of the day you at least see something for your

money and with good prospects of overseas sales to friendly countries.

## Racal-Decca

When David Elsbury joined Racal as a line test engineer back in 1956, straight out of national service in the Royal Air Force, he may have been ambitious but he could hardly have dreamed that one day he would be Chairman and Chief Executive of the Decca Group, now re-named Racal-Decca.

Elsbury, still a young 44-year-old, has long been tipped as the natural successor to Ernest Harrison who has led Racal to the top ranks in electronics with an unparalleled growth and export record. Now he is faced with the most challenging task of his career. Can Elsbury inject Racal go-go into ailing Decca? A spectacular instant turnaround of fortune cannot be expected. But Elsbury-watchers, including Harrison himself, have every confidence that he can and will succeed.

David Elsbury's move to his new office at Chessington has opened the way to further well-deserved promotion for other Racal stars such as Gerry Whent and Bill Blake within Racal Tacicom and Racal Communications.

Among the flood of recent Racal announcements one is deserving of special mention. This is Racal-Redac's entry into the MPU business. Up to now Racal-Redac's computer-aided design (CAD) systems have been based on bought-in computers married to Racal-Redac software. The new low-cost (£20,000) Cadet printed circuit board design system is based on microprocessors and will be built entirely in-house. Such is the confidence of Eric Wolfendale, Racal-Redac's managing director, that he has put down a production line for 250 systems, an unprecedented figure for this type of equipment.

## Plessey Success

Plessey Semiconductors, often the subject of ridicule in the past, had a record year in 1979/80 with 47 per cent increase in sales and excellent growth in the U.S.A. and Japanese markets. Almost 50 per cent of all production is now exported as a result of an intensive export drive. Turnover, at £19 million, is still modest by world semiconductor industry standards but an increase to £25 million in the current financial year has been forecast by a newly confident Ken Bradshaw, sales director.

Plessey Semiconductors will get some extra business through an agreement with the Canadian company Mitel on manufacture of ISO-CMOS circuits, as will GEC-Marconi. The ISO-DMOS integrated circuit is a refinement of CMOS and is particularly applicable to the telecommunications industry. The BPO has set up a pilot plant at the Telecom Research Centre and will establish an industry standard for the devices. While it is understood that main production from Marconi and Plessey will be for Britain's telephone network there will also be applications in other equipment for general sale.

# DISCO DESK

**T**HIS series describes a discotheque control desk intended for use with high power, high fidelity sound systems. Whilst it is primarily intended for mobile work, it is also eminently suited to permanent installation in clubs, and can be readily modified for recording and broadcasting, e.g: Hospital radio.

## BLOCK DIAGRAM

Referring to Fig. 1, the disc signal is equalised in two stages in order to achieve an excellent overload margin, good noise performance and low distortion. The disc input stage provides moderate gain and RIAA cut.  $VR_A$  doubles as an output attenuator and as a preset balance control. After the mode selection switch and crossfader, RIAA bass boost is applied to the signal. The line signal does not require this boost and it would normally be necessary to operate an 'RIAA equalisation cancel' switch whilst crossfading from a disc to a line source. This can be an awkward operation under the pressure of a live performance, therefore the line input features RIAA bass cut, which eliminates the need for such a switch. The line input is buffered and applied to the mode switch via a fader and a passive equalisation network, which closely matches the bass portion of the RIAA record characteristic. The use of two stage disc equalisation and preamplification ensures that the op-amps always have plenty of loop gain, hence ensuring low distortion.

## Part 1 BEN DUNCAN


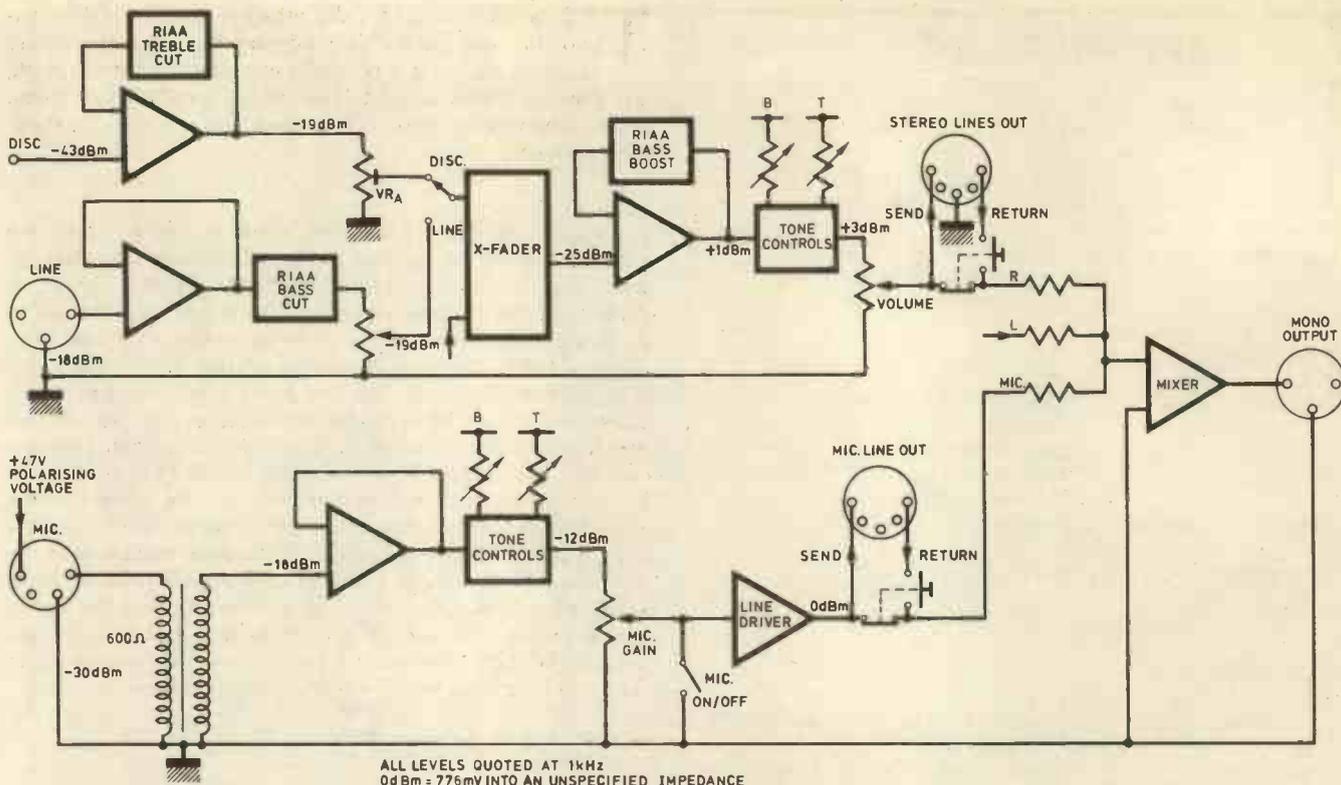


Fig. 1. Block diagram of main circuitry


In a design of this nature, the tone control characteristics can be emphatic without embarrassing consequences. For instance, the very low hum level makes possible a bass boost characteristic which approximately compensates for typical loudspeaker deficiencies. This permits the reproduction of low bass at lifelike levels, assuming that suitable loudspeakers and low rumble turntables are available. The plentiful bass boost is also helpful when 'thin' recordings are encountered; EP singles are often lacking in the lowest bass notes. The bass boost curve rolls off sharply below the audio band in order to minimise the amplification of rumble. Further rumble filtering is provided in the preceding stage. The treble control provides moderate boost and cut over a wide band of frequencies, without excessive midrange or high treble boost. The commonly encountered 20dB boost at 18kHz is simply not required in a good sound system, and

readily causes amplifier or horn overload and 'tinny' treble; deficiencies above 10kHz usually indicate worn discs or styli, or an inadequate loudspeaker system. Most of the distortion in the disc and line channels is generated in this stage.


The tone control stage feeds the send-return socket via the volume control. In its normal position, the send-return switch allows the signal to pass directly to the mono output, via the mixer, and also out of the 'send' pins on the socket. Thus both mono and stereo outputs are provided simultaneously. Depressing the send-return switch forces the signal to pass via auxiliary equipment and allows the signal to return by closing the switch in series with the 'return' pins on the send-return socket. Finally, the stereo music lines are mixed down to mono, together with the microphone signal, by a unity gain mixer.

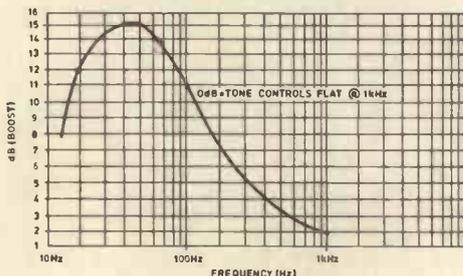

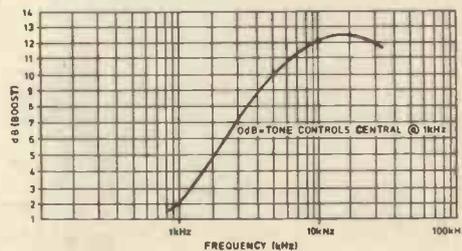
(Left) Mic bass boost curve  
(Right) Disc treble boost curve



### Response Curves

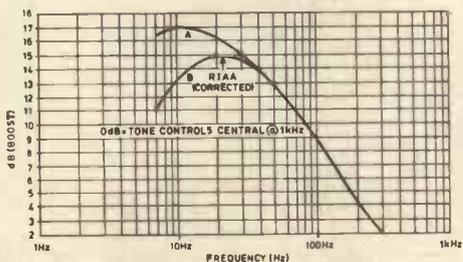

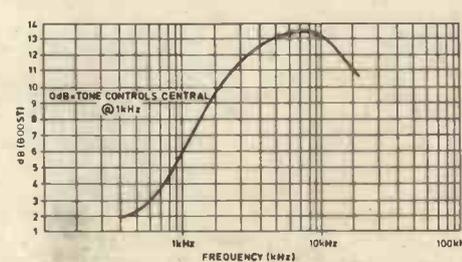(Left) Disc bass boost curve  
(Right) Mic treble boost curve



## SPECIFICATIONS

### Disc

Input impedance	47k
Sensitivity $\pm \frac{1}{2}$ dB	-43dBm at 1kHz ref 0dBm out (5.5mV)
Hum	-80dB, unweighted
Noise	-70dB, unweighted, 20Hz to 20kHz
Frequency response	12Hz-25kHz at -3dB points
Input overload margin	41dB
Distortion, harmonic at +10dBm, 30Hz	-0.06%
	1kHz-0.01%
	10kHz-0.03%

### Line inputs

Input impedance	100k
Sensitivity $\pm \frac{1}{2}$ dB	-18dBm at 1kHz ref. 0dBm out (100mV)
Hum	-105dB unweighted
Noise	-76dB, unweighted, 20Hz to 20kHz, 600 ohm input load
Frequency response	30Hz-50kHz at -3dB points
Input overload margin	38dB
Distortion, harmonic at +10dBm, 30Hz	-0.06%
	1kHz-0.008%
	10kHz-0.03%

### Microphone

Input impedance	600 ohms
Sensitivity	-30dBm at 1kHz ref. 0dBm out (25mV)
Hum	-93dB, unweighted
Noise	-80dB (unweighted), 20Hz-20kHz, 200 ohm input load
Frequency response	32Hz-22kHz at -3dB points
Input overload margin	-40dB
Distortion, Harmonic at +10dBm, 30Hz	-0.01%
	1kHz-0.02%
	10kHz-0.1%

### General

Slew rate, all stages	$\geq 5.5\text{V}/\mu\text{s}$
Distortion, any input,	$\leq 0.1\%$ at 10dBm, 30Hz-18kHz
Output clip level	+20dBm
Mono and mic outputs provide 0dBm at 100 ohm source impedance and will drive 600 ohm lines at +20dBm	
Stereo lines provide 0dBm at 350 ohm source impedance	
Tone controls & RIAA equalisation matched to within $\frac{1}{2}$ dB	
0dBm = 776mV into an unspecified impedance	

## COMPONENTS

### Card 1

#### Resistors

R1-4	47k
R5-8	7k5
R9-12	470R
R13-16	560R
R17-20	100k

(All  $\frac{1}{2}$  watt metal oxide, 2%)

#### Potentiometers

VR1-4	22k enclosed cermet (RS components type 186-198)
VR5-8	1k dual log (Rivlin CS60 type, Maplin order code HB OOA)

#### Capacitors

C1-4	1 $\mu$ polycarbonate
C5-8	22p ceramic
C9-12	10n polycarbonate
C13-16	6n8 polycarbonate
C17-20	680n polycarbonate
C21-24	22 $\mu$ 25V PC mounting electrolytic
C25-28	470n polyester, C 280AE series
C29-32	22p ceramic
C33-36	18n polycarbonate
C37-38	100 $\mu$ , 40V axial electrolytic
C39-40	100n polyester, C280AE series

#### Semiconductors

IC1-IC8 NE5534N or NE5534AN, 8 pin d.i.l. version

#### Miscellaneous

SKT1, 2—XLR 3 pin female sockets (Maplin BW90X)  
 SW1, 2—Miniature toggles (RS components type 316-973)  
 "Copper-clad single-sided epoxy-glass p.c.b. board incorporating 0.1" pitch edge connector (RS type 434-150)  
 8 x 8 pin d.i.l. sockets  
 185 x 90mm aluminium screen, 22 s.w.g.

## Facilities and functions (see numbered photo)

### Music

Two stereo disc inputs from internal turntables A & B (1-2)  
 A+B line and disc inputs selected by rotary switches (A&B)  
 Two stereo line inputs from female XLR's A & B (3-4)  
 Internal preset disc balance controls  
 Line input level controls (5-6)  
 Line input earth-isolation switches (7-8)  
 Slider crossfading between line & disc in any of 4 combinations (9)  
 Bass, treble and volume controls (10-12)  
 Music send-return socket provides stereo lines at 0dBm (13)  
 Music send-return switch activates stereo return for insertion of graphic equalisers, limiters, expanders, etc. (14)  
 Music 'cancel' switch for audience participation and emergency announcements (15)

### Microphone

Capacitor microphone input (Readily modified for moving coil microphones) from female XLR (16)  
 Bass and treble controls specially contoured for vocal applications (17-18)  
 Microphone gain control and on-off switch (19-20)  
 XLR send-return socket providing (mono) microphone output at 0dBm for routing to vocals amplifier (21)  
 Microphone send-return switch activates return for insertion of graphic equaliser, special effects, etc (22)

### Output

XLR mono output from stereo lines and microphone line via a unity gain mixer. This output can be exclusively microphone or music if required, by depressing appropriate send-return switch. Also XLR stereo music output. (23)

### Auxiliary

Output and PFL monitoring, the latter switchable to all music inputs (24-25)

#### Monitor level control (26)

4 watts into 4 ohms monitor amplifier, for phones or monitor speaker, with short circuit and thermal protection (27)

A & B cueing indicators (yellow panel l.e.d.s) illuminate when disc modulation begins or line input exceeds an equivalent threshold (28-29)

Left and Right peak indicators (Red panel l.e.d.s) are set to illuminate at the nominal r.m.s. input level of the systems power (30-31), e.g: 500mV, whilst VU meters provide the desk 0dB reference across the stereo lines (32-33)

Autofader on-off switch and locking panel-presets for depth, rate and sensitivity adjustments (34-37)

Remote push button turntable start switches and turntable lamp switches. Jack socket sound-to-light modulator output (38-42)

High reliability remote power supply with comprehensive protection.



### MICROPHONE CHANNEL

The microphone input is designed for the Calrec CM654 capacitor microphone but input stage modifications are given to cover the majority of moving coil and capacitor microphones, including those which are balanced or phantom powered. A good vocals microphone is essential for discotheque applications, where 'close miking' is the rule. All cardioid microphones provide strongly accentuated low bass under these conditions. Windshields help, but microphones intended for vocal applications often incorporate compensation for 'close miking'. This virtually eliminates 'pop' and other explosive breath sounds and minimises the input transformer's overload margin requirements. A discotheque microphone may also be required to handle SPLs in excess of 100dB if the operator shouts; capacitor microphones are particularly suited to handling high SPLs with low distortion.

Most of the distortion in the microphone channel is generated by the input transformer, but it is predominantly 2nd harmonic and quite inaudible under normal conditions. The input stage has unity gain in order to avoid overloading the tone control stage, bearing in mind the high outputs

produced by close miking. The tone controls have been contoured as far as possible to suit vocals requirements, ie: for frequencies between 100Hz and 10kHz. The fundamentals of male and female speech lie around 130Hz and 200Hz respectively. These low frequencies provide the voice with body and character whilst the harmonics, particularly those around 1kHz-3kHz are essential for intelligibility.


With this in mind, the treble boost curve has been contoured to give relatively large amounts of boost around these latter frequencies, thus allowing vocals to 'cut through' if desired. It is difficult using the Baxandall network to bring the maximum boost up to the fundamental frequencies of the human voice. Maximum boost occurs, therefore around 50Hz but in practice the characteristic is satisfactory provided a vocally compensated microphone is used.

The microphone signal passes to a line driver, capable of providing some +20dBm into a 600 ohm load, via a gain control and the on-off switch. The microphone send-return switch is wired in the same manner as that previously described, and finally the microphone line feeds the mono mixer.

### ANCILLARY FUNCTIONS

The auxiliary functions are shown in Fig. 2. The autofader drives an f.e.t. which shunts the music lines; attenuator  $VR_A$  controls the fade depth.  $VR_C$  and  $VR_B$  adjust the sensitivity (i.e. microphone level required to trigger) and the fade-up rate of the circuit respectively.  $S_A$  disconnects the f.e.t. when the autofader is not required. A four way switch selects the right hand disc and line inputs for PFL (pre-fader listen) monitoring. In turn, a two way switch selects either PFL or output monitoring. A 4 watt amplifier is provided to drive either headphones or a monitor loudspeaker.

The cue l.e.d.s allow discs to be lined up rapidly and without the use of headphones.  $VR_D$  is set to discriminate between rumble and music modulations on typical discs. The VU meter driver preset is normally set such that 776mV on the stereo lines gives an 0 VU reading, though this is not conventional practice in broadcast sound equipment. The peak indicator switches on its associated l.e.d. for a few hundred milliseconds whenever a signal peak exceeds the nominal input sensitivity of the power amplifiers, eg: 500mV

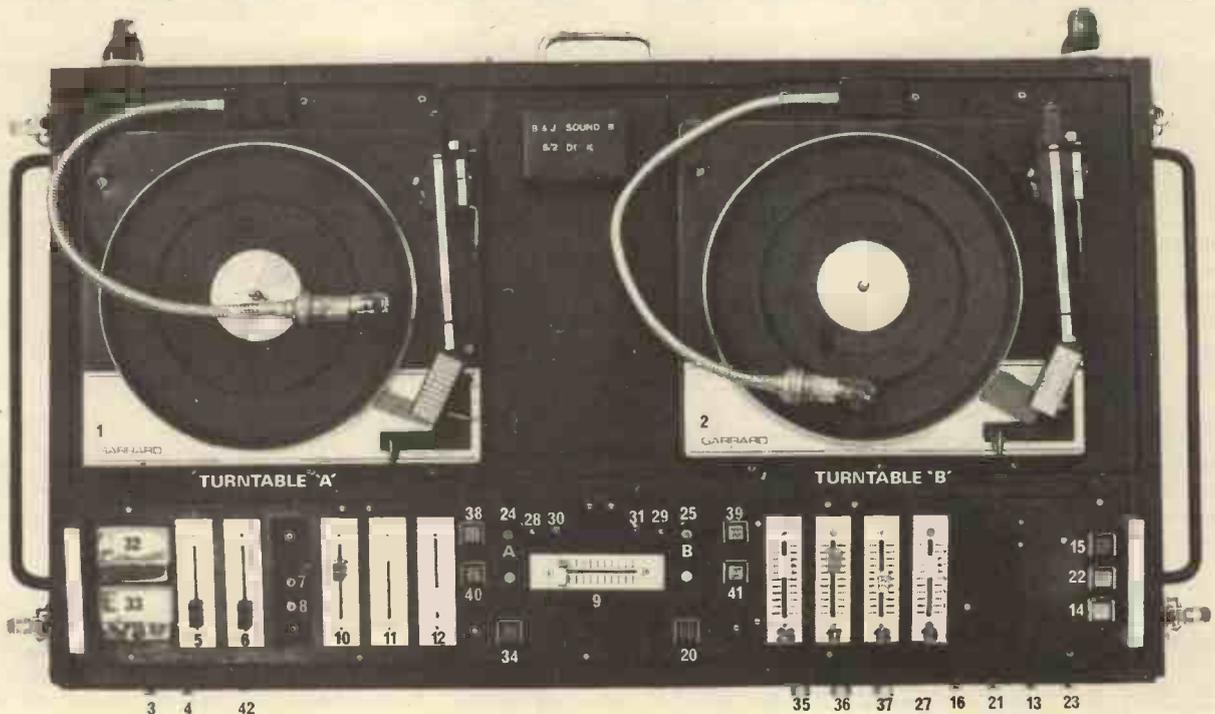

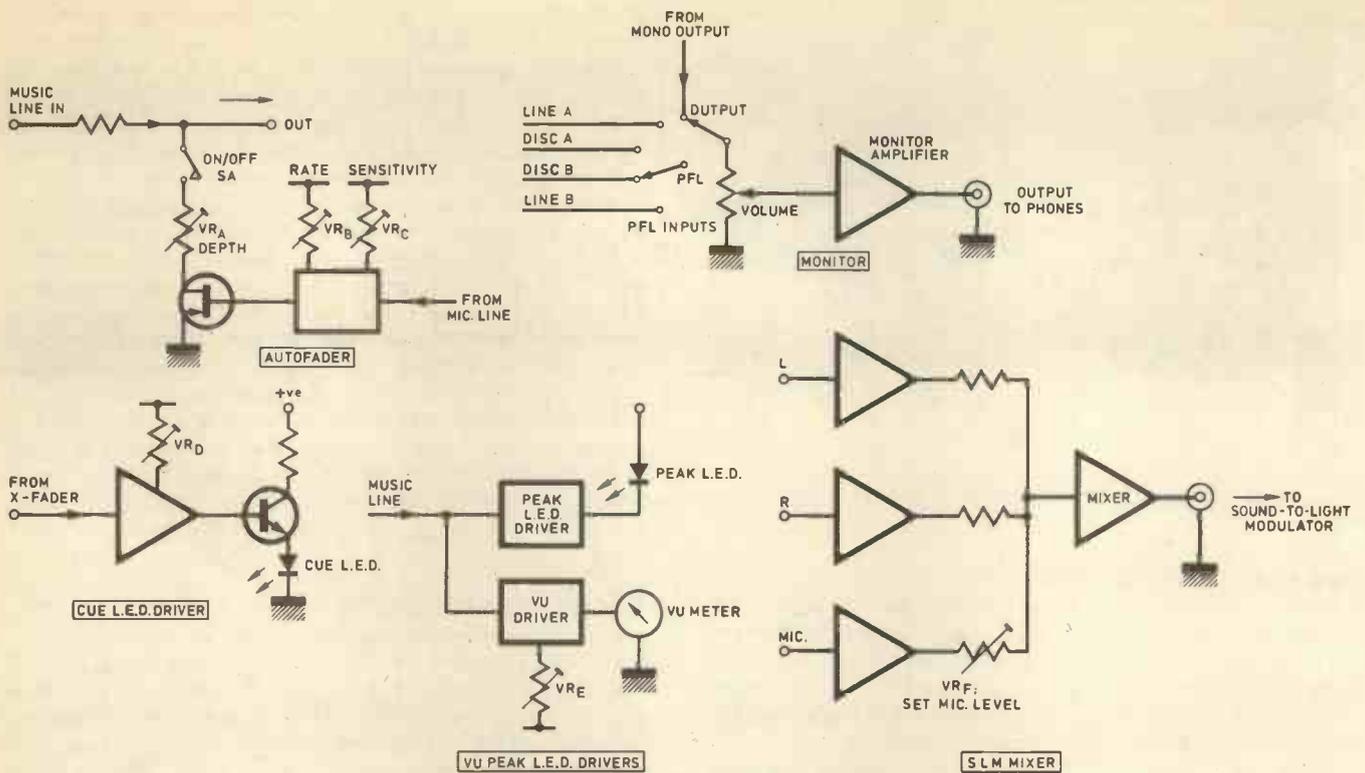


Fig. 2. Block diagram of auxiliary functions

( $-3\frac{1}{2}$ Bm). In this way, they warn that the power amplifiers are being driven close to clipping.

The 'sound-to-light mixer' provides a +10dBm output for lighting effects. The microphone level in the mix is adjusted to match the level of the music signals under normal 'miking' conditions by means of preset VR<sub>F</sub>.

### CONSTRUCTION

Apart from the monitor amplifier, all the circuitry is contained on four pluggable cards; this greatly simplifies construction and debugging. Fig. 3 will be found helpful as construction progresses, as it shows how the circuitry on each card is interconnected. The power supply, whilst sophisticated, is simple to construct and is unlikely to require debugging. For this reason it will be presented later. For initial tests,  $\pm 15$ V and +12V supplies are required. To test individual cards, very little current is required (<100mA) and batteries are quite adequate if a good bench power supply is not available.

All the audio circuitry is built around the Signetics NE5534 op amp. This was introduced to Britain some 18 months ago and is truly described as 'high performance' in that it is the first op amp to approach the performance of the best discrete circuits. As a result, it has found wide acceptance in professional audio equipment. It has pin compatibility with the 741C and features internal compensation for gains in excess of 10dB. However, the addition of a small compensation capacitor ensures stability without compromising performance in the audio band. The low noise version, designated 'NE5534AN' is expensive but may be used to advantage in the disc input stage if desired.

The NE5534N, like the 741 is a hardy bi-polar device and does not require special handling precautions. However, it is not as cheap as the 741 and when the cards are initially tested it is wise to substitute the latter.




### CARD 1

This card contains the disc and line input stages. With reference to Fig. 4, R1 provides the input bias current for IC1 and also the standard load for a magnetic cartridge. At high frequencies, the gain of IC1 falls to unity, therefore external compensation (C5) is required. R5 and R9 provide a gain of 24dB and together with C9 also furnish RIAA treble cut. However, in the series feedback configuration used here, the gain of IC1 cannot fall below unity. Thus R13 and C13 are required to maintain treble cut at high frequencies. The electrolytic capacitor C21 has significant reactance above 1kHz and therefore C17 is added to ensure good treble response. Wherever possible throughout the audio circuitry non-electrolytic coupling capacitors have been specified for this reason. VR1 doubles as a preset balance control and output attenuator as previously described.

IC5 provides unity gain and C33 with the crossfinder provides bass cut which closely complements the RIAA bass boost characteristic. For optimum screening and RF1 suppression all the disc inputs have independent 0V connections and are quasi-balanced. This procedure is not so important at line input levels, and the 0V connection for each stereo line input is commoned at the XLR input connector in any case. Panel mounted earth isolation switches are provided on these inputs to facilitate the control of hum loops. The supply rails adjacent to each op amp are



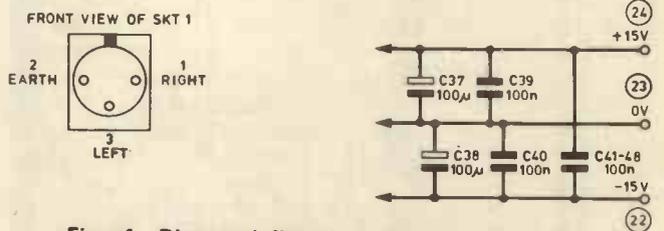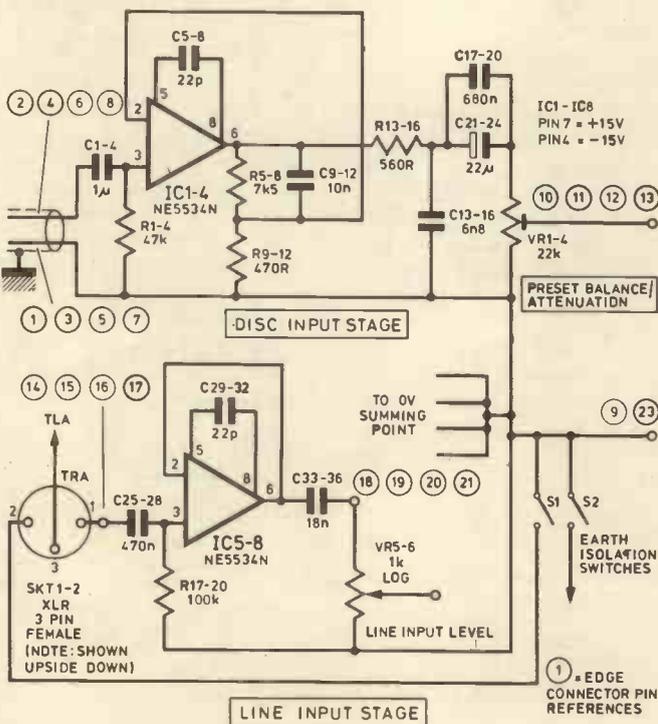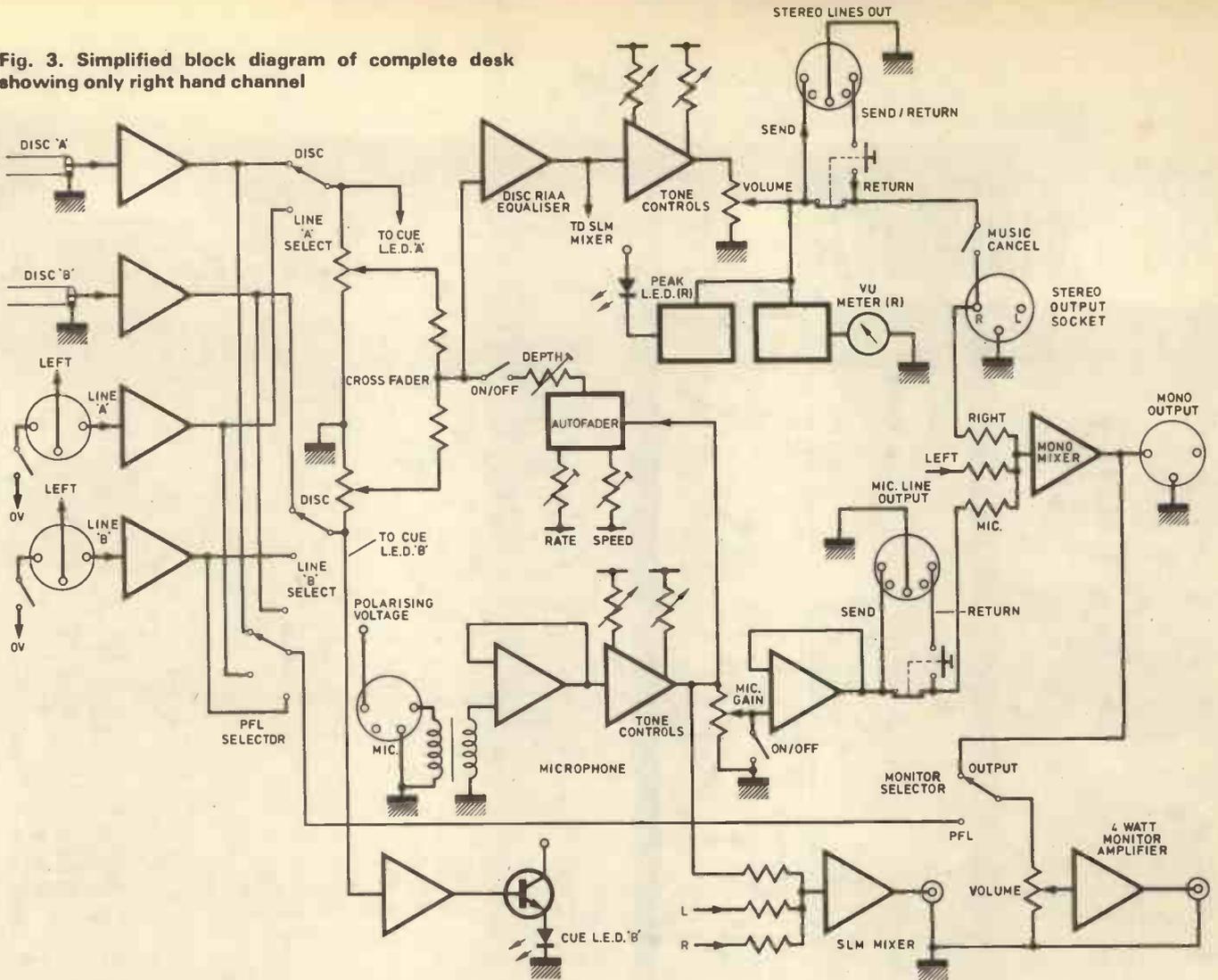**Fig. 3. Simplified block diagram of complete desk showing only right hand channel**

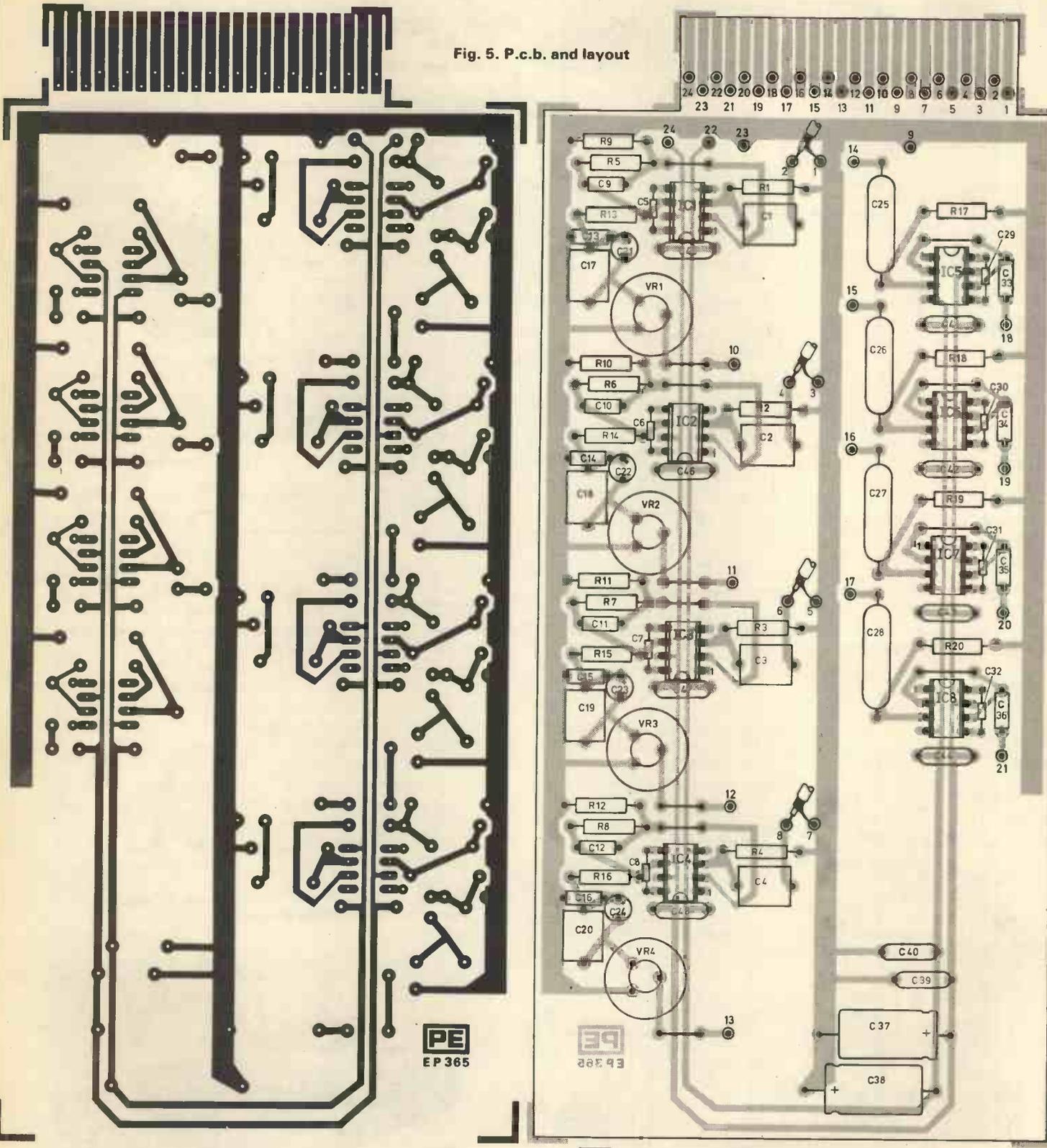


**Fig. 4. Disc and line input stages (Card 1), socket detail and line decoupling**



# CARD 1

Fig. 5. P.c.b. and layout



### Card 1 Edge Wiring

There are two line and disc (T and D) inputs, named A + B, and each has a left (L) and a right channel (R).

For turntable "A", the inputs are  $D_{RA} + D_{LA}$


For turntable "B", the inputs are  $D_{RB} + D_{LB}$

For line input "A", the inputs are  $T_{RA} + T_{LA}$


For line input "B", the inputs are  $T_{RB} + T_{LB}$

Disc input earth connections are designated OV together with the appropriate code.

Pin No.	Connection	
1	OV, $D_{RA}$	} Disc inputs from magnetic cartridge
2	Live, $D_{RA}$	
3	OV, $D_{LA}$	
4	Live, $D_{LA}$	
5	OV, $D_{RB}$	
6	Live, $D_{RB}$	
7	OV, $D_{LB}$	
8	Live, $D_{LB}$	
9	OV Summing point	
10	$D_{RA}$	} Disc outputs to mode switches
11	$D_{LA}$	
12	$D_{RB}$	
13	$D_{LB}$	
14	$T_{RA}$	} Line inputs. (OV via S1/S2 to pin 9)
15	$T_{LA}$	
16	$T_{RB}$	
17	$T_{LB}$	
18	$T_{RA}$	} Line input amplifier outputs to mode switches
19	$T_{LA}$	
20	$T_{RB}$	
21	$T_{LB}$	
22	-ve, 15V	} To power supply busbars
23	OV	
24	+ve, 15V	

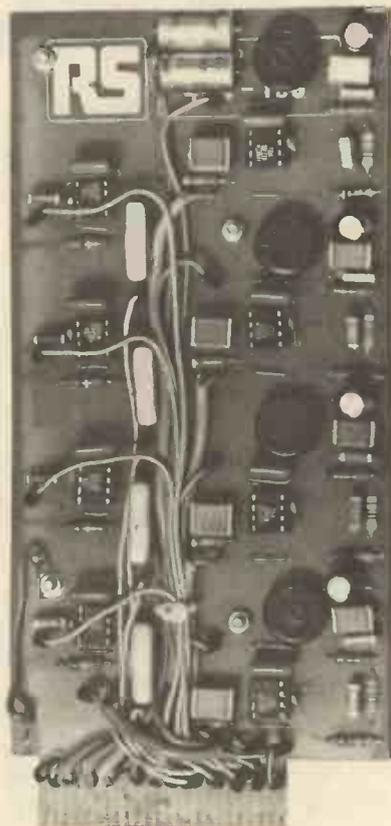

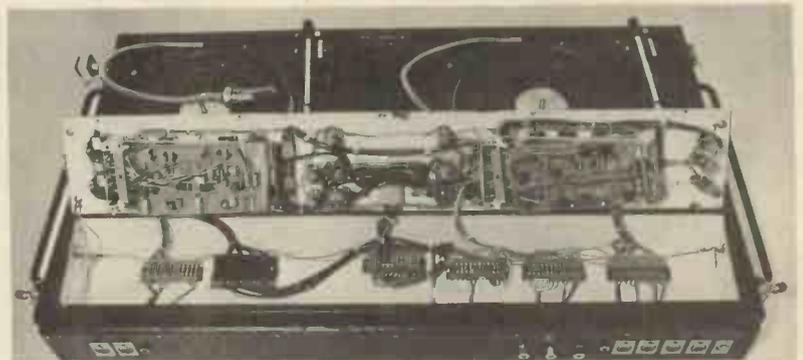Showing a completed Card 1 and below a desk with the board assembly lid pulled back



decoupled at high frequencies for stability (C41 etc) and additional capacitors (C37-40) are provided to attenuate common mode RF1 and to decouple the supply rails at audio frequencies.

### CARD 1 LAYOUT

The physical layout of Card 1 is shown in Fig. 5. The copper clad board specified in the components list must be cut to size. Note that the card aperture is not symmetrical and marking out and cutting should be done from the *copper side* of the board if the aperture position is to correspond to Fig. 4. Accurate cutting is facilitated by using a jigsaw fitted with a very fine blade, together with an  $\frac{1}{8}$  in strip of straight aluminium as a guide along the inside of the cutting line.

The 24 edge connector strips should be covered with enamel paint to protect it during etching; paint is more consistent than etch resistant ink over such large areas. The p.c.b. pins are wired direct to the edge connector pins by 7/0.2 cable, except for pins 1-8 which require screened cable, and pins 9 and 23, which should be brought to the edge connector with 16/0.2 cable to ensure a low impedance connection. Because the edge connector pins are cramped, all the leadout wires should be sleeved. Apart from allowing a high component density, 'hard wiring' in this fashion permits control over stray capacitance which cannot be achieved first go with 24 parallel p.c.b. tracks!

When the board is completed, scrape away excess flux, using methylated spirits as a solvent, together with a stiff brush where necessary.

Check carefully for errors, then load the 8 sockets, preferably with 741s. Note that the op amps belonging to the line inputs face in the opposite direction to those handling the disc inputs. Short all the inputs to OV and apply  $\pm 12V$  or  $\pm 15V$  via 100R current limiting resistors in each supply rail. If the supply current exceeds 30mA (741s) or 70mA (NE5534s), disconnect the supply and look for errors. If all is well, load the card with NE5534s and reconnect the supply. Then check the offset voltages at pin 6 on the i.c.s; note that a carelessly placed probe may prove fatal to the devices here. If the offset voltage is greatly in excess of 300mV, disconnect and check again for errors, or for floating inputs. Finally, reconnect the supply and check the polarity of the offset at pin 6 on I.Cs 1-4. Then reorientate C21-24 if necessary. The screen can then be added (Fig. 5) and Card 1 is now completed. The same constructional and setting up procedure applies to the remainder of the cards; remember to allow for notably lower power consumption however on Card 2, and to short all inputs to the OV rail.

**Next Month**—more circuits.

# PROGRAMMABLE SOUND GENERATOR

D. COUTTS

**T**HE GENERAL INSTRUMENT AY-3-8912 Programmable Sound Generator was designed to produce a variety of complex sounds under software control. By using a register stack the processor can load values into the sound chip and then carry on with other tasks while the sound is being generated.

It is easy to interface the i.c. with the UK101 and to add sound to your BASIC programs by means of the POKE command.

## BLOCK DIAGRAM

Fig. 1 is a block diagram of the 8912 i.c. There are three tone generators and a noise generator. The three tones can be fed out to outputs A, B and C. The noise can be added to any or all of the tones, or it can be output instead of a tone. The amplitudes of the noise and tones can be set to one of sixteen fixed values, or they can be varied by means of an envelope generator. The envelope generator amplitude modulates the outputs and can be set for various options of fast or slow attack and decay, single shot or repeat, etc. allowing a wide variation of sounds. The three outputs are logarithmic.

## PSG REGISTER ARRAY

Fig. 2 shows the register array in detail. Register 0 and register 1 are cascaded to give a 12-bit word which sets the period of tone A, the top 4 bits of register 1 not being used and the bottom 4 bits forming bits 8, 9, 10 and 11 of the 12-bit word. The register can be set to any value between 1 and 4095 decimal. As the clock is divided by 16 before being fed to the tone generator, the output frequency is:

$$f = \frac{f_{\text{clock}}}{16 \times R}$$

where R lies between 1 and 4095. Registers 2, 3 and 4, 5 similarly control tone generators B and C. Register 6 is used to control a pseudo random noise generator. Only the bottom 5 bits are used, and again, the clock is divided by 16 before being fed to the noise generator.

Register 7 is the output control register. Bits 6 and 7 should always be set to one as we are outputting data to the PSG (Programmable Sound Generator). Setting bit 0 low will enable tone A to be output to channel A. If at the same time bit 3 is set low the noise generator will be mixed with tone A. If bit 0 is now set high only noise will be output on channel A. Likewise bits 1 and 4 control tone B and noise to channel B, and bits 2 and 5 control tone C and noise to channel C. Remember it requires a low or 0 to select a tone or noise, for example, writing 254 decimal to register 7 selects tone A.

Register 8 is used to set the amplitude of channel A in the fixed output level mode. Bits 5, 6 and 7 are not used. If bit 4 is set to 0 then the output amplitude is set at one of sixteen fixed levels by means of bits 0 to 3. If bit 4 is set to a '1', however, bits 0 to 3 have no effect and the output amplitude is set by the envelope generator. Registers 9 and 10 are

used similarly for channels B and C. Registers 11 and 12 are cascaded to give a 16-bit word to set the envelope period. The clock is divided by 256 before being fed to the envelope control, so with a 2MHz clock we can get a period range of about 0.1Hz to 7800Hz.

Register 13 determines the shape/cycle of the output as follows.


The envelope generator further counts down the envelope frequency by 16, producing a 16-state per cycle envelope pattern as defined by its 4-bit counter output, E3, E2, E1, E0. The particular shape and cycle pattern of any desired envelope is accomplished by controlling the count pattern (count up/count down) of the 4-bit counter and by defining a single-cycle or repeat-cycle pattern.

This envelope shape/cycle control is contained in the lower 4 bits (B3-B0) of register 13. Each of these 4 bits controls a function in the envelope generator, as illustrated in the following:


Envelope Shape/Cycle Control Register (R13)

B7	B6	B5	B4	B3	B2	B1	B0	FUNCTION
----	----	----	----	----	----	----	----	----------


Not Used

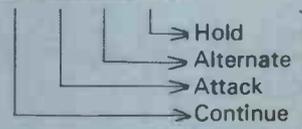

To Envelope Generator

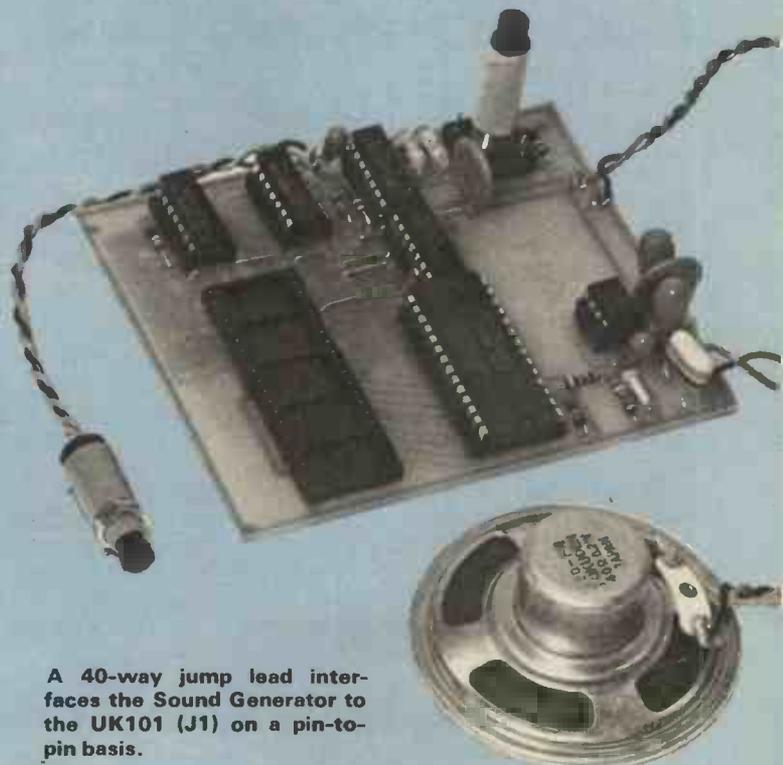

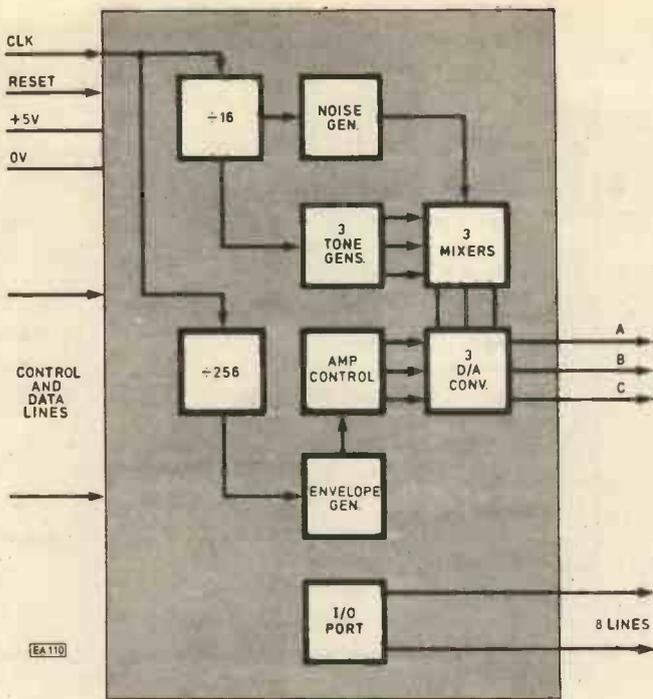A 40-way jump lead interfaces the Sound Generator to the UK101 (J1) on a pin-to-pin basis.



The definition of each function is as follows:

**Hold** When set to logic 1, limits the envelope to one cycle, holding the last count of the envelope counter (E3-E0 = 0000 or 1111, depending on whether the envelope counter was in a count-down or count-up mode, respectively).

**Alternate** When set to logic 1, the envelope counter reverses count direction (up-down) after each cycle.

**NOTE:** When both the Hold bit and the Alternate bit are ones, the envelope counter is reset to its initial count before holding.

**Attack** When set to logic 1, the envelope counter will count up (attack) from E3, E2, E1, E0 = 0000 to E3, E2, E1, E0 = 1111: when set to logic 0, the envelope counter will count down (decay) from 1111 to 0000.

**Continue** When set to logic 1, the cycle pattern will be as defined by the Hold bit. When set to logic 0, the envelope generator will reset to 0000 after one cycle and hold at that count.

To further describe the above functions could be accomplished by numerous charts of the binary count sequence of E3, E2, E1, E0 for each combination of Hold, Alternate, Attack and Continue. However, since these outputs are used (when selected by the Amplitude Control registers) to amplitude modulate the output of the Mixers, a better understanding of their effect can be accomplished via a graphic representation of their value for each condition selected, as illustrated in Fig. 3.

Register	BIT								
	B7	B6	B5	B4	B3	B2	B1	B0	
R0	8-BIT Fine Tune A								
R1	Channel A Tone Period				4-BIT Coarse Tune A				
R2	8-BIT Fine Tune B								
R3	Channel B Tone Period				4-BIT Coarse Tune B				
R4	8-BIT Fine Tune C								
R5	Channel C tone Period.				4-BIT Coarse Tune C				
R6	Noise Period				5-BIT Period Control				
R7	Enable		IN/OUT		Noise		Tone		
B8	Channel A Amplitude			M	L3	L2	L1	L0	
R9	Channel B Amplitude			M	L3	L2	L1	L0	
R10	Channel C Amplitude			M	L3	L2	L1	L0	
R11	8-BIT Fine Tune E								
R12	Envelope Period				8-BIT Coarse Tune E				
R13	Envelope Shape/Cycle				CONT.		ATT.	ALT. HOLD.	
R14	I/O Port A Data Store								
	8-BIT PARALLEL I/O on Port A								

Fig. 2. Register array of AY-3-8912

```

10 R = 61680 : V = 61681      60 Y = INT (RND(7)-15):
20 FORT = 0 TO 14 : X = INT   FOR T = 1 TO 255:
  (RND(5)*255) + 1          POKER,Y POKEV,T
25 IF RND(9)<.5 THEN        70 NEXT
  POKER,7 : POKEV,248       75 FORT = 255 TO 1 STEP -
26 IFRND(4)<.5 THEN         1: POKER,Y : POKEV,T
  POKER,1 : POKEV,0        76 NEXT
30 GOSUB 1000              80 GOTO 20
40 NEXT                    1000 POKER,T: POKEV,X:
50 FORT = 1 TO 5000 : NEXT  RETURN

```

Let the Sound Generator create its own sounds with this random program. Push it through a power amplifier for maximum effect.

Register 14 is the output port. Writing data to this register outputs it on pins 7 to 14 of the AY-3-8912.

### CIRCUIT DIAGRAM

Fig. 5 shows the circuit diagram of the unit. IC3a and b provide a 1 to 2MHz clock to the PSG. IC3c and IC4a provide a reset to the chip, R2 and C3 providing power on reset. The three output channels of the 8912 are mixed together and are amplified by IC6. The UK101 data lines D0 to D7 are fed to pins 28 to 21 of IC5. Pins 7 to 14 of IC5 are the output port lines from register 14.

Two addresses are used to load the PSG, F0F0H and F0F1H. IC1 decodes when address bits 2<sup>4</sup> to 2<sup>7</sup> and 2<sup>12</sup> to 2<sup>15</sup> are high. IC2 decodes when address bits 2<sup>1</sup> to 2<sup>3</sup> and 2<sup>8</sup> to 2<sup>11</sup> are low and R/W is low. Address bit 2<sup>0</sup> goes to IC4C. When you write to address F0F0H pins 18 and 20 of IC5 go high and the data on the data lines is written into an address latch in the PSG, i.e. if you write 0 to F0F0H the address latch in the PSG points to register 0. If you now write to address F0F1H then the data on the data lines will be written into the register pointed to by the address latch, i.e. if you write 128 to F0F1H then 128 will be written into the register pointed to by the address latch, in this case register zero.

### CONSTRUCTION

Construction is straightforward using the circuit diagram, Fig. 5 and component layout, Fig. 7. Fit the wire links followed by the sockets (it is advisable to use sockets with CMOS and MOS devices). Fit the resistors and capacitors then fit the coil former L1 and wind on 60 turns of 30 SWG enamelled wire. fit two cores into L1. A Molex plug can be fitted to the output port if it is needed. Fit wires for reset switch S1 and for the speaker. Add wires for 0V and +5 volts. If preferred the +5 volts could be brought in from the UK101 via the spare pin on J1 (pin 11). The p.c.b. is connected to the UK101 via a 40 to 40 pin jumper cable.

If IC6 and IC7 are not fitted in the UK101 it will be necessary to fit two dil plugs in place of them, wired as shown in Fig. 8.

### TESTING THE UNIT

Check the p.c.b. very carefully for any solder splashes causing shorts. Fit the i.c.s, connect the unit to the UK101 via a 40-way jumper cable and power up.

As stated previously, writing a number between 0 and 14 to address F0F0H (DECIMAL 61680) will set up an address latch in the i.c. to point to one of the registers R0 to R14. If you then write to address F0F1H (61681 DECIMAL) you can write data into the appropriate register.

Load the following program:

```

10 POKE 61680, 0 (POINT TO REGISTER 0)
20 POKE 61681, 255 (LOAD 255 INTO REG. 0 (TONE))
30 POKE 61680, 7 (POINT TO REG. 7)
40 POKE 61681, 254 (SELECT REG. 0 TO O/P)
50 POKE 61680, 8 (POINT TO REG. 8)
60 POKE 61681, 15 (SELECT O/P AMPLITUDE)
100 END

```

and run.

This outputs a single tone. To add noise change line 40 and ADD 70 and 80:

```

40 POKE 61681, 246 (SELECTS TONE AND NOISE ON A)
70 POKE 61680, 6 (SELECTS REG. 6)
80 POKE 61681, 1 (ENTERS NOISE VALUE)

```

and run.

Fig. 3. Envelope shape control



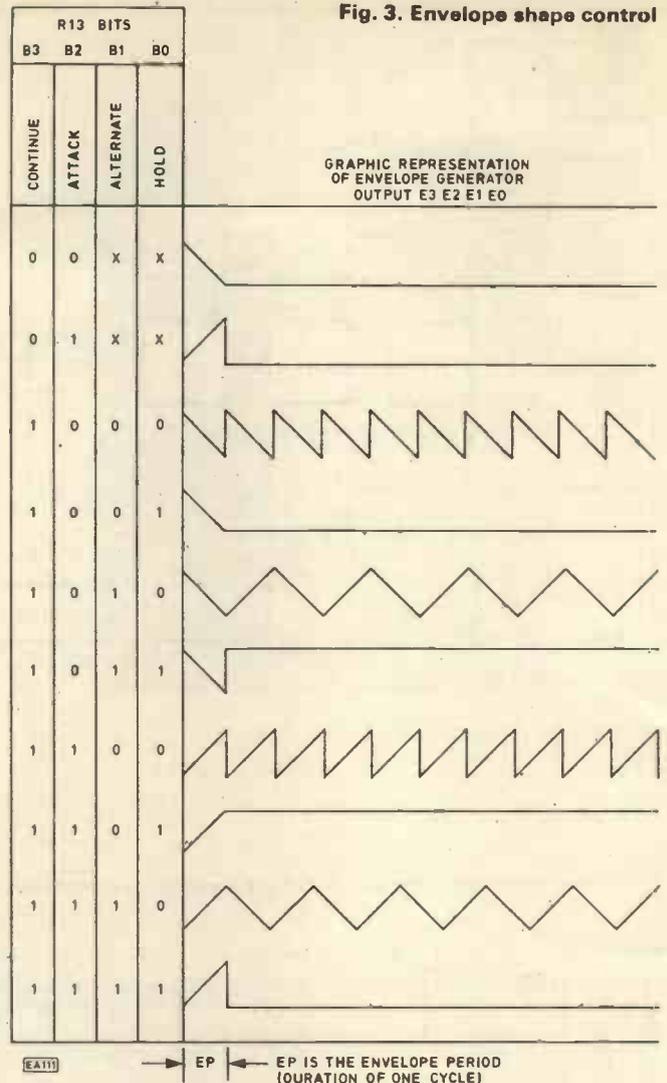


Fig. 4. AY-3-8912 pin-outs

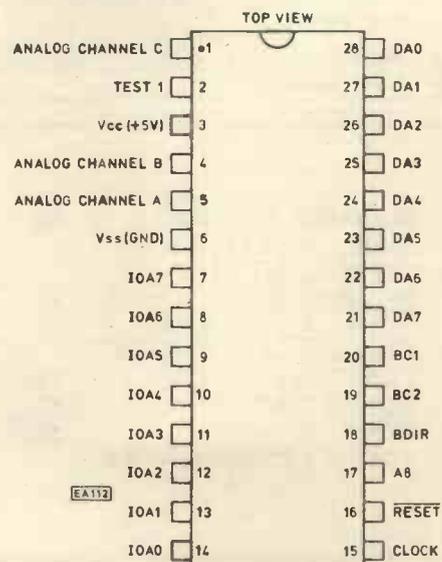

**Fig. 5. Circuit diagram of Programmable Sound Generator**

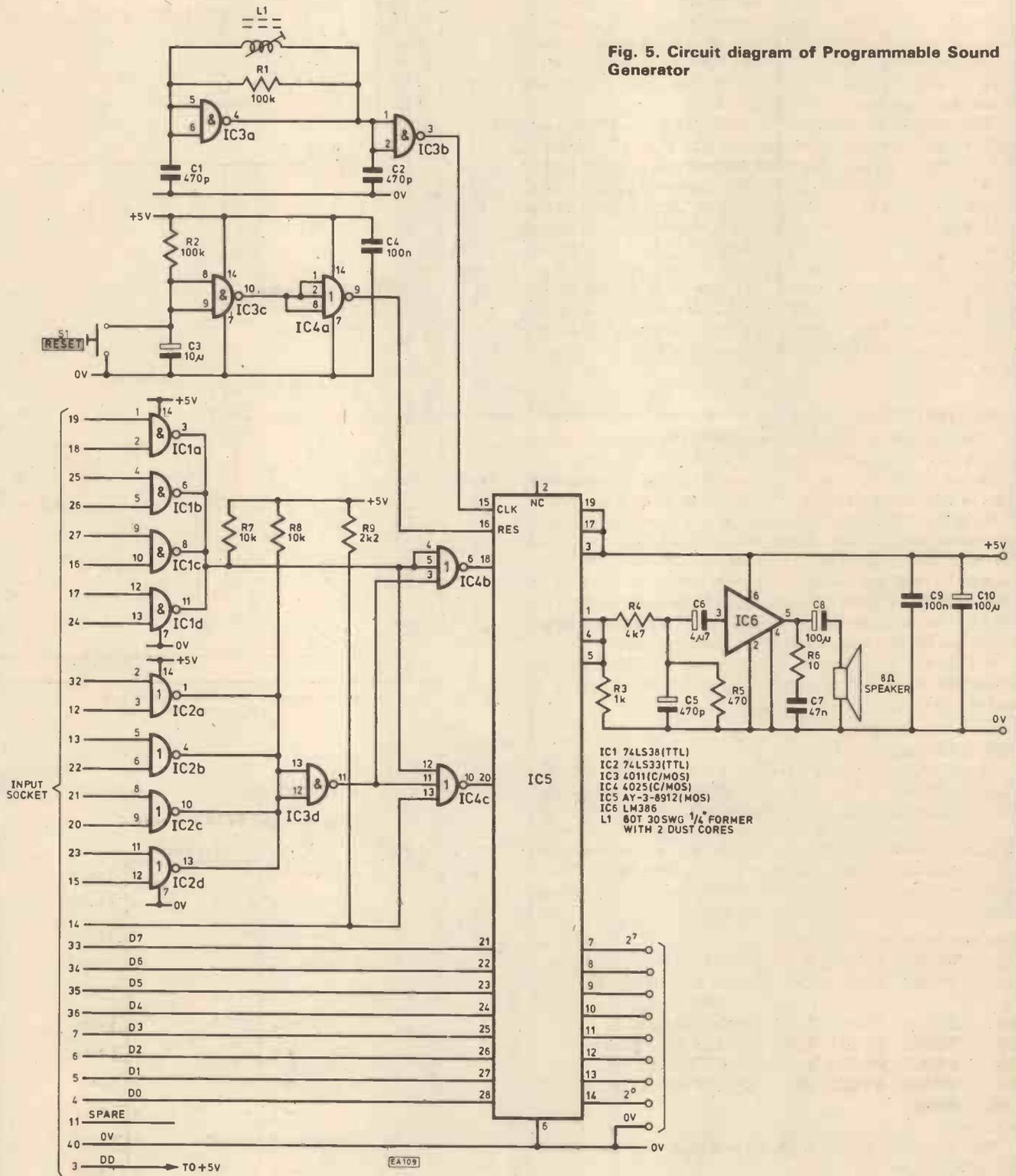


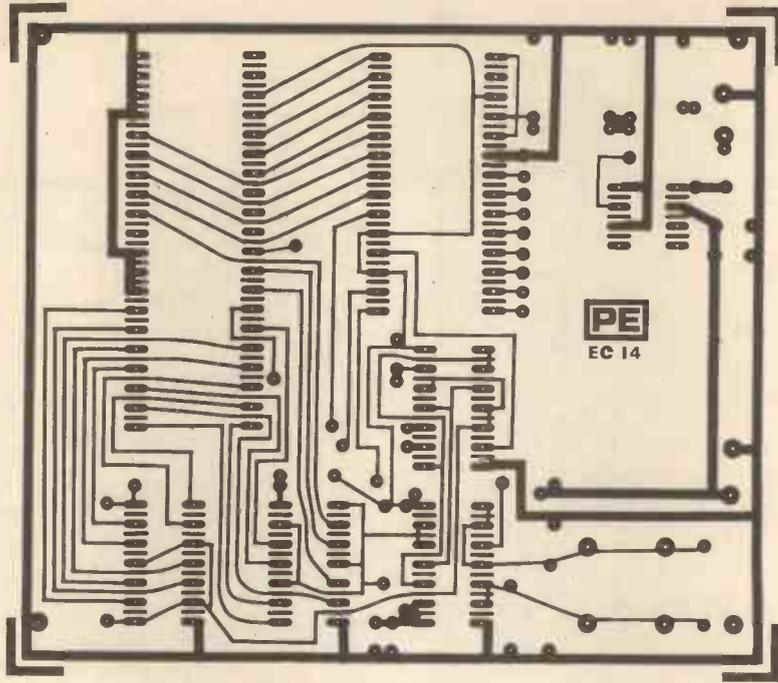


Fig. 6. Printed Circuit layout (actual size)

Fig. 7. Component layout

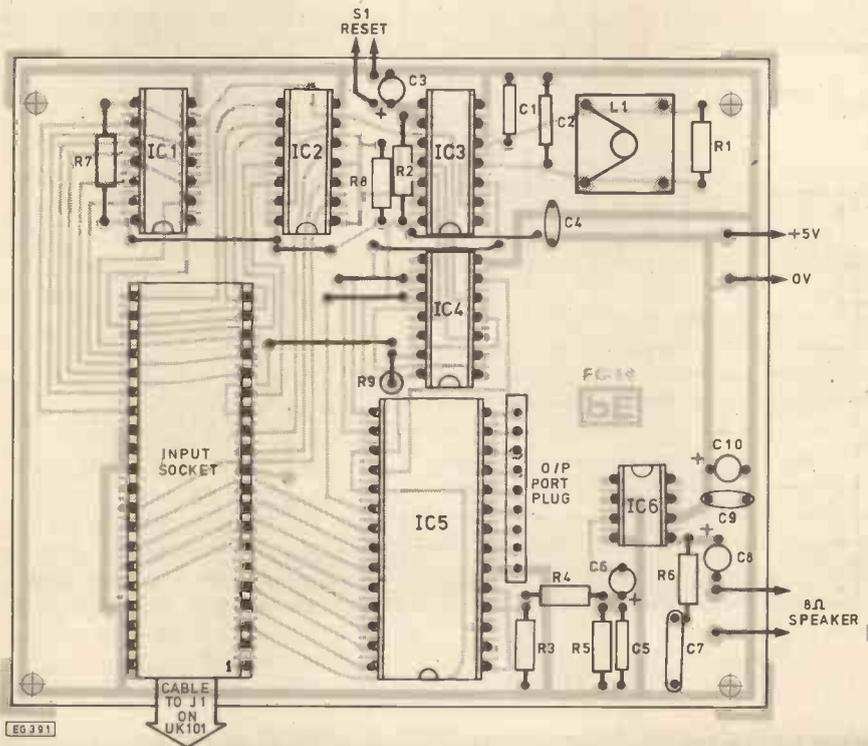

## COMPONENTS . . .

### Resistors

R1, R2	100k (2 off)
R3	1k
R4	4k7
R5	470
R6	10
R7, R8	10k (2 off)
R9	2k2

### Capacitors

C1, C2, C5	470p (3 off)
C3	10 $\mu$ tant., 10V
C4, C9	100n (2 off)
C6	4 $\mu$ 7 tant. 10V
C7	47n
C8, C10	100 $\mu$ tant. 10V (2 off)

### Integrated Circuits

IC1	74LS38
IC2	74LS33
IC3	4011
IC4	4025
IC5	AY-3-8912
IC6	LM386

### Miscellaneous

L1	RS coil former: 228-090 + 2 cores: 228-107
S1	SPST push button
Speaker	8 $\Omega$

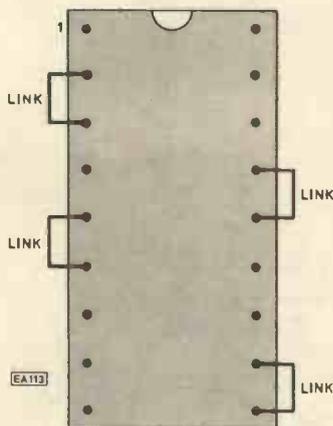


Fig. 8. Blanking plugs for IC6 and IC7 sockets on the 101

To check envelope shapes clear above program by typing NEW.

Enter the following:

```

10 POKE 61680, 1
20 POKE 61681, 2
30 POKE 61680, 7
40 POKE 61681, 254
50 POKE 61680, 8
60 POKE 61681, 31
70 POKE 61680, 12
80 POKE 61681, 64
90 POKE 61680, 13
100 POKE 61681, 0
110 END

```

and run.

Change line 100

```
100 POKE 61681, 4
```

and run.

Change line 100

```
100 POKE 61681, 8
```

and run.

By referring to Fig. 3 you can check out all the waveforms by altering line 100.

Sweep frequency effects. Enter the following program:

```

10 LET A = 100 (INITIALISE A)
20 POKE 61680, 2
30 POKE 61681, A (LOAD A INTO REG. 2)
40 POKE 61680, 7
50 POKE 61681, 253 (SELECT CHAN. B O/P)
60 POKE 61680, 9
70 POKE 61681, 15 (SELECT FULL AMP. O/P)
80 LET A = A+2
90 IF A < 200 GOTO 20
100 GOTO 10

```

and run. You get a decreasing sweep frequency.

Change the following lines:

```

10 LET A = 200
80 LET A = A-2
90 IF A > 100 GOTO 20

```

and run. You get an increasing sweep frequency.

That checks out the unit. As you can see there is plenty of scope to add sound effects to your program. Short bursts of noise sound like gun shots, larger bursts sound like explosions. Tones can be played and the 3 channels allow chords to be output. All it takes is practice.

The unit may be fitted in a small case on its own or it may be mounted inside the computer case, as it is quite small.

```

10 INPUT "REGISTER"; R
20 INPUT "CONTENT"; C
30 POKE 61860, R: POKE 61681, C
40 GOTO 10

```

Learning to drive the sound generator will be much assisted by using the above program. You can load any register with any value directly, and discover how various control signals translate into actual sound. If you get in a pickle, push the reset button and start again.

# UK101-TELEPRINTER INTERFACE

BY J. J. TREVILLION

THIS interface allows the use of a *surplus* teleprinter with the UK101 or similar 6502 microprocessor based machine. To constructors on a restricted budget, this is a practical alternative to an expensive line-printer, accepting such disadvantages as the low rate of print, the restricted character set and the noisy mechanism.

A simple hardware addition is used, connected directly to the UK101 bus expansion socket, whilst the software has been designed for ease of use. Description centres on the use of a CREED Type 54 teleprinter, which the author purchased relatively cheaply from a local surplus equipment dealer, although there is no reason why the interface could not be used with other 50 baud, solenoid operated teleprinters, with a minimum of modification.

## HARDWARE

The author's teleprinter is fitted with a 240 volt synchronous motor which is to be preferred since it requires no setting up of speed. The teleprinter is operated by a solenoid which requires a drive of  $\pm 35\text{mA}$  for MARK/SPACE. This is obtained in the circuit of Fig. 1 by switching the polarity of 24 volts across the solenoid using a relay. This voltage is *high* to allow the inclusion of a series resistor, R2, to maintain the switching speed of the solenoid, due to its relatively high inductance. The relay is driven by direct memory-mapped software control, such that writing to address F100 sends a MARK, and F101, a SPACE.

Power for the additional logic can just be derived from the UK101 five volt supply, since only an additional 20mA will be drawn by the low-power schottky devices.

No constructional details, or circuits of the  $\pm 12$  volt supply, are given since these are not critical.

## SOFTWARE

A disassembled listing of the program (produced via the described interface) with a hexadecimal dump of the look-up tables used by the program, is shown in Fig. 2, whilst the flow-chart of Fig. 3 makes the listing understandable.

The program is located in the last 512 bytes of RAM of a UK101 containing 8K of RAM, and uses RAM between addresses 0222 and 0266 for temporary storage. The program can


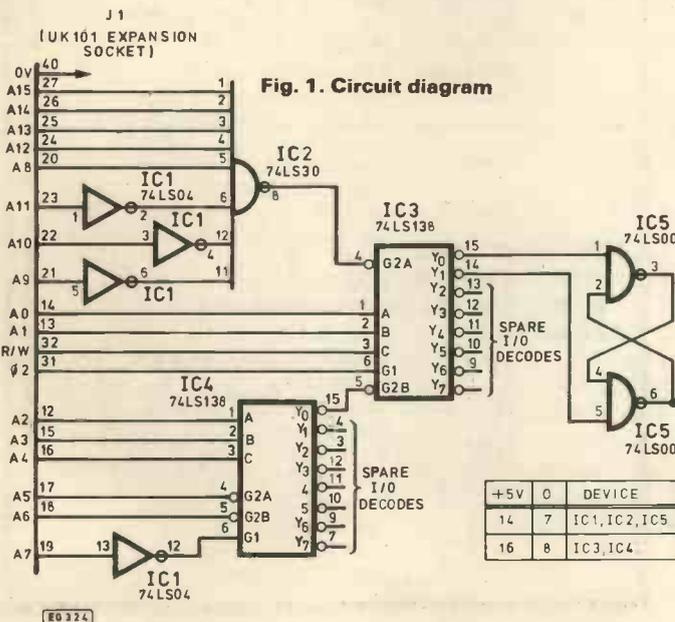


Fig. 1. Circuit diagram

1E00 48 PHA	1E97 D0FA BNE \$1E93	1F31 BD961F LDA \$1F96,X
1E01 A900 LDA \$800	1E99 8E2302 STX \$0223	1F34 F009 BEQ \$1F3F
1E03 802302 STA \$0223	1E9C 8E2402 STX \$0224	1F36 EB INX
1E06 802402 STA \$0224	1E9F 4C191F JMP \$1F19	1F37 CD2202 CMP \$0222
1E09 A91D LDA \$81D	1EA2 C912 CMP \$812	1F3A F0CA BEQ \$1F06
1E0B 8D1A02 STA \$021A	1EA4 F003 BEQ \$1EA9	1F3C EB INX
1E0E A91E LDA \$81E	1EA6 CE2402 DEC \$0224	1F3D D0F2 BNE \$1F31
1E10 8D1B02 STA \$021B	1EA9 4C4B1F JMP \$1F4B	1F3F 207B1F JSR \$1F7B
1E13 8A TXA	1EAC A200 LDX \$800	1F42 4C0C1F JMP \$1F0C
1E14 48 PHA	1EAE AC2302 LDX \$0223	1F45 00 BRK
1E15 98 TYA	1EB1 BD0C1F LDA \$1F0C,X	1F46 A96E LDA \$86E
1E16 48 PHA	1EB4 F01E BEQ \$1ED4	1F48 8D2602 STA \$0226
1E17 20461F JSR \$1F46	1EB6 CD2202 CMP \$0222	1F4B A207 LDX \$807
1E1A 4C661E JMP \$1E66	1EB9 D014 BNE \$1ECF	1F4D A014 ASL A
1E1D 2020BF JSR \$BF2D	1EBB E8 INX	1F4E 9006 BCC \$1F56
1E20 48 PHA	1EBD BD0C1F LDA \$1F0C,X	1F50 8D00F1 STA \$F100
1E21 AD0502 LDA \$0205	1EBF 992702 STA \$0227,Y	1F53 4C591F JMP \$1F59
1E24 D002 BNE \$1E28	1EC2 EE2402 INC \$0224	1F56 8D01F1 STA \$F101
1E26 68 PLA	1EC5 E8 INX	1F59 205F1F JSR \$1F5F
1E27 60 RTS	1EC6 BD0C1F LDA \$1F0C,X	1F5D D0EE BNE \$1F4D
1E28 68 PLA	1EC9 8D2202 STA \$0222	1F5F D0EE BNE \$1F4D
1E29 D8 CLD	1ECC 4C41E JMP \$1ED4	1FF5 F0A0 LDY \$80A
1E2A C900 CMP \$800	1ECF E8 INX	1F61 48 PHA
1E2C F0F9 BEQ \$1E27	1ED0 EB INX	1F62 A9C8 LDA \$8C8
1E2E C90A CMP \$80A	1ED1 E8 INX	1F64 8D2502 STA \$0225
1E2F F0F5 BEQ \$1E27	1ED2 D0DD BNE \$1EB1	1F67 CE2502 DEC \$0225
1E32 8D2202 STA \$0222	1ED4 AD2202 LDA \$0222	1F6A D0BB BNE \$1F67
1E35 48 PHA	1ED7 C961 CMP \$861	1FC8 88 DEY
1E36 8A TXA	1ED9 900A BCC \$1EE5	1FD0 D0F3 BNE \$1F62
1E37 48 PHA	1EDB C978 BCS \$878	1F6F 68 PLA
1E38 98 TYA	1EDD B006 BCS \$1EE5	1F70 60 RTS
1E39 48 PHA	1EDF 38 SEC	1F71 A9D0 LDA \$8D0
1E3A AD2202 LDA \$0222	1EE0 E920 SBC \$820	1F73 8D2602 STA \$0226
1E3D C920 CMP \$820	1EE2 8D2202 STA \$0222	1F76 A97E LDA \$87E
1E3F D006 BNE \$1E47	1EE5 C941 CMA \$841	1F78 4C4B1F JMP \$1F4B
1E41 207B1F JSR \$1F7B	1EE7 9036 BCC \$1F1F	1F7B A912 LDA \$812
1E44 4C0C1F JMP \$1F0C	1EE9 C95B CMP \$85B	1F7D D0F9 BNE \$1F78
1E47 C909 CMP \$809	1EEB B032 BCS \$1F1F	1F7F A90A LDA \$80A
1E49 D017 BNE \$1E62	1EED AE2602 LDX \$0226	1F81 204B1F JSR \$1F4B
1E4B AD2302 LDA \$0223	1EF0 F00B BEQ \$1EFD	1F84 A232 LDX \$832
1E4E C940 CMP \$840	1EF2 20711F JSR \$1F71	1F86 205F1F JSR \$1F5F
1E50 F014 BEQ \$1E66	1EF5 AE2302 LDX \$0223	1F89 CA DEX
1E52 207B1F JSR \$1F7B	1EF8 D003 BNE \$1EFD	1F8A D0FA BNE \$1F86
1E55 EE2302 INC \$0223	1EFA 2071F JSR \$1F7F	1F8C 60 RTS
1E58 A907 LDA \$807	1EFD AD2202 LDA \$0222	1F8D A922 LDA \$822
1E5A 2D2302 AND \$0223	1F00 38 SEC	1F8F 204B1F JSR \$1F4B
1E5D D0EC BNE \$1E48	1F01 E940 SBC \$840	1F92 A208 LDX \$808
1E5F 4C191F JMP \$1F19	1F03 0A ASL A	1F94 D0F0 BNE \$1F86
1E62 C90D CMP \$80D	1F04 AA TAX	
1E64 D046 BNE \$1EAC	1F05 CA DEX	
1E66 AD2402 LDA \$0224	1F06 BD961F LDA \$1F96,X	
1E69 F01E BEQ \$1E89	1F09 204B1F JSR \$1F4B	
1E6B 20461F JSR \$1F46	1F0C EE2302 INC /0223	
1E6E 2071F JSR \$1F7F	1F0F AD2302 LDA \$0223	
1E71 A200 LDX \$800	1F12 C940 CMP \$840	
1E73 BD2702 LDA \$0227,X	1F14 9003 BCC \$1F19	
1E76 8E2202 STX \$0222	1F16 4C661E JMP \$1E66	
1E79 20A21E JSR \$1EA2	1F19 68 PLA	
1E7C AE2202 LDX \$0222	1F1A A8 TAY	
1E7F E8 INX	1F1B 68 PLA	
1E80 AD2402 LDA \$0224	1F1C AA TAX	
1E83 F004 BEQ \$1E89	1F1D 68 PLA	
1E85 E040 CPX \$840	1F1E 60 RTS	
1E87 90EA BCC \$1E73	1F1F AD2602 LDA \$0226	
1E89 208D1F JSR \$1F8D	1F22 D0DD BNE \$1F2F	
1E8C 2071F JSR \$1F7F	1F24 20461F JSR \$1F46	
1E8F A912 LDA \$812	1F27 AD2302 LDA \$0223	
1E91 A240 LDX \$840	1F2A D003 BNE \$1F2F	
1E93 CA DEX	1F2C 2071F JSR \$1F7F	
1E94 9D2702 STA \$0227,X	1F2F A200 LDX \$800	
		1F96
		2D 62 3F 4E 3A 3A FF 4A
		1F9E
		33 42 25 5A 40 2E 18 16
		1FA6
		38 32 07 6A 28 7A 29 26
		1FAE
		2E 1E 2C 1A 39 0E 30 36
		1FB6
		31 76 34 2A 27 52 35 06
		1FBE
		37 72 30 3E 32 66 27 5E
		1FC6
		36 56 2B 46 22 52 23 5A
		1FCE
		26 1E 00 00 00 00 00 00
		1F 6
		00 00 00 00 00 00 21 1E
		1FDE
		27 24 5E 53 2A 46 58 3B
		1FE6
		1A 3A 3C 62 28 3E 62 29
		1FEE
		5E 52 49 00 00 00 00 00
		1FF6
		00 00 00 00 00 00 00 00

Fig. 2. Operating software

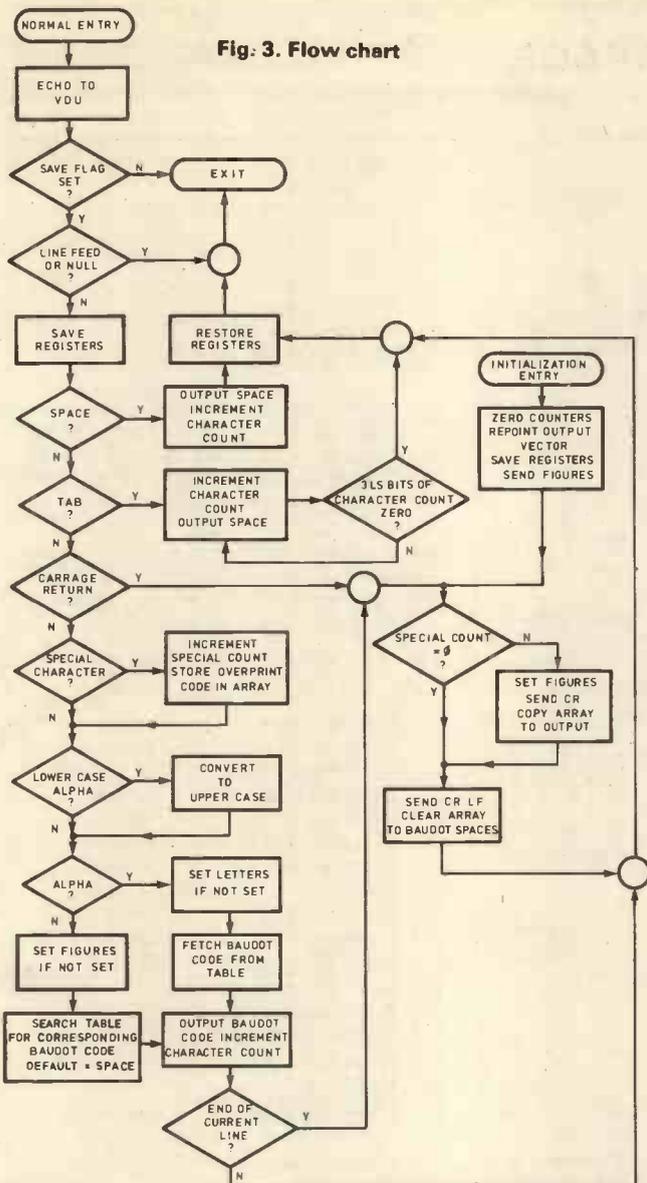

EQ 320

EXCLAMATION MARK	=	!
CURRENCY SYMBOL	=	£
ASTERISK	=	*
SEMI-COLON	=	;
LESS THAN	=	<
GREATER THAN	=	>
UP ARROW	=	↑

**Fig. 4. Improved characters**

easily be relocated for machines with less memory, and it is worth considering storing the routines in EPROM for convenience.

The routines provide the required ASCII to BAUDOT conversion by the use of a look-up table. A second table is used to increase the limited BAUDOT character set by *overprinting* BAUDOT characters. The characters so produced are demonstrated in Fig. 4, the overprinting being achieved by storing the BAUDOT codes to be overprinted in an array (0227 to 0266) and copying them at the end of a line of text.

Other features of the software include automatic lower case to upper case conversion, and the simulation of the TAB function (CONTROL I) to aid formatting.

A memory map of the program, including the entry points for useful subroutines, is shown in Table 1.

**BASIC OPERATION**

The software has been designed so that with a change to the UK101 output vector, address 021A, the teleprinter can be brought into use. Thereafter the output is controlled by the SAVE flag, address 0205, with output directed to the teleprinter only when the flag is set.

The initialisation subroutine provides a routine to change the output vector, clear the temporary storage used by the program, and position the teleprinter at the start of a new line.

At the beginning of a BASIC program, with the printer routines loaded and protected, the procedure to output to the teleprinter would be:

- 1 POKE 11,0 : POKE 12,30 : X =USR(X) : REM INITIALISATION
- 2 POKE 517,1 : REM SET SAVE FLAG
- 3 REM ALL OUTPUT NOW GOES TO TELEPRINTER AND VDU.

In machine code applications the procedure is also simple:  
JSR \$1E00 For initialisation.

Thereafter:

JSR \$1E1D Outputs the ASCII character in the accumulator to the VDU and, if the SAVE flag is set, to the teleprinter.

**Table 1. Memory map.**

ADDRESS	FUNCTION
0222	Accumulator Temporary Store.
0223	Character Count.
0224	Overprint Character Count.
0225	Delay Counter.
0226	Figures Case Flag.
0227	Array Of Overprint BAUDOT Character Codes. (64 Locations.)
1F96	Start of Main Look-Up Table. (Terminated by 00.)
1FDC	Start of Overprint Table. (Terminated by 00.)
ADDRESS	SUBROUTINE
1E00	Initialisation Routine.
1E1D	Main Printing Routine.
1F46	Send FIGURES Case & Set Figures Flag.
1F4B	Output BAUDOT Code In Accumulator.
1F5F	2 milli-second Delay.
1F71	Send LETTERS Case & Clear Figures Flag.
1F7B	Output Space.
1F7F	Output Carriage Return.
1F8D	Output Line Feed.

# MICRO PROMPT.

The hardware and software exchange point for PE computer projects

## EXPANDING GROUP

We have received the first newsletter proper from the UK101 User Group, which is accumulating members in the British Isles and overseas.

The group is doing some important work now, such as investigating the "sticking" FRE function, which Adrian Waters, the club organiser points out, is the tip of a serious iceberg concerning string data storage. A complex sound board is nearing completion, whilst behind the scenes the program library is swelling with games and educational software, and new languages such as PILOT.

The Newsletter, ROM, carries software news, hardware modifications, useful ROM and RAM locations, i.e. routine entry points, and a problem page. Equipment reviews are to become a regular feature.

There is no entry fee, and the subscription for six months membership is £2.50, which should be made payable to Adrian Waters, at: 117 Haynes Rd., Hornchurch, Essex.

The following hardware modification was supplied by the 101 User Group, the details having originated from club member Mr. R. Freeman.

## 2MHz conversion

In the normal machine, the clock frequency of 1MHz is presented at pin 37 of the 6502 chip by the B output pin of IC29. Because the 6502 can accept a faster clock, many members have increased the speed of their machines by the following modification:


The 2MHz signal can be obtained from pin 8 of IC29 and applied to the 6502 by the 00 line at pin 37. The conversion can be implemented by cutting the track of the p.c.b. as shown in Fig. 1 and substituting the new link. Many members have included a changeover switch, although this cannot be used whilst the machine is working, without getting "hung up".

## MODEM TO TANDY?

Sir—Firstly, thank you for an excellent magazine, it rivals any we have in the States.

Secondly, I picked up a copy of your February 1980 issue and am very interested in the Modem article by K. Amor. After much difficulty I also obtained part 2 in the March issue—expecting to learn how to connect this System to my Tandy TRS-80 16K Level II—only to be very disappointed. I would be very interested in any information you or your readers might have to offer. I would also be interested in exchanging hardware and software with any of your readers. Thank you.

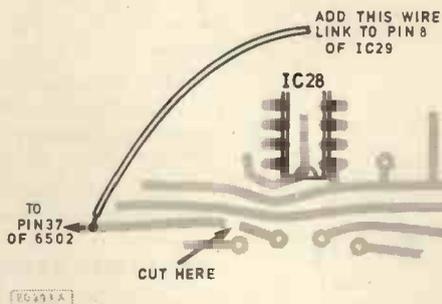From the desk of Bryan McPhee,  
Capt., USAF,  
2742 Virginia Trail,  
Browns Mills,  
N.J. 08015, U.S.A.



## SHIFTY CHARACTERS

Sir—The following useful feature of the UK101 is not mentioned in your series of articles or the instruction manual:

With Shift Lock up, the keyboard returns lower case letters. To input a few upper case letters or figures, press L.H. Shift and the key for the character required (i.e. L.H. Shift cancels the effect of Shift Lock being up).

To obtain the normally shifted characters (eg. ") then press R.H. Shift and the appropriate key.

Please continue to publish the very useful articles in Micro Prompt on this excellent machine.

K. W. Lambert,  
Halesowen,  
W. Midlands.

Sorry, we thought people knew—Ed.

## GET KEY FOR UK101

To get a key from the keyboard without stopping the program, as in the input statement, run the following program, then each time you require a "Get Key" statement write:

```
(Line number) AS = "Space" : POKE 11,  
34 : POKE 12, 2 : X = USR(X)
```

After this line AS will be a space unless a key was pressed, in which case AS will be equal the character of the key which was pressed.

Any S variable can be used, including array's. This can be used to replace the 'GET AS' statement as used on the PET.

To set up the subroutine:

```
10 FOR A = 546 TO 597  
20 READ B : POKE A, B : NEXT  
30 DATA 169, 2, 32, 190, 252, 32  
40 DATA 198, 252, 208, 7, 10, 208  
50 DATA 245, 169, 32, 208, 28, 74  
60 DATA 32, 200, 253, 152, 133, 252  
70 DATA 10, 10, 56, 229, 252  
80 DATA 133, 252, 138, 74, 32, 200  
90 DATA 253, 24, 152, 101, 252, 168  
100 DATA 185, 207, 253, 160, 0, 41  
110 DATA 127, 145, 105, 96, 0
```

Once run this program can be erased if required.

J. L. Brice, Ashford, Kent.

## ERROR MESSAGE ERROR

Sir—I am a UK101 user who has, like many, been frustrated by the rather graphic error messages. The result of this has been the following short program to produce "standard" Microsoft BASIC error messages:

Enter monitor

```
type :0222/29 (carriage return)  
7A     "  
AC     "  
2D     "  
BF     "
```

Reset and enter BASIC.

Type: POKE 538, 34 : POKE 539, 2

All error messages will then be standard. The program works by masking off the most significant bit of all characters printed. The BASIC stored messages all have the MSB set on the last character, and it is the omission of an instruction to clear this bit which caused the original error messages. Considering the complexity of the BASIC, such an omission in the error routine is understandable, but I hope this will be corrected.

## New error messages

Syntax error	SN error
Double dimension	DD error
Division by zero	D0 error
Undefined statement	US error
Undefined function	UF error
Bad subscript	BS error
Long string	LS error
Out of memory	OM error
Overflow	OV error
Continue error	CN error
String temporaries	ST error
Type mismatch	TM error
Next without FOR	NF error
Function call error	FC error
Illegal direct	ID error
Out of string space	OS error
Out of data	OD error

D. J. Anderson,  
London.

## MAP READING

Sir—You may wish to pass on to your readers an error discovered in the memory map of the UK101, found whilst implementing an 6821 I/O port, at a dedicated address.

The ACIA which resides at F000—F001 is due to page select decoding repeated at a further 127 locations through Hex page F0. The memory map should thus be amended to show that ACIA resides from F000—F0FF.

Readers might also like to note that an unbuffered data bus, terminates in a patch pad with 0.1 inch pitch spacing, to the left of the AC1A chip i.c. 14. This can only be used with selectable tristate logic, but as most 6502 compatible support devices have this facility, the cost of the AT28's may be saved.

M. C. Mannering,  
Walthamstow.

# CAMBRIDGE LEARNING

# Self- Instruction Courses

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

## Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

### DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:  
Book 1 Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.  
Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.  
Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.  
Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.

### DESIGN OF DIGITAL SYSTEMS £12.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.


Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.  
Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.  
Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.  
Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).  
Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.  
Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

## Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

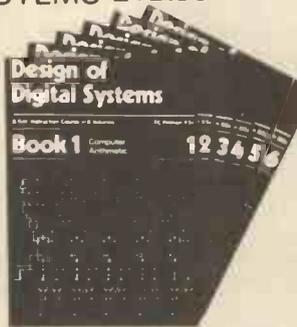
### THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.


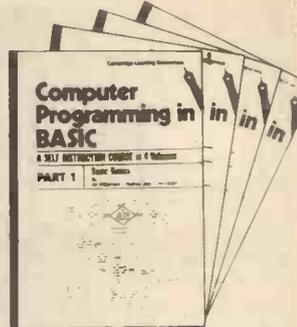
## Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.



### COMPUTER PROGRAMMING IN BASIC £9.00

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.  
Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.  
Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.  
Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

### THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

### FORTRAN COLORING BOOK £5.40

"If you have to learn FORTRAN, no one actually wants to assimilate it for the color. Buy this book. Forget the others - this one is so good it will help you understand the standard, dense, boring, unintelligible FORTRAN." *New Scientist*.

### A.N.S. COBOL £4.40

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

### GUARANTEE - No risk to you

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

- .... Digital Computer Logic & Electronics @ £7.00
- .... Design of Digital Systems @ £12.50
- .... Algorithm Writer's Guide @ £4.00
- .... Computer Programming in BASIC @ £9.00
- .... BASIC Handbook @ £11.50
- .... Fortran Coloring Book @ £5.40
- .... A.N.S. Cobol @ £4.40

#### FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M.Ch. Barclay/Trust/Visa  Am. Exp.  Diners
- 4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service

Card No. .... Signed.....  
THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL: Eur, N.A.F. Mid.E. add 1/2 to price of books: Jpn. Aus. N.Z. Pcfc add 1/2; elsewhere add 1/2

Name .....  
Address .....

U.K. Delivery: up to 28 days


**CAMBRIDGE LEARNING,**  
Unit 24 Rivermill Site, FREEPOST, St. Ives, Huntingdon,  
Cambs. PE17 4BR England.

Reg. in Eng. No. 1328762

# PE TELETEXT

## with INFRA-RED REMOTE CONTROL

David Shortland

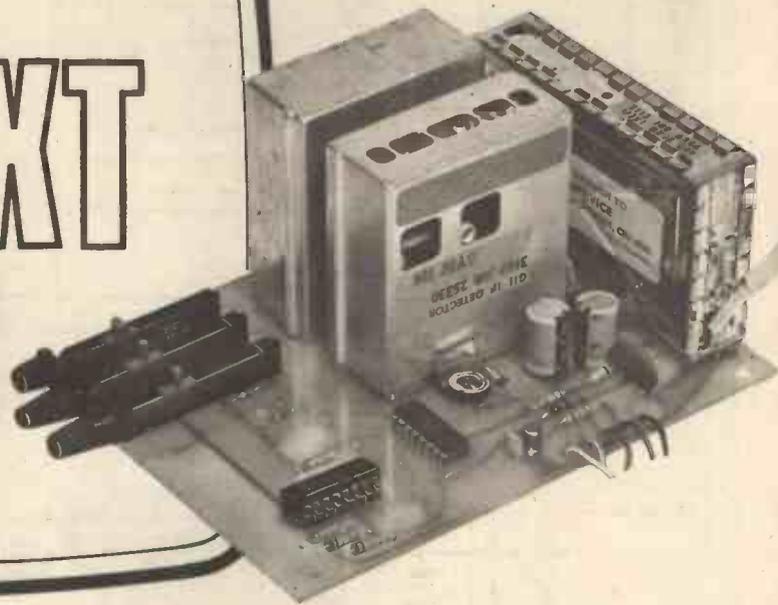

### PART 2... TUNER & DECODER

In common with all teletext decoders, the Mullard module requires a high quality video signal from which the information is extracted. Since most readers will have little or no experience of working at TV i.f. frequencies (around 40MHz) and insufficient test equipment, the use of a pre-aligned signal section becomes almost mandatory. The solution chosen is shown in block diagram form in Fig. 2.1.

The tuner is the Mullard U321 which is specifically designed for use in the UK. It features a PIN diode attenuator to provide very good signal handling when the signal from the aerial is too large and the a.g.c. system comes into operation. It is used by several TV setmakers and is thus readily available.

The i.f. section is that used in the Philips G11 TV chassis and comprises two modules which are soldered directly onto the p.c.b. The i.f. output from the tuner is applied to pin 1 of the vision selectivity module (VSM). This, as its name implies, carries out the required bandshaping to produce the correct response as determined by the specification of the broadcast signal in the UK. The output from this module is applied to pin 1 of the vision detector module (VDM). This detects the signal to produce a video output; generates an automatic frequency control (a.f.c.) signal which is externally added via R31 to the tuning voltage to counteract any tuning drift; generates an a.g.c. current which is applied to both the vision selectivity module and to the tuner; filters to the 6MHz intercarrier sound signal which is added to the modulator since the video signal is stripped off this inside the module. Other filtering which is performed by this module is not of interest to us.

Turning our attention to the circuit diagram shown in Fig 2.2, it can be seen that the way the tuner and two modules are interconnected forms an extremely simple i.f. section with very few peripheral components. It runs from the stabilised +12V rail which is decoupled at r.f. and l.f. by R29, C11 and C13. The a.g.c. signal to the tuner is decoupled by C14 and C12 and current limited by R32. As mentioned earlier, a.g.c. is applied to both the i.f. pre-amplifier and to the tuner. The latter control signal is delayed, i.e., a.g.c. is gradually applied to the i.f. section first and when this reaches a certain point it is then also applied

to the tuner. This point is called the a.g.c. takeover point and is determined by the setting of VR1 in conjunction with D1.

The a.f.c. signal from pin 7 of the VDM is added to the tuning voltage via R31. Resistors R33 and R34 determine the quiescent voltage (around 5.7V).

Turning our attention to IC1, this is a b.c.d. to 1 or 10 decoder/varicap driver which is operated from the stabilised 33V rail. Only four of the available channels are used in our design. The i.c. decodes the four-bit word according to the table below:

A	B	C	D	O/P
0	0	0	0	1
0	0	0	1	2
0	0	1	0	3
0	0	1	1	4
0	1	0	0	5
0	1	0	1	6
0	1	1	0	7
0	1	1	1	8
1	0	0	0	9
1	0	0	1	10

When a channel is decoded, the output of the SL470 goes high and connects the appropriate tuning potentiometer to the +33V stabilised supply. The tuning voltage is applied to the varicap diodes in the U321 tuner via R30.

The SL470 is driven by the buffer IC3 (4050).

#### SETTING UP

It is imperative that no attempt is made to adjust any of the coils in the tuner or modules. In fact the only adjustment to be made is the a.g.c. crossover point. This is done by tuning into a station and adjusting VR1 until the picture becomes slightly noisy (snow). The control is then backed off until the noise disappears and then backed off a little more from that point.

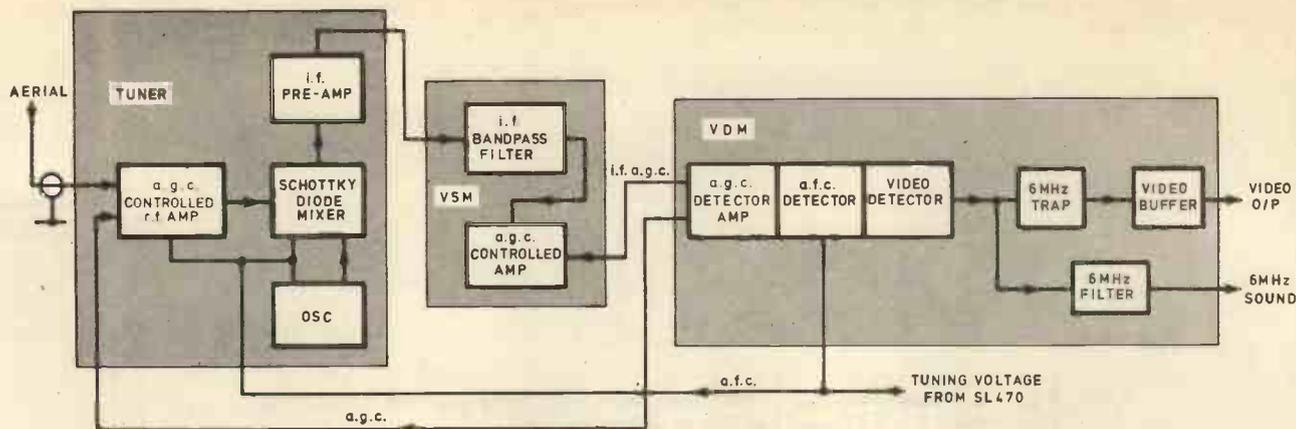


Fig. 2.1. Block diagram of the Tuner

EC 18

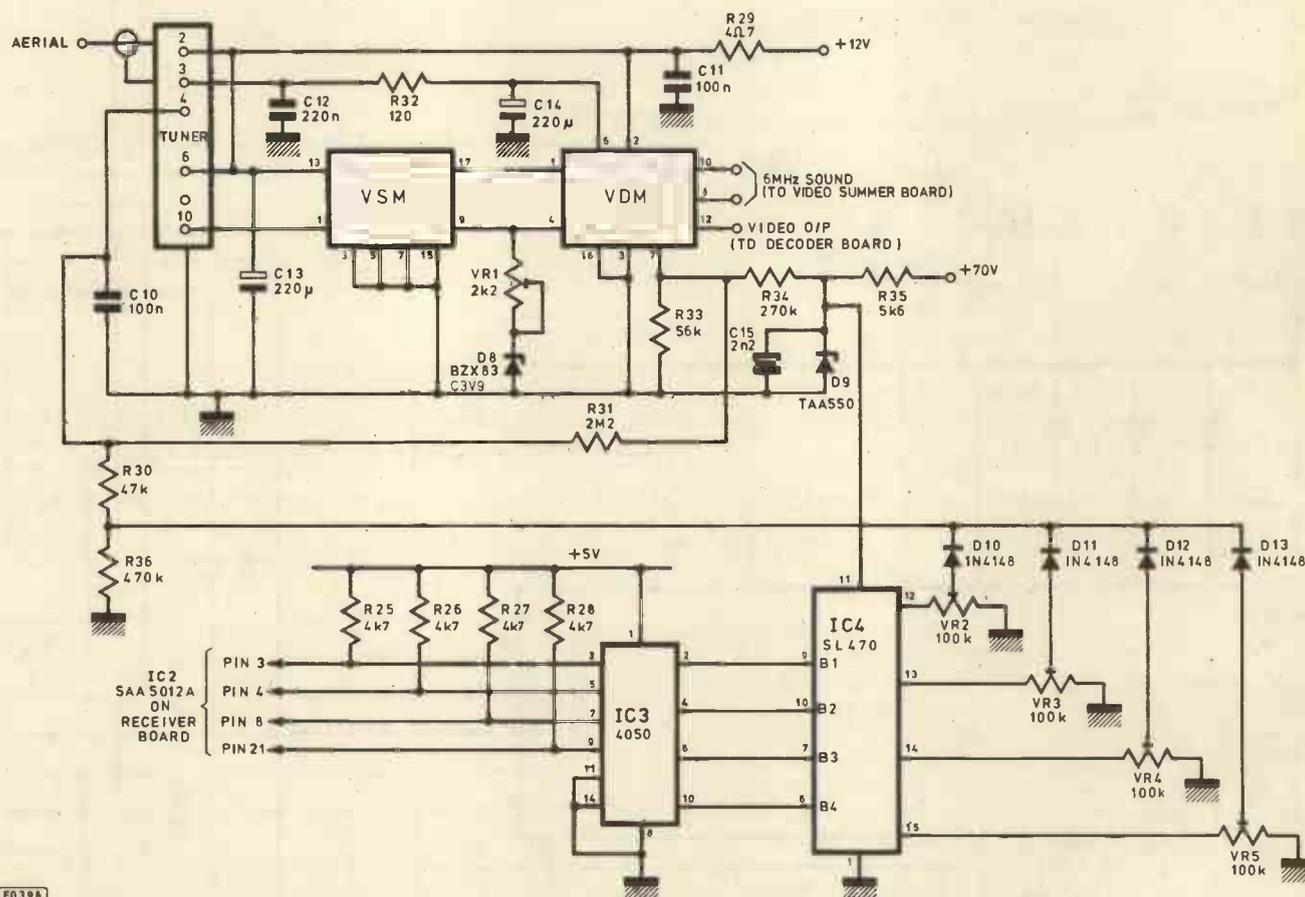


Fig. 2.2. Circuit diagram of the Tuner Circuit

EQ396

## CONSTRUCTION

The p.c.b. design for the tuner is shown in Fig. 2.3 with the component layout in Fig. 2.4. The smaller components should be mounted first and the tuner, VSM and VDM mounted last. There is a wire link which should be fitted near one end of IC4.


The eleven connections from the tuner can be wired using ribbon cable. After soldering check the board carefully for any solder splashes and if everything is alright insert the two i.c.s.


## DECODER

The circuit diagram of the decoder unit is shown in Fig. 2.5. The decoder has been designed around four dedicated LS1 integrated circuits. The main functions of the four i.c.'s are:

- SAA 5020 (TIC) Timing chain
- SAA 5030 (VIP) Video input processor
- SAA 5040 (TAC) Teletext data acquisition and control
- SAA 5050 (TROM) Teletext ROM, character generator

Fig. 2.5. Circuit diagram of the Decoder Board. Note that the decoupling capacitors C37 to C46 are not shown in the diagram

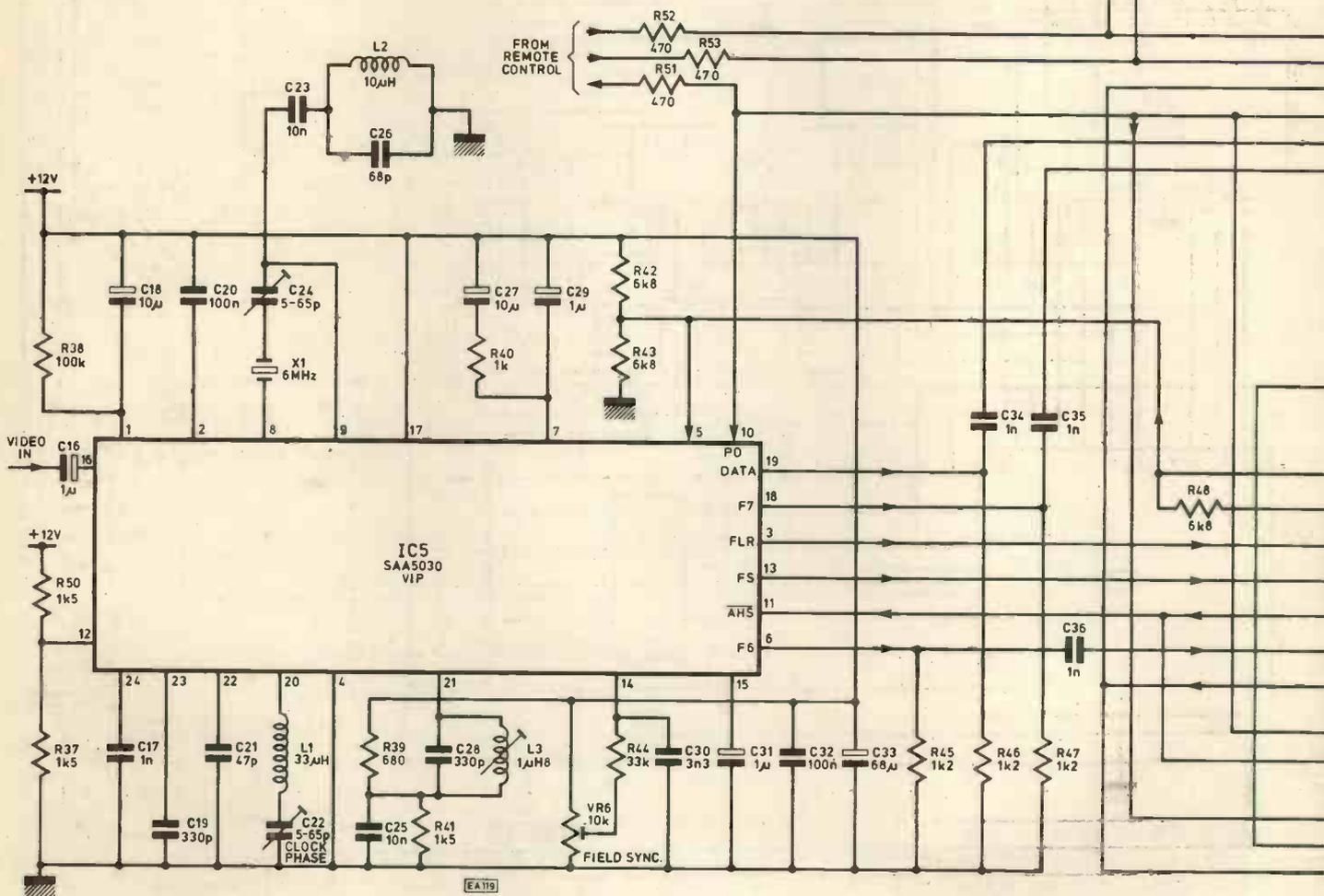

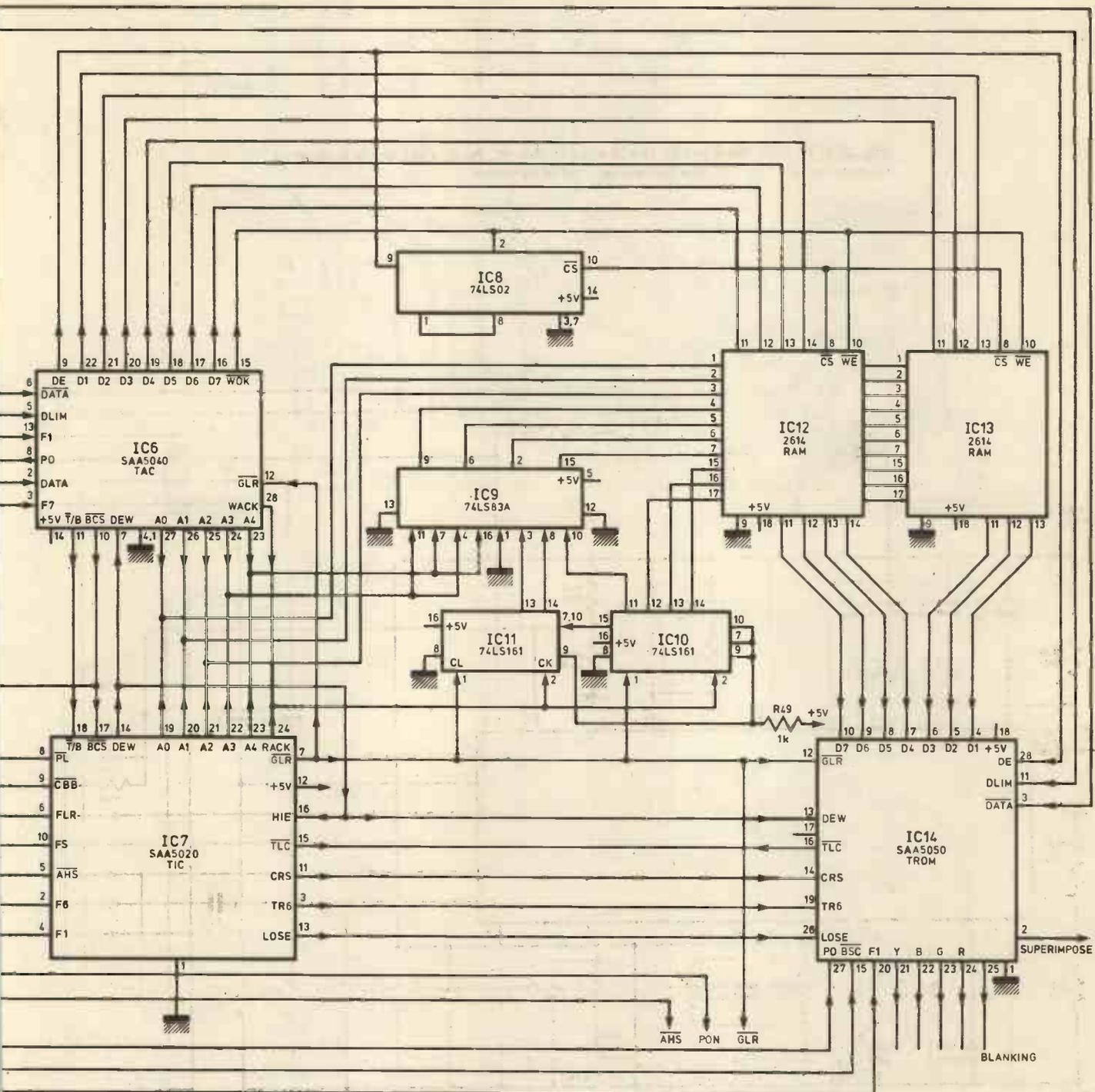

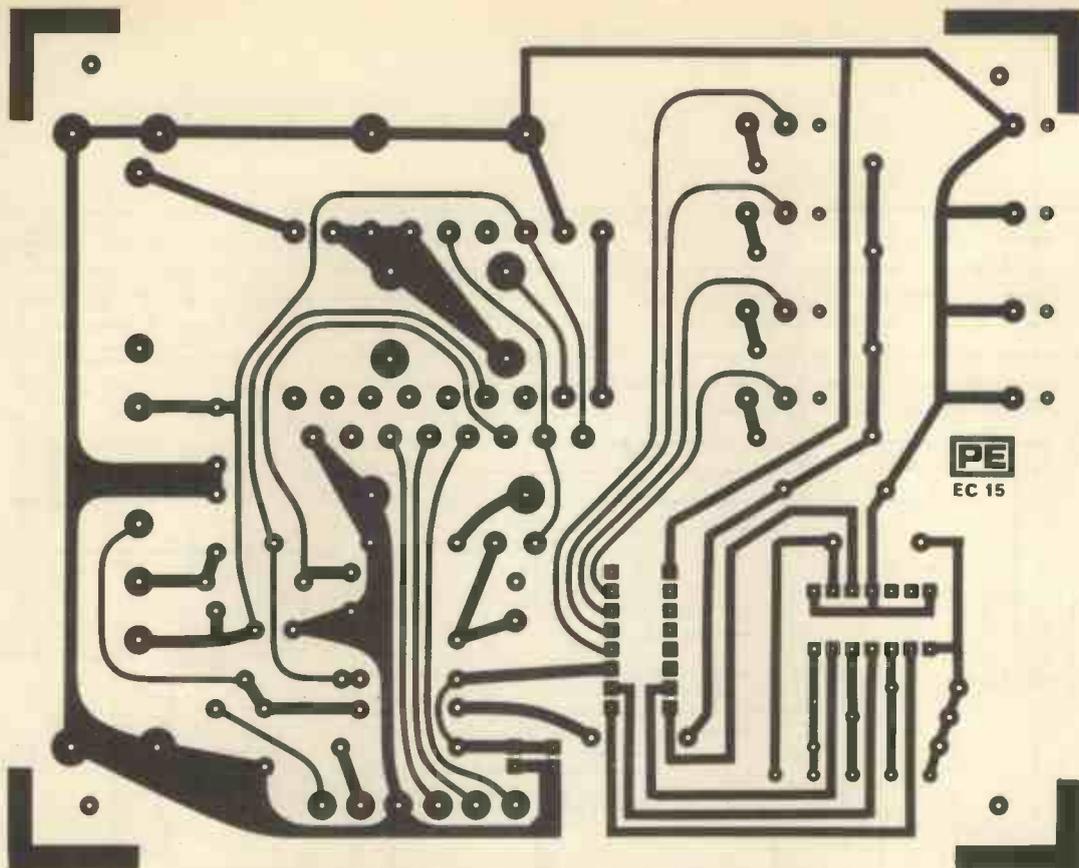


Fig. 2.3. P.c.b. design of the Tuner

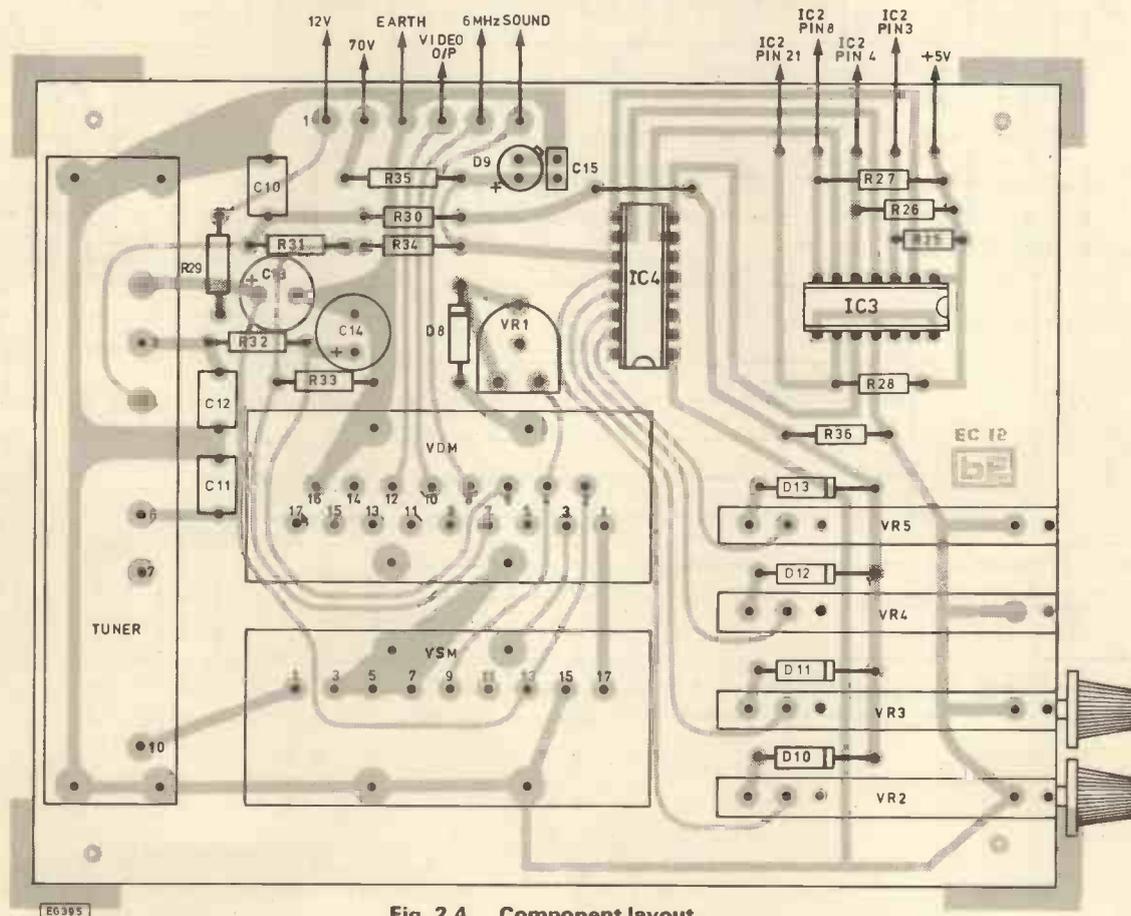


Fig. 2.4. Component layout

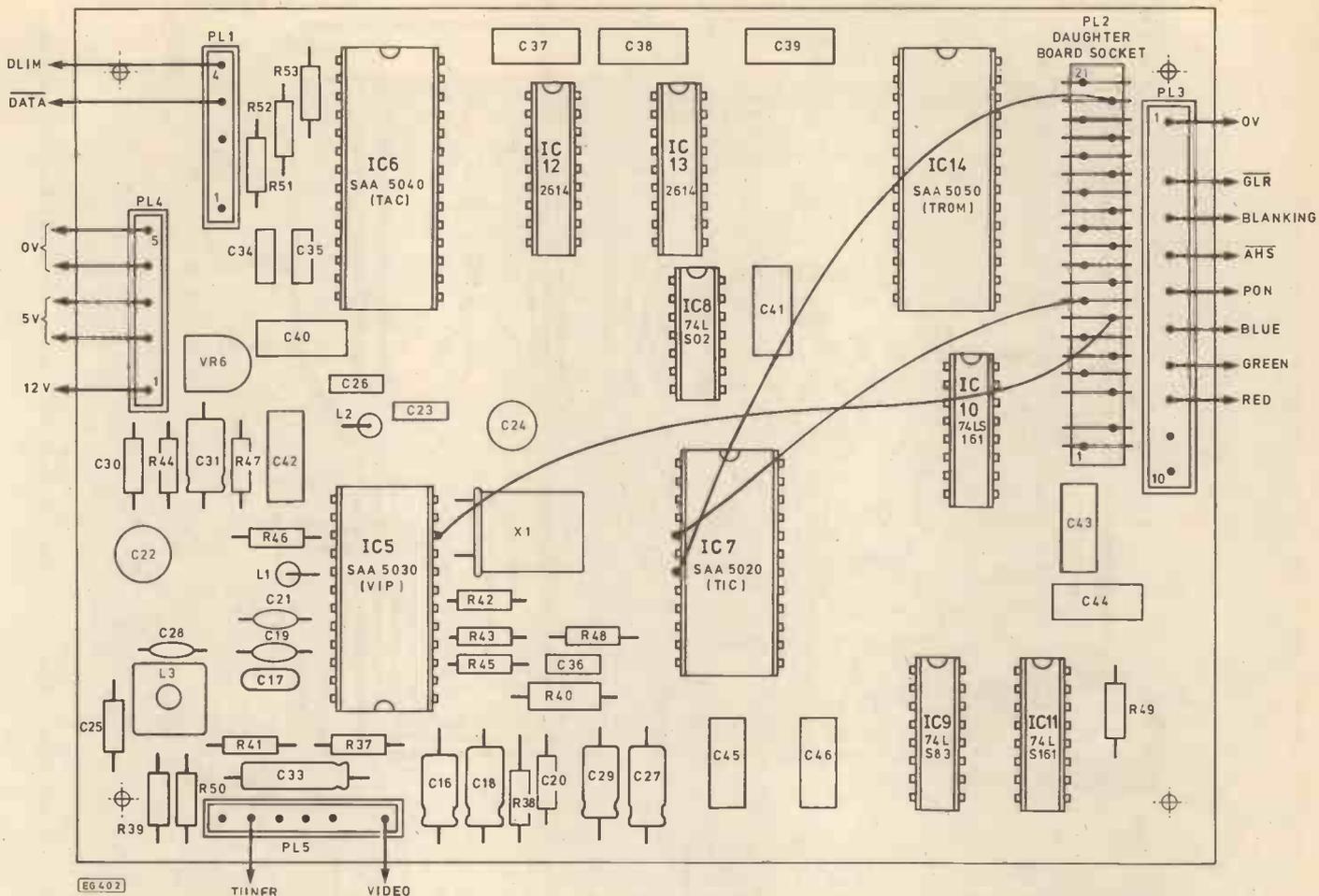


Fig. 2.6. Component layout of the Decoder Board. Note C32 is not used on the supplied board

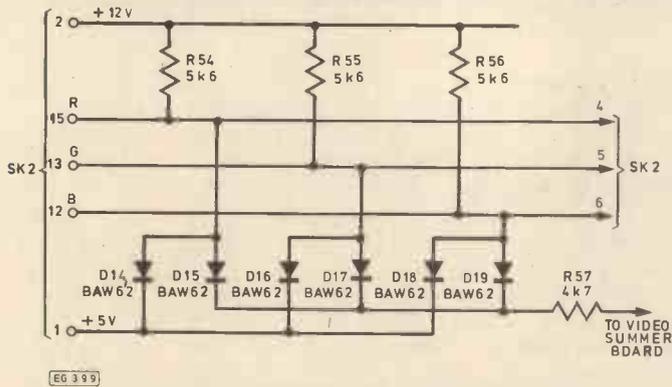


Fig. 2.7. Circuit diagram of the Daughter Board

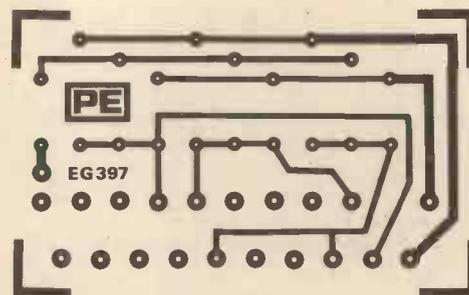


Fig. 2.8. P.c.b. design for the Daughter Board

## COMPONENTS... DAUGHTER BOARD

### Resistors

R54, R55, R56 5k6 (3 off)  
R57 4k7

### Diodes

D14 to D19 BAW 62 (6 off)

### Sockets

SK2 21-way socket  
P.c.b.

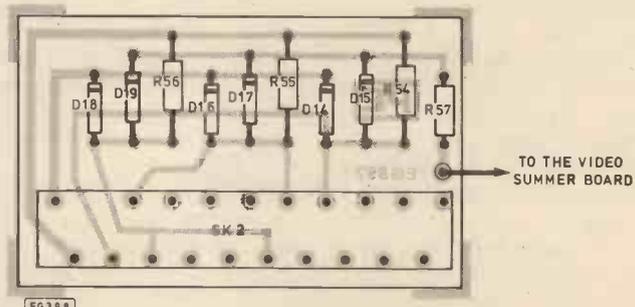


Fig. 2.9. Component layout

## COMPONENTS . . .

### TUNER

#### Resistors

R25, R26, R27, R28	4k7 (4 off)
R29	4 $\Omega$ 7
R30	47k
R31	2M2
R32	120
R33	56k
R34	270k
R35	5k6 0.5W
R36	470k

All resistors  $\frac{1}{4}$ W 5% carbon except where otherwise stated.

#### Capacitors

C10, C11	100n (2 off)
C12	220n
C13, C14	220 $\mu$ 16V (2 off)
C15	2n2

#### Semiconductors

D8	BZX 83 C3V9
D9	TAA 550
D10 to D13	IN4148 (4 off)
IC3	4050
IC4	SL470

#### Potentiometer

VR1	2k2 preset
VR2 to VR5	100k tuning pots (4 off)

#### Miscellaneous

Tuner 3113 108 6246  
VSM 3113 108 25350  
VDM 3113 108 25330  
P.c.b.

### DECODER

#### Resistors

R37, R41, R50	1k5 (3 off)
R38	100k
R39	680
R40, R49	1k (2 off)
R42, R43, R48	6k8 (3 off)
R44	33k
R45, R46, R47	1k2 (3 off)
R51, R52, R53	470 (3 off)

All resistors  $\frac{1}{4}$ W 5% carbon

#### Capacitors

C16, C29, C31	1 $\mu$ 25V (3 off)
C17, C34, C35, C36	1n (4 off)
C18, C27	10 $\mu$ 25V (2 off)
C19, C28	330p (2 off)
C20, C32	100n (2 off)
C21	47p
C22, C24	5-65p (2 off)
C23, C25	10n (2 off)
C26	68p
C30	3n3
C33	68 $\mu$ 25V
C37 to C46	100n (10 off)

#### Semiconductors

IC5	SAA 5030
IC6	SAA 5040
IC7	SAA 5020
IC8	74LS02
IC9	74LS83A
IC10, IC11	74LS161 (2 off)
IC12, IC13	2614 (2 off)
IC14	SAA 5050

The TIC, TAC and TROM i.c.'s are MOS N-channel devices whereas the VIP is a monolithic bipolar type.

The decoder has two main functions: to extract the teletext data from the incoming video signal and to process it, writing the page data into memory this function uses the VIP and TAC chips. The second function is to convert the information in the memory into a video signal to display the text on the screen. The generation of characters is carried out by the TROM and the TIC provides all the timing signals from the TIC which are synchronised to the incoming video signal so that the text and television picture may be displayed together.

The video signal from the Tuner board is fed to pin 16 of the VIP via a coupling capacitor (C16). The VIP has two separate sections: a data retrieval section and a display clock generator.

The incoming video signal contains picture, sync and teletext data which is sliced and then the teletext information extracted. A clock signal is generated from the sliced data using the tuned circuit connected to pin 21. This signal (F7) is used to clock the data into the TAC chip.

The 6MHz clock oscillator (pins 8, 9) has its output (pin 6) taken to the TIC chip where it is used to provide a clock pulse every 64 $\mu$ s. This pulse is then passed back to the VIP where it is compared with the incoming line sync signals. This enables the timing system of the teletext display to be phase-locked with the incoming television picture signal.

### TAC SAA5040

The principle function of the data acquisition section of the TAC is to process the teletext data so that it can be written into the memory. The control section of the TAC receives information from the remote control (pins 5, 6). This information is processed and then used to operate the various display functions of the decoder (i.e. time, page selection, status etc.)

The data acquisition section checks the incoming data from the VIP and any words having a single bit error are corrected. Address words having two bits wrong are rejected.

The input (pin 2) receives a serial data stream of teletext data from the 5030 the data rate is 6.9375 MHz. The information is clocked into the TAC (pin 3) by the clock output from the 5030.

The memory block which consists of two 1K x 4 static RAMs receives character data from pins 16 to 22 of the TAC. Whenever a character is written into memory, WOK (write OK) pin 15 is activated. After each character a clock signal WACK (write address clock) pin 28 is supplied to the address counters to address the next memory location.

The DEW (data entry window) signal from pin 14 of the TIC enables the TAC to operate in the data entry mode by enabling the data and row address outputs. The data acquisition circuits of the TAC are reset at the end of every line by a  $\overline{\text{GLR}}$  (general line reset) pulse from pin 7 of the TIC.

The PO (picture on) output to the 5012A, 5030 and 5050 from the TAC is used to switch the television video on or off (a 'high' for picture on and a 'low' for picture off).

A 'high' DE (display enable) output to the TROM enables the teletext display whilst in its 'low' state the display is disabled.

The  $\overline{\text{BCS}}$  (big character select) output to the 5020 and the 5050 is used to select the double height characters. A 'high' output is used for normal characters and a 'low' for double height characters.

The T/B (top/bottom) output to the 5020 (pin 18) selects whether a top or bottom half page is selected (a 'high' for top, and a 'low' for bottom).

The three state outputs for the memory addresses (pin 23 to 27) AO to A4 specify in which of the 24 screen rows the teletext data is to be written.

### TIC SAA 5020

The 6MHz clock signal (F6), which is used to derive the basic timings from the teletext display, is fed to pin 2 of the TIC from pin 6 of the 5030. This signal is sub-divided by the TIC down to 25Hz, the frame rate of the television to generate all the timing signals for the teletext display.

The F1 output (pin 4) is a 1MHz clock signal for the TROM and the TAC chips. The television display is synchronised by the internally generated sync signal  $\overline{\text{AHS}}$  (after hours sync) output from pin 5. The CRS (character rounding select) output signal is required for correct character rounding of the small characters within the character generator.

The internal data processing and sync circuits of the VIP are reset using the  $\overline{\text{CBB}}$  (colour burst blanking). The internal control character flip-flops of the TROM chip are reset at the

start of each display line by the LOSE (load output shift register enable) output from pin 13.

### TROM SAA 5050

The basic input to the TROM is character data from the teletext page memory. This is in the form of a 7-bit code which is fed to pins 4 to 10. The TROM converts the data into a dot matrix pattern. The character generator ROM (4.3K bits) generates 96 alphanumeric and 64 graphic characters.

The video output signals consist of a monochrome output (pin 21) and red, green and blue signals (pins 24, 23, 22) which contain both character and background colour information. A blanking output signal is provided to blank out the television video when a newflash or subtitle is displayed.

### CONSTRUCTION

The decoder board is supplied ready built, tested and aligned. Before the board is installed the three wire links shown in Fig. 2.6. should be soldered. Check these wires carefully. The wiring for the decoder is also shown in Fig. 2.6. but it is recommended that constructors leave the wiring of the system until all the boards have been assembled.

### DAUGHTER BOARD

The decoder board is interfaced to the video summer board via the interface circuit shown in Fig. 2.7. The RGB outputs from the TROM have pull-up resistors to 12V with catching diodes to prevent the outputs rising above 5V. These outputs are then diode ORed together and produce a current via R57 which is then added to the luminance channel at the delay line input on the summer board.

The daughter board is mounted on the p.c.b. shown in Fig. 2.8. with the component layout shown in Fig. 2.9.

**NEXT MONTH: VIDEO SUMMER AND P.S.U.**



# Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

## PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for.....(amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.  
Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53626. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

# Marshall's

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA  
Industrial Sales: 01-628 1009  
Mail Order: 01-624 8582  
Also retail shops: 325 Edgware Road, London W2.  
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.  
108A Stokes Croft, Bristol.

Build the P.E./Marshall's Teletext Project and convert your standard colour television receiver to receive Teletext and Oracle. We can supply either a complete kit of parts at £200 inclusive of VAT/postage & packing, alternatively kits of parts for the various sub assembly as follows:

1. Transmitter	£19.00	
2. Receiver	£13.00	
3. Decoder (supplied as a complete unit)	£87.00	All prices inclusive of VAT,
4. Summer Board	£27.00	postage & packing.
5. Tuner	£60.00	
6. Power Supply	£16.00	
7. Hardware and other parts	£ 9.00	

We accept American Express: Access: Barclay Card: Diners Card: also our own Marshall's Credit Charge.

Phone your order now to Margaret O'Donnell on 01-624 0805

*Get a great deal from*  
**Marshall's**

## — CLEF KITS —



### ELECTRONIC ROTOR

Two speed organ rotor simulation plus a three phase chorus generator on a single p.c.b. (8" x 5"). Kit includes all components/IC sockets throughout/mains operation and stereo headphone. Driver p.c.b. Easily integrates with existing organ.

COMPONENT KIT - £89

### KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

49 NOTE C-C	£23.80
73 NOTE F-F	£37.00
88 NOTE A-C	£48.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

### BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you - see lists.

### INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & Insurance.

### VISITS

Are welcome by appointment, otherwise Mail Order Only.

### EXPORT

Enquiries welcome - in Australia please contact JAYCAR (Sydney).

Back up TELEPHONE advice is available from the Designer to supplement the clear instructions included with the above Kits.

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

### JOANNA 72 & 88 PIANOS

Six and 7 1/2 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. Build this widely acclaimed professional instrument, for either domestic or Stage use, from our top quality Component Kits.

SIX OCTAVES - £207  
7 1/2 OCTAVES - £232

### P.E. STRING ENSEMBLE

The versatile Siring Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT - £169

### P.A.'s - SPEAKERS - CABINETS

Units can be supplied to add to the Piano Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

## CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. PE) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU.  
061-439 3297



4 1/2 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £5.10. 50p P. & P.

**MICROPHONES FOR TAPE RECORDERS**  
DM228R 200 ohm with 3.5 and 2.5mm Jack Plugs **£1.70**  
DM229R 50K with 3.5 and 2.5mm Jack Plugs **£2.25**  
DM18D 200 ohm with 5 and 3 pin Din Plugs **£1.99**  
Postage on above microphones 17p



### CARDIOID DYNAMIC MICROPHONE

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. **£8.02.** 50p P. & P.

2 1/2 in x 2 1/2 in meters 500µA, £4.14  
17p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £4.00.  
26p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.

### MULTI-METER

7N 360TR  
20,000 ohm/volt  
RESISTANCE  
RANGES  
X1, X10, X1K,  
X10K  
**£13.30**  
P. & P. 75p



**TRANSFORMERS Primary 240V**  
6-0-6V 100mA £0.75  
9-0-9V 75mA £0.75  
12-0-12V 50mA £0.85  
12-0-12V 100mA £1.05  
Post on above transformers 45p.  
9-0-9V 1A £1.80  
12-0-12V 1A £2.15  
15-0-15V 1A £2.51  
30-0-30V 1A £3.10  
6-3V 1 1/2A £1.80  
6-0-6V 1 1/2A £2.20  
Post on above transformers 75p.

PL258 Plug 33p; Socket 33p; PL259/SO239 Angled Connector 70p; 1 watt dummy lead 95p; 2m Rubber Neck Aerial with PL259 Plug **£3.30.**  
POST ON ABOVE ITEMS 14p.

All above prices include V.A.T. Send 40p for new 1980 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

**M. DZIUBAS**  
158 Bradshawgate · Bolton · Lancs. BL2 1BA

# PATENTS REVIEW...

Copies of Patents can be obtained from:  
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price £1.25 each.

## COBALT MAGNET ALTERNATIVES

There is now a serious world shortage of cobalt metal. This is largely due to the fact that cobalt is produced as a by-product of copper mining and most of the cobalt-copper ore mines are in Central Africa where the political situation is very unstable. The military and aerospace have first call on cobalt because it is an essential ingredient of high temperature alloys, as used for instance in jet engines. Loudspeaker manufacturers have for years used cobalt alloy magnets, for instance Alnico (aluminium-nickel-cobalt), because it offers high flux density. In turn this facilitates low leakage design by potting a compact magnet in a shield. In a colour TV set flux leakage sours the picture colours and hence potted cobalt magnets have been used almost exclusively in colour TV production. But the rising cost of cobalt has stimulated research into alternative approaches.

Two recent patents reflect this research and the worldwide trend away from cobalt as a magnetic material. UK patent application 2 031 247, filed under the New Laws by Hokuto Onkyo Co. Ltd. of Tokyo and dating from 3rd October 1978, contains a legally very broad claim to the basic concept of potting ferrite instead of cobalt. Figures 1 and 2 show known, but supposedly unsatisfactory, designs in which a ferrite magnet 10 is shielded by a pot or cup. Figure 3 shows the Onkyo design. Yoke 1 houses ferrite magnet 2. Pole 3 extends through a gap in the yoke 1 which also houses voice coil 5. The pole 3 has a cylindrical part 3a which merges into a tapered or frusto-conical part 3b. According to the rather vague wording of the patent this construction, along with the gap formed between pole cylinder 3a and yoke 1, decreases permeance between the pole and yoke. The greater the sectional area of the magnet the easier it is to keep the permeance low. The inventor claims that this decreased permeance reduces flux leakage, making the magnets suitable for use in a colour TV loudspeaker.

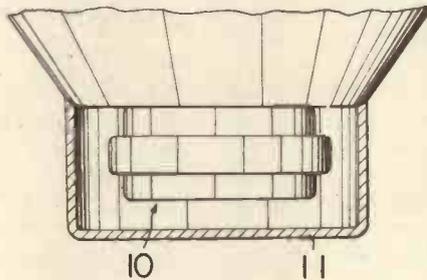


Fig. 1

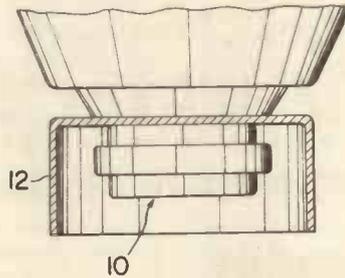


Fig. 2

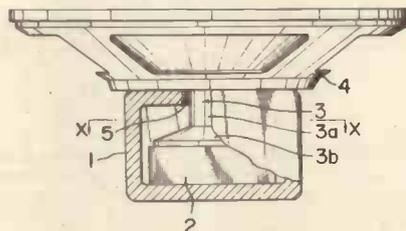


Fig. 3

A similar claim is made by a Danish inventor in UK patent application 2 034 154, (which was filed under the New Laws) and dates back to October 1978. Although the aim is the same the approach is different. Figure 4 shows a known Alnico design. Central rod 4 is a permanent Alnico magnet inside a cylindrical pot 6. The Alnico rod backs onto base disc 2 and pole disc 18. As the inventor points out, such a compact fully shielded design has been possible because the Alnico rod 4 can be small due to the high magnetic efficiency of cobalt-based materials. But ferrite is less efficient and this makes similarly compact designs of inadequate magnetic strength. The new design is shown in Figure 5. A large ring 4 of ferrite is housed in a pot 6 which is integrated with rear pole disc 2. Front pole piece 18 is slightly larger than the ring

magnet 4 and the whole combination is mounted in a cup 22. An alternative design, based on a solid disc magnet 4 is shown in Figure 6. The point of the invention is that the voice coil 12 is of much larger diameter than usual. This enables the large ferrite magnet to be used inside a pot rather than around the voice coil as an annular magnet. Again the claim is to a loudspeaker with insignificant flux leakage.

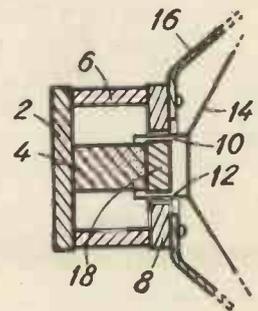


Fig. 4

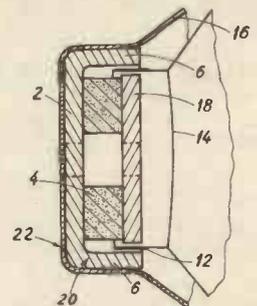


Fig. 5

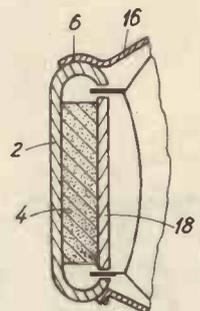


Fig. 6

LAST month the general principles of the GEB detector were explained, and construction of a machine began with a p.c.b. comprising power supply, auto-tuning and output stages. This month the remainder of the construction will be covered.

### SEARCH COILS

It's best to begin by winding the search coils, which will be required for testing the front-end circuit board at various stages. The Magnum uses a pinpoint coil, for reasons explained last month; these are slightly harder to make than widescans but the results obtainable are well worth the effort. The coil assembly is based on a 10in dia. 'Melaware' plate, made from a very rigid plastic, obtainable from most stores selling picnic tableware.

The inside of the plate is thoroughly roughened with glasspaper to enable glassfibre resin to stick to it, and two 'L' shaped plastic brackets are bolted to the top as in Fig. 6. These were cut from a thick, strong square-shaped clip intended for mounting square section plastic drain pipes to exterior walls, obtained from a local builders' merchants. They are bolted to the plate with 2BA countersunk screws with the heads inside, so nothing protrudes to foul the coils. A hole is drilled just behind one of the brackets to allow a 4-core screened cable to pass through.

The two coils are wound on pins pushed into a suitable board. The larger transmitting coil is made with just five pins positioned as shown in Fig. 7a, on which 60 turns of 32 s.w.g. enamelled copper wire is wound. It can be tied temporarily with a few twists of wire and removed from the pins—this is fiddly but not too difficult—bent to the shape of Fig. 7b, and bound tightly with a spiral of thin bare wire such as 5 amp fusewire, leaving a loop near the lead wires for use as a connection. Remove the temporary ties as the binding proceeds. A strip of aluminium cooking foil is then wrapped over the bare wire to form a Faraday shield, and this is held in place with another tight binding of the bare wire. Note that both wire bindings and the foil *must* have a gap—this is most important, as if the Faraday shield were allowed to form a complete 'turn' around the circumference of the coil it would render it useless.

### PICKUP COIL

The pickup coil is made in the same manner, consisting of 200 turns of 36 s.w.g. enamelled copper wire wound around 16 pins placed in a 4in diameter circle. Faraday shielding is fitted as on the transmitting coil, again with the all-important gap.

The transmitting coil can now be fixed in place on the former using a small quantity of fibreglass resin. A Holts' 'Fibreglass Repair Kit', obtainable from motoring accessory

shops, was used in making the prototype. The coil is best fixed in stages, using clothes pegs and weights to keep it in place as necessary. Apply the resin with a soft brush and have a jar of cellulose thinners handy to dunk the brush into the moment it starts to 'gel'. Push the 4-core screened lead through the hole in the plate, connect the coil leads to two of the cores, and the Faraday shield to the screens. It can be difficult to keep the lead in place whilst the resin sets; one way of doing this is to drill two tiny holes on each side of it and secure it flat against the plate with a couple of twists of thin wire. The pickup coil is not fitted at this stage.

### FRONT-END PCB


Start building the 'front-end' circuit board by fitting all the links. Then fit R1 to 3, C1, 2, and 26, D1, and TR1. Hook up the transmitting coil and apply power from the supply board. Continue using a resistor in series with the 18 volt battery in case any faults arise during tests, as described last month. The transmit oscillator should now be running, at between 15 and 16kHz. This can be checked by placing a radio tuned to a weak longwave station very close to the coil—faint whistles due to harmonics of the transmitted signal beating with station carries should be present. Faint is the word, however, as the Magnum's oscillator produces a very clean signal. This and other parts of the circuit can be more easily checked with a 'scope of course, but if you have one you'll probably have realised this anyway.

Next fit R4 to 13, C3 to 8 and IC1. Apply power and check that IC1's d.c. output voltage (at pin 6) is equal to 5.6V. Fit IC2, apply power and check IC2's d.c. output is 5.6V. Fit IC3, hook up VR1 across points I and J, VR2 across points G and H, and fit some lengths of wire so that point M may be shorted to points K or L, and short one of these. It doesn't matter which at this stage. Apply power and check that IC3's d.c. output (pin 6) is 5.6V. The output of IC2 should actually be switching from rail to rail at the oscillator's frequency but the average value of output should be 5.6V. A fault will usually result in its being fully driven to one of the supply rails, so this is a useful test. Check that settings of VR1 (M shorted to L) and VR2 (M to K) makes little or no difference to IC3's output voltage.


It might be of interest to explain that in the original design, the pots were connected directly as they are in this test, and a 2-way switch was fitted to M, K and L. This provides 'Ground Reject' (VR2) and 'Discriminate' (VR1). However, on the first beach outing it was found that the 'Beach Effect' could only be rejected with the 'Discriminate' control: a predictable effect since beaches are usually conductive. This prevented the discrimination from being used to reject foil, of which large amounts are to be found on most beaches. To overcome this problem the switching was

# PE MAGNUM METAL LOCATOR

PART 2... ANDY FLIND

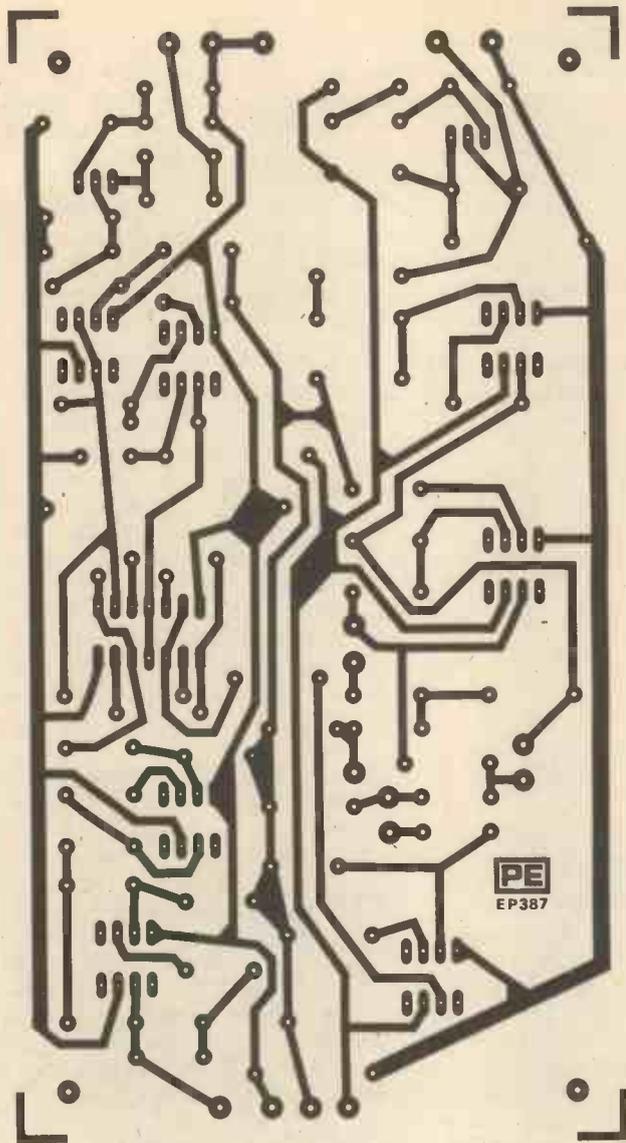

**FRONT-END BOARD**

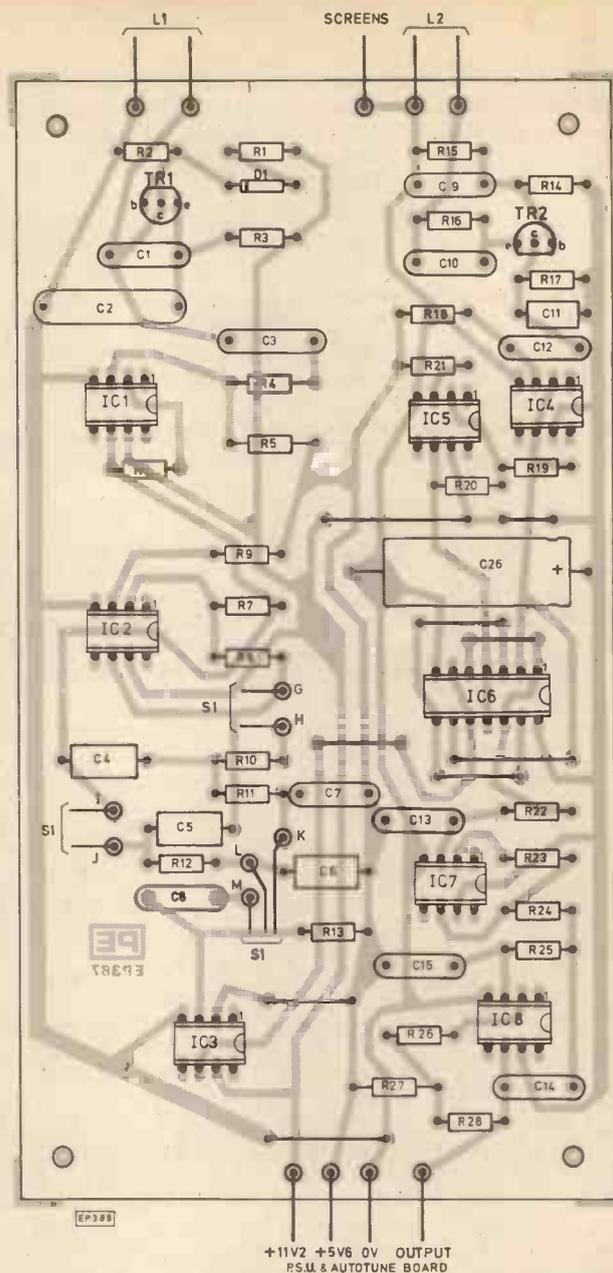

rearranged to provide a third 'Beach' position, in which VR2 is effectively switched into the discriminate circuit instead of the ground one. Thus VR2 can then be used to reject false signals from wet beaches in the same way as from ground, whilst VR1 can once again be used to check finds as intended.

Continue the construction by fitting R14 to 21, C9 to 12 and TR2. Connect the pickup coil temporarily, apply power and check that the emitter voltage of TR2 is approximately 0.6 volts above the negative rail. Fit IC4, apply power and check IC4's output voltage (pin 6) is 5.6V. Fit IC5, apply power and check that the output of IC5 is also V/2.

Fit R22 to 28 and C13 to 15. Fit IC6, observing the usual CMOS handling precautions for this chip. Place the pickup coil in approximate position over the transmitting coil, apply power and monitor the top end of R22 with a meter. The voltage present should be somewhere between 2 and 8 volts and should alter if VR1 or VR2 (whichever is selected by shorting M to K or L) is moved. Adjust the pickup coil position to obtain 5.6V at the top end of R22. Note that the Faraday shields of the coils shouldn't touch even though they are both connected to the lead screens: if they touch on

both sides they can form a 'shorted turn' in the middle of the assembly. Small pieces of card should be placed between them to prevent this from happening.

Fit IC7, check it's output is the same as that at the top of R22, i.e. 5.6V. Fit IC8. Check 5.6V is still present at IC7 pin 6—if not adjust coil position. Then check that 5.6V is also present at the output of IC8. This completes the construction of the front-end p.c.b.


### HARDWARE ASSEMBLY

The rest of the hardware can be constructed next. This is made mainly from  $\frac{3}{4}$ in diameter plastic plumbing pipe and fittings, assembled as shown in Fig. 8. It's simply glued and pushed together, making a very presentable handle and stem in a surprisingly short time. Wood dowelling is inserted at strategic points of the stem to prevent it from flattening when bolts are passed through it and tightened. The search coil is fixed by a length of studding passing through the two brackets and the end of the stem, with a wingnut at each end, so that it's tilt may be easily adjusted by the user. The control box base is secured to the shaft with two bolts, and the tuning button is fitted into the end of a bicycle handlebar

grip which is then pushed onto the plastic pipe, threading the wires through the pipe to emerge through a small hole close to the control box.


### CONTROL BOX ASSEMBLY

The electronics now have to be assembled into the control box. The top should be cut to accept meter, pots and switch in the layout shown in Fig. 9. Note that the top only fits the base one way round before starting this! A pattern of holes can be cut in one of the aluminium side panels to act as a speaker fret, the speaker being glued into place. A clip to hold the three PP3 batteries is fashioned from sheet

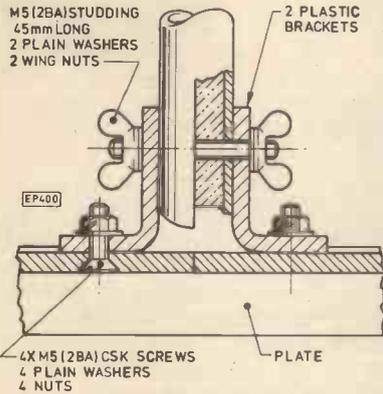

**Fig. 6 (left). Search plate mounting assembly**

**Fig. 7 (right). (a) Winding the transmitting coil; (b) Transmitting coil bent to shape; (c) Pick-up coil; (d) Positioning the coils**

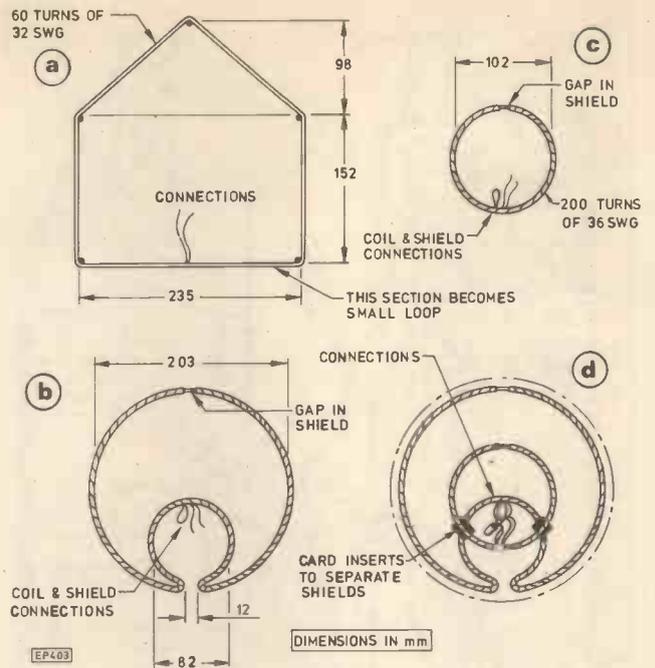



aluminium and wood and bolted to the same panel, and to the ends of the bolts a piece of Veroboard is attached to act as a connecting block for the leads from the batteries and tuning button. Four 4BA bolts passing up through the base of the box act as stand-off pillars on which the two p.c. boards are mounted one above the other, the front-end board being uppermost.

The best way to make all the connections to the boards is with ribbon cable, soldering this to them before fitting them into the case and noting the point to which each coloured wire goes. A headphone socket is optional: if required it may be connected as shown in Fig. 5. 'R' will have to be selected for the phones to be used, in the prototype a value of 100 ohms was found to be suitable. A 5-pin DIN plug and socket was used for the coil lead, whilst not strictly necessary this does allow for experimenting with different coils at a later date.

The box specified is supplied with feet which were discarded, the securing bolts being shortened a little to compensate.

### SETTING UP THE SEARCH COILS

When all the components have been wired up the final tricky part has been reached; the setting up of the search coils. This must be done with metal parts such as the securing bolt and wing nuts in place, though there is no need to have the coil assembled to the stem. There should be no large metal objects close to the coil during this stage. This might also be a good time to mention that the machine can be affected by line timebase radiation from 625-line TV sets, so if you get a 'mushy' sound or a pulsed audio effect from it, check this first. Coil adjustment is actually not as critical as it is for a normal IB machine, but there is a best point and for a GEB machine it is the position where absolute minimum residual amplitude output (and maximum phase shift effect) is obtained from the pickup coil. (Conventional IBs usually work best with a slight 'offset' from absolute null.) This cannot be monitored with the phase sensitive detector in the machine itself, so the circuit of Fig. 10. should be lashed up and connected to IC4 output (top end of R19) and used with

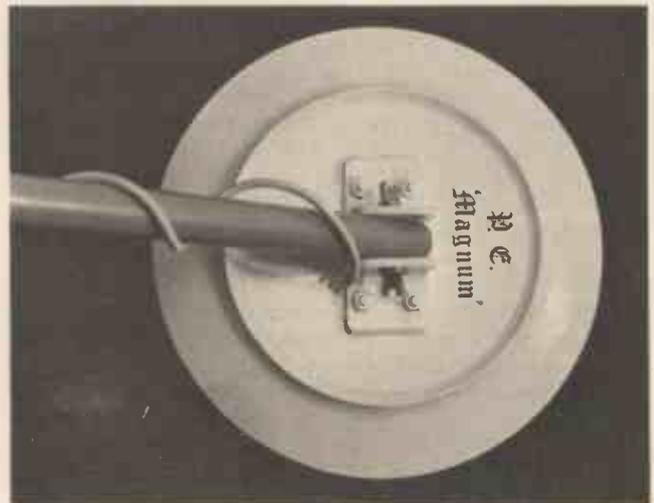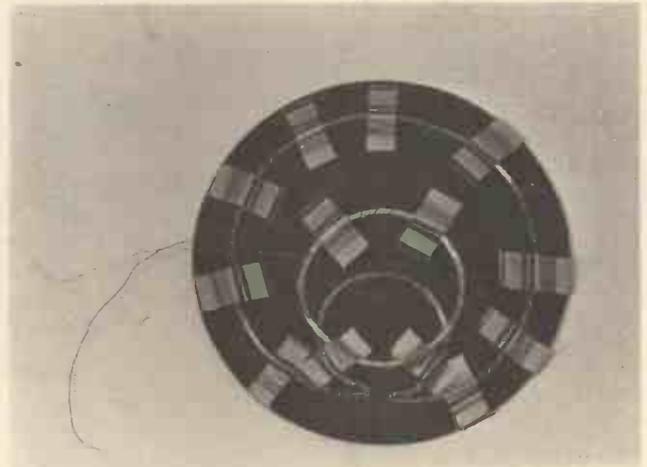

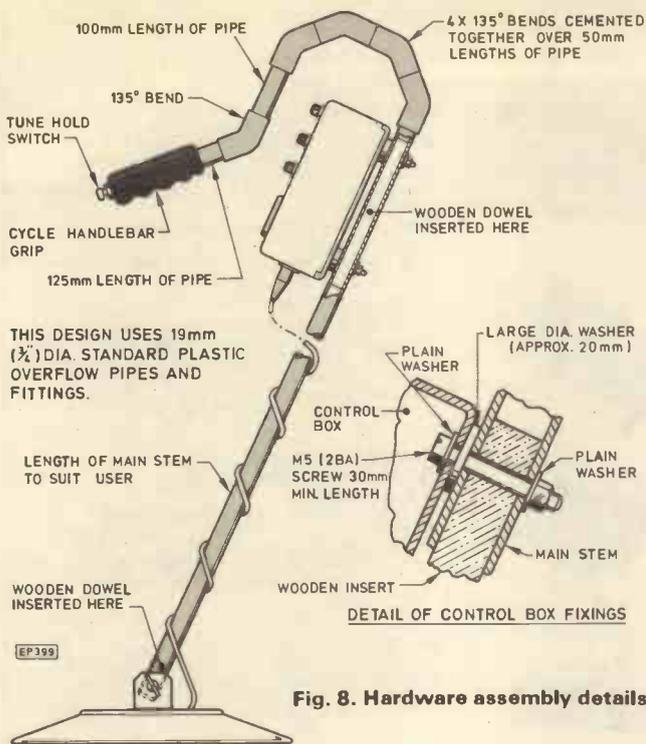


Fig. 8. Hardware assembly details

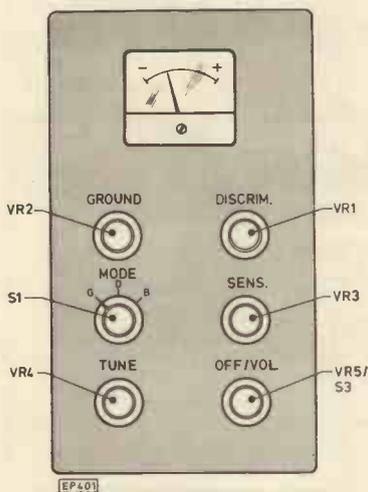


Fig. 9 (left). Control fascia; (above) Detail of battery mounting

the 1 volt range of a testmeter to facilitate setting up minimum amplitude.

Set VR1, VR2 and VR3 to mid-point. Switch to 'Discriminate' and switch on. The meter monitoring amplitude will probably indicate full scale. Carefully adjust the pickup coil position until the reading falls—this may take some patience as it's easy to push the coil right past the null position without noticing it if you're too hasty. Remember to keep those Faraday shields apart! Once you have the coils somewhere near the null, try presenting metal objects to the coil whilst watching the centre-zero meter. A non-ferrous object such as a copper coin should cause it to rise, whilst a ferrous object such as a nail should cause a fall. If the opposite happens the phase of the pickup coil must be reversed, either by turning it over or by reversing its lead connections.

Once correct coil phase has been established setting up

consists of adjusting the pickup coil position for absolute minimum output from the amplitude monitoring test circuit, use resin to stick it down in stages, rechecking the adjustment at each stage. Final fine trimming can be done with only a small section of the pickup coil still moveable.

After the positioning of the coils has been completed the coils can be given a coat of resin, followed by a layer of chopped strand glassfibre mat and more resin, which produces a search head assembly that is neat, tough and totally waterproof. One word of caution; don't use more resin than you have to or the finished head may be heavier than necessary.

### FINAL ASSEMBLY AND TESTS

All the test components can now be removed and the machine finally assembled and tested. If you've never used a GEB machine before, you're in for some pleasant surprises.

On switching on, the meter should self-zero within a couple of seconds and the tuning control should then be set just below the threshold of the audio tone. The sensitivity of this machine is quite incredible; on most inland sites you'll probably need to keep the sensitivity control set to around mid-point. With the switch in 'Ground' position, a point can be found on the 'Ground' control where moving the head to and from the ground has no effect whatever—on one side of this point there will be positive ground effect, on the other negative, so it's not difficult to find. Adjusting this control for wet beaches is the same, except that the switch should be set to 'Beach'.

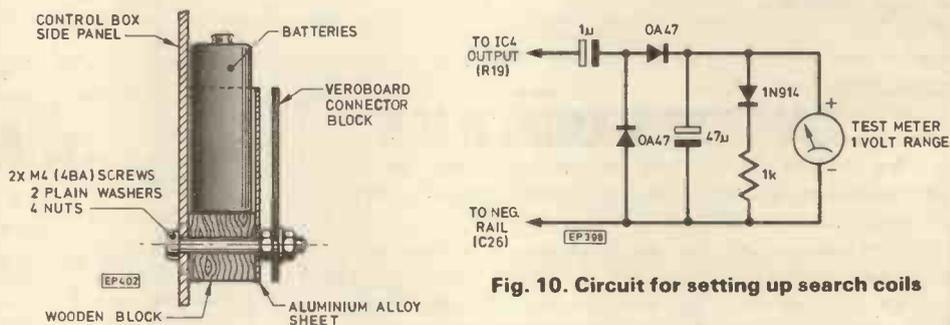


Fig. 10. Circuit for setting up search coils

Once an object has been located, the machine should be switched to 'Discriminate' and the nature of the object determined. A certain amount of ground effect will be apparent in this mode, depending upon the actual terrain being searched. Ferrous objects produce a negative response at all settings of the discriminate control, but as this control is advanced so the machine will begin to reject small pieces of silver paper, then larger pieces, thick foil, and finally pull rings. It should be noted that in the pull-ring reject setting, however, it will also reject silver coins up to about 10p size. All discriminators suffer from this problem; but the ability to reject scrap iron and foil without difficulty is an absolute boon. Some practice with assorted objects—coins, nails and scraps of foil etc., is recommended before setting forth with this machine.

The tuning 'Hold' button will be found necessary for discriminating and for pinpointing the exact position of finds.

So, Good Hunting! Don't forget you need a licence for your detector; application forms for this can be obtained from: The Home Office, Radio Regulatory Dept., Waterloo Bridge House, London SE1.

# AITKEN BROS

35, High Bridge, Newcastle upon Tyne  
Tel: 0632 26729



EXP300



PB6 Kit

**EXP300**  
550 contacts with two 50-point BUS bars. Size 152x53mm. £8-95.  
**PROTO-BOARD 6 KIT**  
630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10-98.

## CSC LOGIC PROBES LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. £20-95.

LP-1 Memory Probe £35-65  
LP-3 High Speed Memory Probe £56-76  
CSC catalogue available. Please send S.A.E.

## CALSCOPE SUPER 6 £186-30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1μs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

## CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

## SINCLAIR LOW POWER PORTABLE OSCILLOSCOPE SC110 £159-85

The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided, including bright line, auto with TV line and frame positions. Please send for full spec. and illustrated brochure.

**TMK 500 MULTIMETER** 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts. 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50μa, 5mA, 50mA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included. PRICE £25-95.

## CSC EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.

**SINCLAIR DM350** £83-95  
**SINCLAIR DM450** £114-95

Size 255 x 148 x 40mm.  
DM350 3 1/2 digit display DM450 4 1/2 digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (100μV on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

## Sinclair PFM200 frequency meter

Size 157 x 76 x 32mm.  
Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. £57-95.

## SINCLAIR PDM35 DIGITAL POCKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200mA. Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £39-95 AC Adaptor £4-25 de luxe padded carrying case £1-95 MN 1604 Battery £1-28. Size 157 x 76 x 32mm.

## SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER.

DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1mV to 750V AC & DC current 1μa to 1000mA Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £60-98. Carrying case £8-95. AC adaptor/charger. £4-25. Rechargeable Battery Pack. £8-95. Size 255 x 148 x 40mm.

## PANEL METERS

DIMS 60MM x 45MM. 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, "S", "VU" 50-0-50μa, 100-0-100μa, 500-0-500μa. PRICE £5-95.

## DESOLDERING TOOL SUCTION PUMP. £6-45

Education Establishment Orders Accepted.  
PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER  
ALL PRICES INCLUDE POSTAGE AND VAT.



BARCLAYCARD

VISA

We welcome Access

## CONGRESS AMPLIFIER

We supply all the designer approved parts for this exceptional kit, including high quality printed circuit boards and transformer.

Complete kit, excluding metalwork with 20% discount on parts. £73.74

All parts to assemble pre-amp i.e. R's, C's, PCB's, semicons, controls etc, but excluding transformer with 10% discount on parts. £41.79

All parts to build main amp board £20.48

Mains transformer £12.82

Smoothing caps & clips £8.86

Front Panel £3.20

Chassis (unpainted, pre-punched) £13.40

Front panel and chassis not subject to reduction but if ordered together with complete kit available at special price of £11.50

*This offer also applies to previous purchasers of complete kits.*

### MAIL ORDER ONLY.

Prices include VAT and p&p

Please send A5 S.A.E. for full price details.

Terms: Cash with order. Cheques etc. should be made payable to:

### CONGRESS ELECTRONICS PROJECT

Allow 14-21 days after sending order for delivery. Send order to:

Photostat of article available at £1.20.

WICCA SYSTEMS LTD,  
24 HILLCREST PARADE, COULSDON, SURREY.  
Tel. 01-668 5256

## J. BIRKETT

(Partners: J. H. Birkett, J. L. Birkett)

Radio Component Suppliers

25 The Strait, Lincoln. LN2 1JF

**MAINS TRANSFORMERS** 240 Volt Input, Output 43 Volt 50 mA, 11 Volt 2.5 Amp, 22-0-22 Volt 150 mA, 16 Volt 120 mA, 15 Volt 1.5 Amp, 20V 275 mA at £3.90 (P&P £1.20).

**MULLARD OR TCC ELECTROLYTIC CAPACITORS** 2240uf 40v.w. £ 40p, 4500uf 25v.w., £ 40p, 6400uf 16v.w., £ 20p, 6400uf 25v.w., £ 35p, 16000uf 10v.w., £ 20p, 47,000uf 10v.w., £ 50p.

**6 TO 12 VOLT RELAY** Single Pole C.O. 5 Amp Contacts £ 60p.

**CAR TYPE LONG DOLLY ON-OFF SWITCHES** £ 35p.

**HOUSE CODED TTL I.C.'s** 7400, 7410, 74100, 7453, 7430 All at 6 for 50p.

**ELECTRET MICROPHONE INSERTS** with FET Pre-Amp £ 1.85.

**50. BC 107-8-9 TRANSISTORS** untested assorted £ 60p.

**SPECIAL 5 NPN DARLINGTON PAIRS** in 14 PIN DIL Package MFE 5000, 10 Volt 500 mA £ 50p, 3 for £1.

**10 WATT ZENERS** Stud Mounting. 4.7, 6.8, 7.5, 8.2, 12, 15, 18, 20, 24, 27, 30, 33, 36, 39, 43, 47, 51, 62, 68, 75, 82, 91, 100, 120, 130, 150, 180, 200 Volt All Good Devices £ 50p each.

**5 WATT PLASTIC WIRE ENDED** 3.6, 4.3, 5.6, 6, 6.2, 7.5, 8.2, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 22, 24, 27, 28, 30, 33, 36, 39, 40, 47, 51, 56, 60, 62, 68, 87 Volt at 30p each.

**QUAD COMPARATORS TYPE LM 339** with date £ 50p.

**PAPER CAPACITORS** 10uf 370 Volt A.C.W. size 5 1/2 x 2 1/4 £ 1.50.

**CLOSE TOLERANCE CAPACITORS** 1288pf, 1670pf, 5979pf, 19669pf All 1% 125v.w., at 5p., 01uf 2%, 11uf 2% at 8p, 100,000pf (1uf) 1% £ 12p.

**CRYSTALS** Glass Wire Ended. 28 KHz, 28.5 KHz Both £ 50p.

**WIRE WOUND POTENTIOMETERS** 2 Watt 2K, 5K, 10K, 4 Watt 100K All 30p each.

**MINIATURE TRANSISTOR TRANSFORMERS** Input Types. Impedance Ratio. 100K to 1K £ 35p, Ratio 150K to 1K £ 35p, Ratio 20K to 1K £ 35p, Input Type 10K to 2K £ 35p, Output Types 250mW 1.2K to 8 ohm £ 35p, 250mW 500 ohm to 8 ohm £ 35p, 500mW 400 ohm to 8 ohm £ 35p.

**THYRISTORS (S.C.R.'s)** 10 Amp Type 100 PIV £ 28p, 400 PIV £ 55p, 800 PIV £ 65p.

**LM 7542 DUAL CORE MEMORY SENSE AMPLIFIER** £ 50p.

**SUB-MINIATURE TOGGLE SWITCHES** SPCO £ 50p each.

**MINIATURE 1.75" Dia. 8 OHM LOUDSPEAKERS** £ 85p.

**25 ASSORTED PRE-SET POTENTIOMETERS** For 60p.

**POWER NPN TRANSISTORS** 8D 207 £ 55p, 8D 167 £ 25p, 8D 175 £ 25p.

**MAINS TRANSFORMERS** 240 Volt Input. Type 1. 24 Volt Tapped at 14 Volt 1 Amp £ 1.30 (P&P 25p). Type 2. 30-0-30 Volt 500 mA £ 1.30 (P&P 25p). Type 6. 16 Volt 2 Amp £ 1.60 (P&P 25p). Type 10. 12 Volt 1 Amp £ 1.60 (P&P 25p).

**200 ASSORTED 1/4, 1/2 WATT RESISTORS** for 75p.

**2N 706 TRANSISTORS** unmarked good at 12 for 50p.


**SIGNETICS HIGH SPEED TTL PRESETABLE DECADE COUNTER 8290** £ 20p each.

Please add 20p for post and packing on U.K. orders under £2.

Overseas postage charged at cost.

# SPECIAL OFFER!

## AUTORANGING DMM'S

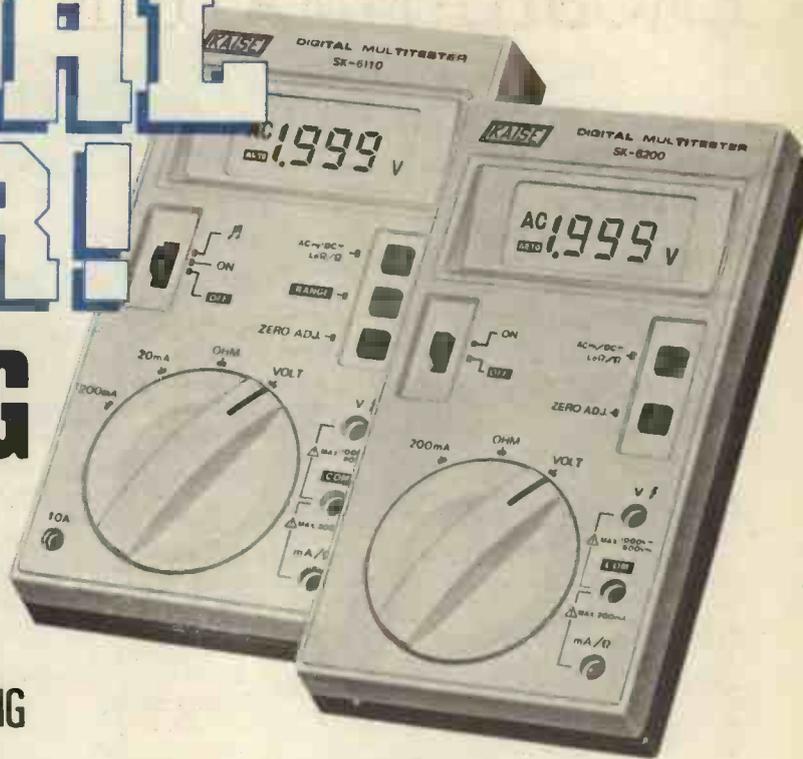

PRICES INCLUDE V.A.T. POSTAGE & PACKING

SK 6110 **£59.95**  
 SK 6200 **£34.95**

PE is pleased to have been able to arrange this very special offer for readers on KAISE digital multimeters. The meters employ dual slope integration,  $3\frac{1}{2}$  digits, 10mm high l.c.d. with unit and sign indications, autoranging on volt and ohm ranges and autopolarity. Battery life is approximately 200 hours and battery low indication, overrange indication, and push button zero adjustment on the lowest range are provided. Both meters measure approximately 155 x 85 x 28mm and weigh approximately 250g.

Unfortunately we do not have the space to give a full specification, which would take up the whole page. However, a condensed version for both instruments is given below:

**DC Voltage** 200mV, 2V, 20V, 200V, 1000V, accuracy  $\pm 0.5\%$  (6110) and  $\pm 0.8\%$  (6200), impedance approx: 10M $\Omega$  on all ranges except 200mV which is 100M $\Omega$ .

**AC Voltage** (frequency 40Hz to 500Hz) 2V, 20V, 200V, 600V, accuracy  $\pm 1\%$ , impedance approx 10M $\Omega$ .

**DC Current** 20mA (6110 only), 200mA, 10A (6110 only) accuracy 6110  $\pm 1\%$ , 6200  $\pm 1.2\%$ , impedance 20mA—10 $\Omega$ , 200mA—1 $\Omega$ , 10A—0.01 $\Omega$ .

**AC Current**, as DC Current but  $\pm 1.3\%$  (6110),  $\pm 1.4\%$  (6200).

**Resistance** 200 $\Omega$ , 2k $\Omega$ , 20k $\Omega$ , 200k $\Omega$ , 2M $\Omega$ , accuracy  $\pm 0.5\%$  and  $\pm 1.8\%$  (2M $\Omega$  range) for 6110,  $\pm 0.8\%$  and  $\pm 2\%$  (2M $\Omega$  range) for 6200.

**Low Power Resistance**, as resistance but without 200 $\Omega$  range, accuracy  $\pm 1\%$  and  $\pm 2\%$  (2M $\Omega$  range) for 6110,  $\pm 1.2\%$  and  $\pm 2\%$  (2M $\Omega$  range) for 6200. Maximum open circuit voltage on this range is 0.4V.

The 6110 also has a buzzer for continuity test and additional audible warning of overrange.

To: Maclin-Zand Electronics Ltd. (PE Offer), 38 Mount Pleasant, London WC1X 0AP. Tel. 01-837 1165.

### Mail order only

Please send me

<input type="checkbox"/>	SK 6110
<input type="checkbox"/>	SK 6200

Multimeter/s at £59.95 (6110) or £34.95 (6200) each

I enclose PO/ Cheque No. .... Value .....

Name .....

Address .....

.....

.....

Please allow 28 days for delivery

**OFFER CLOSSES FRIDAY, OCTOBER 24, 1980**

Name .....

Address .....

.....

.....

To: Maclin-Zand Electronics Ltd. (PE Offer), 38 Mount Pleasant, London WC1X 0AP. Tel. 01-837 1165.

Please complete both parts of the coupon in BLOCK CAPITALS

# Class A Amplifier

K. Garwell

THIS type of amplifier which was designed whilst looking for a suitable unit to use in a theatre has been developed with two particular requirements in mind: reliability and short circuit protection of the output.

## DESIGN CONSIDERATIONS

Class A was attractive for two reasons, which can be illustrated by reference to the conventional R.C. coupled stage shown in Fig. 1. The circuit is asymmetrical, there being only one transistor, which gives a low component count. Also the quiescent current through the stage is defined by the resistors and hence is not temperature sensitive. There is a bonus also from this type of circuit, as the output transistor is never turned off, there is no crossover distortion.

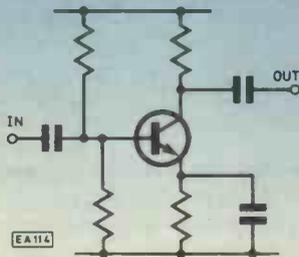


Fig. 1. Conventional R.C. coupled stage

There is, of course, one serious drawback with Class A, it's poor electrical efficiency. Sometimes referred to as conversion efficiency; the ratio between actual power into the load and power supplied from the d.c. supply. The best that can be achieved is about 17 per cent and that ignores the emitter resistor. Which would mean that a 50 watt amplifier consumed at least 294 watts and getting rid of 244 watts of heat (294-50) can be something of a problem.

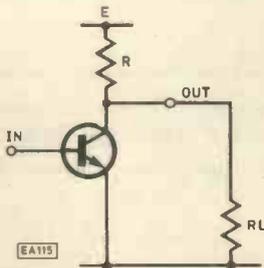


Fig. 2. Simple Class A circuit

If we look at a simplified Class A circuit without the complications of biasing and coupling as in Fig. 2 and consider the two limiting conditions. Firstly with TR1 just about cut off, i.e. the maximum positive excursion of the output. The current through the load  $R_L$  is  $E/R + R_L$ , but this current also flows through the collector resistor  $R$ ; hence if  $W$  watts appears in the load, then  $WR/R_L$  watts appear in this resistor,

which is wasted power. If  $R$  could be made very small this wasted power would also be small.

The other limiting condition appears when TR1 is just about saturated (ignoring the small collector-emitter voltage), the current through  $R_L$  is zero and hence the power is zero whilst the current through the collector resistor  $R$  is  $E/R$  and the power  $E^2/R$ , all the power is wasted. If  $R$  could be made large then this wasted power would be reduced.

This shows the two conditions have conflicting requirements. When the output is positive going  $R$  must be small, when the output is negative going  $R$  must be large.

An emitter follower, Fig. 3, has the property of impedance


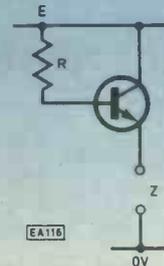


Fig. 3. Emitter follower circuit

reduction. The impedance  $Z$  measured between emitter and OV (ground or signal earth) will be considerably less than the value of the base resistor  $R$ . Very roughly, it will be reduced in proportion to the current gain of the transistor, e.g. if the current gain is  $A$  then

$$Z = \frac{R}{A} \text{ approx.}$$

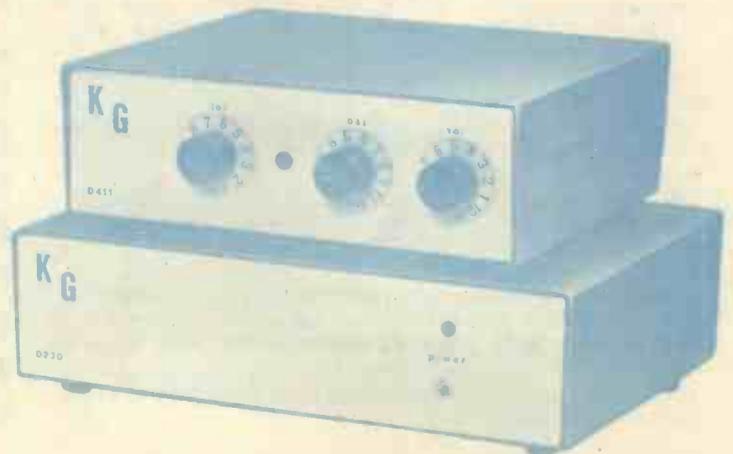Returning to Fig. 2. If an arrangement having the characteristics of an emitter follower could be associated with  $R$  the collector resistor; and in addition, if this arrangement could be switched on whilst the output signal was positive going (made low resistance) and inhibited (high resistance) whilst the signal was negative going, then this would solve the conflicting requirements.



The requirement is to reduce the value of R whilst the output is positive going, i.e. supplying current (conventional flow) not during positive half cycles, the two are quite different. The same point must be made about the converse situation. The value of R must be increased whilst the output is negative going, i.e. demanding current, not the same thing as during negative half cycles.

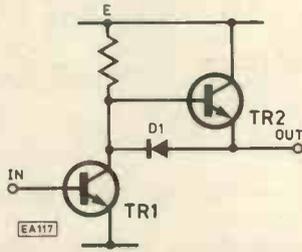


Fig. 4. Basic Class A stage with an emitter follower

Fig. 4 shows a basic combination of a Class A stage (Fig. 2) and emitter follower (Fig. 3). This combination is called Composite Collector Load Class A. The emitter follower being switched in or out of use by the diode D1.

Considering first the positive going situation where current is being supplied to the output. The collector potential of TR1 will rise in an attempt to supply current to the output or load. This situation will reverse bias diode D1 and forward bias the base emitter junction of TR2 which then behaves as an emitter follower supplying current to the load. The current through R will be only a small proportion of the load current, or looking at it another way the combined ef-

fect will be that of a collector resistor considerably smaller than R actually is.

Now consider the opposite situation when TR1 collector is negative going attempting to draw current from the output. The diode D1 will be forward biased and the base emitter junction of TR2 reverse biased. TR2 is thus out of action and the effective collector resistance is R only. TR1 thus absorbs the current from the load plus a small current via the resistor R.

### CIRCUIT DESCRIPTION

The basic circuit shown in Fig. 4 illustrates the principle involved. To convert this to a practical design requires the addition of components to provide d.c. bias, the necessary a.c. drive to the base of TR1 and negative feedback to improve the performance. As shown in Fig. 5.

Resistors R1 and R2 establish the overall gain between input and output, which is equal to  $R2/R1$ . R2 also establishes the quiescent output voltage as equal to 0V as the other input of the op-amp IC1 is referenced to 0V.

Resistors R3 and R5 provide local negative feedback over the discrete components TR1, TR2 and TR3. This provides for a much more stable amplifier and greatly improves the distortion figures.

Resistor R4 serves two purposes. It reduces the power dissipated in TR3 enabling a TO5 assembly to be used and it also prevents any avalanche condition in the event of failure. For example, if TR2 failed in the short circuit mode the output would be driven fully positive. The negative feedback via R2 would cause TR3 to be turned hard on in an attempt to restore the output voltage and, of course, TR3 would break down. However, the presence of R4 will limit the current through TR3 to a safe value under these fault conditions.

The split collector resistor R6 and R7, together with C4, provides for bootstrapping to ensure that the base of TR2 never runs out of current, even as the output approaches the positive rail voltage. As the output voltage becomes more positive C4 causes the junction of R6 and R7 to also become more positive. This maintains a substantially constant current through R7 and hence the current handling capability of the output is reasonably constant also.

Capacitor C1 provides phase correction to the feedback loop. This may or may not be necessary and depends on component types used. The action of the switching diode D1 generates small transients and these are suppressed by C2 and C3.

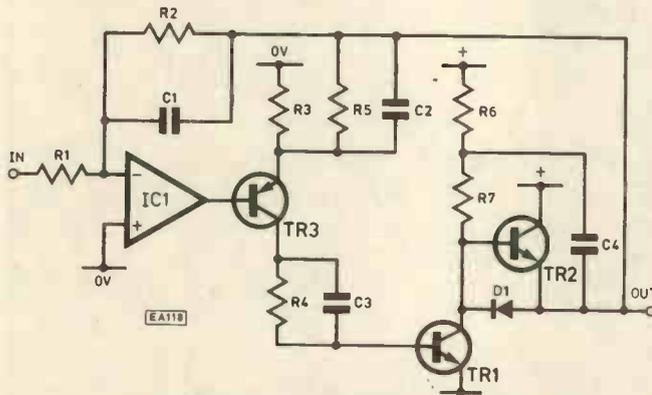


Fig. 5. Improved Class A circuit

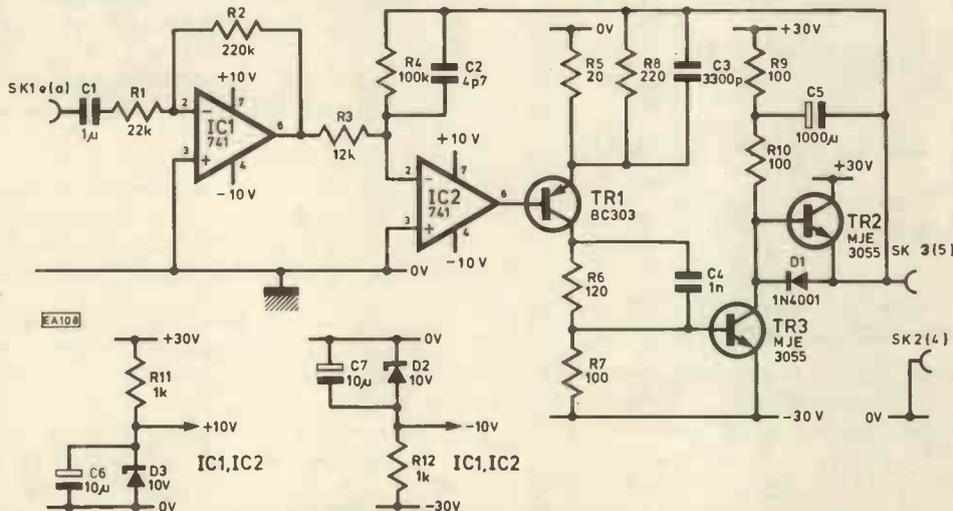


Fig. 6. Circuit diagram of one channel of the Class A amplifier. (Connections for R.H. channel shown in brackets.)

Having discussed the theory behind the Class A design we can now look at a practical implementation of the idea.

### PRACTICAL AMPLIFIER

The construction of a practical amplifier, as opposed to the discussion of a theoretical one, inevitably involves compromise, and the most important compromise is between power output and readily available components.

The complete circuit diagram of the amplifier is shown in Fig. 6 (the left channel). This design is quite capable of delivering 30W into an 8 ohm load. Full drive (30 watts) is obtained with 350mV peak input. However, it was felt that it would be desirable to have a higher transient capability, hence the power supply design shown in Fig. 7 provides for  $\pm 30$  volts as the quiescent supply voltages giving a transient capability approaching 60 watts. (The amplifier couldn't sustain this level for long as such a load rapidly reduces the supply voltages.)


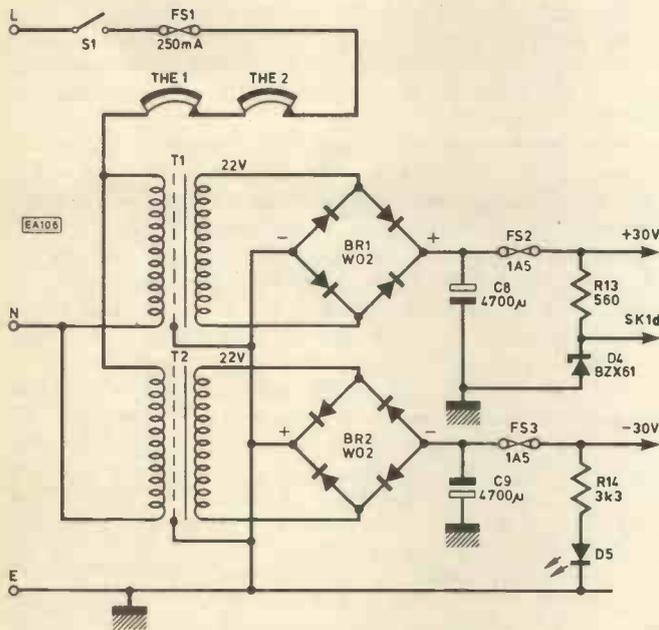


Fig. 7. Power supply circuit

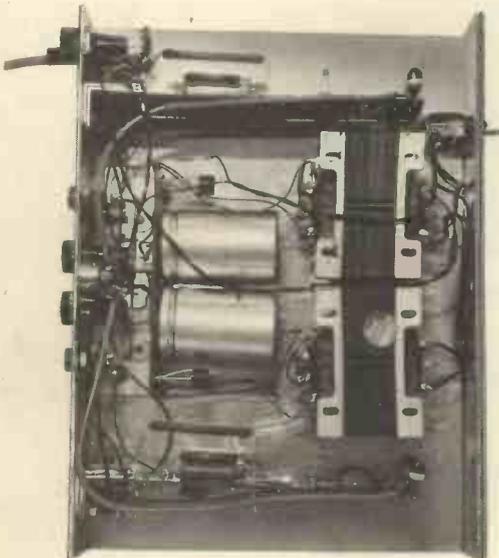

Internal view of amplifier

## COMPONENTS . . .

### Resistors

*R1	22k
*R2	220k
*R3	12k
*R4	100k
*R5	20
*R6	120 1W
*R7	100
*R8	220 1W
*R9	100 7W
*R10	100 3W
*R11, R12	1k $\frac{1}{2}$ W (2 off)
R13	560
R14	3k3

All resistors  $\frac{1}{4}$  or  $\frac{1}{2}$ W except where otherwise stated

### Capacitors

*C1	1µ polyester
*C2	4p7
*C3	3300p
*C4	1n
*C5	1000µ 25V
*C6, C7	10µ 25V (2 off)
C8, C9	4700µ 40V (2 off)

### Semiconductors

*D1	1N4001
*D2, D3	10V Zener BZY88 (2 off)
D4	20V Zener BZX61
D5	LD57A
TR1	BC303
TR2, TR3	MJE 3055 (2 off)
BR1, BR2	Bridge rectifier WO2 (2 off)
IC1, IC2	741 (2 off)

### Miscellaneous

- THE1, THE2 thermal safety switch 70°C (RS 339-308) (2 off)
- Fuse holders (3 off)
- 250mA fuse (slow blow)
- 1.5A fuse (2 off) (quick blow)
- \*P.c.b.
- Banana sockets (4 off)
- 6-way DIN socket
- Mains toggle switch
- Suitable case
- Veroboard
- Transformer Douglas MT 79 FT (2 off)

\* Two required for stereo design

### CONSTRUCTION

The p.c.b. design for one channel of the amplifier is shown in Fig. 8 with the component layout in Fig. 9. All the components except TR2 and TR3 can be mounted on the board. The two resistors R9 and R10 should be set at least 10mm from the p.c.b.

The mounting details of the p.c.b.s, thermal switches and output transistors are shown in Fig. 10. The transistors TR2 and TR3 should be mounted onto the heatsink using mica washers.

The Veroboard layout for the power supply unit is shown in Fig. 11. The prototype was fitted into a case 250 x 180 x 60mm. The wiring diagram for the rear panel is shown in Fig. 12. The mains switch and the l.e.d. should be mounted onto the front panel.

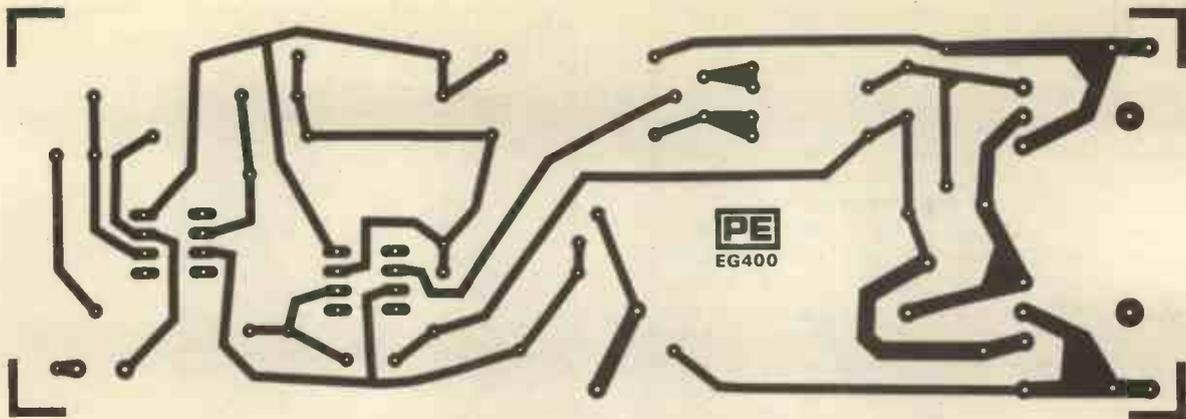


Fig. 8. P.c.b. design for one channel of the amplifier.

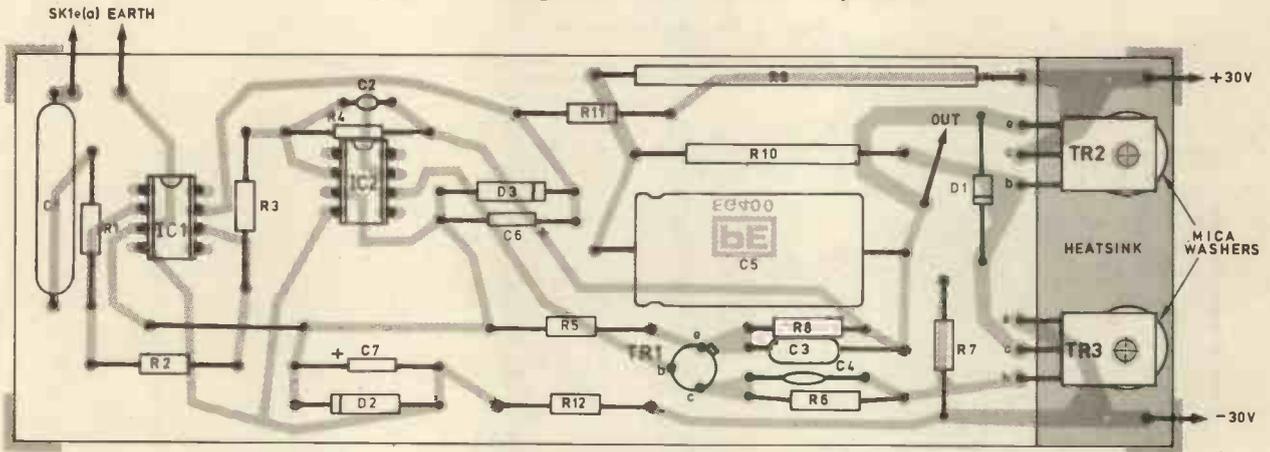


Fig. 9. Component layout

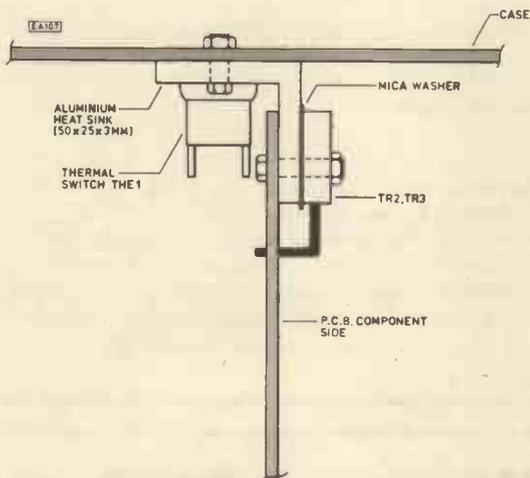


Fig. 10. Mounting details for the heatsink


### TEST PROCEDURE

- With the mains input fuse FS1 fitted and FS2 and FS3 removed, connect a 6k ohm 10 watt resistor in series with mains live and apply power. The power rails should run up to approximately their correct voltage ( $\pm 30V$ ). Switch off and discharge the rails using a convenient resistor.
- Fit FS2 and FS3 and with no speakers connected apply power again via the 6k resistor. A small voltage should appear at each rail, about half a volt or so.
- If the two previous checks are good. Switch off, remove the 6k resistor and apply full power. Check across each pair of speaker sockets in turn that there is no more than a few millivolts of d.c. present.

- If check c fails, check first the voltages supplying IC1 and IC2.  $\pm 10V$ .
- Check there is no a.c. voltage at the speaker terminals.
- With speakers (8 ohm) connected but no input connection there should be a noticeable, but not loud, 100Hz buzz.
- Check that this buzz disappears completely when the input pins are connected to 0V. Pins a and e connected to pin f on socket 1. Under these conditions there should be no sound from the speakers.
- Check that there is +20V at pin d of socket 1.

### OPERATION

The amplifier is now ready to accept a nominal input of 350mV peak output from a preamplifier. For inputs other than this the values of R1 and R2 should be changed, the

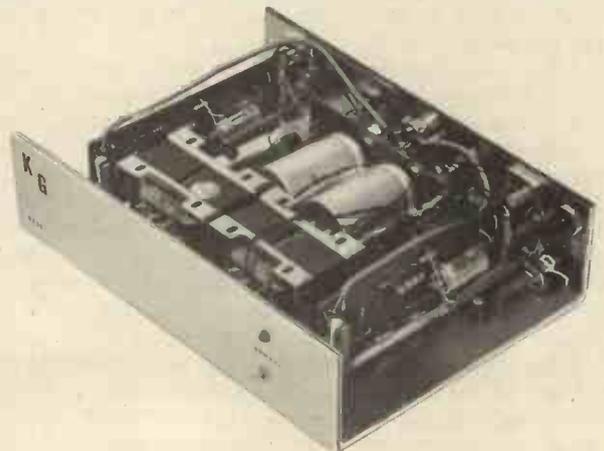

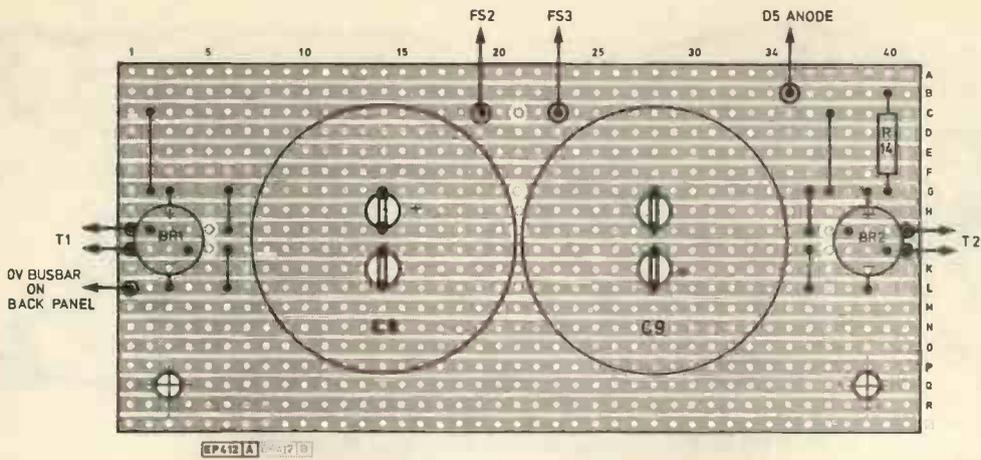


Fig. 11. Veroboard layout of the p.s.u

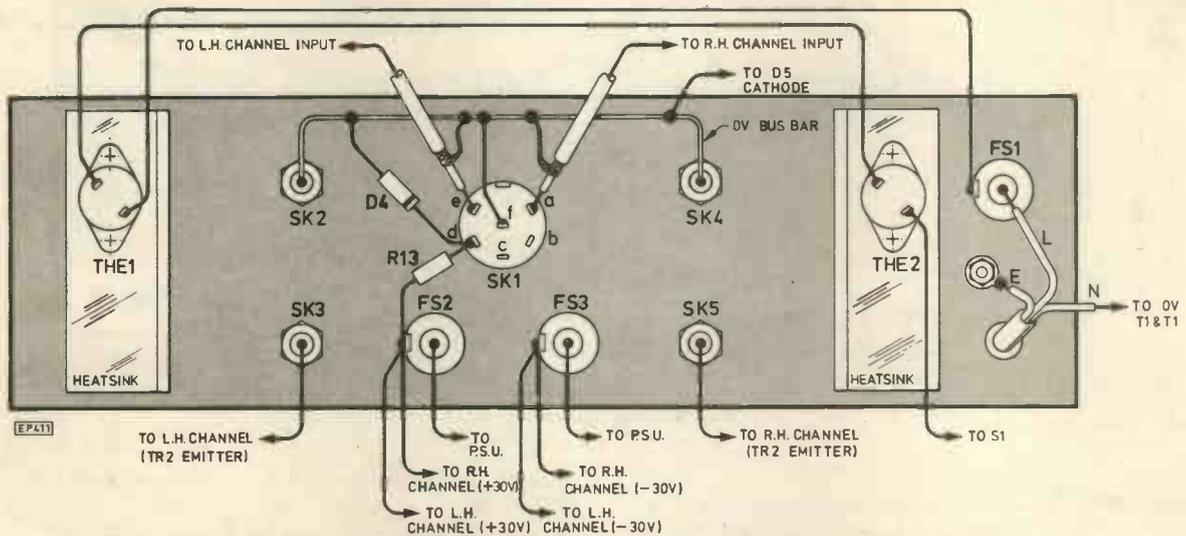


Fig. 12. Wiring diagram for the rear panel.

relationship being a direct one, i.e. for a peak input of 175mV the gain must be doubled which will be achieved by halving the value of R1. For a peak input of 700mV the gain must be halved, achieved by halving the value of R2. The limitations are that R2 should not be made larger than 220k. On the other hand, the 3dB point of C1, R1 is 18Hz, halving R1 without altering C1 will raise this to 36Hz by which point the loss of bass will be noticeable. Halving R1 and doubling C2 will maintain the status quo but values of C2 (which is not polarised) much more than 2 $\mu$ F start to give an uncomfortably large component.

For those who would like to experiment with the circuit rather than build a Hi-Fi system there are a number of comments which may be helpful. If higher continuous outputs are required the power supply must be uprated and the output stage fitted with cooling fins.

The circuit in Fig. 6 is deliberately bandwidth limited. It will be seen that the circuit is d.c. coupled with the exception of the input C1 and the bootstrapping C5. For d.c. coupling omit C1 and C5. The op-amp IC1 will require offset compensation and the output voltage/current capability will be limited by the current available in R9 and R10.

The high frequency capability is limited to avoid undue emphasis on system noise and to enable readily available components to be used, in particular the MJE3055 and 741 op-amp. To increase the high frequency capability these

components would have to be replaced. The 741s with op-amps with a better bandwidth and the MJE3055s with a superior high frequency device. The switching time of D1 at high currents and high frequencies will start to become noticeable and it will have to be replaced with a high speed device. Experiment with the values of C2, C3 and C4 if the type of op-amp or output transistor is changed. ★

## News Briefs

### COMPUTING CLUB

A COMPUTING Club has been formed in the Falkirk area, to be known as the "Central Scotland Computing Club".

A Committee has been formed and it is planned to hold monthly meetings in Falkirk College of Technology, Grangemouth Road, Falkirk.

The Secretary is: James G. Lyon, 78 Slamannan Road, Falkirk, FK1 5NF, Tel: Falkirk 22430.

# next month...

**PE** TRANSISTOR IDENTICHART **PE**

**FREE** IN THE  
OCTOBER ISSUE  
TRANSISTOR IDENTICHART

Pin data on nearly 900 popular transistors including f.e.t.s and u.j.t.s, also comparable types.

## CINE FRAME COUNTER



An accurate three digit frame counter which should prove a valuable aid in the production of fades and single frame sequences.

## AUDIO LEAD TESTER

Many of the problems that occur in mobile PA systems are the direct result of lead failure. This unit provides a complete test sequence for the rigorous analyses of mono jack and cannon connectors to obviate this.

PRACTICAL

# ELECTRONICS

OUR OCTOBER ISSUE WILL BE ON SALE FRIDAY, SEPTEMBER 12, 1980



**FRANK W. HYDE**

## RE-RUN FOR RUSSIA

The success of Salyut-6 will influence Russia's thinking in the immediate future. Six new unmanned spacecraft have flown since June this year. The new thinking will involve considerable changes for they see this as an opportunity to catch up in the development of world space matters. To this end the new design will see a change in the interior layout of spacecraft. For example, in the past the instruments have been placed along the sides of the vehicles. In the future it is intended that the equipment shall be placed along the central axis of the station to facilitate man-machine interface.

Recently an official said that 'a considerable duration increase of time spent in space has shown us that this is economic and that we are now able to more reasonably assess the feasibility of long manned flights, particularly manned flights to Venus and Mars.' That the thoughts of Soviet scientists are turned in this direction by saying 'in the not too distant future', seems to show that they have hopes of catching up with the United States. Certainly the launch of Salyut-6 has paved the way to such activities.

Already the Russians have plans for a station some 25 tons heavier than Skylab. The reports are that such a station will have a weight of 220,000lb and be manned on a permanent basis with a constant complement of 12 cosmonauts. This is planned for the 1980s with a new launcher capable of 10-14 million pound thrust. This is more powerful than Saturn-5. This of course can easily manage manned flights to the Moon and Mars.

The cosmonauts at present on Salyut-6 Valeriy Ryumin and Leonid Popov are, at the time of writing this page, in the eleventh week of the present mission. It is expected that they will stay for 6 months. The tasks that have currently been carried out successfully in-

cluded materials processing of which one was concerned with germanium. The team also replaced an outdated module in the stabilisation system and in the medical field carried out a special examination of each other's physical condition including an electrocardiogram after performing certain prescribed exercises.

A special simultaneous experiment was carried by the cosmonauts from the space craft and another group operating a Soviet launched balloon within the Earth's upper atmosphere. This was to monitor charged particles from above and below, as it were. It is intended to fly medical doctors on future space missions as do the United States. No significant problems have arisen during the Salyut-6 manned missions. There was an occasion when cosmonaut Romanenko had bad toothache. This was dealt with by medicine from the spacecraft's medical kit with instructions from the ground medical team. Dental equipment was sent up to the space station in case the patient should become worse. Medical opinion in the Russian ranks was that appendectomy could be successful in zero gravity. This being the case there was little to be feared on long missions.

In June Russia announced more details of the Soyus-T. Both the standard Soyus and the first Soyus-T will continue to be used in service while the new Soyus-T is improved and possibly this situation will continue until the Soviet winged recovery vehicle is ready for service. Work continues on this vehicle. The Soyus-T is more efficient in the use of fuel and one way in which fuel is conserved is by separating the orbital module before the re-entry burn. This saves 10% in fuel. For the first time since the flight of the first Soyus in 1971 it was possible to fly round the Salyut and examine it visually and also with a camera.

New windows have been fitted to the Soyus because the previous design resulted in the windows becoming black during re-entry. The new design has layered windows, the blackened layer is to be jettisoned after re-entry to allow the crew full visibility. There are new spacesuits also for the Soyus-T crews. These are lighter and more efficient being free and manoeuvrable.

## THE SATELLITE POWER SYSTEM

In the last issue of *Spacewatch* I gave some notes which covered the general idea of the Satellite Power System and answered some questions. In this issue more details will be given about the system.

## THE SATELLITE

The Satellite will be a rectangular construction 10 kilometres in one direction and 5 kilometres at right angles to it. This will support the arrays of photo voltaic cells. The cells may be of gallium arsenide or silicon. Such a structure will be of considerable weight and of the order of 36,000 metric tons. As a great deal of it will be constructed in space the weight is only involved in the initial transportation first into a low earth orbit and then raised to synchronous orbit.

The transmitting antenna with the conversion units on which are mounted the DC/RF

converters will form the individual sub-assemblies of the transmitting antenna. This will have a diameter of 1 kilometre. Thus it will appear as an assembly of waveguides with a high density beam direct to the Earth. The transmitting antenna will be so arranged that the profile as presented to the ground antenna, the RECTENNA, has a highpower centre to the beam and taper off at the edges. This has been necessary because of the possible effects to the environment over a long period and short term effects due to local conditions (weather, accidental intrusion from other causes) and safety in general. To appreciate these necessities a description of the rectenna is needed.

## THE RECTENNA

The Rectenna is a vast array of collecting dipoles and covers an area of 130 Km<sup>2</sup>. It is expected to be in the form of 10 kilometres east to west and 13 kilometres north and south. By any standards this is a large area and involves the effect on the ground beneath it and the vagaries of meteorological conditions which may at one and the same time vary widely, differing from side to side or from end to end. Indeed considerations such as the number of lightning strikes, which are quite considerable in the latitude of 35° north, the position contemplated for the rectennas across America.

The centre of the microwave beam at a frequency of 2.45 GHz will at the rectenna have a power density of 23mW/cm<sup>2</sup>. The density will fall off towards the edges in such a way that at the site safety boundary will have reached the low level of 0.1mW/cm<sup>2</sup>. At the overspill edge the beam will have a density of 1.0mW/cm<sup>2</sup>. From the point of view of safety to human life the density of the beam will be way below possible ill effects. The hazards are more likely to effect other mechanical considerations and as suggested freak weather conditions.

These considerations will all come under the scrutiny of observers and research teams. This aspect will be dealt with in later issues of *Spacewatch*.

## CONVERSION OF THE MICROWAVE POWER

The Conversion of the Microwave Power is likely to take the form of sub-units of RF-LF converters arranged in such a way that around the periphery of the rectenna site feed lines will link with normal grid system in operations. It will take different forms as to the distribution voltages depending on local medium and long distance transmission networks to be fed. The order of the thinking is to insert the SPS into the existing power grid. Cost and convenience will determine this for it might call for local decisions as to which is the more economical. The first of the considerations is the effect on the environment as related to the public but also the possible long term effects on the flora and fauna of America and indeed its possible effect through modification of near space in terms of communications and meteorology. Of these matters more will appear in future issues of *Spacewatch*.

# CASIO

# METAC

### CORRECTION

Unfortunately there were some errors in our Casio Watch Offer published in the July issue. Since our offers are arranged for the benefit of readers, we would like to bring these errors to your attention.

1. We indicated that the front cover illustration was of an older watch, this is not the case.
2. The watch is stainless steel encased.
3. The watch on offer is 9.65mm thick and not "less than 9mm" as originally stated.
4. The alarm sounds for 30 seconds unless cancelled, not 60 seconds as originally stated.

These mistakes were due to our late decision to change to a watch with a constant time and date display. Since we have unintentionally misled readers on these points, we will be pleased to refund their money and postage if they so wish. We would like to make it quite clear that the guarantee will be honoured by Metac.

We have published a corrected special offer page here for those that wish to take advantage of it.



# WATER

# £21.95

Including VAT Postage and Packing

### THE OFFER

For some time PE has been trying to arrange a special offer on one of the very popular range of Casio watches. Until now this has not been possible due to the control of supply by Casio. However, Metac have now been able to purchase Casio outside the UK and this offer is the result.

We do not expect readers to be able to find this Casio watch advertised at less than the Metac price.

### THE WATCH

#### CASIO ALARM CHRONO TYPE 83 QS 41B

Stainless steel, less than 10mm thick, mineral glass, water resistant to 2 atmospheres (66 feet), Lithium battery giving approximately four years' life, four year calendar, accurate to within 15 seconds a month, full one year's guarantee.

### THE FACILITIES

- ★ Hour, minute, second, am/pm, date.
- ★ Hour, minute, am/pm, day, date.
- ★ Stopwatch to 12 hours measuring in 1/10 second giving net time, lap time and 1st-2nd place times. Indicator shows chronograph is running when normal time is displayed.
- ★ Alarm setting, hour, minute, am/pm. Alarm sounds for 30 seconds unless cancelled. Indicator shows alarm is set.
- ★ User optional hourly chime (two bleeps).
- ★ Back-light.

To: METAC Electronics and Time Centre (P.E. Offer)  
67 High Street, Daventry, Northants. Tel. 032 72 76545.

To: METAC Electronics and Time Centre (P.E. Offer)  
67 High Street, Daventry, Northants. Tel. 032 72 76545.

Mail order only

Please send me .....watch/es at £21.95 each

I enclose P.O./Cheque No.....Value.....

Name .....

Address .....

.....

.....

Please allow 21 days (maximum) for delivery (more for overseas orders)

**OFFER EXTENDED TO OCTOBER 3, 1980**

Name .....


Address .....

.....

.....

From: METAC Electronics and Time Centre (P.E. Offer), 67 High Street, Daventry, Northants.

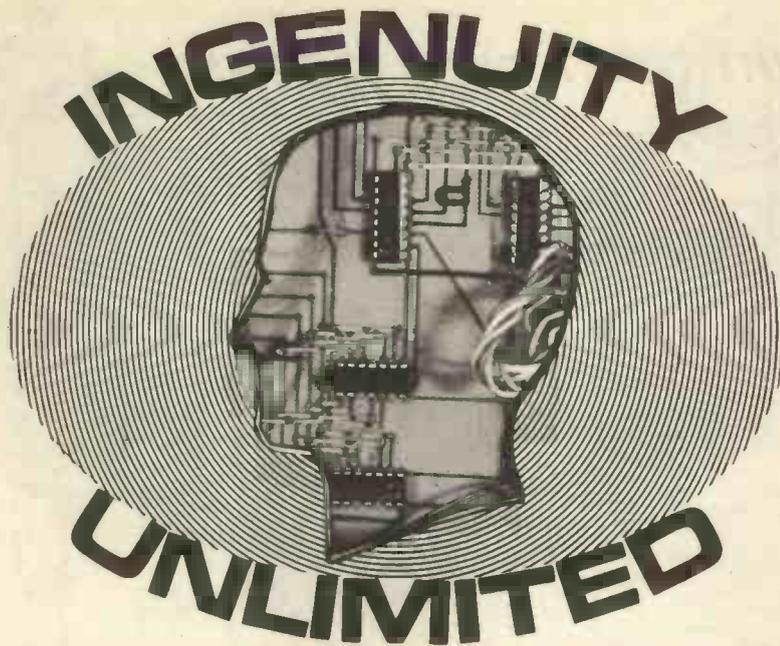Please complete both parts of the coupon in BLOCK CAPITALS



A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere.

ONE result of the pressures of modern living is the alarm clock. However, the type which must be set each night have a habit of being forgotten and the type which sound unless turned off tend to awaken their owners when they want a lie-in on Saturday morning. This circuit enables the user to selectively inhibit the alarm of his clock for either of the following two days—normally this would be operated on a Friday to stop the alarm for the weekend.


The complete circuit diagram is shown at right. The input on the left is a CMOS input which comes from the clock circuitry or mechanism. When the alarm of the clock is on, this output is high but when it is not on, or has been cancelled, it is low.

The two halves of IC1 are connected as a two stage shift register. Every time the clock input is taken high, the data in the register is shifted one place to the right. Since the input of the register is low, zeros are shifted in from the left.

The complementary output of IC1b ( $\bar{Q}2$ ) is "ANDed" with input signal in IC2b and IC2c. Normally the shift register is full of zeros so that  $\bar{Q}2$  is high. This means that the output of the unit is the same as the input.

Suppose that IC1b is in the one state.  $\bar{Q}2$  would then be low and the output of the unit would remain low for the duration of any input pulse. However at the end of the pulse, the output of IC2a would go high and the shift register would be clocked. This would mean that another zero would be clocked into IC1a but the one in IC1b would be replaced by the zero in IC1a.  $\bar{Q}2$  would go high and a further pulse would be passed without interruption. The action of the circuit has been to suppress one pulse applied to its input. It can be seen that the state of IC1b determines whether the next pulse will be inhibited and the state of IC1a does the same

## ALARM CLOCK WEEKEND LOCKOUT

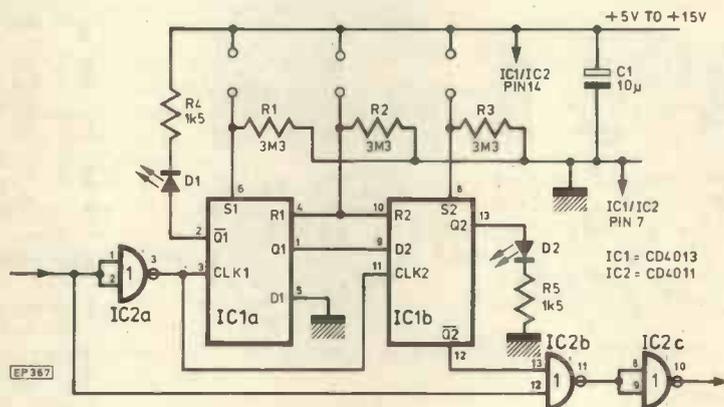

thing for the next pulse but one. Since the input is an alarm signal, the circuit will selectively inhibit this signal for the following two days.

To set the state of the flip-flops, three touch switches are used. Two of these set IC1a and IC1b respectively whilst the third resets both. Normally, the set and reset inputs are held low by R1–R3 but skin resistance across the touch contacts is much lower than these resistors so the input is pulled high, setting or resetting the desired flip-flops.

To indicate the state of the flip-flops, i.e. to tell the user which inhibits he has selected, two l.e.d.s are used. These are connected to  $\bar{Q}1$  and  $Q2$ ; since these signals are of opposite logical polarity, D1 is returned via a current limiting resistor to the positive supply line whereas D2 is returned to the ground rail. This means that either l.e.d. is on when the corresponding flip-flop is in the one state.

Both the input and output of the unit are at CMOS levels and it is up to the user to interface these to his clock and alarm circuitry: this should normally present no problem. The power supply can be anywhere between 5V and 15V and can often be borrowed from the clock. C1 is necessary to prevent noise on the power line from triggering the flip-flops.


The number of flip-flops could of course be made greater than two but this was thought to be the maximum needed since it corresponds nicely with a weekend.

Construction is not at all critical and can take any desired form. The touch switches and l.e.d.s can then be mounted on a convenient position on the clock.

P. M. Jessop,  
Solihull,  
West Midlands.
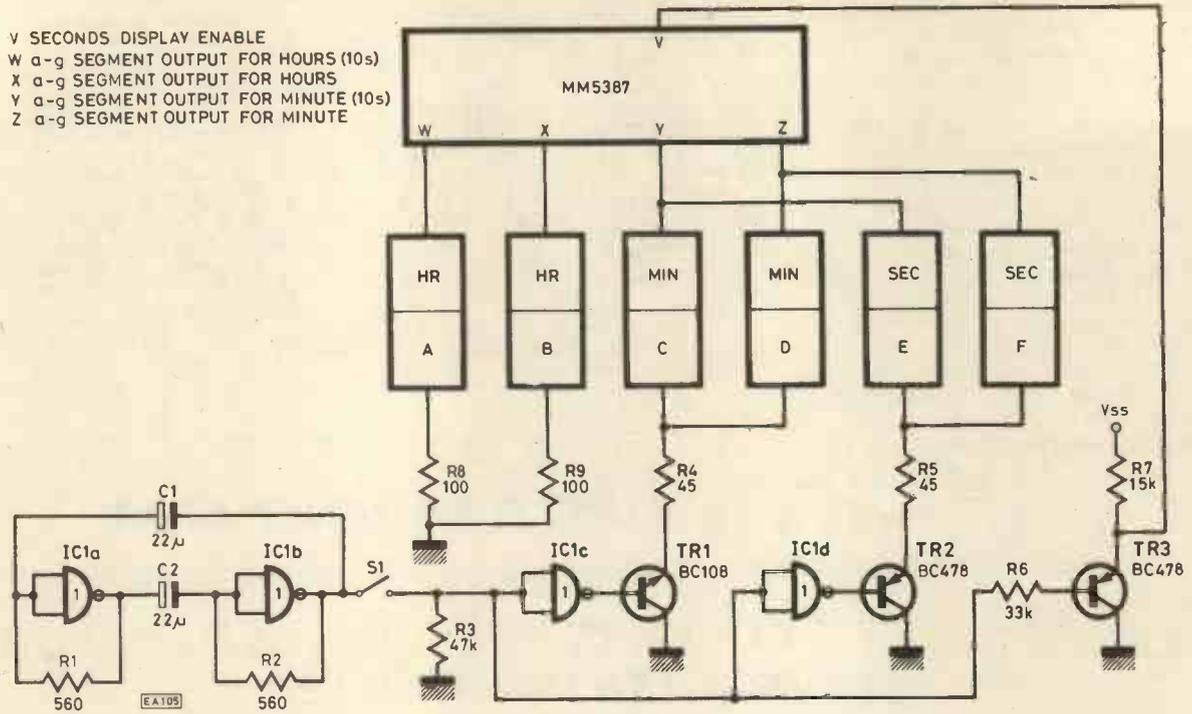
# FOUR DIGIT TO SIX DIGIT CLOCKS

V SECONDS DISPLAY ENABLE  
 W a-g SEGMENT OUTPUT FOR HOURS (10s)  
 X a-g SEGMENT OUTPUT FOR HOURS  
 Y a-g SEGMENT OUTPUT FOR MINUTE (10s)  
 Z a-g SEGMENT OUTPUT FOR MINUTE



**T**HERE are plenty of digital clocks in the market today. Most of them are four digit types with few of six digits available. These don't have functions like alarm, radio on and off etc. I have a design which might benefit those who own a four digit clock but would like to have a six digits displaying hours, minutes and seconds. A simple straightforward multiplexing method was used with a minimum number of components to reduce cost and complexity.

A MM5387 clock chip was used. This is the same as a MM5316 except it can drive displays directly. The circuit is for a common cathode i.e.d. display clock only.

The connections are as follows—the tens of hours and hours segment outputs from the i.c. are connected normally. The

tens of seconds and seconds segments were connected parallel to tens of minutes and minutes segments respectively. Two gates of a 7400 quad NAND gate form an oscillator and switch IC1c and TR3. They also switch TR1 and TR2. These control the displaying and blanking of seconds and minutes displays. TR3 switches the seconds display option of the clock.

The oscillator provides a square wave that switches IC1c/d, TR3. TR1 is *n.p.n.* and TR2 is *p.n.p.* Therefore when one conducts the other will be cut off. When TR1 is conducting, the seconds display enable of the clock i.e. will go negative and the clock will be programmed to display hours and minutes. At the same time TR1 will also be conducting which enables displays

C and D.


When TR2 is not conducting, the seconds displays enable of the clock i.e. will go positive. This will program the clock to display seconds. At this time TR2 will be conducting enabling displays E and F.

As the oscillator functions at about 200 hertz the displaying of hours, minutes and seconds will be displayed continuously.

The circuit works well, the only problem being that there are problems in setting time so S1 was included which will cut off the six digit function. The time should be set with this in the off position.

P. Ratnam,  
 Penang,  
 Malaysia.

# QUIZ WIN INDICATOR

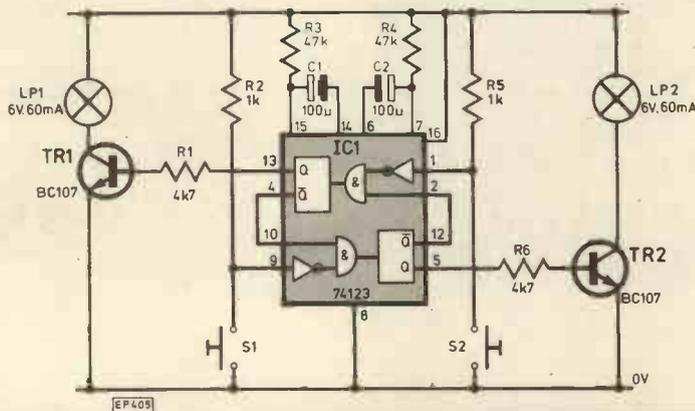

**I**F S1 is shorted, the one shot will be triggered and LP2 will light for about 3 seconds assuming that the other stage is not already in a triggered state. While lamp one is alight any closure of S2 will not cause LP1 to light as the one shot is inhibited by a logical 0 at pin 2. The same applies if the order is reversed.


Two contestants are positioned either side of the unit with fingers on the buttons. A question is asked and the first to answer pushes his button and his lamp lights. The other lamp is inhibited and the win lamp resets itself after about 3 seconds ready for the next question.

J. Sarns,  
 West Mersea,  
 Essex.

**T**HE circuit shown was designed to program a VCO in a synthesiser. Two waveforms are available; A sawtooth output from the wiper of VR3 and a squarewave from VR4. Both signals have a level of about 2 volts (peak to peak) about earth.

The novelty lies in the fact that the shape of both waveforms is continuously variable via VR1 which provides base bias to both transistors. This in turn alters the ratio of the currents in each. Because the current flowing out of the transistors is passed into an integrator, then the voltage at pin 6 of IC1 is a function of the control. The remaining circuitry is of the standard integrator—Schmitt trigger loop, the output of IC2 deciding which transistor is turned on by forward biasing. VR2 will vary the current available to the transistors and hence the frequency of oscillation.

M. Rodgers.  
Maltby,  
S. Yorkshire.

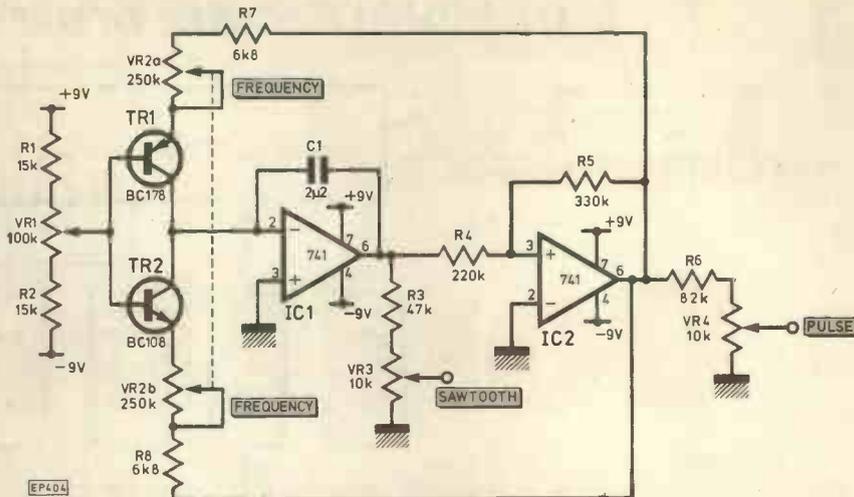



## FUNCTION GENERATOR

## SLAVE FLASH CONTROLLER

**T**HIS 555 circuit is used to control the operation of a slave flash unit. Here the phototransistor responds to ambient light levels. The 470k variable resistor is used to set the l.e.d. to the 'just off' condition. When the master flash unit operates the CSR conducts operating the slave unit.

S1 allows the slave unit to be set without discharging the flash.

R. C. MacKay,  
Grangemouth.

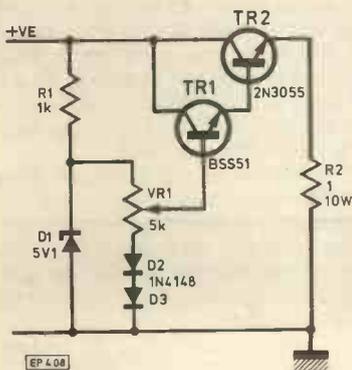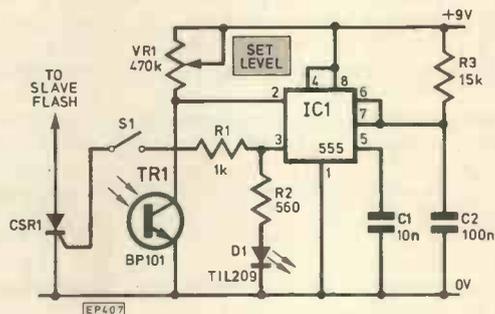

**W**HEN carrying out battery capacity checks, it is extremely useful to have a load that does not need constant adjustment to maintain a steady current as the voltage falls.

This circuit fulfills the requirement in that once the load is set the load current remains constant throughout the discharge time of the battery. In practice the 2N3055, and the 1 ohm resistor are mounted on a suitable heatsink. The circuit was used to test 12V batteries and the load is variable between 0 and 3 amps.

D. Halliday,  
Tewkesbury,  
Glos.

## BATTERY CHECK

# N Watch NEWS

JULY 1980

60p

## SPECIAL REPORT


Just £1  
to all readers

# Don't buy a digital watch until you read this report

There are so many digital watches on the market, with varying functions, that the average person is bound to feel somewhat confused.

A new survey of the electronic watch industry has been produced to clarify this confusion and to give an unbiased and objective answer to the many questions that are constantly being raised.

by Trevor Raven.  
C.Eng. AMBIM. MIERE

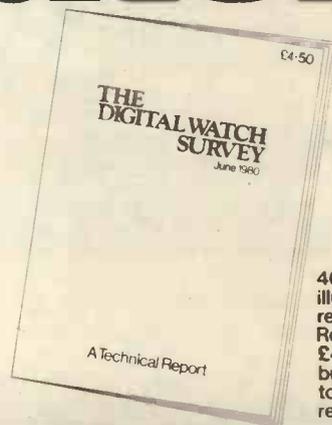

40 page  
illustrated  
report.  
Retail price  
£4.50  
but just £1  
to our  
readers.

- \* How accurate are electronic watches?
- \* Who makes Seiko's?
- \* What is the importance between brand names?
- \* Is solar power worth the extra money?
- \* What are the most important features in a watch?
- \* When will prices stop falling?

The survey answers all of these questions and tells you what to look for in a quartz watch; how they work; why the prices vary so much; what the future holds.

### SPECIAL OFFER

Send today for this technical report, plus news of a unique Metac offer to beat all special offers.

Complete the coupon below and send it FREEPOST (no stamp required) and we will post, Same Day Despatch, the technical report giving you all you need to know about electronic watches and details of our special offer.

## Which is the best watch?



These four watches are very different in price, durability and functions. How would you choose between them?

This unbiased and objective report helps you to make this decision and gives you a deeper insight into the rapidly changing and exciting world of the micro-chip.

For your copy of the report complete and return the coupon to: Metac Electronic & Time Centres, 24-hour Despatch Centre, FREE-POST, 47A High St., Daventry, Northants.

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_


PE9

## RUN YOUR HOME BY REMOTE CONTROL

How many times have you considered building a remote control project for the house but were put off by the dozens of ICs, special coils, lenses and other hard to get components, not to mention the need for a well equipped lab. To set the unit up. T. K. ELECTRONICS have changed all that. Three ICs can build a sophisticated system that requires only a capacitor and resistor to set the clock frequency (which can drift by up to 20% without affecting performance). Control radios, hi-fi (including bass, treble and volume), lighting, toys, garage doors, etc. Still not convinced? then look at the prices!

LD271	IR Emitting Diode	36p
SFH205	Photodiode Detector	95p
SL480	IC Pulse Amplifier	£1.70
SL490	Keyboard Controlled Encoder/Transmitter	£2.40
ML922	10-channel Receiver & 3 Analogue Outputs	£4.20
ML926	16-channel Receiver (4 Momentary binary outputs)	£1.40
ML928	16-channel Receiver (4 latched binary outputs)	£1.40
	Data sheets (per device)	5p

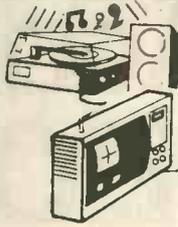These ICs can also be used with ultrasonic and radio links, depending on range, cost and speed of operation. For more details, why not give us a ring - or send sae. We will be pleased to advise you.



### NEW KIT +++ NEW KIT +++ NEW KIT +++ NEW KIT

If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel ON/OFF infra red transmitter and receiver. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a preamplifier, bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. The minimum range is 20 feet. A suitable box for the receiver is available if required.

ONLY **£12.00**

### MINI TRANSFORMERS



Standard mains primaries 240V a.c.  
100mA secondaries  
6-0-6V 80p  
9-0-9V 85p  
12-0-12V 90p

### D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	36p

### TK's SPECIAL OFFERS OF THE MONTH

ORDERS MUST BE RECEIVED BY 30.9.80

5	TIC 106D 5A/400V SCR	£1.75
5	TIC 206D 3A/400V TRIAC	£2.00
5	TIC 226D 8A/400V TRIAC	£2.50
10	Rectangular Green LED	£1.75
10	Rectangular Yellow LED	£1.75
5	78 LIS 12V 100mA regulator	£1.10
5	78D5 5V 1A regulator	£2.25

## CT4000 CLOCK/APPLIANCE TIMER KIT

The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay kit (MK2). The kit includes a PCB, keyswitches, I.C., 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.

**£25.25**

Size: 10x12x4.5 cms.  
Colour: Black.

### MINI KITS

### DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

**DL1000K** This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.60**

**DL21000K** A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**

Optional Opto Input DLA1 **60p**

These Kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

**MK1 TEMPERATURE CONTROLLER/THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max), and triac to switch heater.  
500W **£3.20** 1KW **£3.50**

**MK2 SOLID STATE RELAY**  
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

**MK3 BAR/DOT DISPLAY**  
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

**MK4 PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C.  
1.5KW **£5.25** 3KW **£5.55**

**MK5 MAINS TIMER**  
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW **£4.50**

### D.V.M. THERMOMETER KIT

Based on the ICL7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). **£20.75**

### INTEGRATED CIRCUITS

555 Timer	21p
741 Op Amp	19p
AY-5-1224 Clock	£2.80
AY-5-1230/2 Clock/Timer	£4.20
AY-3-1270 Thermometer	£4.20
ICL7106 DVM (LED drive)	£7.00
LM377 Dual 2W Amp	£1.45
LM379S Dual 5W Amp	£3.50
LM380 2W Audio Amp	80p
LM382 Dual low noise preamp	£1.00
LM386 250mW low voltage amp	75p
LM1830 Fluid Level Detector	£1.50
LM2907 f.v. Converter	£1.50
LM3909 LED Flasher/Oscillator	55p
LM3911 Thermometer	£1.20
LM3914 Dot/Bar Driver	£2.10
MM57180 (stack) Timer	£5.90
MM74C911 4-digit display controller	£5.50
MM74C915 7-segment BCD converter	£4.50
MM74C926 4-digit counter with 7-seg outputs	£2.50
S966B Touchdimmer	£4.85
S9263 Touchswitch 16 way	58p
T8A800 5W Audio Amp	85p
T8A810AS 7W Audio Amp	£1.00
TDA1024 Zero Voltage Switch	£2.85
TDA2020 20W Audio Amp	£1.80
ZN1034E Timer	5p

All ICs supplied with data & circuits. Data sheets only



All components brand new and to BARCLAYCARD specification. Add V.A.T. AT CURRENT RATE TO ABOVE PRICES PLUS 35p P & P. Mail Order. Callers welcome by appointment.



TK ELECTRONICS (PE) 106 Studley Grange Road, London W7 2TX. Tel: 01 579 5794



## The MIGHTY MIDGETS SOLDERING IRONS AND ACCESSORIES

	RETAIL PRICE ex inc. V.A.T.	POSTAGE extra
18 WATT IRON FITTED WITH NO. 20 BIT AVAILABLE IN: 12V, 110V, or 240V	£4.43	26p
SPARE BITS	52p	—
STANDS	£4.23	75p
SOLDER: SAVBIT 20'	61p	10p
" 10'	37p	6p
LOWMELT 10'	76p	12p
I.C. DESOLDERING BIT	£1.04	12p
BIT SIZES:	NO. 19 (1.5mm) NO. 20 (3mm) NO. 21 (4.5mm) NO. 22 (6mm)	

From your Local Dealer or Direct from Manufacturers

## S & R BREWSTER LIMITED

86-88 UNION ST. PLYMOUTH PL1 3HG  
Tel: 0752 65011 TRADE ENQUIRIES WELCOME



PLEASE QUOTE YOUR NUMBER WHEN ORDERING

# ELECTROVALUE FOR COMPONENTS THAT COUNT



<b>SIEMENS</b> SEMI-CONDUCTOR CAPACITORS FERRITES	<b>NASCOM</b> MICRO COMPUTERS AND ANCILLARIES	<b>VERO</b> BOARDS CASES & KITS
<b>ISKRA</b> RESISTORS	<b>RADIOHM</b> POTENTIOMETERS OP TO-ELECTRONICS	<b>BREADBOARDS</b> <b>SOLDER TOOLS</b> <b>SWITCHES</b> <b>CATALOGUE 10</b>

GOOD DISCOUNTS AND FREE POSTAGE ON SUBSTANTIAL C.W.O. U.K. ORDERS  
COMPUTER-CONTROLLED SERVICE AIDS PROMPT DELIVERY  
128-PAGE CATALOGUE FREE FOR THE ASKING


**ELECTROVALUE LTD., (PE8), 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London 87) STD 0784. Telex 264475.**

**NORTHERN BRANCH (Personal Shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.**

Unique in concept - the home computer that grows as you do!
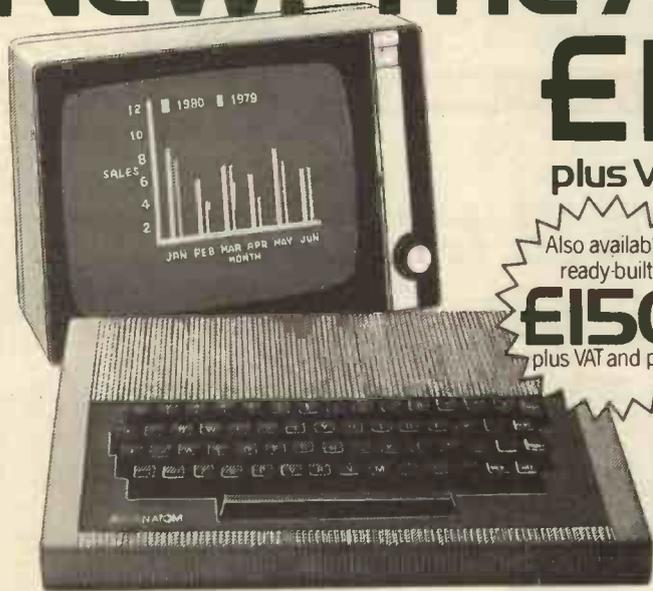
# New! - The Acorn Atom

**£120** An outstanding personal computer kit  
plus VAT and p&p.



Also available ready-built

**£150**  
plus VAT and p&p

The ATOM - a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now - tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!

\*The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom.

### The standard ATOM kit includes:

- Full sized QWERTY keyboard ● Rugged polystyrene case
- Fibreglass PCB ● 2K RAM ● 8K ROM ● 23 integrated circuits
- Full assembly instructions including tests for fault-finding. (Once built, connect it to any domestic TV and power source)
- Power requirement: 8V at 800 M A. ATOM power unit available.

See coupon. PLUS FREE MANUAL written in two sections - teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.



### The ATOM concept

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMs may be linked to each other - or to a master system with mass storage/

hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally.


So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

### The ATOM hardware includes:

- Memory from 2K to 12K RAM on board (up to 35K in case)
- 8K to 16K ROM (two 4K additions) ● 6502 processor ● Video Display allows high resolution (256 x 192) graphics and red, green and blue output ● Cassette Interface - CUTS 300 baud
- Loudspeaker allows tone generation of any frequency
- Channel 36 UHF Modulator Output ● Bus output includes internal connections for Acorn Eurocard.
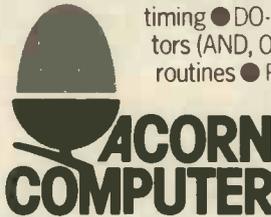
### The ATOM software includes:

- 32-bit arithmetic ( $\pm 2,000,000,000$ ) ● High speed execution
- 43 standard/extended BASIC commands ● Variable length strings (up to 256 characters) ● String manipulation functions
- 27 32-bit integer variables ● 27 additional arrays ● Random number function ● PUT and GET byte ● WAIT command for timing ● DO-UNTIL construction ● Logical operators (AND, OR, EX-OR) ● LINK to machine-code routines ● PLOT DRAW and MOVE.



4a Market Hill,  
CAMBRIDGE CB2 3NJ

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. All components are guaranteed with full service/repair facility available.

Please send me the following items:

Quantity	Item	Item price inc. VAT+p&p	TOTALS
	ATOM KIT 8K + 2K (MIN)	@ £140.00	
	ATOM ASS 8K + 2K (MIN)	@ £174.50	
	ATOM KIT 12 + 12K (MAX)	@ £255.00	
	ATOM ASS 12 + 12K (MAX)	@ £289.50	
	1K RAM SETS	@ £11.22	
	4K FLOATING POINT ROM	@ £23.30	
	PRINTER DRIVE	6522 VIA @ £10.35	
		Buffer (LS 244) @ £3.17	
	MAINS POWER SUPPLY (1.5 amps)	@ £10.20	
		TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £

Please debit my Access/Bardcard No.

Signature

Name (Please print)

Address


Telephone No.

Registered No: 1403810. VAT No: 215 400 220

PE/9/80





# Simply ahead...

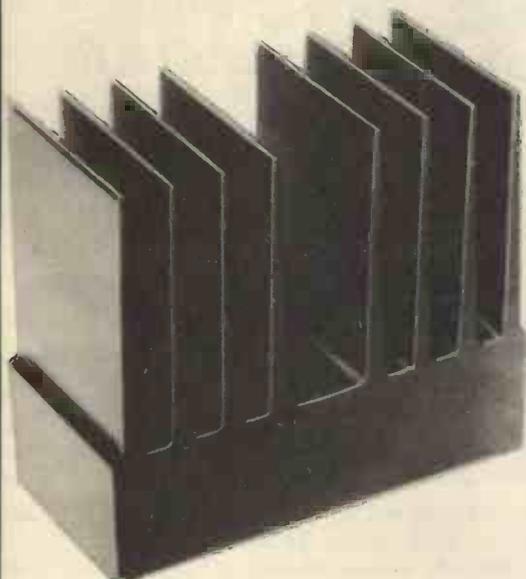
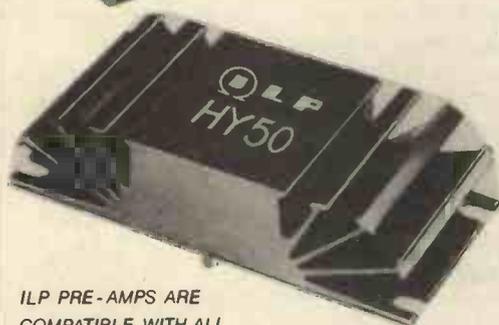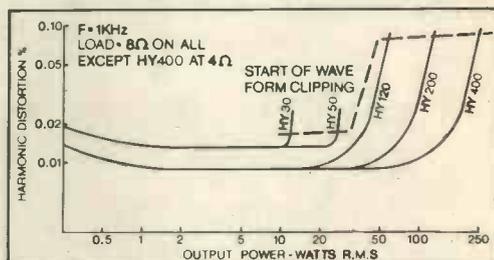
## POWER AMPLIFIERS

ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pickups, tuners, etc. using digital or analogue sound sources.



ILP PRE-AMPS ARE  
COMPATIBLE WITH ALL  
ILP POWER AMPS AND PSUs

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	100 dB	-20 -0+ +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	100 dB	-25 -0+ +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100 dB	-35 -0+ +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100 dB	-45 -0+ +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100 dB	-45 -0+ +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4 Ω - ∞  
Input sensitivity - all models 500 mV  
Input impedance - all models 100K Ω  
Frequency response - all models 10Hz - 45 KHz - 3dB

## POWER SUPPLY UNITS



ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and apart from PSU 30 and 36 which are smaller PSU's - in all the other ILP manufactured PSU's, ILP toroidal transformers are used which are half the size and weight of laminated equivalents. They are also more efficient and have greatly reduced radiation.

PSU 30 ± 15V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + £0.68 VAT


THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS  
PSU 36 for 1 or 2 HY30's £8.10 + £1.22 VAT  
THE FOLLOWING INCLUDE TOROIDAL TRANSFORMERS

PSU 50 for 1 or 2 HY50's £8.10 + £1.22 VAT  
PSU 60 for 1 HY 120 £9.75 + £1.46 VAT  
PSU 70 for 1 or 2 HY120's £13.61 + £2.04 VAT  
PSU 90 for 1 HY200 £13.61 + £2.04 VAT  
PSU 180 for 1 HY400 or 2 x HY200 £23.02 + £3.45 VAT



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.

# this time with two new pre-amps

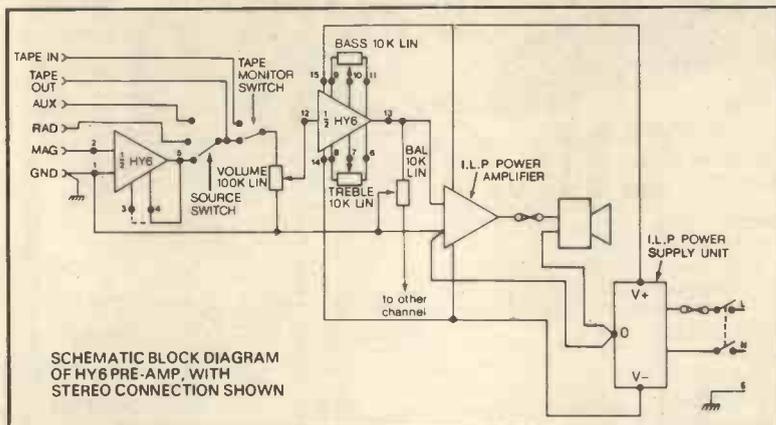

## HY6 mono HY66 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers – HY6 for mono operation, HY66 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

Sizes – HY6 – 45 x 20 x 40 mm. HY66 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity – Mag. P.U. – 3mV: Mic – selectable 1-12mV: All others 100mV: Tape O/P – 100mV: Main O/P – 500mV: Frequency response – D.C. to 100KHz – 3dB.

### HY6

mono

£5.60

+ VAT 84p

### HY66

stereo

£10.60

+ VAT £1 59

Connectors included

B6 Mounting Board

78p + 12p VAT

B66 Mounting Board

99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90 dB (Mag. P.U. – 68 dB).
- HIGH OVERLOAD FACTOR – 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$ V to  $\pm 60$ V.

NO QUIBBLE  
5 YEAR GUARANTEE  
7-DAY DESPATCH ON ALL ORDERS  
BRITISH DESIGN AND MANUFACTURE  
FREEPOST SERVICE  
- see below

★ ALL U.K. ORDERS DESPATCHED POST PAID  
HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope – we pay postage on all letters sent to us by readers of this journal.

**ILP**  
**ELECTRONICS LTD.**

FREEPOST 2 Graham Bell House, Roper Close,  
Canterbury, Kent CT2 7EP.  
Telephone (0227) 54778 Telex 965780

Please supply ..... PE.9.

..... Total purchase price £.....

Enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No.....

NAME .....

ADDRESS .....

Signature .....

# TRANSFORMERS + VAT 15%

**30 VOLT RANGE**  
Pri 220/240 Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.93	1.10
3	2.0	6.85	1.10
20	3.0	7.39	1.31
21	4.0	8.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.99	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	20.0	32.40	O.A.

## CONTINUOUS RATINGS

All voltages given are at full load

**60 VOLT RANGE**  
Pri 220/240V Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24-0-24V or 30V-0-30V.

Ref	Amps	Price	P&P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	1.21
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.
189	12.0	37.47	O.A.

**50 VOLT RANGE**  
Pri 220/240V Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	32.88	O.A.

**MAINS ISOLATORS (SCREENED)**  
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
107	20	4.54	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	58.52	O.A.
158	2000	87.99	O.A.
159	3000	95.33	O.A.

\*Pri. 0-220-240V Sec 115 or 240V. Stale sec. volts required.

**CASED AUTO TRANSFORMERS**  
240V cable in 115V USA flat pin outlet.

VA	Price	P & P	Ref
20	6.55	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
250	12.55	1.67	69W
500	20.15	1.89	67W
1000	30.67	2.65	84W
2000	44.97	O.A.	95W

## 12 OR 24V OR 12-0-12V

Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0.5	0.25	2.42	0.82
213	1.0	0.5	2.90	0.90
71	2		3.88	0.90
18	4		4.48	1.10
85	5	2.5	6.18	1.10
70	6	3	6.99	1.10
108	8	4	8.18	1.31
72	10	5	8.18	1.31
116	12	6	9.89	1.52
17	16	8	11.79	1.80
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

## AUTO TRANSFORMERS

Voltage for step up or step down

Ref	VA	(Watts)	£	P&P
113	15	0-115-210-240	2.73	0.81
34	75	0-115-210-240	4.41	1.10
4	150	0-115-200-220-240	5.70	1.10
67	500	0-115-200-220-240	12.09	1.91
84	1000	0-115-200-220-240	20.64	2.39
93	1500	0-115-200-220-240	25.81	O.A.
95	2000	0-115-200-220-240	38.31	O.A.
73	3000	0-115-200-220-240	65.13	O.A.
80S	4000	0-115-200-220-240	84.56	O.A.
57S	5000	0-115-200-220-240	98.45	O.A.

## CONNECTORS

Thorn, Cannon, Plessey, Bendix, Greepar, available on request.  
W/W Resistors 2.5W, 6W, 10W, 12W, available on request.

P.W. Purbeck oscilloscope transformer 250-0-250V 6.9V:12-9V £8.42. P.&P. £1.04.

## NEW RANGE TRANSFORMERS

2 windings - 0-36V-48V/36V-0-36V 48V-0-48V 72V or 96V.

Amps	Ref	Price	P&P
0.5	430	4.88	0.76
1.0	431	8.12	0.99
2.0	432	13.35	1.31
3.0	433	16.17	1.40
4.0	434	20.65	2.11
5.0	435	29.30	2.47
6.0	436	36.69	O.A.
8.0	437	40.03	O.A.

## Bridge Rectifier

Ref	Price	P&P
100V 25A	£2.40	
200V 4A	.45	
200V 4M	.65	
400V 4A	1.85	
400V 6A	£1.25	
500V PM7A6 12A	£3.25	

## AVO TEST METERS

Ref	Price	P&P
AVO 8 Mk5	£100.50	
AVO 71	£40.80	
AVO 73	£55.40	
AVO MM5 minor	£35.95	
AVO Wee Megger	£82.20	
AVO TT169 in circuit transistor tester	£42.60	
AVO EM272 316K - Volts	£63.40	
AVO DA116 digital	£110.90	
AVO BM7 Megger	£55.40	
AVO clamp metre to 300A	£55.10	

## 20,000 ohm/V Multimeter

mirror. Scale ranges AC/DC to 1000V DC current to 250ma. Resistance to 3 M Ohms 5"x3"x1" £14.38. P.&P. £1.00. VAT 15%.

## U4315 Budget Meter

20kV/2 Ranges to 1000V. 2.5A AC/DC 500K Res. In steel case £15.85 P&P £1.32

## SPECIAL OFFER Multimeter (20KOhm/V with combined audio/LF test oscillator at 1KHz and 455 KHz AC/DC to 1000 volts DC current to 500 MA resistance to 1µΩ size 160x97x40mm £8.50, P&P £1.00, VAT 15%

## Split Bobbin Type - 0-12-15-20-24-30V.

Ref 009 - 1 Amp £2.98. P. & P. £1.10. Ref 010 - 2 Amp £4.65. P. & P. £1.10 open frame fixing. Other types available.

## "Educational" Meters (Moving coil)

0-10A, 0-1A, 0-2A, 0-15V, 0-30V. Free standing large scale easily read meters with top screw terminals for quick connections. £4.50 P&P 66p + VAT

## PANEL METERS

43mm	43mm	82mm	78mm
0.50VA	6.20	0.50VA	6.70
0.500µA	5.95	0.500VA	6.70
0-1mA	5.95	0-1mA	6.70
0-30V	5.95	0-30V	6.70
VU ind. Panel 48mm x 45mm or 40mm x 40mm 250µA fsd		5V041 Edge VU centre zero fsd £2.60	

Carriage 76p. VAT 15%  
Send 20p stamp for catalogue  
Prices correct 31/6/80

## 15V Range 0-C Tap (1.5V-0-7.5V)

171 500mA	2.30	0.52
172 1A	3.26	0.92
173 2A	3.95	0.90
174 3A	4.13	0.99
175 4A	6.30	1.10

## Burglar Alarm - ultrasonic, 20ft range, no installation costs. Key operated; built in siren (external can be added). Looks like a speaker. £98.00 £2.00 P&P + VAT.

## SCREENED MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0-3	2.83	0.63
212	1A, 1A	0-6-0-6	3.14	0.90
13	100	9-0-9	2.35	0.44
235	330, 330	0-9-0-9	2.19	0.44
207	500, 500	0-8-9, 0-8-9	3.05	0.85
208	1A, 1A	0-8-9, 0-8-9	3.88	0.90
236	200, 200	0-15, 0-15	2.19	0.44
214	300, 300	0-20, 0-20	3.06	0.80
221	700(OC)	20-12-0-12-20	3.75	0.90
206	1A, 1A	0-15-20-0-15-27x26.64	2.09	1.10
203	500, 500	0-15-27-0-15-27x26.64	3.19	1.10
204	1A, 1A	0-15-27-0-15-27x26.64	3.88	0.90
239	50	12-0-12	2.88	0.43
234	500	6	2.19	0.44

**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL

# DISCO LIGHTING KITS!!!

First class constructional projects, c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

- |                     |   |                      |   |
|---------------------|---|----------------------|---|
| <b>LK1</b><br>£9.90 | 3 channel sound-to-light<br>300 w/channel 1v - 100w input                               | <b>LK2</b><br>£17.90 | 3 channel 3k W<br>zero voltage firing<br>200mV - 100 watts input.     |
| <b>LK3</b><br>£5.50 | 2kW slider dimmer<br>suitable for clubs/pubs.<br>A professional unit c/w<br>face plate. | <b>LK4</b><br>£16.50 | 4 channel 4k W<br>audio - forward/reverse<br>auto - two speed ranges. |

ALL KITS C/W Facia panel, circuit, comprehensive instructions & full parts guarantee

Suitable case for LK 1/2/4 £3.50  
100w spots ES or BC £1.50.  
Coloured pigmy lamps 65p.

Carriage on above 70p

## UNREPEATABLE HI-FI BARGAIN

### 3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

- Comprises:
- ★ 6 1/2" linen surround bass unit
  - ★ 5" mid-range unit
  - ★ 3" tweeter
  - ★ 3 way crossover, fixing screws & baffle
  - ★ 20 watts handling capability.
- Full instructions provided  
Must be heard to be believed!!  
£9.95 + £1 carr. or two kits for £20 carr. free.



JAYkit + Standard Parts =

**DM-2**

DIGITAL MULTIMETER

- ★ DC Volts ..... 1mV to 1000V
- ★ AC Volts ..... 1V to 500V
- ★ DC Current ..... 0.1mA to 0.2A
- ★ Resistance ..... 1Ω to 20MΩ
- ★ 3 1/2 digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

**FG-1a**

FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £30 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayden Developments, 21 Gladside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments  
21 Gladside, Bar Hill,  
Cambridge CB3 8DY  
Tel: (0954) 80285

Name \_\_\_\_\_  
Address \_\_\_\_\_

Please send:  
 DM-2 @ £5.45  
 FG-1a @ £4.95  
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

**JAYkits**

# 'TUSCAN' FROM TRANSAM



## Take a step up to your next Computer!

### THE CONCEPT

How many ways are there to build an S100 system? Not many, and all expensive. TUSCAN changes all that.

Five S100 boards on one single board — just for starters. Plus five extra slots for future expansion.

What a combination! Z80 and S100 with the TRANSAM total package of system and applications software.

How do we do it? Our prices start at £195 and you can build up in easy stages to a fully CP/M compatible disc based system. Something to think about!

### THE HARDWARE

The first Z80 single board computer with integral S100 expansion. British designed to the new IEEE (8 BIT) S100 specification, the TUSCAN offers total system flexibility. A flexibility available now.

The board holds the equivalent of a Z80 cpu card, 8k ram, 8k rom video and I/O cards with 5 spare S100 expansion slots and offers a price/performance ratio which is hard to beat.

Just compare our price with a commercial S100 ten slot motherboard with this specification.

### THE SOFTWARE

TUSCAN offers the user the choice of system monitor, editor, resident 8k basic, resident Pascal compiler or full CP/M disk operating system. All options are upwards

compatible and fully supported with applications software. Both 5¼" and 8" drives are supported in double density.

### THE PACKAGE

TUSCAN is available in kit form or assembled. With several hardware and software options to suit your requirements and budget. Attractive desk top case also available holds 2 x 5¼" Drives.

# TRANSAM

## NOBODY DOES IT BETTER!

Send to Transam Components Ltd., 59/61 Theobalds Road, WC1

I am interested in the TUSCAN Z80 based single board computer with S100 expansion and enclose a S.A.E. for further details.

Name \_\_\_\_\_

Address \_\_\_\_\_

Telephone \_\_\_\_\_

TRANSAM COMPONENTS LTD., 59/61 THEOBALDS ROAD, WC1. TEL: 01-402 8137. TELEX: 444198

WHAT WILL THEY THINK OF NEXT

NEW

CASIO'S NEW LCD ANALOGUE AND DIGITAL STOPWATCH 56 QS-508. COUNTDOWN 12/24 hr DISPLAY. R.R.P. (£39.95) £34.45  
**TIME DISPLAY.** Digital: Hours, minutes, seconds, AM/PM (optional 12 or 24 hour display) Analogue: Seconds.  
**TIME-CALENDAR DISPLAY.** Digital: Month, date, day, Analogue: Hour, minute.  
**STOPWATCH:** Measuring net, lap and first and second place times from 1/10 second to 59 minutes 59.9 seconds.  
**COUNTDOWN.** Measuring capacity 60 minutes, in 1/10 second units. Setting to 1 second Countdown can be stopped and restarted for net time measurement.  
**CALENDAR.** Auto 4 year. Case all stainless steel 8.3mm thick Water resistant. Mineral Glass Backlight. 2 year battery.  
 As above 56 QS-388 with chrome plated case. R.R.P. (£29.95) £24.45.

BEST BUYS

- 81 QS-358 ALARM CHRONOGRAPH. Stainless steel. Mineral glass. Water resistant. 8 year battery. Hours, minutes, seconds, day; and day, date, month and year. 12 or 24 hour display. 24 hour alarm, hourly chimes. Stopwatch from 1/100 second to 1 hour, net, lap and 1st and 2nd place times. R.R.P. (£34.95) £28.45
- 83 QS-40B as above with chrome plated case. R.R.P. (£29.95) £24.45
- 83 QS-41B ALARM CHRONOGRAPH. Stainless steel encased. Mineral glass. Water resistant. 3 year battery. Hours, minutes, seconds and date, AM/PM; or hours, minutes, alpha day, date, AM/PM. 24 hour alarm, hourly chimes. Stopwatch from 1/10 second to 12 hours; net, lap and 1st and 2nd place. Nightlight. R.R.P. (£29.95) £24.45
- 83 QGS-41B as above gold plated case and strap £29.45
- F.80 as 83DS-41B black resin strap and case, stainless steel back and front trim. R.R.P. (£24.95) £19.45 only

C.80 CALCULATOR WATCH

Finger touch keyboard. Hours, minutes, seconds, AM/PM, day, date, month auto calendar programmed to 2009. With 24 hour stopwatch; net, lap and 1st and 2nd place times. To 1/100 sec. Dual time. 8 digit calculator. Nightlight, water resistant, mineral glass, black resin case/strap. R.R.P. (£29.95) ONLY £24.45



NEW STAINLESS STEEL CASE/STRAP VERSION OF C.80. R.R.P. (£34.95) £29.45

ALL OTHER CASIO WATCHES EX. STOCK MOST MODELS

ALL OTHER CASIO CALCULATORS EX. STOCK MOST MODELS

CASIO Details. Send 20p for full details of Watches and Calculators. TERMS OF BUSINESS: Please note all CASIO items PRICE INCLUDES VAT, P&P and Insurance. Please send cheques or P.O.s or quote Access or Barclaycard No. to: B. BAMBER ELECTRONICS 24 hour phone service. (0353) 860185. Callers welcome Tues-Sat 9.30-5.30 pm.

NEW IT BRINGS MUSIC TO YOUR EARS AND EASY ON YOUR POCKET CASIO'S ML.90.

**CLOCK:** Hours, minutes, seconds, AM/PM  
**HOURLY TIME SIGNAL** Every hour on the hour.  
**CALENDAR** programmed to Dec. 31 1999, year, month and date.  
**ALARMS.** Alarm 1 buzzer (30 secs) or 7 different melodies. Alarm 2 buzzer (30 secs) or a fixed melody.  
**DATE MEMORY.** 1, 4 fixed melody, 2 two selectable melodies ie happy birthday, wedding march etc. Dec 24-25 Jingle Bells. Tunes programmed 12 popular melodies.  
**STOPWATCH.** Up to 9 hrs, 59 mins, 59 secs, and 9/10 of a second. Net, lap and 1st and 2nd place times  
**MUSICAL FUNCTION.** Manual or pre-programmed melody playing.  
**CALCULATOR** +/-/-x/-, automatic accumulation in four calculations. Memory, %  $\frac{1}{x}$ , 8 digits  
 1 year continuous battery life  
**IF YOU WANT MUSIC WHILE YOU WORK PLAY A ONLY £19.45** • Fine leatherette case ML.90, R.R.P. (£22.95)  
**ML 81 MUSICAL CLOCK CALCULATOR.** 2 musical alarms, countdown timer, stopwatch from 1/10 second to 12 hours. Net, lap, 1st and 2nd place Calculator with full memory +/-/-x/-, %  $\frac{1}{x}$ , 1 year batteries. R.R.P. (£25.95) £22.45  
**ML 71 as above with one melody alarm mini-card.** R.R.P. (£25.95) £22.45  
**ML 82 MUSICAL CLOCK CALCULATOR** with alarm, calendar, stopwatch, R.R.P. (£22.95) £19.95  
**AQ2200** permanent display of full month calendar, clock, alarm, hourly chimes, stopwatch from 1/10 second to 10 hours; net, lap 1st and 2nd place times. Calculator with full memory %  $\frac{1}{x}$ . One year battery. R.R.P. (£21.95) £19.45  
**AQ1500** similar to above without month display. No alarms. R.R.P. (£17.95) £14.45



CASIO'S LATEST SCIENTIFIC CALCULATORS

- FX8100 Hours, mins, sec, AM/PM, day, Calendar pre-programmed to 1999. 24 hour alarm. Alarm timer, interval timer, or 1/100 sec. Stopwatch; net lap and 1st, 2nd place times. Fractions, % cube roots, 5 levels of parenthesis, hyperbolics, standard deviations, co-ordinates, conversions. 48 scientific functions 1 year batteries. R.R.P. (£27.95) £24.45
- FX7100 as FX8100 only 30 scientific functions, 8 digits, 1 alarm. No hyperbolics, fractions, or calendar, 1 countdown alarm or 24 hour alarm. Hourly chimes. Mini card size. Complete with leatherette wallet. R.R.P. (£27.95) £24.45
- FX501P 11 memories and 128 programming steps, 10 digit. R.R.P. (£64.95) £52.95
- FX502P 22 memories and 256 programming steps, 10 digit. R.R.P. (£84.95) £72.95
- FA1 adaptor for 501P and 502P programme on to cassette tape. R.R.P. (£24.95) £18.95

- TRIO CS1566 20MHz triggered sweep oscilloscope. £339.00 + VAT
- TRIO CS1562A 10MHz triggered sweep oscilloscope £259.00 + VAT
- HAMEG oscilloscope HM307 LPS triggering bandwidth d.c. to 10MHz. Component tester. Timebase 0, 2 us-0, 2 s/cm. £149.00 + VAT
- HAMEG H236 switchable probe for HM307. £11.00 + VAT
- DACTRON PK40Z 13.8 DC 3 amp continuous 4 amp max Fully stabilised power supply with overload protection. £19.95 + VAT
- DACTRON PH 5000 13.8 DC 5 amp continuous. £39.50 + VAT
- DIN PANEL METERS DIN 75: 0-5 amps DIN 715: 0-150 volts DIN 730: 0-300 volts DIN 750: 0-500 volts 72 x 72 mm range £8.00 + VAT
- EAGLE DD7 paging microphone impedance 600 ohm or 50K ohms sensitivity 2.25mV at 50K ohms. Frequency response 300-900Hz, Desk or wall mounted. £14.85 + VAT
- EAGLE MULTI-METER EM50 50,000 DPV DC volts: 0-1200 volts AC volts 0-1200 volts DC current 0-6A resistance 0-10 Meg ohms. £19.95 + VAT
- DRAPER SUPER CHROME 1/4" sq drive socket sets, 33 piece 9 AF hexagon 3 AF 8i-sq sockets, 11 mm hexagon sockets 9 BA hexagon sockets 6 Access. £12.75 + VAT
- SPIRALUX AND DRAPER nut spanners and sets. Large selection Refer to catalogue or S.A.E. for full details.
- WELLER TCP3 tongs 24 volt series 3 wire power units. For application requiring earthed top. Also PU30 power units. TCP3 £13.84 + VAT PU30 £24.12 + VAT
- WELLER INSTANT HEAT GUNS Model No 81000 £13.21 + VAT
- WELLER CORDLESS Model No WC100 £25.47 + VAT
- SUPA SERVISOL Switch cleaner £0.72 + VAT
- MARYPLASS storage boxes 5P2 combination draw pack interlocking storage boxes (contains 1 x 600 2 x 501 5 x 101) Per Pack £4.40 + VAT
- DRYX DE SOLDER TOOLS Model SR3A desoldering pump with built in safety guard. Price £8.50 + VAT
- I.C. TEST CLIPS Clip over IC while still soldering to PCB or in sock. Gold plated pins. Ideal for experiments of service engineers. 28 pin DIL £1.76 40 pin DIL £2.00 or save buy one of each. For £3.50 + VAT
- I.C. AUDIO AMP P.C.B. Output 2 watts into 3 ohm speaker. 12V DC supply. Size approx 5 1/2 in x 1 1/2 in x 1" high with integral heatsink complete with circuit. £2.00 each + VAT

CALL IN AND SEE US OUR NEW SHOP IS OPEN

CATALOGUE 1999. Send 40p and you will receive our 104 page catalogue, products by Eagle, Yeasu, Standard, Trio, Hameg, Microwave, Modules, Amtron Kits & Boxes, Vero, Draper, Spiralux, Knipex, Weller, Servisol, Jaybeam, Books by Barnaro & Babani - Newnes and many more.  
 TERMS OF BUSINESS: Cheques, P.O.s or Phone Access or Barclaycard No. 24 hour phone service. Please add VAT AT 15% on all above goods. CARRIAGE and packing charges for all orders under £5.00 net invoice value add 75p. Orders over £5.00 and under £20.00 add 50p. Orders over £20.00 carriage free. Callers welcome 9.00 am-5.30 pm Tues-Sat. (0353) 860185.



B. BAMBER ELECTRONICS DEPT: PE 5 STATION ROAD LITTLEPORT CAMBS GBG 1QE

SOUTH EAST ENGLAND'S ELECTRONICS CENTRE

Interested in Electronics? Then why not pay us a visit and see our vast range of Test Equipment, Oscilloscopes, PSUs, Computer Equipment, Government Surplus, VDUs, ICs, Transistors, Relays, Motors, Bulbs, Cable Transformers, PCBs, Resistors, Amplifiers, etc., etc.

★ ★ ★ THIS MONTHS SPECIALS ★ ★ ★

ASR 33 TELETYPES  
 ASCII, RS 232, 110 BAUD  
 GOOD WORKING ORDER £235 PLUS VAT.

MINUTES OTHER PRINTERS  
 FROM ONLY £40

4116 16K 200ns RAMS  
 £28.50 FOR 8.

NE555 10 for £2.40. 741 10 for £1.80. 1N4004 18 for £1.00. 0.125" RED LEDS 12 for £1.00. 2N3055H (RCA) 4 for £2.25. 1S44/1N4148 50 for £1.00. Stock list 50p. Where P&P not shown please add 40p per order. Prices include VAT.

- ★ ELECTRONIC EQUIPMENT AND COMPONENTS PURCHASED FOR CASH
- ★ OPEN 9.30 TO 5.30 MONDAY TO SATURDAY
- ★ RETAIL AND TRADE
- ★ NO PARKING RESTRICTIONS
- ★ ACCESS & BARCLAYCARD



64-66 MELFORT ROAD  
 THORNTON HEATH  
 SURREY. 01-689 7702

<p><b>MULLARD CAPACITORS</b>                  Special purchase of factory clearance capacitors enables us to offer: C280 Polyesters (Liquorice Allsorts) at £2 for 100 mixed. And Miniature Electrolytics at £1.50 for 100 mixed. Pack of each only £3.                  These consist of spillages, floor sweepings, cosmetic imperfections etc. As we have no time to sort them they are magnificent value for the constructor.</p>	<p><b>MINIATURE MAINS TRANSFORMERS</b>                  Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250 MA 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY 90p. 3 for £2.20.                  2,200 <math>\mu</math>F 40V Radial. 1 1/2" x 2" 50p. 3 for £1.50.                  1,000 <math>\mu</math>F 100V Radial. 1 1/2" x 2" ONLY 70p. 3 for £1.50.</p>
<p><b>HUMIDISTATS</b>                  Don't Let Your Environment Dehydrate You!                  Buy our Honeywell Humidity Controller.                  Membrane actuated, very sensitive. 1/4" shaft. 250V. 3.75A Contacts. Ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost. 90p. ea. 3 for £2.</p>	<p><b>TRANSISTOR PACKS</b>                  100. Full spec, new and marked. Includes BC148, BC184L, MED412, 8F274, BC154 etc. £4.95                  200 as above and includes AC128, 2N3055, BFY50, BD131, BF200 etc. £9.95                  Buy bulk and save money, these packs are worth at least double.</p>
<p><b>20 ASSORTED ZENER DIODES</b>                  1 watt and 400mW. £1.50</p>	<p><b>P/B SWITCH BANKS</b>                  These cost a fortune! Were made for various music centres includes independent and interdependent latching types multi pole etc etc. Can be modified. Can't be repeated. 3 Banks for £1.</p>
<p><b>100 MIXED DIODES</b>                  Includes: Zener, power, bridge, germanium, silicon etc. All full spec. £4.95</p>	<p><b>BULK BARGAINS. STOCK UP FOR SUMMER</b>                  300 mixed 1/4 &amp; 1/2 watt resistors £1.50                  150 mixed 1 &amp; 2 watt resistors £1.50                  300 mixed capacitors, modern, most types £3.75                  100 mixed ceramic and plate caps £1.20                  400 mixed film resistors £2.85                  100 mixed polystyrene caps £2.20                  25 pots and presets £1.50                  25 presets, staforon etc. £1.20                  20 VDRs and thermistors £1.20                  100 Hi-wattage resistors wirewound at £2.75                  100 electrolytics, nice values £2.20                  300 printed circuit resistors £1                  300 printed circuit components £1.50</p>
<p><b>2" LED's</b>                  Red 4 for 50p. Green and Yellow 4 for 60p.</p>	<p><b>100K MINIATURE THUMBWHEEL SLIDER POTS</b>                  Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1.</p>
<p><b>ULTRASONIC TRANSDUCERS</b>                  Transmitter and receiver 40 kHz 14 mm dia. £3.25 pair.</p>	<p><b>MINIATURE LEVEL/BATT. METERS 200<math>\mu</math>A</b>                  F.S.D. as fitted to many cassette recorders 80p</p>
<p><b>MINIATURE REED SWITCHES</b>                  We are the cheapest! 12 for £1.00 100 for £4.20</p>	
<p><b>G.E.C. UHF TRANSISTOR TV TUNERS</b>                  Rotary type with slow motion drive, leads and aerial socket. £1.50 3 for £3.50 "for G.E.C. "2010" series etc."</p>	
<p><b>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS</b>                  Includes 150 sq. ins. copper clad F/G. board, 1 lb ferric chloride 1 dolo etch resist pen. Abrasive cleaner, Etch tray plus instructions. Special Price £4.95                  1 lb FE. C1. To mil. spec. £1.25                  5 lb FE. C1. To mil. spec. £5.00                  150 sq. in. Single sided board £2.00                  150 sq. in. Double sided board £3.00</p>	

50p P & P on all above items. Cheque or P.O. with order to:  
**SENTINEL SUPPLY, DEPT. P.E.**  
 149A BROOKMILL RD., DEPTFORD, LONDON, SE8

# New from Newnes Technical Books



## Practical Electronics Handbook

Ian Sinclair

A useful and carefully selected collection of standard circuits rules-of-thumb and design data.

Covers passive and active components, discrete component circuits and linear and digital i.cs.

Describes the volume and function of typical circuits whilst keeping mathematics to a minimum.

160 pages    216 x 138mm    £3.95    US\$9.00

Please send me Practical Electronics Handbook by Ian Sinclair 0 408 00447 9. Find £..... enclosed

Name .....

Address .....

.....

.....

PE980

## Newnes Technical Books

Borough Green, Sevenoaks, Kent, England.



## Wilmslow Audio

*THE firm for speakers!*

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

**WILMSLOW AUDIO (Dept. P.E.)**


**SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF**

Tel: 0625 529599

FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.

Tel: 0625 526213

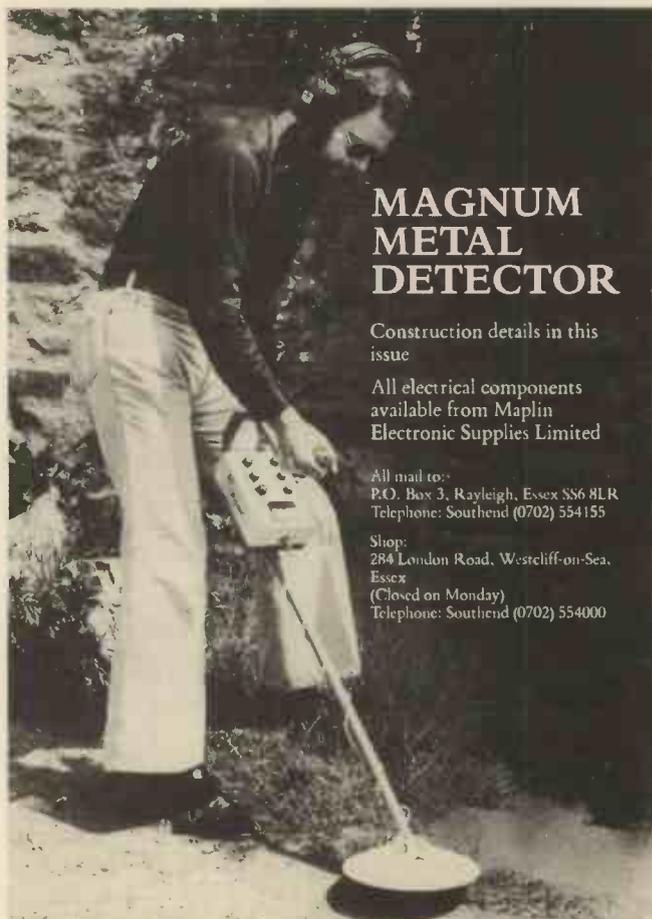(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS



## MAGNUM METAL DETECTOR

Construction details in this issue

All electrical components available from Maplin Electronic Supplies Limited

All mail to:  
P.O. Box 3, Rayleigh, Essex SS6 8LR  
Telephone: Southend (0702) 554155

Shop:  
284 London Road, Westcliff-on-Sea,  
Essex  
(Closed on Monday)  
Telephone: Southend (0702) 554000

# LIGHTING & AMPLIFIER MODULES FROM L & B



RING 01-689 4138



**LB31000SLC**  
**£29.90**




19 x 9.5 x 3cm.

**LB31000SL SOUND TO LIGHT. A SUPERB PERFORMING SYSTEM AT AN INCREDIBLY LOW PRICE.** 3 channels 1000w each. Fully fused. Very high input impedance. Operates from 1/2 to 300w sound input. Triac zero voltage triggering. Third order filters. Zero voltage fired. Master Vol/Bass/Mid/Treble controls.

**LB31000SLC SOUND TO LIGHT/CHASER.** THE MOST ADVANCED SOUND TO LIGHT MODULE AVAILABLE. WITH AUTOMATIC SWITCHING TO CHASE UPON ABSENCE OF A MUSIC INPUT.

3 Channels, 1000w each. Fully fused. Very high input impedance. Electronic filters. 5HZ to 70KHz bandwidth. Operates from 1/2 to 300w sound input. Triac zero voltage triggering. Master Vol/Bass/Mid/Treble/Chase speed controls.

**LB31000SL**  
**£21.40**

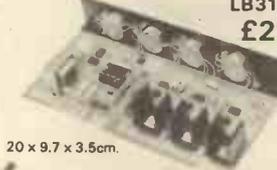

20 x 9.7 x 3.5cm.

**LB81000LC CHASER** A FULLY DIGITAL 8 CHANNEL CHASER, ALLOWING VARIATION OF CHASE SPEED AND CHASE RETURN DELAY.

1000w per channel. CMOS circuitry. Zero voltage fired. Can be footswitch triggered. Additional modules can be cascaded to form 16, 24, 32 chan etc.

**£26.50**

**LB81000LC**


19 x 9.5 x 3cm.

**LB41000LS SEQUENCER** LOGIC RANDOM SEQUENCER, WITH TWO SPEED CONTROLS OFFERING A WIDE RANGE OF EFFECTS.

4 channels, 1000w each. CMOS circuitry. Zero voltage fired.



**LB31000LD**

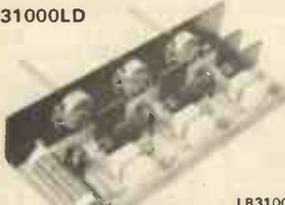

20 x 7.8 x 3.5

**POWER AMPS, 250, 150, 100 & 25W RMS. RUGGED TOUGH DEALING POWER AMP MODULES.** Full spec available in our catalogue.


LB250	LB150	LB100	LB25
10Hz TO 25KHz S/N 110dB THD 0.1% 0.5v SENS	10Hz TO 25KHz S/N 110dB THD 0.1% 0.5v SENS	10Hz TO 25KHz S/N 110dB THD 0.1% 0.5v SENS	20Hz TO 60KHz S/N94dB THD 0.07% 0.5v SENS
<b>£39.50</b>	<b>£26.50</b>	<b>£18.20</b>	<b>£11.20</b>

## PREAMPS

**LBPA3.** Complete stereo disco preamp system. Comprising of L&R deck mixers, mic mixer, deck and mic tone stages, mic auto fade over decks, PFL output drivers and its own regulators.

**LBPA2.** General purpose 4 chan. mixer/tone stage.

**LBPA1.** Stereo Hi-Fi System

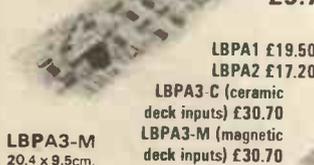

**LBPA1** £19.50  
**LBPA2** £17.20

**LBPA3-C** (ceramic deck inputs) £30.70  
**LBPA3-M** (magnetic deck inputs) £30.70

**LBPA3-M**  
20.4 x 9.5cm.

YOU REQUIRE A BOARD THAT'S MIGHTY COMPETITIVE, RELIABLE, MANUFACTURED FROM THE HIGHEST QUALITY COMPONENTS, OF HIGH PERFORMANCE, TESTED AND INSPECTED, SUPPLIED WITH CONNECTION AND CCT, DGM AND GUARANTEED. IN TWO LETTERS YOU REQUIRE L & B.

All prices shown are inclusive of VAT (15%) P/Packing 50p in the UK except power supplies (\*) Trade and Overseas inquiries welcome. For your FREE catalogue send a 12p stamp to:

**L & B** 45 WORTLEY ROAD  
WEST CROYDON  
SURREY CR03EB  
ELECTRONIC (PE) TEL. 01-689 4138

## NEW! LBAC01

3 channel active crossover module with 18dB boost control, to lift Bass mid or treble bands. Available with cross-over frequencies of 200 or 300 and 2k or 3kHz (please specify) - £17.90. LBPSU1 + 15v supply for LBAC01 - £6.20.

**ROPELIGHTS NOW AVAILABLE!** 8 metres in length Red/blue/green/yellow. R.R.P. £45 + 6.75 VAT. Complete control units with forward/reverse and automatic options from 2/sec to 2/min. R.R.P. £69 + 10.35 VAT.

## POWER SUPPLIES

Four types of powerful supply units for our power amps. Consisting of a varnish-impregnated mains transformer and rectifier board (fuse protected)

## LBRLD1

Relay delayed speaker connecting device, placed between Amp & Spk. **£5.70**

**LB250PS** £24.50 (p/p £1.70)  
**LB150PS** £18.00 (p/p £1.40)  
**LB100PS** £14.70 (p/p £1.40)  
**LB25PS** £11.20 (p/p £1.20)

## LB250PS



# ON SALE NOW!

## PE POPULAR PROJECTS... CONTENTS

### MOTORING

SOLID STATE CAR INSTRUMENTS by Michael Tooley B.A and David Whitfield B.A. M.Sc.

1. BATTERY VOLTAGE INDICATOR	2
2. REV COUNTER	7
3. AMMETER	10
4. ENGINE TEMPERATURE	13
5. DWELL METER	16
HAZARD WARNING AND CASCADING	18
HEADLIGHT WARNING by P. G. Wagstaff	21
AUTOMATIC CAR AERIAL by S. M. Bennett	26

### HOUSEHOLD

DIGITAL TEMPERATURE CONTROLLER by D. Coulls and P. McAlister	27
ULTRASONIC BURGLAR ALARM by G. Davies	32
HOME FREEZER ALARM by P. E. Chaplin	37

### PHOTOGRAPHIC

PE DIAMATIC by J. R. Ames B.Sc. and W. L. Blyth B.Sc.	40
DIGITAL EXPOSURE TIMER by John Becker	55

### MUSICAL EFFECTS

SMOOTH FUZZ by D. S. Gibbs and I. M. Shaw C. Eng. M.I.E.E.	62
PHASER by D. S. Gibbs and I. M. Shaw C. Eng. M.I.E.E.	65
GUITAR SOUND MULTIPROCESSOR by Dr. M. Sawicki and A. Kowalewski B.Sc.	69

### RADIO CONTROL

R. C. FAILSAFE by Tony Jenkins	85
--------------------------------	----

### TEST GEAR

WAVEFORM GENERATOR by Michael Tooley B.A and David Whitfield B.A. M.Sc.	88
PULSE GENERATOR by Michael Tooley B.A and David Whitfield B.A. M.Sc.	93

## PRACTICAL ELECTRONICS Publication...

With electronics playing such an important role in every aspect of modern living PE have pleasure in presenting the pick of some of its most popular projects in this 96-page book. Two of these projects are completely new, the remainder are as originally published in PE save for the incorporation of certain designer approved amendments or corrections.

Our new book *PE Popular Projects* is now on sale at newsagents and components stores; the contents of this book are shown above. The book costs £1.25 from retail outlets and is also available for £1.50, UK post paid or £1.80, overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

## PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L2 2DY  
SEMICONDUCTORS: Texas R1038 TO3 power trans. 50p. 741 8 pin 22p. NE555 24p. TAG4443 SCR 45p. 723 14 PIN REGS. 35p. AD 1612 MATCHED PAIRS 70p. 2N5062 SCR 18p. TL209 RED LEDS 10 for 75p. BD238 28p. BD438 28p. MPU131 P.U.T.'s 40v. 200mA. 375MMW 15p each. 2N3733 £1.75. Infra Red 0.2" LEDs 30p. Rectangular Red LED's 12p each. CA3020 I.C.'s 40p each.  
MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY. 6-0-6 100mA. 9-0-9 75mA. 12-0-12 50mA all 75p each. 12V 200mA 75p. 6V 500mA £1.10p. 0-6V-0-6V 280mA £1.30.  
PULSE TRANSFORMERS. 1:1 (GPO type) 30p. 1:1 plus 1 min. P. C. mounting 60p.  
MINIATURE SOLID STATE BUZZER. 33x17x15mm. output at 3 feet 70db, only 15mA drain, operating range 4-15VDC 75p each.  
LOUD BUZZER. 6-12 volts 63p. Rotary Alarm siren, 12VDC, Red plastic body and mounting bracket 68x75mm £4.50p.  
POCKET MULTIMETER. MODEL NH55 2,000 ohms per volt, 1,000 volts AC/DC, 100mA DC current, 2 resistance ranges to 1 meg £8.50p.  
SOLDER SUCKER. High suction/teflon nozzle, £4.85p.  
MURATA TRANSUDERS. 40KHz, REC/SENDER £3.50 pair.  
MOTORS. 3V model type 22p. 6V cassette motor £1.20p. Replacement 12VDC 8 track motors 65p. Ex. equip. 5-7 volt cassette motors 70p. Low rev. mains motor 240VAC motor with gearbox 2 1/2 RPM 75p.  
AMPHENOL COAX CONNECTORS. Plugs 47p. Sockets 42p. Elbows 90p. Reducers 13p. Back to back sockets 65p. Back to back plugs 65p.  
HIGH IMPEDANCE HEADPHONES, mono 2,000 ohms imp. transducer type, adjustable band and padded ear-piece £2.75.  
SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only £2.95p  
INTERCOM UNITS (can be used as baby alarm) supplied with approx. 60 cable, call button. 2 was £6.25 pair, 3 way £7.25p. WIRELESS INTERCOM, 2 units both operate on 240VAC and mains connected. AM frequency 180KHz, £29.95p.  
MINIATURE TIE PIN MICROPHONE. Omni, 1K imp., use deaf aid battery (supplied) £4.95p. LOW COST CONDENSER MIKE. Stick type, Omni, 600 ohms, on/off switch, standard Jack plug only £2.95p. EM607 CONDENSER MICROPHONE. Highly polished metal stick mike, uni directional, 600 ohms, 30-18KHz, on/off switch only £7.95p. DYNAMIC STICK MIKE. CARDIOD, dual imp., 600 ohms or 20K. 70-15KHz, attractive black metal case only £7.75p.  
PUBLIC ADDRESS HORN SPEAKERS. Suitable for outdoor use. 5" round 8 Watts, 8 ohms, adjustable bracket £4.95p, 6" 15 Watts 8 ohms adjustable bracket £8.25p.  
CRIMPING TOOL, for standard terminals also 6 gauge strip and wire cutter, insulated handles only £2.30.  
Cash with order please, official orders welcome from schools etc. please add 30p post and packing, VAT inclusive, SAE for latest illustrated stock list. ALL ORDERS DESPATCHED BY RETURN POST

# CHROMASONIC electronics

56 FORTIS GREEN ROAD MUSWELL HILL LONDON N10 3HN  
TELEPHONE 01-883 3705 01-883 2289

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS

## PETS

2001-8N (8K RAM)

**£399**

2001-16N (16K RAM) **£499**

2001-32N (32K RAM) **£599**

ALL WITH NEW KEYBOARD AND GREEN SCREEN.

### PERIPHERALS

Service & Assistance available.


Interfaces available are:

X-Y plotters, analogue to digital converter, 16 channel interfaces, bi-directional interfaces, etc.

EXTERNAL CASSETTE DECK SUITABLE FOR ALL PETS **£55**



NEW LOW PRICE

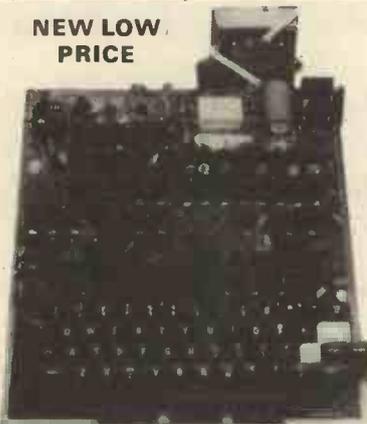

## UK101

**£179 in kit form**

**£229 ready built & tested**

**£249 complete in case**

NO EXTRAS REQUIRED

- \* FREE SAMPLER TAPE
- \* FULL QWERTY KEYBOARD
- \* 8K BASIC
- \* RAM EXPANDABLE TO 8K ON BOARD (4K INC)
- \* KANSAS CITY TAPE INTERFACE

\* New monitor allows full editing & cursor control.

**£22**

INVADER TAPE **£5.00**

ASSEMBLER EDITOR TAPE **£14.95**

## LATEST STOP PRESS AND PRICE LIST

SEND SAE OR PHONE FOR UP TO DATE PRICES OF ALL OUR RANGE OF ITEMS STOCKED.

### CASES

Available for UK101, Superboard, NASCOM. Approx. dim. 17" x 15" 435mm x 384mm

**Price £24.50**

Post and packing £1.50

### TAPES

Unique stackable tape storage unit. Interlocking drawers. 5 drawers each containing 2 C12 tapes.

10 drawers **£9.50**

5 drawers **£5.25**

Single drawer **£1.10**

### MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2114's. Each board has 16K RAM capacity.

Kit contains:

- \* On board power supply
- \* 4K EPROM expansion
- \* Fully buffered for easy expansion via 40 pin socket

\* **8K KIT £99.95**

\* **16K KIT £139.90**

### MEMORY

D. RAMS	£ p.
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	4.35
S. RAMS	
2102A	1.09
2102A-2	1.09
2112A	2.25
21L02	98
2114-4045	2.95
4035	1.07
4044-5257	6.93
BULK PURCHASE	
8 x 2114	22.50
8 x 4116	29.95
8 x 21L02	7.00
BULK PURCHASE	
16 2114	39.95
16 21L02	13.00
32 21L02	25.00
64 21L02	45.00

### EPROM'S

2708	4.95
2716 (5v)	13.95
2532	39.95

### ROM'S

2513(UC)	5.95
2513(LC)	5.95

### CPU'S

6502	9.50
8080	4.75
9900	25.95
6800	5.90
Z80	8.95

### BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	52
SN74366	52
SN74367	52
SN74368	52
8T26	1.75
8T28	1.75
8T95	1.57
8T96	1.57
8T97	1.50
8T98	1.57

### BAUD RATE GENS

MC14411	8.75
MM5307	8.75

### UARTS


AY-5-1013	3.45
AY-5-1015	3.98
MM5503	4.75
TMS 6011	3.55

### PRINTERS

**TX-80 £395**

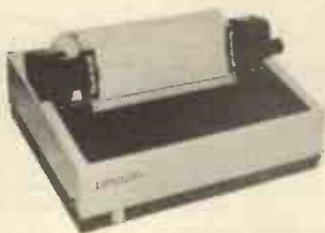**EPSON TX-80 £395**

Dot-matrix printer with Pet graphics Interface: Centronics parallel, options: PET, Apple and serial.



PLEASE ADD VAT 15% TO ALL PRICES. POSTAGE ON COMPUTERS, PRINTERS & CASSETTE DECKS CHARGED AT COST. ALL OTHER ITEMS P&P 30p. PLACE YOUR ORDER USING YOUR ACCESS OR BARCLAYCARD (Min. Tel. order £5.00). TRADE & EXPORT ENQUIRIES WELCOME, CREDIT FACILITIES ARRANGED.





# SMALL ADS

The prepaid rate for classified advertisements is 24 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £8.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

## RECEIVERS AND COMPONENTS

**TUNBRIDGE WELLS COMPONENTS.** Ballards, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquiries S.A.E.

**CLEARANCE PARCELS:** Transistors, Resistors, Boards, Hardware. 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75. BC108, BC171, BC204, BC230, 2N5061, CV7497 Transistors 10 70p, 100 £5.80. 2N3055, 12n for £3.50. S.A.E. Lists: W.V.E. (2), 15 High Street, Lydney, Gloucestershire.

**TURN YOUR SURPLUS** Capacitors, transistors, etc., into cash. Contact **COLES-HARDING CO.**, 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

**BOURNEMOUTH/POOLE.** Electronic components for the hobbyist, and friendly service. Why not pay us a visit. **H & H ELECTRICS LTD.**, 353 Ashley Road, Parkstone. 742643.

## MODULAR SENSOR SYSTEMS

**SPEED SENSOR** £10.95  
**FLOW SENSOR** £13.65

### Signal processing/display systems:

**Gal/Hr** PCB and 4 digit display without case requires 5V DC 400 cycles input time base £34.80

**RPM** PCB and 4 digit display without case requires 5V DC, 320 c/sec time base input £35.95

**Total Galls** Complete system in case with reset. £29.95

**Total Litres** 12V DC power supply. £29.95

**MPG, Km/L** Complete system in case. £44.75

**All above prices include VAT, p&p UK.** These systems are ideally suitable for automotive and other speed/flow measurement projects.

## ENVIROSYSTEMS LTD.,

Hampsfell Road, Grange-over-Sands, Cumbria LA11 6BE.  
Telephone: 044 84 4233/4

## BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
0.47, 1.0, 2.2, 4.7 & 10 Mfd. — 5p.  
22 & 47 — 51p. (50V — 6p). 100 — 7p. (50V — 8p).  
220 — 8p. (50V — 10p). 470 — 11p. (40V — 16p).  
1000/16V — 15p. 1000/25V — 18p. 1000/40V — 35p.

**Subminiature bead tantalum electrolytics.** — 14p.  
0.1, 0.22, 0.47, 1.0 & 35V. 4.7 & 6.3V. — 15p.  
2.2/35V. 4.7/25V — 15p. 10/25V. 15/16V — 20p.  
22/18V. 33/10V. 47/6V. 68/3V & 100/3V — 30p.  
15/25V. 22/25V. 47/10V — 35p. 47/16V — 80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
2% 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.  
10% 390 pf. to 4700 pf. — 4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.

**Polystyrene E12 Series. 63V. Horizontal Mtg.**  
10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
0.1 to .068 — 4p. 1 — 5p. 15, 22 — 6p. 33, 47 — 10p.  
.68 — 12p. 1.0 — 16p. 1.5 — 22p. 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
.001, .0022, .0047 — 3p. .01, .022, .04 — .04, .05, 0.1 — 6p.

**Miniature Film Resistors Highgate. E12 Ser. 5%.**  
0.125W mixed carbon/metal 10Ω to 1MΩ — 1p.  
0.25W Carbon 10Ω to 10MΩ (10% over 1MΩ) — 1p.  
(E24 Series av. in 1W C. Film 10Ω to 5MΩ).

0.25W, 0.5W & 1.0W Metal Film 10Ω to 2MΩ — 2p.  
1N4148 — 3p. 1N4002 — 4p. 1N4006 — 6p. 1N4007 — 7p.  
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7 — 10p.  
8 Pin i.c's. 741 Op. amp. — 18p. 555 Timer — 24p.  
Dil Holders 8 pin — 9p. 14 pin — 12p. 16 pin — 14p.  
LED's. 3 & 5mm. Red — 10p. Green & Yellow — 14p.  
Grommets for 3mm. — 1p. 2 p.c. holders 5mm. — 2p.  
20mm. O.B. Fuses 15, 25, 5, 1, 2, 3 & 5A — 3p.  
20mm. Anti Surge 100mA. — to 5.0A — 5p.  
0.2mm. Fuseholders P.C. or Chassis Mtg. — 6p.  
Solid A1. knobs 15mm. — 25p. 25mm. — 30p. 30mm. — 50p.  
400mW Zener diodes E24 series 2V7 to 33V — 8p.

Prices VAT inclusive Post 15p. (Free over £5.00).

## THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S80RN.

**POTENTIOMETERS.** Resistors, D.I.L. Sockets-Quality Components at Keen prices. Send Large S.A.E. for lists. T. Milner. 203 Goodman Park, Slough, Berkshire SL2 5NP.

**100 DIODES 85p. 50 Transistors 95p. 10 I.C.s 75p.** All mixed. Post Paid. Lists 15p. Sole Electronics, (P.E.) 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

**100. ASSORTED COMPONENTS 115p.** 100. assorted resistors 60p. 100. assorted capacitors 150p. 50. reed switches 200p. 10. mains neons 50p. 10. Micro Switches 150p. Add 25p P&P. DURRANTS, 9 St. Mary's Street, Shrewsbury, Salop.

## MISCELLANEOUS

**UK 101 SOFTWARE.** Try our original programmes (on cassette) **GRAPHIC PAINT BRUSH-GRAPHIC PLOTTER** etc. Working programmes that will give you ideas of your own. S.A.E. M & B SERVICES, 182a, High Street, Margate, Kent.

**PRINTED CIRCUIT BOARDS.** Glass Fibre tinned & Drilled, Prototypes to batch runs. Quick turn-round, competitive prices. Send S.A.E. for quotations. R.D. ELECTRONICS, 12, Whiteoaks Road, Oadby, Leicester. 0533 716273.

## GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble bass, overdrive, 12 months guarantee. Unbeatable at £48, 60 watt £39; 200 watt £85; 100 watt twin channel sep. treble/bass per channel £51; 60 watt £50; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £98; slaves 100 watt £34; 200 watt £50; fuzz boxes, great sound £10.00; bass fuzz £10.90; overdrive fuzz with treble and bass boosters £20.00; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £98; twin channel £108; bass combo £108; speakers 18in. 100 watt £38; 12in. 100 watt £23; 60 watt £16; microphone Shure Uridyne 8 £28.

Send cheque or P.O. to:

**WILLIAMSON AMPLIFICATION**  
62 Thorncliffe Avenue, Dukinfield, Cheshire.  
Tel: 061-308 2064

**LOGIC ANALYSER/PULSE CATCHER** in kit form £8.75 inc. p & p. **TARGET A** variable speed game to test your reactions in kit form

£9.75 inc. p & p.

Both projects supplied with full instructions and high quality glass fibre tinned P.C.B.'s.

## HERTS ELECTRONICS,

16 Dunlin Road, Hemel Hempstead, Herts HP2 6LU.

**DIGITAL WATCH BATTERIES,** any sort 75p each + p.p. Send S.A.E. or 15p with number or old battery to Disclec, 511 Fulbridge Road, Werrington, Peterborough PE4 6SB.

## BUILD YOUR OWN PROJECTS!

from, our Electronic Construction Kit Oats Sheets.

Complete sets of plans now available for:-

ECK 2 - 8 trans U/VHF Multiband radio £2.00

EV 6 - 6 trans MW/LW radio £9.25+p.p. £1.50

Pocket 5 - 8 trans MW/LW radio £1.75

Air Converter Unit - range up to 100 miles £2.50

Edu-Kit Major - 15 super projects £2.00

SKB 2 - 2 band 8 trans SW radio £2.00

RK 1 - 8 trans multiband radio £3.00

RK 3 - 13 trans VHF/AM 9 wavebands £3.00

Post and packing for each of the above 25p

**Global Special Introductory Offers**

Car radio. Five push button MW/LW £16.40 p.p. £1.75

Car radio. Manual tuning MW/LW +SP £9.25+p.p. £1.50

Car Speaker stereo set. 4 ohms 5 watts £3.95+p.p. £1.50

Electric car aerial £8.26+p.p. £1.25

Car Cassette Radio. AM/FM/MPX £31.95+p.p. £2.00

Sharp LCD Calculators 6 functions & MEM £6.95+ p.p. 85p

Cheques and P.O.'s made payable to

**GLOBAL ELECTRONIC ENTERPRISES**  
St. John's Works, St. John's, Bedford, Beds.  
Free catalogue sent with order or on request with s.a.e.

## NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state **Transmitter-Receiver Kit**. Only £12.95 plus 35p P. & P. "Brain-Freeze" 'em with a **MINI-STROBE** Electronics Kit, pocket-sized "lightning flashes", vari-speed, for discos and parties. A mere £5.95 plus 35p P. & P. Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher: ready-made multi-function modules £6.85 each plus 35p P. & P. **LOTS MORE!** Send 30p for lists. Prices include VAT.

## BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh Ewell, Surrey (P.E.)

**BURGLAR ALARM EQUIPMENT.** Latest Discount Catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

**CLEARING LABORATORY:** scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

## CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No  
100 ALARM TRIGGER MODULE, 100% Solid State. Battery operation, Pos & Neg Rings, N/C for 4-wire contacts N/D for Mats etc. One Amp switching capacity. Only £9.95p  
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT + matching magnet. £1.10p  
220 Surface 4-wire MAGNETIC REED CONTACT £1.50p  
240 PRESSURE MAT, Standard Size 4-wire 30" x 15" £2.20p  
250 PRESSURE MAT, Stair Size 4-wire 23" x 61" £1.73p  
260 VIBRATION DETECTOR, Pendulum Type in Ivory Case with contacted Lid + self-adhesive backing. Adjustable Sensitivity £3.50p  
380 SIX INCH UNDER DOOR BELL £3.95p  
390 BEST QUALITY BELL HOUSING, P.V.C. coated Metal, not to be confused with cheaper decoy covers. Fully Sign Written with our Centurion insignia £9.50p  
400 DECOY P.V.C. BELL COVER £6.60p

Note: All Equipment Operates on 12 Volts DC

**710 SCOOP Offer SMOKE ALARMS, Self-Contained Ionisation Type (1.5% obscuration) With Low Battery Warning at the UNREPEATABLE PRICE OF ONLY £8.75p While Stocks Last!!!**

No Minimum Order. Access telephone

Orders welcome on 0484-3527 or Send

S.A.E. for Full List to

WE welcome Access



**CENTURION ALARMS ELECTRONIC SALES.**  
Dept. PE, 265 Wakefield Rd., Huddersfield, W. Yorks, HD5 9BE.

## TIME WRONG?

**MSF CLOCK** is ALWAYS CORRECT - never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and leap year, also parallel BCD output for computer and can record when an event occurs, receives Rugby time signals, built-in antenna, 1000K range, now get ABSOLUTE TIME - always £54.80.

**SIG. GEN.,** 10Hz-200KHz, logic and variable sine and square wave outputs, of harmonics, £12.80.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, money back assurance so SEND off NOW.

## CAMBRIDGE KITS

45 (FJ) Old School Lane, Milton, Cambridge.

**MAKE YOUR OWN PRINTED CIRCUITS**  
Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £1.60. Large range of single sheets in stock at 34p per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.80. Drafting film (30 x 21cm) 22p per sheet.

17p stamp for lists and information. P&P 30p/order

**P.K.G. ELECTRONICS**  
OAK LODGE, TANSLEY, DERBYSHIRE.

**PRACTICAL ELECTRONICS P.C.B.'s**

Professional quality glassfibre, Fry's roller thinned and drilled.

For full list and current pcb's please send SAE. Pcb's also produced to customers own masters. Trade enquiries welcome. Please write for quote.

**PROTO DESIGN**

14 Downham Road, Ramsden Heath  
Billericay, Essex CM11 1PU  
Telephone 0268-710722

**THE SCIENTIFIC WIRE COMPANY**  
PO Box 30, London E.4

**ENAMELLED COPPER WIRE**

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 40	3.40	2.00	1.10	0.80
41 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

**SILVER PLATED COPPER WIRE**

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

**TINNED COPPER WIRE**

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices include P&P, VAT and wire Data.

SAE for list. Dealer enquiries welcome.

Reg office 22 Coningsby Gardens.

**Cabinet and Flightcase Fittings**

Fretcloths, Coverings, Handles, Castors etc., Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilar Compression Drivers, AKG Mics, Celestion Speakers, ASS, Glassfibre Horns.

Send 30p postal order for illustrated catalogue to:-

**ADAM HALL (P. E. SUPPLIES)**

Unit G, Carlton Court, Grainger Road,  
Southend-on-Sea, Essex SS2 5BZ.

**RYDER ORGAN SYSTEM**

The W.W. classical design for full-size keyboards, including couplers. Expanded range of units now includes chorus, vibrato, combination stop-control and a new reverb. Data, p.c. boards, from:

**HIYKON LTD. (P.)**

Woodside Croft, Ladybridge Lane,  
Bolton BL1 5ED.

**ENAMELLED COPPER WIRE**

SWG	1 lb	1/2 lb	1/4 lb
10-19	2.95	1.70	0.85
20-29	3.05	1.75	0.95
30-34	3.45	1.90	1.00
35-40	3.75	2.10	1.15
41-43	4.95	2.75	2.15
44-46	5.90	3.50	2.40

FREE WIRE TABLES WITH EACH ORDER.

**INDUSTRIAL SUPPLIES**

102 Parrswood Road, Withington,  
Manchester 20.

Prices include P&P in UK.

**ULTRASONIC TRANSDUCERS.** £2.85 per pair + 25p P&P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/Packing 60p. **WHITE HOUSE ELECTRONICS, P.O. Box 19, Castle Drive, Penzance, Cornwall.**

**SEEN MY CAT?** 5000 Odds and ends. Mechanical. Electrical. Cat free. Whiston Dept. PRE, New Mills, Stockport.



Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c.boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills.

All immediately available.  
Catalogue 15p stamps please to:

**RAMAR CONSTRUCTOR SERVICES,**  
Masons Rd. Stratford on Avon  
Warwks. CV37 9NF 0789-4879

**SOUND-EFFECTS & MUSIC** FOR UK101, PET, SUPERBOARD, NASCOM

Add phasers, explosions, music and other effects just like the professional arcade machines, to your own programs. Controlled by simple poke statements or if desired in machine code, this 3 channel synthesizer can produce almost any sound. Using stereo output and carefully designed hardware truly dynamic effects can be created using a minimum of processor time. The unit also includes 2 8-bit parallel I/O ports for control/monitoring/keyboard scanning applications. Complete built and tested with demonstration program and instructions. Send S.A.E. or phone for details. Sample of sounds on C12 data cassette with details 55p inc.

EX STOCK **£45** ALL INC.  
**Easicomp** 0508 - 46484 Ltd. Day or Evening  
57 Parana Court, Sprowston, Norwich.

7 SEGMENT LED's at low cost 0.3in, RH decimal, common cathode. FND70 series. Base diagram included. £2 plus SAE for three. F. Rose, 33, Wallace Drive, Eaton Bray, Beds.

**UK101 Hardware:**

**Programmable Sound Generator**

Add another dimension to your UK101. We will supply the P.C.B. list of parts, Hardware and Software Instructions and Software on tape. All for only £9.50.

**UK101 Software on Tape:**

Our most popular programs: 4K Alien Invaders; 8K Home Finance. Our latest program: 8K Asteroid Runner, and our other firm favourites: 4K Snakes and Ladders; 4K Fruit Machine; 4K The My-my Game; 4K Drawing Machine. £3.00 each or £5.00 for any two including P&P. Cheque or P.O. or just S.A.E. for details to MaricK Dept. 12, 1 Branksome Close, Paignton, S. Devon TQ3 1EA.

**DIGITAL WATCH BATTERY REPLACEMENT KIT**



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, also one doz. assort. push pieces, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send £9.00 for complete kit and get into a fast growing business. Prompt despatch.

**BOLSTER INSTRUMENT CO. (PE16)**

11 Percy Avenue, Ashford, Middx. TW15 2PB.

**SUPERB INSTRUMENT CASES BY BAZELLI,** manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low £1.05. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.

**PLEASE MENTION PRACTICAL ELECTRONICS WHEN REPLYING TO ADVERTISEMENTS.**

**EDUCATIONAL**



**NORTH CHESHIRE COLLEGE**  
**SERVING THE COMMUNITY**  
**2 'A' LEVEL PASSES? WHAT NEXT?**

We can offer you a pleasant campus MIDWAY BETWEEN LIVERPOOL AND MANCHESTER...

A Study bedroom of your own... A Friendly Social Life...

And we still have places on our UNIVERSITY OF MANCHESTER VALIDATED B.A. and B.Ed. COURSES.

**B.A. (Combined Humanities)** Subjects on offer: Audio-Visual Communications, English, Environment, Sociology, Physical Education, Theatre Studies.

Nearly all combinations of two of these subjects are possible. The most popular combinations result in the following programmes:-

LITERATURE AND THEATRE STUDIES

MEDIA AND COMMUNICATIONS

RECREATION AND ENVIRONMENT.

**B.Ed. WE OFFER TWO THREE YEAR COURSES:-**

Primary School Teaching

Secondary School Teaching in either English, Environmental Studies or Physical Education

(Supporting studies in some shortage subjects are available)

**A FOURTH YEAR STUDY COULD LEAD TO THE B.Ed. (Hons) DEGREE.**

For further information and application forms contact:-

**ADMISSIONS (PLET),**  
**North Cheshire College,**  
**Padgate Campus,**  
**Fearnhead,**  
**Warrington WA2 0DB.**  
**Telephone: Padgate 814343.**

# TV & COMPUTER SYSTEMS SERVICING

**18 MONTHS full-time Modular Diploma course to include a high percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO-TV & CCTV
- COLOUR TV & VCR
- DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS

Each of the above Modules are 12 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £360 per Module. - Computer Module £450.

Next session starts September 15th.

(Also available 2½ year course in Marine Electronics & Radar.)

Prospectus from:

## LONDON ELECTRONICS COLLEGE

Dept: PEA9, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Y272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Y272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Y272 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### FOR SALE

NEW BACK ISSUES of "Practical Electronics" available 80p each Post Free. Open P.O./Cheque returned if not in stock - BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

UK 101 CASED & ASSEMBLED with colour graphics, 8K RAM manual and cassettes £350 o.n.o. Tel. 0767 317550 or 0767 317317.

### SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

### SITUATIONS VACANT

**INDUSTRIAL ELECTRONICS:** Are you an Electronic Test Technician or Service Mechanic? Have you had an apprenticeship followed by at least 5 years recent practical experience with a manufacturing or servicing organisation? If so we can offer you employment as an INSTRUCTOR, with good promotion opportunities and pensionable security at Gloucester, Bristol, and Swindon skillcentres. Starting salary £6,000 p.a. rising by two increments to £7,110 p.a. For more information contact Miss A. Curran, M.S.C. T.S.D. 11, Park Place, Clifton, Bristol, Telephone Bristol 20661.

**INDUSTRIAL ELECTRONICS:** Are you an Electronic Wireman/Tester or Prototype Wireman? Have you had an apprenticeship followed by at least 5 years recent practical experience? If so we can offer you employment as an INSTRUCTOR, with good promotion opportunities and pensionable security at Bristol, and Swindon skillcentres. Starting salary £6,000 p.a. rising by two increments to £7,110 p.a. For more information contact Miss A. Curran, M.S.C. T.S.D. 11, Park Place, Clifton, Bristol, Telephone Bristol 20661.

### BOOKS AND PUBLICATIONS

ANY REQUESTED SERVICE SHEET £1 + Large S.A.E. Full repair data any named TV £5.50 (with circuits, layouts etc. £7). SAE brings newsletter, bargain offers, etc. AUSPEL, 76 Church St, Larkhall, Lanarks ML9 1HE.

BOOKS. BOOKS. BOOKS. - Large range of Electronic Books in stock. Send S.A.E. for list. Servio Radio, (Dept PE9), 156/8 Merton Road, Wimbledon, SW19 1EG.

# FLADAR TRANSFORMERS

PRIMARY 0-240V 50Hz

SEND FOR OUR TRANSFORMER CATALOGUE PRICE £1.00 WHICH INCLUDES A 50p VOUCHER OFF YOUR FIRST PURCHASE.

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
06FE06	6+6	0.5A EACH	1.99	60p	06FE60	15-0-15	0.4A	1.95	60p
12FE06	6+6	1A EACH	2.66	75p	08FE40	8-0-8	1A	2.35	60p
20FE06	6+6	1.6A EACH	3.36	75p	08FE60	15-0-15	0.6A	2.30	60p
50FE06	6+6	3A EACH	4.02	90p	12FE40	9-0-9	1.5A	2.60	75p
60FE06	6+6	4A EACH	5.03	125p	12FE50	12-0-12	1A	2.60	75p
					12FE60	15-0-15	0.8A	2.60	75p
06FE09	9+9	0.3A EACH	1.99	60p	20FE50	9-0-9	2A	3.30	75p
08FE09	9+9	0.5A EACH	2.40	60p	20FE60	15-0-12	1.6A	3.30	75p
12FE09	9+9	0.7A EACH	2.66	75p	20FE70	15-0-12	1.2A	3.30	75p
20FE09	9+9	1A EACH	3.38	75p	20FE80	20-0-20	1A	3.30	75p
50FE09	9+9	2.5A EACH	4.02	90p	20FE100	30-0-30	0.6A	3.30	75p
60FE09	9+9	3A EACH	5.03	125p	50FE50	9-0-9	5A	4.00	90p
					50FE70	15-0-15	3A	4.00	90p
06FE12	12+12	0.2A EACH	1.99	60p	50FE80	20-0-20	2A	4.00	90p
08FE12	12+12	0.3A EACH	2.40	60p	50FE110	30-0-30	1.4A	4.00	90p
12FE12	12+12	0.8A EACH	3.36	75p	60FE70	15-0-15	4A	5.00	125p
50FE12	12+12	1.8A EACH	4.02	90p	60FE80	20-0-20	3A	5.00	125p
60FE12	12+12	2.5A EACH	5.03	125p	60FE100	28-0-28	2.2A	5.00	125p
80FE12	12+12	3A EACH	6.20	125p	60FE110	30-0-30	3A	5.00	125p
06FE15	15+15	0.2A EACH	1.99	60p	80FE40	12-0-12	6A	6.15	125p
08FE15	15+15	0.25A EACH	2.40	60p	80FE50	15-0-15	5A	6.15	125p
12FE15	15+15	0.4A EACH	2.66	75p	80FE60	20-0-20	4A	6.15	125p
20FE15	15+15	0.6A EACH	3.36	75p	80FE80	28-0-28	2.5A	6.15	125p
50FE15	15+15	1.2A EACH	4.02	90p	80FE70	24-0-24	3A	6.15	125p
60FE15	15+15	2A EACH	5.03	125p	80FE90	30-0-30	2.3A	6.15	125p
80FE15	15+15	3A EACH	6.20	125p					
					90FE80	15-0-15	5A	6.30	150p
06FE20	20+20	0.15A EACH	1.99	60p	90FE80	28-0-28	3A	6.30	150p
12FE20	20+20	0.25A EACH	2.66	75p	90FE90	30-0-30	3A	6.30	150p
20FE20	20+20	0.5A EACH	3.36	75p	100FE50	15-0-15	4A	6.60	150p
50FE20	20+20	1.2A EACH	4.02	90p	100FE26	26-0-26	3.5A	6.60	150p
60FE20	20+20	1.5A EACH	5.03	125p	100FE28	28-0-28	3A	6.60	150p
80FE20	20+20	2A EACH	6.20	125p	100FE30	30-0-30	3A	6.60	150p
					100FE36	36-0-36	3A	6.60	150p
					150FE15	15-0-15	6A	8.20	160p
					150FE26	26-0-26	5A	8.20	160p
					150FE30	30-0-30	4A	8.20	160p
					150FE36	36-0-36	4A	8.20	160p
					150FE42	42-0-42	3A	8.20	160p
					250FE28	28-0-28	8A	9.02	200p
					250FE30	30-0-30	7A	9.02	200p
					250FE42	42-0-42	5A	9.02	200p

#### BATTERY CHARGER TRANSFORMERS

48FE12	0-8-12	4A	5.00	125p
68FE12	0-8-12	5A	5.80	125p
70FE12	0-8-12	5A	6.15	150p
90FE12	0-8-12	8A	7.40	150p
06FE30	6-0-6	1.5A	1.95	60p
06FE40	9-0-9	0.5A	1.95	60p
06FE50	12-0-12	0.5A	1.95	60p

FLADAR ELECTRIC  
SOUTHVIEW DRIVE  
P.O. BOX 19  
WESTCLIFF-ON-SEA  
ESSEX O702-613314


TRADE ENQUIRIES  
WELCOME

PAYMENT TERMS:  
C.W.O. Cheques,  
Postal Orders  
All Prices include 15% V.A.T.

### AT BLINKIN' LAST
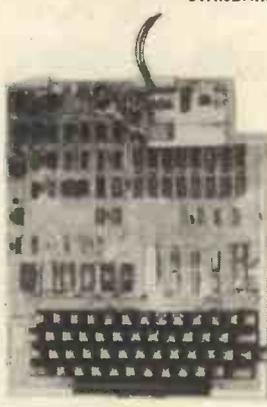
## COLOURBOARD II

THE NEW 50HZ COLOUR VERSION OF OHIO SCIENTIFIC'S SUPERBOARD II IS HERE AND LIKE A TON OF BRICKS DOWN CRASHES THE PRICE OF STANDARD SUPERBOARD II



50HZ UK BLACK AND WHITE SUPERBOARD II £159.95+15% VAT POST FREE.  
COLOURBOARD II £205 + 15% VAT.

THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST

- ★ If bought with superboard or colour board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit £7.95 (£11). 4K extra ram £20 (£24). Case £23 (£26). Cassette recorder £13 (£15). Colour Conversion Board £45 (£45). Super Print 800MST printer £399 (£399).

#### BATTERY ELIMINATOR KIT

100ma radio types with press-stud connectors 4.1v £1.49, 6v £1.49, 9v £1.49, 4½+4½v £1.92, 6+6v £1.92, 9+9v £1.92. Stabilized TTL computer supply 5v 2A £7.44, 5v 4A £12.60. Stabilized 8-way types 3/4 1/8 7/8 1/2 1/15 1/8v 100ma £2.60, 1A £6.50, 2A £9.84. Stabilized variable voltage models 2-18v 100ma £2.60, 1-30v 1A £6.75, 1-30v 2A £12.10, 12v car converter 6/7 1/2 9v 1A £1.35.

#### BATTERY ELIMINATORS

3-way switched type with 4-way multijack 6/7 1/2 9v 300ma £3.14. 100ma radio models with press-stud connectors 9v £3.77, 9+9v £4.99. Fully stabilized model 3/8 7/8 9v 400ma £6.50. Car converter 12v dc input, output 3/4 1/8 7/8 9v 12v 800ma £2.78.

#### SINCLAIR (THANDAR) PRODUCTS



SC110 10MHz oscilloscope (illustrated) £144.95. PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, mains adaptor £6.88. PDM35 £34.23, mains adaptor £4.20, case £2.07. DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models: rechargeable batteries £7.95, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95. TG105 pulse generator £87. Bench frequency counter £150.

### SWANLEY ELECTRONICS

Dept. PE, 32 Gosdale Rd., Swanley, Kent BR8 8EZ.  
Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13%. Official credit orders welcome.

## BUILD A SYNTHESISER!

SPECIAL SKILLS  
SPECIAL EQUIPMENT REQUIRED



Using **Dewtron** (Reg'd)  
PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules. Also "Mister Bassman" Bass Pedal Units. Send 35p for Musical Miracles Catalogue NOW!

**DESIGN ENGINEERING (WOKINGHAM) LTD.**  
254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR.

**QUALITY REEL TO REEL & CASSETTE TAPE HEADS + MECHANISMS**

**POPULAR UNIVERSAL CASSETTE TAPE HEADS**

B12-01 Mono Playback.....	£1.89	C42RPH04 Stereo GLASS FERRITE R/P.....	£11.60
B12-02 Mono Record/Playback.....	£4.02	C42RPS18 Stereo TWIN GAP R+P.....	£25.21
B24-01 Stereo Playback.....	£3.30	E12-09 Mono/Stereo erase.....	£ 1.85
B24-02 Stereo Record/Playback.....	£6.66	B22-02 Twin 1/2 track R/P.....	£ 5.97
B24-07 Stereo R/P, (Dolby Stm).....	£7.87	C44RPH03 Quad 1/2 track R/P.....	£13.17
C42RPH20 Stereo SENDUST R/P.....	£9.28	C44RP2ESD1 Quad 1/2 track combined R/P + Erase.....	£26.45
C42RPIESD1 Stereo combined R/P + Erase.....	£10.93	C22ESD2 Twin half track erase.....	£ 4.72

SEND FOR OUR FULL CATALOGUE 50p including P. & P.

**MONOLITH**

THE MONOLITH ELECTRONICS CO. LTD.  
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER

ALL PRICES INCLUDE VAT

## FUEL ECONOMY in kit form



**FUELSTRETCHER**, the leading UK in-car petrol computer, now available in kit form to save £££££'s from start to finish.

You have a choice from two kits:

**FSX20** gives accurate instantaneous digital mpg readings to obtain maximum fuel economy. Standard features include choice of two update frequencies, automatic clear down under idling and owner calibration facility.

**FSX10** gives a digital gallons used reading to allow determination of total fuel and average mpg.

Kits are complete with all necessary components and comprehensive instructions. All components guaranteed for 12 months, full technical back-up services available.

ENVIROSYSTEMS LTD., Dept. PE,  
Hampfell Road, Grange-over-Sands, Cumbria, LA11 6BE.  
Tel: 044 84 4233/4

Name .....

Address .....

Phone your order with Access or Barclaycard

	inc. VAT & p&p.	Qty Rqd.	I enclose cheque/ POs for £ .....
FSX20	£47.50		Cheque No. ....
• PI option	£65.90		* Petrol Injection
FSX10	£34.80		

## Summertime Special Offers

A further



All our normal discount prices



A further



All our normal discount prices for **ALARM CHRONOGRAPHS** and **CALCULATOR WATCHES**

**OFFER CLOSES  
SEPTEMBER 6th 1980  
SUBJECT TO AVAILABILITY**

Send 25p for our illustrated catalogue

Our normal service is **BY RETURN OF POST**. However in anticipation of heavy demand, please allow up to 14 days for delivery.

### TEMPUS

Tempus (Dept. PE)  
FREEPOST, 164-167 East Road  
Cambridge CB1 1BR. Tel. 0223 312866

**BAKER 50 WATT AMPLIFIER**

£69



Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.

**BAKER 150 Watt AMPLIFIER 4 Inputs £89**

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Printed circuit and components Post 50p £3.25

**STEREO PRE-AMP KIT.** All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95

**R.C.S. SOUND TO LIGHT DISPLAY MK 2**

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi £18 and all Disco Amplifiers. Cabinet extra £4.50. Post 50p 200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4, or 12 for £5.50

**MAIN TRANSFORMERS Primary 240V A.C. ALL POST 99p**

250-0-250V 70mA, 6-5V, 2A.....	£3.45
250-0-250V 80mA, 6-3V 3-5A, 6-3V 1A.....	£4.60
330-0-330V 200mA, 6-3V 3V 2A, 6-3V 2A.....	£10.00
300-0-300V 120mA, 2x6-3V 2A C.T., 5V 2A.....	£2.50
220V 45mA, 6-3V 2A.....	£2.50
<b>GENERAL PURPOSE LOW VOLTAGE.</b>	
Tapped outputs available	
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V.....	£6.00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....	£9.50
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....	£12.50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....	£16.00
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....	£21.00
6V, 500mA.....	£2.00
12V, 100mA.....	£1.30
12V, 750mA.....	£1.75
10-0-10V 2 amp.....	£3.00
30V 5 amp and 17V 0-17V.....	£3.25
2 amp.....	£4.00
0-5, 8, 10, 16V, 1 amp.....	£2.50
9V, 3 amp.....	£3.50
15-0-15V 2 amp.....	£3.75
30V, 2 amp.....	£3.50
30V, 1 1/2 amp.....	£3.30
9V, 1 amp.....	£1.50
<b>AUTO TRANSFORMERS 115V to 240V 500W.....</b>	
£10.00	
<b>CHARGER TRANSFORMERS - CHARGER RECTIFIERS</b>	
6-12V 3a.....	£4.00
6-12V 4a.....	£5.50
6-12V 2a.....	£1.80
6-12V 4a.....	£2.00

**R.C.S. LOUDSPEAKER BARGAINS**

3 ohm, 6x4in. £1.50, 7x4in. £1.50, 8x5in. £2.50, 6 1/2in. £2.20, 8in. £2.60, 10in. £3.50, 12in. £4.50.

8 ohm, 2 1/2in. £1.50, 3in. £1.50, 5in. £2.20, 8in. £2.60, 10in. £3.50, 12in. £4.50, 16 ohm 6 x 4in. £1.50, 7 x 4in. £1.50, 5in. £1.50, 8in. £3.10, 10in. £3.50, 12in. £4.50, 10 x 6in. £3.50.

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 50p £2.95**

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

**PP BATTERY ELIMINATOR**

Mains stabilised power pack 9 volt 400 ma max. with overload cutout. Size 5x3 1/2 x 2 1/2 price £4.50 post 50p.

**THE "INSTANT" BULK TAPE ERASER**

Suitable for cassette, and all sizes of tape reels. C. mains 200/249V. Leaflet S.A.E. £7.50 Post 50p

**HEAD DEMAGNETISER PROBE £5.00**

A.C. ELECTRIC MOTORS POST 50p, 2 Pole, 240V, 2 Amp Spindle - 1.43 x 0.21in. £1.75, 2 pole, 240V, 1.5 Amp. Double spindle - 1.75 x 0.16in. Each £1.50, 2 Pole, 120V, .5 Amp, Spindle - 0.75 x 0.2in. Two in series=240V, 75p each. Brush Motor. From a Food Mixer 240V, .3 Amp. High Speed and Powerful. Spindle - 0.5 x 0.25in. £2.95

**BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p;**

8 x 6in. £1.40, 10 x 7in. £1.55, 14 x 9in. £1.90, 16 x 6in. £1.85, 12 x 3in. £1.20, 16 x 10in. £2.20, 12 x 8in. £1.70.

**ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p;**

10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1.16.

**ALUMINIUM ANGLE BRACKETS 6 x 1 x 1/2in. 25p.**

**ALUMINIUM BOXES, MANY SIZES IN STOCK.** 4 x 2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1.30; 8 x 6 x 3in. £2.10; 12 x 5 x 3in. £2.30; 6 x 4 x 3in. £1.60; 10 x 7 x 3in. £2.50.

**HIGH VOLTAGE ELECTROLYTICS**

8/800V.....£1.20 50/500V.....£1.20 50+50/500V.....£1.80  
16/500V.....75p 220/450V.....95p 40+80/500V.....£2  
32/500V.....75p 16+32+32/500V.....£2

**DE LUXE BSR HI-FLA AUTOCHANGER**

Plays 12in., 10in., or 7in records. Autor Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With CERAMIC STEREO CARTRIDGE

BSR Single Player P207 cueing device, ceramic cartridge. £15  
Garrard Single Player 6-200 metal turntable, cueing device, aluminium arm, Stereo cartridge. £22

BSR, P182, Snake arm, flared Aluminium Turntable ADC QLM30 Magnetic Cartridge. £30

B.S.R. Auto Changer. 11in. Turntable. Budget price. £17.50  
Stereo ceramic, reliable unit, 3-speed.  
RSC Disco Deck 3 speed stereo £9.95 or £18 pair

Rapid Mail Order Service. Callers Welcome. Access - Visa. Lists 20p. Closed Wed.

**Radio Components Specialists**  
337 WHITEHORSE ROAD  
CROYDON, SURREY. U.K. TEL 01-684 1665

**SCS COMPONENTS**

Halifax Road, Keighley, West Yorkshire BD21 5HR

All our products are guaranteed high quality components from leading Semiconductor Manufacturers.

<b>CMOS</b>	4055 1.23 4000 .19 4001 .26 4002 .22 4006 .86 4007 .26 4008 .78 4009 .40 4010 .40 4011 .26 4012 .22 4013 .40 4014 .78 4015 .78 4016 .40 4017 .74 4018 .78 4019 .40 4020 .92 4021 .98 4022 .87 4023 .22 4024 .66 4025 .20 4026 1.58 4027 .40 4028 .72 4029 1.04 4030 .45 4031 2.08 4032 1.10 4033 1.37 4034 1.99 4035 .92 4037 .96 4038 1.03 4040 .98 4041 .77 4042 .89 4043 .84 4044 .84 4045 1.27 4046 1.09 4047 .82 4048 .50 4049 .40 4050 .45 4051 .70 4052 .70 4053 .70 4054 1.05	4056 1.23 4058 1.23 4059 4.45 4060 1.10 4063 1.05 4068 .48 4067 3.60 4068 .22 4069 .28 4070 .33 4071 .24 4072 .24 4073 .24 4075 .21 4076 .93 4077 .30 4078 .22 4079 .22 4081 .22 4082 .22 4085 .75 4086 .75 4089 1.40 4093 .68 4094 1.70 4095 .95 4096 .95 4097 3.15 4098 1.05 4099 1.25 4502 .97 4508 2.35 4510 .87 4511 .87 4512 .85 4514 2.21 4516 2.21 4518 .97 4519 .97 4527 1.37 4532 1.07 4556 .59 4558 1.02 40106 .85 40160 .74 40161 .74 40162 .74 40163 .74 40174 .74 40174 .74 40194 .93	<b>LINEAR</b> CA555CG .20 CA741CG .38	<b>DIODES</b> IN4001 .05 IN4002 .05 IN4003 .06 IN4004 .06 IN4005 .06 IN4006 .07 IN4007 .07 IN4148 .04	<b>ZENERS</b> BZY88 3.3V to 30V 400mW .07 each	<b>RESISTORS</b> 5% carbon film resistors. High stability, low noise $\pm$ W £24 range of values 1R-1M .07 for 5 places 1 value only.	<b>TRANSISTORS</b> ZTX107 .09 ZTX108 .09 ZTX109 .09 ZTX300 .10 ZTX310 .10 ZTX320 .11 ZTX330 .11 ZTX450 .12 ZTX500 .12 ZTX502 .12 ZTX504 .12 ZTX750 .20	<b>DIL SOCKETS</b> 8P .09 14P .11 16P .13 18P .15 20P .17 22P .18 24P .20 28P .25 40P .35	<b>SWITCHES</b> <b>Toggle</b> 829K7 - 3 amp SPST .98 7321K3 - 6 amp SPST .85 8810K6 - 10 amp SPDT 1.14 8372K8 - 3 amp DPST .82 7320K3 - 6 amp DPST .82 8824K5 - 10 amp DPST 1.66 <b>Miniature Toggle</b> E2012 - 3 amp SPDT .59 E2022 - 3 amp DPDT .74 <b>Slide Switches</b> SM1-1 - 1 amp SP on/off .23 SM2-2 - 1 amp DPST .31 SM2-3 - 1 amp DPDT .61 <b>LED's</b> MAN3640 - 7.6mm Orange 1.70 MAN6640 1.90 MAN6660 - 14.2mm Orange 2.00 MV50 - 2.3mm Red 1.04 MV53 - 2.3mm Green .21 MV5021 - 4.7mm Red .21 MV5054/1 - 5mm Red .15 MV5054/2 - 5mm Red .17 MV5054/3 - 5mm Red .10 MV50748 - 3mm Red .43 MV52124 - Rectangular Green .64 MV53124 - Rectangular Yellow .44 MV57124 - Rectangular Red .44
-------------	---	---	---	---	---	--	--	--	---

Cash/Cheques/P.O.'s with order. P & P add 30p to all orders. Add 15% VAT to total order. All items ex. stock - orders by return post.

**ELECTRONIC TESTING & FAULT DIAGNOSIS**

by G. C. Loveday Price: £5.50

**DIGITAL TECHNIQUES & SYSTEMS**

by D. C. Green price: £5.50

**ELECTRONIC FAULT DIAGNOSIS**

by I. R. Sinclair Price: £3.50

**ELECTRONIC DESIGNER'S H/B**

by K. Hemingway Price: £13.50

**HANDBOOK OF ELECTRONICS CALCULATIONS FOR ENGINEERS & TECHNICIANS**

by M. Kaufman Price: £14.70

**H/B OF MICROCIRCUIT DESIGN & APPLICATION**

by D. F. Stout Price: £19.20

**UNDERSTANDING MICROPROCESSORS**

by Texas Inc. Price: £4.00

**INTRODUCTION TO MICROCOMPUTER PROGRAMMING**

by P. C. Sanderson Price: £4.50

**THE COMPLETE MICROCOMPUTER SYSTEMS H/B**

by E. L. Safford Price: £8.25

**TOWERS' INTERNATIONAL TRANSISTOR SELECTOR**

by T. D. Towers 1980 Price: £10.50

\*ALL PRICES INCLUDE POSTAGE\*

**THE MODERN BOOK CO.**

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

**MAINS INTERCOM**

NO BATTERIES NO WIRES ONLY £36.99 PER PAIR + VAT £5.55

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/2 mile on the main phase. On/off switch. Volume control, with "buzzer" call and light indicator. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. £1.75

F.M. 2 channel "touch" model £47.95 + VAT £7.20 + P. & P. £1.85.

**NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER**

£18.95 + VAT £2.85 + P & P £1.15

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £20.95 + VAT £3.15. P. & P. £1.15p.

**DOOR ENTRY SYSTEM**

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boom for the invalid, the aged and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock), mains power unit, cable (8-way) 50 ft and wiring diagram. Price £49.95 + VAT £7.50 + P. & P. £1.85. Kit with two Telephones £59.95 + VAT £9.00 + P. & P. £1.95.

10-day price refund guarantee on all items. WEST LONDON DIRECT SUPPLIES (PE9) 169 KENSINGTON HIGH STREET, LONDON W8

VISA

MASTERCARD

10-day price refund guarantee on all items.

WEST LONDON DIRECT SUPPLIES (PE9)

169 KENSINGTON HIGH STREET, LONDON W8

# MONITORS MONITORS MONITORS



Uncased from 3" to 12"  
Cased from 5" to 20"

Semi professional or professional available from stock.

Monitor PCBs including Transformers and Tubes also in stock.

Phone or write for details.

## CROFTON ELECTRONICS

Crofton Electronics Limited  
35 Grosvenor Road, Twickenham, Middx.  
Tel: 01 891 1513

## TOP PRIORITY for every constructor...



### HOME RADIO CATALOGUE

Price £1.50 including postage, packing, insurance.

- Over 2,000 items clearly listed.
- Profusely illustrated throughout
- Over 100 A-4 size pages.
- Bargain list included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.,  
Dept. PE., P.O. Box 92, 215 London Road, Mitcham, Surrey.  
Phone 01-543 5659

POST THIS COUPON  
with cheque or P.O. for £1.50

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

HOME RADIO (Components) LTD., Dept. PE  
P.O. Box 92, 215 London Road, Mitcham, Surrey.

(Regn. No  
London 912966



# 2 SUPERB NEW KITS!

£2 OFF  
SPECIAL OFFER



## C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection): electronic variable dwell circuit (maximises spark energy at all speeds): pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TC1).

What's In the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer.

Fully illustrated comprehensive instructions and full technical back up service.

# SUREFIRE ELECTRONIC IGNITION

Suretron Systems (UK) Ltd. Dept. PE2  
Piccadilly Place, London Rd., Bath BA1 6PW. Tel: Bath (0225) 23194

Name.....

Address.....

\*Phone order with Access Barclaycard  
VAT and P & P inc

Quantity  
required

ES200: Neg	£13.95	£11.95	
C300: Pos	£17.95	£15.95	
C300: Neg	£17.95	£15.95	
Tacho Adapt. TC1		£3.90	

I enclose  
cheque/P.O.'s  
£  
Chq No.

# Marshall's

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA  
Industrial Sales: 01-328 1009  
Mail Order: 01-624 8582  
Also retail shops: 325 Edgware Road, London W2.  
40 Crickwood Broadway, London NW2. 85 West Regent St., Glasgow.  
108A Stokes Croft, Bristol.

## CAPACITORS:

Mullard Ceramic 63v range  
1pF to 10,000pF E 24 range  
all at £0.06 each  
Siemens Ceramic 63v B37448/9  
.01: .022: .033: .047Mf @ £0.06  
.068: .1mf @ £0.08: .22mf @  
£0.11  
CSF High Voltage Ceramic Discs  
Prices £0.07 to £0.18 Range  
100pF to 10,000pF  
Voltage range up to 6Kv.  
See catalogue for details.  
Comprehensive range Siemens  
Layer Polyester Caps: .001 to  
3.3mf  
Prices £0.07 to £0.63.  
See catalogue for details.  
Large range of Mullard/Siemens  
Electrolytic Axial/Radial  
Capacitance values 1.0mf to  
10,000mf  
Voltage ranges 25v: 40v: 63v:  
100v:  
Prices and types as catalogue  
Also Mullard C280; Siemens  
B32231/4 and B32110. All prices  
net + VAT and postage/packaging.

## TOOLS BAHCO

Side Cutter with Bezel.  
Side Cutter without Bezel.  
End Cutter without Bezel.  
Vero Metal Shears.  
Other items as catalogue.



## BOXES & CASES

See catalogue for full range.  
Aluminium boxes 13 sizes.  
Rexine Covered boxes 7 sizes.  
**NEW RANGE TMEC CASES**  
Send S.A.E. for details & types  
Price range, £14.04 to £17.00  
**ABS PLASTIC BOXES**  
3" x 2 1/4" x 1 3/8" Prices as  
3 3/4" x 2 3/4" x 1 3/8" catalogue  
4 1/2" x 3 3/4" x 1 1/2"  
8" x 4 3/4" x 3"  
**BAZELLI INSTRUMENT CASES**  
5 sizes.

Miscellaneous hardware  
including  
Vero Board: Superstrips:  
Vero Breadboard.  
Vero boxes (see catalogue for  
full range).



Card Frames: Fliptop boxes:  
etc etc.

## 1980 CATALOGUE

U.K.: 65p post paid  
Europe 85p post paid  
Rest of World £1.25  
post paid  
Mail order: 01-624 8582



## TTL see catalogue for full range

SN7400N	£0.14	SN7491AN	£0.54
SN7401N	£0.14	SN7492N	£0.31
SN7402N	£0.14	SN7493N	£0.32
SN7403N	£0.14	SN7494N	£0.80
SN7404N	£0.14	SN7495N	£0.55
SN7405N	£0.15	SN7496N	£0.34
SN7406N	£0.34	SN7497N	£1.80
SN7407N	£0.26	SN74100N	£1.10
SN7408N	£0.15	SN74107N	£0.21
SN7409N	£0.16	SN74118N	£0.76
SN7410N	£0.15	SN74119N	£1.20
SN7411N	£0.15	SN74121N	£0.25
SN7412N	£0.20	SN74122N	£0.48
SN7413N	£0.28	SN74123N	£0.42
SN7414N	£0.47	SN74124N	£0.53
SN7416N	£0.22	SN74125N	£0.40
SN7417N	£0.22	SN74141N	£0.50
SN7420N	£0.15	SN74145N	£0.64
SN7423N	£0.15	SN74151N	£1.05
SN7425N	£0.19	SN74150N	£0.79
SN7426N	£0.19	SN74151N	£0.55
SN7427N	£0.19	SN74153N	£0.55
SN7430N	£0.15	SN74154N	£0.90
SN7432N	£0.17	SN74155N	£0.60
SN7437N	£0.21	SN74157N	£0.59
SN7438N	£0.21	SN74160AN	£0.70
SN7440N	£0.15	SN74161AN	£0.70
SN7441AN	£0.52	SN74162AN	£0.70
SN7442N	£0.40	SN74163AN	£0.70
SN7445N	£0.66	SN74164AN	£0.80
SN7446AN	£0.48	SN74165N	£0.80
SN7447AN	£0.48	SN74167N	£1.20
SN7448N	£0.45	SN74174N	£0.80
SN7450N	£0.15	SN74175N	£0.63
SN7451N	£0.15	SN74176N	£0.74
SN7453N	£0.15	SN74177N	£0.73
SN7454N	£0.15	SN74180N	£0.70
SN7460N	£0.15	SN74181N	£1.85
SN7470N	£0.26	SN74182N	£0.83
SN7472N	£0.24	SN74184N	£1.29
SN7473N	£0.25	SN74185AN	£1.10
SN7474N	£0.25	SN74186N	£1.35
SN7475N	£0.31	SN74188AN	£1.84
SN7476N	£0.26	SN74189N	£2.26
SN7480N	£0.39	SN74190N	£0.74
SN7481N	£0.71	SN74191N	£0.79
SN7482N	£0.65	SN74192N	£0.79
SN7483N	£0.60	SN74193N	£0.79
SN7484N	£0.95	SN74196N	£0.74
SN7485N	£0.70	SN74197N	£0.74
SN7486N	£0.66	SN74198N	£1.09
SN7489N	£1.66	SN74199N	£1.09
SN7490AN	£0.33		

## KNOBBS & SWITCHES

Big selection as catalogue  
Also Resistors; Presets; Pots;  
Opto; Semiconductors etc.

## SOLDERING EQUIPMENT

**IRONS-ANTEX**  
15 watt C15 £3.95  
15 watt CCN £4.20  
17 watt CX17 £4.20  
25 watt X25 £4.20  
Stand £1.50



## DESOLDERING TOOL

Solder £6.50



## SINCLAIR INSTRUMENTS

Digital Multimeter  
" " PDM35 £ 34.50  
" " DM235 £ 52.50  
" " DM350 £ 72.50  
" " DM450 £ 99.00  
Digital Frequency Meter  
PFM200 £ 49.80  
Low Power Oscilloscope  
SC110 £139.00

## CRIMSON ELEKTRIK HI FI MODULES

CE608 Power Amp £18.26  
CE1004 " " £21.30  
CE1008 " " £23.91  
CE1704 " " £30.43  
CE1708 " " £30.43  
CPS1 Power Unit £16.96  
CPS3 " " £20.43  
CPS6 " " £26.09  
CPR1 Pre Amp £29.57  
CPR15 Pre Amp £38.70  
All prices + VAT + postage/  
packaging

## NEW COMPONENTS

- |          |   |
|----------|---|
| Pack No. |   |
| A10      | 10 PP3 battery leads. 50p   |
| A30      | 10 Red or black crocodile clips. 45p  |
| A60      | 10 Red or black phono plugs. 80p  |
| A61      | 10 single phono sockets. 70p  |
| A70      | 10 2.5mm unscreened jack plugs. 80p   |
| A72      | 10 3.5mm unscreened jack plugs. 80p   |
| A73      | 10 3.5mm chassis sockets. 80p   |
| A74      | 10 Standard mono jack plugs. 130p   |
| A75      | 10 Standard switched jack sockets. 170p   |
| A84      | 10 5 pin 180° DIN plugs. 120p   |
| A85      | 10 5 pin 180° DIN chassis sockets. 100p   |
| C10      | 5 Standard toggle switches SPST. 190p   |
| C20      | 10 Miniature DPDT slide switches. 130p  |
| C30      | 10 Miniature push to make switches. 130p  |
| C31      | 10 Miniature push to break switches. 170p   |
| C40      | Pair of ultrasonic transducers. 350p  |
| C50      | 20 Texas 8 pin sockets. 170p  |
| C51      | 20 Texas 14 pin sockets. 200p   |
| C52      | 20 Texas 16 pin sockets. 220p   |
| E10      | Resistor kit 10 each value 4.7Ω to 1M. 1W type.<br>Total of 650 resistors. 490p<br>1W 5% carbon resistors. 18p per 20.<br>Multiples of 20 per value only. |
| E33      | 10 4.7u 63v radial electrolytics. 50p   |
| E34      | 10 10u 25v radial electrolytics. 80p  |
| E37      | 10 100u 25v radial electrolytics. 75p   |
| E44      | 10 1u 35v tantalum capacitors. 100p   |
| E50      | 10 0.01u Mullard C280 polyester. 50p  |
| E54      | 10 0.1 Mullard C280 polyester. 50p  |
| F11      | 10 BC108 transistors. 90p   |
| F15      | 10 BC184L transistors. 90p  |
| F17      | 10 BC214L transistors. 90p  |
| F25      | 10 2N3702 transistors. 80p  |
| F26      | 10 2N3704 transistors. 80p  |
| F27      | 10 2N3819 transistors. 190p   |
| F29      | 10 2N3905 transistors. 90p  |
| F41      | 4 2N3055 transistors. 200p  |
| F46      | 5 7805 1A 5V regulators. 300p   |
| H10      | 20 1N4002 rectifier diodes. 75p   |
| H50      | 20 OA91 signal diodes. 110p   |
| H60      | 100 1N4148 signal diodes. 180p  |
| H70      | 5 C106D 4A 400V thyristors. 200p  |
| H75      | 5 TIC246D 16A 400V triacs. 520p   |
| J10      | 20 0.2in red LEDs. 170p   |
| J15      | 50 0.2in red LEDs. 400p   |
| J20      | 100 0.2in red LEDs. 750p  |
| J30      | 20 0.2in green LEDs. 280p   |
| J50      | 20 0.2in yellow LEDs. 280p  |
| J80      | 4 FN0500 displays. 350p   |
| K10      | 5 741 operational amps. 8 pin. 90p  |
| K25      | 5 LM301A operational amps. 8 pin. 140p  |
| K30      | 1 LM324 operational amplifiers. 50p   |
| K80      | 5 CA3140 operational amps. 225p   |
| K80      | 5 NE555 timers. 110p  |
| M10      | 8 2114LP memories. 2800p  |
| N5       | 1 Dalo printed circuit board pen. 80p   |

All prices include VAT. Please add 50p carriage on all orders below £10. Send SAE for our detailed list. Mail order only.

## RAPID ELECTRONICS

Millcroft House, Station Road, Eynsford, Kent.

## MICROTYPE



PRODUCED IN BLACK ABS PLASTIC, COMPLETE WITH SCREWS AND INSTRUCTIONS.  
SPACE FOR EXPANSION, FORCE FEED FAN, NUMERIC PAD AND ADDITIONAL KEYS.  
ONLY £24.50 + £1.50 P&P + VAT.  
SEND CHEQUES OR P.O.'S FOR £29.90 TO:  
MICROTYPE, P.O. BOX 104, HEMEL HEMPSTEAD, HERTS. HP2 7QZ  
SAE FOR DETAILS. DEALER & OEM ENQUIRIES WELCOME.

## MICROTYPE STAK-PAK

CASSETTE STORAGE SYSTEM FOR EASY PROGRAM FILING.



- Each drawer section takes 2 cassettes
- Drawers lock together vertically.
- Each twin pack comes with 2 C10 digital cassettes.
- Each 'pak' is complete with index cards, cassette and drawer labels.

FIVE TWIN PAKS (10 CASSETTES) FOR £60 INC. VAT & P&P

Send cheques or Postal Orders to:  
MICROTYPE, PO Box 104,  
HEMEL HEMPSTEAD,  
HERTS HP2 7QZ.


## Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD,  
COPNOR, PORTSMOUTH, HANTS.,  
PO3 5BJ

GIANT 0.8" LED clock display, common cathode, non-multiplexed. With data £3.95 each. ALARM clock module with 0.7" LED display. With data £5.99 each. LIQUID crystal clock display, 0.5" digits. With data and FREE socket, £5.25 each. FLUORESCENT reject calculators. Modern, 10 function with full memory. Most repairable but no 'teas' £2.99 each. TEN, transistors I.F. transformers. All brand new. May include several types. 55p for 10. CLOCK CHIP MM5316 I.C. (has alarm output). Brand new, with data £2.35 each. POLARIZING filter, plastic, 0.006" thick. Any size cut from 1 sq. in. to max. size 19" x 250 feet. 3p. per sq. in. MOMENTARY (push to 'make') switch. Red cap. 15p each. SLIDE switch, 2 pole c.o. 16p each. TWO calculator keyboards (not compatible with 4204 calc. chip). 99p the pair. MULTIMETER CHIP. MM5330 i.c. to build 4 1/2 digit d.m.m. (needs additional circuitry). With data £3.55 each. KNOBS Slider control knobs, fits 5 or 8mm shafts. State colour 14p each. Rotary control knobs, black (18mm diam) with coloured cap, state colour required. 20p each. Skirted rotary knob, same as rotary control knob above but has 'flared' skirt around base. State cap colour required. 27p each. Colours available, black, red, green, blue, yellow, grey, white. 8 DIGIT common cathode calculator display. 0.1" multiplexed, with data, 99p each. LED WRISTWATCH CHIP with data, 95p each. LED WRISTWATCH DISPLAY matches above watch chip. With data, 95p each. NOTE the wristwatch chip and display are housed in 'legless flatpack' style and require some fairly fine soldering. QUALITY jack sockets. mono 25p each, stereo 30p each. LM555 timer i.c. with applications booklet. 25p each. MEMORIES 2102 static RAM, with data, 99p each. NORTEC 4204, 4 function calc. chip. With data, 80p each. UNTESTED 0.1" LED displays. 10 single digit displays for 95p. 'U' to test.

POST AND PACKING PLEASE ADD 40p  
(Overseas Orders Add £1)  
For your FREE copy of our latest catalogue please send MEDIUM sized SAE  
ADD 15% TO TOTAL COST  
V.A.T. (Including Post and Packing).  
'CASH BACK' Satisfaction Guarantee on all items.

# Toroidal Transformers

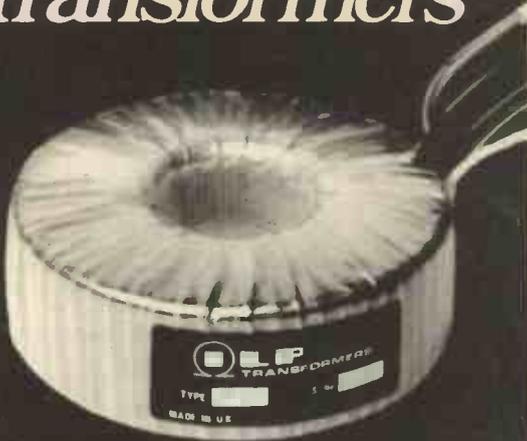

Yet another new development from I.L.P

(covered by 5 year guarantee)



**I.L.P. TRANSFORMERS**

A division of  
I.L.P. ELECTRONICS LTD.  
Graham Bell House, Roper Close,  
Canterbury CT2 7EP  
02271 54778. Telex 965780

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents within the range and are appreciably more efficient. Our toroidals cost virtually the same as their now outdated laminated equivalents and hum is down to a negligible tenth of what it used to be. Each I.L.P. toroidal transformer is supplied with rigid mounting kit comprising centre bolt, two neoprene and one steel washer.

TYPE	VA	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	DIMENSIONS OIA-HT	WEIGHT KG	PRICE
2X010 2X011 2X012 2X013 2X014 2X015 2X016	50	6+6 9+9 12+12 15+15 18+18 22+22 25+25	4.16 2.77 2.08 1.66 1.38 1.13 1.00	70x40mm	0.9	TRANSFORMERS IN THIS RANGE <b>£5.40<sub>ea</sub></b> + £1.10 P/P + £0.98p VAT
3X010 3X011 3X012 3X013 3X014 3X015 3X016	80	6+6 9+9 12+12 15+15 18+18 22+22 25+25	6.64 4.44 3.33 2.66 2.22 1.81 1.60	90x30mm	1.0	TRANSFORMERS IN THIS RANGE <b>£5.70<sub>ea</sub></b> + £1.20 P/P + £1.04 VAT
4X010 4X011 4X012 4X013 4X014 4X015 4X016	120	6+6 9+9 12+12 15+15 18+18 22+22 25+25	10.00 6.66 5.00 4.00 3.33 2.72 2.40	90x40mm	1.2	TRANSFORMERS IN THIS RANGE <b>£6.72<sub>ea</sub></b> + £1.30 P/P + £1.20 VAT
5X016 5X017	180	25+25 30+30	3.20 2.66	110x40mm	1.8	<b>£8.88</b> + £1.40 P/P + £1.54 VAT
6X016 6X017	300	25+25 30+30	6.00 5.00	110x50mm	2.6	<b>£12.27</b> + £2.50 P/P + £2.22 VAT

NOTE: For 220V Primary please insert 1 in place of X in type number.  
For 240V Primary please insert 2 in place of X in type number.

Example: 120VA 240V 15+15V. 4A --- 42013.  
Custom design and O.E.M. enquiries welcomed.

## FREEPOST

We pay postage on your enquiries and orders. Simply address your envelope: **FREEPOST T2, I.L.P. ELECTRONICS, Graham Bell House, Roper Close, Canterbury CT2 7EP.** (No stamp required).

I.L.P. ELECTRONICS, ROPER CLOSE, CANTERBURY CT2 7EP

Please supply .....

I enclose Cheque  Postal Orders  International Money Order  Access

Barclaycard Account No. ....

Name .....

Address .....

# INDEX TO ADVERTISERS

Acorn Computers	71	Fladar	82	North Cheshire College	81
Adam Hall (P.E. Supplies)	81	Global	80	Phonosonics	6, 7
Aitken Bros	56	G.M.T.	12	PKG Electronics	81
Barrie Electronics	74	Heathkit	10	Progressive Radio	78
B. Bamber	76	Herts Elec.	80	Proto Design	81
BIB Hi-Fi	4	Hiyon Ltd.	81	Radio Component Specialists	84
BIET	12	Home Radio	85	Radio & T.V. Components	16
Birkett J.	56	I.C.S. Intertext	7, 82	Ramar Constructor Services	81
Boffin Projects	80	I.L.P. Electronics	72, 73, 87	Rapid Electronics	86
Bolster Instruments Co.	81	Industrial Supplies	81	Saxon Entertainments	4, 74
Brewster, S. & R.	70	Jayen Developments	74	Science of Cambridge	14, 15
British National Radio & Electronics School	5	Keelmoor	13	Scientific Wire Co.	81
Butterworths	77	Lascar	3	Service Trading	Cover III
Cambridge Kits	80	L & B Electronics	78	Semi-Comp Northern	84
Cambridge Learning	41	London Electronics College	82	Sentinel Supply	76
Centurion Alarms & Electronics	80	Maplin Electronics	77, Cover IV	Suretron	85
Chromasonic Electronics	79	Marick	81	Swanley Electronics	82
Clef Products	50	Marshall A.	50, 86	Tandy	8, 9
Codespeed	86	Metac	69	Tempus	83
Computer Components (Teleplay)	Cover II	Micro Circuits	11	T.K. Electronics	70
Continental Spec.	22	Micro Type	86	Technomatic	88
Crofton Electronics	85	Modern Book Co.	84	Transam Components	75
C.R. Supply Co.	80	Monolith	83	Watford Electronics	2, 3
Davian	12			West London Direct Supplies	84
Design Engineering (Wokingham) Ltd.	83			Wicca Electronics	56
Display Electronics	76			Williamson Amplification	80
Doram	10			Wilmslow Audio	77
Dziubas M.	50				
Easicomp Ltd.	81				
Electrovalue	70				
Enviro Systems	83				



# SERVICE TRADING CO

**FT3 NEON FLASH TUBE**  
High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc.  
£1.50. P. & P. 25p (£2.01 incl. VAT) 3 for £3. P. & P. 50p (£4.03 incl. VAT & P.)

## WHY PAY MORE?

**MULTI RANGE METER** Type MF15A a.c. d.c. volts 10 - 50 250 500 1000 Ma 0-5; 0-10 0-100 Sensitivity 2000V 24 range diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.63 incl. VAT & P.)

## METERS (New) - 90 mm DIAMETER

**A.C. Amp.** Type 62T2, 0-1A, 0-5A, 10A, 0-20A, 50A A.C. Volt. 0-150V, 0-300V.  
**D.C. Amp.** Type 65C5, 0-2A, 5A, 0-10A, 0-20A, 0-50A, 0-100A.  
**D.C. Volt.** 15V, 30V.  
All types £3.50 ea. + P. & P. 50p (£4.60 incl. VAT), except 0-50A, 0-100A D.C. price £5.00 + 50p P. & P. (£6.33 incl. VAT).

**HEAVY DUTY SOLENOID** mf by Magnetic Devices. 240V. A.C. intermittent operation. Approx. 20 lb. pull at 1.25 in. Ex-repair. Tested. Price: £4.75 + 75p. P. & P. (£6.33 incl. VAT & P.)

## 12V D.C. SOLENOID

12V D.C. heavy duty Solenoid 4 Kp. pull. Easily removable from plate. All chassis containing 4-24V. D.C. Push Solenoids (1 1/2 lb. approx.), 5-fig. Counter, 5 min. photo cells, Sub-min. Micro switches etc. etc. Ex-repair. London Transport Printer. Price: £9.00 - £10.00. P. & P. (total incl. VAT £11.50).  
12V D.C. Solenoid approx. 1lb. pull. Price: £1.40 + p. & p. 30p. (total incl. VAT £1.96).

## SOLENOIDS

**WESTOOL SERIES D6 Model A3** 24V. D.C. Price £1.50 + 50p p. & p. (Total incl. VAT £2.30).  
**WESTOOL SERIES D4 Model A1** 24V. D.C. Price £1.00 + 30p p. & p. (Total incl. VAT £1.50).  
**AG/GT 24V. D.C. 70 ohm Coil** Solenoid. Push or Pull. Adjustable travel to 3/16 in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25 mm. Price: £3 for £2.40 + 30p. P. & P. (min 3 off) (£3.11 incl. VAT & P.).

## 800 WATT DIMMER SWITCH

Easily fitted. Will control up to 800 W. of all lights except fluorescent at mains voltage. Price: £3.90 + 50p. p. & p. (£5.06 incl. VAT).

**REED SWITCHES.** Size 28mm x 4mm dia. Price: 10 for £1.00 + p. & p. 20p. (total incl. VAT £1.38). 100 for £8.00 + p. & p. 30p. (total incl. VAT £9.55).

## MICRO SWITCHES

Sub. Min. Honeywell Lever m/s type 3115m 906ft. 10 for £3.50 post paid (£4.03 incl. VAT).  
These V3 types.  
**Button type (Pye)** 10 for £3.00 (£3.45 incl. VAT)  
**Short lever type** 16amp. rating (Grouzet) £4.00 (£4.60 incl. VAT)  
**Roller type (Bonnelia)** 10 for £3.50 (£4.03 incl. VAT). N.M.S.  
D.P. C/O lever m/s/switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total incl. VAT £2.93 (min. 10).

## MERCURY SWITCH

Size 27mm x 5mm, 10 for £5.00 - 30p P. & P. (incl. VAT £6.12) min quantity 10.  
Heavy duty type, size 38 x 16 x 10mm, minimum quantity 10. £7.50 post paid (£8.63 incl. VAT & P.).

## A.E.G. CONTACTOR

Type L58/L11. Coil 240V 50 Rs. Contacts - 3 make: 600V: 20amp. 1 break: 600V: 20 amp. Price: £5.50 + 50p P. & P. (£6.90 incl. VAT & P.).

**ARROW-HART MAINS CONTRACTOR**, Cat. No. 130A30. Coil 250V, or 400V. A.C. Contacts. 3 make 50 amp up to 660V. A.C. 20 h.p. at 450V, 3 phase 50 Hz. Price: £7.75 + p. & p. 10c. (incl. VAT, total £10.08). N.M.S.

## SMITH BLOWER

Type FF8. 1706. Small, quiet, smooth running. 240V. A.C. operation. Output aperture 45x40cm. Overall size 135 x 165 cm. Flange mounting. Price: £4.28. P. & P. 75p. (Total: £5.75 inc. P. & VAT. N.M.S.)  
Other types available. S.A.E. for details

## AIRFLOW DEVELOPMENT LTD.

Centrifugal Blower Unit powered by GEC 230/250V. 2850 r.p.m. motor producing approx. 120 c.f.m. Aperture 65x90mm. Overall size 222 x 225 x 195mm. Incl. Starter Capac. Price: £16.00 + £2.00 p. & p. (Total incl. VAT £20.70). N.M.S.

## 24 volt. D.C. BLOWER UNIT

Precision 24 volt. D.C. 0.8 amp Blower that works well on 12V 0.4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P. & P. 75p (incl. VAT £6.04). N.M.S.

## INSULATION TESTERS NEW!

Test to I E E Spec Rugged metal construction suitable for bench or field work constant speed clutch Size L 8in W 4in H 6in weight 6lb, 500V, 500 megohms, £49. Post 80p (£57.27 incl. VAT & P.). 1,000V 1,000MΩ, £65. Post 80p (£84.17 incl. VAT & P. SAE for leaflet).  
Yet another outstanding offer.

## IMFD 600V Dubilier

wire ended capacitors N.M.S. 10 for £1.50 p&p 50p (£2.30 incl. VAT + p&p) (Min 10)

## 230V a.c. FAN ASSEMBLY

Powerful continuously rated a.c. motor completely with 5 blade 6in. or 4 blade 3in. aluminium fan. Price £3.00. P. & P. 65p (£4.20 incl. VAT & P.).

# VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200 watt (1 amp inc. exc. voltmeter)	£14.50
0.5 KVA (2 amp IMAX)	£17.00
1 KVA (5 amp MAX)	£22.50
2 KVA (10 amp MAX)	£37.00
3 KVA (15 amp MAX)	£45.50
5 KVA (25 amp MAX)	£74.00
10 KVA (50 amp MAX)	£168.00
15 KVA (75 amp MAX)	£260.00

## 3-PHASE VARIABLE VOLTAGE TRANSFORMERS

3KVA (max. 15 amp.)	£106.43
6KVA (max. 30 amp.)	£159.37
10KVA (max. 50 amp.)	£327.43

## LT TRANSFORMERS

13-0-13V at 1 amp £2.50 P. & P. 50p (£3.45 incl. VAT)  
0-4V/6V/24V/32V at 12 amp £18.50 P. & P. £1.90 (£23.46 incl. VAT & P.)  
0-6V/12V at 20 amp £14.70 P. & P. £1.50 (£18.63 incl. VAT & P.)  
12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£15.83 incl. VAT & P.)  
0-6V/12V at 10 amp £8.25 P. & P. £1.25 (£10.93 incl. VAT & P.)  
0-6V/12V/17V/18V/20V at 20 amp £19.00 P. & P. £1.50 (£23.58 incl. VAT & P.)  
0-10V/17V/18V at 10 amp £10.50 P. & P. £1.50 (£13.80 incl. VAT & P.)  
Other types in stock; phone for enquiries or send sae for leaflet.

## HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Hy-Light Strobe Kit Mk Iv. £22.00 + £1.50 P. & P. (incl. VAT total £27.03). Specially designed case and reflector for Hy-Light £9.00. Post £1.50 (£12.08 incl. VAT & P.). Super Hy-Light Strobe (approx. 16 joules) Price £33. P. & P. £1.50 (incl. VAT total £39.88).  
Suitable case £11.00 + £1.50 P. & P. (£14.30 incl. VAT & P. & P.).

## XENON FLASHGUN TUBES

Range available from stock S.A.E. for details

## ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 Watt £8.70 incl. VAT £10.00 (callers only).  
2ft. 20 watt £6.20. Post 75p (£7.99 incl. VAT + P.)  
(For use in stan bi-pin fittings).  
12in. 8 watt £2.80. Post 35p (£3.62 incl. VAT + P.)  
9in. 6 watt £2.25. Post 35p (£2.99 incl. VAT + P.)  
6in. 4 watt £2.25. Post 35p (£2.99 incl. VAT + P.)  
Complete ballast unit for either 6" or 12" tube 230V AC op £4.50. Post 45p (£5.69 incl. VAT + P.) Also available for 12V DC op £4.50. Post 45p (£5.69 incl. VAT + P.)  
400 watt UV lamp and ballast complete £38.00. Post £3.60 (£47.73 incl. VAT + P.). 400 watt UV lamp only £14.00. Post £1.50 (£17.83 incl. VAT + P.).

## WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details.  
**PROGRAMME TIMERS**  
240V A.C. operation. 12 individually adjustable cams. £7.50 + 75p P. & P. (£8.49 incl. VAT). R. T.  
6 adjustable 6 fixed cams. Price £8.00 + 75p p. & p. (£9.75 incl. VAT). R. & T.

## Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.  
25 WATT 10/25/50/100/250/500/1kΩ  
1.5kΩ £2.40. Post 20p (£2.99 incl. VAT & P.)  
50 WATT 2500 £2.90. Post 25p (£3.62 incl. VAT & P.)  
100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £6.90 p. & p. 35p (£8.34 incl. VAT).  
Black, Silver, Skirted knob calibrated in Nos. 1-9 1/2 in. dia brass bush ideal for above Rheostats 24p each.

## RELAYS

Wide range of A.C. and D.C. relays available from stock. Phone or write in your enquiries.  
Other types available - phone for details. N.M.S.  
230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.96 incl. VAT & P.).  
T.E.C. open type 3 c/o. 10 amp £1.10 (£1.50 incl. VAT & P.).  
MKMI Relay. 230V. A.C. 1 c/o. open type 10 amp contact, mf. by "Kevswitch" 80p. + 20p. p. & p. (£1.15 incl. VAT). 5 for £3.75 post paid (£4.32 incl. VAT).

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 incl. VAT & P.) Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.38 incl. VAT & P.) Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.67 incl. VAT & P.) Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.78 incl. VAT & P.) 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.78 incl. VAT & P.) (lamps = contact rating). P&P on any Relay 20p.

Hallermann Deutch. Hermetically sealed sub-min. Relay. 12-24V. D.C. 2 c/o. 850 ohm coil. 0.2 p. ch. P.C. mounting. L. 20 mm. W. 10mm. H. 12mm. Fraction of maker's price: £2.50 post paid (£2.88 incl. VAT). N.M.S.

Diamond H heavy duty P.C. Relay 230/240V a.c., two C/O contacts 25 amps res at 250 a.c. £2.50 p&p 50p (£3.45 incl. VAT + p&p). Special base 50p. (incl. VAT 58p) N.M.S.

## GEARED MOTORS

4.5rpm SIGMA motors approx. 35lbs inch  
7rpm KLAXON motors approx. 25lb inch  
28rpm WYNSCALE motors approx. 20lb inch  
71rpm WYNSCALE motor approx. 10lb inch  
Above four motors are designed for 110V. A.C. supplied with auto transformer 240V. A.C. operation. £7.75 p. & p. 75p. Total incl. VAT £9.78. N.M.S.

19 rpm. FHP 220/240V a.c. reversible; torque 1.5 kg. Gear ratio 44:1. Brand new including capacitors. mf. CITENCO. Price: £14.25 + £1.25 P. & P. (£17.83 incl. VAT). N.M.S.

30 rpm. 230/240V. a.c. 50lb. in. mf. PARVALUX. Price: £15.00 + £1.50 P. & P. (£18.98 incl. VAT). N.M.S.

56 rpm. 240V. a.c. 50lb. in. 50Hz 0-7 amp. Shaft length 35mm. Dia. 16mm. Wt. 6kg. 600g. mf. FRACMO. Price: £15.00 + £1.50 P. & P. (£18.98 incl. VAT). N.M.S.

100 rpm. 110V. a.c. 115lb. in. 50Hz. 2.8 amp. single phase split capacitor. Immense power. Totally enclosed. In-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm. length 145mm. Tested. Price: £12.00 + £1.50 P. & P. (£15.53 incl. VAT). R. & T. Suitable transformer for 230/240V operation. Price £8.00 + 75p. P. & P. (£10.06 incl. VAT).

200 rpm. 35 lbs. in. 115V 50Hz. Price: £16.00 + £1.50 P. & P. (£20.13 incl. VAT). N.M.S. Suitable transformer for 230/240V a.c. Price: £8.00 + £1.00 P. & P. (£10.35 incl. VAT). N.M.S.

1 rpm 230/240V. a.c. Synchronous geared Motor, mf. HAYDON. 2 rpm 230/240V. a.c. Synchronous geared Motor, mf. CROUZET. Either type £2.90 + 30p. P. & P. (£3.88 incl. VAT). N.M.S.

1.400 rpm 115V. a.c. Motor, HP 1/2 continuously rated. Fitted with anti-vibration cradle mounting. Mf. FRACMO. Supplied complete with Transformer for 230/240V. a.c. operation. Price: £10.00 + £1.00 P. & P. (£12.85 incl. VAT). N.M.S.

## 24V. D.C. GEARED MOTOR

24V. D.C. 200 rpm 10lbs/ins. continuously rated geared Motor mfg. by either Parvalux or Carter. Easily removable from heavy all chassis containing 9-24V. D.C. Solenoids, microswitches, friction clutch, precision gearing etc. etc. Ex-equipment London Transport Ticket Printer. Price: £11.00 + £2.00 p. & p. (total incl. VAT £14.95).

## 24V. D.C. REVERSIBLE MOTOR

Parvalux type SD12L. 24 D.C. shunt wound Motor, either 133 rpm 65lbs in Gearbox ratio 30:1. Current 6.8 amp. Rating continuous. Will operate on reduced power and speed at 9V D.C. or less. Shaft Dia 16mm, Width 150mm, Shaft dia. 16mm. Price £16.00 + £2.00 p. & p. (£20.70 incl. VAT). N.M.S. or 60 rpm 100lb in rating. Price as above. N.M.S.  
100W Rheostat 1 ohm speed control available £6.90 (£7.94 incl. VAT).

## ROTARY CARBON VANE VACUUM & COMPRESSOR

Direct coupled to 1/3 hp. 110/115V. A.C. Motor 4.2 amp. 1380 rpm. Motor manu. by A.E.I. or G.E.C. Pump by Williams. Max. Vac. 25" H.G. Max. pressure cont. 10 p.s.i. Int. 15 p.s.i. Max. airflow 3 c.f.m. at 0" H.G. Price: £30.00 + £3.00 P. & P. (£37.95 incl. VAT). N.M.S.  
Suitable transformer for 240V op. £10.00 P. & P. £2.00 (£13.80 incl. VAT). N.M.S.

## COMPRESSOR

Precision built USA. Horizontally opposed twin head diaphragm type producing 20lbs. approx. P.S.I. per head. 3.5 plus C.F.M. Output virtually pulse free. Powered by 110V A.C. motor size 30 x 23 x 15cm. Weight 7 kilos. Price £25.00 + £2.00 P. & P. (Total incl. VAT £31.05). N.M.S.  
Suitable transformer for 240V op. £8.00 P. & P. £1.50 (£10.93 incl. VAT).

## VERY EXCEPTIONAL OFFER REDUCTION DRIVE GEAR BOX.

Ratio 72:1. Input spindle 1/2 x 1/2 in. Output spindle 1/2 x 3 in. long. Overall size approx: 120 x 98 x 68 mm. All metal construction. Ex-equip. tested. Price: £2.00 + 50p. (incl. VAT £2.88).

## A.C. Wkg. TUBULAR CAPACITORS.

Fraction of makers price. Motor start etc.			
1.5 mfd. 440V. A.C.	80p	7.5 mfd. 200V. A.C.	£1.00
2 mfd. 250V. A.C.	80p	10 mfd. 250V. A.C.	£1.00
2 mfd. 450V. A.C.	75p	10 mfd. 400V. A.C.	£1.75
2.2 mfd. 440V. A.C.	75p	14 mfd. 400V. A.C.	£3.00
3 mfd. 440V. A.C.	£1.00	15 mfd. 250V.	£1.50
4.1 mfd. 440V. A.C.	£1.00	(Block)	£1.50
5 mfd. 400V. A.C.	£1.25	19 mfd. 280V. A.C.	£2.00
5.3 mfd. 180V. A.C.	60p	20 mfd. 250V. A.C.	£2.25
5.4 mfd. 280V. A.C.	75p	50 mfd. 370V.	£5.00
6.5 mfd. 280V. A.C.	£1.00	(Block)	

P. & P. up to 2.5 mfd. 25p. 3 mfd tp 20 mfd. 50p. 50 mfd. £1.50. All plus V.A.T. N.M.S.

## Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs at any manually pre-set time 36 Hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £9.00. P. & P. 75p (£11.22). R. & T.

## SANGAMO WESTON TIME SWITCH

Type 525 1 200/250V a.c. 2 on/2 off every 24 hours 20 amp contact with override switch dia. 4 x 3 price £8.00 P. & P. 50p incl. VAT £9.78. Also available with Solar dial. R. & T.

N.M.S. New Manufacturers Surplus R & T Reconditioned and Tested

# SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01 995 1600

All Mail Orders Callers Ample Parking Space Showroom open Mon-Fri.

ACCOUNT CUSTOMERS MIN. ORDER £10.00

Personal callers only Open Saturdays 9 Little Newport Street, London WC2H 7JJ Phone 01-437 0576

# STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy  
and **STEP UP TO  
MAPLIN SERVICE  
NOW**



Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_



PE 980

## **MAPLIN**

**ELECTRONIC SUPPLIES LTD**

All mail to:-

**P.O. Box 3, Rayleigh, Essex SS6 8LR.**

**Telephone: Southend (0702) 554155.**

**Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).**

**Telephone: Southend (0702) 554000.**

**Catalogue now available in all branches of WHSMITH  Price £1.00**