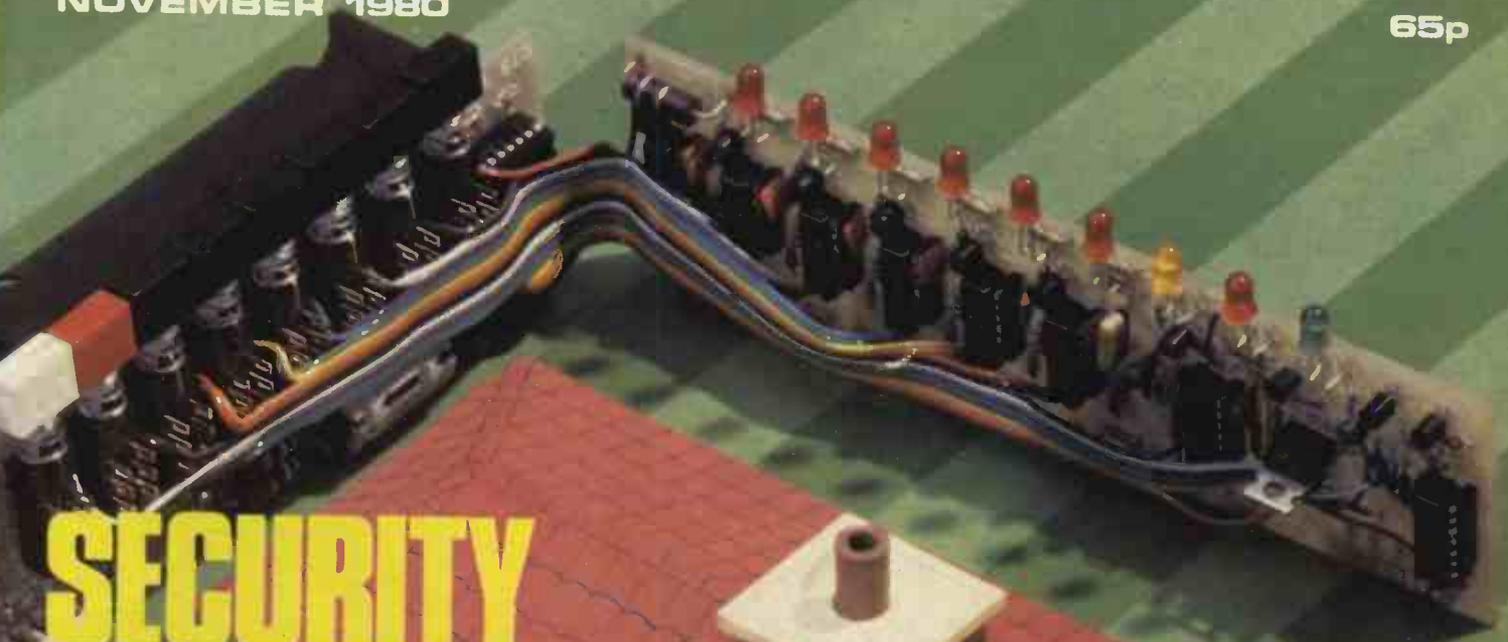


PRACTICAL

ELECTRONICS


NOVEMBER 1980

65p



SECURITY SENTINEL

Also...
SPEECH SYNTHESIS - Part 1

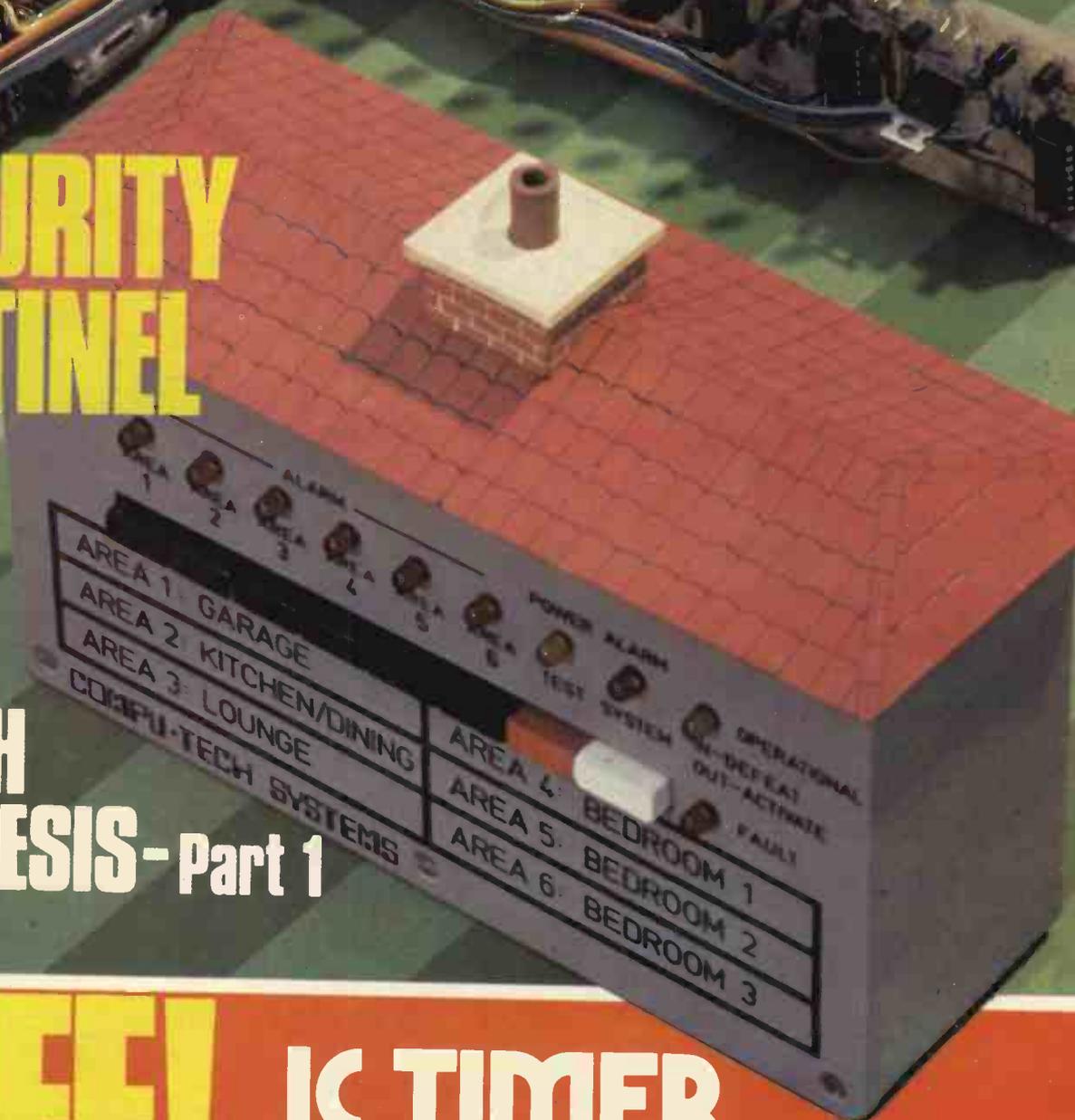

FREE!

Chart

IC TIMER NOMOGRAPHS

Unique in concept—the home computer that grows as you do!


The Acorn Atom

£120

plus VAT and p&p

Special features include

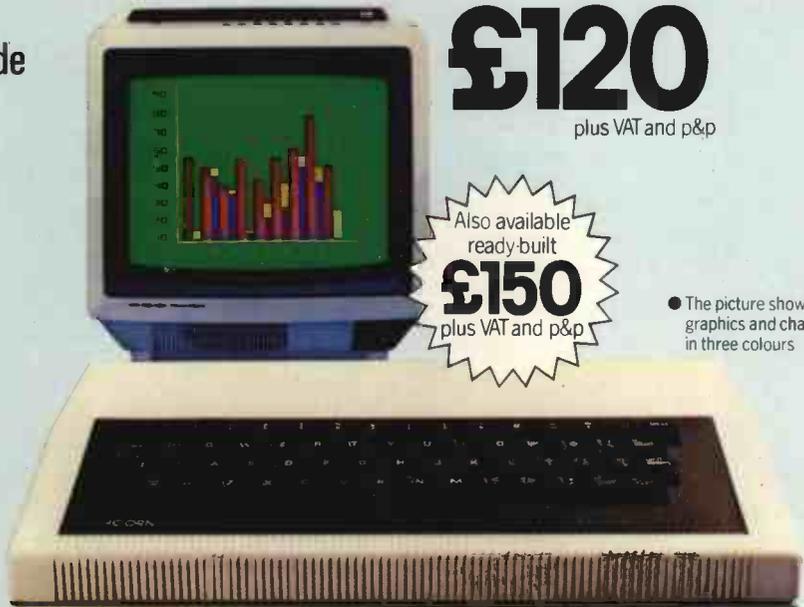- * FULL SIZED KEYBOARD
- * ASSEMBLER AND BASIC
- * TOP QUALITY MOULDED CASE
- * HIGH RESOLUTION COLOUR GRAPHICS*



Also available ready-built


£150

plus VAT and p&p

● The picture shows mixed graphics and characters in three colours

*.optional

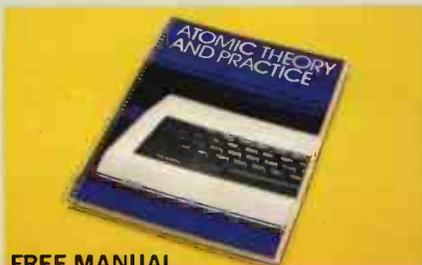The Acorn Atom is a definitive personal computer. Simple to build, simple to operate. A powerful, full facility computer with all the features you would expect. Just connect the assembled computer to any domestic TV and power source and you are ready to begin. (Power requirement: 8V at 800mA). There is an ATOM power unit available - see the coupon below.



FREE MANUAL

Free with every ATOM, kit or built, is a computer manual. The first section explains and teaches you BASIC, the language that most personal computers and the ATOM operate in. The instructions are simple and learning quickly becomes a pleasure. You'll soon be writing your own programs. The second section is a reference

manual giving a full description of the ATOM's facilities and how to use them. Both sections are fully illustrated with example programs.

The standard ATOM includes:

HARDWARE

- Full-sized QWERTY keyboard
- 6502 Microprocessor
- Rugged injection-moulded case
- 2K RAM
- 8K HYPER-ROM
- 23 integrated circuits and sockets
- Audio cassette interface
- UHF TV output
- Full assembly instructions

SOFTWARE

- 32-bit arithmetic ($\pm 2,000,000,000$)
- High speed execution
- 43 standard/extended BASIC commands
- Variable length strings (up to 256 characters)
- String manipulation functions
- 27 x 32 bit integer variables
- 27 additional arrays
- Random number function
- PUT and GET byte
- WAIT command for timing
- DO-UNTIL construction
- Logical operators (AND, OR, EX-OR)
- Link to machine - code routines
- PLOT commands, DRAW and MOVE

The ATOM modular concept

The ATOM has been designed to grow with you. As you build confidence and knowledge you can add more components. For instance the next stage might be to increase the ROM and RAM on the basic ATOM from 8K + 2K to 12K + 12K respectively. This will give you a direct printer drive, floating point mathematics, scientific and trigonometric functions, high resolution graphics.

From there you can expand indefinitely. Acorn have produced an enormous range of compatible PCB's which can be added to your original computer. For instance:

- A module to give red, green and blue colour signals
 - Teletext VDU card (for Prestel and Ceefax information)
 - An in-board connector for a communications loop interface - any number of ATOMs may be linked to each other - or to a master system with mass storage/hard copy facility
 - Floppy disk controller card.
- For details of these and other additions write to the address below.



ACORN COMPUTER 4a Market Hill, CAMBRIDGE CB2 3NJ

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. All components are guaranteed with full service/repair facility available.

Please send me the following items:

Quantity	Item	Item price inc. VAT+p&p	TOTALS
	ATOM KIT - 8K ROM + 2K RAM (MIN)	@ £140.00	
	ATOM ASSEMBLED-8K ROM+2K RAM (MIN)	@ £174.50	
	ATOM KIT - 12K ROM + 12K RAM (MAX)	@ £255.00	
	ATOM ASSEMBLED-12K ROM+12K RAM (MAX)	@ £289.50	
	1K RAM SETS	@ £11.22	
	4K FLOATING POINT ROM (inc in 12K Version)	@ £23.30	
	PRINTER DRIVE	6522 VIA @ £10.35	
	(inc in 12K version)	LS244 Buffer @ £3.17	
	MAINS POWER SUPPLY (1.3 amps)	@ £10.20	
		TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £ _____

Please debit my Access/Barclaycard No. _____

Signature _____

Name (Please print) _____

Address _____

Telephone No. _____

Registered No: 1403810. VAT No: 215 400 220

PE/11/80



PRACTICAL ELECTRONICS

VOLUME 16

No. 11

NOVEMBER 1980

CONSTRUCTIONAL PROJECTS

GAMES TIMER by <i>Stephen Ibbs</i>	23
With "booby" delay for added suspense	
SECURITY SENTINEL Part 1 by <i>W. C. Dickinson</i>	32
Control Unit for a complete home security system	
PE TELETXT Part 4 by <i>David Shortland</i>	48
Wiring and Testing—conclusion of series	
PE DIAMATIC UPDATE by <i>J. R. W. Ames and W. L. Blyth</i>	52
Overcoming two common problems	
DISCO DECK Part 3 by <i>Ben J. Duncan</i>	56
Final Cards	

GENERAL FEATURES

SPEECH SYNTHESIS Part 1 by <i>Dr. A. A. Berk</i>	26
Fundamental theory of synthesised speech	
SEMICONDUCTOR UPDATE by <i>R. W. Coles</i>	39
HNVM3008 MM58174 TLO11	
MICROPROMPT	40
Help, and calls for help	
RESIDENT EDITOR by <i>N. A. Climpson</i>	43
Put the Editor in Monitor for instant use	
INGENUITY UNLIMITED	68
TTL Logic Tester—Light Triggered Variable Pulse—R/C Failsafe and Servo Tester—Logic Probe Op-Amp Tester—Shoot Game	

NEWS AND COMMENT

EDITORIAL	17
MARKET PLACE	18
New Products	
INDUSTRY NOTEBOOK by <i>Nexus</i>	20
Looking on the bright side . . .	
SPECIAL OFFER . . . PE CONGRESS	31
Save £15 on the Congress Amplifier kit	
NEWS BRIEFS	44
SPACEWATCH by <i>Frank W. Hyde</i>	47
False Alarms—The Viking Mission—The Sun	
COUNTDOWN	51
POINTS ARISING	51
Micro Prompt—Programmable Sound Generator—PE Magnum	
PATENTS REVIEW	55
Ingenious ideas from original thinkers	
READOUT	61
A bumper batch of your letters	
BOOK REVIEW	62
TURNTABLE OFFER	66
For Disco and general audio applications	

OUR DECEMBER ISSUE WILL BE ON SALE FRIDAY, 14 NOVEMBER 1980

(for details of contents see page 65)

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum order £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 40p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: (Axial Lead Type)

400V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 99p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 48p; 1µF 64p; 2µF 82p; 4µF 85p, 1000V: 10n, 15n, 20n; 22n 22p; 47n 26p; 100µ 42p; 470n 80p; 1µF 175p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:

10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p, 680n 19p; 1µF 22p; 2µF 30p; 2µF 34p.

ULTRASONIC TRANSDUCERS

.40KHz 350p pr.

ELECTROLYTIC CAPACITORS: (Values in µF)

500V: 10 50p; 47 78p; 250V: 100 85p; 83V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 9p; 10, 15, 22 11p; 32, 47, 50 14p; 63, 100, 27p; 50V: 100, 220 25p; 470 32p; 1000 80p; 40V: 22, 33µF 8p; 100 12p; 220, 330 85p; 470 115p; 35V: 10, 33 8p; 330, 470 32p; 25V: 10, 22, 47, 100 8p; 160, 220, 250 15p; 470 25p; 640, 1000 35p; 1500 40p; 2200 54p; 3300 77p; 4700 92p; 18V: 10, 40, 47 7p; 100, 125 8p; 220, 330 16p; 470 20p; 1000, 1500 30p; 220 36p; 10V: 1007p.

ULTRASONIC TRANSDUCERS

.40KHz 350p pr.

TANTALUM BEAD CAPACITORS:

35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 1.5, 2.2, 3.3, 4.7, 25V: 10, 20p each. 1µF, 2µF, 4µF, 10, 20p each. 5K-2M single gang 29p 5K-2M dual gang D/P switch 69p 5K-2M dual gang stereo 89p 1W Wire-wound 500-20K 105p

POTENTIOMETERS: Carbon Track, 0.25W Log & Linear Values.

500Ω, 1K & 2K (LIN ONLY) Single 29p 5K-2M single gang 29p 5K-2M single gang D/P switch 69p 5K-2M dual gang stereo 89p 1W Wire-wound 500-20K 105p

MYLAR FILM CAPACITORS

100V: 0.001, 0.002, 0.005, 0.01µF 6p 0.015, 0.02, 0.03, 0.04, 0.05, 0.056µF 7p 0.1µF 8p; 50V: 0.47µF 12p.

SLIDER POTENTIOMETERS

0.25W log and linear values 60mm track 5KΩ 500KΩ Single gang 60p 10KΩ 500KΩ Dual gang 80p Self-Stick graduated Alum. Bezels 36p

CERAMIC CAPACITORS: (50V)

Range: 0.5pF to 10nF 4p 15nF, 22nF, 33nF, 47nF 5p 100nF/30V 7p; 220nF/5V 8p

PRESET POTENTIOMETERS

0.1W 500-2.2M Min. Vert. & Horiz. 7p 0.25W 100Ω-3MΩ Horiz. larger 10p 0.25W 250Ω-4.7MΩ Horiz. 10p Precision Cermet 1W 100Ω-100K 90p

POLYSTYRENE CAPACITORS:

10pF to 1nF 8p; 1.5nF to 47nF 10p.

SILVER MICA (pF)

2, 3, 3.3, 4.7, 6.8, 8.2, 10, 12, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180, 200, 220 11p each 250, 270, 300, 330, 360, 390, 470, 600, 800 & 820pF 1000, 1000, 200, 1800, 2000, 470 28p each

TRIMMERS miniature

2.5pF-3.10pF 3p 3pF-30pF 28p 5-25pF 65pF 88pF 35p

COMPRESSION

3-40pF: 10-80pF 30p 15-200pF 33p 100-500pF 45p 100-1200pF 55p

RESISTORS—Erie make 5% carbon

Miniature High Stability, Low Noise Range: 1.99 - 100.0 0.25W 202-4-M7 E24 2p 1p 0.5W 202-4-M7 E12 2p 1p 1W 202-10M E12 5p 3p 2% Metal Film 100-1M 6p 4p 1% 0.5W 51Q-1M E24 8p 6p 100.0 price applies to Resistors of each type not mixed values.

TRANSISTORS

AC107	28	BC307B	14	BFX86	28	TIP33C	78	2N1132	28
AC125	36	BC306B	12	BFX87	16	TIP34A	88	2N1303	50
AC126	25	BC328	15	BFX88	28	TIP34C	88	2N1304	50
AC127	22	BC337	14	BFY50	21	TIP35A	188	2N1305	35
AC128	20	BC338	12	BFV51	21	TIP35C	170	2N1306	35
AC141	27	BC441	30	BFV52	21	TIP36C	190	2N1308	48
AC142	28	BC461	30	BFV56	32	TIP36E	170	2N1670	150
AC187	26	BC516	35	BFY64	40	TIP41A	55	2N1671B	215
AC176	26	BC517	38	BFY81	99	TIP41B	60	2N2192A	22
AC179	60	BC518	38	BRV39	39	TIP42A	60	2N2202A	25
BC547	60	BC547	60	BSX20	20	TIP42B	82	2N2222A	20
BC548	60	BC548	60	BSX29	10	TIP120	90	2N2222A	20
BC549	60	BC549	60	BSV29	10	TIPT1	190	2N2369A	17
BC548C	60	BC548C	60	BU105	170	TIP141	90	2N2646	48
BC549C	60	BC549C	60	BU205	170	TIP142	125	2N2784	55
BC559	60	BC559	60	BU205	170	TIP147	125	2N2902A	28
BC559C	60	BC559C	60	BU205	170	TIP2955	60	2N2905A	25
BC570	60	BC570	60	BU205	170	TIP3055	60	2N2906	22
AD149	75	BCY71	14	IMD8001	225	TIP3055	60	2N2907A	22
AD161	42	BCY72	20	IMJ491	175	TIS43	30	2N2907A	22
AD162	42	BD121	78	IMJ2955	95	TIS44	45	2N2926G	10
AD162	42	BD123	98	IMJ340	54	TIS45	45	2N3053	55
AD162	42	BD124	115	IMJ370	54	TIS88A	50	2N3054	55
AD162	42	BD125	115	IMJ370	54	TIS90	30	2N3055	48
AD162	42	BD126	115	IMJ370	54	TIS91	32	2N3442	140
AD162	42	BD127	115	IMJ370	54	UC73A	65	2N3504	55
AD162	42	BD128	115	IMJ370	54	UC73A	65	2N3504	55
AD162	42	BD129	115	IMJ370	54	UC73A	65	2N3504	55
AD162	42	BD196	115	IMJ370	54	UC73A	65	2N3504	55
AD16									

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES		BRIDGE RECTIFIERS		SPEAKERS	
AA129	25	2A/50V	20	80.0.3W	75
AA215	15	1A/100V	22	2x2.5"	79
BY100	24	1A/200V	25	40Q 2.5"	88
BY127	12	1A/400V	29	80Q 2.5"	80
CRO33	158	1A/600V	34	80.5W	80
OA9	45	2A/50V	35	7"x4"	250
OA47	18	2A/100V	44	8Q 3W	150
OA70	12	2A/200V	46	6"x4"	160
OA79	12	2A/400V	53		
OA81	15	2A/600V	65		
OA85	15	4A/100V	72		
OA90	8	6A/100V	73		
OA91	8	6A/200V	78		
OA95	8	8Y164	86		
OA200	9	8Y168	85		
OA202	9	8Y180	85		
IN914	6				
IN916	6				
IN4003	6				
IN4004/5	6				
IN4006/7	7				
IN4148	4				
IS44	20				
3A/100V	18				
3A/400V	20				
3A/600V	27				
3A/1000V	30				
SCR's		Noise Diode		VEROBOARD	
0.8A30V	28	Z5J	180	Pitch	
0.8A100V	30			0-1	0-15
0.8A200V	35			0.15	0.15
1A/100V	42			(copper clad)	(plain)
1A/200V	47			2x3x3"	66p 59p 47p 34p
1A600V	70			2x5x5"	75p 69p 51p 39p
3A/400V	75			3x3x3"	75p 51p 34p 25p
5A300V	35			3x5x5"	86p 92p 72p 83p
5A600V	43			3x7x7"	296p 260p 210p 178p
8A300V	48			4x2x7"	387p 280p
12A300V	59			Pkt of 36 pins	20p VQ board 144p
12A500V	92			Spot face cutter	107p DIP board 32p
12A800V	150			Pin insertion tool	147p Veroblock 324p
15A700V	195				
BT116	150				
BT118	150				
C106D	38				
MCR101	32				
TC144	22				
TC145	22				
2N4444	140				

OPTO ELECTRONICS		VOLTAGE REGULATORS		CRYSTALS	
LEDS Plus, Clip		1A TO3 +ve -ve		100kHz	300p
TIL209 Red 125"	13	5V 7805 145p	7905 220p	455kHz	370p
TIL211 Grn 125"	18	12V 7812 145p	7912 220p	1.2MHz	392p
TIL212 Yellow	22	18V 7815 145p		1MHz	295p
0.2" Yel. Gm. Amber	15	18V 7818 145p		1.008MHz	383p
Rectangular LEDs	18	1A	TO220 Plastic Casing	1.80MHz	300p
Red, Green and Yellow	30	5V 7805 60p	7905 85p	1.8432MHz	305p
2N5717 45; OCP71	120	12V 7812 60p	7912 85p	2.4576MHz	290p
ORP12	63	18V 7815 60p	7915 85p	3.2768MHz	290p
LD271 Infra Red (emit)	40	15V 7818 60p	7918 85p	3.57954M	150p
TIL32 Infra Red (emit)	58	24V 7824 60p		4MHz	290p
SFH205 (detector)	70	100mA TO92 Plastic Casing		4.032MHz	323p
TIL78 (detector)	70	5V 78L05 30p	79L05 65p	4.433619M	135p
OPTO isolators		8V 78L62 30p		5.0MHz	355p
IL74	48	6V 78L82 30p		5.24288	425p
TIL 111/2 or 117	100	12V 78L12 30p	79L12 85p	6.0MHz	392p
7 Seament Displays		15V 78L15 30p	79L15 65p	6.5536MHZ	200p
TIL 312 & 313 0.3"	105	CA3085	95	7.680MHz	323p
TIL322 5" C.An	115	LM300H	170	8.0MHz	392
TIL322 5" C.Ch	115	LM305H	140	8.0833M	382p
DL704 3" C.Ch	99	LM309K	135	8.867MHz	323p
DL707 3" C.Anod	99	LM317K	350	9.375MHz	323p
DL747 6" An	180	LM273	39	10MHz	323p
.8" Orange C.A.	250	78H05 5V/5A 595p	TA6258	10.7MHz	323p
FND357 or 500	120	UA78HG +5 to +24V 5A	650	12MHz	392p
.3" Green C.A.	150			14.318118M	300p
±1.3" Red or Green	150			18MHz	323p
Bargraph 10 seq. Red	225			18.432M	392p
				20MHz	362p
				26.69MHz	390p
				27.648MHz	350p
				38.6667M	250p
				48MHz	323p
				100MHz	323p

SWITCHES		SUB-MIN TOGGLE		DIL PLUGS (Headers)	
SLIDE 250V		TOGGLE 2A 250V		14 pin 35p; 24 pin 85p	
1A DPDT	14	SPST	32	16 pin 39p; 40 pin 295p	
1A DPDT C/OFF	15	DPDT	44	(DIL Sockets on opp. page)	
1A DPDT	13	4 pole on off	54		
4 pole 2-way	24				
PUSH BUTTON		SP changeover	59		
Spring loaded red		SPST on off	54		
button. Latching		SPDT c/off	70		
SPST on off	65	SPDT Biased	85		
SPDT C/over	75	DPDT 6 tags	70		
DPDT 6 Tag	95	DPDT C/OFF	79		
		DPDT Biased	115		
		3 pole c/over	150		
		Push to make	15p		
		ROCKER: 5A, 250V, SPST	30p		
		ROCKER: (white) 5A 250V SPDT	52p		
		changeover	52p		
		ROCKER: With neon lights red when on.	85p		
		3A 250V. OPST	85p		
		ROCKER: (White) 10A/250V DPDT	85p		
		ROTTARY: "Make-A-Switch" Make your own multiway Switch as required. Shifting assembly has adjustable stop. Accommodates up to 6 Wafers	90p		
		Break before make Wafers. Silver contacts.	90p		
		1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6 pole/2 way	62p		
		Mains DPST Switch to fit	60p		
		Screen & Spacers	6p		
		ROTTARY: (Adjustable Stop Type)			
		1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	45p		
		ROTTARY: Mains 250V AC, 4 Amp	52p		

COMPUTER CORNER	
● SUPERBOARD II Ready-built & tested (requires PSU)	Only: £150
● PSU 5V/3A for above incl. UHF Mod.	£24
● UK10 Expansion Board (8K)	£150
● UK101 Complete Kit incl. Instructions	£179
● Challenger 1P Cased	£188
● Plastic Case for Superboard, fits UK101, NASCOM etc.	£25
● Space Invaders for Superboard (4K)	£5
● PRINTER 800. Ideal for PET, Apple, TRS80, Superboard etc.	Only: £325
● VIDED GENIE based on TRS80 16K RAM	Only: £290
● STRINGY FLOPPY (economy of Cassette, speed of Disc)	Only: £169
● SOFTY. Intelligent EPROM Programmer Kit	£99
● Ready-Built & Tested PSU for above (Bullit)	£20
● TEX UV EPROM Eraser. Erases up to 32 ICs in 15-30 min.	£33
● UHF MODULATORS 6MHz	280p
● UHF MODULATORS 8MHz	450p
● KEYPADS 4 x 4 matrix	350p
● Model 756 ASCII Keyboard	£40
● 10 x C12 Cassettes in stockable racks	£5.50
We stock a wide selection of Computer Books.	

TRANSFORMERS (mains Prim. 220-240V)	
6-0-6V 100mA; 9-0-9V 75mA; 12-0-12V 75mA	98p
8VA type: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A 215p.	
12VA: 4.5-1.3A 4.5V-1.3A; 6V-1.2 6V-1.2A 12V-5A 12V-5A 235p (30p p8p)	
24VA: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A 15-8A; 20V-6A 20V-6A 320p(55p p8p)	
50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-1A 30V-1A 365p (60p p8p)	
100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A 695p(74p p8p)	
AUTO (Step Down) TRANSFORMERS:	
Prim: 240V Sec. 115V 50/60Hz	
50VA: £5.95 (60p); 100VA: £7.40 (70p)	
150VA: £9.95 (70p); 250V: £14.75 (85p)	
(N.B. P&P charge to be added above our normal postal charge.)	

3 1/2 DIGIT LCD MULTI-METER KITS



BUILD YOUR OWN PROFESSIONAL QUALITY DMM AS ALREADY USED BY HUNDREDS OF LABORATORIES, RESEARCH UNITS, UNIVERSITIES ETC. THE LASCAR RANGE OF MULTIMETERS IS NOW ALSO AVAILABLE IN KIT FORM, CONTAINING ALL PARTS NEEDED TO CONSTRUCT THESE SUPERBLY STYLED MULTIMETERS - EVEN BATTERIES AND TEST LEADS. BOTH TYPES FEATURE FIVE FUNCTIONS (AC AND DC VOLTS, AC AND DC CURRENT RESISTANCE) WITH ABILITY TO CHECK DIODES. 0.5" LCD DISPLAY WITH 'BATTERY LOW' WARNING. AUTO-POLARITY, AUTO-ZERO. FULL PROTECTION AGAINST OVERLOADS AND TRANSIENTS, CAN WITHSTAND MAINS ON ANY RANGE. RUGGED ABS CASES AND A COMPREHENSIVE 1-YEAR WARRANTY.

The LMM 200 has been featured as a project in the July 80 Practical Electronics. It is a compact handheld multimeter with a 0.5% basic accuracy and 15 different ranges. It measures AC/DC voltage from 0.1mV to 500V, AC/DC current from 0.1µA to 2 Amps and resistance from 0.1Ω to 2MΩ. 200 hours battery life.

The LMM 100 is suitable for field or bench use. It has a basic accuracy of 0.1% and 25 different ranges. It measures AC/DC voltage from 0.1mV to 1kV, AC/DC current from 0.1µA to 2 Amps and resistance from 0.1Ω to 20MΩ. Battery life is over 2,000 hours. It also features a unique 'digital hold' facility and adjustable carrying handle.

We also offer a calibration service (£5.00 + VAT = £5.75) and a trouble-shooting and calibration service (£7.50 + VAT = £8.62).

	£	P & P	VAT	TOTAL
LMM 200 Kit (PE DMM)	32.95	1.00	5.09	39.04
LMM 100 Kit	58.95	1.75	9.10	69.80
LMM 200 FULLY ASSEMBLED (INC. LEADS)	39.70	1.25	6.14	47.09
LMM 100 FULLY ASSEMBLED (INC. LEADS)	77.50	1.75	11.88	91.13

Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data LMM 200 Kit £39.04 LMM 100 Kit £69.80 Assembled LMM 200 £47.09 Assembled LMM 100 £91.13

Name _____
 Address _____
 Tel. No. _____
 I enclose cheque/P.O. value

Orders may be phoned quoting your Access or Barclaycard No. Official orders accepted.



Marshall's

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr. service
Also retail shops: 325 Epsom Road, London W2
40 Cricklewood Broadway, London NW2 85 West Regent St., Glasgow
108A Stokes Croft, Bristol

We now supply the extremely reliable and cost conscious LEADER range of testgear.

SINGLE TRACE OSCILLOSCOPES		
LBO 510A 5" 4MHz 20mV		£125.00
LBO 517A 5" 10MHz 10mV		£170.00
LBO 513A 5" 10MHz 10mV		£215.00
LBO 507A 5" 20MHz 10mV		£230.00

DUAL TRACE OSCILLOSCOPES		
LBO 308S 3" 20MHz 2mV		£419.00
LBO 568A 5" 20MHz 10mV		£298.00
LBO 570A 5" 35MHz 5mV		£375.00
LBO 514 5" 10MHz 5mV		£250.00

T.V. RADIO TEST GEAR		
LSG 16 Signal Generator		£ 49.00
LSG 231 F.M. Stereo Signal Generator		£109.00
LCG 397U P.A.I. B Pattern Generator		£189.00


AUDIO TEST GEAR		
LAC 26 Audio Generator		£ 60.00
LAC 120A Audio Generator		£119.00
LDM 170 Distortion Meter		£225.00
LFM 39A Wow Flutter Meter (Dist)		£249.00
LIM 39A Wow Flutter Meter (Dist)		£289.00
LAV 191 Audio Tester		£249.00
LAC 125 Low Distortion Audio Generator		£229.00

GENERAL TEST GEAR		
LCH 740 LCR Bridge		£135.00
LTC 906A Transistor Checker		£ 90.00
LVT 72 FET Transistor Checker		£119.00
LTC 907 Transistor Checker		£139.00
LAT 47 Attenuator		£135.00
LAT 45 Attenuator		£ 75.00
LFG 1300 Sweep Function Generator		£299.00

AMATEUR RADIO		
LDM 815 DIP Meter		£ 43.00
LIM 870A Antenna Impedance Meter		£ 41.00
LPM 880 RF Power Meter		£ 69.00
LPM 885 SWR Watt Meter		£ 44.00
LAC 895 Antenna Coupler		£ 85.00
LAC 896 Antenna Coupler		£ 41.00
LAC 897 Antenna Coupler		£ 41.00

Please send large SAE for special catalogue. All prices exclusive VAT/carriage.

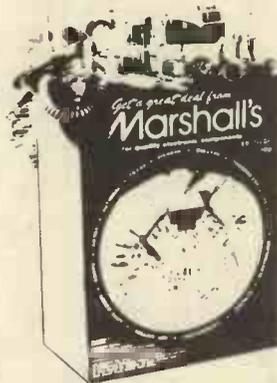The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.



Lots of old friends, but also many new products including leader test gear, Crimson Hi Fi Modules, Rechargeable Ni Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc. Available by post, UK 75p post paid: Europe 95p post paid: Rest of world £1.35 post paid.

SINCLAIR INSTRUMENTS

Digital Multimeter		
"	PDM35	£ 34.50
"	DM235	£ 52.50
"	DM350	£ 72.50
"	DM450	£ 99.00
Digital Frequency Meter		
	PFM200	£ 49.80
Low Power Oscilloscope		
	SC110	£139.00

NEW

TF200	Frequency Meter	
		£145.00
TGF105	Pulse Generator	
		£ 85.00

CRIMSON ELEKTRIK HI FI MODULES

CE608	Power Amp	£20.09
CE1004	" "	£23.43
CE1008	" "	£26.30
CE1704	" "	£33.48
CE1708	" "	£33.48
CPS1	Power Unit	£19.52
CPS3	" "	£23.52
CPS6	" "	£30.00
CPR1	Pre Amp*	£32.17
CPR1S	Pre Amp	£42.52

All Prices + VAT + postage/packaging

Don't forget! We also carry an impressive range of semi-conductors, passive components, electro mechanical components, tools etc.

DISCO LIGHTING KITS!!!

First class constructional projects, c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 £9.90	3 channel sound-to-light. 300 w/channel 1v - 100w input	LK2 £17.90	3 channel 3kW zero voltage firing 200mV - 100 watts input.
LK3 £5.50	2kW slider dimmer suitable for clubs/pubs. A professional unit c/w face plate.	LK4 £16.50	4 channel 4kW audio - forward/reverse auto - two speed ranges.

ALL KITS C/W

circuit, comprehensive instructions & full parts guarantee



Carriage on above 70p

Suitable case for LK 1/2/4 **£3.50**
100w spots ES or BC **£1.50**
Coloured pigmy lamps **65p**.

UNREPEATABLE HI-FI BARGAIN

3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:
★ 6 1/2" linen surround bass unit
★ 5" mid-range unit
★ 3" tweeter
★ 3 way crossover, fixing screws & baffle
★ 20 watts handling capability.
Full instructions provided
Must be heard to be believed!!

£9.95 + £1 carr. or two kits for **£20 carr. free.**

SAXON ENTERTAINMENTS

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.
(01) 684 8007

Order by phone - Access/Barclaycard/C.O.D.
Open Mon. - Sat. 9am - 5pm.

DORAM

DORAM
ELECTRONICS
LTD

Fitzroy House, Market Place,
Swaffham, Norfolk, PE37 7QH.

New Catalogue



40p

FREE
competition entry
with catalogue

to be refunded
with first order

REF. Dept. PE

Please send me a copy of your new catalogue

NAME

ADDRESS

I enclose cheque/postal order for 40p

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

- Book 1 Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.
- Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.
- Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.
- Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.



DESIGN OF DIGITAL SYSTEMS £12.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

- Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.
- Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

GUARANTEE No risk to you.

If you are not completely satisfied, your money will be refunded upon return of the books in good condition.

CAMBRIDGE LEARNING LIMITED, UNIT 26
RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON,
CAMBS., PE17 4BR, ENGLAND.
TELEPHONE: ST. IVES (0480) 67446

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice).

Please allow 28 days for delivery in U.K.

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.



COMPUTER PROGRAMMING IN BASIC £9.00

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL £4.40

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

ORDER FORM

Please send me the following books:-

- Digital Computer Logic & Electronics @ £7.00
- Design of Digital Systems @ £12.50
- Algorithm Writer's Guide @ £4.00
- Computer Programming in BASIC @ £9.00
- BASIC Handbook @ £11.50
- ANS COBOL @ £4.40
- Your Booklist (Free)

I enclose a *cheque/PO payable to Cambridge Learning Ltd.

for £..... (*delete where applicable)

Please charge my:

*Access/American Express/Barclaycard/Diners Club/Eurocard/Visa/
Mastercharge/Trustcard

Credit Card No.....

Signature

Telephone orders from credit card holders accepted on 0480 67446 (Ansafone).

Overseas customers (incl. Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name

Address

Cambridge Learning Limited, Unit 26, Rivermill Site,
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England.
(Registered in England, No. 1328762)

D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



BASIC COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. MINISONIC MK2 SYNTHESISER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available) and PCBs (incl. layout charts)

KIT 38-25 £80.12
£1.00

"Sound Design" booklet

P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic comps, PCBs and charts

KIT 76-7 £35.56
£1.36

Set of text photocopies

P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic comps, PCBs and charts

KIT 86-5 £33.60
£1.84

Set of text photocopies

P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser.

Set of basic comps, PCBs & charts

KIT 77-8 £107.86

ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic comps and PCBs (as publ.)

KIT 80-9 £148.66

Additional 3-octave extension and basic parts and PCBs (as published)

KIT 80-10 £56.38

Set of text photocopies

£1.81

ELEKTOR FORMANT SYNTHESISER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.)

KIT 66-14 £255.45

Set of text photocopies

£7.83

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90ms can be extended up to 450ms using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.)

KIT 78-3 £55.40

Extension unit basic comps and PCB (as publ.)

KIT 78-4 £52.77

Text photocopy

86p

ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100ms, and the additional set extends this up to 200ms. May be used in either mono or stereo mode.

Main unit basic component set

KIT 83-1 £29.49

Additional Delay basic components

KIT 83-2 £20.07

PCB (as publ.) to hold both kits

PCB9973 £4.52

Text photocopy

67p

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic comps & PCB (as publ.)

KIT 87-2 £6.84

Text photocopy

38p

NEW KITS

ELEKTOR CHOROSYNTH

A 2½-octave Chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage.

Basic comps, PCBs and charts but excl. sw's

KIT 100-8 £44.39

Text photocopy

70p

ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.)

KIT 101-1 £22.53

Text photocopy

60p

ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music signals.

Basic comps, PCB (as publ.)

KIT 99-1 £9.60

Text photocopy

40p

ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.)

KIT 98-1 £5.48

Text photocopy

20p

P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart

KIT 102-3 £17.58

Text photocopy

65p

P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart

KIT 96-1 £3.98

DISCO-CROSS FADER

The cross-fade between 2 decks is switch-initiated and can be preset on the panel for a cross fade rate of between about ½ sec & 24 secs. Basically a stereo unit but may be used in mono.

Basic comps, PCB & chart

KIT 94-1 £11.83

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic comps, PCBs & charts (excl. SWs)

KIT 85-5 £54.56

Set of text photocopies

£2.52

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic components, PCB & chart

KIT 88-1 £10.69

2-Notch extension, PCB & chart

KIT 88-2 £6.36

Text photocopy

68p

ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart

KIT 70-2 £21.67

Text photocopy

67p

ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic comps, & PCB (as publ.)

KIT 82-2 £22.45

Text photocopy

57p

P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart

KIT 42-3 £10.37

Text photocopy

28p

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic components, PCB & chart

KIT 56-3 £11.22

Text photocopy

68p

P.E. SMOOTH FUZZ

Basic components, PCB & chart

KIT 91-1 £6.40

Text photocopy

55p

TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Basic components, PCB & chart

KIT 54-1 £3.74

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.

Basic components, PCB & chart

KIT 74-1 £5.19

Text photocopy

39p

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, PCB & chart

KIT 75-1 £6.73

Text photocopy

38p

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control.

Basic components, PCB & chart

KIT 51-1 £4.93

P.E. AUTO-WAH UNIT

Automatically gives Wah or Swell sounds with each note played.

Basic components, PCB & chart

KIT 58-1 £9.68

Text photocopy

58p

ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space sawtooth, regular triangle, or square-wave with variable mark-space.

Basic comps, PCB & chart, but excl. sw's

KIT 67-1 £9.24

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Basic components, PCB & chart

KIT 89-1 £4.34

Text photocopy

78p

P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control depth.

Basic components, PCB & chart

KIT 53-1 £2.92

P.E. SYNTHESISER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Basic comps, PCBs & charts

KIT 23-33 £167.57

Set of text photocopies

£8.21

10% DISCOUNT VOUCHER (PE 83)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly coded. C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E. Does not apply to credit card orders.

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.70 each. Other goods: Under £5 add 50p. under £20 add 75p. over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 35p, other countries send 75p. **Note that we do not offer a C.O.D. service and that our terms are payment in advance.**

PHONOSONICS · DEPT PE88 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components

OVERSEAS enquiries for list Europe—send 35p; other countries—send 75p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £26.50 4 Octave (49 notes) £32.25 5 Octave (61 notes) £39.75

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each KBO note:
Type GJ — SPCO 33p ea. Type GB — 2 pr N/O 37p ea.

P.E. V.C.F.

A voltage controlled filter extracted from P.E. Minisonic project.
Basic comps, PCB & chart KIT 65-1 £8.45

P.E. RING MODULATOR

Extracted from P.E. Minisonic project.
Basic comps, PCB & chart KIT 59-1 £8.35

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.
Basic comps, PCB & chart KIT 28-1 £4.84
Text photocopy 28p

P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.
Basic comps, PCB & chart KIT 44-1 £5.73
Text photocopy 49p

P.E. ENVELOPE SHAPER WITH VCA

Has an Integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.
Basic comps, PCB & chart KIT 50-1 £8.03
Text photocopy 58p

P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.
Basic comps, PCB & chart KIT 63-2 £7.62
Text photocopy 58p

P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.
Basic comps, PCB & chart KIT 81-1 £3.90

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.
Set of basic components, incl. power supply, PCBs & charts KIT 46-3 £23.32
Text photocopy 97p

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.
Basic components, PCB & chart, but excl. sw. KIT 69-1 £8.19
Text photocopy 58p

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.
Basic comps, PCB & chart KIT 62-1 £5.31

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.
Basic components, PCB & chart KIT 79-4 £31.35
Text photocopy 78p

P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances.
Basic components, (excl. sw's.) and set of PCBs and charts. KIT 90-8 £61.25
Extra 2-channel set with PCB KIT 90-9 £11.62
Set of Text photocopies £1.50

STEREO HEADPHONE AMPLIFIER

Extracted from P.E. 6 channel mixer.
Basic components, PCB & chart KIT 92-1 £5.68

DIGITAL EXPOSURE UNIT

Controls up to 750 watts in $\frac{1}{2}$ second steps up to 10 minutes, with built-in audio alarm.
Basic components, PCBs & charts KIT 93-3 £23.27
Text photocopy £1.20

P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation, and with extra audio input.

Basic components, PCB & chart KIT 57-2 £26.12
Text photocopy 78p

RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, 128 beat almost infinite pattern, and pre-programmed 16 pattern using either M252 or M253 rhythm chips. A selection of effects instrument circuits is also available.

P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for discos.
Basic components, PCB & chart KIT 30-1 £4.37
Text photocopy 28p

P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.
Basic components, PCB & chart KIT 97-1 £8.07
Text photocopy 75p



PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name _____


Address _____

Age _____




To ICS, Dept 273A, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

Pure ind

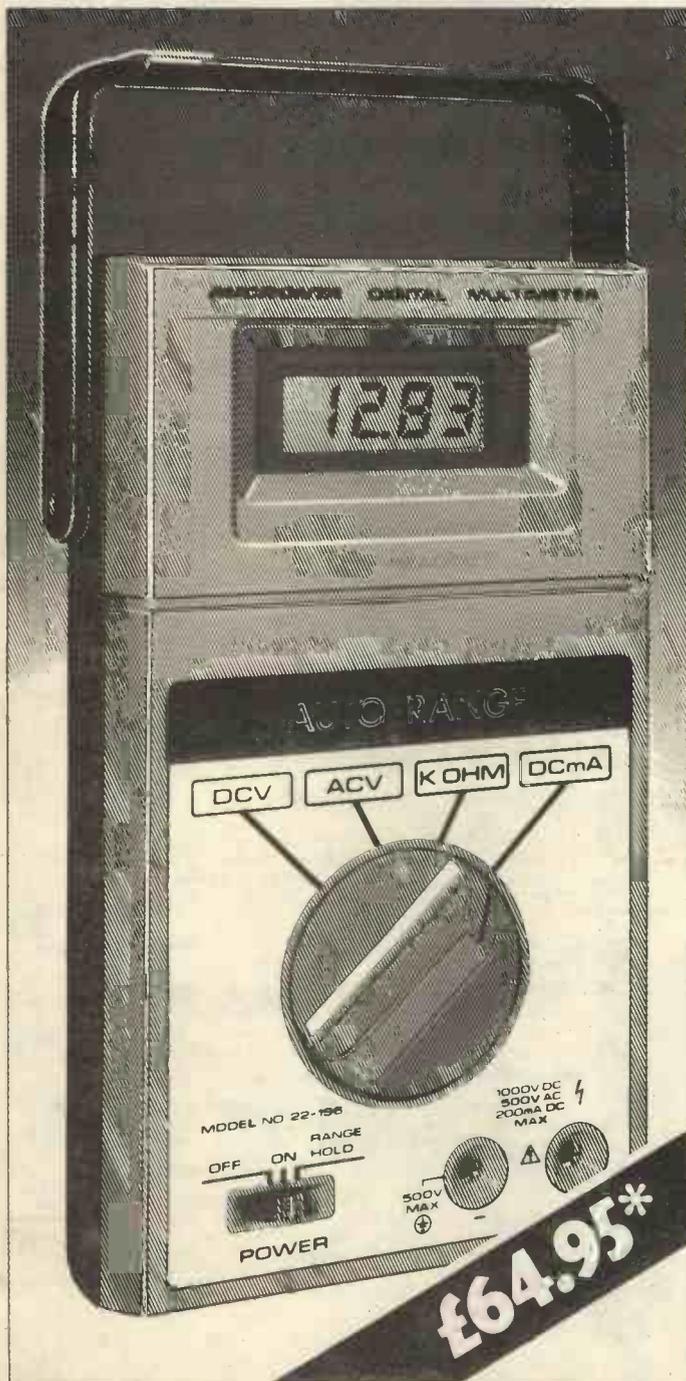

£64.95*

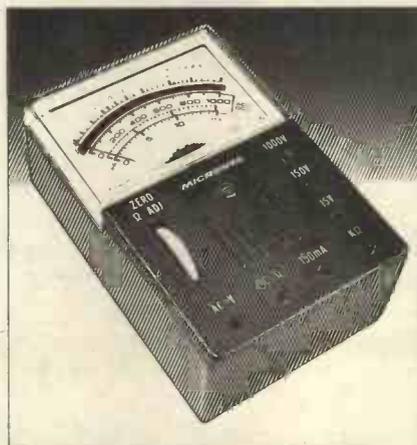Micronta Auto Range Multimeter Gives you correct polarity, range and measurement — every time. Single function switch lets you choose DC 4 ranges; AC 4 ranges; DC current resistance. 4 ranges. LCD readout. Exclusive range hold facility. 22-196



£6.95*

Micronta 1000 Ohms/Volt Multitester Very compact at 89 x 59 x 32 mm. Easy to read colour meter, pin jacks for all 8 ranges. Reads AC V, DC current and ohms. Mirrored scale. 20-027



£9.95*

Micronta Transistorized Signal Tracer Spot circuit troubles, check RF, IF and audio signals from aerial to speaker on all audio equipment. It has built in 5 cm speaker with volume control. 50 x 143 x 38 mm. 22-010





£9.95*

Micronta Dynamic Transistor Checker Shows current gain and electrode open and short circuit. Tests low medium or high power PNP or NPN types. Go/no-go tests from 5-50 m A on power types. "Quick-check" sockets. 22-024

Intelligence.

Realistic Direct Entry Programmable Scanning Receiver Hear real-life drama on six exciting bands. With direct access to all frequencies, you can punch in actual frequencies for monitoring, storing in the computer's memory or just exploring. Big fluorescent display. Phase locked loop security. 20-9111

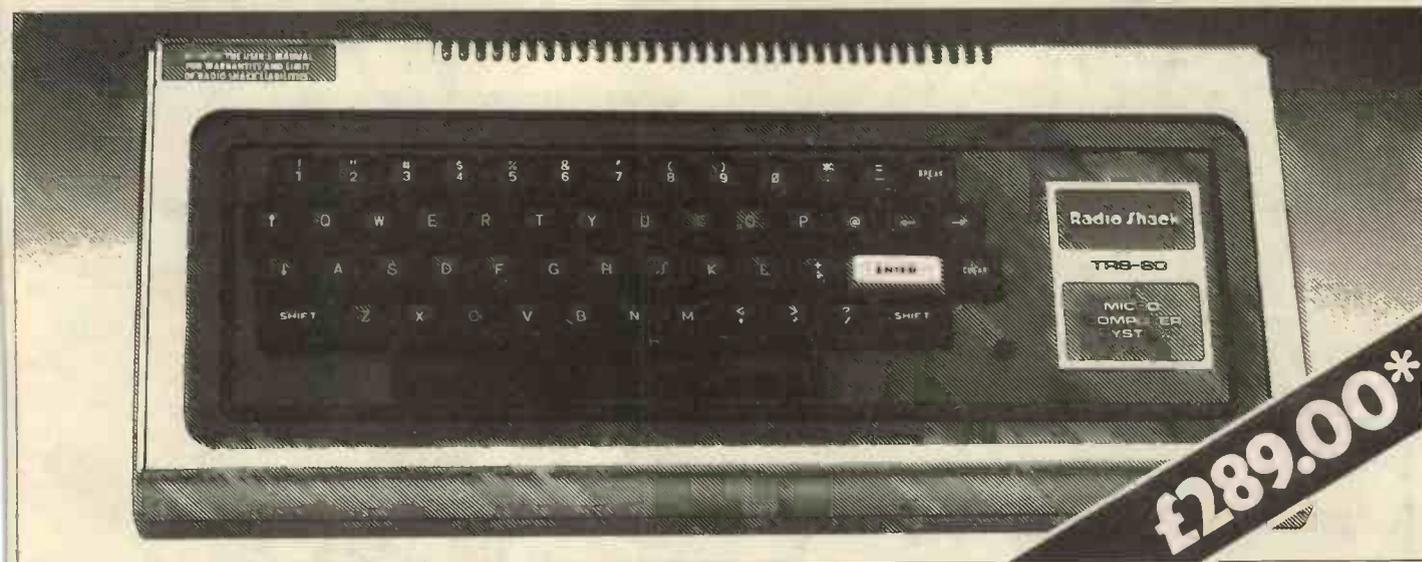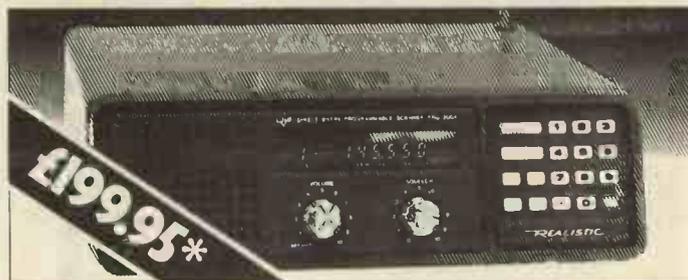TRS-80 Model I C.P.U.'s Ready to run from your TV monitor. Plug in and start computing. Contains 4096 bytes of user memory and can be expanded to 16K. 26-9051



- | | | | | | | | | |
|---|---|---|--|--|--|---|--|--|
| <p>ACCRINGTON
37 Union Street</p> <p>ALDRIDGE
15 Central Area Development</p> <p>BARNESLEY
56 Market Street</p> <p>BASINGSTOKE
Ward End</p> <p>BIRMINGHAM
887 Washwood Heath Road</p> <p>BIRKENHEAD
Wedgebury</p> <p>BRADFORD COMPUTER CENTRE
2/4, Forster Square</p> <p>BIRMINGHAM AREA</p> <p>BULL RING
528 Bridge Link</p> <p>CAPE HILL
44-46, Cape Hill</p> <p>CITY CENTRE
57-58, Dale End</p> <p>CORPORATION STREET
80, Corporation Street</p> <p>DALE END
57-58, Dale End</p> <p>EDGBASTON COMPUTER CENTRE
Edgbaston Shopping Centre</p> <p>EDWINGTON
218 High Street</p> <p>HALESOWEN
5-7, Queensway</p> <p>NORTHFIELD
749 Bristol Road South</p> | <p>PERRY BARR
20 Lynton Square</p> <p>SHELDON
226B Coventry Road</p> <p>SMETHWICK
44/46 Cape Hill</p> <p>WARD END
887 Washwood Heath Road</p> <p>WEDNESBURY
Bilston Road</p> <p>BOLTON
3 Nelson Square</p> <p>BOSCOMBE
548 Christchurch Road</p> <p>BOURNEMOUTH
132/4 Commercial Road</p> <p>BRADFORD
9 Pterigate</p> <p>BRIGHTON
70 London Road</p> <p>BRISTOL AREA</p> <p>BRISTOL
13 Gloucester Road</p> <p>BRISTOL COMPUTER CENTRE
Colston Centre</p> <p>CLIFTON
146 Whiteclades Road</p> <p>DOWNEND
5 Badminton Road</p> <p>KNOWLE
Broadwalk Shopping Centre</p> <p>WYE
4 North Parade</p> | <p>BROMSGROVE
6/8 St. John Street</p> <p>BROWNHILLS
60 High Street</p> <p>BURY (Lancs)
91 The Rock</p> <p>CARDIFF
72 Merrion Centre</p> <p>CHELTENHAM
31 Cambray Place</p> <p>CHESTER
Kwik Save Centre</p> <p>SEALAND ROAD
4 Hayes Street</p> <p>CREWE
12 Market Street</p> <p>DARLINGTON
15/16 Prestigate</p> <p>DERBY
33 Victoria Street</p> <p>DONCASTER
32/34 Kingsgate</p> <p>DUDLEY
Tinsdale Road Roundabout</p> <p>EASTBOURNE
Langley Shopping Centre</p> <p>EXETER
13 Pans Street</p> <p>GRIMSBY
Riverhead Centre</p> <p>HARROGATE
34 Oxford Street</p> | <p>HUDDERSFIELD
Packhorse Shopping Centre</p> <p>HULL
Status City, Clough Road</p> <p>LEAMINGTON SPA
83 Warwick Street</p> <p>LEEDS
72 Merrion Centre</p> <p>LEEDS
3 Eastgate</p> <p>LEICESTER
Market Street</p> <p>LETCHEWORTH
25 Commerce Way</p> <p>LINCOLN
High Street</p> <p>LIVERPOOL AREA</p> <p>ALLERTON
90 Allerton Road</p> <p>BOOTLE
New Strand Precinct</p> <p>OLD SWAN
64B Prescott Road</p> <p>ST. JOHNS PRECINCT
168 Market Way</p> <p>LONDON AREA</p> <p>BARKING
8/10 North Street</p> <p>BARNWATER
The Colonades</p> <p>Pocheater Road</p> | <p>BECKENHAM
144 High Street</p> <p>CATFORD
23 Catford Broadway</p> <p>CHESHURT
92 Turners Hill</p> <p>CHINGFORD
3 Hall Lane</p> <p>CLAPHAM
84 Clapham High Street</p> <p>COLLIER ROW
27 Collier Row</p> <p>CRUICK END
42 The Broadway</p> <p>DAGENHAM
297 Heathway</p> <p>EDGWARE
128 Burnt Oak</p> <p>EDMONTON
23, North Mall</p> <p>ENFIELD
10 Colman Parade</p> <p>HAMMERSMITH
142/4 King Street</p> <p>HENDON
24 Sentinel Square</p> <p>DRIPPINGTON
5, The Watnats</p> <p>PALMERS GREEN
379 Green Lanes</p> <p>ROMFORD
27 Collier Row Road</p> <p>SEACOTE
1/2C, Seacote Lane</p> | <p>STREATHAM
254 Streatam High Road</p> <p>TOTTENHAM
455 High Road</p> <p>WALTHAMSTOW
123 High Street</p> <p>WALWORTH
239 Walworth Road</p> <p>WANDSWORTH
107/9 High Street</p> <p>WELLING
7 Embassy Court</p> <p>WIMBLEDON
124/6 The Broadway</p> <p>LUTON
157 Dunstable Road</p> <p>MANCHESTER AREA</p> <p>ARNDALE
Unit 71, Arndale Centre</p> <p>BRAMHALL
147/15 The Centre</p> <p>CHADDERTON
67 High Street</p> <p>CHEADLE
62 High Street</p> <p>DEANSGATE COMPUTER CENTRE
36, Market Place</p> <p>HYDE
4/8 The Mall</p> <p>RADDCLIFFE
25 Blackburn Street</p> <p>SALE
The Mall</p> | <p>CITY CENTRE
Arndale Centre</p> <p>STRETFORD
Arndale Centre</p> <p>NEWBURY
14 Bartholomew Street</p> <p>NORTHAMPTON
Weston Favel Shopping Centre</p> <p>NOTTINGHAM AREA</p> <p>ARNOLD
126/8 Front Street</p> <p>BEESTON
30 The Square</p> <p>NUMERATION
1 Church Street</p> <p>OXFORD
9/10 St. Clements</p> <p>PAIGNTON
35 Hyde Road</p> <p>PLYMOUTH
64 Royal Parade</p> <p>PORT TALBOT
Aberystwyth Centre</p> <p>READING
18 The Butts Shopping Centre</p> <p>RUGBY
25 Church Street</p> <p>RUNCORN
120 Runcorn Shopping City</p> <p>SCUNTHORPE
140 High Street</p> | <p>SHREWSBURY
20 Shop Latch</p> <p>SITTINGBOURNE
20 The Forum Shopping Centre</p> <p>SLOUGH
293 High Street</p> <p>SOUTHAMPTON
East St. Centre</p> <p>STAFFORD
6 Sheridan Shopping Centre</p> <p>ST. HELENS
Fingerpost Centre</p> <p>STURKE-ON-TRENT
Hanley 16 Charles Street</p> <p>SUNDERLAND
4 Fawcett Street</p> <p>SURREY
206 High Street</p> <p>SUTTON (Surrey)
206 High Street</p> <p>TORQUAY
134 Union Street</p> | <p>TYNE AND WEAR AREA</p> <p>NEWCASTLE
23 Newgate Centre</p> <p>SHEFFIELD
19-20, Hillsborough Shopping Centre</p> <p>SHIELDS ROAD
184/6 Shields Road</p> <p>WASHINGTON NEW TOWN
Galleries</p> <p>WAKEFIELD SHOPPING CENTRE</p> <p>WAKEFIELD
Kirkgate Shopping Centre</p> <p>WALSALL
74 Bradford Street</p> <p>WALLASEY
The Precinct</p> <p>WORCESTER
8 St. Nicholas Street</p> <p>WORKSOP
7/9 St. Aage Place</p> <p>YORK
5 Church Street</p> |
|---|---|---|--|--|--|---|--|--|

*All prices include VAT.

IT'S POSSIBLE, ONLY AT Tandy
Better Equipment. Lower Prices. No Middlemen.

Others subject to availability. Instant credit available in most cases. Prices may vary in individual stores. Access: Barclaycard and Trustcard welcome. Most items also available at Tandy Dealers. Look for this sign in your area.



2 SUPERB NEW KITS!

£2 OFF SPECIAL OFFER



1st
Top of all systems tested by independent national authority July 79

C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection): electronic variable dwell circuit (maximises spark energy at all speeds): pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In its ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TCI).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service.

SUREFIRE ELECTRONIC IGNITION

Suretron Systems (UK) Ltd.
Bayer Buildings, Lower Bristol Rd, Bath, BA2 3EF
Dept. PE4
Tel: (0226) 332317

Name

Address

*Phone order with Access/Barclaycard
VAT and P & P inc

Quantity required

ES200: Neg	£13.95	£11.95	
C300: Pos	£17.95	£15.95	
C300: Neg	£17.95	£15.95	
Tacho Adapt. TCI		£3.90	

I enclose
chq/PO's
£
Chq No.



MUSICAL MICRO 24 TUNE DOOR BELL



BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

- ★ Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware
- ★ Texas Instruments TMS 1000 microcomputer
- ★ Comprehensive kit manual with full circuit details
- ★ Ready drilled and legended PCB included

ONLY £11.95
+ 75p p&p
UK ONLY

Plays 24 well-known tunes including:

Star Spangled Banner, William Tell Overture, Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful, plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

TMS 1000N



-MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed. This unique chip can be used not only for electronic door chimes but for other projects requiring musical output: Car Horns Musical Boxes Alarms Amusement Machines Public Address etc. **£4.95** (UK 30p shipping)

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY
CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

Please send me:
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.
Telephone (0279) 418611

NAME _____ PE/11/80
ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

BAKER 50 WATT AMPLIFIER

£69
Post £2



Superior quality ideal for Halls/PA systems, Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outputs 4, 8, 16 ohm. AC 240V (120V available). White working on black cabinet.

BAKER 150 Watt Amplifier 4 Inputs £89

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains.
Printed circuit and components Post 50p **£3.25**

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. **£2.95**

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi £18 and all Disco Amplifiers. Cabinet extra £4.50. Post 50p
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lamps. Edison Screw 75p each or 6 for £4. or 12 for £7.50.

MAINS TRANSFORMERS Primary 240V A.C. ALL POST 99p
250-0-250V 70mA, 6-3V 2A £3.45
250-0-250V 80mA, 6-3V 3-5A, 6-3V 1A £4.60
300-0-300V 200mA, 6-3V 3A+6-3V 2A+6-3V 2A £12.00
300-0-300V 120mA, 2x6-3V 2A C.T.; 5V 2A £10.00
220V 45mA, 6-3V 2A £2.50

GENERATOR POSITIVE LOW VOLTAGE.
Tapped outputs available:
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £6.00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £16.00
6V, 500mA £2.00
12V, 100mA £1.30
12V, 750mA £1.75
10-0-10V 2amp £3.00
30V, 5 amp and 17V 0-17V £4.00
2 amp £2.00
0-5, 8, 10, 16V, 1 amp £2.50
9V, 3 amp £3.50
15-0-15V 2 amp £3.75
30V, 2 amp £3.50
30V, 1 1/2 amp £3.50
9V, 1 1/2 amp £1.50

AUTO TRANSFORMERS 115V to 240V 500W £10.00
CHARGER TRANSFORMERS - CHARGER RECTIFIERS
6-12V 3A £4.00
6-12V 4A £6.50
6-12V 2A £1.00
6-12V 4A £2.00

R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6x4in. £1.50, 7x4in. £1.50, 8x5in. £2.50, 6 1/2in. £2.20, 8in. £2.60, 10in. £3.50, 12in. £4.50.
8 ohm. 2 1/2in. £1.50, 3in. £1.50, 5in. £2.20, 8in. £2.60, 10in. £3.50, 12in. £4.50, 16 ohm 6 x 4in. £1.50, 7 x 4in. £1.50, 5in. £1.50, 8in. £3.10, 10in. £3.50, 12in. £4.50, 10 x 6in. £3.50.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 50p £2.95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage

PP BATTERY ELIMINATOR. BRITISH MADE.

Mains power pack 9 volt 400 ma stabilised, with overload cutout. Size 5 1/2 x 2 1/2 price £4.50 post 50p.


THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. **£7.50** Post 50p



HEAD DEMAGNETISER PROBE £5.00

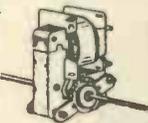A.C. ELECTRIC MOTORS POST 50p.
2 Pole, 240V, .2 Amp. Spindle - 1.43 x 0.212in. £1.75, 2 pole, 240V, .15 Amp. Double spindle - 1.75 x 0.16in. Each £1.50, 2 Pole, 120V, .5 Amp. Spindle - 0.75 x 0.2in. Two in series - 240V, 75p each. Brush Motor, From a Food Mixer 240V, .3 Amp. High Speed and Powerful. Spindle - 0.5 x 0.25in. £2.95



BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides. 6 x 4in. 95p; 8 x 6in. £1.40; 10 x 7in. £1.55; 14 x 9in. £1.90; 16 x 6in. £1.85; 12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70.

ALUMINIUM PANELS. 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 5in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1.16.

ALUMINIUM ANGLE BRACKETS 6 x 1 x 1/2 in. 25p.

ALUMINIUM BOXES, MANY SIZES IN STOCK.
4 x 2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 3in. £1.30; 8 x 6 x 3in. £2.10; 12 x 5 x 3in. £2.30; 6 x 4 x 3in. £1.60; 10 x 7 x 3in. £2.50.

HIGH VOLTAGE ELECTROLYTICS
8/800V £1.20
16/500V 75p
32/500V 75p
32+32/350V 50p
50+50/500V £1.80
40+80/500V £2
16+32+32/500V £2

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in., 10in., or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With CERAMIC STEREO CARTRIDGE **£20** Post on All Decks £2.



BSR Single Player P207 cueing device, ceramic cartridge. **£15**

Garrard Single Player 6-2000 metal turntable, cueing device, aluminium arm. Stereo cartridge. **£22.**

BSR P182. Snake arm, flared Aluminium Turntable ADC QLM30 Magnetic Cartridge. **£30**

B.S.R. Auto Changer. 1 lin. Turntable. Budget price. **£17.50**

Stereo ceramic, reliable unit, 3-speed. **£9.95 or £18 pair**

RSC Disco Deck 3 speed stereo

Rapid Mail Order 50p minimum postage. Closed Wines Welcome. Access - Visa. Lists 20p. Callers Wed.

Radio Components Specialists

337, WHITEHORSE ROAD CROYDON, SURREY, U.K. TEL: 01-684 1665.

SCS COMPONENTS

C/MOS prices as in previous issues.

DATA	
RCA C/MOS Data Book	3.50
RCA Power Data Book	3.50
RCA Linear Data Book	3.50
RCA Microprocessor Data Book	3.50
GIM Applications Booklets	0.25

POWER			
2N 2102	.60	2N 4036	.55
2N 3063	.31	2N 5038	3.01
2N 3055	.39	2N 6240	1.83
2N 3439	.61	2N 5294	.42
2N 3440	.43	2N 5296	.35
2N 3442	.99	2N 6320	.51
2N 3553	1.58	2N 5756	.91
2N 3773	1.70	2N 5838	1.40

Miniature Toggle	
E2012 - 3 amp SPDT	.59
E2022 - 3 amp DPDT	.74

Slide Switches	
SM1-1 - 1 amp SP on/off	.23
SM2-2 - 1 amp DPST	.31
SM2-3 - 1 amp DPDT	.61

LED's	
MAN3640 - 7.6mm Orange	1.70
MAN4640	1.90
MAN6660 - 14.2mm Orange	2.00
MV50 - 2.3mm Red	.14
MV82 - 2.3mm Green	.21
MV53 - 2.3mm Yellow	.21
MV5021 - 4.7mm Red	.20
MV5054/1 - 5mm Red	.18
MV5054/2 - 5mm Red	.17
MV5054/3 - 5mm Red	.40
MV5074B - 3mm Red	.13
MV5214 - Rectangular Green	.44
MV5312 - Rectangular Yellow	.44
MV5712 - Rectangular Red	.44

DIL SOCKETS	
8P	.09
14P	.11
16P	.13
18P	.17
20P	.17
22P	.18
24P	.20
28P	.25
40P	.35

This is only a sample of our stock of over 2,500 components, if not listed please enquire.

Cash/Cheques/P.O.'s with order. P & P add 30p to all orders. Add 15% VAT to total order. All items ex. stock - orders by return post.

Halifax Road, Keighley, West Yorkshire BD21 5HR

All our products are guaranteed high quality components from leading Semiconductor Manufacturers.

BARGAIN BASEMENT

Bargain box including: 6 off IN4148 2 off 2N3055H 2 off CA555CG 2 off CA741CG **£2.00**

Plastic box 7.5mm x 5mm x 1.5mm
Mixed bag of one dozen assorted heat sinks including DIL flat pack and TO3 **£1.00**

7106 CPL digit to LCD - A/D Converter **£8.98**
7107 digit to LED - A/D Converter **£8.48**

Resistors - Vitreous Enamelled
W21 1R2 5% 13.50 per 100
W21 8R2 5% 13.50 per 100
W22 75R 5% 11.70 per 100
W22 180R 5% 11.70 per 100

AY-3-0214 Top Octave Generators 6.00
AY-3-9410 Dual Tone Frequency Generators 2.33

24V 16W Soldering Irons 2.00
240V 25W Soldering Irons 2.50
Soldering Iron Stands - metal type 0.80
- spring type 1.40


Branwick Solderwick 2mm wide x 1 metre long 0.30 per reel
TO3 Heatsinks 10 for 0.50
V8-800 DIL Heatsinks 12 for 0.50

Bargain Box including: 6 off IN4148 2 off 2N 3055 H 2 off CA 555 CG 2 off CA 741 CG **£2.00**

7106 CPL digit to LCD - A/D Converter 8.98
7107 digit to LED - A/D Converter 8.48
MAN 3M 0.48

FREE - one TO3 and one DIL Heatsink with every order received over £5.00 in value.

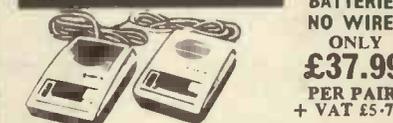INTERCOM NO BATTERIES NO WIRES ONLY £37.99 PER PAIR + VAT £5.70



The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/4 mile on the same mains phase. On/off switch. Volume control, with 'buzzer' call and light indicator. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. £1.85 Also F.M. 2 channel "touch" model £49.95 + VAT £7.50 + P&P £1.95.

NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER £18.95 + VAT £2.85 + P & P £1.25



Latest transistorised Telephone Amplifier, with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording, model at £20.95 + VAT £3.15. P&P £1.25.

DOOR ENTRY SYSTEM

No door/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged, and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock); mains power unit, cable (8-way) to 50 and wiring diagram. Price £59.95 + VAT £9.00 + P&P £1.95. Kit with two Telephone £69.95 + VAT £10.50 + P&P £2.15

10-day price refund guarantee on all items
WEST LONDON DIRECT SUPPLIES (PE 11)
169 KENSINGTON HIGH STREET, LONDON, W8

ELECTRONICS/ BUILD & LEARN

by R. A. Penfold price: **£3.40**

DIGITAL TECHNIQUES & SYSTEMS by D. C. Green price: **£5.50**

ELECTRONIC FAULT DIAGNOSIS by I. R. Sinclair Price: **£3.50**

ELECTRONIC DESIGNER'S H/B by K. Hemingway Price: **£13.50**

HANDBOOK OF ELECTRONICS CALCULATIONS FOR ENGINEERS & TECHNICIANS by M. Kaufman Price: **£14.70**

H/B OF MICROCIRCUIT DESIGN & APPLICATION by D. F. Stout Price: **£19.20**

UNDERSTANDING MICROPROCESSORS by Texas Inc. Price: **£4.00**

INTRODUCTION TO MICROCOMPUTER PROGRAMMING by P. C. Sanderson Price: **£4.50**

THE COMPLETE MICROCOMPUTER SYSTEMS H/B by E. L. Safford Price: **£8.25**

TOWERS' INTERNATIONAL TRANSISTOR SELECTOR by T. D. Towers 1980 Price: **£10.50**

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.


BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

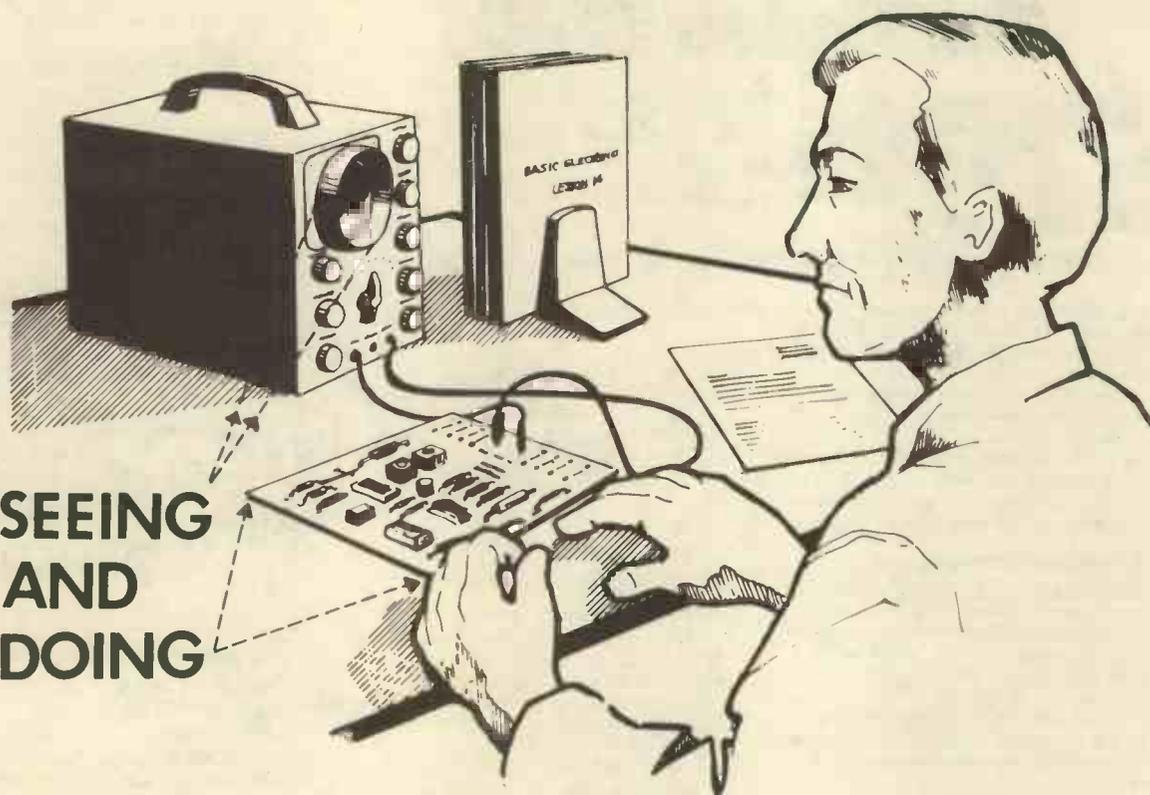Master Electronics the new Practical way.



**SEEING
AND
DOING**

Conquer the 'Chip' – Easy-Fast-Exciting !

AND MASTER ALL THE NEW TECHNIQUES
IN MODERN ELECTRONICS.

- Build an Oscilloscope.
- Carry out over 40 full experiments including work on Digital Electronic Circuits.
- Recognition of Electronic Components.
- Understand and draw Circuit Diagrams.
- Experience with handling Solid State Circuits and "Chips".
- Testing and Servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

Colour Brochure – without any obligation. Post to :-

PE/11/812

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
4 Cleveland Road, Jersey, Channel Islands.

Name

Address

.....

.....

BLOCK CAPS PLEASE

FREE

Britain's first com computer kit.

The Sinclair ZX80.

£79.95

Price breakdown
ZX80 and manual: £69.52
VAT: £10.43
Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); *everything!*

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done; connect it to your TV... link it to an appropriate power source*... and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVED and LOADED on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter, and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:


- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions. USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines. And Benchmark tests show that the ZX80 is faster than all other personal computers.

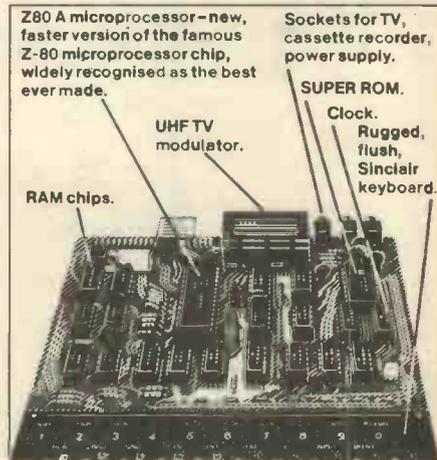No other personal computer offers this unique combination of high capability and low price.



NEW

PRACTICAL ELECTRONICS PROJECT 125 WATT POWER AMP KIT

SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response Measured at 100 watts 25Hz-20kHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.M.D. @ 50 watts 4 ohms load 0.1 %
 Dimensions 205 x 90 and 190 x 36 mm

The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, the

output stage uses four 115 watt transistors normally only two would be used, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is performed and ready to use, supplied with all parts and circuit diagrams.

125 watt power amp kit **£9.50** plus £1.00 p&p
ACCESSORIES £1.00 plus 20p p&p
 Suitable L.S. coupling electrolytic
 Suitable Mains Power Supply Unit £7.50 plus £2.75 p&p
 sufficient for one power amp

ACCESSORIES available only when purchasing packs.



AS FEATURED IN PRACTICAL ELECTRONICS OCTOBER ISSUE

DIY STEREO BARGAIN PACKS FEATURING FAMOUS BUILT MULLARD PREAMP MODULES

MULLARD STEREO PREAMP MODULES AND TWO 12 WATT POWER AMP KITS.



In easy to build form P.C.B.s backprinted, etched and drilled ready to use.

BUILD A 12 WATTS PER CHANNEL STEREO AMPLIFIER ACCESSORIES AND L.S. KIT EXTRA (not available separately) **£6.00**

DIY PACK 1 2 x power amp kits LP1182/ preamp module, suitable for ceramic and auxiliary inputs. **£6.00** plus £1.10 p&p
 DIY PACK 2 2 x power amp kits LP1184 preamp module suitable for magnetic ceramic and auxiliary inputs. **£8.50** plus £1.15 p&p
 DIY SPEAKER KIT Two 8" x 5" approx. 4 ohm bass. **£3.50** plus £1.70 p&p



DIY ACCESSORIES Mains transformer smoothing capacitor rectifier 4 x slider controls, for base, treble and volume.

£3.00 plus £1.60 p&p

ACCESSORIES: Available only at time of purchase of Bargain Packs

12 + 12 WATT AMPLIFIER KIT

NOTE: for use with 4 to 8 ohms speakers.

With up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 3/4" x 4" approx.

NOTE:

for use with 4 to 8 ohms speakers

£13.95 plus £2.55 p&p

BSR chassis record player deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus £2.75 p&p when purchased with amplifier available separately **£10.50** plus £2.75 p&p.



TWO WAY SPEAKER KIT. 2 Philips 8" approx speakers **£4.75** per stereo pair plus £1.50 p&p when purchased with amplifier available separately **£6.75** plus £1.50 p&p.

ALSO AVAILABLE Stereo magnetic pre-amp conversion kit all components including P.C.B. to convert your ceramic input on the 12 + 12 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use.



£12.25 OUR PRICE plus £2.75 p&p

Size approx 13" x 11"

PHILLIPS RECORD PLAYER DECK GC037

Size approx 15 1/2" x 12 1/4"



Hi Fi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge—LIMITED STOCK. UNBEATABLE OFFER AT

£27.50 complete plus £2.75 p&p

OFFER! SAVE MONEY by purchasing 12 + 12 amp kit, BSR record deck and speaker kit together for only **£25.50** p&p £4.50.

PRACTICAL ELECTRONICS CAR RADIO KIT

(Constructors pack 7)

£10.50

plus £1.75 p&p

2 Wavebands MW and LW



- * Easy to build * 5 push button tuning
- * Modern styling design * All new unused components
- * 6 watt output * Ready etched & punched P.C.B.
- * Incorporates suppression circuits * Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

Complete with instructions.

CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete **£1.95** per pack. Pack 7A may only be purchased at the same time as Pack 7.

NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

FEATURED PROJECT IN PRACTICAL ELECTRONICS.



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx.

READY TO PLAY **£32.90** plus £3.30 p&p



323 EDGWARE ROAD, LONDON W2 21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers ALL PRICES INCLUDE VAT AT 15% All items subject to availability. Price correct at 1.9.80 subject to change without notice.

For further information send for instruction booklet 20p plus stamped addressed envelope.

NOTE:

Persons under 16 years not served without parent's authorisation.

BARGAIN OFFER!!



ARISTON PICK UP

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00

£11.95 plus £2.50 p&p


100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls. Size approx 14" x 4" x 10 1/2". Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

£76.00 plus £4.00 p&p

50 WATT MONO DISCO AMPLIFIER

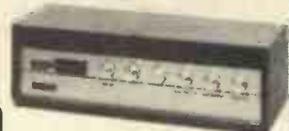Size approx 13 1/2" x 5 1/2" x 6 1/2". 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



£30.60 plus £3.20 p&p

NOSTALGIA!

THE industrial revolution left its mark and today early machinery is a fascinating reminder of how things developed. A traction engine at full song, or one of the well preserved steam engines powering out of a station are awe inspiring sights. We can all explain something of their operation to the kids and show them the stack of coal, the fire and the steam. Even an old typewriter can be quite fascinating, but what will we leave behind from the m.p.u. revolution for others to marvel at!

The fascination of a UK101 or a PET in seventy-five years' time does not seem to carry the same feelings—and how many of us could explain the basic operation? Presumably a few nostalgic types will keep them alive and perhaps specialist firms will make outdated chips to order. BASIC will probably be a lost language to most and maybe some will marvel at that old fashioned p.c.b. and the push button keys for communicating with the beast.

Possibly the preservation of a 6502 under a microscope will be of interest, but we doubt it. As technology moves on at its ever increasing pace "the man in the street" has less and less knowledge of the theory and circuit

operation of the equipment. As the operation of new technology products becomes easier, that already basic knowledge will diminish even further until we will blindly use the products without even trying to understand them.

This situation is of course already coming about; we wonder how many musicians understand the operation of the modern "computer organ" or of the new generation of programmable rhythm generators now becoming popular. Of course it is still necessary to understand music in order to do one's own original programming, but just how much longer will even that be necessary.

KEEPING UP

We hope that PE can continue to keep readers abreast of the general principles of high technology devices. It has always been our policy to explain circuit operation, although these days we cannot go into detailed circuit operation of l.s.i. devices. The *PE Master Rhythm* project starting next month will explain the principles of operation, in addition to providing full constructional information, on a rhythm unit we believe to be better than its commercial counterparts.

This issue looks at the next significant step in the development of artificial intelligence—the synthesised voice. We will show how to construct an interface for a speech synthesiser module so that our UK101 can tell us where to get off. The computer is one of the main uses for synthesised speech, but not by any means the only one; we intend to publish a digital readout project with an add-on speech board for those that want it. The project, with luck, will come out early next year.

Finally we are pleased to bring you another component supplier's catalogue—free with next month's issue. Regular readers will have collected a number of free catalogues over the past few years and we anticipate this situation continuing. Next month all UK copies will carry the new larger format, 68 page Electrovalue catalogue. Electrovalue were the first British mail order component supplier to computerise their business and are now highly experienced in stock control, order processing, etc., by computer. They have had a working system for many years—some things are not as new as they seem.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries will not be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

ADVERTISEMENT MANAGER D. W. B. Tilleard } 01-261 6676
SECRETARY Christine Pocknell }
AD. SALES EXEC. Alfred Tonge 01-261 6819
CLASSIFIED MANAGER Colin Brown 01-261 5762

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4.30 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £11.80 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by
David Shortland

and
Jasper Scott

TOUGH CASE

With provision to accommodate almost everything except the kitchen sink, the Antler D532 deluxe tool case should be everything the budding service engineer needs.

With a frame made from hardened aluminium and moulded ABS shells, the case combines light weight with strength. Inside, there is a multi-pocket lid wallet to hold manuals, and tension tool straps which can be



swiftly adjusted to hold any shape or size of tool. The base area is left open to hold larger tools and instruments. As the case is likely to be quite heavy when in use, the swing handle is bolted on. Overall size of the case is 460 x 340 x 145mm.

Priced at £42.50 plus VAT, the Antler D532 is available from:

Toolrange Ltd., Upton Road, Reading RG3 2JA.

THE PLATMETER

A dual range, dual accuracy indicator designed for use with platinum resistance thermometers with characteristics to BS 1904 or

DIN 43760 is announced by the Platline Division of Rosemount Engineering Co Ltd.

The 'Platmeter', which has an l.c.d. read-out, is part of the Platline range of associated devices using platinum resistance technology. Designed to fill a gap between hand-held devices and bench-mounted instruments, the indicator is light in weight, readily held while in operation, and can also be placed on any flat surface for easy reading.




Its dual range facility enables temperature in the range of 120°C to 700°C to be resolved at the flick of a switch without the need to change the indicator or probe. This eliminates the tolerance errors in indicator and probe that are applicable to a single-range instrument.

The Platmeter is supplied complete with nickel cadmium batteries and charger. A warning that the battery voltage is low is indicated automatically at least 30 minutes before recharging is essential. An electrical interlock disconnects the battery when the probe is disconnected from the unit, preventing battery discharge.

Further information on the Platmeter is available from: **Rosemount Engineering Co. Ltd., Durban Road, Bognor Regis, Sussex PO22 9QX (0243 863121).**

TWELVE PLUS TWELVE

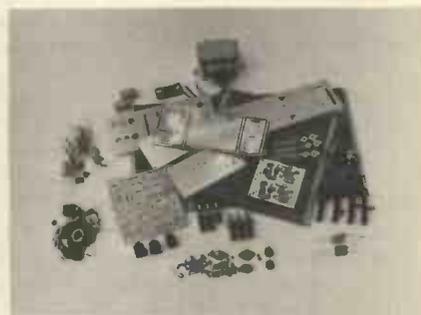Pictured below is the 12 + 12 watt stereo amplifier kit from RT-VC. Succeeding their 10 + 10 watt model, the kit is based around the Mullard LP1183 pre-amp module. The amplifier features slider level controls, push button switches, and inputs for tape, tuner, mic and ceramic cartridge.



The kit comes complete with metalwork and an easily assembled wood finish cabinet—all that is needed are screws, solder and wire. The instructions and diagrams are quite easy to follow provided that they are thoroughly studied. As well as resulting in a satisfying finished product, the kit should provide the less experienced constructor with a good introduction to building more ambitious projects.

Priced at £13.95 plus £2.55 postage and packing, the kit is available from:

RT-VC, 21b High Street, Acton, London W3 6NG.

SOLAR EFFICIENCY

A new differential temperature switch (DTS) for use in solar heating systems is now available from Microvitec Limited. The DTS1 is controlled by silicon chips and is programmed to operate the circulating pump to achieve maximum energy transfer efficiency.


Microvitec analysed the latest research in this field which showed that the pump could consume more energy than a solar system extracted, if it operated at the wrong temperature differential. This is particularly important at low winter temperatures. A differential of 4.5°C between the panels and the pre-heating cylinders proved optimal. With these figures Microvitec designed the DTS1 using semiconductor sensors which are capable of monitoring differential temperatures accurately.

The DTS1 has two probes, one to monitor temperature at the exit point of the panels, the other at the exit from the cylinder to the pump. Thus they are placed at the highest and lowest temperature points in the system. The pump starts to operate when the temperature in the panels is 4.5°C above that in the cylinder. The sensors continue to read the temperature and the pump is switched off when the differential drops to 1.5°C. The DTS1 temperature hysteresis is therefore 3°C nominal.

The use of silicon chips has several advantages over thermistors which are traditionally used in these systems. The linear probes are highly stable and do not age. This means that performance does not vary and so considerably improves long term stability. The inclusion of integrated circuits, both in the

probes and the control panel, ensures long maintenance free operation. In addition, the DTS1 has been fitted with a test socket to allow the system to be checked without being dismantled.

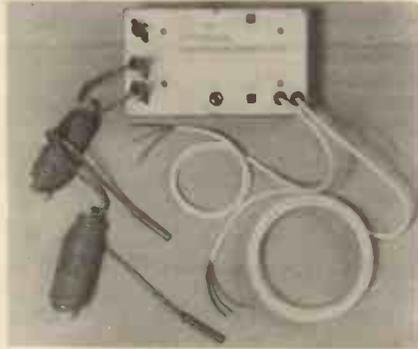The whole unit is encased in a fire-proof metal box making it easy and safe to handle. A further economic advantage is the low power consumption—the DTS1 needs only 2VA (excluding the pump) to run. It is also interference free because of built-in suppression.



The DTS1 has been designed to British Standards 415 and 3861. The pump control switch can be changed to an override position from the normal automatic mode to check pump performance. Neon indicators show when the system is powered and also when the pump is working.

Microvitec's DTS1 is in full production and has already been installed by one manufacturer of domestic solar heating equipment with very satisfactory results.

Further details are available from: John Martinez-Perez, Microvitec Ltd., PO Box 188, Bradford BD8 9HH (0274 499672).

CASIO PRESET SYNTHI

Casio, acknowledged as the world leaders in the calculator and watch market have just launched a new range of keyboards—musical, that is. With the painstaking market research that is characteristic of the Japanese, I've no doubt that they will prove popular, as they combine novelty with a compact size which is ideal for the modern home.

The Casiotone 201 has a 49 note keyboard with 29 digitally synthesised voices selectable by pressing any one of the 29 white keys. It is possible to preselect a total of four voices at any one time and alternate between these



whilst playing, so providing tonal variety. It is partially polyphonic inasmuch that chords of up to eight notes can be played together.

The internal amplifier delivers 2 watts and there are tone and vibrato facilities to expand its entertainment capability. Connections are provided for rhythm unit, reverb or external amplifier. The latter dramatically expands the possibilities of the 201 when used as a combo solo instrument, as was demonstrated by the Dooleys who helped Casio with the launch promotion.

The M-10 is a smaller instrument of 2½ octaves and four preset voices.

The 201 is priced at £285 and the M-10 £79. For further information contact: Casio Electronics, 28 Scrutton Street, London EC2A 4TY.

THANDAR DMM

The latest addition to the Thandar range of low-cast test equipment is the TM352 i.c.d. multimeter. This is a battery operated 3½ digit instrument with a 0.5in display with over-range indication.

The TM352 has an input impedance of 10MΩ and covers 16 ranges: d.c. volts 100μV to 1000V (5 ranges), a.c. volts 100mV to 1000V (2 ranges), d.c. current 100nA–10A (5 ranges) and resistance 1Ω to 10MΩ (4 ranges).

There is an audible continuity check feature which will sound if the resistance is less than 130Ω ± 50Ω and an hfe measurement facility. Range and function selection is via side mount-

ted push-button switches. The unit, which will operate for in excess of 150 hours from a single PP3 battery, has all its ranges protected by a 0.5A fuse except for the 10A range which is unprotected.

The TM352 is supplied complete with battery and test leads and accessories include a



universal test set, 40kV high voltage d.c. probe and carrying case.

The TM352 is priced at £49.95 excluding VAT and p&p.

A. Marshall's (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA. (01-624 0805)

TANDY POCKET POWER

The new Tandy TR5-80 Pocket Computer is the latest addition to the TRS-80 range. This pocket-sized unit measures only 175×70×15mm and retails at £119 including VAT.

The unit is battery powered and programmes can be loaded, and retained for up to 300 hours (the life of the battery), even when the power is switched off.

There are already eight packages of software available to cover varying needs. These include civil engineering, aviation, maths drill, business statistics, real estate, personal finance and a games package. These will

be priced from £8.95 to £13.95 (including VAT).

The Tandy Pocket Computer has a 4-bit CPU consisting of two microprocessors. It can carry 1.9K of user memory (RAM) and a total of 11K of ROM—7K for the BASIC interpreter and approximately 4K for the monitor. Using the cassette interface (£17.95), multiple programmes can be loaded from cassette tape without the previous programme being erased. Each programme in RAM can be executed selectively by a simple key input.

The machine has a display screen and a 57-key alpha-numeric keyboard. A user manual is included.





INDUSTRY NOTEBOOK

By Nexus



The Economy

The economic squeeze continues accompanied by well orchestrated cries of disaster from pressure groups under real or imagined threats. As I have often pointed out in this column, if all UK industry achieved the overall performance of the electronics industry there would be few problems.

But even electronics is now feeling the pinch. One sector which always gets a hammering in times of economic stringency is test and measuring instruments. Potential buyers tend to hold back and make do with what they already have. Instrument salesmen, faced with declining sales, have always been prone to make private deals with special discounts for favoured customers and not only for bulk orders.

Now I note that one leading company has publicly slashed catalogue prices by some 10 percent due, it is claimed, to increased manufacturing efficiency and production levels. The claim is no doubt entirely honest but it is market forces that have resulted in the reduction. In effect, the savings are being passed on to the buyer, or at least shared by both parties. If sales volume rises, then the manufacturer can still win. In fact everybody wins. It is the problematic 'if' in the equation that is the root of worry for the manufacturer who has traded some of his profit margin in the expectation of greater volume.

This homely example of elementary economics is the central theme of the Government economic strategy aimed at increasing the efficiency and therefore the competitive position of British industry. Critics of Government policy say that the strategy is too simplistic for what is called a complex modern industrial society. But at least it is something that people can understand. Of course nothing is starkly black and white, and never will be, but as a general principle it is true that firms have

the option of pricing themselves in or out of a market and that people can price themselves in or out of jobs.

It is impossible to forecast the eventual outcome of the squeeze if only because of the many factors which cannot be under Government influence. The general world recession in trade, for example, or the loss of a particular market like Iran and political instability elsewhere which may temporarily upset trade.

What can be said is that present policy is a marked change from former policies which have been tried and found wanting. It is a harsh doctrine, often seemingly unfair, and not without controversy in the Conservative party itself.

Monopolies

One of the most extraordinary facets of present economic policy is the almost quiescent reception given to proposals considered outrageous by many people only a couple of years ago, a heartening indication of public acceptance of the need for change. It seems hard to believe that the state monopoly in telecommunications has been in existence for 111 years. Now it is to go and there will be a free market for telecommunications services more like the American system where competition is fierce and efficiency unparalleled anywhere in the world.

Response was muted from the BPO and the Post Office unions. The Government played safe by only relaxing the existing monopoly and not smashing it. The same with the postal services. The changes were well discussed in advance and, from the viewpoint of those directly affected in entrenched positions, were probably less drastic than once feared.

The big surprise however, was in electricity supply which, subject to future legislation, will no longer be a state monopoly. Any organisation will be able to generate and distribute electricity on a commercial basis. This is a big jump from present legislation which allows private generation providing it is not a main part of the business. Some 15 percent of total electrical power consumption in the UK is already generated privately by industrial users.

Even if the legislation is introduced, and no date has yet been fixed, it is unlikely that it will have much practical effect in terms of direct competition with the electricity boards. Nonetheless, it will have a psychological effect in gingering up the performance of the state industry.

The erosion of the great state monopolies is an opportunity for private industry to step in. Whether and how the opportunity will be seized is still a matter for speculation although there is already considerable activity in telecommunications where the opportunities are greatest.

Inmos

So Inmos has received its second £25 million from public funds. The decision was

a long time coming and probably reflects on Government distaste for state funding. But Inmos had to give way on the siting of the UK production plant which is now to be in South Wales. This, again, is against the general principle of Government non-intervention in industrial management. It suggests that behind a facade of rigid conviction there is in fact at least a measure of flexibility in bending policy to meet political situations as they arise.

But six valuable months have been lost during which the other semiconductor manufacturers have not been idle. Revised schedules in Inmos are for UK production of memories by mid-1982 and microprocessors in 1983. Sample Inmos memories are now available to the trade with first production from the US plant at Colorado Springs early next year. The UK plant, when it starts production, will have the advantage of moving straight into a mature product already de-bugged. A published revenue plan shows a fantastic growth curve starting at £0.3m this year rising to £145.9 million by 1984. Perhaps wisely, there was no public forecast of profits.

Buoyancy

Despite all the gloom stories the electronic industry remains buoyant. True that Plessey, at the time of writing, looks likely to lose a plum hoped-for contract worth £400m in Iraq to the French company Thomson CSF. But Plessey is prospering in general and so are others in electronics, both large and small.

TV, radio and the popular press are so obsessed with disaster that they fail to report success. An example is the Marconi Avionics contract from the US Air Force for new-technology head-up displays for fitting in F-16 fighters and A-10 close support aircraft. The development programme is for \$13 million and production options make the contract worth a potential \$100 million. Another is Standard Telephones and Cables £20m contract for a new submarine cable between Greece and Cyprus. And there are plenty of other examples of enterprise virtually ignored.

Despite the excellent results of the past few months, industry leaders are hedging their bets by claiming only 'cautious optimism'. Even Racal Group chairman Ernie Harrison, normally bullish in sentiment, qualifies his optimism by referring to the inflation rate and the strength of the pound sterling. Yet Racal's order books are at record level as, indeed, are GEC-Marconi Electronics and Plessey.


One wonders why Britain's balance of payments last July, the best ever, were greeted by the media with utter scepticism rather than joy. Or why the mid-year reduction in inflation had a similar reception. Of course it would be stupid to ignore the many industrial and economic problems which will be with us for a long time yet. But, equally, we should not ignore the many bright aspects of our industrial performance.

The NEW

VIDEOTONE

YOU CANNOT BUY CHEAPER - YOU CAN ONLY GET LESS FOR YOUR MONEY!

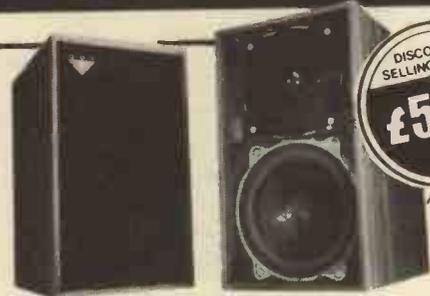Introduces DIRECT SELLING - the Ultimate Discount!!!



LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. Now at lowest ever prices.

D 100	£38
Minimax 11	£44
GB3	£50
GB2	£60
GBS	£207
D 93	£40

DISCOUNT SELLING PRICE
£50.00



ELECTRONICS

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

30 watt amp MC input SA4130	£75.00
Stereo Tuner ST4120	£68.00
Cassette full features SC3200	£98.00
50 Watt amplifier WA7700	£77.00
20 Watt amplifier LA2020	£58.00

DISCOUNT SELLING PRICE
£68.00

DISCOUNT SELLING PRICE
£75.00



DISCOUNT SELLING PRICE
£9.69

HEADPHONES

HP 90 Headphone	£12.65
HP 80 Headphone	£9.69

Superbly made with top flight performance.

CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL UK's No. 1 Cartridge

MC 81	£48.87
777EX	£35
777E	£25

MOVING MAGNET

555SX	£7.28
555E	£14.22
666E	£32.48



HEAD AMP

H300	£51.75
T100	£24.75

HEADSHELLS

S100	£6
S101	£7
S200	£4



MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

TURNTABLES

Sansui SR222 Mk2	£69.00
JVC LA 11	£64.00
JVC SLQ 3	£140.00

A MESSAGE FROM VIDEOTONE


Dear Customer

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly on to you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving Value for Money. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. Remember, you have 21 days trial period on all products. That is the measure of our confidence.

Videotone

SEND FOR OUR LATEST FREE BROCHURE

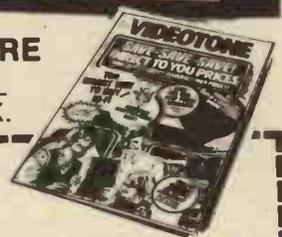AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.



VIDEOTONE
98 CROFTON PARK ROAD,
CROFTON PARK, LONDON SE4
Tel: 01-690 8511/2

Please send me your Direct Selling Brochure and list of sales outlets.

Name _____

Address _____

PE/11/80

ALL PRODUCTS ON DISPLAY & CONTINUOUS DEMONSTRATIONS

ALL PRICES INCLUDE VAT

VIDEOTONE

AITKEN BROS

35, High Bridge, Newcastle upon Tyne
Tel: 0632 26729



EXP300



PB6 Kit

EXP300
550 contacts with two 50-point BUS bars. Size 152x53mm. **£6.95.**
PROTO-BOARD 6 KIT
630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. **£10.98.**

CSC LOGIC PROBES LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. **£20.95.**

- LP-1 Memory Probe **£35.85**
- LP-3 High Speed Memory Probe **£56.75**

CSC catalogue available. Please send S.A.E.

CALSCOPE SUPER 6 £186.30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1μs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

CALSCOPE SUPER 10 £251.85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

SINCLAIR LOW POWER PORTABLE OSCILLOSCOPE SC110 £159.85

The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided, including bright line, auto with TV line and frame positions. Please send for full spec. and illustrated brochure.

TMK 500 MULTIMETER 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50μA, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries, leads, and carrying case included. **PRICE £22.95.**

CSC EXPERIMENTER BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.

SINCLAIR DM350 £83.95 SINCLAIR DM450 £114.95

Size 265x148x40mm.
DM350 3 1/2 digit display DM450 4 1/2 digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (1000V on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

Sinclair PFM200 frequency meter

Size 157x76x32mm.
Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. **£57.95.**

SINCLAIR PDM35 DIGITAL POCKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £39.95 AC Adaptor £4.25 de luxe padded carrying case £1.95 MN 1604 Battery £1.28.**
Size 157x76x32mm.

SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER.

DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1mV to 750V AC & DC current 1μA to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. **PRICE £60.98.** Carrying case **£8.95.** AC adaptor/charger. **£4.25.** Rechargeable Battery Pack. **£8.95.**
Size 265x148x40mm.

PANEL METERS

DIMS 60MM x 45MM. 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, "S", "VU", 50-0-50μA, 100-0-100μA, 500-0-500μA. **PRICE £5.95.**

DESOLDERING TOOL SUCTION PUMP. £6.45

Education Establishment Orders Accepted.
PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER
ALL PRICES INCLUDE POSTAGE AND VAT.

STEVENSON

REGULATORS

78L05	33p
78L12	33p
78L15	33p
78L12	70p
78L15	70p
7912	85p
7915	85p
TIC246 16A 400V Triac	115p
C106D 4A 400V SCR	45p

SPEAKERS

64mm 8Ω	110p
64mm 64Ω	110p
70mm 8Ω	140p
70mm 80Ω	170p
56mm 8Ω	100p
Pair of ultrasonic transducers	380p
Magnetic earphone + 3.5mm plug	17p
Crystal earphone + 3.5mm plug	48p

POTENTIOMETERS

Preset var. for hor. 8p
Rotary 5K-1M Log or Lin 33p
Rotary 5K-1M stereo 110p
Slide 60mm travel 5K-500K log or Lin, single 65p
Suitable knobs for above with coloured caps in red, blue, green, grey, yellow and black. Rotary 16p. Slide 12p each.

CONNECTORS

DIN	Plug	Socket	Chassis	Line
2 pin	9p	8p	12p	12p
3 pin	12p	10p	12p	12p
5 pin 180	13p	11p	16p	16p
JACK	Plug	Scr. plug	Socket	
2.5mm	10p	16p	9p	
3.5mm	11p	18p	9p	
std.	17p	30p	22p	
Stereo	25p	39p	25p	

SPECIAL OFFERS

2708 EPROM	490p
AY5-1013 UART	290p
TDA1022 Delay line	550p
MM57160 STAC timer	500p
SN76477 Sound generator	180p
NE567 Tone decoder	100p
LM318N Op. amp.	70p
5 x C106D SCR	200p
4 x FND500 displays	350p
3 x 7905 or 7912	150p
2 x CA3046 arrays	100p

10 x TL081 op. amps	350p
100 x 1N4148	180p
20 x 1N4001 diodes	70p
20 x 0.125 red LED's	150p
20 x 0.125 green LED's	260p
20 x 0.125 Yellow LED's	260p
4 x HP7 rechargeable cells	500p
3 x LM339 Quad comp.	140p
10 x 2N3707 transistors	50p
10 x BC157 transistors	60p
10 x Miniature slide switches	150p
20 x 8 pin DIL sockets	160p
3 x 4P3W rotary switch	100p
10 x T05 heatinks	100p

TRANSISTORS

AC127	25p	BC547	8p	ZTX108	12p
AC128	25p	BCY71	18p	ZTX109	12p
AD161	40p	BD131	35p	ZTX300	14p
AD162	40p	BD132	35p	ZTX500	15p
BC107	10p	BD139	35p	2N3053	25p
BC108	10p	BD140	35p	2N3055	55p
BC109C	12p	BFX29	25p	2N3702	9p
BC147	9p	BFX84	26p	2N3703	9p
BC178	16p	BFY50	23p	2N3704	9p
BC182	10p	BFY51	23p	2N3819	22p
BC182L	10p	MJ2955	98p	2N3905	10p
BC184	10p	TIP29C	60p	2N5777	50p
BC184L	10p				
BC212	10p	1N914	4p	1N4148	3p
BC212L	10p	1N4001	4p	1N4002	5p
BC214	10p	1N4006	7p	1N5401	14p
BC214L	10p	8ZY88 series	6p each.		

CMOS

4001	25p	4028	90p
4002	25p	4029	110p
4006	95p	4040	110p
4007	25p	4042	85p
4011	30p	4046	110p
4013	50p	4047	95p
4015	85p	4049	50p
4016	48p	4050	50p
4017	90p	4052	80p
4018	90p	4058	120p
4020	110p	4060	63p
4022	100p	4066	63p
4023	25p	4068	25p
4024	80p	4069	25p
		4070	25p
		4071	25p

LINEAR

741	18p	LM324	52p	MM57160	650p
747	70p	LM339	55p	NE531	140p
748	40p	LM348	100p	NE555	23p
7106	850p	LM377	170p	NE566	60p
CA3046	70p	LM378	230p	NE567	120p
CA3080	75p	LM380	85p	RC4136	100p
CA3140	100p	LM381	140p	SN76477	230p
CA3140	100p	LM382	120p	TBA800	80p
LF347	170p	LM386	90p	TBA811	110p
LF351	45p	LM387	120p	TDA1022	630p
LF353	90p	LM1458	40p	TL081	45p
LF356	95p	LM1830	180p	TL082	85p
LM301A	30p	LM3900	60p	TL084	125p
LM318	85p	LM3909	72p	XR2006	390p
		LM3911	120p	ZN414	80p
		LM3914	320p	ZN425E	475p
		LM3915	320p		

SKTS

Low Profile	Texas
8 pin	9p
14pin	11p
16pin	12p
18pin	16p
20pin	18p
22pin	20p
24pin	22p
28pin	26p
40pin	38p

OPTO

Red	TIL209	TIL220	10p
Green	TIL211	TIL221	16p
Yellow	TIL213	TIL223	16p
Clips			3p
DL704	0.3in CC		130p
DL707	0.3in CA		130p
FND500	0.5in CC		100p

PACKS

Specially designed packs intended for development work at a considerable saving.

- 1/4w resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 530p each.
- 1/2w resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 875p each.
- Presets. Pack of 5 of each value from 100ohms to 1 Megohm. a total of 65 presets. 390p each.
- LED's. Pack containing 10 of each colour LED 0.2 size. Total of 30 Led's + clips. 450p each.
- Zeners. Pack of 5 of each value from 2V7 to 33V a total of 130 zeners. 780p each.

CAPACITORS

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1	12p
4.7, 5.6, 10uF @ 25V	20p
22 @ 16V, 47 @ 6V, 100 @ 3V	26p
POLYESTER (Multid 280 series)	
0.01, 0.015, 0.022, 0.033, 0.047, 0.1	6p
0.15, 0.22	8p
0.33, 0.47	12p

RADIAL LEAD ELECTROLYTICS

63V 0.47 1.0 2.2 4.7 10	7p
25V 10 22 33 47 9p	
100	7p
	9p
	20p
1000	32p

Send 50p for your copy of our catalogue, containing 100 illustrated pages detailing over 3000 line items. You will receive:
• A mail order form to facilitate rapid despatch
• A 50p discount voucher.
All prices include VAT. Please add 50p carriage on all orders below £15. Minimum order £5.
Access & Barclaycard welcome
Sales office: 01-464 5770.

76 College Road, Bromley, Kent BR1 1DE.



GAMES TIMER

S. IBBS

MANY board games suffer from one disadvantage; boredom for all players except one at any particular time. The project described here provides increased involvement for all players, and makes use of a well known fact that in games there is nothing more satisfying than another person's downfall. Each player has a randomly chosen time limit in which to make his move. If he fails to do so before a pulsing alarm sounds, he loses his turn. The author found that it raised Scrabble to a very exciting level. Two "booby" time delays of a few seconds can be included, and of course all players *except the one making the move* hope that the "booby" has been chosen. A flashing l.e.d. is included to show that the timer is functioning, and the alarm was made to pulse to give the player, perhaps 5 pulses, to put his word down.

HOW IT WORKS

Two gates of IC1 (a & b) are connected as a fast astable multivibrator, see Fig. 1, whose frequency is within the audio range. The other two gates are connected as a slow oscillator, which drives the l.e.d. The output from the fast oscillator is fed to the clock pin of a 4017 decade counter with 10 decoded outputs, only one of which is high at any one time. Pin 13 (Clock inhibit) is held high by R6, but when the pushbutton S2 is pressed, pin 13 goes low, allowing the 4017 to clock between the various outputs at very high speed. When the pushbutton is released, only one output remains high and causes C3 to charge up, the rate of which is dependent on the value of resistor randomly selected.

Diodes were needed to isolate the resistor outputs from each other, otherwise the capacitor would discharge through the other 9 outputs which are low. The capacitor feeds into a 555 via pins 2 and 6, which have also been brought low by the pushbutton. This has caused the output pin 3 to go high. As the capacitor charges up, so it crosses the threshold voltage, and pin 3 goes low. This is connected to one input of IC4d, thus allowing the slow oscillator pulses from IC1c and IC1d to be fed through, inverted, and gate the fast oscillator IC1a and IC1b via IC4a. The resulting audio pulses go via a one transistor amplifier to LS1.

Pushing S2 automatically resets IC3 by driving its inputs low, discharges C3, and sets the 4017 clocking through the various outputs again, ready for the next player.

COMPONENTS ...

Resistors

R1	27k
R2	68k
R3, R4	4M7 (2 off)
R5	1k
R6	100k
R7	6k8
R8-R17	see text (10 off)

Capacitors

C1	10n polyester
C2	330n polyester
C3, C4	100µ elect.

Transistors and Diodes

TR1	BC109
D1-D12	IN 4148
D13	Red l.e.d.

Integrated Circuits

IC1	4011
IC2	4017
IC3	555
IC4	4001

Miscellaneous

LS1	miniature loudspeaker
S1	SPST toggle
S2	push to make

P.c.b.
Battery clip
L.e.d. clip
Box

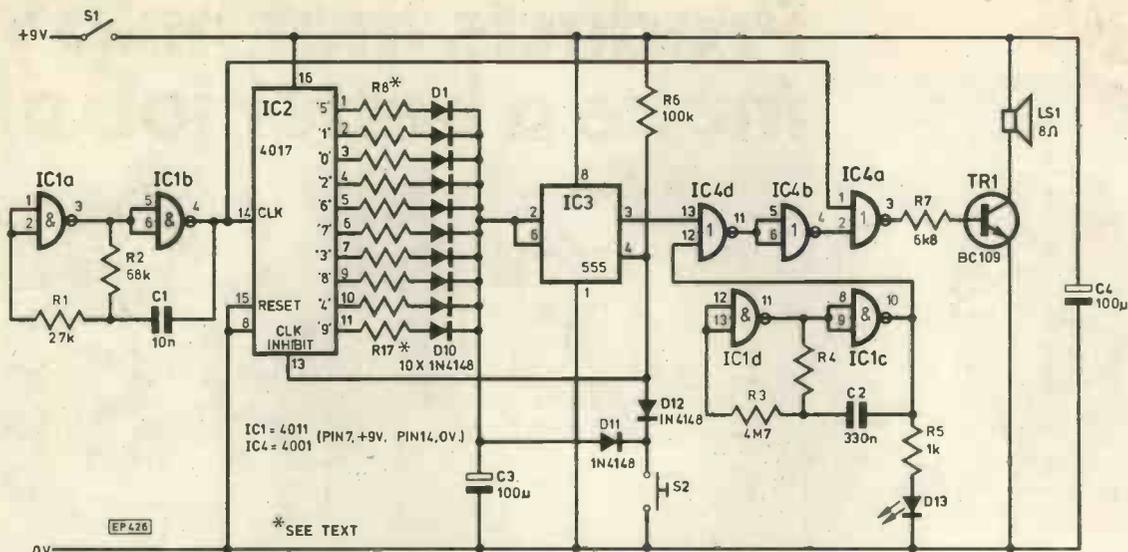


Fig. 1. Circuit diagram

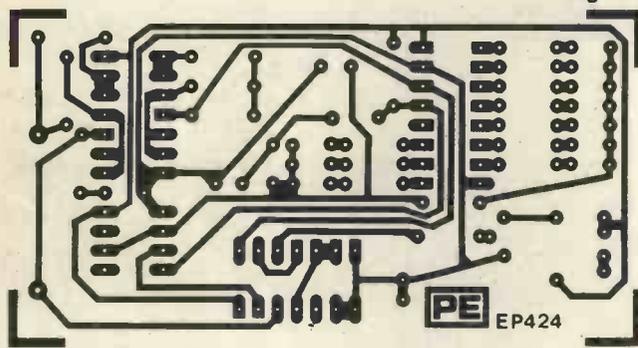


Fig. 2. Printed Circuit (actual size)

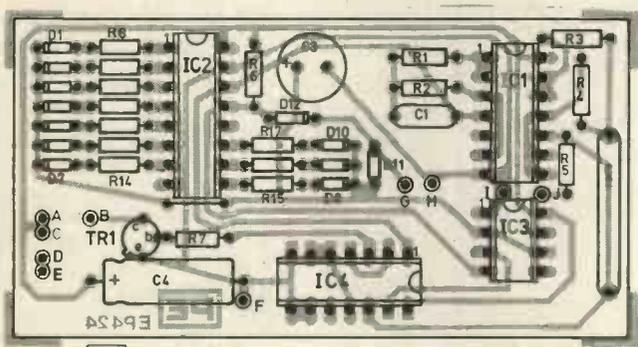



Fig. 3. Component Layout

- A & B to LS1
- C & D to S1
- E to batt. pos.
- F to batt. neg.
- G & H to S2
- I to l.e.d. anode
- J to l.e.d. cathode

CONSTRUCTION

Use of a p.c.b. is recommended for trouble free construction, and a suggested design is given in Fig. 2. Do not forget to include the wire link. Make sure you get the orientation of the i.c.s and the polarity of the capacitors and diodes correct. Refer to Fig. 3. Any small suitable box may be used to house the project. In the prototype case small plastic feet were included, but this prevented the use of mounting bolts, which would have protruded too far, so the p.c.b. was held in place with two double sided sticky pads. The l.e.d. and switches were mounted on the top panel, as was the speaker, using impact adhesive. There is room for a PP6 battery and this provides many months of use.

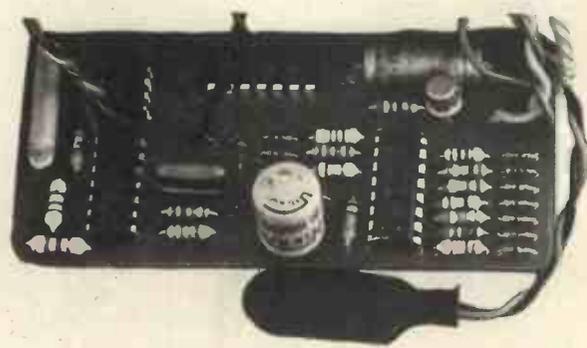The values of resistors for R8-R17 is really the choice of the individual constructor. The author chose values between 100k and 1M which gives a range of approx 15 secs. to 2 mins., but then decided to include two booby resistors of 47k + 68k to give delays of about 5 secs. This added extra spice to the game.



In use, as each player completes a move, he/she presses the reset button for the next player. If the alarm sounds the player has his 5 pulses to make the move before it is forfeited. ☆



Products that help you make a better job of it.

The biggest name in solder worldwide



Arax Multicore Solder.
Economy pack for general non-electrical use.
Replaces solid wire and stick solder. (B.S. 219 Grade L).
Econopak 200g reel of 3mm dia. Size 16A.
£4.14 per reel.



Toolbox Reels.
Multicore 5-core solder for general use. Suitable for electrical joints (B.S. 219 Grade C).
40/60 tin/lead. 1.6mm dia. Size 3. £3.91 per reel.
Savbit.
Multicore 5-core solder for radio, TV and similar work.
Reduces copper erosion. Suitable for service engineers and manufacturers using small quantities of solder.
1.2mm dia. Size 12. £3.91 per reel.



Multicore Wick.
Multicore solder-wick for removing solder from virtually any joint.
1.7mm dia. Size AB10. £1.38 per reel.



Aluminium Soldering.
Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed.
1.6mm dia. Size 4. £11.50 per reel.



Handy Dispensers

PC115	for printed circuits.	Per pack
SV130	for radio and TV repairs.	£1.15
AR140	for non-electrical applications, except aluminium for stainless steel and silver jewellery.	£1.61
SS160	for printed circuit boards - non-corrosive.	£1.38
19A	solder cream for stainless steel, jewellery and household products (non-electrical).	£2.53
AL150	solder cream for electronic and electrical use.	96p
BCA16	all purpose solder cream, non-electrical jointing and repainting.	£1.93
BCR10		£3.22
BCA14		£1.38
		£1.38

Tip Kleen.
Multicore Tip Kleen.
Soldering-iron tip wiping pad.
Replaces wet sponges. (Should not be used above 350°C).
81p per pack.



Soldering Flux Pastes.
Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose soldering.
Rosin R.F.10. 35g net. 69p per pack.
Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical.
Arax A.F.14. 35g. 69p per pack.




Econopak.
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications.
1.2mm dia. 200g Econopak. Size 13A. £4.14 per reel.



Metal Soldering.
Arax Multicore 4-act-d-core solder for metal fabrication (not aluminium) and repairs.
40/60 tin/lead. 1.6mm dia. Size 11. £3.91 per reel.



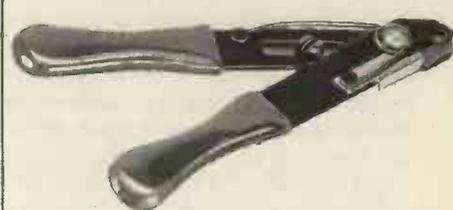TV and Radio Soldering.
Savbit Multicore for radio, TV and similar work. Reduces copper erosion.
1.2mm dia. Size 5. 90p per handy dispenser.
Econopak.
General purpose solder suitable for all electrical joints.
40/60 alloy 1.2mm dia. Size 6. 58p per handy plastic dispenser.



Wire Stripper and cutter.
Wire stripper and cutter with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.
Ref: 9. £2.69 per pair.

have constructed a brass head which talked. The immediate result of this was, of course, an accusation of practising magic! In the Thirteenth Century, the very knowledgeable Albertus Magnus constructed an earthenware head which his disciple is said to have smashed in fright upon hearing it talk.

It is possible that some substance may exist for the claims of some of these early workers, by the action of reeds and organ pipes, but the principles offered by some philosophers are amusing at best. It was thought by one that a hollow pipe could be fashioned to collect human sounds and indeed complete sentences, and return them to the ear when uncorked. By this means, he thought, messages could be sent without paper, and talking heads constructed!

Such was the state of the art by the seventeenth and eighteenth centuries: the desire for progress outstripping, as usual, technology's capability for its fulfilment. Deception was still very common, and not very advanced. Charles II and his court were astonished by a speaking head, shown by one Thomas Irson, which answered questions whispered in its ear.

speech synthesis

Dr. A.A. BERK · part 1

THESE articles describe the fundamental theory of the synthesis of human speech, and the application of this technique to general microcomputer output. An interface board, developed by Modus System Ltd., and based on an American product, is described as a project. This board, very much as the PE VDU did in its "day", provides any microcomputer user with output in the most up to date manner possible. As examples of its application, interfaces are described for the EDUKIT and the CompuKIT UK 101.

HISTORY

Since time immemorial, mankind has tried to emulate the natural phenomena of bird flight and song, the colours of flowers, human activity and speech, and many other things. To some extent, of course, time has produced a degree of success in each of these areas.


In early Greek and Roman times, apparent emulation of human speech was important for the purpose of convincing people of the validity of such religious institutions as oracular pronouncements and idol worship. Even in those times, technology was of some use in aiding this deception. The priests of antiquity were aware of the properties of the speaking tube, and some instances have come down to us of statues speaking by virtue of such a device connecting an unseen talker with the unmoving lips. In the Middle Ages, speech synthesis was professed by some individuals for less supernatural reasons, namely to prove their ingenuity, and often to impress the monarch. In Pope Sylvester II's reign (999 to 1003), he is said to

At the height of their wonderment, a page discovered in an adjoining room a "Popish priest" answering through a speaking tube. Other deceptions involved the exhibiting of figures seated on boxes filled with bellows and sound boxes etc, which upon very careful examination concealed a dwarf.

In 1779, The Imperial Academy of St Petersburg decided to offer their annual prize for solving the problem of describing the difference between the vowel sounds: A, E, I, O and U, and constructing a device to voice these sounds. Professor C. G. Kratzenstein (the inventor of the vibrating reed resonator as used in the harmonica) solved the problem. He produced five resonant cavities, excited by vibrating reeds, very much as the human vocal chords excite the vocal cavities.

In 1791 came Wolfgang Von Kempelen's invention consisting of a bellows to supply a constant supply of air, as with the lungs, to a vibrating reed and hand operated resonant cavity. Several other cavities and additions such as "hissing" sounds were included to emulate all the human sounds. The device was even capable of uttering complete sentences, a fact which has been later proved by Sir Charles Wheatstone in 1837 by his reconstruction (see Fig. 1) and subsequent improvement to the original device.

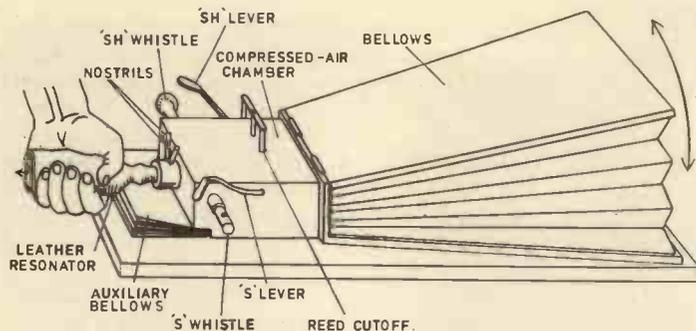The general prevalence of deceptions, however, made it difficult for this first complete mechanical synthesis device to be accepted. Especially as the inventor, Von Kempelen, was himself party to a deception involving a supposed chess playing automaton which won many games before a legless Polish general was found concealed within!



(Scientific American 1972 226:48/58)

Fig. 1. Sir Charles Wheatstone's reconstruction of Van Kempelen's speaking machine. A bellows fed air into a reed which excited the hand controlled resonator. Four separate restricted passages were included for the consonants and nasals.

Von Kempelen's synthesiser marked a major milestone in the art, and remained essentially unmatched until electronics took over, and a machine called the "VODER" was constructed for the New York World's Fair in 1939. Up to this point, the general method of synthesis revolved around copying the actual physics of the human vocal tract, (Fig. 2.)

The physics of natural voice production are those of acoustic filtering. A "wide band noise source" is employed in the glottis, where the vocal chords vibrate under the action of the air forced from the lungs. This vibration excites the cavity between the glottis and the lips, and/or the nasal cavity depending upon the position of the velum. The filtering action which occurs, accentuates certain frequencies, and modifies the sound from the noise source in a complex but well understood manner.

The Voder worked on these principles but took the important step of creating an electronic analogy. Instead of actually expelling air through a set of controllable cavities, a broad band electrical noise source and a random noise generator were filtered electronically, and then amplified and fed to a loudspeaker. The control of the sounds was via a set of hand and foot controls, and as no logic existed for synthesising words, each word had to be produced by the deft manipulation of the controls "in real time". The difficulty of the process, and the complexity of the instrument, can be assessed from the fact that each operator required a year's training, six hours a day, to produce continuous intelligible speech.

PRINCIPLES OF VOICE PRODUCTION

A description of human speech may be given in two different but connected ways. An analysis of the basic phonetic components from which each word in the English language is composed may be performed, and those "phonemes", as they are termed, may be synthesised by a machine, and "called up" as required to produce any given word when written in terms of its phonemes. The other analysis of the voice involves a classification of the exact types of sound which are produced during the enunciation of a word. This would classify the frequencies, speed of production, volume, attack and decay, etc., of these sounds as the word is spoken. To form a word, the necessary frequencies must be produced and mixed in "real time".

The former of these two approaches is termed "phonetic synthesis", and the latter, "frequency synthesis" in the following.

PHONETIC SYNTHESIS

The phonetics of human speech may be split, broadly, into three main components. They are the "voiced", "fricative" and "plosive" sounds. These are described in Table 1. In some cases,

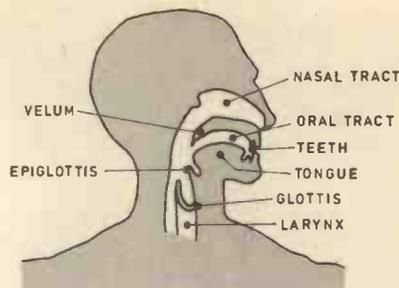


Fig. 2. The Human vocal system consists of two main tracts: The oral tract and the nasal tract. Sounds are produced in the glottis and resonances set up within one or both cavities depending upon the position of the velum.

CLASS	DESCRIPTION	EXAMPLE
VOICED	Continuous sounds such as vowels—the glottis resonates	"a" as in "far" "o" as in "toe"
FRICATIVES	Hissing sounds—the glottis is not required	"s" as in "sound" "sh" as in "wash" "h" as in "hat"
PLOSIVES	Short sharp sounds	"t" as in "hat" "k" as in "make"
MIXTURES	More than one of these sounds may be produced at once	"th" as in "that" is a mix of the fricative "th" and a neutral voiced sound

Human speech may be broken into three main classes of sound or mixtures of these.

TABLE 1

two such sounds may blend into one, an example is given under "mixtures" in Table 1. The fricatives are produced by expelling air through a restricted opening such as between the tongue and the teeth. Try saying "this" slowly—you will notice that your tongue starts behind the teeth and moves back. Two fricatives are thus produced one after the other, the first of which is a mixture of a voiced sound (the vowel I) and a fricative (th). By this means, you could build up a complete catalogue of the types of sound necessary to produce each word in the English language. To do this, you would have to classify a few more scales of sound than the three simple ones shown above. This type of analysis is very valuable for speech synthesis, and is called "phoneme analysis". There are some thirty to fifty such phonemes, or basic speech units, from which the majority of English words may be synthesised. If a machine can be built to reproduce these noises, then each word can be written in terms of its phonemes, the information fed digitally to the machine and words produced. Table 2 lists some of the common phonemes with examples of their use, but is by no means complete.

There are several devices on the market which allow you to perform this type of phoneme construction. The word is first written in a code unique to each machine, and the data fed in, often under BASIC. The speech synthesiser then produces the

PHONEME	USAGE
VOWELS: aw ae ah a e eh er	<u>ta</u> ught <u>ma</u> n <u>ca</u> lf <u>ma</u> ke <u>be</u> <u>ex</u> cellent <u>sur</u> ge
PLOSIVES: b k t	<u>b</u> ad <u>c</u> omputer <u>t</u> op
FRICATIVES: th sh h	<u>th</u> anks <u>rash</u> <u>h</u> ave
SEMI-VOWELS: w y	<u>w</u> ith <u>y</u> ours
NASALS: m n	<u>m</u> an <u>ma</u> n
OTHERS: l r	<u>l</u> aw <u>r</u> an

English words may be broken down into a number of basic units from which any word may be synthesised—these units are called phonemes. Some of them are illustrated here.

TABLE 2


phonemes thus indicated, in the correct time sequence to be heard as a word. The Microspeech Board by Tim Orr (see *Micro Bus*, PE June 1979) is an example of this type of system.

FREQUENCY SYNTHESIS

To understand the second type of speech synthesis, it is necessary to appreciate the exact frequency structure of the voice sounds themselves. The sound we hear when a word is spoken is composed of several basic frequencies which are mixed together in varying proportions as the word is spoken. In addition, the actual frequency pitches themselves change over the time of the word.

To view the actual frequencies and sounds encountered, the vocal tract should be examined again (Fig. 2.) It is clearly seen that there are essentially two resonators available to us during oral speech. These are the full vocal tract from the Glottis to the lips, and the nasal tract. Each of these contributes to word production. It should be borne in mind that they act as resonant filters on the noise produced by the Glottis. The most important cavity of the two, is the tract ending in the lips. In English, the nasal passage is used for only a few sounds (n and m). The main tract may be viewed, ideally, as a single ended resonant cavity of around 17cms in length. (Fig. 3.) Some 'O' level physics reveals that the sort of resonances which such a pipe may suffer are only those of odd-multiple quarter-wavelength as shown. For the length of 0.17m and the speed of sound under normal conditions of 330 m/s, the first three (and most significant) resonances will be as shown. Since the "noise source" which makes the cavity resonate contains all these frequencies, and more, these are available to be accentuated, or filtered out by the cavity. They are called the first three "Formants", and they change continuously during any utterance. Their ranges are given, very approximately. The reason for the frequency variations during word production, is concerned with the complexity of the vocal tract and the constant adjustments made by the musculature during normal speech.

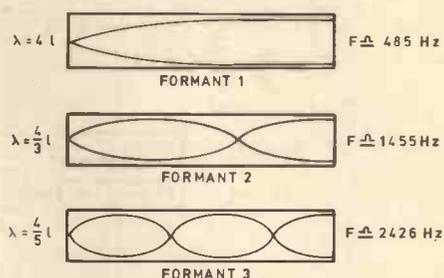VELOCITY OF SOUND APPROX: $v = 330 \text{ m/s}$
CYLINDER LENGTH: $l = 0.17 \text{ m}$
FREQUENCY: $F = v/\lambda = \text{VELOCITY/WAVELENGTH}$



APPROX VOCAL FORMANT RANGES (FOR COMPARISON)
FORMANT 1: 200 Hz - 800 Hz
FORMANT 2: 800 Hz - 2400 Hz
FORMANT 3: 2400 Hz - 3000 Hz

EG 418

Fig. 3. The first three resonances of a 17cm long cylinder (with one closed end) are shown here. This gives a guide to the main resonances (Formants) of the vocal tract.

These formants may be adjusted in pitch and mixed in different amplitudes to produce the pure voiced vowel sounds. However, they are not sufficient to produce the nasal sounds, which rely on a separate resonator, or the fricatives which are full of random noise. Two more generators are thus necessary for the complete sound. This gives just five different generators to be controlled for a full synthesis. However, these controls involve volume as well as pitch over the time envelope of each word. This type of real time control requires something of the complexity of a microprocessor.

CONSTANT VOWELS

	F1	F2	F3
ee as in <u>seed</u>	240	2300	2900
oo as in <u>wood</u>	420	950	2400
o as in <u>rod</u>	770	1100	2500
aw as in <u>door</u>	570	900	2400


DIPHTHONG VOWELS:

	F1	F2
<u>toy</u>	400-500	1100-2100
<u>pro</u>	400-700	1700- 900

English vowel sounds are produced by adjusting the mix of formants present in the final sound. Diphthongs are produced by smoothly running vowels into each other.

TABLE 3

To illustrate the formant variation during voice production, Table 3 gives typical values to the formants during the constant and diphthong vowel sounds. To appreciate the difference, try saying these sounds to yourself in a normal tone, and listen for the pitch changes, you should not drop your voice as you say the words. The constant vowels use, essentially, constant pitches for the formants, while the diphthong gains its variation by changing the formant pitches as the vowel is sounded. Diphthongs may be considered as mixtures of vowel sounds, which run into each other. The total structure of the voice sounds includes fricative pitch and amplitude changes, as well as nasals. A com-

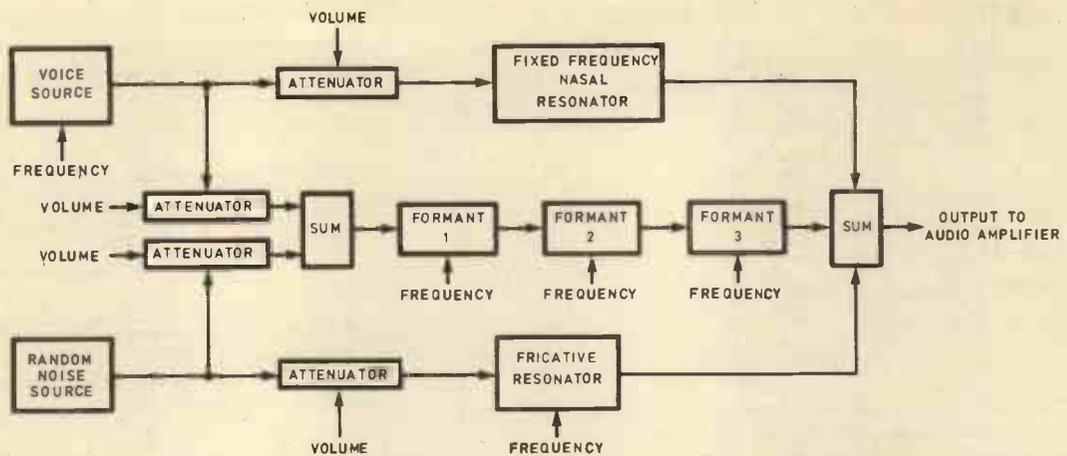

EQ 417

Fig. 4. This "classical" voice synthesis unit requires just nine parameters to specify a single sound (four "volumes" and five frequencies). The "frame" of nine parameters is updated (typically) fifty times a second during the production of a word.

plete list is beyond our present scope, but a fuller picture is introduced below, when electronic voice synthesis is described in more detail.

STORAGE OF SPEECH

One interesting aspect of the above is concerned with the storage of speech in ways other than the conventional manner of grooved disc or magnetic tape. One's first instinct is to think of a system which simply digitises the sound waveforms, and stores them in memory for later retrieval and faithful reproduction. The simplest calculation, based on the evidence, shows that around 8K to 10K Bytes of memory are required for each second of speech-quality recording. This amount of memory is probably best handled by such devices as magnetic tape memories!

The best method for storing speech for output from a computer, is to use one of the approaches suggested by the above two analyses. Words may be stored as phonemes in comparatively small memory blocks, and presented to a "phoneme player" for output. Alternatively, information of frequency, amplitude, fricative content etc is stored digitally, for feeding to a set of sound generators in the correct time sequence, very much as the operators of the VODER would have done.

By one of these means, the common elements of English words are used to reduce the amount of storage necessary for each utterance. The complexity is confined to hardware frequency synthesisers, and controllers.

ELECTRONICS

The electronics of speech synthesis are very interesting, and some of the techniques can now be examined.

Once again it would be tempting to think of some very straightforward approach to the frequency synthesis in the second approach above. Perhaps variable oscillators would be useful, and when their outputs are mixed a perfect synthesis would result. However, it turns out to be considerably easier to attain a natural sound by simply copying nature, and applying controllable resonant filters to the output of a broad band noise generator. (Fig 4.) This provides an almost classical approach to speech synthesis, and would form the electronics for both approaches mentioned above. The first approach would accept phoneme data, and under microprocessor control adjust the frequencies and amplitudes accordingly. The second approach would store the actual values of all those variables and present them to the synthesiser at some sample rate to produce the complete word.

The different sounds arise as follows. The general pitch of the utterance is controlled by adjusting the frequency of the voice source. Pure vowels are produced by one volume and three frequency adjustments to the three formants, and perhaps the nasal resonator volume. Fricatives are produced by a frequency parameter and a volume, and plosives include sudden adjustment to the volume of random noise fed into the voiced channel. In Tim Orr's system, this "frame" of nine parameters is updated fifty times a second. The total effect of the system is considerably greater efficiency of storage than simply digitising speech without analysis.

The other common electronic system is that of Linear Predictive Coding, described below.

LINEAR PREDICTIVE CODING

This technique takes frequency synthesis to a logical ending, and filters, in an "intelligent" manner, the necessary formants and frequencies from a single excitation. It is important to realise that the central principle to which all these techniques are aimed is that of reducing speech to a small set of parameters for efficient memory storage. To this end, the number of parameters needed to specify a sound should be of the order of 10 or 12, and this "frame" should be updated at a rate of around 40 or 50 times per second. The number of bits per parameter in a frame is the main variable, and the more bits, the more accurately the frame is specified. The Texas Instruments "Speak and Spell" unit is based around a Linear Predictive Coding (LPC) system. This system uses a maximum of 48 bits per frame at 50 frames per second i.e. 2400 bits of storage per second of speech.

Words are coded into special binary patterns by speaking them into a microphone connected to a large computer. On this machine, a program is running to convert the sound into codes for storage, and eventually for driving the synthesis unit. In this manner any word may be stored on ROM for later selection and playing.

Each word has a unique set of addresses in the final ROM, and a custom vocabulary may thus be formed. When a word is selected the bits associated with it are fed to the synthesiser which consists of a noise generator, and a 10 stage digital lattice filter, (Fig. 5.) The bits from the ROM are used to set up the filter components in order to produce a binary number which is fed to a digital to analogue converter. As the word is produced, the binary number changes, and the analogue output sounds like speech. In order to prevent sudden changes between frames, a certain amount of linear interpolation is included in the process.


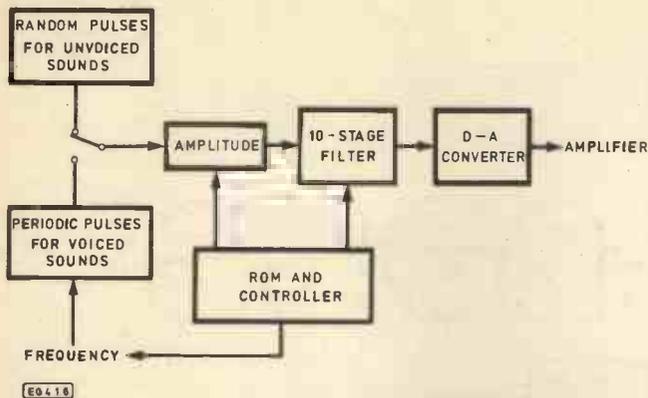


Fig. 5. The Texas Instruments Linear Predictive Coding System codes words into the coefficients of a ten-stage digital filter. A maximum of 2400 bits of data per second of speech are required to adjust the filter coefficients, type of excitation and pitch and frequency as a word is produced.

which is controlled by a form of TI's TMS1000.

The excitation has two time varying parameters, amplitude and pitch. For voiced sounds, a periodic excitation is used, for unvoiced sounds, pseudo random noise of constant amplitude is fed in.

The filter components themselves are quite interesting and along with the controller, ROM and all the other components, illustrates the complexity possible with modern microelectronics. Each of the ten stages (Fig. 6.) contains two adders, two multipliers and a shift register delay circuit. The filtering is thus produced by binary calculation in real time to model the time

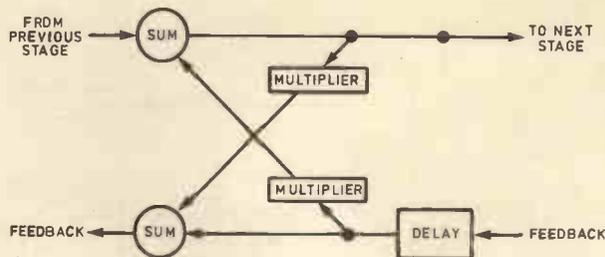

EG 4.13

Fig. 6. This illustrates one of the ten stages in the lattice filter used to electronically model the Human Vocal Tract—The multiplication factor (used in both multipliers) is fed from the speech storage ROM.

varying functions of normal speech. A 10 kHz sampling rate is used for the filter; thus during the 100 micro seconds of one sample, two 14 bit additions, and two multiplications are performed. It is due to the difference in speed between these two operations that the delay is necessary. The ROM supplies just the multiplier coefficients for each stage. With judicious use of data, an average data rate of 1500 bits per second of speech may be achieved, giving 165 words, approximately, in a 131K bit ROM. The output sounds excellent, and may be improved upon by incorporating more stages to the filter.

NEXT MONTH: SPEECH SYNTHESISER DESIGN

This project which will add speech synthesis to any micro-computer will be described along with interface examples for two popular microcomputers.

There will also be a special offer of a 24-word speech board available for £39.95 (plus VAT).

**I.C.
REMOVAL
TOOLS**

**IT'S NOT
TOO
LATE!**



Last October we gave you a free I.C. removal tool, and we still have a limited number available for those of you who missed out last time.


All you need to do is send a postal order for thirty pence (made payable to IPC Magazines) and a stamped self addressed envelope to:

Practical Electronics (I.C. Removal Tool), Westover House, West Quay Road, Poole, Dorset BH15 1JG.
(Please do not enclose any other correspondence.)

SPECIAL OFFER...

PE CONGRESS

30W I.C. STEREO AMPLIFIER

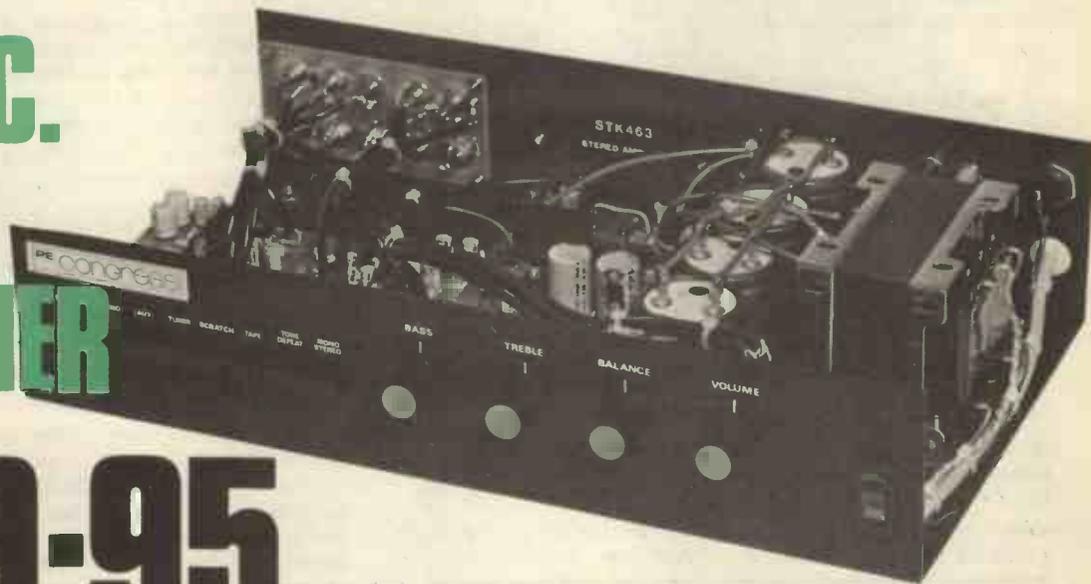

£69.95

Including V.A.T. Postage & Packing

PE, in conjunction with Wicca Systems Ltd., have arranged a special offer price on the *PE Congress* amplifier kit. The Congress amplifier was originally published in April, May and June 1980 and a full spec. and description appeared in the April issue. A brief spec. is given below for those not familiar with this design. The published specification was a result of independent tests carried out by Gordon J. King, the well-known hi-fi reviewer.

The normal price of the kit is over £85, but for the period of this offer PE readers can buy it for £15 less. Photostat copies of the original series of articles are available from Wicca for £1.20. The kit includes metalwork and printed front panel but not a case.

SPECIFICATION

Output, 30W continuous sinewave per channel both channels driven

Distortion factor at 1kHz, 0.024%

Intermodulation distortion 19kHz + 20kHz, 10dB o/p per channel, 0.03% 1kHz product

Slew factor, >5 (ref. 14.8dB, 1kHz, 8Ω)

Damping factor, 66

PU overload threshold at 1kHz, 185mV

Signal to Noise ratio (CCIR/ARM weighting), 85.7dB and 75dB (p.u. input)

Stereo separation at 1kHz, 72dB and 70dB (p.u. input)

Crosstalk at 1kHz, 84dB and 77dB (p.u. input)

Frequency response \approx 5.5Hz—109kHz (—3dB points)

Offer limited to UK and BFPO addresses only.

Offer limited to UK and BFPO addresses only.

To: WICCA Systems Ltd. (P.E. Offer), 24 Hillcrest Parade, The Mount, Coulsdon, Surrey.

Please complete both parts of the coupon in BLOCK CAPITALS

Please send meCongress kits at £69.95 each

I enclose P.O./Cheque No. Value.....
Make cheques payable to Congress Electronics Project

Name

Address


Please allow 28 days for delivery
OFFER CLOSES FRIDAY 28th NOVEMBER

Name

Address

From: WICCA Systems Ltd. (P.E. Offer), 24 Hillcrest Parade, The Mount, Coulsdon, Surrey.

SECURITY

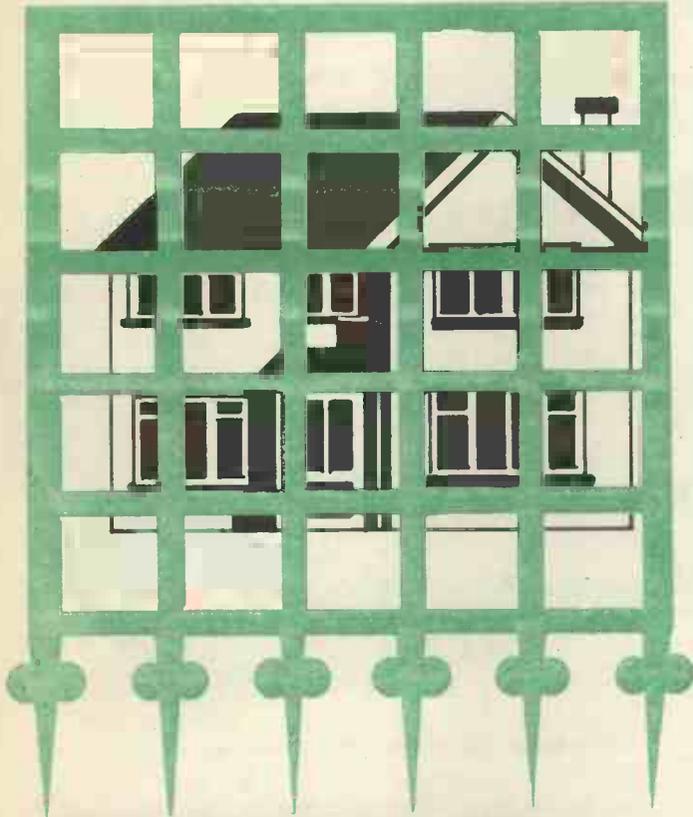

SENTINEL...

Part 1 W.C. Dickinson

THE major problem with many available alarm units is that they can be easily disarmed without being triggered. Alarms are generally sensed by magnet/reed switches on doors and windows, metal foil on window glass and pressure mats under carpets. Unfortunately, as the use of alarm systems has become more widespread, the techniques of defeating these systems have also become common knowledge. The simple magnet/reed switch combinations that form the basis of most systems are easily detected with a compass. Once they are located they can be magnetically shunted with a powerful magnet or the glass cut and the switch shorted with a jumper wire. In large commercial systems these 'perimeter' sensors are usually employed as the first line of defence. They are then backed up by several other devices. Most domestic installations cannot be this elaborate due to the costs of the wiring involved. More often than not the economic considerations of domestic installations result in closed loop magnet/reed-

switch detectors being the sole method of detecting an intrusion. Whilst some form of alarm system is better than none at all, a conventional system does not offer as much in the form of a deterrent as it used to. This alarm unit has six independent alarm channels, each protecting a specific area of the premises, and these will respond to any combination of the following alarm conditions:

- Pressure pad stepped on (normally open, close for alarm)
- Magnet-switch(es) opened (normally closed, open for alarm)
- Magnet-switch(es) shunted with a magnet or jumper wire (tampering by thief)
- Window glass foil broken (normally closed, open for alarm)
- Window foil shunted (tampering by thief)
- Alarm wires cut (tampering by thief)
- Alarm wires shorted (tampering by thief)

Standard fire detectors can be included in the loop.

Every alarm condition described above is detected using only one twin-conductor wire per channel. This feature not only improves the integrity of the system but also simplifies the installation of the system.

Each channel can be selected (Activated or Defeated) individually. Any alarm condition, even a momentary one, detected whilst the alarm system is activated will latch the alarm channel into alarm status. A noise suppression circuit prevents a.c. hum and impulse noise spikes which may be picked up by the field wiring from being sensed as an alarm. Alarm status is indicated by a flashing l.e.d. above the channel selector switch. This enables the source of the alarm to be identified and located quickly. Each channel can provide an immediate alarm or a delayed alarm, as required. Exit and entry delay timers are provided so there is no necessity to fit an external key switch. On activation the exit delay is initiated which allows you one and a half minutes to leave the premises before the system automatically arms itself. Upon re-entry the alarm channel which monitors the entrance will immediately trigger and lock into alarm status. The entry delay timer allows you one minute to defeat the alarm before the siren is triggered. If the alarm is not defeated within the allowed time the siren will begin sounding. An automatic validation circuit resets all alarm channels after the siren has been sounding for one and a half minutes. If the source of the alarm is no longer present the siren will silence and the alarm system will re-arm itself. If the alarm is still present or another channel is sensing an alarm the siren will continue to sound until the next validation cycle one minute later. The validation cycle will continue indefinitely until all channels are clear of alarms or the



system is manually reset. All timing intervals are easily adjusted to suit individual requirements.

SYSTEM TEST

One of the major problems presented by conventional designs which employ exit delays is that you never know if the system is in an alarm condition when you activate it. To find out you must generally go through an elaborate and time consuming test procedure. Another drawback is the uneasy feeling you get unless you make a hurried exit in order to "beat the clock". Clearly, neither of these circumstances is desirable.

The first problem has been eliminated by a completely automatic confidence test on activation of the system. Each time the alarm system is activated every alarm channel is enabled for 0.8 seconds. If any channel detects an alarm condition, the alarm status i.e.d. will begin to flash. Any selected (activated) alarm channel detecting an alarm during the 0.8 second test will cause the alarm system to abort the test cycle and lock into 'system fault'. This is indicated by an i.e.d. on the front panel. Only when all channels are clear of alarm conditions for the duration of the 0.8 second test cycle (or channels which have alarm conditions are defeated) will the system proceed with the exit delay. When the system has passed the activation tests, the 'exit' delay will be initiated. This is indicated by an i.e.d. marked SYSTEM OPERATIONAL on the front panel and the green i.e.d. at the remote mimic illuminating. When the 'system operational' i.e.d. illuminates, you can leave the premises in confidence, knowing that the selected alarm channels will not initiate an alarm after the exit delay has ended.

The second problem has been alleviated by providing an i.e.d. mimic outside the normal exit point. This mimic duplicates two of the indications provided at the alarm control centre via two coloured i.e.d.s which are connected via a single twin-conductor wire. 'System operational' is indicated by the green i.e.d., 'system alarm' is indicated by the red i.e.d. When you close the exit door as you leave the premises a quick glance at the mimic will indicate the status of the system. The green i.e.d. indicates all clear, the red i.e.d. indicates you were too slow in leaving the premises. The 'system alarm' output of the control centre can also be wired to a solid-state signal unit mounted in your bedroom to provide a pre-siren alarm signal.

OPERATING CURRENT

During the design of this system special emphasis was placed on quiescent and operating current demands. When the alarm system is operating normally from the mains and the system is defeated, the only significant current is the 120 milliampere charge current for the nickel-cadmium batteries and 'power on' i.e.d. The remainder of the system only requires a negligible 10 microamperes. When the alarm system is activated and is passive, i.e. no alarms detected, the maximum battery current in the event of mains failure is 400 microamperes. This low current drain enables the alarm system to operate in the passive mode for well over three months without mains and still have plenty of power in reserve to operate the siren if an alarm is detected. Having the capability to operate for prolonged periods without mains power is particularly advantageous when you leave your house unattended during your holidays and wish to shut off the mains supply to minimise the risk of fire in your absence.

CIRCUIT DESCRIPTION

The complete circuit diagram of the system is shown in Fig 1.1. Each of the eleven logic blocks has been given a

series of numbers for component designations (1, 10, 20, 30, 40, etc): The alarm sensing circuit has three operating modes.

- (a) It can detect an open circuit caused by the wires being cut, the opening of any of the series connected switches or if the metal foil tape on a window is broken.
- (b) It can detect a short circuit caused by the wires being shorted, any of the specially modified series connected switches being shorted, or if a pressure pad is stepped on.
- (c) The circuit will also detect if any of the modified switches is being magnetically shunted.

The operation of each of the six channels is the same and only one channel is shown in Fig 1.1.

ALARM CIRCUIT

IC10C and IC10D are cross coupled to form an alarm latch set-reset flip-flop. IC10B ensures that the 'reset' (defeat) signal is given priority over the 'set' (alarm) signal. When the system is defeated a logic '1' from the reset bus is presented to pin 1 of IC10B and pin 13 of IC10D. This locks the flip-flop in a stable state with a '1' at the output of IC10C and a '0' at the output of IC10D. When the reset bus goes to '0' the flip-flop is free to latch into the alarm state upon presentation of a '1' to either input of IC10A. Pin 6 of IC10A is connected to the 'test bus' which is held at '0' by the pulldown resistor R5. When the 'test' switch, S70, is depressed, a '1' is applied to the 'test bus' which simulates an alarm condition at each of the six alarm channel inputs. The other input of IC10A monitors the alarm sensors in the area being protected. If the channel detects an alarm whilst the system is activated the output of IC10C will go to '0'. This is coupled through D10 and S10 to the 'delayed alarm bus'. When IC10C goes to '0' IC10D goes to '1'. If D11 is installed this '1' will be coupled to the 'immediate alarm bus' via S10. If S10 is open both alarms will be ignored by the alarm control logic. The '1' at the output of IC10D is also coupled to TR10 via R12 driving TR10 into conduction. The voltage at the anode of D10 via R13 is pulsating at 4Hz. Therefore D10 will flash whenever the channel detects an alarm. D10 will flash regardless of the position of S10.

TRI-MODE ALARM

Switch SA, diode D and resistor R are inside the enclosure for SA and form the heart of the 'Tri-Mode' operation. SA is positioned within the field of the magnet. Switch SB is positioned just outside the field of the magnet. When the door or window being protected is closed, SA will be pulled closed by the field of the magnet. SB will remain open.

IC70 is a 4Hz astable multivibrator which is used to flash the channel alarm indicator. If we momentarily lock the 4Hz multivibrator into a stable state with \bar{Q} at '0' and Q at '1' this senses continuity in the alarm loop. Providing that SA is closed, diode 'D' will pull down the input of IC10A to '0'. Germanium type diodes have been selected for use in this circuit as they have a low forward voltage drop (0.2V). Four modified switches in series will drop 0.8 volts.

In order to ensure stability under low voltage conditions and maintain a high degree of immunity to noise, each channel should be limited to a maximum of four modified switches. As there are no voltage drops in the unmodified switches, any number of these can be used. If the closed loop is broken by cutting the wires or opening SA, R10 and VR10 pull the input of IC10A to '1' via R14. R11 and C10 have a time constant of approximately 60ms. This ensures maximum immunity from any noise impulses picked up by the wiring between the alarm control centre and the sensing

COMPONENTS ...

Resistors

R1, R2	68 $\frac{1}{2}$ W (2 off)
R3	68
R4, R101	47 (2 off)
R5	27 $\frac{1}{2}$ W
R10, R20, R30, R40, R50, R60	47k (6 off)
R11, R21, R31, R41, R51, R61, R14, R72, R74, R80, R87, R88, R95, R98, R99	10M (15 off)
R12, R22, R32, R42, R52, R62, R73, R82, R86, R93, R96	10k (11 off)
R13, R23, R33, R43, R53, R63, R85, R94, R97	330 (9 off)
R70, R90	100k (2 off)
R71, R92	1M (2 off)
R75, R100	1k (2 off)
R81	200k
R83, R84	390k (2 off)
R89	560k
R91	3M9

All resistors $\frac{1}{2}$ W 5% carbon except where otherwise stated.

Capacitors

C1	1000 μ 25V elect
C10, C20, C30, C40, C50, C60	10n ceramic plate (6 off)
C70, C80, C81, C82	4 μ 7 10V tant (4 off)
C2, C71, C72, C83, C90, C91	16 μ 10V tant (6 off)
C92	47n polyester

Potentiometers

VR10, VR20, VR30, VR40, VR50, VR60	100K sub min vertical pre-set (6 off)
------------------------------------	---------------------------------------

Diodes

LED1	0.2" yellow LED
LED10, LED20, LED30, LED40, LED50, LED60, LED80, LED90, LED91	0.2" red LED (8 off)
D1, D2, D3	0.2" green LED
D4, D6	IN4001 (3 off)
	OA91 (2 off)

D5, D10, D20, D30, D40, D50, D60, *D11, *D21, *D31, *D41, *D51, *D61, D70, D80, D81, D82, D83, D84, D85, D90, D91, D92, D93, D100	IN4148 (25 off)
ZD1, ZD3	BZY88C7V5 (2 off)
ZD2	BZY88C3V6

Transistors

TR1, TR10, TR20, TR30, TR40, TR50, TR60, TR70, TR71, TR80, TR90	BC337 (10 off)
TR91, TR100	BC327 (2 off)
TR101	TIP31A

Integrated Circuits

IC10, IC20, IC30, IC40, IC50, IC60, IC70, IC80, IC81	CD4001 (9 off)
IC90	CD4011

Switches

S10, S20, S30, S40, S50, S60, S80	p.c.b. mounted 2 pole changeover (7 off)
S70	p.c.b. mounted, 2 pole changeover (momentary)

Miscellaneous

20mm fuse holder
20mm 100mA fuse
4-way p.c.b. terminal block (4 off)
3-way p.c.b. terminal block
Low profile i.c. sockets 14 d.i.l. (10 off)
Veropins
Transformer 6VA sec. 6-0-6V 500mA
Battery holder for four HP11 size batteries
Ni-Cad battery HP11 (4 off)
Case
Ribbon cable
p.c.b.
Siren (Carters Minimite)
*See text

Constructor's Note

A complete kit of parts for the Security Sentinel is available from **Compu-Tech Systems, Laundry Loke Industrial Estate, Gaymers Way, North Walsham, Norfolk.**

devices in the area being protected.

When the output of the 4Hz multivibrator is reversed and locked ('Q' to a '1' and 'Q' to a '0') the system senses if any of the sensors are shunted within the alarm loop. Assume that SA is closed and SB is open. Under these circumstances the input of IC10A will be '0'. This is established by the ratio between Resistor 'R' in SA and the combined resistance of R10 and VR10. Resistance 'R' will always be greater than the combined resistance of R10 and VR10. Variable resistor VR10 provides compensation for component tolerances and the logic threshold of IC10. A feature of

CMOS integrated circuits is that the logic thresholds 'track' changes in the supply voltage. As any changes in supply voltages will be present on the 'Q' and 'Q' buses as well, the circuit remains stable over the full discharge voltage curve of the batteries. With the ratio between resistor 'R' and R10 + VR10 setting the input of IC10A at '0' but only slightly below the threshold for '1' any reduction in the value of resistance 'R' will cause the input of IC10A to go to '1'. If the wiring to switch SA is shorted, 'R' will be zero ohms and an alarm is sensed. If the burglar brings another magnet near the sensing switches, SB will close which again will reduce

'R' to zero and will be sensed as an alarm, with the maximum number of modified switches (four) in series shunting any one of the switches reduces the total loop resistance to $\frac{3}{4}$ of its nominal value. This reduction in loop resistance will also cause the Input of IC10A to go to '1', providing VR10 is adjusted properly. If a pressure mat or other shunt device is used the effect is similar to SB being closed.

AUTOMATIC SYSTEM TEST

Each time the system is activated an automatic system test is carried out. If this section is used in conjunction with the manual test switch (S70) the entire system can be checked in a few seconds.

If no alarms are detected and switch S80 is in the 'defeat' position a '1' is presented to pin 2 IC80B and the inputs of IC81C via pull up resistors R84. The timing capacitor C82 is shunted by S80 and is discharged. The resistor R84 and capacitor C82 form timer 'A' with a time constant of 1.6 secs.

A '1' is provided directly by S80 to pin 13 of IC80D and to pin 1 of IC81B via D83. C81 and R83 form timer 'B' with a time constant of 1.6 seconds. IC80C and IC80D are cross-coupled to form a confidence latch set-reset flip-flop. With a '1' at pin 1 of IC80B the output of IC80B will be '0' which pulls down pin 8 of IC80C and discharges C80 via D81. R81 and C80 form timer 'C' with a time constant of 0.8 seconds. With a '0' at pin 8 of IC80C and a '1' at pin 13 of IC80D the flip-flop will be locked into a stable state with a '1' at the output of IC80C and a '0' at the output of IC80D.

When switch S80 is switched to 'activate', timer A is initiated which enables all the alarm channels: Providing that the system does not detect an alarm for 0.8 seconds (timer B) the system will pre-empt timer A and the exit delay will be initiated which is indicated by the 'system operational' l.e.d. illuminating. Once the l.e.d. is extinguished the system is armed and any alarm detected will start the alarm sequence.

R74 pulls pin 13 of IC80D down to '0' allowing the set-reset flip-flop to change states if a '1' is presented to pin 8 of IC80C. The negative side of C82 is switched to V- by S80. This pulls pin 2 of IC80B and the inputs of IC81C to '0'. R84 will begin to charge C82 towards '1' (timer 'A'). A '0' at the inputs of IC81C results in a '1' at its output. This '1' is coupled to pin 9 of IC81D via R88. The '1' at pin 9 of IC81D causes the output of IC81D to go to '0'. This '0' enables (activates) all of the alarm channels for the duration of timer 'A', 1.6 seconds. The '0' provided by timer 'A' to pin 2 of IC80B allows IC80B to respond to the logic level at pin 1. Providing that no alarms are detected, pin 1 of IC80B will remain at '0'. A '0' at both inputs of IC80B result in a '1' at its output which begins to charge C80 through R81 (timer 'B'). In approximately 0.8 seconds a '1' will be presented to pin 8 of IC80C which will cause the set-reset flip-flop to reverse states and lock with a '0' at the output of IC80C and a '1' at the output of IC80D. Once the confidence latch flip-flop has changed states it will remain locked in this mode until S80 is moved to the 'defeat' position. As soon as the flip-flop changes states the '1' at the output of IC80D is coupled to pin 1 of IC80B via D82. The '1' at pin 2 of IC80B forces its output to '0' and dumps the charge on C80 via D81. This ensures that no ambiguous inputs can be applied to the inputs of the flip-flop. The '1' at the output of IC80D also charges C82 to '1' via D82 and pre-empts timer 'A' which switches the output of IC81C to '0' causing the output of IC81D to go to '0' disabling all the alarm channels. The '0' at the output of IC80C is passed to pin 5 of IC81A which allows IC81A to respond to any subsequent alarm signal presented to pin 6. The '1' at the output of IC80D is passed to pin 8 of IC90A

via interboard wire 'k'. This '1' also begins to charge C83 through R87. C83 and R87 form the 'exit delay' timer and have a time constant of approximately one and a half minutes. The output of IC81D will remain at '1' which inhibits the alarm sensing action of the alarm channels until the exit delay has elapsed and a '1' has developed across C83. This is presented to pin 8 of IC81D which causes its output to go to '0' which enables the alarm channel. Providing the system passes the activation test as detailed above, pin 8 of IC90A will remain at '1' for as long as the system is activated. Pin 9 of IC90A will only remain at '1' for the duration of the exit delay. When both inputs of IC90A are at '1' its output will be '0'. A '0' at the output of IC90A forward biases TR91, via R96, illuminating LED91, indicating that the system has passed the activation tests and the exit delay is in progress. R97 limits the current through LED91, the 'system operational' l.e.d. and also develops the potential required by the external mimic l.e.d. As soon as the exit delay has elapsed the output of IC90A will return to a '1' and LED91 (and the remote mimic) will extinguish, indicating that the system is now armed.

ALARM STATUS

If the alarm is detected before timer B times out, the system will lock into 'system fault' and the alarm sequence will be disabled. The alarm channels will remain enabled after timer A has timed out so that the channel which caused the alarm can be indentified.

The '0' provided by timer 'A' to pin 2 of IC80B allows IC80B to respond to the logic level at pin 1. If any of the selected alarm channels pull down the delayed alarm bus to '0' during the 0.8 second timing interval of timer 'B' the following sequence takes place. The '0' at the inputs of IC80A is inverted to a '1' and is presented to pin 1 of IC80B. This causes the output of IC80B to go to '0' which dumps any charge that had developed on C80 via D81. The '0' on the delayed alarm bus also pre-empts timer 'C' by discharging C81 via R82 and D80. At this point the set-reset flip-flop will remain in its original state with a '0' at the output of IC80D as pin 8 of IC80C never reached '1' within the 0.8 seconds allowed. The '0' at the output of IC80D is coupled to pin 2 of IC81B. Pin 1 of IC81B is pulled to '0' by the common alarm bus at mentioned above. Both inputs of IC81B at '0' results in a '1' at its output. This '1' forward biases TR80, via R86, illuminating LED80. R85 limits the current through LED80, the 'system fault' l.e.d. The '1' at the output of IC81B is also coupled to the input of IC81D via LED85. R88 ensures that the output of IC81B has priority over the output of IC81C. Pin 8 of IC81D is pulled to '0' by the output of IC80D via D84. With pin 9 of IC81D locked to '1' the output of IC81D will remain at '0'. This ensures that any alarm channel which detected an alarm will remain locked in alarm status when timer 'A' times out. Since the set-reset flip-flop never changes states, pin 5 of IC81A will remain at '1' which prevents the alarm signal from initiating the alarm sequence by locking the output of IC81A to '0'. The output of IC80D holds the input of IC81A at '0' via interboard wire 'k' and D91, again locking the output of IC81A to '0'. This prevents the 'immediate alarm bus' from initiating the alarm sequence.

ALARM SEQUENCE

When the system has passed its activation tests and is armed, if any alarm channel detects an alarm then the alarm latch flip-flop will lock into alarm status and the channel alarm l.e.d. will begin flashing. If the alarm channel is selected the delayed alarm bus will be pulled down to '0'. The '0' at pin 5 of IC81A combined with a '0' from the delayed

alarm bus at pin 6 of IC81A causes the output of IC81A to go to '1'. This '1' is connected to the alarm logic p.c.b. via interboard wire 'Q' and forward biases TR90 via R93 illuminating LED90, the 'system alarm' i.e.d. R94 provides current limiting for LED90 and develops the potential required by the external mimic and pre-siren signalling unit.

The '1' is coupled directly to pin 5 of IC90C and begins to charge C90 through R91. C90 and R91 form the 'entry delay' timer and have a time constant of 1 minute. If the alarm channel has been wired for an immediate alarm the '1' at the output of IC10B will force the immediate alarm bus to '1' via D11. This '1' will charge C90 via R89 and interboard wire 'r'. The time constant of ten seconds provided by R89 and C90 serves to confuse anyone tampering with the system. The 'immediate alarm' is in fact a 10 second delayed alarm. As the siren will not go off immediately when the system has been tampered with the intruder never knows exactly what he has done to set off the alarm. This anxiety serves to deter any attempt to return and try again. If S80 is switched to defeat at any time the system will abort any sequences in progress and return to its quiescent state. R92 and R99 in conjunction with TR100 provide hysteresis at the inputs of IC90B converting it to a Schmitt trigger. When C90 has charged sufficiently to present a '1' to IC90B the output of IC90B goes to '0'. TR100, R101, and TR101 form a saturated switch with very high gain and very low saturation voltage across TR101. When TR100 is forward biased via R100 it drives TR101 into saturation via R101. When TR101 is conducting, an earth return is provided for the siren and it will begin to wail. D100 absorbs the spikes created by the commutator in the siren.

When C90 presented a '1' to IC90B it also presented a '1' to pin 6 of IC90C. IC90C now has a '1' at both inputs which causes its output to go to '0'. C91 will now begin to discharge into IC90C through R98. C91 and R98 are the 'validation reset' timer and have a time constant of one and a half minutes. In one and a half minutes C91 has discharged sufficiently to provide a '0' to the inputs of IC90D. Several things happen in rapid succession at this point depending on the status of the alarm sensors.

AUTOMATIC RESET

If we look at the sequence of events based on the assumption that the alarm originally detected is no longer present. Also that, when no alarms are being sensed by any of the other alarm channels and the input of IC90D reaches '0' the output will go to '1'. This is coupled to the 'master reset bus' via D93 and charges C93 immediately. When the 'master reset bus' goes to '1' all of the channel alarm latches are reset to a 'safe' condition which causes the 'delayed alarm bus' to return to '1'. The 'delayed alarm bus' '1' is coupled to pin 6 of IC81A forcing its output to '0'. TR90 will no longer be forward biased so LED90 will extinguish. C90 will discharge into IC81A via R90, R91 and D90. The time constant of R90, R91 and C90 is approximately one second. When C90 has discharged sufficiently to present a '0' to the input of IC90B which forces its output to '1', the saturated switch (TR100 and TR101) will cease to conduct silencing the siren. The '0' at the output of IC81A is also coupled to pin 5 of IC90C which forces its output to '1'. C91 is charged immediately via D92 and presents a '1' to the input of IC90D. The output of IC90D goes to '0'. C92 now discharges into the output of IC81D via R95 and interboard wire 'J'. The time constant of C92 and R95 is approximately 300ms which ensures that the 'master reset bus' remains at '1' long enough to completely clear the charge on C91. In effect, C92 and R95 develop a 300ms 'validation reset' pulse from the output of IC90D. Once the 'master reset bus'

returns to '0' the alarm channels are re-activated and will continue to monitor the status of the field sensors.

If the original alarm is still present or if another channel is detecting an alarm when the 'validation reset' pulse is generated, then after the 300ms delay, provided by C92 and R95, has elapsed and the 'master reset bus' has returned to '0', the alarm channel will immediately lock into alarm status. This will pull down the 'delayed alarm bus' to '0' which returns the output of IC81A to '1'. As C90 has only been discharging through D90, R90 and R91 for 300ms as mentioned above, the time constant of R90, R91 and C90 is one second. Therefore, if an alarm is sensed the moment the 'validation reset' pulse ends, C90 will not have had sufficient time to discharge to '0' and silence the siren. The effect of this is that the siren will continue to sound until the source of the alarm is cleared and the 'validation reset' pulse resets the system or until the system is manually reset. The 'validation reset' timer will continuously attempt to reset the system approximately once every minute for as long as the siren continues to run.

As mentioned above, once the 'entry delay' has been initiated, the only way to prevent the siren from going off at the end of the 'entry delay' is to manually defeat the system via S80. Once the siren begins to sound it can also be silenced by manually defeating the system. For the purpose of discussion, let us assume that the system has been activated for some time and you have just entered the premises. The moment you enter the premises the alarm channel which monitors the door you just entered will latch into alarm status and pull down the 'delayed alarm bus' to '0'.

MANUAL REST

If the 'system defeat' switch, S80, is depressed, the following takes place. A '1' is applied to the 'inhibit bus' which disables the 4Hz multivibrator and applies a reset signal to the 'operational' flip-flop (IC80C and IC80D). The 'operational' flip-flop is reset to a stable state with a '1' at the output of IC80C and a '0' at the output of IC80D. The '0' at the output of IC80D dumps any charge that was developed across C90 via D91 and interboard wire 'k'. This pre-empts the 'entry delay' and prevents the siren from sounding by locking the output of IC90B to '1'. The '0' at the output of IC80D also dumps the charge on C83 via D84 and presents a '0' to pin 8 of IC81D. The '1' on the 'inhibit bus' charges C81 via D83 and presents a '1' to pin 1 of IC81B ensuring that its output remains at '0'. The output of IC81C will remain '0'. This results in both inputs of IC81D having '0' conditions. The output of IC81D will now go to '1' which forces the 'reset bus' to '1' via interboard wire 'J'. This '1' resets all alarm latch flip-flops to their 'safe' condition. At this point the entire system is in a power down mode and will ignore the status of all alarm inputs. The only loads on the mains supply will be the charging of the nickel-cadmium batteries and the illumination of the 'power on' i.e.d. The maximum load on the batteries in the event of mains failure will be the negligible 10 microamperes required by the logic.

In summary, placing S80 in the defeat position instantaneously pre-empts any activity in progress, resets all timers, and forces the system into a quiescent state with negligible current demands. The only loads present are placed on the mains supply; should the mains be lost in this mode the system will draw negligible current from the batteries.

NEXT MONTH: CONSTRUCTION

THIS WAY YOUR ELECTROVALUE CATALOGUE IS ALWAYS UP TO DATE



EVERY THREE MONTHS WE PUBLISH AN UP TO DATE PRICE LIST FOR USE WITH OUR CURRENT CATALOGUE. THESE ARE MAILED FREE VIA OUR COMPUTER TO REGULAR CUSTOMERS. IF YOU WOULD LIKE A FREE COPY JUST WRITE OR PHONE. ALSO FOR CURRENT 120 PAGE CATALOGUE FREE IF YOU SO WISH.

OUR MINI-SELECTION POINTS THE WAY! EXAMPLE ONE — SOLDERING IRONS

Oryx 50	£12.08 net	Antex X25	£4.83 net
Isotip	£25.90 net	Desolder tool SR3A	£7.48 net
Antex C	£4.83 net	500 gm reel solder	£7.59 net

EXAMPLE TWO — PRINTED CIRCUIT MATERIALS

PCB's 300 x 150 mm		Etch Resist Pen	£1.21
SRBP S/S £1.38	D/S £1.73	Breadboards	
F/Glass S/S £2.19	D/S £2.48	Bimboard 12	£9.23
Positive resist 75cc	£1.67	Eurobreadboard	£5.56 net
Ferric Chloride 500g	£3.45	T-DeC	£5.18

EXAMPLE THREE — SWITCHES

Chrome toggle		13A time switch adaptors	
Std. SPST 65p	DPDT 89p	Smiths TS 100	£14.43 net
Min. SPDT 66p	DPDT 92p	Wavechange Lorlin, 1P12W, 2P6W,	
		3P4W, 4P3W	48p each

EXAMPLE FOUR — CAPACITORS BY SIEMENS

Polyester 7.5mm PCM
1, 1.5, 2.2, 3.3, 4.7nF, 10, 15, 22, 33, 47nF 8p each, 0.1u 12p, 0.15u 14p, 0.22u 18p, 0.33u 21p, 0.47u 27p, 0.68u 34p, 10mm PCM 1u 37p.
Electrolytic, axial, (uF/V)
1/40 15p, 1/100 12p, 2.2/25 15p, 2.2/63 12p, 4.7/16 15p, 4.7/40 12p, 10/25 12p, 10/40 13p, 22/25 13p, 22/40 13p, 22/63 19p, 47/10 13p, 47/25 16p, 47/40 19p, 47/63 20p, up to 1000/16V 32p, then 1000/25V 44p, etc.
Also full supporting ranges of other ceramic, plastic and electrolytic caps.

EXAMPLE FIVE — POTENTIOMETERS BY RADIOHM

Single gang lin or log	34p	(Twin types stereo matched)	
Twin gang lin or log	93p	Slider knobs	10p each
Mono slider lin or log	83p	Presets lin, horiz. or vert.	12p
Twin slider lin or log	136p		

EXAMPLE SIX — RESISTORS

1/4, 1/2, 1W 2.3p 1W 6p
Wirewound from 23p

WE ARE STOCKISTS
FOR I.L.P.
TOROIDAL TRANSFORMERS

THIS LIST IS BUT A FRACTION
OF WHAT WE CARRY

1N914	6p	40362	75p	8B103	43p	MPSA63	44p	TIP3055	69p
1N4007	9p	40638	£1.69	8B104	70p	OA47	14p	TIS43	40p
1N4148	5p	40673	99p	8B105	37p	OA90	8p	W02	35p
1N5402	19p	555	34p	C106D1	46p	OC29	16p	ZN425E	£4.49
2N1599	£1.01	556	58p	CA140E	46p	OC29	£1.23	ZTX107-9	14p
2N2389A	24p	AC128	36p	E1110	92p	OC36	£1.18	ZTX300	14p
2N3055	81p	AC176	67p	E1210	92p	T2800D	£1.20	ZTX500	16p
2N3702	11p	AD136	£4.25	LM301AN	35p	TIP31A	52p		
2N4443	£1.78	AD149	£1.01	LM324N	87p	TIP32A	52p		
2N4444	£2.28	AD161	40p	LM380N	£1.14	TIP41A	69p		
2N4991	72p	AD162	52p	LM3900N	78p	TIP41C	74p		
2N6457.9	45p	AF127	43p	MJE2955	£1.38	TIP42A	69p		
40HF40	£2.25	AL102	£1.84	MJE3055	£1.20	TIP42C	74p		
40361	49p	BA379	29p	MPSA12	42p	TIP2955	69p		

INFORMATION — To show everything we supply would take about seven pages of closely packed type in this journal — the range is enormous, including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! ITS ALL IN CATALOGUE 10 — OUR 120 PAGE CATALOGUE FREE FOR THE ASKING.

PRICES AND V.A.T. — All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

POSTAGE — For orders up to £5.75 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

DISCOUNTS — 5% allowed on non-net items if order value exceeds £11.50, 10% if order value exceeds £29. Quantity discount prices on most components.


ELECTROVALUE LTD. DEPT. PE/10, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 (STD 0784, London 87). Telex 264475 Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA Phone (061) 432 4945.

SPECIAL PURCHASE



OF TOP QUALITY LCD MULTIMETERS

AC/DC
CURRENT
22
RANGES

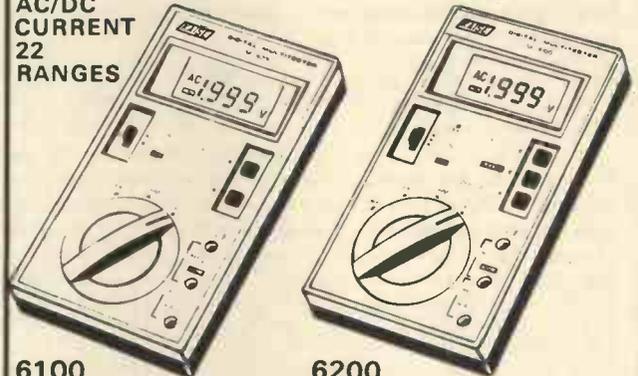

6100

6200

CHOOSE FROM FOUR MODELS

- 3½ digit autoranging (volts/Ohms)
- 200 hours battery life (2 pencils)
- 10 amp AC/DC (6220 & 6100)
- 1000v DC 600v AC
- 200 mA AC/DC (6200 & 6100)
- Range hold facility (6100 & 6110)
- Unit and range sign (6110 & 6220)
- Continuity buzzer (6100 & 6110)

RESOLUTION

100 uVDC, 1 mVAC
10 uA AC/DC, 0.1 Ohm
10 mA on 10A AC/DC

ACCURACY 6100/6110

0.5% DC Volts
1% DC Current
1.2% AC Current
0.5% Resistance

OTHER FEATURES (ALL MODELS)

Low power Ohms range.
Zero Adjust key.
Battery Warning.

6200/6220

0.8% DC Volts
1.3% DC Current
1.4% AC Current
0.8% Resistance

In circuit resistance test.

Size 155 x 85 x 28 mm. 250 g.

6200 **£39.95**

6220 **£49.95**

- All prices include batteries/leads and UK VAT (UK c/p 65p)

6100 **£64.95**

- Order by post or telephone with Barclay or Access.

6110 **£74.95**

OR CALL IN AND SEE FOR YOURSELF

Prices correct at 1/10/80 E&OE

Cubegate Limited OPEN 9-6 SIX DAYS A WEEK

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON, W2 1BN

TELEPHONE 01 724 3564



FREE CATALOGUE!
Send large SAE (175p UK) Schools, Companies, etc. free on request.

From Mr/Mrs/Miss (Block caps please)..... Ref P.E.
Address

Please supply Qty Model(s)

I/We enclose (incl. 65p post)

Chq/PO Value

Or debit Barclay/Access No.

Semiconductor UPDATE...

FEATURING HNVM3008 MM58174 TLO11

R. W. Coles

EPROM CHALLENGE

When microprocessor programs have been developed and debugged in RAM, they can then be stored on cassettes or floppy discs for reloading when required, but many systems cannot afford the delay or the expense associated with "backing stores" of this type, and so for them, the speed and simplicity of ROM based software is required.

Read Only Memories come in all shapes and sizes, but the simplest and cheapest, the masked ROM, suffers from the serious disadvantage that the data is programmed in during the manufacturing process, and is thereafter immutable. This type of ROM is OK for software which is tried and tested and for distribution to a large market, but for the one-offs or ten-offs, or for microprocessor software which may still contain elusive "bugs", a less final method of inscribing the stored instructions is required.

Until recently, the most acceptable compromise between tapes and masked ROMs has been the EPROM (Erasable, Programmable, Read Only Memory). Those devices have appeared in three "generations" typified by the 1702A, 2708, and 2716 devices from Intel, with the latest devices being much easier to use and program than their predecessors. Despite the improvements made in recent years, however, the EPROM is still a difficult beast to handle. To erase the stored data, the chip itself must be exposed to dangerous, short wave, Ultra Violet light of high intensity for periods of up to one hour. To programme a single location, a voltage source of 25V or more must be available, and a programme pulse lasting 50 milliseconds must be applied. This means a 2Kx8 2716 device takes about two minutes to program, slow by RAM standards. (To write the same quantity of data into a RAM array would take less than one millisecond.)

Despite these disadvantages, the EPROM is extremely popular and available from numerous manufacturers, but things may start to change now that a new device, the EEPROM is becoming available. The extra "E" stands for "Electrically" making the new chips Electrically Erasable, Programmable, Read Only Memories. The new technology is a strong candidate to eventually replace the EPROM in most, if not all, of its present applications, and consequently, the race is now on to produce the most successful EEPROM in the hope of fostering the next "Industry Standard."

One notable example of the new technology has recently been introduced by Hughes in the form of the HNVM3008 which is a 1Kx8 replacement for the popular 2708. The catalogue of desirable features

is extensive. Erasure takes not tens of minutes under a UV lamp, but only 100 microseconds and the application of a 17 volt supply in place of the operating supply of 5 volts. Programming is just as easy, requiring the same supply voltage as erase and only 100 microseconds per byte, rather than the 25 volts and 50 milliseconds of the EPROM. The sophisticated HNVM3008 chip uses a mixture of CMOS and NMOS circuitry to gain the very low power consumption of 10 milliwatts (operational) and 25 milliwatts (during programming).

To sweep the field completely, the new EEPROMs must come down in price and go up in capacity, but already they represent a serious challenge to the traditional dominance of the EPROM.

IF YOU WANT TO KNOW THE TIME . . .

Ask an MM58174 from National Semiconductor.

If you happen to be a microprocessor, you now have another cheap simple way to tell the time of day and the date. Much better than those awful delay loops which kept you hanging around all day just decrementing a register and whizzing round a silly loop without a minute to yourself to do anything really useful. That programmer deserved to be shot, treating you just like so much clockwork and wasting all those sophisticated resources tucked away in your logic arrays on nothing more than the creation of a clock. It's enough to make you trade in your crystal for a CR timing network! Mind you, it wasn't much better when he discovered interrupts, was it.

Every ten milliseconds. Wham! off you had to go to that sneaky interrupt routine, incrementing and decrementing counters when you had just settled down to some really serious number crunching. And what a bother, zooming around saving your registers to stop that clock routine getting its grubby hands on them, and then all the fuss of getting them all back off the stack so that you could get on with the real job. And how about that awful wet Sunday when he decided to play about with the stack pointer to have data around. Along came that fateful interrupt, and off you went to the clock routine as usual, but when you executed the RETI instruction and tried to POP the return address into your Program Counter, all you got was a branch into the look-up table. It's a wonder you ever got out alive! All he has to do is look at his watch when he wants to know the time—he doesn't have to spend all day counting the seconds, and no one comes along and kicks him up the backside every minute so that he can cross it

off on his time sheet either. No, fellow microprocessors; it is high time that we of the thinking classes were treated with a little more respect, and provided with a proper timepiece, such as the MM58174.

The new device, a programmable real-time clock, should make micros everywhere very happy. It's completely self-contained, it will keep good time even when your micro is switched off for the night, and it is completely independent of the microprocessor while time keeping. Inside the chip, there are twelve count registers, toggling at rates between tenths of a second and tens of months, fed from a crystal timebase of 32.768 KHz. Talking to the clock is easy for the average microprocessor, each of the registers can be read via a four bit data bus so that information on the time of day, day of week, and date is available within a few microseconds. The micro stays boss too. Each of the count registers can be preset via the data bus after a valid address has been set out on the address bus to select it. The device is housed in a 16 pin DIL package, and will operate on less than 10 microamps when the supply voltage is reduced to 2.2V from the normal operating level of 5V.

For those programmers who still insist on interrupts, the MM58174 has an output which can be programmed to generate an interrupt at half second, five second, or one minute intervals, either continuously or on a one-off basis.

ON REFLECTION

A new solution, looking for problems to solve, has arrived from Texas Instruments in the form of a family of Wilson Current Mirrors. Up to now, current mirrors have only existed inside complex analogue integrated circuits where the tight matching of transistors on the same chip made them a possibility for the first time. Texas have decided that it's a shame not to let this useful circuit configuration see the light of day, and so they have produced a family of devices which are true three terminal mirrors, as used in all the best ICs!

They aren't too sure what you are going to do with them yet, they have even started a competition for the best application idea, but to help you on your way, let me say that the one thing the mirror is very good at is generating constant currents. The new devices all provide a constant current output proportional to a reference current input and independent of output voltage or temperature changes. The TLO11 has a fixed input/output current ratio of 1:1, the TLO12 1:2, the TLO14 1:4, and the TLO21 2:1. They'll work with reference currents of up to 1 milliamp (2 for the TLO21) and they come in small three pin transistor packages.

MICRO PROMPT

The hardware and software exchange point for PE computer projects

M/C FOR TELEWRITING

Another method for direct telewriting on the UK101 has been submitted by T. Wilson of Sittingbourne, Kent.

First set up in BASIC by pressing C and limiting the memory size.

10 POKE 11, 00 : POKE 12, 5
20 X=USR (X) : P=PEEK (1536)
30 PRINT CHR\$ (P) ; : GOTO 20

Then enter machine code by restarting and pressing M. Type in the following:

```
0500 20 00 FD      JSR FD00
0503 8D 00 06      STA 0600
0506 60            RTS
```

Using Warm Start you may now type out all the standard characters, and more, by using CTRL plus a key. Use return and LF to start a new line, and CTRL/C to exit.

CLEAR OFF

SIR—The manual supplied with UK101 kit includes a short machine code routine for clearing the VDU screen. The following routine is shorter, and arranged for the specific task for clearing screen. The manual version is a more general routine for loading any section of memory of any length with a specified data byte.

```
nhhh A9 20      LDA #20
A0 00      LDY #000
99 00 D0    STA $D000, Y 'fill'
99 00 D1    STA $D100, Y
99 00 D2    STA $D200, Y
99 00 D3    STA $D300, Y
C8        INY
D0 F1      BNE 'fill'
```

Michael Wood,
Wakefield.

DREADFUL!

Sir—I am delighted to see that you are devoting space to supporting the UK101, which you published as a series of articles last year.

There is a need for a good system of data storage for this machine. The SAVE routines published are all very well but they lack sophistication and the other essential—simplicity!

If one compares a true SAVE operation on other computers, one can only describe these genuine attempts at a solution as a dreadful way to have to carry on, and with only limited commands.

We had mini-floppies, there is a Philips digital cassette recorder, and now the stringy-floppy.

How about an article/series on how to add on one of these to the UK101? For people like me this would preferably be available as a ready-constructed add-on as an alternative to a kit, which would appeal to many readers.

Allan Batch,
Rugby.

EDITOR'S MAILBAG

Sir—Congratulations to Mr. Climpson for the very useful screen editor published in July's Micro Prompt. It gets rid of the cursor on Superboard after CONTROL Ø too, which is quite an achievement!

It had been pointed out that in the list of page zero addresses given by Mr. Hocking in his save-variables program location 0088 is, in fact, the high byte of the current BASIC line number in use and locations 008B, C are the GOSUB pointer.

E. J. Keeley,
National Personal
Computer Users
Association.

Sir—I have found the Editor program (by Nigel Climpson, in July PE) most interesting and useful, and I wish to thank you for not forgetting the Superboard owners. I have made the following addition to the program to cause it to limit the memory automatically for my 8K machine without the need for remembering the memory size; 50001 POKE 133,184: POKE 134, 30 For a 4K machine the line would be: 50001 POKE 133,184: POKE 134, 14

When saving the program on tape I carried out the following routine:

1. Type SAVE (Return) LIST
2. Start recording (Return)
3. When program is completely SAVED do not stop the recorder, but instead slowly type RUN (Return)
4. When OK appears press return as required to activate the program and then use the Editor itself to copy line 50074, altering the line number to 50000.
5. Type LIST (Return), which gives an assurance that only the new line 50000 exists.
6. Stop tape recorder.

To load the program from tape it is only necessary to play back the whole tape. The program is loaded and run, the line is copied and the editor is ready for use. Various error signals are given but all is well as long as the new line appears three times. To activate the editor after a warm start type RUN50000 (Return).

The reason for typing RUN slowly when recording is to give time on playback to stop loading if it is desired to delete line 50076 before use.

For my Superboard I have found that byte 1F65 should be 1C (or 28 decimal in line 50040) to allow the cursor to reach all lines on my screen, and eight Control D's are required to avoid blanks when a line is carried over.

I send you the above information in the hope that most of it is applicable to the UK101 or can easily be adapted for it.

F. S. Dewhurst,
Keighley.

RAMLESS MESSAGES

Sometimes it can be helpful to print messages on tape before a LISTING to give information that does not need to be put into RAM, particularly if a lot of RAM is being used for variables and strings. The problem is that a straight:

PRINT "THIS IS A MESSAGE"

in SAVE mode will be recorded and played back, but there will be an accompanying Syntax Error message which looks tatty. The answer is to start the message with a colon.

PRINT ":"THIS IS A MESSAGE"

will play back without a syntax error and will not load into RAM. This means that when the program has been fully developed it can be recorded with additional comments by adding a routine on the lines of the following:

50000 SAVE:?:?:?: THIS IS A
MESSAGE ABOUT THE PROGRAM"
50010?:?: WRITTEN JULY 1980"
etc.

50090 LIST—49999
the program is SAVED by RUN 50000

The resulting recording will contain the message but not lines 50000 onwards. The colon is also useful for improving the appearance of LISTING, as it can be used instead of REM to produce a blank line for spacing.

A further elegance can be added by getting the Compukit to print "RUN" instead of "OK" at the end of the listing, thus giving you a self running tape. The OK message is printed by a JMP \$A8C3 in locations 3,4,5 of the memory. As has been pointed out in the First Book Of Osi, changing the \$4C to \$60 in location 3 disables the OK, but if instead you put in a jump to your own message routine it will print anything you like. The ROM message printer prints a message which starts at an address loaded into its Y (hi byte) and X (lo byte) registers; the message being terminated by a NULL. Thus, in the routine shown it prints (CR) (LF) RUN (CR) (LF). It is activated by POKE 4,40:POKE 5,2 and will stay activated until COLD start or further POKES.

Any message is possible provided it is terminated by a Null.

```
0228 AO O2      LDY@02; Load
                  address of message
                  (Hi)
022A A9 2F      LDX@2F ; Load
                  address of message (Lo)
022C 4C C3 A8   JMP $A8C3 ; Message
                  printer from loc. 3,4,5,
022F            .BYTE 13,10, 'RUN',
                  13,10,0
022F OD
0230 OA
0231 52
0232 55
0233 4E
0234 OD
0235 OA
0236 OO
```

Roger Derry,
London.

SHIFTY CHARACTERS—2

Sir—Oh dear, nearly a whole column wasted with a table of characters of the keyboard of the 101—a table one can so easily find for oneself by playing with the machine. And, Mr. Schofield has missed the whole point of the Shift Lock. Press it, and all the lower case letters (including k) are available where the upper case used to be. That is the reason, presumably, why the normal position of the Shift Lock is down, as it works in the same mode as a standard typewriter keyboard. Viz. up for lower case and down for upper case. Note also that when it is up, the Shift keys are still operative, so that if you wish to mix l.c. and u.c. (and you probably do!) then your strings are entered exactly as on a typewriter. Care is necessary with digits and punctuation, however.

What I would like to know is what CTRL.O does to disable the keyboard (except for Return) if tapped once. Tapping twice (or holding down) will produce the "large house." CTRL.M gives Return. What, if anything, do other control characters do?

May I conclude by saying how I enjoy reading your magazine. I would like to see some circuits which will enable the 101, the Edukit and similar machines to interface with the real world of temperature sensors, infra-red detectors, electric door locks and so on. As a teacher of Computer Studies it is more important to show pupils how the electronics can move mountains rather than win at games.

G. R. Morris, B.Sc.,
Cheshunt, Herts.

Oh dear, don't blame Mr. Schofield, we foreshortened his original material.

CONVERSION—POKE SOMEWHERE?

Sir—I have followed your series of articles on the COMPUKIT UK101 with great interest as several months ago I purchased an Ohio Superboard—unfortunately just before your series. However, undaunted I set about modifying my Superboard to become a UK 101.

I've now got the machine operating via a sub-board on 50Hz. The sub-board runs on a 8MHz clock and plugs into the original counter chain's i.c. sockets. The other aim was to get 48 characters per line instead of the difficult to read 24.

The problem is that there is something in the firmware that tells each line to only be 24 characters wide, because I now have viz:

Line 1 Line 2
Line 3 Line 4
Line 5 Line 6
etc.

With the help of our Digital Engineer at the T.V. station where I work I've PEEKed and POKEd but without success.

If I purchased the UK 101 Monitor ROM and/or the BASIC ROM(s) would this cure the problem? Or can I POKE somewhere.

B.F. Bailey,
N.S.W., Australia.

INT AINT ACCURACY

The following is an extract from a letter from Mr. J. Plews of Sheffield:

"If I combine the truncated integer function with an exponential expression, I begin to get problems where accuracy is vital. eg:

```
PRINT INT(10/(2 ↑ 1))
```

The 101 comes back with 4"

Is there any way of solving this problem by fooling the system etc? Has anyone else encountered this obstacle? Is there any chance of a new interpreter?

I would be interested in your response to this letter.

Help! Actually, if you run your example without INT you may find that the 101 is returning 4.99999 etc. Although the result may be as close as a gnat's whisker to the correct figure, you will automatically be ditching this accuracy for the next lowest integer when you implement INT. Any machine would do it! Presumably you don't want all those decimal places.

Try:

```
10 INPUT N  
20 PRINT INT(N*10/(2 ↑ 1))/10
```

If N=10 this should return 4.9... a little closer!

Dr. BERK'S UPDATE

Sir—As you requested in your article in Practical Electronics, March 1980, I would like to let you know that I have carried out your suggested modification to run a 110 baud teletype from the 101 and all the evidence to date would indicate that it is very successful indeed.

I have made the modification switchable, the teletype being a fairly new Olivetti T.E.300.

Thank you for your most useful and informative articles; I look forward to more of them.

J.R. Haldene,
Midlothian.

NEW ROOM ERROR

Sir—I have unearthed a simple error on the instruction card that accompanies the new UK101 monitor, that nonetheless can cause a lot of difficulty.

The instruction card gives a helpful list of vector addresses and subroutines entries, with Hex and Decimal versions of the addresses. Using these I couldn't get BASIC to set (POKE) my NMI vector and thus couldn't get my data collecting interrupt routine to run during BASIC programs. (All was OK so long as I stuck to machine code in the Monitor.) Although it took quite a while to find, the answer was simple—I had replied on the Decimal addresses on the instruction card, but some of them are wrong. The printed list goes wrong at 021A Hex, listed erroneously as 540, should be 538. Thus NMI vector should go in Decimal 547 and 548 (an IRQ in 550 and 551) and not as printed on the card. The Hex addresses given on the card seem to be perfectly correct. The monitor seems to function well in every respect.

N. Blurton Jones,
University of London.

ARRAY OR DISARRAY?

Sir—I write with reference to a point raised in your March issue, within "Microprompt". The point to which I refer is: ?FRE(N) after running part, or whole of a program containing a DIM statement for a string variable array. e.g. DIMAS(10).

The way to avoid the UK101 "locking up" is to type: CLEAR: ?FRE(N).

This clears all variables and arrays. It does of course prevent you from finding out how much memory is occupied by variables or arrays used.

As a matter of interest, numerical values occupy 6 bytes. Within an array they occupy only 4 bytes, plus an overhead for the whole array, which is dependant upon whether it is 1-, 2-, or 3-dimensional. The overheads for 1-, 2-, and 3-dimensional arrays are 13, 21 and 29 bytes respectively. For example, an array dimensioned with DIMX(9,9) will hold $10 \times 10 = 100$ variables. It would therefore occupy 100×4 plus the overhead of 21 = 421 bytes.

This is true when some values have been assigned to all dimensions. An empty array overhead is 6 bytes less per dimension. For instance, the same array X, above, would have an overhead of only $21 - 12 = 9$ bytes whilst empty, or $21 - 6 = 15$ bytes with one dimension empty. (Why some one should dimension an array and leave it empty I don't know!)

Each string variable occupies the same number of bytes as characters it contains with an overhead of 6 bytes. How much room a string variable array occupies I do not yet know!

I hope this is of some interest. Finally, I would like "Microprompt" to be larger and in every issue. Certainly not Bi-monthly!

E. Cottam,
Par, Cornwall.

GETTING INTO PRINT PROBLEM

Sir—A short while ago I bought a second-hand Data Dynamics 390 ASCII printer. In spite of the fact that I was assured by the vendor that it was easy to link up to my UK101 (new MONITOR), I have been unable to find out how to do so. The only information that I have is that the printer requires an eleven bit word (one start bit, two stop bits, eight data bits) and that it has a current loop input and works at 110 Baud.

If any of your readers can help me to get the printer working, I should be most grateful.

Alan E. Wilmshurst,
Crowborough,
E. Sussex.

It should be emphasised that material presented in Prompt has not necessarily been proven by us. Neither can compatibility with all generations of the computer equipment to which it relates be guaranteed.

Software and hardware designs submitted should be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

BASIC LINE RENUMBER

This program will renumber a UK101 BASIC program, or part of a program up or down. It will not, however, alter GOTO or GOSUB line numbers. The program can be loaded at any time when programming, and is brought into operation by typing RUN 20000. It is useful to use to "space out" part of a program to allow extra lines to be inserted. To understand the operation of the program, the workings of the BASIC interpreter, in particular, how it stores data in RAM, needs explaining.

```
20000 REM*** LINE RENUMBERER FOR UK101 *****
20010 REM*** I. PAWSON FEBRUARY 1980 *****
20020 INPUT"RENUMBER OLD LINES FROM":X
20030 INPUT"THROUGH TO":Y
20040 IFX=YTHEN20020
20050 INPUT"AS NEW LINE NUMBERS FROM":Z
20060 INPUT"IN STEPS OF":P
20070 B=256
20080 DIMN(100,2)
20090 N(1,1)=769
20100 FORT=1T0100
20110 A=N(1,1)
20120 N(T,1,1)=PEEK(A+1)+B*PEEK(A)
20130 N(T,2)=PEEK(A+3)+B*PEEK(A+2)
20140 PRINTN(T,2)N(T,1)
20150 IFN(T,2)=YTHEN20170
20160 NEXT
20170 FORT=1T0100
20180 A=N(T,1)+2
20190 IFN(T,2)(XTHEN20240
20200 POKEA,2-INT(Z/B)+B
20210 POKEA+1,INT(Z/B)
20220 Z=Z+P
20230 IFN(T,2)=YTHEN20250
20240 NEXT
20250 PRINT:PRINT
20260 PRINT"RENUMBERING COMPLETED"
20270 REM*** END OF PROGRAM *****
```

As the program is in BASIC, all numbers are in decimal. The data is stored from address 769 onwards; the first two locations are the address of the start of the next line. The format is that the second location contents are multiplied by 256 and added to the contents of the first location. The following two locations contain the line number, in the same format as the address. The contents of the line follow, terminated by a 0. The commands, GOTO, GOSUB are stored as a single number, 136 and 140. The line number following is stored in ASCII format, ie 100 as 49 48 48, 200 as 50 48 48 and so on. The main problem, in adapting the program to renumber GOTO's and GOSUB's would be if the new line number had more or less digits than the previous one. This program is presented as a starting point for a complete renumberer, and I should be interested in readers' comments. Line 20140 can be omitted if a print-out is not required.

I. Pawson, Leicester

PEVDU KEMITRON STYLE

Because the Thompson-CSF CRTS chip is really intended for use in serial or "glass teletype" terminals, and is therefore equipped with its own rather slow cursor control system, problems can arise when attempting to use the PE VDU to best advantage as a memory-mapped VDU. As is mentioned briefly in part 3 of the PE VDU article, if a monitor program which generates its own cursor in software is to be used, the cursor control lines C₀C₁C₂ are best permanently set to 0, and an initial pulse applied to the ST line (Fig. 4, part 3). This can be easily achieved if the ST line is wired to the reset circuit of the MPU. However, this is not the whole story. We

are now left with a flashing character and cursor line at the top left-hand corner of the screen. The cursor line is generated by the CRTS disabling the character generator at the appropriate time, and therefore this can be removed by breaking the track joining pin 15 of the CRTS to pin 11 of the 2513, and permanently grounding the latter.

This leaves the 2513 permanently enabled. To avoid the flashing character in the top left hand corner, the output routines in the interpreter or monitor used can be arranged to ignore completely the extreme left-hand column of the screen, while the clear-screen routine must of course include this column. This is the system adopted in the Kemitron NIBL-MM-memory mapped BASIC interpreter for the SC/MP, one version of which is specially configured to work with the PE VDU—though the principles described above could of course be incorporated in any interpreter or monitor program for any processor.

Details of the Kemitron system can be obtained from Greenbank Electronics, or the Chester Computing Centre, 21-23 Charles Street, Chester.

JUST A LITTLE SOMETHING . . .

```
100 REM*** 8 DIGIT BINARY TO
    DECIMAL CONVERT ***
110 REM*** I. PAWSON DEC
    1979 *****
120 PRINT:PRINT
130 INPUT "INPUT 8 BIT
    BINARY NUMBER"; AS
140 IFLEN(AS) <> 8 THEN 100
150 B=0
160 FORX=1 TO 8
170 YS=MIDS(AS,X,1)
180 READA
190 C=VAL(YS)
200 B=B+(A*X)
210 NEXT
220 PRINT
230 PRINT "THE DECIMAL VALUE
    IS"; B
240 RESTORE
250 PRINT
260 GOTO130
270 DATA128, 64, 32, 16, 8, 4, 2, 1
280 REM*** END OF PROGRAM
    *****
```

LINE LENGTH HINTS

Sir—T. D. Allen of Poole wants to display 64 characters per line on his TV from a UK101. He has a problem! The suggestions that he makes are all based on software but the problem is mainly in the hardware.

As far as the software is concerned, changes must be made to a ROM in program locations FFE0 and FFE1, cursor starting point and line length respectively.

The main problem is physically displaying the characters. The VDU RAM is scanned as 16 lines of 64 characters with TV horizontal sync pulses added at the end of every line. As everybody knows, a few characters are not displayed at each end of

the line. What is not often said is that more characters are lost during the fly-back of the TV trace and these can never be displayed.

The write-up in the UK101 book about VDU operation explains that clock pulse C7 is not used and the result is that every row of dots is displayed twice. The logical conclusion is that using C7 instead of C6 to generate the horizontal sync should give a line twice as long with the 2 rows of dots side-by-side instead of one on top of the other. Putting the right values into FFE0 and FFE1 (try BF and 3F) should then enable a complete set of 64 locations to be displayed, assuming that you can adjust and/or modify the TV as necessary. Display on a normally adjusted TV would not be possible.

You will have gathered that I have not tried this and there may well be problems, although the theory sounds good. It should at least give food for thought.

R. L. Taylor,
Shepperton,
Middlesex.


PSG BUG

We received correspondence from Mr. Gossage of Harrow, Middlesex, pointing out an error in the address decoding of the PSG:

"It is stated that the Hex address used is F0F0. On the UK101 the whole 256 word block from F000 to F0FF is used as the ACIA location—the two addresses are repeated throughout the page and so cannot be used by the PSG. Secondly, however, the circuit given will not show only at F0F0 but appear at many addresses from 00C0 upwards. Inspection reveals that IC1 is not acting as an 8 input NAND gate but as a 4-wide 2-input NAND OR gate—the output going low when any pair of inputs go high."

"The circuit will apparently work since it is, in effect, 'write only memory' and so although it appears at many memory locations it will not interfere with the micros use of the RAM."

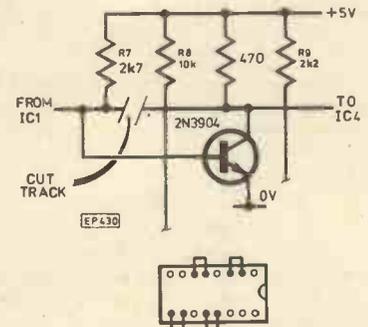The author, Mr. D. Couatts, has provided a fix for this, and apologises for the error: Change IC1 to 74LS09 (same pin-outs), and add 2N3904 transistor and 470Ω resistor as shown below. This gives the PSG one address



only, and requires minimal interference to the p.c.b. Our correction to Fig. 8, is included too. Also, Mr. Gossage suggests transposing address lines A7 and A8 to place the PSG at F170 and F171—away from the ACIA.

RESIDENT EDITOR

BY NIGEL CLIMPSON

MOST owners of microcomputers would be pleased if, for minimal hardware changes, they could provide themselves with an extra 1000 or so bytes of ROM storage. Into these 1000 bytes could be placed favourite machine code programs or perhaps some system software to extend the capabilities of their machines. These programs would of course be available from switch-on and be permanently stored.

This can be done for the UK101, but of course there is a snag. You will have to obtain a single supply 2716 EPROM and find some means of programming it.

The secret of this miraculous amount of available space lies in the Monitor ROM. Examination of the contents of the ROM discloses that it contains two almost identical sections at addresses in the ROM of 000-3FF and 400-7FF where 000 is located in the machine's memory map at F800. The major differences in the two sections are that some of the jumps are to different addresses, and that one of the sections contains a routine to clear 2K of video memory as against 1K in the other.

The UK101 only uses one of these two sections and I suspect that this comes about due to the machine's OSI heritage.

The point of all this is that we can dispose of the contents of the ROM from 000-3FF and the UK101 still works quite happily. It should be possible to gain a bit more space if you don't have a disc drive by removing part of the floppy bootstrap which runs from 400-4D4, but beware because some of the subroutines in this section are called from other areas of the Monitor.

```
990 98 48 AC F9 92 AD F8 02 91 F9 88 CE F9 92 20 3B
910 F9 68 AB A9 00 60 4C 00 F8 98 48 20 45 F9 AC F9
020 02 A9 23 91 F9 EE F9 92 D0 02 E6 FA C8 20 3B F9
930 68 AB A9 00 60 CA 10 04 EB 4C 99 A3 8A 48 98 48
940 AC F9 02 AE 00 92 AD FA 92 F0 05 AD F8 02 91 F9
950 A9 20 9D 00 D3 CA 88 CE F9 92 CE 00 02 A9 9A 9D
960 00 D3 CE F6 92 AD FA 92 F0 03 2B F9 68 AB 68
970 AA A9 00 60 20 BA FF C9 15 F0 1A C9 1C F0 36 C9
980 04 F0 96 C9 02 F0 8F C9 96 F0 6F C9 0D F0 50 20
990 1D F9 4C 99 A3 38 98 48 AD FA 02 F0 08 AC F9 92
9A0 AD F8 02 91 F9 EE FA 92 AD FA 92 C9 10 F0 1F C9
9B0 01 D0 96 AD 90 02 8D F9 92 AD F9 92 E9 40 30 02
9C0 C6 FA 8D F9 02 A8 20 3B F9 68 AB A9 00 60 A9 03
9D0 8D FA 02 A9 D3 E5 FA AD 00 02 8D F9 92 D0 E6 A9
9E0 00 8D FA 92 85 F9 A9 D3 E5 FA A9 20 8D F8 92 A9
9F0 CD 8D F6 92 8D F9 92 A9 9D 60 98 48 20 45 F9 AD
100 F8 92 AC F9 92 91 F9 8D F7 92 C8 EE F9 92 D0 02
110 E6 FA 20 3B F9 68 AB AD F7 92 4C 99 A3 48 AD 00
120 02 CD F6 92 10 9D 38 AD F9 92 E9 40 30 02 C6 FA
130 8D F9 92 AD 00 92 8D F6 92 68 60 31 F9 8D F8 02
140 A9 9A 91 F9 60 A9 48 C5 0F D0 08 AD F9 92 E9 30
150 4C 58 F9 AD F9 02 E5 0F C9 0C F0 10 C9 4C F0 0C
160 C9 8C F0 98 C9 CC F0 04 20 1D F9 60 48 AC F9 02
170 A9 20 91 F9 68 18 69 40 90 02 E6 FA 8D F9 02 20
180 1D F9 60 A9 00 85 E1 AB A9 D9 85 E2 A9 20 91 E1
190 C8 C0 00 D0 F9 A6 E2 E0 D3 F0 06 E8 86 E2 18 90
1A0 ED 60 AD 06 FA 88 90 05 CE F5 02 F0 09 CA D3 F5
1B0 AE FA 92 4C A2 F9 60 FF FF FF FF FF FF FF FF FF
1C0 FF FF 20 5E FA C9 3B F0 13 C9 24 D0 F5 20 3F FA
1D0 8D 24 02 20 3F FA 8D 23 92 4C 6C FA A9 00 8D 23
1E0 02 8D 24 02 20 2C FA AA 20 2C FA 85 FA 20 2C FA
1F0 85 F9 8A 48 A2 00 20 2C FA 81 F9 68 AA E6 F9 D0
200 92 E6 FA CA D9 CE 20 3F FA CD 24 02 AD 22 02 60 20
210 FA CD 23 92 F9 AC A0 00 B9 74 FA F0 06 20 EE FF
220 C8 D9 F5 20 61 FA C9 47 D0 F9 F0 96 20 3F FA 18
230 6D 23 02 8D 23 92 90 93 EE 24 02 AD 22 02 60 20
240 42 FA 20 5E FA C9 41 90 92 E9 97 29 9F 0A 9A 9A
250 9A A3 94 2A 2E 22 02 88 D0 F9 AD 22 02 60 A9 83
260 0C A9 10 8D 93 02 20 BA FF AC EE F9 A9 93 8D 03
270 92 6C 23 92 9D 9A 9A 4F 42 4A 20 43 48 45 43 43
280 53 55 4D 20 45 52 52 9D 9A 52 45 57 49 4E 44 20
290 50 41 53 54 20 45 52 52 20 54 59 50 45 20
2A0 47 20 54 4F 20 52 45 53 54 41 52 54 00 C9 4C D0
2B0 93 4C 7C FE C9 51 F9 93 4C 39 FE 4C C2 F9 A9 BA
2C0 8D 18 02 A9 FF 8D 19 02 4C 00 FE FF FF FF FF FF
```

and then FFs until . . .

Of course you can't change the contents of the existing ROM and that is where the 2716 single supply EPROM comes in.

HARDWARE CHANGES

Assuming you have programmed the new ROM with the half of the Monitor you need to keep and with your own programs, now you need to make the hardware changes. To ensure that the 2716 is enabled properly some minor modifications need to be made to the computer's circuit board, and this is made slightly harder than necessary by the fact that the ROM addressing cir-


EDITOR-IN-MONITOR ROM

```
3F0 FF FF
400 20 0C FC 6C FD 90 20 9C FC 4C 09 FE A0 00 8C 91
410 FF 8C 09 C9 A2 94 BE 91 C0 8C 03 C0 88 8C 92 C0
420 8E 03 C0 8C 02 C0 A9 FB D0 09 A9 02 2C 00 C9 F0
430 1C A9 FF 8D 02 C0 20 A5 FC 29 F7 8D 92 C0 20 A5
440 FC 09 98 8D 02 C0 A2 18 20 91 FC F0 DD A2 7F 8E
450 02 C0 20 91 FC AD 99 C0 30 FB AD 00 C0 10 FB A9
460 93 8D 19 C0 A9 58 8D 10 C0 20 9C FC 85 FE AA 20
470 9C FC 85 FD 20 9C FC 85 FF A0 00 20 9C FC 91 FD
480 C8 D0 F8 E6 FE C6 FF D0 F2 86 FE A9 FF 8D 02 C0
490 60 A0 F8 88 D0 FD 55 FF CA D0 F6 60 AD 10 C0 4A
4A0 90 FA AD 11 C0 60 A9 93 8D 90 F0 A9 11 8D 00 F0
4B0 60 48 AD 00 F0 4A 4A 90 F9 68 8D 91 F0 60 49 FF
4C0 8D 00 DF 49 FF 60 48 20 CF FC AA 68 CA E8 60 AD
4D0 90 DF 49 FF 60 C9 1C F0 93 4C 7A A3 CA 10 94 E8
4E0 4C 59 A3 8A 48 AE 90 92 A9 20 9D 90 D3 CE 00 02
4F0 CA A9 9A 9D 00 D3 68 AA 4C 59 A3 FF FF FF FF FF
500 8A 48 98 48 A9 91 20 3E FC 20 C6 FC D0 95 9A D0
510 F5 F0 53 4A 90 09 2A E0 21 D0 F3 A9 1B D0 21 20
520 C8 FD 98 8D 13 02 0A 9A 9A 38 ED 13 02 8D 13 02
530 8A 4A 20 C8 FD D0 2F 18 9E 6D 13 02 AE 39 CF FD
540 CD 15 02 D0 26 CE 14 02 F0 2B A0 05 A2 C8 CA D0
550 FD 88 D0 F8 F0 AE C9 91 F9 35 A0 00 C9 02 90 47
560 A0 C0 C9 20 F0 41 A9 90 8D 16 02 8D 15 92 A9 92
570 8D 14 02 D0 8F AE 26 CD 16 02 D0 92 A2 14 8E 14
580 92 8D 16 92 A9 91 20 BE FC 20 CF FC 4A 90 33 AA
590 29 93 F0 03 A9 10 AD 15 92 10 9C A3 F0 D0 93 AA
5A0 90 90 20 D0 92 A0 C9 AD 15 92 20 7F C9 20 F0 97
5B0 8C 13 02 18 6D 13 02 8D 13 02 68 AB 68 AA AD 13
5C0 02 60 D0 92 A0 20 D0 DF A0 08 8E 9A 99 FC 60 D0
5D0 BB 2F 20 5A 41 51 2C 4D 4E 42 56 43 58 43 4A 48
5E0 47 46 44 53 49 55 59 54 52 45 57 90 00 0D 5E 4F
5F0 4C 2E 90 1C 2D BA 30 39 38 37 36 35 34 33 32 B1
600 A2 28 A9 D8 EA EA
610 85 FF A9 00 85 FE 85 FB EA EA EA EA EA EA EA EA EA
620 E6 FF E4 FF D0 F5 84 FF F0 19 20 E9 FE C9 2F F0
630 1E C9 47 F0 17 4C AD FA EA 20 93 FE 30 EC A2 92
640 20 DA FE B1 FE 85 FC 20 AC FE D0 9E 6C FE 90 20
650 E9 FE C9 2E F0 D4 C9 D0 D0 9F E6 FE 90 02 E6 FF
660 A0 00 B1 FE 85 FC 4C 77 FE 20 93 FE 30 E1 A9 00
670 20 DA FE A5 FC 91 FE 20 AC FE D0 93 85 FD F9 CF
680 AD 00 F0 4A 90 FA AD 01 F0 EA EA EA EA EA EA EA EA
690 00 90 90 C9 30 30 12 C9 3A 30 93 C9 41 30 9A C9
6A0 47 10 96 38 E9 97 29 0F 60 A9 80 60 A2 03 A0 90
6B0 B5 FC 4A 4A 4A 4A 20 CA FE 85 FC 20 CA FE CA 10
6C0 EF A9 20 8D 62 D1 8D 63 D1 60 29 90 09 09 30 3A
6D0 30 93 18 69 97 99 5E D1 C8 60 A0 04 0A 9A 9A 9A
6E0 2A 36 FC 36 FD 88 D0 78 60 A5 F3 D0 93 4C 90 FD
6F0 74 F8 69 FF 93 FF 8B FF 96 FF 30 01 93 FE C0 01
700 D3 A2 28 9A A0 0A B9 EF FE 99 17 02 88 D0 F7 20
710 A6 FC 8C 12 02 8C 03 02 8C 05 02 8C 96 92 AD E3
720 FF 8D 90 92 A9 20 99 03 83 99 00 D2 99 00 D1 99
730 90 D0 C8 D0 F1 39 5F FF F0 96 20 2D BF C8 D0 F5
740 20 BA FF C9 4D D0 93 4C 3E FA C9 57 D0 93 4C 00
750 00 C9 43 D0 93 4C 11 3D C9 44 D0 A4 40 00 FC 44
760 2F 43 2F 57 2F 4D 20 3F 00 20 2D 3F 48 AD 05 02
770 F0 22 68 20 B1 FC C9 D0 D0 13 48 8A 48 A2 9A A9
780 00 20 31 FC CA D9 FA 68 AA 68 50 48 CE 93 02 A9
790 00 8D 95 02 68 60 48 A9 91 D0 F6 AD 12 92 D0 19
7A0 A9 FE 80 00 DF 2C 00 DF 70 09 A9 F3 8D 00 DF 2C
7B0 00 DF 70 05 A9 93 4C 36 A6 60 2C 93 02 10 19 A9
7C0 FD 8D 90 DF A9 10 2C 90 DF F0 9A AD 00 FF 4A 90
7D0 EE AD 01 F0 60 EE 03 92 4C 00 FD FF FF FF FF FF
7E0 CD 2F 00 00 03 FF 9F 00 03 FF 9F 6C 18 02 6C 1A
7F0 02 6C 1C 02 6C 1E 92 6C 20 02 30 20 00 FF C0 01
```

cuit given in the COMPUKIT manual is not strictly accurate. The circuit changes are shown in Fig. 1 and are also described.

1) Locate pads W6 and W7. When I received my machine I had to cut the tracks on W6 and W7 and rewire them in the opposite sense to enable the standard Monitor ROM properly. For a 2716 these must be returned to their original state. This is because the 2716 requires a low on pins 18 and 20 to enable it.

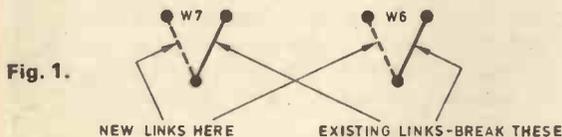2) Pin 21 is the naughty one. It is shown in the manual as being held at +5V. On my machine at least it was not, but instead was strapped to pin 20 with a circuit board track. This means its



logic level goes up and down with pin 20 which is okay for the Standard ROM but stops a 2716 from working. It is necessary to cut this track and take it to +5V.

Now, as to what to fill those 1000 or so empty holes with is

up to you. As an example this is how I partially filled mine.

EDITOR

The screen editor that was published in the July Microprompt now resides at 000-182 with the necessary address changes and an extension to compensate for terminal width. By changing two bytes at 6F0 and 6F1 to 74 and F8 the EDITOR works immediately BASIC is called from RESET.

A rapid clear screen routine is located at 183-1A1, and 1A2-1B6 contain a program to generate tones of selectable frequency and duration through a small decoding circuit and speaker.

Finally a checksum loader occupies locations 1C2-2BD. This is very useful for loading and executing programs saved in checksum format from the Extended Monitor or Assembler/Editor. With all this there is still about 300 bytes to spare in the ROM so what next? Maybe a Renumberer or a Disassembler or a...?

This system has been working in my machine for about three months now and I haven't noticed any ill effects from the missing bits, and since the cost of 2716 EPROMs is continually falling you may consider it a worthwhile thing to do. ★

ON SALE NOW!

PE POPULAR PROJECTS... CONTENTS

MOTORING

SOLID STATE CAR INSTRUMENTS by Michael Tooley B.A. and David Whitfield B.A., M.Sc.	2
1. BATTERY VOLTAGE INDICATOR	7
2. REV COUNTER	10
3. AMMETER	13
4. ENGINE TEMPERATURE	16
5. DWELL METER	18
HAZARD WARNING AND CASCADING	21
HEADLIGHT WARNING by P. G. Waystaff	24
AUTOMATIC CAR AERIAL by S. M. Bennett	

HOUSEHOLD

DIGITAL TEMPERATURE CONTROLLER by D. Coultis and P. McAllister	27
ULTRASONIC BURGLAR ALARM by G. Davies	32
HOME FREEZER ALARM by P. E. Chaplin	37

PHOTOGRAPHIC

PE DIAMATIC by J. R. Ames B.Sc. and W. L. Blyth B.Sc.	40
DIGITAL EXPOSURE TIMER by John Becker	55

MUSICAL EFFECTS

SMOOTHFUZZ by D. S. Gibbs and I. M. Shaw C. Eng. M.I.E.E.	62
PHASER by D. S. Gibbs and I. M. Shaw C. Eng. M.I.E.E.	65
GUITAR SOUND MULTIPROCESSOR by Dr. M. Sawicki and A. Kowalewski B.Sc.	66

RADIO CONTROL

R. C. FAILSAFE by Tony Jenkins	85
--------------------------------	----

TEST GEAR

WAVEFORM GENERATOR by Michael Tooley B.A. and David Whitfield B.A., M.Sc.	88
PULSE GENERATOR by Michael Tooley B.A. and David Whitfield B.A., M.Sc.	93

PRACTICAL ELECTRONICS Publication...

With electronics playing such an important role in every aspect of modern living PE have pleasure in presenting the pics of some of the most popular projects in this 96-page book. Two of these projects are completely new, the remainder are as originally published in PE save for the incorporation of certain designer approved amendments or corrections.

Our new book *PE Popular Projects* is now on sale at newsagents and components stores; the contents of this book are shown above. The book costs £1.25 from retail outlets and is also available for £1.50, UK post paid or £1.80, overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

News Briefs

BRAINS AND BRAWN

BEWARE, the intelligent public telephone is on the way! The Plessey designed PP2000 payphone might not only have a higher IQ than its user, it will probably prove tougher too—should it come to blows.

Vandal-proof, fraud-proof, the stainless steel machine is said to be capable of withstanding an attack with a sledge hammer, chisel or crowbar. So far so good, but the microprocessor controlled creep doesn't hit back, it secretly sends out a 999 call.

Up to 80,000 of the "public call office" versions are expected to be in use in the UK before 1985 (1984 again). These telephones are honest. If you insert coins to the value of 60 pence for a long distance call, the machine will not only display digitally your diminishing credit as the call progresses, but should you hang up with, say, 10 pence still on the clock, it will refund the difference.

The PP2000 payphone is powered entirely from the telephone line, is very flexible in the face of rate increases or coinage changes, and informs the post office when the cash box is nearly full; and with that kind of versatility Plessey believe they should be able to grab a good share of the estimated overseas market of £50m p.a.



The PP2000 is a microprocessor controlled payphone developed by Plessey engineers at Liverpool

SUPER OFFER

to
Practical Electronics
readers

mini 20 multimeter only £19.50



**INCLUSIVE OF POST PACKAGE
V.A.T.**

The Mini 20 Multimeter is an ideal instrument for the constructor.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10 on the normal retail price.

The 21 ranges cover all likely requirements. Operation is straight-forward, just turn the 22-position selection switch to the required range.

Please complete both parts of the coupon in **BLOCK CAPITALS**
ALCON INSTRUMENTS LTD,
19 Mulberry Walk, London SW3 6DZ.

Sensitivity 20kΩ/V d.c. 4kΩ/V a.c.

Ranges extend from
100mV to 600V d.c. 15V to 1500V a.c.
50µA to 600mA d.c. 30mA to 3A a.c.
0 to 2kΩ 0 to 2MΩ

Movement protected by internal diode and fuse.
The instrument is supplied complete with case, leads and instructions.

OFFER CLOSES DECEMBER 31st, 1980
Please allow 28 days for delivery

Name

Address

From: Alcon Instruments Ltd. (P.E. Offer)
19 Mulberry Walk, London SW3 6DZ

To: Alcon Instruments Ltd. (P.E. Offer)
19 Mulberry Walk, London SW3 6DZ


Mail order only

Please send memeter/s at £19.50 each

I enclose P.O./Cheque No..... Value

Name

Address

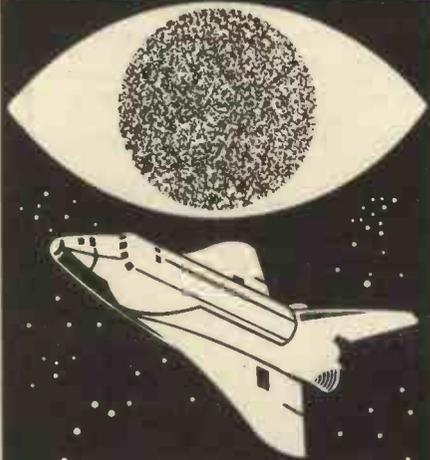

SPACEWATCH

FRANK W. HYDE

FALSE ALARMS

A number of false alarms have been detected recently in the American security networks which monitor possible attacks. It seems that the computers are in fact the culprits. There is a move to replace them because they now seem to be 'prone' to such mistakes.

Unfortunately there are other areas of definite danger of false alarms which are not so easily avoided. It is even more disturbing that the source of the false information was from the Vela satellite. It has taken ten months to solve the problem recorded in September 1979 and known as the 'event' of September 22. The task of the Vela satellites was to specifically monitor nuclear blasts. A statement released recently by the Department of Defence said that the 'event' was a nuclear blast. On the same day the official report of the panel of scientists, set up by the White House, was released and stated that the 'event' was probably not a nuclear explosion.

The panel set up by the White House was briefed to determine if the flash of light seen by the United States Vela satellite was or was not a nuclear blast. The work of the panel was carried out using computers and other relevant equipment in non government departments. The data examined and rechecked had the result that from the data over ten years the 'event' of September 22 differed from all the nuclear blasts recorded in one vital particular. This essential feature was 'that the light recorded by the two detectors on board differed'. If the detectors were in fact recording a nuclear blast, this would be at a great distance and therefore the two detectors would have recorded equal light intensity. As it turned out the records showed, in the case of 'event' September 22, that there was a difference in intensity.

The explanation therefore must be that the effect was caused by some happening. The pattern of the recordings were significantly different from that expected from a nuclear explosion near the surface of the Earth. Such

anomalous behaviour was never observed in the 'Bhangmeter' recordings. The name Bhangmeter is given to the special recordings that are made of such incidents. There were similarities even to the characteristic 'double hump' profile. The panel came to the final conclusion that this particular event could be common to a number of other similar events.

The panel of investigators also compared the September 'event' with signals from thousands of incidents from the Vela spacecraft and others. These data included astronomical events, ordinary lightning, superbolt lightning, sunlight reflections from other spacecraft, sunlight reflections from meteorites near the satellites in regular orbits, and sunlight reflected from particles ejected from meteorites on collisions with spacecraft. Finally it was to be concluded that the last item, particles ejected from meteoroids, fitted the facts.

The investigation, apart from the reassurance, that, so far as the nuclear blast was concerned a false alarm was raised, held a bonus. Previous unexplained light flashes from the recordings of Pioneer 10, on its way to Jupiter, as it passed through the asteroid belt. Collisions with small particles showed these light flashes. Such an event could be statistically expected from a Vela spacecraft once every ten years. A wider conclusion of data from all sources available leads to the conclusion that there was no corroborative evidence. The data included radioactive fallout, seismic signals and such incidents. There is a lesson here perhaps. Snap decisions are very dangerous and that all spacecraft should be under surveillance. Self monitoring would seem to be one solution. We have the technology.

THE VIKING MISSION

The Viking 1 Orbiter has run out of fuel. After four years circling the planet Mars, it has now been shut down. No more signals will be returned to Earth. However the Viking 1 lander will continue to operate and will be sending information back to Earth until 1994 according to present information.

The Viking 1 lander was the first spacecraft to land on another planet and continue sending data for more than a few minutes. It was launched from Earth on August 20, 1975 and arrived at Mars on June 19, 1976. The Viking 1 lander touched down on the surface the next day. The next mission Viking Orbiter 2 and Viking lander 2 was launched on September 9, 1975 and arrived at Mars on August 1976. The Viking 2 lander searched for a suitable landing place for almost a month before making its descent on September 3, 1976. Viking 2 Orbiter ran out of fuel on July 25, 1978 and the lander was turned off by control on April 12, 1980.

This leaves the Viking 1 lander operating on the surface of Mars at the Chryse Planitia 22.3 deg. North, 48.0 deg. West. The extension of the Mars mission beyond the four month period expected has proved more successful than was originally anticipated. The two spacecraft with their landers sent back more than 54,000 photographs of Mars and its two satellites. Each photographic frame contained twenty times more information than the previous Mariner mission in 1971. The

two Viking landers took 4,500 pictures which included high resolution pictures and stereoscopic pictures of the landing sites. The result of this mission is that 97% of the planet has now been mapped.

No organic molecules were detected. This does not necessarily mean that there is no life on Mars only that none was found at the landing sites. All the same it seems now very remote that there is life of a kind that our technology could recognise. Carbon dioxide was already known, so also was oxygen and water but in addition nitrogen, argon, neon, krypton and xenon were found in the atmosphere. The elements suggest that the Martian atmosphere must have been much denser in the past. The soil of the planet is similar to iron-rich clay.

Weather at the north site was much more variable than that at the southern site which was 20 degrees south. Here there were cyclones and weather fronts with ground frost. The highest temperature at the south site minus 31 deg. centigrade and the lowest pre-dawn temperature at the northern site was minus 124 centigrade. It is still thought that under the sandy soil there exists an overall coverage of permafrost containing water which could be released if the surface got warm enough. There is considerable data to be studied particularly the geological conditions. This will occupy teams for several years.

LATE NOTE

Using the Goldstone radar antenna the operational team have detected water just below the surface of Mars in an area called Solis Lacus. They suggest that it lies 0.5-1 metre below the surface over an area 480km by 960km. It is possible that there is a kind of pool, possibly of wet sand or a pool of soil. The observations which led to this conclusion were based on the changing reflection of the surface as the temperature changed.

THE SUN

Confirmation that the Sun has increased its energy output since the last solar minimum is now certain. The increase, a little under a half of one per cent, is significant. This is given in a report from the team at Lowell University. The principal person concerned is G. W. Lockwood. In the period of the solar minimum he suggested that there was evidence to show that the increase of the energy of the Sun could be determined by the increase in brightness of the planets and their satellites. The results of the work since 1976 has confirmed that Lowell was right. The satellites of Jupiter, Io, Europa and Callisto, together with the satellite Rhea of Saturn, have been monitored continuously since 1976 and now provides further confirmation that the Sun is a variable star.

Another major event came from the concentration of astronomers from 18 counties on a particular region of the Sun. Two large flares appeared on the Sun and each was on the limb. This enabled the maximum data to be recorded. The Solar Maximum Mission Satellite was also involved. All seven of the instruments aboard were in operation at the same time, so again maximum data was available.

PE TELETEXT

with INFRA-RED REMOTE CONTROL

David Shortland

PART 4... WIRING AND TESTING

AFTER all the p.c.b.s have been constructed, carefully check each board against its component layout. Also check that all the joints have been soldered and there are no solder splashes shorting out any of the tracks.

A suitable layout for the case is shown in Fig. 4.1. Do not fit any of the p.c.b.s until all the case drilling has been completed. Make sure there are no pieces of swarf either in the case or on any of the boards before they are fitted into position. The UHF sockets should be mounted first and the p.s.u. board then fitted to the rear of the case. The two voltage regulators should be bolted directly to the case and then the transformer, mains switch, fuse and neon fitted. The three voltage rails should be checked before any connections are made to the system.

The decoder board holes should be drilled next and then the tuner board which is mounted above the decoder drilled. The tuner board is mounted using aluminium strips, formed as shown in Fig. 4.1, taking care that the top of the VSM, VDM and tuner do not protrude above the top of the case. The front panel must also be drilled to allow the four tuning pots to protrude.

The video summer board holes can be drilled next and then the receiver board mounted on the front panel with a hole drilled for the infra-red detector diode.

With all the case holes drilled the wiring between the boards can now be carried out. A complete wiring diagram of the system is shown in Fig. 4.2. Wiring and testing problems will be simplified if ribbon cable is used.

Using co-ax cable, solder the two UHF sockets; one should go to the tuner and the other to the modulator. The connections for the tuner and modulator are to the pins on the side of the components with the earth braid soldered onto each case.

BUFFER MODIFICATION (5050)

The F1 output (pin 20) from the SAA5050 TROM chip should be buffered as shown in Fig. 4.3 to ensure correct operation under all conditions. The resistor and transistor for the buffer can be soldered directly onto the decoder board as shown in Fig. 4.3.

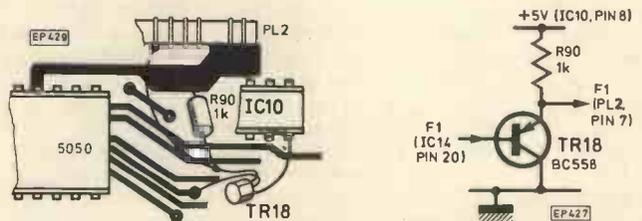


Fig. 4.3. Buffer circuit modification for the decoder board. It may be necessary to increase the length of the leads of TR18 using tinned copper wire. Resistor R90 should be soldered to plug PL2 with the daughter board removed

TESTING

Before all the p.c.b.s are finally fitted into position the wiring should be very carefully rechecked. It is very important that the power supply rails to each p.c.b. are carefully checked. Take care that the daughter board is plugged in the right way round. Also check the three wire links on the daughter board. If everything is correct switch the unit on and check the supply rails on each p.c.b. If all the rails are correct, switch the system off and using two co-ax leads connect the aerial to the tuner via the UHF socket and the TV to the modulator via the other UHF socket.

With the TV switched on and tuned to channel 36, switch

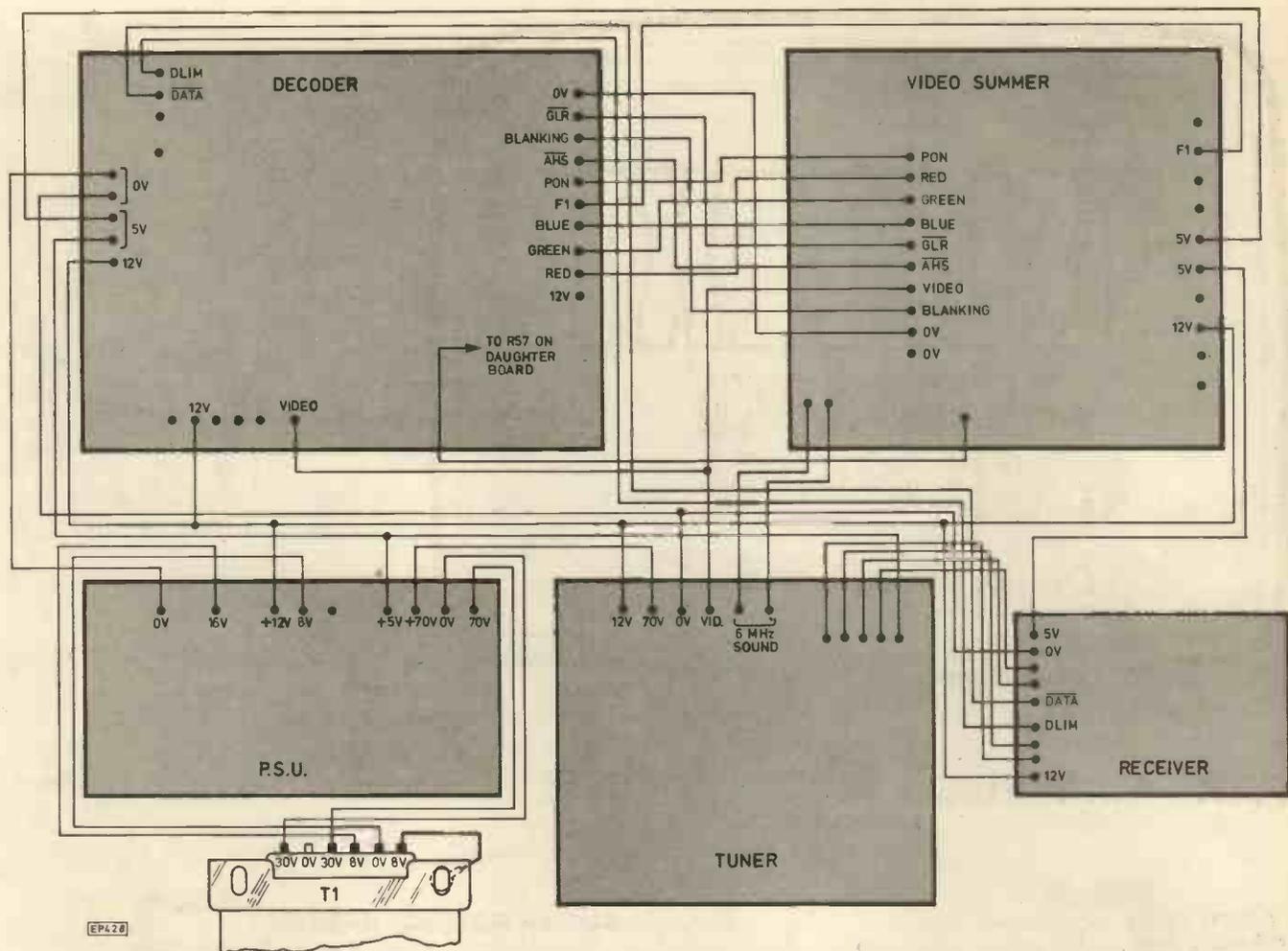


Fig. 4.1. Wiring diagram for the complete system. Note the annotation of plug PL3 on the decoder board was shown incorrectly in Fig. 2.4 (F1 was omitted)

the system on. It should be possible to adjust the BBC1 tuning pot to obtain a picture. If there are any problems, the video output of the tuner board can be taken directly to the modulator on the video summer board. This will enable the tuner board to be set up if there are any problems with the decoder or video board adjustments. With the tuner adjusted using the setting up procedure given in Part 2 for the best picture available, remove the link to the modulator.

It should be possible to obtain a reasonable picture with the tuner correctly set up, which will allow the video summer board to be adjusted. (See Part 3.)

When the system is first switched into the teletext mode page 100 of the Ceefax magazine should be displayed. If there are any problems with the remote control circuits the output from IC1 pin 16 can be directly wired to the base of TR6 on the receiver unit, by-passing the infra-red link.

The audio section of the system has been designed around the TBA120S. The volume can be controlled by VR9 and the Quad coil L6 should be adjusted for the best sound reproduction.

TUNING POTENTIOMETERS

The tuning potentiometer VR2 should be adjusted for BBC1, VR3 for BBC2 and VR4 for ITV. This will ensure the correct channel is displayed when the channel is changed or the status button pressed.

CORRECTIONS

The p.c.b. layout for the tuner board which was shown in Fig. 2.3 is incorrect. The 4050 (IC3) buffer is a 16 pin not a 14 pin device. The correct design for the tuner board is shown in Fig. 4.4.

ALIGNMENT OF THE TELETEXT DECODER

The teletext board is supplied ready aligned and should require no adjustment. In the event of incorrect or no data being received, inspection of the remote control and i.f. sections of the receiver should be carried out first. These adjustments do not affect the actual display of characters on the TV screen. The four adjustments on the board are designed to take up tolerances in the SAA5030 and should therefore only be changed if the SAA5030 on the board is replaced. They should be carried out in the following order.

1. *Field Sync. Adjustment.* Using a scope, look at the video input to the decoder and the voltage on pin 13 of the SAA5030, adjust the 10kΩ potentiometer until the leading edge of the pulse on pin 13 is $48 \pm 5\mu\text{s}$ from the field sync. datum (the beginning of the first broad pulse as shown in the diagram).

2. *Crystal Frequency Adjustment.* A 5–65pF trimmer capacitor in series with the crystal adjusts the free running frequency of the oscillator. Connect pin 1 of the SAA5030 to +12V so that the oscillator free runs and connect a 5MΩ

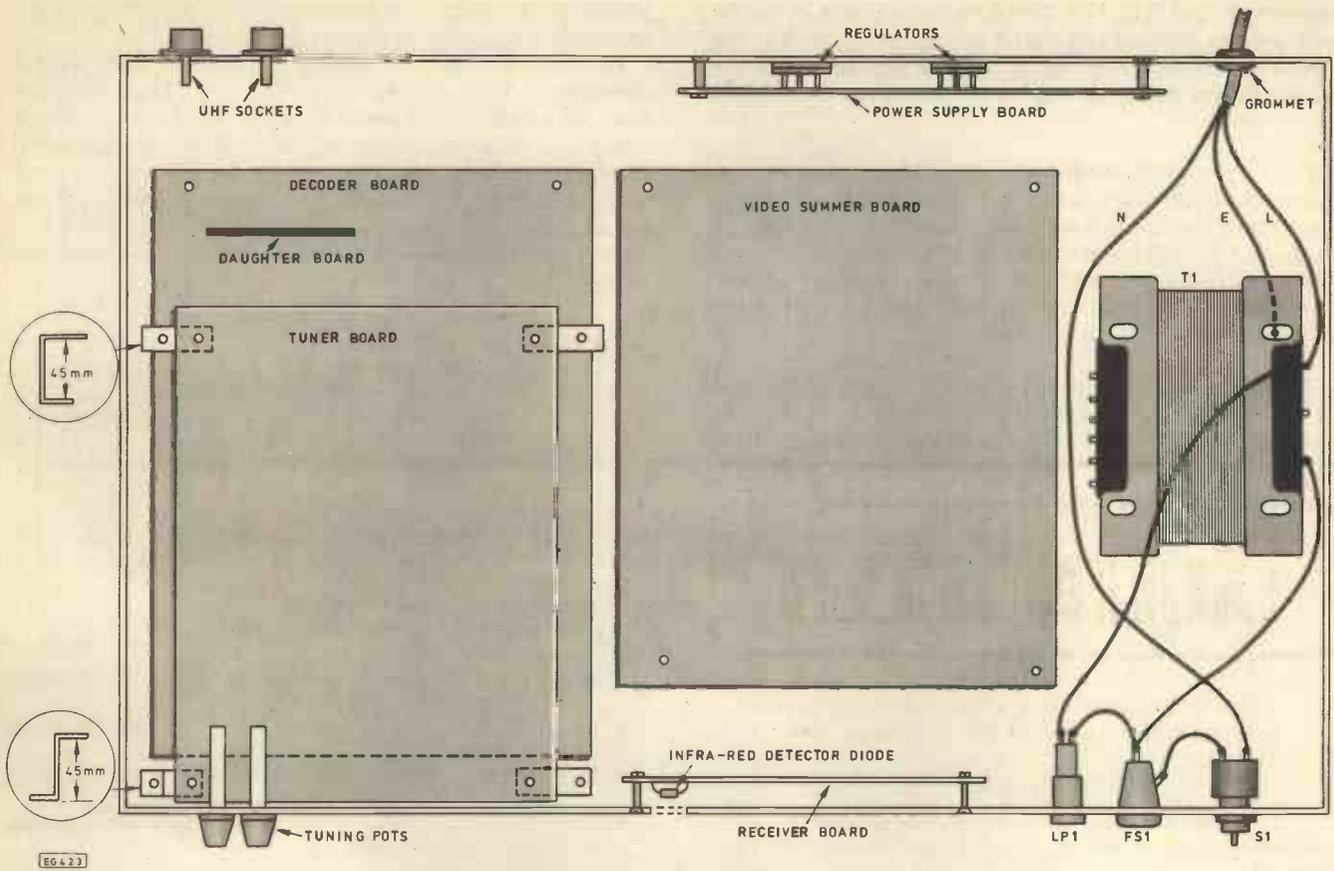


Fig. 4.2. Internal layout of the case

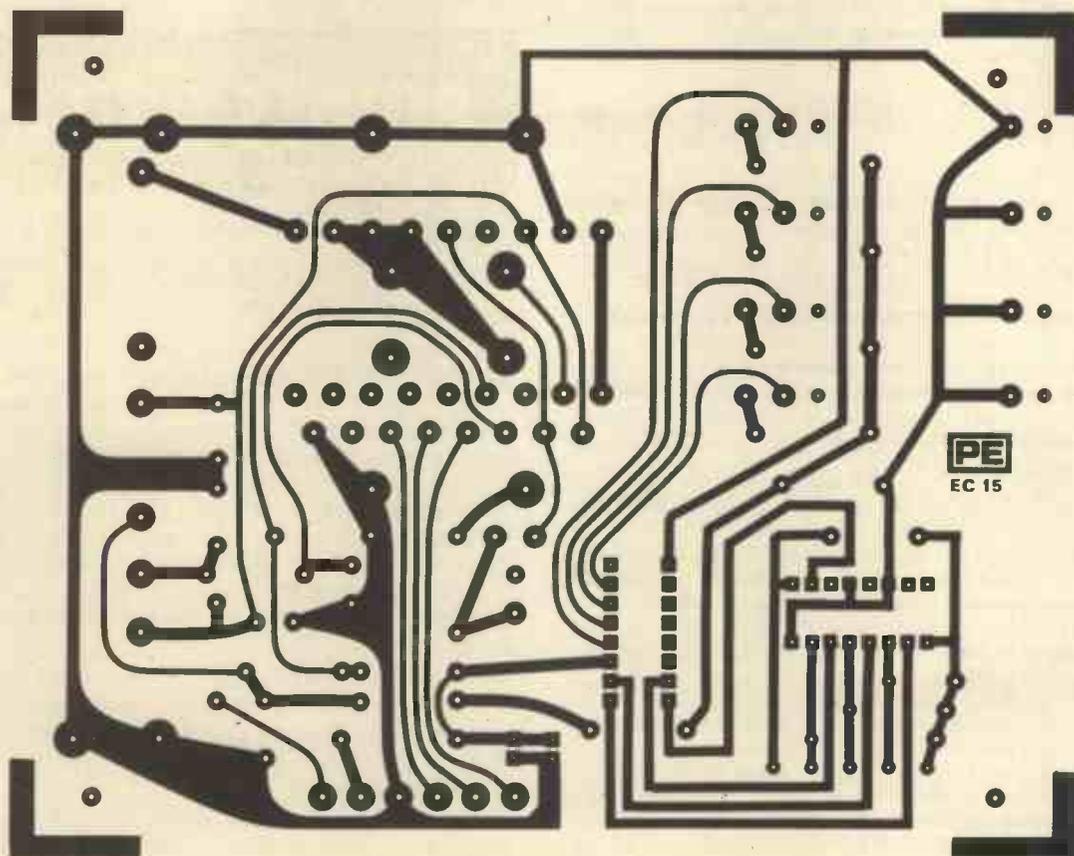


Fig. 4.4. Corrected p.c.b. design for the Tuner board

resistor from pin 7 to 12V. Using the scope, look at the incoming video and the sandcastle waveform on pin 5 at the SAA5030. The trimmer should now be adjusted until the two signals are stationary relative to each other. Remove the link and resistor.

3. *Clock Phase Adjustment.* Pin 20 of the SAA5030 may have a 33µH choke and a 5–65pF trimmer connected to it. This trimmer is used to adjust the phase of the data clock to ensure that the teletext data is latched at the optimum time. If for some reason the SAA5030 is replaced, these components should be removed and replaced with a 1nF capacitor connected from Pin 20 to ground.

4. *Clock Coil Adjustment.* As stated earlier, the clock coil is pre-aligned using specialised test equipment and cannot be correctly set-up without such equipment. However, if the

SAA5030 is changed for some reason, it can be aligned approximately by using the following procedure.

Put the decoder in teletext mode and call up the 'Engineering Clock-Cracker' page. This is a special test page used for assessing the performance of the data clock. Now rotate the clock coil core clockwise until the decoder starts to make mistakes. Note this position. Rotate the core anti-clockwise until the decoder makes mistakes again. Note this position. Set the core midway between the two marks. This should correspond to approximately one turn out from fully screwed in.

ACKNOWLEDGEMENTS

The author would like to thank Luke Theodossiou, who designed the Tuner circuit, for his help and assistance with the overall design, also Ian Stuchbury, who developed the Video Summer, for his helpful comments. ★

Countdown

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below.

Semiconductor International 80 Nov. 25–27. Metropole Convention Centre. **T1**

BEX 80 Nov. 26–27. Exhibition Centre, Bristol. **K**

Breadboard Nov. 26–30. Royal Horticultural Halls, Westminster. **T**

BEX 81 Feb. 4–5. Pavilion, Bournemouth. **K**

Microsystems 81 (exhibition and conference) March 11–13. Wembley Conf. Centre, London. **Z1**

INSPEX 1981 March 16–20. NEC, Birmingham. **Z1**

Seminex 81 (seminars only) March 23–27. Imperial College, London. **H1**

BEX 81 March 25–26. Metropole, Brighton. **K**

The Northern Electronic Test & Measurement Exhibition 81 March

31–April 2. Wythenshawe Forum, Manchester. **T**

BEX 81 April 8–9. Centre Hotel, Liverpool. **K**

All Electronics Show 81 April 22–24. Grosvenor Ho., Park Lane, London. **F1**

Computer Graphics 1981 April 28–30. The Barbican Centre, London. **O**

BEX 81 April 29–30. Dragonara Hotel, Leeds. **K**

Entertainment 81 May 9–17 (weekday mornings trade only). NEC, Birmingham. **B2**

The European Consumer Electronics Show 81 May 10–13, Nuremberg Fair Centre, W. Germany. (Trade) **I**

BEX Train May 11–22. Calling at: Cambridge, Norwich, Leicester, Sheffield, Newcastle, Middlesbrough, Hull, Nottingham, Reading and Portsmouth. **K**

Defence Components Expo 81 May 12–14. Brighton Metropole. **I**

Semlab 81 June 2–5. Grand Hall, Olympia, London. The international scientific, educational, medical and industrial laboratory equipment exhibition. (Trade) **I**

Transducer Tempcon 81 June 9–11. Wembley Conf. Centre, London. **T**

Components 81 (Electronic Components Industry Fair) June 9–12. Earls Court, London. This show will alternate yearly with Electronics, now that the IEA amalgamation with Electrex has ceased. **I**

International Word Processing Exhibition & Conf. 81 June 23–26. Wembley Conf. Centre, London. **Z**

Solar Energy Exhibition Aug. 23–28, 1981. Brighton. **M**

International Business Show 81 Oct. 20–29. NEC, Birmingham. **A2**

Electronics 82 (Sub-titled International Electronics Control and Instruments Exhibition) May 24–28, 1982. NEC. **I**

I Industrial Trade Fairs. ☎ 021-705 6707

K Douglas Temple Studios, 1046 Old Christchurch Road, Bournemouth

M Montbuild. ☎ 01-486 1951

O Online Conferences. ☎ 0895 39262

T Trident International Exhibitions. ☎ 0822 4671

H1 Seminec Ltd. ☎ 0892 39664

T1 Kiver Communications UK, Millbank House, 171/185 Ewell Road, Surbiton, Surrey KT6 6AX.

Z1 IPC Exhibitions Ltd., 40 Bowling Green Lane, London EC1R 0NE. ☎ 01-837 3636

A2 Hart Browne & Curtis Ltd., 29 Sackville Street, Piccadilly, London W1X 1DR. ☎ 01-439 8556

B2 Brintex Exhibitions Ltd., 178-202 Great Portland Street, London W1N 6NH. ☎ 01-637 2400

POINTS ARISING

MICRO PROMPT (September 1980)

The short m/c program under "Error Message Error" should read:

```
7F and not 7A
4C          AC
2D  ✓      2D  x
BF          BF
```

PROGRAMMABLE SOUND GENERATOR (September 1980)

Line 60 of the "Random Sound" program should read:

Y = INT(RND(7)* 15): etc.

Also, see Micro Prompt for details of a decoding fix for the PSG.

MAGNUM METAL LOCATOR (Sept 80)

The p.c.b. shown on page 53 is not same size. A correctly sized one is available on application.

PE DIAMATIC Update

J.R.W. AMES
W.L. BLYTH

Overcoming problems that might have arisen in this popular design

MANY constructors are successfully using 'Diamatic' (published in *PE* Nov. 79 and now available *PE Popular Projects*) units both with two identical projectors and with two projectors of different model or manufacture. In a small number of cases though, problems have arisen when different projectors are used. This article describes the causes of the two problems and the way in which they can be overcome.

PHASE ERRORS

The Diamatic will not function correctly if there is a large phase difference between the 24 volt supplies of the two projectors although it is very unusual to find such a phase error because of the resistive load presented to the transformers by the projector bulbs. In some projectors however, the fan motor is connected auto-transformer fashion to the transformer primary and this highly inductive load causes a phase shift which appears on the secondary winding. Since the phase reference for both of the triac dimmers is taken from only one of the projectors—projector B—the lamp in projector A can behave in an unpredictable manner, especially at the extreme ends of the dimmer range.

The fault usually shows up when projector A is at its brightest and can result in a sudden switch to half power or even completely dark at the extreme end of the control range or when the 'Change' button is pressed. In this instance the triac in projector A is being fired very early in the mains cycle (Fig. 1a) and if A lags B firing can occur very close to the end of the previous cycle (Fig. 1b). The results of this change in the firing instant are not easy to predict, especially when the phase error is small and the firing pulses overlap the zero crossing.

EARTHING PROBLEMS

Some projectors have internal circuitry which is tied to earth, hence the lamp supply is not fully floating and when the centre rail of the Diamatic power supply is earthed large currents can flow causing damage to components in either the projector or the Diamatic. Clearly these problems can only occur if projector B from which the Diamatic derives its power supply, has a three core mains lead fitted as standard. If either of your projectors has a two core lead then use this as projector B and you will have a fully floating supply. If neither has a two core lead then it is safest to use a separate 24V transformer to power the Diamatic. RS Components transformer No. 207-201 is suitable for this purpose. Remove the wire leading to SK2 pin 10 and connect this to one side of the 24V supply, connect the other side to the junction of D3, D5 and R1, first having broken the track between here and TR201.

This will use the transformer to provide both power and phase reference. Provided no phase error problems are introduced this is a complete answer to earthing problems.

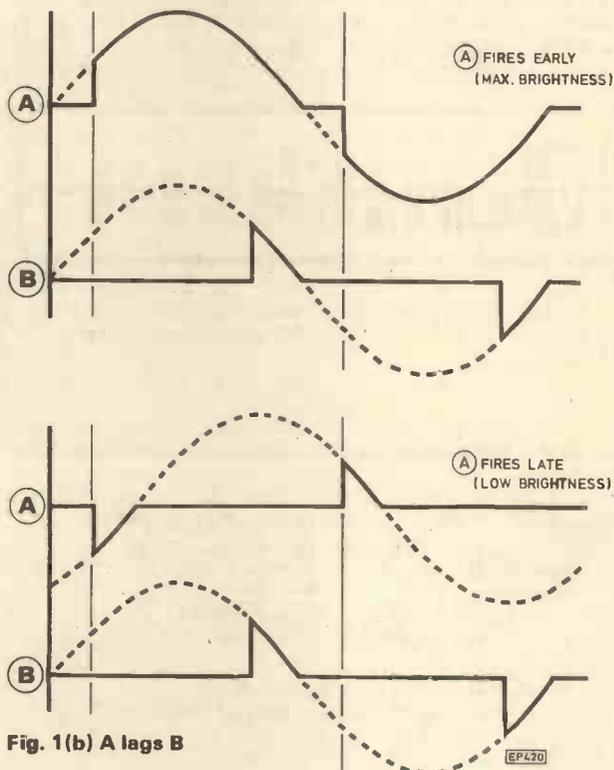


Fig. 1 (b) A lags B

A NEW PHASE REFERENCE

If it is necessary to derive a separate phase reference for projector A or if the phase reference derived from the separate transformer is not satisfactory a method has to be found of generating a phase reference from the projector without introducing or reintroducing earthing problems. The simplest method is to use an opto-coupler. Inside this is an l.e.d. which illuminates the base of a phototransistor; when the l.e.d. is turned on the output transistor conducts without any physical connection being necessary. Signals can therefore be passed between two circuits at very different potentials with respect to earth, modern devices can offer a breakdown voltage of 2500V or more.

Fig. 2 shows the circuit of the new phase reference pulse generator. D301-304 rectify the voltage across the secondary of projector A transformer can apply it via the current limiter (TR301, R302, 303 D305, 306) to the opto-coupler l.e.d. The l.e.d. must illuminate sufficiently to saturate the output transistor early in the mains cycle if sufficiently narrow pulses are to be obtained. If a resistor were used to produce this current (15mA) within the required 300 μ s of the start of the cycle then the current in the l.e.d. in mid-cycle would be 790mA—13 times the maximum rated

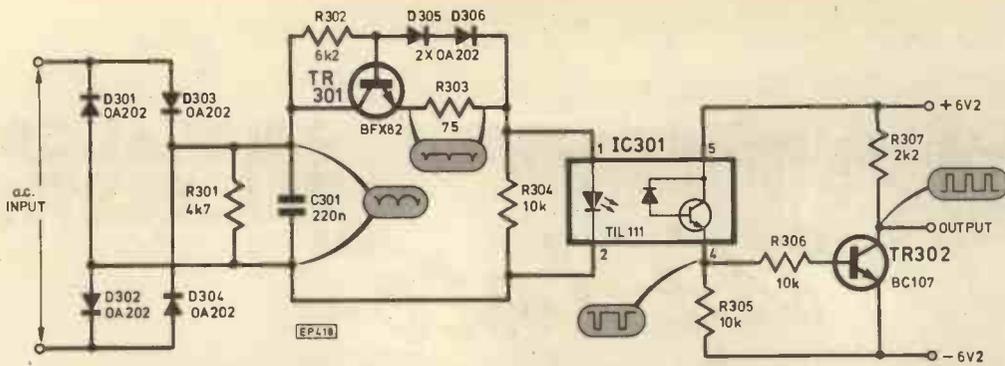


Fig. 2 Circuit diagram of new phase reference pulse generator

current! Clearly a limiter is needed to remove the peaks, TR301, which saturates until D305, 306 conduct providing a reference to the base, performs this function. R301 ensures that some current always flows in the rectifier diodes and R304 helps the i.e.d. to turn off quickly by providing a path for the removal of minority carriers when TR301 switches off at the end of the cycle. C301 removes switching spikes which would otherwise disturb the operation of the circuit.

On the output side the V_{ce} saturation voltage of the transistor within the isolator is too high to drive the Diamatic directly so TR302, R305-307 provide a signal that is compatible with the original unit.

CONSTRUCTION AND INSTALLATION

The simple module may be built either on Veroboard or on the printed wiring board whose layout appears in Fig 3.

Before installing the module make a connection from the unused side of projector A transformer to the Diamatic unit. If the wiring diagrams of the original article have been followed this point will be available in the triac box between the projector A tags for 'change' and 'g' of CSR101. Take this signal via the spare core in the lead to the Diamatic, to pin 11 of PL2. Now connect the a.c. inputs of the new module to pins 2 and 11 of SK2, thereby connecting the module directly across the secondary of transformer A.

Next join the module +6.2V lead to the Diamatic positive supply and the -6.2V lead to the negative supply (this connection can be made to any of several convenient links on the original p.c.b.). Finally remove the link on the main printed wiring board which joins the collector of TR1 to R101, 104 and connect the output of the module to the junction of these two resistors.

Connections are now complete and Fig. 4 shows how the module relates to the circuits of the main system. As the setting up of the Diamatic will only have to be changed very slightly a full functional test can now be carried out followed by slight adjustments to the presets for projector A if required.

If a separate power supply is used for the Diamatic it may be necessary to derive separate phase references for each projector. If this is the case build two of the new modules and connect one as previously described. To install the second module remove TR1 D1, 2, C1, R1, 3, 27, 28 and connect the output of the module to the junction of R201, 204. Connections to projector B transformer is via pins 6 and 10 of SK2 and the \pm power supplies are derived as previously described. An earth for the Diamatic box and its circuits can now be taken to the mains earth via the power supply cable with no danger of damage to any of the components.

In order to avoid earth and phase problems completely the 'belt and braces' approach is to use a separate transformer to power the Diamatic and two opto-isolator modules. ★

COMPONENTS

Resistors		Semiconductors	
R301	4k7	TR301	BFX85
R302	6k2	TR302	BC107
R303	75ohm	IC301	TIL111 (Texas)
R304	10k		R-S 307-979
R305	10k	C301	0.22 μ F Polyester
R306	10k		
R307	2k2	D301-306	OA202


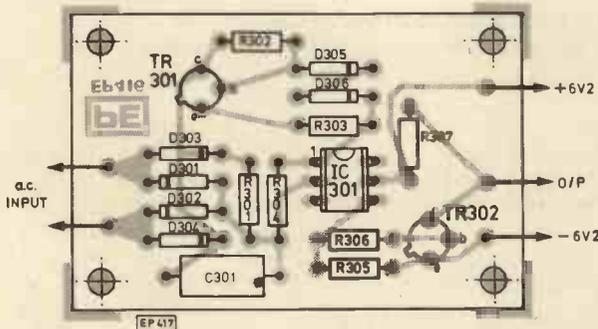
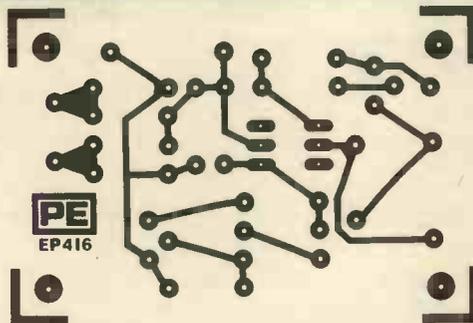


Fig. 3 (Above) P.c.b. and component layout

Fig. 4 (Right) Connection to rest of system

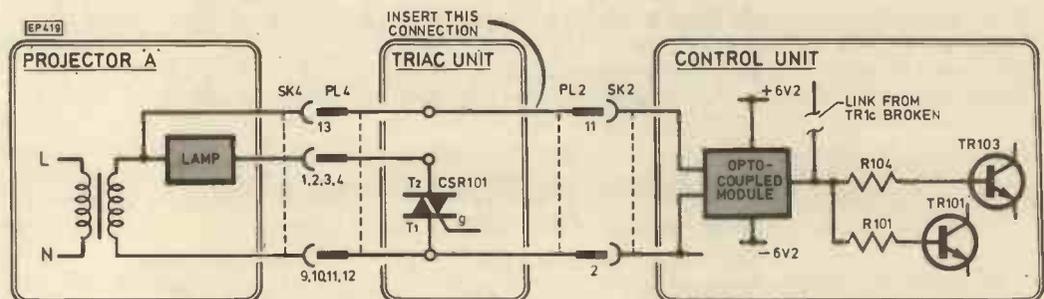

BREADBOARD '80

COMPONENTS DEMONSTRATIONS SPECIAL OFFERS MAGAZINES BOOKS



It's all at Breadboard '80

This is **the** exhibition for the electronics enthusiast. From November 26 -30 there is only one place in the universe for the electronics enthusiast to be — Breadboard '80, at the Royal Horticultural Hall in London. The majority of leading companies will be exhibiting, including all the top monthly magazines in the field. There will be demonstrations on most stands and many feature special offers that are EXCLUSIVE to Breadboard!

All aspects of this fascinating field are catered for, from CB to home computing, so whether you want to buy a soldering iron or a synthesiser — or just keep up to date with your hobby — don't miss Breadboard '80.

With every order of FOUR or more advance tickets we will send you a FREE copy of E.T. 1-1989 (£1.50 normally!)

**Royal Horticultural Halls
Elverton Street
Westminster London SW1
November 26-30 1980**

26th Nov — WEDNESDAY — 10am-6pm
27th Nov — THURSDAY — 10am-8pm
28th Nov — FRIDAY — 10am-6pm
29th Nov — SATURDAY — 10am-6pm
30th Nov — SUNDAY — 10am-4pm

Send to: **AVOID QUEUES — GET ADVANCE TICKETS**
Advance Tickets, Modnags Ltd, 145 Charing Cross Rd, London WC2H 0EE
Please send: tickets @ £1.50 (Student/Child/OAP)
I enclose P.O./Cheque for £.....

DISCO DESK

Part 3 BEN DUNCAN

THIS part rounds off card construction together with the Monitor amplifier board. The circuit for the final card (Card 4) is given in Fig. 12.

CARD 4

The Autofader is driven by a signal derived from the top of the microphone gain control. In the absence of a signal, the n -channel f.e.t.s TR3, TR4, are pinched off by negative bias applied via VR2 and R4. When a signal is applied to pin 3 on IC1, in excess of the voltage on pin 2, the output of IC1 saturates positively and charges C3. This lowers the negative bias on TR3 and TR4 and causes their drain/source resistance to decrease, thereby attenuating the music signal. The degree of attenuation is governed by the setting of VR3, which forms a potential divider in conjunction with R3, R4 and VR1 in Fig. 6. The input sensitivity of the Autofader is governed by the voltage set up on pin 2 of IC1 by VR1. Immediately an announcement finishes, IC1 reverts to its quiescent state and C3 discharges slowly at a rate set by VR2. Preset pots VR1—3 are all panel mounted because adjustments are required to suit different hall acoustics and miking techniques. Spindle locks are provided to protect the shafts and to prevent accidental adjustments.

The stereo lines are applied to IC2 and 3. These are connected as unity gain buffers and feed the Sound-To-Light Mixer (IC5). The microphone line is applied to IC4, the gain of which is controlled by VR4. This preset is adjusted so that normal miking provides a signal at the mixer output that is roughly equal to the signal level from the stereo lines. The Cue I.e.d. Driver is simply a high gain amplifier (IC6) with limited frequency response (to minimise spurious operation) which turns TR1 hard on when a signal of suitable level is present. In turn, TR1 turns on the I.e.d.

The scintillating light caused by the peak detecting nature

of this circuit is smoothed by C12. R22 and C14 attenuate the current spikes and hence noise generated by rapid switching of TR1. VR5 is set so that the I.e.d. discriminates between the lead-in grooves and the onset of modulation on a typical disc.


MONITOR AMPLIFIER

This utilises the SGS-Ates TBA810P i.c. power amplifier which has been chosen for its comprehensive protection and the ready availability of a p.c.b. The latter is particularly useful, since in common with all i.c. power amplifiers, the board layout is quite critical and finding a satisfactory p.c.b. layout is very much a 'cut and try' process. The circuit board is bolted directly to the front panel. The input to VR1 is either PFL (point 'Z' on Fig. 6) or from the mono output (pin 7 on Fig. 8); this switching is shown in detail later. It is important to note that the PFL signal is derived prior to RIAA bass boost, and is therefore lacking in low frequencies. However, the PFL is intended primarily for cueing up records, and the lack of low frequencies is of no consequence. In fact, the predominantly midrange and treble response of the PFL signal is helpful in that it 'cuts through' amidst high ambient SPLs.

If the amplifier is required to drive headphones only, R4 should be inserted to reduce the output power to some 400mW. This resistive attenuation is preferable to lowering the gain (set by R1) because it does not affect the input overload margin. The value of R1 shown gives an input sensitivity of around 10mV and input saturation occurs at 220mV. C5 and C6 determine the bandwidth of the amplifier (15kHz as shown) and may be increased in value if any h.f. instability occurs. Note that C5 is approximately five times the value of C6—this relationship must be maintained if the values are changed.

In this application, IC1 is protected against output short circuits, supply polarity inversion and also features thermal shutdown. The latter allows an area of copper on the p.c.b. to be used with confidence as a heatsink. To test the monitor amplifier, connect a 12V supply and a loudspeaker. If l.f. instability occurs, check the earthing arrangements; interaction between input earth currents (pin 9) and the output return current (pin 10) is usually responsible. If all is well, apply a signal <100mV to VR1, which should be temporarily wired to the p.c.b. to provide an input bias path.

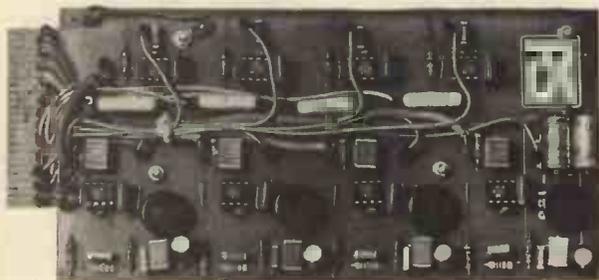
The earlier version of the TBA810, suffixed 'S', is substantially similar to the latest 'P' version and can be directly substituted. However, the ripple rejection in particular is not so good, and it may be necessary to increase the value of C4.



Card 4 prototype

CARD 3

Fig. 10. P.c.b. and layout

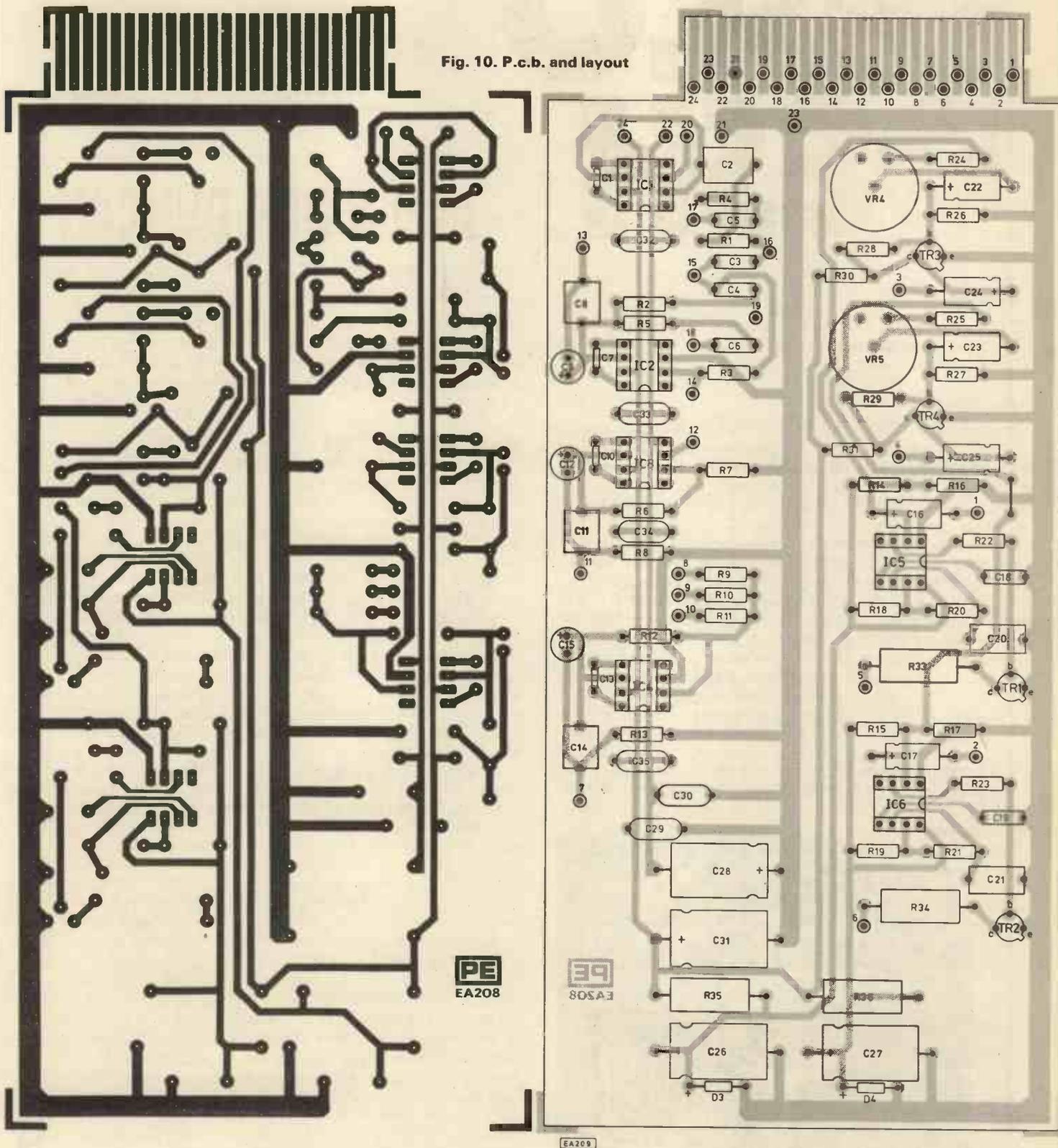

Monitor Amplifier

Resistors

R1	33R ½ watt 5%
R2	100R ½ watt 5%
R3	1R ½ watt 5%
R4	33R 1 watt 5% (see text)

Potentiometer

VR1	10k single log slide pot (Maplin type FX57M)
-----	--

Capacitors

C1	100n polyester C280AE series
C2	100µ 40V axial electrolytic
C3	100µ 40V axial electrolytic
C4	100µ 40V axial electrolytic
C5	3n3 polycarbonate
C6	680p ceramic or polystyrene
C7	100n polyester C280AE series
C8	100µ 40V axial electrolytic
C9	1000µ 16V axial electrolytic

Semiconductors

TBA 810P (SGS-ATES)

Miscellaneous

SKT1—standard jack socket, insulated


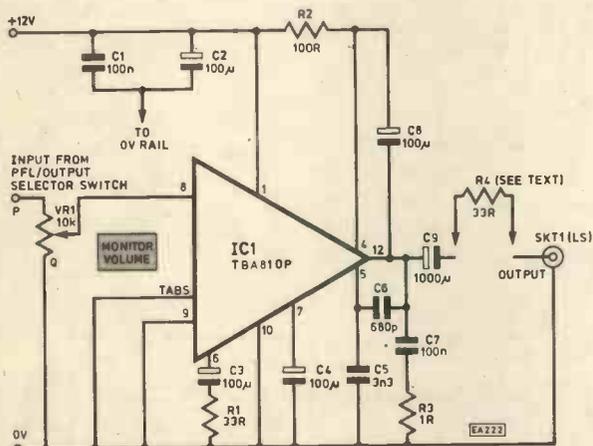


Fig. 11. Monitor Amplifier circuit with p.c.b. below and layout right

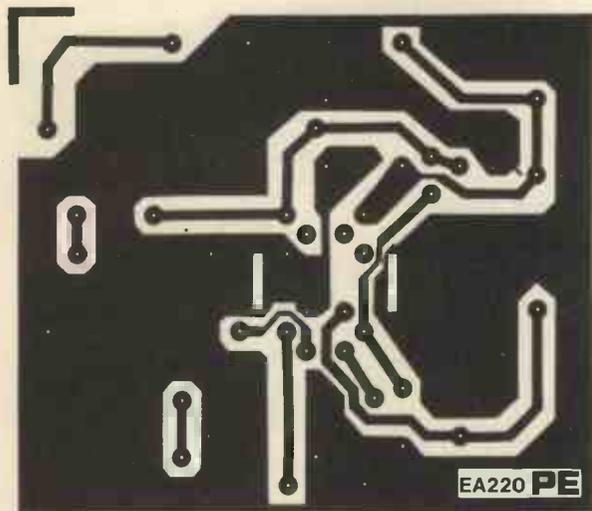

Card 4

Resistors

R1	10k
R2	8R2
R3	100k
R4	5k6
R5—6	1M
R7—9	100k
R10—12	22k
R13	1k
R14	22k
R15	100k
R16—17	330k
R18	1k
R19—20	10k
R22—23	470R, ½ watt
All ½ watt, 5% unless otherwise stated	

Potentiometers

VR1	1k rotary lin pot
VR2	470k rotary lin pot
VR3	1k dual rotary lin pot
VR4	47k open cermet preset
VR5, 6	100k open cermet preset

Capacitors

C1	25µ 25V axial electrolytic
C2	220n polycarbonate
C3	4µ 7 25V axial electrolytic
C4, 5, 6, 7	470n polyester C280AE series
C8, 9	100n polyester C280AE series
C10, 11	1µ 25V axial electrolytic
C12, 13	10µ 25V axial electrolytic
C14, 15	100µ 25V axial electrolytic
C16, 17	100µ 40V axial electrolytic
C18, 19—23	100n polyester C280AE series


Semiconductors

IC1—7	74IC, 8 pin d.i.l. version
TR1, 2	BC107
TR3, 4	2N3819
D1	BZY88C9V1
D2	1N914
D3, 4	Panel l.e.d., green (RS type 586-541)

7 x 8 pin d.i.l. sockets

JK1—Standard jack socket, insulated

Spindle locks, set of 3 (RS type 509-816, one pack only required)

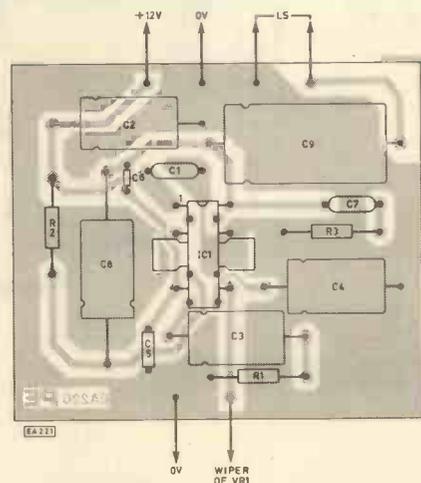


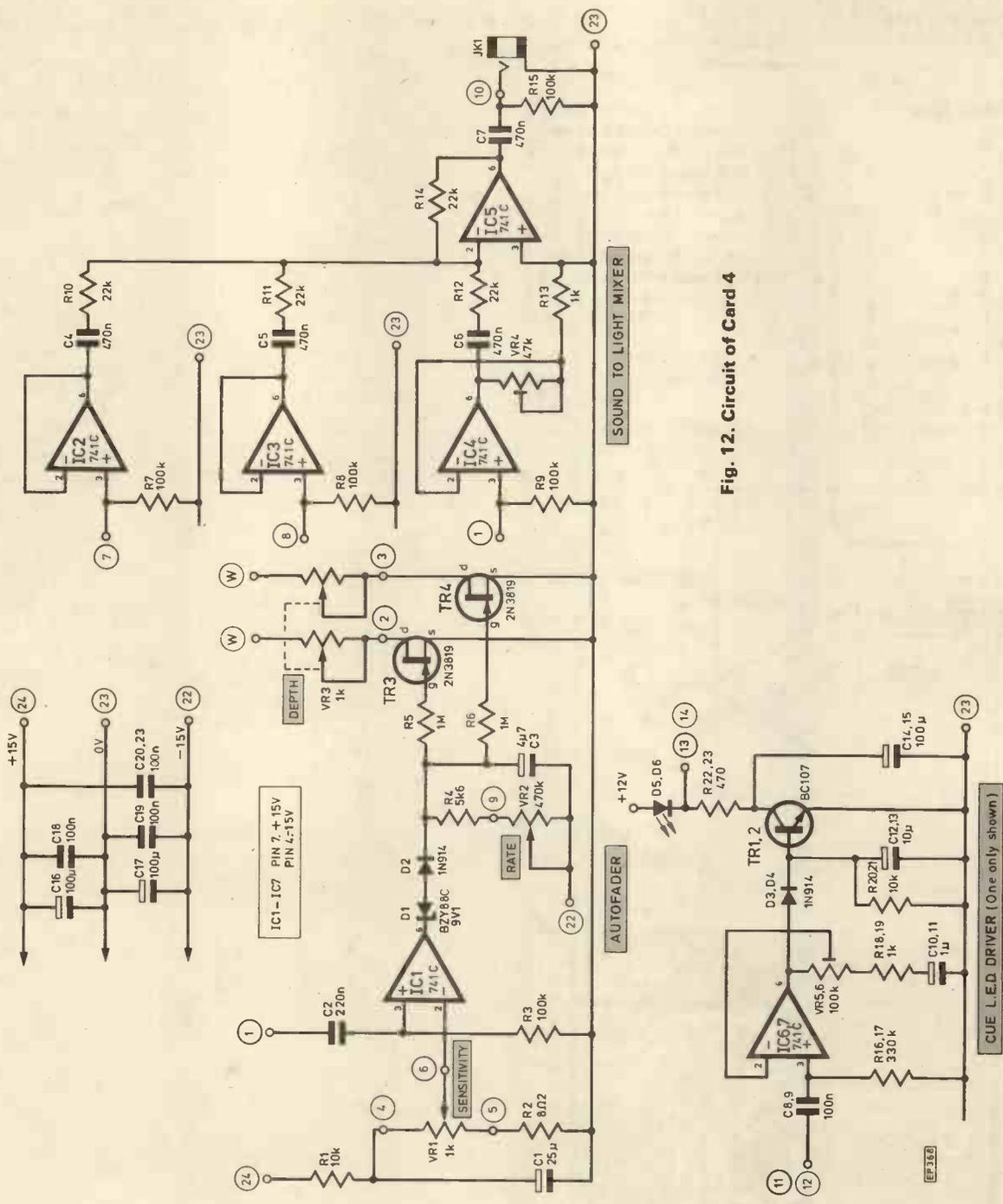


Fig. 12. Circuit of Card 4

CARD 4

Fig. 13. P.c.b. and layout

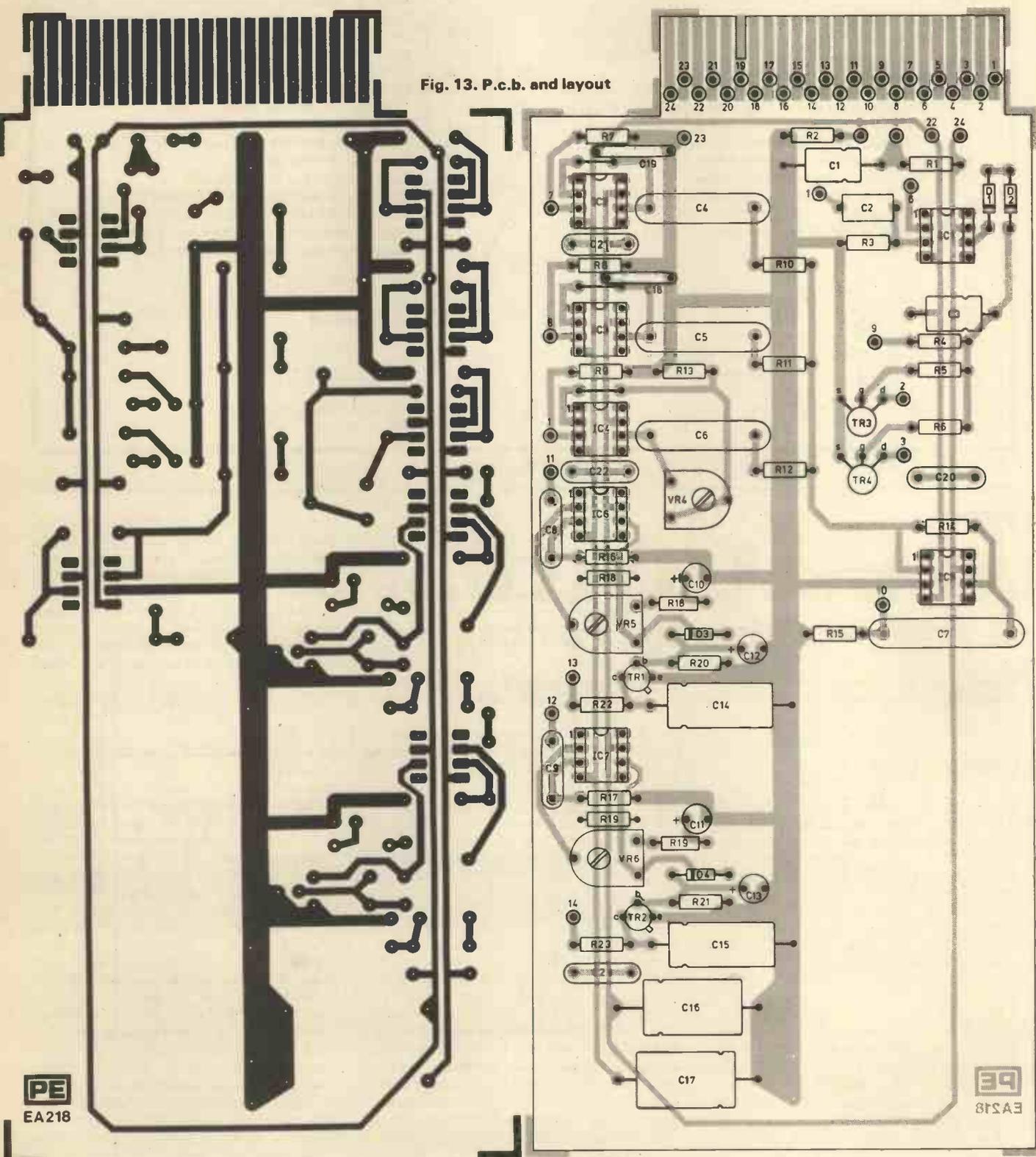

PE
EA218

EA
EA218

EA219

Edge wiring

Card 4

Pin No.	Card 3 Connection	Pin No.	Card 4 Connection
1	Left input from music lines to peak indicator	1	Input to autofader and SLM mixer from 13 on Card 3
2	Right input from music lines to peak indicator	2	Left autofader output to depth pot } Then to Right autofader output to depth pot } point 'W'
3	Left output to VU meter	3	
4	Right output to VU meter	4	To 'top' of autofader sensitivity pot
5	Peak indicator output (Left) to indicator l.e.d. cathode	5	To 'bottom' of autofader sensitivity pot
6	Peak indicator output (Right) to indicator l.e.d. cathode	6	To slider of autofader sensitivity pot
7	Mono output to 3 pin male XLR socket	7	Left music line into SLM mixer
8	Left music input to Mono Mixer	8	Right music line into SLM mixer
9	Right music input to Mono Mixer	9	To autofader rate control
10	Microphone line into Mono Mixer	10	SLM mixer output to jack socket
11	Microphone line, output to send-return switch	11	Input to cue l.e.d. driver 'A' from point 'X'
12	Input to Microphone Line Driver from VR3 (Slider)	12	Input to cue l.e.d. driver 'B' from point 'Y'
13	Output of microphone equalisation stage to 'top' of VR3	13	Output from cue l.e.d. driver 'A' to l.e.d. cathode
14	T.CEN	14	Output from cue l.e.d. driver 'B' to l.e.d. cathode
15	B.CEN	15	} No connection
16	B.MA	16	
17	T.MA	17	
18	T.MI	18	
19	B.MI	19	
20	Microphone input from transformer	20	} No connection
21	Screen (OV) connection to transformer	21	
22	-ve, 15V	22	-ve, 15V
23	OV, to central earth point	23	OV, to central earth point
24	+ve, 15V	24	+ve, 15V

Next Month: Wiring details

Readout...

A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Velikovsky

Sir—As one who has made an extensive study of Dr. Velikovsky's work, and that of the considerable number of scientists, historians, archaeologists, and others who have contributed towards further investigation of his theory, I would like to ask F. W. Hyde just exactly where and when did Velikovsky express a "conviction that the Earth came into being less than 4000 years ago", and just exactly when and where did he state that he "(did) not believe that there was a system before 1500 B.C. or thereabouts"?

Perhaps F. W. Hyde would care to consider rebutting his own mis-statements before tackling the statements Velikovsky actually made. Like the majority of Velikovsky-detractors, Hyde must prove his ability to read before I, for one, will be gullible enough to harken to his bizarre ideas.

I can find no reason to put Velikovsky's predictions within quotation marks. I find them to be perfectly logical and valid deductions from his main thesis, and, whilst I do not accept all that he claims, it is a fact that his record of success exceeds that of any other theorist. You may also care to note that my

own further investigations of his theory were considered of sufficient scientific merit to be accepted for publication in the Journal of Physics, part A: Maths & Gen. (Oct 1978, vol. 11 no. 10 pp. 2107-2130), and that paper has been commented upon (without derision) in New Scientist, Physics Bulletin, Science Digest, Electrical Review, and elsewhere, and a voluminous correspondence from many parts of the world, including well-known centres of learning, has been most encouraging.

As for Mr. Birch, he may like to know that Dr. Velikovsky was a scientist. He was a long-time colleague and personal friend of A. Einstein. At the time of Einstein's death, he had open on his desk a copy of one of Velikovsky's books, which, unlike so many other scientists(?), he was reading and taking very seriously. And, Mr. Birch, it is high time you learnt to read, as well. Velikovsky did *not* put forward the idea that hydrocarbons in ordinary comet tails would burst into flames when passing through the Earth's atmosphere. You have obviously taken your information second-hand from your guru Asimov (or was it Sagan?), and not bothered to do what any good scientist should do, i.e. check the data. Asimov (or Sagan), incidentally, in his (or his) latest book, states that if the world's rotation were to be stopped suddenly, then all loose ob-

jects would go flying off. Think about it, Mr. Birch BSc, then tell me again who is talking nonsense. Velikovsky didn't make silly mistakes like that. Asimov (and Sagan) make far too many.

And, by the way, I am not a gullible member of the non-scientific public. I am a qualified physicist and mathematician with twenty years' worth of experience in scientific research.

P. Warlow,
Brentwood.

Sir—Mr. Hyde in his reply to Mr. Austin (Spacewatch June 1980) that 'there is no difficulty in dealing with Velikovsky's claims' but in fact there has been little critical analysis by the scientific fraternity. Mr Hyde admits that when Velikovsky came into the academic eye he was very badly treated but that since then he has been given a fair hearing reaching a peak in 1974 at the AAA symposium. Is Mr Hyde aware of the nature of this symposium, of the original proposal and its terms of reference and how after reading his paper Carl Sagan pleaded a prior appointment to dash away before his arguments could be discussed? The prior appointment was an appearance on the Johnny Carson t.v. show.

I too would like to see a reasoned argument from Hyde for the rejection of Velikovsky's theory especially since Mr. Hyde has already produced many thousands of words on the subject. Dr. Velikovsky in 'Worlds in Collision' made reference to plagues in Egypt in the wake of a cometry upheaval and now we have a new book by Prof. Fred Hoyle and N. C. Wickramasinghe titled 'Diseases from Space' wherein they propound the theory that epidemics on earth are due to this planet encountering a cloud of micrometeorites. No mention is made of Velikovsky in the

Bibliography or the Index of this book and no doubt the authors claim it to be original work despite the 30 years since the publication of 'Worlds in Collision'.

Reading Velikovsky's book 'Earth in Upheaval' it will be apparent that notable scientists over the past two hundred years have investigated geological and archeological evidence indicating cataclysmic upheaval of recent origin completely at variance with astronomers' claims of an orderly and unchanging solar system. Velikovsky produced a synopsis to explain a possible cause of these catastrophes. Established astronomers sensed a threat and attempted to suppress the publication of Velikovsky's books. The bizarre often attracts the attention of a very large number of people (as Mr. Hyde in Spacewatch April 1980 states) but then such publications do not arouse among the Scientific Establishment the furore that accompanied the publication of 'W in C'.

The ultimate (in the August issue) belongs to David Birch who quotes his B.Sc to show that he is not a member of the 'gullible non-scientific public'. Original thought is obviously not necessary in attaining such qualification and indeed could be a handicap. If Mr. Birch were a little less vitriolic in his condemnation of Velikovsky relying less on copying Dr. Asimov's 'fascinating essays' but rather forming his own opinion after reading Velikovsky's books then his letter might be taken seriously.

Sorry point not taken.

R. K. G. Williams,
Sutton Coldfield.

Sir—Many thanks for the opportunity to reply to the Letters published in your magazine in response to my communication on the theories of Velikovsky. I am sure that the tone of the letters, which both came from ardent pro-Velikovskians and spent more time niggling at me than defending against my criticisms, has served only to convince your readers that there is as little in Velikovsky's theories as they suspected. Both writers seem to think that my qualifications in Physics make me less able than them to talk on the subject and both infer that if I only read WinC I would be instantly converted to their way of thinking. Well, I have read it—I have also read most of the works of Von Daniken and the brothers Grimm. I enjoyed all but believed none.

Your readers may also wonder why one of the writers makes a sneering reference at an out of context quote from a book which he read so intently that he was unable to remember whether it was by Dr. Asimov or Carl

Sagan (both of whom are distinguished scientists and writers). The quote concerns a sudden halt in the rotation of the Earth. Why? Well, another of Velikovsky's claims is that the comet Venus stopped the Earth rotating, hence accounting for the story of Joshua in the bible. Now, the Earth is rotating at several kilometres per second. Should this rotation suddenly cease, Joshua and his soldiers (and all other loose objects) would continue moving at this speed! Furthermore, the Earth's energy of rotation would be dissipated as heat melting the Earth's crust!

Nonsense? I think Velikovsky supplies enough for all of us.

David G. W. Birch,
Swindon.

Owing to a lack of space, Frank Hyde's reply will appear in the next issue. This correspondence is now closed.

Metal Detector

Sir—Following the publication of my metal detector circuit in Ingenuity Unlimited in the April 1980 issue of *PE*, a number of would-be treasure hunters have contacted me with problems regarding the operation of the unit. It appears that many constructors have found that the metal detector produces a continuous tone which cannot be defeated by the adjustment of VR1.

This has been found to be due to large leakage currents in C8 when an aluminium electrolytic is used, producing a large offset voltage at the inputs of IC1, which is outside the offset null range of VR1. A tantalum capacitor therefore MUST be used for C8. If offset problems are still encountered, then R10 could be reduced to 560k to increase the range of VR1.

Additionally, using a tantalum capacitor for C7 would tend to improve the stability, but it should not be considered essential as the prototype units were quite satisfactory with aluminium types.

P.R. Williams
Stevenage

Beyond BASIC

Sir—We are running a part-time 1 year course on the FORTH computer language, for Micro Computer enthusiasts who want to know 'what lies beyond BASIC?'.

To answer this question we are extending the kit building approach to software. Partici-

pants are asked to provide their own hardware. An 8K UK101 or any micro with equivalent facilities is suitable.

By courtesy of the Forth Interest Group the college is able to provide a language model and assembly listings for the 8080 Z80 6800 6809 and 6502. The aim of the course is to help participants install and program in, this very interesting language.

The course runs for 1 year on Wednesday afternoons, fees will be around £35.

Bill Stoddart,
Department of Science,
Willesden College of Technology,
London NW10

Marvellous Magnum

Sir—I must send praise to Mr. Andy Flind on his design of his metal locator. We have built two locators so far, both working first go with no problems (except the p.c.b. in the final article is not full size), with the possibility of another being built. Indeed, you now have three more regular readers.

On completion of the locator we spent most of the Bank Holiday using it. We used it over various terrain and modes, from our back garden to pebbles, sand, wet sand, rocks and salt water, and it worked every time and was stable. The only point of interest was that on our sandy beach the ground control became more critical. However, we have built various designs from b.f.o. to l.b. and no other locator has worked on that beach.

We have not as yet found a fortune, but we have located nails down to 9 inches, part of a gold ring 6 inches down, fishing weights down to 12 inches. Believe it or not we have located iron plates on the beach down to 3 feet, but became wary of these and discarded them. We have also discovered that it will pick up meteorites and stones containing iron, so beware.

We hope to get quite a bit of pleasure from this locator and indeed to recover some of the cost of making it. For interest the batteries are going low on our locators after approximately 50hrs use. But it is still working with the batteries down to 6V. The audio one isn't yet affected. I hope to see more publications from Mr. Flind. Please can you forward our thanks to him for a super design which is stable and works well. Also the step by step guide was a great help in construction, as well as the coil set up procedure.

I. West,
Newhaven, Sussex.



BOOK REVIEWS

INTEGRATED CIRCUITS

by R.G. Hibberd

Published by The Butterworth Group

112 pages 110 x 165 mm. Price £1.55

ANOTHER in the popular wide ranging 'questions and answers' series this book is aimed at helping anyone to understand something about these common devices.

It answers questions on fabrication technology and packaging. Introduces the various families; TTL, ECL, MOS, CMOS, digital, linear etc and concludes with a chapter on microprocessors.

The questions are shrewdly angled to produce portmanteau answers so that even in a few pages a great deal of information is contained.

No other field of engineering has progressed so fast or so far as that of integrated circuits and any practising engineer or technician in electronics who requires an introduction to this important subject will find in this a suitable introduction.

G. G.

See us on STAND 826,
Green Hall at INTERNEPCON

The Proto-Board®

Now circuit designing is as easy as pushing a lead into a hole . . .
No soldering
No de-soldering
No heat-spoilt components
No manual labour
No wasted time



For quick signal tracing and circuit modification
For quick circuit analysis and diagramming
With or without built-in regulated power supplies
Use with virtually all parts — most plug in directly, in seconds.
Ideal for design, prototype and hobby

NO	MODEL NO	NO OF SOLDERLESS TIE POINTS	IC CAPACITY (14 pin DIP's)	UNIT PRICE	PRICE INC P&P 15% VAT	OTHER FEATURES
1	PB 6	630	6	9.20	11.73	Kit
2	PB 100	760	10	11.80	14.72	Kit
3	PB 101	940	10	17.20	21.21	
4	PB 102	1240	12	22.95	27.83	
5	PB 103	2250	24	34.45	41.34	
6	PB 104	3060	32	45.95	54.56	
7	PB 203	2250	24	55.15	65.14	5V @ 1A
8	PB 203A	2250	24	74.70	87.63	5V ± 15V
9	PB 203AK	2250	24	59.00	69.57	5V ± 15V & Kit

Tomorrow's tools for today's problems

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 5U
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477

C.S.C. (UK) Ltd., Dept. 5U Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

1	Qty Req	2	Qty Req	3	Qty Req	4	Qty Req	5	Qty Req	6	Qty Req	7	Qty Req	8	Qty Req	9	Qty Req
---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard, Access,

American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The C.S.C. 24 hour 5 day a week service
Telephone (0799) 21682 and give us your Barclaycard, Access,
American Express number and your order will be in the post immediately

For FREE catalogue
tick box



...An issue you can't afford to miss

To avoid disappointment place an order with your newsagent now.

ENGINE TUNE-UP UNIT



A versatile digital bench test instrument that measures Volts, Amps, Ohms, Dwell, RPM.

Thus providing accurate information for engine tuning.



INDEX...

Complete Volume 16 (1980) index with cross referencing for Constructional Projects, also lists all I.U.s, Points Arising, news, features, etc.

In Car Entertainment Offer...

A very special offer for PE readers on an AM/FM stereo radio/cassette player or two different stereo cassette players and a choice of three types of speaker. All at prices that will blow your mind.

Master Rhythm... Programmable rhythm generators can now produce very realistic and versatile imitations of percussion instruments. Next month we commence construction details of an up-to-the-minute design that compares with anything commercially available.

Plus... FREE with all U.K. copies

The Electrovalue catalogue; 68 pages packed full of products from this well known supplier.

PRACTICAL

ELECTRONICS

OUR DECEMBER ISSUE WILL BE ON SALE FRIDAY, 14 NOVEMBER 1980

Special RECORD DECK

Offer

£24 EACH



**INCLUDING STEREO MAGNETIC CARTRIDGE and V.A.T
POSTAGE £2.50 for ONE or £3.75 for TWO DECKS**

To tie up with our *Disco Desk* series PE has been able to arrange a special offer on these BSR decks either singly or in pairs. The decks are also excellent for use with general purpose audio systems.

THE DECK

- ★ **BSR P182**
- ★ **Fitted ADC, QLM 30 Mk III stereo magnetic cartridge**
- ★ **Automatic cueing for 7, 10 or 12 inch records**
- ★ **Manual cue lever with viscous damping in both directions**
- ★ **S shaped pick-up arm with counter balance weight**
- ★ **3 speed with idler wheel drive**
- ★ **Automatic and manual pick-up arm clip**
- ★ **Dynamically balanced 4 pole motor**
- ★ **Flared aluminium turntable**
- ★ **Rumble > -29dB relative to 1000Hz at 1.2 cm/sec**
- ★ **Wow < 0.03% r.m.s. Flutter < 0.08% r.m.s.**
- ★ **Ready wired phono output sockets**
- ★ **240V 50Hz with 450mm (approx) long double insulated flying mains lead**
- ★ **Transit screws**
- ★ **Size approx 290 x 330mm**

To: RT-VC, 21B High Street, Acton, London W3 6NG

Mail order only

Please send me

	Deck/s
--	--------

One deck £24 plus £2.50 p&p (£26.50)
Two decks £48 plus £3.75 p&p (£51.75)

I enclose PO/Cheque No. Value

Name

Address

.....

.....

Please allow 28 days for delivery

OFFER CLOSSES FRIDAY NOVEMBER 14 1980

Name

Address

.....

.....

To: RT-VC, 21B High Street, Acton, London W3 6NG

Please complete both parts of the coupon in BLOCK CAPITALS

Buy a microcomputer for under £1,000 and you could be on your own! Unless it's a Commodore PET.



Commodore produce Britain's number one microcomputer. But we don't stop there. We also insist on providing comprehensive support throughout our national dealer network.

Our dealers can examine your needs and demonstrate which hardware and software will suit you best. Their trained engineers are always at hand and a 24-hour field maintenance service is available. Your local dealer can tell you more about the following Commodore Services.

C The Commodore PET

The Commodore PET computer range covers everything from the self-contained unit at under £500 to complete business systems at under £2,500.

C Commodore Business Software and Petpacks

Our software range covers hundreds of applications. Business software includes Sales and Purchase Ledgers, Accounting, Stock Control, Payroll, Word Processing and more. In addition over 50 Petpacks are available covering such titles as Strathclyde Basic Tutorial, Assembler Development System, Statistics, plus our Treasure Trove and Arcade series of games.

C Commodore Approved Products

Compatible products of other manufacturers with Commodore's mark of approval are also available.

C Commodore Courses

Commodore offer a range of residential training courses and one day seminars. An excellent start. And when you have installed your system the PET User's Club Newsletter can keep you informed of new ideas and latest developments.

LONDON AREA

Add Computers Ltd.
W5, 01-579 5845
Advanced Management Systems.
EC2, 01-638 9319
Bytshop Computerland,
W1, 01-636 0647
C.S.S. (Business Equipment) Ltd.
E8, 01-254 9293
Capital Computer Systems,
W1, 01-636 3863
Centralex-London Ltd.
SE13, 01-318 4213
Cream Microcomputer Shop,
HARROW, 01-863 0833
Da Vinci Computer Shop,
EDGWARE, 01-952 0526
L & J Computers,
NW9, 01-204 7525
Home and Business Computers.
E12, 01-472 5107
Merchant Systems Limited,
EC4, 01-353 1464
Metyclean Ltd.
SW1, 01-828 2511
Micro Computation,
N14, 01-882 5104
Micro Computer Centre,
SW14, 01-878 3206
Sumlock Bondain Ltd.
EC1, 01-250 0505
Sumlock Bondain Ltd.
EC4, 01-626 0487
T.L.C. World Trading Ltd.
WC2, 01-839 3894
TOPS TV Ltd.
SW1, 01-730 1795

HOME COUNTIES

G. M. Marketing,
ANDOVER, 790922
HSV Microcomputers,
BASINGSTOKE, 62444
MMS Ltd.
BEDFORD, 40601
Elex Systems Ltd.
BRACKNELL, 52929
DDM Direct Data Marketing Ltd.
BRENTWOOD, 229379
Amplicon Micro Systems Ltd.
BRIGHTON, 562163
RUF Computers (UK) Ltd.
BURGESS HILL, 45211
T & V Johnson (Microcomputers
Etc) Ltd, CAMBERLEY, 20446
Cambridge Computer Store,
CAMBRIDGE, 65334
Wego Computers Ltd.
CATERHAM, 49235
Dataview Ltd.
COLCHESTER, 78811
South East Computers Ltd.
HASTINGS, 426844
Alpha Business Systems,
HERTFORD, 57423
Brent Computer Systems,
KINGS LANGLEY, 65056
Isher-Woods Business Systems,
LUTON, 416202
South East Computers Ltd.
WALDSTONE, 681263
Micro Facilities Ltd.
MIDDLESEX, 01-979 4546
J. R. Ward Computers Ltd.
MILTON KEYNES 562850
Sumlock Bondain (East Anglia) Ltd.
NORWICH, 26259
T & V Johnson (Microcomputers
Etc) Ltd, OXFORD, 721461
H.S.V. Microcomputers,
SOUTHAMPTON, 22131
Super-Vision,
SOUTHAMPTON, 774023
Xitan Systems Ltd.
SOUTHAMPTON, 38740
Stuart R Dean Ltd.
SOUTHEND-ON-SEA, 62707
The Computer Room,
TUNBRIDGE WELLS, 41645
Orchard Electronics,
WALLINGFORD 35529

Petaltek Ltd.
WOKING, 63901
Oxford Computer Systems,
WOODSTOCK, 811976

MIDLANDS AND SOUTH HUMBERSIDE

Bytshop Computerland,
BIRMINGHAM, 622 7149
CPS (Data Systems) Ltd.
BIRMINGHAM, 707 3866
Camden Electronics,
BIRMINGHAM, 773 8240
Computer Services Midlands Ltd.
BIRMINGHAM, 382 4171
Catlans (Computers) Ltd.
BURTON-ON-TRENT, 812380
Ibek Systems,
COVENTRY, 86449
Jondane Associates Ltd.
COVENTRY, 664400
Davidson-Richards Ltd.
DERBY, 366803
Caddis Computer Systems Ltd.
HINKLEY, 613544
H.B. Computers,
KETTERING, 83922
Taylor-Wilson Systems Ltd.
KNOWLE, 6192
Machsize Ltd.
LEAMINGTON SPA, 312542
Office Computer Techniques Ltd.
LEICESTER, 28631
Lowe Electronics,
MATLOCK, 2817
Betos (Systems) Ltd.
NOTTINGHAM, 48108
Bytshop Computerland,
NOTTINGHAM, 40576
Keen Computers Ltd.
NOTTINGHAM, 583254
Tekdata Computing,
STOKE-ON-TRENT, 813631
Systems Micros,
TEL FORD, 460214
McDowell Knagges & Associates,
WORCESTER, 427077

YORKSHIRE AND NORTH HUMBERSIDE

Ackroyd Typewriter & Adding
Machine Co. Ltd, BRADFORD, 31835
Allen Computers,
GRIMSBY, 40568
Microware Computers Ltd.
HULL, 562107
Microprocessor Services,
HULL, 23146
Holdene Ltd.
LEEDS, 459459

South Midlands Communications Ltd.
LEEDS, 782326
Yorkshire Electronics Services Ltd.
MORLEY, 522181
Computer Centre (Sheffield) Ltd,
SHEFFIELD, 53519
Electronic Services,
SHEFFIELD, 668767
Hallam Computer Systems Ltd,
SHEFFIELD, 663125

NORTH EAST

Dyson Instruments,
DURHAM, 66937
Currie & Maughan,
GATESHEAD, 774540
Wards (Office Supplies) Group,
GATESHEAD, 605915
Elfton Ltd.
HARTLEPOOL, 61770
Fiddes Marketing Limited,
NEWCASTLE, 815157
Newcastle Computer Services,
NEWCASTLE, 615325
Format Micro Centre,
NEWCASTLE, 21093
Tripoint Associated Systems
Consultants Ltd,
SUNDERLAND, 73310

SOUTH WALES AND WEST CENTRE

Radan Computational Ltd,
BATH, 318483
Computer Corner,
SHREWSBURY, 59788
Bristol Computer Centre,
BRISTOL, 23430
C.S.S. (Bristol) Ltd.
BRISTOL, 779452
T & V Johnson (Microcomputers
Etc) Ltd, BRISTOL, 422061
Sumlock Tabdown Ltd.
BRISTOL, 26685
Sigma Systems,
CARDIFF, 34869
Office and Business Equipment
(Chester) Ltd, DEESIDE, 817277
A.C. Systems,
EXETER, 71718
Micro Media Systems,
NEWPORT, 59276
J.M. Computer Services Ltd.
NEWQUAY, 2863
Devon Computers,
PAIGNTON, 526303
J.A.D. Integrated Services,
PLYMOUTH 62616
Business Electronics,
SOUTHAMPTON, 738248
Computer Supplies (Swansea),
SWANSEA, 290047

NORTH WEST AND NORTH WALES

Tharstern Ltd.
BURNLEY, 38481
B + B (Computers) Ltd.
BOLTON, 26644
Preston Computer Centre,
PRESTON, 57684
Catlans (Computers) Ltd.
WILMSLOW, 527166

LIVERPOOL

Aughton Microsystems Ltd.
LIVERPOOL, 548 7788
B.E.C. Computers,
LIVERPOOL, 263 5738
Rockcliff Brothers Ltd,
LIVERPOOL, 521 5830

MANCHESTER AREA

Bytshop Computerland,
MANCHESTER, 236 4737
Computastore Ltd,
MANCHESTER, 832 4761
Cytex (U.K.) Ltd,
MANCHESTER, 872 4682
Executive Reprographic Ltd.
MANCHESTER, 228 1637
N.S.C. Computer Shops Ltd,
MANCHESTER, 832 2269
Sumlock Electronic Services
(Manchester) Ltd,
MANCHESTER, 834 4233
Professional Computer Services Ltd.
OLDHAM, 624 4065
D. Kipping Ltd,
SALFORD, 834 6367
Automated Business Equipment Ltd.
STOCKPORT, 061-432 0708

SCOTLAND

Holdene Microsystems Ltd.
EDINBURGH, 668 2727
Microcentre,
EDINBURGH, 556 7354
Aethrol Consultancy Services,
GLASGOW, 641 7758
Bytshop Computerland,
GLASGOW, 221 7409
Robox Ltd,
GLASGOW, 221 5401
Mac Micro,
INVERNESS, 712203
Thistle Computers,
KIRKWALL, 3140

IRELAND

Softsch Ltd.
DUBLIN, 784739
Medical & Scientific Computer
Services Ltd, LISBURN, 77533

To: Commodore Information Centre,
360 Euston Road, London W1 3BL. 01-388 5702

Please send me further information about the Commodore PET.

Name _____

Position _____


Address _____

Intended application _____

Do you own a PET? YES NO

commodore

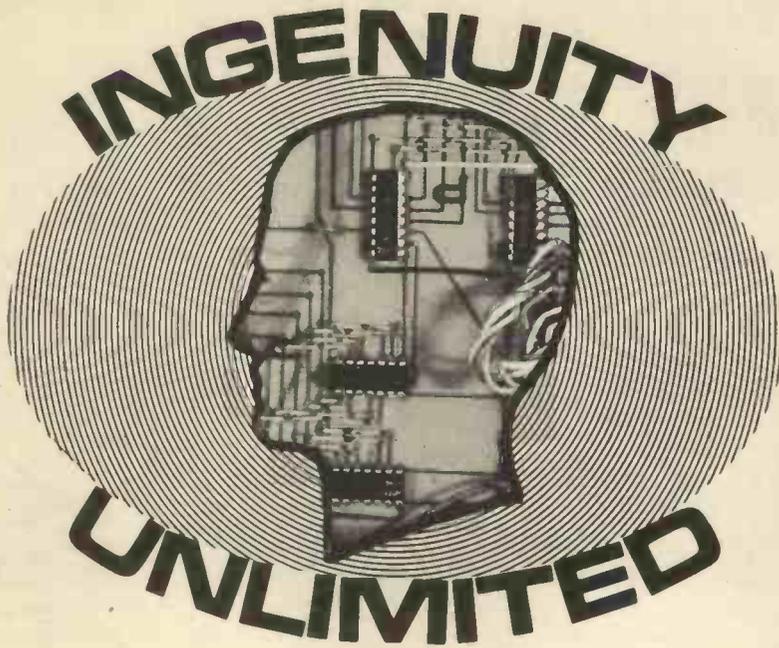This list covers dealers participating in our advertising.




A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere.

TTL LOGIC TESTER

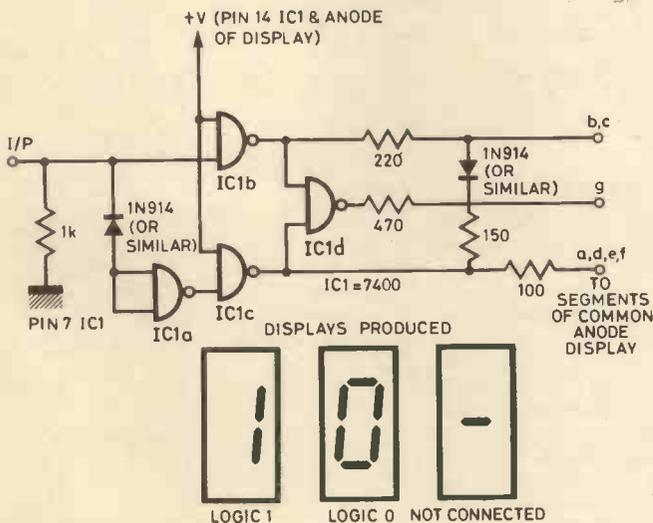

EA216

THIS circuit for yet another logic tester differs from others by instead of lighting one l.e.d. for logic 1 and another for logic 0, actually displaying a 1 or a 0 on a common anode seven-segment display:

When a pin is not connected or in tristate high impedance a dash is displayed. It utilises a single 7400 so if an "out-of-spec" display is obtained it can be built extremely cheaply. When the input is at 1 the output of IC1b goes low and segments b and c are lit. When the input is at 0 IC1c goes low and segments a, d, e, and f and b and c via the diode are lit. When the input is not connected and IC1b and c are high so IC1d goes low and segment g is lit. The prototype was constructed on a piece of Veroboard and put in a small plastic box with a window cut-out for the display. An old meter test lead was used for the probe. The +ve and ground must obviously be relatively low input impedance. The tester doesn't upset logic circuits unless they are on the very limit of fan-out. The circuit could probably be adapted for CMOS by using a 4011 (or 74C00) and increasing the 1k resistor accordingly.


A. C. Twist,
Leicester.

LIGHT TRIGGERED VARIABLE PULSE


THIS relatively simple circuit, gives a standard pulse output, whose duration can be set by VR2 and C2. Every time the light falling on the photodiode is interrupted, the voltage on pin 2 of IC1 falls, this is compared to the potential on pin 3, which is set by VR1, causing the output on pin 6 to go high, this pulse is shaped and buffered by the two Schmitt triggers, IC2a and IC2b. The NAND gate inverts this pulse, which is changed back to a positive pulse by IC2c, the high pulse from IC2b, also charges up C2 via VR2. On reaching the threshold of Schmitt IC2d, the output of IC2d goes low, this switches off the NAND gate, consequently limiting the duration of the output pulse.

In the prototype a 15 watt bulb at 2 feet. was used for the light source.

M. Miller,
Reading,
Berks.

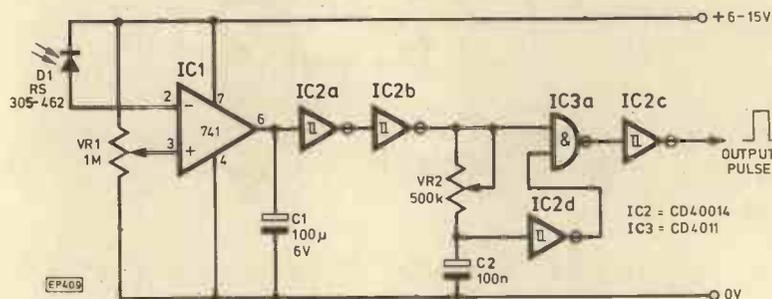

R/C FAILSAFE AND SERVO TESTER

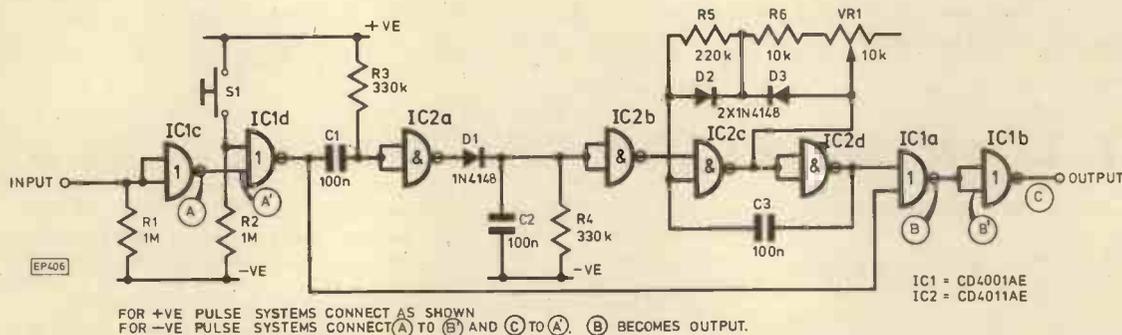

PROPORTIONAL R/C servos are controlled by pulses of 1 to 2ms which are repeated at approximately 20ms intervals. If through some malfunction of the transmitter or receiver these pulses are not present, this circuit, which is connected between the receiver and servo, detects this condition and activates its own pulse generator to drive the servo. The pulse generator is adjustable enabling the servo to be driven to any desired "fail safe" position e.g. throttle to low position. A push button is also provided to inhibit the normal pulse input so that the servo may be driven from the internal pulse generator for the purpose of testing. By a simple rearrangement of the input and output circuitry, versions suitable for positive or negative pulse R/C systems may be constructed.

The circuit shown, consists essentially of a monostable (IC2 a/b) driving a gated oscillator (IC2 c/d). An OR gate (IC1 a/b) driven by the oscillator and input signal via the input inhibitor (IC1 c/d) ensures that the output to the servo is provided from either the input signal or the gated oscillator. The monostable period is greater than 20ms, therefore, the normal pulse input keeps it in its triggered state (output low). This inhibits the operation of the oscillator, whose output also remains low, thus allowing the input pulses to pass through the OR gate to the output. Should the input pulses cease, the monostable output goes high and the oscillator is enabled. Diodes in the oscillator circuit give an asymmetrical output consisting of an adjustable 1 to 2ms pulse with a fixed 20ms interval, similar to the original input

pulses.

The circuit shown above is suitable for positive pulse R/C systems which are by far the most commonly used. For negative pulse R/C systems (e.g. Horizon) the pulse input is inverted before and after the circuit.

J. R. Shield,
Blaydon,
Tyne and Wear.

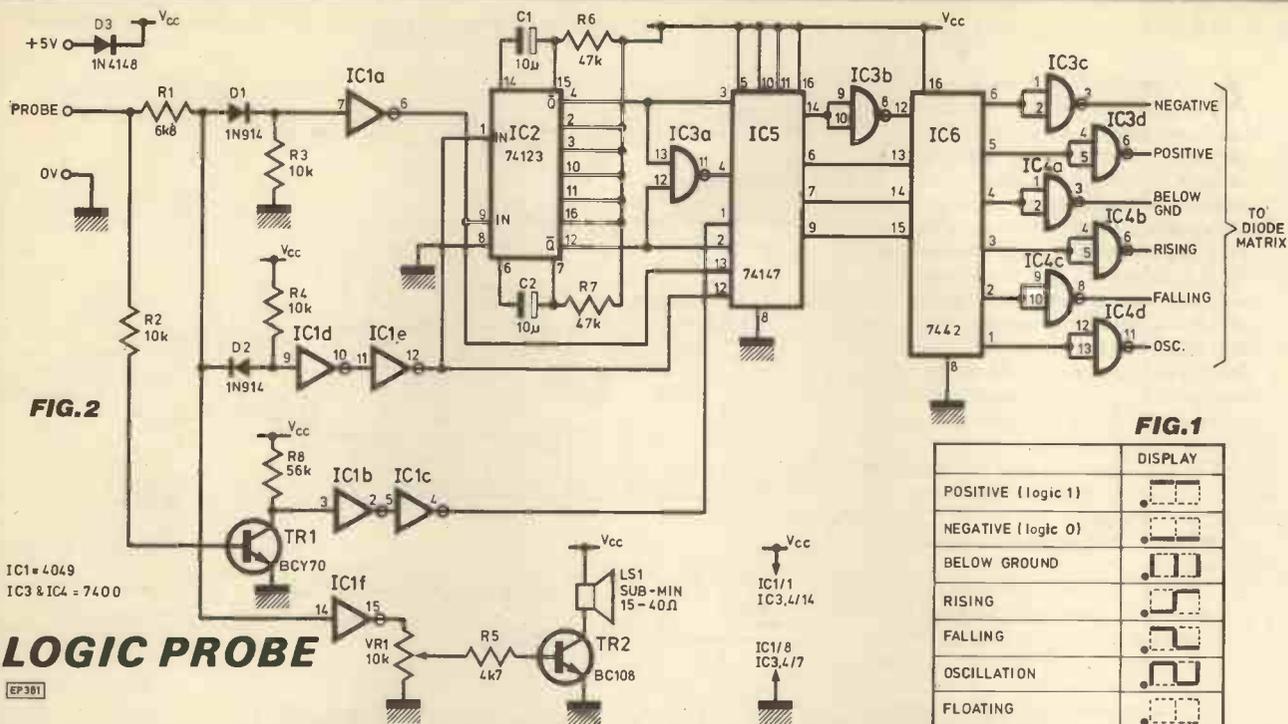


FIG. 2

IC1 = 7409
IC3 & IC4 = 7400

LOGIC PROBE

EP381

FIG. 1

	DISPLAY
POSITIVE (logic 1)	
NEGATIVE (logic 0)	
BELOW GROUND	
RISING	
FALLING	
OSCILLATION	
FLOATING	

THIS logic probe uses a seven segment display on its side to indicate, in an easy to understand way, the state of the probe (Fig. 1). The symbols were designed to look like the trace on an oscilloscope. The decimal point is used to indicate that the probe is on, the other segments are used as in Fig. 1, and the loudspeaker (LS1) is used to indicate the frequency of an oscillation (if it is audible). IC1f buffers the input to VR1 which acts as a volume control, TR2 amplifies the signal to LS1 which may need a series resistor if the speaker has a low resistance. The symbols were chosen as the probe was designed for fault finding on a microprocessor system with logic levels of +5V, 0V, and -12V. The circuit consists of three basic sections—detection, priority encoding (Fig. 2) and display encoding (Fig. 3).

The detection stage consists of several circuits each detecting a different thing—below ground detection is achieved by TR1 which is turned on by an input which is below 0V. If a different type of transistor is used R2 and R8 may need altering. When TR1 switches on, the output of IC1b goes high and the output of IC1c goes low. When the input is positive (logic


1) D1 conducts and the output of IC1a goes low. When the input is negative (logic 0), D2 conducts and the output of IC1e goes low. Transitions are detected by a 74123—IC2a, b wired up to detect falling edges and give an output pulse of approximately 1/2 a second. When the output of IC1a goes low (as the input rises to logic 1), IC2b is triggered, and its Q output (pin 12) goes low for 1/2 a second—indicating a rising edge. A similar thing happens when the input goes negative and the output of IC1e goes low triggering IC2b, indicating a falling edge. The time for which these symbols are displayed can be varied by altering R1, R2 or C1 and C2.

If the input goes low and high (rises and falls) within the 1/2 second for which the monostables are triggered, both Q outputs will be low and the output of IC3a will also go low indicating an oscillation. These signals cannot be fed straight to a display as several occur at the same time, e.g. for an oscillation to occur rising and falling must also be present. If these were fed straight to a display all three symbols would appear on top of each other. The priority encoding stage ensures that only one symbol is displayed at once. The

operation of this stage is shown tabled. IC5 a 74147 decimal to BCD converter and priority encoder—converts decimal inputs into BCD but only the highest decimal input is converted into BCD. From the table (below)—the signal with the highest priority is oscillation with a decimal value of 7. The 74147 has inverted outputs, so 7 in inverted BCD is 1,000 (on pins 9, 7, 6 and 14 of IC5). As IC6 does not have inverted inputs the signals are swapped over—oscillation decimal 7 on IC5 becomes decimal 0 to IC6. The outputs of IC6 are inverse so they need inverting by IC4a, b, c, d and IC3c, d.

These signals are fed to the diode matrix (D4—D18) which generates the required symbol (Fig. 1). The display is a common cathode type used on its side. The decimal point is connected to Vcc through a 330 resistor. The i.c.s are protected against reversed supply connection by D3. The complete probe was built into a small box with three sockets on the top for +5V, ground and probe.


I. Mercer,
Loughborough,
Leicestershire.

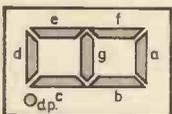

ARRANGEMENT OF SEGMENTS

FIG. 3

Detection Signal	IC5 pin	IC5 dec. i/p	IC5 BCD DCBA	After IC3b DCBA	IC6 pin	IC6 dec. o/p
Oscillation	4	7	1000	0000	1	0
Falling edge	3	6	1001	0001	2	1
Rising edge	2	5	1010	0010	3	2
Below ground	1	4	1011	0011	4	3
Positive	13	3	1100	0100	5	4
Negative	12	2	1101	0101	6	5

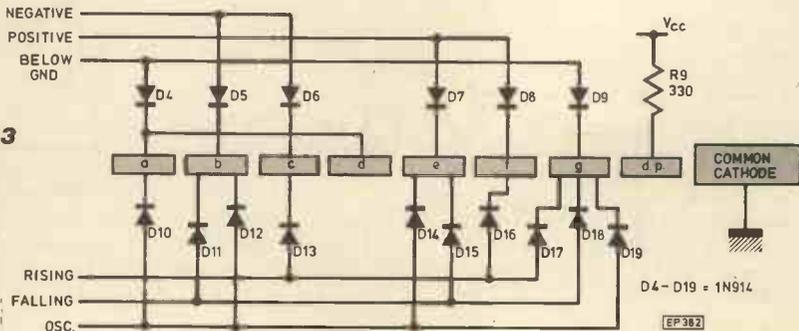

D4—D19 = 1N914


EP382

A 1Hz oscillator feeds an EX-OR gate directly, and via the op-amp under test, connected as an inverter. The gate output will be high only if the two inputs disagree (i.e. antiphase). A green l.e.d. indicates the condition while the red l.e.d. shows up agreement. The tester is powered by a single 9V battery with two Zeners giving a split supply. The c.m.o.s. gates use 4.3 volts for V_{DD} and -4.3 volts for V_{SS} . A 4093 quad NAND Schmitt is used as the 1Hz oscillator and l.e.d. drivers. A 4030 quad EX-OR is used as the phase detector. The op-amp is plugged into a test socket, which may be patched if desired for non-standard pinouts.

- Op-amp functioning: A and B are antiphase, C is high, green on, red off.
- Op-amp open circuit: A and B are in phase, C is low, green l.e.d. off, red l.e.d. on.
- Op-amp stuck at fixed level: A and B alternately agree and disagree, C oscillates at 1Hz, l.e.d.s flash alternately. On switch on the red l.e.d. will light first if the op-amp is stuck above ground and conversely if below ground.

S. Callaghan,
Gt. Baddow,
Essex.

OP-AMP TESTER

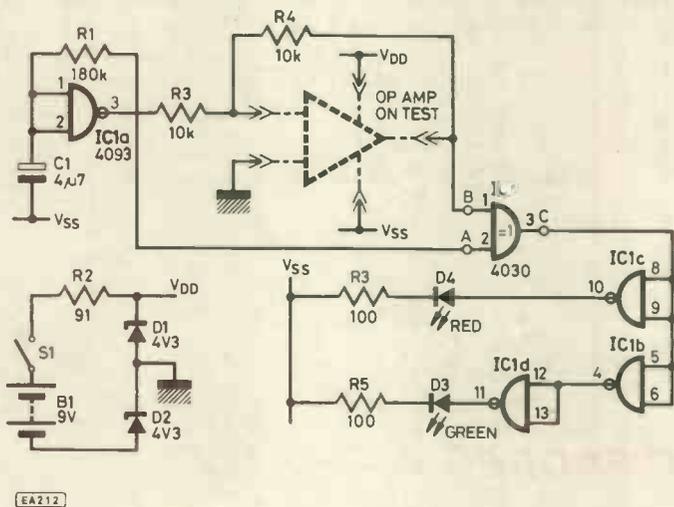

EA212

THIS circuit is similar to the PE version a couple of years ago.

Fig. 1 is basically an electronic game, using l.e.d.s and a decade counter divider i.c., the clock frequency of which is obtained from a two NAND gates (IC2) oscillator. The l.e.d.s should be arranged in sequence, so that when l.e.d. 5 (pin 1, IC2) is logic 1 and S1 is pressed, the clock is stopped or inhibited by the gate output of IC2 (c).

Cheats who press the button before l.e.d. 5 illuminates, find the sequence resetting at 3 until SW1 is released.


An alternative "Fire" button arrangement using one single throw push switch and an extra i.c. is shown in Fig. 2.

Completely disconnect R5 and replace this circuit in between xx and yy.

The speed of the oscillator can be changed by varying the values of C1 and R2.


L. Privett,
Barking,
Essex.

SHOOT GAME

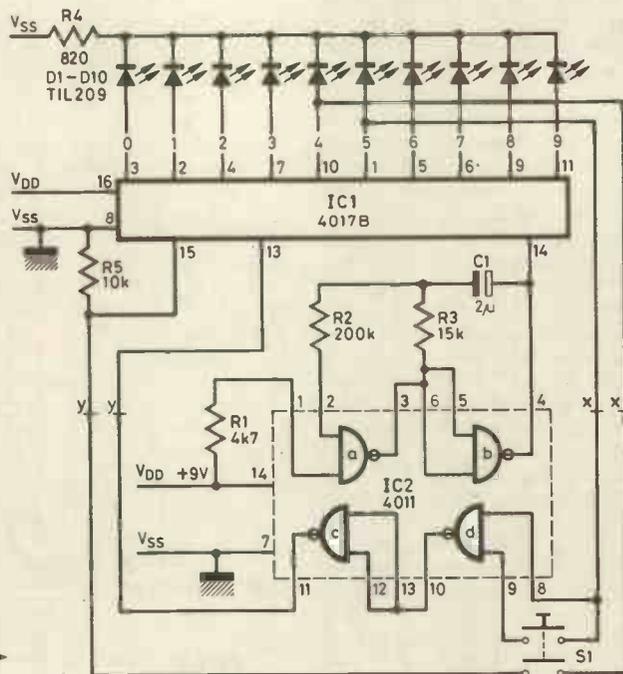

EA211

Fig. 1

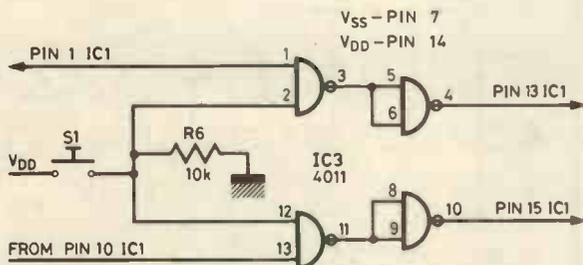

EA217

Fig. 2

TRANSISTORS

74 SERIES TTL ICs

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	£0.25	BC134	£0.21	BD178	£0.78	BF79	£0.12	ZTX109	£0.22	2N3416	£0.33	7400	£0.10
AC113	£0.23	BC135	£0.17	BD179	£0.86	BF80	£0.32	ZTX300	£0.14	2N3417	£0.33	7401	£0.13
AC115	£0.23	BC136	£0.21	BD180	£0.86	BF82	£0.25	ZTX301	£0.14	2N3614	£1.15	7402	£0.13
AC117	£0.35	BC137	£0.21	BD181	£0.98	BF83	£0.35	ZTX302	£0.18	2N3615	£1.21	7403	£0.13
AC117K	£0.39	BC139	£0.37	BD182	£1.04	BF84	£0.25	ZTX303	£0.18	2N3616	£1.21	7404	£0.13
AC121	£0.23	BC140	£0.35	BD183	£1.09	BF85	£0.28	ZTX304	£0.23	2N3646	£0.10	7405	£0.13
AC122	£0.16	BC141	£0.32	BD184	£1.27	BF86	£0.29	ZTX305	£0.17	2N3702	£0.09	7406	£0.25
AC125	£0.23	BC142	£0.25	BD185	£0.78	BF87	£0.25	ZTX500	£0.15	2N3703	£0.09	7407	£0.25
AC126	£0.23	BC143	£0.25	BD186	£0.78	BF88	£0.25	ZTX501	£0.14	2N3704	£0.08	7408	£0.23
AC127	£0.23	BC145	£0.53	BD187	£0.86	BF90	£0.43	ZTX502	£0.18	2N3705	£0.12	7409	£0.15
AC128	£0.22	BC147	£0.08	BD188	£0.86	BF90	£0.20	ZTX503	£0.14	2N3706	£0.09	7410	£0.13
AC128K	£0.30	BC148	£0.08	BD189	£0.90	BF91	£0.20	ZTX504	£0.29	2N3707	£0.09	7411	£0.20
AC132	£0.23	BC149	£0.08	BD190	£0.90	BF92	£0.20	ZTX531	£0.29	2N3708	£0.08	7412	£0.17
AC134	£0.23	BC150	£0.23	BD195	£1.04	BF93	£0.18	ZTX550	£0.18	2N3708A	£0.08	7413	£0.28
AC137	£0.23	BC151	£0.25	BD196	£1.04	BF90	£0.95	2N3880	£0.41	2N3709	£0.08	7414	£0.58
AC141	£0.25	BC152	£0.25	BD197	£1.09	BF19	£0.44	2N388A	£0.64	2N3710	£0.08	7415	£0.25
AC141K	£0.35	BC153	£0.29	BD198	£1.09	BF20	£0.44	2N404	£0.23	2N3711	£1.84	7416	£0.26
AC142	£0.42	BC154	£0.22	BD199	£1.14	BF19/20	£0.92	2N524	£0.46	2N3772	£1.84	7420	£0.23
AC142K	£0.35	BC157	£0.12	BD200	£1.14	BSX25	£1.67	2N527	£0.58	2N3773	£2.53	7421	£0.23
AC151	£0.23	BC158	£0.12	BD201	£0.92	BSX19	£0.21	2N598	£0.46	2N3819	£0.21	7422	£0.18
AC153	£0.25	BC159	£0.12	BD202	£0.92	BSX20	£0.21	2N599	£0.53	2N3820	£0.40	7423	£0.24
AC153K	£0.35	BC160	£0.30	BD201/2	£1.96	BSY25	£0.18	2N698	£0.15	2N3821	£0.69	7424	£0.23
AC155	£0.23	BC161	£0.14	BD203	£0.92	BSY26	£0.18	2N697	£0.14	2N3823	£0.89	7426	£0.26
AC155K	£0.23	BC162	£0.14	BD204	£0.92	BSY28	£0.18	2N699	£0.37	2N3904	£0.12		
AC156	£0.23	BC168	£0.14	BD204	£0.92	BSY28	£0.18	2N699	£0.37	2N3904	£0.12		
AC157	£0.23	BC169	£0.10	BD203/3	£0.90	BSY29	£0.18	2N708	£0.12	2N3905	£0.12		
AC165	£0.23	BC169C	£0.12	BD204	£1.96	BSY29	£0.18	2N708	£0.12	2N3905	£0.12		
AC167	£0.23	BC170	£0.10	BD205	£0.92	BSY38	£0.22	2N707	£0.55	2N4058	£0.14		
AC167K	£0.23	BC171	£0.10	BD206	£0.92	BSY40	£0.33	2N706	£0.16	2N4059	£0.16		
AC168	£0.23	BC172	£0.10	BD207	£0.92	BSY41	£0.33	2N711	£0.35	2N4060	£0.16		
AC169	£0.23	BC173	£0.10	BD208	£0.90	BSY51	£0.29	2N717	£0.35	2N4061	£0.14		
AC171	£0.29	BC174	£0.17	BD222	£0.90	BSY95	£0.15	2N718	£0.29	2N4062	£0.14		
AC176	£0.23	BC175	£0.40	BD225	£0.54	BSY98	£0.15	2N718A	£0.52	2N3901	£0.92		
AC176K	£0.30	BC178	£0.18	BD232	£0.53	BRY39	£0.82	2N726	£0.33	2N4923	£0.75		
AC178	£0.29	BC179	£0.18	BD233	£0.55	BU105	£1.84	2N727	£0.33	2N5135	£0.25		
AC179	£0.29	BC179	£0.18	BD234	£0.63	BU105/02	£2.24	2N743	£0.23	2N5136	£0.12		
AC180	£0.23	BC180	£0.29	BD235	£0.63	BU204	£1.81	2N744	£0.23	2N5138	£0.12		
AC180K	£0.32	BC181	£0.10	BD236	£0.67	BU205	£1.81	2N744	£0.23	2N5138	£0.12		
AC182	£0.32	BC182	£0.10	BD237	£0.67	BU206	£1.81	2N744	£0.23	2N5138	£0.12		
AC181K	£0.32	BC182L	£0.10	BD238	£0.89	BU208/02	£2.59	2N929	£0.17	2N5272	£0.46		
AC187	£0.21	BC183	£0.10	BD239A	£0.58	MJE2955	£1.04	2N930	£0.21	2N5294	£0.39		
AC187K	£0.32	BC183L	£0.10	BD240A	£0.58	MJE3055	£0.69	2N946	£0.46	2N5296	£0.41		
AC188	£0.21	BC184	£0.10	BDX32	£2.53	MJE3440	£0.60	2N1131	£0.21	2N5457	£0.37		
AC188K	£0.32	BC184L	£0.10	BDY11	£1.50	MPB113	£0.60	2N1132	£0.21	2N5458	£0.37		
AC190	£0.40	BC186	£0.25	BDY17	£2.07	MPF102	£0.32	2N1302	£0.17	2N5459	£0.40		
AC191	£0.40	BC187	£0.25	BDY20	£0.92	MPF104	£0.40	2N1303	£0.21	2N5551	£0.41		
AC191K	£0.40	BC187	£0.25	BDY20	£0.92	MPF105	£0.40	2N1304	£0.21	2N6027	£0.39		
AC192	£0.40	BC187	£0.25	BDY20	£0.92	MPSA00	£0.23	2N1305	£0.21	2N6121	£0.81		
AC192K	£0.40	BC187	£0.25	BDY20	£0.92	MPSA06	£0.23	2N1306	£0.29	2N6122	£0.81		
AC193	£0.40	BC187	£0.25	BDY20	£0.92	MPSA55	£0.23	2N1307	£0.29	2S301	£0.49		
AC194	£0.40	BC187	£0.25	BDY20	£0.92	MPSA56	£0.23	2N1308	£0.35	2S302	£0.49		
AC195	£0.40	BC187	£0.25	BDY20	£0.92	MD120	£0.21	2N1309	£0.35	2S302A	£0.49		
AC196	£0.40	BC187	£0.25	BDY20	£0.92	OC20	£2.13	2N1599	£0.40	2S303	£0.64		
AC197	£0.40	BC187	£0.25	BDY20	£0.92	OC22	£1.73	2N1613	£0.23	2S403	£0.82		
AC198	£0.40	BC187	£0.25	BDY20	£0.92	OC23	£1.73	2N1711	£0.23	2S305	£0.92		
AC199	£0.40	BC187	£0.25	BDY20	£0.92	OC25	£1.15	2N1890	£0.52	2S307	£0.92		
AC200	£0.40	BC187	£0.25	BDY20	£0.92	OC25	£1.15	2N1890	£0.52	2S307	£0.92		
AC201	£0.40	BC187	£0.25	BDY20	£0.92	OC26	£1.15	2N1893	£0.35	2S321	£0.66		
AC202	£0.40	BC187	£0.25	BDY20	£0.92	OC28	£0.92	2N1247	£0.86	2S322	£0.66		
AC203	£0.40	BC187	£0.25	BDY20	£0.92	OC29	£1.09	2N1248	£0.81	2S322A	£0.66		
AC204	£0.40	BC187	£0.25	BDY20	£0.92	OC35	£1.04	2N2160	£0.08	2S323	£0.66		
AC205	£0.40	BC187	£0.25	BDY20	£0.92	OC35	£1.04	2N2160	£0.08	2S323	£0.66		
AC206	£0.40	BC187	£0.25	BDY20	£0.92	OC41	£0.23	2N193	£0.44	2S325	£0.80		
AC207	£0.40	BC187	£0.25	BDY20	£0.92	OC42	£0.25	2N194	£0.44	2S326	£0.80		
AC208	£0.40	BC187	£0.25	BDY20	£0.92	OC44	£0.28	2N2217	£0.25	2S327	£0.82		
AC209	£0.40	BC187	£0.25	BDY20	£0.92	OC45	£0.23	2N2218	£0.26	40311	£0.42		
AC210	£0.40	BC187	£0.25	BDY20	£0.92	OC70	£0.28	2N2218A	£0.23	40313	£1.09		
AC211	£0.40	BC187	£0.25	BDY20	£0.92	OC72	£0.28	2N219A	£0.28	40316	£1.09		
AC212	£0.40	BC187	£0.25	BDY20	£0.92	OC74	£0.30	2N2220	£0.23	40317	£0.46		
AC213	£0.40	BC187	£0.25	BDY20	£0.92	OC75	£0.35	2N2221	£0.23	40326	£1.09		
AC214	£0.40	BC187	£0.25	BDY20	£0.92	OC76	£0.40	2N2221A	£0.25	40327	£0.52		
AC215	£0.40	BC187	£0.25	BDY20	£0.92	OC77	£0.58	2N2222	£0.23	40346	£0.52		
AC216	£0.40	BC187	£0.25	BDY20	£0.92	OC81	£0.25	2N222A	£0.28	40347	£0.75		
AC217	£0.40	BC187	£0.25	BDY20	£0.92	OC82	£0.28	2N2368	£0.21	40348	£0.92		
AC218	£0.40	BC187	£0.25	BDY20	£0.92	OC83	£0.28	2N2369	£0.16	40380	£0.41		
AC219	£0.40	BC187	£0.25	BDY20	£0.92	OC82D	£0.35	2N2369A	£0.18	40382	£0.44		
AC220	£0.40	BC187	£0.25	BDY20	£0.92	OC83	£0.30	2N2411	£0.29	40406	£0.52		
AC221	£0.40	BC187	£0.25	BDY20	£0.92	OC84	£0.44	2N2412	£0.29	40407	£0.40		
AC222	£0.40	BC187	£0.25	BDY20	£0.92	OC139	£0.92	2N2646	£0.54	40408	£0.60		
AC223	£0.40	BC187	£0.25	BDY20	£0.92	OC140	£0.92	2N2711	£0.25	40409	£0.88		
AC224	£0.40	BC187	£0.25	BDY20	£0.92	OC169	£0.40	2N2712	£0.25	40410	£0.88		
AC225	£0.40	BC187	£0.25	BDY20	£0.92	OC170	£0.40	2N2714	£0.25	40411	£0.88		
AC226	£0.40	BC187	£0.25	BDY20	£0.92	OC201	£0.40	2N2904	£0.21	40430	£1.09		
AC227	£0.40	BC187	£0.25	BDY20	£0.92	OC200	£0.44	2N2904A	£0.24	40436	£0.84		
AC228	£0.40	BC187	£0.25	BDY20	£0.92	OC201	£1.09	2N2905	£0.21	40494	£0.81		
AC229	£0.40	BC187	£0.25	BDY20	£0.92	OC202	£1.38	2N2905A	£0.23	40495	£0.92		
AC230	£0.40	BC187	£0.25	BDY20	£0.92	OC203	£0.98	2N2906	£0.18	40512	£1.59		
AC231	£0.40	BC187	£0.25	BDY20	£0.92	OC204	£1.04	2N2906A	£0.22	40534	£1.04		
AC232	£0.40	BC187	£0.25	BDY20	£0.92	OC205	£1.32	2N2907	£0.23	40591	£1.27		
AC233	£0.40	BC187	£0.25	BDY20	£0.92	OC206	£0.33	2N2907A	£0.25	40596	£1.27		
AC234	£0.40	BC187	£0.25	BDY20	£0.92	OC207	£0.40	2N2923	£0.17				

Send your orders to:—
DEPT PE11, PO BOX 6, WARE, HERTS. Tel 0920-3182
 Visit our NEW shop: **3 BALDOCK ST., WARE HERTS. Tel: 817861**

BOOKS BY BABANI

BOOK NO	DESCRIPTION	£ P
BP6	Engineers & Machinists Ref. Tables	0.75
BP14	2nd Book Transistor Equivs & Subs	1.10
BP24	52 Projects Using IC741 (or equiv)	0.95
BP26	Radio Antenna Book Long Distance Reception & Transmission	1.00
BP27	Giant Chart of Radio Electronic Semi-conductor & Logic Symbols	0.60
BP32	Build Metal & Treasure Locators	1.00
BP34	Practical Repair & Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Preamplifier	1.25
BP36	50 Ccts use Germ/Sil/Zener Diodes	1.25
BP37	50 Projects using Relays / SCRs / Triacs	1.25
BP39	50 Field Effect Trans Projects	1.25
BP40	Digital IC Equivs & Pin Connection	2.50
BP41	Linear IC Equivs & Pin Connection	2.75
BP43	How to make Walkie Talkies	1.50
BP44	IC555 Projects (Revised & Enlarged Edition)	1.75
BP45	Projects on Opto-electronics	1.25
BP46	Radio Circuits using ICs	1.35
BP47	Mobile Discotique Handbook	1.35
BP48	Electronics Projects for Beginners	1.35
BP49	Popular Electronic Projects	1.45
BP50	IC LM3900 Projects	1.35
BP51	Electronic Music & Creative Tape Recording	1.25
BP52	Long Distance Television Reception (TV-DX) For the Enthusiast	1.95
BP53	Practical Electronic Calculations & Formulas	1.35
BP55	Radio Stations Guide	1.45
BP56	Electronic Security Devices	1.45
BP57	How to Build Your Own Solid State Oscilloscope	1.50
BP58	50 Circuits using 7400 Series ICs	1.35
BP59	Second Book of CMOS IC Projects	1.50
BP60	Practical Construction of Pre-amps / Tone Controls / Filters & Attn	1.45
BP61	Beginners Guide to Digital Techniques	0.95
BP62	Elements of Electronics — Book I	2.25
BP63	Elements of Electronics — Book II	2.25
BP64	Elements of Electronics — Book III	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors & Computing	1.75
BP67	Counter driver & numeral Display projects	1.75
BP68	Choosing & Using your Hi-Fi	1.85
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.50
BP160	Call Design & Construction Manual	0.75
BP202	Handbook of Integrated Circuits Equivs & Substitutes	1.00
BP211	First Book of Diode Characteristics & Equivalents & Substitutes	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP215	Showpage Circuits & Gear for Experimenters & Radio Hams	0.85
BP221	28 Tested Transistor Projects	1.25
BP224	50 CMOS IC Projects	0.95
BP226	Build Advanced Short wave receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
RCC	Resistor Colour Code Disc	0.20

BRACKETS

Right-angle mounting brackets. Ideal for mounting PCB panels at cetera into boxes and cases.
 18SWG — Mild steel — short face has slotted hole 6.5cm x 3.7cm long face has 3.7cm diam. hole
 O/N0.1726 Height 15cm, length 15cm, width 10cm £0.06
 O/N0.1727 Height 25cm, length 15cm, width 10cm £0.07

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.16
DPDT standard slide	1974	£0.17
Toggle switch SPST 1 1/2 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on-off mains switch	1977	£0.88
Push switch — Push to make	1978	£0.16
Push switch — Push to break	1979	£0.21

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST — moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.35
	BLACK	1981	£0.35
	WHITE	1982	£0.35
	BLUE	1983	£0.35
	YELLOW	1984	£0.35
	LUMINOUS	1985	£0.35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.81
Miniature SPST toggle 2 amp 250V ac	1959	£0.86
Miniature DPDT toggle 2 amp 250V ac	1960	£0.92
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.09
Push-button SPST 2 amp 250V ac	1962	£1.04
Push-button SPST 2 amp 250V ac	1963	£1.09
Push-button DPDT 2 amp 250V ac	1964	£1.38

MIDGET WAFER SWITCHES
 Single back water type — suitable for switching at 250V ac 100mA or 150V dc in non-reactive loads make-break-contact. These switches have a spindle 0.25 in dia and 30 indexing

Description	No.	Price
1 pole 12 way	1985	£0.55
2 pole 6 way	1986	£0.55
3 pole 4 way	1987	£0.55
2 pole 3 way	1988	£0.55

MICRO SWITCHES	No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac	1970	£0.29

OPTOELECTRONICS

NEW INCREASED RANGE—ALL 1ST QUALITY LEDS (diffused)

O/N0. Type	Size	Colour	Price
1501 ARL209 (TIL209)	3mm (-125)	RED	£0.12
1502 MIL3232 (TIL211)	3mm (-125)	GREEN	£0.22
1503 MIL3331 (OPL212A)	3mm (-125)	YELLOW	£0.22
1504 ARL4850 (FLV117)	5mm (-2)	RED	£0.12
1505 MIL5251 (TIL222)	5mm (-2)	GREEN	£0.22
1506 MIL5351 (MV5353)	5mm (-2)	YELLOW	£0.22
1509 FLV111	5mm (-2)	CLEAR (ill. Red)	£0.13

SUPER 'HI BRITE' TYPE	Size	Price
1521 MIL32	3mm (-125)	£0.12
1522 MIL52	5mm (-2)	£0.12
1514 ORP12	Light dependent resistor	£0.63
1520 OCP71	Photo transistor	£0.40

LED CLIPS	Price
1508/125 pack of 5 125 clips	£0.17
1508/2 pack of 5 2 clips	£0.21

DISPLAYS	Price
DL703 7 segment D P left (30° height) Common Anode	£0.85
RED Single Digit Common Anode	O/N0. 1523
DL707 7 segment D P left (30° height) Common Anode	O/N0. 1510
RED Single Digit Common Anode	O/N0. 1510
DL527 7 segment D P left (50° height) Common Anode	O/N0. 1524
RED Two-Digit Reflector Common Anode	O/N0. 1524
DL727 7 segment D P right (~10° height) Common Anode	O/N0. 1512
RED Two-Digit Light Pipe Common Anode	O/N0. 1512
DL747 7 segment D P left (630° height) Common Anode	O/N0. 1511
RED Single Digit Light Pipe	O/N0. 1511

OPTO-ISOLATORS

Isolation Breakdown—Voltage 1500—continuous fwd. current 100 mA

CL174 Single Channel 6 pin DIP standard type—optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor	O/N0. 1497	£0.61
CL174 Multi-Channel B pin DIP Two Isolated Channels	O/N0. 1498	£1.22
CL174 Multi-Channel 16 pin DIP Four Isolated Channels	O/N0. 1499	£2.69

MELL II (TIL81) NPN LIGHT DETECTOR
 Silicon Photo Darlington Amplifier—VCC0 30V VECO 10V Ic 100mA Ptot 300mW Lin. Min. 0-5 Typ 2mA Id 100mA nA O/N0. 1495 £0.29

WIRE CONNECTORS

Entirely new range of connectors for discrete wire. Uniquely designed Wirepost is soldered to the P.C. Board. A pre-stopped wire is inserted into the connector and easily locked by pressing the housing down. The wire is alternatively removed by lifting the housing. Tin alloy plated contacts ensure good as gold performance.

1728 Single connector in red/black or white	£0.12 inc. VAT
1729 Three-way connector black ONLY	£0.23 inc. VAT
1730 Four-way connector black ONLY	£0.28 inc. VAT

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0.18
1 1/2in x 1/2in chassis mounting	507	£0.14
1 1/2in car inline type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1 1/2in	510	£0.37

QUICK BLOW 20mm	Type	No.	Price
150mA 611 7p	1A	615	6p
250mA 612 6p	1.5A	616	7p
550mA 613 6p	2A	617	6p
800mA 614 8p	2.5A	618	7p

ANTI-SURGE 20mm	Type	No.	Price
150mA 622 1A	625	3A	619 6p
250mA 623 2A	626	4A	620 10p
500mA 624 1.6A	627	5A	621 6p

QUICK-BLOW 1 1/2in	Type	No.	Price
250mA 631	500mA	632	800mA 634

NUTS AND BOLTS

BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50	Type	No.	Price
1in 08A	839	1 1/2in 48A	846
1 1/2in 08A	840	2in 48A	847
1in 28A	842	2 1/2in 68A	848
1 1/2in 28A	843	3in 68A	849
1in 28A	844	3 1/2in 68A	850
1in 48A	845		

BA NUTS — packs of cadmium plated full nuts in multiples of 50	Type	No.	Price
08A	855	48A	857
28A	856	68A	858

RA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50	Type	No.	Price
08A	859	48A	861
28A	860	68A	862

SOLDER TAGS — Hot tinned supplied in multiples of 50	Type	No.	Price
08A	851	48A	853
28A	852	68A	854

AUDIO LEADS

No.	Type	Price
107	FM Indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug Length 1.5m	£0.86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 Length 1.5m	£0.98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4 Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.21
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones Length 0.2m	£1.04
120	Car stereo connector Variable geometry plug to fit most car cassettes, 8-track cartridge and combination units. Supplied with lined fuse power lead and instructions	£0.69
123	6.6m Coded Guitar Lead Mono Jack plug to Mono Jack plug, Black	£1.73
124	3 pin DIN plug to 2 pin DIN plug Length 1.5m	£0.86
125	5 pin DIN plug to 5 pin DIN plug Length 1.5m	£0.86
126	5 pin DIN plug to Tinned open end Length 1.5m	£0.86
127	5 pin DIN plug to 4 Phono Plugs All colour coded Length 1.5m	£1.50
128	5 pin DIN plug to 5 pin DIN socket Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN socket 1 & 4 and 3 & 5 Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN plug Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs Connected pins 3 & 5 Length 1.5m	£0.86
134	5 pin DIN plug to 2 Phono sockets Connected pins 3 & 5 Length 2.3cm	£0.78
135	5 pin DIN socket to 2 Phono plugs Connected pins 3 & 5 Length 2.3cm	£0.78
136	Coded stereo headphone extension lead Black Length 6m	£2.01
178	AC mains lead for calculators, etc	£0.52

TRANSFORMERS

MINIATURE MAINS Primary 240V	No.	Secondary	Price
2021		6V-0-6V 100mA	£1.04
2022		9V-0-9V 75mA	£1.04
2023		12V-0-12V 100mA	£1.29

MINIATURE MAINS Primary 240V with two independent secondary windings	No.	Type	Price
2024		MT280-0 6V 0-6V RMS	£1.84
2025		MT150-0 12V 0-12V RMS	£1.84

1 AMP MAINS Primary 240V	No.	Secondary	Price
2026		6V-0-6V 1 amp	£2.88 P & P 45p
2027		9V-0-9V 1 amp	£2.30 P & P 45p
2028		12V-0-12V 1 amp	£2.99 P & P 55p
2029		15V-0-15V 1 amp	£3.16 P & P 66p
2030		30V-0-30V 1 amp	£3.97 P & P 86p

STANDARD MAINS Primary 240V	No.	Secondary	Price
2031		1/2 amp	£3.91 P & P 86p
2032		1 amp	£5.06 P & P 86p
2033		2 amp	£6.27 P & P £1
2035		240V Primary 0.55V @ 2A Secondary	£7.30 P & P £1

CASES AND BOXES

INSTRUMENT CASES. In two sections vinyl covered top and sides aluminium bottom front and back	No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.73	
156	11in	6in	3in	£2.92	
157	6in	4 1/2in	1 1/2in	£1.79	
158	9in	5 1/2in	2 1/2in	£2.43	

ALUMINIUM BOXES. Made from bright ali. folded construction each box complete with half-inch deep lid and screws	No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.85	
160	4in	4in	1 1/2in	£0.85	
161	4in	2 1/2in	1 1/2in	£0.85	
162	5 1/2in	4in	1 1/2in	£0.97	
163	4in	2 1/2in	2in	£0.87	
164	3in	2in	2in	£0.80	
165	8in	5in	2 1/2in	£1.83	
166	8in	6in	3in	£1.83	
167	6in	4in	2in	£1.18	

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back top & front — strong construction easily accessible	No.	Length	Width	Height	Price
169	2 1/2in	5 1/2in	2 1/2in	1 1/2in	£5.45
168	1 1/2in	7 1/2in	4in	1 1/2in	£8.21

Terms cash with order. Cheques/Postal Orders made payable to Bi-Pak at above address



KEELMOOR Quality...

Keelmoor Ltd is a company which has been established for a long time – we supply the products you have often bought from other companies. Our precision watches and electrical goods are renowned for their superb quality and reliability. We differ from other companies in that we import direct world-wide – that difference is passed on to you at unbeatable prices. You receive the goods faster and we provide a service and no catch guarantee of which we are justly proud. We employ experts world-wide whose job it is to seek out products of the highest quality at the lowest possible prices. Illustrated here is just a tiny selection of our comprehensive range. Just compare these items with those seen elsewhere – we are confident the prices will amaze you. You can save £££'s.

GENTS 5 FUNCTION LCD

A



This is the foundation of our range and is ideal for the man requiring the basic functions of hours, minutes and seconds, with month and date. A backlight is included and the stainless steel strap provided is fully adjusted to suit any size of wrist. Guaranteed for one year, this watch represents fantastic value at only

£4.95p

ILLUSTRATED BELOW IS THE LADIES 5 FUNCTION LCD. This watch has the same time and auto calendar functions as the basic gents model described above, together with backlight and adjustable strap to suit the daintiest of wrists. It's compact, pleasing appearance makes it a very practical day watch and it is also often used for boys and girls. Available in black or white face.

These are just a few of our fantastic offers remember. A free colour catalogue is posted with every order. Or just send large S.A.E. and we'll send you one.

B



£5.95p

GENTS LCD ALARM WATCH

This model represents fantastic, incredible value for money. The 6 digit display continuously shows hours, minutes and seconds, or may be changed at will to hours, minutes and date. Its effective alarm is extremely useful and may be set to any time within a 24 hr. period. In addition, there is an alarm indicator, 4 year calendar and snooze repeater.

£8.95p



FULLY GUARANTEED

We must emphasize all these items are fully guaranteed for one year. All electronic goods come complete with demonstration batteries which cannot be guaranteed. New batteries are available for only 60p.

BARCLAYCARD AND ACCESS CARD WELCOME. SEE COUPON.

HERE IS THE AMAZING 12/24 HOUR ALARM/CHRONOGRAPH

D



Along with the usual time and date displays, this multi-functional timepiece has a 24 hour alarm and a 1/10 second stopwatch. The time may be set to operate in 12 or 24 hour mode and the date can be in English or American format. The day of the week is continuously indicated and the stopwatch display may, on command, be frozen to show split/laptime while the stopwatch continues to run. Stopwatch operation does not effect normal time keeping. £12.95 only for this model. Also available with solar energy panel to conserve energy during daylight hours for £14.95

FROM **£12.95p**

From Watches to Clocks, from Calculators to Radios, from Binoculars to Tool Kits – KEELMOOR is the name for the right quality at the right price. Your personal catalogue will tell you more – free with every order.

E LADIES QUARTZ LCD DRESS WATCH

This attractive ladies model with the standard 5 functions of hours, minutes, seconds, month and date has literally sold in tens of thousands. Available in gold or silver colours with 'sugar coated' finish. Please state first and second choice of square, round or oval design.

£8.95p



THE ULTIMATE GENTS LCD CALCULATOR/ALARM WATCH

If you want a watch from the top end of the market this is the one for you. Full calculator functions plus memory and percentage are combined with time and alarm functions to make this item an outstanding buy. Manufactured in Japan at the same factory that produces models for probably the most famous name in the watch business, this device represents sheer quality at an unbelievable price. Comes complete with backlight and button operating tool carried in the strap clasp. We advise you to order quickly whilst stocks last.

£39.95p



F

at Keener Prices

FREE
With every order.
Big colourful
Keelmoor catalogue
featuring hundreds of
products at bargain
prices.

We don't think you'll find items of this quality anywhere else at the price we offer. Order now, Christmas is round the corner and this is the way to make gift buying easier – and cheaper too.

WE ARE PROUD TO INTRODUCE THE AMAZING MELODY ALARM CHRONOGRAPH




ACTUALLY PLAYS THE YELLOW ROSE OF TEXAS
BUT AS YOU CAN SEE FROM THE DETAILS BELOW THIS CHRONOGRAPH IS NO MERE NOVELTY

Today's technology has produced this fine watch which incorporates a musical alarm which plays a complete verse of 'The Yellow Rose of Texas.' Other functions included are as for model number 1.

G
£14.95p

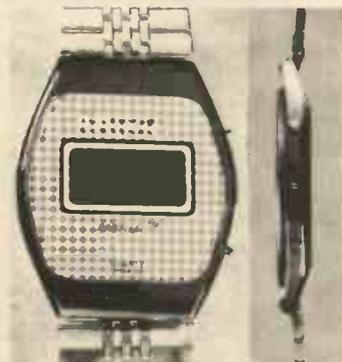NEW TO OUR RANGE, WE COMBINE PRECISION AND STYLE IN THIS—THE SUPER SLIM GENTS 5 FUNCTION CHRONOGRAPH



JUST TO GIVE YOU AN IDEA OF THE ULTRA SLIMNESS OF THESE WATCHES WE HAVE ILLUSTRATED A SIDE VIEW OF THE SUPERSLIM DIGITAL. BELOW, WE HAVE ELABORATED ON SOME OF THE TECHNICALITIES:—

These watches need no special functions to make them stand out in a crowd – their slimness serves that purpose. If you've been put off digital quartz watches in the past because you require an ultra-slim design, now is the time to change. Is equipped with standard 5 functions and backlight.

£9.95p

Keelmoor Ltd, 78 Castle Street, Melbourne, Derbyshire, DE7 1DY.

MAINS DIGITAL ALARM CLOCK



A very practically sized mains operated digital alarm clock – this item is extremely well finished and looks equally at home by the bedside or in the living room. With snooze/repeater alarm you could not even buy the components to build your own for this price. Available at the amazingly low price of only

£8.95p

AND FINALLY, WHAT MUST BE THE ULTIMATE IN SQUEEZING A QUART INTO A HALF PINT POT! THE INCREDIBLE MINIATURE LCD TRAVEL/ALARM CLOCK



As you can see from the photograph above this device is tiny and yet it continuously displays hours and minutes with auto calendar and night light. Invaluable for the busy traveller or simply for use in the modern home, it comes complete with its own travelling case and can easily be carried in top pocket or the smallest of handbags. It has even got a stand for upright position on table, shelf or sleeping compartment. An unusual gift to yourself or others at only £10.95. **J**

Every order dispatched by return, and is sent by recorded delivery. That is Keelmoor's Promise To You.

THE KEELMOOR PROMISE

Keelmoor have a tremendous reputation to uphold, both in the retail and wholesale trades and so, with every product sold, we automatically give the Keelmoor Promise. This includes:—

- **NO RISK GUARANTEE.** Try any of these items for 15 days and if you are not completely satisfied with the quality and value simply return it for a complete refund
- **ONE YEAR'S FULL GUARANTEE** on all products
- **BACK UP SERVICE** second to none

15 DAY TRIAL COUPON.

To Keelmoor Ltd, 78 Castle Street, Melbourne, Derby DE7 1DY
Please send me the items indicated in the boxes below. I understand that if I am not completely satisfied, I may return the goods undamaged within 15 days and my money will be refunded in full.

A	B	C	D	E	F	G	H	I	J	Just indicate with a tick, item required, if more than one required tick plus number - e.g. 3
TOTAL AMOUNT = £										

NAME Mrs, Miss, Ms, Mr. _____
ADDRESS _____

POSTCODE _____
I enclose a cheque (P) to **KEELMOOR LTD**
Or charge my Access or BARCLAYCARD (tick as applicable)

No. _____
TOTAL — £ Please add 50p per item P & P.
The advertisements to watch for quality precision at the right price.
All goods dispatched by return.

PE 5

24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit £14.90
CT1000KB with white box (56/131 x 71mm) £17.40
Ready Built £22.50

MINI KITS

These Kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/ THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max), and triac to switch heater. 1KW £4.00

MK2 SOLID STATE RELAY

Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. £2.60

MK3 BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

MK4 PROPORTIONAL TEMPERATURE CONTROLLER

Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. 3KW £8.55

MK5 MAINS TIMER

Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW £4.50

TRIACS



400V Plastic Case (Texas)

3A 49p
8A 59p 16A 95p
12A 85p 25A 190p
6A with trigger 80p
8A isolated tab 85p
Diac 18p

MINI TRANSFORMERS



Standard mains primaries 240V a.c.
6-0-6V 80p
9-0-9V 85p
12-0-12V 90p

TRADE ENQUIRIES WELCOME

CMOS

4000	.17	4019	.42	4069	.19
4001	.18	4023	.22	4070	.19
4002	.18	4025	.21	4071	.18
4007	.17	4026	1.30	4077	.26
4011	.19	4027	.40	4081	.20
4012	.17	4028	.50	4093	.54
4013	.38	4040	.80	4501	.24
4015	.75	4049	.38	4511	.90
4016	.35	4050	.40	4514	1.80
4017	.70	4060	1.08	4516	1.80

SPECIAL OFFERS

Orders must be received by 30/11/80.

3 1/2 digit Liquid Crystal Display, 0.5" digits, d.i.l. package. Can be backlit for viewing in the dark. £5.95
2N3442 Power Transistor 2 for £1.80


INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp.	19p
AY-5-1224 Clock	£2.60
AY-5-1230/2 Clock/Timer	£4.50
AY-3-1270 Thermometer	£8.20
ICL7106 DVM (LCD drive)	£7.00
LM377 Dual 2W Amp.	£1.45
LM3795 Dual 6W Amp.	£3.50
LM380 2W Audio Amp.	80p
LM382 Dual low noise Preamp	75p
LM386 250mW low voltage Amp.	£1.00
LM1830 Fluid Level Detector	£1.50
LM2907 f-v Converter (8 pin)	£1.40
LM2917 f-v Converter (14 pin)	£1.60
LM3909 LED Flasher/Oscillator	£0.20
LM3911 Thermometer	£6.20
LM3914 Dot/Bar Driver	£2.10
MM74C911 4 digit display controller	£8.50
MM74C915 7 segment-BCD converter	96p
MM74C926 4 digit counter with 7 seg. o/p	£4.50
S566B Touchdimmer	£2.50
S9263 Touchswitch 16-way	£4.85
SN76477 Complex Sound Generator	£2.52
TBA800 5W Audio Amp.	88p
TBA810AS 7W Audio Amp.	£1.20
TDA1024 Zero Voltage Switch	£2.85
TDA2020 20W Audio Amp.	£1.80
ZN1034E Timer	

All ICs supplied with data sheets.
Data Sheets only. 10p each device.

AND NOW A DIMMER THAT MAKES TOUCH DIMMERS OBSOLETE

Two years ago TK Electronics launched a touchdimmer kit, the TD300K, which made knob touchdimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW, TK have designed a touch dimmer kit with an Infra Red Remote Control, enabling you to switch and control the brightness of your lights from the comfort of your armchair etc. (as well as manually by touching the frontplate or by using the TDE/K extension kit). As with all our kits, these units come complete with all components, including RFI suppression, frontplate, a neon to help you find the switch in the dark and a neat box for the transmitter. The plastic frontplate has no metal parts to touch, ensuring complete safety and enabling the plate to be covered with a decorative finish to blend with your room decor.

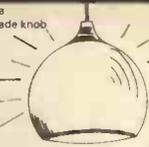

We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.



In two years' time everyone will be selling remote control dimmers but you can have your TDRK300K kit NOW for only £14.30 for the dimmer unit and £4.20 for the transmitter. For the more athletic of you, the TD300K is still available at £6.50 and the TDE/K at £2.00.

DON'T FORGET to add 40p P&P and 15% VAT to your total purchase.

REMOTE CONTROL COMPONENTS

LD271 IR Emitting Diode	36p
SF205 Photodiode Detector	95p
SL480 IC Pulse Amp.	£1.70
SL490 32 command encoder/transmitter	£2.40
ML922 10 channel receiver + 3 analogue outputs	£4.20
ML926 16 channel receiver 4 momentary binary o/p	£1.40
ML928 16 channel receiver 4 latched binary o/p	£1.40
ML929 16 channel receiver 4 latched binary o/p	£1.40
Data sheets per device	10p

These ICs can be used with infra red, ultrasonic or radio links, depending on range, cost and speed of operation.

RC500K KIT

If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel on/off infra red transmitter and receiver kit. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a pre-amplifier bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. Range: approximately 20 ft. £12.50.

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER - CALLERS WELCOME BY APPOINTMENT

TK Electronics
(P.E.), 11 Boston Road, London
W7 3SJ. TEL. 01-579 9794



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMANS ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO (Dept. P.E.)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Tel: 0625 529599
FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.
Tel: 0625 526213
(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

<h3>MULLARD CAPACITORS</h3> <p>Special purchase of factory clearance capacitors enables us to offer: C280 Polyester (Liquorice Allsorts) at £2 for 100 mixed. And Miniature Electrolytics at £1.50 for 100 mixed. Pack of each only £3. These consist of spillages, floor sweepings, cosmetic imperfections etc. As we have no time to sort them they are magnificent value for the constructor.</p>	<h3>MINIATURE MAINS TRANSFORMERS</h3> <p>Top quality. Split bobbin construction will give 4-5V-0-4-5V at 250 MA. 1 1/2" x 1 1/2", all sorts of uses. ONLY 90p 3 for £2.20. 2,200 VA 40V Radial 1 1/2" x 2" 60p 3 for £1-50. 1,000 VA 100V Radial 1 1/2" x 2" ONLY 70p 3 for £1-50.</p>
<h3>HUMIDISTATS</h3> <p>Don't Let Your Environment Dehydrate You! Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive, 1/2" shaft, 250V, 3.75A Contacts. Ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 90p ea. 3 for £2.</p>	<h3>TRANSISTOR PACKS</h3> <p>100. Full spec, new and marked Includes BC148, BC184L, ME0412, BF274, BC154 etc. £4.95 200 as above and includes AC128, 2N3055, BFY50, 8D131, BF200 etc. £9.95 Buy bulk and save money, these packs are worth at least double.</p>
<h3>20 ASSORTED ZENER DIODES</h3> <p>1 watt and 400mW. £1.50</p>	<h3>P/B SWITCH BANKS</h3> <p>These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole o/c etc. Can be modified. Can't be repaired. 3 Banks for £1</p>
<h3>100 MIXED DIODES</h3> <p>Includes: Zener, power, bridge, germanium, silicon etc. All full spec. £4.95</p>	<h3>BULK BARGAINS. STOCK UP FOR SUMMER</h3> <p>300 mixed 1/2 & 1 watt resistors £1.50 150 mixed 1 & 2 watt resistors £1.50 300 mixed capacitors, modern, most types £3.75 100 mixed ceramic and plate caps £2.20 400 mixed film resistors £2.95 100 mixed polystyrene caps £2.20 25 pots and presets £1.50 25 presets, skeleton etc. £1.20 20 VDRs and thermistors £2.75 100 Hi wattage resistors wirewound at £2.75 100 electrolytics, nice values £2.20 300 printed circuit resistors £1 300 printed circuit components £1.50</p>
<h3>2" LED'S</h3> <p>0-2" LED'S with 2 piece clips.</p>	<h3>100K MINIATURE THUMBWHEEL SLIDER POTS</h3> <p>Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1</p>
<h3>ULTRASONIC TRANSDUCERS</h3> <p>Transmitter and receiver 40 kHz 14 mm dia. £3-25 pair.</p>	<h3>MINIATURE LEVEL/BATT. METERS 200uA</h3> <p>F.S.D. as fitted to many cassette recorders 60p</p>
<h3>MINIATURE REED SWITCHES</h3> <p>We are the cheapest! 12 for £1.00 100 for £4.20</p>	
<h3>G.E.C. UHF TRANSISTOR TY TUNERS</h3> <p>Rotary type with slow motion drive, leads and aerial socket. £1.50 3 for £3.50 "for G.E.C. "2010" series etc."</p>	
<h3>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS</h3> <p>Includes 150 sq. ins. copper clad P.C. board 1 lb ferric chloride 1 dolo etch resist pen. Abrasive cleanser. Etch tray plus instructions. Special Price £4.95 1 lb FE. C1. To mil. spec. £1.25 5 lb FE. C1. To mil. spec. £5.00 150 sq. in. Single sided board £2.00 150 sq. in. Double sided board £3.00</p>	

50p P & P on all above items. Cheque or P.D. with order to:
SENTINEL SUPPLY, DEPT. P.E.
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

— CLEF KITS —



High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS

Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action as used in the P.E. JOANNA, which electronically simulates piano key inertia – a feature not available in any other design. Build this widely acclaimed professional instrument, for either domestic or Stage use, from our top quality Component Kits.

SIX OCTAVES – £207
7½ OCTAVES – £232

P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT – £169

P.A.'s – SPEAKERS – CABINETS

Units can be supplied to add to the Piano Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

ELECTRONIC ROTOR

Two speed organ rotor simulation plus a three phase chorus generator on a single p.c.b. (8" x 5"). Kit includes all components/IC sockets throughout/mains operation and stereo headphone. Driver p.c.b. Easily integrates with existing organ.

COMPONENT KIT – £89

KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

49 NOTE C-C £23.80
73 NOTE F-F £37.00
88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you – see lists.

INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & Insurance.

VISITS

Are welcome by appointment, otherwise Mail Order Only.

EXPORT

Enquiries welcome – in Australia please contact JAYCAR (Sydney).

Back up TELEPHONE advice is available from the Designer to supplement the clear instructions included with the above Kits.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. PE) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU.
061-439 3297

Make sure of your Heathkit catalogue... write now.



Autumn
1980
catalogue
out now.

Keep up to date with the world's finest electronic kits – with the Heathkit catalogue.

48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers.

Heathkit make it easy to build, easy on your pocket, and as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (PE 11),
Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue.

I enclose 25p in stamps.

Name _____
Address _____

Soldering Iron offer FREE N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.



TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course – or, refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

Courses in
C & G Elect. Technicians
C & G Elect. Installations
Telecomms. Technicians Exams
Television Servicing
Radio Maint. & Repairs (BIET)
Pract. Radio & Electronics
Plus over 60 other
home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept TPE08, Reading RG7 4PF.

NAME (Block capitals please) _____

ADDRESS _____

POSTCODE _____

Other Subjects _____ AGE _____

Accredited by CACC Member of ABCC



Freeport E
Birmingham
B19 1BR
021-233-2400

- FREEPOST ON ORDERS
- ACCESS
- VAT INCLUSIVE PRICES
- VISA
- CASH
- ADD 30p P&P
- CHEQUE
- 24 HR PHONE ANSWERING SERVICE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MOS (BUFFERED)

HEF4000	22	HEF4044	103	HEF4512	136
HEF4001	22	HEF4046	133	HEF4516	127
HEF4002	22	HEF4047	109	HEF4517	476
HEF4006	119	HEF4049	37	HEF4518	118
HEF4007	22	HEF4050	57	HEF4519	92
HEF4008	100	HEF4051	87	HEF4520	118
HEF4011	22	HEF4052	90	HEF4521	235
HEF4012	22	HEF4053	90	HEF4522	90
HEF4013	37	HEF4056	57	HEF4532	126
HEF4014	105	HEF4067	475	HEF4534	638
HEF4015	100	HEF4068	22	HEF4539	138
HEF4016	37	HEF4069	22	HEF4585	122
HEF4017	100	HEF4070	22	HEF4724	214
HEF4018	100	HEF4071	22	HEF4097	113
HEF4019	38	HEF4072	23	HEF4099	92
HEF4020	112	HEF4073	23	HEF4108	78
HEF4021	107	HEF4075	23	HEF4160	149
HEF4022	103	HEF4076	130	HEF4097	149
HEF4023	22	HEF4077	22		
HEF4024	76	HEF4078	23		
HEF4025	22	HEF4081	23		
HEF4026	244	HEF4086	23		
HEF4027	57	HEF4094	219		
HEF4028	89	HEF4086	80		
HEF4029	113	HEF4093	63		
HEF4030	58	HEF4094	219		
HEF4031	250	HEF4104	206		
HEF4033	136	HEF4502	114		
HEF4040	107	HEF4503	714		
HEF4041	94	HEF4508	130		
HEF4042	83	HEF4510	235		
HEF4043	100	HEF4511	157		

LINEAR

CA3046	94	IN914	5	IC182L	12
CA308E	77	IN4001	5	IC184	11
CA310E	99	IN4002	5	IC184L	12
CA310E	48	IN4004	7	IC217	11
CA318E	293	IN4007	6	IC217L	12
LM301A	34	LM148	4	IC214	11
LM339A	78	LM542	15	IC214L	12
LM339A	104	2N2369	21	IC547	13
LM381A	106	2N2646	46	IC548	13
LM7800N	75	2N2926G	13	IC549	12
NE531	131	2N3054	55	IC548	18
NE53T	259	2N3055	55	IC70	18
NE555N	78	2N3702	9	ICV71	18
NE556N	66	2N3704	9	BD131	39
NE566A	171	2N3705	10	BD132	39
NE570N	485	2N3773	297	BD139	39
NE571N	505	2N3819	22	BD140	39
NE581E	146	2N3830	39	BF960	233
TR41205	88	2N3504	9	BF286	29
TD1022	713	2N4537	39	BFV90	17
TD10348	239	2N4559	35	BFV91	17
TL081CP	84	40073	88	BRV39	50
TL084CN	156	8C107	14	BSX20	21
UA741CN	20	8C106	14	IC8960	7850
UA741CT	47	8C108C	18	TP31	48
Zener		8C109	14	TP32	54
8C109B	19	TP41C	76		
8C109C	20	TP42C	76		
8C148	10	TP2955	76		
8C158	10	TP3055	60		
8C177	17	TS43	36		

Voltage Regulators

LM309DAIK1	119
UA723CN	42
UA7805CU	78
UA7812CU	78
UA7815CU	78
UA7818CU	97
UA78L05CS	38
UA78L12CS	38
UA78L15CS	38

CAPACITORS

Electrolytic Axial		Polyester Radial Leads		Order Code		Electrolytic Radial Leads		Order Code	
-10% to +50% Tol.		Disposed Type, C280/352 Style		Cap 352		-10% to +50% Tol.		Cap 034 + P	
µF		Moistured Type, 10mm Pinch		+ Value		µF		+ Value	
1.0	10	9	352	380	µF	382	380	60	7
1.5	2	9	.001	7	1	7	9	1.0	7
2.2	3	9	.0015	7	15	9	10	1.5	7
4.7	6	9	.0022	6	22	9	11	2.2	7
10	10	9	.0033	6	33	11	11	3.3	7
22	15	8	.0047	6	47	14	14	4.7	7
47	20	8	.0068	6	68	17	17	6.8	8
100	25	8	.01	6	10	21	10	7	8
220	30	8	.015	6	15	24	15	7	8
470	35	8	.022	6	22	35	22	7	8
1000	40	8	.033	6	33	47	33	8	9
1500	45	8	.047	6	47	68	47	8	9
2200	50	8	.068	7	68	100	68	9	11

D.I.L. Sockets

8 Pin Low Profile Socket Tin	12	DIL SKT 8
16 Pin Low Profile Socket Tin	14	DIL SKT 14
16 Pin Low Profile Socket Tin	16	DIL SKT 16

P.C.B. Components

Date Pen, Blue Ink, Slow Drying	88
---------------------------------	----

RESISTORS

Carbon Film, Fixed		Skeleton Presets, Miniature		Order Code	
E75W, E24 Values, 100-10M, 5% Tol.		0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting		8 Min. Preset H	
2 each Rns RD%		0.1W, E3 Values, 100R-1M, Lin. Horizontal Mount		8 Min. Preset H	
100/100 (Multi 10/Value)		Skeleton Presets, Standard		11 Std. Preset H	
Q5W, E12 Values, 10R-4M7, 10% Tol.		0.2W, E3 Values, 100R-4M7, Lin. Vertical Mounting		11 Std. Preset H	
3 each Rns RD%		0.2W, E3 Values, 100R-4M7, Lin. Horizontal Mount		11 Std. Preset H	
Metal Film, Fixed		Potentiometer, Rotary		39 Ro Pot Lin	
0.8W, E24 Values, SR-1M, 2% Tol.		0.5W, E3 Values, 1K-2M2 Lin.		39 Ro Pot Log	
8 each Rns MR30		0.25W, E3 Values, 4K7-2M7 Log.		39 Ro Pot Log	
2.5W, E12 Values, 10R-27K, 5% Tol.		Potentiometer, Slider		45 S/Pot Lin	
Rns PR52		0.5W, E3 Values, 2K2-47K Lin.		45 S/Pot Log	
Metal Glaze, Fixed		0.25W, E3 Values, 1K0-1M0 Log.		45 S/Pot Log	
0.5W, E24 Values, 1M-33M, 5% Tol.				45 S/Pot Log	
16 each Rns VR37				45 S/Pot Log	
+ Value					

MAINS TRANSFORMERS

Secondaries may be connected in series or parallel to give wide voltage range		Plastic Boxes - Boss Industrial Mouldings		Order Code	
Primary: 0.220, 240V		Moulded Box and Close Fitting Flanged Lid		L112 W6 D31 90	
BVA - Clamp Type Construction		ABS Base, C/W Bress Bushes, and Lid in Orange		L190 W80 D50 131	
236 each				L190 W110 D80 222	
Approx 18% Regulation F C 54, H36, W35		Plastic Boxes with Metal Lids		Order Code	
0.4-5V, 0.4-5V Secondaries		Recessed Top Box		L85 W58 D29 112	
Trans 5VA		ABS Base, C/W Bress Bushes, in Orange		L111 W71 D42 180	
0.12V-0.12V		Iron Aluminium Top Panel Finished Grey		L181 W98 D53 208	
0.15V-0.15V				Order Code	
0.20V-0.20V				L112 W63 D31 124	
20VA - Clamp Type Construction		Ducati Box and Flanged Lid		L182 W82 D50 218	
360 each		Aluminium Box and Lid in Natural Finish		L192 W113 D81 334	
Approx 18% Regulation F C 70, H48, W46				Order Code	
0.4-5V, 0.4-5V Secondaries				L112 W63 D31 124	
Trans 20VA				L182 W82 D50 218	
0.8V, 0.8V				L192 W113 D81 334	
0.12V, 0.12V					
0.15V, 0.15V					
0.17V, 0.17V					
0.20V, 0.20V					

VERO ELECTRONICS PRODUCTS

2.5" x 8" 1" pitch Veroboard	71	200-2109A
3.75" x 8" 1" pitch Veroboard	79	200-2107D
2.5" x 1" 1" pitch Veroboard (S)	85	200-2107C
3.75" x 5" 1" pitch Pin Board	88	200-2107H
5.82" x 9.8" 1" pitch V-DI Pin Board	136	200-2109E
Socket Face Cutter	107	203-2103A
Pin Insertion Tool For -040 type pin	147	203-2103F
DS Pins, 040 (100)	44	200-2108D
55 Pins, 040 (100)	44	200-2107H
Veroboard Kit (Econ. 2 wire, 25 comb)	484	200-2134D
Veroboard Kit (25)	109	200-2138F
Veroboard Wire (2)	100	200-2130G



SWITCHES

Miniature Toggle - Moneywell		Order Code	
SPDT	67	SW BA1011	
SPDT C/DH	81	SW BA1021	
SPDT Double Bias To Centre	80	SW BA1043	
DPDT	99	SW BA2011	
DPDT C/DH	111	SW BA2021	
Miniature Push - C & K		Order Code	
SP Push To Make, Momentary	62	SW 8531	
SP Push To Break, Momentary	62	SW 8533	


GMT ELECTRONICS PROJECTS

	KIT	BUILT UP
FREE-STANDING COMPLETE TELETEXT UNIT - FULL SPEC	£199-90	£275-00
TELETEXT DECODER BOARD + REMOTE HAND CONTROL	£135-90	£160-00
TELETEXT COMPATIBLE TUNER AND P. S. U.	£ 46-90	£ 57-00
TELETEXT COMPATIBLE PAL ENCODER + MODULATOR	£ 22-90	£ 35-00
F. E. T. OUTPUT 100W MONO POWER AMPLIFIER MODULE	£ 27-50	£ 35-00
X-BAND DOPPLER RADAR ALARM MODULE - MARK II	£ 35-90	£ 44-00
ONE AMP P.S.U. MODULE (SPECIFY 5 OR 12 VOLTS)	£ 7-50	£ 10-00
SIMULATED INERTIA MODEL TRAIN CONTROLLER	£ 22-50	£ 35-00
SIMULATED INERTIA SLOT RACER CONTROLLER	£ 27-50	£ 40-00
MODEL TRAIN STEAM SOUND SIMULATOR MODULE	£ N/A	£ 5-00

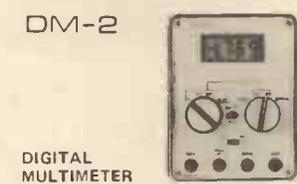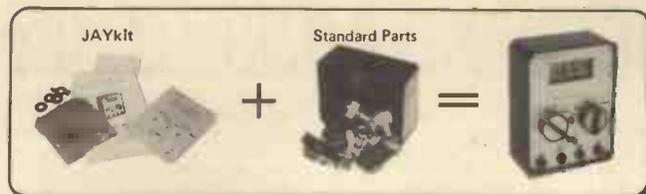GMT ELECTRONICS, P.O. BOX 290, HAMPTON STREET, BIRMINGHAM B19 3JR



DIGITAL MULTIMETER

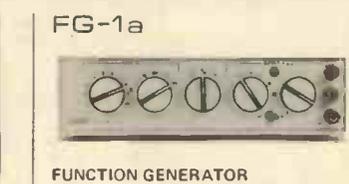

FUNCTION GENERATOR

- ★ DC Volts 1mV to 1000V
- ★ AC Volts 1V to 500V
- ★ DC Current 0.1mA to 0.2A
- ★ Resistance 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayden Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

Name _____

Address _____

Tel: (0954) 80285

Please send:

DM-2 @ £5.45

FG-1a @ £4.95

(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.



Codespeed Electronics

P.O. Box 23, 34 Seaford Road, Copnor, Portsmouth, Hants. PO3 5BJ

SOUND EFFECTS PCB brand new, made for spaceman robot toy. Gives 5 spaceman sounds with flashing LED's (speaker not supplied). Entertain the kids for only 85p. FLUORESCENT REJECT CALCULATORS modern, ten function calculators with full memory. Most repairable but no guarantees, £2.50 each. ALARM CLOCK CHIP MM5316 digital alarm clock I.C. With data, £2.35 each. GIANT LED CLOCK DISPLAY non-multiplexed, common cathode display panel. With data, £3.95 each. WRISTWATCH LED DISPLAY tiny, bright displays for led watches. Note display is housed in 'legless flatpack' package and requires fairly fine soldering. Supplied with data, 95p each or 2 for £1.50. DIGITAL MULTIMETER CHIP to build an Auto-polarity, 4½ digit multimeter (requires additional circuitry). With data sheet, £3.55. 8 DIGIT CALCULATOR DISPLAY common cathode, multiplexed, 0.1" digits. With data, 99p each. PLASTIC POLARIZING FILTER 0.006" thick plastic film. Any size cut from 1 square inch up to a maximum size of 19 inches x 250 feet. Only 3p per square inch. SUPER QUALITY JACK SOCKETS gold plated contacts for high reliability. Mono 25p Stereo 30p each. CALCULATOR KEYBOARDS excellent value, 2 for 99p. LM 555 TIMER I.C. suitable for most timer applications, and is supplied with applications booklets, 25p each. CALCULATOR CHIP NORTEC 4204, four function and constant. With data and diagram, 80p each. PUSH-BUTTON SWITCHES with 1 n.o. contact (momentary action). With red button, 15p each. MINIATURE SLIDER SWITCHES with 2 pole change-over contacts, 16p each. STATIC RAMS 2102 memories, with data, only 99p each. REJECT LED CALCULATORS some repairable but excellent value for spares. Yields lots of parts. £2.50 each. LIQUID CRYSTAL DISPLAY nice style display gives black digits on grey background. Could also be used for freq. meters, dvm's etc. With data £5.25. PROFESSIONAL QUALITY CONTROL KNOBS rotary knobs satin finish black nylon knobs to fit standard 1" D" shaped shafts. Coloured snap-in caps also have position indicator line. Cap colours available, black, white, grey, red, green, blue and yellow. Knob and coloured cap 20p (state cap colour required). Skirted rotary knobs AS above but has 'flared' nut cover around base of knob, 27p each. (State cap colour required). Slider control knobs fits 5mm or 8mm shafts. Available in black, white, grey, red, green, blue and yellow. 14p each (state colour required). QUALITY REED SWITCHES tiny but sensitive reed switches, ideal for burglar alarms etc. Only 39p each. RECTANGULAR BAR MAGNETS small but powerful. Purchased for use with above reed switches. 59p each. REED RELAYS 12v d.c. coil, one n.o. contact. Small enough for PCB mounting, 79p each. POWER RELAYS 12v d.c. coil. Two change-over contacts, each rated at 10 amps. Contacts solid silver for high reliability. Only £2.55 each. Relay bases for above relays are 35p each. TRANSISTOR RADIO I.F. TRANSFORMERS all brand new. May include several types. Ten transformers for 55p. NYLON CABLE TIES 25 for 35p (ties are 4" long). SHRINK TUBE available in 3 bore sizes. Shrinks by approx 50% when heated, 2.4mm bore 15p per metre, 4.8mm bore 16p per metre, 12.7mm bore 23p per metre. TEN UNTESTED LED DISPLAYS Gamber? - try these. Ten 0.1" common cathode displays for 99p. You to test.

A comprehensive range of resistors and capacitors are now in stock, as follows:- Resistors, 1W, 5%, 10hm to 10 Megohms. ELECTROLYTIC CAPACITORS, (25v) 1µF to 470µF. MYLAR CAPACITORS (100v) 0.001µF to 0.1µF. MULLARO CERAMIC PLATE CAPACITORS (100v) 1 8pF to 4700pF. For full range of values and prices see our free catalogue.

SATISFACTION GUARANTEED ON ALL ITEMS OR FULL CASH REFUND NEW CATALOGUE (No. 8) NOW AVAILABLE - JUST SEND MEDIUM SIZED S.A.E. POST AND PACKING PLEASE ADD 40p (OVERSEAS ORDERS ADD £1.00)

V.A.T. ADD 15% TO THE TOTAL COST OF YOUR ORDER (INCLUDING POST AND PACKING)

CHROMASONIC electronics

56 FORTIS GREEN ROAD MUSWELL HILL LONDON N10 3HN
TELEPHONE 01-883 3705 01-883 2289

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS

PETS

8N (8K RAM)

£399

16N (16K RAM) **£499**

32N (32K RAM) **£599**

ALL WITH NEW KEYBOARD AND GREEN SCREEN.

PERIPHERALS

Service & Assistance available.

Interfaces available are:

X-Y plotters, analogue to digital converter, 16 channel interfaces, bi-directional interfaces, etc.

EXTERNAL CASSETTE DECK SUITABLE FOR ALL PETS **£55**



MEMORY

D. RAMS	£ p.
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	4.35
S. RAMS	
2102A	1.09
2102A-2	1.09
2112A	2.25
21L02	98
2114-4045	2.95
4035	1.07
4044-5257	6.93
BULK PURCHASE	
8 x 2114	22.50
8 x 4116	29.95
8 x 21L02	7.00
BULK PURCHASE	
16 x 2114	39.95
16 x 21L02	13.00
32 x 21L02	25.00
64 x 21L02	45.00

UK101

£179 in kit form

£229 ready built & tested

£249 complete in case

INVADER TAPE
£5.00

ASSEMBLER EDITOR TAPE
£14.95

NO EXTRAS REQUIRED

- * FREE SAMPLER TAPE
- * FULL QWERTY KEYBOARD
- * 8K BASIC
- * RAM EXPANDABLE TO 8K ON BOARD (4K INC)
- * KANSAS CITY TAPE INTERFACE

* New monitor allows full editing & cursor control.

£22

EPROM'S

2708	4.95
2716 (5v)	13.95
2532	39.95

ROM'S

2513(UC)	5.95
2513(LC)	5.95

CPU'S

6502	9.50
8080	4.75
9900	25.95
6800	5.90
Z80	8.95

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	52
SN74366	52
SN74367	52
SN74368	52
8T26	1.75
8T28	1.75
8T95	1.57
8T96	1.57
8T97	1.50
8T98	1.57

BAUD RATE GENS	
MC14411	8.75
MM5307	8.75

UARTS

AY-5-1013	3.45
AY-5-1015	3.98
MM5503	4.75
TMS 6011	3.55

LATEST STOP PRESS AND PRICE LIST

SEND SAE OR PHONE FOR UP TO DATE **PRICES** OF ALL OUR RANGE OF ITEMS STOCKED

CASES

Available for UK101, Superboard, NASCOM.
Approx. dim. 17" x 15"
435mm x 384mm

Price £24.50

Post and packing £1.50

TAPES

Unique stackable tape storage unit. Interlocking drawers. Drawers each containing 2 x C12 tapes.

10 drawers **£9.50**

5 drawers **£5.25**

Single drawer **£1.10**

MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2114's. Each board has 16K RAM capacity.

Kit contains:

- * On board power supply
- * 4K EPROM expansion
- * Fully buffered for easy expansion via 40 pin socket

* **8K KIT £99.95**


* **16K KIT £139.90**

PRINTERS

TX-80 £375

EPSON TX-80 £375

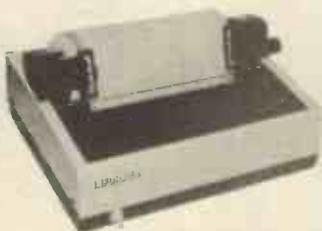Dot-matrix printer with Pet graphics Interface: Centronics parallel, options: PET, Apple and serial.



PLEASE ADD VAT 15% TO ALL PRICES. POSTAGE ON COMPUTERS, PRINTERS & CASSETTE DECKS CHARGED AT COST. ALL OTHER ITEMS P&P 30p. PLACE YOUR ORDER USING YOUR ACCESS OR BARCLAYCARD (Min. Tel. order £5.00). TRADE & EXPORT ENQUIRIES WELCOME, CREDIT FACILITIES ARRANGED.



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETs, and are easier to mount. Connections via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**




Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4 8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4 8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are in consideration while maintaining optimum performance with high quality and wide choice of models. From domestic hi-fi to disco and P.A. for instrument amplification, these are the best choice of bipolar amplifiers available. Profile extrusions with their computer-verified thermal efficiency and improved mounting tabs. Connections are simple, via five pins on the underside and with our new pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4 8Ω	0.015%	15V/μs	5μs	100dB	£6.34 + 95p
HY60	30W into 4 8Ω	0.015%	15V/μs	5μs	100dB	£7.24 + £1.09
HY120	60W into 4 8Ω	0.01%	15V/μs	5μs	100dB	£15.20 + £2.28
HY200	120W into 4 8Ω	0.01%	15V/μs	5μs	100dB	£18.44 + £2.77
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£27.68 + £4.15

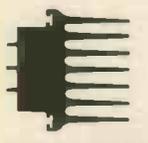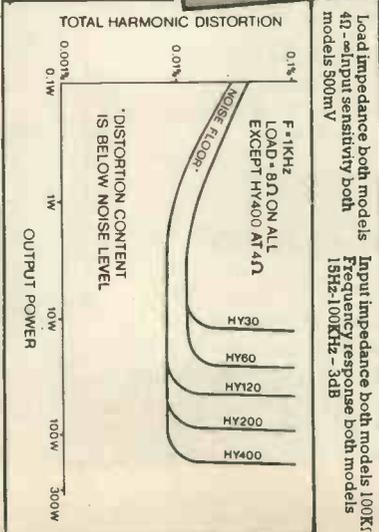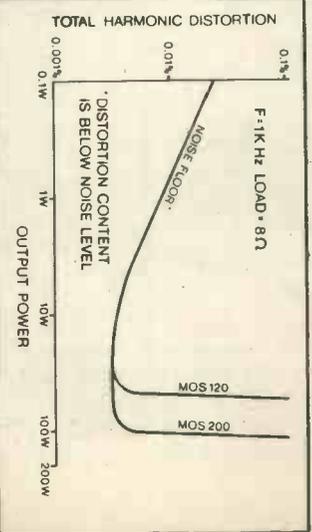I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE



THE NEW PROFILE EXTRUSIONS

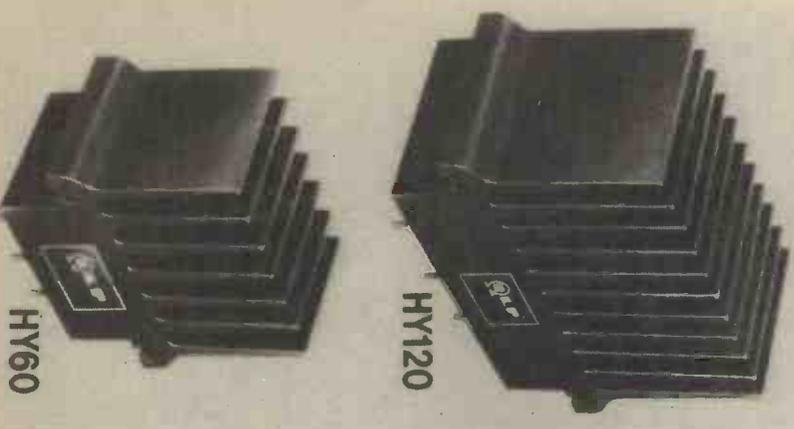The introduction of standard heat sink extrusion for all I.L.P. power amplifiers achieves many advantages. Research shows that the new profile allows for easy mounting, satisfactory dissipation, and easy pouring of compound. Surfaces are matt black, modified for lower thermal conductivity. Extrusions vary in size according to module number.



NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. **Inputs Sensitivity** - Mag. PU. - 3mV; Mic - selectable 1-12mV. All others 100mV. **Tape O/P** - 100mV. **Main O/P** - 500mV. **Frequency response** - D.C. to 100KHz - 3dB.

HY6 mono £5.60 + 84p VAT Connectors included

HY66 stereo £10.60 + £1.59 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT

B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

PSU30 ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT

THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS

PSU36 for 1 or 2 HY30's

PSU50 with toroidal transformer for 1 or 2 HY60's £8.10 + £1.22 VAT

PSU60 with toroidal transformer for 1 HY120 £9.75 + £1.46 VAT

PSU65 with toroidal transformer for 1 MOS120 £9.75 + £1.46 VAT

PSU70 with toroidal transformer for 1 or 2 HY120's £13.61 + £2.04 VAT

PSU75 with toroidal transformer for 1 or 2 MOS120 £13.61 + £2.04 VAT

PSU90 with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT

PSU95 with toroidal transformer for 1 MOS200 £14.75 + £2.21 VAT

PSU180 with toroidal transformer for 1 HY400 or 2 HY200 £23.02 + £3.45 VAT

PSU185 with toroidal transformer for 1 or 2 MOS200 £24.20 + £3.63 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ **TO ORDER** Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.




I.L.P. ELECTRONICS LTD.

FREEPOST 2 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 547778 Telex 9657780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

COMPATIBLE WITH ALL I.L.P. MODULES

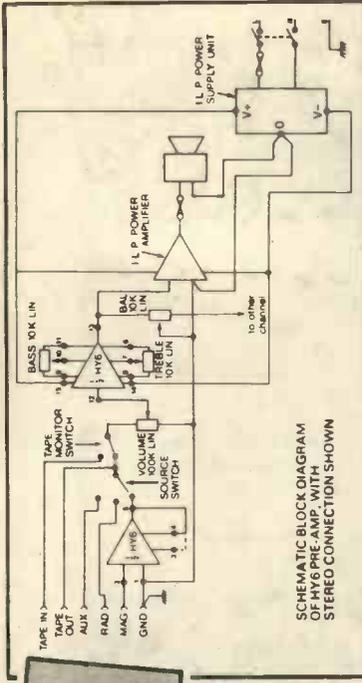

SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP, WITH STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 V

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, as a young man in 1971, Ian L. Potts founded his now world-famous company, he realised the need for a different and more rational approach to the maximum potential of modular construction. New thinking was badly needed. The result was a range of modules completely revolutionary in concept. The rightness of Ian Potts' thinking is shown in the size of the company today. Its new factory, its vast exports, its ace planes and better New as the modules to build with. The range grows and better. New lines (the way replacing existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there - we don't rest on our laurels.

BRITAINS FASTEST GROWING MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply.....

Total purchase price £.....

I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.....

NAME.....

ADDRESS.....

Signature.....

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE



I.L.P. ELECTRONICS LTD.


FREEPOST 2 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 547778 Telex 9657780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

ALL U.K. ORDERS DESPATCHED POST FREE

VERO VERO VERO

Metal Cases

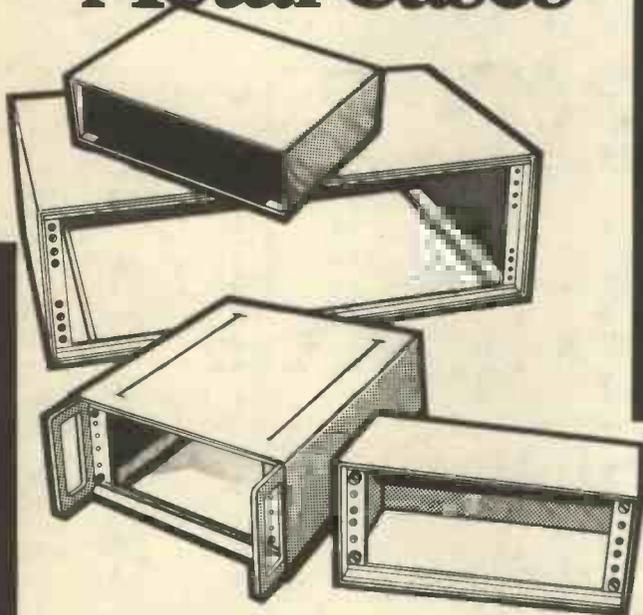

Our catalogue contains small metal enclosures for every application including the attractive new G range cases, with unique integrated chassis and sloping visor front and the inexpensive kit-form Veropak. We've also got circuit boards, accessories, module frames and plastic boxes — all to the highest standard to give your equipment the quality you demand. Send 40p to cover post and packing and the catalogue's yours.



VERO ELECTRONICS LTD RETAIL DEPT.
Industrial Estate, Chandler's Ford,
Hampshire SO5 3ZR
Tel: (04215) 62829

MONITORS MONITORS MONITORS



Uncased from 3" to 12"
Cased from 5" to 20"

Semi professional or professional available from stock.

Monitor PCB's including Transformers and Tubes also in stock.

Phone or write for details.

CROFTON ELECTRONICS

Crofton Electronics Limited
35 Grosvenor Road, Twickenham, Middx.
Tel: 01 891 1513

FLADAR TRANSFORMERS

PRIMARY 0-240V 50Hz


SEND FOR OUR TRANSFORMER CATALOGUE PRICE £1.00 WHICH INCLUDES A 50p VOUCHER OFF YOUR FIRST PURCHASE.

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
08FE06	6+6	0.5A EACH	1.99	60p	08FE60	15-0-15	0.4A	1.95	60p
12FE06	6+6	1A EACH	2.66	75p	08FE40	9-0-9	1A	2.35	60p
20FE06	6+6	1.6A EACH	3.38	75p	08FE60	15-0-15	0.5A	2.35	60p
50FE06	6+6	3A EACH	4.02	90p	12FE40	9-0-9	1.5A	2.60	75p
60FE06	6+6	4A EACH	5.03	125p	12FE50	12-0-12	1A	2.60	75p
					12FE60	15-0-15	0.8A	2.60	75p
08FE09	9+9	0.3A EACH	1.99	60p	20FE50	9-0-9	2A	3.30	75p
08FE09	9+9	0.5A EACH	2.40	60p	20FE60	12-0-12	1.6A	3.30	75p
12FE09	9+9	0.7A EACH	2.66	75p	20FE70	15-0-15	1.2A	3.30	75p
20FE09	9+9	1A EACH	3.36	75p	20FE80	20-0-20	1A	3.30	75p
50FE09	9+9	2.5A EACH	4.02	90p	20FE100	30-0-30	0.6A	3.30	75p
60FE09	9+9	3A EACH	5.03	125p	50FE50	9-0-9	5A	4.00	90p
					50FE70	15-0-15	3A	4.00	90p
08FE12	12+12	0.2A EACH	1.99	60p	50FE80	20-0-20	2A	4.00	90p
08FE12	12+12	0.3A EACH	2.40	60p	50FE110	30-0-30	1.4A	4.00	90p
20FE12	12+12	0.8A EACH	3.36	75p	60FE70	15-0-15	4A	5.00	125p
50FE12	12+12	1.8A EACH	4.02	90p	60FE80	20-0-20	3A	5.00	125p
80FE12	12+12	2.5A EACH	5.03	125p	60FE100	28-0-28	2.2A	5.00	125p
80FE12	12+12	3A EACH	6.20	125p	60FE110	30-0-30	3A	5.00	125p
08FE15	15+15	0.2A EACH	1.99	60p	80FE40	12-0-12	6A	6.15	125p
08FE15	15+15	0.25A EACH	2.40	60p	80FE50	15-0-15	5A	6.15	125p
12FE15	15+15	0.4A EACH	2.66	75p	80FE60	20-0-20	4A	6.15	125p
20FE15	15+15	0.6A EACH	3.36	75p	80FE80	28-0-28	2.5A	6.15	125p
50FE15	15+15	1.5A EACH	4.02	90p	80FE70	24-0-24	3A	6.15	125p
60FE15	15+15	2A EACH	5.03	125p	80FE90	30-0-30	2.3A	6.15	125p
80FE15	15+15	3A EACH	6.20	125p					
08FE20	20+20	0.15A EACH	1.99	60p	90FE50	15-0-15	5A	6.30	150p
12FE20	20+20	0.28A EACH	2.66	75p	90FE80	28-0-28	3A	6.30	150p
20FE20	20+20	0.5A EACH	3.36	75p	100FE30	30-0-30	3A	6.30	150p
50FE20	20+20	1.2A EACH	4.02	90p	100FE26	26-0-26	3.5A	6.60	150p
60FE20	20+20	1.5A EACH	5.03	125p	100FE28	28-0-28	3A	6.60	150p
80FE20	20+20	2A EACH	6.20	125p	100FE30	30-0-30	3A	6.60	150p
					100FE36	36-0-36	3A	6.60	150p
BATTERY CHARGER TRANSFORMERS									
48FE12	0-6-12	4A	5.00	125p	150FE15	15-0-15	6A	8.20	180p
66FE12	0-6-12	5A	5.80	125p	150FE28	26-0-26	5A	8.20	180p
70FE12	0-6-12	6A	6.15	150p	150FE30	30-0-30	4A	8.20	180p
90FE12	0-6-12	8A	7.40	150p	150FE38	36-0-36	4A	8.20	180p
					150FE42	42-0-42	3A	8.20	180p
06FE30	6-0-6	1.5A	1.95	60p	250FE28	28-0-28	8A	9.02	200p
06FE40	9-0-9	0.5A	1.95	60p	250FE30	30-0-30	7A	9.02	200p
06FE50	12-0-12	0.5A	1.95	60p	250FE42	42-0-42	5A	9.02	200p

FLADAR ELECTRIC
SOUTHVIEW DRIVE
P.O. BOX 19
WESTCLIFF-ON-SEA
ESSEX 0702-613314

TRADE ENQUIRIES
WELCOME

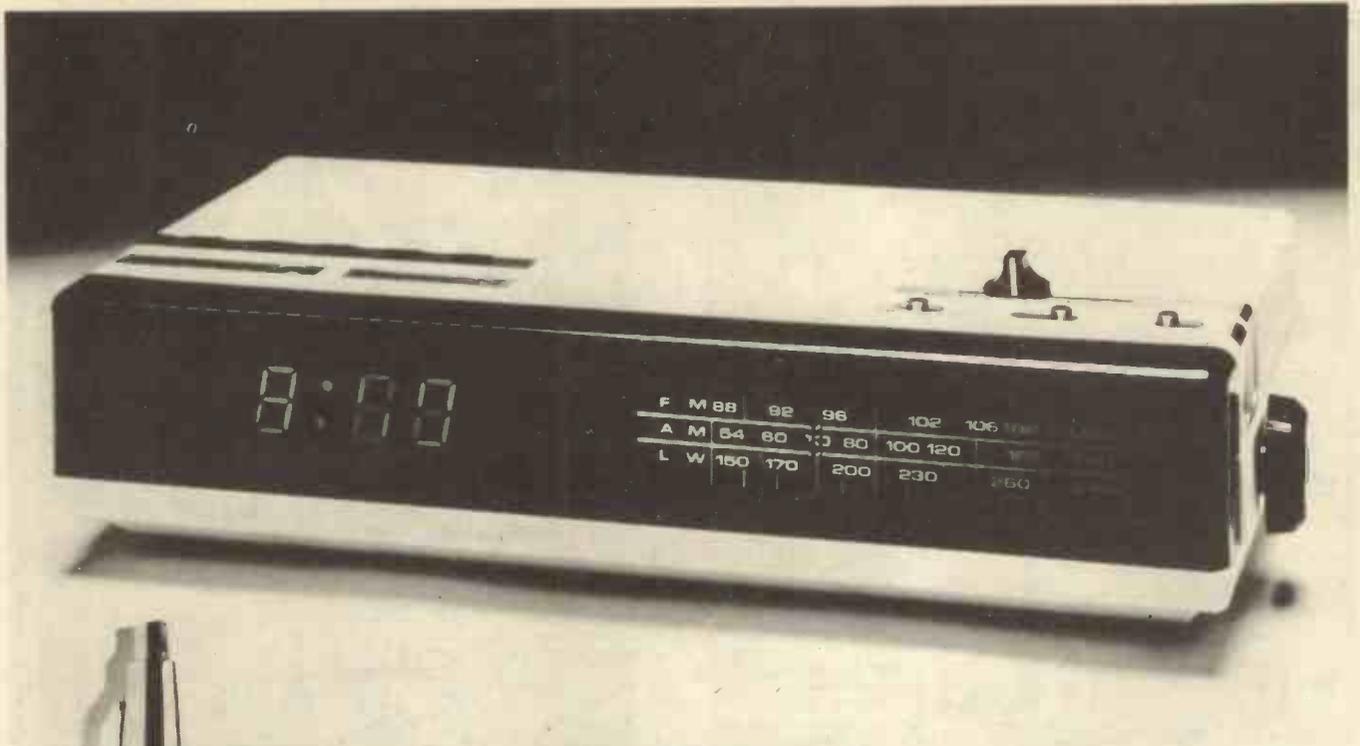PAYMENT TERMS:
C.W.O. Cheques,
Postal Orders
All Prices include 15% V.A.T.



MITRAD

The premier mail order house specialising in quality products and superior after-sales care.

ZETRON CLOCK RADIO Full fidelity AM-FM-LW radio with green tube electronic time display. Alarm, settable anywhere in 24 hour period, can also activate radio to provide wake-to-music facility. 60 minute sleep timer with auto shut-off and touch snooze control. Auto brightness control. Power failure indication.

£16.95 + 85p p&p.

SEIKO QUARTZ LCD MEMORY-BANK CALENDAR WATCH

Displays hour, minute, second, month, day of the week and date in 12 hour indication – or 24 hour at the touch of a button. Button touch also display month and year and dates for

a designated month with Sunday dates flashing. Stores dates in memory up to 11 ahead, flashes 'MEMO' on designated dates. Illuminated time and calendar display. Display flashes when battery nears life end. Stainless steel case and wrist strap (adjustable). In presentation case with instructions.

£49.95 + 85p p&p.

PANTER QUARTZ PEN WATCH

Five function LCD pen watch showing hours, minutes, seconds, month and date. Computerised four year date memory. Ball point pen. Stainless steel case. Price includes presentation case and full instructions.

£12.00 inc. p&p.

From the collection of 12 month guaranteed leading make products offered through Mitrad's 48 hour distribution system and backed by Mitrad's own service organisation. For complete product range, ring or write for catalogue. Trade price list available for bulk buyers.



To: Mitrad, 68-70 High Street, Kettering, Northants.

Please send me:

Zetron clock radio(s) at £17.80 inc p&p

Seiko Watch(es) at £50.80 inc p&p

Pen Watch(es) at £12.00 inc p&p

Total value of my order £

I enclose cheque/PO or debit my Access/Barclaycard



No. _____ Signature _____

Name _____ (block letters please)

Address _____



Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention. All orders despatched within 48 hours. Delivery subject to availability. Full refund if not completely satisfied. Mitrad. Registered in England No. 1500613. Code: PE/11/80



MITRAD 68-70 High St.,
Kettering, Northants.
Telephone 0536 522024

3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC **£29.90**



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

STEREO DISCO MIXER/PREAMP

LBPA3
M - Magnetic
C - Ceramic **£30.70**



Magnetic or ceramic deck versions - please state NEW ADVANCED MODEL AVAILABLE All the requirements of a stereo disco preamp on one board, left and right deck mixers/controls/mic, mixer/tones/mic auto fade over decks and P.F.L. The unit can be used with either LB100/150/250. LBPA3PS - Regulated supply - **£10.50**. Full set of pots - **£8.63** Sliders - **£11.21**

3 CHANNEL SOUND/LIGHT

LB31000SL **£21.40**



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

LPBA2 **£17.20** LPBA1 **£19.50**

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots £2.74, sliders £8.23.

A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots £3.27, sliders £4.49.

3-WAY ACTIVE CROSSOVER

LBAC01 **£17.90**



LBPSU1 **£6.20**

Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01.

2/4/8 CHANNEL CHASER

LB81000LC **£26.50**



An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

POWER AMPLIFIERS

Tough driving power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatinks and rugged o/p devices (all operate down to 4 ohms).

25W R.M.S.	100W R.M.S.	150W R.M.S.	250W R.M.S.
20Hz to 60K 0.07% THD	5Hz to 25K 0.1% THD	5Hz to 25K 0.1% THD	5Hz to 25K 0.1% THD
96DB S/N LB75	110DB S/N LB100	110DB S/N LB150	110DB S/N LB250
£11.20	£18.20	£26.50	£39.50

Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

4 CHANNEL SEQUENCER

LB41000LS **£17.50**



A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

POWER SUPPLIES

LB25PS **£11.20** P/P £1.20
LB100PS **£14.70** P/P £1.40
LB150PS **£18.00** P/P £1.40
LB250PS **£24.50** P/P £1.70

LBRLD1 **£5.70**

A de-thump unit for use with any LB power amps.

1 AND 3 CHANNEL DIMMERS

LB31000LD **£14.70**



Single channel version LB11000LD **£6.70**

Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppression. The unit is also available without rotary pots for use with sliders - LB31000LD (no pots) **£13.50** Sliders **75p** each.

PIEZO HORNS

£5.75 P/P 50p



ROPE LIGHTS/DRIVER

LB41000LC-S **£22.70**



24 feet ropes Red/Yellow Blue/Green

ROPE LIGHTS **£41.40**

A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control

CELESTION LOUSPEAKERS

(8 ohms)

G12-65 (12 inch 65W)	G12-100 (12 inch 100W)	G12-125 (12 inch 125W)
£20.70 P/P £1.70	£26.45 P/P £1.70	£46.00 P/P £2.00

NEW - MINI MODULES - NEW

Ingenuously designed mini pre-amplifier building blocks for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.

LBMM1 Pre-amp for mics, guitars etc.
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5
LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5
LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5
LBPSU1 ± 15V supply for up to 8 modules
LBPSU ± 15V regulated for up to 50 modules
MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £6.70; MM5 £6.70; PSU1 £6.20; RPSU £14.50.

L & B ELECTRONIC MODULES


PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon, Surrey CR0 3EB. Tel. 01-689 4138

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months. All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.O. (registered cash/bac/credit card) or access number. C.O.D. service £1 extra. For the new Autumn catalogue send 50p. (Full spec. shown.)

OHIO SCIENTIFIC SUPERBOARD II

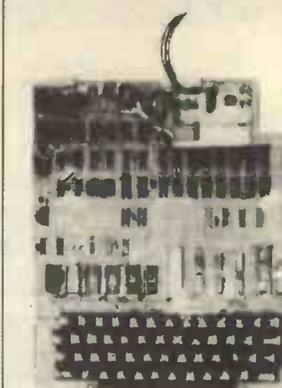50HZ BLACK AND WHITE SUPERBOARD II £159.95 + 15% VAT POST FREE. 50HZ COLOURBOARD II, THE NEW COLOUR VERSION £205 + 15% VAT.



50HZ UK BLACK AND WHITE SUPERBOARD II £159.95 + 16% VAT POST FREE. COLOURBOARD II £205 + 15% VAT.

THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST

- ★ If bought with superboard or colourboard these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit £7.95 (£11). 4K extra ram £20 (£24). Display expansion kit approx 30 lines - 54 characters £15 (£20). Case £23 (£26). Colour conversion board fully assembled £45 (£45). Cassette recorder £13 (£15). Extended monitor £20 (£20).
- ★ Assembler/Editor £25 (£25). 610 Expansion board £160 (£160).
- ★ Minifloppy with psu and 2 copies DOS £275 (£275).

COMPUTER GAMES

Chess challenger 7 £79. Atari videogame computer £129. Space invaders cartridge £27.50 (only £17 if bought with the videogame computer).

SINCLAIR (THANDAR) PRODUCTS

SC110 10MHz oscilloscope £144.95. PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, mains adaptor £6.88. PDM35 £34.23, mains adaptor £4.20, case £2.07. DM350 £76.70. DM450 £102.17. DM235 £55.55. Accessories for all 3 models:- rechargeable batts £7.99, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95. TG105 £87. TF200 £150.

SUPER PRINT BOOMST



The ideal impact matrix printer for Superboard, UK101, pet, apple, trs80, 60 lines/minute, 5 print densities of 72, 80, 96, 120 or 132 chr/line. Tractor and friction feed for up to 91" tractor paper. Graphics with user definable set in ram. RS-232 20ma, IEEE488 and centronics I/O. SPECIAL OFFER:- Supplied with free word processor program and interface components £359 + 15% VAT.

SWANLEY ELECTRONICS

Dept. PE, 32 Golds Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13%. Official credit orders welcome.

PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L2 2DY

SEMICONDUCATORS. Texas TI038 TO3 power trans. 50p. 741 8 pin 22p. NE555 24p. TAG4443 SCR 45p. 723 14 PIN REGS. 35p. AD 161/2 MATCHED PAIRS 70p. 2N5062 SCR 18p. TL1209 RED LEDS 10 for 78p. B0238 28p. B0439 28p. MPT111 P.U.T.'s 40V, 200ma, 375mW 15p each. 2N3733 £1.78. Infra Red 0.2" LEDs 30p. Rectangular Red LED's 12p each. CA3020 I.C.'s 40p each.

MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY. 6-0-6 100ma. 9-0-9 75ma. 12-0-12 50ma. all 75p each. 12V 200mA 75p. 6V 500mA £1. 10p. 0-6V-0-6V 280mA £1.30.

PULSE TRANSFORMERS. 1:1 (GPO type) 30p. 1:1 plus 1 min. P.C. mounting 80p.

MINIATURE SOLID STATE BUZZER. 33x17x15mm. output at 3 feet 70db, only 15mA drain, operating voltage 2 types 6 or 12VDC 75p each.

LOUD BUZZER. 6-12 volts 63p. Rotary Alarm siren. 12VDC. Red plastic body and mounting bracket 68x75mm £4.50p.

POCKET MULTIMETER. MODEL NM86 2,000 ohms per volt. 1,000 volts AC/DC. 100mA DC current. 2 resistance ranges to 1 meg £5.50p.

SOLDER SUCKER. High suction/teflon nozzle. £4.85p.

TRANSducers. 40KHz. RESENDER £3.50 pair.

MOTORS. 3V model type 22p. 6V cassette motor £1.20p. Replacement 12VDC 8 track motors 55p. Ex. equip. 5-7 volt cassette motors 70p. Low rev. mains motor 240VAC motor with gearbox 2 1/2 RPM 75p.

AMPHENOL COAX CONNECTORS. Plus 47p, Sockets 42p, Elbows 90p, Reducers 13p. Back to back sockets 65p. Back to back plus 65p.

HIGH IMPEDANCE HEADPHONES. mono 2,000 ohms imp. transducer type, adjustable band and padded earcups £2.75.

SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only £2.95p.

INTERCOM UNITS (can be used as baby alarm) supplied with approx. 60 cable, call button, 2 wds £5.28 pair. 3 way £7.25p. WIRELESS INTERCOM, 2 units both operate on 240VAC and mains connected. AM frequency 180KHz. £29.95p.

MINIATURE TIE PIN MICROPHONE. Omni. 1K imp. uses dead air battery (supplied) £4.95p. LOW COST CONDENSER MICROPHONE. Stick type. Omni, 500 ohms, on/off switch, standard jack plug only £2.95p. EM807 CONDENSER MICROPHONE. Highly polished metal stick mike, uni directional, 600 ohms 30-18KHz, on/off switch only £7.95p. DYNAMIC STICK MIKE. CARDIOD. dual imp. 600 ohms or 20K. 70-15KHz, attractive black metal case only £7.75p.

JACKSONS (280 50p each. VARIABLE CAPS. 50p each.

Special clearance offer of tools. (1) Side Cutters, (2) Long nosed Pliers, (3) Heavy duty pliers. insulated handles, all at £1.00 each.

CRIMPING TOOL, for standard terminals also 6 gauge stripper and wire cutter, insulated handles only £2.30. Cash with order please, official orders welcome from schools etc. please add 30p post and packing. VAT inclusive. ALL ORDERS DESPATCHED BY RETURN POST

Top Priority for every constructor-HOME RADIO CATALOGUE

- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

Send cheque or P.O. for £1.50

HOME RADIO Components LTD

Dept. PE, P.O. Box 92, 215 London Road, Mitcham, Surrey. 01-543 5659

Marshall's

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582
Also retail shops: 325 Edgware Road, London W2.
40 Crickwood Broadway, London NW2. 85 West Regent St., Glasgow.
108A Stokes Croft, Bristol.

Build the P.E./Marshall's Teletext Project and convert your standard colour television receiver to receive Teletext and Oracle. We can supply either a complete kit of parts at £200 inclusive of VAT/postage & packing, alternatively kits of parts for the various sub assembly as follows:

- | | | |
|--|--------|------------------------------|
| 1. Transmitter | £19.00 | |
| 2. Receiver | £13.00 | |
| 3. Decoder (supplied as a complete unit) | £87.00 | All prices inclusive of VAT, |
| 4. Summer Board | £27.00 | postage & packing. |
| 5. Tuner | £60.00 | |
| 6. Power Supply | £16.00 | |
| 7. Hardware and other parts | £ 9.00 | |

We accept American Express: Access: Barclay Card: Diners Card: also our own Marshall's Credit Charge.



Phone your order now to Margaret O'Donnell on 01-624 0805

Get a great deal from
Marshall's

NEW! LERNA-KITS!

● HIGH QUALITY EDUCATIONAL KITS

- LATEST SOLID STATE TECHNOLOGY – DESIGNED & MADE IN THE U.K.
- DETAILED STAGE BY STAGE BUILDING INSTRUCTIONS
- FREE ADVISORY SERVICE THROUGHOUT THE BUILDING
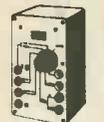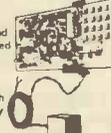
<p>LK1 OSCILLOSCOPE Solid state circuitry; D.C. coupled; 7 cm. dia. tube; Y input 0.3 v/cm to 50 v/cm.; X input 1 volt/cm.; 1x and 10x. cal. signals; response to 1MHz; Time base ranges to 8µs per cm.; Size 230 x 130 x 190mm. Wt. 2 Kg. Operates from 110 volt or 220/240 volt A.C. High quality kit complete with carrying case</p>  <p>£130.00</p>	<p>LK2 DIGITAL MULTIMETER Solid state circuitry with large digital display. Ranges are up to 1000v. D.C. and A.C. and current D.C. to 100mA. Resistance ranges 100 K ohms. Battery operated. Size 185 x 110 x 90mm. Digital display: 37 x 16mm</p>  <p>£40.00</p>	<p>LK5 DIGITAL ELECTRONIC TECHNIQUES Experiments carried out on a P.C. board, size 190 x 150mm covering operational amplifiers; integrators; basic logic circuits; NAND, NOR gates; Flip-Flops; Multi-vibrators; clock generators; 8 bit comparator feed back; analogue switching; building simple digital meter circuits; Timer. Note:- for full benefit with this kit a C.R.O. is desirable although circuits can be built without one.</p>  <p>£35.00</p>	<p>LK6 LOGIC DEMONSTRATION PANEL Basic introduction to computer technology; AND and OR gates; NOR and NAND; Data line selector; Truth tables; AND and INVERT gate; Half and Full Adder; Latches; Flip-Flops; Shift register; Binary coded decimal counter. Over 16 experiments are performed with panel. Battery operated.</p>  <p>£70.00</p>
<p>LK3 HOME COMPUTER Ideal simple computer for beginners. Microprocessor has 8 bit data bus and 12 bit address bus. Ready programmed ROM has 4K bits. RAM of 0.5 x 8k bits fully addressable. 8 digit LED display. Hexadecimal read out. Hexadecimal keyboard. Reset switch and single shot facility. Power supply kit included. Provision for cassette and V.D.U. operation.</p>  <p>£190.00</p>	<p>LK4 AUDIO GENERATOR Covers 10Hz to 100kHz in four switched stages. Variable voltage output. Distortion below 0.02%. Sine and square wave output. Ideal for Hi-Fi work and as signal tracer.</p>  <p>£40.00</p>	<p>LK7 ANALOGUE TEST METER Basic multi range test meter kit with 20,000 ohm/volt sensitivity. Ranges: D.C. and A.C. volts 0.5, 0.25, 0.100, 0.500; 2.5kV. D.C. 0.5mA, 0.500mA, 0.50µA. Resistance 0.50K; 0.5M. Size 150 x 75 x 50mm.</p>  <p>£17.00</p>	<p>LK8 SHORT WAVE RECEIVER A simple 3 stage short wave only radio receiver for the amateur. Very good selectivity and sensitivity and will give hours of enjoyment. Simple to construct by people of any age.</p>  <p>£25.00</p>

LERNAKITS, 4 Cleveland Road, Jersey, Channel Islands. (Est. 40 years)

To:— LERNAKITS, 4 Cleveland Road, Jersey, Channel Islands. (Est. 40 years)

PE/11/819

Please supply Kit at £..... add £2 postage U.K. only.

£10 postage overseas Air Mail.

Catalogue available on receipt 12p stamp.

BLOCK CAPS PLEASE

NAME

ADDRESS

ALL CREDIT CARDS ACCEPTED

Name of Card

No.

(Dispatch is normally within 1 week of receipt of order)

Signature

Base 2

MODEL 800MST 80 COLUMN HIGH PERFORMANCE
IMPACT PRINTER

- suitable for most Micros.

JUST LOOK AT THESE STANDARD FEATURES:-

*RS-232, 20mA, IEEE 488 and Centronics I/O
*15 Baud rates to 9,600 *100 Chrs. per second -
Bidirectional *6 print densities 60, 72, 80, 96,
120 or 132 Chr/line * Self test switch * 96 Chrs.
ASC II Standard * Auxilliary User Defined Ch.
set * Tractor and fast paper feed/graphics
* 2k Buffer * Accepts 8 1/2" max. paper pressure
feed and 9 1/2" max. paper tractor feed.

FREE
INTERFACE
CABLE
WORTH
£25

ONLY
£359 + VAT

Compukit UK101 DISC DRIVES

with up to 32k RAM expansion

free
games
disc

* 9 Digit extended Basic
* Plugs straight into 8k Compukit requires
no hardware mods. (5v.5A required for 610)
610 Expansion (8k) ONLY £159 + VAT
Disc Drive with DOS ONLY £285 + VAT

VERBATIM 5 1/4" DISCS £1.85 each (min. 10) + VAT STATIC RAM 2114 1-12 £3 each + VAT 13+ £2.50 each + VAT

EXATRON Stringy Floppy

COMBINES ECONOMY OF CASSETTE
WITH SPEED & RELIABILITY OF DISC

16k loads in approx. 24 secs. - Wafers to
75ft (48k approx.)

ONLY
£188
+ VAT

Versions for
PET
APPLE
TRS80

Stringy Floppy with 10 Wafers (Tapes)
BUS EX. 2 for 1. Machine Lang. Monitor

Ohio Superboard II & Challenger IP with FREE RAM

- the no fuss start to Micro's.

* Ready Built *8k Microsoft in ROM, 6 digit floating
point basic plus full features. 4k RAM - expandable to 32k



FREE
ADDITIONAL
4k RAM with
SII & CI
WORTH £24

All 50Hz
operation

SUPERBOARD II (24x24 format) £159 + VAT
SUPERBOARD II (48x32 format) £199 + VAT
POWER SUPPLY 5v.3A. . . . £27 + VAT
CASE £29 + VAT
CHALLENGER 1P (24x24 format) £219 + VAT
CHALLENGER 1P (48x32 format) £259 + VAT
(Superboard is used in Challenger)

Mighty Micro

for a Mighty good deal !!!

Please add V.A.T. at 15%. Carriage extra, will advise at time of order. Official orders welcome.

61 NEW MARKET SQUARE, BASINGSTOKE, HAMPSHIRE. RG21 1HW

Telephone: Basingstoke (0256) 56468 and 56417

Buy in confidence. If on receipt of your order the goods do not meet with your satisfaction,
return within 7 days for full refund. Credit facilities arranged.



J. BIRKETT

(Partners: J. H. Birkett, J. L. Birkett)

Radio Component Suppliers

25 The Strait, Lincoln. LN2 1JF

Telephone: 20767

TTL SN 7474 DUAL D TYPE TRIGGERED FLIP-FLOP = 15p.
6 To 12 VOLT MINIATURE RELAYS SPCO 5 Amp Contacts = 60p.
GLASS WIRE ENDED CRYSTALS 28 KHz, 28.5 KHz, 29.75 KHz, 31.5 KHz All
at 50p each.
87G CRYSTALS 3600 C/S or 3660 C/S Both £1.30 each.
TTL SN 7486 QUAD EXCLUSIVE OR GATE = 15p.
PLASTIC BC 108 or BC 212 TRANSISTORS 6 for 50p.
ST53 PLESSEY RF SIGNAL TRANSISTORS NPV at 6 for 50p.
500 METRE OF PVC CABLE 13 Strands 1.019 at £10. Carr. Paid.
20 WAY LUCAR TAG CONNECTING BLOCKS = 60p.
POWER TRANSISTORS BDY 57 120 Volt 25 Amp = £1.30, BDY 91 100 Volt 15 Amp =
80p, 2N 5039 120 Volt 10 Amp = £1.15, 2N 6354 150 Volt 10 Amp 80 MHz = £1.15, 2N
6496 150 Volt 10 Amp 60 MHz = £1.15.
GERMANIUM PNP OC 20 = £1, AL 103 = 75p, AD 149 = 75p.
WIRE WOUND POTENTIOMETERS 2 Watt 2K, 5K, 10K, All 30p each. 4 Watt 2.2K, 10K
Both at 30p.
TOGGLE SWITCHES Long Dolly Type On-Off = 35p.
CHROME BULGIN ONE MAKE ONE BREAK = 30p.
9 VOLT ITRON 9 DIGIT SEVEN SEGMENT DISPLAY FG95A = £1.80.
MIDGET MICRO SWITCHES with Lever SPCO = 20p.
QUAD COMPARATOR LM 339 with data = 50p.
INTEL P4001 256X8 MASK PROGRAMMABLE ROM AND 4 BIT IN-OUT PORT with
data = 60p.
87G CRYSTALS 327.56 KHz, 327.86 KHz, 10.025 KHz, MINIATURE DUAL CRYSTAL
20.1875 MHz + 20.2375 MHz All at 50p each.
HOUSE CODED TTL I.C.'s 7400, 7410, 7400, 7430, 7453 All at 6 for 50p.
20 PHOTO TRANSISTORS AND DARLINGTONS Assorted Untested for £1.
50. OC 71 TRANSISTORS Untested for 75p.
MINIATURE MULTI-TURN POTENTIOMETERS 5K Lin = 30p.
MINIATURE POTENTIOMETER 250K Lin, 1 Meg Lin Both 4 for 50p.
WIRE ENDED 30 UH R.F. CHOKES at 25 for 50p.
MIKE INSERTS TYPE YA 8548 at 40p each.
TRANSFORMERS 240 Volt Input, Output Type 1. 24 Volt Tapped at 14 Volt, = £1.30 (P&P
25p). Type 2. 30-0-30 Volt 500 mA = £1.30 (P&P 25p). Type 3. 45 Volt 2 Amp, 45 Volt 500
mA = £3.50 (P&P 90p). Type 4. 20 Volt 1 Amp Twice 10 Volt 1 Amp Twice = £4.50 (P&P
95p). Type 6. 16 Volt 2 Amp = £1.60 (P&P 25p). Type 9. 13 Volt 1 Amp = £1.60 (P&P 25p).
TANTALUM CAPACITORS .1uf 35v.w., .22uf 35v.w., .33uf 35v.w., .47uf 35v.w., 1uf
35v.w., 2.2uf 35v.w., 3.3uf 16v.w., 4.7uf 16v.w., 4.7uf 35v.w., 6.8uf 35v.w., 10uf 10v.w., 10uf
25v.w., 2.2uf 16v.w. All at 9p each. 100uf 10v.w., 150uf 10v.w., Both 25p each.
OP-TO ISOLATOR 1L74 at 50p each.
0.9 OHM 100 WATT W.W. RESISTOR ON CERAMIC FORMER = 75p.
50 SILVER MICA CAPACITORS assorted for 75p.
300 TO 75 OHM BALUM TRANSFORMERS = 20p.
MINIATURE TRANSISTOR TRANSFORMERS input types Impedance Ratio 100K To 1K
= 35p, Ratio 150K To 1K = 35p, Ratio 20K To 1K = 35p, Driver Types 10K To 2K = 35p, Out-
put Types 25mV 1.2K To 8 ohm = 35p, 250mV 500 ohm To 8 ohm = 35p, 500mV 400
ohm To 8 ohm = 35p.

Please add 20p for post and packing on U.K. orders under £2.
Overseas orders postage charged at cost.

MAIL ORDER PROTECTION SCHEME

INTRODUCTION

The Office of Fair Trading have agreed that the notice of the
Mail Order Protection Scheme to appear in periodicals carrying
mail order advertising should appear as follows:—

"MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to
the British Code of Advertising Practice. In respect of mail order
advertisements where money is paid in advance, the code re-
quires advertisers to fulfill orders within 28 days, unless a
longer delivery period is stated. Where goods are returned un-
damaged within seven days, the purchaser's money must be
refunded. Please retain proof of postage/despatch, as this may
be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this
magazine and pay by post in advance of delivery, Practical
Electronics will consider you for compensation if the Advertiser
should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned;
and
- (2) You write to the Publisher of Practical Electronics sum-
marising the situation not earlier than 28 days from the
day you sent your order and not later than two months
from that day.

Please do not wait until the last moment to inform us. When
you write, we will tell you how to make your claim and what
evidence of payment is required.

We guarantee to meet claims from readers made in ac-
cordance with the above procedure as soon as possible after the
Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct
response to an advertisement in this magazine not, for example,
payment made in response to catalogues etc., received as a
result of answering such advertisements. Classified adver-
tisements are excluded."

SERVICE TRADING CO

GEARED MOTORS

FT3 NEON FLASH TUBE

High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50, P. & P. 25p (£2.00 incl. VAT) 3 for £3. P. & P. 50p (£4.03 incl. VAT & P.).

WHY PAY MORE?

MULTI RANGE METER Type MF15A a.c. d.c. volts 10 - 50 250 500 1000 Ma 0-5 0-10 0-100. Sensitivity 2000V 24 range. diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.63 incl. VAT & P.)



METERS (New) - 90 mm DIAMETER

A.C. Amp., Type 8272, 0-1A, 0-5A, 10A, 0-20A, 50A A.C. Volt. 0-150V, 0-300V.
D.C. Amp., Type 65C5, 0-2A, 5A, 0-10A, 0-20A, 0-50A, 0-100A.
D.C. Volt. 15V, 30V.



All types £3.50 ea. + P. & P. 50p (£4.60 incl. VAT), except 0-50A, 0-100A. D.C. price £5.00 + P. & P. (£6.33 incl. VAT).

HEAVY DUTY SOLENOID m.f. by Magnetic Devices 240V. A.C. Intermittent operation. Approx. 20 lb. pull at 1.25 in. Ex-equip. Tested. Price: £5.50 + 75p. P. & P. (£7.19 incl. VAT & P.).



12V D.C. SOLENOID

12V, D.C. heavy duty Solenoid 4 Kp. pull. Easily removable from plate. All chassis containing 4x24V. D.C. Push Solenoids (1 lb. approx.). 5-fig. Counter. 6 min. photo cells. Sub-min. Microswitches etc. Ex-equip. London Transport Printer. Price: £9.00 + £1.00 p. & p. (total incl. VAT £11.50).

12V, D.C. Solenoid approx. 1lb. pull. Price: £1.40 + p. & p. 30p. (total incl. VAT £1.96).

SOLENOIDS

WESTOOL SERIES D6 Model A3 24V, D.C. Price £1.50 + 50p p. & p. (Total incl. VAT £2.30)
WESTOOL SERIES D4 Model A. 24V, D.C. Price £1.00 + 30p p. & p. (Total incl. VAT £1.50)
AG/GT 24V, D.C. 70 ohm Coil Solenoid. Push or Pull. Adjustable travel to 3/16 in. Fitted with mounting brackets and spark suppressor. Size: 100 x 85 x 25 mm. Price: 3 for £2.40 + 30p. P. & P. (min 3 off) (£3.11 incl. VAT & P.).

800 WATT DIMMER SWITCH

Easily fitted. Will control up to 800 W. of all lights except fluorescent at mains voltage. Price: £3.90 + 50p. p. & p. (£5.06 incl. VAT).



REED SWITCHES. Size 28mm x 4mm dia. Price: 10 for £1.00 + p. & p. 20p. (total incl. VAT £1.38). 100 for £8.00 + p. & p. 30p. (total incl. VAT £9.55).

MICRO SWITCHES

Sub. Min. Honeywell Lever m/s type 3115m 906ft. 10 for £3.50 plus post paid (£4.03 incl. VAT)
These V3 types
Button type (Pye) 10 for £3.00 (£3.45 incl. VAT)
Short Lever type 16amp. rating (Grouzet) £4.00 (£4.80 incl. VAT)
Roller Type (Bonnella) 10 for £3.50. (£4.03 incl. VAT). N.M.S.a
D.P. C/O lever m/s with mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total incl. VAT £2.93 (min. 10).



SOLID STATE EHT UNIT

Input 230V ac. Fully isolated output 10mm spark. Approx. 15kV. Built in 10 sec. Timer. Easily modified for 20 sec. 30 sec. to a continuous operation.
Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg. supplying neon or argon tubes etc., EHT, starter or ignitons for lamps VAC die GRAFF generator, loss of vacuum detector, OUDN coils etc.
Size: Length 155mm, width 85mm, height 50mm. Weight 530 grammes. Price £5.00 + 75 pence post & packing. Total incl. VAT £6.71.

A.E.G. CONTACTOR

Type LS6/L11. Coil 240V 50 Hz. Contacts - 3 make: 600V: 20amp. 1 break: 600V: 20 amp. Price: £5.50 + 50p P. & P. (£6.90 incl. VAT & P.).

ARROW-HART MAINS CONTRACTOR. Cat. No. 130A30. Coil 250V, or 500V. A.C. Contacts. 3 make 50 amp up to 660V. A.C. 20 hp at 440V. 3 phase 50 Hz. Price: £7.75 + p. & p. £1.00 (incl. VAT, total: £10.06). N.M.S.

SMITH BLOWER

Type FFB. 1706. Small, quiet, smooth running. 240V. A.C. operation. Output aperture 45x40cm. Overall size 135 x 165 cm. Flange mounting. Price: £4.25. P.&P. 75p. (Total: £5.75 inc. P. & VAT. N.M.S.)

Other types available. S.A.E. for details

AIRFLOW DEVELOPMENT LTD.

Centrifugal Blower Unit powered by GEC 230/250V. 2850 rpm. motor producing approx. 120 c.f.m. Aperture 65x90mm. Overall size 222x225x195mm. Incl: Starter Capac. Price: £18.00 + £2.00 p. & p. (Total incl. VAT £20.70)

24 volt. D.C. BLOWER UNIT

Precision 24 volt. D.C. 0-8 amp Blower that works well on 12V 0-4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P. & P. 75p (incl. VAT £5.04). N.M.S.

INSULATION TESTERS NEW!

Test to I E E Spec Rugged metal construction suitable for bench or field work constant speed clutch Size L Bin W 4in H 6in weight 6lb, 500V, 500 megohms, £49.30 Post 80p (£57.27 incl. VAT & P.). 1,000V, 1,000MΩ, £65. Post 80p (£64.17 incl. VAT & P. SAE for leaflet).
Yet another outstanding offer.



IMFD 600V Dubilier wire ended capacitors. N.M.S. 10 for £1.50 p&p 50p. (£2.30 incl. VAT + p&p) (Min 10)

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200 watt (1 amp inc. a.c. voltmeter)	£14.50
0.5 KVA (2 amp MAX)	£18.00
1 KVA (5 amp MAX)	£24.00
2 KVA (10 amp MAX)	£39.00
3 KVA (15 amp MAX)	£47.00
5 KVA (25 amp MAX)	£76.00
10 KVA (50 amp MAX)	£168.00
15 KVA (75 amp MAX)	£280.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual Input 200-240V. or 380-415V. Star connected.
3KVA 5 amp per phase max. £106.43
6KVA 10 amp per phase max. £159.37
10KVA 16 amp per phase max. £327.43
Carriage, packing & VAT extra.

LT TRANSFORMERS

13-0-13V at 1 amp £2.50 P. & P. 50p (£3.45 incl. VAT)
0-4V/6V-24V/32V at 12 amp £20.35 P. & P. £2.30 (£26.05 incl. VAT & P.)
0-6V/12V at 20 amp £16.20 P. & P. £1.00 (£19.78 incl. VAT)
0-12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£15.53 incl. VAT & P.)
0-6V/12V at 75 amp £9.10 P. & P. £1.50 (£12.19 incl. VAT)
0-6V/12V/17V/18V/20V at 20 amp £20.90 P. & P. £2.00 (£26.34 incl. VAT & P.)
0-10V/17V/18V at 10 amp £11.55 P. & P. £1.80 (£15.35 incl. VAT)
Other types in stock; phone for enquiries or send see for leaflet.

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f/s. Light output greater than many (so called 4 Joule) strobes. Hy-Light Strobe Kit Mk IV. £22.00+£1.50 P. & P. (incl. VAT total £27.03). Specially designed case and reflector for Hy-Light Strobe. Post £1.50 (£2.08 incl. VAT & P.). Super Hy-Light Strobe (approx. 16 joules) Price £33. P. & P. £1.50 (incl. VAT total £39.68). Suitable case £11.00 + £1.50 P. & P. (£14.38 incl. VAT & P.).
Super Hy-Light Strobe Kit, details on receipt of foolscap see

XENON FLASHGUN TUBES

Range available from stock. S.A.E. for details.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 Watt £8.70. incl. VAT £10.00 (callers only).
2ft. 20 watt £6.20. Post 35p (£7.99 incl. VAT + P.)
(For use in stan bi-pin fittings).
12in. 8 watt £2.60. Post 35p (£3.62 incl. VAT + P.)
9in. 6 watt £2.25. Post 35p (£2.99 incl. VAT + P.)
6in. 4 watt £2.25. Post 35p (£2.99 incl. VAT + P.)
Complete ballast unit, for either 6", 9" or 12" tube 230V AC op. £4.50. Post 45p (£5.69 incl. VAT + P.). Also available for 12V DC op. £2.00. Post 45p (£2.99 incl. VAT + P.)
40 watt UV lamp and ballast complete £38.00. Post £3.50 (£47.73 incl. VAT + P.). 400 watt UV lamp only £14.00. Post £1.50 (£17.83 incl. VAT + P.).

WIDE RANGE OF DISCO LIGHTING EQUIPMENT S.A.E. (foolscap) for details.

PROGRAMME TIMERS

240V A.C. operation. 12 individually adjustable cams £7.50 + 75p P. & P. (£9.49 incl. VAT). R. T.
6 adjustable 6 fixed cams. Price £8.00 + 75p p. & p. (£7.76 incl. VAT). R. T.

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.
25 WATT 10/25/50/100/250/500/1kΩ/1.5kΩ, £2.80. Post 20p (£3.45 incl. VAT & P.).
50 WATT 250Ω £2.90. Post 25p (£3.62 incl. VAT & P.).
100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £6.90 p. & p. 35p (£8.34 incl. VAT).
Black, Silver, Skirted knob calibrated in Nos. 1-9 1/2 in. dia. brass bush. Ideal for above Rheostats 24p each.



RELAYS

Wide range of A.C. and D.C. relays available from stock. Phone or write in your enquiries. N.M.S.
Other types available — phone for details.
230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.96 incl. VAT & P.).
T.E.C. open type 3 c/o. 10 amp £1.10 (£1.50 incl. VAT & P.).

MMK1, Relay, 230V, A.C. 1 c/o. open type 10 amp contact, mf. by "Keyswitch" 80p. + 20p. p. & p. (£1.15 incl. VAT). 5 for £3.75 postpaid (£4.32 incl. VAT).

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 incl. VAT & P.) Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.38 incl. VAT & P.) Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.67 incl. VAT & P.) Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.78 incl. VAT & P.) 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.78 incl. VAT & P.). (amps = contact rating). P&P on any Relay 20p.

Hellermann Deutsch. Hermetically sealed sub-min. Relay. 12-24V. D.C. 2 c/o. 850 ohm coil. 0.2 pitch. P.C. mounting. L 20mm. W. 10mm. H. 12mm. Fraction of maker's price: £2.50 postpaid (£2.88 incl. VAT). N.M.S.

Diamond H heavy duty A.C. relay 230/240V a.c. two C/O contacts 25 amps res at 250 a.c. £2.50 p&p 50p. (£3.45 incl. VAT + p&p). Special base 50p. (incl. VAT 50p) N.M.S.

71rpm KLAXON motors approx. 25lb inch


28rpm WYNSCALE motors approx. 20lb inch
71rpm WYNSCALE motor approx. 10lb inch
Above four motors are designed for 110V. A.C. supplied with auto transformer 240V. A.C. operation, £9.25 p. & p. 75p. Total incl. VAT £11.50. N.M.S.



19 rpm FHP 220/240V. a.c. reversible, torque 14.5kg. Gear ratio 144-1. Brand new including capacitors. mf. CITENCO. Price: £14.25 + £1.25 P. & P. (£17.83 incl. VAT). N.M.S.



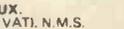30 rpm 230/240V. a.c. 50lb in. mf. PARVALUX. Price: £18.00 + £1.50 P. & P. (£19.98 incl. VAT). N.M.S.



56 rpm. 240V. a.c. 50lb in. 50Hz 0.7 amp. Shaft length 35mm. Dia. 16mm. Vt. 6kg. 600p. mf. FRACOM. Price: £15.00 + £1.50 P. & P. (£18.98 incl. VAT). N.M.S.




100 rpm. 110V. a.c. 115lb in. 50Hz. 2.8 amp. single phase split capacitor. Immense power.



Totally enclosed. In-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 16.5mm, length 145mm. Tested. Price: £12.00 + £1.50 P. & P. (£15.53 incl. VAT). R. & T. Suitable transformer for 230/240V operation. Price £8.00 + 75p. P. & P. (£10.06 incl. VAT).

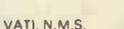200 rpm. 35 lbs in. 115V. 50Hz. Price: £16.00 + £1.50 P. & P. (£20.13 incl. VAT). N.M.S.



Suitable Transformer for 230/240V. a.c. Price: £9.00 + £1.00 P. & P. (£10.35 incl. VAT). N.M.S.

1 rpm 230/240V. a.c. Synchronous geared Motor, mf. HAYDON.
2 rpm 230/240V. a.c. Synchronous geared Motor, mf. CROUZET. Either type £3.90 + 30p. P. & P. (£4.83 incl. VAT).

230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2 in. or 4 blade 3 in. aluminium fan. Price £3.50 P. & P. 65p (£4.77 incl. VAT & P.).



24V. D.C. GEARED MOTOR


24V. D.C. 200 rpm 10lbs/ins. continuously rated geared Motor mfg. by either Parvalux or Carter. Easily removable from heavy all. chassis containing 9x24V. D.C. Solenoids, microswitches, friction clutch, precision gearing etc. Ex-equipment London Transport Ticket Printer. Price: £11.00 + £2.00 p. & p. (total incl. VAT £14.95).

24V. D.C. REVERSIBLE MOTOR

Parvalux type SD12L, 24 D.C. shunt wound Motor, either 133 rpm 6lbs in Gearbox ratio 30:1. Current 6.8 amp. Rating continuous. Will operate on reduced power and speed at 9V D.C. or less. Size Dia. 1.6mm. Width 150mm. Shaft dia. 16mm. Price £16.00 + £2.00 p. & p. (£20.70 incl. VAT). N.M.S. or 60 rpm 100lb in rating. Price as above. N.M.S.
100W Rheostat 1 ohm speed control available £6.90 (£7.94 incl. VAT).

ROTARY CARBON VANE VACUUM & COMPRESSOR.

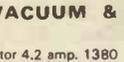Direct coupled to 1/3 hp. 110/115V. A.C. Motor 4/2 amp. 1380 rpm. Motor manuf. by A.E.I. or G.E.C. Pump by Williams. Max. Vac. 25" H.G. Max. pressure cont. 10 p.s.i. Int. 15 p.s.i. Max. airflow 3 c.f.m. at "0" H.G. Price: £30.00 + £3.00 P. & P. (£37.95 incl. VAT). N.M.S.



Suitable transformer for 240V. op. £10.00 P. & P. £2.00 (£13.80 incl. VAT). N.M.S.

COMPRESSOR

Precision built USA. Horizontally opposed twin head diaphragm type producing 20lbs. approx. P.S.I. per head. 3.5 plus C.F.M. Output virtually pulse free. Powered by 110V A.C. motor size 30x23x15cm. Weight 7 kilos. Price £25.00 + £2.00 P. & P. (Total incl. VAT £31.05). N.M.S.



Suitable transformer for 240V op. £8.00 P. & P. £1.50 (£10.93 incl. VAT).

VERY EXCEPTIONAL OFFER

REDUCTION DRIVE GEAR BOX.
Ratio 72:1. Input spindle 1/4 x 1/2 in. Output spindle 1/2 x 3 in. long. Overall size approx: 120 x 98 x 68 mm. All metal construction. Ex-equip. tested. Price: £2.00 + 50p. (incl. VAT £2.88).

A.C. Wkg. TUBULAR CAPACITORS.

Fraction of makers price. Motor start etc.			
1.5 mfd. 400V. A.C.	80p	7.5 mfd. 200V. A.C.	£1.00
2 mfd. 250V. A.C.	80p	10 mfd. 250V. A.C.	£1.00
2 mfd. 450V. A.C.	75p	10 mfd. 400V. A.C.	£1.75
2.2 mfd. 440V. A.C.	75p	14 mfd. 400V. A.C.	£3.00
3 mfd. 440V. A.C.	£1.00	15 mfd. 250V.	
4.1 mfd. 440V. A.C.	£1.00	(Block)	£1.50
5 mfd. 400V. A.C.	£1.25	19 mfd. 280V. A.C.	£2.00
5.3 mfd. 160V. A.C.	80p	20 mfd. 250V. A.C.	£2.25
5.4 mfd. 280V. A.C.	75p	50 mfd. 370V.	£5.00
6.5 mfd. 280V. A.C.	£1.00	(Block)	
P. & P. up to 2.5 mfd. 25p. 3 mfd 20 mfd. 50p. 50 mfd. £1.50. All plus V.A.T. N.M.S.			

Time Switch Venner Type

ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £9.00. P. & P. 75p (£11.21). R. & T.



SANGAMO WESTON TIME SWITCH

Type S251 200/250V. a.c. 2 on/2 off every 24 hours 20 amps contacts with override switch dia. 4 x 3 price £8.50 P & P 50p incl. VAT £10.35. Also available with Solar dial. R. & T.

N.M.S. New Manufacturers Surplus R & T Reconditioned and Tested

SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01 995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10.00

All Mail Orders Callers

Ample Parking Space Showroom open Mon-Fri.

Personal callers only Open Saturdays

9 Little Newport Street, London WC2H 7JJ Phone 01-437 0576

Toroidal TRANSFORMERS



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as their now outdated laminated equivalents and hum is down to a negligible tenth of what it used to be. Supplied with rigid mounting kit with centre bolt, two neoprene and one steel washer. Available so far in a range of 37 sizes with more to come.

TYPE	VA	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	DIA. x HT in mm	WEIGHT Kg	PRICE
2X010	50	6+6	4.16	80 x 35	0.9	EACH £5.40 +£1.10 P&P +98p VAT
2X011		9+9	2.77			
2X012		12+12	2.08			
2X013		15+15	1.66			
2X014		18+18	1.38			
2X015		22+22	1.13			
2X016	25+25	1.00				
3X010	80	6+6	6.64	90 x 30	1.0	EACH £5.76 +£1.20 P&P +£1.04 VAT
3X011		9+9	4.44			
3X012		12+12	3.33			
3X013		15+15	2.66			
3X014		18+18	2.22			
3X015		22+22	1.81			
3X016		25+25	1.60			
3X028		110	0.72			
3X029		220	0.36			
3X030		240	0.33			
4X010	120	6+6	10.00	90 x 40	1.2	EACH £6.72 +£1.30 P&P +£1.20 VAT
4X011		9+9	6.66			
4X012		12+12	5.00			
4X013		15+15	4.00			
4X014		18+18	3.33			
4X015		22+22	2.72			
4X016		25+25	2.40			
4X028		110	1.09			
4X029		220	0.54			
4X030		240	0.50			
5X016	160	25+25	3.20	110 x 40	1.8	EACH £8.88 +£1.40 P&P +£1.54 VAT
5X017		30+30	2.66			
5X028		110	1.45			
5X029		220	0.72			
5X030		240	0.66			
6X016	300	25+25	6.00	110 x 50	2.6	EACH £12.27 +£1.50 P&P +£2.07 VAT
6X017		30+30	5.00			
6X018		35+35	4.28			
6X026		40+40	3.75			
6X025		45+45	3.33			
6X028		110	2.72			
6X029		220	1.36			
6X030		240	1.25			

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.

For 220V Primary insert 1 in place of "X" in type number.

For 240V Primary insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

* TYPES TO SPECIFICATION CAN BE SUPPLIED TO ORDER IN QUANTITY, AGENCIES IN CERTAIN COUNTRIES AVAILABLE ENQUIRIES INVITED

FREEPOST facility.

We pay postage on U.K. enquiries and orders. Simply address envelope to FREEPOST T5 to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order.

I.L.P. TRANSFORMERS
A division of I.L.P. ELECTRONICS LTD

FREEPOST T2 GRAHAM BELL HOUSE ROPER CLOSE
CANTERBURY CT2 7EP Phone (0227) 54778 Telex 965 780

TUNE IN to the new-look

NOVEMBER 1980

Practical wireless

65p

FOR THE RADIO ENTHUSIAST...

FREE

SURVEY OF 2m MULTI-MODES
'SLIM JIM' FOR 28MHz

AND FEATURING

HELDFORD PART 1

FREE LEAD BENDING GAUGE

HF SSB TRANSCEIVER

- New series featuring full instructions for constructing the **PW 'HELDFORD' Amateur Bands Transceiver**
- 'Slim Jim' for 28 MHz
- Survey of 2m Multi-Modes

November issue
OUT NOW 65p

Practical wireless

- December issue out Friday November 7
- Full instructions for making a **Synthesised Broadcast Bands Receiver** electronically tuned to automatic scanning facility.
- Plus **FREE WORKSHOP TWEEZERS**

Everything for OSI...

The superior Superboard...



Ohio Scientific's Superboard has been around for some time now — a superb introduction to small computing. Mutek now offer the superior Superboard — the same superb BASIC, the same keyboard, utterly reliable cassette interface and other features, but modified to run at double the standard speed and with more than double the standard display: 32 lines of 48 characters. More than twice the execution speed for BASIC than Commodore's Pet®; twice the display area of the UK101. The superior Superboard — a superbly practical small computer.

Enhanced C1 (C1E) £255
Complete with power supply, metal case and 4K user memory.

Superboard E £195
Uncased version of C1E.

Upgrade service or kit to convert existing Superboard, C1 or UK101 systems to Mutek's enhanced specification (ask for details) .. £40

All prices quoted exclude VAT.

a superior monitor...

CEGMON, 'the best thing for OSI systems since OSI itself', is now available! CEGMON is a new monitor PROM for all Ohio Scientific BASIC-in-ROM systems (Superboard/C1, C2 and C4 series) and UK101, written by the organisers of the OSI UK User Group. It gives these systems the kind of features that only appear on machines at least twice the price — a full screen editor, an incredibly versatile screen-handling system, a built-in expanded machine-code monitor, and much more.

□ **Full screen editing** — more flexible than simple line editing, the built-in twin-cursor screen editor allows you to edit, combine, copy or renumber program lines or text, copying from anywhere on the screen.

□ **Advanced display features** — all output to the screen display can be directed through 'windows' whose position, height and width are all user-definable, and can be changed within programs quickly and easily. The 'window' format allows free mixing of text and graphics; protected non-scrolling areas; and sophisticated use of multiple scrolling and non-scrolling zones. 'Window' and screen-clear routines and cursor-positioning controls; text is printed from the top of the current 'window'. Probably the most flexible screen-handling system available today, it offers a whole new world in small-computer display.

□ **Machine-code support** — memory 'modify' allows entry of text or graphics as well as hex instructions; tabular hex display of memory contents; breakpoint handler; complete load and save routines.

□ **and more!** — revised keyboard routine for word-processing use; user-definable input/output; OSI-compatible floppy-disc bootstrap on Superboard/C1, C1E and UK101 versions.

All this packed into a single replacement PROM! Versions available for standard Superboard/C1; Mutek's enhanced Superboard/C1; OSI C2 and C4 series (cassette only); and UK101. Further details available on request; please specify version required when ordering.

Price: £29.50 includes full documentation and reference card.

Mutek — improving personal computing... for less than you expect

Mutek — the independent Ohio Scientific specialists — Quarry Hill, Box, Wilts. Tel: Bath (0225) 743289



DESIGNER APPROVED KITS



PE PHASER UNIT P.E. APRIL 1979

A superb six stage phaser that really gives your guitar lift off. Equals the best commercial models. Uses latest FET op-amps. Glassfibre p.c.b.

COMPLETE KIT OF ALL PARTS AS SPECIFIED.....£16.50

- Pack 1. All semiconductor devices.....£8.00
- Pack 2. Resistors, capacitors & preset pot.....£3.75
- Pack 3. Footswitch, jacks, pot, knob, printed circuit & hardware.....£4.75
- Pack 4. Diecast box and feet.....£2.50

Separate parts: TLO82 80p, BF245B 50p, PC8 £1.50, 8 pin sockets (not included in kit) 21p each.

PE SUSTAIN UNIT P.E. OCT. 1977

Superb quality, low noise, low distortion sustain unit equal to the very best commercial models. Suits all guitars. Glassfibre p.c.b.

COMPLETE KIT OF ALL PARTS AS SPECIFIED.....£8.50

- Pack 1. Resistors, capacitors & p.c.b.....£1.75
- Pack 2. All semiconductor devices.....£1.75
- Pack 3. Footswitch, jacks, pot, knob, and battery clip.....£3.25
- Pack 4. Diecast box and feet.....£2.50

Separate parts: XC5053R 50p, RPY58A 75p, Printed circuit board 95p, Footswitch £1.80 each.

ORION AMPLIFIER

Complete set of semiconductors.....£9.75
Quality glass fibre p.c.b., printed with component locations.....£3.50

PE TV SOUND SEPARATOR

Complete set of semiconductors.....£2.30
High quality glass fibre p.c.b.....£1.50
Murata filters: SFE6.0MA 50p, CDA6.0MC 50p.

P.E. SMOOTH FUZZ UNIT

(P.E. September 1979)

This is the Fuzz unit you have been waiting for! Smooth, clean tone with low noise and low current drain. Uses glassfibre p.c.b. and latest FET op-amp.

COMPLETE KIT OF ALL PARTS AS SPECIFIED.....£8.50

POSTAGE & PACKING 25p per order. Orders over £10.00 post free.

All devices are top grade, brand new and to full manufacturers spec.

PRICES DO NOT INCLUDE VAT. Add 15% to all prices.

MAIL ORDER ONLY
CALLERS BY APPOINTMENT

DAVIAN ELECTRONICS

13 DEEPDALE AVENUE, ROYTON, OLDHAM OL2 6XD.

Rapid Electronics

■ Guaranteed same day Despatch

■ Quality Product

■ Free Catalogue

■ Vast Stocks

■ Competitive Prices

Pack		Pack			
A10	10 PP3 battery leads	50p	F11	10 BC108 trans.	90p
A72	10 3.5mm jack plugs	80p	F26	10 2N3704 trans.	80p
A73	10 3.5mm jack sockets	80p	F27	10 2N3819 trans.	190p
A74	10 Std. jack plugs	130p	H11	20 1N4002 diodes	75p
A75	10 Std. jack sockets	170p	H50	20 0A91 diodes	110p
A84	10 5 pin 180 DIN plug	120p	H60	100 1N4148 diodes	180p
A85	10 5 pin 180 sockets	100p	H70	5 C106D thyristors	200p
C20	10 Min. slide switch	130p	J10	20 0.2in. red LEDs	170p
C30	10 Push to make sw.	130p	J15	50 0.2in. red LEDs	400p
C31	10 Push to break sw.	170p	J20	100 0.2in. red LEDs	750p
C40	Pair Ultrasonics	350p	J30	20 0.2in. green LEDs	280p
C32	Submin. SPST toggle	60p	J50	20 0.2in. yellow LEDs	280p
C33	Submin. DPDT toggle	80p	J80	4 FND500 CC displays	350p
C50	20 Texas 8 pin sockets	170p	K5	5 741 op amps.	90p
C51	20 Texas 14 pin sockets	200p	K40	1 LM324 op amp.	50p
C52	20 Texas 16 pin sockets	220p	K20	5 CA3140 op amps.	225p
E10	Resistor kit. 10 ea value ±W 4.7Ω 1M.650 resistors	480p	K85	5 NE555 timers	110p
E34	10 10u 25V radial elec	50p	L8	5 4011 CMOS	130p
E37	10 100u 25V radial	75p	L9	4013 CMOS	40p
E44	10 1u 35V tantalum	100p	L11	4017 CMOS	75p
E54	10 0.1 C280 polyester	50p	L19	4049 CMOS	45p
			M20	Dalo pen	80p

■ For quality components at competitive prices by return of post Rapid Electronics must be your first choice!

All prices include VAT. Please add 50p postage and packing on orders below £10. Send SAE for our complete catalogue.

Rapid Electronics Limited

Hillcroft House, Station Road, Eynsford, Kent

Now Casio take a giant step forward in time with

THE ULTIMATE WATCHES

Send 12p for details of this amazing range of watches NOW!



AA81 LCD ANALOGUE/DIGITAL Alarm Chronograph with countdown

Analogue. Independent hours and minutes with syn-chronous digital seconds. Dual time ability.
Digital. Hours, minutes, seconds, day and date.
Stopwatch. 1/100 second to 12 hours. Net, lap and 1st and 2nd place. Start/stop and 10 minute signals.
Alarm. For 30 seconds with amazing "Star Burst" flashing display.
Countdown Alarm. Normal and net times to 1 hour.
Time signal. Half hourly and hourly chimes. Tone control. Lithium battery. Light. Water Resist. case. 8.65mm thick. Mineral glass (£34.95).

Analogue
Display

Digital
Display

ONLY £29.95
for around 40 functions.

12 MELODY ALARM CHRONOGRAPHS

Countdown alarm. Date memories.

Hours, minutes, seconds, am-pm, 12 or 24 hour.
Day, date and month auto calendar.
Alarm. 7 melodies, one for each day of the week.
Hourly time signal. With "Big Ben" type tune.
Date memory. "Wedding March" or "Trinkled"
choice.
Birthday and Christmas Memory.
Countdown alarm. From 1 second to 1 hour. After zero, count continues positively.
Stopwatch. 1/10 second to 1 hour. Net, lap etc. Pic-turesque moving display of notes played. Light.
Lithium. Glass. Water Resist. cases. M-12 resin, s/s trim. M-1200 all s/s 9.0mm thick.



£24.95

£29.95

100 METRE WATER RESISTANT

Alarm Chronographs with countdown.

Amazing 5 year lithium battery life. Hours, minutes, seconds, am/pm, day, date and month, 12 or 24 hour. Time is always visible regardless of display mode.
Stopwatch. 1/100 second to 1 hour. Net, lap, 1st and 2nd. Start/stop signal. 10 minute signal.
Alarm. Sounds for 30 seconds.
Time signal. Half hourly and hourly chimes.
W-100. All resin. W-150B. All metal. W-150C (not il-lustrated) metal case/resin strap £25.95.



£19.95

£32.50

JOIN THE KEYBOARD REVOLUTION!

With the amazing new CASIOTONE 201

A remarkable new concept in electronic keyboard instruments using a totally new technology to faithfully reproduce the pitch, timbre and harmonics of 29 instruments. A 4-sound memory function allows switching between any 4 pre-selected in-struments. This polyphonic instrument can play full chords of up to 8 notes on its 29 white and 20 black keys spanning 4 octaves. Vibrato and tone switches. Foot volume and sustain pedal options. Echo jacks. 3x33½x9½ inches. Weight 15lbs. Black or woodgrain finish. AC only.



ONLY £245 (r.r.p. £285)

CASIOTONE M-10 Four instruments on the move!

Polyphonic playing of piano, organ, violin and flute. 19 white and 13 black keys span 2½ octaves. Vibrato switch. 2x16½x5½ inches. Weight 3.5lb. Integral speakers. O/p jack. Mains/battery.



ONLY £69 (r.r.p. £79)

★ MG-880 Space Game/Melody Calculator. Action packed speed game. We promise you hours of skillful entertainment (£12.95) £10.95. ★

Price includes VAT, P&P. Send your remittance or phone your credit card number to:

TEMPUS

Dept. PE, Beaumont Centre, 164-167 East Rd.,
Cambridge CB1 1DB Tel: 0223 312866

SECURITY SENTRY/SENTINEL

If you are considering building either of these alarm systems save yourself time, aggravation and £££ by purchasing one of our kits. Each kit contains detailed step-by-step assembly and installation instructions and every item required to build an alarm control centre as illustrated in the articles. There are no extras to buy. Prices are all inclusive (U.K. only) and are valid for six months. Terms: CWO; Access and Barclaycard orders welcome.

SECURITY SENTRY (July PE)

- SCA01 Security Sentry Alarm Control Centre. Includes: Silk screened and drilled case, drilled and tinned PCB, all PCB components, IC sockets, battery holder (less batteries) and all mounting hardware. **£12.95**
- SCA/PPP01 Consists of the above kit and a caravan protection kit comprising: Siren, seven pin socket, magnet and reed switch, 20 Mtrs wire, wire staples & hardware. **£26.70**

SECURITY SENTINEL

- DAS01 Security Sentinel Alarm Control Centre. Comprising: silk screened & drilled case, silk screened, drilled & tinned PCB's, IC sockets, all PCB components, battery holder (less batteries), mains transformer, and all hardware. **£45.95**
- DAS02 As above but includes nickel-cadmium batteries. **£53.95**
- CS02 Siren Kit. (Can also be used with SCA01): Siren, 10 Mtrs wire, wire staples, and mounting hardware. **£8.75**
- TMS01 Tri-Mode switch kit comprising: two magnet and reed switch assemblies, diode, resistors, & hardware. **£1.95**

Interested in a vehicle alarm system kit?? Write for details.

COMPU-TECH SYSTEMS

Laundry Loke Industrial Estate,
North Walsham, Norfolk
Tel: North Walsham 5600

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ahr	SUB 'C' 1.2Ahr	'C' (HP11) 1.65Ahr	'C' (HP11) 2.0Ahr	'D' (HP2) 4.0Ahr	PP3 0.1Ahr
1-24	£0.85	£1.38	£1.69	£2.25	£2.97	£3.79
25-49	£0.82	£1.28	£1.58	£2.10	£2.77	
50-99	£0.80	£1.24	£1.52	£2.02	£2.67	
100 up	£0.70	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are "VENTED" devices suitable for fast charge.

CHARGERS - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04

DUAL O/P CHARGER £5.72

TRANSFORMERS - as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Cheques, P.O.'s Mail Order to:-

SOLID STATE SECURITY,
Dept. (PE), Bradshaw Lane,
Parbold, Wigan, Lancs.
Telephone 02576-3018.

Data and charging circuits free with orders over £10 otherwise 30p post.
P&P 10% if order less than £10, 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order.



THIS MONTH'S SNIP!

"Let us quote for your hard to get components for PE projects"

CLAIREX CL705HL — £4.50 ea.
PMI REF 02 — £4.00 ea.

RS ITEMS A SPECIALITY!

Send s.a.e. for priced parts list of PE projects (max. 4) stating month and project title.

ACE MAILTRONIX LTD
Dept. PE, 3A Commercial St.
Batley, W.Yorks. WF17 5HU



I enclose 30p* please send catalogue

name _____

address _____

*refundable with future order over £5.00



TITAN TRANSFORMERS AND COMPONENTS
CENTRAL HALL CHAMBERS
GRIMSBY SOUTH HUMBERSIDE
 MAIL ORDER ONLY
 PAYMENT C.W.O. CHEQUES, POSTAL ORDERS
 ALL PRICES INCLUDE 15% V.A.T.

PRINTED CIRCUIT BOARD TYPES

0-6v 0-6v

REF	AMPS	PRICE	P/P
TTP 446	0.5-2	1.79	50
TTP 447	0.75-2	2.14	60
TTP 449	1.0-2	2.36	70
TTP 450	2.0-2	2.99	85
TTP 451	4-18-2	4.57	120
TTP 452	8-33-2	5.68	120

TRANSFORMERS

0 100 120 0 120 INPUT 120 220 240

PRIMARY 0 120V OR 240V 50Hz
 SECONDARY SERIES OR PARALLEL
 P.C.B. OR CHASSIS MOUNTING

LINK CONNECT

CHASSIS MOUNTING TYPES

0-9v 0-9v

REF	AMPS	PRICE	P/P
TTP 460	0.30-2	1.79	50
TTP 461	0.50-2	2.14	60
TTP 463	0.60-2	2.36	70
TTP 464	1.38-2	2.99	85
TTP 465	2.77-2	4.57	120
TTP 466	5.55-2	5.68	120

0v-6v 0v-6v

REF	AMPS	PRICE	P/P
TTC 446	0.5-2	1.85	50
TTC 447	0.75-2	2.20	60
TTC 449	1.0-2	2.45	70
TTC 450	2.0-2	3.10	85
TTC 451	4-18-2	4.70	120
TTC 452	8-33-2	5.85	120

0v-9v 0v-9v

REF	AMPS	PRICE	P/P
TTC 480	0.30-2	1.85	50
TTC 461	0.50-2	2.20	60
TTC 463	0.60-2	2.45	70
TTC 464	1.38-2	3.10	85
TTC 465	2.77-2	4.70	120
TTC 466	5.55-2	5.85	120

0v-12v 0v-12v

REF	AMPS	PRICE	P/P
TTP 467	0.25-2	1.79	50
TTP 468	0.38-2	2.14	60
TTP 470	0.50-2	2.36	70
TTP 471	1.0-2	2.99	85
TTP 472	2.0-2	4.57	120
TTP 473	4-16-2	5.68	120

0v-12v 0v-12v

REF	AMPS	PRICE	P/P
TTC 467	0.25-2	1.85	50
TTC 468	0.38-2	2.20	60
TTC 470	0.50-2	2.45	70
TTC 471	1.0-2	3.10	85
TTC 472	2.0-2	4.70	120
TTC 473	4-16-2	5.85	120

0v-15v 0v-15v

REF	AMPS	PRICE	P/P
TTC 474	0.20-2	1.85	50
TTC 475	0.30-2	2.20	60
TTC 477	0.40-2	2.45	70
TTC 478	0.83-2	3.10	85
TTC 479	1.66-2	4.70	120
TTC 480	3.33-2	5.85	120

0-15v 0-15v

REF	AMPS	PRICE	P/P
TTP 474	0.20-2	1.79	50
TTP 475	0.30-2	2.14	60
TTP 477	0.4-2	2.36	70
TTP 478	0.83-2	2.99	85
TTP 479	1.66-2	4.57	120
TTP 480	3.33-2	5.68	120

0v-24v 0v-24v

REF	AMPS	PRICE	P/P
TTC 495	0.13-2	1.85	50
TTC 496	0.19-2	2.20	60
TTC 498	0.25-2	2.45	70
TTC 499	0.52-2	3.10	85
TTC 500	1.0-2	4.70	120
TTC 501	2.0-2	5.85	120

MOUNTING KITS FOR P.C.B. TYPES INCLUDES 4 NUTS SCREWS WASHERS + SPACERS

VA	KIT REF	PRICE
12	SK 12	45
25	SK 25	48
50	SK 50	52
100	SK 100	58

VA = VOLTS * AMPS P/P IN C.

0-24v 0-24v

REF	AMPS	PRICE	P/P
TTP 485	0.13-2	1.79	50
TTP 496	0.19-2	2.14	60
TTP 498	0.25-2	2.36	70
TTP 499	0.52-2	2.99	85
TTP 500	1.0-2	4.57	120
TTP 501	2.0-2	5.68	120

MAINS ADAPTORS
 3 PIN 13AMP PLUG IN ADAPTORS, MADE IN U.K.

REF	OUTPUT	PRICE	P/P
TT 100	6-7.5-9v	3.85	40
TT 101	6-7.5-9v REGULATED	4.70	40

COMPONENTS

TYPE	QTY	PRICE	P/P
BRIDGE 1A 50V	5	85	10
IN 4001	10	45	10
1000UF 25V	4	95	15
1000UF 16V	5	105	15
470UF 16V	5	85	15

DIGITAL VOLTMETER MODULE



Fully built and tested, ONLY
£11.95 V.A.T

- * Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- * Requires only single supply between 7 & 12 volts (220mA)
- * High accuracy +0.1% +1 digit
- * Large bright 0.43" high efficiency displays
- * 4 readings per second sampling rate
- * Size only 41 x 95 x 10mm
- * Supplied with full data & applications information

This brand new, quality module manufactured by Autona Limited (who are one of the U.K.'s largest module manufacturers) means you can build accurate test equipment, multi-meters, thermometers, etc. easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.

Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50pp. & p. = £14.24) now to:-

Dept. P.E.2 **BUCKINGHAMSHIRE'S NEW ELECTRONICS CENTRE**
 21 Duke Street
 Princes Risborough
 Bucks. HP17 0AT Telephone: (084 44) 6326

EX-STOCK DELIVERY

FURTHER BARGAIN OFFER TO READERS OF THIS MAGAZINE

A QUANTITY OF MIRRORS THAT CHANGE INTO CLOCKS THE MAGIC MIRROR MAINS ELECTRIC DIGITAL CLOCK EMBODYING ELECTRONIC CIRCUITRY

With a recommended retail price of £32.00, now offered new with full guarantee but slightly marked cases for £11.95 each inc. V.A.T. or 5 for £10.95 each inc. V.A.T.

LARGER QUANTITY DISCOUNTS AVAILABLE (U.K. only).



Optional touch sensor or manual switch will make the display disappear or reappear. Specification:

Blue fluorescent display
 Hours - Minutes - Seconds
 Alarm with 9 minute snooze facility

Send cheque or P.O. to:-

PRESCOTT CLOCK & WATCH CO. LTD.
 Prescott House, Humber Road, London, NW2 6ER.
 Tel: 01-452 9871

Details of other offers available for the amateur and hobbyist.

**PLEASE MENTION
 PRACTICAL ELECTRONICS
 WHEN
 REPLYING TO
 ADVERTISEMENTS**



4 1/4 x 3 1/2 INCH METER. 30µA, 50µA or 100µA, £5.10. 50p P. & P.

MICROPHONES FOR TAPE RECORDERS
 DM228R 200 ohm with 3-5 and 2-5mm Jack Plugs **£1.70**
 DM229R 50K with 3-5 and 2-5mm Jack Plugs **£2.25**
 DM18D 200 ohm with 5 and 3 pin Din Plugs **£1.99**
 Postage on above microphones 17p



CARDIOD DYNAMIC MICROPHONE

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £8.02. 50p P. & P.

2in x 2in meters 500µA, £4.14 17p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £4.00. 26p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.

MULTI-METER



7N 360TR
 20,000 ohm/volt
 RESISTANCE RANGES
 X1, X10, X1K, X10K
£13.30
 P.&P. 75p

TRANSFORMERS Primary 240V

6-0-6V	100mA	£0.75
9-0-9V	75mA	£0.75
12-0-12V	50mA	£0.85
12-0-12V	100mA	£1.05
Post on above transformers	45p.	
9-0-9V	1A	£1.80
12-0-12V	1A	£2.15
15-0-15V	1A	£2.51
30-0-30V	1A	£3.10
6-3V	1 1/2A	£1.80
6-0-6V	1 1/2A	£2.20
Post on above transformers	75p.	

PL258 Plug 33p; Socket 33p; PL259/SO239 Angled Connector 70p; 1 watt dummy load 95p; 2m Rubber Neck Aerial with PL259 Plug £3.30. POST ON ABOVE ITEMS 14p.

All above prices include V.A.T. Send 40p for new 1980 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

M. DZIUBAS
 158 Bradshawgate · Bolton · Lancs. BL2 1BA



SMALL ADS

The prepaid rate for classified advertisements is 24 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £8.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfd. — 5p.
22 & 47 — 8p. (50V — 6p). 100 — 7p. (50V — 8p).
220 — 8p. (50V — 10p). 470 — 11p. (40V — 16p).
1000/15V — 15p., 1000/25V — 18p., 1000/40V — 35p.
Subminiature bead Tantulum electrolytics. — 14p.
0.1, 0.22, 0.47, 1.0, 2.2, 3.5V, 4.7, 8, 3V — 8p.
2.2/35V, 4.7/25V — 15p., 10/25V, 15/16V — 20p.
22/16V, 33/10V, 47/8V, 68/3V & 100/3V — 30p.
15/25V, 22/25V, 47/10V — 35p., 47/16V — 80p.
Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf. — 3p., 56 pf. to 330 pf. — 4p.
10% 390 pf. to 4700 pf. — 4p.
Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.
Polystyrene E12 Series 63V. Horizontal Mounting.
10 pf. to 820 pf. — 3p., 1000 pf. to 10,000 pf. — 4p.
Miniature Polyester 250V Vert. Mtg. E6 Series.
0.1 to 0.68 — 4p., 1 — 5p., 15, 22 — 6p., 33, 47 — 10p.
68 — 12p., 10 — 15p., 1.5 — 22p., 2.2 — 24p.
Mylar (Polyester) Film 100V. Vertical Mounting.
0.01, 0.022, 0.047 — 3p., 0.1, 0.22 — 4p., 0.4, 0.5, 0.1 — 6p.
Miniature Film Resistors Highstab. E12 Ser. 5%.
0.125W mixed carbon/metal 100 to 1MΩ — 1p.
0.25W Carbon 10 to 10MΩ (10% over 1MΩ) — 1p.
E24 Series av. in 3W C Film 10 to 5MΩ (10%).
0.25W, 0.5W & 1.0W Metal Film 100 to 2MΩ — 2p.
1N4148 — 2p., 1N4002 — 4p., 1N4006 — 6p., 1N4007 — 7p.
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7 — 10p.
8 Pin i.c.'s 741 Op. amp. — 18p., 555 Timer — 24p.
DI Holders 8 pin — 9p., 14 pin — 12p., 16 pin — 14p.
LED's 3 & 5mm. Red — 10p., Green & Yellow — 14p.
Grommets for 3mm. — 1½p., 2 pce. holders 5mm. — 2½p.
20mm. Q.B. Fuses .15, .25, .5, 1, 2, 3 & 5A — 3p.
20mm. Anti Surge 100mA. to 5.0A — 5p.
20mm. Fuseholders P.C. or Chassis Mtg. — 6p.
Solid A1. knobs 15mm. — 25p., 25mm. — 30p., 30mm. — 50p.
400mW Zener diodes E24 series 2V7 to 33V — 8p.
Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

MIXED. 100 transistors £3.50. 25 I.C.s £1.50. 100 Diodes £1. Post paid. Early radios. Valves. Interesting lists 15p. Sole Electronics, P.E. 37, Stanley Street, Ormskirk, Lancs. L39 2DH.

CLEARANCE PARCELS: Transistors, Resistors, Boards, Hardware, 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75. BC108, BC171, BC204, BC230, 2N5061, CV7497 Transistors 10 70p, 100 £5.80. 2N3055, 10 for £3.50. S.A.E. Lists: W.V.E. (2), 15 High Street, Lydney, Gloucestershire.

TUNBRIDGE WELLS COMPONENTS. Ballards, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquiries S.A.E.

100 ASSORTED COMPONENTS 115p. 100 Assorted Resistors 60p. 100 Assorted capacitors 150p. 50 reed switches 200p. 10 mains neons 50p. 10 Micro switches 150p. Add 25p P&P. Durrants, 9 St. Mary's Street, Shrewsbury, Salop.

SERVICE SHEETS

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

G.T. TECHN. INFO. SERVICE

76 Church St., Larkhall, Lanarks ML9 1HE
Any single service sheet £1 + large SAE
1,000s of sheets/manuals always in stock.
Sole suppliers of all T.V. Repair Systems
Giant Diagram Manual for Washing Machines
Single tubs/twin tubs/auto — only £13.50
Repair Data any named T.V. £5.50 (with circuits, etc. £7.00). SAE for newsletter, bargain offers etc.
Phone 0698 883334 after 4pm.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SOFTWARE

MORE UK101 SOFTWARE from the guy who wrote "Le Passe-Temps". 4K logic: Bridge-it. 4K Graphics: Bomb-run, Breakout, Wall-ball, Piranha. 8K: Galactic Hitchhiker (adventure), Startrek. Prices for these and previously advertised games: 4K £1.50: 8K £3.00. Circuit diagrams/Instructions for 4 P.I.A.s 1/2 Meg, 110/300/600 Baud conversions £2.00. All inclusive prices from: Mr. S. Knight, 28, Simonside Walk, Ormesby, Cleveland.

UK 101 PROGRAMS

GENERAL SUBROUTINES
GRAPHIC SUBROUTINES
PROGRAMMABLE SOUND GENERATOR ROUTINES
MANY USEFUL PROGRAMS AND FACILITIES

380 Z PROGRAMS

MAINLY WITH AN EDUCATIONAL BIAS.
BEARINGS, MATRICES, MORSE, ETC.
S.A.E. for LIST.

DOLA SOFTWARE,
117 BLENHEIM ROAD,
DEAL, KENT.

COMPUKIT software, well documented: Machine-code Life £4.00, Dogfight £3.00. Send SAE for catalogue: B. Strulo, Meadow Cottage, Buxhall, Stowmarket, Suffolk IP14 3DR.

UK101 SHORTHAND BASIC. Machine Code Program loaded from Basic enables a whole Basic word to be typed one key (after command key). State old or new monitor and 8K or 4K memory size. Cassette and instructions for £5 + 30p P&P from P. P. PATAY, 3 West View, Tandridge, Oxted, Surrey.

UK101 KEYBOARD GRAPHICS. Program allows direct Keyboard access to all special graphic characters. Single key entry and display. User RAM not affected. Listings/notes £1. FORWARD, 54 Bourne Vale, Hayes, Bromley, Kent.

BOOKS AND PUBLICATIONS

ANY REQUESTED SERVICE SHEET £1 + Large S.A.E. Full repair data any named TV £5.50 (with circuits, layouts etc. £7). SAE brings newsletter, bargain offers, etc. AUSPEL, 76 Church St, Larkhall, Lanarks ML9 1HE.

THE MK14 BOOK. Published by Macmillan, this big 216 page book covers every aspect of MK14 programming in 17 chapters. SAE for full details. Also details of 1½K memory expansion. £5.95 + 35p p&p. REDDITCH ELECTRONICS, 21 Ferney Hill Avenue, Redditch, Worcs. B97 4RU.

FOR SALE

NEW BACK ISSUES of "Practical Electronics" available 80p each Post Free. Open P.O./Cheque returned if not in stock — BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

SINCLAIR ZX80, as new, used twice, complete with manual and PSU. £60. Sheffield (0742) 737763.

PHILIPS PM3210 Twin Beam 25MHz Portable Oscilloscope. Excellent condition. £275. Ring. 01 427 8984.

ZX-80/TRS-80 cassette programmes. Automatic calculator. Metric converter. @ £2.40 each inc. p&p. S.A.E. for list. Toth. Dept. P.R., 46, Fist Avenue, Grimsby DN33 1DA.

SERVICES

EPROM PROGRAMMING SERVICE. For types: 2708, 2704, 2716 Dual rail. And 2508, 2758, 2516, 2532 Single rail. Please telephone Uxbridge 59130.

EDUCATIONAL

TV & COMPUTER SYSTEMS SERVICING

18 MONTHS full-time Modular Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS

Each of the above Modules are 12 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £400 per Module. 7 Computer Module £500.

Next session starts January 5th.

(Also available 2½ year course in Marine Electronics & Radar.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. PEA11, Penyern Road, London SW5 9SU. Tel: 01-373 8721.

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272A Intertex House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272A Intertex House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272A Intertex House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CAREERS in Marine Electronics. Courses commencing September and January. Further details, the Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

SITUATIONS VACANT

UNIVERSITY OF SUSSEX SCHOOL OF ENGINEERING AND APPLIED SCIENCES

Electronics Technician

A vacancy exists in the School of Engineering and Applied Sciences for an Electronics Technician. The successful applicant will be required to assist in the teaching and research laboratories on a variety of interesting projects, should have had considerable experience with electronic circuits, preferably some experience of Teletype Servicing.

Salary on the scale £4431-£5097 pa or £4776-£5577 pa depending on experience and qualifications.

Applications, in writing should be addressed to:

The Laboratory Superintendent,
School of Engineering and Applied Sciences,
University of Sussex,
Falmer, Brighton BN1 9QT.

MISCELLANEOUS

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £12.95 plus 35p P. & P. 'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £5.95 plus 35p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher: ready-made multi-function modules £6.85 each plus 35p P. & P.
LOTS MORE! Send 30p for lists. Prices include VAT.

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

7 SEGMENT LED's at low cost 0.3in, RH decimal, common cathode, FND70 series. Base diagram included. £2 plus SAE for three. F. Rose, 33, Wallace Drive, Eaton Bray, Beds.



Readily available Hardware and Accessories for Home Constructors, Dev Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c. boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills. All immediately available. Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,

Masons Rd. Stratford on Avon
Warwks. CV37, 9NF 0789-4879

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

NEW IC ULTRASONIC ALARM KITS

Single Unit construction - screw connections. 240V operation with battery back-up option. 15-foot detection range internally preset. Delay on leaving and entry, invalid movement delay, self-cancelling alarm, approx 2 mins. KITS INC. F/G PCB, ABS BOX, HARDWARE ALL COMPS. 240V UA/S (Piezo drive output) £16.95. 240V UA/R (relay output contacts) £19.65. Piezo Sounder 12V 18mA 105db 1 mtr. £8.20. Built and tested units KIT price + £7.00. All prices inclusive - CWO - UK mail order.

G.J.D. ELECTRONICS, 105 Harper Fold Road
Radcliffe, Manchester, M26 0RQ



VIDEO MUSIC

The amazing Videograph, as featured recently in Electronics Today International, links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically-minded, a square-wave signal generator is built-in, permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

DIY KIT ONLY **£33.95**
Case & Controls £15.95
or READY BUILT £69.95

All prices include VAT and postage

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road,
Herongate, Brentwood,
Essex CM13 3SD.
Telephone: Brentwood (0277) 810244

SEEN MY CAT? 5000 Odds and ends. Mechanical. Electrical. Cat. free. Whiston Dept. PRE. New Mills, Stockport.

MAKE YOUR OWN PRINTED CIRCUITS


Eth Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £1.60. Large range of single sheets in stock at 34p per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.80. Drafting film (30 x 21cm) 22p per sheet. 17p stamp for lists and information. P&P 30p/order

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

PRINTED CIRCUIT BOARDS. Glass fibre tinned & drilled, proto types to batch runs. Quick turn-round. competitive prices. Send s.a.e. for quotations R. D. ELECTRONICS, 12, Whiteoaks Road, Oadby, Leicester. 0533-716273.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/Packing 60p. WHITE HOUSE ELECTRONICS, P.O. Box 19, Castle Drive, Penzance, Cornwall.

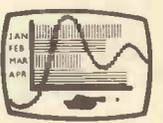

UK101 NASCOM 1 & 2

ADD-ON COLOUR SYSTEM

DAZZLING COLOUR GRAPHICS FOR UK101 & NASCOM

- Professional bit-addressable 'pixel' system
- 3072 colour cell definition
- 8 Colours foreground + 8 background
- FREE SOFTWARE: Plot, Line, Circle (Basic + Z80)
- Animated Demonstration Program
- Modulator included for use with normal TV

KIT: only **£45** Built & Tested: only **£60**

Also available separately:

COLOUR MODULATOR

- R G B inputs, PAL/UFH output
- Unlimited colour combinations
- TTL etc interface details supplied
- 1000's already in use!

KIT: only **£12** Built & Tested: only **£18**

— please add VAT at 15% to all prices
— Barclay/Access orders accepted by telephone

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low £1.05. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.

PRACTICAL ELECTRONICS P.C.B.'s

Apr. 80	2 Wire Train Controller EP320	£2.93
May 80	Two Wire Train Controller EP326	£3.02
	EP328/30	£1.20 pair
Jun. 80	Dynamic Semiconductor Tester EG311/2	£1.83 pair
	MasterTune EP343	£3.80 (Not plated through)
	Greenhouse Temp. Control EP358	£1.90
Jul. 80	Tape Slide Synch EP353	£1.28
Sept. 80	DISCO deck EP365	£3.26
	Sound Gen. EC14	£2.53

For full list and current pcb's please send SAE. Pcb's also produced to customers own masters. Trade enquiries welcome. Please write for quote. CWO Please. Postage. — Please add 30p postage and packing to complete order. Europe 65p.

PROTO DESIGN
14 Downham Road, Ramsden Heath
Billericay, Essex CM11 1PU
Telephone 0268-710722

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No

100 ALARM TRIGGER MODULE. 100% Solid State Battery operation. Pos. & Neg Rings N/C for 4-wire contacts N/O for Mats. etc. One Amp Switching Capacity.	£9.95
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT + matching magnet	£1.10
220 Surface 4-wire MAGNETIC REED CONTACT	£1.50
240 PRESSURE MAT. Standard size 4-wire 30" x 15"	£2.20
2250 PRESSURE MAT. Stair size 4-wire 23" x 6"	£1.73
260 VIBRATION DETECTOR. Pendulum type in Ivory Case with contacted lid + self-adhesive backing. Adjustable sensitivity	£3.50
360 SIX INCH UNDER DOME BELL	£9.95
380 BEST QUALITY BELL HOUSING. PVC coated metal, not to be confused with the cheaper decoy covers. Fully signwritten with our Centurion insignia	£9.50
400 DECOY P.V.C. BELL COVER	£6.60

Note: All equipment operates on 12 Volts DC.
710 SCOOP Offer SMOKE ALARMS. Self-contained Ionisation type (1.5% obscuration) with low battery warning at the UNREPEATABLE PRICE of only £8.78 White Stocks Last!!!
Terms: Add 15% VAT to Prices + 40p Postage & Packing.

No Minimum Order.

Access telephone orders welcome on: 0484-35527 or send S.A.E. for Full List to:

CENTURION ALARMS & ELECTRONIC SALES, Dept. ME, 265 Wakefield Road, Huddersfield, W. Yorks HD5 9BE.



WESTERN MAGAZINE

**For the very first time
legend teams up
with reality**

The West as it really was. And the West as you've always enjoyed it. What a magnificent combination!

Now, at long last, here's a magazine that's packed with new stories written by best-selling Western authors and illustrated by top Western artists—plus the raw truth that lies behind the fiction.

Thrill to the explosive action, gory gunfights, cattle stampedes, jaw-crunching saloon riots, smouldering passion and Indians on the war path...

Read about **real** people and real events—crazy pioneers, lonesome cowhands, crooked lawmen, blood-lusting Indians and fun-loving dance-hall girls...

DON'T MISS YOUR COPY!

**WESTERN
MAGAZINE**

The West as it really was.

**EVERY MONTH
70p**

INDEX TO ADVERTISERS

Ace Mailtronix	90	Electrovalue	38	Radio Component Specialists	12
Acorn	Cover II	Fladar	82	Radio & T.V. Components	16
Adam Hall (P.E. Supplies)	94	GJD Electronics	93	Ramar Constructor Service	93
Aitken Bros.	22	Global	94	Rapid Electronics	89
Alcon	45	GMT	78	Riscomp Ltd.	91
Ambit	46	GT Technical Information Service	92	Safgan	64
Audio Elec.	38	Heathkit	77	Saxon Entertainments	4
Barrie Electronics	64	Hiykon Ltd.	94	Science of Cambridge	14, 15
BIB Hi-Fi Accessories	25	Home Radio	84	Scientific Wire Co.	93
BIET	77	I.C.S. Intertext	7, 93	SCS Northern	12
Bi-Pak	72, 73	I.L.P. Electronics	80, 81, 88	Sentinel Supply	76
Birkett J.	86	Industrial Supplies	94	Service Trading	87
Boffin Projects	93	Jayen Developments	78	Solid State Security	90
Bolster Instruments Co.	94	Keelmoor	74, 75	Stevenson	22
Breadboard Exhibitions 1980	54	Lascar	3	Sumico	64
British National Radio & Electronics School	13, 85	L & B Electronics	84	Suretron	10
Cambridge Kits	94	London Electronics College	92	Swanley Electronics	84
Cambridge Learning	5	Maplin Electronics	Cover IV	Tandy	8, 9
Centurion Alarms	93	Marshall A.	4, 85	Technomatic	96
Chromasonic Electronics	79	Micro Circuits	11	Tempus	90
Chromatronics	10	Midland Trading	83	Titan	91
Clef Products	77	Mighty Micro	86	T.K. Electronics	76
Codespeed	78	Modern Book Co.	12	University of Sussex	93
Commodore	67	Mutek	89	Vero	82
Computech	90	Parndon	64	Videotone	21
Computer Components (Teleplay)	Cover III	Phonosonics	6, 7	Watford Electronics	2, 3
Continental Spec.	63	PKG Electronics	93	West London Direct Supplies	12
Crofton Electronics	82	Prescott Clocks	91	Williamson Amplification	94
C.R. Supply Co.	92	Progressive Radio	84	William-Stuart Systems	93
Davian	89	Proto Design	93	Wilmslow Audio	76
Dola Software	92				
Doram	4				
Dziubas	91				

EXTENDED WARRANTY BY COMPUKITE

only £349 + VAT



TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply - Cassette Leads - Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available.

Interface to Centronics Parallel for TRS80 £75.00 + VAT

only £295 + VAT

Expand your TRS80 by 32K
32K Memory on board
Centronics parallel port
Disk controller card
Real time clock
Requires Level II Basic Interface for 2 cassette decks complete with power supply

TRS80 EXPANSION INTERFACE



TEAC DISK DRIVES

Single Disk Drive £225 + VAT
Double Disk Drive £389 + VAT

- TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.
- The FD-50A can be used in double density recording mode.
- The FD-50A is Shugart SA400 interface compatible.
- Directly compatible with Tandy TRS80 expansion Interface.
- Also interfaces with Video Genie, SWTP, Heathkit, North Star Horizon, Superbrain, Nascom, etc, etc.
- Address selection for Daisy chaining up to 4 Disks.
- Disks plus power supply housed in an attractive grey case.

THE ATARI VIDEO COMPUTER GAMES SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!



Most Cartridges only £13.90 + VAT


Prices may vary with special editions Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle, Codebreaker*, Miniature Golf.
Extra Paddle Controllers *Keyboard Controllers
- £14.90 + VAT - £16.90 + VAT
SPACE INVADERS NOW IN STOCK £25

YOU NEED NEVER MISS AN IMPORTANT CALL AGAIN TWO CORDLESS TELEPHONE SYSTEMS - DIRECT FROM USA




THE ALCOM only £147 + VAT

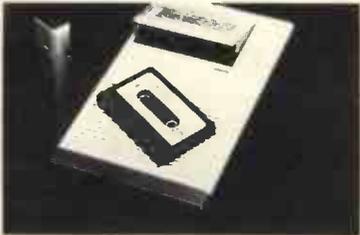Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling - Bleeps when call arriving - Nicad rechargeable batteries. Charger in base unit.



LOW COST TELEPHONE ANSWERING MACHINE only £99.95 + VAT

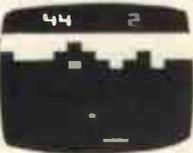Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.



NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games.

You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.

MINI KIT - PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. £14.90 + VAT

OR PCB £2.90 MAIN LSI £8.50 Both plus VAT



EUROPE'S FASTEST SELLING ONE BOARD COMPUTER COMPUKIT UK101

* 6502 based system - best value for money on the market. * Powerful 8K Basic - Fastest around * Full Qwerty Keyboard * 4K RAM Expandable to 8K on board. * Power supply and RF Modulator on board. * No Extras needed - Plug-in and go. * Kansas City Tape interface on board. * Free Sampler Tape including powerful Disassembler and Monitor with each Kit. * If you want to learn about Micros, but didn't know which machine to buy then this is the machine for you.

40 pin Expansion Jumper Cable for CompuKit expansion £8.50 + VAT

Build, Understand and Program your own Computer for only a small outlay **KIT ONLY £179 - VAT NO EXTRAS NEEDED**

Available ready assembled, tested & ready to go £229 + VAT

NEW MONITOR FOR COMPUKIT UK101

- In 2K Eprom 2716
- Allows screen editing
- Saves data on tape
- Flashing cursor
- Text scrolls down £22.00 + VAT

FOR THE COMPUKIT

Assembler/Editor	£14.90
Screen Editor Tape	£5.90

Game Packs

1. Four Games	£5.00
2. Four Games	£5.00
3. Three Games 8K only	£5.00

Super Space Invaders (8K)	£8.50
Space Invaders	£5.00
Chequers	£3.00
Real Time Clock	£3.00
Case for CompuKit	£29.50

All Prices exclusive VAT

NEW REDUCED PRICES

8K £399
16K £499
32K £599

VAT

RRP £795 for 32K



The PEDIGREE PETS

Very popular for home & business use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard. All with green screen. Cassette Deck £55 extra. Full range of software available. Interface PET IEEE - Centronics Parallel. Not decoded £49.00 + VAT Decoded £77.00 + VAT

NOW IN STOCK SUPER 80 COLUMN PET
only £825 + VAT

ENGLISH COLOUR TV / AMERICAN NTSC COLOUR MONITOR

Suitable for Apple, Atari and Texas 99/4
£295 + VAT

EXTENDED WARRANTY BY COMPUKITE

We give a full one year's warranty on all our products.

WE ARE NOW STOCKING THE APPLE II EUROPLUS AT REDUCED PRICES



16K £599
32K £649
48K £690

+ VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:

- BASIC - The Language that Makes Programming Fun.
- High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays.
- Sound Capability that Brings Programs to Life.
- Hand Controls for Games and Other Human-Input Applications.
- Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package.
- Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

NOW OPEN

OUR NEW SHOWROOM AND SALES CENTRE AT

311 Edgware Road, London W2
Telephone: 01-262 0387

Please add VAT to all prices - including delivery. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number.

MAIL ORDER AND SHOP:

14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station - Moorgate Line).
Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G

NEW WEST END SHOWROOM:

311 Edgware Road, London W2. Telephone: 01-262 0387

OPEN - 10am - 7pm - Monday to Saturday

- IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933
- COMP SHOP USA, 1348 East Edinger, Santa Ana, California, Zip Code 92705. Telephone: 0101 714 5472526



"Europes Largest Discount Personal Computer Stores"



(Part of the Compshop Ltd. Group)



MAPLIN

announce the opening of their new LONDON shop

159-161
King St.
Hammersmith
London W6
01-748 0926



- Excellent metered parking
- Close to Hammersmith Underground Station for Piccadilly, District & Metropolitan Lines
- Bus no's 260·266·704·27·91 267·290 stop outside



Opens Tuesday 16th September, 1980


Opening Hours 9.45 am to 5.30 pm Tuesday to Saturday (Closed Monday)

Maplin mail-order –
Now better than ever!

- * Up to 8% discount for use with next order
- * All prices include VAT
- * Same day service on in-stock lines
- * Over 95% of our stock lines in stock
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components – no rejects – no re-marks
- * Competitive prices
- * Your money is safe with a reputable Company

On price, service, stock, quality and security, it makes sense now more than ever to make **Maplin** – your first choice for components every time!

Stereo Cassette Tape Deck

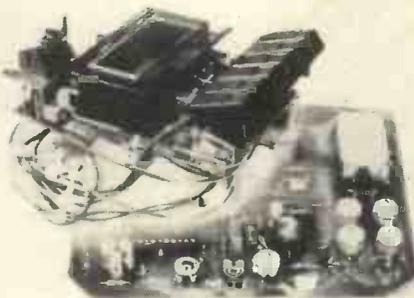

Utilising the superb JVC deck made for Tandberg and a ready-made pre-aligned, tested and guaranteed module, this cassette deck has a superb sound and a high quality specification. We've got everything you need (except cabinet) including full instruction leaflet for only £39.95. Order as XY36P (Cassette Recorder Kit)

Space Invaders

Fight the space invaders, be a polaris captain or a spaceship commander. Full colour action on your own TV set and over 450 games to play.

Basic console with Combat cartridge (AC00A) £99.50 + £2.50 carriage

All cartridges available including:

Space Invaders (AC26D)	£29.95	Adventure (AC22Y)	£23.95
Indy 500 (AC24B)	£34.50	Skydiver (AC13P)	£16.95
Chess (8levels) (AC28F)	£34.50	Breakout (AC05F)	£16.95
Golf (9holes) (AC18U)	£16.95	Slot Racers (AC19V)	£16.95
Air Sea Battle (AC01B)	£16.95	Programming (AC27E)	£34.50
Space War (AC02C)	£16.95	Olympics (AC04E)	£16.95
Brain Games (AC16S)	£16.95	Street Racer (AC14Q)	£16.95
Outlaw (AC03D)	£16.95	Keyboards per pair (AC29G)	£11.95

All prices include VAT and carriage except where shown.

Post this coupon now for your copy of our 1979-80 Catalogue price 70p

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46 p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

Name _____

Address _____

PE.11.80

MAPLIN

Maplin Electronic Supplies Ltd

All mail to:- P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea,
Essex. (Closed on Monday)
Telephone: Southend (0702) 554000.



Catalogue now available in all branches of WHSMITH Price £1.00

WMS 21